

461 Meadgate

EVERYDAY **ELECTRONICS** and computer **PROJECTS**

AUGUST 1984

90p

What is radiation?

BBC Micro Temperature Interface



**Microwave Alarm System
Kitchen Appliance Timer**

Australia \$1.60 New Zealand \$1.75 Malaysia \$4.95

BI-PAK BARGAINS

HIGH QUALITY MODULES FOR STEREO, MONO & OTHER AUDIO EQUIPMENT

Audio Amplifiers

| O/No. | POWER O/P | R.M.S. | MAX SUP. VOLTAGE | PRICE |
|--------|-----------|--------|------------------|--------|
| AL 30A | 10 Watts | 30V | 30V | £4.95 |
| AL 60 | 25 Watts | 30-50V | 30-50V | £5.92 |
| AL 80 | 35 Watts | 40-60V | 40-60V | £8.75 |
| AL 120 | 50 Watts | 50-70V | 50-70V | £15.22 |
| AL 250 | 125 Watts | 50-80V | 50-80V | £20.60 |

Stabilised Power Supplies

Output current 2.5 Amps

O/No. AC Input Price

SPM 120/45 40-48V £8.05

SPM 120/55 50-55V £8.05

SPM 120/65 60-65V £8.05

ELECT & PIEZO BUZZERS




PIEZO
Miniature round piezo electronic buzzer. White plastic. Low consumption.
Frequency: 4kHz approx.
Output: 70dB (A) @ 1 typ.
Power: 12Vd.c. 4mA
Dims: 22 (dia) x 11.5mm
Fixing Centres: 26.5mm



O/No. VP 107
95p



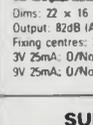PIEZO
Piezo buzzer. White plastic. 90mm leads. For use on a.c. mains.
Frequency: 3.5kHz approx.
Output: 85dB (A) @ 1m typ.
Power: 240V a.c. 5mA
Dims: 32 (dia) x 14mm
Fixing centres: 38mm



O/No. VP 108
£1.15



ELECTRONIC
Miniature electronic buzzers. Solid state. Ivory plastic. 150 leads. Frequency: 500 Hz approx.
Dims: 22 x 16 x 15mm
Output: 82dB (A) @ 1m typ.
Fixing centres: 25mm
3V 25mA: O/No. VP 82
9V 25mA: O/No. VP 84
6V 25mA: VP 83
12V 25mA: VP 86
80p each




SUB-BOX
A neat swivelling disc provides close tolerance substitution resistors of 36 preferred values from 50ohms to 1Kohm. Simply fix clips into circuit and swivel until optimum result is achieved.
O/No. VP 112
£4.75



MINIATURE VICE
Miniature plastic and metal vice with strong suction base for portability. Single action to secure or release suction. Plastic jaws with rubber pads 20mm wide, open out to 40mm. Dims: 85 x 65 x 60mm approx.
FANTASTIC VALUE
O/No. VP 95 ONLY £1.60



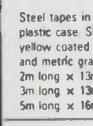LEARN A LINGO!
PILLOW SPEAKER
Slim under pillow unit. 8ohms 2" speaker. 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65 (dia) x 17mm.
O/No. VP 88
£1.25




METRIC & BRITISH MEASURES
Steel tapes in sturdy ABS plastic case. Silk wrist strap. These yellow coated convex tapes have inch and metric graduations. Automatic push-button return.
2m long x 13mm wide: O/No. VP 89 £1.00
3m long x 13mm wide: O/No. VP 90 £1.50
5m long x 16mm wide: O/No. VP 91 £2.00



BATTERY TESTER
Tests all types of battery including standard NICAAD, Alkaline etc. Takes all standard sizes including 6V lantern batteries and watch/hearing aid cells. Also tests fuses and lamps by means of internal 9V (PP3) battery. Can also be used to recharge NICAAD batteries by means of external 3-12Vd.c. power supply (not included).
Full instructions provided. Dims: 185 x 103 x 30mm
O/No. VP 101 £7.00 (approx.)



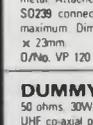FM MONITOR
FM monitor for 2 metre band. All metal. Attached earphone. PL259/SO239 connectors. 144MHz. 10W maximum. Dims: (Body) 55 x 30 x 23mm
O/No. VP 120 £4.20



DUMMY LOAD
50 ohms 30W. UHF coaxial plug fitting (PL259).
O/No. VP 121 £5.20



PICK-UP COIL
Large telephone pick-up coil for high sensitivity. Suction pad to stick to telephone. 90cm lead to 3.5 jack plug. Connects direct to cassette recorder. Dims: 32 (dia) x 17mm (body) 36mm (dia) sucker.
O/No. VP 87 £1.00

VALUE PACKS

| No. | Qty | Description | Price |
|------|-----|---|-------|
| VP1 | 300 | Assorted Resistors Mixed Types | £1.00 |
| VP2 | 300 | Carbon Resistors 1/4 Watt Pre-Formed | £1.00 |
| VP3 | 200 | Assorted Capacitors All Types | £1.00 |
| VP4 | 150 | 1 Watt Resistors 100 ohm-1M Mixed | £1.00 |
| VP5 | 200 | Ceramic Caps Miniature - Mixed | £1.00 |
| VP7 | 100 | Mixed Ceramic Disc 1pf - 56pf | £1.00 |
| VP8 | 100 | Mixed Ceramic Disc 68pf - 015pf | £1.00 |
| VP9 | 100 | Assorted Polyester/Polystyrene Caps | £1.00 |
| VP10 | 60 | C20 Type Caps Metal Foil Mixed | £1.00 |
| VP11 | 100 | Electrolytics - All Sorts | £1.00 |
| VP12 | 60 | Bead Type Polystyrene Mini Caps | £1.00 |
| VP13 | 50 | Silver Mica Caps Ass. 5pf - 150pf | £1.00 |
| VP14 | 50 | Silver Mica Caps Ass. 180pf - 4700pf | £1.00 |
| VP15 | 50 | High Voltage Disc. Ceramic 750v - 8kv Mixed | £1.00 |
| VP16 | 50 | Wirewound Res. 9W (avg) Ass. 1 ohm - 17K | £1.00 |
| VP17 | 50 | Metres PVC Covered Single Strand Wire Mixed Colours | £1.00 |
| VP18 | 30 | Metres PVC Covered Multi Strand Wire Mixed Colours | £1.00 |
| VP19 | 40 | Metres PVC Single/Multi Strand Hook Up Wire Mixed | £1.00 |
| VP20 | 6 | Rocker Switches 5 Amp 240V | £1.00 |
| VP21 | 20 | Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes | £1.00 |

| | | | |
|------|-----|---|-------|
| VP22 | 200 | Sq. Inches Total. Copper Clad Board Mixed Sizes | £1.00 |
| VP23 | 20 | Assorted Slider Pots Mixed Values | £1.00 |
| VP24 | 10 | Slider Pots 40 mm 22K 5 x Log 5 x Lin | £1.00 |
| VP25 | 10 | Slider Pots 40 mm 47K 5 x Log 5 x Lin | £1.00 |
| VP26 | 20 | Small 125° Red LEDs | £1.00 |
| VP27 | 20 | Large 2° Red LEDs | £1.00 |
| VP28 | 10 | Rectangular 2° Green LEDs | £1.00 |
| VP29 | 30 | Ass. Zener Diodes 250mW - 2W Mixed Vtgs. Coded | £1.00 |
| VP30 | 10 | Ass. 10W Zener Diodes Mixed Vtgs. Coded | £1.00 |
| VP31 | 10 | 5 Amp SCRs TO 66 50-400V Coded | £1.00 |
| VP32 | 20 | 3 Amp SCRs TO 66 Up To 400V Uncoded | £1.00 |
| VP33 | 200 | Sil. Diodes Switching Like IN4148 DO 35 | £1.00 |
| VP34 | 200 | Sil. Diodes Gen Purpose Like OA20D/BAX13/16 | £1.00 |
| VP35 | 50 | 1 Amp IN4000 Series Sil. Diodes Uncoded All Good | £1.00 |
| VP36 | 8 | Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vtgs. Coded | £1.00 |
| VP37 | 8 | Black Instrument Type Knobs With Pointer 1/2 Std | £1.00 |
| VP42 | 10 | Black Heatsinks To Fit TO-3, TO-220 Ready Drilled | £1.00 |
| VP43 | 4 | Power-Fin Heatsinks 2 x TO-3 2 x TO-66 Sure | £1.00 |

TRANSISTOR CLEARANCE

All Sorts Transistors. A mixed bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack Includes Instructions For making Simple Transistor Tester. Super Value.
Order No. VP60
£1.00

BI-PAK SOLDER-DESOLDER KIT

Kit comprises: O/No. VP 80
1 High Quality 25 Watt General Purpose Lightweight Soldering Iron 240V mains incl. 3/16" (4.7mm) bit
1 Quality Desoldering Pump High Suction with automatic ejection Knurled anti-corrosive casing and Teflon nozzle 1.5 metres of De-Soldering braid on plastic dispenser.
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt too tweezer Type
Total Retail Value over £12.00
OUR SPECIAL KIT PRICE £9.95

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12Vd.c. incl. 3 collets & 3 x Twist Bits
1 Sheet PCB Transfers 210mm x 150mm
1 Etch Resist Pen
1 3/4 pack FERRIC CHLORIDE crystals
3 sheets copped clad board
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards
Retail Value over £15.00
OUR BI-PAK SPECIAL KIT PRICE £9.95
ORDER NO. VP 81

TECASBOTY THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!

This collection of Components and Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR's, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY for ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920-3182/3442 and order just **£6.50** with your Barclaycard or Access Card - 24hr Answerphone Service NOW. Order No. VP 85.

OUR GREAT NEW 1984 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.
We hold vast stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.
To receive your NEW 1984 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

BI-PAK



Send your orders to Dept E88 BI-PAK PO BOX 6 WARE, HERTS
SHOP AT 3 BALDOCK ST. WARE, HERTS
TERMS CASH WITH ORDER. SAME DAY DESPATCH. ACCESS.
BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING

Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order.
Total Postage add 75p per Total order.

EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 13 NO. 8 AUGUST 1984

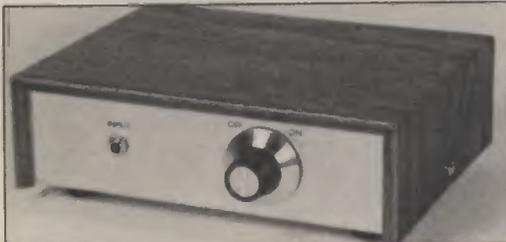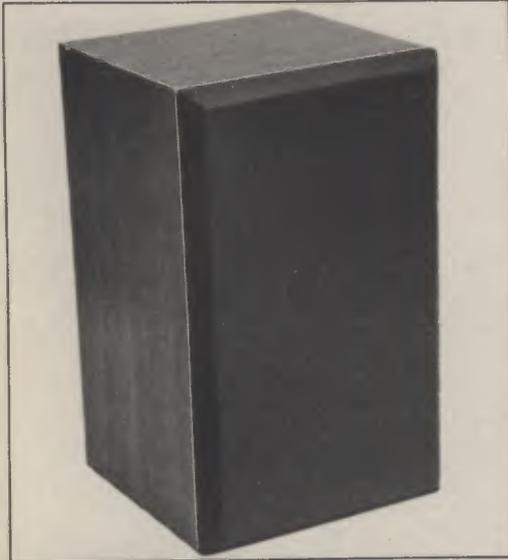PROJECTS . . . THEORY . . . NEWS . . .
COMMENT . . . POPULAR FEATURES . . .



© IPC Magazines Limited 1984. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our September 1984 issue will be published on Friday, August 17. See page 531 for details.

PROJECTS

KITCHEN APPLIANCE TIMER

by T. R. deVaux Balbirnie

488

An extra help in the home

BBC MICRO TEMPERATURE INTERFACE

by R. A. Penfold

492

Provides temperature input of -50° to $+150^{\circ}$ Centigrade

CAR RADIO BOOSTER

by R. A. Penfold

504

Boosts output up to 17W

MICROWAVE ALARM SYSTEM

by I. F. H. Goult

516

Invisible protection for your home

WASHER FLUID MONITOR

by A. R. Winstanley

532

Car screen washer warning

THERMOSTATIC SEED PROPAGATOR

by John Lewis

538

Warm up your seed trays

SERIES

TEACH-IN 84

by George Hylton

498

Part II: New Developments

ANATOMY OF YOUR MICRO

by Owen Bishop

508

Part Two: Data flow and memory

OSCILLATORS

by J. R. Davies

524

Part 3: Digital CMOS Devices

FEATURES

EDITORIAL

Funtronics Around The World

487

NEW PRODUCTS

Facts and photos of instruments, equipment and tools

497

EVERYDAY NEWS

What's happening in the world of electronics

502

FOR YOUR ENTERTAINMENT

by Barry Fox

507

Canal Turn; Video Opera; Digital Pictures

WHAT IS RADIATION?

by A. J. Bentley

512

Introduction; types of radiation

PLEASE TAKE NOTE

Spectrum Bench Power Supply (July 1984)

513

SQUARE ONE

Beginners' Page: CMOS Devices

515

RADIO WORLD

by Pat Hawker G3VA

523

In-Car Radio; Private Robot, Infantryman; Consumer Risks;

30-line Museum Piece

COUNTER INTELLIGENCE

by Paul Young

530

A retailer comments

SHOP TALK

by Dave Barrington

534

Product news and component buying

CIRCUIT EXCHANGE

A forum for readers' ideas

536, 540

PRINTED CIRCUIT BOARD SERVICE

541

Readers' Services • Editorial and Advertisement Departments

425

Multicore makes soldering

The Five Core Advantage

Only Multicore wire solders have a 5-core, or 4-core flux construction. The 5-cores identify non corrosive fluxes; the 4-core, water soluble fluxes.

If you were to slice through a section of Multicore cored solder you would see separate round cores of flux symmetrically arranged around its perimeter. Only a thin wall of solder separates the flux cores from the surface.

What are the advantages of the Multicore construction?

1. Because the flux is peripherally arranged it will react and flow faster.
2. Flux voids are eliminated with Multicore. That's why you can depend on continuity of the flux stream for complete wetting... every time.
3. Because wetting is faster, complete and uniform, you use less solder and transmit less heat to the joint area. With Multicore Solders, you get the highest purity metals, vigorous fluxing action and a wire solder that meets all applicable International standards.



Ersin Multicore

Contains 5 cores of non-corrosive flux.
Uses: For all electrical joints.
Handy Pack: Size 19A 60/40 tin/lead 1.22mm dia
£1.50
Tool Box Reel: Size 3 60/40 tin/lead 1.6mm dia
£4.37



Multicore Savbit

Increases the life of your soldering bit by 10 times.
Uses: For all electrical work.
Reduces copper erosion.
Handy Pack: Size 5 1.2mm dia **£1.38**
Tool Box Reel: Size 12 1.2mm dia **£4.37**



Ersin Multicore

Contains 5 cores of non-corrosive flux.
Uses: Small transistors, components and fine wire
Handy Pack: Size PC115 60/40 tin/lead 0.7mm dia
£1.61
Tool Box Reel: Size 10 60/40 tin/lead 0.7mm dia **£4.37**



All prices stated are Recommended Retail and include VAT

MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY
THIS IS THE AGE OF ELECTRONICS!
the world's fastest growth industry...

Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer. All the training can be carried out in the comfort of your own home and at your own pace.

A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE!
COLOUR
BROCHURE

Please send your brochure without any obligation to

I am interested in:

NAME _____
ADDRESS _____

- COURSE IN ELECTRONICS as described above
 RADIO AMATEUR LICENCE
 MICROPROCESSORS
OTHER SUBJECTS please state below

Post now to:

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 1BR



OR TELEPHONE US
0734 51515 OR
TELEX 22758
(24 HR SERVICE)

ng easy, fast and reliable

Multicore Solder Cream
Mixture of powdered 60/40 (tin/lead metal alloy and rosin flux).
Uses: Micro electronics and printed circuits.
Handy Tube: Size BCR 10
£1.73



Bib Wire Strippers and Cutters
With precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.
Wire Strippers: Size 9
£2.88



Multicore All Purpose Handyman Solder Pak
Contains three types of solder for electrical, metal and aluminium repairs, all in handy easy to use dispensers.
Handy Pak: Size 8
£2.99

Multicore Alu-Sol
Contains 4 cores of flux.
Uses: Suitable for aluminium and aluminium alloys. (non-electrical).
Handy Dispenser: Size HP27
1.6mm dia £0.99
Tool Box Reel: Size 4
1.6mm dia £7.82



Multicore Solder Wick
Absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.
Handy Pack: Size AB10
£1.43



Bib Audio/Video Products Limited,
(Solder Division),
Kelsey House, Wood Land End,
Hemel Hempstead, Hertfordshire, HP2 4RQ
Telephone: (0442) 61291 Telex: 82363



If you have difficulty in obtaining any of these products send direct adding 50p for postage and packing. For free colour brochure and Hints on soldering booklet send S.A.E.

MOTORIZED GEARBOX

As featured in 'Computer Control of Small Vehicles' in May issue. Complete set of components (not PCB) + Gearbox & Wheels (as recommended by the authors) for £37.



These units are as used in a computerized tank, and offer the experimenter in robotics the opportunity to buy the electro-mechanical parts required in building remote controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors etc. £5.95. Suitable wheels also available: 3" Dia plastic with blue tyre, drilled to push-fit on spindle, 2 for £1.30 (limited qty). 3" dia aluminium disc 3mm thick, drilled to push-fit on spindle, 2 for 68p.

NICAD CHARGERS

Versatile unit for charging AA, C, D and PP3 batteries. Charge/test switch, LED indicators at each of the 5 charging points. Mains powered. 210 x 100 x 50mm £7.95.
Model A124. Unit plugs directly into 13A socket, and will charge up to 4 AA cells at a time. Only £4.80.

NICAD BATTERIES

AA size 99p each; C size 199p; D size 220p; PP3 size 395p.

SPECIAL!! 6 x 'D' size, only £11.00!!

THE 1984 GREENWELD 84 PAGE CATALOGUE NOW AVAILABLE!!

It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1.00!

ROTATING Einstein COLOUR MICRO COMPUTER

- ★ 64k RAM + 16k for Display
- ★ Built-in Disc Drive, 500k
- ★ 16 colours, 32 sprites
- ★ Runs CP/M
- ★ 3 Channel Sound
- ★ Proper keyboard
- ★ RS232 Interface
- ★ Centronics printer port
- ★ Monitor or UHF Output
- ★ Switched mode PSU

All for £499.95

14" Colour Monitor £240.35
Dot Matrix Printer £228.85

Send for Colour Brochure

Official orders welcome - minimum invoice charge £10. No. min. on CWO. Goods normally despatched by return of post. Our shop has enormous stock of components and is open from 9.30 Mon-Sat. Come & see us!

GREENWELD
443D Millbrook Road Southampton
SO1 0HX Tel (0703) 772501/783740
ALL PRICES INCLUDE VAT: JUST ADD 60p P&P

KITS FROM £7 ...TO £60

Sparkrite

Buy Sparkrite Brand Leading Auto Electronics in self-assembly kit form - And save pounds!!

- Electronic Ignition systems - contact triggered and contactless
- Electronic Car Security Systems - including a new ultrasonic unit
- Car Drive Computer - with 12 functions

SEND FOR FREE LITERATURE PACK - TODAY!

8 SOPHISTICATED KITS TO CHOOSE FROM.



SPARKRITE (A Division of Stadium Ltd.), Queensway, Enfield, EN3 4SD.
Telephone: 01-804 4343

NAME

ADDRESS

Rapid Electronics

MAIL ORDERS:
Unit 3, Hill Farm Industrial Estate,
Boxed, Colchester, Essex CO4 5RD.
Tel. Orders: Colchester (0206) 36412.
Telex: 987756.

ACCESS AND
BARCLAYCARD
WELCOME

MIN. D CONNECTORS

| | | | |
|------------------|-----------|-----------|--------|
| 9 way | 15 way | 25 way | 37 way |
| Plugs solder lug | 60p 85p | 125p 170p | |
| Right angle | 120p 180p | 240p 350p | |
| Sockets lug | 90p 130p | 195p 290p | |
| Right angle | 160p 210p | 290p 400p | |
| Covers | 100p 90p | 100p 110p | |



SOLDERING IRONS

| | |
|--------------------------------|-----|
| Antex CS 17W Soldering Iron | 495 |
| 2.3 and 4.7mm bits to suit | 85 |
| CS 17Wor XS 25W element | 210 |
| Antex XS 25W | 525 |
| 3.3 and 4.7mm bits to suit | 85 |
| Solder pump (desoldering tool) | 490 |
| Spare nozzle for above | 70 |
| 10 metres 22swg solder | 100 |

CONNECTORS

| | |
|--------------------------------|------|
| DIN Plug Slt Jack Plug Slt | |
| 2 pin 9p 9p 2.5mm 10p 10p | |
| 3 pin 12p 10p 3.5mm 9p 9p | |
| 5 pin 13p 11p Standard 16p 20p | |
| Phono 10p 12p Stereo 24p 25p | |
| 1mm 12p 13p 4mm 18p 17p | |
| UHf (CB) Connectors: | |
| PL259 Plug 40p. Reducer 14p. | |
| SO2295 square chassis skt 30p. | |
| SO2295 round chassis skt 40p. | |
| IEC 3 pin 250V/6A | |
| Plug chassis mounting | 38p |
| Socket free hanging | 60p |
| Socket with 2m lead | 120p |

SCRs

| | |
|----------|----|
| 400V BA | 30 |
| 400V 12A | 95 |

VOICE SYNTHESISER!

Now your computer can talk.
The GI SP0256 speech processor is able through stored program to synthesise speech. Allophone (extended phoneme) system gives unlimited vocabulary.
Easily interfaced with any digital system. TTL compatible signals are used to select the allophones.
SP0256AL2 550 Data: 50p.

MICRO

| | | | |
|---------------|---------------|------------|--------------|
| 2114L2 200 | 6551 ACIA 650 | 81LS96 85 | 8259 390 |
| 2716 295 | 6800 CPU 220 | 81LS97 85 | MC1488 55 |
| 2532 290 | 6802 CPU 250 | 80B0A 250 | MC1489 55 |
| 2712B 25 2150 | 6809 CPU 620 | 80BSAC 340 | Z80A CPU 290 |
| 2732 440 | 6810 RAM 115 | 8156 350 | Z80APIO 260 |
| 2764-88C 680 | 6821 140 | 8212 110 | Z80A CTC 260 |
| 2764 600 | 6840 660 | 8216 100 | Z80ASIO 900 |
| 4116P20 85 | 6850 110 | 8224 120 | Z80ADMA 1150 |

COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. **W 5%**
Resistor kit. Contains 10 of each value from 4.7ohms to 1M (total of 650 resistors) 530
Ceramic Cap. kit. 5 of each value - 22p to 0.01u (135 caps) 370
Polyester Cap. kit. 5 of each value from 0.01 to 1uF (65 caps) 575
Resist kit. Contains 5 of each value from 100 ohms to 1M (total 65 resistors) 425
Nut and Bolt kit (total 300 items): 180p
25 6BA 1/2" bolts 50 6BA washers 50 6BA nuts
25 6BA 3/4" bolts 25 4BA 1/2" bolts 50 6BA washers
50 6BA nuts 25 6BA 3/4" bolts.

SWITCHES

Submit toggle.
SPST 50p. SPDT 60p. DPDT 65p.
Miniature toggle.
SPDT 90p. SPDT centre off 90p.
DPDT 90p. DPDT centre off 100p.
Standard toggle.
SPST 35p. DPDT 40p.
Miniature DPDT slide 14p.
Push to make 14p.
Push to break 22p.
Rotary type adjustable stop.
1P12W, 2P6W, 3P9W all 55p each.
DIL switches:
4SPST 80p 6 SPST 80p. BSPST 100p.

SOCKETS

| Low profile | Wire-wrap |
|-------------|-----------|
| 8 pin 6p | 28p |
| 14 pin 8p | 45p |
| 16 pin 9p | 55p |
| 18 pin 12p | 60p |
| 20 pin 13p | 68p |
| 22 pin 16p | 75p |
| 24 pin 18p | 82p |
| 28 pin 23p | 95p |
| 40 pin 25p | 135p |

LINEAR

| | | | | | |
|---------------|--------------|-----------|------------|-----------|----------|
| 555CMOS 80 | ICL7106 680 | LM339 40 | LM3911 120 | NE566 140 | TL064 96 |
| 556CMOS 150 | ICL7611 95 | LM348 60 | LM3914 225 | NE567 100 | TL071 30 |
| 709 25 | ICL7621 180 | LM358 50 | LM3915 225 | NE570 370 | TL072 45 |
| 741 14 | ICL7622 180 | LM377 170 | LM3916 105 | NE571 375 | TL073 45 |
| 748 35 | ICL8038 295 | LM382 120 | LM3920 120 | PC4136 55 | TL081 25 |
| 9400CJ 350 | ICL8211A 200 | LM382 120 | LM3921 120 | PC4558 40 | TL082 45 |
| AY-3-1270 720 | ICM7224 785 | LM382 120 | LM3922 120 | SL480 170 | TL084 90 |
| AY-3-8910 370 | ICM7555 80 | LM382 120 | LM3923 120 | SL480 170 | TL084 90 |
| AY-3-8912 540 | ICM7555 80 | LM382 120 | LM3924 120 | SL480 170 | TL084 90 |
| CA3046 60 | LF353 48 | LM382 120 | LM3925 120 | SL480 170 | TL084 90 |
| CA3080 85 | LF353 48 | LM382 120 | LM3926 120 | SL480 170 | TL084 90 |
| CA3089 190 | LM101 325 | LM382 120 | LM3927 120 | SL480 170 | TL084 90 |
| CA3090AQ 375 | LM301A 50 | LM382 120 | LM3928 120 | SL480 170 | TL084 90 |
| CA3130E 85 | LM311 70 | LM382 120 | LM3929 120 | SL480 170 | TL084 90 |
| CA3140E 36 | LM318 120 | LM382 120 | LM3930 120 | SL480 170 | TL084 90 |
| CA3161E 100 | LM324 100 | LM382 120 | LM3931 120 | SL480 170 | TL084 90 |
| CA3189 290 | LM334Z 100 | LM382 120 | LM3932 120 | SL480 170 | TL084 90 |
| CA3240E 100 | LM335Z 125 | LM382 120 | LM3933 120 | SL480 170 | TL084 90 |

TRANSISTORS

| | | | | | | |
|-----------|-----------|----------|----------|-----------|-----------|------------|
| AC126 30 | BC149 9 | BC547 40 | BF337 40 | MPSU56 60 | ZTX108 10 | 2N3055 50 |
| AC127 30 | BC157 8 | BC548 10 | BF394 23 | TIP29A 30 | ZTX109 12 | 2N3442 120 |
| AC128 30 | BC158 8 | BC549 10 | BF498 23 | TIP29B 55 | ZTX300 30 | 2N3702 8 |
| AC176 25 | BC160 45 | BC550 10 | BF499 23 | TIP29C 37 | ZTX301 16 | 2N3703 9 |
| AC187 22 | BC168C 10 | BC551 10 | BF529 25 | TIP30A 35 | ZTX302 18 | 2N3704 8 |
| AC188 22 | BC169C 10 | BC552 10 | BF530 25 | TIP30B 50 | ZTX303 17 | 2N3705 9 |
| AD142 120 | BC170 8 | BC553 10 | BF531 25 | TIP30C 37 | ZTX304 17 | 2N3706 9 |
| AD149 80 | BC171 8 | BC554 10 | BF532 25 | TIP30D 37 | ZTX305 17 | 2N3707 9 |
| AD161 40 | BC172 8 | BC555 10 | BF533 25 | TIP30E 37 | ZTX306 17 | 2N3708 9 |
| AD162 40 | BC177 18 | BC556 10 | BF534 25 | TIP30F 37 | ZTX307 17 | 2N3709 9 |
| AF124 60 | BC179 18 | BC557 10 | BF535 25 | TIP30G 37 | ZTX308 17 | 2N3710 9 |
| AF126 50 | BC180 18 | BC558 10 | BF536 25 | TIP30H 37 | ZTX309 17 | 2N3711 9 |
| AF139 40 | BC182 10 | BC559 10 | BF537 25 | TIP30I 37 | ZTX310 17 | 2N3712 9 |
| AF186 70 | BC182L 8 | BC560 10 | BF538 25 | TIP30J 37 | ZTX311 17 | 2N3713 9 |
| AF239 75 | BC183 10 | BC561 10 | BF539 25 | TIP30K 37 | ZTX312 17 | 2N3714 9 |
| BC107 10 | BC183L 10 | BC562 10 | BF540 25 | TIP30L 37 | ZTX313 17 | 2N3715 9 |
| BC107B 12 | BC184 10 | BC563 10 | BF541 25 | TIP30M 37 | ZTX314 17 | 2N3716 9 |
| BC108 12 | BC184L 7 | BC564 10 | BF542 25 | TIP30N 37 | ZTX315 17 | 2N3717 9 |
| BC108B 12 | BC212 10 | BC565 10 | BF543 25 | TIP30O 37 | ZTX316 17 | 2N3718 9 |
| BC108C 12 | BC212L 10 | BC566 10 | BF544 25 | TIP30P 37 | ZTX317 17 | 2N3719 9 |
| BC109 10 | BC213 10 | BC567 10 | BF545 25 | TIP30Q 37 | ZTX318 17 | 2N3720 9 |
| BC109C 12 | BC213L 10 | BC568 10 | BF546 25 | TIP30R 37 | ZTX319 17 | 2N3721 9 |
| BC114 18 | BC214 10 | BC569 10 | BF547 25 | TIP30S 37 | ZTX320 17 | 2N3722 9 |
| BC115 22 | BC214L 8 | BC570 10 | BF548 25 | TIP30T 37 | ZTX321 17 | 2N3723 9 |
| BC117 18 | BC237 8 | BC571 10 | BF549 25 | TIP30U 37 | ZTX322 17 | 2N3724 9 |
| BC119 36 | BC238 12 | BC572 10 | BF550 25 | TIP30V 37 | ZTX323 17 | 2N3725 9 |
| BC137 40 | BC309 12 | BC573 10 | BF551 25 | TIP30W 37 | ZTX324 17 | 2N3726 9 |
| BC139 40 | BC327 14 | BC574 10 | BF552 25 | TIP30X 37 | ZTX325 17 | 2N3727 9 |
| BC140 28 | BC338 14 | BC575 10 | BF553 25 | TIP30Y 37 | ZTX326 17 | 2N3728 9 |
| BC141 30 | BC337 14 | BC576 10 | BF554 25 | TIP30Z 37 | ZTX327 17 | 2N3729 9 |
| BC142 25 | BC338 14 | BC577 10 | BF555 25 | TIP30A 37 | ZTX328 17 | 2N3730 9 |
| BC143 25 | BC339 14 | BC578 10 | BF556 25 | TIP30B 37 | ZTX329 17 | 2N3731 9 |
| BC147 8 | BC340 14 | BC579 10 | BF557 25 | TIP30C 37 | ZTX330 17 | 2N3732 9 |
| BC148 8 | BC341 14 | BC580 10 | BF558 25 | TIP30D 37 | ZTX331 17 | 2N3733 9 |

The Rapid Guarantee
★ Same day despatch ★ Competitive prices
★ Top quality components ★ In-depth stocks

CABLES

| |
|---|
| 20 metre pack single core connecting cable ten different colours. 75p |
| Speaker cable .10p/m |
| Standard screened 16p/m |
| Twin screened 24p/m |
| 2.5A 3 core mains 22p/m |
| 10 way rainbow ribbon 26p/ft |
| 20 way rainbow ribbon 47p/ft |
| 10 way grey ribbon 14p/ft |
| 20 way grey ribbon 28p/ft |

HARDWARE

| | |
|-------------------------------|-----|
| PP3 battery clips | 6 |
| Red or black crocodile clips | 6 |
| Black pointer control knob | 15 |
| Ultrasonic transducers | 390 |
| 6V Electronic buzzer | 60 |
| 12V Electronic buzzer | 65 |
| PB2720 Piezo transducer | 75 |
| 64mm 8 ohm speaker | 70 |
| 64mm 4 ohm speaker | 70 |
| 20mm panel fuseholder | 25 |
| Red or black probe clip | 35 |
| 4mm terminals | 33 |
| 12 way 'chocolate' block | 30 |
| ultra-min. 6 or 12v rel. SPDT | 130 |
| ditto, but DPDT | 195 |

CAPACITORS

| |
|---|
| Polyester, radial leads. 250v. C280 type: 0.01, 0.015, 0.022, 0.033 - 10p, 0.047, 0.068, 0.1 - 7p, 0.18, 0.22 - 9p; 0.33, 0.47 - 13p; 0.68 - 20p; 1u - 73p |
| Electrolytic, radial or axial leads: 4.7/63V, 1.6/3V, 2.2/63V, 4.7/25V, 10/25V - 7p; 22/25V, 47/25V - 8p; 100/25V - 9p; 220/25V - 14p; 470/25V - 22p; 1000/25V - 30p; 2200/25V - 50p |
| Tag and power supply electrolytics: 2200/40V - 110p; 4700/40V - 160p; 2200/63V - 140p; 4700/63V - 210p; 2200/100V - 100p; 4700/100V - 150p; 2200/150V - 150p; 4700/150V - 210p; 2200/200V - 210p; 4700/200V - 210p; 2200/250V - 210p; 4700/250V - 210p |
| Tantalum bead: 0.1, 0.22, 0.33, 0.47, 1.0 @ 35V - 12p; 2.2, 4.7, 10 @ 25V - 20p; 15/16V - 30p; 22/16V - 27p; 33/16V - 45p; 47/16V - 27p; 47/16V - 90p; 68/16V - 40p; 100/10V - 90p. Cer. disc. 2p-0.01u 50p, 3p each. Multilayer miniature ceramic plug: 1.8p F to 1000F 6p each. |
| Polyethylene, 5% tol: 10p-1000p, 6p; 1500-4700, 8p; 6800-0.012u, 3p. Trimmers. Multilayer 808 series: 2-10 pF, 22p; 2-22pF, 30p; 5.5-65pF, 35p |

REGULATORS

| | |
|------------|-----------|
| 78L05 30 | 75L05 45 |
| 78L12 30 | 78L12 45 |
| 78L15 30 | 78L15 45 |
| 7805 35 | 7805 40 |
| 7812 35 | 7812 40 |
| 7815 35 | 7815 40 |
| LM309K 130 | LM723 35 |
| LM317K 270 | 78H05 550 |
| LM323K 420 | |

EURO CONNECTORS

| | | |
|--------------|-----------|-----------|
| Gold flashed | Rt. angle | Wire-wrap |
| contacts | plug | socket |
| 64 way A+B | 195 | 230 |
| 64 way A+C | 220 | 270 |
| 96 way A+B+C | 320 | 330 |

DIODES

| | |
|----------|----------------|
| BY127 12 | 1N4002 5 |
| 0A47 10 | 1N4006 7 |
| 0A90 8 | 1N4007 7 |
| 0A200 8 | 1N5401 12 |
| 0A202 8 | 1N5404 16 |
| 1N914 4 | 400mWzen 6 |
| 1N4148 3 | 1.3W zeners 13 |

OPTO

| | |
|---------------|---------------|
| 3mm red 7 | 5mm red 7 |
| 3mm green 10 | 5mm green 10 |
| 3mm yellow 10 | 5mm yellow 10 |

JUMPER LEADS

| | | | | |
|--|-------|-------|-------|-------|
| Length | 14pin | 16pin | 24pin | 40pin |
| Single ended DIP (header plug) jumper | 50 | 50 | 50 | 50 |
| SPECTRUM 2 x 28 way edge connector wire-wrap | 200 | | | |
| Dble ended DIP (header plug) jumper | 50 | | | |
| 25 way D Connector jumpers: | | | | |
| 18ins. long single ended male 495p. | | | | |
| 18ins. long single ended f/male 525p. | | | | |

COMPUTER CONNECTORS

| | |
|---|-----|
| ZXB1 2 x 23 way edge connector wire-wrap for ZKB1 | 150 |
| 24 way IEEE IDC | 450 |
| 32 way Centronics IDC | 490 |

RIBBON CABLE

| | |
|------------------------------------|---------------|
| Grey Ribbon cable. Price per foot: | |
| 10 way | 14 34 way 58 |
| 16 way | 18 40 way 68 |
| 20 way | 28 50 way 90 |
| 26 way | 38 60 way 100 |

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w of lighting

- TDR300K Remote Control Dimmer £14.95
- MK5 Transmitter for above £4.50
- TD300K Touchdimmer £7.75
- TS300K Touchswitch £7.75
- TDE/R Extension kit for 2-way switching for TD300K £2.50
- LD300K Rotary Controlled Dimmer £3.95



DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7108 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter; only a few additional resistors and switches are required (details supplied) or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day for 7 days a week. **Price £15.50**

JK113 MW RADIO KIT
Based on ZN414 IC, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cm. Requires PP3 9V battery. IDEAL FOR BEGINNERS. **£5.50**

ELECTRONIC LOCK KIT

With hundreds of uses in doors, garages, car anti-theft devices, electronic equipment etc. Only the correct easily changed four digit code will open it! Requires a 5 to 15V dc supply. Output 750mA. Fits into standard electrical wall box. Complete kit (excl. front panel) **JK101 £11.50**

Electronic lock mechanism for use with the above kit. **70150 £14.95**

WE ALSO STOCK A WIDE RANGE OF ELECTRONIC COMPONENTS

SEE CATALOGUE FOR DETAILS

MINI KITS

- MK1 ELECTRONIC THERMOSTAT Uses LM3911 IC to sense temperature (80°C max) and trace to switch heater (1KW). Mains powered. **£4.80**
- MK2 SOLID STATE RELAY Switches 240V ac motors, lights, heaters from logic/computer circuits. Zero voltage switching, opto isolated. Supplied without trace. **£2.90**
- MK4 PROPORTIONAL TEMPERATURE CONTROLLER Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine making, etc. Max load 3KW (240V ac). Temp. range up to 90°C. **£6.50**
- MK5 MAINS TIMER Mains powered timer enabling a load up to 1KW at 240V ac to be switched on (or off) for a variable time from 20 mins to 35 hrs. Longer or shorter periods possible with minor component changes. **£6.50**
- MK16 DUAL LATCHED SOLID STATE RELAY Comprises two MK12s with latch circuit enabling the MK12s to control two mains loads independently. Two output traces not supplied. (See remote control kits.) **£6.50**

NEW! MK19 DC CONTROLLED AUDIO AMPLIFIER
May be used with virtually any stereo audio amplifier to control bass, volume, treble and balance remotely either using a wire link or the MK11 infra red receiver. A 1 of 10 decoder with LEDs is also included for remote input selection/display. (See remote control kits.) **£10.70**

3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS. Order as **XX 102. £5.50**

INFRA RED GARAGE DOOR CONTROLLER KIT



For opening and closing motorised garage doors plus switching garage and drive lights on and off up to a range of

40ft and numerous other applications like controlling lights and TV's etc. in the home. Ideal for aged or disabled persons, this coded kit comprises of a mains powered infra red remote control receiver with a normally open relay output plus two latched transistor outputs; battery-powered four button transmitter and an opto isolated solid state mains switch. As with all our kits, full instructions are supplied.

JK103 £25

Extra transmitters

JK105 £10.00

MICROPROCESSOR CONTROLLED MULTI-PURPOSE TIMER



Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, eg. to control your central heating (including different switching times for weekends!), just connect it to your system programme and set it and forget it - the clock will do the rest.

NOW ONLY £39.00

- 7mm LED 12 hour display
- Day of week, am/pm and output status indicators
- 4 open collector outputs for driving relays, traces, etc.
- 50/60Hz mains operation
- Battery backup saves stored programmes and continues time keeping during power failures (Battery not supplied)
- Display blanking during power failure to conserve battery power
- 18 programme time sets
- Powerful "Everyday" function enabling output to switch everyday but use only one time set
- Useful "sleep" function - turns on output for one hour
- Direct switch control enabling output to be turned on immediately or after a specified time interval
- 20 function keypad for programme entry

(Kit includes all components PCB, box assembly and programming instructions)
Order as **CT16000**

JK114 OPTIONAL RELAY KIT
Kit includes one relay, PCB to accommodate up to 4 relays, terminal blocks, etc., to fit inside CT16000 box. Provides up to 4amp 240V AC changeover contacts. **£3.90**
Additional relays **£1.65 each**

COMPONENT PACKS

- PACK 1 650 Resistors 47 ohm to 10 Mohm - 10 per value **£8.00**
- PACK 2 40 x 16V Electrolytic Capacitors 100µF to 1000µF - 5 per value **£3.25**
- PACK 3 60 Polyester Capacitors 0.01 to 1µF 250V - 5 per value **£5.55**
- PACK 4 45 Sub miniature Presets 100 ohm to 1 Mohm - 5 per value **£2.90**
- PACK 5 30 Low Profile IC Sockets 8, 14 and 16 pin - 10 of each **£2.40**
- PACK 6 25 Red LEDs 5mm dia **£1.50**

HOME CONTROL CENTRE

This kit enables you to control up to 16 different appliances by means of coded pulses in the mains wiring which may be decoded by special receivers anywhere in the house. The transmitter may be controlled manually or by the computer interface enabling your favourite morning, switch lights anywhere in the house, or your electric blanket in your bedroom. Just think of the possibilities - and no wiring!



The Kit comprises a transmitter with pre-drilled box and two receivers.

JK112 £42.00

ADDITIONAL RECEIVERS

JK111 £10.00

DISCO LIGHTING KITS

DL 1000K
This value for money kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers and incorporates a master dimming control. **£15.95**

DL 21000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **£8.95**

Optional opto input DLA1
Allowing audio ("beat") - light response **60p**

DL3000K
This 3 channel sound to light kit features zero voltage switching, automatic level control and built-in mic. No connections to speaker or amp required. No knobs to adjust - simply connect to mains supply and lamps. (15w channels) **Only £12.95**

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kw on and off at preset times once per day. Kit contains: **AY5-1230 IC**, 0.5" LED display, mains supply, display drivers, switches, LEDs, traces, PCBs and full instructions.

CT1000K Basic Kit £14.90
CT1000K with white box (56x131 x 71mm) £17.40
(Ready Built) **£22.50**

LCD 3 1/2 DIGIT MULTIMETER

19 ranges including DC voltage (200mV-100V) and AC voltage, DC current (200mA-10A) and resistance (0 - 2M) Ω NPN & PNP transistor gain and diode check. Input impedance 10M. Size 180 x 140 x 50mm. Complete with battery, test leads and carrying case. **ONLY £32.00**

REMOTE CONTROL KITS

These kits have been designed to enable infra red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The exact application will determine the interface circuitry required between the receiver and the device to be controlled. In many cases this could be a relay or trace. General instructions and applications are supplied with the kits. The kits are coded and provide a high degree of noise immunity and security.

- MK18 Transmitter Kit For use with MK17 MK12 Receivers and MK18 13 keyboards. Requires PP3 battery. Size 8.2 x 1.3 cms. Range approximately 60ft. **£1.80**
 - MK11 Receiver Kit Mains powered. Provides 10 latched plus 3 analogue outputs. Ideal for controlling audio amplifiers, TV or lighting circuits where control of lamp brightness is required. **£13.50**
 - MK13 Transmitter Keyboard **£4.35**
 - MK18 DC Controlled Stereo Amplifier Kit. If control of stereo amplifiers required the MK19 may be used providing for remote control of base, treble and volume for balance. This kit also includes a one of 10 decoder with LEDs for remote selection of programme or channel. May be connected between the pre-amp and power amp sections of almost any audio amplifier. **£10.70**
 - MK12 Receiver Kit. Mains powered. Provides up to 16 latched or momentary on/off outputs. This latched version is suitable for applications where only one of the 16 outputs is to be on at any one time, eg. TV channel selection. The momentary version provides an output only during transmission. Lines may be latched separately if required (extra supply). This may be used in conjunction with the MK15 Dual Latched Solid State Relay to switch mains loads, eg. radio, lights, TV. **£13.50**
 - MK12 Stereo Latched or Momentary Kit **£13.50**
 - MK10 16 way Transmitter Keyboard **£5.40**
 - MK15 Dual Latched Solid State Relay **£6.50**
- SINGLE CHANNEL UNCODED INFRA RED KITS**
- MK6 Transmitter - supplied with hand held plastic box. Requires a 9V PP3 battery. Range approximately 20ft. **£4.50**
 - MK7 Receiver - Mains powered with infra output to switch up to 500W at 240V ac. On/off momentary output available. **£10.50**
 - MK16 Mains Powered Transmitter for continuous operation such as burglar alarms, automatic door operators, etc. Range approximately 6ft. May also be powered from 9v dc. **£3.50**
 - MK17 12V dc Receiver for use with MK6 or MK16. Relay output with DP 3A change over contacts. May be used as latched momentary or break beam receiver. Operates from 6.13V dc. **£10.50**

Send SAE 9" x 6" for our FREE YELLOW CATALOGUE. It's packed with a full list of our stock range all at very competitive prices.

Add 65p postage & packing + 15% VAT to total Overseas Customers;
Add £2.50 (Europe), £6.00 (elsewhere) for p&p
Send S.A.E. for further STOCK DETAILS.
Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri)
10am to 4pm (Sat)

COMPUTER SHOWROOM TOP HARDWARE, LATEST SOFTWARE PERIPHERALS, ACCESSORIES AND MUCH, MUCH MORE!

FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to -



ELECTRONICS

11-13 Boston Road
London W7 3SJ

01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL AFTER 3PM



ALL PRICES EXCLUDE VAT

EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 13 NO. 8 AUGUST 1984

Editor
MIKE KENWARD

Secretary
PAULINE MITCHELL

Consultant Editor
FRED BENNETT

Assistant Editors
DAVE BARRINGTON (Production)
DAVID SHORTLAND (Technical)

Technical Editor
MIKE ABBOTT

Projects Editor
DAVID BRUNSKILL

Technical Sub-Editors
RICHARD BARRON
BRIAN BUTLER

Art Editor
JACK POUNTNEY

Assistant Art Editor
KEITH WOODRUFF

Senior Technical Illustrator
JOHN PICKERING

Technical Illustrator
ISABELLE GREENAWAY

Editorial Offices
EVERYDAY ELECTRONICS EDITORIAL
WESTOVER HOUSE
WEST QUAY ROAD, POOLE, DORSET BH15 1JG
Phone: Poole (0202) 671191
We regret that lengthy technical enquiries
cannot be answered over the telephone

Advertisement Manager
DAVID TILLEARD 01-261 6676

Secretary
CHRISTINE POCKNELL 01-261 6676

Advertisement Sales Executives
ALFRED TONGE 01-261 6819
RICHARD WILLETT 01-261 6865

Classified Supervisor
BARBARA BLAKE 01-261 5897

Advert Make-Up and Copy Department
JULIE FISH 01-261 6615

Advertisement Offices
EVERYDAY ELECTRONICS ADVERTISEMENTS
KING'S REACH TOWER
STAMFORD STREET
LONDON SE1 9LS
Telex 915748 MAGDIV-G

Readers' Enquiries

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope or International reply coupons.

We cannot undertake to engage in lengthy discussions on the telephone.

Component Supplies

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

FUNTRONICS

PERHAPS one of the most enjoyable aspects of editing EE is that you never know what the post will bring, or who will phone up to discuss future projects or plans. The high standing and reputation for excellence that EE has achieved over the years, plus total issue sales that are 177 per cent that of our nearest rival, means that all sorts of individuals, companies and educational establishments have been and continue to be, deeply involved with the future of EE.

Just recently the post brought us a new idea for a page entitled *Funtronics*; the artwork came in "out of the blue" from a reader with whom we had had no previous contact. The page submitted was of a very high standard—good to look at, fun, interesting and informative to read. It has plenty of good data, cartoons, puzzles, tables, etc. and must be rated as one of the best innovations in EE ever. Furthermore, the man behind the idea and the artwork has plenty of exciting ideas that we hope will come into the page in the future. To get the flavour of *Funtronics*, see page 531 and don't miss the first one next month. You will not be disappointed!


AROUND THE WORLD

Also popping up in our postbag, and sometimes on the phone, are enquiries and requests from readers around the globe. It is not unusual for us to get phone calls from Scandinavia, Australia or almost anywhere else. Perhaps the most interesting aspect of such correspondence is the similarity in interests of hobbyists in electronics around the world. Obviously not all countries are at the same technical level as the UK, but most hobbyists seem to find ways of getting components and building our projects.

One recent letter from Portugal brought a complaint that we cover projects for computers and few people can yet afford such items. This shows how lucky we are in the UK where most of our readers own a microcomputer or at least have the use of one at work, school, college, evening institute or university. Perhaps we take such things for granted, but in many countries computers are still not widely available at realistic prices.

With every aspect of life being "invaded" by new technology, it will become more and more important to have some understanding of electronics and computing. It will also be necessary for many people, now employed in industries that are being modernised or ones that are becoming outdated, to be retrained. Our series on electronics and computing will provide an excellent grounding for all.

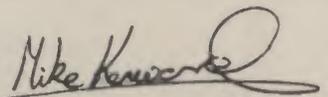The understanding that can be gained from *Anatomy of the Microcomputer* or our *Teach-In* series could provide the difference necessary to secure a promotion or even employment. We will continue to publish such information so that you can help yourselves!



Back Issues

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

Binders

Binders to hold one volume (12 issues) are available from the above address for £4.60 inclusive of postage and packing worldwide. Please state which Volume.

Subscriptions

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

KITCHEN APPLIANCE TIMER

T. R. de Vaux Balbirnie

ELECTRIC food mixers and blenders are common items in every modern kitchen. Although taking much of the hard work out of food preparation, most models have one major drawback. They do not have a built-in timer so a lot of time is wasted "clock watching". This simple project frees the hands of the busy cook by providing a mains power socket which switches on kitchen appliances for a selected time. Although designed principally for food mixers there could be other uses for this project, as an enlarger timer, for example.

The Kitchen Timed Outlet appears as a plastic box which plugs into the mains. A 13-amp socket, rotary switch and two push-button switches are mounted on top. The rotary switch selects the required time interval from a choice of eleven values or "continuous". The push-button switches initiate the process and end it prematurely if need me. Safety features include: a fuse, and a double-pole mains on-off switch with neon indicator.

The electronic part of the circuit is battery-powered for reasons of low cost and simplified construction. Excellent service should be given by the battery since it is totally disconnected from the circuit except while actually timing. The battery may be replaced without removing the lid of the case. Although construction is straightforward, this project does involve

making mains connections and readers are advised to seek help if they are unsure of their ability to make a safe job.

CIRCUIT DESCRIPTION

The circuit for the Timed Outlet is shown in Fig. 1. The timing section consists of a 555 timer integrated circuit and associated components. These are connected as a *monostable*. This means that when IC1 is triggered by taking pin 2 low, the output (pin 3) will go high for a time then revert to its original state. The time period is determined by the values of C1 and the "switched resistance" (R1 to R11). In this circuit C1 has a fixed value so timing depends on the value of the switched resistance (R1 to R11). The rotary switch, S1, selects R1 + R2 + R3, etc, to gain the required timing. VR1 is the calibration control whereby the timings are adjusted accurately. This is necessary since the value of C1 is not known precisely due to its range of tolerance.

The output of the 555 is far too small to operate mains equipment and this is where the relays RLA and RLB are necessary. Both these components have normally-open contacts. While IC1 is on, both relay coils will be energised. The contacts of RLB connect the appliance to

the mains. Meanwhile, the contacts of RLA short-circuit the "start" switch, S2. Thus, when S2 is pressed for an instant, the i.c. will be triggered by the pulse of charging current to C2 taking pin 2 low. The contacts of RLA then "take over" from S2 in allowing battery current to flow until the end of the timing cycle. Timing may be interrupted at any time by momentary breaking of battery current by means of S3 which is a push-to-break switch.

The reason for using *two* relays instead of just one component with two pairs of contacts, is to keep the battery and mains totally separate. This avoids the possibility of "flash over" from one set of contacts to the other.

D1 is necessary to prevent false triggering which could occur in its absence. No diode need be connected in parallel with either relay coil as would be normal practice, as RLA has a diode already built in which serves RLB also. A diode is important in by-passing the reverse voltage spike which occurs when the magnetic field in a relay core collapses.

MAINS RELAY

The choice of RLB deserves special mention. This component must have at least one pair of normally-open or changeover contacts. Readers who are not using the specified relay must give consideration to *contact current rating, coil operating voltage, coil resistance* and overall physical size.

For mixers and blenders a maximum load figure of 500 watts will be found adequate (that is, about 2 amps on 240V mains). The relay contacts must be rated to this figure at least. Catalogues often specify contact ratings for a *resistive* load; for a motor or other *inductive* load de-rating is necessary. In practice, a resistive contact rating of 5 amps will be satisfactory. The coil should operate from as low as 6 volts. Some relays have an 8.4 volt coil which is not suitable, especially as the battery ages. The relay coil should have as high a resistance as possible to minimise drain on the battery.



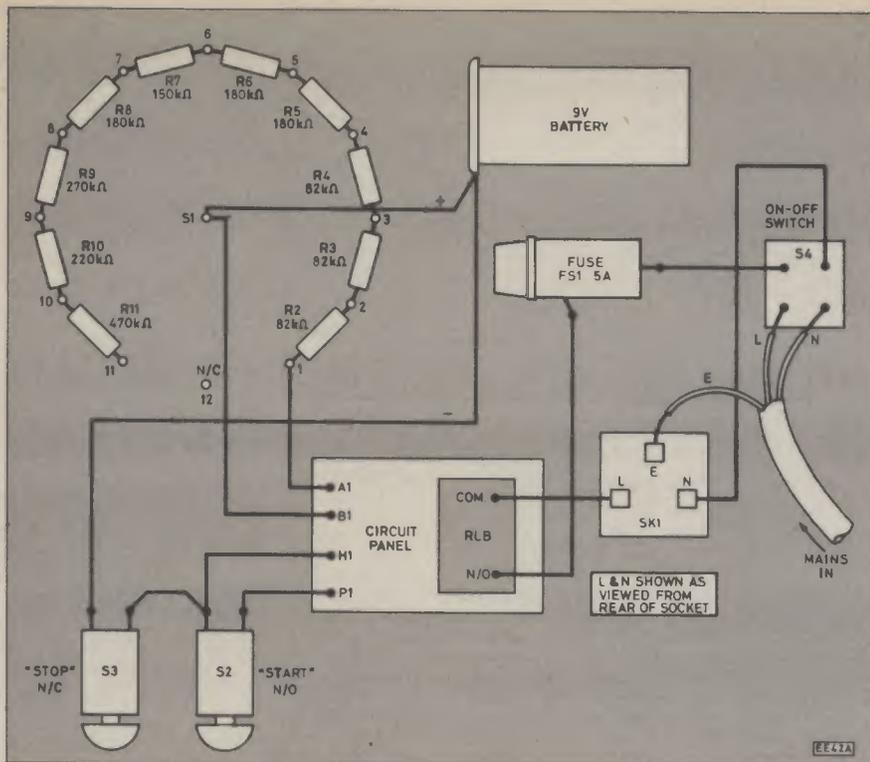


Fig. 2. Wiring details of the Kitchen Appliance Timer.

mounting and connecting details. After soldering the pins of RLB to the copper strips, these strips should then be broken in several places, as indicated, to isolate them from the battery part of the circuit. Carefully-made connections should be made to the normally-open contacts of RLB on the *topside* of the panel using 15 centimetres of 3A stranded wire. A careful check should be made to ensure that no contact connections to RLB make contact with the low voltage side of the panel.

Insert the 555 into its holder then solder 15 centimetres of connecting wires to each of the copper strips A, B, H and P. The rotary switch, S1, may now be prepared by soldering the resistors R2 to R11 around its contacts 1 to 11 (see photograph). Note that R1 is already on the circuit panel and contact 12 has no resistor connected to it as this is the "continuous" setting.

Prepare the case by making holes in the lid for the mains outlet socket and for S1, S2 and S3. Make holes in the side of the box for the mains on-off switch, fuse, inlet lead and battery drawer. All remaining components should be assembled and the wiring completed as in Fig. 2. Make a scale of times for S1 and fit this and the knob in position.

ON NO ACCOUNT MOUNT RLB BY BOLTING IT TO THE CASE. THIS IS BECAUSE THE FRAME OF THE RELAY IS "LIVE" AND THE HEADS OF THE BOLTS WOULD BE "LIVE" TOO.


TESTING

Before operating this project from the mains for the first time, it is essential to test it and adjust VR1 using a battery. To do this, connect the live and neutral pins of a discarded 13A plug to a 6-volt bulb. Plug this into the mains outlet socket to simulate the mixer. Connect the mains inlet wires to the terminals of a 6 or 9-volt battery. Adjust the slider of VR1 to approximately mid-track position. Place a PP3 battery in the drawer and the fuse in its holder. Set the mains switch to "on" and S1 to "15 seconds". Press S2. The lamp should light for a time then go off. VR1 may be adjusted for an accurate 15 seconds. Clockwise rotation of the slider will increase the time. Check operation on other time settings and adjust VR1 for best overall performance. Check the "stop" switch, S3.

When the system is operating correctly, *replace the lid of the case, plug a mixer into the outlet socket and test the unit on the mains. Never remove the lid of the case while the project is plugged in.*

OTHER APPLICATIONS

This timer can be used for any low power operation of mains equipment, such as photographic timers, hi fi or video application. □

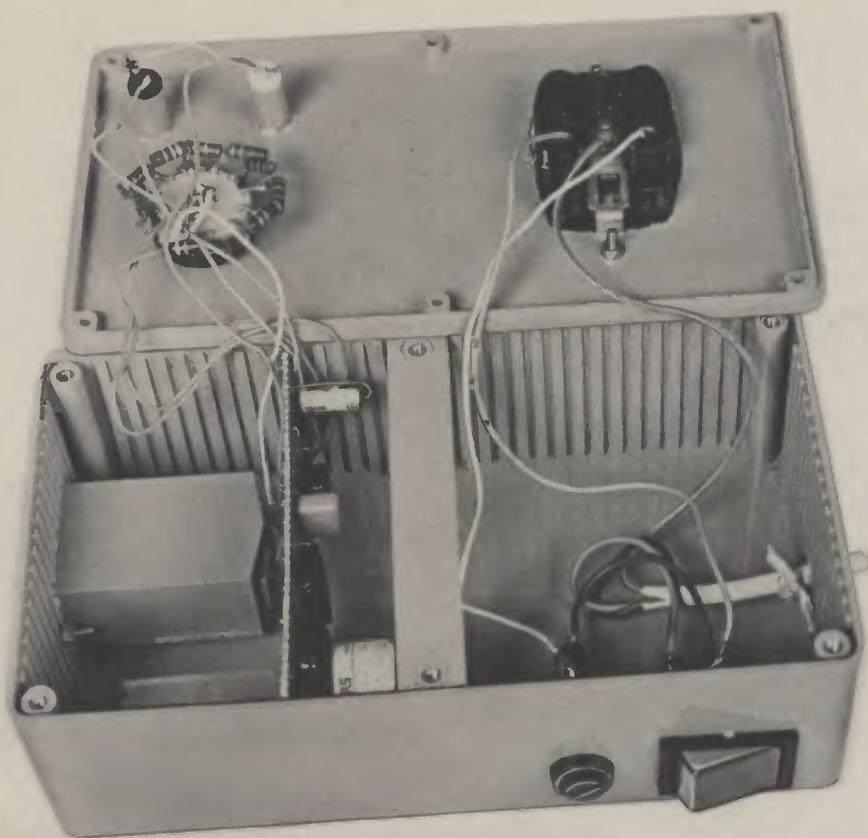

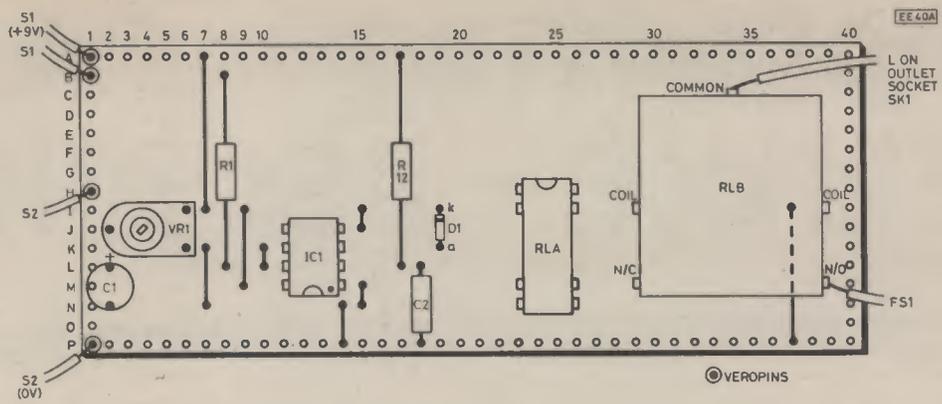


Fig. 3. Component layout of matrix stripboard for Kitchen Appliance Timer.


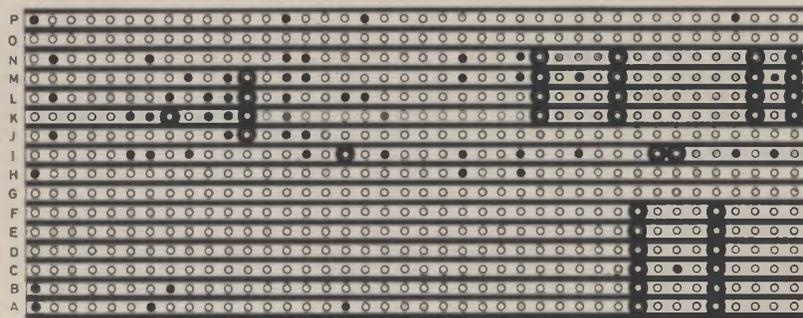


Fig. 4. Drilling details of matrix stripboard for Kitchen Appliance Timer.

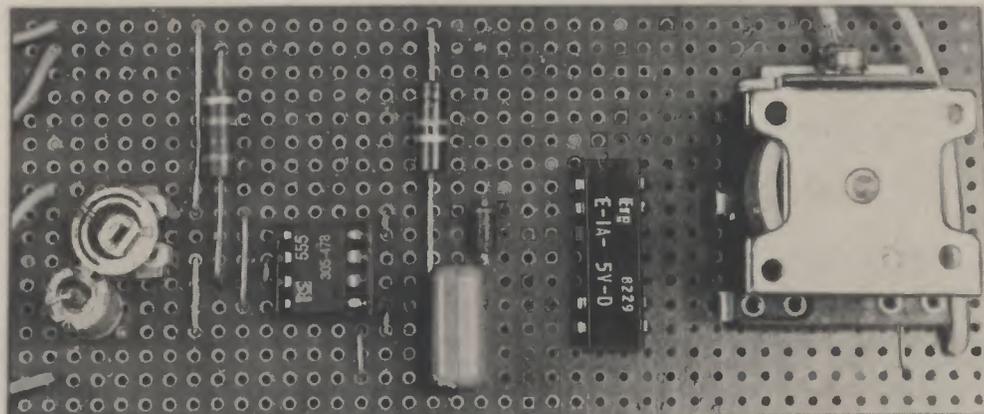

TEMPERATURE INTERFACE - BBC MICRO

R.A. PENFOLD

A HOME COMPUTER is ideal for use in many measurement applications since it can be used as a digital readout, or results can be displayed on the monitor or TV screen as a graph or in some similar form. With the aid of a suitable printer it is even possible to produce hard copies of graphs or charts.

This article describes a simple temperature interface for the BBC model B microcomputer, and it makes use of the machine's four channel analogue-to-digital converter. This converter has only a rather limited sampling rate of once every 40ms if all four channels are used, or once every 10ms if only channel 1 is used. However, in an application such as this the response time of the sensor is very slow and the limited sampling rate of the analogue-to-digital converter is of no consequence. The converter is a 12-bit type which gives the system good resolution, and as there are four inputs it is possible to simultaneously use up to four temperature interfaces with the unit.

The interface uses a semiconductor temperature sensor which gives good linearity and accuracy over a wide temperature range of -50 to +150 degrees centigrade.

THERMISTOR SENSOR

Perhaps the most obvious way of providing a temperature interface for the machine is to use a simple thermistor type such as the one outlined in Fig. 1. There are just two components used here; thermistor RTH1 and resistor R1. These are wired as a simple potentiometer connected between the 0V rail and the 1.8 volts reference output of the analogue port. The output of the divider circuit is connected to the channel 1 input of the analogue port. This responds to input voltages of between 0V and 1.8 volts, and the output of the potential divider must therefore be within the correct voltage range.

The specified thermistor is a negative temperature coefficient type, in that its resistance falls as the applied temperature is increased. Thus, increased temperature results in a higher voltage from the circuit, decreased temperature produces a lower output voltage, and it would be reasonably easy to devise software that would convert the values returned from

the A/D converter into the correct temperature values. A slight problem with this arrangement is that the linearity is only good over a fairly narrow range of temperatures, and this would complicate the software if a wide temperature coverage was required. Also, a very wide temperature range could not be achieved properly since the voltage changes produced at the extremes of the range would be inadequate.

One final problem is that if several circuits of this type were to be connected to the computer the software for each channel would need to be slightly different in order to compensate for the tolerances of the thermistors and resistors.

Despite these limitations, there are applications where a simple interface of this type will suffice, and where the use of a more sophisticated circuit would just be over complicating matters. With the circuit of Fig. 1 the nominal centre of the temperature range is 25 degrees centigrade, and the value returned from channel 1 of the A/D converter changes by approximately 650 per degree centigrade for temperatures about 20 degrees or so either side of the centre point.

THE LM335Z

The LM335Z is a high quality temperature sensor integrated circuit which is contained in a standard TO-92 plastic en-

capsulation and looks much like an ordinary plastic cased transistor. The two basic methods of using this device are shown in Fig. 2.

This device can be regarded as a high quality voltage regulator, but the voltage developed across the component depends on its temperature, and is nominally 10 millivolts per degree Kelvin. In terms of degrees centigrade this represents 2.732 volts plus 10 millivolts per degree centigrade (or minus 10 millivolts per degree for temperatures below zero). The circuit of Fig. 2(a) can be used to trim the device for optimum accuracy, but for most purposes the simple method of Fig. 2(b) is adequate. These circuits are not significantly affected by normal supply voltage fluctuations, and it is only necessary to stabilise the supply if there would otherwise be extremely large variations in the supply potential.

BLOCK DIAGRAM

The block diagram of Fig. 3 shows the general arrangement used in the temperature interface. The temperature sensor drives the analogue port of the computer via a buffer amplifier which provides a low output impedance. A variable attenuator is used between the sensor and the buffer stage since the nominal output voltage swing of the sensor is 2 volts (200 degrees \times 10

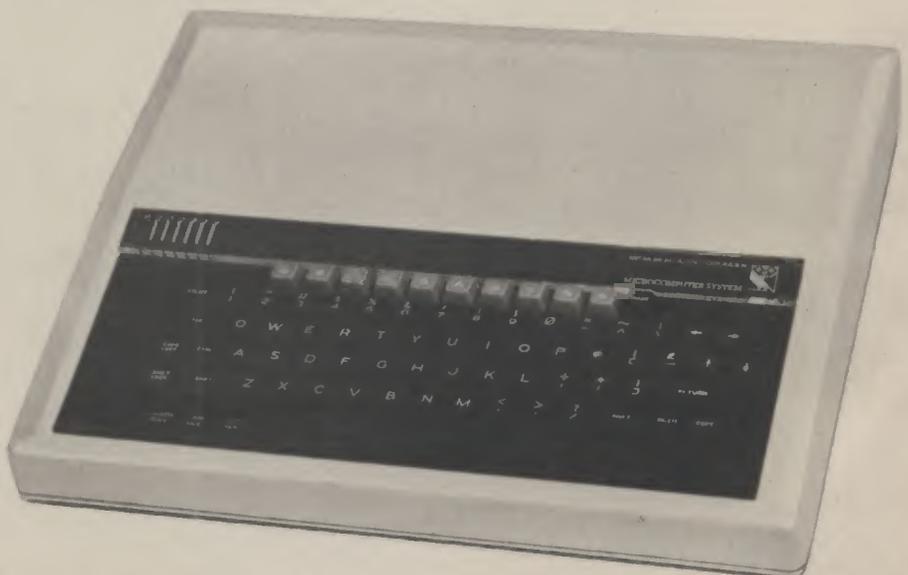


Fig. 1. Simple thermistor circuit.

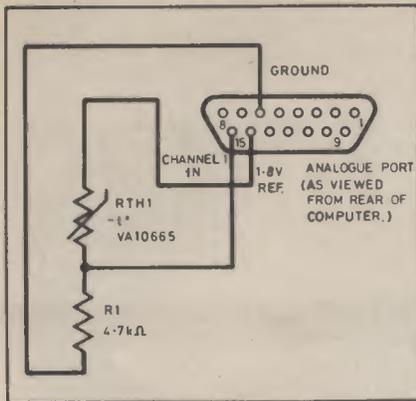


Fig. 2. Basic methods for using the LM335Z.


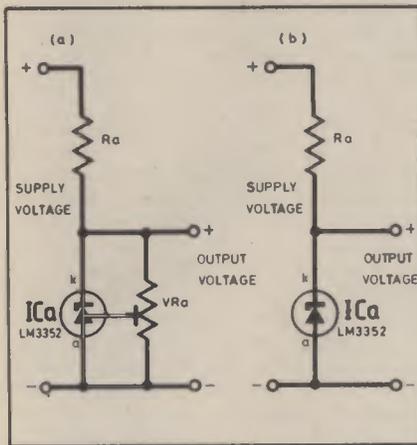


Fig. 3. Block diagram of the Temperature Interface.

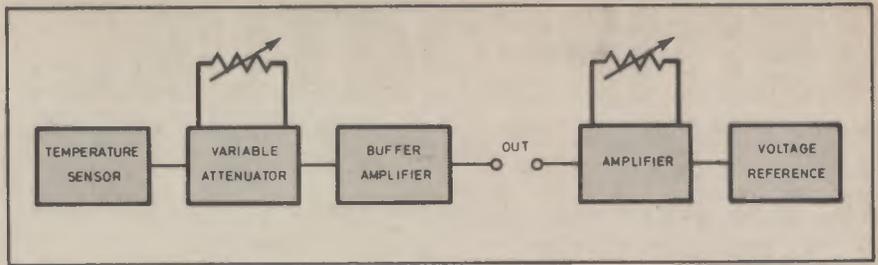

millivolts = 2000 millivolts or 2 volts) and the computer requires an input voltage swing of 1.8 volts, as explained earlier.

A minimum output voltage of 0 volts is required, but the sensor circuit gives a minimum output potential of about 2.232 volts. Originally a circuit in series with the output which provided a suitable voltage drop was tried, but the bridge circuit was finally adopted as this was found to give better results. With this system a precision voltage regulator is used to provide a 2.232 volts reference level, and when the output to the computer is taken from the output of the sensor and the reference level, rather than between the output of the sensor and the 0V rail. The computer is fed with the potential difference across the two outputs, and with the sensor at its minimum operating temperature the two outputs are at the same potential and the voltage difference is zero. At higher temperatures the sensor produces a higher voltage and a potential is produced across the outputs. This is effectively the same as reducing the output


of the sensor by the desired amount, but it must be borne in mind that neither output of the circuit is at its 0V supply potential. The voltage reference is made variable so that it can be adjusted to give precisely the required potential, and it actually consists of a fixed voltage source feeding a variable gain amplifier.

CIRCUIT DESCRIPTION

The full circuit diagram of the temperature interface is shown in Fig. 4.

IC1 is the precision fixed voltage (1.2 volts) reference device, and R1 is its load resistor. The ZN423E requires a current flow of about 10 milliamps in order to operate efficiently and R1 therefore has a fairly low value. If low current consumption is considered important IC1 can be replaced with the more expensive 8069 device and R1 can be increased to 10kΩ in value. Note that this application requires the use of a high quality voltage regulator having temperature compensation, and a simple regulator using a cou-

Fig. 4. Circuit diagram of the Temperature Interface.

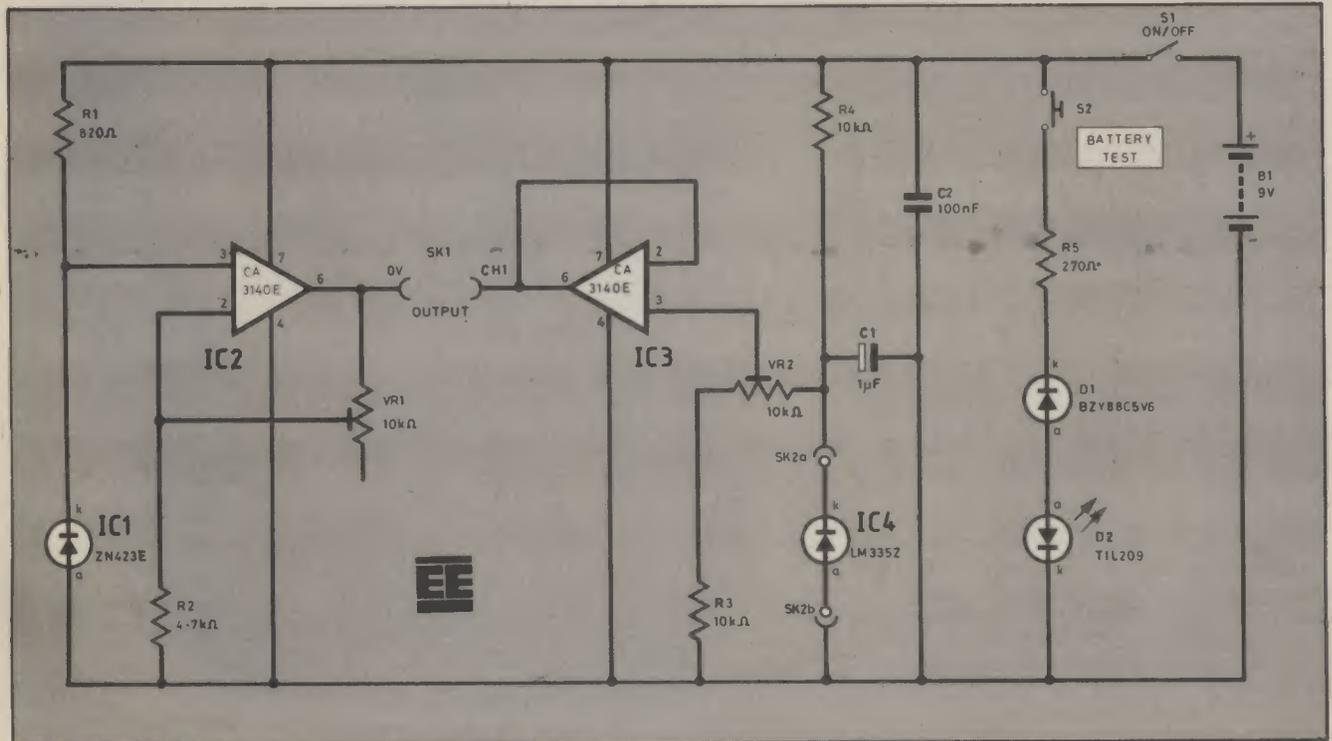

ple of forward biased silicon diodes or something of this type would not be adequate.

IC2 is an operational amplifier which is used in the non-inverting mode, and amplifies the potential developed across IC1. The gain of the amplifier can be varied by means of R3 from unity to about three times, giving an output voltage range of about 1.2 volts to 3.6 volts. A CA3140E is used in the IC2 position because this has an output which can swing down to virtually the negative supply potential. Most i.c. operational amplifiers are not quite able to supply the minimum output voltage called for in this circuit.

TEMPERATURE SENSOR

IC4 is the temperature sensor and this will normally need to be located away from the main unit. It is therefore coupled to the rest of the circuit via a twin lead and SK2. C1 helps to filter any mains hum or other electrical noise which is picked up in the connecting cable (which can be several metres long if necessary). R3 and VR2 form the variable attenuator, and IC3 is another CA3140E operational amplifier, but in this case it is used as a straightforward unity gain buffer stage.

BATTERY CHECK

A battery check facility is built into the unit to reduce the risk of misleading readings being obtained due to an inadequate battery voltage. When S2 is operated R5, D1 and D2 are connected across the supply lines. About 7.5 volts must be developed across D1 and D2 before they will conduct, and the supply voltage must therefore be slightly higher than this level before a significant voltage is developed across R5 and the circuit passes a high enough current to cause D2 to light up. If D2 switches on when S2 is operated this indicates that the battery voltage is sufficient.

The current consumption of the circuit is about 14 milliamps, and a PP3 size 9-volt battery is adequate to power the unit provided it will not be used for prolonged periods. If it will be used for long periods of time it would be advisable to use a larger 9-volt battery such as a PP9 size, or rechargeable NiCad cells would probably be the most practical power source if the unit is to be used for many hours at a time.

CONSTRUCTION

PRINTED CIRCUIT BOARD

Provided the unit is to be powered from a small 9-volt battery a plastic case measuring about 120 x 80 x 35mm is large enough to comfortably accommodate all the components. The simple front panel layout of the prototype can be seen from the photographs, but any sensible layout is acceptable.

COMPONENTS

See
**Shop
Talk**

Resistors

| | |
|-------|------------------------------------|
| R1 | 820Ω |
| R2 | 4.7kΩ |
| R3,4 | 10kΩ (2 off) page 534 |
| R5 | 270Ω |
| VR1,2 | 10kΩ 15 turn Cermet preset (2 off) |

Fixed value types are $\frac{1}{4}W \pm 5\%$

Capacitors

| | |
|----|----------------------------|
| C1 | 1μF 63V axial electrolytic |
| C2 | 100nF polyester |

Semiconductors

| | |
|-------|--|
| D1 | BZY88C5V6 5.6V 400mW Zener |
| D2 | TIL209 red l.e.d. or similar (with panel holder) |
| IC1 | ZN423E 1.2V precision regulator |
| IC2,3 | CA3140E MOS op-amps (2 off) |
| IC4 | LM335Z temperature sensor |

Miscellaneous

| | |
|--|-------------------------------------|
| S1 | Rotary on/off switch |
| S2 | Push-to-make, release-to-break type |
| SK1,2 | 3.5mm jack (2 off) |
| B1 | 9-volt PP3 size |
| Plastic box 120 x 80 x 35mm, printed circuit board, two 8-pin d.i.l. sockets, control knob, battery connector, 15-way D connector, screened lead, two 3.5mm jack plugs, 6BA fixings, Veropins, wire. | |

Approx. cost
Guidance only


£8.85

Apart from the LM335Z sensor the small components are all mounted on a printed circuit board which measures 70 x 35mm. The p.c.b. design and the component layout and wiring are shown in Figs. 5 and 6. IC2 and IC3 have MOS input stages and should therefore be mounted in (8 pin) d.i.l. sockets. They should not be fitted in place until the rest of the board is complete, and they should be handled as little as possible once removed from their anti-static packaging.

VR1 and VR2 must be the appropriate Cermet multi-turn trim pots if they are to fit onto the printed circuit properly. The use of ordinary preset resistors is not recommended as fine adjustment of the unit would be very difficult using these, and it is likely that they would not have adequate resolution anyway.

Veropins are fitted to the board at points where connections to off-board components will be made, and then the completed board is mounted on the rear panel of the case using 6BA fixings. The unit is then completed by adding the hard wiring.

The LM335Z temperature sensor is wired to SK2 by way of a twin lead terminated in a 3.5mm jack plug. If the lead is more than about one metre long it is advisable to use screened cable with the outer braiding connected to the barrel of the plug and the inner conductor to the tip. Note that the LM335Z must have its + (cathode) terminal connected to the tip of the plug and its - (anode) terminal connected to the barrel. Also note that IC4 must be an LM335Z temperature sensitive voltage source and not the LM335 which is a temperature sensitive current source and is used in a slightly different way. Use sleeving over the leadout wires of IC4 to prevent them from accidentally short circuiting together, and this component must be

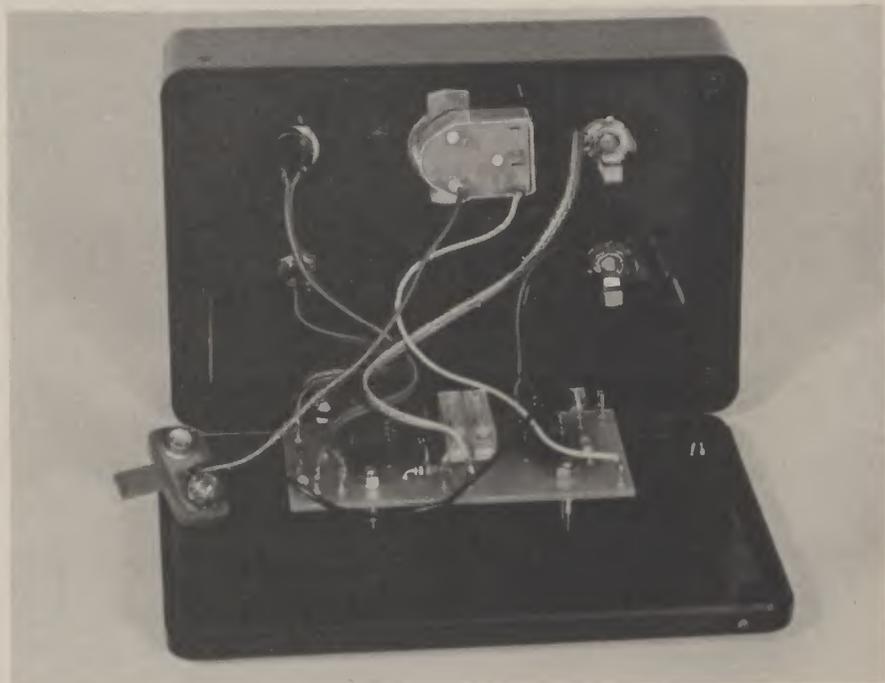

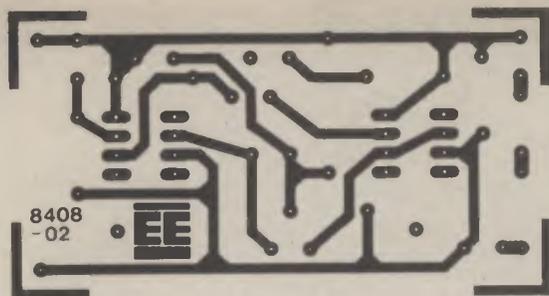


Fig. 5. P.c.b. design.

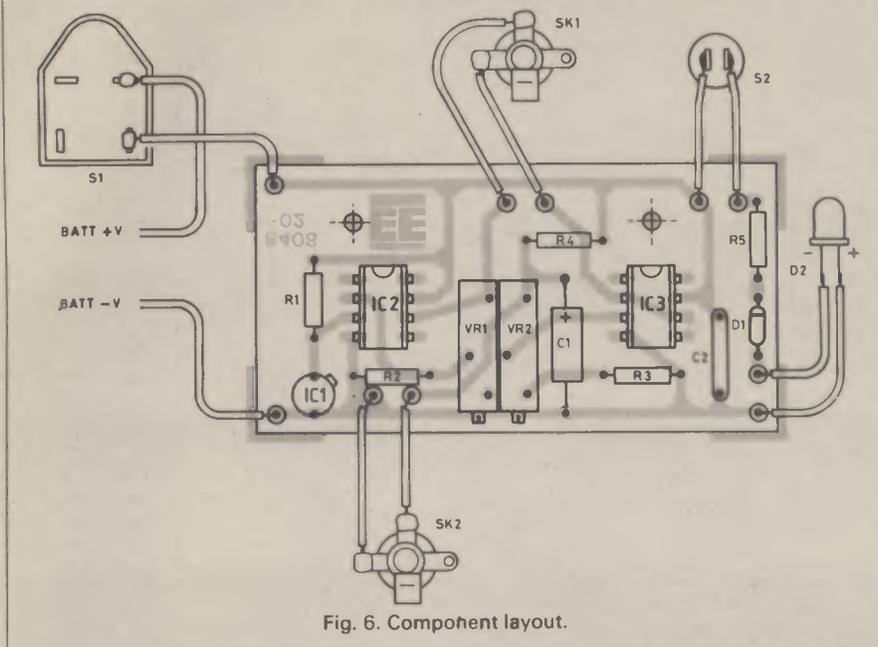


Fig. 6. Component layout.

fitted in a probe of some kind (such as a small test tube) if the unit is to be used to measure the temperature of liquids. Apart from protecting the sensor against corrosion this is also essential to prevent current from flowing from one terminal of the sensor to another through the liquid and giving spurious results.

TESTING AND CALIBRATION

When initially testing and calibrating the unit it is necessary to immerse the sensor in water, but a simple measure such as covering the leadout wires with Bostik Blue Tack is sufficient to temporarily insulate the leadouts during this setting up procedure.

The connection to the computer is made via a screened lead about one or two metres long fitted with a 3.5mm jack plug at one end and a 15-way D type connector at the other. The barrel of the jack connects through to pin 5 of the D plug (analogue ground) and the tip connects to pin 15 of the D plug (channel 1 input). Refer to Fig. 1 of this article or to the "User Guide" for the computer pin numbering of the D connector. If you wish to use any of the other analogue inputs, channels 2, 3 and 4 are at pins 7, 12 and 4, respectively.

ADJUSTMENT

Before connecting the unit to the computer it is advisable to set the output from IC2 at approximately the right voltage. This is just a matter of adjusting VR1 to give about 2.2 volts from pin 6 of IC2 to the negative supply rail. VR2 should be adjusted to give almost maximum output from IC3.

The number returned from a reading of an analogue channel is from 0 to 65520, and presumably the 12-bit output of the converter is fed to the 12 most significant bits of a 16-bit word so that the number obtained is effectively multiplied by sixteen. Anyway, to give suitable scaling the following simple program can be used:

```
10 X%=ADVAL(1)/32
20 Y=X%-500
30 Z=Y/10
40 PRINT Z
```

The first line simply takes the reading from channel 1 of the converter and divides it by 32 to give an integer value of between 0 and 2047. Line 20 deducts 500 from this quantity so that negative numbers are obtained if fairly low values are returned from the converter. Line 30 then divides this result by ten to give an output

range of -50 to +154.7 in 0.1 increments, which obviously covers the required -50 to +150 with no significant overflow at either end of the scale. Finally, line 40 prints the result on the screen, and a simple loop could be used to automatically update the reading.

The next step is to adjust the interface so that readings obtained correlate properly with the temperature of the sensor. Probably the easiest way of doing this is to first place the sensor in water kept at 0 degrees centigrade with the aid of ice cubes. VR1 is then adjusted for a reading of 0, but note that noise in the system might cause the reading to fluctuate very slightly (by no more than about plus or minus 0.1 degrees). The sensor is then placed in water at a higher temperature of about 50 degrees centigrade or so, and a thermometer is used to monitor the exact temperature of the water. VR2 is then adjusted to give the correct reading.

This procedure is repeated several times until no further improvement in accuracy can be obtained. Note that it takes at least a few seconds for the sensor to adjust to a large change in temperature, and that any probe assembly in which it is placed will further reduce its response time. Let the reading stabilise properly before adjusting VR1 or VR2.

PROGRAM SUGGESTIONS

Because there are so many possible ways of using the temperature interface, it is not practicable to provide a single program to cover all uses. The programs provided are not intended to be fully-finished stand-alone programs, but rather collections of ideas, to show what can be done. The various procedures and functions can be extracted from these and incorporated into your own programs. However, these programs can be used as they are, if they suit a particular purpose.

The best way of converting the ADVAL reading into a temperature reading is by a defined function. The basic function to produce a centigrade reading is:

```
100 DEF FNtemp(c)
110 LOCAL reading,temp
120 reading=ADVAL(c)/32
130 temp=(reading-500)/10
140 =temp
```

The parameter c is the ADVAL channel number, which can be passed as a constant or a variable, i.e., PRINT FNtemp(1) or temp=FNtemp(channel). You can use one or more of the four available channels as required.

The first listing shows how a three-channel system can be set up to record maximum and minimum readings, in addition to the current reading, separately for the three channels. The readings are displayed in bar-graph form, and also in digital values.

Any particular channel can be updated at any time by pressing the appropriate number key. Lines 50 and 60 deal with out-of-range values.

```

> LIST
10 REM 3-channel max/min
20 DIM maxtemp(2):DIM mintemp(2)
30 DIM initialisation%(2)
35 MODE 2:PRINT "Channel?"
40 channel%=GET#:channel=VAL(channel%)
50 IF channel<1 channel=1
60 IF channel>3 channel=3
70 PROCbarGraph(FNtemp(channel),mintemp(channel-1),maxtemp(channel-1))
80 GOTO 40
90 END
100 DEF FNtemp(c)
110 LOCAL reading,temp
120 reading=ADVAL(c)/32
130 temp=(reading-500)/10
140 PROCminmax(c,temp)
150 =temp
200 DEF PROCminmax(c,newtemp)
210 IF initialisation%(c-1)=0 THEN PROCinit(c,newtemp)
220 IF newtemp>maxtemp(c-1) THEN maxtemp(c-1)=newtemp
230 IF newtemp<mintemp(c-1) THEN mintemp(c-1)=newtemp
240 ENDPROC
300 DEF PROCinit(c,temp)
310 maxtemp(c-1)=temp
320 mintemp(c-1)=temp
330 initialisation%(c-1)=1
340 ENDPROC
400 DEF PROCbarGraph(now,min,max)
410 CLS:PROClabels(now,min,max)
420 MOVE 600,400:DRAW 1200,400
430 MOVE 600,300:DRAW 600,700
440 MOVE 700,400:GCOL 0,4
450 DRAW 700,400+2*min:PLOT 85,800,400:PLOT 85,800,400+2*min
460 MOVE 900,400:GCOL 0,2
470 DRAW 900,400+2*now:PLOT 85,1000,400:PLOT 85,1000,400+2*now
480 MOVE 1100,400:GCOL 0,1
490 DRAW 1100,400+2*max:PLOT 85,1200,400:PLOT 85,1200,400+2*max
500 ENDPROC
1000 DEF PROClabels(now,min,max)
1010 COLOUR 1:PRINT TAB(1,2)"TEMPERATURE GRAPH"
1020 COLOUR 4:PRINT TAB(0,14)"MIN":PRINT TAB(0,15);min
1030 COLOUR 2:PRINT TAB(0,17)"NOW":PRINT TAB(0,18);now
1040 COLOUR 1:PRINT TAB(0,20)"MAX":PRINT TAB(0,21);max
1050 COLOUR 7:PRINT TAB(3,30)"CHANNEL";channel
1055 VDU 23,1,0;0;0;0;
1060 ENDPROC

```

Listing to record maximum and minimum reading.

```

>MODE 7
> LIST
10 REM temperature readings
20 REM at timed intervals
30 CLS:MODE 1
40 channel=1
50 PROCraticule
60 PROCtempGraph
70 STOP
100 DEF FNtemp
110 LOCAL reading,temp
120 reading=ADVAL(channel)/32
130 temp=(reading-500)/10
140 =temp
200 DEF PROCraticule
210 GCOL 0,1
220 MOVE 200,100:DRAW 200,900
230 MOVE 200,300:DRAW 1200,300
240 MOVE 200,100:PLOT 21,1200,100
250 MOVE 1200,500:PLOT 21,200,500
260 MOVE 200,700:PLOT 21,1200,700
270 MOVE 1200,900:PLOT 21,200,900
280 MOVE 1200,100:DRAW 1200,900
290 PROClabels
300 ENDPROC
400 DEF PROClabels
410 PRINT TAB(3,22)"0"
420 PRINT TAB(1,28)"-50"
430 PRINT TAB(1,16)"+50"
440 PRINT TAB(1,10)"100"
450 PRINT TAB(1,4)"150"
460 ENDPROC
500 DEF PROCtempGraph
510 MOVE 200,300:GCOL 0,2
520 FOR X=200 TO 1200 STEP 100
530 Y=300+4*FNtemp
540 DRAW X,Y
550 T=TIME
560 REPEAT UNTIL TIME=T+1000
570 NEXT X
580 ENDPROC

```

Listing to record temperature changes over a period of time.

The maximum and minimum values are stored in two arrays, dimensioned in line 20. Remember, BBC BASIC numbers array elements from 0, so these arrays have three elements. Note also the complications this causes in lines 70, 210-230, and elsewhere. The other array, declared in line 30, is used to "remember" whether a particular channel has been used. On first use, minimum and maximum values are set to the current value, by PROCinit. Thereafter, they are up-

dated as appropriate by PROCminmax.

The rest of this program is fairly straightforward graphics. PROCbarGraph has been written using the absolute commands MOVE, DRAW, and PLOT 85, to keep it easily understandable for the inexperienced. It can be slightly shortened by using the relative drawing commands.

Line 1055 keeps things tidy by turning off the cursor. This particular line will only work with 0.5. 1.0 onward.

The second listing shows how the computer's TIME function can be used to record temperature changes over a period of time. In this case, the temperatures are recorded as a graph, but they could also be displayed as digital values, or stored in an array or on tape/disc for later analysis.

This program takes 10 readings at 10-second intervals, but much longer intervals and/or more readings are of course quite possible. □

NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

ADHESIVE FOR P.C.B. ASSEMBLY

COMPONENTS such as transformers, coils, and edge connectors need to be mechanically secured to a printed circuit board. The Electronics Tak Pak has been specially developed for this purpose and makes a strong, permanent mechanical bond within fifteen seconds.

The adhesive is non-conductive, and designed to remain effective over a temperature range of -100 to $+175$ degrees Fahrenheit. It will not affect electrical functions or attack insulation.

The Electronics Tak Pak, together with over 3,000 other tools and production aids, can be found in the current Toolrange catalogue.



Toolrange Ltd.,
Dept EE,
Upton Road,
Reading,
Berkshire RG3 4JA.

REMOTE CONTROL FOR SECURITY CAMERAS

A ROTATABLE mounting for closed-circuit TV cameras, or CB or f.m. radio aerials is available from Semiconductor Supplies at £49.45 by mail order.

The cast-metal mounting will support equipment weighing up to 100lb, and is weatherproof. Called the 200XL, it is designed to accept a spigot mounting for cameras, but clamps on top of the rotator allow tubular aerial masts to be fitted if required. One complete revolution under remote control takes 65 seconds.

The control box is connected to the rotator by means of ordinary p.v.c.-sleeved cable, and this allows the unit to be controlled at distances of 30 to 40ft. Greater distances are possible by making use of heavy-duty cable.

The control box has a heavy base for precise operation of the control knob, and a follower arrow on the dial indicates the relative position of the rotator unit. When the follower arrow coincides with the direction of the pointer the rotator is in position.

Semiconductor Supplies Ltd.,
Dept EE, Sutton,
Surrey.

ULTRA-SLIM STEREO RADIO

THE WORLD'S thinnest and lightest f.m./a.m. personal stereo radio was recently exhibited in London.

Panasonic's RF-07 measures 91mm by 55mm by 3.9mm, and weighs just 38g. Powered by rechargeable Ni-Cad batteries, the RF-07 comes complete with carrying case, stereo earphones and battery charging stand. The retail price for this package has not yet been finally decided, but Panasonic say it is likely to be a three-figure sum.

To achieve such a small size, the local oscillator, mixer, and


amplification circuits have had to be redesigned, and an ultra-thin a.m. aerial developed.

The printed wiring board has also been reduced in thickness from 0.5mm to 0.3mm and has been designed as an integral part of the radio's rear panel.

The RF-07 will not be generally available in this country before the end of the year, but further information is available from:

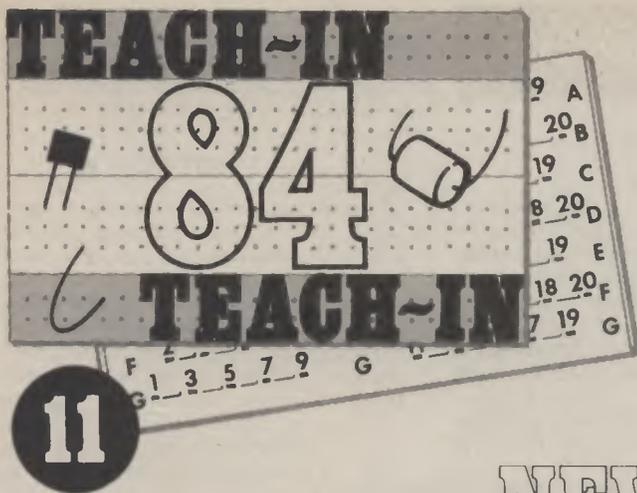Panasonic UK Ltd.,
Dept EE, 300-318 Bath Road,
Slough,
Berkshire SL1 6JB.





11

A TWELVE-PART HOME STUDY COURSE IN THE PRINCIPLES AND PRACTICE OF ELECTRONIC CIRCUITS. ESSENTIALLY PRACTICAL, EACH PART INCLUDES EXPERIMENTS TO DEMONSTRATE AND PROVE THE THEORY.

USE OF A PROPRIETARY BREADBOARD ELIMINATES NEED FOR SOLDERING AND MAKES ASSEMBLY OF CIRCUITS SIMPLE.

THE IDEAL INTRODUCTION TO THE SUBJECT FOR NEWCOMERS. ALSO A USEFUL REFRESHER COURSE FOR OTHERS.

By GEORGE HYLTON

NEW DEVELOPMENTS

LAST month I mentioned the attractions of designing one's own electronics system. It so happens that many of the practical problems which electronics can help to solve call for techniques and components not yet well established in the consumer field. To give an elementary example, if you indulge in home brewing you may wish to have a temperature controller and instruments for measuring chemical quantities such as acidity. Historically, such things were around for a long time in industry before they began to enter the home.

It often happens that the very latest electronic devices and materials appear first in military equipment. Integrated circuits arrived by this route. The first experiments were made at a British government establishment then the idea was taken up by the Americans. The incentive was the chance of developing lightweight, reliable electronics for use in aircraft, missiles, computers, space vehicles, and so on.

OPTICAL CABLES

The communications industry has always been a breeding-ground for inventions. Readers will be aware that there is a revolution now going on in cable communications, where the transmission of information in the form of electrical signals is being superseded by techniques where the information-carrier is light.

This development of optical cables will produce many useful spin-offs in other spheres. It's quite possible, for instance, that the car driver of the future will turn his headlamps on or off not by a switch which controls the current directly but by one which sends light along glass-fibre to the lamp. On arrival, the light will turn on an opto-electronic current switch. In this way, instead of running heavy copper cables from battery to instrument panel and from instrument panel to headlamps,

short direct cables from battery to headlamp will suffice.

In the long run optical cables are bound to be cheaper than copper ones because the raw materials are cheaper. Systems on these lines have already been developed for use in aircraft where the saving of weight makes it economic despite the present high cost of "fibre optics".



The eye of a needle gives some idea of the scale of a typical optical fibre cable.

NOTHING NEW . . .

Oddly enough, the designer can also learn from the past. It may not be absolutely true that there's no new thing under the sun. (The originator of that idea was thinking of the course of nature, not technology.) All the same, most of the new technical developments we see have

their roots in past ideas. This means that, buried in the files of the Patent Office (which are open to anybody, by the way) and in old books and magazines there must be a wealth of long-forgotten ideas which came to nothing because of some problem which has now been solved.

Let me give you an example. Alexander Graham Bell, the man who in 1876 made the first successful telephone, also invented an instrument which we today would call a metal detector. Bell called it an induction balance. He used it, on one occasion, to locate an assassin's bullet in the body of an American president.

METAL DETECTORS

The history of metal detectors is instructive. When radio was developed it was realised that the presence of metal near the coil of an LC tuned circuit altered the tuning. The reason is that signal currents in the coil produce an a.c. field which induces voltages in adjacent metal. Currents then flow round and round in the metal (they are called "eddy currents") and in turn create magnetic fields. These oppose and partly cancel the coil's own field. The effect is to alter the inductance.

In radio this can be a nuisance. But in time it was realised that the effect could be put to good military use in searching for buried land mines. In this case the coil (called a search coil) is deliberately shaped so as to create a large "stray field" around itself. If this field links with buried metal the resulting change in inductance can in principle be detected.

BEAT FREQUENCY TECHNIQUE

If World War II designers of metal detectors had made use of Bell's induction balance their efforts would have been more successful. Instead, they went off on

a different, more "electronic" tack. (Bell's work was pre-electronic; that is, long before the invention of the radio valve.) They used the search coil as the tuning coil of an oscillator and detected the change in frequency as the coil approached a metal-cased mine. The change is small, perhaps one part in 10,000. If the oscillator operates on 1kHz then the frequency change is only 0.1Hz which is not detectable by ear.

The solution adopted was to work at about 100kHz. A change of one part in 10,000 then gives a frequency shift of 10Hz. This was made audible by "mixing" the 100kHz with a nearby frequency derived from a second oscillator. If the resulting beat frequency is set at 250Hz (which is close to "middle C" on the piano) a shift of 10Hz is audible to anybody with a reasonable sense of pitch.

The beat-frequency oscillator (b.f.o.) type of metal detector still exists. But the vast majority of modern detectors use an induction balance technique, just as Bell's did. They are of course full of transistors and i.c.s and even microcomputers. But the basic principle (Fig. 11.1) is Bell's.

INDUCTION BALANCE

Referring to this diagram, A is the "transmit" coil. It is energised by an oscillator. (Bell used a mechanical oscillator, a trembler switch which chopped up battery current into a mixture of a.c. and d.c.). Coil B is the pick-up coil.

If A and B overlap exactly, large amounts of voltage are induced in B. If A is moved just outside B so there is no overlap some induction still takes place. But the induced voltages are now of the opposite polarity. If there is a small overlap, both effects take place. Opposing voltages are induced in B. At one critical degree of overlap the opposing voltages exactly cancel. There is no pick-up. The induction is balanced.

This fine balance is upset when the coils are brought near metal. Voltage now appears across B, is amplified and detected. By using a high gain tiny amounts of unbalance can be detected. Also, the sensitivity no longer depends on frequency.

CHOICE OF FREQUENCY

The designer can use any frequency he likes. He usually likes rather low frequencies (for example 10kHz) because the effects of iron objects can then easily be distinguished from those of non-ferrous objects.

This is of interest to "treasure hunters" who want to find coins but ignore rusty nails. It is also of medical use. Detectors exist which can find tiny bits of metal in the eye; if iron it may be possible to remove them with a magnet. So, after a century, Bell's induction balance is again finding medical applications.

EXPERIMENT 11.1

METAL DETECTOR EXPERIMENTS

I have gone on about the history of metal detection because it illustrates some important points about how inventions appear, are forgotten and rediscovered. It also illustrates the principle of balance which crops up again and again in electronics and can be a very powerful aid to the designer. But it's high time you did a bit of practical work.

You can use the medium-wave receiver described in Part 9 (Fig. 9.5) as a crude short-range metal detector. Set the reaction control so that the circuit oscillates. Tune to a strong station and adjust to get a pleasant musical beat note. Metal held near the ferrite rod will cause the note to change.

One reason why the detection range is very short is that the ferrite concentrates the magnetic field inside itself. Real-life metal detectors use circular coils with a diameter of 150mm (six inches) or more, and no core.

Even so, the range is still quite short. (For a small object such as a coin it's usually less, in a b.f.o. detector like this, than the diameter of the coil.) This is because the field strength falls off very rapidly as you move away from the coil.

This is a case where the designer is up against a law of nature, which no amount of ingenious circuitry can get round. So even the most sophisticated metal detectors can do little better than find a fairly large coin at a depth of 300mm (one foot).

TRANSDUCERS

When electronic equipment has to interact with the outside world special devices are needed to turn non-electronic quantities into electronic ones, or vice-versa. These devices have the general name, transducers. A microphone is a

transducer. It converts sound waves (which are air-pressure variations) into voltages and currents. A loudspeaker, which does the reverse, is a transducer. A gramophone pick-up converts movement into electrical signals. In the world of industry and science many kinds of transducer exist. Any sort of physical quantity: temperature, pressure, vibration, light, nuclear radiation, velocity, chemical properties . . . can be made to yield an electrical signal.

The art of chemical transducer-making has just been extended in a very electronic fashion. It has become possible to replace the gate electrode of a field effect transistor (f.e.t.) with a film of material sensitive to particular chemicals. The current through the f.e.t. is then proportional to the concentration of the chemical.

In principle, f.e.t.s sensitive to almost any chemical substance can be made, including biochemicals. The medical possibilities are exciting. You might use a "biofet", for example, to monitor the insulin level in the bloodstream of a diabetic and automatically turn on a tiny pump to give him a dose if the level falls too low.

EXPERIMENT 11.2

HIGH TEMPERATURE ALARM

In your kit of parts for this *Teach-In* you have the means of making an experiment which illustrates some of the principles of a typical "electronics meets outside world" situation.

People, and the goods they use, are sensitive to temperature and it's important to take remedial action if it gets too hot (or too cold for that matter). There are many ways of producing an electrical signal in response to a rise in temperature. Most thermostats make use of the different rates of thermal expansion of different metals to actuate a contact, when a preset temperature is reached.


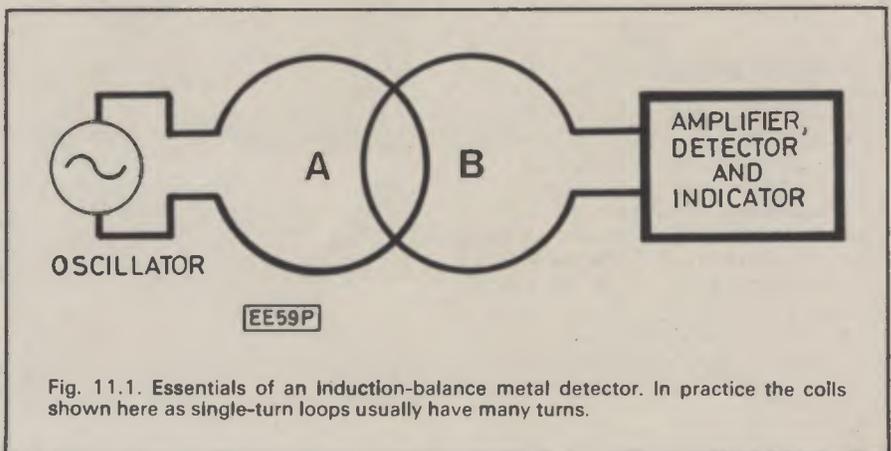


Fig. 11.1. Essentials of an induction-balance metal detector. In practice the coils shown here as single-turn loops usually have many turns.

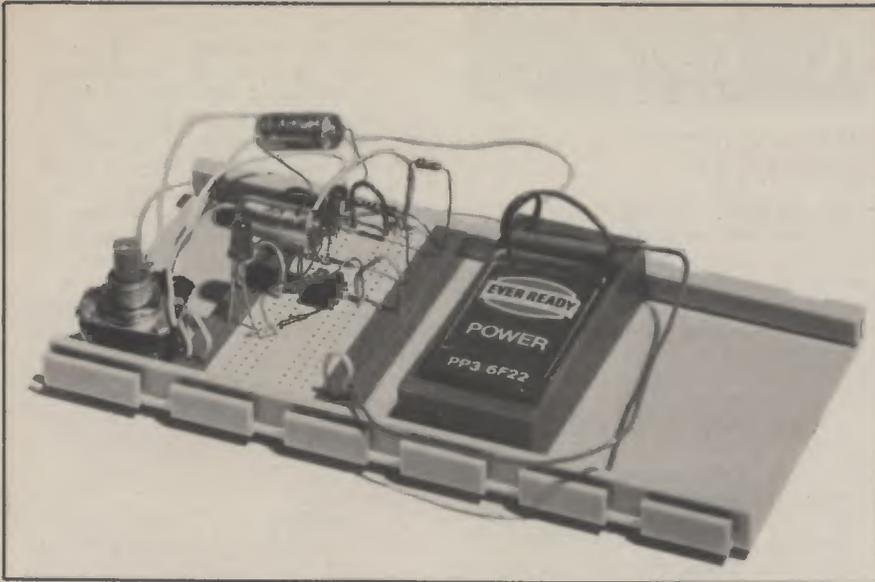

Armed with your knowledge of metal detection you might envisage winding a little coil round the stem of a mercury thermometer so that when the thread of mercury enters the coil the change of inductance can be detected.

In our temperature alarm, however, we'll make use of the fact that any ordinary bipolar transistor is sensitive to temperature. Earlier in this *Teach-In* we saw this as a nuisance, which it is, normally. But if you want to detect temperature changes it can be useful.

CIRCUIT OPERATION

In Fig. 11.2, TR1 is the temperature sensor. As the temperature rises, the size of the base-emitter bias voltage needed to turn it on falls. By setting VR1 carefully it

can be arranged that TR1 is non-conducting at temperatures below the "too hot" level but conducts at higher temperatures.

Conduction causes a sharp fall in collector voltage because of the high collector load (R2) of 1MΩ.

The op-amp IC1 is used to compare the collector voltage (on pin 2) with a fixed voltage on pin 3. Once the voltage on pin 2 becomes less positive than that on pin 3 the op-amp output goes high (remember that a positive on the inverting terminal, pin 2, gives a negative at the output and vice-versa).

The l.e.d. lights when the output goes high. This, in our case, is the alarm, but clearly the same change in output could be made to ring a bell, turn on a sprinkler, or whatever is needed.

If VR1 is set so that the l.e.d. just fails to light, then warming TR1 with the fingers will light it, showing that quite a small temperature rise above the set temperature (which is room temperature in the present case) is enough to set off the alarm.

The critical base-emitter voltage of TR1 falls by about 3mV per degree C over a very wide range of temperatures, so if the op-amp is sensitive enough to turn a 3mV input into enough output to sound the alarm, the circuit should be capable of being set up within one degree C.

Possible uses include freezer alarms, which should sound off when the temperature inside a deep-freeze rises substantially above its nominal value (usually about -40 degrees).

FAIL SAFE

The design as it stands has two obvious defects. One is that the accuracy of temperature setting is affected by the supply voltage. VR1 taps off a bit of the supply voltage to apply the appropriate base-emitter voltage to TR1. If the supply voltage changes then the wrong VBE is applied. One way out of the difficulty might be to use two transistors, one as shown and the other connected in place of R4.

If the transistors were identical then both should apply the same voltage to the op-amp if both were at the same temperature. By exposing TR1 alone to temperature change while insulating the second transistor from change only TR1 could then set off the alarm. Changes in VCC would affect both the transistors equally and not upset the balance of the circuit.

The other obvious defect is that the circuit does not fail safe. If the power supply

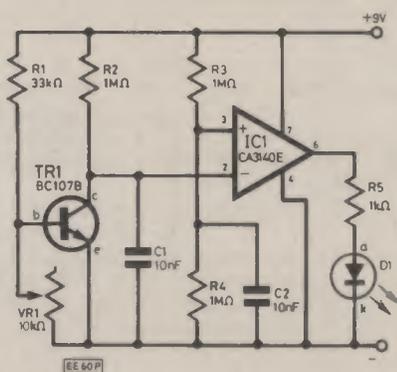


Fig. 11.2. Circuit of Temperature Alarm.

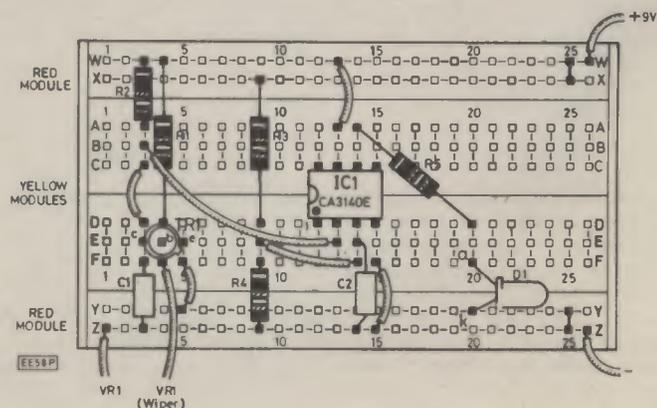


Fig. 11.3. EBBO i.c. board layout for Fig. 11.2.

fails the alarm becomes inoperative. One possible answer would be to operate from a rechargeable battery kept charged by a mains power pack. If the mains failed the circuit would go on operating from its battery (for a time). A mains-failure alarm could draw attention to the problem so that the mains power could be restored before the battery ran out.

IMAGING

Imaging, that is making pictures of things by technical methods, is a rapidly-growing field in which electronics plays a large part. We are all familiar with television. But ordinary TV cameras can't see in the dark. (Some special TV cameras can give pictures in what seems to human eyes to be darkness but is actually not total darkness.)

Even in total darkness images can still be obtained, by using heat. All things in the world contain thermal energy. If they are warmer than their surroundings they radiate heat. If cooler they absorb it. If your eyes could see heat, the warmer objects would look bright and the cooler ones dark. They can't, but cameras which can see heat (or infra-red radiation, which is what heat rays are) can be made.

For military reasons, infra-red imaging has become very important. It enables you to see your enemy at night. As usual, civilian spin-offs from this technology have appeared. There are infra-red intruder alarms and night-watch gear, and infra-red body scanners which enable doctors to see hot spots on the skin which give clues to medical conditions below it.

NUCLEAR MAGNETIC RESONANCE

Images can be obtained in other ways. X-ray scanners linked to powerful computers can give images of sections through the head or body. A more recent development does it without X-rays. When liquids are put in a steady magnetic field their molecules become tuned to radio frequencies. The frequency of tuning depends on the field strength and the nature of the liquid, including what is dissolved in it.

This effect, called nuclear magnetic resonance, NMR for short, enables the body—which is mostly liquid—to be explored with radio waves. By processing the results in a computer images can be made.

For instance, the computer can produce a map of a slice through the body, a map showing where the water is. Since different organs contain different amounts of water the map shows the shapes of the organs. It so happens that NMR is good at seeing the soft tissues of the body, which don't show up well on X-ray pictures.

CHECK YOUR PROGRESS

Questions on *Teach-in 84 Part 11*
Answers next month

Q11.1 A b.f.o. type metal detector is to be fitted with an indicator based on a frequency discriminator which produces a voltage proportional to the beat frequency. This voltage rises linearly from zero to 1V d.c. over the range 0–1kHz. To improve sensitivity, changes in this voltage are amplified 1,000 times by an op-amp. If the output of the op-amp must change by 500mV to produce a clear indication:

- What is the minimum detectable frequency change?
- If the search oscillator operates at 100kHz, what is then the sensitivity in parts per million?

- If changes of temperature of the search coil cause the search frequency to change at a rate of 100 parts per million (p.p.m.) per minute, how often will the user need to re-tune to keep the detector working properly?

ANSWERS TO PART 10

A10.1 High. When any even number of inverters are "cascaded" like this the output and input have the same polarity.

A10.2 (a) 5V; (b) Still 5V approx., because if the gate is CMOS the very high input resistance of CMOS gates makes this type of bias circuit insensitive to resistance changes.

A10.3 Frequency falls to about 160Hz. (In RC oscillators increases in the time constants reduce the frequency, usually in proportion.)

RADAR IMAGES

The very latest integrated circuits and computing techniques are being used to enable aircraft to make very detailed maps of the ground by radar. These new radars transmit bursts of microwave energy and detect their echoes from the ground just like older radars. But by using a technique first developed for quite a different purpose (radio astronomy) much finer detail can now be seen.

In this "synthetic aperture radar" (SAR) objects about the same size as the diameter of the radar "dish" are detectable at long range. Images constructed by computer from SAR information look very like aerial photographs. Features like roads and buildings show clearly. One discovery made by SAR was archaeological. SAR images of tropical forests in Latin America show the remains of ancient irrigation channels, hidden from sight by foliage but still detectable by radar.

SYSTEMS AND CIRCUITS

I've been talking about these new developments because they illustrate a basic point which beginners in electronics can easily overlook. It's this. There are two kinds of electronic engineering. There's circuit design, which occupies a lot of space in magazines like EVERYDAY ELECTRONICS, and there's systems engineering.

Systems engineering looks at a need as it were from a distance, and tries to view it in perspective, mapping out the things which have to be done to make the system work without getting down to details.

For radio, TV, audio and other common areas of electronics this was done long ago and need not be repeated in every article on these subjects. But for new applications of electronics, systems engineering is necessary.

Instead of saying: "I need a circuit for doing this new task" it usually pays to say: "What do I need to know before I can get down to circuits?" The answer to this question may not be an electronic answer at all.

If you are designing an electronically controlled system for cooling a hot room by blowing cold air into it, then long before you get down to electronics you need to establish what airflow speeds and temperatures can be tolerated by the people in the room before reaching the point where they complain of cold draughts. This is not an electronic question, but the answer to it will certainly affect your ultimate design.

It's more than likely that you'll come up against problems which call for a systems-engineering approach, so be prepared. Also, be encouraged. It's very satisfying to come up with something that works because you yourself have made it work, breaking new ground in the process.

Next month: Aids to Design

EVERYDAY news

... from the world of

EXPERIMENT IN SPACE

SCHOOLS BATTLE FOR SPACE ON 1986 SHUTTLE LAUNCH

AN EXCITING and quite unique competition is now open to all secondary school students and apprentices in the UK.

The challenge is to recognise the potential that space offers their future, and to create an experiment that takes into consideration the special environmental conditions in space, in particular vacuum and weightlessness.

The winning entry will have a reserved spot in the payload bay of the space shuttle due to be launched in early 1986. The simpler the project the better its chances as it must be small and simple enough to be housed in a self-contained cylinder no larger than 502mm diameter, 359mm long with an all up weight restriction of 27.2kg (60lb).

The competition is being run by ITN (Independent Television News), one of Europe's leading space consultants SSI (Space Services International) and NASA (National Aeronautics and Space Administration).

NASA's technological expertise is undoubted and it would be easy for the entrant, in this prestigious company, to get "too technical". Don't forget that (as far as we know) the most basic of Earthbound natural phenomena have never been asked to perform in space.

The ITN-SSI competition will be judged by a panel of experts in the space sciences. Finalists will be asked to construct the winning package from their own resources.

Full details and conditions can be obtained by sending a large stamped addressed envelope to: *Experiment in Space, ITN, PO Box 4BY, London W1A 4BY.*



HITACHI TO LAUNCH HOME COMPUTER

Hitachi is to enter the UK home computer market with the launch this autumn of its MSX product, the Hitachi MB-H80, in good time for the Christmas buying season. MSX is based on the hardware specifications and computer language developed by ASCII Microsoft of Japan.

Giving preliminary details of the new home computer, Colin Leader of Hitachi Sales (UK) Limited explained that Hitachi was one of the original group of companies to subscribe to the development of hardware to meet the MSX specification in Japan—a success that he expects to be repeated in the UK.

"But we are not just taking the Japanese version of the MB-H80 and bringing it to the UK. We carried out a great deal of research into UK market needs, and enhanced the MB-H80 accordingly, with the result that we now have one of the most powerful and flexible machines in the MSX range.

"The MB-H80 is one of the most sophisticated of the MSX offerings, giving a total of 80K of RAM, made up of 64K user RAM and 16K video RAM controlled by its own video display processor. In addition, the system has 40K of ROM. It features two cartridge slots, allowing expansion up to 576K and the facility to connect the soon to be announced Hitachi MSX disc drives.

"The two joystick ports are sensibly situated on the side of the machine, as is the socket for an ordinary cassette recorder, together with the r.f. output for TV sound and picture. The MB-H80 has a full QWERTY typewriter style keyboard which includes numerics, cursor control and five special function keys."

Current projected price for the Hitachi MB-H80 is less than £200, and it is expected to be popular as a family computer.



The Hitachi H-1 model MSX microcomputer on which will be based the MB-H80 family computer for the UK market.



EXPORT BAN

Exports from the UK of spacecraft and launch vehicles, military thermal imaging equipment, and equipment for manufacturing or testing printed circuit boards are now covered by an "Export of Goods" control and an export licence must first be obtained.

The new controls, introduced for strategic and security reasons, are in line with similar controls agreed with the other members of the Western Alliance.

BRITISH FIRM WINS OLYMPICS

Thousands of visitors to Los Angeles, during the July Olympics, will be able to keep right up-to-date with results thanks to a new Teletext decoder from Greendale Electronics of Dronfield, Derbyshire, part of the Crystalate Group of companies.

Greendale have won an order worth £848,000 from Keyfax National Teletext Magazine—the first US company to provide such a service—for several thousand decoders. One hundred of these will be used during the Olympics in prime public locations, such as bank lobbies, hotels, airports and restaurants, to enable customers to access results via a hand-held remote control.

Colin Wemyss, Greendale's managing director said: "We are concentrating on the US market because no-one manufactures ready converted televisions as in the UK. This means cable TV users rely on adaptors for both cable and teletext—and our product meets both needs."

The Olympic's teletext project is called "KTTV's Metrotex" and operated by KTTV, a metromedia television station in Los Angeles. The station will originate a 100-page teletext magazine using the world system technology.

EXHIBITIONS

"The International Computer Graphics User Show and Conference" is the first of an annual series of shows and conferences in the UK for computer graphics users to be sponsored by the World Computer Graphics Association (WCGA).

The exhibition, aimed at improving productivity and

technological advancement by computer graphics, is to take place from 19-21 February, 1985 at London's Barbican Centre.

An exhibition and conference devoted to the use of computers in the hotel industry, HOTECH '84, takes place at the Royal Garden Hotel, London, from October 3-4, 1984.

Computer Clinic

Lion Micro, who recently announced the opening of their giant computer store "Micro Systems at Lion House" in Tottenham Court Road, London, have announced that, together with General Computer Systems UK Ltd. (GCS Bus Shop), they will be providing over-the-counter maintenance and repair services in the store.

A team of engineers will provide over-the-counter service on a wide range of micros and other associated peripherals. The service is not only aimed at Lion customers, but at anyone in the London area who has a microcomputer and is without satisfactory service.

Customers hand their micros over the counter and an engineer will, wherever possible, identify and rectify minor faults "on-the-spot" or advise as to the likely time of repair with, of course, an estimate. All repairs are fully guaranteed.

Top Spot for Sinclair

Britain's Sinclair Research continued to dominate the UK personal computer market during the first quarter of 1984, achieving 43 per cent of unit sales—according to independent market research organisation, Audits of Great Britain Ltd. (AGB), who sampled 25,000 households.

Reporting total quarterly unit sales through all outlets of 215,000, up sharply from 129,000 (Q1, 1983). AGB gave second and third places to Commodore (28 per cent), and Acorn (10 per cent). Sinclair's ZX Spectrum remained the most popular model with an individual 36 per cent share, up 2 per cent from fourth quarter 1983.

BRITTOIL has chosen the GRiD Compass personal computer for a range of professional staff to use in their day-to-day planning and analytical work.

JAPANESE DISH FOR HALLEY'S COMET

Mitsubishi Electric Corporation recently finished assembling a huge, 64-metres-diameter antenna for observation of the Halley's Comet. When completed in late October this year, it will be Japan's largest deep space probing antenna.

The antenna is being built for the Education Ministry's Institute of Space and Astronautical Science which is in charge of the PLANET-A Project to observe Halley's Comet approaching the sun in 1986. It will be installed in Usuda Town, Nagano Prefecture, for communications with the PLANET-A, a Halley's Comet probe. The comet comes close to the sun every 76 years.

The 70-metres-high gigantic antenna weighing approximately 1,900 tons can horizontally rotate, carried by six platform cars that run on rails. As it is also able to change its vertical angle, the parabolic antenna can be trained in any direction.

To track the deep space probe 180 million kilometres away and receive its very weak, 5-watt radio waves and telemetric data, and give instructions to the probe, Mitsubishi Electric introduced various new technologies to the antenna. These advanced technologies include: homology designing to always hold the parabola's shear down to 1.5 millimetres or less from an ideal parabola; the world's first beam transmission system that reduces noise and enables the use of various frequencies; and a master collimator which ensures high directional accuracy of 0.003 degree.

The antenna will also be used for probing the moon and planets, and astronomical experiment programs to be conducted in cooperation with overseas deep space probe stations.



Car Radio BOOSTER

R.A.PENFOLD

ALTHOUGH primarily intended as a booster amplifier for a car radio to give either 9 watts r.m.s. into an 8-ohm impedance speaker, or about 17 watts r.m.s. into a 4-ohm type, this circuit can be used in any similar application where a fairly high output power is needed using only a 12-volt supply. The booster amplifier is simply connected between the radio (or other high level signal source) and the loudspeaker, and it is therefore very easy to install.

The prototype booster is a negative earth monophonic unit, but as explained in more detail later on in this article, it can easily be built as a stereo and (or) positive earth amplifier.

BRIDGE AMPLIFIER

When using an ordinary transformerless power amplifier and a 12-volt supply, the maximum nominal peak-to-peak voltage swing that can be applied to the speaker is 12 volts. This gives an output power of only about 2.25 watts into an 8-ohm load, or 4.5 watts into a 4-ohm load.

Amplifiers of the type described here use two amplifiers in a bridge circuit to double the maximum output voltage swing available for a given supply voltage, and therefore produce a fourfold increase in maximum output power (bearing in mind that doubling the output voltage also doubles the output current, and thus gives the fourfold boost in output power).

A bridge circuit uses the basic arrangement shown in Fig. 1. One amplifier is fed with the input signal in the normal way, and its output couples to one terminal of the loudspeaker. However, the other loudspeaker terminal does not connect to earth, but is instead connected to the output of the other amplifier of the bridge arrangement. This second amplifier stage has a voltage gain of unity, inverts its input signal, and is fed with the output signal of the first amplifier stage.

Under quiescent conditions both amplifiers have an output voltage of about half the supply voltage, giving no significant voltage across the loudspeaker. If an input signal is applied to the circuit, the output voltage of each amplifier stage changes by an identical amount, but one will be positive going while the other is negative going. Thus if the amplifier is fully driven, when the output of one amplifier stage is fully positive the output of the other stage is fully negative. The loudspeaker is therefore driven with the full supply voltage with one polarity, and then driven with the full supply voltage but with the opposite polarity, giving a peak-to-peak output voltage swing of double the supply voltage.

Of course, a practical amplifier will not give quite this voltage swing at the output as there will inevitably be voltage drops through the output devices, but the maximum output voltage swing is still considerably in excess of the supply voltage, and a very high output power is available

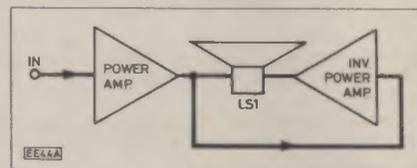


Fig. 1. Schematic diagram of bridge circuit.

for a given speaker impedance and supply potential. There are other ways of obtaining similar or even higher output powers, but these are all more expensive and in general much more complex.

COMPONENTS

Resistors

| | |
|----------------------------------|-----------------------|
| R1 | 120k Ω |
| R2,4,5 | 560k Ω (3 off) |
| R3 | 2.2 Ω |
| R6,7 | 6.8k Ω (2 off) |
| All $\frac{1}{2}$ watt $\pm 5\%$ | |

Capacitors

| | |
|----|------------------------------|
| C1 | 220nF polyester (C280) |
| C2 | 47nF polyester (C280) |
| C3 | 330nF polyester (C280) |
| C4 | 3.3 μ F 25V electrolytic |
| C5 | 100nF polyester |
| C6 | 100 μ F 25V electrolytic |

Semiconductors

| | |
|-------|-----------------|
| IC1,2 | TDA2006 (2 off) |
| D1-4 | 1N4002 (4 off) |

Miscellaneous

S1 Rotary on/off type
 Metal case 152 x 114 x 44mm;
 0.1in matrix stripboard; 3.5mm jack (SK1); 2-way terminal panel (SK2,3); 20mm chassis mounting fuseholder; 3A quick blow fuse; 2-way connector block; control knob; 18 s.w.g. aluminium for mounting bracket; wire, solder, etc.

Approx. cost
 Guidance only

£10.00



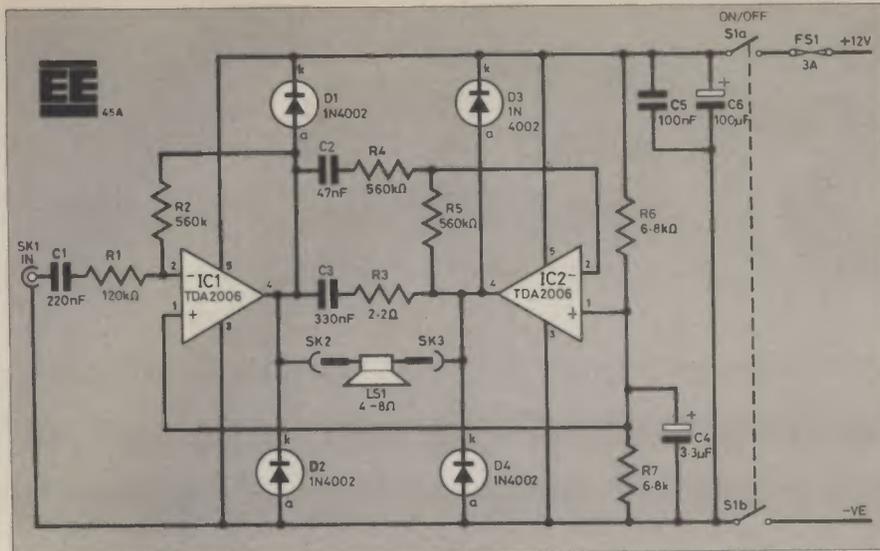


Fig. 2. Circuit diagram of the Car Radio Booster.

THE CIRCUIT

The circuit is based on two TDA2006 audio power amplifier i.c.s, as can be seen by referring to the circuit diagram in Fig. 2. The TDA2006 is a five terminal device which is rather like an operational amplifier, but the output stage is a high power class B type. This device has both output short circuit and thermal shut-down protection circuitry.

Both amplifiers have their non-inverting inputs biased to about half the supply voltage by R6 and R7, with C4 being used to decouple any noise on the supply lines. IC1 is used as an inverting amplifier and has its inverting input biased by R2. R2 together with R1 also sets the closed loop voltage gain of the amplifier, and although the gain is only about 4.5 times, this is more than adequate in this application where an input signal of several volts peak-to-peak will be available. C1 provides d.c. blocking at the input of the unit.

IC2 has purposely been biased in exactly the same way as IC1 so that the two output voltages will be accurately balanced, and only a very small quiescent output current will be fed to the loudspeaker. Input resistor R4 has been given a value which is identical to that of feedback resistor R5 so that the required closed loop voltage gain of unity is obtained. C2 couples the output of IC1 to the input of the second amplifier stage.

PROTECTION AND STABILITY

D1 to D4 are protective diodes, while R3 plus C3 form a Zobel network and aid the stability of the circuit. The unit has only one control, and this is the on/off switch S1. The quiescent current consumption is only about 40mA, but this rises to over 1 amp at full output into 8 ohms, and over 2 amps at full output into 4 ohms. These figures would normally be much less than this on speech and music

signals (rather than a sine-wave test signal), but a car battery is well able to supply currents of this order anyway.


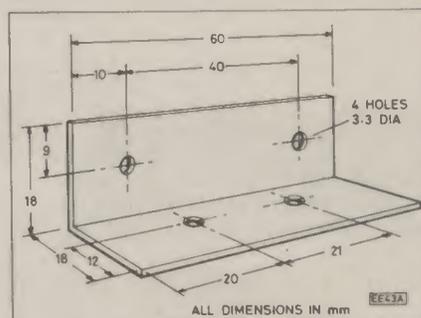


Fig. 3. Dimensions of mounting bracket/heatsink.

Photograph showing stripboard layout.

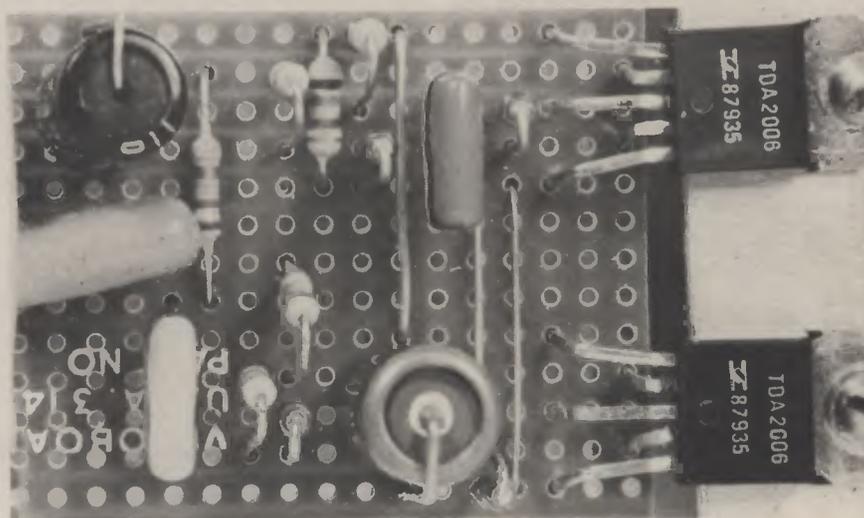

CONSTRUCTION starts here

HOUSING DETAILS

The unit must be housed in a metal case as this is used as the heatsink for the two integrated circuits. An instrument case measuring about 152 x 114 x 44mm was used as the cabinet for the prototype, and this readily accommodates all the components.

The switch and input socket, S1 and SK1 are mounted on the front panel, and SK1 can be a 3.5mm jack or any other 2-way audio connector. The right-hand side of the rear panel (as viewed from the rear) is drilled with a hole to take the power input leads, and this should be fitted with a p.v.c. or rubber grommet. The loudspeaker terminals (SK2 and SK3) are also fitted on this side of the panel.

A mounting bracket/heatsink for the component panel is fitted on the other side of the rear panel, and Fig. 3 gives details of this bracket. It is constructed from 18 s.w.g. aluminium, and it is not advisable to use a thinner gauge than this. Thicker material is perfectly suitable, but making the right angled bend in the bracket might then become very difficult. The completed bracket is bolted to the rear panel using M3 or 6BA fixings.

The 20mm fuseholder and a 2-way terminal block are fitted to the base panel of the case in the vacant area between the input socket and the speaker terminals. Reference to the interior photograph of

the unit will show the general layout of the unit and help with the positioning of the main components. The connector block, incidentally, is used as a convenient way of connecting the power input leads to the amplifier. It is usually only possible to obtain connector blocks in 12-way lengths, and so it will be necessary to cut a 2-way block from one of these. A sharp knife is sufficient to do this.

STRIPBOARD LAYOUT

Most of the circuitry is fitted onto a 0.1in matrix stripboard which measures 13 copper strips by 18 holes. Details of the component panel, plus all the other wiring of the amplifier, are provided in Fig. 4. Construction of the board is very straightforward as there are no breaks in any of the strips and no mounting holes to be drilled. Make sure that the three link wires are not omitted. C3 and R3 are not mounted on the component panel, but are soldered onto the output terminals, as shown in Fig. 4.

When the component panel and all the point-to-point wiring has been completed, it is only necessary to mount the compo-

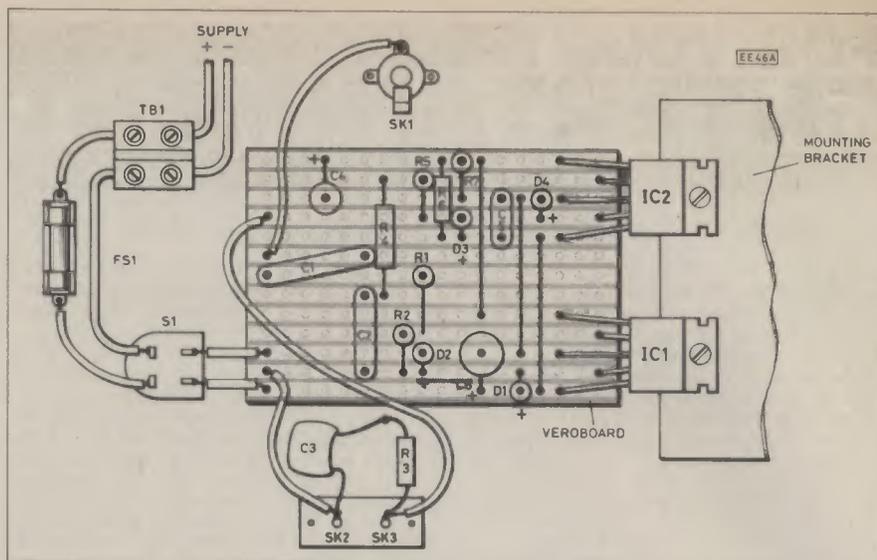


Fig. 4. Stripboard and wiring diagram.

nent panel in order to complete the unit. The panel is mounted by bolting IC1 and IC2 onto the mounting bracket fitted on the rear panel. M3 fixings are suitable here.

USING THE AMPLIFIER

It is a good idea to check all the wiring of any newly constructed project before connecting it to a power supply and switching on, and is especially important in the case of a project of this type which is powered from a low impedance power source which can supply heavy currents.

When quite sure that all is well, connect the amplifier to the 12-volt supply, the output to a loudspeaker of adequate rating, and the output of the radio or cassette unit to the input of the amplifier. The lead carrying the input signal to the amplifier does not need to be screened since it is a low impedance high level signal in the lead. One output lead of the radio or cassette unit will probably be earthed, and this must be the one that connects to the chassis of the amplifier if the unit is to function correctly (reversing these leads will result in the input signal being short circuited). Note that neither speaker lead is at earth potential, and neither lead should be earthed. The TDA2006 i.c.s have output short circuit protection, as was mentioned earlier, and no damage to the unit should occur if one of the output terminals or leads should be accidentally short circuited to earth.

If a positive earth version of the unit is required, IC1 and IC2 must be insulated from the heatsink and case using the usual insulating washers and bushes, since their heat-tabs connect internally to their negative supply leadout wires. FS1 should be wired into the negative supply input lead rather than the positive one, and the chassis should be wired to the positive supply using a lead between the appropriate tags of S1 and SK1.

For a stereo unit it is necessary to build two amplifiers, but these can share a common cause, on/off switch, and supply input connector block. □



FOR YOUR ENTERTAINMENT

BY BARRY FOX

Voicebank

There is some interesting technology behind Voicebank, British Telecom's new answering service. According to BT it's aimed at people who don't want to own their own answering machine.

As far as I can see the only real advantage to Voicebank is that it doesn't tie up your phone line. But at what cost!

Voicebank subscribers are allocated an extra phone number which callers must dial to leave a message. As the message is spoken the sound is converted into digital code, by the technique known as delta modulation.

Whereas for PCM (pulse code modulation) the digital bits are arranged in words, for delta modulation (DM) only signal changes up or down are coded. This lets BT record speech with the very low data rate of 32 kilobits a second and still achieve normal telephone speech quality.

The digital code is recorded onto eight Winchester computer hard discs, each with a capacity of 66 megabytes. The discs together hold a total of 40 hours of speech and BT hopes for 5,000 subscribers.

Snag number one is that each subscriber is only allowed seven messages, of up to 25 seconds each. Snag number two is that the messages are only stored for 12 hours. After that they are automatically erased. So you would have to call in twice a day to be sure of getting any messages left.

Service Charge

To simplify things, and avoid this call-in routine, the system can automatically page subscribers by radio when there is a message to be heard. The Winchester discs are under control of Z-80 micros which are hooked into the BT's paging system.

Provided you are within paging range you get a beep when you have a message. But this is where the cost really mounts up. You pay £45 plus VAT for the Voicebank key pad. Then you pay £35 plus VAT for rental a quarter for Voicebank.

For paging you pay £31.50 plus VAT per quarter for coverage in the London area. The rest of England is divided into 40 zones, which cost an extra £1.50 a zone per quarter.

So, with VAT the full Voicebank and paging service costs the best part of £145 a quarter. This is far more than you would pay for the outright purchase of some telephone answering machines. And these machines will store far more than seven messages of 25 second lengths for as long as you like.

Of course, answering machines go wrong. But no-one, not even BT, can guarantee that the Voicebank micros will never crash.

I use Telecom Gold, the electronic mail service which runs on a similar principle for written messages that you pick up by computer. Quite often the computer is temporarily out of service. If the Voicebank micros go out of service everyone will be in the same boat; they can't pick up their messages.

Frankly I'll be very surprised if Voicebank is a commercial success.

Video Opera

Late in April, Channel 4 TV screened "Perfect Lives", described as a video opera in seven parts. If you missed it don't worry, it will doubtless be repeated.

If you didn't miss it you may well be wondering how some of the technical effects were achieved. In fact, although it is unlikely that anyone realised it, there was not a single moment of audio or video signal in the whole three and a half hour performance that had not been artificially processed in one way or another.

I only know because producer Robert Ashley told me. The clever part was that the effects were often so subtle and ordered that they were easily mistaken for reality.

The technology used were digital effects processors, made by British firm Quantel and American firm Ampex. Most pop music promotion films are made using the same technology, but pictures which continually and obviously spin, fold, squeeze, zoom and wipe can be very fatiguing, simply because the effects are so obvious.

Although Robert Ashley talks about the story line of "Perfect Lives" as if it were an episode from any TV soap opera, the story on screen is so obscure as to be virtually invisible. He says he wanted a "repertory effect" which would sustain repeated viewing, like unpeeling the many layers of an onion. He certainly achieved that.

The poetry and jazz dialogue and slightly surreal visuals are either enterprising art or pretentious rubbish, depending on how you look at it. But from a technical point of view "Perfect Lives" was unique.

Ashley hit on the idea of tailoring the picture content so that throughout the entire seven episodes there is consistent colour and contrast level. If the picture is analysed electronically, he says, it shows almost no change in energy content even though the picture images on the screen are continually changing.

For the soundtrack, Ashley used a CBS domestic organ, of the popular semi-automatic type which enables non-musical people to pretend they are playing music. He programmed the CBS organ to play rhythm backing tracks and then added orchestral music over the top. This was

Canal Turn

If you were driving in Holland recently and thought you were on Candid Camera, I can explain. It's all thanks to video.

The flat country is criss-crossed with canals. The road bridges are low so have to be raised, like Tower Bridge, every time a boat comes through.

Until recently every bridge had its own man in charge, to stop the traffic. Now a subsidiary of Philips has rigged up an optical fibre system which pipes video pictures of a bridge several miles upstream to a central control point. When they see a boat coming, they switch the road traffic lights to red and raise the bridge.

The operators wanted to demonstrate this

overlaid with improvised jazz piano and spoken poetry during the video filming.

It was the video post production work, however, that gave him what he wanted; "a cartoon effect just slightly beyond realism". This took three months in a video studio.

Digital Pictures

The technology of digital picture processing is very new. It dates back only to 1976 when British firm Quantel was first to build a solid state memory store which could freeze a full TV picture in digital code.

While the picture is stored in code it can be altered under computer control, by what is really nothing more than pure mathematics. This technique allows pictures to be changed in shape, viewed from a changing angle, rotated through a full circle, and even turned inside out to create a mirror image.

The processing all happens in real time, but only after laborious preparation of the geometrical transitions through which the picture will pass. This alone took Ashley and his team 300 hours of studio time.

To get all the picture sequences looking superficially similar, he used artificial colouring, often into pastel shades. Almost nothing on screen is seen with an exactly natural colour balance contrast range. But because the processing follows a planned and consistent theme, nothing jars.

Why did it take until 1976 for digital processing to become possible? For a start you need a very rapid action analogue-to-digital converter. Then you need a battery of memory chips capable of holding enough digital bits for a full broadcast quality TV picture.

The black and white or luminance information is sampled at 13.5MHz and two chrominance or colour signals are sampled each at 6.75MHz. The samples are then described in 8-bit words or bytes.

A European TV picture has around 575 active lines (the rest aren't seen on the screen), which means you need a memory store of around 0.5 megabytes for the luminance and the same again for chrominance. This adds up to a total memory store of around 1 megabyte, or 8 megabits, which has to be built up from 64K bit RAMs, each holding 8K bytes.

That's a total of well over 100 64K RAM chips, just to store one picture frame. The store is refreshed at the rate of 25 pictures a second (30 pictures a second for the American NTSC TV standard) and for some effects, like the zooming and picture compression, the sampling rate is continually varied as the picture is processed.

to the press recently. But there wasn't a boat in sight. So they stopped the traffic and raised the bridge anyway.

Watching on monitors several miles away we could see puzzled car drivers get out of their vehicles and wander in bewilderment as the bridge ahead rose for an invisible boat. The remote operator then played his ace. A microphone in his control cabin is hooked up to hidden loudspeakers. "Get back into your cars. It is dangerous," he bellowed.

On the monitors we watched a gaggle of frightened Dutchmen run back to the safety of their cars. The year is 1984, and in some places Big Brother really is watching on a TV screen.

ANATOMY OF YOUR MICRO

PART TWO

OWEN BISHOP

THE Z80 microprocessor has many features in common with the 6502, but has several more registers. There are also differences in the way we can handle the numbers in these registers. In general, the Z80 is a more powerful microprocessor than the 6502 and has many more op codes. However the 6502 retains its popularity in spite of this. Among the recently introduced micros, we have the Commodore 64 and the BBC microcomputer, both based on the 6502.

The Z80 has two control lines for read and write operations. These are called RD and WR (Fig. 2.1). Normally these are both at a "high" level, but one or the other is made low by the microprocessor when it wants to read or write data. The Z80 also has another pair of control lines concerned with reading or writing data. These are called the MRQ (memory request) and IORQ (input/output request). When the Z80 wants to read from or write to memory, it not only makes either the RD or WR line low, but also the MRQ line. This indicates to the memory chips that it is engaged in transferring data between itself and memory. Two BASIC statements which cause this to happen are POKE and PEEK. When the Z80 wants to read data from or write data to a peripheral device, such as a telephone modem, it makes RD or WR low but does not make MRQ low. The memory chips will therefore ignore the read or write operation. Instead it makes the IORQ line low. This alerts all the peripheral devices and the addressed one responds. The two BASIC statements which bring about this type of operation are IN and OUT. This is not to say that IORQ is necessarily used for communicating with peripherals for it is possible to allot some memory addresses to these and treat them as if they were part of memory. This is often done in small machines. The chief advantage of IORQ is that it allows all the memory space to be occupied by memory (all 64 kilobytes if you want), and peripherals are addressed independently. This is the usual approach in machines with large memory or where the designers want to cater for maximum memory expansion.

MEMORY MAPS

The memory map of a well-known 6502 based micro is shown in Fig. 2.2. Note the addresses reserved for peripherals (I/O). Unlike the Z80, the 6502 does not have an IORQ line. The rest of memory is divided into two parts, RAM (or random access memory) and ROM (or read-only memory). We will look into these in more detail later but, for the moment, it is sufficient to note that it is possible to both read data from RAM and write data into it. In other words, the contents of RAM can be changed. Also the contents are lost for ever when the power supply is interrupted or switched off. ROM can be read from but cannot be written to (except during manufacture, which we shall deal with later). ROM is permanent; its contents do not disappear when the power supply is discontinued.

ROM is used for storing the programs which the computer needs when first switched on. These include the monitor program which is usually a short program to initialise the system and make the micro ready to receive instructions typed in at the keyboard. It may also in-

clude short routines to put a greetings message such as "CBM BASIC V2, 3583 BYTES FREE" on the screen as with VIC-20. Most popular micros have their BASIC interpreter program in ROM. This means that the language is available from the moment the computer is switched on.

An exception is the Jupiter Ace, which has the FORTH language in ROM, instead of BASIC. The Sord M5 has no resident language (as a language in ROM is called). Instead, the user is provided with a plug-in cartridge containing additional ROM which holds its BASIC. The Sharp MZ-80A and MZ80-B require BASIC to be loaded from tape. The advantage of not having a resident language is that it leaves the user free to choose which language to use with the machine. The required language can then be either plugged in as a cartridge or loaded into RAM from tape or disk. If part of the memory space is already taken up by the ROM for a language you do not want to use, this space is wasted. The language you prefer must then be put into RAM taking up a large part of this and leaving less for program storage. Many computers do not have all their ROM present when you first buy them. The VIC-20, for example, can accept plug-in cartridges containing games programs or utilities. In effect, you are plugging in extra ROM. The BBC micro has empty sockets to take additional ROMs containing programs such as "VIEW", a word processor program.

Another type of ROM which is found in micros is the character generator. This contains the codes used by the micro when putting together the signals used for displaying letters, numerals and other symbols. It may have addresses in memory space, or may be separate, as part of the video circuits.

The other kind of memory, RAM, is mainly used for storing the program that the computer is currently running (or which you are writing). Programs may be put into RAM either by typing them in at the keyboard, by loading them from tape or disk, or by down-loading them from Teletext or Prestel. The greater part of the

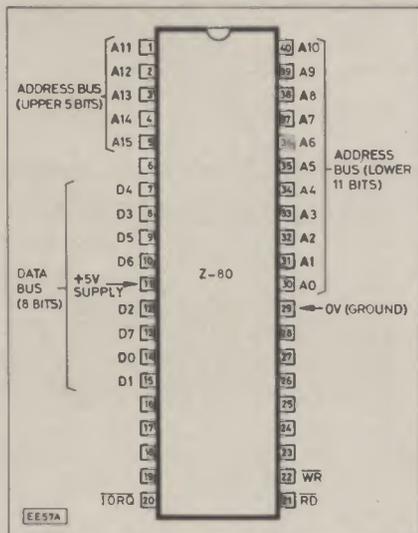


Fig. 2.1. The Z80 microprocessor, showing the connections referred to in the text.

space used is normally taken up by the program itself, but other areas of RAM need to be set aside for storing the data used by the program. There will be a variable table in which the current values of each variable are stored. If many of the variables are string variables, this may take up a sizeable proportion of available RAM. The contents of arrays are also stored in part of RAM set aside for this purpose.

RESERVED AREAS

Certain parts of RAM are reserved for use by the MPU itself. It needs somewhere to keep important information such as the present position on the screen of the cursor, the name of the most recently pressed key, the colour currently selected as foreground colour. In 6502-based machines, such data is usually stored at the very beginning of RAM (Fig. 2.2). This takes advantage of a simplified addressing mode which can be used with addresses in "zero page" (0 to 255). Another section of RAM may be set aside for storing program lines or text which is on its way from one part of the system to another. Such areas are called buffers. There is nearly always a keyboard buffer (or input buffer) where a program line is stored while it is being entered. When "RETURN" is pressed, this line is then transferred to the end of the program, stored in the main RAM. If you have a disk system, an area of RAM is reserved for materials being sent to the disc or being read from it.

Another section of memory may be taken up for storing the characters which are to appear on the TV or monitor screen. This is often referred to as Video RAM. The amount of memory required for Video RAM depends on a number of factors, including the degree of resolution of the screen image, the number of rows and columns of characters, and the extent to which colours are used. A high-resolution colour display may take several tens of kilobytes of RAM, leaving relatively little for the program. Certain micros, such as the TRS-80 have special Video RAM chips, which are under the control of video circuits. There is thus no conflict between requirements for picture generation and requirements for program storage.

Before leaving memory maps, it is worth noting that the map for a Z80 system is quite different in layout from the one shown in Fig. 2.2. As well as having zero-page storage, which means that the lowest areas of memory must be RAM, the 6502 always reads certain addresses at the very top of memory when it first begins to operate. Here it finds the addresses of the routines to which it must go to initialise the system. Consequently, the top addresses in memory *must* be ROM. It is usual for the whole of the monitor program to be placed at the top. By contrast the Z80 always begins reading its program from address 0, so ROM must occupy the lowest addresses in memory.


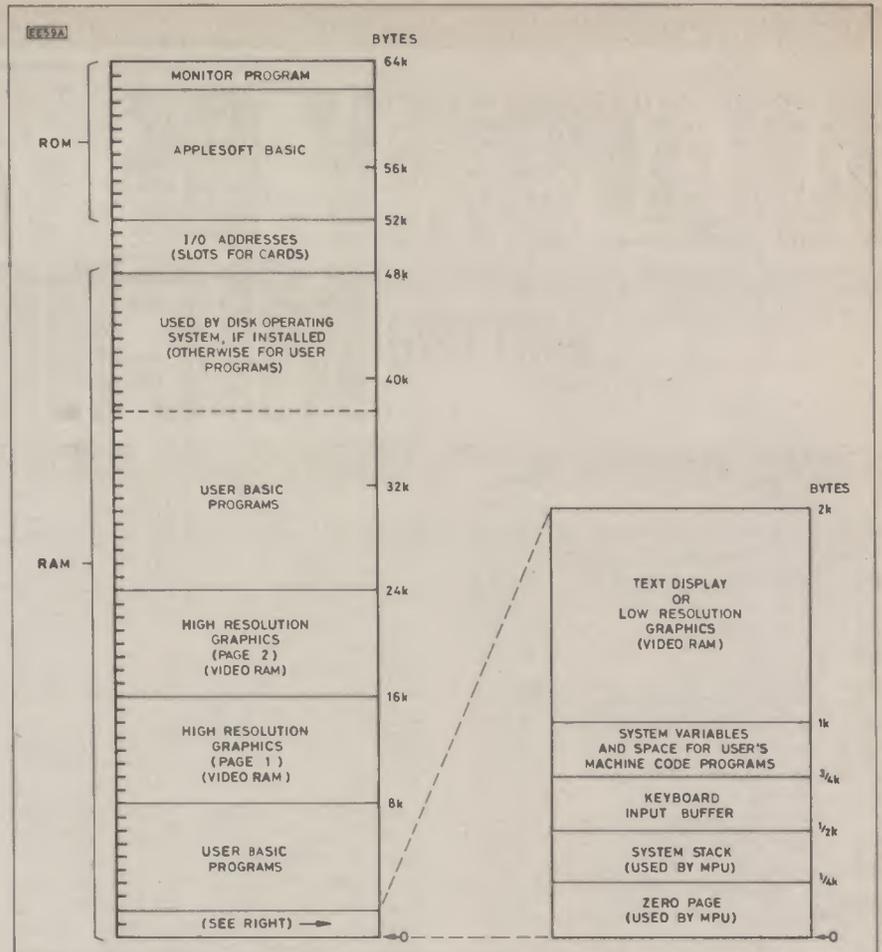


Fig. 2.2. The memory map of a Apple II. Apart from the lower 2K, the whole of RAM is available for BASIC programs, unless part of it is taken over for the Disk Operating System or for High Resolution Graphics. Note the relatively large amount of memory required for high-resolution colour graphics.

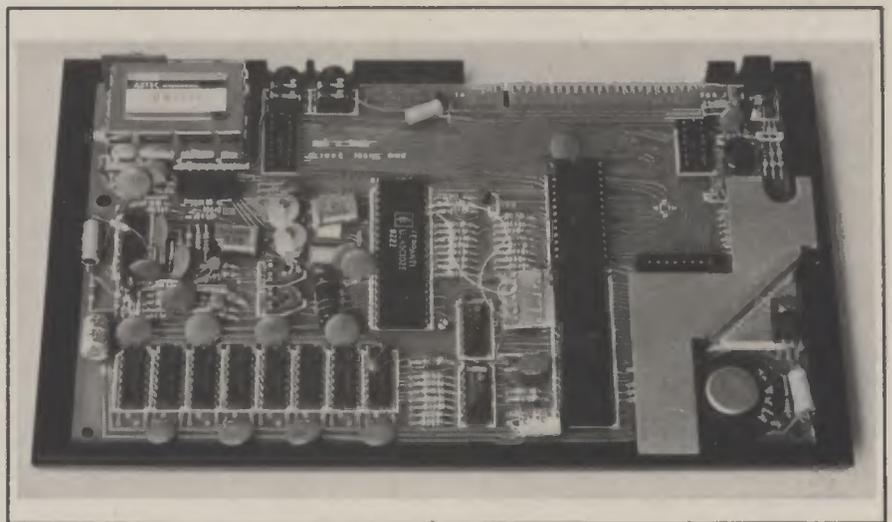

Inside the Sinclair ZX Spectrum. The three large chips are the microprocessor, Read-Only Memory, and an Uncommitted Logic Array (ULA). The ULA is a specialised device which takes the place of a large number of discrete logic components. The rest of the circuitry comprises the RAM chips, and the interfacing for the cassette recorder and TV output.

RAM

Two identical RAM i.c.s connected in parallel are shown in Fig. 2.3. This is necessary because each i.c. has only four connections to the data bus. One is connected to the lower four lines (D0 to D3) and the other to the upper four lines (D4 to D7). The other connections to each i.c. are identical, so that they act together to deal with all eight lines (one byte).

There are 10 address bus connections, (the 10 lower lines of the bus). The addresses within the i.c. run:

| | Decimal | Binary |
|------|---------|--------------|
| From | 0 | 00 0000 0000 |
| To | 1023 | 11 1111 1111 |

This gives 1024 addresses, which is normally referred to as one kilobyte. Each of these addresses refers to an array of four bistable circuits, the members of which can either be set (giving "1" output) or reset (giving "0" output). Depending on which address is present on the bus, one of these arrays of four bistables is put into connection with the data input/output pins.

The \overline{WE} input determines whether the chip is to be read from (read bistable outputs) or written to (set or reset the bistables). \overline{WE} could be connected directly to the R/ \overline{W} of the 6502, so that the write operation is enabled when the R/ \overline{W} line is "low". However, we do not want the i.c. to take in data every time R/ \overline{W} goes low, for such data might be intended for other sections of memory. This is where the "chip select" input (\overline{CS}) is important. The i.c. is incapable of receiving or sending out data except when \overline{CS} is low.

The level on \overline{CS} is determined by the output from an address decoder circuit. This may be made up from a collection of simple logic i.c.s or a special decoder such as that shown in Fig. 2.4. This has three "select" inputs which may be connected to three address lines, as shown. These are the next three above those used for addressing the RAM i.c.s. When all three lines are "low", output "0" goes low, so enabling the pair of RAM i.c.s connected to this line. The effect is that these RAMs have the address range:

| | Decimal | Binary |
|------|---------|-----------------|
| From | 0 | 00000 0000 0000 |
| To | 1023 | 00011 1111 1111 |

A second pair of RAMs is connected to output "1" of the decoder, which goes low when the input to the decoder is "001". The address of this pair of RAMs is:

| | Decimal | Binary |
|------|---------|-----------------|
| From | 1024 | 00100 0000 0000 |
| To | 2047 | 00111 1111 1111 |

In each case, the lower 10 bits are decoded within the RAM i.c. covering one kilobyte of memory. The upper three bits are decoded by the decoder, allowing us to use up to eight pairs of RAMs, and

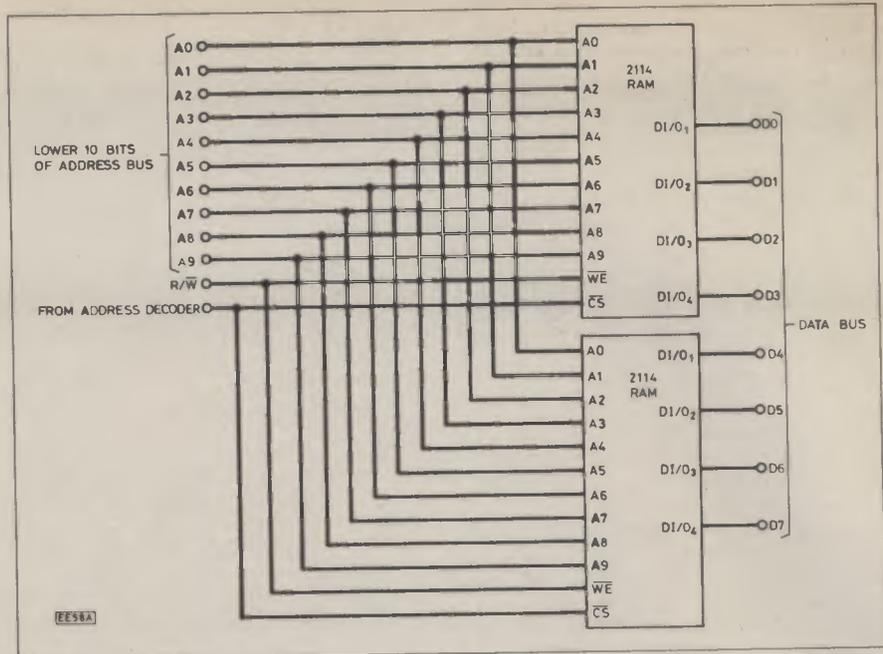


Fig. 2.3. Two 2114 RAM i.c.s wired to store 1 kilobyte of data.

covering an address range of eight kilobytes. As Fig. 2.4 shows, the decoder also has some strobe inputs which can in turn be fed from another decoding circuit, so allowing several 8K blocks of memory to be addressed individually.

In many of the smaller machines, it is unnecessary to decode all 16 bits of the address bus. Fourteen lines address 16384 locations (16K) and there may not be need for more. To save cost and complexity, the top two lines may be omitted from the system. Alternatively, they may be reserved for special functions, such as controlling a printer. This makes the design of the computer easier, though it gives problems to those who want to design and build add-on circuits.

ROM

The most frequently used kind of ROM is that known as a *mask programmed ROM*. It is programmed during manufacture so that addressing any given location always produces the same byte of data from its data bus outputs. The term "mask" refers to the photographic masks used in preparing the chips for etching. These are custom-designed to set each memory location as required. For example, the masks might be designed so that the finished ROM contains a monitor program or a word-processor program, or perhaps the data required for character generation. Designing these ROMs is costly but, once the design has been

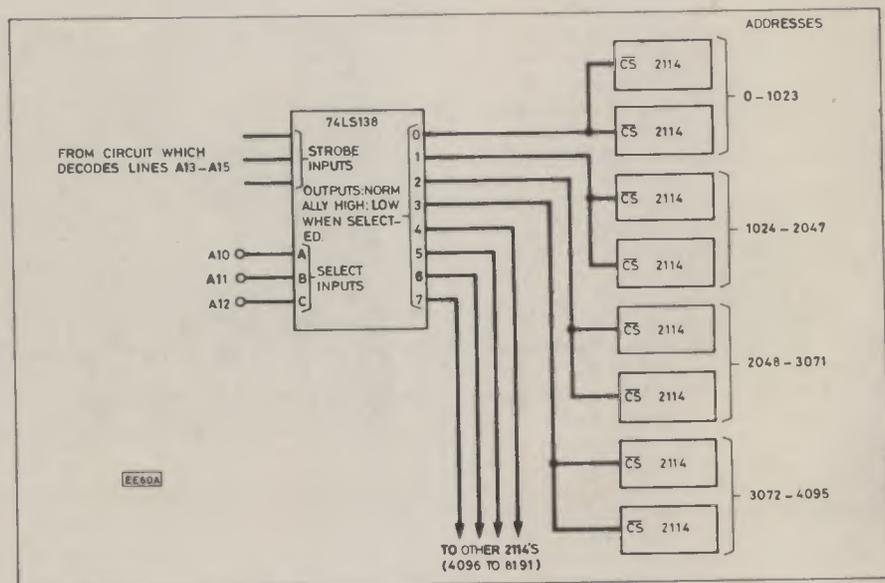


Fig. 2.4. Using the 74LS138 to decode the addresses for 1 kilobyte blocks of RAM.

tested and found correct, it is possible to manufacture such ROMs by the thousand at relatively low cost. This kind of

ROM is certainly not for "one-off" applications. When a system is under development,

or when it is known that only a few identical ROMs will ever be required, it is usual to program each ROM chip individually after manufacture. One type of programmable ROM is the *fusible link* ROM. When manufactured, all memory cells give a "1" output. The ROM may then be programmed by addressing each bit in turn (or perhaps eight at a time) and either "blowing" a thin wire link, by passing a high current, or omitting to blow it. Blowing the link makes that location give a "0" output from then on. The work may be done automatically, under computer control. Once such a device has been programmed it cannot be altered.

The erasable programmable ROM (or EPROM) is very popular, not only for dedicated systems for which the expense of mask programming is not justified, but also for systems in development (as many owners of the BBC micro will know). These are programmed by addressing each location in turn, putting the required data on the bus and then applying a programming pulse of short duration but of relatively high voltage, in order to charge the gate of a field effect transistor (Fig. 2.5). The effect of this is to turn the transistor permanently on or off. When, in future, we address the memory cell of which the transistor is a part, the output is "1" or "0" depending on the state of the transistor. Since the gate is electrically insulated, the charge remains on the gate for years, retaining the stored data indefinitely. Reading from the memory does not reduce the charge, for this is a field effect transistor—its action depends solely on the field created by the charge, and does not require any current to flow from the charged gate.

An EPROM can be programmed automatically by an inexpensive device which can be controlled by a home computer. The advantage is that, if it is subsequently necessary to amend the program, it can be completely erased by exposing the chip to ultraviolet radiation. This is the reason that there is a quartz "window" in the package. Ultra violet radiation is an "ionising" radiation; it produces a copious supply of electrical ions in any material on which it falls. These ions cause the charge to be lost from the gates of the transistors. This erases the stored program in a period of a few tens of minutes. The EPROM may then be reprogrammed.

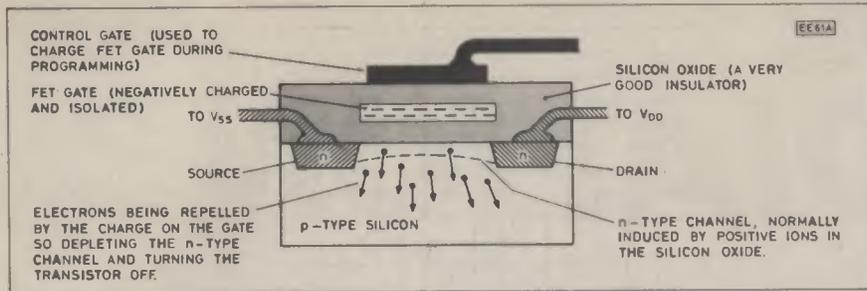


Fig. 2.5. MOSFET with isolated gate, as used in an EPROM.

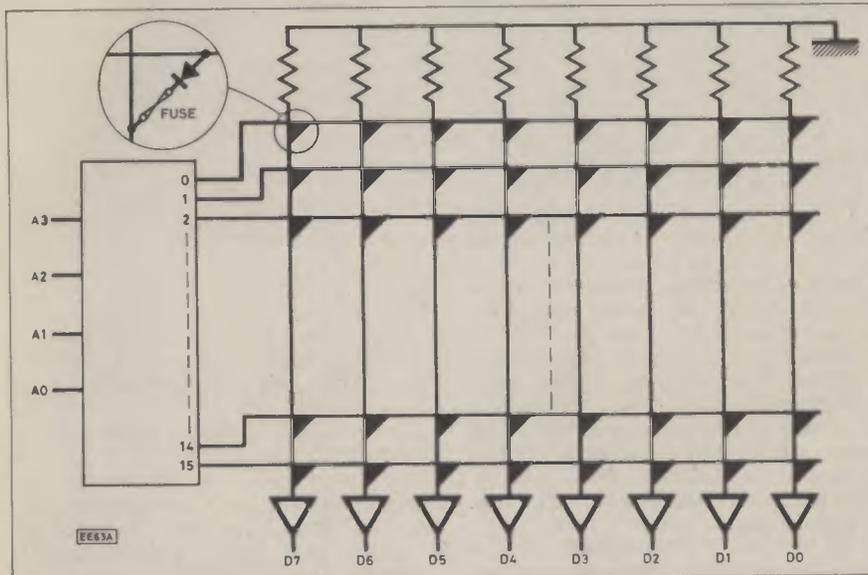


Fig. 2.6a. Unprogrammed 16-byte fusible-link PROM. The address decoder is part of the chip, and as any of the 16 rows is selected (addresses 0000 to 1111), the "1" on the output from the selected row of the address decoder will appear, via the diodes and fusible links as all "1s" on the data bus.


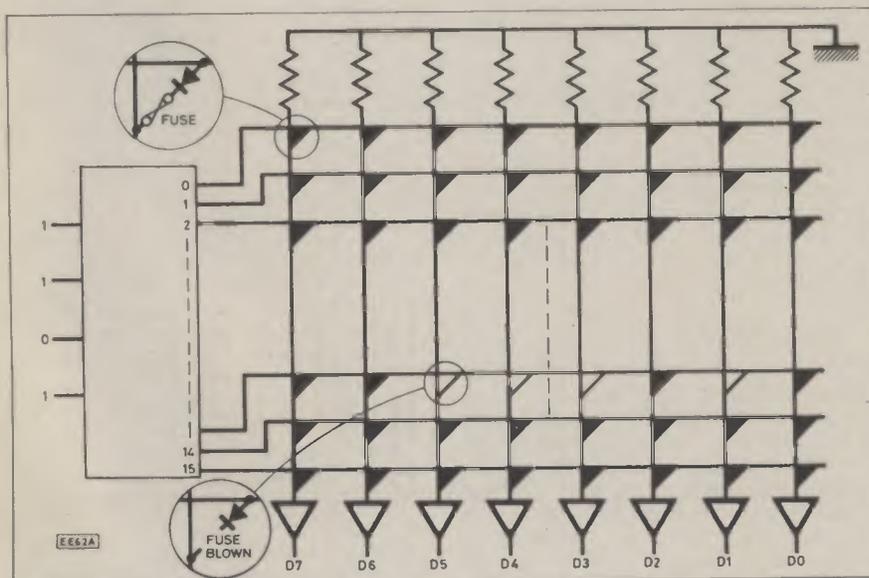


Fig. 2.6b. Programmed EPROM. Address 1101 (thirteen) is shown with fuses blown to give bit pattern 11000101 on the data bus.

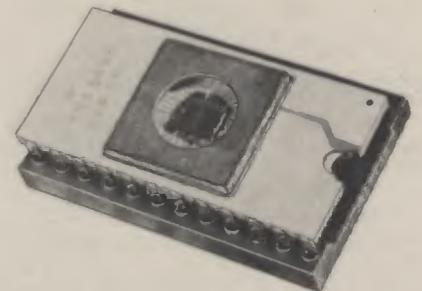

A typical UV EPROM, showing the circular quartz window above the memory circuit. When exposed to ultra-violet light, the whole memory is erased.

What is RADIATION?

A.J. BENTLEY

NUCLEAR Power and the "Bomb" are topics of grave public concern. The bright promise of unlimited cheap electricity is dimmed by the spectre of Nagasaki and Hiroshima and by the grim reminder from Three Mile Island. These very real threats are made doubly menacing by the lack of agreement displayed by opposing groups of "experts". Discussions on the subject opened in the news media rapidly degenerate into acrimony over statistics, with no attempt to make clear what it is that is being argued over. I wonder what sort of an answer we would get from a Politician or a General if a TV Interviewer asked: "O.K. so what is radiation then?"

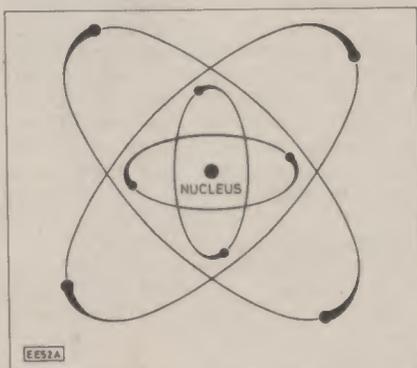


Fig. 1. Classical model of an atom, showing electrons orbiting around a nucleus.

ACTIVE ATOMS

Everything in the world is made of atoms, we have been told. Each atom consists of a central core or nucleus with a collection of orbiting electrons as in Fig. 1. The nucleus has a strong positive electric charge which holds the negatively-charged electrons in orbit. Among the untold numbers of atoms in the universe are certain "rogues" whose nucleus has an ability to "spit", usually only once in its life. This nuclear phlegm is known to us as radiation.

ILLUMINATING DISCOVERY

In order to continue a little more seriously we have to study a bit of history. Around the turn of the century, it was found that certain types of rock were able to fog photographic film even through quite thick wrappings. Apparently this was due to some invisible emanation from the rock. After much effort scientists were able to purify the substances in these rocks which were responsible for the rays. Some of these "radioactive" materials were found to glow in the dark, especially when mixed with other substances.

For a while everyone had great fun with the stuff. You could buy luminous paint and luminous watches and even obtain special intimate garments with sewn-in radium to bathe yourself in its invigorating rays. Meanwhile the scientists plodded on with their investigations and found that there were three distinct types of ray, each with different penetrating powers. These were named Alpha, Beta and Gamma rays from the first letters of the Greek alphabet. Gamma rays are the most penetrating and Alpha rays the least. (Fig. 2).


Many more years of investigation revealed the fact that these three types of ray were in fact sprays of tiny particles which had already been discovered under other circumstances; thus the mystery was dispelled quite simply.

ALPHA RAYS

These turned out to be helium gas atoms moving at incredibly high speed. For some unknown reason, many types of atom are able to suddenly split up into two parts, entirely of their own accord. One of these parts is invariably a helium atom, the other part depends on what is left over from the original atom. This residual atom may or may not also be radioactive.

We do not know yet just why some atoms are stable and others are liable to

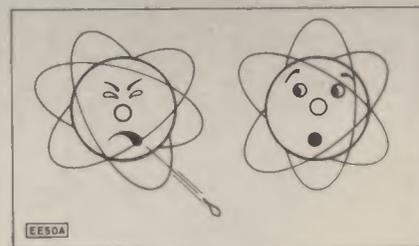split up in this way. Nor do we know why the result is always a helium atom when



this happens. It is known that the helium atom or alpha particle as it is sometimes called is totally stable, perhaps there is a clue there somewhere.


Because the helium atom is moving so fast, it loses its attendant cloud of orbiting electrons (strictly, we should be referring to alpha particles as helium atom nuclei). This means that the particle is positively-charged and can be deflected easily by electric fields. When an alpha particle hits an object it is affected by the local electrostatic field of the surrounding atoms and comes to rest quite quickly. A sheet of paper will stop alpha particles with ease.

BETA RAYS

These are even more easily understood, being nothing more than electrons. They don't come from the orbiting electron cloud but are ejected from the nucleus itself. Sometimes they are antimatter electrons or positrons. This is how antimatter was discovered in fact. Electrons are not so highly charged as alpha particles and being lighter they move rather faster so they are not so easy to stop. Nevertheless, a sheet of metal say 2mm thick will take care of them.

GAMMA RAYS

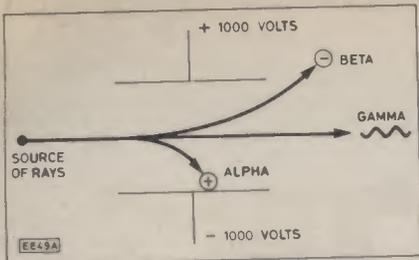Gamma rays are a little different from the other two, being short pulses of incredibly high frequency radio waves, even



The effect of an electric field on radiation. The positive alpha particles are attracted to the negative plate, the negative beta particles to the positive plate. The uncharged gamma "particles" go straight through.

higher than X-rays or light, having a frequency of over one thousand million million Megahertz. They can penetrate several feet of concrete without slowing down. At such high frequencies, these pulses behave much like particles when they "bounce off" things so it is often convenient to regard them as particles in calculations, in which case they are referred to as "photons".

Radiation then, can be described simply in terms of fragments of material shot out of atomic nuclei with a muzzle velocity close to the speed of light. Pushing the analogy with bullets a little further we can add that the calibre is about one million millionth of a millimetre. You can imagine therefore that each one of these projectiles would do very little damage to the human body, and what damage was done would normally be repaired by the body's own healing mechanism. This is true but unfortunately one particle may just happen to strike one of the d.n.a. molecules in a living cell in exactly the right way to initiate a cancer which may or may not be malignant. If we knew what the chances were of this happening with any one particle we could calculate the probability of a person being killed by a specific dose of radiation. This is the sort of thing the "experts" love to argue over, but the truth is we do not really know. There have not been a sufficient number of deaths from measured amounts of radiation for us to form a conclusion.



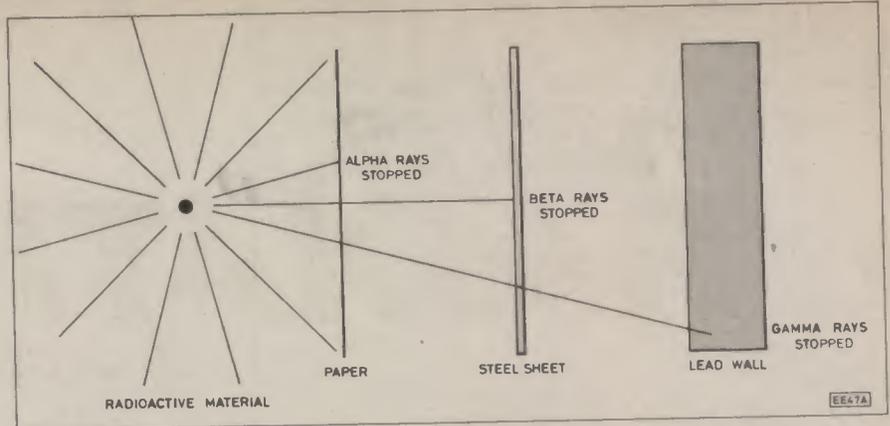


Fig. 2. The penetrating power of radiation.

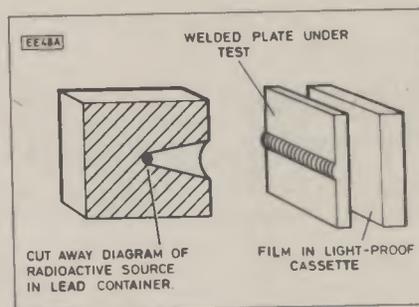

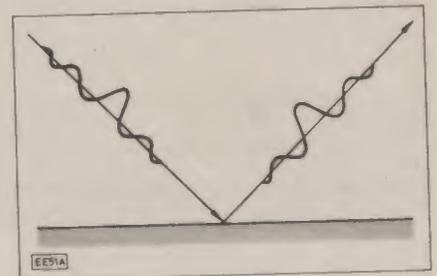Gamma radiography: the first effect of radiation to be discovered is still used in industry to detect faulty welds.



Photons "bouncing". Waves and solid objects both obey the same rule of reflection: angle of incidence equals angle of reflection.


FRIEND OR FOE

The radiation which surrounds us comes from the rocks in the earth and the water in the sea, from dust and gases in the air, even the atoms from which our bodies are made emit radiation. This has always been so since the earth was formed and always will be so. Radioactivity is not some evil man-made thing but a natural consequence of the way the universe is constructed. It is new only in the sense that we have only just become

aware of it. As always there are those who wish to use this discovery to kill others, and there are those who wish the knowledge to be lost and forgotten. It must have been the same when the first shivering cave-dweller discovered fire.


If we compare that first open fire to a modern central heating system, is it too much to hope that we can safely benefit from this find?

NEXT MONTH Fission and Fusion

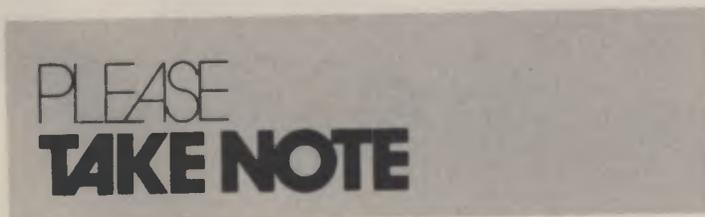

Spectrum Bench Power Supply (July 1984)

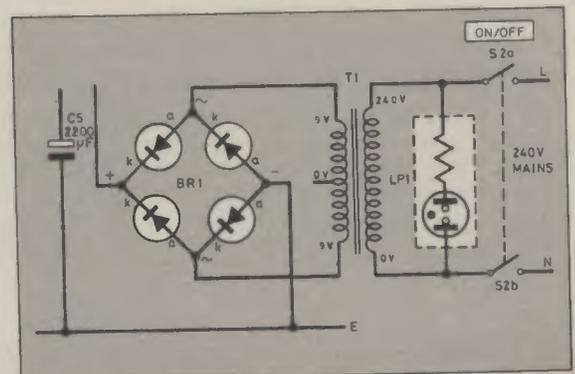The circuit diagram for the Spectrum bench power supply showed the bridge connections short circuited and the diodes reversed. The correct connections are shown in the circuit diagram below. The actual diodes are an integral part of the bridge rectifier.



ELECTROVALUE

Your SPECIALIST SUPPLIERS for SOLDER TOOLS



From a simple 15 watt model to a precision temperature controlled iron, we stock solder irons to suit all manual requirements together with supporting stocks of bits, de-solder tools, materials, etc.

ANTEX

C.240 - 15W/240V;
CSCN - 15W/240V
CS - 17W/240V
CSBP - 17W/240V + 13A plug
XS - 25W/240V
XSBP - 25W/240V + 13A plug
Replacement bits from 3/32" to 1"

De-solder heads, stands, elements and handles.

ERSA

'Sprint' high speed iron: 80/150W, 240V. Heats in 10 seconds!

ORYX

Temperature controlled solder iron TC.82 45W/240V with scale.
Oryx 50 - 50 watt version of above.

Standard types

Oryx 30 - 30W/240V
Viking - 27W/240V

Oryx M.3 - 17 watts, 12 volts

A wide range of replacement tips available for all models, also tips from 0.8 to 6.4mm dia. and flat tips.

Oryx safety stand.

Oryx de-solder tool.

MINIATURE SOLDER STATION

SOLDER and DE-SOLDER BRAID SOLDER in many grades.

Please mention this publication when contacting Electrovalue.

BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS - SEND FOR FREE 32 PAGE A-Z LIST ATTRACTIVE DISCOUNTS - FREE POSTAGE - GOOD SERVICE & DELIVERY

ELECTROVALUE LTD

(0784) 33603; Telex 264475
North - 680 Burnage Lane, Manchester. 061-432 4945.
EV Computing Shop -
700 Burnage Lane, Manchester. 061-431 4866

28 St. Judes Rd.,
Englefield Green, Egham,
Surrey TW20 0HB.

ACCESS AND
BARCLAYCARD
Phoned Orders
Welcome

5

FREE CAREER BOOKLET

Train for success, for a better job, better pay

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today - at no cost or obligation at all.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY


| | | | |
|---|--------------------------|----------------------------|--------------------------|
| ELECTRONICS ENGINEERING | <input type="checkbox"/> | TV & AUDIO SERVICING | <input type="checkbox"/> |
| ELECTRICAL ENGINEERING | <input type="checkbox"/> | RUNNING YOUR OWN BUSINESS | <input type="checkbox"/> |
| Name | | | |
| Address | | | |
| ICS Dept ECS84 160 Stewarts Road, London SW8 4UJ | | 01-622 9911 (all hours) | |

T.V. SOUND TUNER

SERIES II BUILT AND TESTED Complete with case. £26.50 + £2.00 p&p.

In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are common and all this is really quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact and independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains-operated.

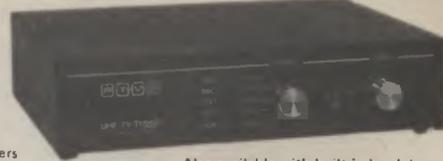This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder. Dimensions: 10 1/2" x 7 1/2" x 2 1/4". E.T.I. kit version of above without chassis, case and hardware. £16.20 plus £1.50 p&p.



Also available with built-in headphone amp. ONLY £32.50 + £2.00 p&p.

PRACTICAL ELECTRONICS STEREO CASSETTE RECORDER KIT

COMPLETE WITH CASE ONLY £34.50 plus £2.75 p&p.

• NOISE REDUCTION SYSTEM. • AUTO STOP. • TAPE COUNTER. • SWITCHABLE E.Q. • INDEPENDENT LEVEL CONTROLS. • TWIN V.U. METER. • WOW & FLUTTER 0.1%. • RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING. • FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TYPES.

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts, i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire. Featured in April P.E. reprint 50p. Free with kit.



125W HIGH POWER AMP MODULES

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

Accessories: Stereo mains power supply kit with trans. £10.50 + £2 p&p. Mono: £7.50 + £2 p&p.

KIT £12.00 + £1.15 p&p. BUILT £17.50 + £1.15 p&p.



SPECIFICATIONS:
Max. output power (RMS): 125 W. Operating voltage (DC): 50 - 80 max. Loads: 4 - 16 ohm. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100w: 400mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.

GOODMANS SPEAKERS AT BARGAIN PRICES

7" 60 watt Bass/Midrange speaker. 8 ohm impedance. Frequency response: 40 - 6,000Hz. 4 1/2" x 1/2" magnet. £14.95 plus £1.75 p&p.



12". 65W, impedance 4 ohms. Frequency response: 35 - 6,500Hz. Magnet: 3/4" x 4 1/2" dia. Foam surround, vinyl laminated cone. For use in Hi-Fi systems up to 65 watts. Bass/Midrange. £13.95 + £2.50 p&p.



BSR RECORD DECKS

Auto-Changer model - takes up to 6 records with manual override. Supplied with stereo ceramic cartridge. £12.95 plus £1.75 p&p.

3 speed, auto, set-down; with auto return. Fitted with viscous damped cue, tubular aluminium counter-weighted arm, fitted with ADC magnetic head. Ideally suited for home or disco use. £25.95

Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco. 13" x 11" approx. £14.95 plus £1.75 p&p.

HI-FI SPEAKER BARGAINS

AUDAX 8" SPEAKER £5.95 + £2.20 p&p.

High quality 40 watts RMS bass/mid. Ideal for either Hi-Fi or Disco use this speaker features an aluminium voice coil and a heavy 70mm dia. magnet. Freq. Res. 20Hz to 7KHz. Imp. - 8 ohms.

AUDAX 40W FERRO-FLUID HI-FI TWEETER Freq. res.: 5KHz - 22KHz. Imp.: 8 ohms. 60mm sq. £5.50 + 60p p&p.

GOODMANS TWEETERS 8 ohm soft dome radiator tweeter (3 1/2" sq) for use in systems up to 40W. £3.95 ea + £1 p&p. £6.95 pr + £1.50.

All mail to: 21A HIGH ST, ACTON W3 6NG, Callers: Mon - Sat 9.30 - 5.30 Half day Wed Access phone orders on 01-992 8430. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 31/3/84 and subject to change without notice. Please allow 14 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. All enquiries send S.A.E. Telephone or mail orders by ACCESS welcome.

STEREO TUNER KIT

SPECIAL OFFER! £13.95 + £2.50 p&p.



This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July '81). For ease of construction and alignment it incorporates three Mullard modules and an i.c. IF System. Front scale size 10 1/2" x 2 1/4" approx. Complete with diagram and instructions.

MONO MIXER AMP

Ideal for halls and clubs. £45.00 + £2 p&p.



50 Watt, six individually mixed inputs for 2 pickups (Cer. or mag), 2 moving coil microphones and 2 auxiliary, 2 moving coil microphones etc. Eight slider controls - 6 for tuner, organs and 2 for master bass and treble, 4 extra treble controls for mic. and aux. inputs. Size: 13 1/2" x 6 1/2" x 3 1/4" app. Power output 50 W RMS (cont.) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

CALLERS TO: 323 EDGWARE ROAD, LONDON W2. Telephone: 01-723 8432. (5 minutes walk from Edgware Road Tube Station) Now open 6 days a week 9 - 5.30. Prices include VAT.



SQUARE One FOR BEGINNERS

FOR SOME YEARS NOW, CMOS devices have been readily available, and this month *Square One* considers how they work, and also the kind of precautions that need to be taken when handling them.

STRUCTURE AND OPERATION

A conventional transistor works by making use of a small current (to the base) to control a larger one (through the collector load). The transistor may be either n-p-n or p-n-p type, but in either case the material used is normally silicon. The designation n-p-n or p-n-p refers to the structure of the transistor: n-type silicon has a relatively large number of free electrons, while p-type has a shortage. Pure silicon is a semiconductor: its ability to conduct electricity lies between that of a conductor and an insulator. When small quantities of phosphorus are added to pure silicon, the resulting "doped" silicon has an excess of electrons and is called n-type. When, instead, boron is used, the boron attracts electrons from the silicon atoms, creating "holes" in the structure. Silicon doped in this way is called p-type. The charge carriers in p-type silicon—"holes"—are locations that electrons can move to easily.

A field-effect transistor (f.e.t.) also makes use of p- and n-type silicon. The basic arrangement for an "n-channel" device is as shown in Fig. 1. When the f.e.t. is conducting, electrons will flow from n-type silicon at the "source" to n-type silicon at the "drain". In order to do this, they need to pass through the

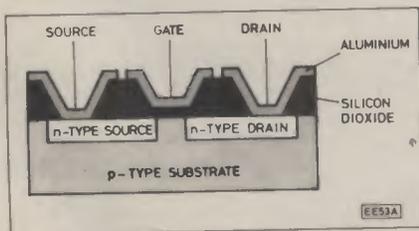


Fig. 1. Basic MOSFET structure.

p-type silicon in between—the substrate. Connections are made to the "source", the "gate" and the "drain"—"source" and "drain" indicate the direction of electron flow. Electrons possess a negative charge, and so the drain terminal is made positive, attracting electrons from the source. This electron flow is controlled by the electric charge on the gate, and this electric charge is related to the voltage on the gate.

Connections are made to metal (usually aluminium) contacts, and in the case of the gate, the metal is insulated from the substrate by a layer of silicon dioxide. Hence there is virtually no current flow possible through the gate; instead, as mentioned above, the voltage on the insulated gate creates an electric field—a positive voltage creating a field that attracts electrons, and a negative voltage repelling them. All this is summed up by the abbreviation MOSFET, standing for Metal-Oxide Semiconductor Field-Effect Transistor.

STANDARD CIRCUITS

When the source is at zero volts and the drain is made positive—say at +12 volts—electrons are attracted to the drain. A smaller positive voltage on the gate—say +5 volts—will repel positive "holes" from the p-type substrate (or, looked at another way, it will attract electrons) and so create a "channel" of n-type silicon between source and drain, as in Fig. 2. Electrons can then pass freely from source to drain.

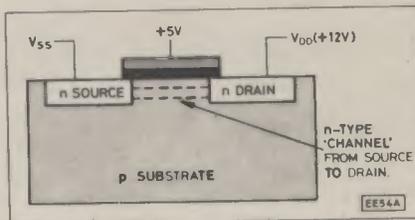


Fig. 2. N-channel MOSFET.

A p-channel device (Fig. 3) works in essentially the same way, except that this time a negative voltage is used to repel electrons from the n-type substrate and so create a conducting channel rich in "holes". The electric current flow is then a flow of "holes" from source to negative drain.

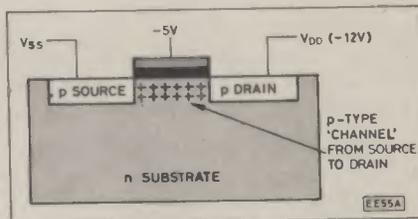


Fig. 3. P-channel MOSFET.

Devices which make use of both p-channel and n-channel f.e.t.s are referred to as CMOS—Complementary Metal-Oxide Semiconductors, and this arrangement offers several advantages. The basic CMOS inverter shown in Fig. 4 works very simply: a high input will make TR2 conduct and turn off TR1. The output will thus be at Vss (ground). A low input will switch off TR2 and switch on TR1 and the output will switch to Vdd (positive). From this inverter, all the usual logic functions can be built up—NAND and NOR gates, flip-flops, registers, as in TTL technology.

The two major advantages of CMOS over TTL are: very low power dissipation; and excellent noise immunity. The low power dissipation is due to the fact that there is only current flow at the input when the device is actually switching. Because the gate is insulated, there is no current flow at any other time. This becomes less advantageous, of course, as the

frequency of switching increases. The good noise immunity is a consequence of the fact that CMOS circuits will work over a wide supply voltage range—anywhere from about +3 volts to +15 volts. So if the device is operated from a +12 volts supply, "noise", in the form of transient voltage spikes, has to be of an amplitude greater than +6 volts to affect the circuit.

The major disadvantage of CMOS is its relatively slow speed of switching (though speeds are increasing all the time). This low switching speed is a direct result of the need for the voltage on the gate to set up an electric field; rather like charging a capacitor, this takes time.

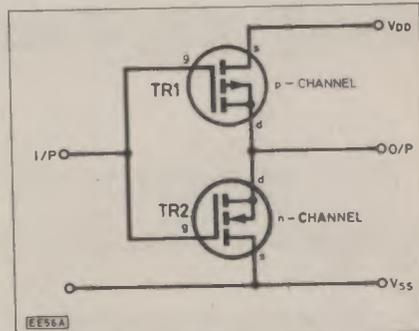


Fig. 4. CMOS inverter circuit.

STATIC SENSITIVITY

The major problem encountered with early CMOS devices was their vulnerability to static electricity. The thin gate insulation will break down at less than 100 volts, and someone walking through a carpeted office can easily acquire a static charge of many thousands of volts. Virtually all CMOS devices now have built-in protection, in the form of diodes to short-out high input voltages before the gate insulation can be damaged, but some care is still necessary when handling them.

Professional workshops and laboratories usually have a "safe-handling area": this is an area in which the workbench is covered in conductive foam, which is in turn connected to ground. The operator wears a wrist-strap made of conductive material, which is also connected to ground. Circuit boards are protected in transit by being packaged in conductive bags (see photo).

For the amateur, the important thing is to keep in mind the fact that CMOS circuits are vulnerable. They are normally sold pushed into a conductive foam pad, and should be left there until actual component insertion; and if possible, the work-area should be at ground potential.



Anti-static packaging for circuits that include static-sensitive devices.

MICROWAVE ALARM SYSTEM

I.F.H. GOULT

Part 3 of the Surveillance series

A CERTAIN mystique is often implied when microwaves are mentioned. This is completely unjustified. Microwave devices are usually very simple, and lend themselves to simple applications. One such application is a motion detector.

The generation of a transmitted wave pattern of specific wavelength and frequency, and the resulting signals received by a receiver have been described in a previous article. Suffice it to say here that reflections from stationary objects result in a received signal at the same frequency as the transmitter. Reflections from a moving object will result in signals having a frequency faster than the transmitted frequency if the object is moving towards the transmitter-receiver system, and slower than the original frequency if the object is moving away from the transceiver. The increase or decrease in frequency will be directly related to the speed to or from the transceiver. This is known as the doppler effect.

If a microwave signal is generated and transmitted in free space having a frequency as recommended by the Home Office for the domestic user of such devices—namely 10.687GHz (ten thousand, six hundred and eighty-seven million cycles per second) then the doppler return signal frequency will be 2Hz for a person moving one foot per second to or from the transceiver. Normal walking speed is about 2ft per second. A typical microwave transmitter-receiver is described here.

MICROWAVE DOPPLER MODULE

Typical modules are illustrated in the photograph. The transmitter-receiver will comprise a microwave oscillator and a mixer diode to compare the original oscillator frequency with the received signal frequency.

The simplest form of oscillator is the gunn diode oscillator. A gunn diode is similar to a conventional diode but has gallium arsenide as the semi-conductor material. Such a diode exhibits a "negative resistance" effect over part of

its voltage current characteristics. Fig. 1 illustrates this effect.

An electrical oscillator is analogous to the oscillating pendulum of a grandfather clock. The pendulum has to be supplied with energy to overcome the frictional resistance of the bearing on which it hangs, otherwise it would stop. The losses in a circuit are the electrical equivalent of the frictional losses of the clock and no electrical oscillations can be sustained unless these resistive losses are cancelled.

The introduction of the gunn diode working in its negative resistance region into a waveguide cavity will cancel out the resistance losses.

A gunn diode placed one half of the required wavelength from the reflecting wall of the cavity, as illustrated in Fig. 2, will sustain electrical oscillation in the cavity. The tuning screw in the cavity provides fine frequency adjustment.

The electrical pressure pattern is transmitted along the waveguide, which is open at the end to radiate the electrical pressure pattern (oscillating at 10GHz) into free space as a radio wave. The wavelength λ will be approximately 3cm.



This radio wave will be reflected back from any solid surface; coming back to the transmitter source at the same frequency, although delayed slightly in time (less than 1 millionth of a second).

THE RECEIVER

The receiver consists of a mixer diode placed in a suitable position in front of the gunn diode; or in an adjacent waveguide cavity having a hole coupling a small amount of leakage from the transmitter waveguide to the receiver waveguide.

The mixer diode gives an electrical output which contains any difference frequencies between the transmitted and received frequencies. These difference frequencies, which must have been caused by motion, can be amplified and used to trigger an alarm.

BASIC CIRCUIT FOR DOPPLER ALARM

The basic circuit arrangement and circuit diagram recommended by one doppler unit manufacturer are shown in Fig. 3. TR1 and IC1 are low frequency amplifiers.


The mixer current will normally be about 400 microamps d.c. due to the coupled signal from the cavity oscillator.

VR1 is set to give a d.c. voltage of about half that of the supply at the collector of TR1. IC1 has 100 per cent negative feedback to d.c. but will amplify low frequency signals.

The amplifier output will be constant for no movement. A signal of a few cycles per second will be amplified by TR1 and IC1, passing through C3 causing TR2 to

SPECIFICATION

| | |
|--|------------------|
| Operating frequency | 10.687GHz |
| Mean transmitted power | <10mW |
| Current consumption in detector mode | 1mA approx. |
| Range | 8 metres approx. |
| No susceptibility to interference from similar units operating locally | |

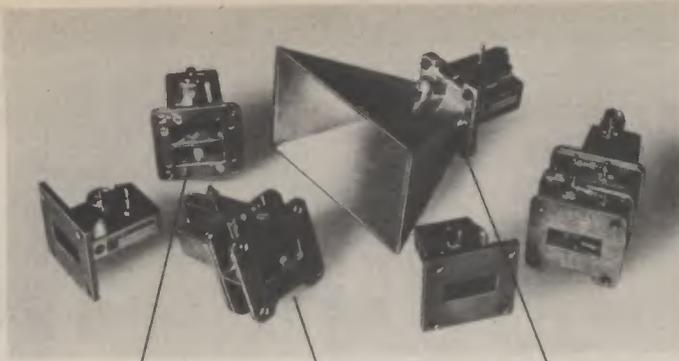

Mixer diode in waveguide adjacent to gunn diode oscillator.

Mixer diode in same waveguide as gunn diode.

Narrow beam horn aerial.

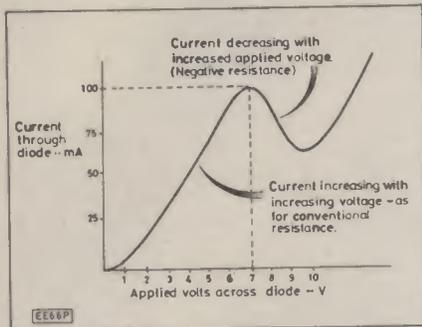


Fig. 1. Typical gunn diode negative resistance characteristics.

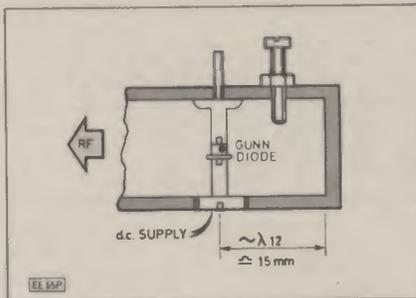


Fig. 2. Waveguide resonant cavity.

conduct during the negative half cycles of the signal. The current through TR4 will progressively charge C4 over several cycles of signal; typically five or six cycles, requiring one or two seconds of continuous movement before the positive potential on C4 is sufficient to switch on transistor TR3.


The sensitivity control VR2 sets the signal gain of amplifier IC1 to ensure that the noise level will not trigger the alarm when there is no movement.

The relay has been held on by the positive potential at the collector of TR3 which holds the positive input of IC2 above the -ve (inverting) input. When TR3 conducts the +ve input of IC2 falls below that of the inverting input cutting off the current in TR4. The relay is now de-energised.

The alarm is arranged to operate in the de-energised state in order to cater for the condition when the power supply wires may be cut by an intruder.

A gunn diode operating continuously takes a current of about 100mA to 125mA. This is too much for battery operation. Most microwave dopplers are usually wired systems.

A-BUY-AND-ADAPT PROJECT

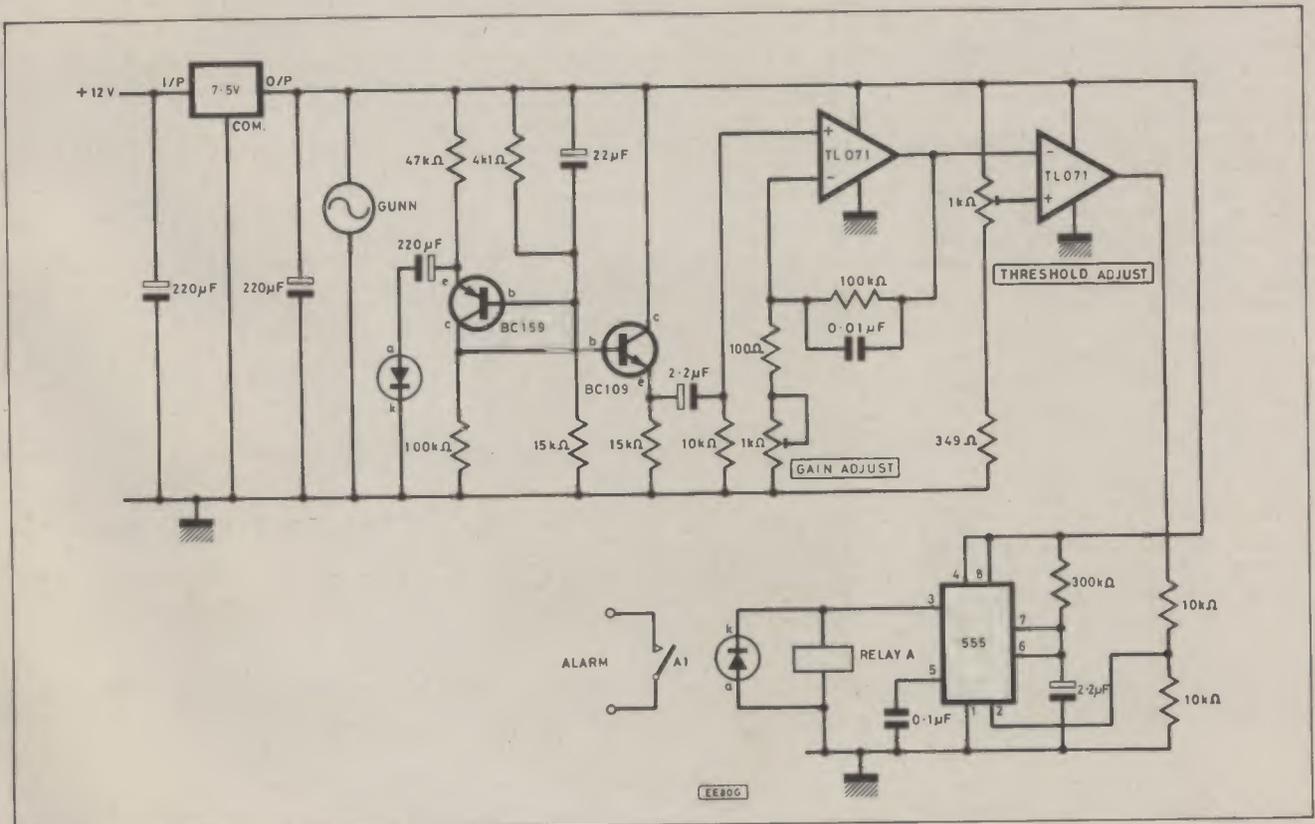

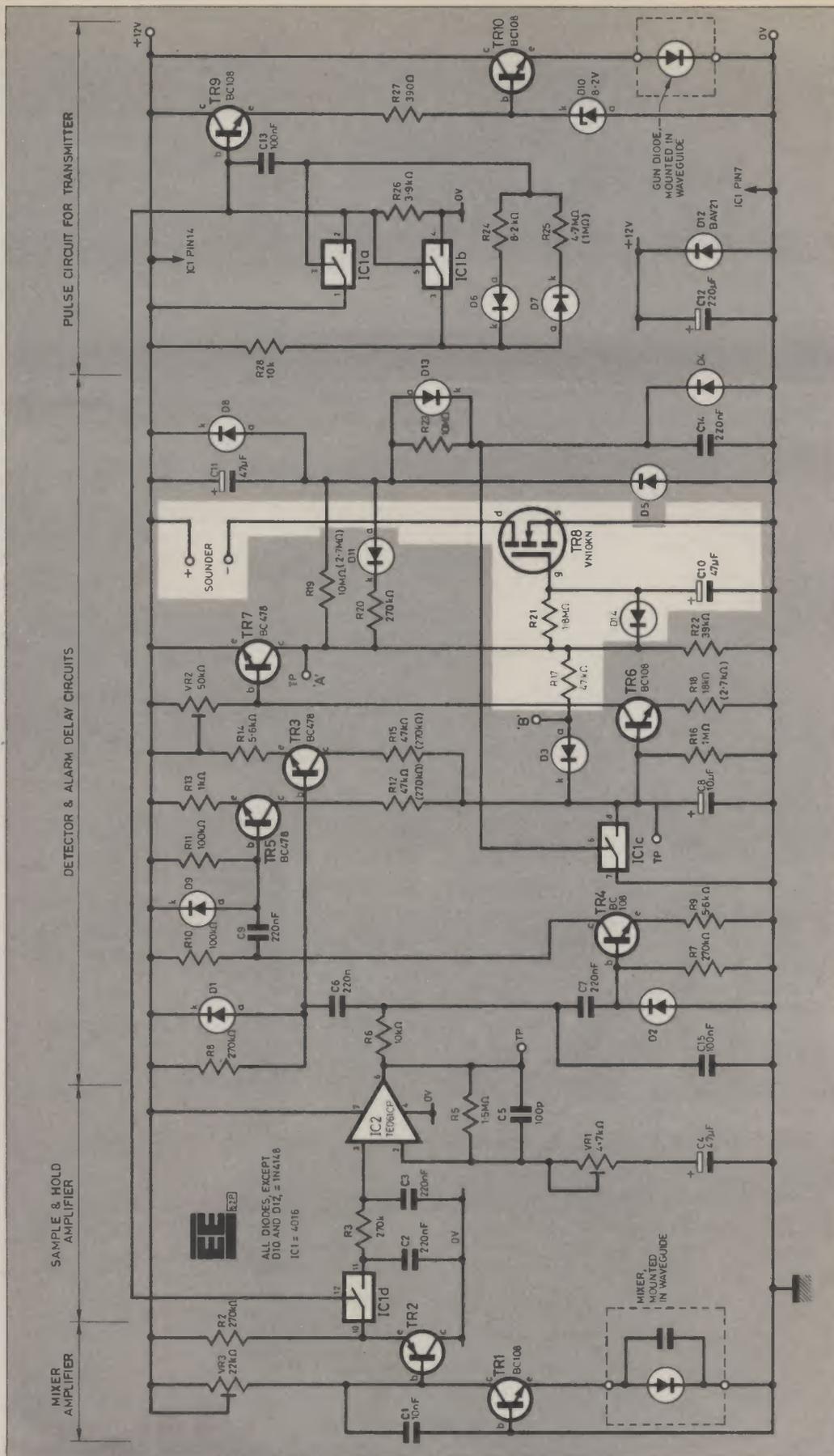


Fig. 4. Circuit diagram of the Microwave Intruder Alarm System as available from Avionic Systems. The non-tinted area shows the components which must be removed by the constructor when incorporating the adaptor kit featured in this article.


SELF-CONTAINED BATTERY UNIT

Fig. 4 illustrates a circuit of a self-contained battery operated unit. Battery power is saved by connecting the switches of IC1 to form a multivibrator which gives a positive pulse output of one millisecond about five times per second. The total current drain is reduced from well over 100 milliamps to about 1 milliamp. This will allow operation for about 1000 hours in the detection mode using eight alkaline type AA cells.

The pulse which switches the Gunn diode is also fed to a switch to connect the received signal to C2 during the transmission period. C2 thereby samples the level of the return signal which will remain at a constant potential if there is no movement: but will receive different potentials each time it is switched if there has been movement during the time between transmission pulses.

The amplifier and detectors will only pass the varying potential. TR8 will be latched ON when a varying signal is received to energise the piezo-electric sounder.

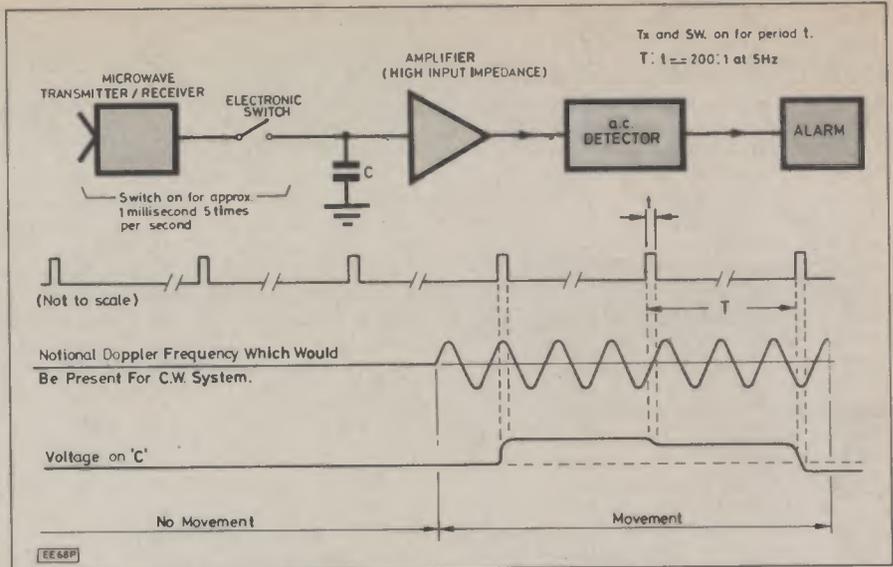When the alarm is on C11 will slowly charge and after about one minute will



A graphic description of how the circuit works.

apply sufficient potential at the input to the switch (pins 6, 8 & 9 of IC1) across C8 causing it to close, discharge C8 and unlatch the alarm to reset the circuit into the detection mode.

This entire self-contained unit can be accommodated into a stylish wood-veneered cabinet which looks very much like a small loudspeaker unit.

The sounder can be replaced by a relay to trigger alternative alarms, lights, etc.

further movement in the area.

On your return you have 10 to 15 seconds to switch off before the alarm will sound.

Domestic pets in the area will trigger the alarm also, fluorescent lights if switched on should be at least 10ft from the unit.

BATTERY CHECK

A push-button near the "ON/OFF" switch will give a green light indication that the batteries are in good condition. If the light does not glow, replace the batteries. The unit requires eight Duracell 1.5V size AA batteries (Duracell MN 1500). The batteries should give approximately 1000 hours of operation with the unit in the detection mode.

It is necessary to check the unit operation from time-to-time. It should be noted that the current consumption is increased by about thirty times when the alarm is sounding. When testing the alarm the sound should be left on for a few seconds only in order to conserve battery life.

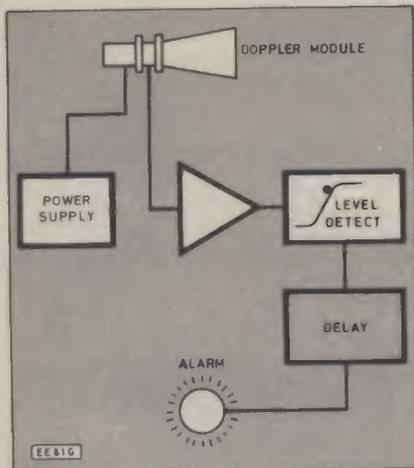



Fig. 5. Block diagram of the doppler module applications system.

OPERATING INSTRUCTIONS

Place unit on firm, steady surface and switch on, using the key provided. Leave the detection area within 30 seconds of switching on. The unit is now set to sound the alarm for any further movement in the area.

If movement is detected there will be a 10-second delay and then the alarm will sound for approximately one minute; after which the unit will reset to its movement detection mode, for example, the alarm will sound again if there is any

Fig. 6. Full circuit diagram of the adaptor kit.

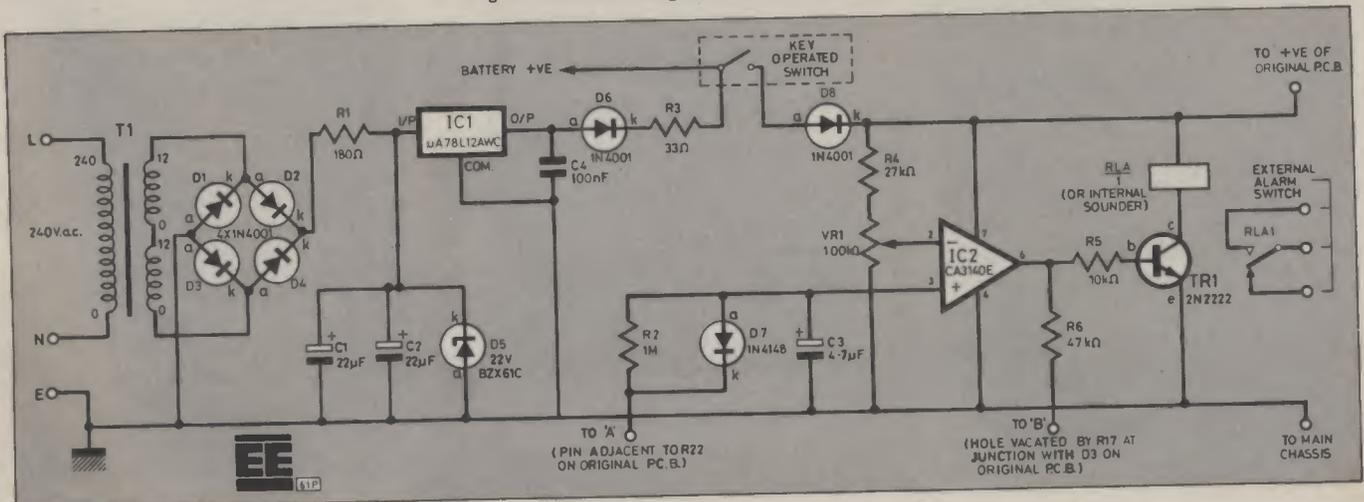

MODIFICATION KIT FOR MICROWAVE ALARM

The self-contained battery unit described in this article, was found to have certain unsatisfactory features. A limited quantity were manufactured, housed in a veneered loudspeaker style cabinet to blend with living-room furniture. The units were never marketed and are now available at cost price to the reader. The modifications listed below overcome the original limitations.

The first operational drawback was battery life. The design target was 1,000 hours using AA style alkaline batteries, but only about half this life was achievable. Thus the modification kit offered adapts the unit to mains operation; with back up Ni-Cad batteries in case of mains failure as an option.

The second problem in the original design was an effect known as "popping" in the gunn diode. This had the effect of giving a momentary kick to the mixer of sufficient level to trigger the alarm, causing false alarms. An additional time delay circuit is introduced by the modification which inhibits the activation of the alarm until continuous movement has been detected over a period of a few seconds.

These modifications take the form of an extra circuit board to add to the microwave unit. The basic microwave alarm unit would not meet with Home Office approval if built by the hobbyist and is not the constructional element of this article. The reader should purchase the alarm from AS(H) at cost price and construct the adaptor board described here.

THE BASIC INTRUDER ALARM UNIT



CIRCUIT DESCRIPTION

Mains transformer T1 and two 12-volt secondary windings: these are connected in series to provide 24V to the bridge rectifier formed by D1 to D2. The ripple is smoothed by R1, C1 and C2. The 22V Zener diode D6 protects the regulator from an excessive input voltage when there is negligible current drain on the circuit. The regulator IC1 provides a constant 12V at its output. This supplies the d.c. supply to the circuits through the ON-OFF key switch on the back of the microwave unit. It will also provide a trickle charge to the Ni-Cad stand-by batteries if fitted. These batteries are optional.

As described earlier, movement detected by the microwave circuit will switch on TR7 in this unit. TR7 collector is connected to point A on the time delay circuit. C3 will start to charge positively at a rate determined by the value of R2 and C3. When the voltage on C3 exceeds that on the slider of VR1 the output of IC3 will change from zero to about 9 volts positive switching on transistor TR1 to operate the relay or sounder.

When the output of IC2 goes positive, current through R6 holds on TR6 until condenser C11 has charged via R19 to switch on the semiconductor switch at pins 8 and 9 of IC1, re-setting the circuit to its stand-by operation.

MODIFICATION INSTRUCTIONS

Remove the back panel of the alarm unit by extracting six Philips head screws.

Remove battery cover. Release the battery box by extracting the four wood screws holding it in place.


The purpose of releasing the battery box is to obtain access to the printed circuit board which may now be released from its plastic holding clips. Fit the mains connector to back panel. Before any circuit modifications are carried out it is advisable to protect the microwave gunn and mixer diodes on the microwave module. Connect a one-inch length of wire first to the earth pin on the body of the unit, then to the mixer/gunn diode pin. The earthed wire should be touching the diode connection all the time the soldering iron is applied.

Remove the following components from the circuit board, R17, R21, R18, R25, R12, R15, R19, D14, C10, TR8 (the plastic transistor with the metal heat-sink).


Disconnect the sounder wires. Replace R12 and R15 with 270k Ω resistors. Replace R18 with a 2.7k Ω resistor. Replace R19 with a 2.7M Ω resistor. Replace R25 with a 1M Ω resistor.

Connect a six-inch length of insulated wire to the position vacated by R17 which connects to diode D3. Connect a six-inch length of insulated wire to TP4 (just above R22).

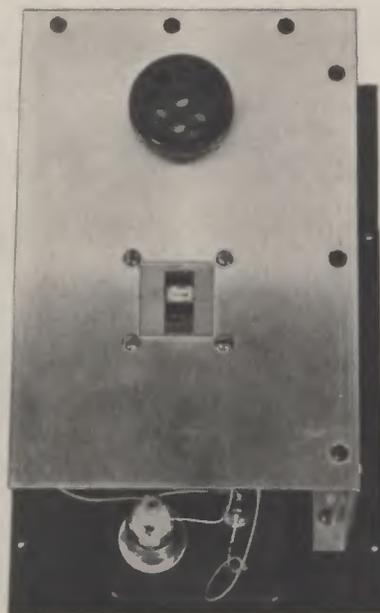Drill the chassis ready to accept the bracket assembly, previously made up as illustrated. Fix the made-up and tested time delay circuit board to the bracket assembly, first having connected the wire from D3 on the original p.c.b. to the land provided at (B) and the wire from the pin adjacent to R22 on the original p.c.b. to



View, showing the gunn diode in its resonant cavity, and the audible sounder.

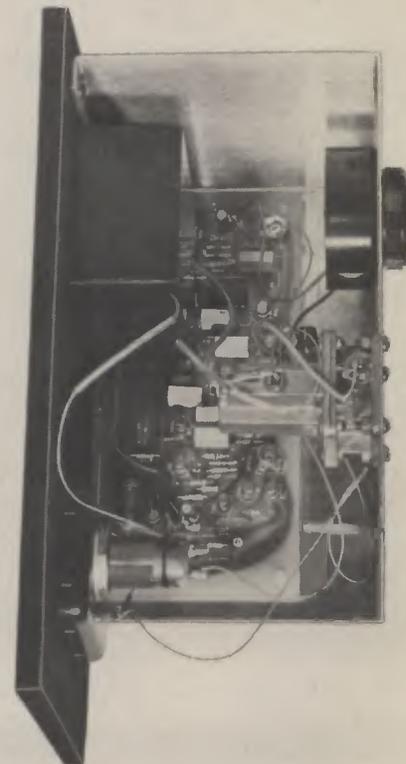

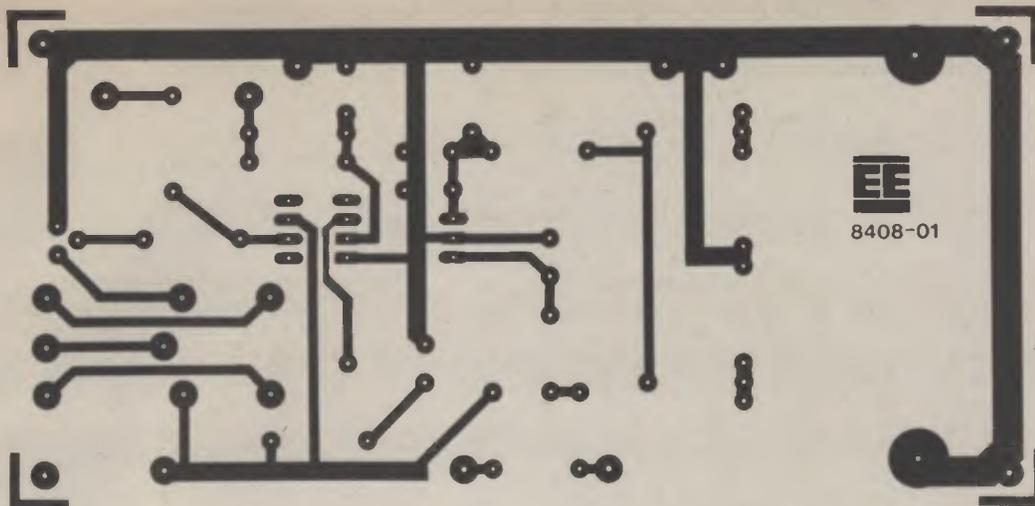


Fig. 7. P.c.b. layout of the adaptor board (actual size). This board is available from the *EE PCB service*, Order code 8408-01.

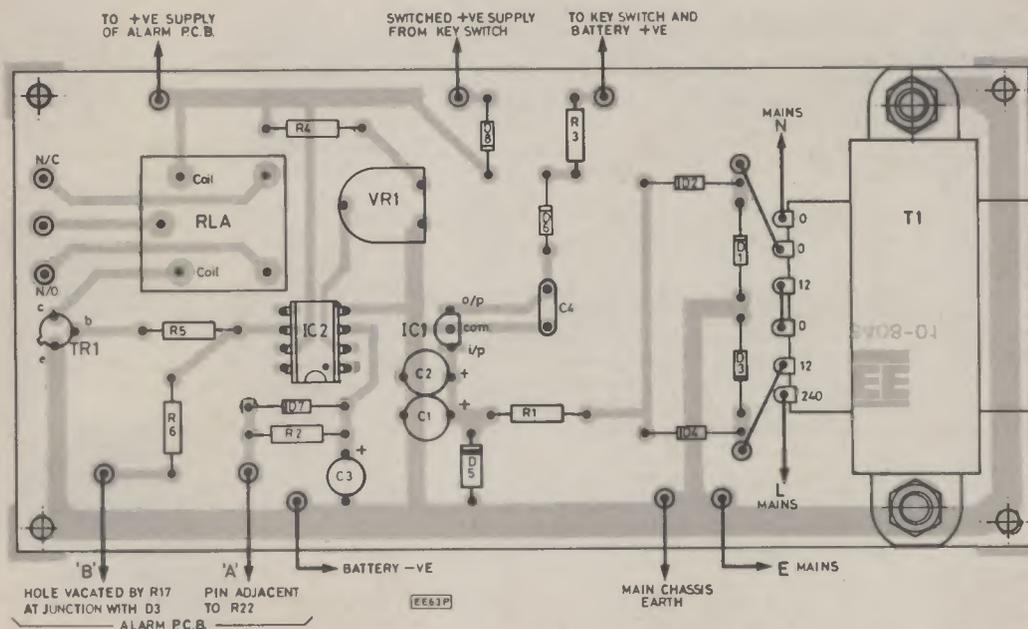


Fig. 8. Component layout of the adaptor board.

COMPONENTS

Approx. cost
Guidance only **£7.00**

Resistors

| | |
|--------|---------------|
| R1 | 180Ω |
| R2 | 1MΩ |
| R3 | 33Ω |
| R4 | 27kΩ |
| R5 | 10kΩ |
| R6 | 47kΩ |
| R12,15 | 270kΩ (2 off) |
| R18 | 2.7kΩ |
| R19 | 2.7MΩ |
| R25 | 1MΩ |

R12,15,18,19,25 for alarm unit
p.c.b. replacement

Potentiometers

| | |
|-----|--------------------|
| VR1 | 100kΩ Maplin WR61P |
|-----|--------------------|

Capacitors

| | |
|------|--------------------------------|
| C1,2 | 22μ/25V tant. bead |
| | Maplin WW73Q (2 off) |
| C3 | 4.7μF 16V or 25V tant. bead |

Diodes

| | |
|----------|------------------|
| D1-4,6,8 | 1N4001 (6 off) |
| D7 | 1N4148 |
| D5 | BZX61C 22V Zener |

Integrated circuits

| | |
|-----|------------------------------|
| IC1 | 12V regulator μA 78L12AWC |
| IC2 | CA3140E |

Transistors

| | |
|-----|--------|
| TR1 | 2N2222 |
|-----|--------|

Miscellaneous

Batteries (optional) Ni-Cad:
size AA.
Maplin YG00A (8 off).
Relay: Maplin YX96E.
Mains plug and Socket:
Maplin HL15R and HL16S
Transformer: Maplin WB10L

See
**Shop
Talk**

page 534

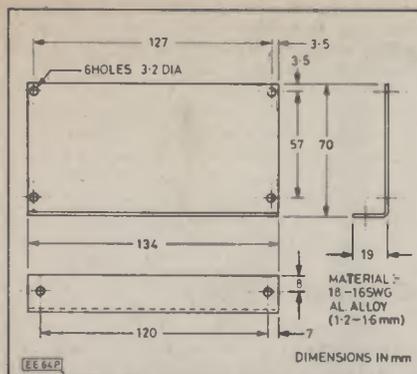


Fig. 9. Mounting bracket for the adaptor p.c.b.

the land provided at the junction of R2 and D3, point "A". Interconnect the switch and power supply wires as illustrated. Note that the switched supply must be disconnected from the alarm unit circuit board and connected to the new p.c.b. The supply line on the alarm unit p.c.b. is now connected to the +ve diode protected supply line on the new p.c.b. The battery leads may be left in their original positions.

Ensure that the p.c.b. is spaced off the bracket assembly sufficiently to avoid a short from the bracket to the track. Finally fix the bracket assembly to the chassis; check and re-assemble the alarm unit.

For mains operation fit only Ni-Cad batteries for standby operation. These will be on continuous trickle charge so long as the mains is connected.

Remove shorting links from the microwave module, disconnecting the earth pin last. Make sure the earth link is touching the diode connection until the soldering iron is removed.

TESTING

The time delay circuit should be checked independently before fitting to the main unit. Temporarily connect "A" to the zero volt line. Connect the sounder as illustrated. Connect to mains supply from the socket to the transformer input, ensuring the mains plug is not in!

Connect to mains supply, voltages at the positive of C1 and C2 should be about 22V d.c. The output at R3 with no batteries connected, should be 12V d.c.—and about 10 volts on the positive supply line when switched on through the key switch. VR1 should be set in the centre of its travel.

Disconnect "A" from earth and connect it to the +ve supply line. Note the time delay before the sounder is energised. Adjust VR1 to give a delay of about five seconds. Always connect "A" to earth for a short time to dump the charge on C3 before re-connecting it to the positive supply line to set the timing.

Complete the fitting of the delay p.c.b. to the chassis. Connect "A" to the pin adjacent to R22 and "B" to D3 using the

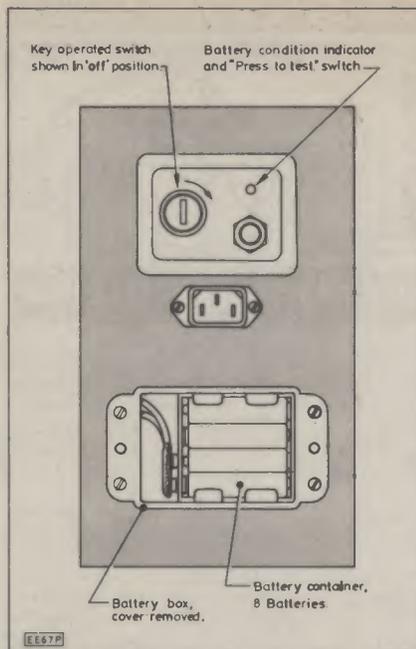


Fig. 10. Rear view of the unit, showing the added mains input socket.

copper land previously used by R17. Fit eight fully-charged Ni-Cad batteries if battery back-up for mains failure is required. The original p.c.b. was factory set and should need no further adjustment.

The system may now be checked by switching on, allowing one half to one minute for the system to settle down and then moving in the room for about five seconds. The alarm should trigger re-set after one to two minutes. The alarm delay time may be altered by adjustment of VR1, but it should be remembered that the shorter the delay time the more likely are false alarms.


RE-SETTING THE DOPPLER UNIT

As stated in the previous section, the original p.c.b. was factory set. If re-setting, either for interest or because the adjustments have been disturbed, is necessary then adopt the following procedure using an oscilloscope. If no oscilloscope is available an alternative procedure is also described using a high resistance voltmeter. Either disconnect the sounder, or temporarily connect a shorting link across C8. VR2 should be at maximum resistance (fully clockwise).

Connect the oscilloscope probe to the collector of TR1. (C1 provides an accessible point for the oscilloscope probe.) The unit should have open space in front of it for at least 5ft.

Switch on unit and allow one minute to settle. A negative-going pulse will be observed on the oscilloscope. VR3 should be set so that the pulse amplitude is 4V negative relative to the positive supply.

Connect the oscilloscope probe to R6

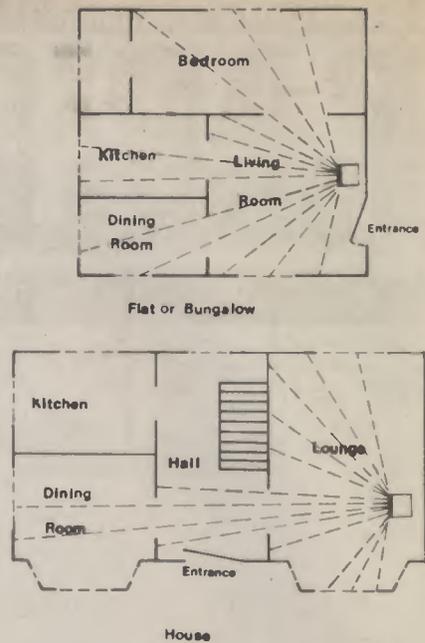

To avoid triggering from outside, place unit well clear of doors and windows

Fig. 11. Locational strategy of the unit.

at output of IC2. The d.c. level on the oscilloscope should be between 6V and 8V d.c. relative to the zero (earth) line. A pulse "spike" will be visible on the oscilloscope trace. This should be less than 1V peak when there is no movement detected by the microwave module. A very slight movement will increase this pulse amplitude.

Connect the oscilloscope probe to the collector of TR4. When there is no movement no pulse should be observed. The slightest movement will create a negative pulse at this point. The sensitivity is adjusted by VR1. VR2 should always be left for maximum resistance (fully clockwise) and no adjustment is necessary. If no oscilloscope is available the pulse level can be set by connecting a high resistance voltmeter to the output of IC2 at R6. VR2 is adjusted to give a d.c. level of 6V to 7V relative to earth. Care must be taken to ensure no movement occurs during this adjustment.


The sensitivity control VR1 is turned clockwise to increase resistance and reduce sensitivity to the point where there are no false alarms when there is no movement within the area. □

NOTE

Although this device radiates negligible radio frequency power, in order to operate, it is necessary to possess a Telapproach System Licence as defined in the Wireless Telegraphy Act 1949.

Application forms processed at:
Home Office Accounts Branch,
Tolworth Tower,
Ewell Road,
SURBITON, Surrey KT6 7DS.

RADIO WORLD

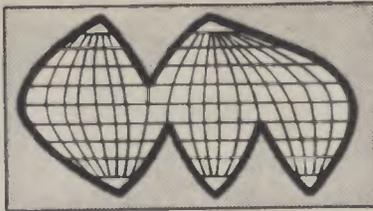

BY PAT HAWKER G3VA

In-Car Radio

For many years it has been accepted that listening to music from a car radio or tape cassette while driving does not represent a safety hazard—indeed may soothe a driver whose temper could otherwise be frayed by delays and traffic jams. But there are still doubts about some aspects of listening to more demanding material, such as the use of stereo headphones by drivers or cyclists and the operation of two-way radio telephones.

About 1966 the Ministry of Transport even announced that it proposed to ban the use of a radio transmitter while a car was in motion. However, following strong representations from the radio communications industry and radio amateurs this idea was dropped.

Although some research into the whole question of using radios in cars was carried out in the UK in the 1960s, little effort has been made to investigate this subject in recent years. Some American States now ban the use of stereo headphones by cyclists or drivers.

In the UK it is a clear offence to drive without proper control of the vehicle or to have a television screen within view of the driver (passengers in the back can be viewers). "Proper control" has been held to make it illegal for a driver to use an electric shaver, but does not cover straightforward use of a microphone. In the States there have been a few cases of mobile transmitter power leads short-circuiting and causing fires.

An article by Lydia Taylor, "Facing the Music," in *Care on the Road* (April, 1984) the journal of the Royal Society for the Prevention of Accidents (RoSPA) shows that there is still concern on some aspects of in-car entertainment.

Dr. Ivan Brown, assistant director of the Medical Research Council's Applied Psychology Unit, is quoted as suggesting that sound inputs to a driver's brain that require "mental processing" can allegedly interfere with his visual inputs. In other words, listening to undemanding music presents no hazard but "road safety could be reduced if drivers use their in-car radio/cassette players to do their Open University homework".

There is also the feeling that the control of some equipment involves too much knob-fiddling and the need for the driver to take his eyes off the road. The use of stereo headphones or over-loud speech or music can, it is suggested, impair the driver's monitoring of useful auditory information, for example, from horns outside the vehicle or any warning signs coming from the engine.

There are EEC regulations governing equipment installed in cars intended to en-

sure that the driver could not be cut by any part of a radio, get his fingers entrapped, or receive an electric shock. Radio/cassette units are expected to be reasonably easy to operate and to have rounded, recessed controls.

European broadcasters are currently investigating a new "radiodata" system which, for example, would automatically tune a radio to a selected programme, etc., without the driver touching any controls, and which might be used in connection with traffic information. But such a system is, operationally, still some way away and is likely to be incorporated only in the more expensive car radios.

There would appear to be few regulations applying specifically to two-way radio, although, for example, the R.S.G.B. does have a list of safety recommendations for mobile operators. With the vast increase in two-way car radios stemming from CB and from the introduction soon of 900MHz cellular radio systems, it is surely time for more detailed research into safety aspects of in-car radio and electronics.

Private Robot, Infantryman

There are many people who regret that such a high proportion of the British and American electronics and communications effort is directed towards what is euphemistically called the Defence Industry. Military communications have advanced a long way from the old wartime sets but it often appears that no sooner has a new system been developed than the same team set about finding an effective way of jamming it, and then a method of countering the jamming, and so on *ad infinitum*.

The electronic equipment fitted in some military aircraft now costs about ten times as much as the basic aircraft; there is also a rule-of-thumb estimate that the cost of maintaining military equipment throughout its operational life can similarly cost ten times as much as the original equipment.

Currently much effort on both sides of the Atlantic is being put into what is called C³I, tactical radio systems for communications, control, command and Intelligence; also in protection of electronic and telecommunications equipment against EMP, the destructive electromagnetic pulse that can follow a high-altitude nuclear explosion; and "stealth" aircraft that would not be detectable by radar or infra-red sensors—not to mention the whole frightful concept of "star wars".

But at least the US Advanced Research Projects Agency is busy working out how to use "artificial intelligence" on the battlefield. One idea is to develop a robot machine that instead of having wheels or

tracks would clomp around the battlefield on legs, remotely or self-guided by means of TV eyes and super-computers to form an autonomous land vehicle, a sort of all-electronic infantryman.

Provided they can be fought out entirely by such robots, preferably in the middle of some remote desert, this sounds a sensible way of fighting wars; an activity from which most humans will be only too glad to opt out!

Consumer Risks

The news that RCA is ending manufacture and marketing of their CED video disc players after losing an admitted \$500-million (and probably a good deal more if all development costs were included) underlines the risks involved even for major firms in attempting to introduce new technology to the consumer-electronics market. Yet, if the video disc, with its very high technical quality and the lower-cost of discs than tape, had been marketed a few years before, instead of after the rival VCR machines, the story might have been very different.

Tape is more expensive, technical quality of the pictures significantly lower, but the VCR has the attractive feature of "record" as well as "playback". That advantage appears to have been decisive in market appeal.

Meanwhile, the City is pondering the financial risks in cable TV, direct broadcasting from satellites, home video networks and the like. It is interesting to note that during 1983 deliveries in the UK of television sets (about 1-million monochrome, 3.5-million colour) was an industry record. The two-set home is becoming the norm and, with home computers and so on, the three-set home is no longer a rarity. But the VCR boom is slowing down with 2.2-million machines delivered in 1983—almost exactly the same figure as for 1982.

30-line Museum Piece

Plessey Radar are to be congratulated on restoring one of the extremely rare 30-line disc £18 Televisors made by Plessey for the original Baird company between 1929 and 1932. This has now been loaned to Douglas Byrne, G3KPO, for his Arreton Wireless Museum on the Isle of Wight. It is believed that this is one of only six still in existence.

But what puzzles me is the fanatic determination of some academics and others to perpetuate the idea that the Baird 30-line system, forced on the BBC by the Post Office and the politicians, ever had any real chance of success.

Apart from the extremely crude pictures, the system had no effective method of providing synchronisation. The disc televisors used a phonic wheel that was expected to lock on to the black edge of the picture, since there were no "blacker-than-black" synchronising signals in the transmitted waveform sent out on the medium-wave band. Effective television had to wait for the coming of v.h.f. and synchronising pulses.

I shall not be popular in Scotland for saying so, but it is stretching credibility to the limit to pretend that Baird was the sole inventor of television! Campbell-Swinton, Zworykin, Blumlein and others deserve an equal share of the credit!

OSCILLATORS

A variety of different types of resistance capacitance feedback oscillators, all having wide use, are described in this short series. Some of the circuits are based on discrete semiconductors, others on familiar i.c.s. In addition to theory of operation, design pointers for particular needs and applications are given. Each part in the series also includes a detailed circuit for a practical project.

Part Three: DIGITAL CMOS DEVICES

By J. R. DAVIES

ALTHOUGH not primarily designed for use as oscillators, digital CMOS inverters, NAND gates and NOR gates can be readily employed in simple RC oscillator circuits. These are dealt with in this chapter. One digital CMOS device, the 4047 monostable/astable multivibrator, is specifically intended to function as an oscillator in its own right and will also be described.

Digital CMOS NAND gates with Schmitt trigger inputs can also be employed as RC oscillators, and this application will be covered in the next part of this series, which describes hysteresis oscillators.

CMOS CIRCUITRY

A basic understanding of the internal functioning of CMOS inverters, NAND gates and NOR gates is desirable before carrying on to their use as oscillators. Fig. 3.1 shows a CMOS inverter comprising a *p*-channel f.e.t. and an *n*-channel f.e.t. When the input voltage on the gate of the *p*-channel f.e.t. is high, that is, at or near the positive rail, this f.e.t. is turned off. If the *p*-channel gate is taken negative

of the positive rail, a gate voltage is reached at which the f.e.t. commences to turn on. The *p*-channel f.e.t. is fully turned on when its gate voltage is low, at or near the negative rail.

The *n*-channel f.e.t. has a similar performance with all polarities reversed, and it is turned off when its gate voltage is low. Taking its gate positive causes the *n*-channel f.e.t. to turn on after a certain voltage is reached, and it is turned fully on when its gate voltage is high.

The device functions as an inverter because when the input is high the *p*-channel f.e.t. is turned off and the *n*-channel f.e.t. is turned on, giving a low voltage at the output; and because when the input is low the *n*-channel f.e.t. is turned off and the *p*-channel is turned on, with a high voltage being given at the output. The gate drive current required at the input is negligibly low, being in the order of pA (picoamps, or millionths of microamps) only.


The typical input curve of Fig. 3.2(a) shows a typical input voltage/output voltage transfer characteristic for a CMOS inverter. The supply voltage is 9 volts. When the input gate voltage is low,

at zero, the output voltage is high, at 9 volts. Both voltages are with respect to the negative rail.

As the input voltage is taken positive, up to about 2 volts, the output voltage stays high, but after this it commences to go low. The rate of change is small at first, increases to a high rate of change at an input voltage of around 4.6 volts, and then slows again until, at an input voltage of around 7.3 volts, the output is fully low. It stays low as the input voltage continues up to 9 volts.

The two broken line curves in Fig. 3.2(a) show outside limits for the transfer characteristic. The CMOS inverter meets specification if its transfer characteristic is within the two outside limits. As may be seen, a fairly wide spread is permissible but the output is always fully high for input voltages below about 1 volt, and is always fully low for input voltages above about 8 volts.

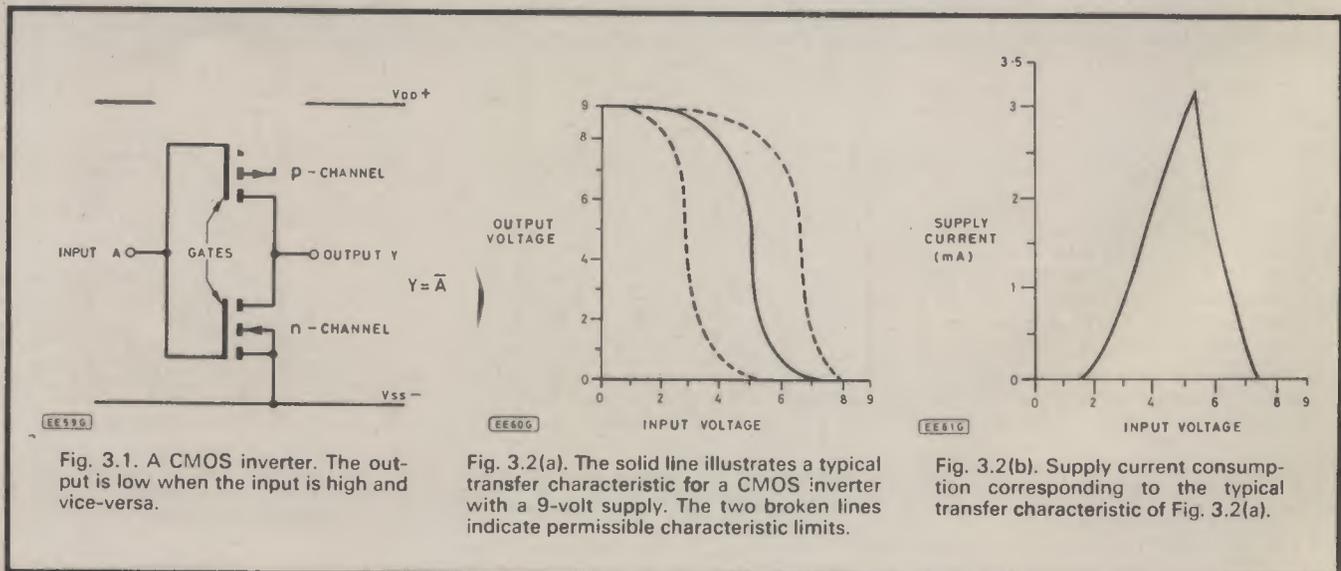A typical curve illustrating inverter supply current drawn from the supply for different input voltages is shown in Fig. 3.2(b). At input voltages nearly up to the point at which the typical transfer characteristic of Fig. 3.2(a) starts to go negative,



the current drawn from the supply is too small to be shown on the graph, and can be expected to be of the order of $0.01\mu\text{A}$.

As the input voltage increases, causing the transfer characteristic to enter its curved section, supply current increases because both the p -channel f.e.t. and the n -channel f.e.t. are now turned on. Supply current increases to a maximum of around 3mA near the input voltage point where the transfer characteristic has maximum slope, then falls off to the negligibly low value in the order of $0.01\mu\text{A}$ for input voltages above some 7.5 volts.

Thus, the supply current drawn by the CMOS inverter can, for nearly all practical purposes, be considered as being negligibly low under quiescent conditions, and it rises to a peak of around 3mA during the transition from one state to the other.

The curves of Fig. 3.2(a) and 3.2(b) are applicable to a supply voltage of 9 volts. They can be scaled up or down, roughly proportionally, for higher or lower supply voltages.

NAND, NOR GATES

Circuit Fig. 3.3 shows a CMOS 2-input NAND gate with its four f.e.t.s identified as TRA to TRD. When both inputs are low, TRA and TRB are turned on, and TRC and TRD are turned off. The output is high. If input A is high and input B is low, TRA is off, TRB is on and TRD is off. TRC cannot turn on because no current is available for it through TRD, and the output is high. Taking input B high with input A low results in TRA being on and TRC being off, so that the output is once more high. The output goes low when both inputs are high because TRA and TRB are then turned off and TRC and TRD are both turned on.

A 2-input NOR gate is shown in Fig. 3.4, and this is virtually the NAND gate turned upside down. When the two inputs are low both the p -channel f.e.t.s are turned on and the output is high. If either one or both of the inputs is taken high, either one or both of the n -channel f.e.t.s turns on and the output goes low.

A 2-input NAND gate can be used as an inverter by connecting together its two inputs to form a single input. Similarly, a 2-input NOR gate becomes an inverter if its two inputs are connected together. Both configurations are shown in Fig. 3.5. When so connected, the NAND gate and NOR gate exhibit the same transfer characteristic and supply current curves as does the simple inverter.

Inverters are available in a number of CMOS devices, including the 14-pin dual-in-line 4007, whose internal circuitry is illustrated in Fig. 3.6(a). This i.c. has one true inverter with an input at pin 10 and an output at pin 12 and two complementary pairs, and all three sections may be interconnected to produce a number of different logic functions. If the 4007 is connected up as in Fig. 3.6(b) it provides three separate inverters.

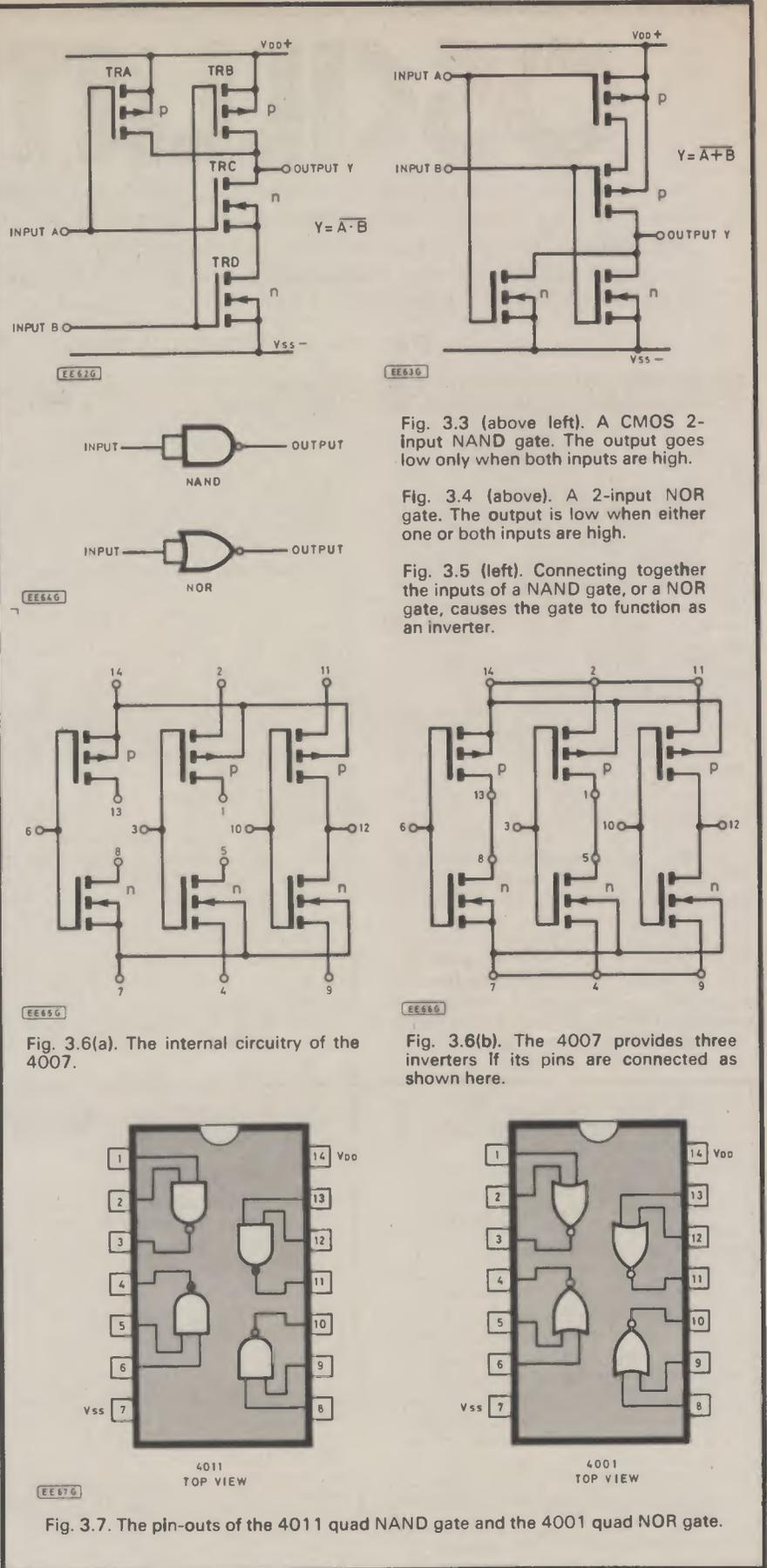


Fig. 3.3 (above left). A CMOS 2-input NAND gate. The output goes low only when both inputs are high.

Fig. 3.4 (above). A 2-input NOR gate. The output is low when either one or both inputs are high.

Fig. 3.5 (left). Connecting together the inputs of a NAND gate, or a NOR gate, causes the gate to function as an inverter.

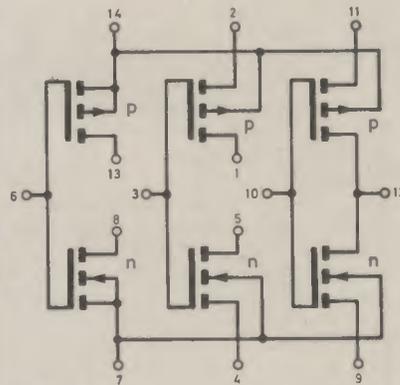


Fig. 3.6(a). The internal circuitry of the 4007.


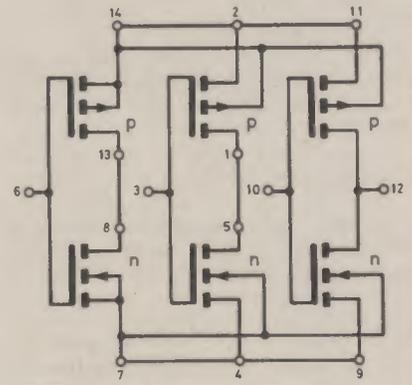


Fig. 3.6(b). The 4007 provides three inverters if its pins are connected as shown here.

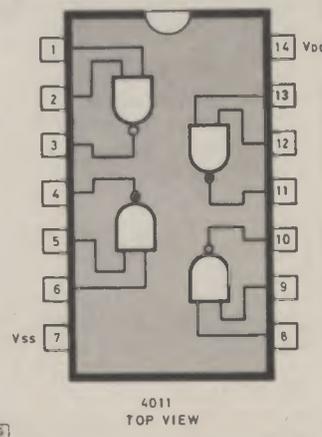

EE696

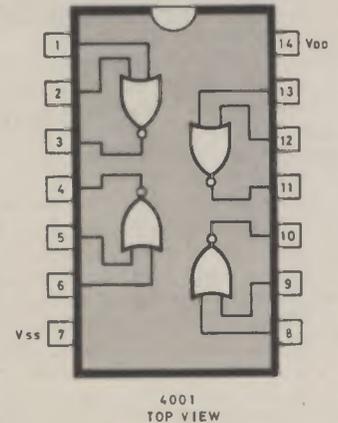


Fig. 3.7. The pin-outs of the 4011 quad NAND gate and the 4001 quad NOR gate.

It has become common practice to use NAND and NOR gates as inverters because these gates are cheap and readily available. Also, if two gates of a quad gate i.c. are connected as inverters and employed in a CMOS oscillator, the two remaining gates can be used for logic circuitry. Two very popular gates for oscillator applications are the quad 2-input NAND gate type 4011 and the quad 2-input NOR gate type 4001. These have the pin-outs shown in Fig. 3.7.

CMOS HANDLING

The current range of digital CMOS devices with the letter "B" immediately following the type number is suitable for supply voltages from 3 to 18 volts with an absolute maximum of 20 volts. (Earlier devices with the letter "A" immediately following the type number had supply ratings of 3 to 12 volts with an absolute maximum of 15 volts.)

The gate insulation in each gate is very thin and can readily breakdown at quite low voltages outside the positive and negative supply rails. The gates are, in consequence, protected by internal diode circuits of the type illustrated in Fig. 3.8. The diodes prevent any gate being taken more than about 0.6 volt higher than the positive rail or more than about 0.6 volt negative of the negative rail.

The diodes do not give full protection against high static voltages, and CMOS devices need to be handled with some care. They should be kept in their conductive packing until required and should be soldered into circuit with an iron having a reliably grounded (earthed) bit.

As we shall next see, the protective diodes play a part in the operation of simple CMOS oscillators.

CMOS OSCILLATOR

What is probably the most commonly encountered digital CMOS oscillator is shown in Fig. 3.9(a). This is illustrated with two NAND gates, and the same results would be given with two NOR gates or two inverters.

At one instant in the oscillator cycle we have the voltage conditions shown in Fig. 3.9(a). The input of gate G1 is low, the output of G1 is high and the output of G2 is low. Capacitor C is therefore charging via R2 with its left-hand plate going positive. Virtually zero current flows through R1 into the input of G1, but this input is still being taken continually positive by left-hand plate of C.

After a time the input of gate G1 goes sufficiently positive for the gate transfer characteristic (see Fig. 3.2(a)) to enter its curved section and the gate output starts to go negative, taking the input of gate G2 similarly negative. After a further period the input of gate G2 also enters the curved section of its transfer characteristic, whereupon there is a chain of linear amplification from the input of gate G1 to the output of gate G2. The circuit then very rapidly changes to its alternate state, with G1 input high, G1 output low

and G2 output high. This is shown in Fig. 3.9(b).

Now, at the instant before this rapid changeover capacitor C was charged, with its left-hand plate positive. Immediately after the changeover, which caused G2 output to go high, the left-hand plate of C is actually taken positive of the positive supply rail for the gates, so that at the start of the half-cycle C is discharging via R1 into the protective diodes at G1 input, as well as into the low G1 output via R2. The discharge current into the diodes continues for a small fraction of the half-cycle until the voltage on the left-hand plate of C falls below that at which the protective diodes conduct. The only current from the capacitor which then flows is through R2 into the low output of gate G1.


Capacitor C1 is now charging in the opposite direction and its left-hand plate is going negative whereupon, after a period, the input of G1 reaches the curved section of its transfer characteristic and, later, so does the input of gate G2.

Again there is a chain of linear amplification through the two gates, and it causes a rapid transition to the first state, with G1 input low, G1 output high and G2 output low.

This time the left-hand plate of C goes negative of the negative supply rail, and current from the capacitor initially flows via R1 into the protective diodes at G1 input. Shortly after, the only capacitor current which flows is via R2 into G1 output and the circuit is in the same state as it was when we started to examine it.


OSCILLATOR FREQUENCY

The best place in the oscillator circuit to take an output is from the output of gate G2. If both gates have a transfer characteristic in the centre of the permissible spread this output is a square-wave whose voltage swings between the positive and negative supply rails. In practice, different transfer characteristics can cause the duty ratio to lie between some 30 per cent and 70 per cent.

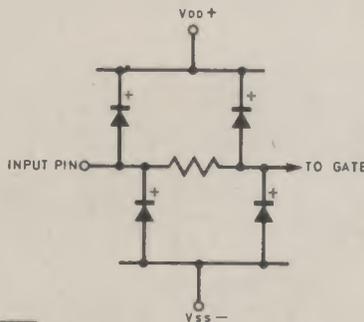


EE69G

Fig. 3.8. Protection circuit for a CMOS input.

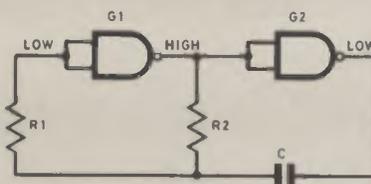


EE69G

Fig. 3.9(a). Two NAND gates connected as a CMOS RC oscillator. At one instant in the oscillator cycle the gate inputs and outputs will have the voltages indicated.

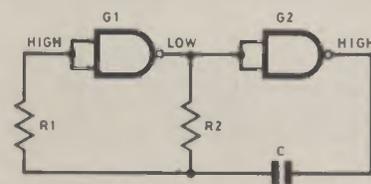


EE70G

Fig. 3.9(b). The input and output voltages change on the alternate half-cycle.

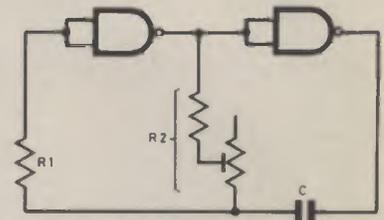


EE71G

Fig. 3.10. Making R2 partly adjustable to provide a specific oscillator frequency.

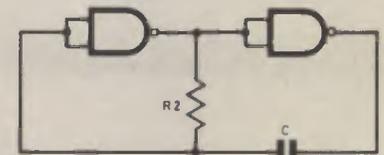

EE72G

Fig. 3.11. Frequently, the oscillator is employed with R1 omitted.

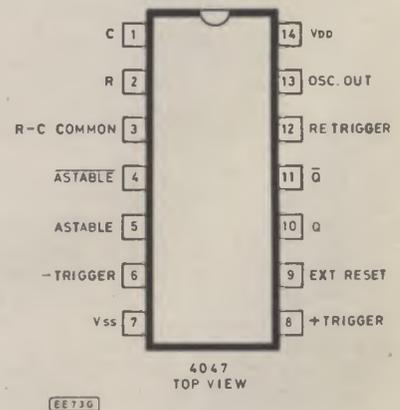

EE73G

The transfer characteristic spread also makes it impossible to calculate oscillator frequency precisely, although it is nevertheless a simple matter to arrive at rough approximations.

During the initial part of each half-cycle current from C flows into the protective diodes at the input of G1 whilst, over the whole half-cycle, the capacitor current flows through R2 into the output of gate G1. If R1 is given a value which is equal to, or greater than, R2 it has only a small effect on oscillator frequency, whereupon the major control is exerted by C and R2 only. It is found in practice that the length of each half-cycle is then very approximately equal to the time constant of C and R2.

If, for instance, C is 0.01 μ F and R2 is 100k Ω (= 0.1M Ω), with R1 having the same or a greater value, the length of each half-cycle calculates as 0.01 \times 0.1, or 0.001 second. The length of the total cycle is 0.002 second, the reciprocal of which gives a frequency of 500Hz. So, if we make C 0.01 μ F and R2 100k Ω , we

can expect the oscillator to operate at around 500Hz.

ADJUSTABLE RESISTANCE

Normally, digital CMOS oscillators of the type described here are not required to have accurately determined frequencies, and variation in frequency from one device to the next is quite acceptable. If a fairly precise oscillator frequency is required, R2 can be made largely variable, as in Fig. 3.10, and its resistance can then be adjusted until the desired frequency is obtained. R2 now consists of a fixed and variable resistor in series.

Should the calculated value for R2 at a required frequency be say 200k Ω , the fixed resistor could be 100k Ω and the variable resistor 220k Ω . It should then be possible to arrive at the required frequency by adjusting the variable resistor.

The oscillator circuit is often used with R1 omitted, as in Fig. 3.11. In many cases this tends to significantly increase the frequency because at the start of each

half-cycle C rapidly discharges into the protective diodes at G1 input. The circuit of Fig. 3.11 saves a resistor and has the slight disadvantage that the frequency of oscillation may be further removed from the approximate value given by calculating the time constant of C and R2.

Suitable practical values for R2 are between some 2k Ω and 1M Ω , whilst those for C lie between about 0.001 μ F and 0.5 μ F. These figures point to maximum and minimum frequencies of about 250kHz and 1Hz, respectively, although oscillator performances may be a little unpredictable at these extremes.

CURRENTS

The supply current drawn by the oscillator is relatively high for a circuit incorporating CMOS devices, and at 9 volts can be of the order of 0.3 to 0.7mA, or even higher. The high current is partly explained by the fact that gate G1 is on the curved part of its transfer characteristic for a significant part of each half-cycle. Also, the two gates pass through their current consumption peak twice during each cycle.

The output current capability of the oscillator, when using 4001, 4007, 4011 and similar devices with a 9-volt supply, is in excess of 2mA both when the output is in the high and in the low condition.

THE 4047

The 4047 is a digital CMOS device which is specifically intended to operate as an astable (free-running) or monostable ("one-shot") multivibrator. It tends to be a little more expensive than the two inverters, NAND gates or NOR gates employed in the previous oscillator circuit, but it offers three advantages.

The first of these is that oscillator frequency is defined by manufacturer's specification and can be readily calculated. The second advantage is that the 4047 offers a true 50:50 squarewave output. The third advantage is that, with a suitable choice of external frequency control components, it is capable of running at very low supply current levels.

The i.c. is housed in a 14-pin dual-in-line package having the pin allocations shown in Fig. 3.12. A block diagram illustrating its logic functions is given in Fig. 3.13. The i.c. contains a low power astable multivibrator whose output, after passing through a buffer amplifier, appears at pin 13. The oscillator frequency is controlled by the external capacitor and resistor connecting to pins 1, 2 and 3. The oscillator output also passes to a divide-by-2 circuit which presents a Q output at pin 10 and a not-Q output (bar over the letter signifies "not") at pin 11.

In this series we are interested in the astable operation of the 4047 and the trigger, retrigger and external reset pins are not involved in this function. These pins are returned to the positive or negative rails as indicated in Fig. 3.14, which shows the circuit required for continuous astable running.

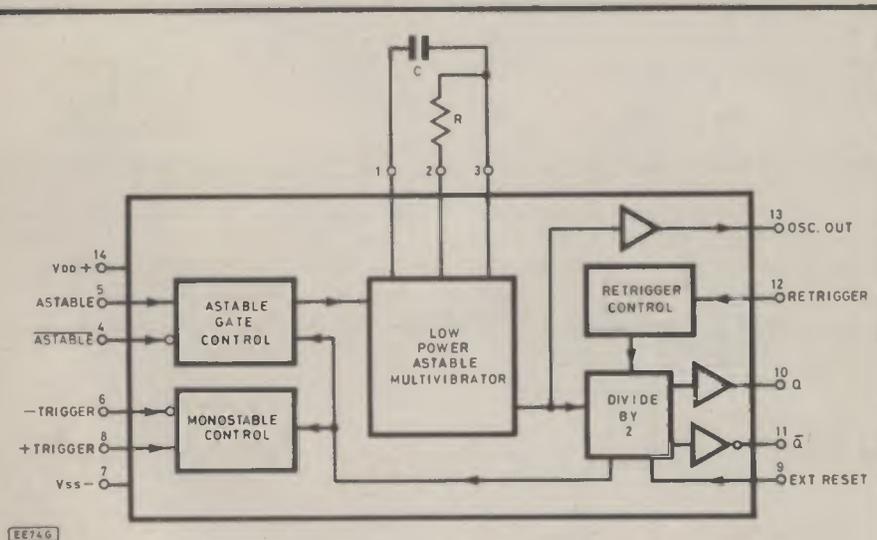


Fig. 3.13 (above). Block diagram illustrating 4047 internal logic circuitry.

Fig. 3.12 (left). The pin allocations of the 4047 monostable/astable multivibrator.

Fig. 3.14 (right). The 4047 connected for continuous astable operation. Outputs are available at pin 13 (oscillator frequency) and at pins 10 and 11 (half oscillator frequency).

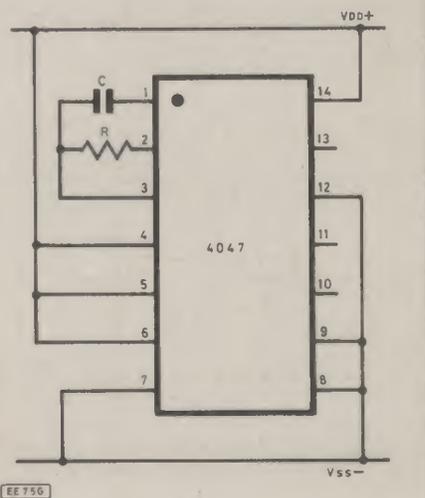


Table 3.1: 4047 FREQUENCIES

| | 0.001μF | 0.0033μF | 0.01μF | 0.033μF | 0.1μF | 0.33μF | 1μF | 3.3μF |
|-------|---------|----------|---------|---------|--------|---------|---------|----------|
| 10kΩ | 22.7kHz | 6.89kHz | 2.27kHz | 689Hz | 227Hz | 68.9Hz | 22.7Hz | 6.89Hz |
| 27kΩ | 8.42kHz | 2.55kHz | 842Hz | 255Hz | 84.2Hz | 25.5Hz | 8.42Hz | 2.55Hz |
| 68kΩ | 3.34kHz | 1.01kHz | 334Hz | 101Hz | 33.4Hz | 10.1Hz | 3.34Hz | 1.01Hz |
| 100kΩ | 2.27kHz | 689Hz | 227Hz | 68.9Hz | 22.7Hz | 6.89Hz | 2.27Hz | 0.689Hz |
| 270kΩ | 842Hz | 255Hz | 84.2Hz | 25.5Hz | 8.42Hz | 2.55Hz | 0.842Hz | 0.255Hz |
| 680kΩ | 334Hz | 101Hz | 33.4Hz | 10.1Hz | 3.34Hz | 1.01Hz | 0.334Hz | 0.101Hz |
| 1MΩ | 227Hz | 68.9Hz | 22.7Hz | 6.89Hz | 2.27Hz | 0.689Hz | 0.227Hz | 0.0689Hz |

An output at oscillator frequency is given at pin 13, and outputs at half oscillator frequency at pins 10 and 11. The output at pin 11 is always opposite in phase to that at pin 10.

The oscillator can be gated by applying control voltages to the astable and not-astable input pins. For astable gating, pin 5 is disconnected from the positive rail and has applied to it an input pulse which swings between the two supply rails, as in Fig. 3.15(a). There are no changes at the other pin connections.

Oscillation is inhibited with pin 5 low, and starts when pin 5 is taken high. When pin 5 is taken low again the oscillation continues until both pin 13 and pin 10 are low, and then stops.

For not-astable gating, pin 5 is taken to the negative rail and the input pulse is applied to pin 4, which is now disconnected from the positive rail, as shown in Fig. 3.15(b). Again, no changes are made at the pins not shown. The oscillator does not run when pin 4 is high and starts when pin 4 is taken low. When pin 4 is taken high again, the oscillation carries on until both pins 13 and 10 are low, and then stops.

WAVEFORMS AND FREQUENCY

The oscillator output at pin 13 is the upper waveform shown in Fig. 3.16. Its duty ratio depends mainly on the transfer characteristic of the internal f.e.t. immediately following pin 3, and is not a guaranteed squarewave. The total time for one cycle is shown as T_{osc}. Immediately below the oscillator waveform is the divided-by-2 waveform available at pin 10. This waveform changes state on alternate positive-going pulse edges in the oscillator waveform and is, in consequence, a true 50:50 squarewave. The total time of one cycle at pin 10 is designated in the diagram as T_Q.

When the f.e.t. following pin 3 has a transfer characteristic in the centre of its permitted spread, the cycle time is given by

$$T_Q = 4.40RC$$

where T_Q is in seconds, and R and C (the external frequency control components) are in megohms and microfarads. If the transfer characteristic goes to its extreme

in either direction (to left or right in Fig. 3.2(a)) the cycle time is given by

$$T_Q = 4.62RC$$

This time is precisely 5 per cent higher than that given with the transfer characteristic at the centre of its spread.

To calculate cycle time, the approach is to work to the 4.40RC figure (which corresponds to f.e.t.s in the centre of the transfer characteristic spread), accepting that the actual time given will have a tolerance of +5 per cent and -0 per cent.

Frequency is the reciprocal of cycle time, so that

$$f = \frac{0.227}{RC}$$

where f is in hertz. This is the frequency available at the pin 10 and pin 11 outputs; the pin 13 frequency has twice this value. To take an example, the calculated frequency given by frequency control

components of 270kΩ and 0.1μF would be equal to the reciprocal of 4.40 × 0.27 × 0.1, or 8.42Hz to three significant figures. Table 3.1 gives calculated frequencies for different values of R and C.

The recommended range of values for R is 10kΩ to 1MΩ. The value of C should be 100pF or more, with no limit on maximum value. The capacitor must be a non-electrolytic component, and the oscillator works reliably with high values. If, for instance, R in Fig. 3.14 is 1MΩ and C is 10μF, the total cycle length at the pin 10 or pin 11 output calculates as 44 seconds, and this cycle length, within the +5 per cent tolerance, is given in practice.

The current drawn by the 4047 running as an astable multivibrator is largely dependent upon the value of the frequency control resistor, and can be made much smaller than the current consump-

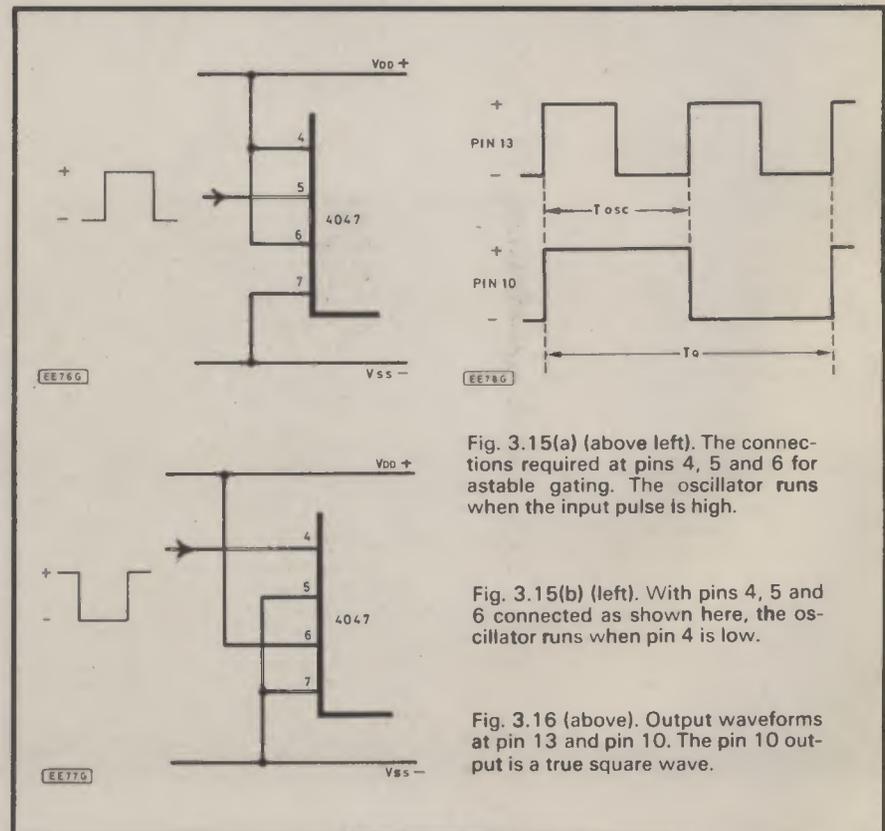


Fig. 3.15(a) (above left). The connections required at pins 4, 5 and 6 for astable gating. The oscillator runs when the input pulse is high.

Fig. 3.15(b) (left). With pins 4, 5 and 6 connected as shown here, the oscillator runs when pin 4 is low.

Fig. 3.16 (above). Output waveforms at pin 13 and pin 10. The pin 10 output is a true square wave.

tion of the 2-inverter CMOS oscillator. With R at $1M\Omega$, a typical current consumption is of the order of $20\mu A$. This increases to around $40\mu A$ when R is $100k\Omega$, and to some $700\mu A$ when R is $10k\Omega$.

All these current figures apply to a supply of 9 volts and a value in C of

$0.001\mu F$ or more. If low current consumption is important, it is obviously desirable to give R a high value. With a 9-volt supply the output current capability at any of the three output pins is in excess of 2mA for both the high and low conditions.

Like all CMOS devices, the 4047

needs to be handled carefully in order that high static voltages are not applied to any of the pins. However, extra care is needed with the 4047 at its pin 3. To permit larger input voltage swings, this pin has a modified diode protection circuit and is more sensitive to high static voltages than are the other input pins.

STORE SENTINEL

A practical project to protect valuables on display in stores or your home

A very useful practical project incorporating a 4047 and a 4011 has the circuit shown in Fig. 3.17. This is a security unit which protects items on display in a store and it employs the familiar approach of threading a guard wire through the handles or other apertures in the goods. If the guard wire is cut or interrupted an alarm sounds.

DESIGN PRINCIPLES

It is necessary for a unit of this nature to be battery driven in order that it remains operational during power cuts and other cessations in the electricity supply. In the interests of economy it then becomes desirable to design the unit so that it has a very low standing current consumption, say less than half a milliamp. Such a supply current would enable standard dry batteries to be used and these would have a very long life.

Conflicting with the low supply current requirement is the fact that, for robust working, the current flowing in the guard wire should be in the order of several milliamps so that false alarms are not

caused due to current leakage between conductors and similar factors.

CIRCUIT DESCRIPTION

These two requirements are reconciled in the circuit of Fig. 3.17 by having a 4047 produce a squarewave which is fed through the guard wire. The current consumption of the 4047 is much less than half a milliamp, but its output current capability is in excess of several milliamps. If the insulation in the guard wire system is good the 4047 supply current will be low. Should the insulation deteriorate for any reason the 4047 will still supply the squarewave, even at leakage currents up to several milliamps, and security will be maintained.

There will, however, be a corresponding increase in battery current. The overall result is that battery current consumption will normally remain low if reasonable care and maintenance is provided, and that the unit will continue to function, with increased battery current, if the guard wire insulation becomes poor.


The 4047 produces a squarewave having a frequency of about 84Hz at its pin 10, and this is fed into the guard wire. The wire consists of flexible audio screened cable which leaves the housing in which the unit is assembled, passes through the goods being protected, then returns to the housing to connect to diode D1. This diode rectifies the squarewave and causes C3 to charge.

The time constant of C3 and the parallel resistor R2 is 0.047 second, and the voltage across these two components is about 0.5 volt lower than the peak-to-peak amplitude of the squarewave. If the guard wire is cut, or if its inner and outer conductors are short-circuited, the voltage across C3 rapidly falls to zero. An output short-circuit does not damage the 4047.

LOGIC

The simple logic in the circuit is provided by the four NAND gates of a 4011, all of which are connected as inverters. The first gate, G1, couples to C3 and R2. The voltage at the gate input is nor-

Fig. 3.17. Protection circuit for displayed items in a store. The bell sounds continuously if the guard wire is momentarily opened or short-circuited.

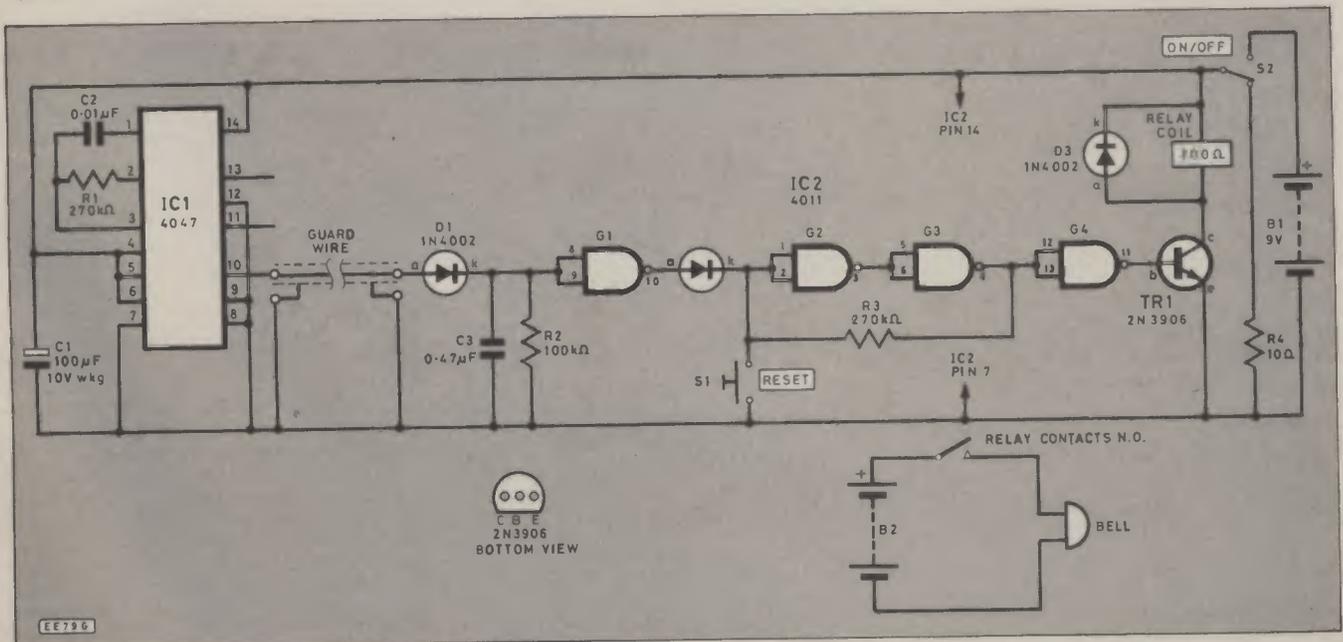

mally high and its output is low. If the guard wire is cut or short-circuited, the gate input goes low and its output goes high.

Gates G2 and G3 form a latch, with the input of G2 and the output of G3 being normally low. The latch maintains this state due to the coupling, through R3, from G3 output back to G2 input. The latch output couples to G4, whose output is normally high. This output connects to the base of the emitter follower, TR1, whereupon no current flows through the relay coil in its emitter circuit.

When the guard wire is cut or short-circuited, G1 output goes high, taking G2 input high via diode D2. The latch now takes up its alternate state with input and output both high, and remains locked in this condition even if G1 output goes low again because D2 is then reverse biased. Thus, it takes only a momentary break or short-circuit in the guard wire to change the latch to its alternate condition, which it then maintains.

When the latch output goes high, the output of gate G4 goes low and TR1 causes the relay to energise. The normally open relay contacts complete the circuit to the alarm bell (or other warning device) and this rings continually until either the unit is switched off or the Reset button is pressed. A separate battery, B2, is used

for the bell to keep bell transients away from the electronics.

The high value capacitor, C1, ensures that the initial relay energising current does not affect CMOS operation if B1 should happen to have a high internal resistance. When the on-off switch is turned off, C1 rapidly discharges through current limiting resistor R4. This discharge of C1 is necessary because the voltage across it, due to the low running current of the unit, would otherwise fall slowly, and the CMOS circuitry would remain active for a significant period after it was supposedly turned off.

SETTING-UP

At switch-on it is possible for the CMOS latch to take up the state in which its input and output are high, and the latch can then be brought to its normal state by momentarily pressing the Reset button. If desired, the button can be pressed at the same time as the unit is switched on at S2. There are other means of ensuring that the latch takes up its normal state at switch-on, but the use of a Reset button is the simplest and most reliable since it offers direct control into the circuit.

The relay can be any type having a coil resistance of about 200Ω or more and

which reliably energises at less than 9 volts. The three diodes are shown as 1N4002, but they are not critical and any other small silicon diode could be used instead.

HOUSING

Apart from the bell, the whole unit can be housed in a small plastic or metal case. The two ends of the guard wire can connect into the main circuit by way of jack plugs and sockets, phono plugs and sockets, or by any other convenient coaxial plugs and sockets. Coaxial line plugs and sockets can be inserted along the length of the guard wire to ease installation and to allow the insertion of extra lengths of screened wire in the loop.

In the quiescent condition, and assuming no leakage in the guard wire system, the total current drawn from battery B1 is approximately 100μA plus the leakage current in C1. About 60μA of this current is charging current for C3. The electrolytic leakage current in C1 can be expected to be of the order of 10μA. When the guard wire is cut or short-circuited, the main current drawn from B1 is that which flows in the coil of the relay.

Part Four of this series will discuss hysteresis oscillators.

COUNTER INTELLIGENCE

BY PAUL YOUNG

Intelligent Computers

With the modern computer trying to emulate the human brain, a question many of us ask ourselves, is it conceivable that it will ultimately surpass the human brain in matters of intelligence and reasoning?

I was reminded again of this conundrum, by the appearance of a book entitled, "The Fifth Generation," by E. A. Feigenbaum and Pamela McCorduck. Subtitled, "Artificial Intelligence and Japan's Computer Challenge to the World", the authors consider the possibility of reasoning computers. Could Arthur C. Clarke's villainous HAL one day become a reality?

It is not easy to come up with a satisfactory answer. The computer is already able to deal with mathematical problems in seconds, that would take the average mathematician weeks to solve. It can play chess up to the standard of a Grand Master. It can diagnose illness with a higher rate of success than most GPs so one can be forgiven for deciding yes, it will happen.

First we must decide on two points: Will the computer ever be able to give out more than has been put into it? Will it ever be possible to program it with heuristic knowledge?

On a more mundane level, I can think of many reasons why they won't replace us. Taking your average *Homo Sapien*, he has a wage packet (at least the lucky ones do) he

(or she) is competitive and wants to keep up with the Jones's. Can you ever imagine the Apricots being worried about not keeping up with the Apples?

Consider the Arts, a computer could compose music at the present moment, but it would only be fit for other computers to listen to. I once read that some genius had worked out that if a group of monkeys were left to scribble for a million years they would write all the Beethoven Symphonies.

By the same token a computer could write them. It seems to me that the fallacy here is, that, the group of monkeys could scribble away for a million years and still not write them.

As for painting, I'm sure any computer worth its software could produce works superior to much that appears at the Royal Academy Summer Exhibition. I don't think writing novels would present much difficulty either, but poetry—could it produce lines like:

*"Kissing with golden face, the meadows green,
Gilding pale streams with heavenly alchymy"*

describing the sun shining on streams and meadows, I very much doubt it.

One scientist stated, that if a computer were constructed with the mental power of the human brain, it would be the size of Europe! If they did achieve all this without

acquiring top heavy heads, could they one day become Members of Parliament? I don't think so, we couldn't program them to be mendacious enough.

Although I have treated the subject with a certain amount of levity, it is a serious one, and one that we shall be arguing about for many years to come.

Rusty Programme

With Cheltenham very much in the news of late, I was rather amused to read the following: It appears that the BBC Radio Station at York had asked permission to erect a medium-sized relay station at Scarborough. A short time after its completion the BBC was asked by the Home Office to reduce its power by 75 per cent.


The reason given was National Security. Apparently a listening station nearby, linked to Cheltenham, tunes into the Russian trawlers. Instead of getting the latest news on the size of the herring catches, they were receiving an up to the minute account of the traffic situation in York.

After the BBC Engineers proved that this was impossible, a very embarrassed security man from GCHQ explained why it was happening. Their listening station had never been cleaned since it was built, and consequently suffers from something known as "Dry Rust". This causes the station not only to hear a report of the number of vehicles on the road at Nether Poppleton but also local pop music as well.


I wonder if this is why I sometimes pick up television on my tape recorder? Perhaps it needs rust-proofing.

Meanwhile the BBC said they would send round engineers to clean the place up with wire brushes, no, not Paul Young's shack, but the listening station. So now we can all sleep soundly in our beds once more.

SEPTEMBER FEATURES...

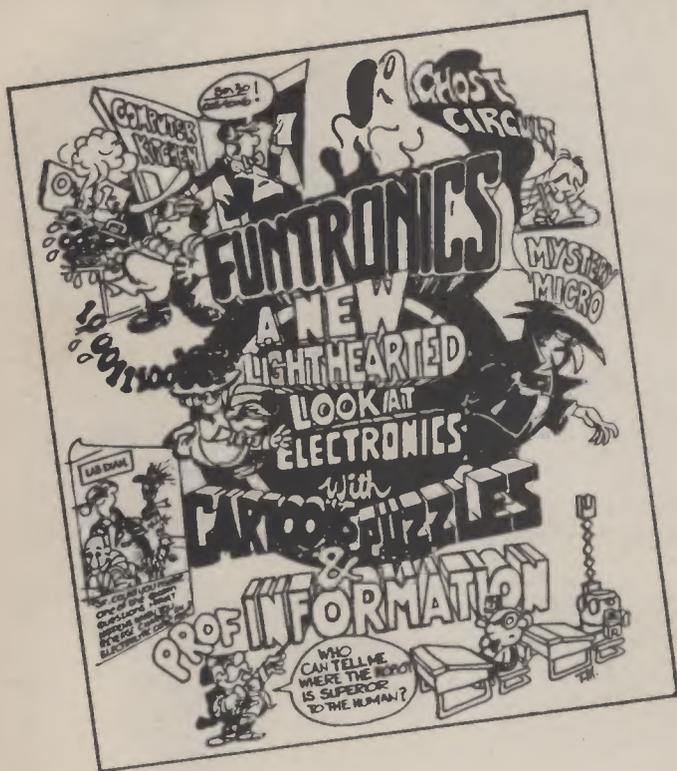

MICROCOMPUTER DIGITISER

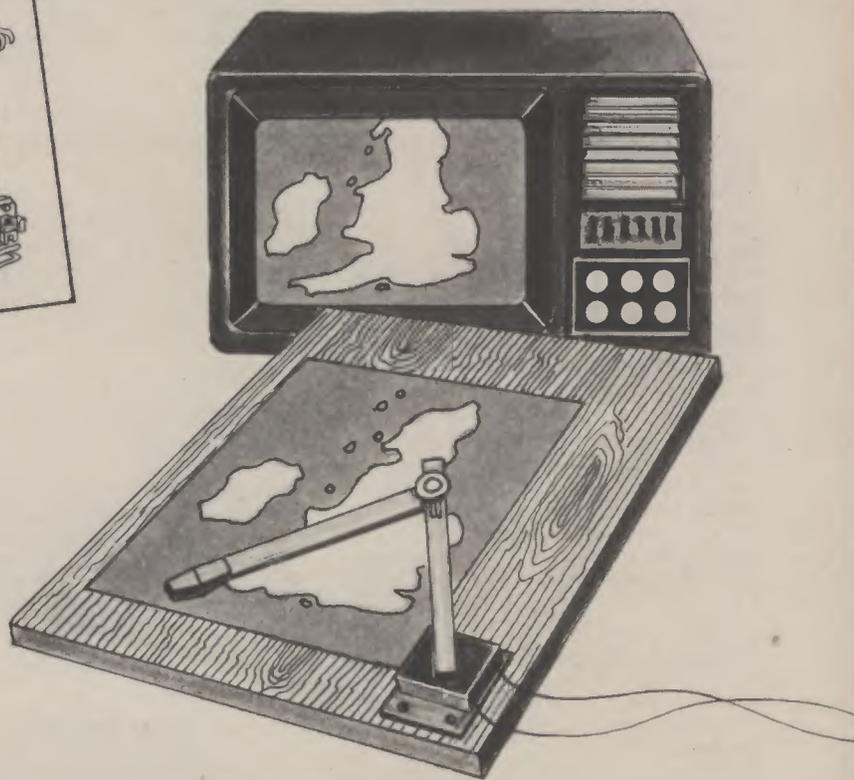

GUITAR HEADPHONE AMPLIFIER

EVERYDAY ELECTRONICS and computer PROJECTS

SEPTEMBER 1984 ISSUE ON SALE FRIDAY, AUGUST 17

WASHER FLUID MONITOR

A.R. WINSTANLEY

ONE of the latest features found on some new high-specification cars is a device which informs the driver when the windscreen washer reservoir is nearly empty, to warn you to replenish it at the earliest opportunity.

The Washer Fluid Monitor is a simple electronic circuit which will tell the motorist by means of a warning lamp that the washer bottle requires re-filling.

The device can be especially useful on long motorway journeys in dirty road conditions; under these circumstances, the screen washers can be in almost continuous use and the Monitor will warn you in good time to pull in at the next stop to re-fill the reservoir. The tell-tale lamp also warns you to economise on screen washer fluid in the meantime!

CIRCUIT DESCRIPTION

The circuit diagram is shown in Fig. 1. Firstly, TR1 and associated components form a simple transistor switch. Two sensor wires are taken from the points shown to the fluid bottle where the two probes dip into the water contained inside. The water, whilst not being a perfect conductor, forms a resistive path between the two probes and thus the base terminal of TR1 is forward biased.

TR1 is therefore permitted to conduct, so the collector terminal goes low, to roughly 0V. In turn, this biases off the base of TR2 and so TR2 is held off by TR1.

Should the water drop to a level below that of the probes, then the base current for TR1 is cut off, switching out that transistor. Base current for TR2 then flows through R4 and so TR2 can switch on. As TR2 switches on the voltage at its collector falls.

A transistor astable multivibrator, comprising TR3 and TR4, forms the collector load for TR2 and the astable is now permitted to oscillate. The astable drives a filament indicator LP1, simple bulbs being more suited, in the author's opinion, to automotive purposes than light-emitting diodes.

The warning lamp will now flash, thereby alerting the driver that the washer fluid level requires topping up.

A capacitor C1 is included to introduce a time delay into the operation of the circuit. This prevents the lamp from flashing for about four or five seconds, so that, should the water level temporarily

fall below the pre-determined point as the car corners or travels along uneven surfaces (like the M1!), the delay will inhibit the operation of the warning light for a short period.

None of the component values are critical: the circuit should function quite normally if nearest-value components from the junk box are employed instead. The same applies to the types of transistors used in the circuit.

CONSTRUCTION

VEROBOARD

All the components, with the exception of LP1, are assembled on 0.1in matrix

Veroboard of dimensions 16 strips x 29 holes, as shown in Fig. 2.

The Veroboard has been cut to fit inside a plastic Bimbox type 2002 and measuring 100 x 50 x 25mm. It is then possible to mount the board horizontally inside the box by employing four "Bimadaptors" cut to length; these slot into the p.c.b. guides moulded within the case. No mounting hardware is therefore necessary for the circuit board.

Start the assembly by cutting the Veroboard to size, and then making the two breaks in the copper tracks as shown in Fig. 2. The components should be soldered in position. As always, take the usual handling precautions with the transistors and ensure that all the polarised capacitors are inserted the right way round.


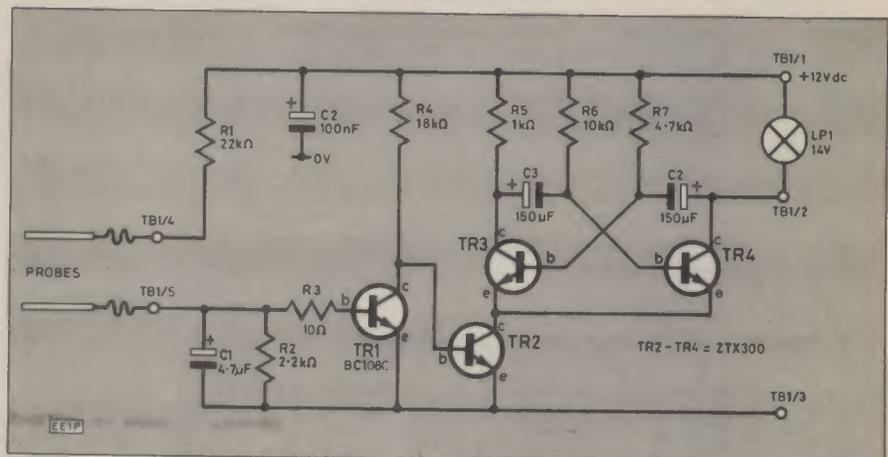


Fig. 1. Circuit diagram of Washer Fluid Monitor

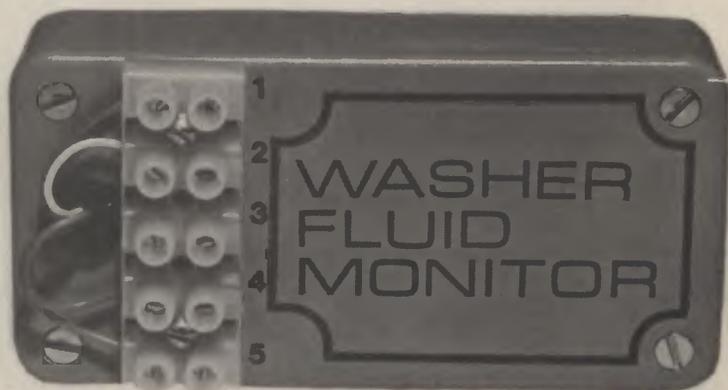

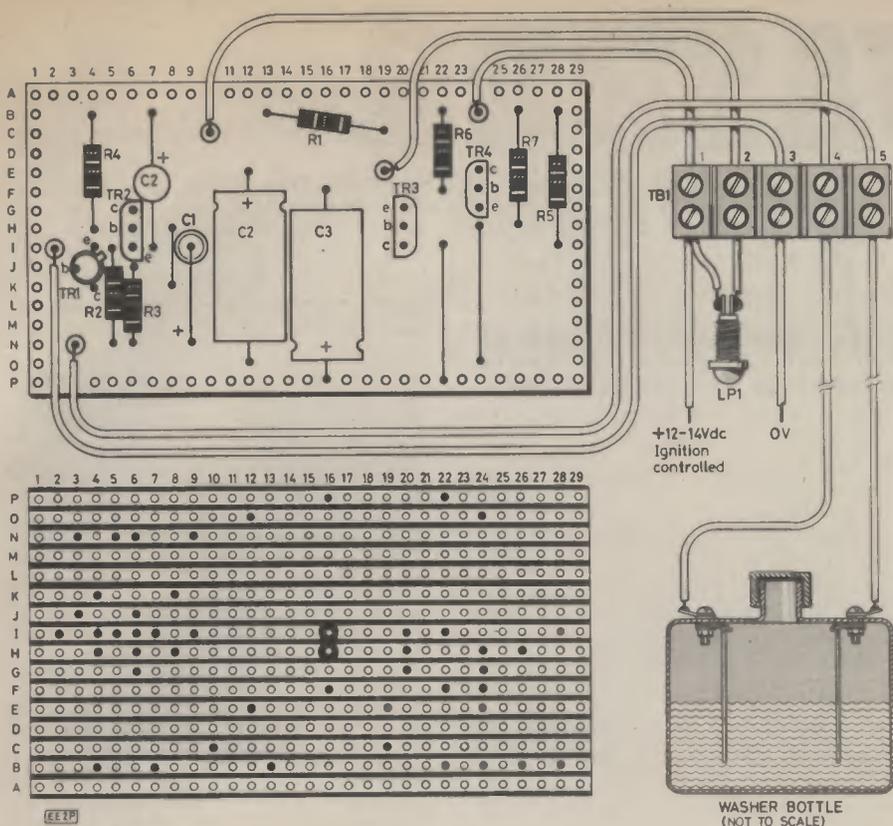


Fig. 2. Veroboard layout, wiring diagram and sensor construction.

CONNECTIONS

The connections to the Washer Fluid Monitor are made via a 5-way screw terminal block mounted on the exterior of the case. Flying leads are then passed from the terminal block and through an adjacent hole in the case to the circuit board inside. You can use Veropins where the wires join the component board.

Note that Terminal 1 shares the connections for both the 12V positive input and one leadout to the lamp. The d.c. input should be taken from an ignition-controlled circuit, for example, the radio or similar. LP1 can be mounted in any convenient position on the dashboard, but it will probably be necessary to extend the lamp's leads with hook-up wire.

The completed module is best fitted inside the passenger compartment out of harm's way. The prototype was stuck inside the centre console by using double-sided adhesive foam strip.

SENSOR CONSTRUCTION

The proposed arrangement for incorporating the fluid-level sensor has been designed to be used in conjunction with plastic bottles of the injection-moulded type: the sensor assembly will not be suitable with those "flexible bag" types found on older cars.

The recommended sensor design is also shown in Fig. 2, and this was used in the author's car with great success.

Firstly, empty out the contents of the bottle. Then drill two 2BA clearance holes in the top of the bottle on either side of the re-fill opening.

Two solid-core uninsulated wires are bolted, via a solder tag, to the inside of the bottle so that the wire forms a probe dipping into the water. It should be possible to reach inside the bottle with a finger in order to feed the bolt through the hole made in the washer bottle.

Another solder tag mounted outside on top of the bottle is used to take a connection away from the probe to the Monitor fitted inside the car.

The probe wires used in the prototype set-up were gold-plated since this kind of wire is resistant to corrosion. A suitable source of this wire is indicated in the components list. Being rather thin, the wires

COMPONENTS

Resistors

| | |
|--------------------------------------|---------------|
| R1 | 22k Ω |
| R2 | 2.2k Ω |
| R3 | 10 Ω |
| R4 | 18k Ω |
| R5 | 1k Ω |
| R6 | 10k Ω |
| R7 | 4.7k Ω |
| All $\frac{1}{4}$ W carbon $\pm 5\%$ | |

See
**Shop
Talk**
page 534

Capacitors

| | |
|------|---|
| C1 | 4.7 μ F 16V axial lead electrolytic |
| C2 | 0.1 μ F 35V tantalum bead |
| C3,4 | 150 μ F 16V axial lead electrolytic (2 off) |

Transistors

| | |
|-------|--------------------|
| TR1 | BC108C npn |
| TR2-4 | ZTX300 npn (3 off) |

Miscellaneous


plastic box, Bimbox type 2002 100 x 50 x 25mm; 0.1in matrix Veroboard, 16 strips x 29 holes; (LP1)—14V 40mA filament indicator, amber; (TB1)—5-way screw terminal block; Bimadaptors, cut to suit; gold-plated wire, cut to length (Maplin); 2BA nuts, bolts, washers, solder tags; interconnecting wire; solder.

Approx. cost
Guidance only

£6.00

should be bent double to introduce an element of rigidity into the probes. Of course, the probes need to be cut to appropriate length, say 25mm to 30mm or so, from the *bottom* of the bottle. When the water drops below the probes, then the warning lamp will flash on the dashboard.

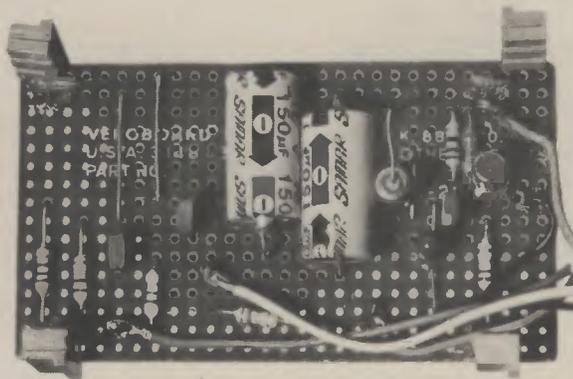With construction and installation completed, and the washer reservoir still empty, now switch on the ignition to connect the Washer Fluid Monitor to the car's electrical supply: the warning lamp on the dashboard should be flashing. Switch off and then repeat the process after having filled up the bottle with water. This time of course the lamp should remain extinguished. □



SHOP TALK



BY DAVE BARRINGTON

Catalogue

The new 450-page "Electronic Superstore" catalogue from Verospeed is their largest edition to date. It now lists over 8000 products, of which 500 are completely new.

Several areas have been expanded and these include, A/D and D/A converters, sealed lead acid batteries, computer peripherals and cleaning kits, drawing aids and a new card frame data-bussing system.

As an indication of the vast amount of information listed in the catalogue it now occupies 300 Megabytes of disc storage. Data stored includes prices and detailed product summaries, together with photos and diagrams.

Altogether, the 450-page catalogue covers a range of products from over 160 suppliers. It is Verospeed's claim that all stock items are available on a "same day despatch" basis.

Copies of the 450-page "Electronic Superstore" catalogue are available from: Verospeed, Dept EE, Stansted Road, Boyatt Wood Industrial Estate, Eastleigh, Hants SO5 4ZY.

High Powered

Following their very successful and now widely accepted 100W bi-polar power amplifier module, BK Electronics have just launched a follow-up, high specification, range of MOS-FET

Power Amplifier models under their OMP brand.

With respective power ratings of 100W, 200W and 300W r.m.s., they are ideal for the designer of instrumental, P.A., disco and hi fi equipment. They are also aimed at the expanding studio and leisure industry.

All models are built on glass-fibre printed circuit boards with aluminium chassis/heatsinks and power supplies, incorporating a toroidal mains transformer. On-board drive circuits are provided to power a compatible eleven segment I.e.d. A Vu-meter is available as an optional extra.

A brief technical specification is as follows: Frequency response: 1Hz to 100kHz; Sensitivity: For maximum output 500mV; Slew rate: 45V/ μ S; Signal-to-Noise Ratio: 125dB; Total Harmonic Distortion (THD): Full power 0.002 (typical 0.001); Power: Output: Into 4 ohms, 100W, 200W and 300W r.m.s. (dependent on model). Amplifiers with a reduced frequency range are also available.

Prices for the OMP/MF100 to MF300 range from approximately £40 to £80, including VAT. These figures do not include postage and packing.

For more details readers should contact: B.K. Electronics, Dept EE, Unit 5, Comet Way, Southend-on-Sea, Essex SS2 6TR.

Tape It

Repairing printed circuit boards and altering prototype layouts is always a tricky undertaking and sometimes it becomes a case of "ditching" the board in frustration and starting again. However, the latest offering from Copperfoil Enterprises should help to alleviate some of the above problems.

Taking the form of adhesive-backed copper tape, Copperfoil can easily be cut to length and placed in position on the "baseboard" to make-up the desired circuit.



Tested and approved at 24V 5A d.c., and conforming to BS safety regulations, Copperfoil is available in 4, 4.75, 6 and 8mm widths in 33m rolls. Inclusive prices per 33m roll are: £2.95, £3.35, £3.95 and £4.25 respectively.

For addresses of nearest stockists readers should contact: Copperfoil Enterprises, Dept EE, 141 Lyndhurst Drive, Hornchurch, Essex RM11 1JP.

CONSTRUCTIONAL PROJECTS

Microwave Alarm System

As the Microwave Alarm System can only be completed by the purchase of the special microwave module, we have been able to convince Avionic Systems that they should offer these units at a discount price. They are prepared to make a special allowance to EE readers and are offering them at below manufactured price.

The microwave alarm unit is being offered at £29 plus £3 post and packing. We understand that this is a saving of £10 on the "bought-in" price.

The unit and the warning sander can be obtained from Avionic Systems (Heathrow) Ltd., Dept EE, Viscount Way, London (Heathrow) Airport, Hounslow, Middx. TW6 2JW.


The remaining components for the "adaptor" should be available from our advertisers.

Seed Propagator

The 1-metre 28 s.w.g. Nichrome wire called for in the Seed Propagator project is available from Scientific Wire Co.

This wire is usually sold in 2oz lots and will cost £3.09, including VAT and p&p, from Scientific Wire Co., Dept EE, Forest Road, London, E17.

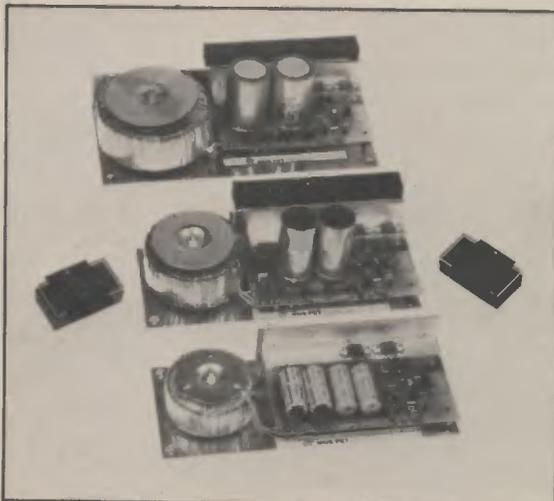We cannot envisage any component buying problems for the rest of this month's constructional projects.




Please mention
**EVERYDAY
ELECTRONICS**

when replying
to products
mentioned
on this page
and to
Classified Ads

all in your
SEPTEMBER
issue!

NEPTUNE


ROBOTS

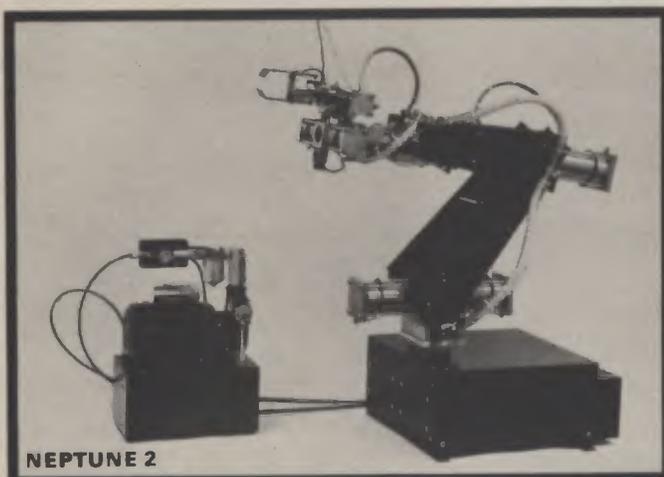

NEPTUNE 2

Of ever increasing interest and importance are robotics, and PE has been at the forefront of this subject, having featured as constructional projects the first educational servo controlled robot and the first low pressure hydraulic robot. These robots are now a common sight in the education institutions and R & D laboratories throughout this country and abroad.

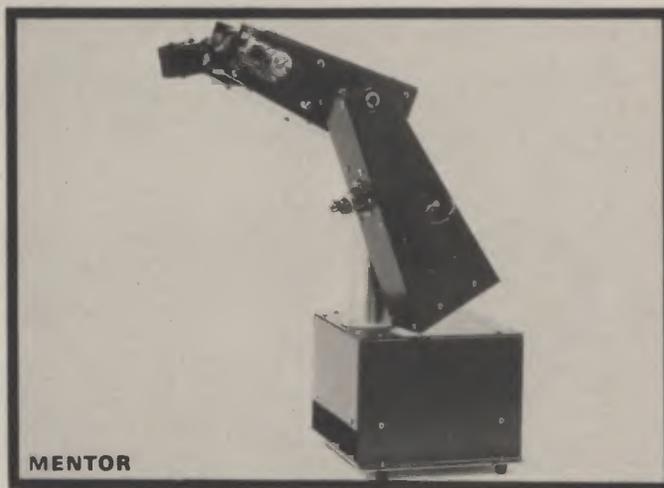Breaking new ground again we present Neptune 1 and 2, hydraulic robots of novel design powered by pure water! Also featured will be Mentor, a rugged little fixed axis electro servo controlled robot which is software compatible with the Nep-



MENTOR

tunes. A pre-publication preview of Neptune and Mentor will be given at the Education Training and Development Exhibition at the National Exhibition Centre, Birmingham, 10-12 July.

MONO/STEREO ECHO & REVERB

Based on the TDA 1097 bucket brigade device this neat solid state unit features echo delays up to 200ms and reverberation to infinity.

DISC DRIVES

This article takes the lid off disc drives and explains how to choose which drive is best for your particular needs and how to get the best from them.

PRACTICAL


ELECTRONICS

ROBOTICS · MICROS · ELECTRONICS · INTERFACING

SEPTEMBER ISSUE ON SALE FRIDAY, AUGUST 3

CIRCUIT EXCHANGE

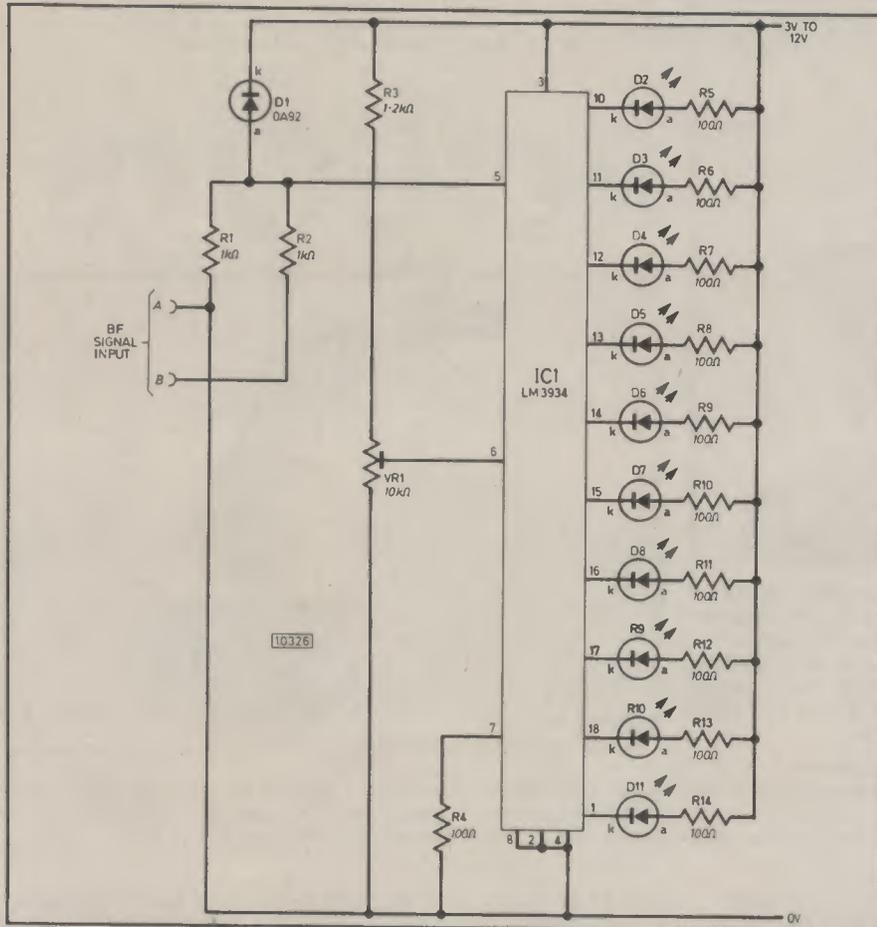This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised. Payment is made for all circuits published in this feature. Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.



LUMINOUS OUTPUT LEVEL INDICATOR

DESIGNED this luminous modulator for my stereo hi fi. It replaces the classic galvanometer type of output indicator.

The project is based on the LM3914N integrated circuit which incorporates 10 op-amps. It can sense analogue voltage levels and directly drive 10 l.e.d.s to provide a linear 10-step display. It has its own adjustable reference source that controls the internal 10-step divider chain.

The audio signal is applied to the inverting terminal (-) of each op-amp (pin 5) via resistors R1 and R2 (points A and B). These op-amps are utilised as comparators, that means when the voltage level of the audio signal applied to the inverting terminal is greater than the reference voltage level applied to the non-inverting (+) terminal (pin 6), the l.e.d. will glow. The reference level is adjusted by potentiometer VR1.

The OA92 diode (D1) mounted between pin 5 and the positive line rectifies the waveform of the audio signal, which eliminates the positive component of the BF signal.


The required power supply is between 3V to 12V. The audio signal is taken from the speaker. For a stereo system, I coupled two circuits together.

Anis Hably,
Beirut,
Lebanon.

EMPTY WINDSCREEN WASHER INDICATOR

THIS circuit provides early warning of an empty windscreen washer bottle. A varying amplitude voltage is applied across two stainless steel electrodes suspended inside the bottle. The varying voltage is used to help prevent coating of the rods. When there is no water present to short out the rods, diode D1 conducts, thus switching TR1 on. Pin 4 of IC2 goes high causing the l.e.d. D2 to flash. If the rods are shorted out again the charge in C4 results in D2 flashing for a further 15 to 20 seconds. This is necessary as the level of water around the rods will not be constant while the car is running.

R. Ormston,
Southampton,
Hants.

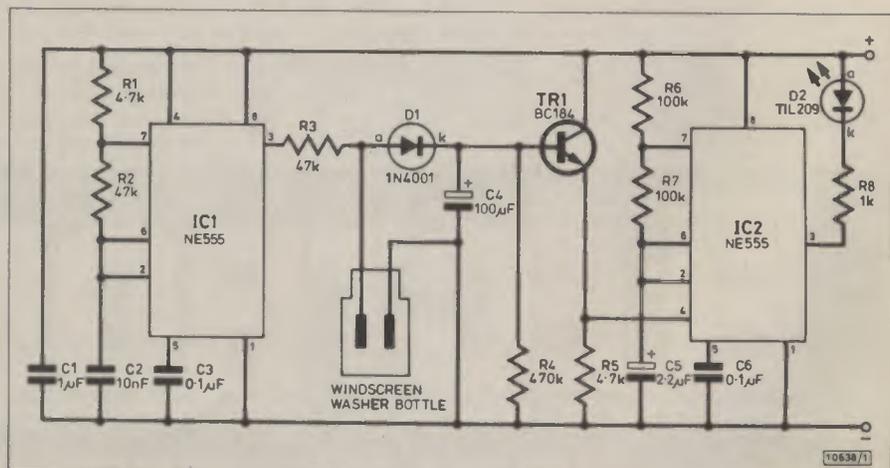

CIRCUIT EXCHANGE


NAUGHTS AND CROSSES

THIS is a simple electronic naughts and crosses game, ideal for passing the time when travelling. The l.e.d.s are arranged in the normal matrix layout, and are operated by a d.i.l. switch arrangement. All the l.e.d.s are Bi-coloured and are supplied via a low voltage current source TR1.


It should be quite easy to construct an attractive little project using this idea. All the components can be mounted on either a strip-board or a p.c.b. which should be mounted inside a suitable box. The l.e.d.s can be brought out to the top of the box and arranged in the standard naughts and crosses, three by three matrix.

Despite being a very simple project, it will provide hours of fun, and can be built by anyone, as all the components are readily available and are quite cheap.

G. McIntock Esq.,
Bishopbriggs,
Glasgow.

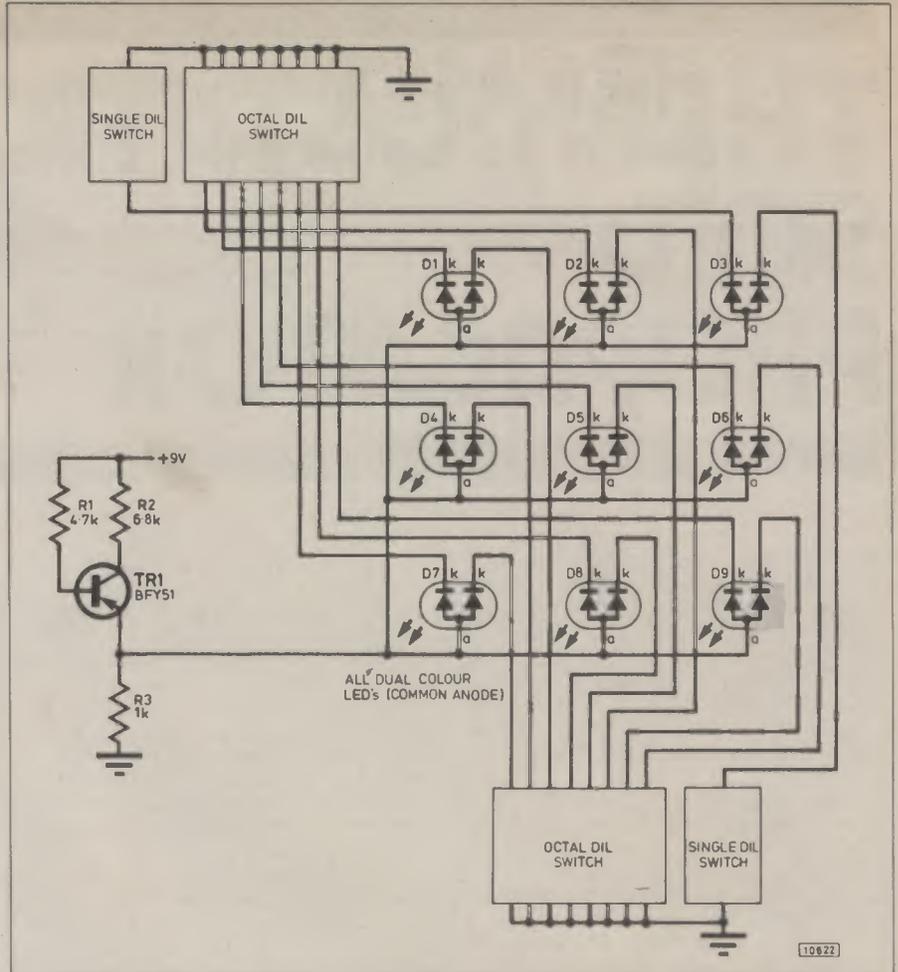

INTELLIGENT TTL LOGIC PROBE

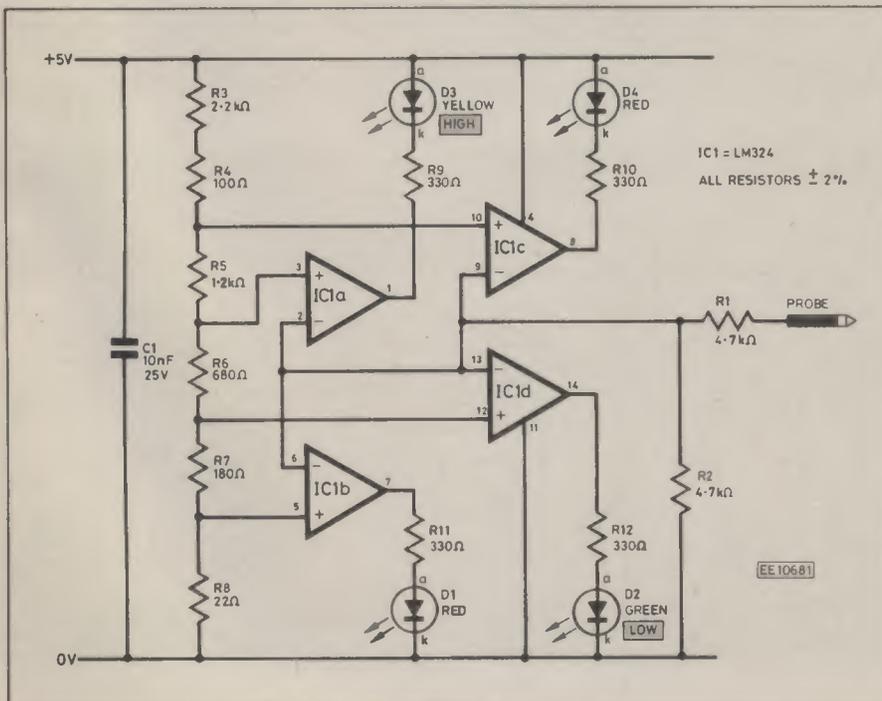

THE Intelligent Logic Probe, unlike any other probe I know of, can distinguish between a logic 0 and ground, or between logic 1 and Vcc. This is achieved by comparing various reference voltages with the probe voltage.

The power for the circuit is derived from the circuit under test, and the measurement is displayed on four l.e.d.s; green represents logic 0, yellow logic 1 and no l.e.d.s indicates undefined. A green and red indicates short to ground and a yellow and red, short to Vcc.


Resistors R1 and R2 act as a potential divider giving a reference of half the probe voltage. Other reference voltages are obtained from the divider chain R3 to R8. To make various comparisons on these references a quad op-amp (LM324) with no feedback is used. Depending on the probe voltage the output of these comparators will be close to Vcc or ground. The outputs are used to drive l.e.d.s via current limiting resistors. This circuit has been tested at a frequency of 15kHz with a square-wave input. However, if a quad comparator such as the LM339 is used then it will probably work at much higher frequencies.

It should be noted that the input impedance of this probe is quite low, and may cause problems if used in circuits with large "fan outs".

D. Kirby,
Walthamstow,
London.

THERMOSTATIC SEED PROPAGATOR

John Lewis

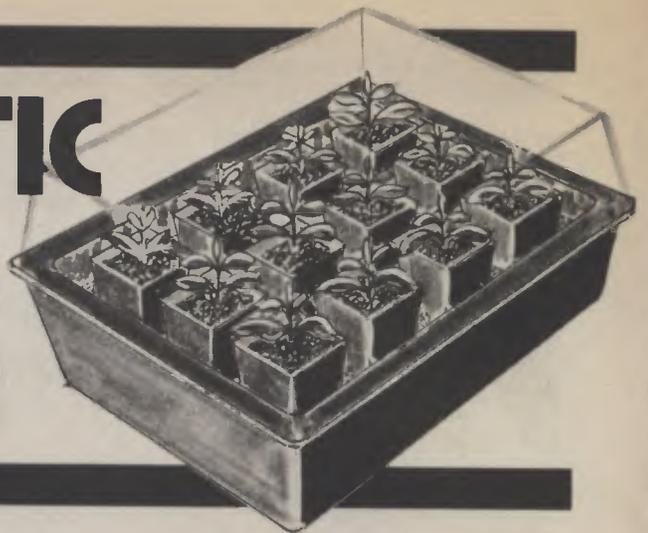

IN SPRING, it is an advantage for the keen gardener to be able to sow seeds in warm, controlled conditions. An electrically heated seed propagator is ideal for this purpose as it avoids the considerable expense of heating the entire greenhouse to a high temperature. It may also be used near a south facing house window where the maximum light may be obtained.

Seed propagators available from garden centres may not be thermostatically controlled and can be quite expensive if this feature is included.

The inexpensive seed propagator described in this article has very good temperature control and provides adequate heating for use in normal conditions.

GENERAL DESCRIPTION

The propagator consists of a modified standard size seed tray which has heating wires covered with sand in its base. A small thermistor senses the sand temperature and an electronic unit controls the 12-volt supply current to the heating element. This element is made from Nichrome wire which is protected by high temperature glass-fibre sleeving.

Square plastic or peat pots are ideal for seed sowing and a number of these can be fitted inside the seed tray, resting on the heated sand. Peat can be packed around the pots to provide extra insulation and a clear plastic cover can be used over the seed tray to help maintain warmth while still allowing light to enter. Sufficient light is important if the plants are to grow well.

The required sand temperature may be set with a variable resistor and an l.e.d. shows when the heating current is switched on. The optimum germination temperature for most seeds is between 18°C and 21°C (65°F and 70°F) and this can be easily achieved with this unit provided that the surrounding temperature is not too low. The unit should be calibrated before use with a thermometer inserted into the sand near the thermistor, a scale can then be drawn under the variable resistor pointer.

CIRCUIT DESCRIPTION

The circuit diagram of the Seed Propagator is shown in Fig. 1.

IC1 is a 741 operational amplifier used to compare two voltages. The non-inverting input on pin 3 of the op-amp is held at a reference voltage of about half the supply voltage by the resistors R1 and R2. VR1 is variable and together with thermistor RTH1 and R3 sets the voltage on the inverting input of the op-amp which is pin 2.


If the voltage on pin 2 is greater than the voltage on pin 3, then the op-amp output on pin 6 is at 0 volts and the transistor TR1 is on. The collector of TR1 is then at 12 volts, the l.e.d. is lit and transistor TR2 is also on so current will flow through the heating element.

As RTH1 warms up, its resistance

decreases and the voltage on pin 2 will decrease until it is just less than the voltage on pin 3. The op-amp then greatly amplifies this small voltage difference and pin 6 changes rapidly to about 11 volts. TR1 switches off, extinguishes the l.e.d. and switches off TR2. The current through the heating element is therefore rapidly switched off. As the thermistor cools, the operation is reversed. R5 provides a feedback loop which gives about 1°C between the switch-on and switch-off temperatures. This reduces the sensitivity of the circuit to a suitable level and prevents an excessive number of switching operations.

C1 smooths the 12-volt power supply which should be capable of providing about 2 amps. It need not be a regulated supply as the circuit is relatively immune to power supply voltage changes.

Fig. 1. Circuit diagram of the Seed Propagator.

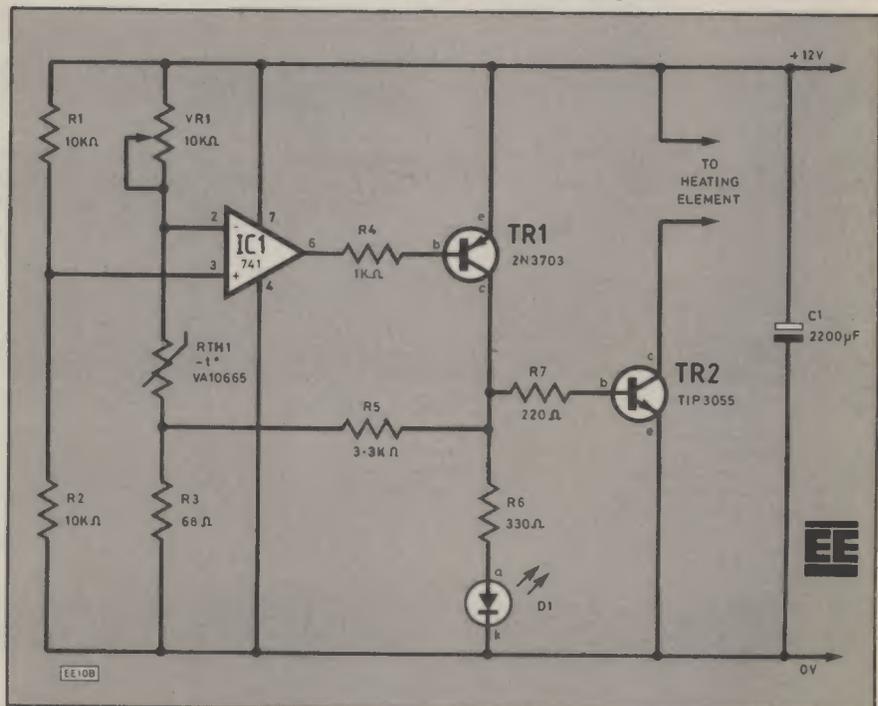

Remember that a mains supply in a greenhouse should be connected through an earth leakage circuit breaker, now referred to as a residual current circuit breaker, this provides a very great deal of protection from electric shocks.

CONSTRUCTION

STRIPBOARD

The circuit is built on 0.1 inch matrix stripboard which is 24 holes wide by 18 strips (Fig. 2 and Fig. 3). The 741 op-amp should be mounted in an 8-way socket which will prevent damage due to overheating when soldering. Care must also be taken when soldering the 2N3703 transistor on the circuit board. The i.c. and the transistor must be correctly inserted into the board as incorrect insertion will cause damage.

A diecast aluminium box about 110 x 60 x 60mm is ideal for containing the circuit board. The variable resistor should be mounted on the box together with the l.e.d. The l.e.d. must be correctly connected, usually the flat side is the negative connection. Note that these devices must never be connected directly across a power supply without a series resistor, this is R6 on the circuit board.

The TIP3055 transistor should be bolted to the inside of the box using an insulated mica washer and a small amount of heatsink compound. The box provides enough heat dissipation and no other heatsink is required unless a plastic or other insulating box is used.

External connections are most conveniently made to a terminal block mounted on the outside of the box (Fig. 4).

HEATING ELEMENT AND SEED TRAY MODIFICATION

The heating element is made from one metre of 28 s.w.g. Nichrome wire which has a resistance of 9.7 ohms. This gives a power of 14.5 watts from a 12-volt supply. Notice that no attempt should be made to run the heating element directly from the mains. The length specified gives

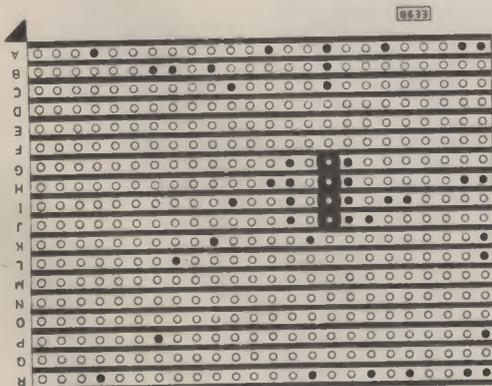


Fig. 2. Stripboard track cutting details.

COMPONENTS

See
**Shop
Talk**

page 534

Resistors

- R1,2 10kΩ (2 off)
 - R3 68Ω
 - R4 1kΩ
 - R5 3.3kΩ
 - R6 330Ω
 - R7 220Ω
 - VR1 10kΩ linear variable
 - RTH1 VA1066S thermistor
- All resistors are 1/4W (±10% tolerance)

Capacitors

- C1 2200μF 25V axial electrolytic

Semiconductors

- D1 light emitting diode (any colour) 0.2in diameter
- TR1 2N3703 *npn* silicon transistor
- TR2 TIP3055 *npn* silicon transistor
- IC1 741 8-pin d.i.l. operational amplifier

Miscellaneous

Stripboard (0.1in matrix), 24 holes wide x 18 strips; 8-pin d.i.l. socket; l.e.d. clip; 1 metre 28 s.w.g. Nichrome wire; 2 metres 2mm glass-fibre sleeving; heatsink compound, mica washer; diecast aluminium box, 110 x 60 x 60mm; 6-way terminal block; connecting wire, assorted nuts and bolts; knob for variable resistor.
*Residual current circuit breaker.
*See text.

Approx. cost **£10.50**
Guidance only

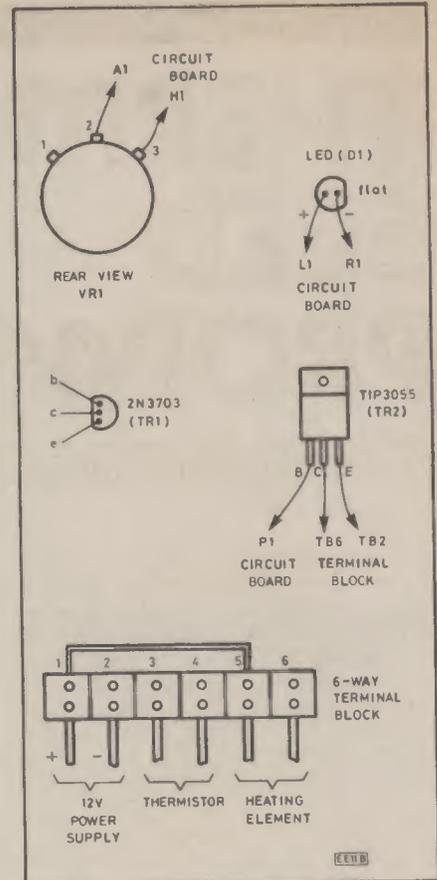


Fig. 4. Wiring details.

a power which is comparable with commercial units of similar size.

To protect the heating wire from corrosion and mechanical damage it must be inside a suitable length of glass-fibre sleeving. Heatsink compound should be smeared over the wire as it is inserted into the sleeving and a liberal amount rubbed over the outside of the sleeving will help to keep moisture out.

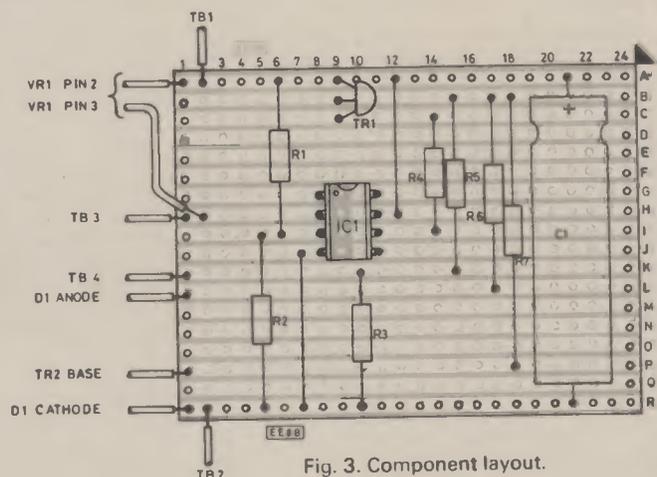


Fig. 3. Component layout.

The seed tray should be a standard full-size tray (350 x 210 x 80mm) made from strong plastic, the drainage holes in its base should be covered with waterproof tape. The heating element should be arranged in a zig-zag pattern on top of a 10mm layer of sand in the base of the tray (Fig. 5). Screw terminals on the side of the tray secure the ends of the heating element, holes for these screw terminals are most easily made with a hot soldering iron rather than with a drill. More sand is then put into the tray to cover the heating element to a depth of about 20mm.

The thermistor is quite delicate and must be protected by being sealed into a plastic pen-top or something similar using epoxy resin or silicone rubber bath sealant. Its leads should also be protected by glass-fibre sleeving, screw terminals on the side of the tray should be provided for connecting these leads.

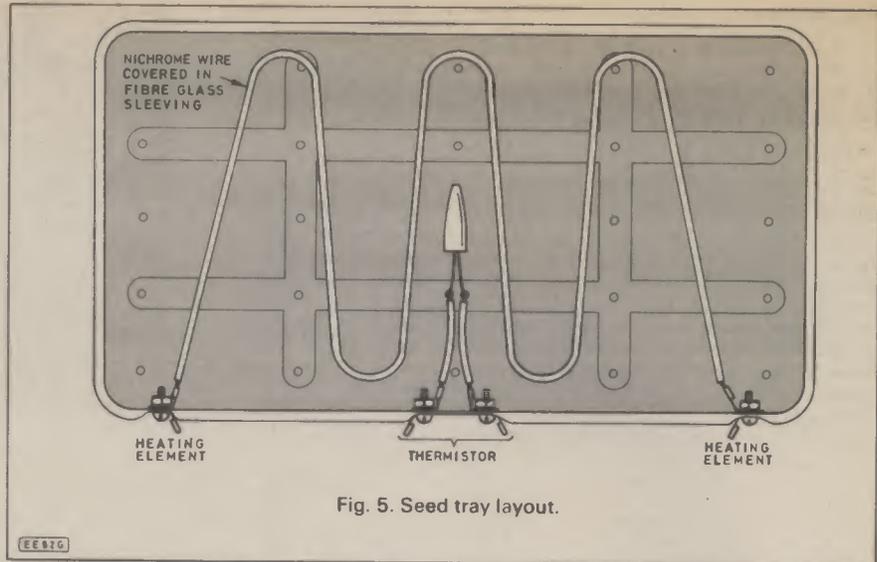


Fig. 5. Seed tray layout.


CIRCUIT EXCHANGE

HEATED rear screens consume large amounts of energy and if left on too long can deplete the battery power reserve, so much so that the task of cold starting can become impossible.

This simple circuit solves this problem by timing out five minutes after activation of the dashboard switch. This time delay allows sufficient time for the heater to do its job efficiently, and if the heater is needed again during the journey, a simple "off-on" movement of the switch will give another five minutes heating.

The circuit is cheap and easy to build and can easily be installed to most cars. Only three connections to the heater relay are required. An l.e.d. is included to indicate that the heater is on, and the heater can be switched off at any time as normal.

AUTOMOTIVE QUICKIE CIRCUIT

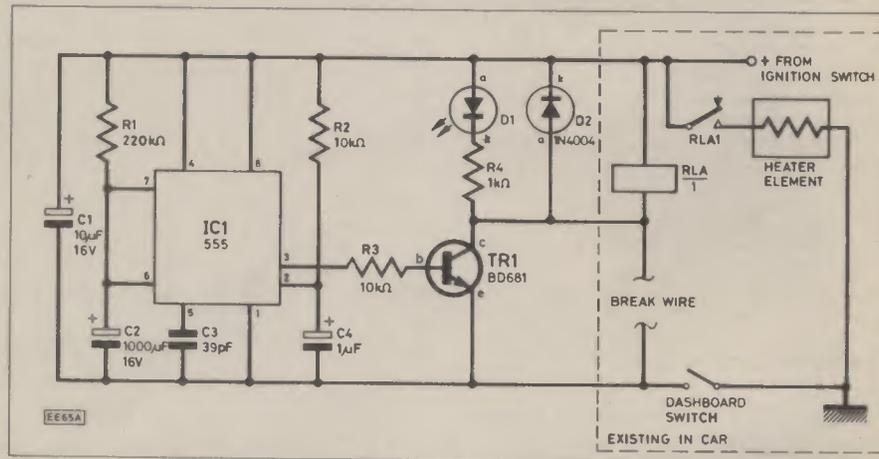

dicating that the heater is on, and the heater can be switched off at any time as normal.


G. R. Cornell,
Chelmsford,
Essex.

TELEPHONE PEN REMINDER

Two RC oscillators form the basis of this telephone pen reminder circuit. After removal of a modified pen from its holder, an alarm will sound after a preset time to remind the user to replace the pen. Only after the pen is replaced will the alarm cease to operate, thus avoiding those times when a pen cannot be found.

The first oscillator, IC1d and e, is tuned by VR1 until WD1 resonates at a frequency of approximately 4.5kHz. The second oscillator, IC1b and c, produces this tone at approximately 0.3Hz, and the inverter IC1a together with R1 and C1 provide a delay when the circuit is activated.

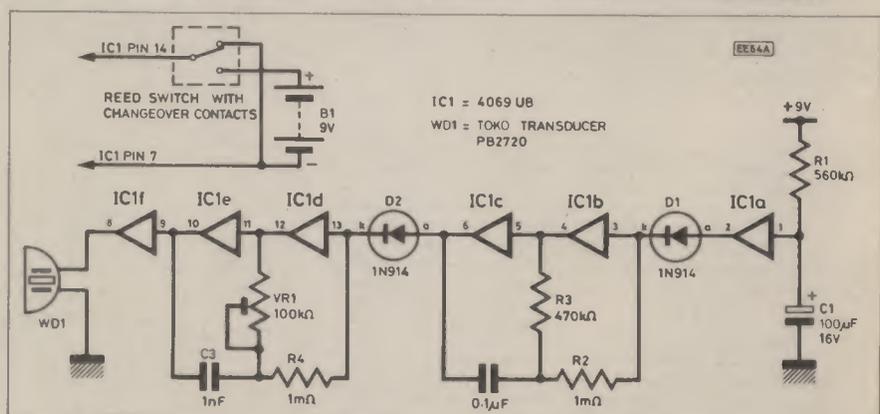A small magnet is glued to a cheap pen, making sure that it will operate the



change-over contacts on the reed switch. In normal use the pen is placed in its holder so as to operate the reed switch and thus discharge C1. When the pen is removed the contact will close and the circuit will energise when C1 charges to a

high logic level. The time delay is set by R1 and with the values shown, will give a delay of approximately 60 seconds.

S. Digby,
Gately,
Stockport.

EVERYDAY ELECTRONICS PRINTED CIRCUIT BOARD SERVICE


Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers ordering both p.c.b.s and software cassettes may send a single cheque/PO for the combined amounts listed.

Readers are advised to check with prices appearing in the current issue before ordering.

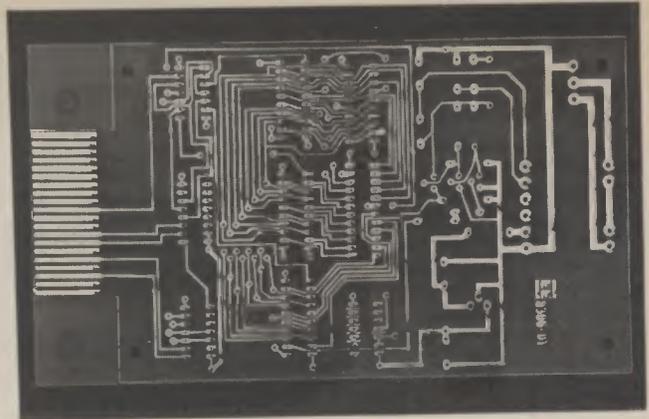NOTE: Please allow 28 days for delivery. We can only supply boards listed here.



| PROJECT TITLE | Order Code | Cost |
|---|------------|-------|
| — JUNE '83 — | | |
| Eprom Programmer, TRS-80 | 8306-01 | £9.31 |
| Eprom Programmer, Genie | 8306-02 | £9.31 |
| Eprom Programmer, TRS-80 & Genie | 8306-03 | £1.98 |
| — JULY '83 — | | |
| User Port Input/Output <i>M.I.T. Part 1</i> | 8307-01 | £4.82 |
| User Port Control <i>M.I.T. Part 1</i> | 8307-02 | £5.17 |
| — AUGUST '83 — | | |
| Storage Scope Interface, BBC Micro | 8308-01 | £3.20 |
| Car Intruder Alarm | 8308-02 | £5.15 |
| High Power Interface <i>M.I.T. Part 2</i> | 8308-03 | £5.08 |
| Pedestrian Crossing Simulation <i>M.I.T. Part 2</i> | 8308-04 | £3.56 |
| Electronic Die | 8308-05 | £4.56 |
| — SEPTEMBER '83 — | | |
| High Speed A-to-D Converter <i>M.I.T. Part 3</i> | 8309-01 | £4.53 |
| Signal Conditioning Amplifier <i>M.I.T. Part 3</i> | 8309-02 | £4.48 |
| Stylus Organ | 8309-03 | £6.84 |
| Distress Beacon | *8309-04 | £5.36 |
| Distress Beacon Pocket Version | 8309-05 | £3.98 |
| — OCTOBER '83 — | | |
| D-to-A Converter <i>M.I.T. Part 4</i> | 8310-01 | £5.77 |
| High Power DAC Driver <i>M.I.T. Part 4</i> | 8310-02 | £5.13 |
| Electronic Pendulum | 8310-03 | £5.43 |
| — NOVEMBER '83 — | | |
| TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i> | 8311-01 | £5.46 |
| Stepper Motor Manual Controller <i>M.I.T. Part 5</i> | 8311-02 | £5.70 |
| Digital Gauss Meter | 8311-03 | £4.45 |
| Speech Synthesiser for BBC Micro | 8311-04 | £3.93 |
| Car On/Off Touch Switch | 8311-05 | £3.11 |
| — DECEMBER '83 — | | |
| 4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i> | 8312-01 | £5.72 |
| 4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i> | 8312-02 | £5.29 |
| TRS-80 Twin Cassette Interface | 8312-03/09 | £7.43 |
| Environmental Data Recorder | 8312-04 | £7.24 |
| Touch Operated Die (Dot matrix) | 8312-05/06 | £4.34 |
| Touch Operated Die (7-segment) | 8312-05/07 | £4.34 |
| Continuity Tester | 8312-08 | £3.41 |

| PROJECT TITLE | Order Code | Cost |
|---|------------|-------|
| — JANUARY '84 — | | |
| Central Heating Pump Delay | 8401-01 | £3.33 |
| Biological Amplifier <i>M.I.T. Part 7</i> | 8401-02 | £6.27 |
| Temp. Measure & Control for ZX Compr | 8401-03 | £2.35 |
| Analogue Thermometer Unit | 8401-04 | £2.56 |
| Analogue-to-Digital Unit | 8401-06/07 | £9.60 |
| Games Scoreboard | | |
| — FEBRUARY '84 — | | |
| Eprom Programmer/ROM Card for ZX81 | **8402-01 | £7.84 |
| Oric Port Board <i>M.I.T. Part 8</i> | 8402-02 | £9.56 |
| Negative Ion Generator | **8402-03 | £8.95 |
| Temp. Measure & Control for ZX Compr | | |
| Relay Driver | 8402-04 | £3.52 |
| — MARCH '84 — | | |
| Latched Output Port <i>M.I.T. Part 9</i> | 8403-01 | £5.30 |
| Buffered Input Port <i>M.I.T. Part 9</i> | 8403-02 | £4.80 |
| VIC-20 Extension Port Connector <i>M.I.T. Part 9</i> | 8403-03 | £4.42 |
| Commodore 64 Extension Port Connector <i>M.I.T. Part 9</i> | 8403-04 | £4.71 |
| Digital Multimeter Add-On for BBC Micro | 8403-05 | £4.63 |
| — APRIL '84 — | | |
| Multipurpose Interface for Computers | 8404-01 | £5.72 |
| Data Acquisition "Input" <i>M.I.T. Part 10</i> | 8404-02 | £5.20 |
| Data Acquisition "Output" <i>M.I.T. Part 10</i> | 8404-03 | £5.20 |
| Data Acquisition "PSU" <i>M.I.T. Part 10</i> | 8404-04 | £3.09 |
| Timer Module | 8404-05 | £3.58 |
| A.F. Sweep Generator | 8404-06 | £3.55 |
| Quasi Stereo Adaptor | 8404-07 | £3.56 |
| — MAY '84 — | | |
| Simple Loop Burglar Alarm | 8405-01 | £3.07 |
| Computer Controlled Buggy <i>M.I.T. Part 11</i> | | |
| Interface/Motor Drive | 8405-02 | £5.17 |
| Collision Sensing | 8405-03 | £3.20 |
| Power Supply | 8405-04 | £4.93 |
| — JUNE '84 — | | |
| Infra-Red Alarm System | 8406-01 | £2.55 |
| Spectrum Bench PSU | 8406-02 | £3.99 |
| Speech Synthesiser <i>M.I.T. Part 12</i> | 8406-03 | £4.85 |
| Train Wait | 8406-04 | £3.42 |
| — JULY '84 — | | |
| Ultrasonic Alarm System | 8407-01 | £4.72 |
| Atom EPROM Simulator | 8407-02 | £3.08 |
| Electronic Code Lock | | |
| Main board | 8407-03 | £2.70 |
| Keyboard | 8407-04 | £3.24 |
| — AUGUST '84 — | | |
| Microwave Alarm System | 8408-01 | £4.36 |
| Temperature Interface-BBC Micro | 8408-02 | £2.24 |

*Set of four boards.

**Calibrated with C1, VR1 and IC3 fitted.

M.I.T.—Microcomputer Interfacing Techniques, 12-Part Series.

EVERYDAY ELECTRONICS AT YOUR

and computer PROJECTS

Reach effectively and economically to-days enthusiasts anxious to know of your through our semi-display and classified pages. Semi-display spaces may be booked at timetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word number 60p extra. All cheques, postal orders, etc., to be made payable to Everyday Electronics crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisement, should be sent to the Classified Advertisement Department, Everyday Electronics and 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone

When replying to Classified Advertisements, please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Security

WHO CAN PUT A PRICE ON PEACE OF MIND
 PROFESSIONAL EQUIPMENT AT LOW/LOWI PRICES.
HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES
 ADVANCED SECURITY PRODUCTS LTD
 2 Ealing Road, Aintree,
 Liverpool L9 0HU, Merseyside.
 Tel: 051-525 3440
 FREE CATALOGUE
 PHONE OR S.A.E.

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
 - HIGHEST QUALITY EQUIPMENT
 - FREE DIY DESIGN GUIDE
 - FULLY ILLUSTRATED
 - MICROCHIP CIRCUITRY
 - QUICK DESPATCH SERVICE
 - FULL INSTRUCTIONS
- SEND SAE OR PHONE

C-TEC SECURITY, Dept EE,
 60 Market St, Wigan WN1 1HX.
 Telephone (0942) 42444



Miscellaneous

FREE! Parcel of components worth £10. Send only 80p postage! D. HORSLEY, 113 Clare Road, Braintree, Essex.

P.C.B. PLANT (Instagraphics) unused £100. Develop, wash etch tanks. Capacity 10" x 8". Temp. control, agitator. BAYFORD (Herts) 397 evenings.

EPROM PROGRAMMER SERVICE from master or hex listings. Low rates, most types. Ring 0438 720671 evenings.

PCB'S MADE to own personal requirements, drilled or undrilled. Send for details. Reasonable rates. B. M. ANSBRO, c/o 38 Poyning Drive, Hove, Sussex.

Receivers & Components

4 PLASTIC BOXES £2

1. Thick black, four screw top, size 90mm by 70mm, deep 26mm.
 2. Thick black four screw top, size 150mm by 84mm, deep 43mm.
 3. Thin white flick on top, size 81mm by 64mm, deep 26mm.
 4. Thin semi-clear white top, size 81mm by 64mm, deep 64mm.
- ONE OF EACH TYPE (sample) £2.00 plus P&P 30p.
 ELECTRONIC MAILORDER,
 62 Bridge Street, Ramsbottom, Lancs, BL0 9AG.
 Tel: (070 682) 3036. - ACCESS/VISA

CAPACITORS, DIL Sockets, Heat-Sinks, LEDs, Regulators, Transistors and Resistors. Send for VAT inclusive price list. HUNT ELECTRONICS, PO Box 57, Derby, DE6 6SN.

TURN YOUR SURPLUS capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

AMERICAN POLICE SIREN KIT. Whooping output (5W/8Ω). Includes case. (£4.25 + 35p P&P). Weatherproof speaker (+ 5.70p) if required. MARTEX ELECTRONICS, 51 Kempton Grove, Fiddlers Green, Cheltenham, Glos. GL51 0JX.

Service Sheets

INVENTORS

Think of something new?
 Write it down!

American industry offers potential royalties for you innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

American Inventors Corporation
 82 Broad Street, Dept. EV,
 Westfield, Massachusetts 01086,
 United States of America

A fee based marketing company

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for Insertions. I enclose Cheque/P.O. for £
 (Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |
| | | | |

NAME
 ADDRESS

.....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

EVERYDAY ELECTRONICS

Classified Advertisement Dept.,
 Room 2612, King's Reach Tower,
 Stamford Street, London SE1 9LS
 Telephone 01-261 5942

Rate:
 33p per word, minimum 12 words
 Box No. 60p extra.

R SERVICE

products and services £7.80 per single column cent (minimum 12 words), box and Computer Projects and ments, together with remit-Computer Projects, Room 01-261 5942).

Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1.50 plus S.A.E. Service Manuals on Colour TV and Video Recorders, prices on request. S.A.E. with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

FULL SIZE SERVICE SHEETS £2 + 1sae; CTV/MusC £3 + 1sae. Repair/circs almost any named TV/VCR £9.50. 1sae free quotations for manuals, sheets - free mag inc. service sheet. T.I.S.E.E. 76 Church Street, Larkhall, Lanarks - Phone 0698 883334.

Courses

CONQUER THE CHIP—master modern electronics the practical way by seeing and doing in your own home. Write for your free colour brochure now to BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, Dept C3, Reading, Berks RG1 1BR.

NO!

If you see an advertisement in the press, in print, on posters or a cinema commercial which makes you angry, write to us at the address below. (TV and radio commercials are dealt with by the I.B.A.)

The Advertising Standards Authority.

ASA Ltd., Brook House, Torrington Place, London WC1E 7HN.



★ BAKER ★

GROUP P.A. DISCO AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp Illustrated £80
 150 watt Output, Slave 500 mv. Input 3 Speaker Outputs £80
 150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs £125
 150 watt P.A. Vocal, 8 inputs High/Low Mixer Echo Socket £129
 100 watt Valve Model, 4 inputs, 5 Outputs Heavy duty £125
 60 watt Valve Model, 4 inputs Low imp and 100v line output £69
 60 watt Mobile 240v AC and 12v DC 4-8-16 ohm - 100v line £89

BAKER LOUDSPEAKERS Post £2 each

| Type | Model | Size | Watts | Ohms | Price |
|------------------|------------|------|-------|--------|--------|
| P.A./Disco/Group | DG50/10 | 10 | 50 | 8/16 | £18.00 |
| Midrange | Mid 100/10 | 10 | 100 | 8 | £25.00 |
| Hi-Fi | Major | 12in | 30 | 4/8/16 | £16.00 |
| Hi-Fi | Superb | 12in | 30 | 8/16 | £26.00 |
| P.A./Disco/Group | DG45 | 12in | 45 | 4/8/16 | £16.00 |
| Hi-Fi | Wooler | 12in | 80 | 8 | £25.00 |
| Hi-Fi | Auditorium | 15in | 60 | 8/16 | £37.00 |
| P.A./Disco/Group | DG75 | 12in | 75 | 4/8/16 | £20.00 |
| P.A./Disco/Group | DG100 | 12in | 100 | 8/16 | £26.00 |
| P.A./Disco/Group | DG100/15 | 15in | 100 | 8/16 | £35.00 |

DISCO CONSOLE Twin Decks, mixer pre amp £105, Carr £6.
COMPLETE DISCO 150 watt £330; 300 watt £390, Carr £30.

DISCO MIXER 240V, 4 stereo channels, 2 magnetic, 2 ceramic/ tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, panel or desk mounting, grained aluminium facia. Tape output facility. £49. Post £1.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. £112 PP £2.
 Headphone Monitor, Mike Talkover Switch. ditto 7 Band Graphic £128.

P.A. CABINETS (empty) Single 12 £30; Double 12 £36, carr £10.
WITH SPEAKERS 60W £27; 75W £52; 90W £71; 150W £80.
HORNBOXES 200 Watt £30, 300 Watt £35. Post £4.

WATERPROOF HORNS 8 ohms 25 watt £20, 30 watt £23, 40 watt £29, 20W plus 100 volt line £38. Post £2.

MOTOROLA PIEZO ELECTRONIC HORN TWEETER, 3in square £5
 100 watts. No crossover required. 4-8-16 ohm, 7 1/2 x 3 1/2 in £10

CROSSOVERS TWO-WAY 3000 c/s 30 watt £2, 100 watt £4.
 3 way 950 cps/3000 cps 40 watt rating £8, 60 watt £6, 100 watt £10

LOUDSPEAKER BARGAINS Please enquire many others in stock
 4 ohm, 5in 7x4in £2.50; 6in 8x5in £3.8in £3.50; 6in 20W £7.50
 8 ohm, 2 1/2in 3in £2; 5x3in 6x4in 7x6in 5in £2.50; 6in 70W £10.00; 8 x 5in £3; 8in £4.50; 10in £5; 12in 8in £6; 25W £6.50.
 15 ohm, 2 1/2in 3 1/2in 5x3in 6x4in £2.50; 6in 10W £3.8in £4; 10in £7.
 25 ohm, 3in £2; 5x3in 6x4in 7x6in £2.50; 120 ohm, 3 1/2in dia £1.

| Make | Model | Size | Watts | Ohms | Price | Post |
|------------|-------------|------------------|-------|------|--------|------|
| AUDAX | WOFFER | 5in | 25 | 8 | £10.50 | £1 |
| GODDMANS | HIFAX | 7 1/2 x 4 1/2 in | 100 | 8 | £30 | £2 |
| GODDMANS | HB WOFFER | 8in | 60 | 8 | £13.50 | £1 |
| WHARFEDALE | WOFFER | 8in | 30 | 8 | £9.50 | £2 |
| CELESTION | DISCO/Group | 10in | 50 | 8/16 | £21 | £2 |
| GODDMANS | HPG/Group | 12in | 120 | 8/15 | £23.50 | £2 |
| GODDMANS | HPD/DISCO | 12in | 120 | 8/15 | £29.50 | £2 |
| GODDMANS | HP/BASS | 15in | 250 | 8 | £32 | £4 |
| GODDMANS | HPD/BASS | 18in | 230 | 8 | £34 | £4 |

RCS SOUND TO LIGHT CONTROLLER KIT
 Printed circuit, Cabinet, 3 channels, 1,000 watts each. Will operate from Hi-Fi or Disco. £19. Post £1.
 Ready Built Deluxe 4 Channel 4,000 watt with chaser + speed + programme controls £69. Post £2

MAINS TRANSFORMERS Price Post
 250 0-250V 80mA 6.3V 3.5A 6.3V 1A £7.00 £2
 350 0-350V 250mA 6.3V 6A CT £12.00 Shrouded £14.00 £2
 250V 60mA 6.3V 2A £4.75 £1
 220V 25mA 6V 1 Amp £3.00 220V 45mA 6V 2 Amp £4.00 £2
 Low voltage tapped outputs available
 1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.00 £2
 ditto 2 amp £10.50 3 amp £12.50 5 amp £16.00 £2

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid
 9V, 3A, 12V, 3A, 16V, 2A, 20V, 1A, 30V, 1A, 30V, 5A, 17-0-17V, 2A, 35V, 2A, 20-40-60V, 1A, 12-0-12V, 2A, 20-0-20V, 1A, 1A, 20-0-25V, 2A

£8.50 post 50p MINI-MULTI TESTER
 Deluxe pocket size precision moving coil instrument. Impedance - Capacity 4000 o.p.v. Battery included 11 instant ranges measure: DC volts 5, 25, 250, 500 AC volts 10, 50, 500, 1000 DC amps 0-250µA, 0-250mA. Resistance 0 to 600k ohms

De-Luxe Range Doubler Meter, 50,000 o.p.v. 7 x 5 x 2in. Resistance 0/20 meg In 5 ranges. Current 50µA to 10A. Volts 0.25/1000V DC, 10v/1000V AC £21.00 post £1

PANEL METERS £5.50 post 50p
 50µA, 100µA, 500µA, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/2 x 1 1/2 Stereo VU 3 1/2 x 1 1/2

ALUMINIUM CHASSIS 18 s.w.g., 4 sides, riveted corners:
 6 x 4 x 2 1/2 in. £1.78; 8 x 6 x 2 1/2 in. £2.20; 14 x 9 x 2 1/2 in. £3.60; 12 x 3 x 2 1/2 in. £1.80; 12 x 8 x 2 1/2 in. £3.20.

ALI ANGLE BRACKET 6 x 1 x 1/2 in. 30p.

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in 55p; 12 x 8in. £1.30; 10 x 7in. 96p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 30p; 16 x 10in. £2.10; 16 x 6in. £1.30

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK
 4 x 2 1/2 x 2in. £1.20; 3 x 2 x 1in. £1.00; 6 x 4 x 2in. £1.90; 8 x 6 x 3in. £3.00; 12 x 5 x 3in. £3.60; 6 x 4 x 3in. £2.20; 10 x 7 x 3in. £3.60; 7 x 5 x 3in. £2.90; 12 x 8 x 3in. £4.30

HIGH VOLTAGE ELECTROLYTICS 32+32/350V 50p
 20/500V 75p 8+8/500V £1 32+32+32/450V £1.50
 32/350V 45p 8+16/450V 75p 125/500V £2
 32/500V 95p 16+16/350V 75p 16+32+32/500V £2

SINGLE PLAY DECKS. Post £2

| Make | Model | Cartridge | Price |
|---------|-------|-----------|-------|
| BSR | P170 | Ceramic | £20 |
| GARRARD | 6200 | Ceramic | £22 |
| BSR | P182 | Ceramic | £26 |
| BSR | P232 | Magnetic | £28 |
| BSR | P200 | Magnetic | £34 |

AUTOCHANGER BSR Ceramic £30

DECCA TEAK VENEERED PLINTH
 Superior finish with space and panel for small amplifier. Board cut for BSR or Garrard 18in x 14in. x 4in. £5
 Black/chrome facia trim. Tinted plastic cover £5 Post £1

TINTED PLASTIC COVERS for Decks, Music Centres, etc. Post £1
 17 x 12 x 3 1/2 in. £5 16 1/2 x 13 x 4in. £5
 22 1/2 x 13 1/2 x 3in. £3 14 1/2 x 13 1/2 x 2 1/2 in. £5
 2 1/2 x 14 1/2 x 2 1/2 in. £5 17 1/2 x 13 1/2 x 4 1/2 in. £5
 14 1/2 x 13 x 3 1/2 in. £5 2 1/2 x 13 1/2 x 4 1/2 in. £5
 18 1/2 x 12 1/2 x 3in. £5 30 1/2 x 13 1/2 x 3 1/2 in. £5
 14 1/2 x 12 1/2 x 2 1/2 in. £5

RADIO COMPONENT SPECIALISTS
 Dept 4, 337, WHITEHORSE ROAD, CROYDON
 SURREY, U.K. TEL: 01-684 1665

ACCESS VISA

Post 50p Minimum Callers Welcome
 Lists 32p Same day despatch, Closed Wed

the leader of the Packs

BIG VALUE RESISTOR PACKS

1 WATT CARBON FILM
 1Ω-10MΩ ten values
 Total 720 resistors. **£5**

1 WATT METAL FILM
 1% 50ppm 10Ω-1MΩ E24 range.
 Total 960 resistors. **£25**

FREE CATALOGUE

Sent to every new customer

AC/DC COMPONENT PACKS

| Pack No. | Qty | Description | Price |
|----------|-----|--|-------|
| TF11 | 12 | RED 5mm LED | £1.00 |
| TF12 | 30 | 500mz ZENERS 5% | £1.00 |
| TF13 | 100 | IN4148 Diode | £1.00 |
| TF14 | 100 | IN4151 Diode | £1.00 |
| TF15 | 50 | 1 amp Rect. Diodes in 4000 series | £1.00 |
| TF16 | 6 | 1 amp Bridge Rect. | £1.00 |
| TF17 | 100 | Transistor pads | £1.00 |
| TF18 | 20 | A/S Fuses 20mm | £1.00 |
| TF19 | 10 | 3A Rect. Diodes | £1.00 |
| TF110 | 2 | ORP 12 | £1.00 |
| TF111 | 5 | BR 100 DIAC | £1.00 |
| TF112 | 10 | BC109B | £1.00 |
| TF113 | 10 | IC's all different | £1.00 |
| TF114 | 50 | BFR86 | £1.00 |
| TF115 | 12 | 8 pin DIL sockets | £1.00 |
| TF116 | 20 | 10mm Horiz. Pre set (10 values) | £1.00 |
| TF21 | 200 | 47pf 160v Polystone cap | £2.00 |
| TF22 | 10 | LM 3900 N | £2.00 |
| TF23 | 10 | Mixed DTL | £2.00 |
| TF24 | 5 | 4700 mf 25v Tag Elect 2" x 1" | £2.00 |
| TF25 | 10 | 1000 mf 63v Ax Elect. | £2.00 |
| TF26 | 50 | 022 mf 400v RAD POLY | £2.00 |
| TF27 | 10 | 100mf 250v Ax | £2.00 |
| TF28 | 10 | 2.2mf 160v Polyester RAD | £2.00 |
| TF51 | 100 | white/red 5mm LED | £5.00 |
| TF52 | 50 | BC 108C | £5.00 |
| TF53 | 2 | 10,000mf 63v comp. grade elect. | £5.00 |
| TF54 | | 1/2 kg reel 22g ersin multicore solder | £5.00 |
| TF55 | 10 | 2N3055 (HRC) | £5.00 |
| TF56 | 5 | OC71 | £5.00 |

ALL PRICES INCLUDE VAT - ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.

TERMS: Cash with order. POST & PACKING: Please add 75p to total order.


AC/DC ELECTRONICS COMPONENTS

DEPT E.E. 45 CHURCH STREET, ENFIELD, MIDDLESEX.

BSR P256 TURNTABLE
 P256 turntable chassis ● S-shaped tone arm
 ● Belt driven ● Aluminium platter ● Precision
 calibrated counter balance ● Anti-skate (bias
 device) ● Damped cueing lever ● 240 volt AC
 operation (Hz) ● Cut-out template supplied ●
 Completely manual arm. This deck has a com-
 pletely manual arm and is designed primarily
 for disco and studio use where all the advan-
 tages of a manual arm are required.
 Price **£33.60** each. **£2.50** P&P



PIEZO ELECTRIC TWEETERS — MOTOROLA
 Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

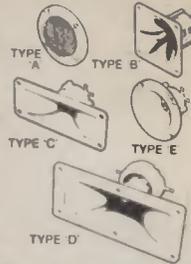


TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price **£4.29** each + 40p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price **£4.99** each + 40p P&P.
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price **£5.99** each + 40p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price **£7.99** each + 40p P&P.
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price **£4.99** each + 40p P&P.

LARGE S.A.E.
 For details of
 disco mixers,
 speakers, kits,
 amp - modules,
 buglar alarms,
 turntables, etc.

OMP POWER AMPLIFIER MODULE

READY BUILT

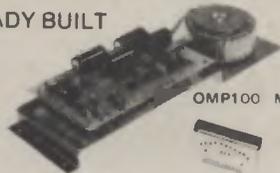

New model.
 Improved specification

NEW OMP100 Mk.II POWER AMPLIFIER MODULE Power Amplifier Module complete with integral heat sink, toroidal transformer power supply and glass fibre p.c.b. assembly. Incorporates drive circuit to power a compatible LED Vu meter. New improved specification makes this amplifier ideal for P.A., Instrumental and Hi-Fi applications

SPECIFICATION
 Output Power:— 110 watts R.M.S.
 Loads:— Open and short circuit proof 4/16 ohms.
 Frequency Response:— 15Hz - 30KHz - 3dB
 T.H.D.:— 0.01%
 S.N.R. (Unweighted):— -118dB ± 3.5dB
 Sensitivity for Max Output:— 500mV at 10K
 Size:— 360 X 115 X 72mm Price:— **£31.99**
 + **£2.50** P&P. Vu Meter Price:— **£8.50** + 50p P&P

MOS-FET HIGH SPEC. MODULES



MOS-FET VERSIONS AVAILABLE UP TO 300 W. R.M.S.
 100 Watt 300mm X 123mm X 80mm Price: **£39.99** + **£2.50** P&P
 200 Watt 300mm X 150mm X 100mm Price: **£62.99** + **£3.50** P&P
 300 Watt 330mm X 147mm X 102mm Price: **£79.99** + **£4.50** P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: **£8.62** + 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: **£13.74** + 75p P&P.

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: **£17.82**. Transmitter 80 x 50 x 15mm (9/12 volt). Price: **£11.27** P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

LOUDSPEAKERS POWER RANGE

THREE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8" See 'Photol Ideal for both Hi-Fi and Disco applications. All units have attractive cast aluminium (ground finish) fixing escutcheons. Specifications and Prices

15" 100 watt R.M.S. Impedance 8 ohms 50 oz magnet. 2" aluminium voice coil. Res. Freq. 20 Hz Freq. Resp. to 25KHz Sens. 97dB Price: **£34.00** each + **£3.00** P&P
12" 100 watt R.M.S. Impedance 8 ohms 50 oz magnet. 2" aluminium voice coil. Res. Freq. 25Hz Freq. Resp. to 4 KHz Sens. 95dB Price **£26.00** each + **£3.00** P&P.
8" 50 watt R.M.S. Impedance 8 ohms. 20 oz magnet. 1 1/2" aluminium voice coil. Res. Freq. 40Hz Freq. Resp. to 6 KHz Sens. 92dB. Black Cone. Price: **£9.50** each. Also available with black protective grille. Price: **£10.50** each. P&P **£1.50**.



12" 85 watts R.M.S. MCKENZIE C1285GP (LEAD GUITAR, KEYBOARD, DISCO) 2" aluminium voice coil, aluminium centre dome, 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 6.5KHz., Sens. 98dB Price **£24.99** + **£3** carriage.
12" 85 watt R.M.S. MCKENZIE C1285TC (P.A., DISCO) 2" aluminium voice coil. Twin cone. 8 ohm imp., Res. Freq. 45Hz., Freq. Resp. to 14KHz Price **£24.99** + **£3** carriage.
15" 150 watt R.M.S. MCKENZIE C15 (BASS GUITAR, P.A.) 3" aluminium voice coil. Die cast chassis. 8 ohm imp., Res. Freq. 40Hz., Freq. Resp. to 4KHz. Price **£49** + **£4** carriage. Cabinets fixings in stock S.A.E.

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★

B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX SS2 6TR TEL 0702-527572



METERS: 110 x 82 x 35mm
 30µA, 50µA, 100µA. **£6.90**
 Post 50p.

METERS: 45 x 50 x 34mm
 50µA, 100µA, 1mA, 5mA, 10mA, 25v, 1A, 2A, 5A 25V. **£3.54**. Post 30p.

METERS: 60 x 47 x 33mm
 50µA, 100µA, 1mA, 5mA, 10mA, 100mA, 1A, 2A, 25v, 50v, 50-0-50µA, 100-0-100µA. **£6.04**.
 VU meters **£6.04**.
 Post on above meters 30p.

Silicone grease 50g **£1.32**.
 Post 16p.

NI-CAD BATTERY CHARGER
 Led indicators charge-test switch. For PP3, HP7, HP11 & HP2 size batteries. Price **£5.85**. Post 94p.

Motorola Piezo Ceramic Tweeter **£5.20** Post 33p

METERS: 60x46x33mm illuminated. Require 6V supply.
 50µA, 100µA, 500µA,
 100-0100µA,
 1mA, 1A, 2A, 25V, 30V & VU.
£4.50 post 30p

ALSO IN STOCK
 2, 3, 4, 6 & 8A Transformers

TRANSFORMERS
240v Primary
 3-0-3v 100mA **82p**
 6-0-6v 100mA **£1.20**
 6-0-6v 250mA **£1.33**
 12-0-12v 50mA **£1.13**
 12-0-12v 100mA **£1.21**
 9-0-9v 75mA **£1.20**
 9-0-9v 250mA **£1.37**
 Post on above transformers 48p.
 9-0-9v 1A **£2.05**
 12-0-12v 1A **£2.52**
 15-0-15v 1A **£3.11**
 6-0-6v 1 1/2A **£2.20**
 Post on above transformers 94p.

Rotary Switches: 1 Pole 12 Way 2P6W, 3P4W, 4P3W **42p**
 Post 16p

Illuminated Rocker Switch
 240V 6A Red **88p** Post 16p

All above prices include V.A.T. Send £1 for a new comprehensive 1983/84 fully illustrated catalogue with a new price list. Send S.A.E. with all enquiries. Special prices for quantity on request.

All goods despatched within 3 days from receipt of the order.

M. DZIUBAS
 158 Bradshawgate, Bolton,
 Lancs. B11 1BA. Tel: 29324

INDEX TO ADVERTISERS

| | |
|-----------------------------|-----------|
| AC/DC Electronics | 543 |
| A.D. Electronics | 542 |
| American Inventors Corp. | 542 |
| Bib Audio | 482, 483 |
| Bi-Pak | Cover II |
| BK Electronics | 544 |
| B.N.R.E.S. | 482 |
| Computronics | 542 |
| Dzuibas M. | 544 |
| Electronic Mail Order | 542 |
| Electrovalue | 533 |
| Greenweld Electronics | 483 |
| ICS Intertext | 533 |
| Magenta Electronics | Cover III |
| Maplin Electronics | Cover IV |
| Radio Component Specialists | 543 |
| R&TVC | 533 |
| Rapid Electronics | 485 |
| Software Index | 484 |
| Sparkrite | 483 |
| T.K. Electronics | 486 |

E.E. PROJECT KITS MAGENTA TEACH IN 84

THIS MONTHS KITS PHONE OR WRITE FOR PRICES

Full Kits inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.

If you do not have the issue of E.E. which includes the project - you will need to order the instruction reprint as an extra - 50p each. Reprints available separately 50p each + p&p 50p.

| | |
|---|--------|
| SPEECH SYNTHESIZER June 84 | £29.22 |
| TRAIN WAIT June 84 | £15.83 |
| CHANNEL SELECTION SWITCH June 84 | £10.28 |
| VARICAP AM RADIO May 84 | £10.43 |
| EXPERIMENTAL POWER SUPPLY May 84 | £18.72 |
| SIMPLE LOOP BURGLAR ALARM May 84 | £13.62 |
| MASTERMIND TIMER May 84 | £5.44 |
| AUDIO SINEWAVE SWEEP GENERATOR Apr. 84 | £28.34 |
| DATA ACQUISITION & CONTROL Apr. 84 | £67.81 |
| FUSE/DIODE CHECKER Apr. 84 | £3.45 |
| QUASI STEREO ADAPTOR Apr. 84 | £10.90 |
| TIMER MODULE FOR CENTRAL HEATING SYSTEMS Apr. 84 | £17.84 |
| DIGITAL MULTIMETER add on for BBC Micro Mar. 84 | £24.98 |
| NI-CAD BATTERY CHARGER Mar. 84 | £9.85 |
| REVERSING BLEEPER Mar. 84 | £6.78 |
| DIN LEAD TESTER Mar. 84 | £8.32 |
| PIPE FINDER Mar. 84 | £3.60 |
| LOW POWER STEREO AMP Mar. 84 | £27.88 |
| IONISER Feb 84 | £23.98 |
| EPROM PROGRAMMER Feb 84 | £14.48 |
| SIGNAL TRACER Feb 84 | £14.89 |
| CAR LIGHT WARNING Feb 84 | £3.76 |
| GUITAR TUNER Jan 84 | £17.73 |
| BIOLOGICAL AMPLIFIER Jan 84 | £19.16 |
| CONTINUITY TESTER Dec 83 | £9.99 |
| CHILDREN'S DISCO LIGHTS Dec 83 | £8.42 |
| NOVEL EGG TIMER Dec 83 inc. case | £10.24 |
| SPEECH SYNTHESIZER FOR THE BBC MICRO Nov. 83 less cable + sockets | £21.98 |
| MULTIMOD Nov. 83 | £16.98 |
| LONG RANGE CAMERA/FLASHGUN TRIGGER Nov. 83 | £13.50 |
| HOME INTERCOM less link wire Oct. 83 | £14.38 |
| IMMERSION HEATER TELL-TALE Oct. 83 | £9.98 |
| SHORT WAVE RADIO less 'phones, Oct. 83 | £25.63 |
| Mono headphones extra | £3.36 |
| DIGITAL TO ANALOGUE BOARD Oct. 83 | £19.98 |
| less cable, case & connector | |
| HIGH POWER DAC DRIVER BOARD Oct. 83 less case | £12.52 |
| A TO D CONVERTER FOR RM380Z Sept. 83 plug | £35.98 |
| HIGH SPEED A TO D CONVERTER Sept. 83 less cable & connector | £27.98 |
| SIGNAL CONDITIONING AMP Sept. 83 no case | £8.98 |
| STORAGE 'SCOPE INTERFACE FOR BBC MICRO Aug 83 less software | £15.38 |
| PEDESTRIAN CROSSING SIMULATION BOARD Aug 83 no case | £10.29 |
| HIGH POWER INTERFACE BOARD Aug 83 no case | £10.38 |
| CAR INTRUDER ALARM Aug 83 | £16.98 |
| AUTOMATIC GREENHOUSE WATERING SYSTEM July 83 | £10.98 |
| TRI BOOST GUITAR TONE CONTROLLER July 83 | £8.35 |
| USER PORT I/O BOARD less cable + plug | £10.49 |
| USER PORT CONTROL BOARD July 83 less cable + plug | £25.14 |
| BINARY BANDIT GAME July 83 less case | £9.88 |
| EPROM PROGRAMMER Jun. 83 less software, TRS80 | £44.99 |
| Genie | £45.73 |
| ENVELOPE SHAPER Jun. 83 less case | £12.33 |
| REAL TIME CLOCK May 83 less software and cases | |
| Apple II £33.98 BBC £39.59 less power plug | |
| MODEL TRAIN CONTROLLER May 83 | £27.17 |
| GUITAR HEADPHONE AMPLIFIER May 83 | £7.62 |
| MW PERSONAL RADIO less case, May 83 | £7.62 |
| MOISTURE DETECTOR May 83 | £5.46 |
| CAR RADIO POWER BOOSTER April 83 | £11.99 |
| FUNCTION GENERATOR April 83 | £45.98 |
| FLANGER SOUND EFFECTS April 83 | £24.17 |
| NOVELTY EGG TIMER April 83 less case | £5.48 |
| ZX SPECTRUM AMPLIFIER April 83 | £9.87 |
| DUAL POWER SUPPLY March 83 | £59.38 |

| | |
|---|---------------------------------------|
| BUZZ OFF March 83 | £4.51 |
| SPEECH PROCESSOR Feb 83 | £11.66 |
| PUSH BIKE ALARM Feb. 83 | £11.73 |
| DOUBLE DICE Jan. 83 | £11.90 |
| ELECTRONIC V/I METER Dec. 82 | £12.52 |
| ZX TAPE CONTROL Nov. 82 | £7.13 |
| SINE WAVE GEN Oct. 82 | £16.11 |
| G. P. PRE-AMP Oct. 82 | £6.09 |
| LIGHTS ON ALERT Oct. 82 | £4.68 |
| CONTINUITY CHECKER Sept. 82 | £5.47 |
| SOUND SPLITTER Sept. 82 | £17.35 |
| SOUND RECOMBINER Sept. 82 | £4.07 |
| SCREEN WASH DELAY Sept. 82 | £4.83 |
| CB ROGER BLEEPER Aug. 82 | £9.32 |
| 2-WAY INTERCOM July 82 no case | £4.52 |
| ELECTRONIC PITCH PIPE July 82 | £5.40 |
| REFLEX TESTER July 82 | £7.77 |
| SEAT BELT REMINDER Jun. 82 | £4.10 |
| EGG TIMER June 82 | £5.44 |
| CAR LED VOLTMETER less case, May 82 | £23.18 |
| V.C.O. SOUND EFFECTS UNIT Apr. 82 | £12.71 |
| CAMERA OR FLASH GUN TRIGGER Mar. 82 | £13.65 less tripod bushes |
| POCKET TIMER Mar. 82 | £4.10 |
| GUITAR TUNER Mar. 82 | £17.19 |
| SIMPLE STABILISED POWER SUPPLY Jan. 82 | £26.98 |
| MINI EGG TIMER, Jan. 82 | £4.40 |
| SIREN MODULE Jan. 82 less speaker | £8.10 |
| MODEL TRAIN CHUFFER Jan. 82 | £8.98 |
| SIMPLE INFRA RED REMOTE CONTROL Nov. 81 | £18.70 |
| CAPACITANCE METER Oct. 81 | £25.81 |
| SUSTAIN UNIT Oct. 81 | £13.99 |
| 'POPULAR DESIGNS' Oct. 81; | |
| TAPE NOISE LIMITER | £4.98 |
| HEADS AND TAILS GAME | £2.75 |
| CONTINUITY TESTER | £4.48 |
| PHOTO FLASH SLAVE | £3.80 |
| FUZZ BOX | £7.98 |
| SOIL MOISTURE UNIT | £6.39 |
| ICE ALARM | £8.70 |
| 0-12V POWER SUPPLY Sept. 81 | £19.48 |
| CMOS CAR SECURITY ALARM Sept. 81 | £9.95 |
| CMOS DIE Sept. 81 | £8.80 |
| CMOS METRONOME Aug. 81 | £8.99 |
| COMBINATION LOCK July 81 less case | £21.58 |
| SOIL MOISTURE INDICATOR E.E. May 81 | £4.49 |
| GUITAR HEADPHONE AM P.E. May 81 | £4.66 |
| PHONE BELL REPEATER/BABY ALARM May 81 | £6.15 |
| INTERCOM April 81 | £24.43 |
| SIMPLE TRANSISTOR & DIODE TESTERS Mar. 81 Onmet version | £2.22 |
| Led version | £2.98 |
| LED DICE Mar. 81 | £9.35 |
| MODULATED TONE DOORBELL Mar. 81 | £7.35 |
| 2 NOTE DOOR CHIME Dec. 80 | £11.35 |
| LIVE WIRE GAME Dec. 80 | £12.87 |
| GUITAR PRACTICE AMPLIFIER Nov. 80 | £14.10 less case. Standard case extra |
| SOUND TO LIGHT Nov. 80 3 channel | £23.40 |
| TRANSISTOR TESTER Nov. 80 | £12.80 |
| AUDIO EFFECTS UNIT FOR WEIRD SOUNDS Oct. 80 | £14.40 |
| IRON HEAT CONTROL Oct. 80 | £6.30 |
| TTL LOGIC PROBE Sept. 80 | £5.68 |
| ZENER DIODE TESTER Jun. 80 | £7.30 |
| LIGHTS WARNING SYSTEM May 80 | £5.20 |
| BATTERY VOLTAGE MONITOR May 80 | £5.66 |
| CABLE & PIPE LOCATOR less coil former Mar. 80 | £4.61 |
| KITCHEN TIMER Mar. 80 | £16.20 |
| CAR MUSIC BOX Feb. 80 | £17.86 |
| Case extra | £3.60 |
| SLIDE/TAPE SYNCHRONISER Feb. 80 | £13.50 |
| MORSE PRACTICE OSCILLATOR Feb. 80 | £4.98 |
| SPRING LINE REVERB UNIT Jan. 80 | £27.20 |
| UNIBOARD BURGLAR ALARM Dec. 79 | £6.70 |
| DARKROOM TIMER July 79 | £3.20 |
| ELECTRONIC CANARY Jun. 79 | £6.40 |
| TRANSISTOR TESTER Apr. 79 | £5.38 |
| MICROCHIME DOORBELL Feb. 79 | £17.48 |
| FUSE CHECKER Sept. 78 | £2.54 |
| SOUND TO LIGHT Sept. 78 | £9.20 |
| CAR BATTERY STATE INDICATOR less case Sept. 78 | £2.29 |
| R.F. SIGNAL GENERATOR Sept. 78 | £31.20 |
| IN SITU TRANSISTOR TESTER Jun. 78 | £7.50 |
| FLASHMETER less calc & diffuser May 78 | £16.50 |
| WEIRD SOUND EFFECTS GENERATOR Mar. 78 | £6.20 |
| AUDIO VISUAL METRONOME Jan. 78 | £6.58 |
| ELECTRONIC TOUCH SWITCH Jan. 78 | £2.99 |
| RAPID DIODE CHECK Jan. 78 | £3.15 |
| PHONE/DOORBELL REPEATER July 77 | £8.20 |
| ELECTRONIC DICE Mar. 77 | £4.96 |

* MAGENTA'S TEACH IN KIT INCLUDES ALL OF THESE TOP *
 * QUALITY ITEMS: resistors, pot, capacitors, semiconductors, *
 * varicap diode, leds, ferrite rod, sockets, crystal earpiece, termi- *
 * nal blocks, wire and of course 2 breadboards. PLUS A FREE *
 * COMPONENT IDENTIFICATION SHEET AND A COPY OF OUR *
 * CATALOGUE & PRICE LIST. AVAILABLE NOW - TEACH IN 84 *
 * KIT. £22.98 inc VAT. P+P 50p. Send now for fast delivery. *
 * Reprints of previously published parts 50p each. Official *
 * school/college orders welcome. *
 * * * * *

SOLDERING/TOOLS

| | |
|--|--------|
| ANTEX X5 SOLDERING IRON 25W | £7.25 |
| SOLDERING IRON STAND | £2.85 |
| SPARE BITS. Small, standard, large, each. For X5+X25 | £1.25 |
| SOLDER. Handy size | £1.38 |
| SOLDER CARTON | £2.50 |
| DESOLDER BRAID | 69p |
| HEAT SINK TWEEZERS | 45p |
| DESOLDER PUMP | £6.48 |
| HOW TO SOLDER LEAFLET | 13p |
| LOW COST CUTTERS | £1.98 |
| LOW COST LONG NOSE PLIERS | £1.99 |
| WIRE STRIPPERS & CUTTERS | £3.57 |
| PRECISION PETITE | |
| 12V PCB DRILL | £14.80 |
| DRILL STAND | £9.78 |
| VERO SPOT FACE CUTTER | £1.90 |
| PIN INSERTION TOOL | £2.68 |
| VEROPINS (pk of 100) 0.1" | 69p |
| MULTIMETER TYPE 1 (1,000 opv) | £5.85 |
| CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips | £1.65 |
| RESISTOR COLOUR CODE CALCULATOR 23p | |
| CONNECTING WIRE PACK TYPE ED. 11 colours | 40p |
| ILLUMINATED MAGNIFIERS | |
| Small 2" dia. (5x mag) | £1.48 |
| Large 3" dia. (4x mag) | £2.52 |
| CORE TRIM TOOL | 72p |
| PRESET TRIM TOOL | £1.90 |
| FREEZER AEROSOL | £1.80 |
| CONTACT CLEANER AEROSOL | £4.99 |
| ELECOTIL CONDUCTIVE PAINT | 39p |
| PVC TAPE (RGB) 3 reels | £2.50 |
| SCREWDRIVER SET | £6.48 |
| POCKET TOOL SET | £2.25 |
| PCB ETCHING KIT | £1.50 |
| ZX81 EDGE CONNECTOR | £2.55 |
| ZX81 EDGE PLUG | £2.55 |
| ZX SPECTRUM EDGE CONNECTOR | £6.45 |
| CRYSTAL EAR PIECE | 62p |
| EUROBREADBOARD | £6.45 |
| PLASTIC TWEEZERS | 69p |



MULTIMETER TYPE 2 (YN360TR) 20K o.p.v. with transistor tester. £17.98 AC + DC volts. DC current. 4 very useful resistance ranges. We've used it and we like it.

HELPING HANDS JIG £7.98

Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2" diameter (2.5" magnifier attached), used and recommended by our staff.



PAIR OF PROBES WITH LEADS (cc). 87p Q MAX PUNCHES 3/8" £4.18; 1/2" £4.24; 5/8" £4.35; 3/4" £4.52.

BOOKS:

| | |
|---|-------|
| A Practical Introduction to Digital IC's | £1.90 |
| How to design and Make Your Own PCB's | £2.15 |
| Simple L.E.D. Circuits Book 2 | £1.50 |
| How to Make Walkie-Talkies | £2.10 |
| Projects in Opto-Electronics | £2.10 |
| Electronic Projects for Beginners | £2.10 |
| How to Identify Unmarked IC's | £2.10 |
| 50 Circuits Using 7400 Series IC's | £1.95 |
| Second Book of CMOS IC Projects | £1.75 |
| Electronic Household Projects | £1.90 |
| Radio Control for Beginners | £2.05 |
| Electronic Synthesiser Projects | £2.05 |
| How to Identify Unmarked IC's | 70p |
| International Diode Equivalents Guide | £2.45 |
| Handbook of Integrated Circuits (IC's) Equiv. & Substitutes | £2.15 |
| Beginners Guide to Building Electronic Projects | £2.15 |
| Second Book of Transistor Equivalents and Substitutes | £2.10 |
| How to Build Your Own Solid State Oscilloscope | £2.15 |
| Semiconductor Data Book Newnes | £8.35 |
| Basic Electronics. Theory and practice | £9.98 |
| Burglar Alarm Systems | £5.95 |
| Electronics, Build and Learn | £4.80 |
| Electronic Projects in Music | £4.55 |
| Electronic Projects in Photography | £4.55 |
| Microprocessors for Hobbyists | £4.98 |
| Electronic Test Equipment Construction | £2.05 |
| BP75 | £2.05 |
| Electronic Projects for Home Security | £4.55 |
| Questions and Answers Electronics | £3.45 |
| 20 Solid State Projects Car and Garage | £4.98 |
| 110 Electronic Alarm Projects | £5.98 |
| 52 Projects using IC741 | £1.75 |
| IC555 Projects | £2.10 |
| Electronic Music Projects | £2.05 |
| Practical Construction of Pre 'Amp' Tone Control Filter + Atten | £2.10 |
| Control Filter + Atten | £2.10 |
| How to Make Walkie Talkies | £2.10 |
| Mobile Disco Handbook | £1.50 |
| More books in our price list | |

* * * * *
FUN WITH ELECTRONICS
 * Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners - children and adults. Only basic tools needed. 64 full colour pages cover all aspects - soldering - fault finding - components (identification and how they work).
 * Also full details of how to build 6 projects - burglar alarm, radio, games, etc. Requires soldering - 4 pages clearly show you how.
 * COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.
 * Supplied less batteries & cases.
FUN WITH ELECTRONICS, COMPONENT PACK £16.98
 * BOOK EXTRA £1.65
 * Book available separately.
 * * * * *

ADVENTURES WITH MICROELECTRONICS

More project kits from our range, similar style to E.E. Instructions/reprint included with these kits providing the code number is quoted.

| | |
|---------------------------------|-----------------------------------|
| GL1. GUITAR ACTIVE TONE CONTROL | less case £12.47 |
| GL2. CHORUS EFFECTS UNIT | £49.48 |
| GL3. PARAMETRIC EQUALISER | £16.90 |
| GL4. DRUM SYNTHESIZER (dual) | £39.98 |
| GL5. ANALOGUE ECHO | £49.98 |
| GL6. COMPRESSOR/EXPANDER | £14.48 |
| GL7. MICRO BASS SYNTHESIZER | £43.98 |
| GL8. KEYED NOISE GATE | £28.48 |
| GL9. ZX81 SEQUENCER | £25.98 |
| GL10. MONITOR AMP | less case £11.98 case extra £6.40 |
| GL11. AUDIO MIXER (4 Inputs) | £48.98 |
| GL12. ADSR ENVELOPE GENERATOR | less case £19.98 case extra £3.98 |
| GL13. PHASER MODULE | less case £18.98 case extra £3.98 |
| GL14. DUAL MIC PRE-AMP | £14.48 |
| GL15. ENVELOPE GENERATOR | £16.98 |
| GL16. GUITAR NOTE EXPANDER | £19.98 |
| GL17. GUITAR PRE AMP | less case £8.99 case extra £3.50 |

ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.

Adventures with Electronics £2.98. Component pack £20.98 less battery.

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST
 Price list included with orders or send see (3 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lists for fast delivery.

Send 80p in stamps or add 80p to order. Free to Schools/Colleges requested on official letterhead.

MAGENTA ELECTRONICS LTD.

EE19, 135 HUNTER ST., BURTON-ON-TRENT STAFFS, DE14 2ST. MAIL ORDER ONLY. 0283 65435, Mon-Fri 9-5. Access/Barclaycard (Visa) by phone or post. 24 hr Answerphone for credit card orders.

ADD 50p P&P TO ALL ORDERS. PRICES INCLUDE VAT. SAE ALL ENQUIRIES. OFFICIAL ORDERS WELCOME. OVERSEAS: Payment must be sterling. IRISH REPUBLIC and BFPO: UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote.



MAPLIN Massive range of components for your hobby....insist on Maplin quality!

MAPLIN'S TOP TWENTY KITS

| THIS LAST MONTH | DESCRIPTION OF KIT | ORDER CODE | KIT PRICE | DETAILS IN PROJECT BOOK |
|---|------------------------------|------------|-----------|-------------------------|
| 1. (1) | 75W Mosfet Amp Module | LW51F | £13.95 | Best of E&MM |
| 2. (2) | Modem | LW99H | £44.95 | 5 XA05F |
| Case also available: YK62S Price £9.95. | | | | |
| 3. (3) | Car Burglar Alarm | LW78K | £7.49 | 4 XA04E |
| 4. (8) | Spectrum Easyload | LK39N | £9.95 | 10 XA10L |
| 5. (4) | Partylite | LW93B | £9.95 | Best of E&MM |
| 6. (6) | Syntom Drum Synthesiser | LW86T | £12.95 | Best of E&MM |
| 7. (11) | Ultrasonic Intruder Detector | LW83E | £10.95 | 4 XA04E |
| 8. (9) | 8W Amp Module | LW36P | £4.45 | Catalogue |
| 9. (10) | Logic Probe | LK13P | £10.95 | 8 XA08J |
| 10. (12) | VIC20/64 RS232 Interface | LK11M | £9.45 | 7 XA07H |
| 11. (7) | Spectrum Keyboard | LK29G | £28.50 | 9 XA09K |
| Also required: LK30H £6.50; Case: XG35Q £4.95 — Total £39.95. | | | | |
| Also available complete ready-built: XG36P £44.95. | | | | |
| 12. (14) | Spectrum RS232 Interface | LK21X | £19.95 | 8 XA08J |
| 13. (5) | ZX81 I/O Port | LW76H | £10.49 | 4 XA04E |
| 14. (16) | Noise Gate | LK43W | £9.95 | Best of E&MM |
| 15. (New) | Car Battery Monitor | LK42V | £6.95 | Best of E&MM |
| 16. (13) | Harmony Generator | LW91Y | £17.95 | Best of E&MM |
| 17. (19) | Guitar Tuner | LW90X | £12.95 | Best of E&MM |
| 18. (New) | 50W Power Amplifier | LW35Q | £15.95 | Catalogue |
| 19. (New) | 80m Amateur Receiver | LK41U | £15.95 | 10 XA10L |
| 20. (17) | Burglar Alarm | LW57M | £49.95 | 2 XA02C |

Over 80 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.



MAPLIN'S FASCINATING PROJECTS BOOKS

Full details in our Project Books Price 70p each.

In Book 1 (XA01B) 120W rms Mosfet Combo-Amplifier • Universal Timer with 18 program times and 4 outputs • Temperature Gauge • 6 Vero Projects.
In Book 2 (XA02C) Home Security System • Train Controller for 14 trains on one circuit • Stopwatch with multiple modes • Miles-per-Gallon Meter.
In Book 3 (XA03D) ZX81 Keyboard with electronics • Stereo 25W Mosfet Amplifier • Doppler Radar Intruder Detector • Remote Control for Train Controller.
In Book 4 (XA04E) Telephone Exchange for 16 extensions • Frequency Counter 10Hz to 600MHz • Ultrasonic Intruder Detector • I/O Port for ZX81 • Car Burglar Alarm • Remote Control for 25W Stereo Amp.
In Book 5 (XA05F) 300 Baud Duplex Modem to European Standard • 100W 240VAC Inverter • Sounds Generator for ZX81 • Central Heating Controller • Panic Button for Home Security System • Model Train Projects • Timer for External Alarm.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 • Module to Bridge two of our Mosfet Amps to make a 350W Amp • ZX81 Sound on your TV • Scratch Filter • Damp Meter • Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20/Commodore 64 • Digital Enlarger Timer/Controller • DXers Audio Processor • Sweep Oscillator • CMOS Crystal Calibrator.
In Book 8 (XA08J) Modem (RS232) Interface for Dragon 32 & Spectrum • Synchime • I/O Ports for Dragon 32 • Electronic Lock • Minilab Power Supply • Logic Probe • Doorbell for the Deaf.

In Book 9 (XA09K) Keyboard with Electronics for ZX Spectrum • Infra-Red Intruder Detector • Multimeter to Frequency Meter Converter • FM Radio needs no alignment • Hi-Res Graphics for ZX81 • Speech Synthesiser for Oric 1 • VIC20 ExtendiBoard • ZX81 ExtendiRAM • Dynamic Noise Limiter for Personal Cassette Players • TTL Levels to RS232 Converter • Logic Pulser • Pseudo-Stereo AM Radio • Ni-Cad Charger Timer •

Adder-Subtractor • Syndrum's Interface • Microphone Pre-Amp-Limiter.
In Book 10 (XA10L) Cassette Easyload for ZX Spectrum • 80m Amateur Receiver • Auto Waa-Waa Effects Unit • Oric 1 Modem Interface • 2.8kW Mains Power Controller • Extendiport for Dragon 32 • 12V Fluorescent Tube Driver • 32-Line Extension for Digi-Tel.

In Book 11 (XA11M) Mapmix Six Channel Audio Mixer • Mk II Noise Reduction Unit • Xenon Tube Driver • Enlarger Exposure Meter • Motherboard for the BBC Micro • Cautious Ni-Cad Charger • Servo & Driver Module • 8 Channel Fluid Detector • Door Alarm • THD Filter • Cassette Processor • Volume Expander • Parametric Equaliser.

1984 CATALOGUE

A massive 480 big pages of description, pictures and data and now with prices on the page. The new Maplin catalogue is the one book no constructor should be without. Now includes new Heathkit section. On sale in all branches of W.H. Smith. Price £1.35 — It's incredible value for money. Or send £1.65 (including p & p) to our mail-order address.


GREAT PROJECTS FROM E&MM

Our book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first Year. Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects. Order As XH61R. Price £1.

Post this coupon now for your copy of the 1984 catalogue. Price £1.35 + 30p post and packaging. If you live outside the U.K. send £2.20 or 11 International Reply Coupons. I enclose £1.65

Name

Address

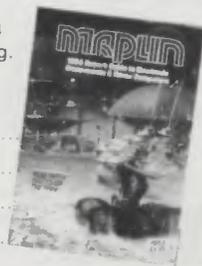

EE 8/84

MAPLIN ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 • Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748-0926. • 8 Oxford Road, Manchester. Tel: 061-236-0281. • Lynton Square, Perry Barr, Birmingham. Tel: 021-356-7292. • 282-284 London Road, Westcliff-on-Sea, Essex. Tel: 0702 554000. • 46-48 Bevois Valley Road, Southampton. Tel: 0703 25831. All shops closed all day Monday. All prices include VAT and carriage. Please add 50p handling charge to orders under £5 total value (except catalogue).

Despatch by return of post where goods available.