

EVERYDAY ELECTRONICS and computer PROJECTS

APRIL 1985

£1-00



Cybervox
Robot Voice
Insulation Tester
Fibrelarm

BI-PAK BARGAINS

HIGH QUALITY MODULES FOR STEREO, MONO & OTHER AUDIO EQUIPMENT

Audio Amplifiers

O/No.	POWER D/P	MAX SUP. VOLTAGE	PRICE
AL 30A	R.M.S. 10 Watts	30V	£4.95
AL 60	25 Watts	30-50V	£5.92
AL 80	35 Watts	40-60V	£8.75
AL 120	50 Watts	50-70V	£15.22
AL 250	125 Watts	50-90V	£20.60

Stabilised Power Supplies

O/No.	AC Input	Price
SPM 120/45	40-48V	£8.05
SPM 120/55	50-55V	£8.05
SPM 120/65	60-65V	£8.05

Mono Pre-Amplifiers - Operating Vtg. 40-65V
 O/No. MPA30. Sup Vtg. 20-30V. Price **£4.75**
 MM 100 Suitable for Disco Mixer **£14.75**
 MM 100G Suitable for Guitar Pre-Amp Mixer **£14.75**

Magnetic Cartridge Pre-Amplifier
 O/No. MPA30. Sup Vtg. 20-30V. Price **£4.29**


Monographic Equaliser
 GE 100 MKII 10 Channel OUR PRICE ONLY **£20.00**

Full Specifications and Data available on request. Please send self-addressed envelope.

HYBRID LED COLOUR DISPLAYS

Red, Green, Yellow - 3, 5, 6 inch Mixed types and colours NUMERIC & OVER-FLOW Common Anode/Cathode. GaAsP/GaP. Brand New. Full Data incl.

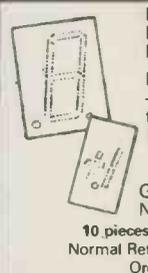10 pieces (our mix) ... **£4.00**
 Normal Retail Value Over **£10.00**
 Order No. VP58



VALUE PACKS

Pak No	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/4-1/2 Watt Pre-Formed	£1.00
VP3	200	1/4 Watt Min Carbon Resistors Mixed	£1.00
VP4	150	1/2 Watt Resistors 100 ohm-1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc. 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf - .015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	50	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5.6pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	25	.01uF 250v Min. layer metallised Polyester Capacitors	£1.00
VP16	50	Wirewound Res. 3W (avg) Ass. 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 5 Amp 240v	£1.00
VP21	15	2in. high bright RED LEDs in plastic encapsulation-Large area light source	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log 5 x Lin	£1.00
VP26	15	Small, 125' Red LED'S	£1.00
VP27	15	Large, 2" Red LED'S	£1.00
VP28	10	Rectangular, 2" RED LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vts. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vts. Coded	£1.00
VP31	10	5 Amp SCR'S TO-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR'S TO-66 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 DO-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like OA200/BAX13/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1/4" Std	£1.00
VP42	10	Black Heatsinks To Fit TO-3, TO-220 Red/Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x 10-3 2 x TO-66 Size	£1.00
VP45	50	BC107/8 Type NPN Transistors Good Gen. Purpose Uncoded	£1.00
VP46	50	BC177/8 Type PNP Transistors Good Gen. Purpose Uncoded	£1.00
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.00
VP48	50	Precision Resistors. 2-1% tol.	£1.00
VP49	40	1N4002 Sil. Rects. 1A 100v preformed pitch	£1.00
VP42	4	40A Power Rectifiers Silicon TO48 300V1P	£1.00
VP43	5	BY187 12KV Sil. Diodes in carriers 2.5mA	£1.00
VP44	4	100K 1in. Multi-turn pots ideal var cap tuning	£1.00
VP45	10	Assorted pots. inc. Dual & Switched types	£1.00
VP46	25	Solid Tantalum Caps. Mixed Values	£1.00

TRANSISTOR PACKS

VP150	20	BC183B Sil. Trans. NPN 30v 200mA Hfe240+ TO92	£1.00
VP151	25	BC171B Sil. Trans. NPN 45v 100mA Hfe240+ TO92	£1.00
VP152	15	TS190 Sil. Trans. NPN 40v 400mA Hfe100+ TO92	£1.00
VP153	15	TS191 Sil. Trans. PNP 40v 400mA Hfe100+ TO92	£1.00
VP154	15	MPSA56 Sil. Trans. PNP 80v 800mA Hfe50+ TO92	£1.00
VP155	20	BF595 Sil. Traos. NPN eqvt. BF184 H.F. TO92	£1.00
VP156	20	BF495 Sil. Trans. NPN eqvt. BF173 H.F. TO92	£1.00
VP157	15	ZTX500 Series Sil. Trans. PNP Plastic	£1.00
VP158	15	ZTX107 Sil. Trans. NPN eqvt. BC107 Plastic	£1.00
VP159	15	ZTX108 Sil. Trans. NPN eqvt. BC108 Plastic	£1.00
VP160	20	E5024 Sil. Trans. PNP eqvt. BC214L TO92	£1.00
VP161	25	BC183L Sil. Trans. NPN 30v 200mA TO92	£1.00
VP162	5	SJE5451 Sil. Power Trans. NPN 80v 4A Hfe20+	£1.00
VP163	2	PNP/PNP pairs Sil. Power Trans. like SJE5451	£1.00
VP164	4	2N6289 Sil. Power Trans. NPN 40v 40w 7A Hfe30+	£1.00
VP165	6	BFT33 NPN Sil. Trans. 80v 5A Hfe50-200 TO39	£1.00
VP166	5	BFT34 NPN Sil. Trans. 100v 5A Hfe50-200 TO39	£1.00
VP167	1	BUY69C NPN TO3 VCB 500 10A 100w Hfe15+	£1.00
VP168	10	BC478 eqvt. BCY71 PNP Sil. Trans. TO18	£1.00
VP169	10	BX521 eqvt. BC394 NPN Sil. Trans. 80v 50mA TO18	£1.00
VP170	10	Assorted Power Trans. NPN/PNP Coded & Data	£1.00
VP171	10	BF355 NPN TO-39 Sil. Trans. eqvt. BF258 225v 100mA	£1.00
VP172	10	SM1502 PNP TO39 Sil. Trans. 100v 100mA Hfe100+	£1.00

TRANSISTORS

100 Silicon NPN Transistors. All Perfect. Coded Mixed. Types With Data And Eqvt. Sheet No Rejects. Fantastic Value. O/No. BP38 **£3.00**

100 Silicon PNP Transistors. All Perfect. Coded. Mixed. Types With Data and Eqvt. Sheet. No Rejects. Real Value. O/No. BP39 **£3.00**

The best known Power Transmitter in the world 2N3055 NPN 115W. Our Bi-Pak Special Offer Price.

10 off	50 off	100 off
£3.50	£16.00	£30.00

BD312 COMPLIMENTARY PNP POWER TRANSISTORS TO 2N3055. Equivalent MJ2955 BD312 TO3. Special Price **£0.70** each. 10 off **£6.50**

SEMICONDUCTORS FROM AROUND THE WORLD

100 A collection of Transistors, Diodes, Rectifiers & Bridges, SCRs, Triacs, I.C.s & Opto's all of which are current every day useable devices. Guaranteed Value Over £10 Normal Retail Price. Data etc. in every pack. Order No. VP56
Our Price £4.00

TRANSISTOR CLEARANCE

100 All Sorts Transistors. A mixed bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes instructions for making Simple Transistor Tester, Super Value.


Order No. VP60. **£1.00**

150 De-soldered Silicon Transistors from boards 10mm leads all good. O/No. VP173 **£1.00**

BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, sizes & colours, together with 7 Segment Displays both anode & cathode plus photo-transistors emitters and detectors. Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over **£12 Normal Price**

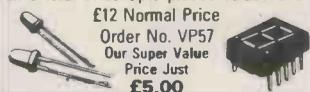Order No. VP57
 Our Super Value Price Just **£5.00**



OPTICALLY COUPLED MODULES

1 pair SD17131 Consisting of 1 x LS600 Silicon Light Sensor & 1 x Matched Gallium Arsenide Light Source - Type TIL23, on ready mounted fibre glass board. Including Data. Ideal Alarm projects etc. O/No. VP147.

BI-PAK Price ONLY £0.60 pr.

LED DISPLAYS


VP130	6	RED 7 Seg. CC 14mm x 7.5mm RDP FND353	£2.00
VP131	4	GREEN 7 Seg. CA 6" LDP XAN6520	£2.00
VP132	5	RED 7 Seg. CC 6" LDP XAN6940	£2.00
VP133	6	RED Over-flow 6" 3 x CA 3 x CC 6630/50	£2.00
VP134	5	GREEN Over-flow 6" CA XAN6530	£2.00
VP135	5	RED 7 Seg. CA 3" XAN3061	£2.00
VP136	3	DUAL RED 7 Seg. 5" CA DL527 DPR	£2.00
VP137	3	DUAL RED 7 Seg. 5" CA DL727 DPR	£2.00
VP138	20	Assorted LED Displays - Our mix with Data	£5.00

RDP = Right Hand Decimal Point CC = Common Cathode
 LDP = Left Hand Decimal Point CA = Common Anode

ANTENNA SWITCH 2 and 3 WAY


Co-axial switch for one transceiver to two antennae or one antenna to two transceivers. O/No. VP 113 **£4.50**

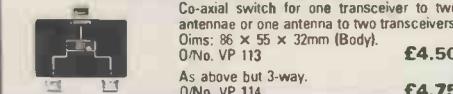As above but 3-way. O/No. VP 114 **£4.75**




HIGH PASS FILTER/SUPPRESSOR

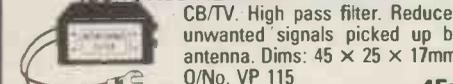CB/TV. High pass filter. Reduces unwanted signals picked up by antenna. Dims: 45 x 25 x 17mm. O/No. VP 115 **45p**



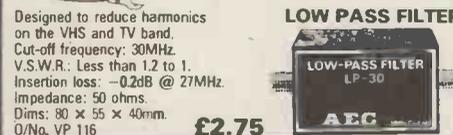Designed to reduce harmonics on the VHS and TV band. Cut-off frequency: 30MHz. V.S.W.R.: Less than 1.2 to 1. Insertion loss: -0.2dB @ 27MHz. Impedance: 50 ohms. Dims: 80 x 55 x 40mm. O/No. VP 116 **£2.75**



LOW PASS FILTER

LOW-PASS FILTER LP-30 **AEG**

IC BARGAINS

40 Assorted TTL CMOS INTEGRATED CIRCUITS 74 Series & CD4000 Series - All new Gates, Flip-Flops - MSI etc. GREAT VALUE Data Book & Sheets included. 40 Pieces (Our Mix) £4.00 O/No. UP40

TECASBOTY THE ELECTRONIC COMPONENTS AND SEMICONDUCTOR BARGAIN OF THE YEAR!


This collection of Components and Semiconductors for the hobbyist is probably the most value-packed selection ever offered, it consists of Resistors, carbon and wirewound of various values. Capacitors: All types, sorts and sizes including electrolytics. Potentiometers - single, dual, slider and preset. Switches, Fuses, Heatsinks, Wire, P.C.B. Board, Plugs, Sockets etc., PLUS a selection of Semiconductors for everyday use in popular Hobby Projects. These include: SCR'S, Diodes, Rectifiers, Triacs & Bridges as well as a first class mix of Transistors and I.C.'s. In all, we estimate the value of this in current retail catalogues to be over £25! So, help yourself to a great surprise and order a Box TODAY - ONLY at BI-PAK. Remember, stocks are limited so hurry! You can call us on 0920 3182/3442 and order with your Barclaycard or Access Card - 24hr Answerphone Service NOW. Order No. VP 85.

just **£7.00**

PIEZO BUZZERS


Miniature round piezo-electric buzzer. White plastic. Low consumption. Frequency: 4kHz approx. Output: 70dB (A) @ 1, typ. Power: 12Vd.c. 4mA. Dims: 22 (dia.) x 11.5mm. Fixing Centres: 26.5mm. O/No. VP 107 **£1.05**

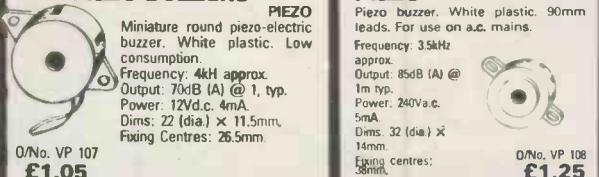PIEZO Piezo buzzer. White plastic. 90mm leads. For use on a.c. mains. Frequency: 3.5kHz approx. Output: 85dB (A) @ 1m typ. Power: 240V a.c. 5mA. Dims: 32 (dia.) x 14mm. Fixing centres: 38mm. O/No. VP 108 **£1.25**



ELECTRONIC BUZZER

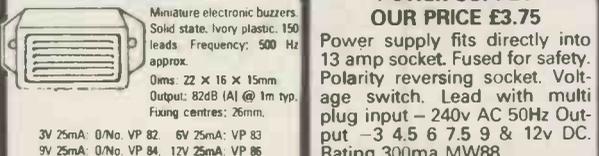Miniature electronic buzzers. Solid state. Ivory plastic. 150 leads. Frequency: 500 Hz approx. Dims: 22 x 16 x 15mm. Output: 82dB (A) @ 1m typ. Fixing centres: 26mm. 3V 25mA O/No. VP 82. 6V 25mA: VP 83. 9V 25mA: O/No. VP 84. 12V 25mA: VP 85 **95p each**



POWER SUPPLY OUR PRICE £3.75

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug input - 240v AC 50Hz Output - 3 4.5 6 7.5 9 & 12v DC. Rating 300mA MW88.

(LEARN A LINGO) PILLOW SPEAKER

Slim under pillow unit. 80ohms 2" speaker, 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65(dia) x 17mm. O/No. VP 88 **£1.25**



EDGE CONNECTORS

2 x 5 way .1 Pitch Edge Connector (Gold) (O/No. AMP163273) **£1.20 each** **£50 per 50 off**

PICK-UP COIL

Large telephone pick-up coil for high sensitivity. Suction pad to stick to telephone 90cm lead to 3.5 jack plug. Connects direct to cassette recorder. Dims 32mm(dia) x 17mm(body) 36mm(dia) sucker. O/No. YP87 **£1.00**



BI-PAK

Send your orders to Dept E4 BI-PAK PO BOX 6 WARE, HERTS SHOP AT 3 BALDOCK ST, WARE, HERTS. TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182, GIRO 388 7006 ADD 15% VAT AND £1.00 PER ORDER POSTAGE AND PACKING





Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add £1.00 per Total order.

EVERYDAY ELECTRONICS and computer PROJECTS

VOL. 14 No. 4 APRIL 1985

ISSN 0262-3617

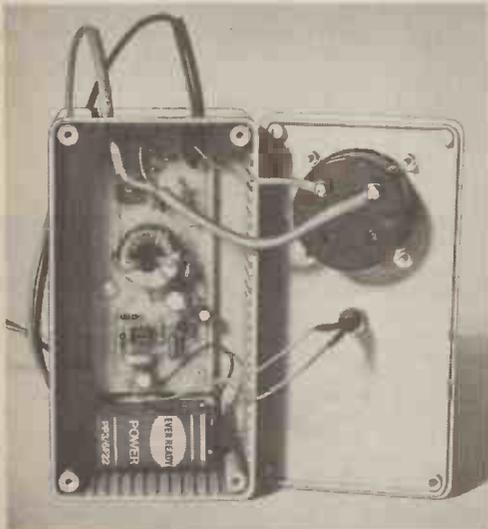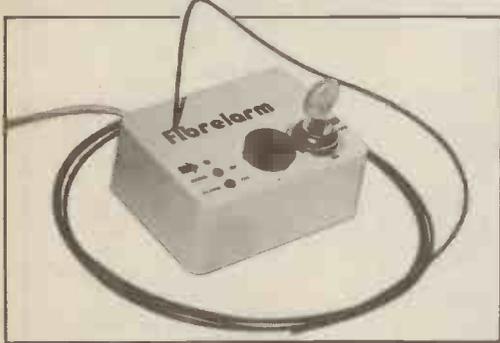PROJECTS . . . THEORY . . . NEWS . . .
COMMENT . . . POPULAR FEATURES . . .



See Page 204

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

PROJECTS

- CYBERVOX ROBOT VOICE** by John M. H. Becker 192
Automatically translates your speech into robot dialect
- INSULATION TESTER** by Mark Stuart 200
Carry out your own safety checks with this low cost instrument
- FIBRELARM** by Gideon Tearle 220
Fail-proof security using fibre optic cable
- IMMERSION HEATER CONTROL** by T. R. de Vaux Balbirnie 230
A hot water *quantity* programmer

SERIES

- COMPUTER CLUB** by Thakery 212
A fun outlook on computing—Simple loop program structure
- ON SPEC** by Mike Tooley BA 214
New regular feature devoted to the Sinclair Spectrum
—Intruder detection system interface
- FAULT FINDING** by E. A. Rule 218
Part Six: The cassette player—its problems and remedies
- DIGITAL ELECTRONICS** by D. W. Crabtree 226
Part Seven: Realistic computer design considerations

FEATURES

- EDITORIAL** 191
- SHOPTALK** by Mike Abbott 199
Product news and component buying
- MAKING PRINTED CIRCUIT BOARDS** by Stephen Ibbs 204
A fundamental look at how to etch your own boards
- DOWN TO EARTH** by George Hylton 209
Operational Amplifiers: theory and applications
- CIRCUIT EXCHANGE** 210
A forum for readers' ideas
- PLEASE TAKE NOTE** 210
Sound Operated Flash; Headlight Activated Switch;
Digital Electronics; Motorcycle Codelock (Circuit Exchange)
- EVERYDAY NEWS** 216
What's happening in the world of electronics
- FOR YOUR ENTERTAINMENT** by Barry Fox 224
Manual for Divorce; Reverse Charge; Hot Line
- COUNTER INTELLIGENCE** by Paul Young 229
A retailer comments
- NEW PRODUCTS** 235
Facts and photos of instruments, equipment and tools
- PRINTED CIRCUIT BOARD SERVICE** 236

Our May 1985 issue will be published on Friday, April 19.
See page 211 for details.

Readers' Services ● Editorial and Advertisement Departments 191

NEW THIS MONTH

"SENSING & CONTROL PROJECTS FOR THE BBC MICRO"

Have you ever wondered what all those plugs and sockets on the back of the BBC micro are for? This book assumes no previous electronic knowledge and no soldering is required, but guides the reader (pupil or teacher) from basic connections of the user sockets, to quite complex projects. The author, an experienced teacher in this field, has provided lots of practical experiments, with ideas on how to follow up the basic principles. A complete kit of parts for all the experiments is also available. Book, 245x185mm 120pp £5.95. Kit £29.95.

GREENWELD

— The Pack People! —

K524 OPTO PACK — a variety of single point and seven segment LEDs (individual types) of various colours and sizes, opto isolators, numicators, multi digit gas discharge displays, photo transistors, infra red emitters and receivers. 25 assorted £3.95; 100 £14.95; 250 £36.

K525 PRESET PACK — Big, Big variety of types and sizes — submin. min and std. MP, slider, multium and cermets are all included. Wide range of values from 20R to 5M. 100 assorted £6.75; 250 £12.95; 1000 £48.

K526 HEATSINK PACK — Lots of different sizes and shapes of heatsink for most diode and transistor case styles. A pack of 25 assorted including several large finned types — total weight over 1kg £5.50; 100 £19.50.

K528 ELECTROLYTIC PACK — All ready cropped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47µF to 1000µF. 6v to 100v £3.95; 250 £8.95; 1000 £32.

K531 PRECISION RESISTOR PACK — High quality, close tolerance R's with an extremely varied selection of values mostly 1/4 and 1/2w tolerances from 0.1% to 2% — ideal for meters, test gear etc. 250 £3; 1000 £10.

K532 RELAYS — Wide selection of styles, voltages and contacts. 4v-240v, AC/DC, SP to 4PCO. 20 for £6; 100 £25.

K517 TRANSISTOR PACK — 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114 117 172 182 183 198 239 251 214 255 320 BF 198 255 394 2N3904 etc. etc. Retail cost £7+; Special low price 275sp.

K523 RESISTOR PACK — 1000 — yes 1000 1/4 and 1/2 watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megohms. Only 250p; 5000 £10; 20,000 £36.

K520 SWITCH PACK — 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p.

K522 COPPER CLAD BOARD — All pieces too small for our etching kits. Mostly double-sized fibreglass 250g (approx 110 sq. ins.). For 100p.

K530 100 ASSORTED POLYESTER CAPS — All new modern components, radial and axial leads. All values from 0.01 to 1µf at voltages from 63 to 1000V Super value at £3.95.

K518 200 DISC CERAMIC CAPS — Big variety of values and voltages from a few pF to 2.2µF; 3v to 3kv £1.00.

K203 100 WIREWOUND RESISTORS — From 1w to 12w, with a good range of values £2.00.

K505 20 ASSORTED POTENTIOMETERS — All types including single, ganged, rotary and slider £1.70.

W4700 PUSH BUTTON BANKS — An assortment of latching and independent switches on banks from 2 to 7 way, DPCC to 6PCO. A total of at least 40 switches for £2.95; 100 £6.50; 250 £14.00.

Goods normally despatched by return of post.

Our shop has enormous stock of components and is open 9-5.30 Mon-Sat. Come and see us!

GREENWELD

All prices include VAT; just add 60p P&P. Min. Access order £5.00 No min. CWO value. Official orders from schools etc. welcome — min invoice charge £10.

1984/85 CATALOGUE

84 page A4 size — Bigger, Brighter, Better — more components than ever before! With each copy there's discount vouchers, Bulk Buyers List, Wholesale Discount List, Bargain List, Order Form and Reply Paid Envelope. All for just £1.00! Winter Supplement now out — Send large SAE for your free copy.

"TORUS"

Computer-controlled Robot built around the gearbox described below. Complete kit of parts inc. PCB, program listings for BBC (other micros shown). £44.85. 20W ribbon cable (min 3m recommended — 5m better) £1.30/m. SAE for illustrated leaflet.




MOTORIZED GEARBOX

The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors.

Two new types of wheels can be supplied (the aluminium discs and smaller plastic wheels are now sold out). Type A has 7 spokes with a round black tyre and is 100mm dia. Type B is a solid heavy duty wheel 107mm dia with a flat rigid tyre 17mm wide.

PRICES: Gearbox with data sheets: £5.95

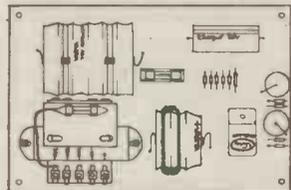Wheel type A: £0.70 ea
Wheel type B: £0.90 ea



NI-CAD CHARGER PANEL

177x114mm PCB with one massive Varta Deac 57x50mm Ø rated 7.2v 1000mAh and another smaller Deac 32x35mm Ø rated 3.6v 600mAh. The price of these Ni-cad stacks new is over £20. Also on the panel is a mains input charger transformer with two separate secondaries wired via bridge rectifiers, smoothing capacitors and a relay to the output taps. The panel weighs 1kgm. All this for just £6.00.

PCB MOUNTING NI-CADS

Much sought after 4.8V 150mA baits with PCB mntg tags on 25mm pitch. Batt size 25x16 Ø. Ideal for paralleling. 99p ea; 10+ 85p; 25+ 70p; 100+ 60p.

NI-CADS: AA 99p; C 199p; D 220p; PP3 395p.

1W AMPLIFIER

Z914 — Audio amp panel 95x65mm with TBA820 chip. Gives 1W output with 9V supply. Switch and vol. control. Just connect batt. and speaker. Full details supplied. Only £1.50; 10 for £12; 25 for £25; 100 £75.

AM TUNER PANEL

Z916 — For use with mono amp above. Neat panel 60x45mm. Only £1.50; 10 for £12.00.

FIBRE OPTICS

Scoop purchase of single and twin cable. For use with visible light or infra-red. Core 1mm dia, overall 2.25mm dia. Single 50p/m; 20m coil £6.30. Twin 90p/m; 20m coil £11.00.

A117 0.90	BC770 8.60	BU191 1.80	TA530 1.00	2N 3771 0.850	JAPANESE	PC685 0.420	LED
A119 0.990	BC771 8.100	BU126 7.000	TA540 1.000	2N 3772 0.850	TRANSISTORS	PC686 0.800	LED 3mm
A122 1.990	BC772 8.100	BU127 7.000	TA550 1.000	2N 3773 1.000	2A71 0.300	PCF200 1.350	RED 0.950
AC107 0.280	BD15 0.200	BU128 7.000	TA560 1.000	2N 4013 0.250	2A104 0.320	PCF801 1.100	LED 3mm
AC108 0.280	BD16 0.200	BU129 7.000	TA570 1.000	2N 4014 0.250	2A105 0.320	PCF802 1.100	YELLOW 0.124
AC127 0.150	BD124 1.100	BU208 0.800	TA820 0.750	2N 4017 0.250	2A203 0.300	PCF805 1.100	LED 3mm
AC128 0.150	BD128 0.350	BU209 0.200	TA830 1.000	2N 4018 0.250	2A204 0.300	PCF810 1.100	GREEN 1.000
AC129 0.150	BD129 0.350	BU210 0.200	TA840 1.000	2N 4019 0.250	2A205 0.300	PCF815 1.100	LED 5mm
AC12X 0.300	BD132 0.250	BU405 0.850	TA850 1.000	2N 4020 0.250	2A206 0.300	PCF820 1.100	RED 0.950
AC12X 0.300	BD135 0.250	BU407 0.750	TA860 2.000	2N 4021 0.250	2A207 0.300	PCF825 1.100	LED 5mm
AC13X 0.200	BD136 0.200	BU408 1.000	TA870 1.000	2N 4022 0.250	2A208 0.300	PCF830 1.100	RED 0.950
AC176 0.180	BD137 0.200	BU500 1.100	TA880 1.000	2N 4023 0.250	2A209 0.300	PCF835 1.100	LED 5mm
AC177 0.180	BD138 0.200	BU501 0.800	TA890 1.000	2N 4024 0.250	2A210 0.300	PCF840 0.550	YELLOW 1.000
AC178 0.180	BD139 0.200	BU525 0.800	TA910 1.000	2N 4025 0.250	2A211 0.300	PCF845 0.550	LED 5mm
AC179 0.180	BD140 0.200	BU527 0.800	TA920 1.000	2N 4026 0.250	2A212 0.300	PCF850 0.550	YELLOW 1.000
AC180 0.170	BD141 0.200	BU733 0.850	TA930 1.000	2N 4027 0.250	2A213 0.300	PCF855 0.550	LED 5mm
AC183 0.230	BD150 0.300	BU764 0.220	TA940 1.000	2N 4028 0.250	2A214 0.300	PCF860 0.550	GREEN 1.000
AC184 0.230	BD157 0.300	BU776 0.850	TA950 1.000	2N 4029 0.250	2A215 0.300	PCF865 0.550	LED 5mm
AC185 0.230	BD158 0.300	BU777 0.850	TA960 1.000	2N 4030 0.250	2A216 0.300	PCF870 0.550	RED 0.950
AC186 0.230	BD159 0.300	BU782 0.320	TA970 1.000	2N 4031 0.250	2A217 0.300	PCF875 0.550	LED 5mm
AC187 0.230	BD160 0.300	BU783 0.320	TA980 1.000	2N 4032 0.250	2A218 0.300	PCF880 0.550	RED 0.950
AC188 0.230	BD161 0.300	BU784 0.320	TA990 1.000	2N 4033 0.250	2A219 0.300	PCF885 0.550	LED 5mm
AC189 0.230	BD162 0.300	BU785 0.320	TA995 1.000	2N 4034 0.250	2A220 0.300	PCF890 0.550	RED 0.950
AC190 0.230	BD163 0.300	BU786 0.320	TA998 0.250	2N 4035 0.250	2A221 0.300	PCF895 0.550	LED 5mm
AC191 0.230	BD164 0.300	BU787 0.320	TA999 0.250	2N 4036 0.250	2A222 0.300	PCF900 0.550	RED 0.950
AC192 0.230	BD165 0.300	BU788 0.320	TA999 0.250	2N 4037 0.250	2A223 0.300	PCF905 0.550	LED 5mm
AC193 0.230	BD166 0.300	BU789 0.320	TA999 0.250	2N 4038 0.250	2A224 0.300	PCF910 0.550	RED 0.950
AC194 0.230	BD167 0.300	BU790 0.320	TA999 0.250	2N 4039 0.250	2A225 0.300	PCF915 0.550	LED 5mm
AC195 0.230	BD168 0.300	BU791 0.320	TA999 0.250	2N 4040 0.250	2A226 0.300	PCF920 0.550	RED 0.950
AC196 0.230	BD169 0.300	BU792 0.320	TA999 0.250	2N 4041 0.250	2A227 0.300	PCF925 0.550	LED 5mm
AC197 0.230	BD170 0.300	BU793 0.320	TA999 0.250	2N 4042 0.250	2A228 0.300	PCF930 0.550	RED 0.950
AC198 0.230	BD171 0.300	BU794 0.320	TA999 0.250	2N 4043 0.250	2A229 0.300	PCF935 0.550	LED 5mm
AC199 0.230	BD172 0.300	BU795 0.320	TA999 0.250	2N 4044 0.250	2A230 0.300	PCF940 0.550	RED 0.950
AC200 0.230	BD173 0.300	BU796 0.320	TA999 0.250	2N 4045 0.250	2A231 0.300	PCF945 0.550	LED 5mm
AC201 0.230	BD174 0.300	BU797 0.320	TA999 0.250	2N 4046 0.250	2A232 0.300	PCF950 0.550	RED 0.950
AC202 0.230	BD175 0.300	BU798 0.320	TA999 0.250	2N 4047 0.250	2A233 0.300	PCF955 0.550	LED 5mm
AC203 0.230	BD176 0.300	BU799 0.320	TA999 0.250	2N 4048 0.250	2A234 0.300	PCF960 0.550	RED 0.950
AC204 0.230	BD177 0.300	BU800 0.320	TA999 0.250	2N 4049 0.250	2A235 0.300	PCF965 0.550	LED 5mm
AC205 0.230	BD178 0.300	BU801 0.320	TA999 0.250	2N 4050 0.250	2A236 0.300	PCF970 0.550	RED 0.950
AC206 0.230	BD179 0.300	BU802 0.320	TA999 0.250	2N 4051 0.250	2A237 0.300	PCF975 0.550	LED 5mm
AC207 0.230	BD180 0.300	BU803 0.320	TA999 0.250	2N 4052 0.250	2A238 0.300	PCF980 0.550	RED 0.950
AC208 0.230	BD181 0.300	BU804 0.320	TA999 0.250	2N 4053 0.250	2A239 0.300	PCF985 0.550	LED 5mm
AC209 0.230	BD182 0.300	BU805 0.320	TA999 0.250	2N 4054 0.250	2A240 0.300	PCF990 0.550	RED 0.950
AC210 0.230	BD183 0.300	BU806 0.320	TA999 0.250	2N 4055 0.250	2A241 0.300	PCF995 0.550	LED 5mm
AC211 0.230	BD184 0.300	BU807 0.320	TA999 0.250	2N 4056 0.250	2A242 0.300	PCF1000 0.550	RED 0.950
AC212 0.230	BD185 0.300	BU808 0.320	TA999 0.250	2N 4057 0.250	2A243 0.300	PCF1005 0.550	LED 5mm
AC213 0.230	BD186 0.300	BU809 0.320	TA999 0.250	2N 4058 0.250	2A244 0.300	PCF1010 0.550	RED 0.950
AC214 0.230	BD187 0.300	BU810 0.320	TA999 0.250	2N 4059 0.250	2A245 0.300	PCF1015 0.550	LED 5mm
AC215 0.230	BD188 0.300	BU811 0.320	TA999 0.250	2N 4060 0.250	2A246 0.300	PCF1020 0.550	RED 0.950
AC216 0.230	BD189 0.300	BU812 0.320	TA999 0.250	2N 4061 0.250	2A247 0.300	PCF1025 0.550	LED 5mm
AC217 0.230	BD190 0.300	BU813 0.320	TA999 0.250	2N 4062 0.250	2A248 0.300	PCF1030 0.550	RED 0.950
AC218 0.230	BD191 0.300	BU814 0.320	TA999 0.250	2N 4063 0.250	2A249 0.300	PCF1035 0.550	LED 5mm
AC219 0.230	BD192 0.300	BU815 0.320	TA999 0.250	2N 4064 0.250	2A250 0.300	PCF1040 0.550	RED 0.950
AC220 0.230	BD193 0.300	BU816 0.320	TA999 0.250	2N 4065 0.250	2A251 0.300	PCF1045 0.550	LED 5mm
AC221 0.230	BD194 0.300	BU817 0.320	TA999 0.250	2N 4066 0.250	2A252 0.300	PCF1050 0.550	RED 0.950
AC222 0.230	BD195 0.300	BU818 0.320	TA999 0.250	2N 4067 0.250	2A253 0.300	PCF1055 0.550	LED 5mm
AC223 0.230	BD196 0.300	BU819 0.320	TA999 0.250	2N 4068 0.250	2A254 0.300	PCF1060 0.550	RED 0.950
AC224 0.230	BD197 0.300	BU820 0.320	TA999 0.250	2N 4069 0.250	2A255 0.300	PCF1065 0.550	LED 5mm
AC225 0.230	BD198 0.300	BU821 0.320	TA999 0.250	2N 4070 0.250	2A256 0.300	PCF1070 0.550	RED 0.950
AC226 0.230	BD199 0.300	BU822 0.320	TA999 0.250	2N 4071 0.250	2A257 0.300	PCF1075 0.550	LED 5mm
AC227 0.230	BD200 0.300	BU823 0.320	TA999 0.250	2N 4072 0.250	2A258 0.300	PCF1080 0.550	RED 0.950
AC228 0.230	BD201 0.300	BU824 0.320	TA999 0.250	2N 4073 0.250	2A259 0.300	PCF1085 0.550	LED 5mm
AC229 0.230	BD202 0.300	BU825 0.320	TA999 0.250	2N 4074 0.250	2A260 0.300	PCF1090 0.550	RED 0.950
AC230 0.230	BD203 0.300	BU826 0.320	TA999 0.250	2N 4075 0.25			

TOP SERVICE WITH LESS TO PAY THAT'S THE TK WAY.

TOP QUALITY COMPONENTS,
LOW PRICES, QUANTITY
DISCOUNTS, FAST SERVICE
FREE P&P OVER £20

LINEAR ICs			CMOS			OPTO			400V TRIACS			NICADS			D CONNECTORS				
555	21	ML526 1.80	4000	16	4028 45	3mm red	9	5mm red 9	4A	49	8A	58	PP3	3.95	C 12Ah 2.00	9w	15w	25w	
556	40	ML527 1.80	4001	18	4040 49	3mm green	12	5mm green 12	5A with diac	85	12A	85	AA	90	O 12Ahr 2.10	Plug	55	65	90
741	22	ML528 1.80	4002	18	4043 42	3mm yellow	12	5mm yellow 12	8A isolated	16A	95		Universal Charger	6.50		Socket	80	1.10	1.30
748	30	ML529 1.80	4007	16	4046 60	LED CLIPS	3		tab	65	25A	2.10	PP3 Charger	3.50		Cover	95	95	95
AD590	3.30	MM74C311 6.50	4011	18	4047 55			Rectangular, square, arrow or triangular (flat face)	8A sensitive gate		Diac	18				Right Angle Plug 15W			1.80
AY38910	3.90	MM74C315 96	4012	18	4049 32											Right Angle Socket 15W			2.10
CA3080	85	MM74C322 3.90	4013	25	4050 35	Red 15	Green 18	Yellow 18											
CA3130	95	MM74C326 4.00	4015	42	4066 55	Bicolour	65	Flashing LEDs											
CA3140	40	MS567 1.25	4016	30	4069 18	Tricolour	Red												
ICL7107	8.00	SS160 2.20	4017	39	4070 18	Round	32	Ref											
ICL7126	8.00	SS160 2.20	4019	28	4071 18	Rectangular	45	Continuous											
ICM7555	95	SAB0529 3.50	4023	16	4077 20	IL74TTL111	55	MOC-3020											
ICM9038	3.10	SA80600 2.50	4024	35	4081 16	IL074	1.70	MOC-3040											
LF351	40	SL440 1.95	4025	16	4093 35	ORP12	75	MEL11											
LF353	70	SL441 1.35	4026	70	4511 48			Seven Segment LED Displays											
LF356	80	SL486 1.85	4027	28	4514 1.00	DL704 3 cc	75	4-Dig 1.8" cc											
LM324	40	SL480 2.05				FN5000 5 ca	85	DIRECT DRIVE											
LM3342	85	TBARD00 7.0				FN5075 ca	85	Display											
LM3352	1.20	TBARD0AS 9.0																	
LM339	40	TDA1024 1.20																	
LM348	55	TDA4290 1.38																	
LM358	48	TL061 4.0																	
LM380	1.20	TL062 6.0																	
LM381	1.40	TL064 8.0																	
LM382	1.10	TL071 45																	
LM386	88	TL072 7.0																	
LM1035	3.95	TL074 1.30																	
LM1458	34	TL081 35																	
LM2917	1.90	TL082 48																	
LM3000	68	TL084 1.00																	
LM3905	80	TL170 5.0																	
LM3911	1.75	TL507C 1.20																	
LM3914	2.40	TMS1121 8.50																	
LM3915	2.40	TMS1601 9.50																	
LM13600	1.10	UA2740 1.45																	
LS710	4.75	ULN2003 75																	
LS720	2.75	ULN2004 75																	
LS725	2.60	ZN114 80																	
MF10C	2.97	ZN425 3.40																	
ML322	3.80	ZN427 5.70																	
ML324	2.50	ZN428 4.50																	
ML925	2.10	ZN1034E 1.90																	

MEMORIES

2715	3.10	2764	4.75
2732	3.20	5810	1.40

SCRs

CT1060	28	6A/50V	35
TC1060	40	6A/200V	35

CRYSTALS

32kHz	80	4.1943M	1.50
1.8432M	2.30	4.1952M	1.80
2.4576M	1.80	5.0M	1.30
3.2768M	1.60	6.144M	1.40
4.0M	1.20		

COMPUTER ICs

5802	2.45	6857	2.40
6809	4.95	Z80A CPU	1.55
6821	1.20	Z80A CTC	1.55
6850	1.50	Z80A PIO	1.55

IDC CONNECTORS

Rt. Ang. PCB Plug	Socket
20 way	90
26 way	100
34 way	1.10
40 way	1.30

SOCKETS

8 pin	7	22 pin	15
14 pin	8	24 pin	17
16 pin	10	28 pin	17
18 pin	12	40 pin	25
20 pin	14		
24 pin	3.20	40 pin	4.20

RIBBON CABLE

GREY per metre	Colour Coded
20 way	95 per metre
26 way	1.50 10 way 70
40 way	2.20 20 way 1.40

DIODES

1N4001	4	1N5401	11
1N4004	6	1N5404	13
1N4007	7	1N4148	3

SWITCHES

Push to Make	15
Push to Break	25
Push on/off (2A mains)	50
Sub. Mtn Toggle	
SPST	50 DPDT 65
DP Centre Off	75
Slider DPDT	15
DIL Switches:	
4 way	80 6 way 90
8 way	1.00
Rotary Switches	
1P12W	3P4W 4P3W 50

TRANSFORMERS

Chassis Mounting	
6.0 6V100mA	1.10
9.0 9V100mA	1.25
12.0 12V100mA	1.25
9.0 9V11A	2.30
12.0 12V11A	2.90
15.0 15V11A	3.40

BOXES

B1 75x56x35mm	85
B2 95x71x35	90
B3 115x95x37	1.10
B4 140x90x55	1.50
B5 207x122x77	2.75
B6 213x142x57	2.70

PRINTED CIRCUITS

Fibre-glass copper clad laminate	
Plan	Sensitised
160x100mm	80 1.80
220x100mm	1.55 2.30
Etch resist transfers:	
Pads, straight/curved tracks	
DI pads (state type)	
Ferric Chloride (250mL)	50
Etch Resist Pen	75
Titan 12V Drill	10.25
Reliant 9V Drill	6.90
Twist Drills	25

SPEAKERS

1.5in Bohm	78	2in Bohm	60
2.25in Bohm	60	2.5in Bohm	70
5.5in Bohm BW Horn			6.15
Crystal Earpiece			45
Magnetic Earpiece			25
Ultrasonic trans. (pair)			3.50
Crystal mic insert			50
Telephone pick up coil			65

BUZZERS

6v Metal 75	12V Metal	83
612V Plastic Electronic		75
Piezo low current 4mA at 12V		85
Piezo 240V ac		1.00
7-tune alarm unit		2.30

For **FREE** 28 page catalogue send 9x6 SAE today!
Telephone Orders Access & Barclay Card
RING 01-567 8910 (24Hrs)
Five Six Seven Eight Nine Ten

REGULATORS

78L05/12/15	30	7805/12/15	50
79L05/12/15	55	7905	55
Variable LM723	40		
LM317T	85	LM338K(ISA)	5.00

KITS

CT1000K	Clock/Timer	£14.90
CT1000KB*	Clock/Timer + Box	£17.40
KK101	Electronic Lock	£11.50
KK102*	3-Note Door Chime	£5.50
KK104	Solid State Switch	£2.40
KK112	Mains Wiring Remote Control	£42.00
KK113	MLR Radio	£5.50
TD300K†	300W Touchdimmer	£7.75
TS300K†	300W Touchswitch	£7.75
LD300K†	300W Lightdimmer	£3.95
TDR300K†	IR Remote Controlled Lightdimmer	£14.95
MK6*	IR Transmitter for TDR300K and MK7	£4.50
TDE/K†	Touchdimmer extension	£2.50
TA300K†	Time Delay Touch Switch (300W)	£5.00
MK1	Thermostat	£4.60
MK2	Solid State Relay	£2.60
MK4	Proportional Temperature Controller	£6.50
MK5	Mains Timer (1KW)	£4.50
MK7	Single Channel Infra Red Receiver (I240V)	£10.60
MK16	Mains Powered IR Transmitter	£3.50
MK17	Single Channel Infra Red Receiver (12V)	£10.50

* Includes box. † Includes front panel.
All kits include PCBs, components and assembly instructions.
For further details send S.A.E.

DISCO LIGHTING KITS

DL1000K	- This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel.	£15.95
DL21000K	- A lower cost uni-directional version of the above. Zero switching to reduce interference.	£8.95
Optional opto input	allowing audio 'beat'/light response (DLA/1)	70p
DL3000K	- 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel.	£12.95

MICROPROCESSOR TIMER KIT

Designed to control 4 outputs independently switching on and off at preset times over a 7 day cycle. LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back up circuit. Includes box. 18 time settings.

CT6000K **£39.00**

XX114 Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A 240V c/o contacts.

701 115 Additional Relays **£1.65**

LCD DIGITAL MULTIMETERS

LOW COST! 10M ohm, 3 1/2 digit 0.4 in display. Auto zero and polarity, low batt. indication, overload protection. Includes test leads, battery, spare fuse, manual, carrying case.

AC Volts: 0-200-500.
DC Volts: 0-2-20-200-1000.
DC Current: 0-20m-200mA.
Resistance: 0-2k-20k-200k-2M.
Size: 138 x 86 x 36mm. (405 202) **£25.95**

Professional - 10M, 0.5 in, 3 1/2 digit. Overrange and low battery indication. Overload protection. Includes leads, spare fuse, battery, manual and case. Transistor Checker. Size: 175 x 93 x 42mm.

AC Volts: 0-200-750.
DC Volts: 0-200m-2-20-200-1000.
DC Current: 0-20u-2m-20m-200mA, 0-10A.
Ohms: 0-200-2k-20k-200k-2M, 0-20M. (405 204) **£33.50**

PANTEC KITS

PN2	FM Micro Transmitter	£7.50
PN3	Stabilised Power Supply	£13.70
PN5	2-10w Stereo Amplifier	£14.50
PN6*	2-40w Stereo Amplifier	£24.95
PN7	Pushbutton Stereo Preamp	£12.80
PN8	Tone & Volume Control	£13.60
PN11	3w FM Transmitter	£11.95
PN13	Single Channel FM Transmitter	£9.80
PN14	Receiver for above	£15.50

DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°C. The kit has a sensitivity of 200mV for a full-scale reading automatic polarity and overload indication. Typical battery life of 2 years (PP

FREE



Practical Wireless
THE RADIO MAGAZINE

MAGNIFYING LENS

Also

- **Direct Conversion Receiver** A high-performance design for the 3.5 and 14 MHz amateur bands.
- **Amateur Bands Occupancy** An analysis of activity on the 3.5 and 7 MHz bands.



OUT NOW!

TELEVISION/COMPUTER FULL-TIME TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN
EDUCATION COUNCIL)

2 YEAR

BTEC National Diploma (OND)

**ELECTRONIC &
COMMUNICATIONS ENGINEERING**

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate (ONC)

ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate (ONC)

COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS

BTEC Higher National Certificate (HNC)

COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

**THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED
PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS**

**SHORTENED COURSES OF FROM 3 TO 6 MONTHS CAN BE ARRANGED FOR
APPLICANTS WITH PREVIOUS ELECTRONICS KNOWLEDGE**

NEXT TWO SESSIONS COMMENCE ON

APRIL 22nd & SEPTEMBER 16th

FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE (Dept EE)

20 PENYWERN ROAD, EARLS COURT,

LONDON SW5 9SU. Tel: 01-373 8721.



METERS: 110 x 82 x 35mm
30µA, 50µA, 100µA. **£8.45**
Post 50p.

METERS: 45 x 50 x 34mm
50µA, 100µA, 1mA, 5mA, 10mA,
25v, 1A, 2A, 5A, 25V.
£4.32. Post 30p.

METERS: 60 x 47 x 33mm
50µA, 100µA, 1mA, 5mA, 10mA,
100mA, 1A, 2A, 25v, 50v,
50-0-50µA, 100-0-100µA. **£7.25**.
VU meters **£6.04**.

Post on above meters 30p.

Silicone grease 50g £1.32.

Post 16p.

**NI-CAD BATTERY
CHARGER**

Led indicators charge-test
switch. For PP3, HP7, HP11 &
HP2 size batteries.

Price **£6.40**. Post 94p.

Motorola Piezo Ceramic Tweeter
£5.52 Post 33p

METERS: 60x46x33mm
illuminated. Require 6V supply.
50µA, 100µA, 500µA,
100-0-100µA,
1mA, 1A, 2A, 25V, 30V & VU.
£5.44 post 30p

ALSO IN STOCK

2, 3, 4, 6 & 8A Transformers

TRANSFORMERS

240v Primary

3-0-3v	100mA	85p
6-0-6v	100mA	£1.38
6-0-6v	250mA	£1.52
12-0-12v	50mA	£1.32
12-0-12v	100mA	£1.40
9-0-9v	75mA	£1.40
9-0-9v	250mA	£1.52

Post on above transformers 48p.

9-0-9v	1A	£2.37
12-0-12v	1A	£2.95
15-0-15v	1A	£3.45
6-0-6v	1½A	£2.38

Post on above transformers 94p.

**Rotary Switches: 1 Pole 12
Way 2P6W, 3P4Way, 4P3W 42p**
Post 16p

Illuminated Rocker Switch
240V 6A Red **88p** Post 16p

All above prices include V.A.T. Send £1 for a new comprehensive
1983/84 fully illustrated catalogue with a new price list. Send S.A.E. with
all enquiries. Special prices for quantity on request.

All goods despatched within 3 days from receipt of the order.

*Catalogue Owners: Please send large s.a.e. for new prices coming in
force 1.11.84*

M. DZIUBAS
158 Bradshawgate, Bolton,
Lancs. BL2 1BA.

Rapid Electronics

MAIL ORDERS:
Unit 3, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
Tel. Orders: Colchester (0206) 36412.
Telex: 987756.

ACCESS AND
BARCLAYCARD
WELCOME

MIN. D CONNECTORS

9 way 15 way 26 way 37 way
Plugs solder lugs 50p 65p 90p 150p
Right angle 90 135p 200p 350p
Sockets solder lugs 80p 100p 135p 260p
Right angle 120p 180p 290p 420p
Covers 100p 90p 100p 110p



SOLOERING IRONS

Antex CS 17W Soldering iron	430
2.5 x 1.1 3mm bits to suit	95
Antex XS 25W soldering iron	530
3.3 and 4.7mm bits to suit	85
Solder pump desoldering tool	480
Spore nozzle for above	70
10 metres 22 awg solder	100
10 way gery ribbon	100
0.5kg 22 awg solder	750

CABLES

20 metre pack single core connect-	75p
ing cable ten different colours.	
Shielded cable	10p/ft
Standard screened	15p/ft
6V Electronic buzzer	24p/m
12V Electronic buzzer	23p/m
10 way rainbow ribbon	26p/ft
20 way rainbow ribbon	47p/ft
10 way grey ribbon	14p/ft
20 way grey ribbon	28p/ft

HARDWARE

PP3 battery clips	8
Red or black crocodile clips	18
Black plastic control knob	18
Pr UltraSonic transducers	390
6V Electronic buzzer	65
12V Electronic buzzer	70
PP3270 Piezo transducer	75
64mm 54 ohm speaker	75
64mm 8 ohm speaker	75
20mm panel fuseholder	25
Red or black probe clip	33
4mm terminals	33
12 way 'chocolate' block	21
Ultra-min 6 or 12x1 rel. SPDT	130
ditto, but DPDT	195

CAPACITORS

Polyester, radial leads, 250V, C280	
type: 0.01, 0.016, 0.022, 0.033 -	
60p; 0.047, 0.068, 0.1 - 7p; 0.15,	
0.22 - 9p; 0.33, 0.47 - 13p; 0.68 -	
20p; 1u - 23p.	
Electronic, radial or axial leads:	
0.47/63V, 1/63V, 2.2/63V, 4.7/63V,	
10/25V - 7p; 22/25V, 47/25V - 8p;	
100/25V - 9p; 220/25V - 9p;	
470/25V - 22p; 1000/25V - 30p;	
2200/25V - 50p.	
Tag and power supply electrolytics:	
2200/40V - 110p; 4700/40V - 160p;	
2200/63V - 140p; 4700/63V - 230p	
Polyester, miniature SMDs: PCB:	
1n, 2n, 3n, 4n, 6n, 10n, 15n, 7p;	
20n, 33n, 47n, 68n, 80n, 100n, 9p;	
150n, 11p, 220p, 330p, 330p, 20p;	
470n, 22p; 680n, 25p; 1u; 33p;	

CONNECTORS

DIN Plug Skt Jack Plug Skt	
2 pin 9p 9p 2.5mm 10p 10p	
3 pin 12p 10p 3.5mm 9p 9p	
5 pin 13p 11p Standard 16p 20p	
Phono 10p 12p Stereo 24p 25p	
1mm 12p 13p 4mm 15p 17p	
UHF (CBI) Connectors:	
PL259 Plug 40p. Reducer 14p.	
SO239 square chassis skt 38p.	
SO295 round chassis skt 40p.	
IEC 3 pin 250V/6A.	
Plug chassis mounting	30p
Socket free hanging	36p
Socket with 2m lead	120p

TRANSFORMERS

3VA PCB Mounting	
2x6V@0.25A, 2x9V@0.15A	
2x12V@0.12A, 2x15V@0.1A 180p	
6VA PCB Mounting	
2x6V@0.5A, 2x9V@0.4A	
2x12V@0.3A, 2x15V@0.25A 270p	
Standard Chassis Mounting	
6VA: 2x6V@0.5A; 2x9V@0.4A	
2x12V@0.3A, 2x15V@0.25A 240p	
12VA: 2x6V@1A; 2x9V@0.6A	
2x15V@0.4A, 2x20V@0.3A 350p	

VERO

Verobloc	395
Veroboard Size 0.1 in matrix	
2.5 x 1.1	26
2.5 x 3.75	95
3.75 x 5	120
3.75 x 17	350
4.75 x 17	485
VPO board	190
Varcaps per 100:	
Single sided	15
Double sided	65
Spot face cutter	145
Pin insertion tool	185
Writing pen	375
Spore spool 75p	Combs 6

REGULATORS

78L05	30	79L05	45
78L12	30	79L12	45
78L15	30	79L15	45
7805	40	7905	45
7812	40	7912	45
7815	45	7915	45
LM317K	270	LM723	40
LM317T	90	LM7805	550
LM323K	420		

EURO CONNECTORS

Gold flashed	Plt. angle	Socket
3000 product lines at	wirecut	
64 way A+B	195	230
64 way A+C	220	270
96 way A+B+C	320	330

SWITCHES

Submin toggle:	
SPST 55p, SPDT 60p, DPDT 65p.	
Miniature toggle:	
SPDT 80p, SPDT centre off 90p.	
DPDT 90p, DPDT centre off 100p.	
Standard toggle:	
SPST 35p, DPDT 40p	
Miniature DPDT slide 14p.	
Push to make 15p.	
Push to break 22p.	
Rotary type adjustable stop:	
1P12W, 2P6W, 3P4W all 55p each.	
DIL switches:	
4PST 80c, 6PST 80p, 8PST 100p.	
Min. DPDT slide 14p, Push-make 15p.	

MICRO

2716	310	2712B-250	1225	6800	200	6522	330
2532	380	6118P3	390	6802	280	6532	520
2732	380	6264P15	2250	6809	600	6551	540
2732	380	4116P4	70	6810	140	8085A	320
2732	380	4164-15	480	6821	140	8156	380
2732	380	41256-15	2850	6840	360	8251	350
2732	380	41256-15	2850	6850	185	8253	370
2732	380	280A P10	320	6852	240	8255	320
2732	380	280A CTC	320	6875	500	8259	400
2764-250	430	280A D10	880	6880	100	MC1488	70
2764 BCC	430	280A SMD	880	6502	370	MC1489	70

DIODES

BY127	12	1N4001	3
0A47	10	1N4006	7
0A90	8	1N4007	7
0A11	7	1N5401	12
0A200	8	1N5404	18
0A202	8	1N5406	17
1N914	4	400M Zener	6
1N1483	3	1.3W zeners	13

DIODES

3mm red	8	5mm red	8
3mm green	11	5mm green	11
3mm yellow	11	5mm yellow	11
Clips to suit - 3p each.			
Rectangular:			
red	12	TIL111	60
green	17	TIL70	40
yellow	17	DRP12	85
ILD74	95	IL074	185
TIL38	35	TIL100	75
2N577	45	Tri-color Led 35	
Seven segment display:			
Com cathode	Com anode		
DL704.0.3	95	DL707.0.3	95
FND500.0.5	100	FND507.0.5	110
10 pin DIL LED display	red	180	
5mm superbright LED 250mcd	red	30	

TRIACS

400V 8A	85
400V 16A	95
400V 4A	50
50 BR100	25

NEW 1985 CATALOGUE

Our new fully illustrated 50 page detailed information on over 3000 product lines at the most competitive prices in the market. The catalogue costs just 70p including postage and free with orders over £20 in value. Send for your copy today!

SOCKETS

8 pin	7p	28p
14 pin	8p	45p
16 pin	10p	55p
18 pin	12p	60p
20 pin	13p	68p
22 pin	15p	75p
24 pin	17p	82p
28 pin	15p	95p
40 pin	25p	135p
Professional ZIF sockets		
24 pin 430p	28 pin 480p	
40 pin 595p		

COMPONENT KITS

0.25W Resistor Kit. Contains 1000 0.25W 5% resistors from 4.7 ohms thru to 10M. Quantities depend upon popularity i.e. 10x10R, 30x470R, 30x10K, 25x470K. Ceramic capacitor Kit. Total of 250 miniature ceramic capacitors from 22p to 0.1u. Polyester capacitor Kit. Total of 110 miniature polyester capacitors from 0.01u to 0.47u. Preset Kit. Total of 110 miniature preset resistors from 100R to 1M. Horizontal mounting type. Radial Electrolytic Capacitor Kit. A pack containing a miniature cap from 1u to 2200u. Nut and Bolt Kit. Contains 800 assorted items. 100 each 68A 1/4in, 1/2in, nuts and washers, 48A 1/4in, 1/2in, nuts and washers. Just £3.20.

OPTO

3mm red	8	5mm red	8
3mm green	11	5mm green	11
3mm yellow	11	5mm yellow	11
Clips to suit - 3p each.			
Rectangular:			
red	12	TIL111	60
green	17	TIL70	40
yellow	17	DRP12	85
ILD74	95	IL074	185
TIL38	35	TIL100	75
2N577	45	Tri-color Led 35	
Seven segment display:			
Com cathode	Com anode		
DL704.0.3	95	DL707.0.3	95
FND500.0.5	100	FND507.0.5	110
10 pin DIL LED display	red	180	
5mm superbright LED 250mcd	red	30	

COMPUTER CONNECTORS

ZXB1 2 x 23 way edge connector	150
wire wrap for ZXB1	150
SPECTRUM 2 x 28 way edge connector	200
connector wire wrap	200
AMPHENOL PLUGS	
24 way IEEE IDC	450
36 way computer IDC	490

BRIDGE RECTIFIERS

2A 200V	40
4A 200V	45
6A 100V	80
6A 100V 95	
1A 50V	20
1A 400V	30
20 VM18 DIL 0.9A	50

IC CONNECTORS

PCB PCB Socket Edge	
Plug Plug Conn.	
St. Plt. St. Ang.	
10 way 70	70
16 way 75	80
20 way 80	130
28 way 100	110
34 way 115	130
40 way 140	145
50 way 165	165
60 way 195	200

LINEAR

IC7611	98	LM358	50	LM3915	265	LM557	130	TD1A024	115
ICL7621	190	LM377	210	LM1380	110	NE570	370	TLO61	40
555CMOS	80	LM380	80	MC1310	150	NE571	370	TLO62	65
556CMOS	150	LM381	150	MC1496	70	NE5532	106	TLO64	105
709	38	LM382	130	MC3302	75	NE5534	105	TLO71	38
741	16	LM384	140	MC3340	65	TL072	65	TLO72	65
749	35	LM385	90	MC3341	30	RC455N	330	TLO74	110
AY31270	720	LM387	120	ML322	180	SL486	195	TLO81	30
AY38910	390	LM390	60	ML924	290	SL490	220	TLO82	50
AY38912	430	LM391	40	ML925	290	SN76018	150	TLO84	105
CA3046	65	LM393	60	ML928	210	SP26477	380	TL170	50
CA3048	65	LM394	60	ML929	210	SP26478	380	TL240	140
CA3089	200	LM395	70	ML928	210	SN76642	425	ULN2003	80
CA3090AD	375	LM397	30	ML929	210	Speech data 50	ULN2004	80	
CA3103E	85	LM398	60	ML929	225	TBA800	70	XR2206	365
CA3140E	38	LM398	135	ML948	35	TBA810	90	ZN414	90
CA3180	95	LM399	60	ML948	170	TBA820M	65	ZN423	135
CA3136	100	LM2017N8	195	NE555	20	TBA820	220	ZN424P</	

E.E. PROJECT KITS

Full Kits inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.

If you do not have the issue of E.E. which includes the project - you will need to order the instruction reprint as an extra - 70p each. Reprints available separately - 70p each + p&p 60p.

INSULATOR TESTER Apr. 85	£16.96
LOAD SIMPLIFIER Feb. 85	£16.98
WASHING MACHINE ALERT Feb. 85	less thermostat £5.45
MAINS MONITOR Feb. 85	£9.49
COMPUTERISED TRAIN CONTROLLER Feb. 85	£27.73
SOLID STATE REVERB Feb. 85	£39.98
MIC PRE-AMP Jan. 85	£4.87
GAMES TIMER Jan. 85	£7.23
SPECTRUM AMPLIFIER Jan. 85	£5.98
TV AERIAL PRE-AMP Dec. 84	£12.36
Optional PSU 12V £2.03.	240V £9.86
MINI WORKSHOP POWER SUPPLY Dec. 84	£34.98
DOOR CHIME Dec. 84	£14.91
FLUID DETECTOR Nov. 84	£8.73
BBC MICRO AUDIO-STORAGE SCOPE INTERFACE Nov. 84	£28.77
DIGITAL MULTIMETER Nov./Dec. 84	£78.95
PROXIMITY ALARM Nov. 84	£17.98
MAINS CABLE DETECTOR Oct. 84	£4.39
MICRO MEMORY SYNTHESIZER Oct. 84	£47.98
DRILL SPEED CONTROLLER Oct. 84	£6.89
GUITAR HEAD PHONE AMPLIFIER Sept. 84	£6.38
OP-AMP POWER SUPPLY Sept. 84	£21.96
SOUND OPERATED FLASH less lead Sept. 84	£5.91
TEMPERATURE INTERFACE FOR BBC MICRO Aug. 84	£19.70
CAR RADIO BOOSTER Aug. 84	£13.87
THERMOSTATIC SEED PROPOGATOR Aug. 84	needs 12V supply £7.99
KITCHEN APPLIANCE TIMER Aug. 84	less socket £17.26
WASHER FLUID MONITOR Aug. 84	£5.28
ULTRASONIC BURGLAR ALARM July 84	inc relay + sounder £28.40
CAR LIGHTS WARNING July 84	£7.99
SPEECH SYNTHESIZER June 84	£29.22
VARI-CAP AM RADIO May 84	£10.43
EXPERIMENTAL POWER SUPPLY May 84	£18.72
SIMPLE LOOP BURGLAR ALARM May 84	£13.62
MASTERMIND TIMER May 84	£5.44
FUSE/DIODE CHECKER Apr. 84	£3.45
QUASI STEREO ADAPTOR Apr. 84	£10.90
DIGITAL MULTIMETER add on for BBC Micro Mar. 84	£24.98
NI-CAD BATTERY CHARGER Mar. 84	£9.85
REVERSING BLEEPER Mar. 84	£6.78
DIN LEAD TESTER Mar. 84	£8.32
PIPE FINDER Mar. 84	£3.60
LOW POWER STEREO AMP Mar. 84	£27.88
IONISER Feb. 84	£23.98
ZX81 EPROM PROGRAMMER Feb. 84	£14.48
SIGNAL TRACER Feb. 84	£14.89
CAR LIGHT WARNING Feb. 84	£3.76
GUITAR TUNER Jan. 84	£17.73
BIOLOGICAL AMPLIFIER Jan. 84	£19.16
CONTINUITY TESTER Dec. 83	£9.99
CHILDREN'S DISCO LIGHTS Dec. 83	£8.42
NOVEL EGG TIMER Dec. 83	inc. case £10.24
SPEECH SYNTHESIZER FOR THE BBC MICRO Nov. 83	less cable + sockets £21.98
MULTIMOD Nov. 83	£16.98
LONG RANGE CAMERA/FLASHGUN TRIGGER Nov. 83	£13.50
HOME INTERCOM less link wire Oct. 83	£14.38
SHORT WAVE RADIO less 'phones' Oct. 83	£25.63
Mono headphones extra	£3.36
DIGITAL TO ANALOGUE BOARD Oct. 83	£19.98
less cable, case + connector	
HIGH POWER DAC DRIVER BOARD Oct. 83	less case £12.52
A TO D CONVERTER FOR RM3802 Sept. 83	inc plug £35.98
HIGH SPEED A TO D CONVERTER Sept. 83	less cable + connector £27.98
SIGNAL CONDITIONING AMP Sept. 83	no case £8.98
STORAGE SCOPE INTERFACE FOR BBC MICRO Aug. 83	less software £15.38
PEDESTRIAN CROSSING SIMULATION BOARD Aug. 83	no case £10.29
HIGH POWER INTERFACE BOARD Aug. 83	no case £10.38
CAR INTRUDER ALARM Aug. 83	£16.98

USER PORT I/O BOARD less cable + plug	£10.49
USER PORT CONTROL BOARD July 83	less cable + plug + case £25.14
ENVELOPE SHAPER Jun. 83	less case £12.33
MODEL TRAIN CONTROLLER May 83	£27.17
GUITAR HEADPHONE AMPLIFIER May 83	£7.92
MW PERSONAL RADIO less case, May 83	£7.62
MOISTURE DETECTOR May 83	£5.46
CAR RADIO POWER BOOSTER April 83	£11.99
FUNCTION GENERATOR April 83	£45.98
FLANGER SOUND EFFECTS April 83	£24.17
NOVELTY EGG TIMER April 83	less case £5.48
ZX SPECTRUM AMPLIFIER April 83	£9.87
DUAL POWER SUPPLY March 83	£59.38
BUZZ OFF March 83	£4.51
PUSH BIKE ALARM Feb. 83	£11.73
DOUBLE DICE Jan. 83	£13.90
ZX TAPE CONTROL Nov. 82	£7.13
SINE WAVE GEN Oct. 82	£16.11
G. P. PRE-AMP Oct. 82	£6.09
LIGHTS ON ALERT Oct. 82	£4.68
CONTINUITY CHECKER Sept. 82	£5.47
SOUND SPLITTER Sept. 82	£17.35
SOUND RECOMBINER Sept. 82	£4.07
SCREEN WASH DELAY Sept. 82	£4.93
CB ROGER BLEEPER Aug. 82	£9.32
2-WAY INTERCOM July 82	no case £4.52
ELECTRONIC PITCH PIPE July 82	£5.40
REFLEX TESTER July 82	£7.77
SEAT BELT REMINDER Jun. 82	£4.10
EGG TIMER Jun. 82	£5.44
CAR LED VOLT/METER less case, May 82	£23.18
V.C.O. SOUND EFFECTS UNIT Apr. 82	£12.71
CAMERA OR FLASH GUN TRIGGER Mar. 82	£13.65 less tripod bushes £4.10
POCKET TIMER Mar. 82	£4.10
GUITAR TUNER Mar. 82	£17.19
SIMPLE STABILISED POWER SUPPLY Jan. 82	£26.96
MINI EGG TIMER Jan. 82	£4.40
SIREN MODULE Jan. 82	less speaker £6.10
MODEL TRAIN CHUFFER Jan. 82	£9.98
SIMPLE INFRA RED REMOTE CONTROL Nov. 81	£18.70
CAPACITANCE METER Oct. 81	£25.81
SUSTAIN UNIT Oct. 81	£13.99
TAPE NOISE LIMITER Oct. 81	£4.98
HEADS AND TAILS GAME Oct. 81	£2.75
CONTINUITY TESTER Oct. 81	£4.48
PHOTO FLASH SLAVE Oct. 81	£3.80
FUZZ BOX Oct. 81	£7.98
SOIL MOISTURE UNIT Oct. 81	£5.39
KC ALARM Oct. 81	£8.70
0-12V POWER SUPPLY Sept. 81	£19.48
CMOS CAR SECURITY ALARM Sept. 81	£9.95
CMOS DIE Sept. 81	£8.80
CMOS METRONOME Aug. 81	£8.99
COMBINATION LOCK July 81	less case £21.58
SOIL MOISTURE INDICATOR E.E. May 81	£4.49
GUITAR HEADPHONE AMP E.E. May 81	£4.66
PHONE BELL REPEATER/BABY ALARM May 81	£5.15
INTERCOM April 81	£24.43
SIMPLE TRANSISTOR & DIODE TESTERS Mar. 81	Ohm meter version £2.22 Led version £2.98
LED DICE Mar. 81	£9.35
MODULATED TONE DOORBELL Mar. 81	£7.35
2 NOTE DOOR CHIME Dec. 80	£11.35
LIVE WIRE GAME Dec. 80	£18.87
GUITAR PRACTICE AMPLIFIER Nov. 80	£14.10 less case, Standard case extra £4.99
SOUND TO LIGHT Nov. 80	3 channel £23.40
TRANSISTOR TESTER Nov. 80	£12.80
AUDIO EFFECTS UNIT FOR WEIRD SOUNDS Oct. 80	£14.40
IRON HEAT CONTROL Oct. 80	£6.30
TTL LOGIC PROBE Sept. 80	£5.88
ZEPHYRUS TESTER Jun. 80	£7.30
LIGHTS WARNING SYSTEM May 80	£5.20
BATTERY VOLTAGE MONITOR May 80	£5.66
MICRO MUSIC BOX Feb. 80	£17.86
Case extra	£3.60
SLIDE/TAPE SYNCHRONISER Feb. 80	£13.50
MORSE PRACTICE OSCILLATOR Feb. 80	£4.98
SPRING LINE REVERB UNIT Jan. 80	£27.20
UNIBOARD BURGLAR ALARM Dec. 79	£6.70
DARKROOM TIMER July 79	£3.20
TRANSISTOR TESTER Apr. 79	£5.38
MICROCHROME DOORBELL Feb. 79	£17.48
SOUND TO LIGHT Sept. 78	£9.20
CAR BATTERY STATE INDICATOR less case Sept. 78	£2.29
R.F. SIGNAL GENERATOR Sept. 78	£31.20
IN SITU TRANSISTOR TESTER Jun. 78	£7.50
FLASHMETER less calc & diffuser May 78	£16.50
WEIRD SOUND EFFECTS GENERATOR Mar. 78	£6.20
AUDIO VISUAL METRONOME Jan. 78	£6.59
ELECTRONIC TOUCH SWITCH Jan. 78	£2.99
RAPID DIODE CHECK Jan. 78	£3.15
ELECTRONIC DICE Mar. 77	£4.96

THIS MONTH'S KITS SAE or 'phone for prices

OUR PRICES INCLUDE VAT

MAGENTA ELECTRONICS LTD.

EE27, 135 HUNTER ST.,
BURTON-ON-TRENT
STAFFS, DE14 2ST.
MAIL ORDER ONLY.
0283 65435, Mon-Fri 9-5.
Access/Bardlaycard (Visa) by
phone or post.
24 hr Answerphone for credit card orders.

ADD 60P P&P TO ALL ORDERS.
PRICES INCLUDE VAT.
SAE ALL ENQUIRIES.
OFFICIAL ORDERS WELCOME.
OVERSEAS: Payment must be sterling.
IRISH REPUBLIC and BFPO: UK PRICES.
EUROPE: UK PRICES plus 10%.
ELSEWHERE: write for quote.



MAGENTA

We offer a range of superb Fischertechnik sets. These cover robotics, electronics, electromechanics, motors & gears, & basic construction.

Robotics kit: build 6 different working models including a robot arm, graphics board, sorting system etc. Note that not all the models can be built at the same time. Simple to assemble. Easily combined with all other Fischertechnik kits. Top quality. Includes 2 motors, an electromagnet, lamps, potentiometers, switches etc.

ROBOTICS kit (554)/E/E £64.99

Construction/base kit (ut1) £37.50

Motors & Gears (ut2) £42.70

Use ut2 to motorise ut1

Electromechanics (ut3) £73.20

Electronics (ut4) £93.90

Extra Lamps & Cables £5.95

Interfaces for the BBC & Spectrum

Computers. Interfaces are available for

controlling the Robotics kit (554),

and the motorised construction kit (ut1

& ut2). Details in our catalogue (£1

or see marked 'FT/EE' (state micro).



fischertechnik

TOOLS

ANTEX MODEL C IRON	£6.98
ANTEX XS SOLDERING IRON 25W	£7.25
ST4 STAND FOR IRONS	£2.85
HEAT SINK TWEEZERS	45p
SOLDER HANDY SIZE 5	£1.39
SOLDER CARTON	£2.50
SOLDER REEL SIZE 10	£4.67
LOW COST PLIERS	£1.98
LOW COST CUTTERS	£1.99
BENT NOSE PLIERS	£1.89
MINI DRILL 12V (MD1)	£8.38
MULTIMETER TYPE 1 1000opv	£6.98
MULTIMETER TYPE 2 20,000opv	£17.98
MULTIMETER TYPE 3 30,000opv	£27.98
MULTIMETER TYPE 4 10M DIGITAL	£39.98
DESOLDER PUMP	£5.48
SIGNAL INJECTOR	£2.98
CIRCUIT TESTER	78p
HELPING HANDS JIG & MAGNIFIER	£7.98
MINIATURE VICE (PLASTIC)	£1.85

ROBOTICS

DIY ROBOTICS & SENSORS BOOKS - with the BBC £7.95; for the Commodore 64 £7.99. Components used in these books are in our catalogue/price list. Catalogue £1. Price list only sale.

SAA1027 driver £5.99; 8 way darlington driver (ULN2803) £2.38; TL081 49p.

ID35 STEPPER MOTOR, 48 Steps, 12V. £14.50

BBC TO ID35 STEPPER MOTOR INTERFACE KIT £13.99

PCB, driver IC, components, connectors & leads included. Demonstration software listings, circuit diagram, pcb layout & construction details given. Requires unregulated 12V dc power supply.

INTERFACE KIT (ref EE) £13.99

OPTIONAL POWER SUPPLY PARTS £4.67

HOW TO MAKE COMPUTER CONTROLLED ROBOTS by Potter/Oxlade, BOOK £3.20. For BBC, Spectrum, C64 & VIC20.

Make a mobile arm robot from simple materials. Electronic parts etc. available from Magenta. Ideal for age 11 upwards & all beginners. Also similar to above HOW TO MAKE COMPUTER MODEL CONTROLLERS, BOOK £3.19.

COMPONENTS

We stock a standard range of electronic components including resistors, pots, ICs, capacitors, relays, transformers, switches, connectors, wire, cases, speakers & breadboards. Full details are in our catalogue. £1.

COMPUTER ACCESSORIES



BBC TRACKBALL CONTROLLER, 2" ball, 2 fire buttons. Analogue input port connector. Includes simple software listing for freehand drawing. Simply incorporates into your programs. £17.98

BBC Digital Joystick. 2 fire buttons. D plug connects to analogue Input. £9.59

ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-DC Breadboard. Gives clear instructions with lots of pictures. 16 projects - including three official, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-DC breadboard and all the components for the projects. Adventures with Electronics £3.58. Component pack £20.98 less battery.

BOOKS

110 Electronic Alarm Projects	£5.98
50 CMOS IC Projects, 244	£1.85
52 Projects Using IC 741, BP24	£1.95
A Practical Introduction to Digital ICs, 225	£1.90
Beginners' Guide to Building Electronic Projects-227	£2.25
Practical Things To Do with a Microcomputer	£2.19
Questions & Answers - Electronics	£3.45
Basic Electronics	£8.98
Burglar Alarm Systems, Cape!	£5.95
Digital IC Projects, BP84	£2.10
Electronic Music & Creative Tape Recording, BP51	£2.10
Electronic Music Projects, BP74	£2.05
Electronic Projects for Beginners, BP48	£2.10
Electronic Projects in Music, Find	£4.55
Electronic Projects in Photography	£4.55
Electronic Science Projects, BP104	£2.25
Electronic Security Devices, BP56	£2.10
Electronic Test Equipment Construction, BP75	£2.05
Handbook of ICs, Equiv. & Subs, 202	£2.15
How to Build Your Own Metal & Treasure Locators, BP32	£2.15
How to Build Your Own Solid State Oscilloscope, BP57	£2.15
How to Get Your Electronic Projects Working, BP110	£2.15
How to Identify Unmarked ICs, BP101	70p
How to Make Walkie-Talkies, BP43	£2.10
IC Projects for Beginners, BP97	£2.15
Interfaces to Microprocessors & Microcomputers	£6.50
International Diode Equiv Guide, BP108	£2.45
Microprocessors for Hobbyists	£4.98
Micro Disc Handbook, BP47	£1.50
Power Supply Projects, BP76	£1.95
Practical Construction of Pre-amps, tone controls, filters & atten, BP60	£2.10
Radio Control for Beginners, BP79	£2.05
Simple LED Circuits - Book 2, BP87	£1.50

FUN WITH ELECTRONICS

Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners - children and adults. Only basic tools needed. 64 full colour pages cover all aspects - soldering - fault finding - components (identification and how they work).

Also full details of how to build 6 projects - burglar alarm, radio, games, etc. Requires soldering - 4 pages clearly show you how.

COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.

Supplied less batteries & cases.

FUN WITH ELECTRONICS, COMPONENT PACK £16.98

BOOK EXTRA £1.75.

Book available separately.

TEACH IN 84

Full kit including 2 EBBO breadboards & a FREE copy of our catalogue. TEACH IN 84 KIT £22.98 inc VAT. Reprints 70p each (12 part series).

CATALOGUE

FULLY REVISED 1985 CATALOGUE. Brief details of each kit, our books, & illustrations of our range of tools & components. Also stepper motor, interface kit & simple robotics. Plus circuit ideas for you to build. If you read Everyday Electronics than you need a copy of the MAGENTA catalogue.

CATALOGUE & PRICE LIST - Send £1 in stamps etc. or add £1 to your order. Price list - 9x4 size.

Catalogue FREE TO SCHOOLS/COLLEGES REQUESTED ON OFFICIAL LETTERHEAD.

EVERYDAY ELECTRONICS and computer PROJECTS

VOL 14 No 4

APRIL '85

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

COMPONENT SUPPLIES

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

OLD PROJECTS

We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used.

We regret that we **cannot provide data or answer queries on projects that are more than five years old**.

SUBSCRIPTIONS

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £13.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

BACK ISSUES & BINDERS

Certain back issues of EVERYDAY ELECTRONICS are available world-wide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

Binders to hold one volume (12 issues) are available from the above address for £5.50 inclusive of postage and packing worldwide.

PCBs

OVER THE past few years more and more EE projects have been built on printed circuit boards rather than Veroboard or any other constructional form. The introduction of the p.c.b. service has encouraged readers to build using this method and we also supply boards to companies, education departments and training establishments both in the UK and around the world.


Of course p.c.b.s are used in virtually all forms of commercial equipment, they are very reliable, make wiring up easier, help to eliminate mistakes, enable easier checking and usually result in a neater job. This does not mean that there is no place for Veroboard or plug-in breadboarding systems; they continue to provide excellent means of building prototype and one off units and Veroboard is particularly suitable for hobby electronics.

In this issue we take a look at how the hobbyist can make his own p.c.b.s, either from our designs or to meet his own requirements. Even if you never intend to make your own board this article is well worth reading since an understanding of the principles involved in p.c.b. manufacture is always good background knowledge for the user.

FIBRELARM

The *Fibrelarm* published in this issue is a development of a Bike-A-Larm which won Gideon Tearle his second consecutive prize in the Schools Design Prize competition organized by The Design Council and sponsored by Thorn EMI. Gideon, who is 14, has designed the first EE project to use fibre optics. The use of the optical fibre in this application is an excellent idea and prevents anyone shorting and cutting the loop, as they could with a wire loop. *Fibrelarm* is very secure and, since it can operate a large loop, is also versatile.

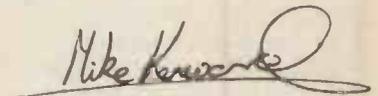We are pleased to be able to encourage such designs and hopefully help a little by publishing the results. It is apparent that EE plays an important part in the dissemination of information and ideas in electronics, particularly in the educational areas. We intend to continue this and indeed develop our involvement in this important sector.



Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL, WESTOVER HOUSE,
WEST QUAY ROAD, POOLE, DORSET BH15 1JG

Phone: Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone

Editor
MIKE KENWARD

Secretary
PAULINE MITCHELL
0202 671191 Ext 259

Advertisement Manager
NIGEL BELLWOOD 01-261 6882

Advertisement Sales Executive
RICHARD WILLETT 01-261 6745

Classified Supervisor
BARBARA BLAKE 01-261 5897

Advert Make-Up and Copy Department
JULIE FISH 01-261 6615

Advertisement Offices
EVERYDAY ELECTRONICS
ADVERTISEMENTS
KING'S REACH TOWER
STAMFORD STREET,
LONDON SE1 9LS
Telex 915748 MAGDIV-G



CYBERVOX ROBOT VOICE

JOHN M.H. BECKER

AS ANY ANDROID knows, cybernetics is a multilimbed field that also includes robotics. Amongst themselves robots probably banter together in a high speed din of binary, but for human-robot chatting, a vocal interface is needed. The "Cybervox" is just such an interface. Translational confrontations are catered for by producing variations of the Dalek dialect, the cavernous cyborg lingo, and some unidentified alien gibberish just in case.

This multi-lingual module consists of a ring modulator, a reverb unit and a voice gate, with five panel controls and two switches to select the desired vernacular. It is battery powered and can be used with many different speech sources including most microphones, cassette decks and pre-amplifiers. Budding robot communicators are referred to the block diagram in Fig. 1.

GENERAL DESCRIPTION

A voice signal is brought into either the high or the low level input socket, pre-amplified at an adjustable gain level, fed to the ring modulator controlled by the variable speed and depth low frequency oscillator. The modulated signal then passes through the mixer to the delay stage through which it travels at a variable rate determined by the frequency of the high speed oscillator.

From there it goes to the first of two filter stages where a proportion can be fed back to the delay loop via the mixer. It also passes through the second filter, and on to the voice gate. This consists of two sections, the first being the gate open-close control activated by the signal from the second pre-amp stage, and the other being the gate itself conducting the processed signal through at a level determined by the control section. The final signal can be fed to a normal amplifier system.

INPUT STAGE

Low level voice signals from sources such as microphones are brought in to the first pre-amp stage IC1a where the gain is set at roughly 100 by the relationship of R2 to R3. From here they go to the

second pre-amp IC1b which also has a separate input, for higher level signals.

Since IC1b is connected as a mixer, signals from both inputs could be brought in simultaneously. It also acts as a gain stage and low pass filter restricting frequencies above the range set by C4 and C5, though the characteristics will be slightly modified by the setting of VR1.

At 200Hz the gain can be varied by VR1 from one-tenth to 10, at 1kHz the maximum gain is about 2.5. The pre-amplified signal is then split to the voice gate control stage, and to the ring modulator.

RING MODULATOR

This is the heart of the Dalek type voice production section. IC3 is a balanced modulator-demodulator chip that has two signal inputs and two carrier inputs. In this circuit only one of each is used for the signal and carrier, but the bias on their counterparts is also important for correct operation.

In simple terms, if a carrier frequency is modulated by another, the frequency at the two antiphase outputs will consist of the sum and the difference of the two. Under ideal conditions, suppose the carrier is at 3kHz and the modulating signal at 2kHz, the output will consist of 5kHz (3 + 2kHz) and 1kHz (3 - 2kHz). In reality life is never that simple and using voice frequencies that consist of numerous harmonics and odd waveforms, other combinations of composite waveforms are produced for a given carrier frequency.

With a low frequency carrier, say between 7Hz and 30Hz, variations on the Dalek modulation theme occur.


As the carrier increases so more exotic sounds are produced, gradually acquiring a "metallic" sort of audio fringe at carrier frequencies above the range set by C4 and C5, though the characteristics will be slightly modified by the setting of VR1. Beyond that they lose their intelligibility until by the maximum of 3.5kHz complete gibberish results.

The carrier frequency is generated by the oscillator around IC2a and IC2b. As the output of IC2a crosses the comparator trip point governed by R39-41 so IC2b changes its output state. C19 then varies its charge accordingly at a rate set by the total resistance of R42 and VR6, until the trip point is again crossed, whereupon the cycle reverses. The output from IC2a is a triangular waveform of some 2.5V peak-to-peak. The frequency range available is basically set by C19, which on its own offers a range of 200Hz to 3.5kHz. S1 can also switch in C18, which reduces the range to about 7Hz to 130Hz. The former range is more suited to exotic modulation effects, becoming unintelligible at the extreme limit, and the latter range more suited to Dalek-type vocalisations.

The output of IC2a is taken via C20 and the attenuator R43 to one carrier input of IC3. In the absence of a signal the two carrier inputs, pins 8 and 10 would be held similarly biased by the voltages applied by the equal resistance series R15/44, R16/45. If both inputs are held in exact equilibrium then the modulation signal from IC1b would have no effect and no output would be produced.



Fig. 1. Circuit diagram of main board and (below left) voice gate. Also block diagram, below right.

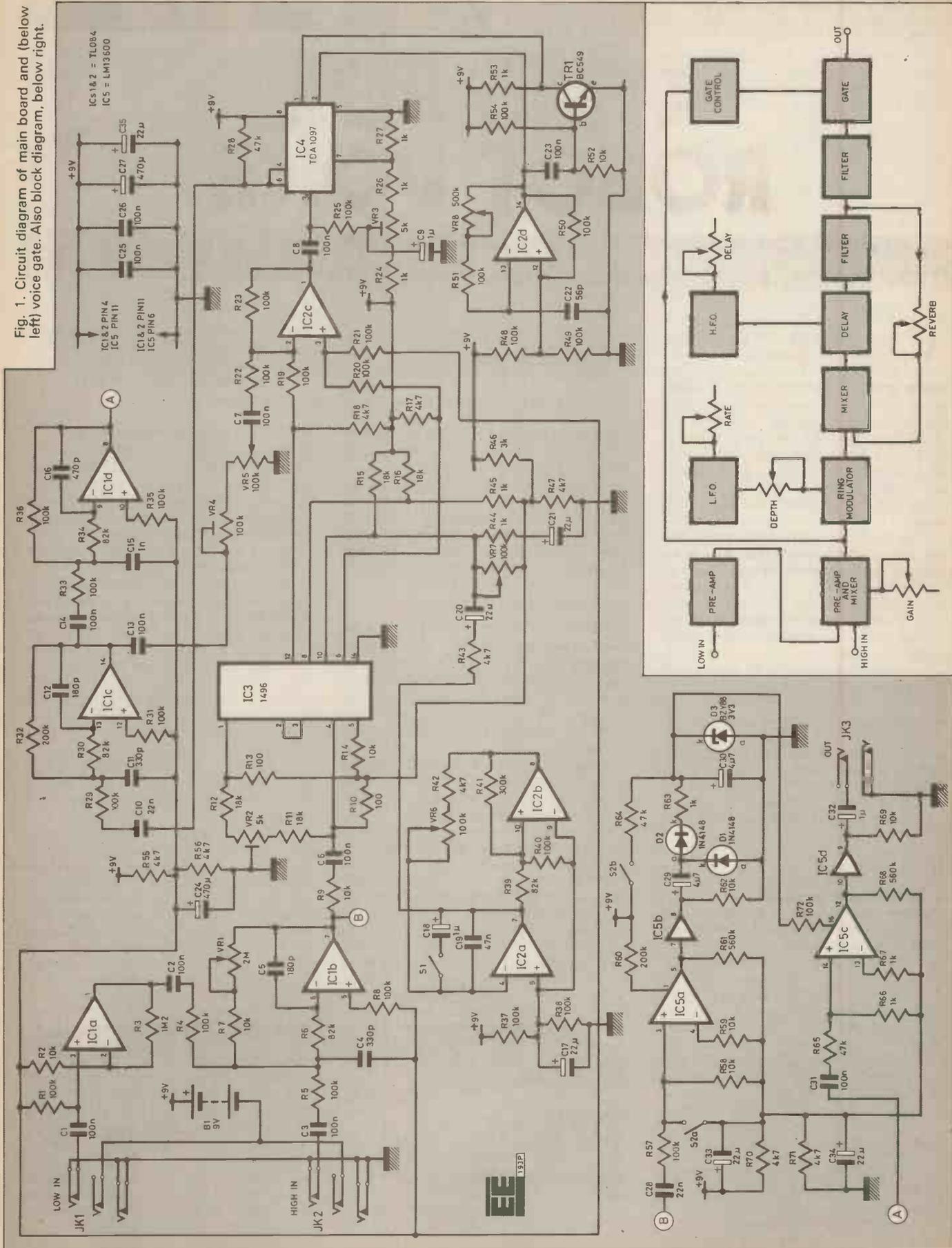

In the presence of a carrier signal or d.c. imbalance, the input signal from IC1b and the carrier interact and a composite output results. The modulation inputs, pins 1 and 4, are similarly held at equilibrium by the resistor series R12/13, and R11/10. VR2 is in series with both so that an exact balance point can be achieved. In the absence of a signal from IC1b, with the modulation inputs held in balance, the carrier signal from IC2a is not allowed to pass through.

In practice full suppression of the carrier signal is not possible, and at full carrier strength of 400mV about 10mV p-p breakthrough at each output of IC3 is likely to be experienced. The implications of this are discussed later. In this unit exact balancing of the carrier input bias is not required as it is desirable to be able to vary the emphasis of the carrier waveform, to the extent of removing it entirely allowing only the voice to pass through. VR7 is used as a variable parallel shunt; at maximum resistance it makes no significant difference to the potential drop at the junction of R15 and R44 and the maximum modulating strength is then governed by the ratio of R43 to R44.


As VR7 is reduced, so too is the carrier level by the diminishing drop across it and R44, and at the same time the balance between the two carrier inputs, pins 8 and 10, is modified. At minimum resistance of VR7, the carrier level is reduced to nil, and the imbalance between the two carrier inputs allows the voice signal to pass through without frequency modification.

The maximum amplitude available at the two outputs of IC3, pins 6 and 12, is governed by the degree of imbalance between the carrier inputs, the current through R14, and the value of the two load resistors R17 and R18. The two antiphase signals are then summed at the differential amplifier IC2c which also serves as a mixer to the feedback loop signal ultimately coming from VR5.

DELAY STAGE

To create a reverberation effect, a time delay has to be given to a signal that is then fed back upon itself. The output from IC2c goes to IC4 which is a 1536 stage delay chip. An optimum d.c. bias is required at its input in order to maintain an even waveform shape of the signal passing through. This bias is delivered from VR3 via R25. IC4 is a recently-introduced, but otherwise standard bucket-brigade device that passes a signal through each "bucket" stage at a rate set by a split-phase clock signal.

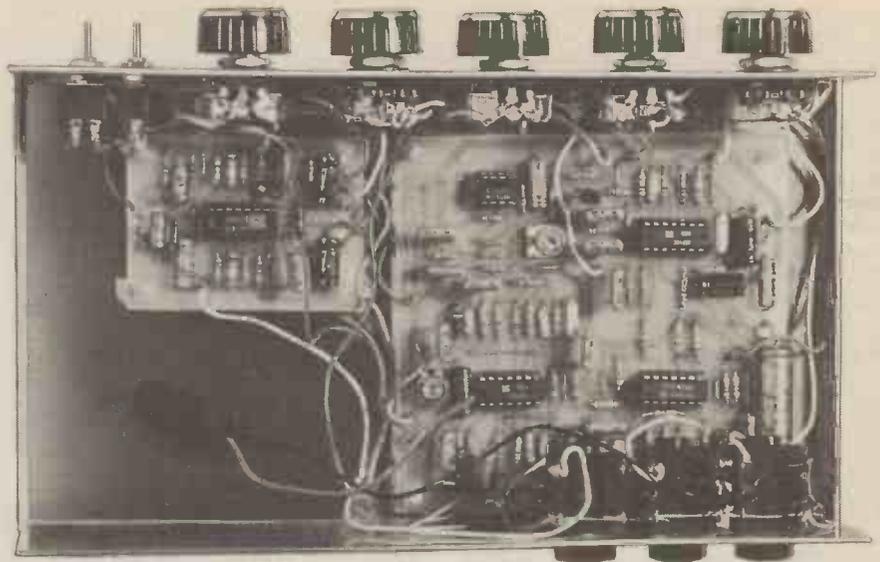The clock is generated by IC2d which is connected as a squarewave oscillator with a frequency set by C22 and its charging rate controlled by VR8 and R51. At maximum resistance of VR8, the clock frequency is at its slowest of around 13kHz, and the time delay in IC4 is at its longest of 59ms. The highest clock of 66kHz gives a delay time of 12ms. The



Internal view of the Cybervox Robot Voice with all interwiring complete.

exact delay in milliseconds for a given frequency can be calculated as—(number of delay stages/clock frequency in Hz) × 500. The antiphase counterpart to the clock is achieved by inverting the square wave at TR1. The amplitude imbalance between the two is unimportant in this instance. The twin outputs of IC4 are summed at R28 and sent for filtering in the circuit around IC1c.

FILTER STAGES

It is inherent in bucket-brigade delay line chips that a proportion of the clocking signal is carried over into the output. Even though this lies above 13kHz, it is still desirable to remove most of it. C11 and C12 cause the first filter IC1c to mop up about 15dB of a 13kHz clock, and progressively more of higher clock frequencies. The resulting output is sufficiently clean to be fed back to the delay loop to produce the reverb effect.

The amount of reverb and its quality is governed by the amount of delay and feedback. If too much feedback is given, a perpetual loop can result, causing howl. VR4 is thus inserted and adjusted to keep the feedback just below the critical howl point when VR5 is fully up. Howl is particularly prone to occur with high level bass signals, and a 6dB cut is given to signals at 100Hz, to slightly restrict the lower end of the audio spectrum. From IC1c, the processed signal has the clock residual further removed by the second filter stage IC1d, with a cut-off point set by C15 and C16, and giving an additional 26dB cut to a 13kHz clock.

VOICE GATE

With an ideal response from IC3, and with no carrier breakthrough the signal would at this stage be suitable for feeding direct to a normal amplifier. However, although the maximum signal output can be around 1.5V and the maximum summed breakthrough is only about

20mV, this 37dB difference was found to be unsatisfactory especially in the absence of a voice input. As the maximum frequency of the carrier is up to 3.5kHz, it is not possible in a simple unit to filter it out without also losing the voice signal—an obviously undesirable solution!

In a more complex unit a steep notch filter tracking with the carrier control, could perhaps achieve the required selective reduction. For this unit though, a voice-operated gate provides a simple alternative. This is not just a straightforward electronic switch operating on and off in response to a voice input, but it has also been given a degree of amplitude-following to smooth the start and finish envelope. The processed signal from IC1d is brought to the voltage controlled amplifier IC5c.

In fact this is a current controlled amplifier, but as the current on its control node will change with the variation of the voltage across R72, it can be regarded as a VCA. The signal is first attenuated by R65 and R66 to a level respected by IC5c. With no current flowing through R72, the gate will not conduct; as the current rises, so the conductance increases and with it the output signal amplitude as additionally set by R68. Buffered by IC5d it can be delivered to the normal amplifier. The control signal is derived from the unprocessed pre-amplified one from IC1b.

This is further amplified due to the current through R60 and the value of R61. IC5b buffers and presents it to the diode pump network C29, D1, D2 to be stored in C30. As the amplitude varies, so does the charge on C30, with a maximum limit set by the Zener D3. The varying charge then controls the current through R72, and thus the output volume. The envelope shape has been selected to give a fast attack set by R63, and a moderate decay set by R72. The overall effect is not only suppression of carrier and other noise breakthrough during speech pauses, but also deliberately introduces a slightly

staccato effect to the robot voice.

This is best emphasised by selecting a gain at IC1b that does not allow external background noise to undesirably trigger the gate. Despite the high gain given at IC5a the crosstalk between all stages of IC5 is not intrusive. When the unit is used without the carrier, the gate can be switched out by S2, which applies a fixed voltage to C30 to maintain a constant signal gain, and to shunt the input of IC5a to the reference line so eliminating the gate controller variations.

POWER SUPPLY

The unit is designed to run from a 9 volt battery drawing only about 25mA. Several intermediate reference levels occur throughout the circuit, the main one which supplies IC1a-d and IC2c is set by R55 and R56 at half the battery voltage level. The large value given to the smoothing capacitor C24 enables the pre-amp stages IC1a/b to give high gain with minimal circuit noise.

The expedient of providing two 0V connection points to the main p.c.b. also minimises high gain noise problems. The circuit will operate from a power supply up to 16V, but only if C24, C27 and C35 have their ratings increased accordingly. Both input jack sockets are wired as battery on/off switches and a mono jack plug must be used with one or other of them for correct operation.

ASSEMBLY

The Cybervox Robot Voice is built on two printed circuit boards. The layout of components on the topside of the Ring Modulator/Reverb board and an actual-size master p.c.b. pattern is shown in Figs. 3 and 4. Layout of components and full-size master pattern for the Voice Gate board is shown in Fig. 5.

Interwiring details of the case-mounted

components is shown in Fig. 2. The key numbers relate to wiring points on the printed circuit boards.

There is nothing complex about the assembly of the printed circuit boards though it is preferable for them to be assembled in order of resistors, diodes, small capacitors, i.e. sockets, presets, short wire links (which can be made from resistor offcut wires), large capacitors and finally the transistor.

Insert only a few parts at a time before soldering them and checking the joints with a magnifier. Do not bend the wires on the track side as this makes them tricky to remove if subsequently an assembly error is found, though it is a good idea to slightly angle them before soldering so that components do not fall out when the p.c.b. is inverted. Next,

neatly carry out the wiring to the panel controls, keeping the wires moderately short, but long enough for inversion of the p.c.b. for examination.

To minimise the chance of error in assembly, lightly cross off from the drawings each component or wire as it is assembled. Diverse colour coded wiring is recommended so that routing can readily be double-checked. Screened leads within the box should not be necessary, but the box should be grounded through one of the pot bodies as shown. Plan out the box drilling before making holes, then use sharp drill bits, if necessary gently removing burred hole edges with a fine file. Upon completion the box can be painted and panel legends applied. Most stationers stock a variety of rub-down lettering that is suitable.



Front and rear view of the assembled unit, showing front panel controls, and the input and output jack-sockets on the rear panel.

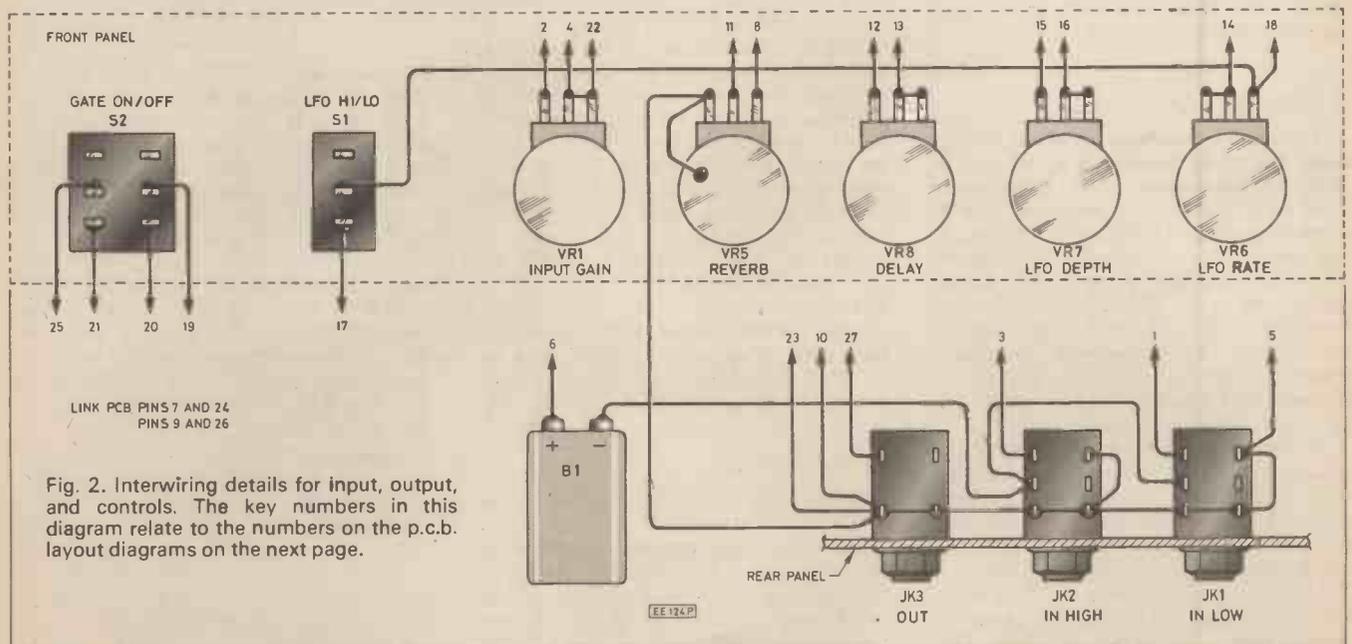


Fig. 2. Interwiring details for input, output, and controls. The key numbers in this diagram relate to the numbers on the p.c.b. layout diagrams on the next page.

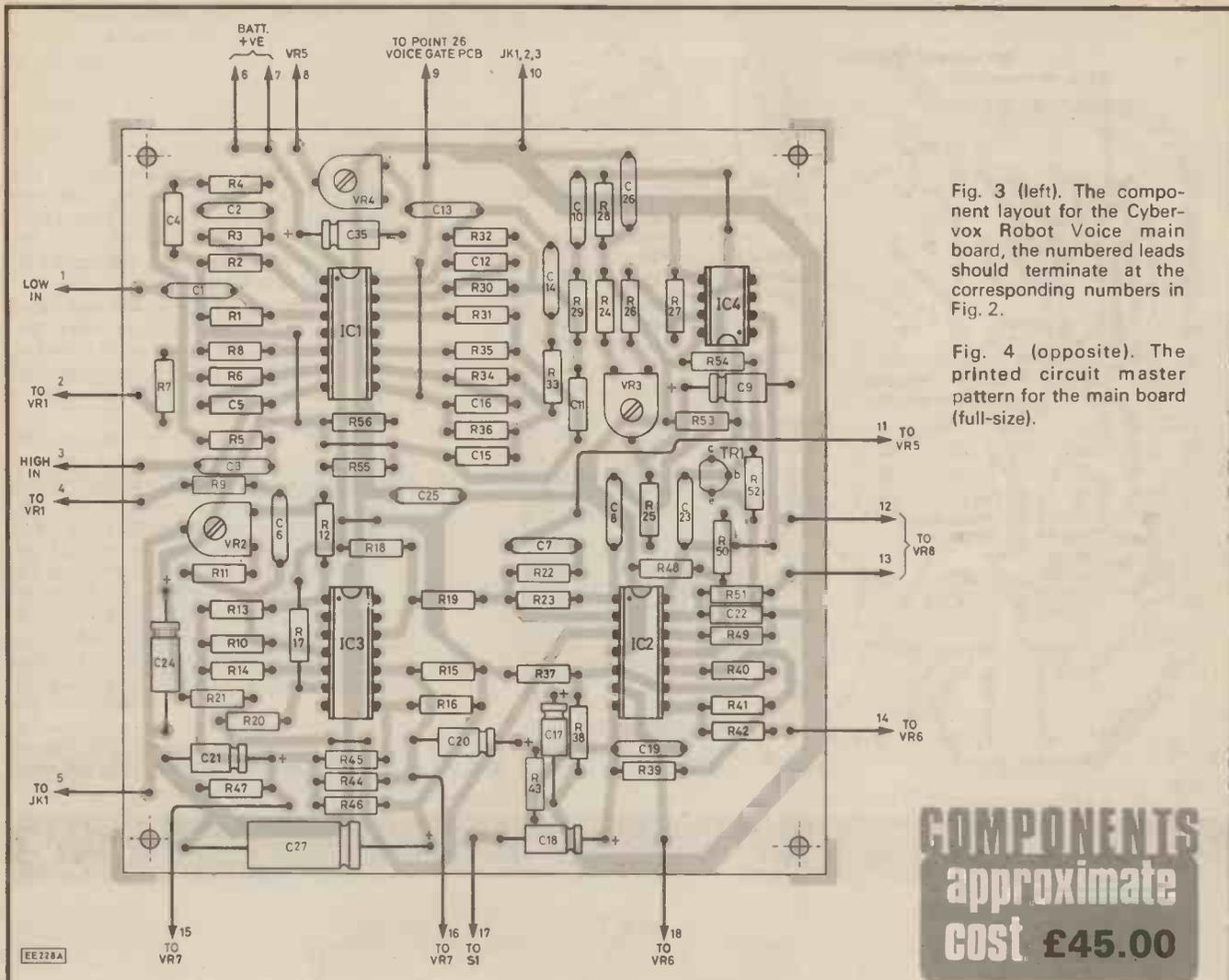


Fig. 3 (left). The component layout for the Cybervox Robot Voice main board, the numbered leads should terminate at the corresponding numbers in Fig. 2.

Fig. 4 (opposite). The printed circuit master pattern for the main board (full-size).

COMPONENTS
 approximate
 cost **£45.00**



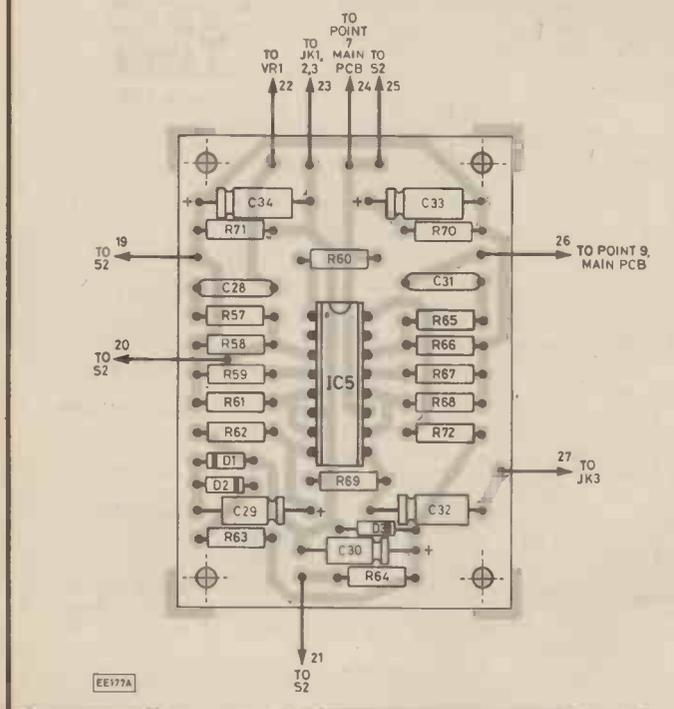


Fig. 5 (left). The layout of components on the topside and (below) actual-size master pattern for the Voice Gate board. See also previous page, for details of the internal layout and wiring.

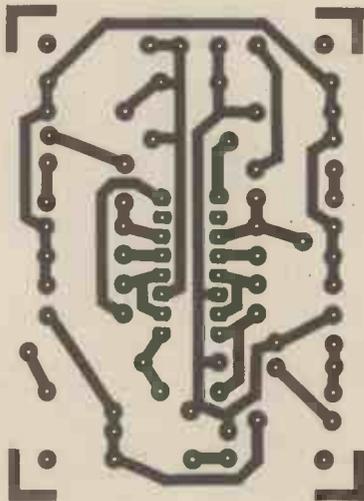

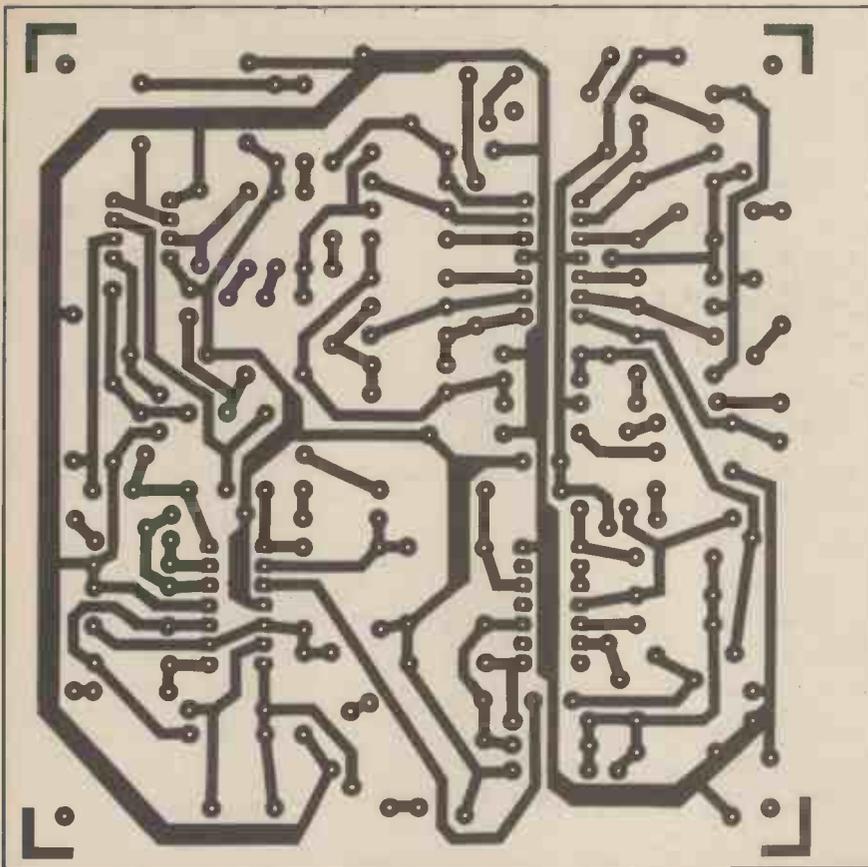

CHECKING AND SETTING

There are only three presets to be adjusted, and although they do not require specialised equipment, it is worthwhile adjusting them with patience to attain the best response. For setting up and general testing it is preferable to use a good voice recording from a cassette deck. This should be as free from background noise as possible and of a consistent amplitude. First, VR1 min, VR2 and VR3 midway, VR8 and VR4 max, VR5, VR6 and VR7 min, S1 down, S2 up.

Plug the cassette into the high input socket, and output into the main amplifier. Check that the cassette recording reaches the main amplifier, adjusting VR1 to suit if necessary in order to achieve a reasonable level.

Adjust VR3 around its midway point until the minimum distortion is apparent at higher signal levels. If no difference is heard, leave midway and ignore until other setting up is completed. Fully rotate VR5 and slowly reduce VR4 until a slight reverb effect is heard. Set VR8 for the slowest clock speed whereupon the reverb will deepen. Further reduce VR4 until the best echoing reverb hollowness is achieved. Taking VR4 too far may result in spontaneous "howl" occurring on heavier voice inputs; if it does, sharply back off VR4 and start again. Aim for the closest you can get without howl. Playing around with VR8 and VR5, the full range of delay effects will be found.

COMPONENTS

Resistors

R10,R13	100 (2 off)
R24,R26,R27,R44, R45,R53,R63,R66,R67	1k (9 off)
R46	3k
R17,R18,R42,R43, R47,R55,R56,R70,R71	4k7 (9 off)
R2,R7,R9,R14,R52, R58,R59,R62,R69	10k (9 off)
R11,R12,R15,R16	18k (4 off)
R28,R64,R65	47k (3 off)
R6,R30,R34,R39	82k (4 off)
R1,R4,R5,R8, R19-R23,R25,R29,R31, R33,R35-R38,R40	100k (25 off)
R48-R51,R54,R57,R72	200k (2 off)
R32,R60	300k
R41	560k (2 off)
R61,R68	1M2
R3	

All $\frac{1}{4}$ W 5% carbon film

Capacitors

C1-C3,C6-C8,C13, C14,C23,C25,C26,C31	100n polyester (12 off)
C10,C28	22n polyester (2 off)
C19	47n polyester
C22	56p polystyrene
C5,C12	180p polystyrene (2 off)
C4,C11	330p polystyrene (2 off)
C16	470p polystyrene
C15	1n polystyrene
C9,C18,C32	1 μ , 63V, axial elect. (3 off)
C17,C20,C21,C33-C35	22 μ , 10V, axial elect. (6 off)
C29,C30	4 μ 7, 63V, axial elect. (2 off)
C27	470 μ , 10V, axial elect.
C24	470 μ , 6-3V, axial elect.



See
**Shop
Talk**
page 199

Semiconductors

IC1,IC2	TL084 (2 off)
IC3	MC1496
IC4	TDA1097
IC5	LM13600
TR1	BC549
D1,D2	1N4148
D3	BZY88 3-3V, 400mW Zener.

Potentiometers

VR2,VR3	5k skeleton, horizontal mounting (2 off) (may be 4k7)
VR4	100k skeleton, horizontal mounting
VR7	100k log., rotary pot.
VR5,VR6	100k rotary pot. (2 off)
VR8	500k rotary pot. (may be 470k)
VR1	2M log., rotary pot.

All linear tracking unless stated otherwise

Miscellaneous

S1	s.p.d.t. switch, sub-min.
S2	d.p.d.t. switch, sub-min.
Printed circuit boards; i.c. sockets; jack sockets; p.c.b. clips; PP3 battery clip; pot knobs.	
Case—9 x 5 $\frac{1}{4}$ x 2 $\frac{1}{2}$ in. approx.; stick-on feet.	

Next, VR5 min, VR8 min (highest clock—shortest delay), S1 up, VR6 midway, VR7 max. A moderate Dalek type modulation to the input voice should be heard. VR7 will vary its depth, and VR6 the rate of modulation. Switch down S1 and the rate will increase dramatically and be accompanied by a high pitch whistle. As the highest setting of VR6 is approached, the voice output will become virtually unintelligible as the extreme modulation effect increases. With the high pitch whistle at its most apparent setting, fully turn down VR1 and also the voice input source volume control so that only the whistle remains.

Do not pull out the jack plug from the input as this will turn off the battery, and thus remove power from the unit. Now very carefully and with patience rotate VR2 around its midway point until the minimum whistle is heard. It will never be completely nullified by VR2 but will drop to a markedly lower level as the modulation input bias of IC3 is absolutely balanced. Turning down VR7 it should totally disappear. The voice gate can now be checked but requires no setting up. With S2 down the gate is under control from the signal coming from IC1b.

The operation of the gate under automatic voice control will of course depend on the level of the signal at IC1b. Too high a level will increase any background noise present and this will be amplified by the control to above the gate operation threshold. Too low a signal and

the gate will be reluctant to open. The best setting of VR1 is that which will cause the gate to open and close regularly for moderately spaced words or phrases. This gives the semi-staccato effect to the unit when the carrier is being used. For the reverb on its own, the gate can usually be switched off allowing the reverb effect to die away of its own accord. With the gate on the reverb will naturally die as the gate closes.

Experiment for a while with various settings of all the panel controls and attain a feeling for the flexibility of the simulator, if necessary slightly adjust any of the presets. Any adjustment to VR2 though should only be made after the unit has been switched on for several minutes as the balance may be slightly temperature sensitive.

USE

Either of the inputs may be used, to suit the strength of the incoming voice signal. Within reason it will not harm the unit to have the wrong strength on the wrong jack socket, it will only produce signal distortion or reduction. IC4 is the most sensitive to overloading and has a maximum desirable signal input level of 1.5V rms.

The maximum output from IC3 is approximately the same as that from IC1b, depending on the setting of VR7 which will give a slight reduction at full carrier

modulation. To this level IC1c can add a similar level via VR5. Substantially this means that the signal from IC1b should be no more than half of 1.5V rms, i.e., 750mV. With the wide reduction and expansion range offered by VR1 the unit will cope with signal levels up to 7.5V. The maximum output though is dictated by the imbalance created between the two carrier inputs of IC3.

Without the reverb in circuit and with VR7 turned down so removing the carrier, the gain factors throughout have been set to give roughly a 1.5 volt output at IC5d for a 1.5 volt output at IC1b. This is the maximum output level that can be expected and increasing VR1 further will be likely to lead to distortion, but not output gain. Incidentally VR1 will only significantly increase signals below the filter cut off region as set by C4 and C5.

There is no reason why the unit should not be used with musical sources if odd effects are required, but the frequency bandwidth is too restricted for full range serious musical use. However, any sort of voice input will produce results. The most dramatic results though come from words spoken in a uniform monotone fashion. For those with drama facilities the unit plus a small amplifier could be inserted into a model robot for supreme realism. But even for lesser time lords without stage props a lot of realistic fun can be had with only the unit, a microphone and an amplifier. Just plug in, switch on and enjoy a spot of social cyberchat. □

PREPARE FOR TOMORROW'S WORLD, TODAY!

An understanding of electronic and computer technology is fast becoming a vital part of today's living. Take out an annual subscription and have

EVERYDAY ELECTRONICS & COMPUTER PROJECTS delivered direct to your door every month...

SUBSCRIPTION RATES

U.K. £12.00
Overseas £13.00

COMPLETE AND POST THIS ORDER FORM TODAY!

EVERYDAY ELECTRONICS and computer PROJECTS

SUBSCRIPTION ORDER FORM

Annual Subscription Rates	
U.K.	£12.00
Overseas	£13.00
(Students: deduct £1 and quote Student number)	

Complete this form and post it, with payment or credit card authorisation to:
Everyday Electronics
Subscription Dept.
Oakfield House,
35 Perrymount Road,
Haywards Heath,
West Sussex RH16 3DH

POST COPIES TO:

NAME: _____

ADDRESS _____

POST CODE: _____

I enclose my cheque/PO. payable to IPC Magazines Ltd. for £ _____

Charge my credit card A/C at quoted rate

_____   

Card valid from: _____ to _____

Signature _____ **21**

SHOP TALK




BY MIKE ABBOTT

Catalogue Received

We have received the latest **Cricklewood Electronics** catalogue, and as a general electronics components supplier with an emphasis on semiconductors we can recommend this company as a useful source of parts for the hobbyist. In addition to multimeters and soldering irons, knobs, boxes and connectors, p.c.b. making accessories, nuts, bolts and heatsinks, there are some surprise items like valves and thermal fuses. Telephone orders can be accepted on most major credit cards by simply quoting your card number and shopping list. To obtain a current catalogue just telephone **Cricklewood** (01-450 0995) with your details and they will arrange to send you one free of charge.

Suck Blow

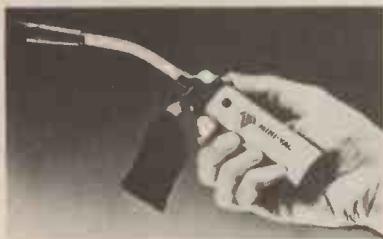Dealing a blow to the underworld of micro-debris is the smallest vacuum cleaner in the world, *as far as we know*. With the Mini-Vac, a lightweight miniature vacuum cleaner powered from a single 9V battery, you can remove dust and filings from your equipment with peace of mind.



As every hobbyist knows, you can always blow swarf from a freshly drilled metal box, but the mischievous debris you seek to remove invariably seizes the opportunity to lodge somewhere more devastating. Mini-Vac will 'bag' the blighters for you, and the bag may be quickly removed for emptying, by way of a Velcro seal.

The tool has an optional attachment to turn it into a blower. The two-brush vacuum head is described as 'lense' quality and is therefore of interest to photographers also.

The vacuum cleaner is clearly not intended for use as a solder sucker. Mini-Vac costs £19.60 + VAT and should be found generally available, otherwise contact **O & S Photographic Co., South Block, The Maltings, Sawbridgeworth, Hertfordshire**, for more information.

Surprising Spectacles

Stand-mounted magnifying glasses are the most widely used aid to fine detail benchwork, but they tend to be bulky and not cost justifiable to the hobbyist. An alternative exists in the shape of the **Leeda Magnifier**. These prismatic, half-lense magnifying spectacles have a focal length of around 255mm (10 ins), and may be perched on your nose whilst modelling or inspecting those terrifyingly minute tracks of a micro computer p.c.b. If nothing else, they will earn you the sympathy of your friends (unless you explain what they're for).



The spectacles seem an obvious idea for today's electronics hobbyist, although (shshsh!) they were originally conceived to assist trout fishermen with their artificial flies! A sobering thought. If you cannot find them locally you can order a pair from **Leeda Ltd., 14 Cannon St., Southampton SO9 2RB**. Send £13.70 to include VAT and P&P.

CONSTRUCTIONAL PROJECTS

Insulation Tester

A full kit of parts for the *Insulation Tester* project is available from **Magenta Electronics Ltd., 135 Hunter St., Burton-on-Trent, Staffordshire DE14 2ST**. The kit price is £16.96.

You may purchase the p.c.b. separately for £2.98, and both these prices include VAT, although 60p extra per order should be sent to cover P&P. All parts for this project are available separately.

Fibrealarm

In fact, there is no cause for alarm with the *Fibrealarm* project. All components are readily available. The light fibre specified is available from **RS Components**, although only in bulk amounts; and from **Maplin** in short lengths. T1 is Tandy No. 273 7011. The **BPX25** phototransistor is available from **Magenta Electronics**, for £4.75.

Immersion Heater Controller

Most of the components required for the *Immersion Heater Controller* are widely available from suppliers such as **Maplin** and a host of other companies which you will find listed in the *Advertisers' Index* at the back of this magazine. A flip through the aforementioned *Cricklewood* catalogue reveals that this company sells the thermistor type **VA1067** (do obtain a catalogue for ordering details), and 2-pole/6-way rotary switches, but no suitable relay for **RLB**, nor the **BTX 18-400** thyristor.

Relay **RLA** can be the **Maplin 10A** mains relay, although any 12V relay with normally open contacts rated at 1A or more at 240V a.c. will do. It is worth noting that when relays and transformers are specified, and very often switches too, substitutes may be found that have adequate electrical characteristics but differ in physical configuration.

'Stripboard layouts, such as the one illustrated in the *Immersion Heater Controller* may of course be altered to accommodate components which are electrical substitutes but which have different physical configurations, or size, although this is unfortunately not so with p.c.b.s. But beware switches, typically rotary switches, when following wiring diagrams because, again, physical variations occur—wiring diagrams, as opposed to circuit diagrams, can sometimes only be a guide.

For **RLA** the author used relay **UOD** featured in the *Cirkit* catalogue, details of which may be obtained from **Cirkit Consumer Division, Park Lane, Broxbourne, Hertfordshire EN10 7NQ**. 0992 444111. Relay **RLB** was selected from **RS Components' range (RS 348-403)** but any 20A mains relay with 240V coil will suffice. A suitable choice would be **Arrow Code No. 30A026 (order code 258-35375E)** from **Verspeed, Stanstead Rd., Boyatt Wood, Eastleigh, Hampshire SO5 4ZY**. 0703 644555.

Robot Voice

A complete kit of parts for *Cybervox Robot Voice* is available from **Phononics, 8 Finucane Drive, Orpington, Kent BR5 4ED**. 0992 37821, and costs £44 inclusive of VAT and P&P. The two p.c.b.s. are available separately for £6.07 inclusive. The **TD1097** can be ordered individually for £12.86 which includes VAT and 50 pence postage. The following components are available also from **RS Components: TDA1097, LM13600 and TLO84**.

The **MC 1496** is available from **Maplin Electronics**. Note that parts from trade supplier **RS Components** can be obtained through: **Ace Mailtronix Ltd., 26 Castle Rd., Wakefield, West Yorkshire WF2 7LZ**. 0924 250375.

INSULATION TESTER

MARK STUART

MOST electronics enthusiasts will at some time have been called upon to install or check domestic appliances and mains wiring.

Using a standard multimeter on resistance range it is easy to check for continuity, and the correct operation of switches etc. The difficulty comes when the *quality* of insulation is to be tested. Most meters use standard 9V or 15V batteries on the 'high' resistance ranges; this voltage is clearly a long way below the working voltage of the wiring and so the readings obtained can be very misleading. Insulation which breaks down dangerously at mains voltage can appear to be fine at 15 volts.

To overcome this limitation it has become standard professional practice to measure insulation at a potential of 500 volts using an instrument known as a 'Megger'. The original Meggers used a small hand cranked generator to produce the 500 volts. Modern versions are now available which derive the test voltage from a few 1.5V cells via an electronic inverter. The problem is that commercial instruments are rather expensive for occasional use by the hobbyist.

This project is a reliable 500 volt insulation tester at a reasonable price.

CIRCUIT

The circuit diagram is shown in Fig. 1. IC1 produces a 30kHz pulse waveform which drives TR2, the inverter output transistor, via R4. The collector of TR2 drives L1, which is the primary of a toroidal transformer. When TR2 is turned on the current in L1 builds up and energy is stored in the ferrite core. At the end of a drive pulse TR2 is turned off.

The sudden interruption of the current in L1 causes a high voltage 'back e.m.f.' pulse to be produced in L1, and in the other windings on the core. This high voltage pulse on L1 is stepped up by the winding ratio of the transformer (50:9) and produces a pulse of 250 volts across L3. The maximum voltage of the pulse is determined by the amount of energy stored in the core of the transformer and by the load connected to L3.

A third winding on the core (L2) provides feedback, which stabilises the voltage of the back e.m.f. pulse regardless of the battery state or the load presented

across the probes. Diode D1 and capacitor C4 rectify and smooth the voltage from L2. The resulting d.c. voltage is fed via D7 to the base of TR1.

If the voltage across C4 rises to more than 3.6 volts TR1 begins to turn on. As TR1 turns on the Threshold Control pin of IC1 is pulled towards the negative supply rail. This alters the output waveform from IC1 resulting in narrower drive pulses being supplied to TR2. In turn this means that less energy is stored in the transformer core during each pulse and the output voltage falls.


This feedback results in the circuit settling so that the voltage across C4 is always maintained at 3.6 volts. Allowing

for the efficiency of D1 this gives a peak voltage of 5 volts across the single turn winding L2. The peak voltage at TR2 collector is $9 \times 5 = 45$ volts and the voltage across L3 is $50 \times 5 = 250$ volts.

The secondary voltage from L3 is connected directly to D2 and also via C5 to D3 and D4. This arrangement works as a voltage doubler producing 500 volts across the series combination of C6 and C7. Resistors R7 and R8 ensure the rapid discharge of the capacitors when power is removed.

The test voltage is fed to the meter via R6, which limits the output current to 500 μ A.

The components around the meter are arranged to remove some of the scale non-linearity which occurs in ohm-meters at high values of resistance. At low currents there is insufficient voltage across the meter to enable D5 to conduct and so the meter acts as a standard 100 μ A meter. Above half scale D5 begins to conduct and introduces the shunting effect of VR1 across the meter. This changes the sensitivity to 500 microamps. In this way the meter can display a wider range of resistance values without scale cramping.

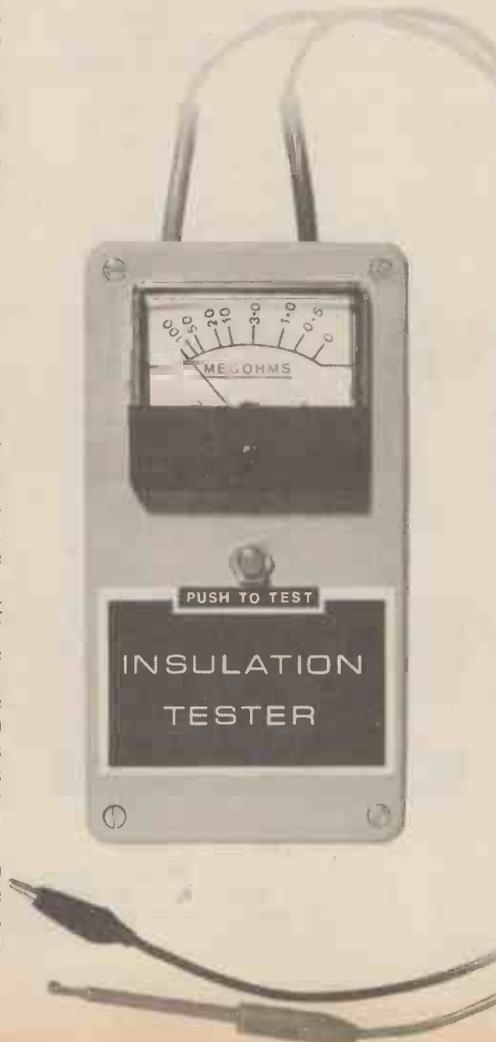

A single p.c.b. is used for this circuit. Fig. 2 shows the copper foil pattern. Refer to Fig. 3, the component layout diagram, and fit the components as shown. The inverter transformer consists of a ferrite toroid core upon which three windings must be threaded for L1, L2 and L3. The windings should be neat single layers positioned as in Fig. 3. Begin by winding L3. Approximately 2 metres of 28 s.w.g. enamelled copper wire are required. Leave approximately 10cm of free wire at each end and secure the winding with adhesive tape. Note that the winding does not need to be covered with tape, use just enough to stop the ends unwinding.

Next use $\frac{1}{2}$ -metre of 28 s.w.g. enamelled wire to wind the primary winding L1. It is important that the windings have the correct polarity. The 'dots' shown on Fig. 1 and Fig. 3 indicate the starts of the windings. Keep the same side of the core uppermost and start each winding by passing the wire up through the centre of the core. The polarities of the windings will then be correct.

When L1 and L3 are complete, wind L2 by passing a length of insulated connecting wire once through the core. Attach the core to the board using a length of insulating sleeving passed around the core and through the holes in the board, as shown in Fig. 3. Do not use bare wires to fix the core as this would become a shorted turn, and prevent the circuit from working.

Carefully scrape away the enamel from the ends of L1 and L3 before soldering the wires to the p.c.b.

It is important to note that only the specified ferrite core should be used. The design of inverter circuits depends upon the inductance of the windings and the properties of the ferrite. Some types of ferrite core may look very similar but be completely unsuitable for this circuit. It is also important to use the specified diodes for D1, 2, 3 and 4. Ordinary rectifiers such as 1N4005 are designed for use at 50Hz. They are practically useless at 30kHz because of their slow response.

When the board is complete the case lid should be cut out to take the meter and the test switch S1. The p.c.b. is mounted in the bottom of the case using two bolts with nuts as spacers—the high

voltage end lies beneath the meter. This leaves sufficient room for a PP3 battery next to the low voltage end of the board. Fig. 5 shows the layout of the components in the case.

Wiring up must be done before the p.c.b. is finally fixed in position. Ensure that leads between the case and the lid are long enough to allow access for setting up adjustments, and battery changing. The two test leads pass out through a grommet at the meter end of the case. Use well insulated flexible leads, about 1 metre long. An insulated crocodile clip on one lead and a hook grip probe on the other are best for the type of measurements that will usually be made.


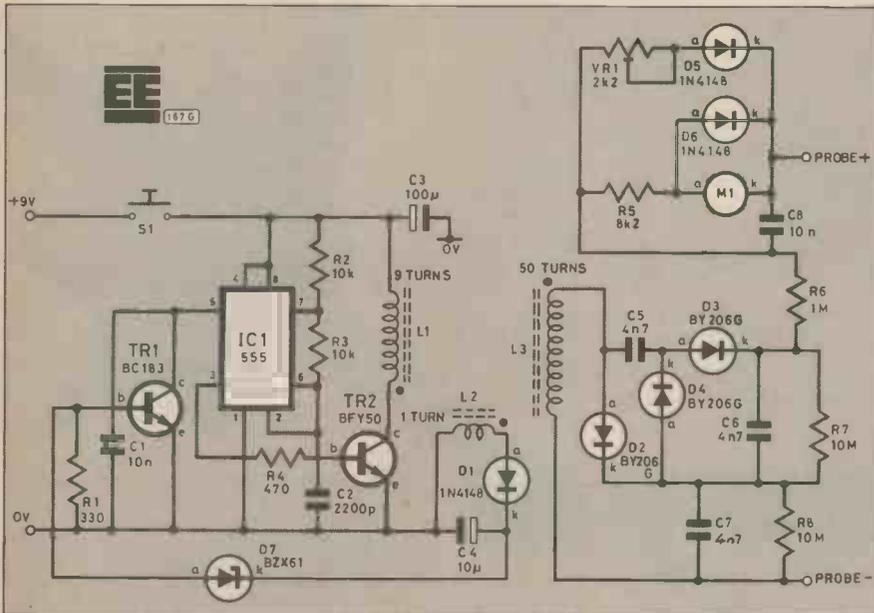


Fig. 1. Complete circuit diagram for the Insulation Tester.

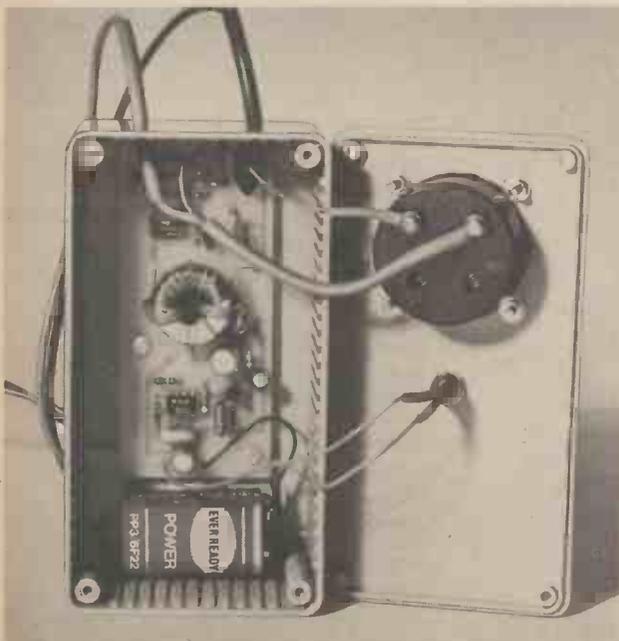

TESTING

Before applying power, double check the transformer windings, and that D1–D6, D7, C3 and C4 are the right way round. If everything looks correct set VR1 to mid position and connect a PP3 battery. Clip the two probes together and press S1. The meter M1 should read somewhere between half and full scale. Set the meter reading to exactly full scale by adjusting VR1. Release S1 and separate the probes. Clip a selection of high value resistors, one by one, across the probes and check the meter reading given for each. Take care—only press S1 when your fingers are away from the probes. The circuit is incapable of producing dangerous levels of current; however, 500 microamps can feel quite unpleasant.

**M
A
I
N
S
A
F
E
T
Y**

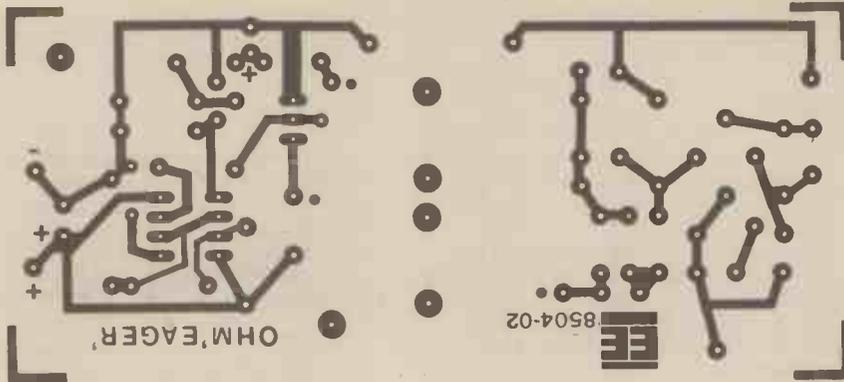


Fig. 2. Printed circuit layout (actual size).

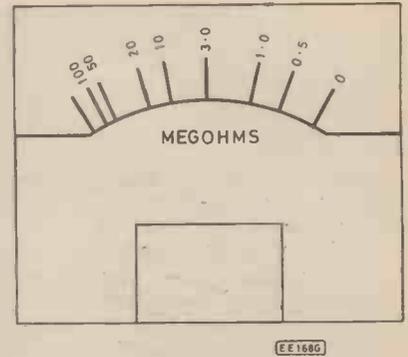


Fig. 4. This scale may be used with the specified meter.

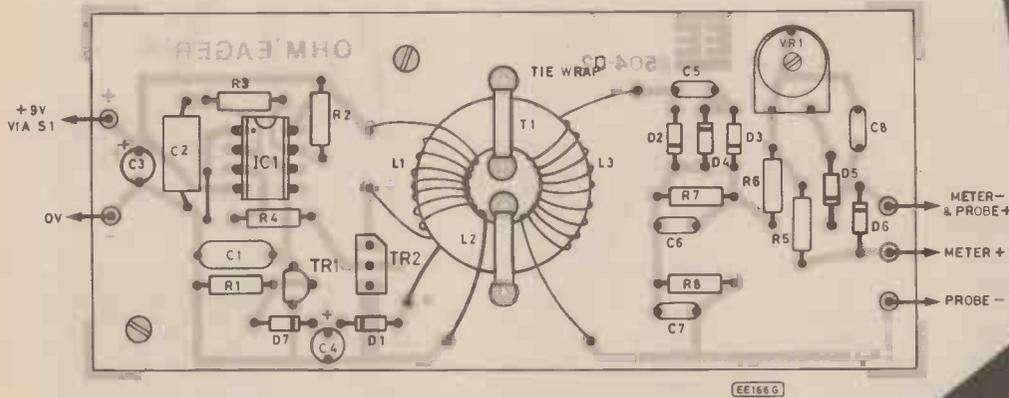


Fig. 3. Component layout on the topside of the printed circuit board. TR2 may be a TO5 can transistor.

COMPONENTS

Resistors

R1	330
R2,3	10k (2 off)
R4	470
R5	8k2
R6	1M
R7,8	10M (2 off)
All resistors $\frac{1}{4}$ W 5% carbon film	

Potentiometer

VR1	2k2 preset
-----	------------

Capacitors

C1	10n C280
C2	2200p poly
C3	100µ 16V elect. radial
C4	10µ 10V elect.
C5,6,7	4n7 ceramic 500V
C8	10n 50V ceramic

Semiconductors

D1,5,6	1N4148
D2,3,4	BY206G high speed 300V
D7	BZX61 C3VO
TR1	BC1B3
TR2	BFY50
IC1	555

Miscellaneous

S1	Momentary action push button switch
T1	Toroidal transformer core type ROF241212
M1	100µA meter approx. 4K resistance (MR45)
Leads—1M red and black well insulated	
Probes—1 probe and 1 crocodile clip	
Case plastic—approx. 150 x 80 x 50mm	
PP3 battery, clips, feet, fixings, 28 s.w.g. enamelled copper wire, sleeving. Printed circuit board	

See
**Shop
Talk**
page 199

CHECKS MAINS
INSULATION
TO 500V

The meter can be calibrated by using a range of resistors and marking the readings each time on a blank piece of paper fitted over the scale. Alternatively, if the specified meter is used Fig. 4 can be cut out or traced and fitted to the meter.

If a multimeter is available the voltage across the probes can be measured. This should be between 450 and 550 volts. The battery current consumption is between 20 and 60 milliamps depending upon the resistance across the probes. With the probes open-circuited the battery current should not exceed 35mA.

USE

An insulation tester is very straightforward to use. Clip the probes across the component or wiring to be tested and press the test button. When testing mains wiring take care to disconnect the power first and check between Live and Earth, and Neutral and Earth, as well as between Live and Neutral. When testing electrical appliances always check for insulation between the mains terminals and exposed metal parts.

Take special care when testing circuits with suppressor capacitors. These will be charged to 500 volts and will give a very nasty shock if touched. To prevent this problem always release the test button and wait for a few seconds before discon-

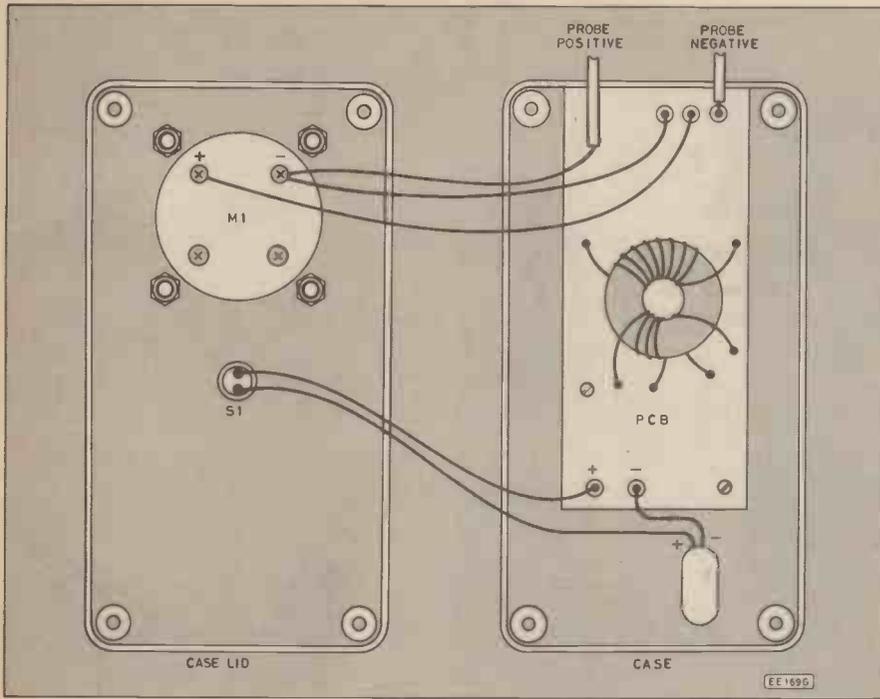


Fig. 5. Wiring diagram and mechanical layout of the Insulation Tester.

necting the probes. This will allow the external capacitor to discharge via R6, R7 and R8.

The tester can be used to check high voltage semiconductors such as power rectifiers and thyristors etc., provided

they are rated above 500 volts. Never use the tester on integrated circuits or low voltage semiconductors. The circuit is designed to withstand being accidentally connected to the mains. The battery life should be very long since current is only

taken during tests. When the battery is getting low it will no longer be possible to get full scale readings on the meter when the probes are shorted. This is a simple test that should be carried out prior to each test. □

Intruder Alarms and Accessories

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

- Control Unit
- Enclosure & mechanical fixings
- Key Switch & 2 keys
- LED's
- 5W Horn Speaker
- 4 high quality surface mounting Magnetic Switches

CA 1250
HW 1250
KS 3901
LED 1
MS 588
MS 1028

With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straightforward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today.
Order Code: CS 1370

EXTENDED SYSTEM CS 1480 Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 plus enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.
Order Code: CS 1480

SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063

only £37.00 + V.A.T.

- Requires no installation. Easily assembled using our professionally built and tested modules.
- Adjustable range up to 25ft
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate
- Provision for an extension speaker
- Fully self-contained
- Uses US 5063, PSL 1865 Key Switch 3901.
- 3" Speaker, 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90dbts of sound or even 110dbts with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063.

RISCOMP LIMITED

Dept 21 Duke Street,
Princes Risborough,
Bucks. HP17 0AT
Princes Risborough (084 44) 6326

ALARM CONTROL UNIT CA 1250

Price £19.95 + V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system - whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charge facility
- Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage
- 2 operating modes full alarm/panic and panic facility
- Screw connections for ease of installation
- Separate relay contacts for external loads
- Test lock facility

HARDWARE KIT HW 1250

only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk-screened label. Size 200 x 180 x 70mm

SIREN & POWER SUPPLY MODULE PSL 1865

only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110dbts at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

NEW

TIMER SWITCH & POWER SUPPLY MODULE DP 3570 Price £13.95 + V.A.T.

The DP 3570 consists of an adjustable timer switch and stabilised 12V power supply for use in a wide range of applications including security, lighting control and automatic switching. The timer section of the module provides switching of loads up to 3A for pre-set times. The duration of which may be set by the user to between 10 secs and 5 mins. The timed period may be triggered by the opening of a loop or the closing of external contacts with the timed period commencing instantaneously or delayed to provide a form of entrance delay. The power supply section of the module provides a 12V output of up to 250mA which is sufficient for most applications. The module operates from either 240V a.c. supply or a 12V battery for which trickle charge facilities are included. Connections to the module are by means of screw terminal connectors with no soldering needed.

For mounting the unit an attractive moulded enclosure is available.

ME 357 only £2.85 + V.A.T.

INFRA-RED SYSTEM IR 1470 only £25.61 + V.A.T.

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50ft operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications. Size 90 x 50 x 35mm

DIGITAL ULTRASONIC DETECTOR US 5063

only £13.95 + V.A.T.

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

- 3 levels of discrimination against false alarms
- Crystal control for greater stability
- Adjustable range up to 25ft
- Built-in delays
- 12V operation

ULTRASONIC MODULE ENCLOSURE

only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063, for US 4012 order SC 4012.

RISCOMP THE SECURITY SPECIALISTS!

FULL RANGE OF ACCESSORIES STOCKED SEND SAE FOR DETAILS

Add 15% V.A.T. to all prices.
Add 70p post and packing to all orders.
Units on demonstration.
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday

Saturday 9.00 to 1.00 p.m.
SAE with all enquiries.
Order by telephone or post using your credit card.

Making PCB's

STEPHEN IBBS

MOST of the projects published in magazines have p.c.b. designs, and yet many readers may be unfamiliar with this form of construction technique and are still using Veroboard, or 'bird's nest' wiring arrangements. This article has been written to sweep away many of the fears, and to show how simple the process really is, given a bit of tenacity in the learning stages.

Printed circuit boards replace as many connecting wires as possible with solid copper tracks bonded to a sheet of material, usually 'Synthetic Resin Bonded Paper' (SRBP), or fibreglass. The components are then mounted on the plain side, with the leads inserted through holes onto the various connecting points (pads) on the track side. They are then soldered to make the inter-connections. The art is in drawing the tracks so that the components can be mounted neatly, and with as few link wires as possible.

If you look at a complicated circuit, you will realise that to join all the components together without any of the tracks crossing each other (which is obviously impossible, as they will short circuit) requires a good deal of forethought and planning with a sheet of graph paper. However, let's start simply. How do you 'draw' the tracks?

When you go to an electronics shop for p.c.b. materials you will be presented with a sheet of plain 'copper-clad' board, either a special pen, or some transfers, and a bottle of horrible brown liquid called 'Ferric Chloride'. Before going any

further a **WARNING**. This liquid gets everywhere and stains everything, so the use of an apron and rubber gloves is recommended. Tracks are drawn on the copper side with the pen or transfers which are etch-resistant, and the board is then placed in a tray containing the Ferric Chloride. The 'tracks' prevent the Ferric Chloride from dissolving away the copper underneath them, and when the process is finished, the board is cleaned. Copper tracks will be left where you have placed the lines, pads, etc. Holes are then drilled, and the components inserted and soldered. The best way of learning this is with simple examples.

PREPARING A SIMPLE PCB

Look at the circuit in Fig. 1 which turns on an l.e.d. when the pushbutton is pressed. The transistor is actually superfluous, but has been included for a special reason, to show that you must think in reverse. You are preparing the drawing for the 'track side', and this will then be turned upside down to insert the components on the 'component side'. Thus the pin-out for a common BC109 npn type transistor from underneath is reversed as in Fig. 2. Usually it is best to try to place the supply lines at the top and bottom of the p.c.b. The following spacings can be used as a rule of thumb. Allow $\frac{4}{10}$ " for a resistor, $\frac{3}{10}$ " for diodes, and $\frac{2}{10}$ " for l.e.d.s, ceramic and tantalum capacitors. Polyester capacitors vary so

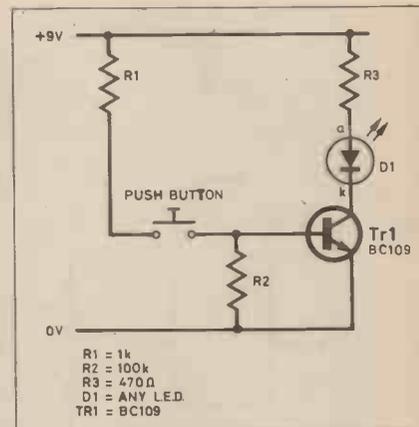


Fig. 1. Simple pushbutton circuit diagram.

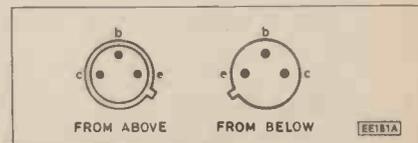


Fig. 2. Pin-out of BC109 from above and below the p.c.b.

much in size that one spacing dimension will not suffice.

From the collector of TR1 we need to have one pad to connect the l.e.d. cathode, then another pad for the anode, $\frac{2}{10}$ " away, linked to the 470 ohm resistor. The spacing for this is $\frac{4}{10}$ ", and it is placed East to West to keep the overall p.c.b. size small (Fig. 3). From this end we need a pad for the 1k resistor, placed North to South, and another pad for the positive supply. The other end of the 1k resistor has a pad attached for one lead to the pushbutton, the other lead being connected to a pad from the base of TR1. Also from the base is a pad for the 100k resistor, again placed East to West. Small pads are used for components, the larger pads used for interconnecting leads, to a) accommodate Veropins, and b) to differentiate them from component pads.

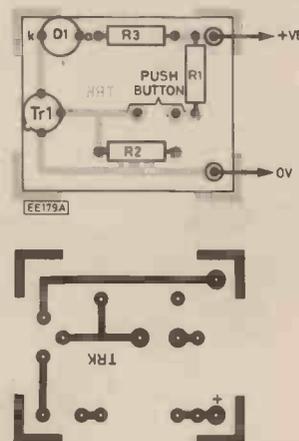


Fig. 3. Track layout and component overlay for the simple pushbutton circuit.

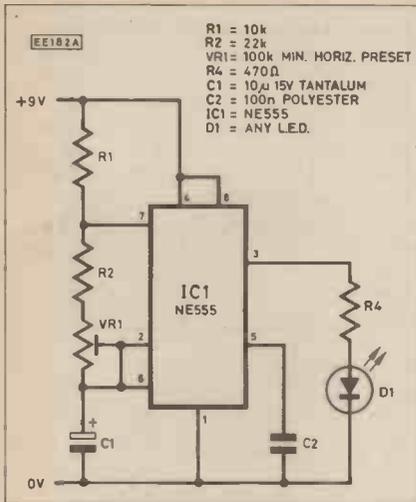


Fig. 4. Circuit diagram for i.e.d. flasher circuit.

ICs, PRESETS, ETC

It may seem pedantic to arrange the components in straight lines but it really does make following the circuit a lot easier; important for other people who may build the same circuit and use your p.c.b. design. This is particularly true as the circuit becomes slightly more complicated as in Fig. 4. This is a simple NE555 based i.e.d. flasher, but it incorporates some more elements into p.c.b. design, namely a polyester capacitor, a preset pot, and an i.c. It is here that the warning about thinking in reverse becomes vitally important. If you look at the i.c. and then turn it upside down, i.e. looking from the track side, you will note that pin 1 is in the top right hand corner. (See Fig. 5.)

It is likely that most designers of p.c.b.s. have forgotten this fact at some time or other, and ruined a p.c.b. because the i.c. was back to front. To avoid wasting numerous p.c.b.s. always use a sheet of $\frac{1}{10}$ " graph paper, and draw the i.c. block in ink, with the pin numbers starting with '1' at the top right, then numbering round clockwise, so that from the beginning the i.c.s will be correct. The use of imperial measurements may seem old-fashioned, but the fact is that i.c. pins are exactly $\frac{1}{10}$ " apart, with the two rows $\frac{3}{16}$ " apart ($\frac{5}{16}$ " for the large i.c.s).


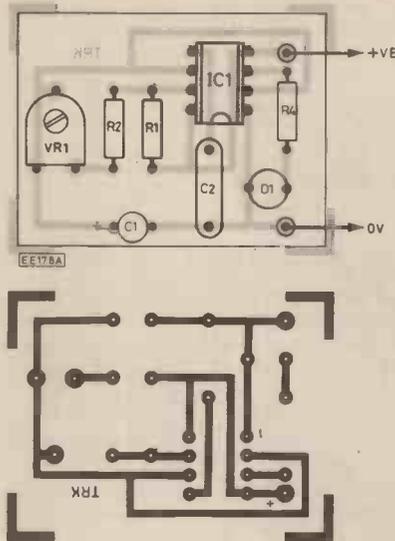
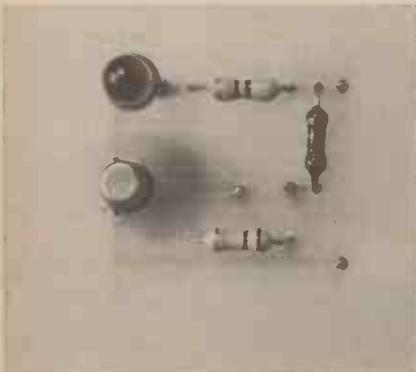


Fig. 5. Track layout and component overlay for the i.e.d. flasher.

Looking at the circuit in detail, the 0.1 microfarad polyester capacitor is allowed a $\frac{4}{10}$ " spacing, and the tantalum $\frac{2}{10}$ ". The components have been spread out a little to help explain the principles; obviously these 'rules' have to be broken if space is at a premium, e.g. resistors may need to be placed on end. Note the preset; this has a spacing of $\frac{2}{10}$ " for the two legs, with the 3rd (the 'wiper' leg) spaced $\frac{4}{10}$ " away (larger pads were used for the preset).

The prototype was drawn using graph paper, so that mistakes are easy to rub out, before committing pen to copper. All the components are again placed N/S or E/W, and the aim is to avoid using link wires. The resistors have been placed $\frac{2}{10}$ " apart and $\frac{2}{10}$ " from the i.c., but in practice they can be closer together, if necessary. The '+ve' Veropin pad has been placed only $\frac{1}{10}$ " away from the end of one resistor, and this is quite acceptable if the soldering is neat. The i.c. has pin 1 to 0ve, so is placed with pin 1 at the bottom of the p.c.b.

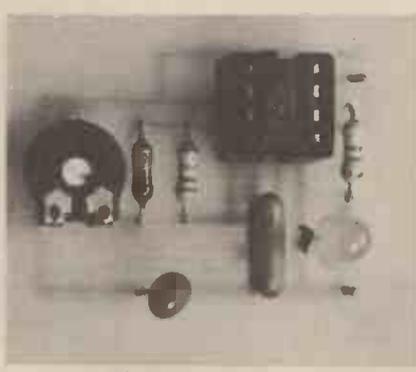When the design is finished, the board can be prepared by cleaning it thoroughly, either with wire wool or a special p.c.b. cleaner (RS 555-308). Lay the graph paper over the copper and secure with 'Sellotape'. Using a sharp




stylus, press the point through the paper to mark the various pads onto the copper. Also mark the corners of all the lines so that they can be drawn straight using a ruler. The paper is then removed and the pads and lines drawn with the pen (or transfers). As a general rule make the lines thick, both in width and in consistency. Pale straggly lines will get eaten away by the solution. Do not touch the cleaned copper, otherwise the grease from the hands will affect the etching process. The board is then placed in the Ferric Chloride.

ETCHING

There are many schools of thought about how the board should be immersed. It is true that placing the board in the bottom of the tray, copper side up will result in a very slow process. This is because as copper is etched away it remains on the board, preventing fresh solution from reaching the copper. Thus the use of a slender container is advised, insert the boards vertically. This has the advantage of enabling double-sided boards (see later) to be etched easily.

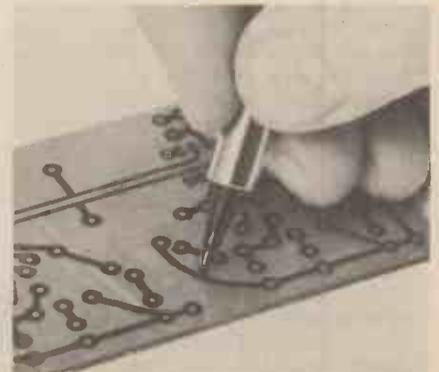
If the solution is bought in powder form it needs to be mixed with water. **Important** This is an 'exothermic' reac-



tion, i.e. it gives off heat, so *do not* add water to the powder, as it will spit and fume. Pour the powder gently into the water.

It is difficult to find a list of recommended mixing amounts, but 4 oz of powder to 10 fl oz of water seems to be about right. Manufacturers' claims of 10 minutes etching time may be rather optimistic; if the solution is cold, allow about 1½ hours! If the solution can be warmed the process will be much faster; standing the container in a bowl of hot water will speed up the process.

When the etching is complete remove the board and rinse with clean water. The etch-resist can be removed with wire wool or scouring powder, after which you should be left with a perfect p.c.b. waiting to be drilled. It is preferable to use a mini-drill with a 1mm bit, after which the components can be inserted with confidence, knowing that the circuit will work first time (you hope). You will find that using a stylus to mark the pad positions has the advantage of providing ready made 'starters' for the mini-drill which would otherwise tend to 'skate' over the smooth copper surface.

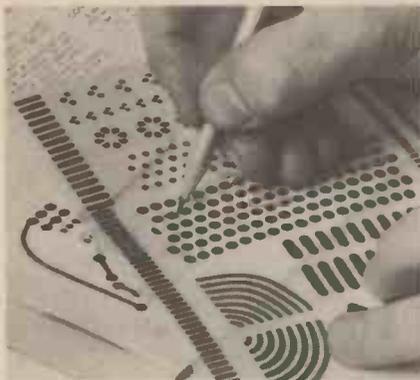

TRANSFERS

You may feel after a time that pens do not give neat results, even using a ruler, and there are aids to make life easier and the result more professional. Rub down transfers can be purchased, and these can be simply placed direct onto the copper (again *very* clean) and etched as normal. Sheets of pads, i.e. configurations, lines, etc., and special crepe tape can be purchased in various thicknesses to quickly produce the lines. They are very simple to use, and the final p.c.b.s look much better.

As a general rule, try to avoid running lines between i.c. pins, but if this is unavoidable, special transfer packs of i.c. designs with lines between individual pins are available. Obviously it is quite easy to run lines between the two separate rows of i.c. pins, usually assume that three can be drawn with relative ease, using very

thin crepe tape; this has, on occasion, been increased to six where necessary. Packs of transfers are available from most electronics shops, and readers may like to note that 'Letraset' and similar makes are also etch-resistant. Very effective badges can be made using lettering and etching, e.g. radio hams' call sign badges.

PHOTO-ETCHING

Taking the production of p.c.b.s a stage further, those readers who are interested in developing their own projects and p.c.b.s will find any of the above methods very time-consuming. This is almost invariable because the p.c.b., after it has been etched, will need modifications, improvements, etc., and to completely redraw the whole board again is very annoying, particularly as copying errors will often creep in.

To alleviate this, a process of photo-etching is possible. This involves using the same transfers, lines, pads, etc., but instead of placing them direct onto the copper they are rubbed onto a clear acetate sheet. Graph paper is placed underneath,



and the process is very similar to that used when drawing the board, with the exception that mistakes, modifications and improvements can be made much more easily by removing the lines and pads from the acetate by gentle scraping.

The completed sheet is then placed onto a piece of photo-sensitive board (which has had its protective plastic layer removed) and inserted into an 'Ultra-violet box'. Make sure the design is the right way round; rub down lettering can be used to add the word 'TRACK' to the p.c.b. side. It is also a good idea to include a small figure '1' by pin 1 of each i.c. to help orientation when inserting the components. The coating on the board is sensitive to Ultra-violet light, so the whole board is exposed for about three minutes. The pads and tracks prevent the light reaching the copper in the required areas, and after the allotted time the board is

placed in a solution of caustic soda (3 teaspoons of powder to 2 beakers of water). The reaction is again 'exothermic', and rubber gloves should be used as this solution is not kind to the hands!

Within a few seconds a stunning change will occur and the p.c.b. design will appear. When this is clear and contrasted, the development time being approx one-two mins, remove the board, and rinse gently in cold water. Do not touch the board as the design is soft and can be easily damaged. Leave to dry and harden for about half an hour, and then etch as normal in the Ferric Chloride. The big advantage of the system is the ease of modification, and repeatability, the disadvantage being the cost of photo-sensitive boards and the light box.

DOUBLE-SIDED BOARDS

Sometimes a circuit is just so complicated that one set of tracks will not suffice, and the choice is between having several link wires, or preparing a second set of p.c.b. tracks on the *component* side (double-sided). This obviously raises many difficulties—avoiding the compo-



nents themselves, matching the two sides together, etc.—but the effect can sometimes be extremely dramatic in shrinking the size of a completed board and making the final assembly straightforward. It is outside the scope of this article to explain how double-sided boards are made. Experimenters, however, may like to know that using the 'photo' technique the acetate sheets can be placed on top of each other, immediately showing up any problem areas where, e.g. the pads from the track side will interrupt the tracks on the component side.

This article has been written not to frighten people off, but to show that with a bit of determination, p.c.b. design and production can be mastered quite easily, it really is worth it. The effect this will have on projects can be dramatic, being neater, easier to fault-find, and possibly more likely to work first time! □



MARCO TRADING

TRANSISTORS

AC128	0.30	BF338	0.38
AC176	0.28	BFX26	0.28
AF239	0.68	BFX94	0.24
BC107	0.10	BFX85	0.26
BC108	0.10	BFX87	0.26
BC109	0.10	BFY50	0.21
A.B.C.	0.12	BFY52	0.21
BC147	0.09	BFY90	0.90
BC182	0.09	BFX20	0.34
BC182L	0.09	BU208	1.55
BC184	0.09	BU407	1.65
BC184L	0.09	MJ2955	0.90
BC212	0.09	OC45	0.58
BC212L	0.09	OC71	0.50
BCY70	0.15	OC72	0.52
BD131/2	0.34	TIP31A	0.44
BD133	0.56	TIP32A	0.42
BD135	0.32	TIP33C	0.88
BD136	0.36	TIP34A	0.72
BF115	0.32	TIP2955	0.60
BF184	0.32	TIP3055	0.60
BF185	0.32	TIS43	0.88
BF194	0.08	TIS88	0.40
BF195	0.10	2N3055	0.45
BF196	0.10	2SC1096	0.68
BF197	0.10	2SC1173Y	0.82
BF200	0.38	2SC1306	0.92
BF224	0.20	2SC1307	0.40
BF244	0.26	2SC1957	0.76
BF244A	0.28	2SC2028	0.73
BF244B	0.30	2SC2029	2.10
BF259	0.32	2SC2078	1.05
BF262	0.30	2SC2166	1.20
BF263	0.30	3SK88	0.65
BF337	0.38	40673	0.80

TRANSFORMERS

British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v.	6-0-6v	100mA	0.58	0.52	0.43
240v.	6-0-6v	500mA	0.65	0.60	0.48

Carnegie 45p per transformer. £1.00 per 10.

SERVICE AIDS

ALL SERVISOL PRODUCTS

Switch Cleaner	0.88
Circuit Freezer	0.96
Foam Cleanser	0.84
Aero Klene Silicone	
Grease (Aerosol)	1.00
Antistatic Spray	0.82
Plastic Seal	0.88
Excel Polish	0.76
Fire Extinguisher, 640g	2.80
Video Head Cleaner	

C-MOS

4000	0.24	4021	0.58	4036A	2.75
4001	0.24	4022	0.96	4038	0.75
4002	0.25	4023	0.35	4039A	2.80
4007	0.25	4024	0.50	4040	0.60
4011	0.24	4025	0.24	4042	0.50
4012	0.24	4027	0.45	4043	0.42
4013	0.56	4028	0.45	4044	0.50
4014	0.60	4029	0.75	4046	0.60
4015	0.60	4030	0.35	4049	0.38
4016	0.40	4031	1.30	4050	0.36
4017	0.60	4033	1.25	4051	0.70
4018	0.60	4034	1.06	4052	0.60
4020	0.85	4035	0.70	4053	0.60

VOLTAGE REGULATORS

78L05/12/15	0.30
7505/12/15	0.55
7905/12/15	0.65
LM317K	3.50

PLASTIC BOXES

3 x 2 x 1"	0.35
3 x 2 1/2 x 2"	0.65
4 x 3 x 1 1/2"	0.70
4 1/2 x 4 x 1 1/2"	0.83
6 x 4 x 2 1/2"	1.15
8 1/2 x 5 x 3 1/4"	2.15

DIODES

IN916	0.04	AA119	0.12
IN4001	0.05	AA129	0.18
IN4004	0.06	AA130	0.16
IN4005	0.06	BA100	0.24
IN4007	0.07	BY126	0.12
IN4148	0.05	BY127	0.10
IN4149	0.06	BY133	0.16
IN5400	0.12	BY184	0.40
IN5401	0.15	OA47	0.10
IN5402	0.15	OA90	0.08
IN5404	0.16	OA91	0.09
IN5406	0.18	OA95	0.18
IN5408	0.20	OA200	0.06

MULTI METER SPECIAL

Requires AA cells (not supplied) and leads, etc.
 Russian type A U4324, 20000 P.V.
 D.C. Voltage: 0.5, 1.2, 3, 12, 30, 60, 120, 600, 1200,
 A.C. Voltage: 3.6, 15, 60, 150, 300, 600, 900;
 D.C. Intensity M/A: 0.06, 0.6, 6, 60, 600, 3000;
 A.C. Intensity M/A: 0.3, 3, 30, 300, 3000;
 D.C. Resistance: 0.2, 5, 50, 500, 5000 kOhm;
 g.e. level dB: -10 to +12.

£12 FANTASTIC SPECIAL PRICE:
 including P/P and VAT

LINEAR I.C.s

CA3011	1.80
CA3012	1.75
CA3014	2.38
CA3018	1.10
CA3020	2.10
CA3028A	1.30
CA3035	2.55
CA3080E	1.80
CA3085	1.20
CA3086	0.68
CA3090AQ	5.00
CA3130E	1.40
CA3140E	0.60
HA1336W	3.15
LM324N	0.55
LM339	0.65
LM348	0.90
LM380	1.65
LM381N	1.45
LM382N	1.45
LM386	0.99
LM387	1.45
LM389N	1.20
LM3914N	2.55
LM3915N	2.60
ML232B	2.10
555	0.35
C-mos555	0.88
741	0.25
SAS560S	1.85
SAS570S	1.85
SL901B	5.20
SL917B	6.25
TA7205AP	1.50
TA7222P	2.12
TDA1004	2.90
TLO72	0.98
TLO81	0.68
TLO84	1.28

SOLDERING AIDS

Antex 15W iron	5.00
Antex 18W iron	5.00
Antex 25W iron	5.20
Antex Elements	2.00
Antex Bits	0.95
Antex stands	1.90
Desolder Tool	4.50
Spare nozzle	0.45
25W Kit-iron with 13A plug & stand	ONLY 6.20

NI-CAD CHARGER

Universal charger to charge PP3, AA, C, D
 PRICE 6.00
 Any 100 28.00

NI-CADS

PP3	4-45, 4	16.00
AA	0-95, 10	8.00
HP11	2-30, 4	8.50
C	2-35, 4	8.75

CHART RECORDERS

Brand new 3 channel pen recorders complete with charts spares kit. Full spec. upon request - Once only bargain £40 + £10 p&p plus 15% VAT.

RESISTOR KITS

1/4W Pack 10 each value E12 10R-1M	ONLY 4.80
Total: 610 resistors	
1/4W Pack 5 each value E12 10R-1M	ONLY 2.75
Total: 305 resistors	
1/2W Pack 10 each value E12 2R2-2M2	ONLY 5.25
Total: 730 resistors	
1/2W Pack 5 each value E12 2R2-2M2	ONLY 3.50
Total: 365 resistors	

TELECOM EQUIP

BT Plug & 3M lead	.125
BT MASTER SOCKET	2.85
BT Sec Skt	1.95
BT 4-core cable .1M 0.15	100M 12.00

ROTARY POTS

0.25W Carbon Log & Lin 1K-2M2	each 0.32
	10 3.00
	Any 100 28.00

VEROBOARD

2 1/2 x 3 1/4	0.85
2 1/2 x 5	1.00
2 1/2 x 17	3.07
3 1/4 x 17	1.05
3 1/4 x 5	1.15
3 3/4 x 17	4.10
4 3/4 x 17 3/4	4.95
Pkt of 100 pins	0.30
Spt face cutter	1.48
Pin insert tool	1.85
Vero Wiring Pen & Spool	4.50
Dip Board	3.85
Vero Strip	1.25

MARCO TRADING (DEPT EE4)
 The Maltings
 High Street
 Wem, Shropshire SY4 5EN
 Tel: 0939 32763 Telex: 35565

ORDERING. All components are brand new and to full specification. Please add 45p postage/packing (unless otherwise specified to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telexphone your Access or Visa number. Official orders from schools, universities, colleges, etc, most welcome (Do not forget to send for our 1985 catalogue - only 65p per copy. All orders despatched by return of mail.
 NEW RETAIL 1,000 sq ft shop now open. Mon-Fri 9.00-5.00, Sat 9.00-12.00.



Our latest 123 page catalogue over 4000 items fully illustrated. Send 65p now for your copy. FREE with orders over £5.00.

hobbyboard

Printed Circuit Hardware & Component Catalogue

- ★ COPPER CLAD LAMINATES
- ★ PHOTO-RESIST LAMINATE & CHEMICALS
- ★ PRINTED CIRCUIT DRAUGHTING AIDS
- ★ VERO BOARD & PROTOTYPING SYSTEMS
- ★ CONNECTORS/CASES/GENERAL HARDWARE
- ★ SELECTION OF COMPONENTS
- ★ EDUCATIONAL COMPUTING
- ★ ELECTRONICS KITS

Send for your free catalogue to:



KELAN ENGINEERING LTD.
 Circuit Products & Components Division.
 27-29 Leadhall Lane, Harrogate.
 North Yorkshire. HG2 9NJ.
 Tel: (0423) 870938. EE/4/85

NAME _____
 ADDRESS _____

CUT PRICE ELECTRICS

SECURITY EQUIPMENT

- Magnetic Contacts from 50p (complete set).
- 6 inch 12v DC Bell £6.75.
- Bell Boxes. All colours and types from £3.95.
- Electronic 108dB two tone hour siren £6.95.
- Microsiren approx 100dB 12v DC £3.95.
- Control panel timed entry and exit dry 12v battery only (ANTI TAMPER) £21.75.
- Control panel timed entry and exit (variable) BS4737 mains battery. Auto Reset includes fused spur block very smart (white) lots of functions £33.50.
- High power xenon beacon. Colours, Red/Blue/Yellow/Amber weather proof. 250mA. 12v DC £7.20.
- 4-core security cable. 100 metres £7.35.
- Pressure mats from £1.05.

We stock everything in Security equipment. CC, TV, Tools, Microwave, Lighting, FCT and Big Name products like Racal, Elkron, Munford & White, A&G, Bentley to name a few.
 P.S. Handy installation guide, lots of very useful information and tips from the trade £1.00 + S.A.E. or free with first order of £75.00 or more.
 Why not become an alarm installer with our extra discount trade prices you could really have a high profit business in no time! All trade enquiries welcome.

ELECTRONIC COMPONENTS

Our Electronic Components department will be fully open Dec 84 with super buy lines like these:
 Electronic buzzer 25mA 12v DC. 55p.
 240v mains transformers, secondary voltage type are:
 4.5v, 4.5 99p
 6v, 6v £1.05
 9v, 9v £1.15
 3. Capacitors from 2.5p each (pc).
 4. Transistors from 4p (popular types).
 5. 2 1/2 inch miniature speakers 8ohm 0.3W 99p.
 6. IN4148 Diodes 2p each.
 7. Resistors from 1p each.
 8. LEDs 3mm & 5mm Red with clips 10p each (Also full range).
 Price Lists send 50p + S.A.E.

ELECTRICAL EQUIPMENT

Once again a few samples of our prices.
 1. 1mm twin & earth, 100 mtrs £9.99.
 2. 13amp plugs 39p.
 3. Twin switched sockets £2.89.
 4. Mini trunking 16mm 16mm x 3 mtrs £1.99 (callers only).
 5. 5 foot fluorescent tube complete with tube £6.55.
 6. 500W tungsten halogen fitting complete £3.95.
 7. 240v bulbs S.E.S. or S.B.C. 40w 60w 100w 25p.

SECURITY EQUIPMENT

Racal 772 12 mtr 13 zone passive infra red movement detector £31.00.
 Passives from £27.50.



TELEPHONES

We now have a large variety of telephones and fittings all at low prices.
 For instance:
 Digital telephones from £10.

All trade enquiries welcome. We have the lowest wholesale and retail prices.

Send 50p + S.A.E. for price list. £2 P&P to be added to all post orders. All prices subject to VAT @ 15%.

Cut Price Electrics Ltd
 Dept E.E. 159 High Street, Strood,
 Rochester, Kent ME2 4TH. Tel: Medway (0634) 727604
 Shop hours 8.30-6pm Mon-Sat.



Mail order & shops:

441 PRINCES ROAD, DARTFORD, KENT DA1 1RB
Telephone: (0322) 91454

ORDERING INFORMATION: P/P 50p on orders less than £20 in value otherwise post free. All components full spec & guaranteed. Discounts available on orders over £50 — phone for details. For unlisted components phone for price. Goods normally despatched by return post.

**NEW CATALOGUE NOW AVAILABLE
CONTAINING THOUSANDS OF LINES
MANY ILLUSTRATED**

This incredible volume contains everything required by the home constructor, amateur radio and CB user and computer enthusiast.

We think the semiconductor section contains more types than have ever been offered to the hobbyist.

Sections are headed as follows:

- Aerials, Amplifiers, Audio Accessories,
- Batteries, Boxes, Bulbs, Capacitors,
- Crystals, Car Components, Car Audio,
- CB & Ham Equipment, Computer
- Connectors, Fuseware, Hardware,
- Headphones, Knobs, Lamps, Leads,
- Loudspeakers, Microphones, Meters,
- OPTO, PCB, Resistors,
- Semiconductors, Special Effect
- Equipment, Switches, Power Supplies,
- Test Equipment, Tools, Transformers,
- Wound Components.

In addition to listed items we continue to provide a procurement service for obsolete and difficult to obtain types.

How many suppliers do you have at the moment that offer a service like this?

Please fill in coupon below and send with £1.25. Print clearly as coupon is used as address label.

Catalogue contains £2.50 discount order form — You make a profit straight away.

NAME

ADDRESS

.....

.....

POSTCODE

**FIND YOUR WAY
THROUGH THE DIGITAL
ELECTRONICS MAZE**




First there was
SUPERKIT

and now ...



SUPERKIT II

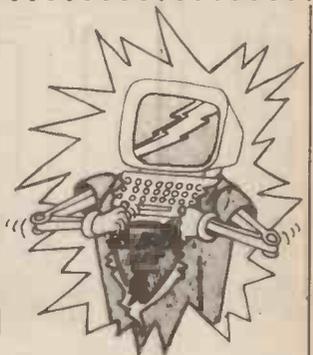

This practical self-instruction kit has been developed to extend the original beginners' SUPERKIT. SUPERKIT II includes an instruction manual and many more components, enabling you to design and use adders, subtractors, counters (ripple, up/down, synchronous, decade and Gray code), registers, pattern recognisers and 7-segment displays. You need the board and components from SUPERKIT to enable you to build the circuits in SUPERKIT II. Together the two kits provide an excellent introduction to digital electronics — what really goes on inside a computer.

SUPERKIT (SUP) £22.00 SUPERKIT II (SUP II) £16.00
Special price £35.00 for both (SUP + II) (inc. VAT and p & p)

The SUPERKIT series is backed by our theory courses, DIGITAL COMPUTER LOGIC (beginners' course), which covers the design of logical circuits, and DIGITAL COMPUTER DESIGN (more advanced), which covers the design of digital computers. MICROPROCESSORS AND MICROELECTRONICS teaches you what a microprocessor is and what it can do.

DIGITAL COMPUTER LOGIC (DCL) £7.00
DIGITAL COMPUTER DESIGN (DCD) £9.50
MICROPROCESSORS AND MICROELECTRONICS (MIC) £6.50

Please send for full information on these and our other courses. **GUARANTEE** If you are not completely satisfied, return the item to us within 28 days for a full refund. All prices include worldwide surface postage (ask for prepayment invoice for airmail). Allow 28 days for delivery in UK. Overseas payment by international credit card or by bank draft drawn on a London bank.

**CAMBRIDGE LEARNING LTD, Unit 39, Rivermill Site,
FREEPOST, St Ives, Cambs PE17 4BR, England.**

Tel: 0480-67446

VAT No 313026022 Transcash No 2789159 Reg No 1328762

Please send me (initial letters used):

..... SUP @ £22.00 DCL @ £7.00
..... SUPII @ £16.00 DCD @ £9.50
..... SUP + II @ £35.00 MIC @ £6.50

I enclose a cheque/PO payable to Cambridge Learning Ltd for £.....
Please charge my credit card.

No Expiry date

Telephone orders from credit card holders accepted on 0480 67446 (24 hrs)

Name

Address

Signature



**CAMBRIDGE
LEARNING**

Unit 39, Rivermill Site, FREEPOST,
St Ives, Cambs PE17 4BR, England.



DOWN TO EARTH

BY GEORGE HYLTON

WHY is it that some operational amplifiers need two batteries and others only one?

Like many integrated circuits, the operational amplifier is a small miracle of technology. Operational amplifiers once existed in non-integrated form; indeed, they existed back in the days of radio valves. When it was realised that quite simple electronic circuits could perform quite difficult mathematical functions (such as integration); engineers set about designing a standardised amplifier which could be adapted for performing mathematical tasks.

NUMBERS

In these tasks, numbers were represented by voltages: $2V = 20$, $3V = 30$, for example. If a circuit was arranged to add, then with the values just given, $20 + 30$ required an output of $5V (= 50)$. Since the input voltages ($2V$ and $3V$) were measured with respect to a zero-voltage ($0V$) line, then the output voltages must also be measured with reference to the same zero line. In other words (Fig. 1), the zero line had to be common to both input and output.

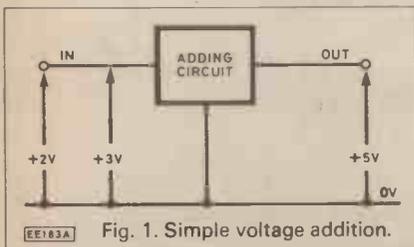


Fig. 1. Simple voltage addition.

Now, valves and transistors have this in common: the output of an amplifier (at a collector or anode) is normally at a different voltage level from the input.

A transistor stage with an input to the base of $0V$ has an output at the collector at some other voltage, such as $+10V$. This is no use in analogue computing, where $+10V$ means a number (in our case, 100). For computing purposes, the steady output must somehow be reduced to zero.

SPLIT SUPPLIES

The solution (Fig. 2) is to use split power supplies. The standing voltage at $TR1$'s collector must be positive with respect to the zero line. The standing voltage at the lower end of $R3$ is negative. The voltage at the junction of $R2$ and $R3$ is somewhere between the collector voltage and $B2-$. If the values of $R2$ and $R3$ are chosen correctly the voltage is zero.

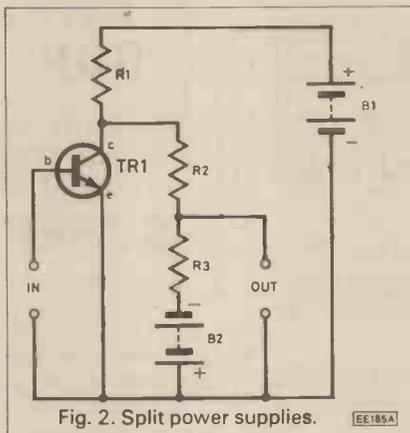


Fig. 2. Split power supplies.

Any change of collector voltage (due to input signal) now changes the output (at the junction of $R2$ and $R3$) from zero. The change can be positive or negative, so the circuit can handle both positive and negative numbers.

OPERATIONAL AMPLIFIERS

The idea of an operational amplifier evolved from such analogue computing circuits.

A pre-requisite was that inputs and outputs should be referenced to a common zero line and this called for split power supplies.

Certain other needs affected the design. One was that the amplifier should have a very high gain: because analogue computing calls for great accuracy. If an operational amplifier has an extremely high gain, and the gain is then reduced to some required value, say 100, by negative feedback, then the reduced gain can be set by two resistances and is virtually independent

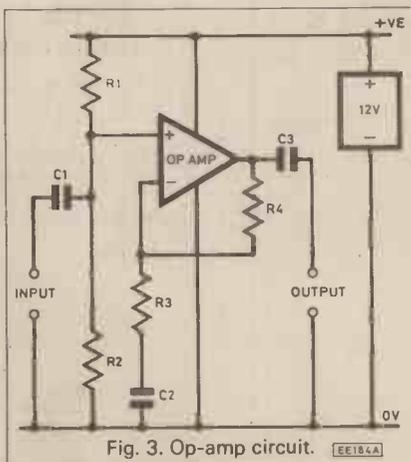


Fig. 3. Op-amp circuit.

of the 'real' or internal gain of the amplifier (called on data sheets the *open loop* gain).

Another requirement was very low output impedance. This ensures that the output voltage stays constant irrespective of the amount of current taken from the output. The amplifier has to be stable (not oscillate) when negative feedback is applied, even when the whole of the output is fed back to the input (which sets the gain to 1 or -1 , a mathematically useful condition).

Finally, the operational amplifier must go on working properly in the face of supply voltage variations, temperature changes, mains pick-up and similar nuisances.

When the small miracles happened, and all this performance was pushed into an integrated circuit, and sold at a low price, everybody wanted to use operational amplifiers. Not just for analogue computing (which is specialised), but for everyday jobs like audio amplification.

For many of these new users there was no need of a common input/output 'zero line'. They were quite happy to take an a.c. output from a point at a d.c. level different from the input. If the d.c. was embarrassing, it was easy enough to insert a coupling capacitor.

CHEATING

Almost any operational amplifier designed for split-supply operation can be worked as an a.c. amplifier from a single supply. The trick is to set the d.c. input and output voltages to half the supply voltage. This is done (Fig. 3) by making $R1 = R2$. Direct current feedback from output to the inverting ($-$) input (via $R4$) then forces the d.c. output voltage to be the same as the voltage applied to the non-inverting ($+$) input; d.c.-wise, the amplifier operates as if its supplies were $6V + 6V$ instead of a simple $12V$; a.c.-wise it doesn't care.

The coupling capacitors $C1$ and $C3$ allow the output to swing about the zero line, going negative or positive, though of course the output terminal of the operational amplifier really sits at $+6V$.

SINGLE-SUPPLY

It would be nice not to have to cheat in this way; i.e., to have an operational amplifier whose inputs could be applied d.c.-wise as well as a.c.-wise, between the input terminals and "zero", without blocking capacitors and d.c. biasing.


Unfortunately, some operational amplifiers have an Achilles' heel. If the voltage at one of their input terminals goes negative with respect to the negative end of the battery, the amplifier draws a large and uncontrollable current and is destroyed.

This is known as latch-up, and since the kind of single-supply operation we are interested in makes it inevitable that the input voltage will swing below battery negative (on the negative half cycles of input signals), something must be done.

Something has been. Single-supply operational amplifiers whose input can safely be taken a little negative of battery minus are now available.

CIRCUIT EXCHANGE

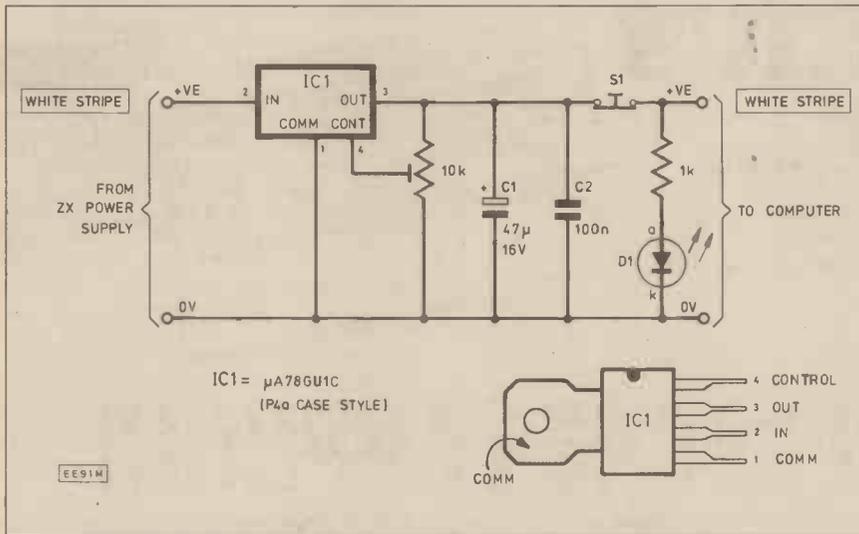This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised. Payment is made for all circuits published in this feature. Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.



The ZX Power Supply Add-On also provides a reset facility.

One of the let-downs of many home computers is the exclusion of an on/off switch or reset facility. As a bonus to the main purpose of this project this facility is provided by a simple break switch.

The push button S1 (which is a push-to-break type) provides a "reset" facility, and D1 shows when power is applied to the computer.

S. L. Walls,
Great Dunmow,
Essex.

ZX POWER SUPPLY ADD-ON

THIS IS a design for a circuit which will reduce the heating effect in the ZX81 by reducing the voltage fed to the regulator. It is suitable for computers which use a 9V supply, such as the ZX81, ZX Spectrum and ZX Spectrum+.

The output of the ZX Power Supply is about 15V of rectified and smoothed a.c., which the internal regulator reduces to 5V for the TTL chips and the processor. The 10V extra voltage leads to heating of the regulator and heatsink, which can cause errors and mechanical failures, due to the high internal temperature.

The circuit included pre-regulates the 15V to about 9V which is fed to the computer.

IC1 should be mounted on an aluminium plate about 50 x 50mm, or the case of an aluminium box. The tab of the i.c. is internally connected to pin 1, so if the unit is boxed in a metal enclosure it should be isolated by mica washers and insulating bushes.

It is recommended that the small power plug which plugs into the computer is cut off with some cable left to connect it to the output of the circuit, and the cable from the ZX Power Supply is connected to the input of the circuit.

The 10k preset should be adjusted so that 9V or just over appears on the output terminals, before connecting it to the computer. When this is done, it is ready to be used with the computer, which should not heat up as much as before.

FOR QUALITY COMPONENTS
BY MAIL ORDER

ELECTROVALUE

FREE
44 PAGE
PRICED AND
ILLUSTRATED
CATALOGUE
ON REQUEST


FREE POSTAGE
GOOD DISCOUNTS
GOOD SERVICE
THOUSANDS OF
STOCK ITEMS
PHONE YOUR ORDER
ACCESS OR
BARCLAYCARD

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham,
Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475
North Branch, 680 Burnage Lane, Manchester M19 1NA
Phone 061 432 4945
Please mention this publication when replying

MAY FEATURES...

MULTIMETER BUYER'S GUIDE...

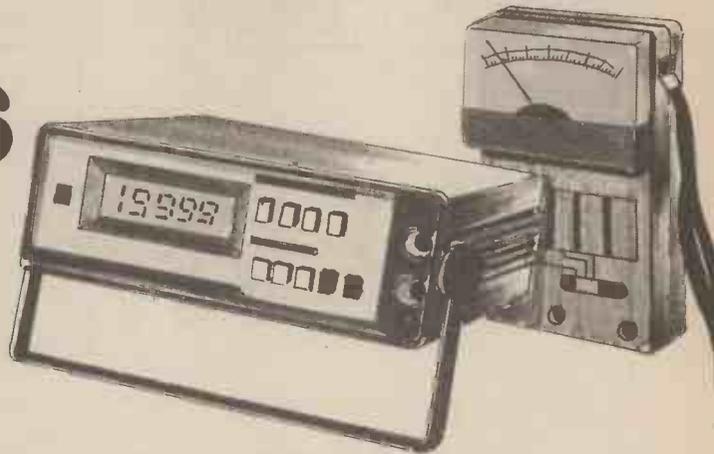For most hobbyists the multimeter is the first major investment in serious electronic construction. Our guide will help to ensure that this investment is well made.





AMSTRAD CPC 464 AMPLIFIER



If you own an Amstrad CPC 464 microcomputer why not build our stereo amplifier add-on, and give your machine true arcade quality sound effects when running games. The amp will also prove handy when developing multi-channel sound programs.

VOLTAGE PROBE

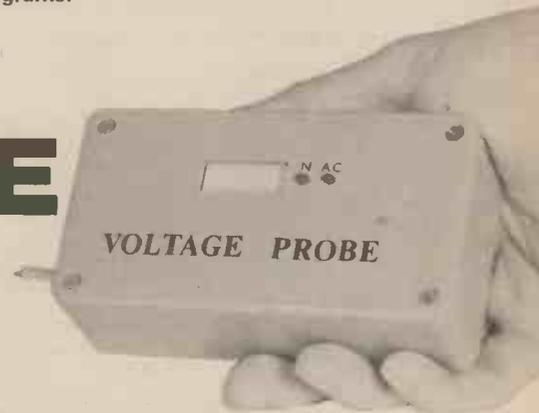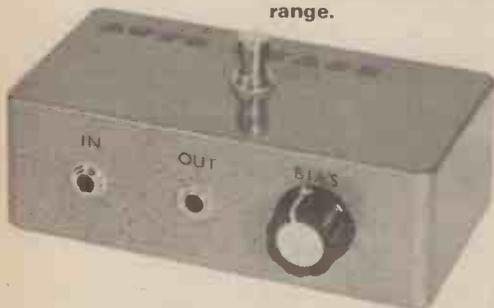This very useful hand-held probe is easy to use and gives an instant bar-graph display of voltage levels up to 12 volts on the low range, and up to 120 volts on the high range.



AUTO PHASE

Musicians—Build a really nasty foot controlled effects box. To be different, this phaser uses signal amplitude to shape the envelope. Auto-phaser is simple and economical to construct.

EVERYDAY ELECTRONICS and computer PROJECTS

MAY 1985 ISSUE ON SALE FRIDAY, APRIL 19

COMPUTER CLUB



Hallo, welcome to Computer Club. We'll be looking at a brand new game this month by Joe Drew. We will also be studying a very short program using a simple LOOP program structure for making a star move back and forth across the screen.



Let's look closely at the Bouncing Star program. The information in the 'clubs' are REMarks (REM for short) and has no effect on the program. Keep it there for future reference during the COURSE on how to write your own computer game BUT ALWAYS TYPE IN REM or these notes WILL become part of the PROGRAM and it will NOT WORK. Don't worry about the abbreviations used...
 COL is COLUMN
 CLS is CLEAR SCREEN
 VDU is VISUAL DISPLAY UNIT
 TAB is TABULATE

- 10 REM Title "Bouncing star"
- 20 ROW=10 REM star will travel along row 10
- 30 COL=0 REM star will start at column 0 which is on the left. NOTE! many items in computing start at 0 rather than 1
- 40 CHANGE=+1 REM change is the amount we add to "col" to change stars position. At first the star moves to the right so change = +1: when it hits the R.H. edge then we change direction by making change = -1
- 50 CLS First thing to do is to clear the screen
- 60 VDU 23,1;0;0;0;0; REM This makes the cursor disappear
- 70 INPUT TAB(0,20) "HOW MUCH DELAY", LONG REM This prints a message at col 0 row 20 asking you to input the length of delay in stars movement
- 80 REM up to here is "INITIALISATION"
- 90 REM *** Here is the beginning of the main program loop. NB There is no end to this loop so to stop the program you must press "ESCAPE"

LINK-UP

Link-up the letters to form a chain of words related to electronics.

START →	R	E	G	E	R				
Y	H	P	A	O	U	E	N	A	T
E	X	T	R	R	L	F	N	O	I
S	N	E	G	O	B	O	T	T	O
O	M	E	T	E	R	G	N	I	M
M	O	D	E	P	M	I			
E	T	E	R	E	X	P	O		
O	M	E	S	I	L	A	N		
S	F	L	T	T	M	I	E		
T	E	B	A	L	U	T	N		

WORD	CLUE
G _ _ R _ _ N	Feedback.
ELU _ _ _ P	Image on screen
X _ E _ S _ T _ R	MEASURES change
B _ _ _ _ G	Below the XNEE
_ P _ _ M _ _ _	Measures impedance
_ P _ _ _ _ _ L	...Curve
M _ _ _ _ T _ B _ _	Not one stable state
_ O _ _ _ I	Metal oxide...

by Thakery

Solutions on page 225

100 PRINT TAB(COL,ROW) "*" REM This prints the "*" at the current value of COL and ROW

110 FOR SLOW=1 TO LONG: NEXT SLOW
 REM This is the delay loop; it is a 'FOR' loop; the variable 'SLOW' starts with the value before the 'to' and is increased by 1 until it is greater than the value after the 'to' ie long

120 IF COL=39 THEN CHANGE=-1

130 IF COL=0 THEN CHANGE=+1

140 PRINT TAB(COL,ROW) " " REM This prints a 'space' over the 'star' to wipe it out from its old position

150 LET COL=COL+CHANGE REM This changes the value of COL in order to change position of 'star'


160 GOTO 100 REM Returns us to the beginning of main loop

170 REM END OF PROGRAM

180 REM Notice that we have GOTO 100. This brings up the point that line numbers in basic programs are used both to 'EDIT' programs while they are being written ie. to put the program into proper order even when its being changed.

190 REM and LINE numbers are used when the program is running so that GOTO statements have a (unique) way of identifying which line you are to GOTO.

>RUN PRESS 'RETURN' KEY

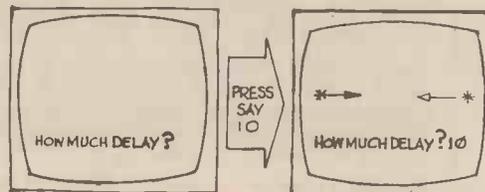

SEEKERS OF GOLD

Their quest to find the valley of the S... before. Although it actually a series of formed a total of 9 can you

CLICK
 click
 click

THIS HAPPENS EVERY WAKE UP AT THREE THE C...

This is a very easy game to play and like all great explorers requires patience

1

VALLEY OF THE SEAL
 KEY TEMPL
 9* GUOM 861
 P6 - TOWERS <91
 001 BAT .91
 V1@ CRAB .9#
 <91 ARCHES ?@-

TOMBS
 ZEN 01#
 SORAH <#
 FLUENT 4?@

Just follow the instructions at each stage and you won't get lost!

The object is very simple! Find the keys: to the Temples so that you may enter the Temple to find the letters for the codes on the R.H. side and so find the Gold Seal!

You can of course guess the key, but you will run out of guesses. OR you could enter the TOMBS first and there find the letters for the keys: So search for the TOMBS in the Valley (say No to Temples till you find the key) and you will gradually find letters to the keys-

2

Explorer has found a Tomb

Press the bar and you will enter the Valley. You will see nothing because the Temples and TOMBS will be hidden but move the explorer and see what happens!

CONTROLS

○ Tomb
 □ Temple

3

STATUS: HIDDEN

Signs on columns

When issue found a letter

Once you've said 'yes' to entering a Tomb a picture like the one shown will appear (A TEMPLE is the same but bigger)

The secrets of the Tomb will be hidden in certain columns. Choose the wrong one (remember the sign on the column) and you'll slip or be returned to the jeep. Return 3 times and you've FALLEN - return to maping and choose another Tomb.

Explore the right columns and arrows will appear directing you towards the secret.

Be careful! Avoid the forbidden signs and don't slip more than once or you'll return to the jeep. And be prepared for the unexpected!

CONTROLS



```

10MODE2:PROCse:REPEATIFA% PROCTab
20REPEATPROCmo:UNTILV%>0:S%=V%-4:L%?S%=0:F%=F%-1:W%=S%-(S%=1)*11
30 PROCv19(V%.W%):PROCTw(2):PRINTN$(S%) ":found"
40REPEATINUTTAB(7,2) "Enter (y/n) " TAB(17,2) T$:UNTILT$="y" ORT$="n"
50 COLOUR128:CLS:IFT$="n" PROCbrd(0,1):a%=0 ELSEPROCtry(C%,R%)
60UNTILF%=0:PROCv19(1,6):COLOUR1:VDU26,4:PRINTTAB(1,20)"Run out of sites!":EN
D
70DEFFPROCtry(C%,R%) a%=2:PROCTab:PROCTw(3)
80 IFS%<5 T%=0:T$="by Key" ELSE T%=1:T$="Free"
90 PRINTTAB(7,0) N$(S%) TAB(2,1)"Entry is " T$:IFT% PROCgt(2):GOTO120
100 T%=3:REPEAT:INUTTAB(0,2) "The KEY?" SPC12 TAB(8,2) T$:T%=T%-1:UNTILT$=K$(
S%) ORT%=0
110 IFT%=0 COLOUR6:PRINTTAB(0,2) "Too many guesses":a%=0:PROCgt(3):PROCv1:ENDP
ROC
120 VDU22,1:PROCv19(3,6):COLOUR3:PROCbrd(1,0)
130 K%=64:O%=0:f%=2:A%=0:PROCu(0):PROCq
140 T%=SGN(C%-x%?S%*5+1):W%=SGN(R%-y%?S%*4+1):N%=T%*8-(W%=1)*190+28
150 C%=608+T%*512:R%=480+W%*320:M%=N%:I%=C%:J%=R%:MOVEC%,R%:PRINTJ$:GCOL3,3:MO
VECX%,R%:PRINTM$
160REPEATPROCmo:V%=6%?N%:IFAZANDV%>5ANDV%<90 PROCfnd
170 IFAZAND(V%=10RV%=2)PROCaf ELSEIFV%=3 A%=(A%+1)MOD3:PROCu(A%)
180 IFV%=4 A%=0:PROCu(0) ELSEIFV%=5ANDAZ%>2 f%=f%+1:PROCu(f%):L%?S%=0
190 IFV%=4ORF%=4 X%=I%:Y%=J%:N%=M%:PROCshft(M$,M$)
200UNTILX%=I%ANDY%=J%ANDZ%=5:a%=1:F%=1:ENDPROC
210DEFFPROCfnd LOCALC%,R%:PROCwr:FORP%=0TO262:PROCv19(3,P%):NEXT:PROCwr
220 GCOL0,1:T%=0:FORR%=96TO864 STEP64:FORC%=64TO1216 STEP64
230 W%=6%?T%:IFW%ANDW%<6 MOVEC%,R%:VDU238 ELSEIFW%>V% THEN250
240 FORP%=1TOU%:IFh%?P%=T%:h%?P%=0:NEXT ELSENEXT
250 T%=T%+1:NEXT:NEXT:GCOL3,3:6%?N%=0:PROCq
260 PROCst(V%):PROCwr:IFL%?S%=0 PROCu(5):f%=4:ENDPROC ELSEENDPROC
270DEFFPROCwr MOVEX%+32,Y%:VDUV%:ENDPROC:
280DEFFPROCst(T%) LOCALO%,S%:IFT%=0THEN330
290 V%=0:REPEATV%=V%+1:UNTILEX%?V%=T%:V%=V%+96
300FORS%=0 TO4:W%=C$(S%):T$=""
310 FORP%=1 TOLENW$:M$=MID$(W$,P%,1):IFM$=CHR$T% T$=T$+CHR$V% ELSE T$=T$+M$
320NEXT:C$(S%)=T$:NEXT
330Q%=0:FORS%=0TO7:W$=H$(S%):W%=LENW$:IFW%=0THEN360
340 T$="":FORP%=1 TOW%:M$=MID$(W$,P%,1):IFM$<>CHR$T% T$=T$+M$:Q%=Q%+1
350 NEXT:H$(S%)=T$
360L%?S%=LENH$(S%):NEXT
370 M$=CHR$239+CHR$8+CHR$11+CHR$240:IFQ%ENDPROC
380 VDU26:MOVE0,1020:GCOL0,3:FORP%=0TO70:PRINT"The seal is found";:NEXT:VDU24
,320;192;928;864;16
390 W%=0:GCOL0,2:X%=288:Y%=224:S%=1:REPEATI%=I%(S%)-15:PROCv:V%=247
400REPEATPROCwr:V%=V%+1:X%=X%+64:IFX%=928 X%=288:Y%=Y%+64
410UNTILV%=252:W%=W%+1:S%=(S%+1)MOD8+1:UNTILW%>23:END
420DEFFPROCu(A%) VDU4,30:PRINT"Status: " A$(A%):VDU7.5:ENDPROC
430DEFFPROCq Q%=0:FORP%=1 TOU%:W%=h%?P%:IFW% Q%=P%
440NEXT:ENDPROC
450DEFFPROCmo REPEATZ%=0:V%=0:X%=C%:Y%=R%
460 IFINKEY(-58) Z%=1:Y%=R%+K%:W%=N%+19:V%=FNsk(C%,C%+104,Y%,Y%)
470 IFINKEY(-42) Z%=3:Y%=R%-K%:W%=N%-19:V%=FNsk(C%,C%+104,R%-36,R%-36)
480 IFINKEY(-122) Z%=2:X%=C%+K%+O%:W%=N%+1:V%=FNsk(X%,X%,R%-28,R%)
490 IFINKEY(-26) Z%=4:X%=C%-K%:W%=N%-1:V%=FNsk(X%,X%,R%-28,R%)
500 IFINKEY(-74) Z%=5 ELSEIFZ%ANDK%=64 V%=FNpt
510UNTILZ%>0ANDV%>TRUE:IFZ%=2 X%=X%-O%
520IFK%=64 N%=W%:PROCshft(M$,M%):ENDPROC ELSEIFV%=0ANDK%=8 PROCshft(B$,J%):END
PROC

```

Only part of the program is given above, more will appear in the next "Computer Club".
 A cassette tape of "Seekers of the Gold Seal" is available for the BBC Micro from the editorial office, price £2.30 including VAT and postage.

ON SPEC

*a regular
feature for
the Spectrum
Owner...*

by Mike Tooley BA

THIS MONTH, as promised, we shall turn our attention to a simple four channel input interface for use with the Spectrum and Spectrum-Plus. This device will allow you to connect up to four switches or TTL-compatible devices which can be "sensed" by the Spectrum in order to determine whether they are "on" or "off". Before going further, let's briefly consider a practical application of such an interface in the form of an "intelligent" security alarm.

Intruder Alarm

Suppose that we wish to protect a room against intruders. To each door and window we could fit a magnetic reed switch. These switches would open whenever their respective window or door is opened and close whenever their respective window or door is shut.

Assuming that the room has three windows and one door, each of the four reed switches could be wired to its own input on the interface. With the aid of some relatively simple software (written in BASIC) it is possible to repeatedly sense the state of all four switches. We could then arrange for an alarm signal to be generated whenever any one, or more, of the switches was found to be open and print an appropriate warning message on the screen to indicate which entrance has been opened.

Sounds complicated? Not at all, the four channel input interface requires only three common TTL integrated circuits and can be built in less than an hour for an outlay of less than £5! The added bonus with using a computer as an

"intelligent" controller is that it becomes very easy to make changes to the operation of the system by simply altering the control software.

If, for example, we wished to incorporate some sort of delay in order to permit brief opening and closing of the door without setting off the alarm, all we need to do is include a suitable delay loop (or PAUSE in ZX BASIC) within our control program. Alternatively, we could include a routine within our software to record each individual opening and closing of a door or window storing also the time and period for which the door or window was opened.

Hardware

The complete circuit of the four-channel input interface is shown in Fig. 1. An eight-input NAND gate, IC2, is used to partially decode the address bus, $\overline{\text{TORQ}}$ and $\overline{\text{RD}}$ signals in order to produce an active-low enable signal for the four-channel tri-state multiplexer, IC3. The decoding produces a low signal to enable IC3 whenever the following address and control bus pattern appears:

$\overline{\text{TORQ}}$	$\overline{\text{RD}}$	A7	A6	A5	A4	A3	A2	A1	A0
0	0	1	X	X	1	1	1	1	1

(where X = don't care)

It should be noted that the $\overline{\text{TORQ}}$ and $\overline{\text{RD}}$ control lines go to logic 0 whenever the Z80 CPU executes an IN instruction (corresponding to the ZX BASIC IN function).

Further address decoding is provided within IC3 which has its select inputs connected to A5 and A6 of the address bus. The particular input port selected is thus governed by the state of these lines and, assuming that all of the other address bus lines are "high", the input port assignment is as follows:

A6	A5	INPUT PORT (decimal)	INPUT CHANNEL (fed to D0 line)
0	0	159	A
0	1	191	B
1	0	223	C
1	1	255	D

The four 1k resistors connected to each input line act as "pull-up" resistors and ensure that a disconnected line or switch open produces a "high" or logic 1 input. Conversely, a closed switch produces a "low" or logic 0 input.

Construction

The interface components are assembled on a small piece of Veroboard measuring approximately 80mm x 80mm. Whilst the precise dimensions of the board are not critical, it must have a minimum of 28 tracks aligned in the vertical plane. The 28-way double sided edge connector is mounted along the bottom edge of the board and will require approximately 5 rows of holes across the full width of the stripboard. The board will thus stand vertically when the connector is mated with the Spectrum.

Before soldering any of the components to the stripboard, it is important to leave some clearance for the rear "overhang" of the case. For the Spectrum this gap should correspond to 8 rows of holes (20mm approx.) whilst for the Spectrum Plus the gap should be increased to 12 rows of holes (30mm approx.).

Whilst component layout is not usually critical, care should be taken to ensure that the supply decoupling capacitors, C1 to C3, are distributed around the board (each preferably associated with an individual integrated circuit supply). Great

care should be taken to ensure that all unwanted tracks are cut (including those which link the upper and lower sides of the 28-way connector).

A purpose designed 'spot-face' cutter may be used for this purpose or, if such a device is not available, use can be made of a small sharp drill bit.

Links on the underside of the board are best made using appropriate lengths of miniature insulated wire of the type normally employed for wire wrapping. Readers requiring further information on the connector should refer to last month's *On Spec*.

When the stripboard wiring has been completed, the three integrated circuit devices should be inserted into their respective sockets (taking care to ensure correct orientation) and the entire board should be carefully checked before connecting to the Spectrum. Note that the Spectrum should *always be disconnected from its supply* before either connecting or disconnecting any interface module.

If all is well, when power is re-applied, the normal copyright message should appear. If not, disconnect the power, remove the interface and check again.

Software

The status of the four input channels may be read from BASIC using IN (port number). For example, to assign the current value of channel D to a variable, d, we could use the following BASIC program line:

```
110 LET d=IN 255
```

Since all of the unused data lines (D1 to D7) will be at logic 1, the value of d will be either 255 or 254 depending upon whether the switch is open (D0 = 1) or closed (D0 = 0) respectively. The following program prints the logical state of input channel D:

```
110 LET d=IN 255
```

```
120 LET d=d-254
```

```
130 PRINT d
```

This simply returns "1" for switch open and "0" for switch closed. Alternatively we could use:

```
110 LET d=IN 255
```

```
120 IF d=255 THEN PRINT "off"
```

```
130 IF d=254 THEN PRINT "on"
```

Sensing

Either of the above routines can be incorporated into a loop so that the state of the input line is repeatedly sensed. In a practical situation, however, it is a good idea to include PAUSE between statements containing IN, as shown in the following program which prints the status of all four input channels (1 = "off", 0 = "on"):

```

1 REM Displays the logical
2 REM state of inputs A to D
105 PAUSE 10
110 LET d=IN 255
112 LET d=d-254
115 PAUSE 10
120 LET c=IN 223
122 LET c=c-254
125 PAUSE 10
130 LET b=IN 191
132 LET b=b-254
135 PAUSE 10
140 LET a=IN 159
142 LET a=a-254
145 PAUSE 10
150 PRINT AT 0,0; "DCBA"
152 PRINT AT 2,0;d;c;b;a
155 GO TO 105
    
```

A complete listing of an intelligent security alarm program is included in our first "Spectrum Update". To receive your copy, you need only send a large stamped addressed envelope to:

Mike Tooley,
Department of Technology,
Brooklands Technical College,
Heath Road,
WEYBRIDGE,
Surrey,
KT13 8TT

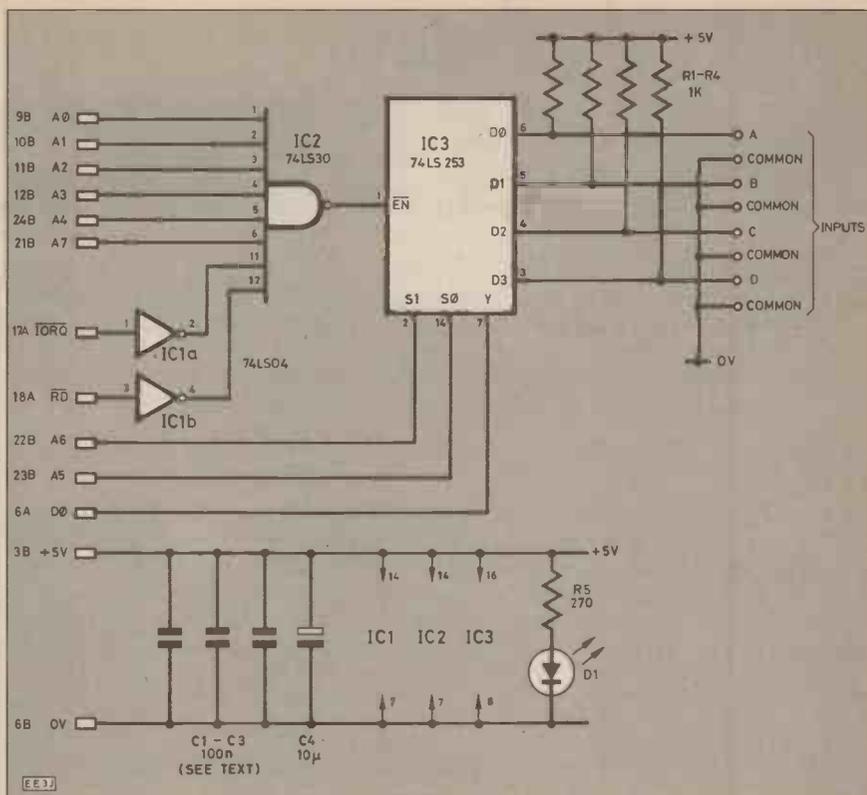


Fig. 1. Circuit diagram of the four-channel interface for the intruder-detection system.

COMPONENTS

Semiconductors

IC1	74LS04
IC2	74LS30
IC3	74LS253
D1	Red l.e.d.

Resistors

R1-R4	1k (4 off)
R5	270
All 1/4W ±5%	

Capacitors

C1-C3	100n polyester (3 off)
C4	10µ 16V electrolytic

Miscellaneous

14-pin low-profile sockets (2 off)
16-pin low-profile d.i.l. socket (1 off)
28-way open end double-sided 2.54mm pitch connector
Terminal pins (8 off) or 8-way 2.54mm pitch p.c. connector
2.54mm hole pitch stripboard measuring approx. 80mm x 80mm (minimum 28 strips)

See
**Shop
Talk**
page 199

COMPONENTS
approximate
cost **£5.00**

It is worth noting also, that a firm called Kelan Engineering make a standard prototype kit for Spectrum and Spectrum-Plus interface projects, which includes double-sided connector, stripboard, and case.

Kelan are at 27-29 Leadhall Lane, Harrogate, and at around £9, their HB/2090 interface port would seem to be

good value. We hope to have more information on interfacing kits in future articles.

Finally, don't forget to include any comments, queries, or suggestions for inclusion in *On Spec*—see you next month!

NEXT MONTH: Interfacing temperature and light sensors.

PAYPHONES for the 21st CENTURY

- * An entirely new range of up-to-date telephone booths will be appearing on Britain's streets as part of a major "shake-up" of BT's payphone services.
- * All new booths will be equipped with the latest push-button payphones.

A GLIMPSE of the 21st Century was the claim being used by British Telecom with the unveiling of a £160 million investment programme to introduce a completely new range of modern telephone booths, using the most up-to-date electronic payphones and new concepts in cashless calling.

Introducing the modernisation programme, Mr Iain Vallance, BT's Managing Director, Local Communications Services, said: "The New British Telecom will take a radical approach to the problems inherent in today's outdated payphone service.

"We aim to encourage greater use of payphones by making them more convenient and attractive to use and by extending the facilities they offer . . ."

Added Mr Nick Kane, Director of Marketing "We are spending £35 million on these new booths over the next ten years and a further £125 million on payphone equipment.

"The familiar red kiosks will not disappear immediately. They may be kept where there are special local reasons such as in conservation areas. But they no longer meet the requirements of our customers. Few people like to use them.

"We are also planning to have payphones which take ordinary credit cards or no cards at all—a customer's own identification number will do".

Kiosks

The new booths have been specially designed with the needs of the handicapped in mind and allow easy access by wheelchair users. It is claimed that they are cheaper to maintain, more brightly lit and fitted with sound proofing and vandal-resistant panelling.

The old traditional, warm and cosy, "red" telephone/bus kiosk was first introduced in 1936 and was operated by the now famous "push button A and button B" sequence. The new, in some cases open to the elements, push-button payphone booth is ideal for wheelchair-bound users.



The range consists of models with and without doors, "walk-in" booths and hoods which cover only the telephone equipment. Decisions on which designs to use at which sites will be taken locally by district managers.

Back-to-back pedestal booths is one solution to the problem of fitting them into crowded town



The new CreditCall phones are fully automatic and accept Access, Visa and American Express charge and credit cards.

Calls from these phones cost the same as normal coin operated ones but there is a 50p initial charge for five units. The cost of calls is charged to the user's credit card account in the normal way.

centre sites. Future designs, for shopping precincts, concourses and busy sites, will also include a triangular-plan design.

The full length booth will be used in quieter locations where traffic noise does not intrude on the conversation. The open design does not allow litter or smells to accumulate but still protects the equipment and the user from the elements.

All new booths will be equipped with the latest push-button electronic payphone.

Payphones

Two new types of cashless payphones are planned. The first service, entitled CreditCall, operates on a customer's own credit card, such as Access, Visa or American Express. The customer inserts his or her card in a special unit attached to the payphones. This reads the card, records the details of the call and transmits the information to special equipment in the telephone exchange. The customer is then charged on his credit card account in the usual way.

Trials are being held in London, at Heathrow Airport, and British Rail Waterloo. The

Heathrow experiment involves equipment fitted with an automatic "voice response" message to guide users.

The other service, entitled AccountCall, will soon go on trial in Bristol. Modern push-button payphones are used, linked to special equipment at the exchange.

The customer dials his account number and personal identification code number before making a call. The call charges are then added to the user's home or business telephone account.

Other payphone developments for the future include extending the "Trainphone" trial on British Rail's Western Region to other services and the introduction of public payphones on express coaches and ferries. This service would be through BT's radio network.

It's not often that you can find fault with BT's services or new products, but in this case for the sum of £160 million a "multipurpose" booth that accepts cash as well as credit cards is surely to be expected. After all not everyone wants to become reliant on "credit cards".—See Barry Fox's comments in "For Your Entertainment", page 224.

SKY RIDER

Cars guided by satellites are being developed by Austin Rover. Just as satellites help with ships navigation, so they will be linked by computer to vehicles to tell the driver which way to go for the quickest, least hazardous or less congested route.—Who knows they may even be able to monitor vehicle speeds on motorways and so prevent some of the fatal pile-ups!

This small peep into the future came about recently when Austin Rover's chief executive, Mr. Harold Musgrove, opened an Advance Technology Centre at Warwick University. The centre is to research ways of applying aerospace technology to the design of future family cars.

Eric Sawkins has been appointed Land-based Sales Manager of Electra Communications, a division of the Marconi International Marine.

Name Change

When Computer Link (UK) Ltd., was first registered a search of UK company names was made but not of foreign registrations. It now transpires that a foreign company exists which has exactly the same name.

Although the foreign company does not supply the same goods they have raised strong objections to the use of the name. So Computer Link (UK) have agreed to change their name. In future they will be trading as R.S.D. CONNECTIONS LTD., PO Box 1, Ware, Herts.

Honeywell on Dole

The prestigious contract to supply minicomputers and terminals to the DHSS for unemployment benefit offices has been awarded to Honeywell Information Systems.

The contract was won from a short list including Honeywell, British Telecom and Standard Telephone & Cables.



BBC SHUT-DOWN

A milestone in the history of British broadcasting came to a close recently when all of the remaining BBC 405-line transmitters were switched off.

When the 405-line service started in 1936 it was described as "The World's first regular public service of high-definition television programmes". The number of viewers had been dwindling since the introduction of the duplicate 625-line ultra-high frequency (u.h.f.) colour service in 1969.

The closure comes as the result of an announcement by the Home Secretary in 1983 that the frequencies used by the 405-line transmitters should be released by the broadcasters for mobile radio communication. The close-down of the last transmitter, at Melvaig in West Scotland, was carried out by Syd Garrioch, the local transmitter manager.

In its hey-day, the 405-line network comprised one hundred and seven transmitters.

Former Engineer-in-Charge at the BBC's Crystal Palace (London) transmitter station, Bill Busby, switched off the 405-line sound transmitter on 2 January 1985.

The purchase of a 27,000 square metres manufacturing facility in Taiwan is announced by Motorola.

Situated in Chung-Li, it will be used to manufacture, assemble and test a variety of products, including integrated circuits.

Cellnet Captures Birmingham

Cellnet became the first cellular operator to move outside the London area when the service opened in the Midlands at the beginning of February. The historic first call was made during a conference held at the Hilton, Park Lane and was seen by the guests by means of a live video link.

The initial City of Birmingham service allows existing customers (more than 750) to extend their use of the system. Additional "cells" will be added over the next few weeks to offer a comprehensive coverage of the West Midlands area.

Work has now started on more than 100 cells which will extend the service along the motorways radiating from London to cover, Birmingham, Liverpool, Manchester and Leeds by April, and Severnside and the south coast from Bournemouth to Brighton by June.

A TOUCH OF CLASS

Now firmly settled in their new modern 9,200 sq ft premises, Watford Electronics have come a long way in only twelve years. Thanks to the entrepreneurial skills of their Managing Director, Mr N. Jessa, they topped the £5 million turnover figure last year, mainly through mail order.

The new premises, located in the High Street, Watford, have been specially designed to meet their every need. This includes improved storage, packing and administration areas, plus customer car parking facilities in front of the building.

Watford stock a very large range of general components, including probably one of the most comprehensive stocks of i.c.s and microprocessor chips in the UK. Also, the range of custom designed BBC Micro peripherals has been highly acclaimed by both amateur and professional alike.

Their pricing strategy on all computer based items is second to none and a visit to their new demonstration "studio" is to be recommended. Their full address is: *Watford Electronics, Jessa House, 250 High Street, Watford, Herts, WD1 2AN.*



FAULT FINDING

E.A. Rule Part 6

THE cassette recorder is found in most homes these days, either used as a means of reproducing music tapes or used with a home computer. In general these machines are very reliable, but they can and do go wrong. From time to time they require servicing if maximum performance is to be maintained. In view of this a brief look at some of the common faults may be helpful.


COMMON FAULTS

One of the most common faults to come into the workshop is where the cassette recorder will not record, and will only replay with either low output or very poor frequency response. In almost every case this is due to dirty record/replay heads. The oxide wears off the tape and builds up onto the heads and tape transport mechanism resulting in the head gap being filled with oxide dust.

Recording/replay heads have a very small gap across which the magnetic flux is transferred either from tape to head or head to tape. Once this gap is filled with oxide dust it is in effect 'shorted out' and it becomes impossible to record. Long before this happens however there is a gradual falling off in high frequency response and volume on replay. This dust can also affect the erase head causing poor erasure and leaving a residual on the tape from earlier recordings.

The first job when servicing a cassette recorder then is to clean the heads and tape transport mechanism. To make a thorough job of this the unit should be removed from its case so that it can be worked on in the open. First clean the heads using a cotton bud (these can be obtained from most chemists) soaked in a specialised video-head cleaning fluid. Gently wipe the cotton bud across the head and also up and down along the line

Fig. 1. Typical cassette recorder layout (before removal from case).

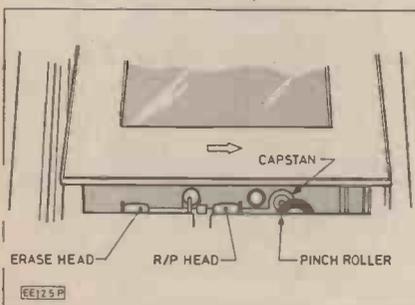

of the gap, with really dirty heads you may need to repeat this a number of times. The final cotton bud should be a clean one. Then use a *dry* cotton bud to finish off.

Once the heads are cleaned, use the same method to clean the tape guides, capstan and pinch roller. Be thorough in your cleaning or you may get misleading results later during the service. Sometimes the capstan is so dirty that a cotton bud just will not remove the oxide dust, in these cases hold a small screw driver blade *very gently* against the capstan while it is rotating and then finish off again with the cotton buds. Use only gentle pressure and *do not touch the heads* with the screwdriver.

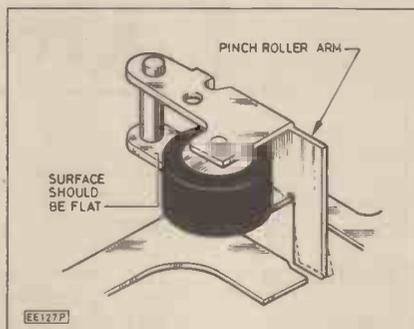


Fig. 2. Pinch roller assembly. Its surface should be flat. Clean with same solvent used for the heads.

Oxide on the capstan can be one reason for a variation in tape speed resulting in a high level of 'wow' but another cause is a faulty pinch roller. The surface of this against the capstan should be clean and flat as its job is to keep the tape in constant contact with the capstan, see Fig. 2.

After much use they become distorted and the surface becomes rounded, when this happens it can cause tapes to 'ride' up and jam. A replacement pinch roller is the only satisfactory answer and you may need the services of a skilled engineer to effect a replacement.

Another cause of speed variations is grease on a drive belt or motor pulley, these can also be cleaned with cotton buds etc. but often the drive belt will be found to have stretched and a replacement may well be required.

Another fairly common fault on cassette units is oscillation on replay. Quite a number of cassette recorders are

received with this symptom in the author's workshop. The cure is simple. Clean the record/replay switching. To do this use an aerosol switch cleaner spray to spray the switch contacts and then operate the switch a number of times. This will clean off the tarnish and oxide from the contacts and it is the high resistance due to this that causes the oscillation. (This is because both inputs and outputs are switched via the same contacts on many cassette recorders.)

Note, because most cassette recorders have a mechanical interlock to prevent accidental recordings, this will prevent the record/replay switch from operating, a simple method of overriding it while cleaning switches is simply to fit a blank cassette into the recorder. (One which has not had the anti-recording tabs removed.)

Do not be tempted to adjust any presets you may find around the recorder. If these are incorrectly set you will need a special recording tape to reset, and these test tapes can set you back about £25, so I repeat do not be tempted unless you really know what you are doing.

Electronic faults can be traced in much the same way as already described in earlier parts of this series. However, an oscilloscope will be found most helpful because in many parts of the circuit you will be dealing with very small audio signals mixed up with high frequency bias signals. Without a scope you will not know what you are measuring. Once servicing is completed the final job should be to demagnetise the heads and tape transport. Suitable demagnetisers are available from a number of sources at reasonable cost and the improvement in signal to noise on recordings makes the investment worth while.

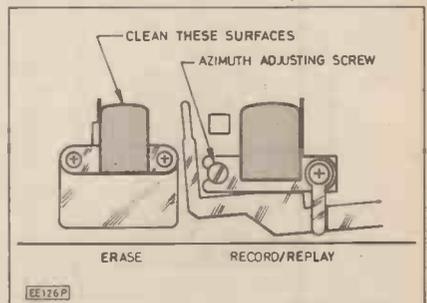


Fig. 3. Enlarged view of heads. These should be cleaned with a specialised head cleaning fluid, such as Bib Video head cleaning fluid.

HEAD CASE

I have not yet mentioned the azimuth adjustment of the record/replay head. To adjust this correctly requires the special test tape, however if the head has been changed or otherwise removed for some reason it is possible to get near to the correct setting by using a good quality commercial music tape. Simply adjust the azimuth screw for maximum high frequency sounds, see Fig. 3.

Worn heads can cause many problems. At first the high frequency starts to fall, then the output volume. Later 'flutter' increases and in extreme cases damage to tape results. The author once had a cassette in for service where the record/replay head had a hole in the front where the gap should be. The customer complained that it was chewing up tapes, no mention of the poor sound quality, it takes all sorts.

Replacing a worn head is not difficult providing you can obtain a suitable replacement. A number of stockists now carry replacement heads and if you tell them the type of machine you have they will advise you on a suitable replacement.

Having obtained a suitable replacement (check it has the same connections) carefully unsolder the leads to the old head, noting which colour leads go to which tag. Remove the old head by undoing the two fixing screws (one each side) one of which will be the azimuth adjustment screw. Note how many turns this re-

quires to remove the head because when fitting the replacement you can screw it down by the same amount. This simple measure will ensure that the azimuth is reasonably near the correct setting. Be careful not to lose any springs, washers etc. It may be easier to solder the leads to the new head before fixing it into position, but this is really a case of personal choice. Be careful not to let the front surface of the new head touch any hard object which could scratch or damage it.

After fitting and setting the azimuth the whole mechanism should be demagnetised. If you have fitted the correct head no difficulties should ensue.

To check for head wear, take a look at the gap surface with a magnifying glass, it should have a 'mirror' finish and be perfectly smooth. If its rough, scratched, or uneven it should be replaced. Erase heads in general do not need replacement and although the author has found about 50 percent of cassettes need new record/replay heads I have never had to replace an erase head. Most cassette recorder faults are due to the mechanical faults mentioned. Electronic faults, if found, can be traced using the same methods as for other equipment.

Next month (final part) we shall look at the various service aids that are available.



Multicore makes soldering easy, fast and reliable




Ersin Multicore
Contains 5 cores of non-corrosive flux.
Uses: For all electrical joints.
Handy Pack: Size 19A 60/40 tin lead 1.22mm dia £1.50 Tool Box Reel: Size 3 60/40 tin/lead 1.6mm dia £4.37



Ersin Multicore
Contains 5 cores of non-corrosive flux.
Uses: Small transistors, components and fine wire. Handy Pack: Size PC115 60/40 tin/lead 0.7mm dia £1.61 Tool Box Reel: Size 10 60/40 tin/lead 0.7mm dia £4.37



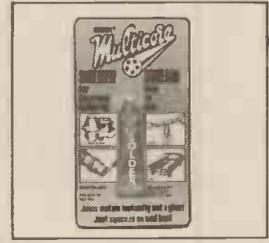Multicore Savbit
Increase the life of your soldering bit by 10 times. Uses: For all electrical work. Reduces copper erosion. Handy Pack: Size 5 1.2mm dia £1.38 Tool Box Reel: Size 12 1.2mm dia £4.37



Multicore Solder Cream
Mixture of powdered 60/40 (tin/lead metal alloy and rosin flux). Uses: Micro electronics and printed circuits. Handy Tube: Size BCR 10 £1.73



Multicore All Purpose Handyman Solder Pak
Contains three types of solder for electrical, metal and aluminium repairs, all in handy easy to use dispensers. Handy Pak: Size 8 £2.99



Bib Wire Strippers and Cutters
With precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles. Wire Strippers: Size 9 £2.99



Multicore Solder Wick
Absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds. Handy Pack: Size AB10 £1.43



Bib Audio/Video Products Limited, (Solder Division),
Kelsey House, Wood Land End, Hemel Hempstead, Hertfordshire, HP2 4RQ
Telephone: (0442) 61291 Telex: 82363

If you have difficulty in obtaining any of these products send direct adding 50p for postage and packing. For free colour brochure and hints on soldering booklet send S.A.E. All prices stated are Recommended Retail and include VAT

FIBRELARM

GIDEON TEARLE

THIS loop alarm system was developed as a unit which could be used as an alternative to conventional wire loop alarm systems which have one major drawback as shown in Fig. 1. This drawback was obviously one which needed to be eradicated, so a more effective loop alarm system was devised using a fibre optic loop.

OPTIC FIBRE

Optic fibre (or fibre optic) is a polymer strand encased in a protective sleeving.

the optic fibre and then picking it up at the other end, and comparing it with the original light source.

CIRCUIT DESCRIPTION

The full circuit diagram of the Fibrelarm is shown in Fig. 2. The mains voltage is stepped down by T1 to 6.3V a.c. which is then rectified by REC 1 and smoothed by C1 to give 9-10V d.c. Power is then applied to D1 and S1 with D1 lighting to show when the unit is connected to the mains.

R5 when pin 3 is high. TR2, a phototransistor at the other end of the optic fibre turns on when it detects light. Its collector is used to turn TR3 on simultaneously. TR3's collector is held low by R6 when TR2 is not conducting.

LIGHT LEVELS

If the logic levels at TR1's collector and TR3's collector are the same, the l.e.d.s, D4 and D5, will not light. This will only be the case if TR2 is receiving light at exactly the same time as D3 sends it, which means that the optic fibre must be in place. If the optic fibre is not in place and TR2 receives daylight constantly then TR3's collector will be high even when TR1's collector goes low. This will cause D4 to light every time TR1's collector goes low.

If the opposite happens and the optic fibre is broken in darkness, TR2 won't conduct so neither will TR3. This means that D5 will light every time TR1 conducts and its collector goes high. In the event of either of the two l.e.d.s going on, TR4, a second phototransistor, will conduct due to its nearness to the two l.e.d.s.

When it conducts it turns on TR5 which in turn energises the relay whose normally open contact keeps the relay on whether or not TR5 is still conducting. The normally closed contact and the common contact of the relay keep the negative terminal of WD1 high when the relay is unenergised, but when the relay energises the negative terminal is brought low by R7 and thus the alarm sounds.

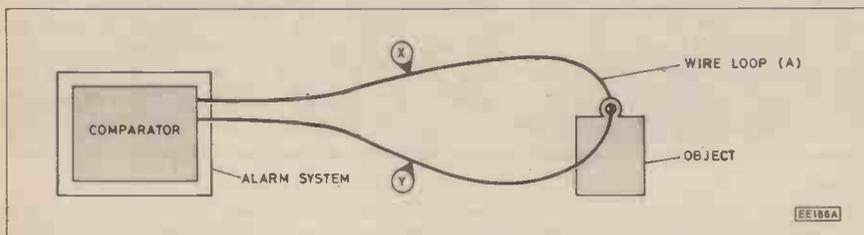


Fig. 1. Conventional loop alarm. The loop can easily be bridged between X and Y, which would foil the system.

The polymer strand is capable of transmitting light round bends whilst still maintaining the brightness and colour of the light.

Thus optic fibre seemed to be the ideal loop. All that had to be designed was some way of sending a light signal down

When the key switch, S1, is closed, power is applied to the rest of the circuit, indicated by D2 lighting. The timer i.c., IC1, and its associated components, R2, R3 and C2, cause pin 3 to alternate between low and high at about six cycles per second. This is used to flash D3, a red l.e.d. shining down the optic fibre loop. The signal also causes TR1 to turn on in sympathy, whose collector is held low by



CIRCUIT BOARD

The circuit is constructed on a p.c.b. as shown in Fig. 3 and Fig. 4. The 555 timer can be mounted on an 8 pin d.i.l. socket at the constructor's discretion. First assemble the printed circuit board and the drill holes in the box to accommodate the components as shown in the photo. All components not mounted on the board except for S1, T1 and D1 should be glued in place (Solderglue was used in the prototype). S1 and T1 should be bolted as

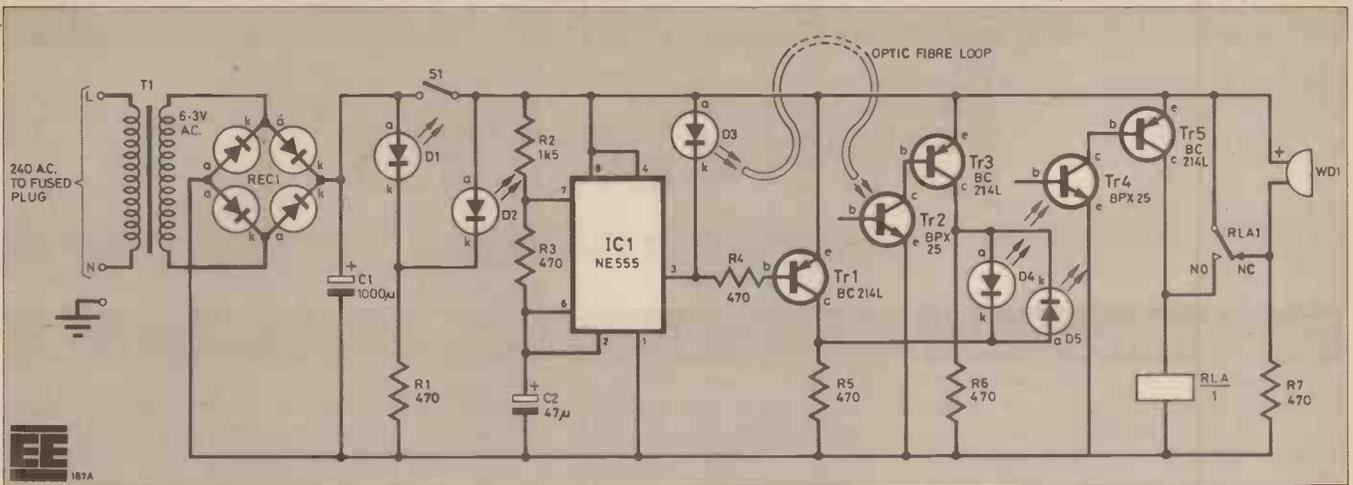


Fig. 2. Complete circuit diagram of the Fibelarm.

place as shown. Then join all off board components to the board using fairly short wires and Veropins at the board end.

The connection between the mains and the primary side of the transformer should be achieved using a terminal block.

OPTIC FIBRE

The optic fibre should be cut off to the desired length with about $\frac{1}{2}$ cm of the sleeving removed from one end. This

should be done very carefully as the sleeving is thick but the fibre is brittle and very easy to fracture. The two ends should be cleaned up by firstly using some fairly coarse sandpaper then draw file the ends with a very fine file.

Check that the ends are good by holding one end up to a light, the light seen at the other end should be exactly the same colour and about the same brightness. It should be realised that the whole unit will not work effectively unless the optic fibre is well polished and unfrac-

tured (the fibre will fracture if it is bent into very small curves).

So that the loop can be removed when the unit is switched off, it is only fixed at one end. The end of the optic fibre which has been stripped is held in place on the board, whilst the end in contact with D3 is inserted into a piece of sleeving stripped from 1 core screened cable into which the diode is fitted as shown in Fig. 6a.

Fix the diode in as shown and then glue the other end of the piece of sleeving into the hole for it in the box. The end of

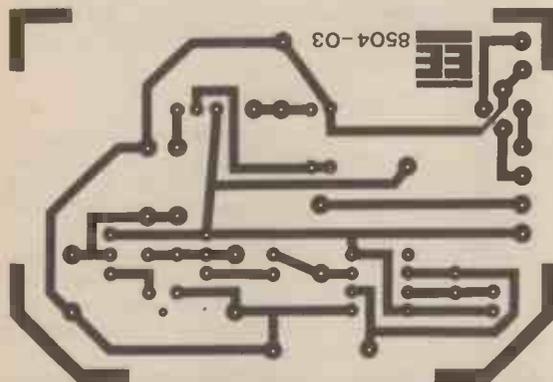


Fig. 3. Actual-size master pattern of the p.c.b. Available from EE PCB Service: Code 8504-03.


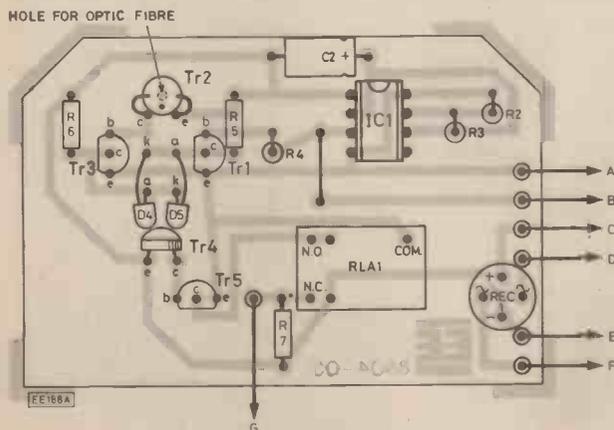


Fig. 4. Component layout of the Fibelarm.

Fig. 5. Wiring diagram of the Fibelarm.

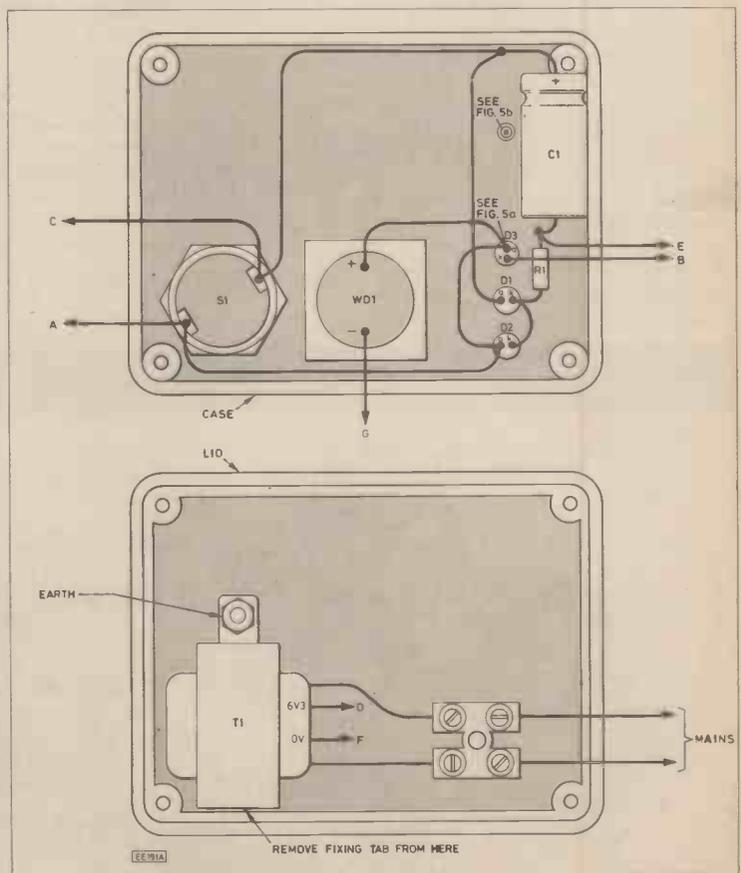

the optic fibre in contact with TR2 should be fixed as shown in Fig. 6b, remembering first to stick a small piece of the sleeving mentioned above into the hole shown and then thread the optic fibre through the sleeving. On no account use Superglue on the optic fibre as this greatly weakens it.

Do not put the back on the unit until you have tested and set up the unit.

TESTING

When the unit is built check over the printed circuit board for joined tracks and incorrectly orientated components. If all is well check the off board components for loose connections and joined wires. Also check the orientation of l.e.d.s.

Next disconnect one of the terminals of the buzzer to preserve your sanity when you come to test the alarm, then connect the unit to the mains making sure the plug is fitted with a 3 amp fuse and that the key switch is in the OFF position.

The l.e.d. marked MAINS ON should light. If it doesn't disconnect the alarm immediately and check the wiring of the mains to 9-10 volts d.c. section of the circuit for faults. If all is well and there are no faults, turn the key switch to the ON position. The l.e.d. marked ALARM ON should light.

Insert the optic fibre and darken the room. Then move the phototransistor, TR2, so that the stripped end of the optic fibre (which you should put through the hole directly underneath TR2) is in contact with the transistor. Move the phototransistor around further so that D4 and D5 flash dimly or not at all; the dimmer they flash the more effective the unit will be. Try to make sure that as you do this the only light source that TR2 can pick up is that from the optic fibre.

When you are happy with the position of the transistor, reconnect the buzzer (after you have turned off the mains) and then put the back on the box. Plug the unit back in to the mains and then break the optic fibre (it is probably easier and financially more beneficial to simulate the breaking of the optic fibre by removing it

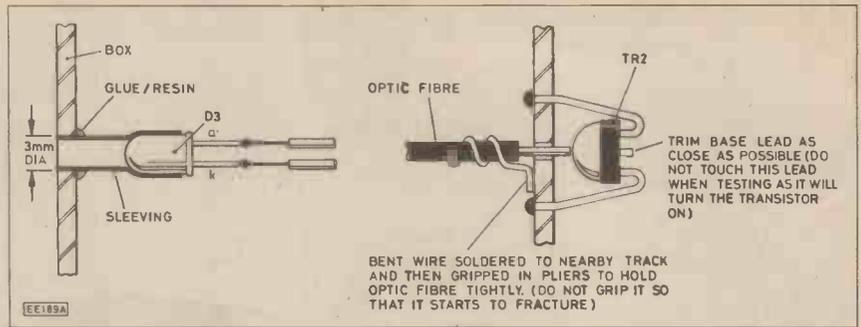


Fig. 6a. The sleeving mounted in the box.

Fig. 6b. Mounting of the optic fibre.

from its piece of sleeving making sure that you remove the optic fibre from the right piece of sleeving).

If the unit is working properly, the buzzer should go off as you 'break' the optic fibre. If it doesn't the problem probably will lie in the positioning of the optic fibre and the phototransistor. If the reader finds that it is very hard to position the optic fibre correctly, it may be wise to

place where it could be easily unplugged, it would seem wise to add some extra components to the circuit as shown in Fig. 7. This expansion will give a certain amount of extra protection in the event of a power cut or when the system is unplugged whilst the key switch is in the ON position. To make this adaptation it may be necessary to use a larger box and to slightly alter the p.c.b.

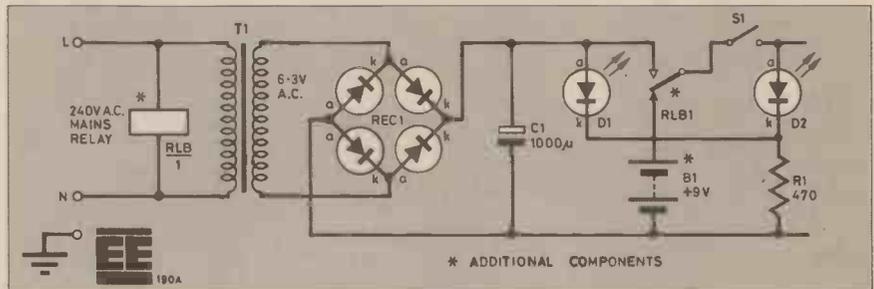


Fig. 7. Additional protection provided by 'mains fail' circuit.

change the phototransistor and replace it with a photodarlington which is more sensitive; a suitable one would be the µE MELL 11. Once the unit works, apply any dry transfer lettering. It may be wise to mark the piece of sleeving connected to D3 so that its obvious which end of the fibre is the mobile one.

FURTHER PROTECTION

If the unit is likely to be in a vulnerable

FREQUENCY

The three components R2, R3 and C2 are only given suggested values. These values may be altered to give different pulse rates at the reader's discretion. It is advised that if the reader wishes to change any of the three values, then IC1, D3, R2, R3 and C2 should be assembled on Verobloc or similar to check that the frequency is acceptable, i.e. it's not too fast or too slow.

COMPONENTS

Approx. cost Guidance only **£26.00**

Resistors

R1, R3-R7 470 (6 off)
R2 1k5
all resistors ¼W ±5%

Capacitors

C1 1000µ 16V elect.
C2 47µ 10V elect.

Semiconductors

D1, D2 0.2" red l.e.d. (2 off)
D3-D5 miniature red l.e.d. (3 off)
TR1, TR3, BC214L pnp (3 off)
TR5
TR2, TR4 BPX 25 phototransistors (2 off)

See **Shop Talk** page 199

IC1 NE555 timer chip
REC1 silicon bridge rectifier 2A

Miscellaneous

RLA subminiature p.c.b. mounted relay n.o. and n.c. contacts 5-10V coil
T1 240V primary, 6.3V sec.
WD1 9-12V sounder/buzzer
S1 key switch

Single core optic fibre; Printed circuit board, EE p.c.b. 8504-03; interconnecting wire; 3 amp 2 core mains cable; 3 amp fuse; plug; grommet; fixing nut and bolt for T1; glue.


BAKERS DOZEN PARCELS

All the parcels listed below are brand new components. Price per parcel is £1.00, but if you order 12 you get one extra free.

- 1 - 5 13 amp ring main junction boxes
- 2 - 5 13 amp ring main spur boxes
- 3 - 25 13 amp fuses for ring mains
- 4 - 5 surface mounting switches suitable insulated for mains voltage
- 5 - 3 flush electrical switches intermediate type, will also replace 1 or 2 way switches
- 6 - 5 in flex line switches
- 7 - 4 in flex line switches with neons
- 8 - 2 80 watt brass cased elements
- 9 - 2 mains transformers with 6v 1a secondaries
- 10 - 2 mains transformers with 12v 1/2a secondaries
- 11 - 1 extension speaker cabinet for 6 1/4" speaker
- 12 - 5 octal bases for relays or valves
- 13 - 12 glass reed switches
- 14 - 4 OCP 70 photo transistors
- 15 - 25 assorted germanium transistors OC45 etc
- 16 - 4 tape heads, 2 record, 2 erase
- 17 - 2 ultra sonic transmitters and 2 ditto receivers
- 18 - 2 15000 mld computer grade electrolytics
- 19 - 2 light dependent resistors similar ORP12
- 20 - 5 diff micro switches
- 21 - 2 mains interference suppressors
- 22 - 2 25 watt crossover units
- 23 - 1 40 watt 3 way crossover unit
- 24 - 250 various screws and self tappers
- 25 - 1 of each wafer switches - 6p 2 way; 4p 3 way; 2p 6 way; 1p 12 way
- 26 - 2 tape deck counters
- 27 - 1 6 digit counter 12v
- 28 - 1 6 digit counter mains voltage
- 29 - 1 BOAC in flight stereo unit (second hand)
- 30 - 2 Nicad battery chargers
- 31 - 1 key switch with key
- 32 - 2 humidity switches
- 33 - 2 aerosol cans of ICI Dry Lubricant
- 34 - 96 x 1 metre lengths colour-coded connecting wires
- 35 - 4 battery operated model motors
- 36 - 2 air spaced 2 gang tuning condensers
- 37 - 2 solid dielectric 2 gang tuning condensers
- 38 - 10 compression trimmers
- 39 - Long and Medium wave tuner kit.
- 40 - 4 x 465 KC IF transformers
- 41 - 8 Rocker Switches 10 amp Mains SPST
- 42 - 6 Rocker Switches 10 amp Mains SPDT
- 43 - 5 Rocker Switches 10 amp SPDT Centre Off
- 44 - 4 Rocker Switches 10 amp DPDT
- 45 - 1 24 hour time switch mains operated
- 46 - 1 6 hour clockwork timeswitch
- 47 - 2 lever switches 4 pole changeover up and ditto down
- 48 - 2 6v operated reed switch relays
- 49 - 10 neon valves - make good night lights
- 50 - 2 x 12v DC or 24V AC AC0 relays
- 51 - 1 x 12v 2C 0 very sensitive relay
- 52 - 1 x 12v 4C 0 relay
- 53 - 2 mains operated relays 3 x 8 amp changeovers (secondhand)
- 54 - 10 rows of 32 gold plated IC sockets (total 320 sockets)
- 55 - 1 locking mechanism with 2 keys
- 56 - Miniature Unselector with circuit for electric jigsaw puzzle
- 57 - 5 Dolls' House switches
- 58 - 2 telephone hand sets incorporating ear piece & mike (s/hand)
- 59 - 2 flat solenoids - ideal to make current transformer etc
- 60 - 5 ferrite rods 4" x 5/16" diameter aerials
- 61 - 4 ferrite slab aerials with L & M wave coils
- 62 - 4 200 earpieces
- 63 - 1 Mullard Thyristor trigger module
- 64 - 10 assorted knobs 1/2 spindles

With most items quantity buyers get good discounts and save on postage costs.

SOUND TO LIGHT UNIT

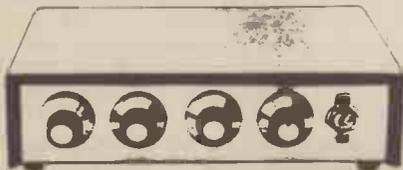

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

MINI MONO AMP on p.c.b., size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio - easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 - 270 KHz, medium wave band 525 - 1650KHz, FM band 87 - 108MHz, mono, stereo & AFC switchable, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (long wave aerial is included for medium and long wave bands. All made up on very compact board Offered at a fraction of its cost: **only £6.00**

+ £1.50 post + insurance.

25w SPEAKER SYSTEMS

By Amstrad

25 watt RMS loading 8" woofer, 4" tweeter with crossover. £12.00 per pair + £4 post. New and unused but cabinets slightly damaged hence this low price, carry our normal guarantee.

CAR STARTER/CHARGER KIT Flat Battery! Don't worry you will start your car in a few minutes with this unit - 250 watt transformer 20 amp rectifiers, case and all parts with data £16.50 or without case £15.00, post paid.

4/5A BATTERY CHARGER Transformer and rectifier £3.95 & £1 post, 3 kits £12 post paid.

PRESTEL UNITS

These are brand new and we understand tested, came with manufacturer's guarantee now void as the manufacturer no longer trades. These originally sold for over £150. We offer them complete, except for 7 plug in i.c.'s and price is only £14.95 (less than the value of the modern included).



STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) - Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation 1% with input variations up to 20% - load regulation 1% from no load to full load - or full load to no load. Complete in heavy duty case - Models available: 5v - 9A £23, 12v - 1.5A £13.25, 15v - 1.2A £13.25, 24v - 2A £23.

25A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £25.00.



THIS MONTH'S SNIP

TOP OF THE POPS LIGHTING if you use our disco switch

These have 12 x 10 amp changeover switches each rated at 10 amps so a whole street could easily be lit with one. Switches adjustable and could be set to give a running light, random flashes, etc. 230 volts main operation. Brand new, made by Honeywell. Offered at approximately one third of cost. **ONLY £6.90**

COMPUTER DESKS

Again available Computer desks - size approx 4' x 2' x 26" high formica covered, cost over £100 each. Our price only from £9.50 - you must collect - hundreds supplied to schools.



FROZEN PIPES. Can be avoided by winding our heating cable around them - 15 mtrs connected to mains costs only about 10p per week to run. Hundreds of other uses as it is waterproof and very flexible. Resistance 60 ohms/metre, Price 28p/metre or 15m for £3.95

FLEXIBLE EXTENSION LEAD twin rubber 5mm ideal grass cutter etc. 250 metre coil £25.00, 50 metre coil £6.75

50 THINGS YOU CAN MAKE

Things you can make include: Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc, etc, and you will still have hundreds of parts for future projects. Our 10Kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, 90% are unused components.

YOURS FOR ONLY £11.50 plus £3.00 post.

REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Framco Company this is a very robust motor size approximately 7 1/2" long, 3 1/2" dia. 3/8" shaft Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

- | | |
|------------------------------------|--------------------------------|
| 1 Framco motor with gear box | 1 push to start switch |
| 1 manual reversing & on/off switch | 2 limit stop switches |
| £19.50 plus postage £2.50 | 1 circuit diag. of connections |

J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. **Established 30 YEARS**

PRICES: All prices include VAT.

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & B/c card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote. Shop open 9.00 - 5.30, Mon to Fri, not Saturday.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95, without case, metal case - £2.95, adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30. Ex-Electricity Board. Guaranteed 12 months.

EXTRACTOR FANS - MAINS OPERATED

Woods extractor, 5" - £5.75, Post £1.25, 6" - £6.95, Post £1.25. 5" Planair extractor £6.50, Post £1.25. 4" x 4" Muffin 115v. £4.50, 230v. £5.75, Post 75p. All the above ex-computer, those below are unused. 4" x 4" £8.50, Post 75p. 9" American made £11.50, Post £2.00. Tangential Blower 10x3 air outlet, dual speed £16.00, Post £1.50.



TANGENTIAL BLOW HEATER

by British Solatron, as used in best blow heaters. 3Kw £6.95 complete with 'cold' half and 'full' heat switch, safety cut out and connection diagram.



Please add post £1.50 for 1 or 3 for £20 post paid 2.5 Kw Kit Still available: £4.95 + £1.50 post. or have 3 for £16 post paid

ROCKER SWITCHES Standard size fit 11.5 x 28 mm cut (single pole on/off - 15p each 1000 for £75. Single pole changeover 20p each - 1000 for £100. Single pole changeover with centre off - 25p each - 1000 for £125. Single pole on/off with neon - 36p - 1000 for £180.

ROCKER SWITCH DP/DT 15 amp 250 volts suitable for motor reversing etc. - 46p - 100 for £34.50, 1000 for £230.

MICRO SWITCHES V3 type all 250 10 amp SpST 20p 1000 - £100 Spdt 30p 1000 - £150, very low tongue Spdt 40p 1000 for £200.

EX-G.P.O. TELEPHONES

Black heavy type £5.50
Lightweight 746 type £7.50
Ex-G.P.O. plug £1.00
Ex-G.P.O. socket £1.00

WALL MOUNTING ROOM THERMOSTAT

By Danloss has a really pretty two tone grey case with circular white scale and dial. Setting temperature from 0 - 30c - 13 amp 250v contacts. Price £4.60. - 10 for £40.

BLEEPERS 6 or 12v battery or transformer operated, ideal for using in alarm circuits but particularly suitable for car and motor cycle alarms. These give a loud shrill note. Price 65p. 1000 for £345. Jap made.



MINIATURE WAFER SWITCHES

2 pole, 2 way - 4 pole, 2 way - 3 pole, 3 way - 4 pole, 3 way - 2 pole, 4 way - 3 pole, 4 way - 2 pole, 6 way - 1 pole, 12 way. All at 25p each or 10 for £2.00

12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle - Price £3.45. Ditto, but double ended £4.25.



MAINS MOTORS

We have very large stocks of motors from 2 watts to 1/2 hp. Most at a price well below cost, let us know your requirements.

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included. £11.95 plus £2.00 post.

OTHER POPULAR PROJECTS

- | | |
|---|--------|
| R C Bridge Kit | £9.9c |
| 3 Channel Sound to Light - with fully prepared metal case | £14.95 |
| Big Ear, listen through walls | £9.50 |
| Silent sentinel Ultra Sonic Transmitter and receiver | £9.50 |
| Car Light 'left on' alarm | £3.50 |
| Secret switch - fools friends and enemies alike | £1.95 |
| 3 - 30v Variable Power Supply | £13.80 |
| 2 Short & Medium wave Crystal Radio | £3.99 |
| 3v to 16v Mains Power Supply Kit | £1.95 |
| Radio telescope - fault finding aid | £4.80 |
| Mug stop - emits piercing squawk | £2.50 |
| Morse Trainer - complete with key | £2.99 |
| Drill control kit | £3.95 |
| Interrupted beam kit | £2.50 |
| Transmitter surveillance kit | £2.30 |
| Radio Mike | £6.90 |
| F M receiver kit - for surveillance or normal F M | £3.50 |
| Insulation Tester - electronic megger | £7.95 |
| Battery shaver or fluorescent from 12v | £6.90 |
| Matchbox Radio - receives Medium Wave | £2.95 |
| 40 watt amp - hifi 20hz - 20KHz | £13.50 |
| 115 Watt Amplifier 5Hz 25KHz | £9.50 |
| Power supply for 115 watt amps | £8.50 |

FOR YOUR ENTERTAINMENT

BY BARRY FOX

Manual for Divorce

I believe the computer industry is on the whole cheating to stay in business. It is selling high technology computers to the general public on the strength of blatantly misleading advertising claims and publicity.

No-one disputes that computers today offer extraordinary power, speed and capacity for their price. They can, and the operative word is *can*, perform all manner of extraordinary tasks. Young people who have been brought up with computers, at school and college, find them easy to tame. Others take up computing as a hobby, like fishing or radio construction.

Up until now the industry has survived mainly on selling computers to people like this, who are computer literate. When they sell to householders and business people who find themselves totally at sea, the computer trade just makes the customer feel guilty for not being able to cope.

That's why so many new computers go straight back into their original boxes and stay in the drawer. That's why businessmen use them only to play games. Even people who get their systems working for business, frequently scratch only the top surface of potential. They use spreadsheets wrongly, never really exploit a data base as intended, and call up only a few word processing demands.

But now the credit is running out. The honeymoon is over. If the computer industry is to continue growing, it must sell to more and more people who are *not* computer literate. As more and more of these people become discontented, and feel cheated, resistance will grow.

In my experience, the main obstacle for people learning about computers in later life is the disgusting state of documentation that goes out with these high technology machines. The computer specialist press is largely to

blame. They have pushed the manufacturers into producing new products and getting them on the market, before they are ready.

They have failed in their duty to protect customers against poor documentation and software. They should have blasted and ridiculed inadequate manuals. It is surely quite unacceptable for a computer specialist to review a new product on the strength of prototype hardware, incomplete software and either a draft manual or no manual at all. But in a mad scramble not to be left behind this is what they do.

If the machine gets a favourable review, there is no incentive for the manufacturer to clean out the bugs and produce a decent manual. They are too busy developing the next generation prototype, software lash-up and sketchy draft documentation.

Enough is enough. If the computer press won't sort this nonsense out, then somebody else has got to do it. Earlier this year I got in touch with the Office of Fair Trading, the Government-backed body which exists to protect consumers from nonsense like this. It was the OFT which bullied Sir Clive Sinclair into promising that he would no longer take customers' money before he was ready to send out their goods by mail order.

The OFT (Field House, Breams Buildings, London EC4A 1PR) will not take up personal complaints, for instance on faulty goods. For that you must contact your local council Trading Standards, or Consumer Protection, Officer, or your local Citizens Advice Bureau. What the OFT does do, is keep an eye on any firm which is consistently playing unfair.

The problem with computers is that most people who don't understand them aren't well equipped to explain in clear terms what is wrong with what they have bought. Computer literate buffs, who find handling new equipment a doddle, aren't going to be bothered to complain anyway. But readers of *Everyday Electronics* are a special breed. They tend not to be dedicated computer buffs, but they do tend to be interested in electronics in general. I know, from letters which I have received over the years, that *EE* readers have one thing in common, and that's electronic common-sense.

Reverse Charge

Sometimes I do wonder whether people who sell things, ever actually *use* them. Recently British Telecom proudly launched its new range of payphones. The plan is to spend £160 million over 10 years, on updating the 76,500 public payphones around the country.

At the press conference Iain Vallance, Managing Director of the division inside British Telecom, which looks after payphones, and his marketing man, Nick Kane, were astonishingly rude about the existing payphone service. Apparently it lost £50 million last year and is the service of which BT is "least proud".

Even in an age when soap powder companies continually imply that what they have previously sold is no good, by bringing out whiter-than-whiter-than-white improvements, I have seldom heard any organisation be so rude about its existing product. In return the audience of press was pretty rude to British Telecom about what it plans. What made many people, including myself, really hot under the collar, was the technical nonsense talked by BT about a ridiculous deficiency of existing payphones.

As everyone, except a chauffeur-driven BT boss with a radio telephone will know, it is a nightmare trying to find a working payphone. Most are either vandalized or won't work because they are full of money; people then vandalize the phone because it is full and won't work.

Although a full-up telephone will still let you make 999 calls, it won't let you dial 100 and make reverse charges calls. This is crazy, because it infuriates the public and loses BT the healthy revenue available from reverse charge calls.

Under pressure the embarrassed Vallance and Kane double act admitted that new phones also wouldn't allow 100 calls

when they are full up or faulty. "It's the software in the microchip," they said. But both 999 and 100 are 3 digit calls, so why can't the system default to both 3 digit options, instead of just 999? Very flustered, Kane and Vallance would say only that they were "actively looking at ways of changing the situation".

Vallance then put his head in a noose by chiding the public for not reporting broken phones. But how can you report a broken phone if you can't dial 100? Vallance then contradicted his own point, by saying that the new phones were self-diagnostic and reported their own faults automatically to the Exchange. So the public needn't report faults after all.

Plessey make the electronics for the old, and new phones. I couldn't believe that Plessey wasn't able to write default software for two 3-digit codes instead of one. And of course they could. The truth of the matter is that Plessey told BT that the new phones should give users the 100 dial option when full or faulty. But heaven knows why BT insisted on 999 only.

Quite recently, with tail between legs, BT went back to Plessey and asked them to change over. Obviously it will take some time, which is why the BT people tried so desperately to hedge the issue at the press conference.

For the record, I am now a BT shareholder. On principle I don't normally own shares because I think it can compromise a journalist to own part of a company which he or she may be writing about. But in the case of BT, I just couldn't miss the chance of going to the annual shareholders meeting, along with around two million other people who are all trying to ask questions like—why can't I dial 100 from a faulty phone?

Fox Hunt

My plan, for 1985, is to pass on to the OFT any documentary evidence which might encourage the Office to start policing the computer industry. Quite clearly it isn't going to police itself.

I started on the OFT with some personal experience. I bought an Apricot Xi, hard disc machine, and was astonished at the appalling documentation. It came with six printed manuals (one more through the post made it seven) and a string of postscripts that roll up on the screen as a "Readme" program.

Instructions grasshopper between manuals and Readme, with never a logical thread and important procedures inadequately explained, often in what I take to be the Martian language. One thing the manuals did make clear, was that it was absolutely vital to make safety copies of the programs stored on the master hard disc. But the one thing they did *not* make clear was how to do it!

I followed what I thought was the right

procedure (it turned out subsequently to be wrong) and ran into trouble. I 'phoned the makers in Birmingham who told me that I was in trouble because some of the programs I was copying were faulty and I should delete them.

When I tried, I ended up deleting the main command program which killed the machine for a week. It sat dead until Apricot sent me the equivalent of a new brain on floppy disc through the post. They then told me by telephone how to do the copying procedure—I never did find it explained in the manuals.

A business friend from America was visiting when I was sitting despondently in front of the newly dead machine. I explained that I had pressed a key twice instead of once and killed it. "Is that the way you do things in this country?" he said in bewilderment.

"When you buy a car you don't expect the steering wheel to fall off if you turn the ignition key in the wrong direction. Or at least if it's going to fall off they put a notice on the dashboard warning you".

At around the same time an insurance broker I know got himself an Apricot and threw up his hands in despair. He paid someone £25 an hour to teach him how to use it but still had to give up.

I wrote a string of letters to ACT, the firm which makes the Apricot, but after a month had heard nothing in reply. If ever you think that journalists get special treatment when they raise queries, think again.

This correspondence has now been forwarded to the Office of Fair Trading. If anyone has similar tales to recount, I'd be pleased to receive them, and forward them too.

Hot Line

If like me, you've been fooled by the cinema into thinking that the "Hot Line" is a red telephone at the end of a line between the White House and Kremlin, think again. It's not, and it never has been. It has always been a text link, not an ordinary speech telephone.

The idea of a hot line dates back to President Kennedy and the Cuba crisis of 1962. Krushchev was putting missiles onto Cuba, and Kennedy blockaded the island. For a while it really did look as if there might be a nuclear war. The main problem was that the two world leaders had to talk to each other through rather clumsy diplomatic channels. So they vowed, never again.

In June 1963 Krushchev and Kennedy signed an agreement for a direct communication link, or DCL, between their offices. It was inaugurated in August 1963. The first DCL worked as an ordinary telex service, using high frequency and microwave radio links. There was also an under-sea telephone cable backup in case the radio links went wrong, or were jammed.

Right from the start they rejected the idea of a speech link, because of the problems of translating inference, implication and innuendo. The typed telex messages were transmitted from America in the English language, and from the Soviet Union in Russian.

Although use of the hot line telex is a classified secret, we know that it was very busy during the 1967 and 1973 Arab-Israeli wars. Almost certainly it prevented escalation.

The radio link soon proved unreliable, because of atmospheric interference. Privately telecoms engineers admitted that they were worried about the submarine cable link, because it relied on copper technology and booster amplifiers and switching stations along the route. Obviously it was vulnerable to anyone who could sabotage a booster or exchange.

In 1978 the radio link was replaced by a dual satellite link. The Russian *Molniya* satellite handles the signal at the same time as the world's telecommunication network of *Intelsat* satellites. But they kept the submarine cable as a last ditch back up.

Now all that is changing. President Reagan has apparently been worrying about the time delay needed to type a message into the telex machine. Also, it's not possible with telex to draw sketches, relay photographs or show troop movements on a map.


So now ITT in America has been commissioned to install a facsimile link. This has already been tested and should by now be in action. Of course we'll never know how it works, unless it goes wrong—in which case there could be a holocaust and we wouldn't know anyway.

Apparently the facsimile can transmit a page of print or a map inside two minutes. The only snag, for which there seems to be no solution, is that messages still have to be typed out before they are sent, even though they aren't now typed direct into a telex.

Let's hope that if there is a sudden world crisis, the White House or Kremlin typing pool isn't on holiday or out to lunch.

LINK-UP

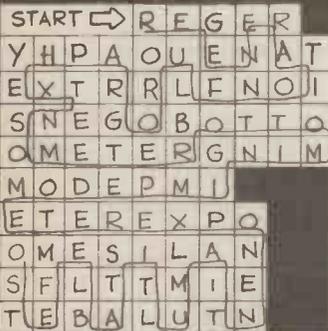Link-up the letters to form a chain of words related to electronics.



WORD	CLUE
REGENERATION	Feedback.
FLUOROGRAPHY	Image on screen
EXTENSOMETER	MEASURES change
BOTTOMING	Below the KNEE
IMPEDMETER	Measures impedance
EXPONENTIAL	...Curve
MULTISTABLE	Not one stable state
MOSFET	Metal oxide...

COMPUTER CLUB

ANSWERS

"IT'S HIS TENTH ATTEMPT AT COPYING A TEN THOUSAND LINE PROGRAMME."



SEEKERS OF THE GOLD SEAL

The two adventurers from the Planet of Knowledge believed that the ancient Egyptians of Earth thought of ELECTRONICS before other Earth civilisations.




Their quest to prove this belief led them to a tomb in the valley of the Seal with a 'hieroglyphic' never seen before. Although it appeared 'hieroglyphic' it was actually a series of LETTER segments. When completed formed a total of 9 words related to ELECTRONICS — can you find them?

DIGITAL ELECTRONICS

D.W. CRABTREE BSc Tech Eng (CEI)


PART SEVEN

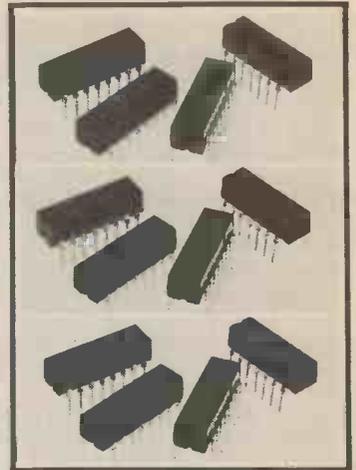

In the last article we looked at the basics of numbering and coding systems, and arithmetic processes which are used by some computers. It is now time to describe the computers themselves.

BASIC DEFINITIONS OF COMPUTERS

Basically, a computer is a device, or more correctly, a group of devices, capable of making mathematical decisions and calculations. It then uses the data thus created to assist it in carrying out a fixed set of instructions, called a program. There are several pieces of hardware involved to manipulate the instructions and data, and each of these pieces are described in brief below. For greater detail of the computer architecture, many good books are available for reference.

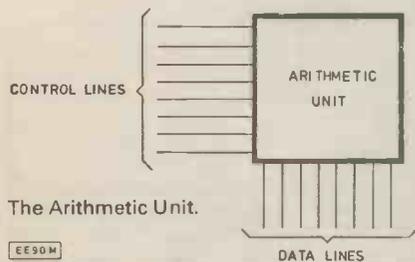

ARITHMETIC UNIT

The purpose of the Arithmetic Unit is to perform the basic mathematical functions of ADD and SUBTRACT, together with other logic functions such as AND, OR and NEGATE. Referring to the diagram above, the function required is selected by the bit pattern on the control lines, with the data put out onto the data lines, called the DATA BUS.

CONTROL UNIT AND DATA BANK

The purpose of the Control Unit is to read and write data to the arithmetic unit, and to control or select the current function being performed by the arithmetic unit.

The purpose of the data bank/memory is to store data used by the system until required. (See diagram).

INSTRUCTION MEMORY


There is an instruction memory built into the computer system whose function is to hold a list of instructions which form the basis of a PROGRAM. This list of instructions is fed, in a logical sequence, to the control unit which then carries out arithmetic logical and data movement operations as required by the information within the instruction being carried out. The details of the instructions are also sent to the data bank in order to select the correct words of data to be operated upon.

The instruction format will be described below and the diagram below shows the basics of the computer layout. The part of the drawing showed within the dotted line represents the Central Processing Unit.

The instruction memory and the data bank will generally be on the physical block. I.e.: The memory or store.

INSTRUCTIONS AND LANGUAGES

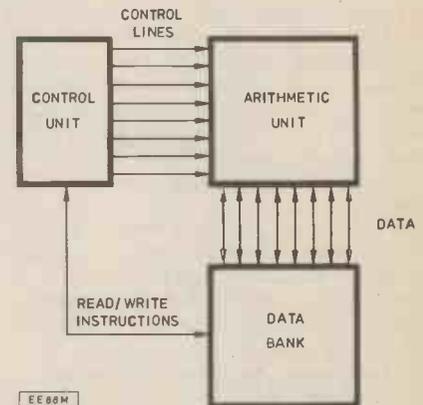
The instructions used by the system generally will fall into two parts, the



The Control Unit and Memory.

operation part and the address part. The operation part specifies the function being carried out, e.g. add or subtract, whilst the address part specifies the address or location of an item of data within the memory.

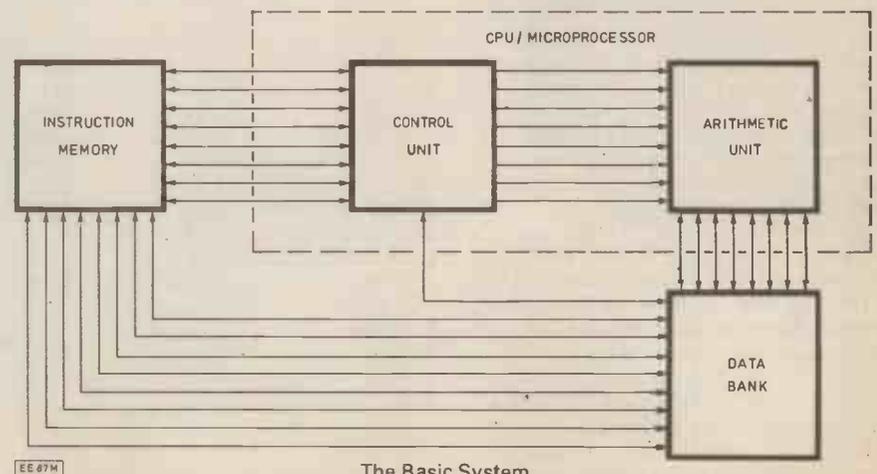The format of the actual instructions used can be of several different types. The actual components within the system only understand machine code language which is the use of binary numbers only, with the size of word being used being dependant upon the type of system being used. For example, early machines used 4-bit word format. Later, 8-bit words became



The Basic System.

used and later still 16-bit words were to be found. Many new machines are now using 32-bit word formats.

Each instruction can carry several words. The format described above is said to be machine readable and is called the Object Program.

Now, for the user, it would become quite tedious to enter an object program into a computer as a series of binary words, especially if 32-bit words were being used. Also, it is likely that many mistakes would result. Instead, the user can write the program as a series of hexadecimal words, usually of 2 digits. This makes the task less tedious but, even then, numbers and figures are still being entered and, again, mistakes are possible.

How much easier it would be to program the computer using a language that was man-readable instead of machine-readable. Well, this is sometimes possible, depending upon the type of system being used. The program can sometimes be entered as mnemonics which is a series of instructions that are fairly easy to understand and read by the user. The mnemonics form the source program and are written in assembly language.

Thus the program is generally written in assembly language (as the source program) and this is then converted by a part of the system called an assembler into the object program that the machine readily understands.

We therefore have three different ways of entering the information of the program into the system, either by entering complete binary words, hexadecimal or by entering mnemonics. Let us now consider a simple piece of a program and look at the comparison of the three different ways of entering the information, without trying to understand what is happening in the program.

Looking at three data words, X,Y,Z, held in three successive memory locations 0200, 0201 and 0202, we compute $A=X+Y-Z$ and store the result in location 0203. (The instructions shown in the table are instructions within the Motorola 6800 microprocessor architecture.)

Now, looking at the three different ways of showing each instruction, using mnemonics must surely be the best method used. It is very useful to see exactly what is happening within a program listing and, using mnemonics, a programmer does have a better idea of what functions are taking place in the program at a particular point. With hexadecimal, the program is listed using pairs of hexadecimal. This is an aid to entering the program into the computer but, at the same time, the task of identifying individual parts of the program, in a long program listing, is very difficult. With binary, the task seems to be almost impossible when the programmer is faced with a continuous stream of 0's and 1's.

Much of what has been said above depends very much on the type of system being used and that system's built-in intelligence but, nevertheless, it should give a useful grounding to the reader.

Instruction	Mnemonic	Hexadecimal	Binary
Load ACC.B from location 0200	LDAB 0200H	F6	11110110
		02	00000010
		00	00000000
Add the contents of 0201 to ACC.B	ADDB 0201H	FB	11111011
		02	00000010
		01	00000001
Subtract the contents of 0202 from ACC.B	SUBB 0202H	F0	11110000
		02	00000010
		02	00000010
Store the contents of ACC.B in 0203	STAB 0203H	F7	11110111
		02	00000010
		03	00000011

Comparison of instructions.

The example of the program used above was written for a Motorola 6800 series microprocessor. This is an 8-bit processor that has two main registers, A and B, an index register, X (which can carry 16 bits of information) and three other special purpose registers. Of these special purpose registers there is:—

(1) THE CONDITION CODE REGISTER (CCR)

This is an 8-bit register which is capable of storing the states (either '0' or '1') of certain flags used by the system. For instance, if an addition takes place within the processor and a carry takes place, then a CCR 'carry flag' will be set.

(2) THE PROGRAM COUNTER (PC)

This is a 16-bit register that always contains the address in memory of the next instruction to be carried out. That is, a program is written by the programmer and a section of memory is set aside to hold the program, so that for any particular byte of the program, a specific memory location is set aside for it. The program counter, therefore, keeps track of which parts of the program have been carried out already and becomes set to the address of the next instruction in memory. Before the program has been started, therefore, the program counter contains the actual start address of the program.

(3) THE STACK POINTER (SP)

Part of the RAM memory is set aside for use as the stack. This is a section that is used to store results, on a temporary basis, during a run of the program. It is called a stack because the system works on a last-in-first-out basis. The stack pointer, therefore, contains the actual address in memory of the stack. I.e.: it points to it by address.

Most of the instructions available for the device, therefore, include functions that encompass one or more of the above registers. The remaining instructions provide other special facilities. But, as stated previously, the above only concerns the Motorola 6800 series of microprocessors. However, other types of microprocessors have similar structures

and similar instructions available. For example the Z80 microprocessor, by Zilog, has, instead of just two main registers, several pairs of main registers together with an alternate set as well. Each pair, say the BC pair, can be used together as a 16-bit register or separately as a B register and a C register, both being 8-bits. As far as the alternate register set is concerned, not all the instructions for the main register set can be used by the alternate register set.

EXTERNAL COMMUNICATION

Computers generally need to have external communication facilities in order to talk to or listen to other devices. Facilities are therefore available to provide communication with printers, visual display units, modems, etc, as well as input/output ports for driving to and from the real world.

MICROCOMPUTER DESIGN

Let us now consider a simple, yet practical microcomputer design. First of all we must formulate our requirements:—

(1) MICROPROCESSOR USED

We must decide which microprocessor should be used as the central processing unit. We have mentioned briefly the Motorola 6800 series and the Zilog Z80 series microprocessors above. Many other processors exist including the Intel 8080, which uses a similar instruction set to that used by the Zilog Z80. The 6800 series offers a limited yet fairly easy to understand instruction set whilst the Z80 offers more computing facilities, if required, by the greater number of registers.

Let us use a Z80 microprocessor in our design.

(2) OPERATING SYSTEM USED

Every computer requires an Operating System, of some kind, to function and usually this is put in firmware form into a ROM (or EPROM) chip. Let us consider that our design utilises a 4K Byte EPROM in the form of two 2716 chips, each of which offers 2K Byte storage of 8-bit words.

(3) TEMPORARY DATA STORAGE USED

Every system needs some form of temporary data storage and as previously stated, this is generally in RAM form. For our design, let us say we require 1K Byte of RAM and we will use two 2114 chips in order to get the 1K Byte required. These chips offer 1K Byte storage of 4-bit words.

(4) INPUT/OUTPUT USED

Let us suppose that our system design requires to include some input/output facilities. This is available using a readily available input/output chip, the 8255, for Z80-based systems and this is the chip that we shall use in our system, giving 24 I/O lines. If we need 24 lines, only one 8255 is required.

All the basic components described above have data lines and address lines and power supply connections. Apart from the Z80 microprocessor we will not consider, the power supply connections, but we will have to show all the data and address line connections for each chip. Now, so far we have discussed all the basic components required but we have not considered how the microprocessor can communicate with each particular chip. Since all the chips utilise the same set of control/data lines, the microprocessor cannot distinguish between one chip and another. Therefore we need to have some type of coding for each chip, so that only the relevant chips are enabled at any one time. Also since all the chips are now going to have a unique coding for each function used, we must have some way of making sure that, in fact, the codes are unique and that no two functions share the same code area. This is called MEMORY MAPPING and is essential if the system design is to be feasible.

MEMORY MAPPING

We look at each component in turn and decide where, in the total possible addressing area, each is to be situated. We split the area up into sections, so much for ROM, so much for RAM and so much for I/O, etc. Hence we are creating a map which shows where each function can be found.

Let us consider the system that we are designing. The Z80 microprocessor has 16 address lines, A_0 to A_{15} , therefore we have facilities to address $2^{16} = 65536$ individual locations. (Note that $65536 = 64K$ Bytes), or in hexadecimal form, from 0000 up to FFFF.

We can now consider each component function and allocate a space within the available 64K Bytes of memory.

	A_0	A_1	A_2	A_3	A_4	A_5	A_6	A_7	A_8	A_9	A_{10}	A_{11}	A_{12}	A_{13}	A_{14}	A_{15}
(DECIMAL)	2	4	8	16	32	64	128	256	512	1K	2K	4K	8K	16K	32K	64K
(HEXADECIMAL)	0002	0004	0008	0010	0020	0040	0080	0100	0200	0400	0800	1000	2000	4000	8000	10000

EPROM

We have 4K Bytes of 8-bit words, and we are using two 2K Byte chips to form the total 4K Bytes. Now 2K Bytes represents $2 \times 1024 = 2048$ in decimal and 0800 in hexadecimal. This last figure is the important one since we can now map our two EPROM chips at memory locations 0000 to 07FF and 0800 to 0FFF, which is a total memory area of 4K Bytes.

RAM

We have 1K Byte of 8-bit words, and we are using two 1K \times 4-bit word chips to form the total required.

Now 1K Byte represents 1024 decimal, which is 0400 in hexadecimal. Let us, therefore, map our RAM at memory locations 1000 to 13FF, which is an area of 1K Byte.

I/O


Now for our Input/Output port, we are using one 8255 I/O chip. This has three 8-bit word lines available. That is, any one of three words can be input or output from the device at any time. Now, we have a function available from the microprocessor that can control whether we read/write to memory or to input/output, we are not able to read/write to both at the same time. Therefore we can locate our I/O port at any location we choose. We have three lines as stated, therefore we can locate our lines at, say, locations 20, 21 and 22 hexadecimal.

Our memory map will now look like this:—

Hexadecimal addresses given)	0000 I/O \uparrow 20 07FF	EPROM (CHIP 1)
	0800 \uparrow 0FFF	EPROM (CHIP 2)
	1000 \uparrow 13FF	RAM
	1400 \uparrow FFFF	SPARE

Now we mentioned, previously, that we needed to code the functions so that each had its own unique memory area. We have now mapped out the memory areas, but we have not yet provided the necessary coding (or decoding to be more specific). Let us consider the first EPROM chip, to be situated at memory locations 0000 to 07FF hexadecimal. We require to enable this chip whenever we are in the area of map from 0000 to 07FF only. Therefore, let us look at the 15 address lines, together with the total possible memory area that each line could enable.

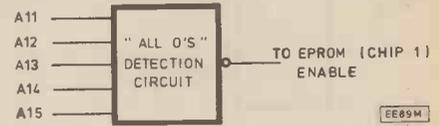Now we need to locate our EPROM memory between 0000 and 07FF, that is, at all times that address lines A_{11} to A_{15} are set to logic '0'. Therefore all we need to do is detect all 0's on A_{11} to A_{15} , and enable our first EPROM chip. Our block diagram for this is shown below:—



Simple Address Decoding.

For our second EPROM chip, we need to locate this at memory area 0800 to 0FFF, therefore we detect when the address lines A_{12} to A_{15} are all 0's and A_{11} is a 1.

We next look at the two 2114 RAM chips and note that they need to be decoded between 1000 and 13FF. We therefore look at address lines A_{10} to A_{15} and decode accordingly.

Finally, for the I/O chip, we need to locate this at 20 hexadecimal which is equal to 32 in decimal. Therefore we AND the A_5 address line with the I/O control line so that the chip is enabled wherever 20 hexadecimal is selected on the address. To select the required I/O line at address 20, 21 and 22 we then look at A_0 and A_1 to see when 20, 21 or 22 is addressed.


We have now memory mapped the complete microcomputer system and so we can now draw the (block) diagram to show our complete design (as shown on opposite page).

It should be noticed that we also send the data lines to each chip as required. For instance, the 2716 chips are 8-bit word chips so we send data lines D_0 to D_7 inclusive. The 2114 chips are 4-bit word chips so we send D_0 to D_3 inclusive to one chip and D_4 to D_7 inclusive to the other, giving 8-bits in total. We similarly send D_0 to D_7 to the 8255 chips.

Each decoding circuit is fed with the $MREQ$ and RD controls from the microprocessor which are (active low) Memory Request and Read/Write controls respectively. Likewise the I/O port is fed with the $IORQ$ (Input/Output Request) control as previously mentioned.

The decoding discussed is called Partial Address Decoding because we are only looking at some of the possible address lines. If we looked at all the address lines, then this would be called Total Address Decoding (not generally required).

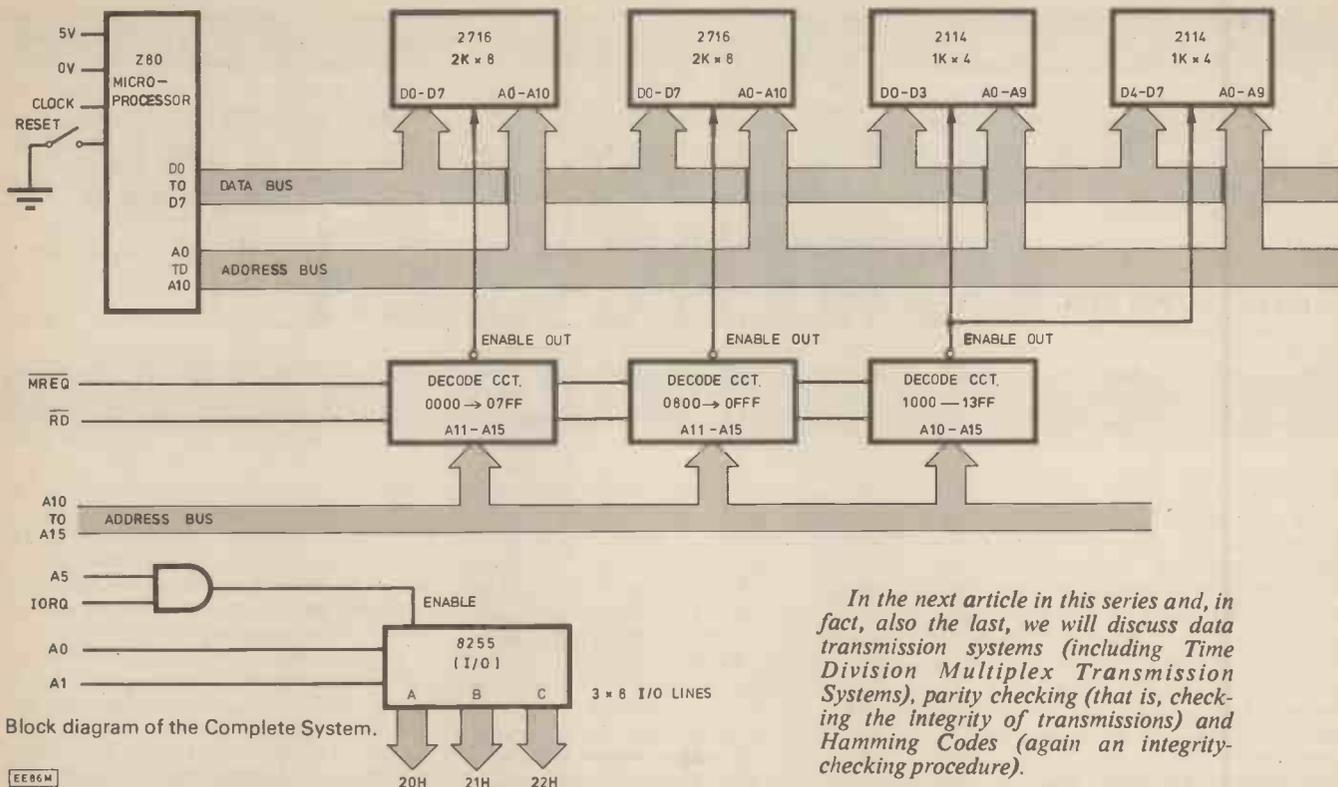Above we have discussed the basics of microprocessor system design and we have tried to describe the best way of going about such a design. For further information, several good books are available.



Block diagram of the Complete System.

EE86M

In the next article in this series and, in fact, also the last, we will discuss data transmission systems (including Time Division Multiplex Transmission Systems), parity checking (that is, checking the integrity of transmissions) and Hamming Codes (again an integrity-checking procedure).

COUNTER INTELLIGENCE

BY PAUL YOUNG

Path Finder

If there is one engineering success that would not exist today without the micro chip and modern electronic technology, it is the aircraft flight simulator. That being so, it is nice to be able to report that one of the foremost leaders in the field is British; I refer to Rediffusion. They are the largest manufacturers of aircraft simulators in Europe, and one of the largest in the world.

I was reminded of this a few weeks ago when I was watching the BBC2 *Money Programme*. It showed the flight deck of a DC10 taking off from Heathrow. A few hundred feet up, there was a sudden severe down draught which the pilot skilfully corrected.

The commentator then told us that even if the pilot had failed to correct it, no one would have been hurt as they were in a simulator. At that moment the pilot turned his head, and I recognised an old friend of mine, Captain Charles Coates. I rang Captain Coates next day and he filled me in on the company and its success record.

The modern simulator is an incredible piece of machinery. Externally it looks like a house on steel stilts, but once inside you are immediately transported on to the flight deck of a Jumbo jet, a Concorde, a Harrier or any other aircraft. So effective is the simulator, that a captain of an American airline flew over from the States in a Jumbo jet, spent the requisite number of hours in a DC10 simulator, went down to Gatwick

and flew a DC10 back to Los Angeles with a full load of passengers, although he had never flown one before.

Apart from the safety angle, they are cost effective, as the cost of training in a real aircraft is twenty times as much as the simulator. Bearing in mind their average price is about five million pounds, they need to be. In spite of the price, there are no lack of orders and they are being exported all over the world, including America and Japan.

Thunder Struck

When Sir Clive Sinclair announced a year ago that he was going to build an electric car, I thought it won't be long now before the oil sheiks are folding their tents and silently departing. I must admit that the end product has been a great disappointment. The C5 is little more than a toy. The range, the speed and the carrying capacity are all too low to be of any practical value.

When I read that it will carry one cubic foot of shopping I nearly fell off my chair laughing. Sir Clive ought to line up at the check-out of any supermarket and observe the matrons with their trolleys piled so high you begin to wonder if they have a small pantechinon in the car park.

However, I haven't given up hope of having an electric car, as I see that Mr. Joe Schwarzkopf (a relative of the singer), with the help of a consortium which includes Varta Batteries, Unipart, Uniroyal Tyres, HB

Switch Gear and Berger Industrial Coatings, is producing a kit to convert the family car into an all-electric vehicle. It will have a range of 140 miles, a top speed of 80, and the running costs and maintenance will be almost nil. In addition, no road tax is required.

The conversion will cost about £3,000, and the following cars are particularly suitable for converting. The Austin Mini and Maestro, Ford's Fiesta, Volkswagen Polo and Ford's Sierra. So I am afraid the Editor will have to rough it in his Rolls for a little longer.

A B747 flight simulator installed at American Airlines Gatwick training academy by Rediffusion Simulation.



IMMERSION HEATER CONTROLLER

T.R.de Vaux Balbirnie

INDISCRIMINATE use of the immersion heater can result in large electricity bills. One method of heating only the water required is to switch on for short times. Unfortunately, it is easy to forget to switch off again. This unit switches off the immersion heater when the water in the copper storage cylinder is heated to a predetermined temperature at some chosen level. It is a *one-shot* system initiated by a push-button switch on the unit. When the immersion heater switches off it will stay this way until the switch is pressed again. Potential savings are high.

OPERATION

As the water heats up, it does so from the top of the cylinder downwards. Thermistors attached to the tank at four points act as temperature sensors. When hot water reaches the chosen level, the circuit is triggered and the heater switches off. The level is selected by a rotary switch representing hot water *quantity* on the front panel of the unit. One red light-emitting diode in a row of four illuminates to confirm the level chosen. A similar row of green i.e.d.s light in sequence following the progress of hot water. In this way, the state of the system is seen at a glance. One additional position on the rotary switch selects *Cancel*, and this serves two purposes. If used while the immersion heater is on, it will switch off immediately. If the system is not operating, the green i.e.d.s will light when the *Start* button is pressed allowing the level of hot water to be checked without operating the heater. Another spare position on the rotary switch gives continuous operation if required.

The new circuit takes over all normal operation of the immersion heater—the existing wall switch is retained simply as an isolator. The temperature at which each sensor operates is adjusted at the testing stage and is performed with the lid of the case in position—an important safety point since there are mains connections inside.

CIRCUIT DESCRIPTION


Fig. 1 shows the entire circuit of the Immersion Heater Controller. The single

integrated circuit, IC1, contains four separate operational amplifiers, IC1a to d, each responsible for one particular water level—IC1a for the top one and so on. When S2 (Start) is pressed, mains current flows through the primary of T1 and the low-voltage output is rectified by REC1 and smoothed by C1. This supplies power to the rest of the circuit. TR1 turns on due to base current flowing through R13 and this operates RLA connected in the emitter circuit. The normally-open contacts of RLA allow mains current to flow through the coil of RLB and this operates the mains load through its pair of normally-open contacts. RLB also allows current to flow to T1 so the action is now self-sustaining and S2 may be released. This all happens so quickly that momentary pressing of S2 is sufficient for the system to operate.

The non-inverting inputs of all op-amps share the common potential divider R5/R6 which applies a voltage of one-half that of the supply (nominally 6V) to them. The inverting inputs have individual potential dividers—VR1 to VR4 in the upper "arms" and R1 to R4 in the lower ones. Thus, the voltages produced at the inverting inputs will depend on the individual adjustments of VR1 to 4 and the temperatures of the thermistors. Since the thermistors are *negative temperature*

coefficient types their resistances *fall* as their temperatures rise. When a thermistor senses hot water, the voltage at the inverting input of the corresponding op-amp will fall. In use, VR1 to 4 will be adjusted so that, under cold conditions, the voltages at the inverting inputs will exceed those at the non-inverting inputs and the op-amps will be off. As the level of hot water progresses, the op-amps will switch on in turn operating the green (Progress) i.e.d.s D1 to D4. One pole, S1a, of the double-pole rotary switch, S1, selects the op-amp output appropriate to the level of hot water required. When this op-amp switches on, thyristor CSR1 is triggered by gate current flowing through R11 and TR1 switches off. RLA no longer maintains the coil of RLB and the mains load switches off. Primary current to T1 is also interrupted so the circuit cannot work until S2 is pressed again. The purpose of CSR1 is to provide a switching action at the critical temperature.

The second pole of S1, S1b, operates the red (*Level*) i.e.d.s D6 to D9 or the yellow (*Continuous*) one D10. The Continuous position of S1a is left unconnected so CSR1 never triggers allowing RLB to operate continuously. The existing thermostat prevents the water from overheating. The *Cancel* position is connected direct to supply positive so CSR1

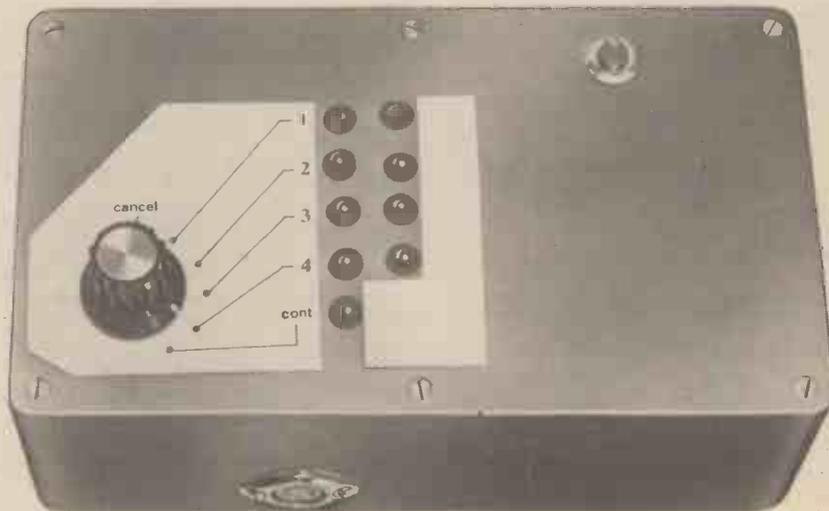

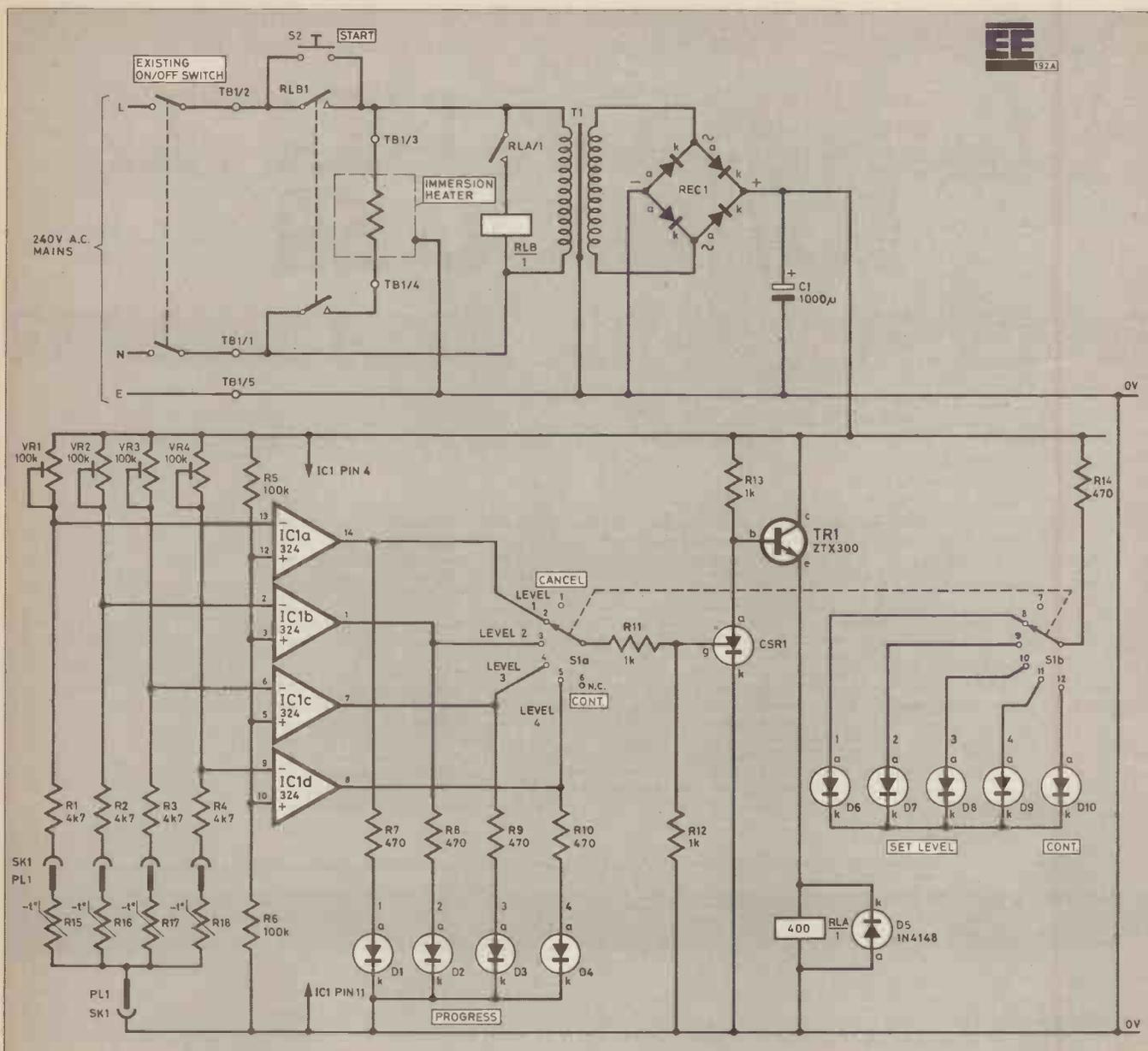


Fig. 1. Circuit diagram. Note: If the mains supply does not come from a 13A fused plug, then a fuse should be inserted in the supply LIVE wire.

is triggered as soon as S2 is operated. This prevents the immersion heater from switching on yet allows the Progress l.e.d.s to operate.

The sensors are glued to the surface of the copper cylinder and connected to the unit by means of an audio-type 5-pin DIN plug and socket.

CONSTRUCTION

Refer to Fig. 2 and construct the circuit panel using a piece of 0.1in. matrix stripboard size 17 strips by 41 holes. Check that this fits the runners of the plastic box securely. Mount the i.c. socket and make all the breaks and inter-strip links. Note especially the breaks between the pins of the i.c. holder but *not* between pins 3 and 12 or between pins 5 and 10. Note also the break at the bridge rectifier. Solder the on-board components noting

that VR1, VR2 and VR4 have one of their connections cut off close to the body and left unconnected—they are adequately supported by the remaining two soldered connections. The breaks in the copper tracks at RLA isolate the mains section from the rest of the circuit. For safety reasons, check that these are completely broken.

For clarity, Fig. 2 shows C1 alongside the circuit panel but when in position its leads are bent so that the lid fits. Connect 20 cm lengths of light-duty stranded wire to the 15 points indicated along the left-hand edge of the panel. Do not make the right-hand connections yet. In view of the possibility of error, it would be wise to use different colours if possible. Make a final check for wiring errors and for accidental solder "bridges" between adjacent copper tracks.

Prepare the case by making holes for the nine l.e.d.s, for S1, S2, SK1 and for mounting T1, RLB and TB1. RLB must be of the heavy-duty pattern specified in the components list and S2 must be rated for mains use. Make holes in the case for the input and output wires which connect to TB1. Measure the positions of VR1-4 on the circuit panel and drill 5mm holes in the side of the case so that they may be adjusted by means of a small screwdriver.

Mount the off-board components (the exact layout will depend to some extent on the size of T1) and, referring to Fig. 3, complete all internal wiring. Note that TB1/5 (mains earth) inter-connects the following: l.e.d. cathodes, solder tag at T1, solder tag at S2 (only needed if this component has a metal body), SK1 body which forms the common thermistor connection and the circuit panel earth lead.

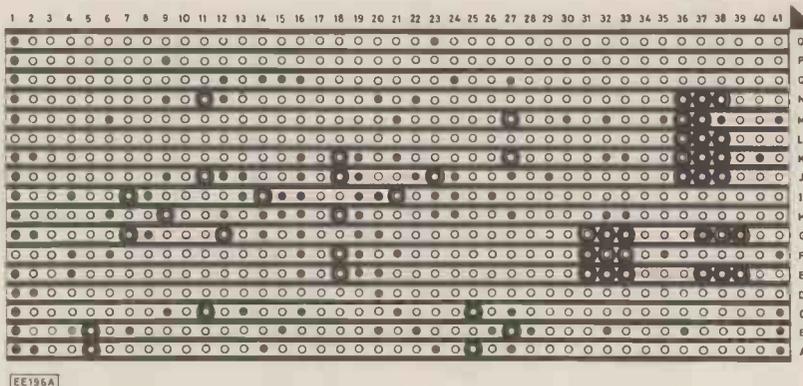
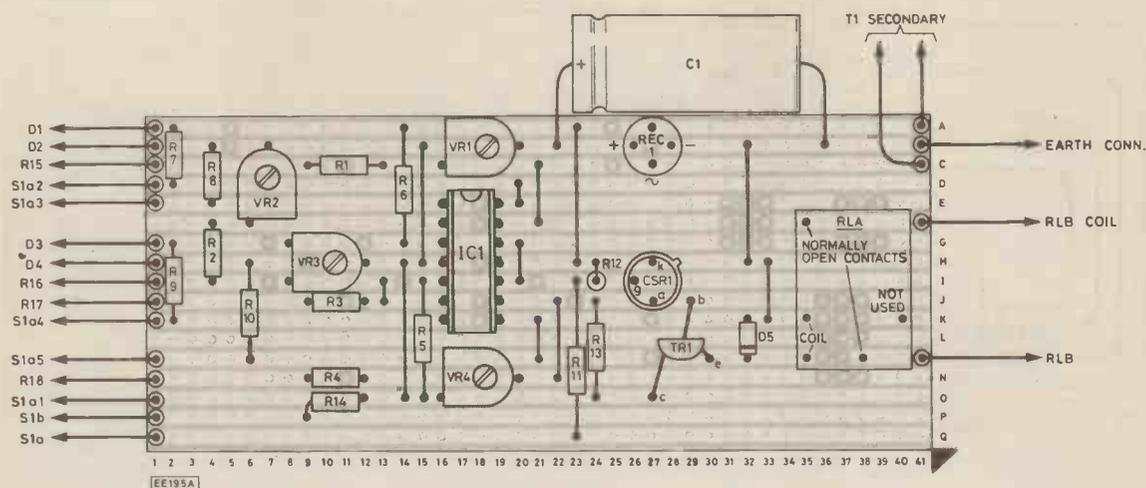


Fig. 2. Stripboard layout of Immersion Heater Controller.

COMPONENTS

Approx. cost £25
Guidance only

Resistors

R1,2,3,4 4k7 (4 off)
R5,6 100k (2 off)
R7,8,9,10,14 470 (5 off)
R11,12,13 1k
All fixed resistors $\frac{1}{4}$ W carbon $\pm 5\%$

Potentiometers

VR1,2,3,4 100k min. hor. preset

Capacitors

C1 1000 μ F 16V elect.

Semiconductors

IC1 LM324N quad op. amp.
CSR1 BTX 18-400 thyristor
TR1 ZTX300 npn silicon
D1,2,3,4 green (4 off)
D6,7,8,9 red (4 off)
D10 yellow
D5 1N4148
REC1 W005 bridge rectifier

Miscellaneous

T1 Miniature mains transformer with 240V primary and 12V secondary. 150mA or more current rating.
S1 2-pole 6-way miniature rotary switch—break-before-make action. Pointer knob to suit S1.
S2 Push-to-make switch with 240V contacts.
RLA P.c.b. mounting relay—400 ohm coil and mains-rated normally-open contacts, e.g. Maplins 10A Mains Relay.
RLB Heavy-duty relay with 240V coil and double-pole changeover contacts rated at 20A (R.S. type 340-403). 14-pin integrated circuit socket.

See
**Shop
Talk**
page 199

5-pin DIN plug and chassis socket.
15A terminal block (5 sections needed).
0.1in. matrix stripboard, size 17 strips by 41 holes.
L.e.d. panel mounting clips (9 off), solder tags, sleeving, 13A mains wire, immersion heater wire, 5-core wire.
ABS box size 190 x 110 x 60mm external.
VA1067S miniature rod thermistors (4 off).

RTH1,
2,3,4

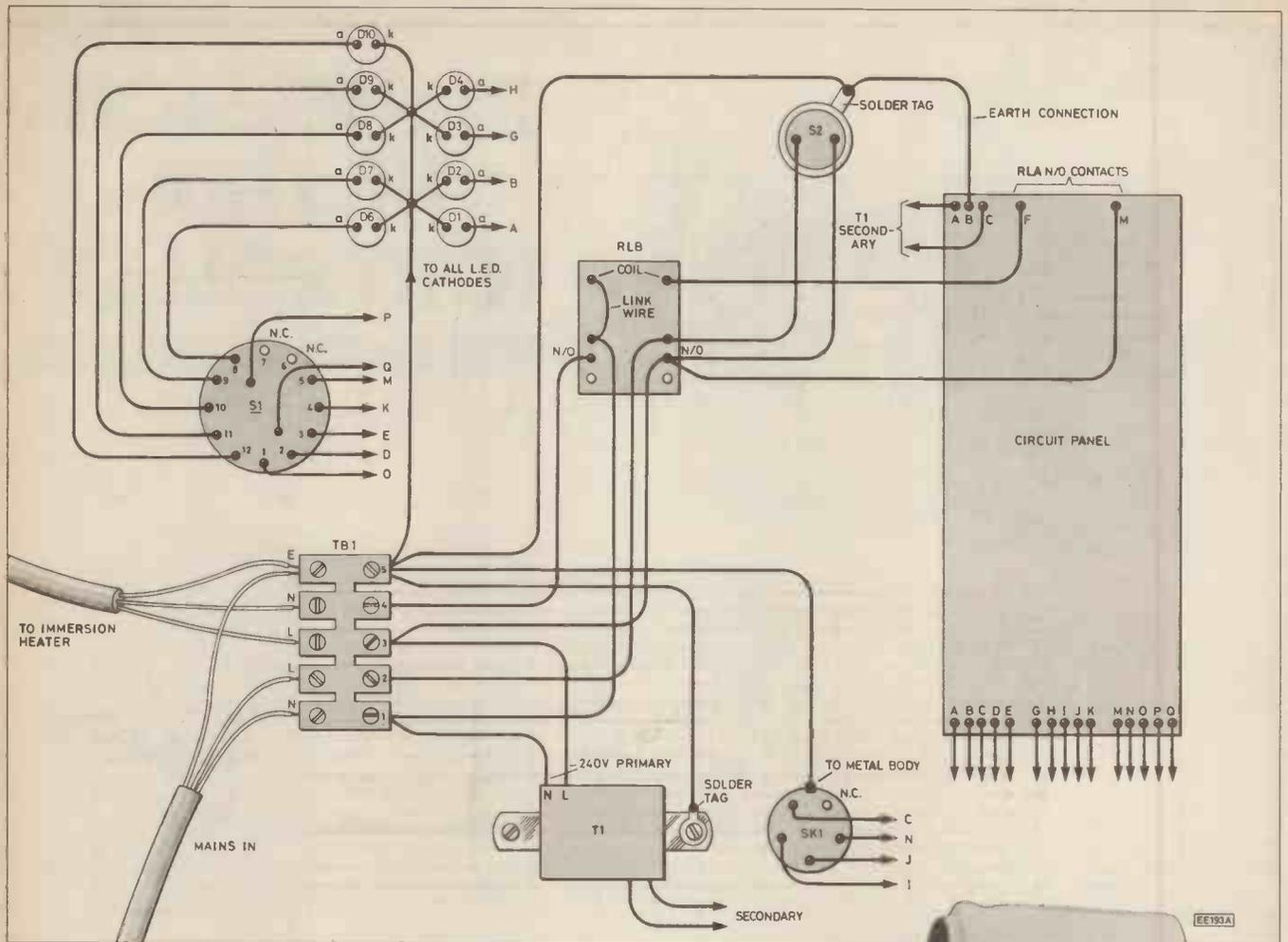


Fig. 3. Wiring diagram.

Make RLB connections using $\frac{1}{4}$ in. connectors. Do not solder the wires direct. Connections between the contacts of RLB and TB1 must be made with mains wire of at least 13A capacity (40/0.2mm). Those between RLA contacts and RLB also the link wire at RLB and connections to S2 are made using light-duty mains wire.


Leave VR1 to 4 adjusted to approximately mid-track position, slide the circuit panel into position and fit the lid of the case bending the leads of C1 as necessary. Check that there are no trapped wires and that the i.e.d. connections do not cause short circuits.

TESTING

Note: All tests and adjustments must be made with the lid of the case on. A basic check may be made on the circuit before attaching the thermistors to the hot water cylinder. Using light-duty mains wire, connect a mains plug to TB1/2, 1 and 5 (Live, Neutral and Earth respectively) and fit a 3A fuse. Connect the Live, Neutral and Earth wires of a table lamp

to TB1/3, 4 and 5 respectively. Connect five short temporary wires to the DIN plug noting that the common one is connected to the metal body. Set S1 to Level 1, plug the unit into the mains and press S2. RLB should click distinctly and the lamp light. D6 should light but all other i.e.d.s remain off. Rotate S1 noting that D7 to D10 light in the correct sequence. With S1 at Level 1, connect the Level 1 and Common sensor wires together. D1 should light. Touch the Level 2 and Level

3 wires to those already connected—D2 and D3 should light. Add the Level 4 sensor wire and the system should switch off. Re-activate the circuit and test the Cancel position of S1. If all is well attention may be given to attaching the thermistors to the copper cylinder. Begin by extending the leads as indicated in Fig. 4. Although 5 separate lengths of light-duty stranded wire could be used, it is more convenient to use 4-core screened wire with the screening forming the common wire. An

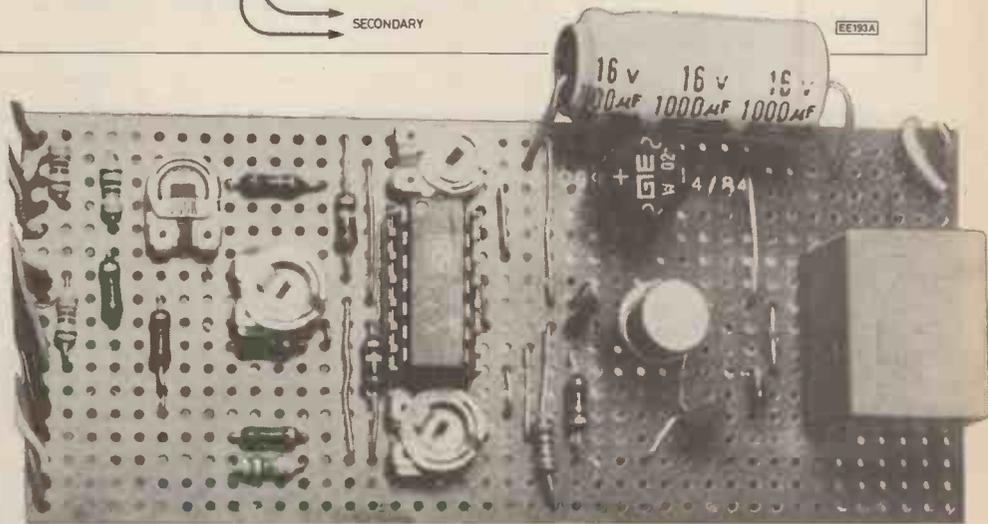

IMMERSION HEATER CONTROLLER


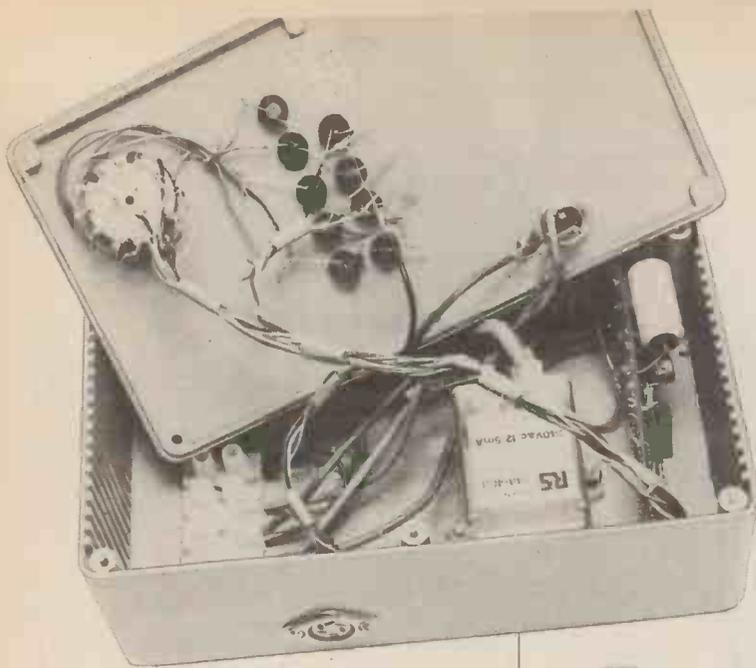


Fig. 4. Wiring between the thermistors and PL1, positioning of the thermistors on the hot water cylinder, and their mode of connection is illustrated


alternative would be to use 4-core telephone line with an additional wire taped to it. Remove the cylinder insulating jacket and clean the copper surface in the chosen areas using emery cloth. In the prototype, these positions were $\frac{1}{5}$, $\frac{2}{5}$, $\frac{3}{5}$, and $\frac{4}{5}$ of the distance from the top of the cylinder. Quick-setting epoxy-resin adhesive should then be used to secure the thermistors. It is necessary to provide insulation between the bodies of the thermistors and the metalwork; if this is not done the circuit will fail to work properly. The film of adhesive provides this insulation but care must be taken not to make it too thick or the free flow of heat will be impaired. Finally, solder the wires to the DIN plug at the other end.

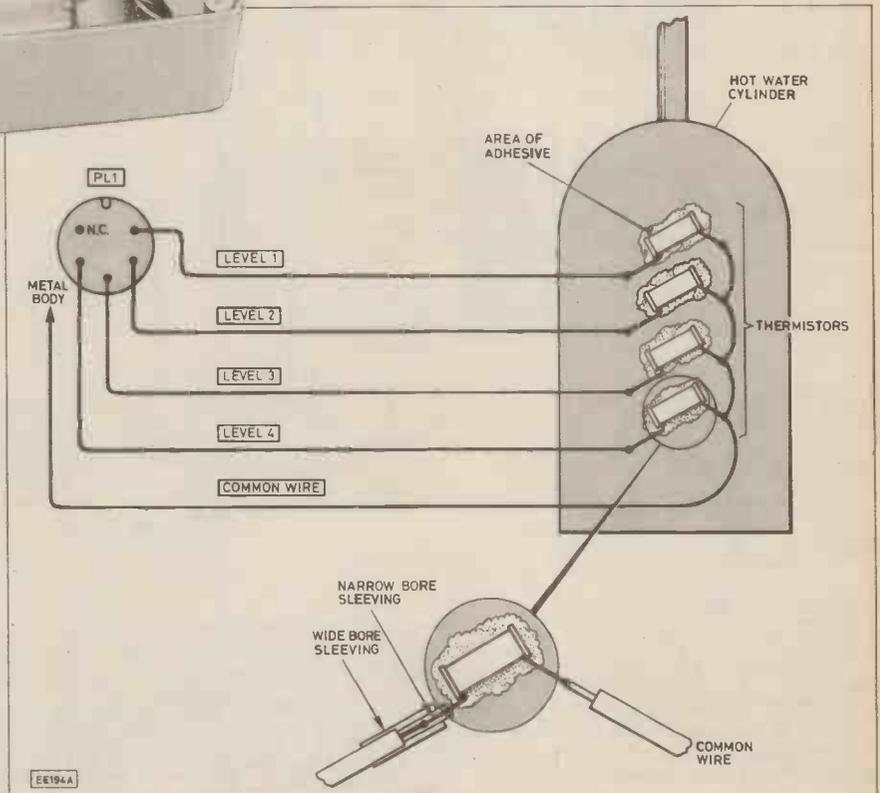

MAINS CONNECTIONS

Make the connections from TB1 to the wall switch and to the immersion heater. It is essential to use wire approved for use in immersion heater installations. This is butyl rubber heat resistant wire of 20A rating. Under no circumstances omit any earth connections. Fit strain relief bushes to the wires where they pass through the case.

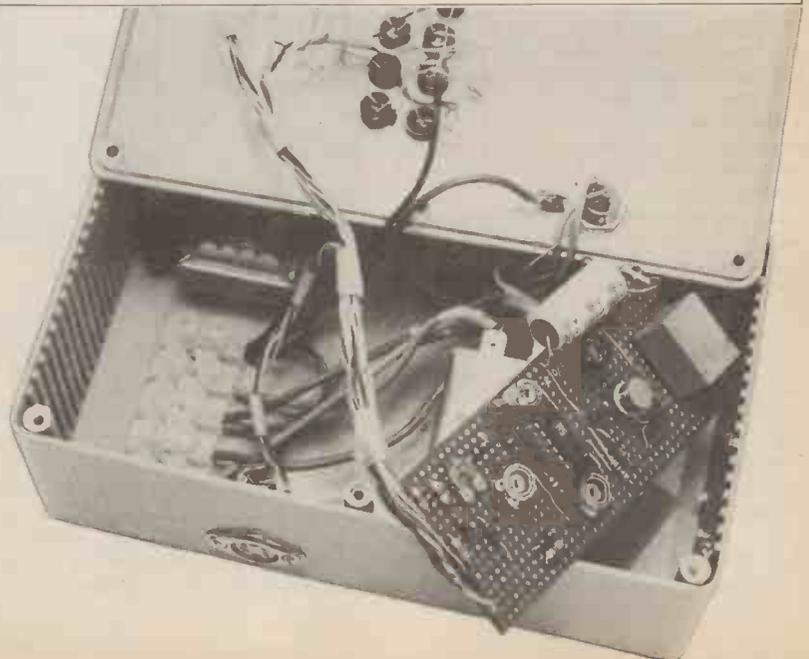After re-connecting the mains supply, the system may be checked and the preset potentiometers adjusted over a period of a few days to give the correct operating temperatures. □



NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

BRIGHT LIGHT

A FAMILY of standard, seven segment l.e.d. displays, driver boards and power supplies are being marketed by Antech Opto-Systems.

The standard range of seven segment l.e.d. displays are available in sizes ranging from 1½ to 4 inches in half-inch intervals, individual l.e.d.s being mounted on printed circuit matrix boards. The displays are fully diffused and available in red, yellow and green.



There are three different power supplies for running 1½ and 2, 2½ and 3, and 3½ and 4in. displays.

A range of ancillary boards are available, including a high power driver board with 32 input/output ports and a splitter board for driving two separate displays, each displaying the same information.

Three control boards are included in the display family, a four digit serial data I/O board, 0-2V or 0-200mV DVM board and a BCD input board. In addition to the standard range of displays, the superbright displays are available in sizes manufactured to customer requirements.

For further information, readers should contact:


*Antech Opto-Systems Ltd.,
Dept EE, 14 Bell Street,
Maidenhead, Berks SL6 1BR.*

CIRCUITMATE

A COMPACT hand-held digital multimeter for only £32.25 (plus VAT) is now being marketed by Beckman Industrial



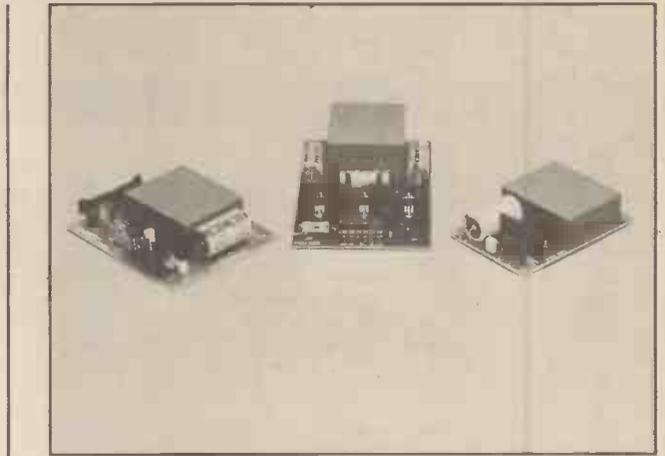and is available from their network of distributors. The meter is the Circuitmate DM10



LOW PROFILE

A RANGE of p.c.b. mounted power supplies has recently been introduced by Lascar Electronics. All have an encapsulated low profile transformer giving a compact and rugged construction. The mains 220-240V a.c. input may be changed to 110-120V a.c. by simply moving an on-board link.

The range includes single rail, twin rail and triple rail types, some being fitted with card handles and connectors for rack mounting. All types are over-current, over-temperature and short-circuit protected.

For details of prices and the complete range of output voltages available readers should contact:

*Lascar Electronics Ltd., Dept EE,
Module House, Whiteparish,
Salisbury, Wilts SP5 2SJ.*

which offers all standard multimeter measuring functions—except a.c. current—in a case size of only 120 x 70 x 24mm.

The DM10 measures d.c. voltage in five ranges from 200mV to 1000V; a.c. voltage in two ranges of 200V and 500V; d.c. current in four ranges from 200µA to 200mA, and resistance in five ranges from 200 ohm to 2 Megohm.

A separate diode test function is also incorporated. Measurements are read on a high-contrast, 3½ digit l.e.d. display.

Addresses of nearest stockists may be obtained from:

*Beckman Industrial Ltd.,
Electronic Technologies Division,
Dept EE, Mylen House,
11 Wagon Lane, Sheldon,
Birmingham B26 3DU.*

TIME FOR GAMES


JOINING Systema's range of dedicated computer games are three new products of strategy and tactics—Backgammon, Checkers and Reversi.

Each game is pocket sized with a large liquid crystal display area and all models have two levels of difficulty and a two player option.

The BM424 Backgammon computer calls for fast thinking and good luck. Your fate rides on the roll of the built-in electronic dice and the keyboard will react as quickly as you can think.

Checkers is better known in the UK as "Draughts" and Reversi also known as "Othello".

All three models are now

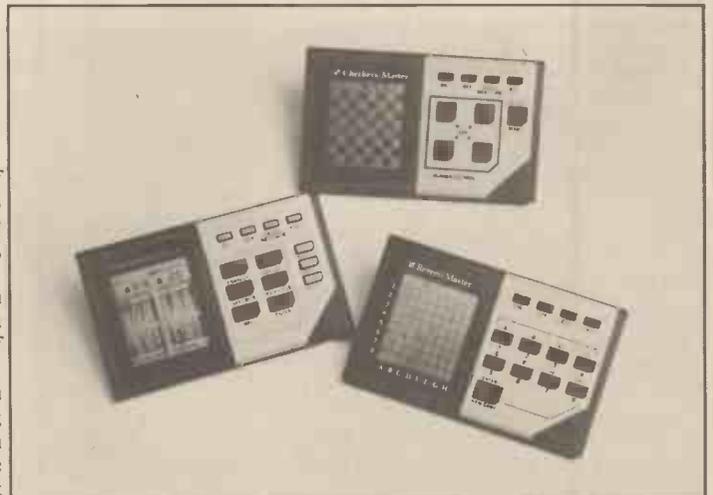

available from Systema and retail for about £40. For more details readers should write to:

*Systema (UK) Ltd.,
Dept EE, 72/74 South Street,
Reading, Berks, RG1 4LG.*

EVERYDAY ELECTRONICS PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed here.

PROJECT TITLE	Order Code	Cost
— JUNE '83 —		
Eprom Programmer, TRS-80	8306-01	£9.31
Eprom Programmer, Genie	8306-02	£9.31
Eprom Programmer, TRS-80 & Genie	8306-03	£1.98
— JULY '83 —		
User Port Input/Output <i>M.I.T. Part 1</i>	8307-01	£4.82
User Port Control <i>M.I.T. Part 1</i>	8307-02	£5.17
— AUGUST '83 —		
Storage Scope Interface, BBC Micro	8308-01	£3.20
Car Intruder Alarm	8308-02	£5.15
High Power Interface <i>M.I.T. Part 2</i>	8308-03	£5.08
Pedestrian Crossing Simulation <i>M.I.T. Part 2</i>	8308-04	£3.56
Electronic Die	8308-05	£4.56
— SEPTEMBER '83 —		
High Speed A-to-D Converter <i>M.I.T. Part 3</i>	8309-01	£4.53
Signal Conditioning Amplifier <i>M.I.T. Part 3</i>	8309-02	£4.48
Stylus Organ	8309-03	£6.84
Distress Beacon	*8309-04	£5.36
Distress Beacon Pocket Version	8309-05	£3.98
— OCTOBER '83 —		
D-to-A Converter <i>M.I.T. Part 4</i>	8310-01	£5.77
High Power DAC Driver <i>M.I.T. Part 4</i>	8310-02	£5.13
Electronic Pendulum	8310-03	£5.43
— NOVEMBER '83 —		
TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i>	8311-01	£5.46
Stepper Motor Manual Controller <i>M.I.T. Part 5</i>	8311-02	£5.70
Digital Gauss Meter	8311-03	£4.45
Speech Synthesiser for BBC Micro	8311-04	£3.93
Car On/Off Touch Switch	8311-05	£3.11
— DECEMBER '83 —		
4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i>	8312-01	£5.72
4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i>	8312-02	£5.29
TRS-80 Twin Cassette Interface	8312-03/09	£7.43
Touch Operated Die (Dot matrix)	8312-05/06	£4.34
Touch Operated Die (7-segment)	8312-05/07	£4.34
Continuity Tester	8312-08	£3.41

*Complete set of boards. **Calibrated with C1, VR1 and IC3 fitted.
M.I.T.—Microcomputer Interfacing Techniques, 12-Part Series.

— JANUARY '84 —		
Central Heating Pump Delay	8401-01	£3.33
Biological Amplifier <i>M.I.T. Part 7</i>	8401-02	£6.27
Temp. Measure & Control for ZX Compr		
Analogue Thermometer Unit	8401-03	£2.35
Analogue-to-Digital Unit	8401-04	£2.56
Games Scoreboard	8401-06/07	£9.60
— FEBRUARY '84 —		
Eprom Programmer/ROM Card for ZX81	**8402-01	£7.84
Oric Port Board <i>M.I.T. Part 8</i>	8402-02	£9.56
Negative Ion Generator	*8402-03	£8.95
Temp. Measure & Control for ZX Compr		
Relay Driver	8402-04	£3.52
— MARCH '84 —		
Latched Output Port <i>M.I.T. Part 9</i>	8403-01	£5.30
Buffered Input Port <i>M.I.T. Part 9</i>	8403-02	£4.80
VIC-20 Extension Port Con. <i>M.I.T. Part 9</i>	8403-03	£4.42
Com. 64 Extension Port Con. <i>M.I.T. Part 9</i>	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro	8403-05	£4.63
— APRIL '84 —		
Multipurpose Interface for Computers	8404-01	£5.72
Data Acquisition "Input" <i>M.I.T. Part 10</i>	8404-02	£5.20
Data Acquisition "Output" <i>M.I.T. Part 10</i>	8404-03	£5.20
Data Acquisition "PSU" <i>M.I.T. Part 10</i>	8404-04	£3.09
Timer Module	8404-05	£3.58
A.F. Sweep Generator	8404-06	£3.55
Quasi Stereo Adaptor	8404-07	£3.56
— MAY '84 —		
Simple Loop Burglar Alarm	8405-01	£3.07
Computer Controlled Buggy <i>M.I.T. Part 11</i>		
Interface/Motor Drive	8405-02	£5.17
Collision Sensing	8405-03	£3.20
Power Supply	8405-04	£4.93
— JUNE '84 —		
Infra-Red Alarm System	8406-01	£2.55
Spectrum Bench PSU	8406-02	£3.99
Speech Synthesiser <i>M.I.T. Part 12</i>	8406-03	£4.85
Train Wait	8406-04	£3.42
— JULY '84 —		
Ultrasonic Alarm System	8407-01	£4.72
Atom EPROM Simulator	8407-02	£3.08
Electronic Code Lock		
Main board	8407-03	£2.70
Keyboard	8407-04	£3.24
— AUGUST '84 —		
Microwave Alarm System	8408-01	£4.36
Temperature Interface—BBC Micro	8408-02	£2.24
— SEPTEMBER '84 —		
Op-Amp Power Supply	8409-01	£3.45
— OCTOBER '84 —		
Micro Memory Synthesiser	*8410-01	£8.20
Drill Speed Controller	8410-04	£1.60
— NOVEMBER '84 —		
BBC Audio Storage Scope Interface	8411-01	£2.90
Proximity Alarm	8411-02	£2.65
— DECEMBER '84 —		
TV Aerial Pre-Amp	*8412-01	£1.60
Digital Multimeter	*8412-02/03	£5.20
Mini Workshop Power Supply	8412-04	£2.78
— JANUARY '85 —		
Power Lighting Interface	8501-01	£8.23
Games Timer	8501-02	£1.86
Spectrum Amplifier	8501-03	£1.70
— FEBRUARY '85 —		
Solid State Reverb	8502-01	£3.68
Computerised Train Controller	8502-02	£3.38
— MARCH '85 —		
Model Railway Points Controller	8503-01	£2.78
— APRIL '85 —		
Insulation Tester	8504-02	£2.53
Fibre larm	8504-03	£3.89

QUALITY COMPONENTS...FAST!

SEMICONDUCTORS				CONNECTORS		CAPACITORS		RESISTORS		
AC127	35p	BU208	280p	W01	34p	40129F	28p	40668E	26p	<p>4mm PLUGS - Black and red 15p EACH. Green, White, Yellow, Brown and Blue - 16p EACH.</p> <p>4mm CHASSIS SOCKETS Above colours - 15p EACH.</p> <p>4mm TERMINAL POSTS Above colours - 44p EACH.</p> <p>PLASTIC PHONO PLUGS - Black, Red, White, Blue, Yellow - All 12p EACH.</p> <p>BNC CONNECTORS Line Plug - 99p Line Socket - £1.15 Chassis Socket - 48p</p> <p>D-RANGE PLUGS 9 WAY - £1.32 15 WAY - £1.42 25 WAY - £1.46</p> <p>D-RANGE SOCKETS 9 WAY - £1.32 15 WAY - £1.96 25 WAY - £1.30</p> <p>BT CONNECTORS Line cord & plug - £1.92 Wall Socket - £2.94</p> <p>DIN PLUGS - 2pin - 12p; 3pin - 15p; 4pin - 33p; 5pin 180 - 17p; 6 pin - 42p; 7pin - 24p; 8pin - 62p</p> <p>SEE THE 1985 CATALOGUE FOR A HUGE RANGE OF COMPONENTS</p>
AC128	35p	CA3046	99p	W02	38p	40138E	38p	40678E	250p	
AD161	58p	CA3080E	135p	W04	44p	40148E	68p	40688E	28p	
AD162	60p	CA3140	90p	W005	30p	40158E	65p	40698E	28p	
BC1078	17p	CA3189	240p	ZM14	120p	40168E	35p	40708E	30p	
BC1082	18p	CA3240	145p	ZT500	22p	40178E	55p	40718E	21p	
BC109C	17p	LF347	175p	ZT502	18p	40188E	65p	40728E	90p	
BC140	37p	LF351	75p	ZT504	32p	40198E	41p	40738E	28p	
BC141	36p	LF353	96p			40208E	65p	40758E	35p	
BC158C	12p	LM301A	35p	1N4001	7p	40218E	68p	40768E	74p	
BC169C	12p	LM311	99p	1N4002	5p	40228E	72p	40778E	32p	
BC182L	12p	LM380	165p	1N4005	6p	40238E	28p	40788E	32p	
BC193L	15p	LM381	180p	1N4007	7p	40248E	48p	40818E	28p	
BC194L	16p	LM382	150p	1N4148	4p	40258E	28p	40828E	28p	
BC212	14p	LM384	170p	1N914	5p	40268E	110p	40858E	59p	
BC214	12p	LM387	175p	2N2219	37p	40278E	38p	40898E	140p	
BC327	14p	LM389	150p	2N2369A	28p	40288E	55p	40938E	40p	
BC328	14p	LM3914	380p	2N2646	30p	40298E	60p	40948E	110p	
BC337	14p	MJ2955	115p	2N2904	32p	40318E	130p	40988E	85p	
BC547	9p	MJ222	505p	2N2907	26p	40328E	65p	40998C	96p	
BC548	12p	MJF102	85p	2N3054	79p	40338E	94p	40106	44p	
BC549	12p	NE555	37p	2N3055H	105p	40358E	65p	40109	86p	
BCY70	22p	NE556	65p	2N3703	14p	40388E	85p	40162	66p	
BCY71	22p	NE565	155p	2N3704	12p	40408E	60p	40174	72p	
BD131	49p	NE566	160p	2N3705	12p	40418E	69p	40194	79p	
BD132	50p	OA200	9p	2N3706	14p	40428E	56p	45028E	60p	
BD135	37p	OA47	21p	2N3708	12p	40438E	60p	45038E	55p	
BD139	40p	OA90	9p	2N3711	11p	40448E	63p	45088E	150p	
BD140	40p	OA91	10p	2N3772	195p	40458E	115p	4510	65p	
BD180	45p	SI490	300p	2N3903	16p	40468E	75p	4511	70p	
BF256	37p	TD11022	640p	2N3904	18p	40478E	75p	45208E	65p	
BF259	37p	TD11024	179p	2N3905	14p	40488E	50p	45688E	310p	
BF299	34p	TIP122	95p	2N4558	59p	40498E	56p	7106	810p	
BF304	34p	TIP127	75p			40508E	38p	7107	810p	
BF385	37p	TIP2955	95p	40008E	23p	40518E	60p	741	28p	
BF387	38p	TIP3055	87p	40018E	28p	40528E	60p	748C	59p	
BF388	35p	TIP31A	39p	40028E	28p	40538E	72p			
BFY50	31p	TIP41A	45p	40038E	75p	40548E	88p			
BFY51	38p	TIP42	45p	40078E	28p	40568E	95p			
BFY52	31p	VN610KM	92p	40088E	75p	40608E	82p			
BU205	200p	VN66AF	188p	40118E	28p	40638E	90p			

PLEASE REMEMBER OUR PRICES INCLUDE 15% VAT!


AB MICROSYSTEMS

P.O. BOX 12, SWINTON, MANCHESTER M27 3WS.

PRICES INCLUDE VAT @ 15%. POSTAGE: PLEASE ADD 30p TO ORDERS UNDER £5. OFFICIAL ORDERS WELCOME. DESPATCH NORMALLY 24 HRS. E.&O.E.

MASTER Electronics - Microprocessors - Now! The PRACTICAL Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic & computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagrams.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

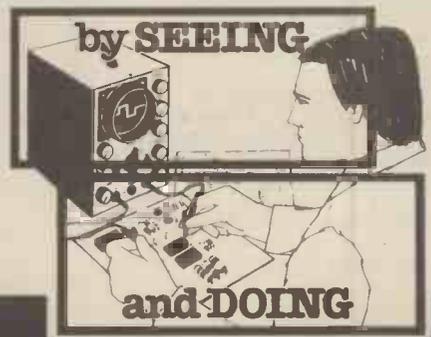

New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

Please send your brochure without any obligation to:- I am interested in:

NAME _____
ADDRESS _____
BLOCK CAPS PLEASE

- ELECTRONICS
 MICROPROCESSORS
 RADIO AMATEUR LICENCE
 CITY & GUILDS EXAMS

Other Subjects _____

EE4

FREE!
Colour Brochure

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ 14 OHS



OR TELEPHONE US
062 687 2598
OR TELEX 22758
(24 HR SERVICE)

EVERYDAY ELECTRONICS AT YOUR and computer PROJECTS

Reach effectively and economically to-days enthusiasts anxious to know of your through our semi-display and classified pages. Semi-display spaces may be booked at timetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word number 60p extra. All cheques, postal orders, etc., to be made payable to Everyday Electronics crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisement, should be sent to the Classified Advertisement Department, Everyday Electronics and 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone

Receivers & Components

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

RESISTORS 1,000 mixed 1/8w, 1/4w, 1/2w, 2%, 5%, 10%, C. film £3.45 inc. P&P. D. J. HOOKER, Romney Marsh Electronics, Pennywood, Clark Road, Romney Marsh, Kent TN28 8PB.

VERY LARGE PACK OF MIXED COMPONENTS. Capacitors, transistors, resistors, diodes, boards, thyristors, multi-pin plugs & sockets and many more items £6.50p post & packing inclusive. G. EVANS, 7 Mendip Close, Pendine Park, Summerhill, Wrexham, Chwyd.

Security

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- LOWEST DISCOUNT PRICES
- HIGHEST QUALITY EQUIPMENT
- FREE DIY DESIGN GUIDE
- FULLY ILLUSTRATED
- MICROCHIP CIRCUITRY
- QUICK DESPATCH SERVICE
- FULL INSTRUCTIONS

SEND SAE OR PHONE

C-TEC SECURITY, Dept EE.

Unit 1, Stephensway Ind Estate, Goose Green, Wigan WN3 6PH. Telephone (0942) 42444

Trade Enquiries Welcome

Security Cont.

WHO CAN PUT A PRICE ON A PEACE OF MIND

PROFESSIONAL EQUIPMENT AT LOW! LOW! PRICES.

HOME SECURITY IS NOW AVAILABLE AT TRADE PRICES

2 Ealing Road, Aintree, Liverpool L9 0HU, Merseyside.

Tel: 051-525 3440

FREE CATALOGUE PHONE OR S.A.E.

Electrical

BENCH AND PROJECT POWER SUPPLIES. Complement your electronics project with one of our quality British designed and manufactured power supplies. Send SAE with your requirements for immediate quotation. COLTECH ELECTRONIC CONTROLS LTD., Holly Lane Industrial Estate, Atherstone, Warwickshire, CV9 2HA. Telephone 08277 4299.

Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

FULL SIZE TOP QUALITY Service Sheets £2.50 + l.s.a.e. CTV/Music centres £3.50 + l.s.a.e. Repair data almost any named TV/video £10.50 in circuits. L.s.a.e. brings any quite-free magazine/pricelists. TISEE, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

Services

INVENTORS

Think of something new?
Write it down!

American industry offers potential royalties for you innovations and new products. We offer free confidential disclosure registration and initial consultation in London regarding your idea's potential value. Write without delay for your free information package.

American Inventors Corporation
82 Broad Street, Dept. EV,
Westfield, Massachusetts 01086,
United States of America
A fee based marketing company

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for Insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)

HEADING REQUIRED:

NAME

ADDRESS

EVERYDAY ELECTRONICS and COMPUTER PROJECTS

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street, London SE1 9LS
Telephone 01-261 5942

Rate:
33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

4/85

SERVICE

products and services £7-80 per single column cent (minimum 12 words), box and Computer Projects and ments, together with remit-Computer Projects, Room 01-261 5942).

Wanted

WANTED BACK ISSUES of Everyday Electronics. Telephone Kings Langley 63708 after 6 pm.

Tuition

IMPROVE YOUR PROSPECTS

with skills that employers want - learn the easy way with modern home study courses from Ideal Schools.

MODERN ELECTRONICS

Train for success in the fastest ever growing industrial sector.

COMPUTER PROGRAMMING

The demand for Programmers is increasing constantly - don't miss out!

For free booklet write today to



Miscellaneous

FREE! PARCEL OF COMPONENTS worth £10. Send only 80p postage! D. HORSLEY, 113 Clare Road, Braintree, Essex.

SCHOOLS AND COLLEGES. Send now for our 1985 catalogue top quality components at very competitive prices. ELECTRON ELECTRONICS, 62 High Street, Croydon, Surrey.

"PROJECT BUILDERS" Our cased transistorised breakdown units will save £££'s. S.A.E. for lists, 5 St Josephs Park, Ballycrotty, Downpatrick, BT30 7EN.

LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec.

This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experiments. Full instructions and 2 circuit diagrams with each S-Dec.

Send Cheque or P.O. to: Roden Products, Dep EE High March, Daventry, Northants, NN11 4DE.

£5.25 including p & p



CATALOGUE PLUS 100 MIXED RESISTORS YOURS FREE

SEE POSTAGE DETAILS BELOW

PROJECTS			BARGAINS	
Catalogue No.	Description	Price	VOLTAGE REGULATORS	
MT 11	Short-Wave Miniature Transmitter	£5.29	1 amp 5v to 220PK	5 for £2.00
A12/BS	Car Alarm System	£9.64	1 amp 12v to 220PK	5 for £2.00
A12/G	— Cabinet	£6.99	Mixed DL Switches up to 8way	5 for £2.00
A12	— Assembled	£21.85	Shaded Pole Motors - Ideal for Record Players	
RT 35	Precision Time Switch	£8.30	24v DC or 240v AC	£2.50 each
AV 300	Antenna Amplifier	£4.11	3" LED Display 7 SEG	£1.00 each
TT 31	Two-Tone Gong	£5.16	4" LED Display 7 SEG	£1.40 each
DE 21	LED VU Meter	£8.92	24 Hour Clock Display Non Multiplex	£2.50 each
SD 6	Sensor-Dimmer	£11.21	DP/AMP MC1456	10 for £5.00
UW 1054	Universal Preamplifier	£8.98	100µF 250v Radial Electrolytic	100 for £3.00
NFV 4W	NFV 4W	£5.29	47µF 16v DC Radial	10 for £1.00
NFV 8W	8W	£5.31	5000µF 12v Radial	10 for £1.00
AV 15	Final Stage Amplifier 15 Watts	£8.30	1000µF 10v DC Radial	15 for £1.00
AV 22	Final Stage Amplifier 22 Watts	£12.56	220µF 40v Axial	15 for £1.00
AV 50	Final Stage Amplifier 50 Watts	£14.61	25µF 50v Axial	20 for £1.00
LNG 33	Power Supply Unit 2-30 V/2A	£15.84	4-7µF 63v Axial	20 for £1.00
K 13	— Cabinet	£19.98	10µF 40v Axial	20 for £1.00
LNG 44.2	Laboratory Power Supply Unit	£19.95	47µF 10v Axial	20 for £1.00
SM 3 P/BS	4 Channel Sound-to-Light System	£13.28		
SM 3 P/G	— Cabinet	£11.27		
SM 3 P	— Assembled	£24.62		
STD 100	Effects Stroboscope 60 WS	£8.62		
STD 200	Effects Stroboscope 120 WS	£11.78		
C 4000	C-Mos Trainer	£37.23		
DS 1000	Disco Stroboscope	£28.57		
LL4/BS	4 Channel Running Lights System	£17.90		
LL4/G	— Cabinet	£5.29		
LL4	— Assembled	£26.51		
SOLDERING			SOLDERING INSTRUMENTS	
Multicore All Purpose Handyman Solder Pak			Order No. Description	
Contains three types of solder for electrical, metal and aluminum repairs. All in handy easy to use dispensers Handy Pak. Size 8 £2.99.			2120 K1000 soldering instrument 12 volt £9.65 each	
Ersin Multicore			2129 K1000 soldering instrument 12 volt £9.65 each	
Contains 5 cores of non-corrosive flux Uses small plastic transistors, components and fine wire. Handy Pack. Size PC115, 60/40 tin/lead 0.7mm dia £1.61. Tool Box Reel. Size 10/50/40 tin/lead 0.7mm dia £4.37.			2130 K1000 soldering instrument 24 volt £9.65 each	
			2139 K1000 soldering instrument 24 volt £9.65 each	
			2140 K1000 soldering instrument 48 volt £9.65 each	
			2149 K1000 soldering instrument 48 volt £9.65 each	
			2150 K1000 soldering instrument 110 volt £9.65 each	
			2159 K1000 soldering instrument 110 volt £9.65 each	
			2160 K1000 soldering instrument 220 volt £9.65 each	
			2169 K1000 soldering instrument 220 volt £9.65 each	
			2170 K1000 soldering instrument 240 volt £9.65 each	
			2179 K1000 soldering instrument 240 volt £9.65 each	
COMPONENT PACKS			MULTIPURPOSE BOXES	
Pack No.	Qty	Description	All Dimensions Internal	
N 11	12	RED 5mm LED	Type No.	A B C Price
N 12	6	Green 5mm LED	13	71 mm 46 mm 22 mm £0.60p
N 13	6	Yellow 5mm LED		(2.80") (1.81") (0.88")
N 51	15	White off Red on LED	MB1-00	75 mm 56 mm 35 mm £0.80p
N 14	25	5mm LED Clips & Rings		(2.95") (2.20") (1.38")
N 52	5	OCF 71	MB2-00	95 mm 71 mm 35 mm £0.95p
N 15	30	500mΩ Zeners 5%		(3.74") (2.87") (1.38")
N 21	100	1 amp Rect. Diodes in 4000 Series	MB3-00	115 mm 95 mm 37 mm £1.10p
N 22	200	4148 Diodes		(4.52") (3.74") (1.46")
N 31	200	4151 Diodes	MB3-50	145 mm 95 mm 55 mm £1.35p
N 23	12	1 amp Bridge Rect.		(5.70") (3.74") (2.16")
N 24	20	3 amp Rect. Diodes	MB4-00	207 mm 122 mm 77 mm £2.52p
N 25	1	ORP 12 Photo Cell		(8.15") (4.80") (3.03")
N 61	720	1/4 watt Carbon Film 1W 10mm	MB5-00	213 mm 142 mm 57 mm £1.90p
		ten of each value		
N 26	250	Mixed Resistors		
N 16	100	Mixed Trans. Hardware		
N 27	10	BR 100 Diac		
N 28	1	2N3055 Power Transistor		
N 17	10	BC 108C		
N 18	15	BC 537		
N 19	10	BC 107		
N 20	10	BC 108		
N 121	15	6FR 86		
N 123	10	BC 109B		
N 124	100	Transistor Pads		
N 29	40	10mm horiz pre-set (10 values)		
N 125	10	Mixed Pot. Inc. slides		
N 126	12	8 pin DIL Sockets		
N 127	10	14 pin DIL Sockets		
N 128	10	16 pin DIL Sockets		
N 230	15	18 pin DIL Sockets		
N 129	15	IC's all different		
N 231	10	LM 3909		
N 232	10	Mixed DTL		
N 233	10	Mixed TTL (7.4 series)		
N 234	5	709		
N 53	10	LM 324		
N 54	1	555 Timer		
N 55	25	741		
N 235	50	Electrolytics Axial		
N 236	50	Electrolytics Radial		
N 237	100	Ceramic Discs		
N 238	100	Ceramic Plates		
N 239	5	4700µF 25v Tag Elect. Z11"		
N 240	10	1000µF 63v Ax. Elect.		
N 241	50	022µF 400v Rad. Poly		
N 242	10	100µF 250v Axial		
N 243	10	2.2µF 160v Rad. Poly		
N 244	20	V.D.R.S.		
N 56	3	10,000µF 40v Comp Grade Elect.		
N 62	12kg	Reel 23g Solder		
N 130	20	500mA A/S 20mm Fuses		

ALL PRICES INCLUDE VAT - ALL GOODS BRAND NEW & NORMALLY DESPATCHED BY RETURN POST.

TERMS: Cash with order. POST & PACKING: Please add 95p to all orders including free offers.

AC/DC ELECTRONICS COMPONENTS

DEPT EE, 45 CHURCH STREET, ENFIELD, MIDDLESEX.

*** BAKER ***
GROUP P.A. DISCO AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp. Illustrated £99
 150 watt Output, Slave 500 mv. Input, 4+8+16 ohm Outputs .. £80
 150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs £125
 150 watt P.A. Vocal, 8 inputs, High/Low Mixer Echo Socket £129
 100 watt Valve Model, 4 inputs, 5 Outputs, Heavy duty..... £125
 60 watt Mobile 240v AC and 12v DC 4-8-16 ohm+100v line £89

MIKES Dual Imp £20, Floor Stand £13, Boom Stand £22, PP £2.

REVERB UNIT for Microphone or Musical Instruments £35 PP £1.
 ELECTRONIC ECHO Machine for mic/etc. £85. Deluxe £95 PP £1.
 H+H AMPLIFIERS 500 watt stereo "Reconditioned" £275 PP £5

BAKER LOUDSPEAKERS Post £2 each

Type	Model	Size	Watts	Ohms	Price
P.A./Disco/Group	DG50/10	10	50	8/16	£18.00
Midrange	Mid 100/10	10	100	8	£25.00
Hi-Fi	Major	12in	30	4/8/16	£16.00
Hi-Fi	Superb	12in	30	8/16	£28.00
P.A./Disco/Group	DG45	12in	45	4/8/16	£16.00
Hi-Fi	Woofers	12in	80	8	£25.00
Hi-Fi	Auditorium	15in	60	8/16	£37.00
P.A./Disco/Group	DG75	12in	75	4/8/16	£20.00
P.A./Disco/Group	DG100	12in	100	8/16	£26.00
P.A./Disco/Group	DG100/15	15in	100	8/16	£35.00

DISCO CONSOLE Twin Decks, mixer pre amp £145, Carr £10.
 Ditto Powered 120 watt £199; or Complete Disco 120 watts £300.
 150 watt £360; 360 watt £410, Carr £30.

DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2 ceramic/ tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, panel or desk mounting, matt black fascia. Tape output facility. £59. Post £1.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. £129 PP £2

Headphone Monitor, Mike Talkover Switch
 As above but 3 deck inputs, 4 line/aux inputs, 2 mic inputs, 2 headphone monitors £145.

P.A. CABINETS (empty) Single 12 £32; Double 12 £38, carr £10.
 WITH SPEAKERS 45W £50; 75W £54; 90W £73; 150W £82.
 HORNBOXES 200 Watt £32, 300 Watt £36, Post £4.

WATERPROOF HORNS 8 ohms, 25 watt £20, 30 watt £23, 40 watt £28, 20W plus 100 volt line £36, Post £2

MOTOROLA PIEZO ELECTRONIC HORN TWEETER, 3 1/2in, square, 65 100 watts. No crossover required. 4-8-16 ohm, 7/8x3 1/2in. £10

CROSSOVERS, TWO-WAY 3000 c/s 30 watt £2, 60 watt £5, 100 watt £6
 3 way 950 cps/2000 cps, 40 watt rating £4, 60 watt £6.50, 100 watt £10.
 LOUDSPEAKER BARGAINS Please enquire, many others in stock.

4 ohm, 5in, 7x4in, £2.50; 6 1/2in, 8x5in, £3, 8in, £3.50 6 1/2in, 25W £7.50.
 8ohm, 7 1/2in, 3in, £2; 5x3in, 6x4in, 7x4in, 5in, £2.50, 6 1/2in, 8x5in £3, 8in, £4.50, 10in, £5, 12in, 18in, 25W £5.50, 8 in Twin, 60W £7, £12, £14.
 15 ohm, 2 1/4in, 3 1/2in, 5x3in, 6x4in, £2.50, 6 1/2in, 10W £5, 8in, £4, 10in, £7.
 25 ohm, 3in, £2; 5x3in, 6x4in, 7x4in, £2.50, 120 ohm, 3 1/4in dia, £2.

Make	Model	Size	Watts	Ohms	Price	Post
AUDAX	WOOFER	5 1/2in	25	8	£10.50	£1
GOODMANS	HIFAX	7 1/2x4 1/4in	100	8	£34	£2
GOODMANS	H8 WOOFER	8in	60	8	£13.50	£1
WHARFEDALE	WOOFER	8in	30	8	£9.50	£2
CELESTION	DISCO/Group	10in	50	8/16	£21	£2
GOODMANS	HPG/Group	12in	120	8/15	£30	£2
GOODMANS	HPD/Disco	12in	120	8/15	£30	£2
H+H	Disco/Bass	15in	100	4/8/16/44	£3	£3
GOODMANS	HPD/BASS	15in	250	8	£72	£4
GOODMANS	HPD/BASS	18in	230	8	£84	£4

METAL GRILLES 8in, £3, 10in, £3.50, 12in, £4.50, 15in, £5.50, 18in, £7.50.

DISCO LIGHTING EQUIPMENT
 READY BUILT DELUXE 4 CHANNEL 4,000 WATT sound chaser + speed + programme controls £69, Mk2 16 programs, £89 PP £2.

PARTY LIGHT 4 Coloured Flood Lamps Flashing to Music. Self contained Sound to Light 410x196x115 £34.95 PP £2.

MAINS TRANSFORMERS Price Post

250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£7.00	£2
350-0-350V 250mA, 6.3V 6A CT £12.00 Shrouded	£16.00	£2
250V 60mA, 6.3V 2A	£5.00	£0
220V 25mA, 6V 1 Amp £3.00 220V 45mA, 6V 2 Amp	£4.00	£1

Low voltage tapped outputs available

1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00	£2	
ditto 2 amp £10.50	3 amp £12.50	5 amp £16.00	£2
31-26-0-26-31 volt 6 amp	£14.00	£2	

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid
 9V, 3A; 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A +17-0-17V, 2A; 35V, 2A; 20-40-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 50V, 2A.

£8.50 post 50p MINI-MULTI TESTER
 Pocket size instrument, o.p.v. DC volts 5, 25, 250, 500 AC volts 10, 50, 500, 1000. DC 0-250mA; 0-250ma. Resistance 0 to 600K.

De-Luxe Range Doubler Meter, 50,000 o.p.v., 7 x 5 x 2in. Resistance 0/20 meg in 5 ranges. Current 50MA to 10A. Volts 0.25/1000V DC, 10v/1000v AC. £25.00 PP £1

PANEL METERS 50MA, 100MA, 500MA, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/4x2 1/4in. £5.50 post 50p

ALUMINIUM PANELS 18 a.w.g. 12 x 12in. £1.80; 14 x 14in. £1.75; 6 x 4in. 55p; 12 x 8in. £1.30; 10 x 7in. 95p; 8 x 6in. 90p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30.

ALUMINIUM BOXES, MANY OTHER SIZES IN STOCK
 4 x 2 1/2 x 2in. £1.20; 6 x 2 x 1in. £1; 6 x 4 x 2in. £1.90; 8 x 6 x 3 in. £3; 12 x 5 x 3in. £3.60; 6 x 4 x 3in. £2.00; 10 x 7 x 3in. £3.60

HIGH VOLTAGE ELECTROLYTICS 20+20/350V 75p

16/450V	50p	220/400V	£2	32+32/500V	£2
20/500V	75p	8+8/500V	£1	32+32/350V	50p
32/350V	45p	8+16/450V	75p	32+32+32/450V	£1.50
32/500V	95p	16+16/350V	75p	16+32+32/500V	£2

SINGLE PLAY DECKS Post £2

Make	Drive	Model	Cartridge	Price
BSR	Belt	12 volt	Ceramic	£20
BSR	Belt	P232	Magnetic	£28
BSR	Rim	P207	Ceramic	£20

AUTOCHANGER BSR Ceramic £20
 AUTOCHANGER GARRARD Ceramic £24

DECCA TEAK VENEERED PLINTH space for small amplifier.
 Board cut for BSR or Garrard 18 1/4in. x 14 1/4in. x 4in. £5, Post £1

TINTED PLASTIC COVERS for Decks. £5 each Post £1

17 x 12 1/8 x 3 1/2in.	14 1/8 x 13 x 3 1/8	14 1/2 x 13 1/2 x 2 3/4in.
22 3/8 x 13 7/8 x 3in.	30 3/4 x 13 3/8 x 3 1/4in.	21 x 13 3/8 x 4 1/2in.
18 1/4 x 12 1/2 x 3in.	21 1/2 x 14 1/4 x 2 1/2in.	

RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEHORSE ROAD, CROYDON
 SURREY, U.K. TEL: 01-684 1665

Post 65p Minimum. Callers Welcome.
 Full Lists 34p Stamps. Same day despatch. Closed Wed.

ACCESS VISA



DON'T MISS OUT ON

CROFTON

CASH & CARRY BARGAINS

TELEPHONE 01-891 1923 **NOW** for details of

- Computer Monitors ● Combined
- Colour TV/Monitors ● ZX81 Key-boards ● Light Pens (BBC) ● TV
- Cameras ● Lenses ● Video Digitisers ● Eprom Erasers ● etc.

HIGH QUALITY PRODUCTS AT AMAZING PRICES

CROFTON ELECTRONICS

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW1 4AD

CRICKLEWOOD ELECTRONICS LTD

FREE!

It's no secret!

that we receive telephone calls, personal visits and postal enquiries from new customers who usually state: 'I've been recommended to you by ...'

Recommendation seems pretty sound evidence that we succeed in providing the right kind of service. Just take a look through our comprehensive component catalogue and you'll see what we mean. Ask for your free copy today, 95% of items are in stock for fast delivery.

CRICKLEWOOD ELECTRONICS LTD.
 40 Cricklewood Broadway NW2 3ET.
 01-452 0161/01-450 9995
 Telex 914977
 ALL MAJOR CREDIT CARDS ACCEPTED
 Phone or write today

INDEX TO ADVERTISERS

AB Microsystems..	237
AD/DC Electronics	239
AC Electronics	238
American Inventors	238
Benning Cross	240
Bib Audio	219
Bi-Pak	Cover II
BK Electronics Cover III	
B.N.R.E.S.	237
Bull J.	223
Cambridge Learning	208
Computronics	238
Cut Price Electronics	207
Cricklewood Electronics	240
Crofton Electronics	240
Dziubas M	188
Etravalue	210
Grandata Limited ..	186
Greenweld	186
Ideal Schools	239
ICS Intertex	186
Kelan Engineering	207
London Electronics College	188
Magenta Electronics	190
Maplin Electronics Cover IV	
Marco Trading	207
Radio Component Specialists	240
Rapid Electronics ..	189
Riscomp Ltd.	203
Roden Products	239
Skybridge Ltd.	208
T.K. Electronics	187

BENNING CROSS ELECTRONICS

67 Vicarage Road, Watford, Herts. WD1 8EJ
 Telephone WATFORD (0923) 36234
 Export orders welcome. All deliveries within 7 days.
 Postage & Packaging 75p. Orders over £15 FREE
 No V.A.T. to add Catalogue £1. Post FREE

INTRODUCTION TO ELECTRONICS. 30 projects to construct on breadboard. "NO SOLDERING" kit includes breadboard and all components to make any of 30 projects as described in 150 page instruction book. £24.95

BEGINNERS TOOL KIT. Soldering iron, solder, heatshunt, stripper/cutter, pliers, screwdriver £14.75

No	Kit Description	Price
1	Electronic Continuity Tester	£6.45
3	Ultrasonic Receiver Remote Switch	£8.95
4	Ultrasonic Transmitter Remote Switch	£6.95
5	Intercom Baby Alarm	£6.75
6	Electronic Metronome	£6.45
7	Sound Flash-Trigger	£12.25
8	B.F.O. Metal Locator	£7.95
9	Sound to Light Unit. Max 750 Watts	£6.95
10	Light Dimmer Module	£4.95
11	Variable Precision-Timer	£9.95
14	3 Watts FM Transmitter. 85 to 115MHz	£9.95
20	Car Radio Aerial Booster FM/MW. Built and Tested	£4.95
26	Power Supply Module 240V AC in 3V 25mA out. 30x20mm	£1.99
27	Power Supply Module 240V AC in 12V 25mA out. 15 high + pins	£1.99



OMP POWER AMPLIFIER MODULES

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B. and Drive circuitry to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.



OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 360 X 115 X 72mm. PRICE £32.99 + £2.50 P&P.



OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 X 123 X 60mm. PRICE £39.99 + £2.50 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 X 150 X 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 X 147 X 102mm. PRICE £79.99 + £4.50 P&P.



VU METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 X 27 X 45mm. PRICE £8.50 + 50p P&P.

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order - Standard or P.A.



19" RACK CASED MOS-FET STEREO AMPLIFIERS with twin power supplies and L.E.D. Vu meters plus X.L.R. connectors. Three models (Ratings RMS into 4 ohms):
 MF200 (100 + 100w) £169.00
 MF400 (200 + 200w) £228.85
 MF600 (300 + 300w) £274.85

Securicor Delivery £10.00

LOUDSPEAKERS

5 to 15 INCH Up to 300 WATTS R.M.S. All speakers 8 ohm Impedance.



Cabinet fixing in stock. S.A.E. for details.

POWER RANGE

- 8" 50 WATT R.M.S. Hi-Fi/Disco. 20 oz magnet. 1" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz Sens. 92dB PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.
- 12" 100 WATT R.M.S. Hi-Fi/Disco. 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. One-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.
- 15" 100 WATT R.M.S. Hi-Fi/Disco. 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. One-cast chassis. White cone. Res. Freq. 20Hz. Freq. Resp. to 2.5KHz Sens. 97dB PRICE £37.49 + £3.00 P&P ea.

McKENZIE

- 12" 85 WATT R.M.S. C1285GP Lead guitar/keyboard/Disco.
- 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB PRICE £24.99 + £3.00 P&P ea.
- 12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone. Res. Freq. 45Hz. Freq. Resp. to 14KHz PRICE £24.99 + £3.00 P&P ea.
- 15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
- 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz PRICE £49.99 + £4.00 P&P ea.

WEM

- 5" 70 WATT R.M.S. Multiple Array Disco etc.
- 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB PRICE £20.00 + £1.50 P&P ea.
- 8" 150 WATT R.M.S. Multiple Array Disco etc.
- 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £27.00 + £1.50 P&P ea.
- 10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
- 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £30.00 + £2.00 P&P ea.
- 12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
- 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £38.00 + £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)

- 5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
- 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB PRICE £9.99 + £1.00 P&P ea.
- 6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
- 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.
- 8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
- 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 + £1.50 P&P ea.

PANTIC HOBBY KITS

Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 X 46 X 14mm (9 volt) Price: £8.62 + 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 X 84 X 12mm (12 volt) Price: £13.74 + 75p P&P.

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 X 70 X 22mm (9/12 volt). Price: £17.82. Transmitter 80 X 50 X 15mm (9/12 volt). Price: £11.27 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

Indoor alarm - Electronic swept freq siren 104dB output.

Outdoor Alarm - Electronic swept freq siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £148.00 Usual Price £228.85

BKE's PRICE £79.99 + £4.00 P&P

? Why buy a collection of self-assembly boards!

IDEAL for Workshops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full Range 45Hz - 20KHz. OMP 12/100 watts 20" X 15" X 12" £125.00 per pair. OMP 10/200 watts 18" X 15" X 11" £145.00 per pair. OMP 12/300 watts 20" X 15" X 11" £169.00 per pair.

Delivery: Securicor £8.00 per pair

STEREO CASSETTE DECK



STEREO CASSETTE DECK

Ideal for installing into Disco and Hi-Fi cabinet/Consoles. Surface mounting (Horizontal). Supplied as one unit with all electronics including mains power supply. * Metal top panel Black finish * Piano type keys including pause * Normal/Chrome tape switch * Twin Vu Meters * 3 Digit counter * Slider Record Level control. Size 171 X 317 mm Depth 110 mm. PRICE £35.99 + £3.00 P&P

1 K-WATT SLIDE DIMMER

* Control loads up to 1Kw * Compact Size 4 1/2" X 1" X 2 1/2" * Easy snap in fitting through panel/cabinet cut out * Insulated plastic case * Full wave control using 8 amp triac * Conforms to BS800

* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc. PRICE £12.99 + 75p P&P (Any quantity).

BSR P295 ELECTRONIC TURNTABLE


* Electronic speed control 45 & 33 1/3 r.p.m. * Plus/Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1/2" cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14V D.C. 65mA. Price £36.99 - £3.00 P&P



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p

PIEZO ELECTRIC TWEETERS MOTOROLA

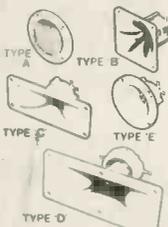Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 Watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £5.39 each + 40p P&P.
 TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P.
 TYPE 'C' (KSN6016A) 2" X 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P.
 TYPE 'D' (KSN1025A) 2" X 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P.
 TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P.
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 X 85 mm. Price £3.99 + 40p P&P

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 X 5 band L/R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features. 5 Inputs with individual faders providing a useful combination of the following: - 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch, Headphone Monitor, Pan Pot, L. & R. Master Output controls. Output 775mV. Size 350 X 280 X 90mm. Price £134.99 - £3.00 P&P



B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572




POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.





All new in the 1985 Catalogue

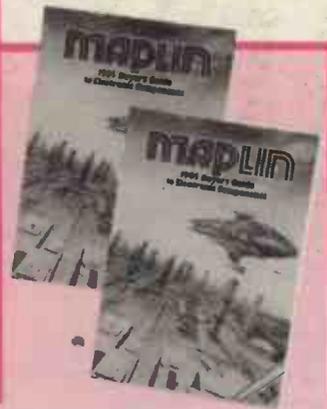

From a gentle purr to a mighty roar, the tightly controlled power of the beast is yours to command!

PROFESSIONAL QUALITY HIGH POWER LOUDSPEAKERS

A new range of superb quality loudspeakers.

- ★ Virtually indestructible high temperature voice-coil reinforced with glass-fibre
- ★ 100% heat overload tolerance
- ★ Advanced technology magnet system
- ★ Rigid cast alloy chassis
- ★ Linen or Plastiflex elastomer surrounds
- ★ 5-year guarantee (In addition to statutory rights)



- Available in 5, 8, 10, 12, 15 and 18 inch models with 8Ω and some 16Ω impedances, and with input powers ranging from 50W to 300W e.g.
 - 5in. 50W 95dB 8Ω: XG39N / 16Ω: XG40T £17.95§
 - 8in. 100W 98dB 8Ω: XG43W £29.95§
 - 10in. 100W 100dB 8Ω: XG46A £29.95§
 - 12in. 100W 101dB 8Ω: XG49D £29.95§
 - 12in. Twin Cone 100W 100dB 8Ω: XG50E / 16Ω: XG51F £31.95§
- Note - the output power doubles for each 3dB increase (ref 1W @ 1m).

PRECISION GOLD MULTIMETERS



A new range of very high quality multimeters offering truly amazing quality at the price.

- Pocket Multimeter, 16 ranges, 2000Ω/V DC/AC £6.95§ (YJ06G)
- M-102BZ with Continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95§ (YJ07H)
- M-2020S with Transistor, Diode & LED tester and 10A DC range, 27 ranges 20,000Ω/V DC £19.95§ (YJ08J)
- M-5050E Electronic Multimeter with very high impedance, FET input, 53 ranges including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95§ (YJ09K)
- M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated PCB for long-term reliability and consistent high accuracy (0.25% +1 digit DCV) £42.50§ (YJ10L)

N.B. All our prices include VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail order (except catalogue).

MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552914

- SHOPS
- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
 - LONDON 159-161 King Street, Hammersmith, W6. Tel: 01-748 0926.
 - MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
 - SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 25831.
 - SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Tel: 0702-554000
- Shops closed all day Monday.

Our huge range of top quality electronic components at very competitive prices are all detailed in our catalogue, and with well over 600 new lines in our 1985 edition and many design improvements, it's well worth getting a copy. Here are just a few examples from the catalogue. (The items below are NOT kits).

- ★ Most phono and jack plugs now with integral strain relief sleeve - gold-plated types also available from 14p (gold from 70p)
- ★ Stereo Disco Mixer with cross-fade, talk-over, cue monitoring, aux input, slide controls. Only £58.95 (AF99H)



- ★ 10-Channel Stereo Graphic Equalisers - 3 models - basic; with peak level meter; and with spectrum analyser - from £77.95



- ★ Digital Delay Line permits Slap-back, Doubling, Flanging, Chorus and Echo. 11 controls. Only £195.00 (AF98G)
- ★ Video Enhancer improves picture quality when recording from one VTR to another, and with TV's with monitor input. Only 28.95 (XG59P)
- ★ Detailed descriptions of the exciting new 74HC range of IC's which combine the advantages of CMOS and TTL. From 46p
- ★ Keyboards: sloping keys, two-tone grey, mounted in steel frame, very smart cases (extra) available. 61 keys, only £33.95 (YJ12N) 79 keys, only £37.95 (YJ13P)
- ★ 1% Resistors now 50ppm/°C, 0.4W, only 2p each!
- ★ Auto transformers 120/240V 50VA, £10.75§ (YJ56L). 100VA £14.95§ (YJ57M). 150VA £16.95§ (YJ58N). 250VA £21.95§ (YJ59P).
- ★ Digital Clinical Thermometer. Only £13.95 (FK51F)



Check our 1985 Catalogue for all our other fascinating new lines.



☎ Phone before 2pm for same day despatch.

1985 CATALOGUE

Pick up a copy now at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).

Post this coupon now for your copy of the 1985 catalogue. Price £1.35 + 40p post and packing. If you live outside the U.K. send £2.40 or 11 International Reply Coupons. I enclose £1.75.

Name

Address

EE/4/85

§ Indicates that a lower price is available in our shops.

All offers subject to availability.

Prices firm until May 11th 1985.