
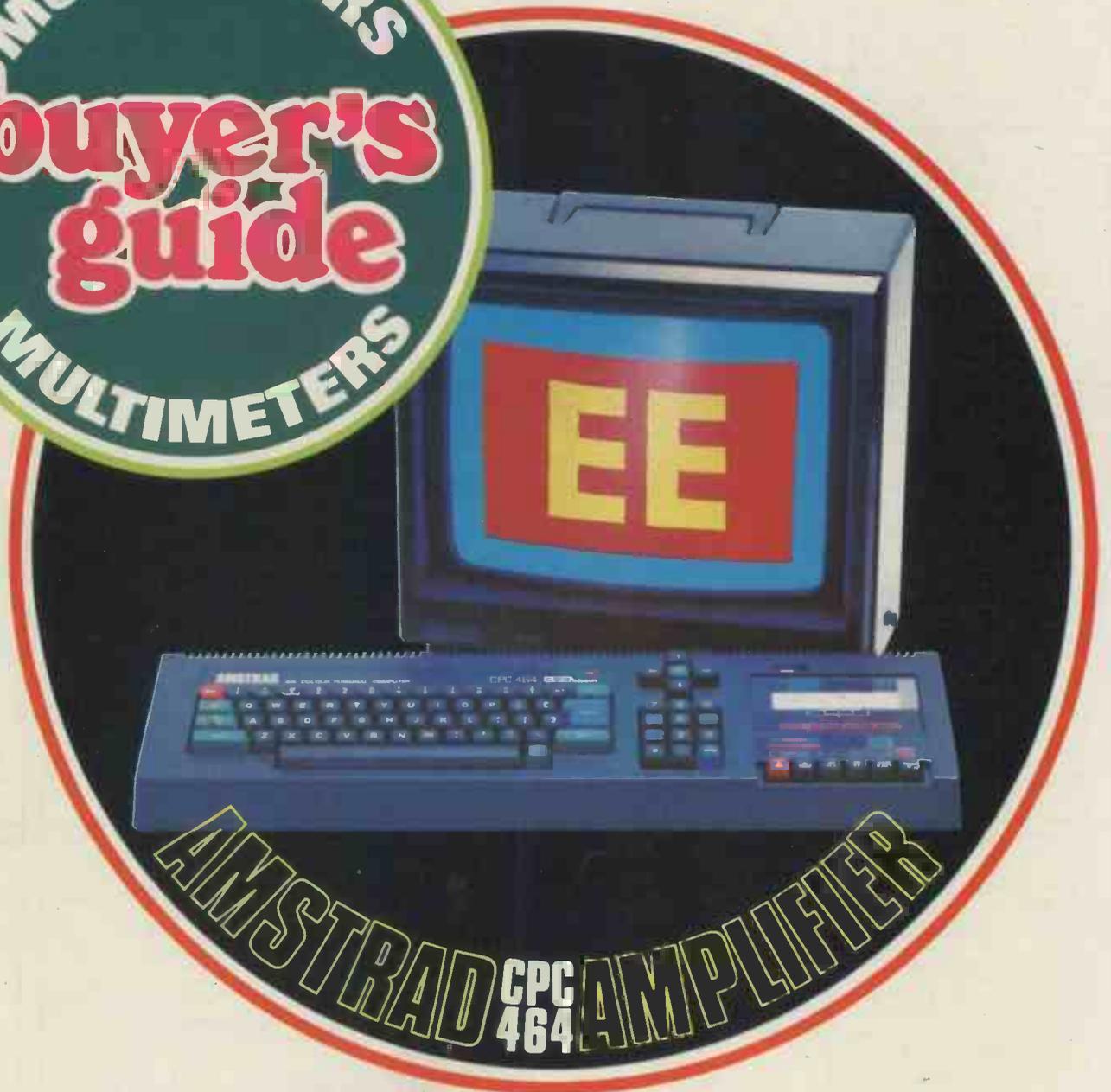


# EVERYDAY **ELECTRONICS** and computer **PROJECTS**

MAY 1985

£1.00

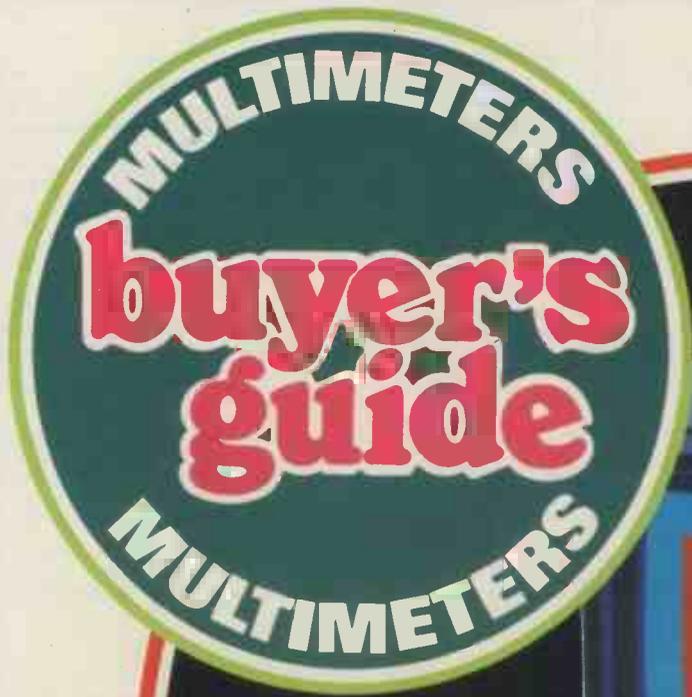

## **AUTO PHASE \* VOLTAGE PROBE**

Australia \$1.75 New Zealand \$1.95 Malaysia \$4.95

# BI-PAK BARGAINS

## HIGH QUALITY MODULES FOR STEREO, MONO & OTHER AUDIO EQUIPMENT

### Audio Amplifiers

D/No.	PDWER D/P	R.M.S. VOLTAGE	MAX SUP. VOLTAGE	PRICE
AL 30A	10 Watts	30V	30V	£4.95
AL 60	25 Watts	30-50V	30V	£5.92
AL 80	35 Watts	40-60V	30V	£8.75
AL 120	50 Watts	50-70V	30V	£15.22
AL 250	125 Watts	50-80V	30V	£20.60

### Stabilised Power Supplies —

Output current 2.5 Amps

D/No.	AC Input	Price
SPM 120/45	40-48V	£8.05
SPM 120/55	50-55V	£8.05
SPM 120/65	60-65V	£8.05

### Mono Pre-Amplifiers — Operating Vtg. 40-65V

O/No.	MPA30. Sup Vtg. 20-30V	Price
MM 100	Suitable for Disco Mixer	£14.75
MM 100G	Suitable for Guitar Pre-Amp Mixer	£14.75

### Magnetic Cartridge Pre-Amplifier

O/No. MPA30. Sup Vtg. 20-30V. Price £4.29


The PA207 is a high quality pre-amplifier unit which features full range tone controls and an input switch. It is designed to drive power amplifiers ranging from the AL50 to the AL250. Order No. PA207. £18.50

Full Specifications and Data available on request. Please send self-addressed envelope.
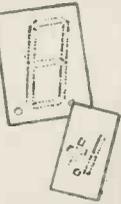
## HYBRID LED COLOUR DISPLAYS

Red, Green, Yellow — 3/5/6 inch Mixed types and colours NUMERIC & OVER-FLOW Common Anode/Cathode. GaAsP/GaP. Brand New. Full Data incl.

10 pieces (our mix) . . . £4.00  
Normal Retail Value Over £10.00  
Order No. VP58



## VALUE PACKS

Pak No	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/4-1/2 Watt Pre-Formed	£1.00
VP3	200	1/4 Watt Min Carbon Resistors Mixed	£1.00
VP4	150	1/2 Watt Resistors 100 ohm-1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature — Mixed	£1.00
VP7	100	Mixed Ceramic Disc. 10p — 56p	£1.00
VP8	100	Mixed Ceramic Disc. 68p — 015p	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	50	Electrolytics — All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5.6p — 150p	£1.00
VP14	50	Silver Mica Caps Ass. 180p — 4700p	£1.00
VP15	25	0.1uF 250V Min. layer metallised Polyester Capacitors	£1.00
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm — 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 5 Amp 240v	£1.00
VP21	15	2in. high bright RED LEDs in plastic encapsulation—Large area light source	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log. 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log. 5 x Lin	£1.00
VP26	15	Small 125° Red LED's	£1.00
VP27	15	Large 2° Red LED's	£1.00
VP28	10	Rectangular 2° RED LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW — 2W Mixed Vtcs. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vtcs. Coded	£1.00
VP31	10	5 Amp SCR's TO 66 50-400V Coded	£1.00
VP32	10	3 Amp SCR's TO 66 10-40V Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 00-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like 0A200/BAX13/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1/4" Std	£1.00
VP42	10	Black Heatsinks To Fit T0-30, T0-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x 10 x 2 x TO 66 Size	£1.00
VP45	50	BC107/8 Type NPN Transistors Good Gen. Purpose Uncoded	£1.00
VP46	50	BC177/8 Type PNP Transistors Good Gen. Purpose Uncoded	£1.00
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.00
VP48	50	Precision Resistors 2-1% tol.	£1.00
VP49	40	IN4002 Sil. Rects. 1A 100v preformed pitch	£1.00
VP142	4	40A Power Rectifiers Silicon TO48 300P/IV	£1.00
VP143	5	BY187 12KV Sil. Diodes in carriers 2.5mA	£1.00
VP144	4	100K 1in. Multi-turn pots ideal vari cap tuning	£1.00
VP145	10	Assorted pots. inc. Dual & Switched types	£1.00
VP146	25	Solid Tantalum Caps. Mixed Values	£1.00

## TRANSISTOR PACKS

VP150	20	BC183B Sil. Trans. NPN 30v 200mA Hfe240+ T092	£1.00
VP151	25	BC171B Sil. Trans. NPN 45v 100mA Hfe240+ T092	£1.00
VP152	15	TIS91 Sil. Trans. NPN 40v 400mA Hfe100+ T092	£1.00
VP153	15	TIS91 Sil. Trans. PNP 40v 400mA Hfe100+ T092	£1.00
VP154	15	MPSA56 Sil. Trans. PNP 80v 800mA Hfe50+ T092	£1.00
VP155	20	BF595 Sil. Trans. NPN eqvt. BF184 H.F. T092	£1.00
VP156	20	BF495 Sil. Trans. NPN eqvt. BF173 H.F. T092	£1.00
VP157	15	ZTX500 Series Sil. Trans. PNP Plastic	£1.00
VP158	15	ZTX107 Sil. Trans. NPN eqvt. BC107 Plastic	£1.00
VP159	15	ZTX108 Sil. Trans. NPN eqvt. BC108 Plastic	£1.00
VP160	20	E5024 Sil. Trans. PNP eqvt. BC214L T092	£1.00
VP161	25	BC183L Sil. Trans. NPN 30v 200mA T092	£1.00
VP162	5	SJE5451 Sil. Power Trans. NPN 80v 4A Hfe30+	£1.00
VP163	2	PNP/PNP pairs Sil. Power Trans. like SJE5451	£1.00
VP164	4	2N6289 Sil. Power Trans. NPN 40v 40w 7A Hfe30+	£1.00
VP165	6	BFT33 NPN Sil. Trans. 80v 5A Hfe50-200 T039	£1.00
VP166	5	BFT34 NPN Sil. Trans. 100v 5A Hfe50-200 T039	£1.00
VP167	1	BUY69C NPN TO3 VCB 500 10A 100w Hfe15+	£1.00
VP168	10	BC478 eqvt. BC771 PNP Sil. Trans. T018	£1.00
VP169	10	BXS21 eqvt. BC394 NPN Sil. Trans. 80v 50mA T018	£1.00
VP170	10	Assorted Power Trans. NPN/PNP Coded & Data	£1.00
VP171	10	BF355 NPN TO-39 Sil. Trans. eqvt. BF258 225v 100mA	£1.00
VP172	10	SM1502 PNP TO39 Sil. Trans. 100v 100mA Hfe100+	£1.00

## TRANSISTORS

100 Silicon NPN Transistors. All Perfect Coded Mixed. Types With Data And Eqvt. Sheet No Rejects. Fantastic Value. O/No. VP38	£3.00	100 Silicon PNP Transistors. All Perfect Coded. Mixed. Types With Data And Eqvt. Sheet. No Rejects. Real Value. O/No. VP39	£3.00
---	-------	--	-------

The best known Power Transmitter in the world 2N3055 NPN 115W. Our Bi-Pak Special Offer Price. 10 off 100 off

£3.50    £16.00    £30.00

BD312 COMPLIMENTARY PNP POWER TRANSISTORS TO 2N3055. Equivalent MJ2955 BD312 TO3. Special Price £0.70 each. 10 off £6.50

## SEMICONDUCTORS FROM AROUND THE WORLD

100 A collection of Transistors, Diodes, Rectifiers & Bridges, SCRs, Triacs, I.C.s & Opto's all of which are current every day useable devices. Guaranteed Value Over £10 Normal Retail Price. Data etc. in every pack. Order No. VP56

Our Price £4.00

## TRANSISTOR CLEARANCE

100 All Sorts Transistors. A mixed bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack includes instructions for making Simple Transistor Tester, Super Value.

Order No. VP60. £1.00

150 De-soldered Silicon Transistors from boards 10mm leads all good. O/No. VP173 £1.00

## BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, sizes & colours, together with 7 Segment Displays both anode & cathode plus photo transistors emitters and detectors. Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over £12 Normal Price

Order No. VP57  
Our Super Value  
Price Just  
£5.00



## OPTICALLY COUPLED MODULES

1 pair SD1/131 Consisting 1 x LS600 Silicon Light Sensor & 1x Matched Gallium Arsenide Light Source — Type TIL23, on ready mounted fibre glass board. Including Data. Ideal Alarm projects etc. O/No. VP147.

BI-PAK Price ONLY £0.60 pr.

## LED DISPLAYS

VP130	6	RED 7 Seg. CC 14mm x 7.5mm RDP FND353	£2.00
VP131	4	GREEN 7 Seg. CA 6" LDP XAN6520	£2.00
VP132	5	RED 7 Seg. CC 6" LDP XAN6940	£2.00
VP133	6	RED Over-flow 6" 3 x CA 3 x CC 6630/50	£2.00
VP134	5	GREEN Over-flow 6" CA XAN6530	£2.00
VP135	5	RED 7 Seg. CA 3" XAN3061	£2.00
VP136	3	DUAL RED 7 Seg. 5" CA DL527 DPR	£2.00
VP137	3	DUAL RED 7 Seg. 51" CA DL727 DPR	£2.00
VP138	20	Assorted LED Displays — Our mix with Data	£5.00

RDP = Right Hand Decimal Point    CC = Common Cathode  
LDP = Left Hand Decimal Point    CA = Common Anode

## DC-DC POWER SUPPLY

DC to DC adaptor. Plugs into car cigar lighter aperture. Output 3, 4.5, 6, 7.5, 9, 12V @ 800mA. Has universal output spider plug, also 9V battery snap and polarity reversing facility. O/No. VP119/138 £3.50

## HIGH PASS FILTER/SUPPRESSOR

CB/TV. High pass filter. Reduces unwanted signals picked up by antenna. Dims: 45 x 25 x 17mm. O/No. VP 115 45p

Designed to reduce harmonics on the VHS and TV band. Cut-off frequency: 30MHz. V.S.W.R.: Less than 1.2 to 1. Insertion loss: -0.2dB @ 27MHz. Impedance: 50 ohms. Dims: 80 x 55 x 40mm. O/No. VP 116 £2.75

## LOW PASS FILTER



## IC BARGAINS

40 Assorted TTL CMOS INTEGRATED CIRCUITS 74 Series & CD4000 Series — All new Gates, Flip-Flops — MSI etc. GREAT VALUE Data Book & Sheets included. 40 Pieces (Our Mix) £4.00 O/No. VP40


## SILICON BRIDGE RECTIFIERS

Comprising 4 x 1 1/2 amp rectifiers mounted on PCB. VRM — 150 vIts IFM — 1.5 Amps Size: 1 inch square 10 off £1.00 50 off £4.50 100 off £7.50

Order No. As:4R1 BRect
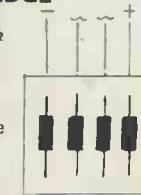
## REGULATED VARIABLE POWER SUPPLY

Stabilised Variable Power Supply. Available from 2-30 volts and 0-2 amps kit includes — 1 — VPS30 Module. 1 — 25 volt 2 amp transformer. 1 — 0-50v 2" Panel Meter. 1 — 0-2 amp 2" Panel Meter. 1 — 470 ohm wirewound potentiometer. 1 — 4K7 ohm wirewound potentiometer. Wiring Diagram included. Order No. VPS30 KIT £20



## SIREN ALARM MODULE

American Police type siren powered from any 12 volt supply into 4 or 8 ohm speaker. Ideal for car burglar alarm, freezer breakdown and other security purposes. 5 watt, 12v max. £3.85 Order No. BP124

## POWER SUPPLY OUR PRICE £3.75

Power supply fits directly into 13 amp socket. Fused for safety. Polarity reversing socket. Voltage switch. Lead with multi plug input — 240v AC 50Hz Output — 3 4.5 6 7.5 9 & 12v DC. Rating 300ma MW88/137

## (LEARN A LINGO) PILLOW SPEAKER

Slim under pillow unit. 800hms 2" speaker. 1.5m lead with 3.5mm mono jack plug. Black. Dims: 65(dia) x 17mm. O/No. VP 88 £1.25



# BI-PAK

Send your orders to Dept EE5 BI-PAK PO BOX 6 WARE, HERTS SHOP AT 3 BALDOCK ST. WARE, HERTS TERMS CASH WITH ORDER, SAME DAY DISPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182, GIRO 388 7006 ADD 15% VAT AND £1.00 PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add £1.00 per Total order.



# EVERYDAY ELECTRONICS and computer PROJECTS

VOL 14 NO5

MAY'85

ISSN 0262-3617

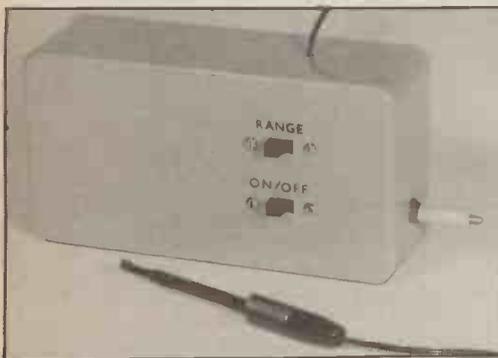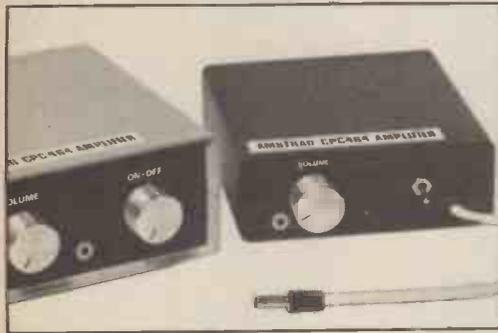PROJECTS ... THEORY ... NEWS ...  
COMMENT ... POPULAR FEATURES ...



© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

## PROJECTS

- AMSTRAD CPC464 AMPLIFIER** by P. Dooley 248  
Turn a hiss into a roar
- VOLTAGE PROBE** by R. A. Penfold 252  
Hand-held indicator for voltage readings up to 120V
- AUTO PHASE** by R. A. Penfold 260  
Amplitude controlled phaser for performers
- CARAVAN INDICATOR CONTROL**  
by T. R. de Vaux-Balbirnie 288  
Operates the caravan lights without overloading the car system

## SERIES

- ON SPEC** by Mike Tooley BA 258  
New regular feature devoted to the Spectrum—Sensors and a signal generator program
- FAULT FINDING** by E. A. Rule 276  
Part Seven: Service aids and aerosols
- DIGITAL ELECTRONICS** by D. W. Crabtree 282  
Part Eight: Putting computers to practical use
- FUNTRONICS** by Thakery 286  
A new outlook to electronics—Radio Control Pt 2

## FEATURES

- EDITORIAL** 247
- SHOPTALK** by Mike Abbott 256  
Product news and component buying
- EVERYDAY NEWS** 274  
What's happening in the world of electronics
- FOR YOUR ENTERTAINMENT** by Barry Fox 278  
Lasers Light The Way; Optical Grating; Electron Analysis
- DOWN TO EARTH** by George Hylton 280  
Operational amplifier current sourcing and sinking
- COUNTER INTELLIGENCE** by Paul Young 281  
A retailer comments
- PLEASE TAKE NOTE** 284  
Sound Operated Flash; Headlight Activated Switch; Motorcycle CodeLock; Digital Electronics Pt 5
- NEW PRODUCTS** 291
- PRINTED CIRCUIT BOARD SERVICE** 292

## BUYER'S GUIDE

- MULTIMETERS BUYER'S GUIDE** 264  
An introduction to meter specifications plus a useful buyer's guide

*Our June 1985 issue will be published on Friday, May 17.  
See page 279 for details.*

## NEW THIS MONTH

### "SENSING & CONTROL PROJECTS FOR THE BBC MICRO"

Have you ever wondered what all those plugs and sockets on the back of the BBC micro are for? This book assumes no previous electronic knowledge and no soldering is required, but guides the reader (pupil or teacher) from basic connections of the user sockets, to quite complex projects. The author, an experienced teacher in this field, has provided lots of practical experiments, with ideas on how to follow up the basic principles. A complete kit of parts for all the experiments is also available. Book, 245x185mm 120pp £5.95. Kit £29.95.

## GREENWELD

— The Pack People! —

**K524 OPTO PACK** — a variety of single point and seven segment LEDs (incl. dual types) of various colours and sizes, opto isolators, numicators, multi digit gas discharge displays, photo transistors, infra red emitters and receivers. 25 assorted £3.95; 100 £14.95; 250 £36.

**K525 PRESET PACK** — Big, Big variety of types and sizes — submin, min and std. MP, slider, multiurn and cermet are all included. Wide range of values from 20R to 1M. 100 assorted £6.75; 250 £12.95; 1000 £48.

**K526 HEATSINK PACK** — Lots of different sizes and shapes of heatsink for most diode and transistor case styles. A pack of 25 assorted including several large finned types — total weight over 1kg £5.50; 100 £19.50.

**K528 ELECTROLYTIC PACK** — All ready capped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47µF to 1000µF. 6v to 100v £3.95; 250 £8.95; 1000 £32.

**K531 PRECISION RESISTOR PACK** — High quality, close tolerance R's with an extremely varied selection of values mostly 1/4 and 1/2w tolerances from 0.1% to 2% — ideal for meters, test gear etc. 250 £3; 1000 £10.

**K532 RELAYS** — Wide selection of styles, voltages and contacts. 4v-240v, AC/DC, SP to 4PCO. 20 for £6; 100 £25.

**K517 TRANSISTOR PACK** — 50 assorted full spec marked plastic devices PNP NPN BF AF. Type numbers include BC114 117 172 182 183 198 239 251 214 255 320 BF 198 255 394 2N3904 etc. etc. Retail cost £7+; Special low price 275p.

**K523 RESISTOR PACK** — 1000 — yes 1000 1/4 and 1/2 watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megohms. Only 250p; 5000 £10; 20,000 £36.

**K520 SWITCH PACK** — 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p.

**K522 COPPER CLAD BOARD** — All pieces too small for our etching kits. Mostly double-sized fibreglass 250g (approx 110 sq. ins.). For 100p.

**K530 100 ASSORTED POLYESTER CAPS** — All new modern components, radial and axial leads. All values from 0.01 to 1uf at voltages from 63 to 1000V! Super value at £3.95.

**K518 200 DISC CERAMIC CAPS** — Big variety of values and voltages from a few pF to 2.2µF; 3v to 3kv £1.00.

**K203 100 WIREWOUND RESISTORS** — From 1w to 12w, with a good range of values £2.00.

**K505 20 ASSORTED POTENTIOMETERS** — All types including single, ganged, rotary and slider £1.70.

**W4700 PUSH BUTTON BANKS** — An assortment of latching and independent switches on banks from 2 to 7 way, DPCC to 6PCO. A total of at least 40 switches for £2.95; 100 £6.50; 250 £14.00.

Goods normally despatched by return of post

Our shop has enormous stock of components and is open 9-5.30 Mon-Sat. Come and see us!

# GREENWELD

All prices include VAT; just add 60p P&P. Min Access order £5.00 No min. CWO value. Official orders from schools etc. welcome — min invoice charge £10.



443D Millbrook Road  
Southampton SO1 0HX  
Tel (0703) 772501/783740

## 1984/85 CATALOGUE

84 page A4 size — Bigger, Brighter, Better — more components than ever before! With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1,001! Winter Supplement now out — Send large SAE for your free copy.

### "TORUS"

Computer-controlled Robot built around the gearbox described below. Complete kit of parts inc PCB, program listings for BBC (other micros soon). £44.85. 20w ribbon cable (min 3m recommended — 5m better) £1.30/m. SAE for illustrated leaflet.




### MOTORIZED GEARBOX

The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors.

Two new types of wheels can be supplied (the aluminium discs and smaller plastic wheels are now sold out). Type A has 7 spokes with a round black tyre and is 100mm dia. Type B is a solid heavy duty wheel 107mm dia with a flat rigid tyre 17mm wide.

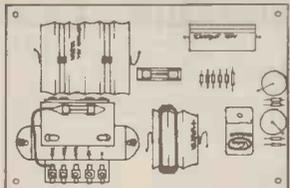Prices: Gearbox with data sheets: £5.95 ea  
Wheel type A: £0.70 ea  
Wheel type B: £0.90 ea



### NI-CAD CHARGER PANEL

177x114mm PCB with one massive Varta Deac 57x50mm 0 rated 7.2v 1000mAh and another smaller Deac 32x35mm 0 rated 3.6v 600mA. The price of these Ni-Cad stacks new is over £20. Also on the panel is a mains input charger transformer with two separate secondaries wired via bridge rectifiers, smoothing capacitors and a relay to the output tags. The panel weighs 1kgm. All this for just £6.00.

### PCB MOUNTING NI-CADS

Much sought after 4.8V 150mA batts with PCB mntg tags on 25mm pitch. Batt size 25x16 0. Ideal for paralleling. 99p ea; 10+ 85p; 25+ 70p; 100+ 60p.

NI-CADS: AA 99p; C 199p; D 220p; PP3 395p.

### 1W AMPLIFIER

Z914 — Audio amp panel 95x65mm with TBA820 chip. Gives 1W output with 9V supply. Switch and vol. control. Just connect batt and speaker. Full details supplied. Only £1.50; 10 for £12; 25 for £25; 100 £75.

### AM TUNER PANEL

Z916 — For use with mono amp above. Neat panel 60x45mm. Only £1.50; 10 for £12.00.

### FIBRE OPTICS

Scoop purchase of single and twin cable. For use with visible light or infra-red. Core 1mm dia, overall 2.25mm dia. Single 50p/m; 20m coil £6.30. Twin 90p/m; 20m coil £11.00.

AA117	9	80V42	20	BF259	18	BU100A	110	TP142A	22	2N 706A	22	BY133	8	Z8B507	58
AA119	9	80V56	16	BF263	18	BU101	110	TP142C	25	2N 706C	22	BY134	40	Z8B514	40
AA120	9	80V70	16	BF265	25	BU105	30	TP147	40	2N 914	28	BY176	85	Z8B605	85
AC107	28	80V71	16	BF270	18	BU108	100	TP148	40	2N 918	28	BY179	85	Z8B609	85
AC108	17	80V76	16	BF275	18	BU110	110	TP150	60	2N 919	60	BY180	25	Z8B629	200
AC127	15	80V115	26	BF311	21	BU111	140	TP151	120	2N 1131	28	BY184	32	Z8B686	76
AC128	15	80V124P	56	BF324	20	BU124	50	TP152	120	2N 1132	28	BY187	32	Z8C1161	110
AC128K	23	80V124	56	BF325	20	BU125	50	TP153	120	2N 1133	28	BY188	32	Z8C1172	158
AC141K	30	80V128	35	BF337	20	BU204	75	TP154	140	2N 1171	24	BY206	11	Z8C1306	30
AC142K	30	80V131	25	BF338	20	BU205	70	TP105	65	2N 1172	50	BY207	11	Z8C1307	100
AC154	23	80V132	25	BF352	28	BU206	75	TP106	65	2N 1180	300	BY208	11	Z8C1309	100
AC176	18	80V135	20	BF362	30	BU208A	90	TP107	65	2N 2218A	24	BY210	22	Z8C1369	130
AC176K	17	80V136	20	BF367	13	BU208B	100	TP110	47	2N 2219A	24	BY223	72	Z8C1372	75
AC181	15	80V137	17	BF371	15	BU209	75	TP111	47	2N 2219	24	BY226	20	Z8C1373	24
AC187K	20	80V138	20	BF414	18	BU209	75	TP112	40	2N 2222	23	BY228	18	Z8C1378	120
AC188	17	80V139	20	BF420	16	BU406	85	TP115	45	2N 2846	40	BY229	20	Z8C1386	20
AC188K	23	80V139	20	BF421	15	BU407	75	TP117	50	2N 2846	40	BY236	20	Z8C1392	20
AC1918	80	80V140	90	BF422	21	BU407	75	TP117	50	2N 2846	40	BY236	20	Z8C1392	20
AD147	49	80V150	30	BF442	16	BU408	75	TP120	43	2N 2846	40	BY236	20	Z8C1392	20
AD149	46	80V158	38	BF451	17	BU409	95	TP122	47	2N 2806	18	BY476	30	Z8C1400	14
AD181	22	80V156	30	BF455	14	BU409	95	TP125	47	2N 2807	18	BY478	15	Z8C1401	8
AD182	22	80V157	30	BF458	17	BU409	95	TP125	56	2N 2807	18	BY478	15	Z8C1401	8
AF124	25	80V179	32	BF459	19	BU500	110	TP127	56	2N 3019	28	BY555000	20	Z8C1402	14
AF125	25	80V181	45	BF461	60	BU506	100	TP141	30	2N 3053	32	BY555000	20	Z8C1402	14
AF126	25	80V182	45	BF462	60	BU506	100	TP142	30	2N 3054	32	BY555000	20	Z8C1402	14
AF126	25	80V183	60	BF469	30	BU806	120	TP145	65	2N 3055	35	BYX70500	32	Z8C1402	14
AF126	22	80V201	33	BF470	28	BU807	95	TP146	30	2N 3056	35	BYX70500	32	Z8C1402	14
AF126	22	80V202	38	BF471	28	CU903	23	TP147	100	2N 3440	58	BYX71600	80	Z8C1402	14
AL112	70	80V203	42	BF479	30	MAJ2500	100	TP255	42	2N 3442	85	0A74	6	Z8C1402	14
AL113	80	80V204	42	BF483	18	MAJ2501	110	TP364	45	2N 3702	9	0A74	6	Z8C1402	14
AS217	100	80V225	31	BF494	16	MAJ255	35	TP355	16	2N 3703	9	0A74	6	Z8C1402	14
AS217	100	80V222	31	BF495	16	MAJ3000	115	TS43	45	2N 3704	9	0A200	7	Z8C1402	14
AU110	110	80V234	32	BF596	16	MAJ3001	115	TS44	40	2N 3705	9	0A200	7	Z8C1402	14
AY102	180	80V507	30	BF597	18	MAJ3002	115	TS45	40	2N 3706	9	0A200	7	Z8C1402	14
AY106	180	80V236	30	BF615	20	MAJ3003	115	TS46	40	2N 3707	9	0A200	7	Z8C1402	14
BA145	10	80V237	21	BF758	41	MAJ340	25	TS49	45	2N 3708	9	0A200	7	Z8C1402	14
BA145	10	80V238	20	BF760	41	MAJ350	60	TS51	18	2N 3711	10	0A200	7	Z8C1402	14
BA154	6	80V244	50	BF870	22	MAJ350	60	TS52	30	2N 3712	10	0A200	7	Z8C1402	14
BA154	12	80V248	50	BF872	23	MAJ2555K	30	VK1010	88	2N 3773	100	0A200	7	Z8C1402	14
BB100	13	80V433	28	BF980	8	OC26	100	VA1084A	100	2N 3819	25	0A200	7	Z8C1402	14
BB103	16	80V434	30	BF983	40	OC29	80	VN 464F	88	2N 3856	66	0A200	7	Z8C1402	14
BB106	16	80V435	31	BF984	38	OC35	100	VN 56AF	100	2N 3856	11	0A200	7	Z8C1402	14
BB106	24	80V437	28	BF988	40	OC36	120	VN 58AF	115	2N 3856	11	0A200	7	Z8C1402	14
BB107	7	80V438	36	BF940	25	OC45	50	VN 89AF	110	2N 3856	11	0A200	7	Z8C1402	14
BB108	7	80V439	40	BF951	21	OC71	30	ZX107	11	2N 3856	11	0A200	7	Z8C1402	14
BB108	7	80V440	40	BF952	20	OC72	30	ZX108	11	2N 3856	11	0A200	7	Z8C1402	14
BB109	10	80V441	40	BF979	25	OC200	180	ZX109	12	2N 4025	25	0A200	7	Z8C1402	14
BB118	11	80V442	40	BF980	52	R0088	52	ZX121	27	2N 4037	25	0A200	7	Z8C1402	14
BB118	11	80V443	50	BF981	50	R0180	100	ZX122	13	2N 4258	13	0A200	7	Z8C1402	14
BB141	19	80V534	30	BF929	20	TAG4443	76	ZX301	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V535	30	BF934	20	TAG4444	76	ZX302	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V536	30	BF935	20	TAG4445	76	ZX303	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V537	30	BF936	20	TAG4446	76	ZX304	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V538	30	BF937	20	TAG4447	76	ZX305	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V539	30	BF938	20	TAG4448	76	ZX306	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V540	30	BF939	20	TAG4449	76	ZX307	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V541	30	BF940	20	TAG4450	76	ZX308	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V542	30	BF941	20	TAG4451	76	ZX309	16	2N 4444	76	0A200	7	Z8C1402	14
BB142	19	80V543	30	BF942	20	TAG4452	76	ZX310	16	2N 4444	76	0A200</			

# TOP SERVICE WITH LESS TO PAY THAT'S THE TK WAY.

TOP QUALITY COMPONENTS,  
LOW PRICES, QUANTITY  
DISCOUNTS, FAST SERVICE  
FREE P&P OVER £20

LINEAR ICs	
555	21 ML927 1.80
566	40 ML928 1.80
741	22 ML929 1.80
AD590	3.30 MM74C911 6.50
CA3080	65 MM74C926 4.50
CA3130	85 NE567 1.25
CA3410	40 S566B 2.20
ICL7107	9.00 S5760 2.20
ICL7126	8.00 SAB0529 3.50
ICM7555	95 SAB0600 2.50
ICM8038	3.10 SL440 1.95
LF351	40 SL441 1.35
LF353	70 SL486 1.85
LF356	80 SL490 2.05
LM324	40 TB8000 70
LM3347	85 TB810AS 90
LM3352	1.20 TDA1024 1.20
LM339	40 TDA4290 1.98
LM348	55 TL061 40
LM358	48 TL062 50
LM390	1.20 TL064 1.30
LM381	1.40 TL071 45
LM382	1.10 TL072 70
LM386	88 TL074 1.30
LM1035	3.95 TL081 35
LM1458	34 TL082 48
LM2917	1.90 TL084 1.00
LM3900	68 TL170 50
LM3909	80 TL507C 1.20
LM3911	1.75 TMS1121 8.50
LM3914	2.40 TMS1601 9.50
LM3915	2.40 ULA2240 1.45
LM13600	1.10 ULN2003 75
LS7210	4.75 ULN2004 75
LS7220	2.75 ZN414 30
LS7225	2.60 ZN425 3.40
MF10C	2.97 ZN427 5.70
ML922	3.80 ZN428 4.50
ML924	2.50 ZN1034E 1.80

CMOS	
4000	16 4040 49
4001	18 4043 42
4002	18 4046 60
4007	16 4047 55
4011	18 4049 32
4012	18 4050 35
4013	25 4060 35
4015	42 4069 18
4016	30 4070 18
4017	39 4071 18
4019	28 4077 20
4023	16 4081 16
4024	35 4083 35
4025	16 4511 48
4026	70 4514 1.00

COMPUTER ICs	
6802	2.45 6852 2.40
6809	4.95 280A CPU 1.55
6821	1.20 280A CTC 1.55
6850	1.50 280A PIO 1.55

MEMORIES	
2716	3.10 2764 4.75
2732	3.20 2810 1.40

CRYSTALS	
4.0M	1.20
32kHz	80 1.1943M 1.58
1.8432M	2.30 4.1952M 1.80
2.4576M	1.80 6.0M 1.30
3.2768M	1.50 6.144M 1.40

REGULATORS	
78L05/12/15	30 7805/12/15 50
79L05/12/15	55 7905 55
Variable: LM723	40
LM317T	85 LM338(ISA) 5.00

OPTO	
3mm red	9 5mm red 9
3mm green	12 5mm green 12
3mm yellow	12 5mm yellow 12
Rectangular, square, arrow or triangular (flat face)	
Red 15	Green 18 Yellow 18
Bicolour	65 Flashing Red 50
Tricolour	Red/ 18
Round	32 Continuous 55
Rectangular 45	
IL74/11L11	55 MOC3020 1.50
IL74/1	1.70 MOC3040 1.50
ORP12	75 MEL11 35
Seven Segment LED Displays	
DL704 3 cc	75 4 Dig 1.8" cc
FNDS005 ca	85 DIRECT DRIVE
FNDS075 ca	85 Display 7.00

BOXES	
B1	75x56x35mm 85
B2	95x71x35 50
B3	115x95x37 1.10
B4	140x90x55 1.50
B5	207x122x77 2.75
B6	213x142x57 2.70

Other boxes including wide range of diecast, aluminium and Vero-boxes in our catalogue.

SPEAKERS	
1.5in. 8ohm	85 2in. 8ohm 70
2.25in. 8ohm	70 2.5in. 64ohm 80
5.5in. 8ohm	8W Horn 6.75
Crystal Earpiece	50
Magnetic Earpiece	25
Ultrasonic trans (pair)	3.50
Crystal mic insert	50
Telephone pick up coil	65

PRINTED CIRCUITS	
Fibreglass copper-clad laminate	
Plain Sensitised	
160x100mm	80 1.80
220x100mm	1.55 2.30
Etch resist transfers.	
Pads, straight/curved tracks.	
DI pads (sata type)	50
Ferric Chloride (250ml)	1.50
Etch Resist Pen	75
Titan 12v Drill	10.25
Reifant 3v Drill	6.50
Twist Drills	25

400V TRIACS	
4A	49 8A 58
6A with diac	65 12A 58
8A isolated	16A 95
tab	65 25A 2.10
8A sensitive	66 Diac 18

DIODES	
1N5401	11
1N5404	13
1N4001	4 1N4148 3
1N4004	6 1.3V Zeners 15
1N4007	7 400mW Zeners 8

BUZZERS	
6V Metal 90	12V Metal 90
61/2V Plastic Electronic	85
Piezo low current 4mA at 12V	95
Piezo 240V ac	1.20
7 tune alarm unit	2.70

RIBBON CABLE	
GH1 per metre	Colour Coded
20 way	95 per metre
25 way	150 10 way 70
40 way	2.20 20 way 1.40
Screened cables and connecting wire also stocked.	

D CONNECTORS	
5w	15w 25w
Plug	55 65 90
Socket	80 1.10 1.30
Cover	95 95 95
Right Angle Plug	15W 1.80
Right Angle Socket	15W 2.10

PANTEC KITS	
PN2	FM Micro Transmitter £7.50
PN3	Biased Power Supply £13.70
PN5	2 x 10W Stereo Amplifier £14.50
PN6	2 x 40W Stereo Amplifier £24.95
PN7	Pushbutton Stereo Preamp £12.80
PN8	Tone & Volume Control £13.60
PN11	3w FM Transmitter £11.95
PN13	Single Channel FM Transmitter £9.80
PN14	Receiver for above £15.50

DVM/ULTRA SENSITIVE THERMOMETER KIT	
Based on the ICL 7126 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required - details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading 0.1°C. The kit has a sensitivity of 200mV for a full scale reading automatic polarity and overload indication. Typical battery life of 2 years (PP3) £15.50	

SECURITY PRODUCTS	
Detects intruder's body heat. Range 10 metres. 12V DC, n/o & n/c contact. Size: 4 x 2 x 2 ins. (950 135) £45.00	
Alarm Control Unit. 4 input circuits, 2-instant and 2-delayed. Adjustable entry, exit and alarm times. Built and tested. Full instructions supplied. Size: 180 x 130 x 30mm. Supply: 12V DC. (950 160) £25.00	
Smoke Detector. Easily installed. No adjustment. 1 year operation from PP3 alkaline battery. Consumption 25uA. Size: 175mm dia. x 45mm. White plastic case. (950 165) £8.50	
8W Horn Speaker. 5.5 ins. 8 ohm. Ideal for sirens, etc. 2.5m lead and 3.5mm jack plug. (403 148) £6.75	
Ultrasonic Burglar Alarm. Self-contained mains or battery powered unit complete with horn and AC adaptor. Inputs for pressure mats and other sensors together with exit/entry delays enable this unit to be used as a complete system. £45.00 + p&p £2.20	

SWITCHES	
Push to Make 15	Push to Break 25
Push on/off (3A mains)	
Sub. Min. Toggle:	
SPST	50 DPDT 70
DP Centre Off	89
Slider DPDT	17
DIL Switches:	
4-way	80 6-way 90
8-way	1.00
Rotary Switches	
1P12W 3P4W	4P3W 50

SOCKETS	
(Low profile)	
8 pin	7 22 pin 14
14 pin	8 24 pin 17
16 pin	10 28 pin 17
18 pin	12 40 pin 25
ZIF Sockets	
24 pin	3.20 40 pin 4.20

IDC CONNECTORS	
Rt. Ang.	Socket
20 way	1.00
26 way	1.10 1.15
34 way	1.10 1.30
40 way	1.30 1.45

COMPONENT PACKS	
1 650 Resistors 47R 10M	4.00
10 per value	
2 40 16V Electrolytics 10-1000µF	3.25
5 per value	
3 60 x Polyester Capacitors	5.55
0.01 10CF 250V 5 values	3.00
4 45 Presets 100R 1M	2.40
5 30 Low Profile IC Sockets.	2.40
6 14 & 16 pin	1.75
6 25 Red LEDs (5mm)	1.75

NOW IN STOCK  
SPQ256AL2 4.15

## BT STYLE PHONE CONNECTORS

NEW LOWER PRICES	
Starter kit (includes Master, Secondary, 20m cable, line cord, clips, etc) all you need to rewire your phone - with instructions	9.50
Master (flush)	2.80
Master (surface)	2.80
Master (mini surface)	3.00
Secondary (flush)	2.00
Secondary (surface)	2.00
Secondary (mini surface)	2.20
Dual outlet adaptor	3.60
4-way line cord with plug to splice terminals	1.75
Extension Leads:	
5m 320 8m 360 20m 700	
4-way line cord (per m)	2.00
Unapproved to BT connector	2.00
Plug-in Extension Ringer	6.00
ICD Insertion Tool	3.00
Cable Clips (per 25)	1.00
NOTE: IDC normally supplied.	

ANTEX IRONYS	
C240	15 Watt 5.60
CS230	17 Watt 5.80
XS240	25 Watts 5.90
ST4	Stand 1.90
Chrome-plated Bits	

## BEGINNERS' PROJECTS PACK

Contains solderless breadboard, components and booklet with instructions to build TEN fascinating electronic projects, e.g. thermostat, burglar alarm, light-operated switch, electronic lock, touchswitch, siren. Requires 9V PP3 battery. £2.50

## INFRA-RED REMOTE CONTROL KITS

These kits are designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The application will determine the interface circuitry between the receiver and the controlled device. General instructions and applications are supplied. The kits are coded and provide a high degree of security and noise immunity.

MK 18 Transmitter Kit	for use with MK 11/MK 12 receivers. Requires PP3 battery. Size 8 x 2 x 13cms. Range approx. 60 ft. £6.80
Keyboards for MK 18	
MK 9 4-way for use with MK 12	£1.90
MK 10 16-way for use with MK 12	£5.40
MK 13 11-way for use with MK 11	£4.35
MK 11 Receiver Kit	mains powered. Provides 10 latched plus 3 analogue outputs ideal for controlling audio amplifiers. TV or lighting where control of light brightness is required £13.50

MK 18 AC Power Controller Kit	for (phase) controlling AC loads from MK 11 analogue outputs, eg lamp dimming. £5.20
MK 19 Stereo Amplifier Controller Kit	for remote control of bass, treble and volume (or balance) by MK 11. Includes a one of 10 decoder remote channel or input selection. May be connected between the pre-amp and power amp of almost any audio system. £10.70

MK 12 Receiver Kit	mains powered with 16 latched or momentary outputs. Latched version is for applications requiring one output on at a time, eg TV channel selection. Momentary type gives an output only during transmission. Lines may be latched as required. £13.50
MK 15 Dual Latched Solid State Relay	for switching mains loads such as lamps, TVs, etc. from the outputs of the MK 12 (momentary). 15 items may be switched independently using 8 MK 15s. Triacs (not supplied) switch at mains zero to reduce interference. £4.50

TRANSFORMERS	
Chassis Mounting	
6-0-6V/100mA	1.10
9-0-9V/100mA	1.25
12-0-12V/100mA	1.25
9-0-9V/1A	2.30
12-0-12V/1A	2.30
15-0-15V/1A	2.40

For FREE 28-page catalogue send 9x6 SAE today!  
Telephone Orders Access 8 Barclay Card  
RING 01-567 8910 (24 Hrs.)  
Five Six Seven Eight Nine Ten

KITS	
CT1000K	Clock/Timer £17.40
CT1000KB*	Clock/Timer + Box £17.40
XK101	Electronic Lock £11.50
XK102*	3-Note Door Chime £5.50
XK104	Solid State Switch £2.40
XK112	Mains Wiring Remote Control £42.00
XK113	MW Radio £5.50
TD3000K†	300W Touchdimmer £7.75
TS3000K†	300W Touchswitch £7.75
LD3000K†	300W Lightdimmer £3.95
TDR3000K†	IR Remote Controlled Lightdimmer £14.95
MK6*	IR Transmitter for TDR300K and MK7 £4.50
TDE/K†	Touchdimmer extension Time Delay Touch Switch (300W) £5.00
MK1	Thermostat £4.60
MK2	Solid State Relay £2.60
MK4	Proportional Temperature Controller £6.50
MK5	Mains Timer (1KW) £4.50
MK7	Single Channel Infra Red Receiver (240V) £10.50
MK16	Mains Powered IR Transmitter £3.50
MK17	Single Channel Infra Red Receiver (12V) £10.50

MICROPROCESSOR TIMER KIT	
Designed to control 4 outputs independently switching on and off at preset times over a 7 day cycle.	
LED display of time and day, easily programmed via 20 way keyboard. Ideal for central heating control (including different switching times for weekends). Battery back-up circuit. Includes box. 18 time settings.	
CT6000K	£39.00
XK114. Relay Kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A 240V c/o contacts	£3.90
701 115 Additional Relays	£1.65

SECURITY PRODUCTS	
Protect your home and property and save by building your own burglar alarm system.	
Stair Mat 23 x 7 in (950 120)	£1.70
Floor Mat 29 x 16 in (950 125)	£2.60
Tamper-proof connecting block (950 110)	£0.30
Door/Window Contacts. Flush mounting, 4 wire, Magnet/switch Per Pair. (950 140)	£0.95
Window Tape 0.5" wide. 50m (950 145)	£2.50
Window Tape Terminations Per Pair. (950 150)	£0.36
Key-operated Switch. 1.5A/250V SPST Heavy chrome metal. (350 120)	£4.50
Passive Infra-Red Detector	

DISCO LIGHTING KITS	
DL 1000K - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. £15.95	
DLZ 1000K - A lower cost uni-directional version of the above. Zero switching to reduce interference. £8.95	
Optional opto input allowing audio 'beat' light response (DLA/1) 70p	
DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. £12.95	

# ELECTRONICS

11-13 Boston Road  
London W7 3SJ

Shop Hours:  
Mon. to Fri. 9am - 5pm  
Sat. 10am - 4pm  
TEL: ORDERS: 01-567 8910  
ENQUIRIES: 01-579 9794

## ORDERING INFORMATION:

ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.  
LOCAL AUTHORITY AND EXPORT ORDERS WELCOME  
GOODS BY RETURN SUBJECT TO AVAILABILITY

# QUALITY COMPONENTS... FAST!

SEMICONDUCTORS				CONNECTORS		CAPACITORS		RESISTORS	
AC127	35p	BU208	280p	W01	34p	40128E	28p	4066RE	28p
AC128	35p	CA3046	99p	W02	38p	40138E	38p	4067BE	250p
AD161	58p	CA3080E	135p	W04	44p	40148E	68p	4068BE	28p
AD162	60p	CA3140	90p	W005	30p	40158E	65p	4069BE	28p
BC107B	17p	CA3169	240p	ZK14	120p	40168E	35p	4070BE	30p
BC108C	15p	CA3240	145p	ZK500	22p	40178E	55p	4071BE	21p
BC109C	17p	LF347	175p	ZK502	18p	40188E	65p	4072BE	90p
BC140	37p	LF351	75p	ZK504	32p	40198E	41p	4073BE	28p
BC141	36p	LF353	36p			40208E	65p	4075BE	35p
BC168C	12p	LM301A	33p	1M4001	7p	40218E	60p	4076BE	74p
BC169C	12p	LM311	99p	1M4002	5p	40228E	72p	4077BE	32p
BC182L	12p	LM380	155p	1M4005	6p	40238E	28p	4078BE	32p
BC183L	15p	LM381	180p	1M4007	7p	40248E	49p	4081BE	28p
BC184L	15p	LM382	150p	1M4148	4p	40258E	28p	4082BE	28p
BC212	14p	LM384	170p	1N914	5p	40268E	110p	4085BE	59p
BC214	12p	LM387	175p	2N2219	37p	40278E	38p	4088BE	140p
BC327	14p	LM389	150p	2N2369A	28p	40288E	55p	4093BE	40p
BC328	14p	LM391A	380p	2N2646	90p	40298E	60p	4094BE	110p
BC337	14p	ML2955	115p	2N2904	32p	40318E	130p	4098BE	85p
BC547	9p	ML922	505p	2N2907	26p	40328E	65p	4099BC	96p
BC548	12p	MPF102	85p	2N3054	79p	40338E	94p	40106	44p
BC549	12p	NE555	37p	2N3055H	105p	40358E	85p	40109	86p
BCY70	23p	NE556	65p	2N3703	14p	40388E	85p	40162	68p
BCY71	22p	NE565	155p	2N3704	12p	40408E	60p	40174	72p
BD131	45p	NE566	160p	2N3705	12p	40418E	69p	40194	79p
BD132	50p	OA200	9p	2N3706	14p	40428E	56p	45028E	60p
BD135	37p	OA47	21p	2N3708	12p	40438E	60p	45038E	55p
BD139	40p	OA90	9p	2N3711	11p	40448E	63p	45088E	150p
BD140	40p	OA91	10p	2N3712	15p	40458E	115p	4510	65p
BD180	45p	SL490	320p	2N3903	16p	40468E	75p	4511	70p
BF256	37p	TDA1022	640p	2N3904	18p	40478E	75p	45208E	65p
BF259	37p	TDA1024	179p	2N3905	14p	40488E	50p	45688E	310p
BFX29	34p	TIP122	95p	2N4558	59p	40498E	56p	7106	810p
BFX64	34p	TIP127	75p			40508E	38p	7107	810p
BFX85	37p	TIP2955	95p	40008E	23p	40518E	60p	741	28p
BFX87	38p	TIP3055	87p	40018E	28p	40528E	60p	748C	59p
BFX88	35p	TIP31A	35p	40028E	28p	40538E	73p		
BFY50	31p	TIP41A	45p	40068E	72p	40548E	88p		
BFY51	38p	TIP42	45p	40078E	78p	40568E	95p		
BFY52	31p	VN1010M	92p	40088E	26p	40588E	82p		
BD206	200p	VN66AF	188p	40118E	28p	40598E	90p		

PLEASE REMEMBER OUR PRICES INCLUDE 15% VAT!

SEE THE 1985 CATALOGUE FOR A FULL RANGE OF COMPONENTS

4mm PLUGS - Black and red 16p EACH. Green, White, Yellow, Brown and Blue - 16p EACH.

4mm CHASSIS SOCKETS Above colours - 15p EACH. 4mm TERMINAL POSTS Above colours - 44p EACH.

PLASTIC PHONO PLUGS - Black, Red, White, Blue, Yellow - All 12p EACH.

BNC CONNECTORS Line Plug - 99p Line Socket - £1.15 Chassis Socket - 48p

D-RANGE PLUGS 9 WAY - £1.32 15 WAY - £1.42 25 WAY - £1.46

D-RANGE SOCKETS 9 WAY - £1.32 15 WAY - £1.36 25 WAY - £1.30

BT CONNECTORS Line cord & plug - £1.92 Wall Socket - £2.94

DIN PLUGS - 2pin - 12p; 3pin - 15p; 4pin - 33p; 5pin 180 - 17p; 6pin - 42p; 7pin - 24p; 8pin - 62p

SEE CATALOGUE FOR FULL DETAILS OF CONNECTORS

ELECTROLYTIC AXIAL TYPE 25V:10uF 8p; 22uF 10p; 47uF 12p; 100uF 15p; 150uF 20p; 220uF 17p; 330uF 20p; 470uF 22p; 1000uF 38p; 2200uF 61p; 3300uF 91p

63V:1uF 9p; 1.5uF 11p; 2.2uF 8p; 3.3uF 8p; 4.7uF 8p; 6.8uF 18p; 10uF 12p; 15uF 15p; 22uF 17p; 47uF 17p; 100uF 21p; 150uF 31p; 220uF 29p; 330uF 32p; 470uF 46p; 1000uF 78p; 2200uF £1.50

TANTALUM BEAD (uF/Volts) 0.1/35 12p; 0.2/35 17p; 0.4/35 18p; 1/35 19p; 2.2/35 21p; 4.7/16 17p; 10/16 26p; 22/25 63p; 100/3 37p; 100/10 £1.28

DISC CERAMIC TYPE 0.01uF 8p; 0.022uF 6p; 0.047uF 8p; 0.1uF 8p

1% POLYSTYRENE TYPE (pF) 100 25p; 150 25p; 220 25p; 270 25p; 330 26p; 390 27p; 470 27p; 1000 28p

SEE CATALOGUE FOR A FULL LIST OF CAPACITORS

1% 0.4 WATT METAL FILM These high quality resistors are supplied singly or in bargain packs. All E24 values 1R - 1M are available:

ONLY 2p EACH! . . . OR PACK 1: 10 of each value = 1210 resistors £21.95

PACK 2: 5 of each value = 605 resistors £10.99

1985 CATALOGUE

PACKED WITH THOUSANDS OF TOP QUALITY COMPONENTS AT COMPETITIVE PRICES AND ALL COVERED BY OUR SUPERB DISPATCH SERVICE!

INCLUDES 3 £1 VOUCHERS AND DETAILS OF OUR DISCOUNT SCHEME FOR REGULAR CUSTOMERS.

SEND 50p CHEQUE/P.O. TODAY FOR YOUR COPY BY RETURN OF POST!

# AB MICROSYSTEMS

All Mail to: P.O. BOX 12, SWINTON, MANCHESTER M27 3WS.

PRICES INCLUDE VAT @ 15%. POSTAGE: PLEASE ADD 30p TO ORDERS UNDER £5. OFFICIAL ORDERS WELCOME. DESPATCH NORMALLY 24 HRS. E.&O.E. REGISTERED OFFICE: 2 HULME STREET, MANCHESTER 1. CALLERS BY APPOINTMENT ONLY

## TELEVISION/COMPUTER FULL-TIME TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN EDUCATION COUNCIL)

**2 YEAR**  
BTEC National Diploma (OND)  
**ELECTRONIC & COMMUNICATIONS ENGINEERING**  
(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

**15 MONTHS**  
BTEC National Certificate (ONC)  
**ELECTRONIC EQUIPMENT SERVICING**  
(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

**15 MONTHS**  
BTEC National Certificate (ONC)  
**COMPUTING TECHNOLOGY**  
(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

**9 MONTHS**  
BTEC Higher National Certificate (HNC)  
**COMPUTING TECHNOLOGY & ROBOTICS**  
(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

SHORTENED COURSES OF FROM 3 TO 6 MONTHS CAN BE ARRANGED FOR APPLICANTS WITH PREVIOUS ELECTRONICS KNOWLEDGE


NEXT TWO SESSIONS COMMENCE ON APRIL 22nd & SEPTEMBER 16th

FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE (Dept EE)  
20 PENYVERN ROAD, EARLS COURT,  
LONDON SW5 9SU. Tel: 01-373 8721.
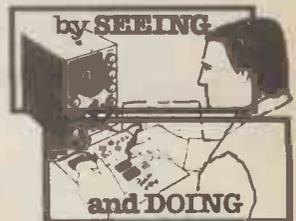
## Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.
- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.



New Job? New Career? New Hobby? SEND THIS COUPON NOW.

FREE! COLOUR BROCHURE

Please send your brochure without any obligation to

OR TELEPHONE US 062 687 2598 OR TELEX 22758 (24 HR SERVICE)



EE15

NAME \_\_\_\_\_ I am interested in

ADDRESS \_\_\_\_\_

ELECTRONICS

MICROPROCESSORS

RADIO AMATEUR LICENCE

CITY & GUILDS EXAMS

Other Subjects \_\_\_\_\_

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS



Full Kits inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.  
If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint as an extra — 70p each. Reprints available separately 70p each + p&P 60p.



## THIS MONTH'S KITS

SAE or 'phone for prices	
INSULATOR TESTER Apr. 85	£16.96
LOAD SIMPLIFIER Feb. 85	£16.98
SOLID STATE REVERB Feb. 85	£39.98
GAMES TIMER Jan. 85	£7.63
SPECTRUM AMPLIFIER Jan. 85	£5.98
TV AERIAL PRE-AMP Dec. 84	£12.36
Optional PSU 12V £2.03.	240V £9.86
MINI WORKSHOP POWER SUPPLY Dec. 84	£34.98
DOOR CHIME Dec. 84	£14.91
BBC MICRO AUDIO STORAGE SCOPE INTERFACE Nov. 84	£28.77
PROXIMITY ALARM Nov. 84	£17.98
MAINS CABLE DETECTOR Oct. 84	£4.39
MICRO MEMORY SYNTHESIZER Oct. 84	£47.98
DRILL SPEED CONTROLLER Oct. 84	£6.89
GUITAR HEAD PHONE AMPLIFIER Sept. 84	£6.38
SOUND OPERATED FLASH less lead Sept. 84	£5.91
TEMPERATURE INTERFACE FOR BBC MICRO Aug. 84	£19.70
CAR RADIO BOOSTER Aug. 84	£13.87
ULTRASONIC BURGLAR ALARM July 84 inc relay + sounder	£28.40
CAR LIGHTS WARNING July 84	£7.99
VARICAP AM RADIO May 84	£10.43
EXPERIMENTAL POWER SUPPLY May 84	£18.72
SIMPLE LOOP BURGLAR ALARM May 84	£13.62
MASTERMIND TIMER May 84	£5.44
FUSE/DIODE CHECKER Apr. 84	£3.45
QUASI STEREO ADAPTOR Apr. 84	£10.90
DIGITAL MULTIMETER add on for BBC Micro Mar. 84	£24.98
NI-CAD BATTERY CHARGER Mar. 84	£9.85
REVERSING BLEEPER Mar. 84	£6.78
PIPE RINDER Mar. 84	£3.60
IONISER Feb. 84	£23.98
ZX81 EPROM PROGRAMMER Feb. 84	£14.48
SIGNAL TRACER Feb. 84	£14.89
CAR LIGHT WARNING Feb. 84	£3.76
GUITAR TUNER Jan. 84	£17.73
BIOLOGICAL AMPLIFIER Jan. 84	£19.16
CONTINUITY TESTER Dec. 83	£9.99
CHILDREN'S DISCO LIGHTS Dec. 83	£8.42
NOVEL EGG TIMER Dec. 83 inc. case	£10.24
SPEECH SYNTHESIZER FOR THE BBC MICRO Nov. 83 less cable + sockets	£21.98
MULTIMOD Nov. 83	£16.98
LONG RANGE CAMERA/FLASHGUN TRIGGER Nov. 83	£13.50
HOME INTERCOM less link wire Oct. 83	£14.38
DIGITAL TO ANALOGUE BOARD Oct. 83	£19.98
less cable, case & connector	
HIGH POWER DAC DRIVER BOARD Oct. 83 less case	£12.52
A TO D CONVERTER FOR RM3802 Sept. 83 inc plug	£35.98
HIGH SPEED A TO D CONVERTER Sept. 83 less cable & connector	£27.98
SIGNAL CONDITIONING AMP Sept. 83 no case	£8.98
STORAGE SCOPE INTERFACE FOR BBC MICRO Aug. 83 less software	£15.38
PEDESTRIAN CROSSING SIMULATION BOARD Aug. 83 no case	£10.29
HIGH POWER INTERFACE BOARD Aug. 83 no case	£10.38

USER PORT I/O BOARD less cable + plug	£10.49
USER PORT CONTROL BOARD July 83 less cable + plug + case	£25.14
GUITAR HEADPHONE AMPLIFIER May 83	£7.92
MW PERSONAL RADIO less case, May 83	£7.62
MOISTURE DETECTOR May 83	£5.45
CAR RADIO POWER BOOSTER April 83	£11.99
FUNCTION GENERATOR April 83	£45.98
FLANGER SOUND EFFECTS April 83	£24.17
NOVELTY EGG TIMER April 83 less case	£5.48
DUAL POWER SUPPLY March 83	£59.38
BUZZ OFF March 83	£4.51
PUSH BIKE ALARM Feb. 83	£11.73
ZX TAPE CONTROL Nov. 82	£7.13
G. P. PRE-AMP Oct. 82	£6.09
CONTINUITY CHECKER Sept. 82	£5.47
2-WAY INTERCOM July 82 no case	£4.52
ELECTRONIC PITCH PIPE July 82	£5.40
REFLEX TESTER July 82	£7.77
SEAT BELT REMINDER Jun. 82	£4.10
EGG TIMER June 82	£5.44
CAR LED VOLTMETER less case, May 82	£23.18
V.C.O. SOUND EFFECTS UNIT Apr. 82	£12.71
CAMERA OR FLASH GUN TRIGGER Mar. 82	£13.65 less tripod bushes
POCKET TIMER Mar. 82	£4.10
GUITAR TUNER Mar. 82	£17.19
SIMPLE STABILISED POWER SUPPLY Jan. 82	£26.98
MINI EGG TIMER Jan. 82	£4.40
SIMPLE INFRA RED REMOTE CONTROL Nov. 81	£18.70
CAPACITANCE METER Oct. 81	£25.81
SUSTAIN UNIT Oct. 81	£13.99
TAPE NOISE LIMITER Oct. 81	£4.98
HEADS AND TAILS GAME Oct. 81	£2.75
CONTINUITY TESTER Oct. 81	£4.48
PHOTO FLASH SLAVE Oct. 81	£3.80
FUZZ BOX Oct. 81	£7.98
SOIL MOISTURE UNIT Oct. 81	£6.39
0-12V POWER SUPPLY Sept. 81	£10.48
COMBINATION LOCK July 81 less case	£21.58
SOIL MOISTURE INDICATOR E.E. May 81	£4.49
GUITAR HEADPHONE AMP E.E. May 81	£4.66
PHONE BELL REPFATER/BABY ALARM May 81	£6.15
INTERCOM April 81	£24.43
MODULATED TONE DOORBELL Mar. 81	£7.45
2 NOTE DOOR CHIME Dec. 80	£11.35
LIVE WIRE GAME Dec. 80	£12.87
GUITAR PRACTICE AMPLIFIER Nov. 80	£4.99
£14.10 less case. Standard case extra	
SOUND TO LIGHT Nov. 80 3 channel	£22.40
TRANSISTOR TESTER Nov. 80	£12.80
AUDIO EFFECTS UNIT FOR WEIRD SOUNDS Oct. 80	£14.40
IRON HEAT CONTROL Oct. 80	£6.30
MICRO MUSIC BOX Feb. 80	£17.86
Case extra	£3.60
SPRING LINE REVERB UNIT Jan. 80	£27.20
UNIBOARD BURGLAR ALARM Dec. 79	£5.70
DARKROOM TIMER July 79	£3.20
MICROCHIME DOORBELL Feb. 79	£17.48
SOUND TO LIGHT Sept. 78	£9.20
CAR BATTERY STATE INDICATOR less case Sept. 78	£2.29
R.F. SIGNAL GENERATOR Sept. 78	£31.20
IN SITU TRANSISTOR TESTER Jun. 78	£7.50
WEIRD SOUND EFFECTS GENERATOR Mar. 78	£6.20
ELECTRONIC DICE Mar. 77	£4.96

## TOOLS

ANTEX MODEL C IRON	£6.98
ANTEX X5 SOLDERING IRON 25W	£7.25
ST4 STAND FOR IRONS	£2.85
HEAT SINK TWEEZERS	45p
SOLDER HANDY SIZE 5	£1.39
SOLDER CARTON	£2.50
SOLDER REEL SIZE 10	£4.67
LOW COST PLIERS	£1.98
LOST COST CUTTERS	£1.99
BENT NOSE PLIERS	£1.89



MINI DRILL 12V (MD1)	£8.38
MULTIMETER TYPE 1 10000opv	£5.98
MULTIMETER TYPE 2 20,000opv	£17.38
MULTIMETER TYPE 3 30,000opv	£27.98
MULTIMETER TYPE 4 10M DIGITAL	£39.98
DESOLDER PUMP	£5.48
SIGNAL INJECTOR	£2.98
CIRCUIT TESTER	78p
HELPING HANDS JIG & MAGNIFIER	£7.98
MINIATURE VICE (PLASTIC)	£1.85

## OUR PRICES INCLUDE VAT

### MAGENTA ELECTRONICS LTD.

EE28, 135 HUNTER ST., BURTON-ON-TRENT STAFFS, DE14 2ST. MAIL ORDER ONLY. 0283 65435, Mon-Fri 9-5. Access/Barclaycard (Visa) by phone or post. 24 hr Answerphone for credit card orders.



## FUN WITH ELECTRONICS

Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification and how they work). Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.

### COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.

Supplied less batteries & cases.

FUN WITH ELECTRONICS, COMPONENT PACK £16.98

BOOK EXTRA £1.75.

Book available separately.



## COMPONENTS

We stock a standard range of electronic components including resistors, pots, ICs, capacitors, relays, transformers, switches, connectors, wire, cases, speakers & breadboards. Full details are in our catalogue. £1.

## COMPUTER ACCESSORIES

BBC TRACKBALL CONTROLLER. 2" ball. 2 fire buttons. Analogue input port connector. Includes simple software listing for freehand drawing. Simply incorporates into your programs. £17.98

6BC Digital Joystick. 2 fire buttons. D plug connects to analogue input. £9.59


## TEACH IN 84

Full kit including 2 EBBO breadboards & a FREE copy of our catalogue. TEACH IN 84 KIT £22.98 inc VAT. Reprints 70p each (12 part series).
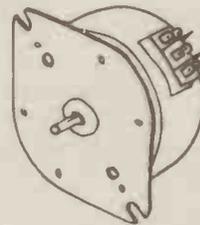
## ROBOTS and MOTORS

DIY Robotics & Sensors Books — with the BBC £7.95; for the Commodore 64 £7.99. Components used in these books are in our catalogue/price list. Catalogue £1. Price list only 50p.

SAA1027 driver £5.99; 8 way darlington driver (ULN2803) £2.38; TL081 49p



ID35 Stepper Motor. 48 Steps. 12V. £14.50

BBC to ID35 Stepper Motor Interface Kit £13.99 Ref. EE.

PCB, driver IC, components, connectors & leads included. Demonstration software listings, circuit diagram, pcb layout & construction details given. Requires unregulated 12Vdc power supply. Interface Kit £13.99; Optional Power Supply Parts £4.67

HOW TO MAKE COMPUTER CONTROLLED ROBOTS by Potter/Oxlade. BOOK £3.20. For BBC, Spectrum, C64 & VIC20.

Make a mobile arm robot from simple materials. Electronic parts etc. available from Magenta. Ideal for age 11 upwards & all beginners.

Also similar to above HOW TO MAKE COMPUTER MODEL CONTROLLERS book £3.19.

PRACTICAL THINGS TO DO WITH A MICROCOMPUTER £2.19. Programs, information & electronic circuits.

UNDERSTANDING COMPUTER GRAPHICS with programs £2.45.

EXPANDING YOUR MICRO £2.45.

FIRST GUIDE TO THE BBC MICRO £2.25 (for youngsters/beginners)

MICROPROCESSOR FOR HOBBYISTS £4.98

ADVENTURES WITH DIGITAL ELECTRONICS £4.25

INTERFACING TO MICROPROCESSORS & MICROCOMPUTERS £8.50


AN INTRODUCTION TO PROGRAMMING THE BBC B BP139 £2.25

## MOTOR — GEARBOX ASSEMBLIES

Miniature precision made. Complete with quality electric motor. Variable reduction ratios achieved by fitting from 1-6 gearwheels (supplied) as required. Operates from 1.5V to 4.5V. Small unit type MGS speed range 3rpm-2200rpm depending on voltage & gear ratio. Large unit type MGL (higher torque motor) 2rpm-1150rpm. Long 3mm dia output shafts. Ideal for robots and buggies.

Small Unit (MGS) £3.49. Large Unit (MGL) £3.98.

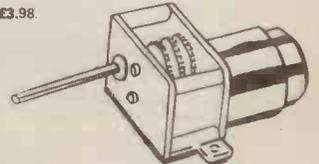Pulley wheels 3mm bore. Metal flange with brass hub. 10mm dia 85p. 20mm dia 98p. 30mm dia £1.21. Metal collar with fixing screw, 3mm bore 24p. Flexible spring coupling 5mm. Length 31mm 68p. Flexible metal coupling (universal) 3mm £2.98



## CATALOGUE

FULLY REVISED 1985 CATALOGUE. Brief details of each kit, our books, & illustrations of our range of tools & components. Also stepper motor, interface kit & simple robotics. Plus circuit ideas for you to build. If you read Everyday Electronics than you need a copy of the MAGENTA catalogue.

CATALOGUE & PRICE LIST — Send £1 in stamps etc. or add £1 to your order. Price list — 9x4 5ae.

Catalogue FREE TO SCHOOLS/COLLEGES. REQUESTED ON OFFICIAL LETTERHEAD.

## ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £3.58. Component pack £20.98 less battery.

# EVERYDAY ELECTRONICS and computer PROJECTS

VOL 14 N°5

MAY '85

## READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply **must** be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

## COMPONENT SUPPLIES

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

## OLD PROJECTS

We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used.

We regret that we **cannot provide data or answer queries on projects that are more than five years old**.

## SUBSCRIPTIONS

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £15.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

## BACK ISSUES & BINDERS

Certain back issues of EVERYDAY ELECTRONICS are available world-wide price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

Binders to hold one volume (12 issues) are available from the above address for £5.50 inclusive of postage and packing worldwide.



## BUYER'S GUIDES

**I**N THIS issue we continue what will become an occasional feature in EE—the buyer's guides. Regular readers will have noted our recent *Monitor Buyer's Guide* in the March issue. Reader response to this guide was good and it appears that the need for basic information on products is growing as the range of products increases. With so many companies selling a wide range of equipment, just knowing what is available in your price range is becoming difficult.

In this issue we carry a fairly extensive guide to multimeters. Rather than just listing available products with a brief specification, each guide will give an introduction to the equipment and try to assist the understanding of the figures being quoted or the various types, etc. In this way, the guides are educational as well as informative.

Since the range of multimeters is vast we have concentrated on the lower priced models likely to be purchased by the average hobbyist. Multimeters are extremely versatile and represent one of the essential items of equipment required by anyone involved in electronics—so take a good look before you buy.

We should point out that we have made no attempt to review or rate the meters shown, neither have they been selected for quality or value. The guide simply shows what is available and assists in giving the data necessary to make your choice. Products purchased as a direct result of the guide are not covered by the mail order protection service unless the supplier has placed a display advertisement for them in the issue. We therefore do recommend that you look carefully at advertisers' products—many of them carry a good range in this particular area of interest—before you purchase.

Would you please mention EE when ordering or requesting more information on any item seen in our pages. By doing this you help to make sure the companies keep us informed of all their products and news so, in turn, we can keep you up to date.

## VALUE

It appears that we have escaped most of the dreaded VAT. It was feared that all publications would be forced to add VAT to their cover price but for the time being this has not happened. We had no wish to increase the price of EE which we believe represents good value, particularly in comparison with our competitors. The information we publish is educational and it would have been a pity to see it taxed. However, VAT on advertising will affect the small companies and that is not very helpful.

## Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL, WESTOVER HOUSE,  
WEST QUAY ROAD, POOLE, DORSET BH15 1JG

Phone: Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone

**Editor**  
MIKE KENWARD

**Secretary**  
PAULINE MITCHELL  
0202 671191 Ext 259

**Advertisement Manager**  
NIGEL BELLWOOD 01-261 6882

**Advertisement Sales Executive**  
RICHARD WILLET 01-261 6745

**Classified Supervisor**  
BARBARA BLAKE 01-261 5897

**Advert Make-Up and Copy Department**  
JULIE FISH 01-261 6615

**Advertisement Offices**  
EVERYDAY ELECTRONICS  
ADVERTISEMENTS  
KING'S REACH TOWER  
STAMFORD STREET,  
LONDON SE1 9LS  
Telex 915748 MAGDIV-G

# AMSTRAD AMPLIFIER

## CPC 464

P. DOOLEY

THE new Amstrad computer is equipped with a three channel sound system, all channels being directed to the internal speaker. To appreciate the full sound capabilities of this machine, a stereo amplifier is required. The stereo signals for driving the amplifier are available at the 3.5 jack socket marked (I/O). When amplified through a stereo system the three channels (A,B, and C) appear as Left, Right and Centre.

Any 8 ohm speakers rated at several watts each will be suitable. The prototype uses a pair of car stereo speakers which are supplied in sloping front enclosures, and perform well. A pair of small hi-fi speakers would also be suitable if they are available. Although the output of the amplifier is only 0.25W, per channel, using speakers of a higher rating will enhance the sound, particularly at lower frequencies, and alleviate distortion at full volume.

### CIRCUIT DESCRIPTION

The amplifier (see Fig. 1) is based on the LM386 audio power i.c. In order to keep the external components count to a minimum, the gain is set internally to 20.

Provision is made to increase the gain using additional components connected to pins 1 and 8, but is not utilised in this application. As the output from the computer is at a fixed level, a volume control, VR1, is required.

Power is derived from a mains transformer which has a secondary winding of 6V. This is then full wave rectified by D1-D4 and smoothed by C7, giving an input voltage of 7.5V to the

regulator, IC3. This is the minimum that can be applied to the device to enable it to function as a 5 volt regulator, and has been kept low to minimise the dissipation. D5 is mounted on the front panel, and serves as a power 'on' indicator.

### CONSTRUCTION

Fit and solder all components to the p.c.b. Note that although a 16-pin socket has been used to mount the two LM386 i.c.s, two 8 pin sockets could be used if they are to hand. Veropins are inserted at all positions where flying leads are terminated.

The prototype uses a plastic case measuring 127×133×54mm, which splits into two halves (top and bottom), and has removable front and rear panels. This greatly simplifies construction, as the p.c.b., mains transformer, and fuse holder can be placed in position and the mounting holes marked. This should be done with the front panel in position with the controls fitted, to ensure clearance from the p.c.b.

The rear panel requires drilling for the speaker sockets and a grommet for the mains cable. See Fig. 2 and Fig. 3 for p.c.b. layout.

### FINAL ASSEMBLY

Install C1,C2, and the 0V link between SK1 and VR1. Position the l.e.d. in the clip and connect the cathode to the 0V terminal on SK1. The completed front

panel, rear panel, p.c.b. transformer and fuse holder can now be fitted in position and all interwiring completed, as shown in Fig. 4. A solder tag must be fitted under one of the transformer mounting screws for connection of the earth lead.

An input lead, of a length to be determined by the constructor, is required, and consists of a length of twin screened cable terminated at both ends with a 3.5 stereo jack plug.

After the usual last check for obvious faults, fit a 250mA fuse and switch on. Check that the l.e.d. is lit and the regulator output is 5 volts. If all is well plug in the speakers and the input lead (with amplifier switched off). Touching the two outer rings of the jack plug should cause a buzzing noise, due to pick-up, in the speakers. If there is a fault on one channel of the amplifier, comparisons can be made with the other.

Connect the amplifier to the computer and load a selection of programs. Some programs will only emerge as mono reproductions, as they only contain single channel commands. If any imbalance is detected on multi-channel programs, this could be due to the software, as the volume, as well as other parameters, is software selectable.



**TWO STEREO AMPS  
TO BOOST YOUR  
AMSTRAD MICRO'S  
SOUND EFFECTS**

**ONE MAINS UNIT  
AND ONE  
MICRO POWERED  
UNIT**

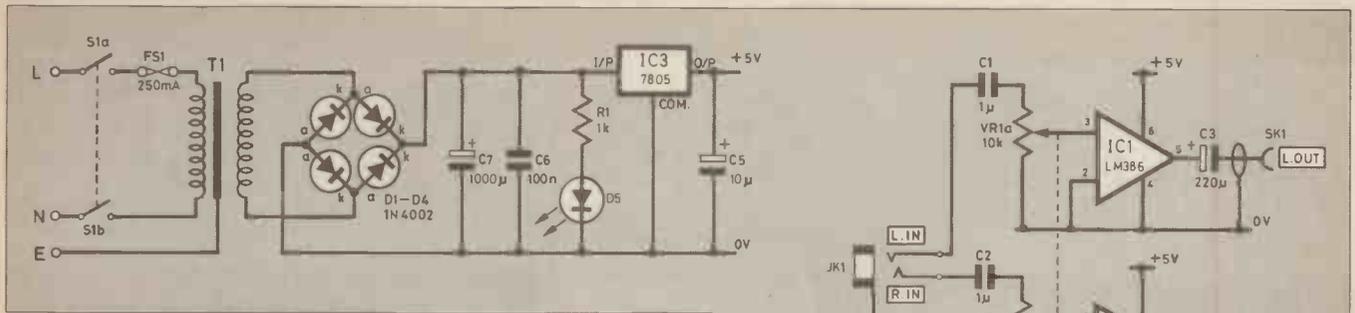


Fig. 1. Circuit diagram of the Mains Powered version, including the p.s.u. section.

## COMPONENTS

### Resistors

R1 1k 1/3 or 1/4W

### Potentiometers

VR1 10k log dual gang

### Capacitors

C1,C2 1 $\mu$  polyester (2 off)  
 C3,C4 220 $\mu$  16V electrolytic axial (2 off)  
 C5 10 $\mu$  16V electrolytic axial  
 C6 100n ceramic disc  
 C7 1000 $\mu$  25V elect axial

### Semiconductors

IC1,IC2 LM386 (2 off)  
 IC3 7805 regulator  
 D1-4 1N4002 (4 off)  
 D5 0.2in red + clip

### Miscellaneous

JK1 3.5mm stereo jack socket  
 SK1,2 phono socket (2 off)  
 S1 rotary mains switch  
 T1 mains transformer—  
 6 volt 500ma secondary  
 FS1 250mA fuse and chassis holder (20mm)  
 Case Tandy 270-218

P.c.b., 2 knobs, 16 pin i.c. socket, p.c.b. pillars, Veropins, connecting wire, twin screened cable, 1 amp mains cable, grommet, 3.5mm stereo jack plug  
 Phono plug (2 off)

See  
**Shop  
 Talk**  
 page 256

Printed circuit board: single-sided  
 106 x 48mm, EE PCB  
 Service, code 8505-02

Approx. cost  
 Guidance only **£15.00**

## COMPUTER POWERED VERSION

For those who intend to use the amplifier solely for the Amstrad, a computer powered version will be described. The unit is basically the same as the mains powered version (see Fig. 5), the differences being as follows:

- 1) The mains transformer, bridge diodes D1 to D4, regulator IC1, and other

## CIRCUIT DIAGRAM

For C1 and C5, 1 $\mu$  non-polarised tantalum capacitors have been used because of their smaller physical size (see Fig. 7). Resistors R1 and R2 and capacitors C3 and C7 are to suppress any tendency for the LM386 to break into oscillation, as is sometimes the case. Capacitors C2, C6 and C9 de-couple the 5 volt supply.

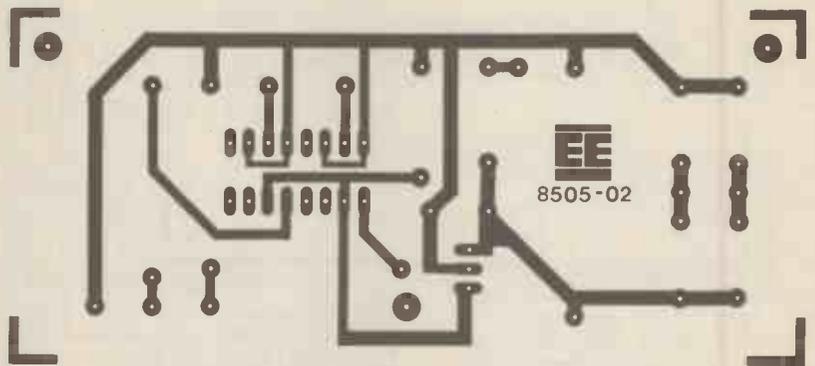


Fig. 2. P.c.b. track layout (actual size).

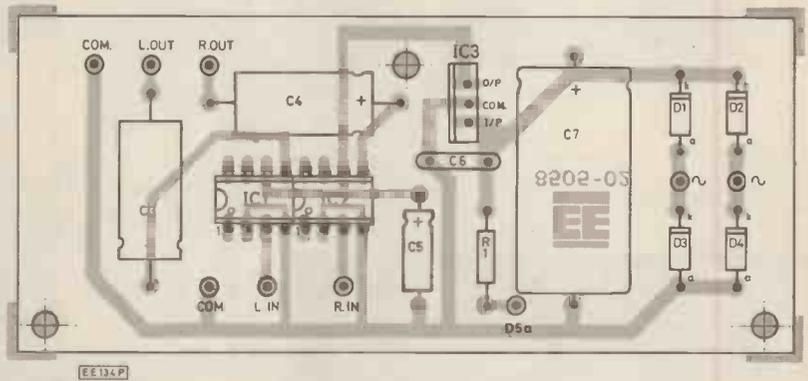


Fig. 3. Component layout.

power supply components, are omitted.


- 2) Extra de-coupling components are added to prevent interference with the computer circuitry and display.
- 3) A smaller case can be used.

## CONSTRUCTION

The p.c.b. shown in Figs. 6 and 7 is 102mm x 41mm, and will slot into the specified case without the need of any mounting hardware. The front and rear panels require drilling. To prevent a volt drop occurring in the power leads, cable with a rating of 3 amps (0.5mm) should be used. For the same reason, the power lead to the computer should be kept as short as possible.



The assembled p.c.b. with all flying leads attached, is slid in to the case. When the front and rear panels have been assembled, they should be laid in a posi-

Not to scale

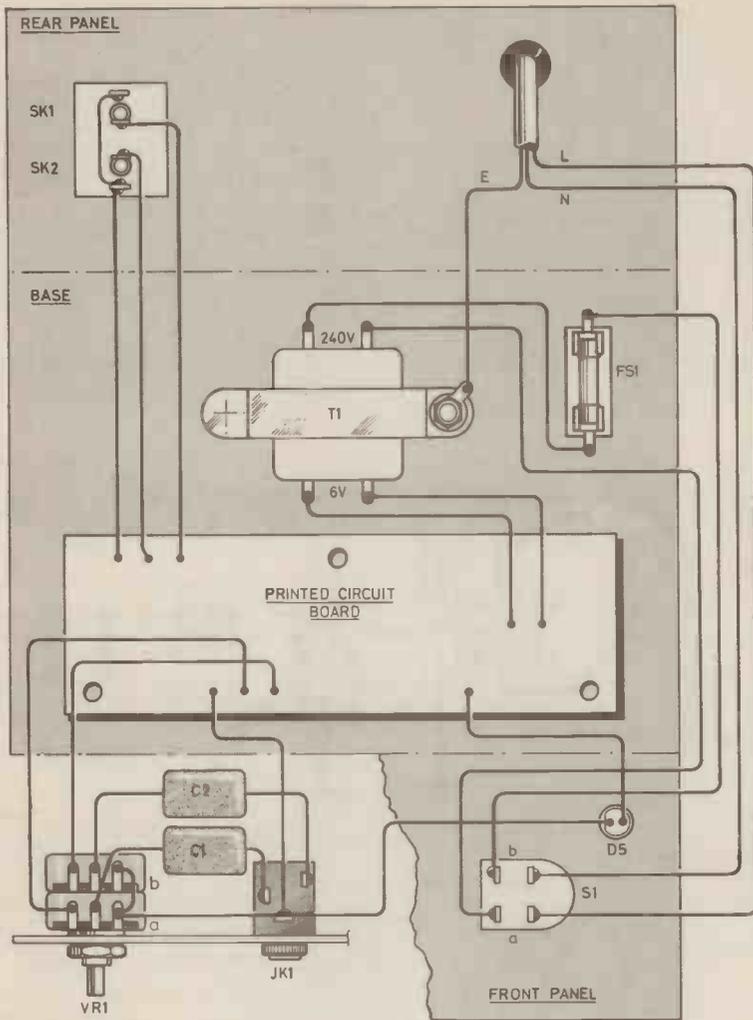

EE138P

Fig. 4. Wiring and layout diagram. Note: C1 and C2 should go to the left-hand tags of VR1 and, instead, the wipers to the p.c.b.

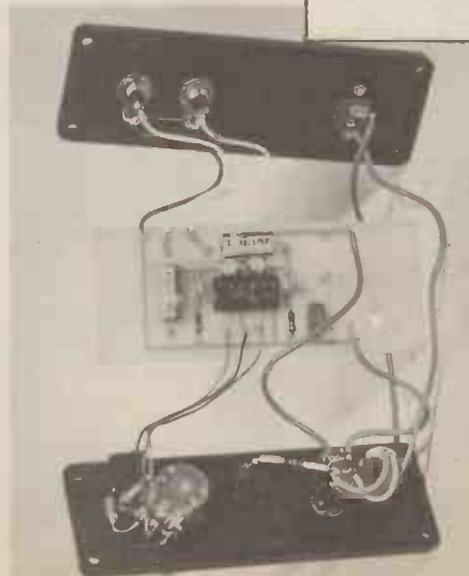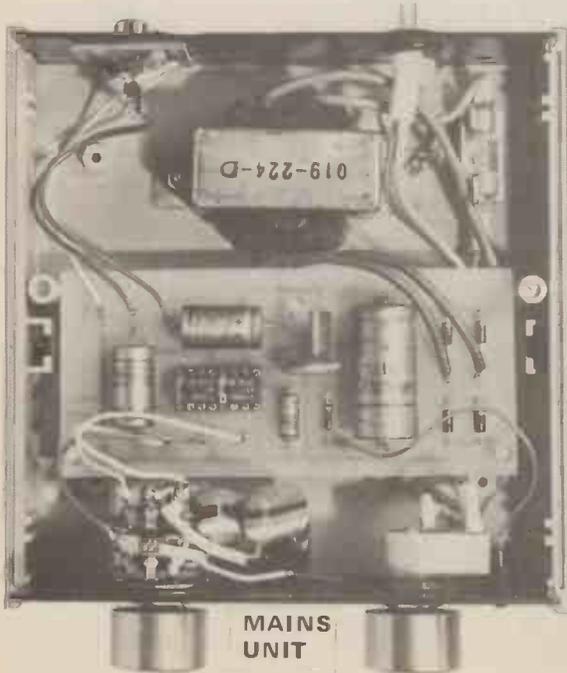

tion to enable the interconnections to be carried out (see Fig. 8).

With all wiring completed, the amplifier can be tested using the procedure previously described. It is recommended that the amplifier be tested using an external supply, e.g. a 6 volt battery or battery eliminator, and not powered by the computer until the unit has been proven to work correctly. The current consumption should be in the region of 100mA at high volume levels. □

## COMPONENTS

### Resistors

R1,R2	10 $\frac{1}{4}$ W (2 off)
R3	1k $\frac{1}{4}$ W

### Potentiometers

VR1	10k dual gang log.
-----	--------------------

### Capacitors

C1,C5	1 $\mu$ tantalum non-polarised (2 off)
C2,C6	10 $\mu$ 10 volt electrolytic (2 off)
C3,C7	47n ceramic (2 off)
C4,C8	220 $\mu$ 16 volt elec. (2 off)
C9	220n polyester

### Semiconductors

IC1,IC2	LM386 (2 off)
D1	0.2in red + clip

### Miscellaneous

JK1	3.5mm stereo jack socket
SK1,2	2 x single phono skts (or 1 double)
SK3	D.c. power skt 2.1mm Tandy 274-1565
S1	D.P.S.T. min toggle switch
Case	Tandy 270-286
P.c.b.	1 knob, 16-pin i.c. skt, p.c.b. pins, connecting wire, 0.5mm wire (power), twin screened cable, grommet, 3.5mm stereo jack plug (for input lead), Phono plug (for speakers) (2 off), D.C. power jack plug 5mm. Tandy 274-1567

Printed circuit board: single-sided  
106 x 48mm, EE PCB  
Service, code 8505-03

See  
**Shop  
Talk**  
page 256

**MICRO-POWERED  
UNIT**

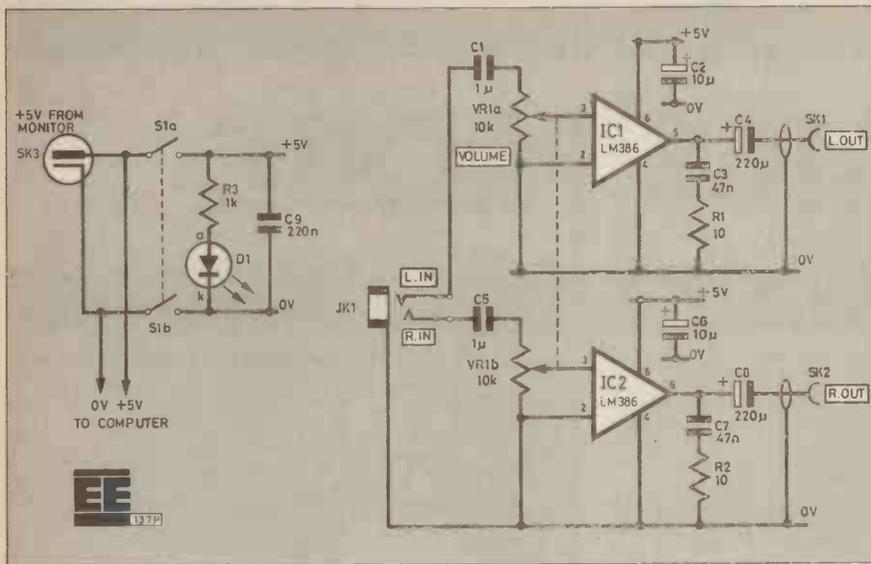


Fig. 5. Circuit diagram of the unit powered from the Amstrad microcomputer itself. The LM386 audio power amplifier i.c. has its gain set internally to 20, although there is a provision for increasing the gain using additional external components. The facility, which is available through pins 1 and 8, is not taken advantage of here, in order to keep the project simple.

**COMPONENTS**  
 approximate  
 cost **£12.00**

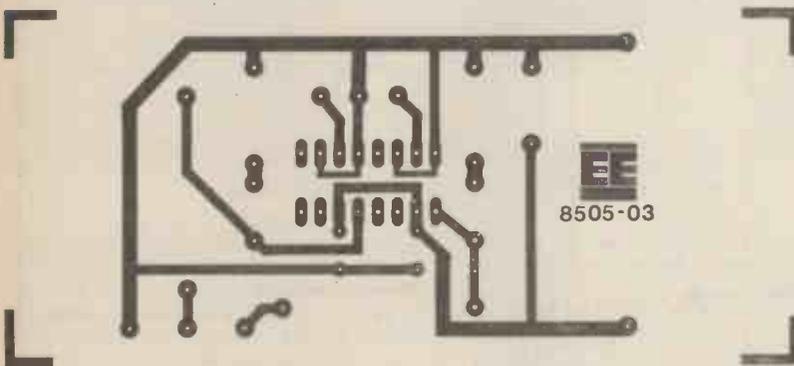


Fig. 6. P.c.b. track layout of the Micro-Powered version (actual size). This p.c.b. is of dimensions which allow it to slide directly (horizontally) into the Tandy box specified in the components list (part No. 270-286).


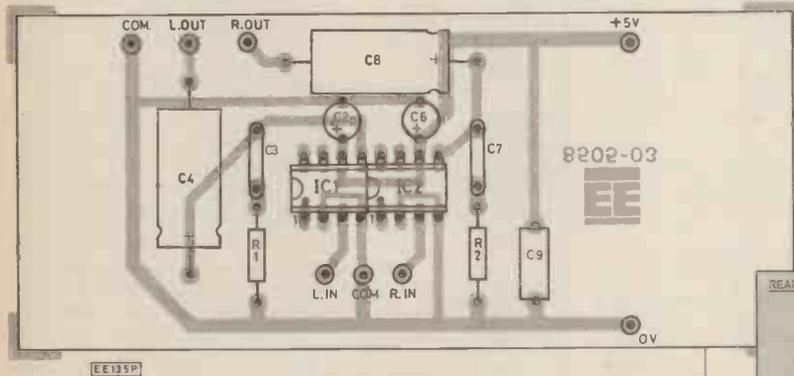


Fig. 7. Component layout. The input capacitors are mounted off the board (between JK1 and VR1) and are non-polarised tantalum types for compactness.

**0.25 WATTS  
 PER  
 CHANNEL**

Fig. 8. Wiring diagram of the Amstrad powered version. Note: VR1a wiper should go to L.IN, not COM, and likewise the 0V wire from JK1, VR1a, etc. should go to COM on the p.c.b.

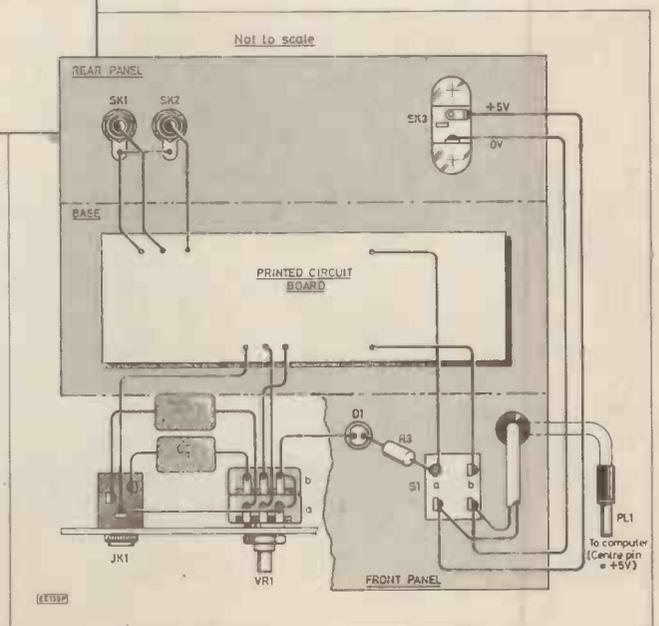

# VOLTAGE PROBE

R.A. PENFOLD

THE STANDARD ITEM of test equipment for making voltage checks on electronic equipment is, of course, an ordinary multimeter. However, there is an alternative which is becoming increasingly popular, and this is the "voltage probe" type of voltage tester. The facilities offered vary considerably from one unit to another, but all have a bargraph i.e.d. display with the i.e.d.s being used to indicate whether or not the test voltage is above certain threshold levels. This obviously gives only a limited degree of accuracy, but the accuracy is sufficient for much electronic servicing, and a voltage probe is very quick and convenient in use.

## DISPLAY

The voltage probe described in this article is a fairly sophisticated type which has a ten i.e.d. bargraph display. Two measuring ranges are available, giving a total of twenty threshold voltage levels. On the most sensitive range the switching levels are at approximately 0.5, 0.75, 1, 1.5, 2, 3, 4.25, 6, 8.5 and 12 volts. On the high voltage range these threshold potentials are boosted by a factor of ten, giving a maximum switching level at about 120 volts.

A logarithmic scale is used so that the ten i.e.d.s cover a wider range of voltages, and although this initially makes results a little more difficult to interpret, one soon gets used to the scaling. It has to be emphasised that the threshold levels are only approximate, and that the unit is not intended for use in applications where

precise measurements are needed. It is intended as a quick checker where limited accuracy is adequate.

The unit will respond to both positive and negative inputs, and a i.e.d. indicates the polarity of the input signal. The unit will also respond to a.c. signals, and a second indicator i.e.d. switches on if the input is an a.c. signal. When the input signal is an a.c. type the unit responds to the peak voltage (which is about 1.4 times the r.m.s. value for sinewave signals). Overload protection against both positive and negative inputs is included in the unit. The sensitivity of the probe is, like a standard multimeter, 20k/volt.

## SYSTEM OPERATION

The block diagram of Fig. 1 helps to explain the overall operation of the probe.

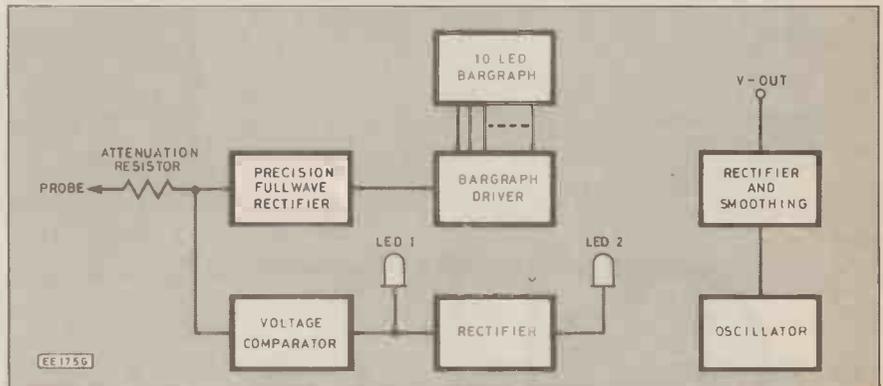


Fig. 1. Block diagram of the Voltage Probe.

An attenuation resistor at the input reduces the sensitivity of the unit to a suitable level. In practice there are actually two switched attenuation resistors which give the units its two ranges. The input signal is applied to a precision fullwave rectifier, and the purpose of this circuit is to give a positive output voltage regardless of the polarity of the input signal, so that the probe will respond to inputs of either polarity. This also makes the unit respond to a.c. as well as d.c. input signals. The output of the precision rectifier is coupled direct to the input of the bargraph driver, and as explained earlier, this is a ten i.e.d. logarithmic type.


In addition to the rectifier, the input signal is applied to a voltage comparator. This activates the polarity indicator i.e.d. if the input is negative of the earth rail. The output of the comparator connects to a rectifier circuit which drives another i.e.d., and with a d.c. input no current is fed to this i.e.d. However, with an a.c. input it is pulsed on at the input frequency, and assuming this frequency is a few tens of hertz or more it will appear to light up continuously.

The voltage comparator and precision rectifier stages require a negative supply rail. Rather than use two batteries to power the unit the negative rail is derived from the positive supply using an oscillator feeding into a rectifier and smoothing circuit.
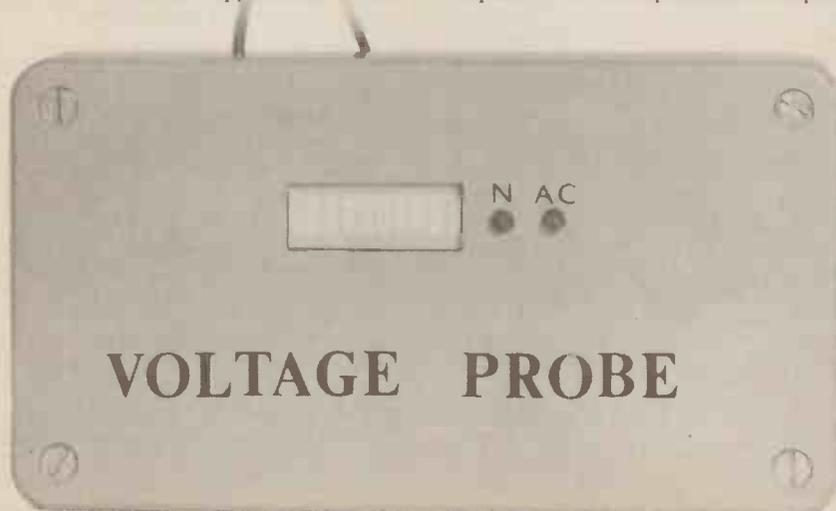
## THE CIRCUIT

Refer to Fig. 2 for the full circuit diagram of the Voltage Probe.

The voltage measuring circuit has an input impedance of 10k and a full scale threshold voltage of 1.2 volts. S1 is the



range switch, and attenuator resistors R1 and R2 nominally reduce the sensitivity by factors of 10 and 100 respectively. D1 to D6 form a bipolar clipping circuit that limits the input voltage to the precision rectifier to no more than about plus and minus 1.9 volts.

### ACTIVE RECTIFIER

A conventional fullwave precision rectifier based on dual operational amplifier IC1 is used, and this is really two half-wave circuits connected in parallel. IC1a

taken from the output of the rectifier. The effect of the negative feedback is to balance the two input voltages of the amplifier.

With a normal buffer stage the input signal is applied to the non-inverting input, and the feedback is taken direct from the output to the inverting input. The output therefore takes up the same potential as the input signal, and unity voltage gain buffering is obtained. In this case the feedback is taken via diode D8, but the same basic action occurs with the inverting input (and thus the output of D8)

The other section of the rectifier operates in what is essentially the same way, but the circuit is based on a unity gain inverting amplifier. A negative input signal therefore gives an identical output voltage that is positive in polarity, while a positive input gives a negative output that is blocked by D10.

C1 smoothes the output of the rectifier, and when using the unit with d.c. inputs this has no significant effect. It helps to give a clearer indication with a.c. signals though, and C1 then charges to the peak output voltage from the rectifier circuit.

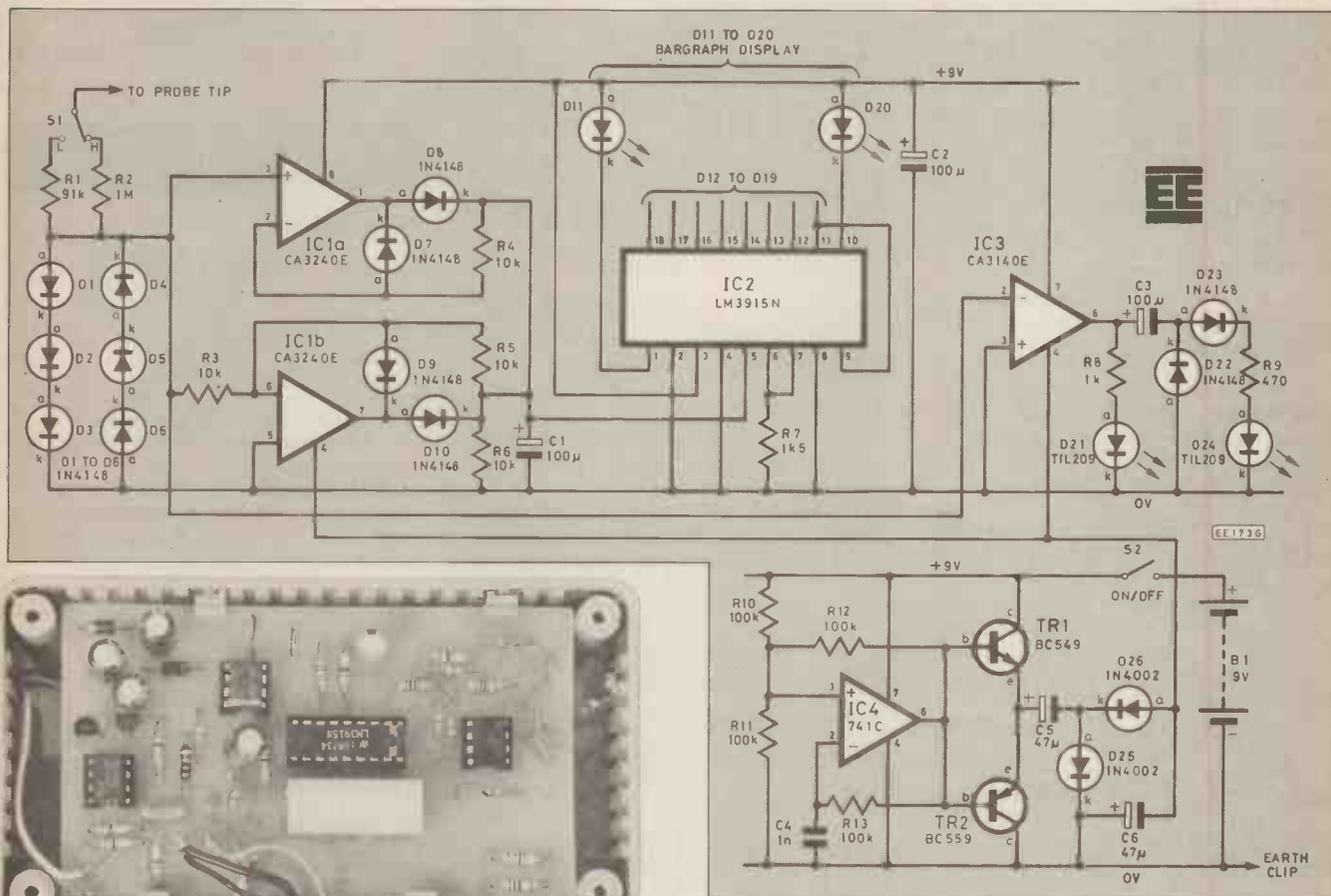


Fig. 2. Complete circuit diagram of the Voltage Probe.

The case lid removed revealing the circuit board, adaptors and guide rails.

handles positive inputs and IC1b handles negative ones. The purpose of using an active rectifier, rather than a simple passive type such as a bridge rectifier, is that the voltage drop through a passive rectifier would give very poor accuracy in this application, especially at the lower indication levels. An active rectifier uses negative feedback to overcome the non-linearity of semiconductor diodes.

If we consider IC1a first, this is virtually an ordinary unity voltage gain, non-inverting buffer stage followed by a diode which provides the rectification. There is an important difference in that the negative feedback is not taken direct from the output of IC1a, but is instead

being maintained at the same voltage as the input signal. There is a typical voltage drop of about 0.6 volts across D8, but the output of IC1a simply goes 0.6 volts more positive in order to counteract this and maintain the voltage balance at the inputs.

All this only applies if the input signal is positive. If it is negative D8 blocks any output current, and ensures that the required rectification is obtained. D7 then provides a negative feedback path and prevents the output of IC1a switching fully negative. This helps to give good high frequency performance, and the circuit will work well at frequencies of up to about 200kHz.

### BARGRAPH

The bargraph driver, IC2, is an LM3915. This is the logarithmic version of the popular LM3914 bargraph driver which will probably be more familiar to most readers. Fig. 3 shows the arrangement used in the LM3914/5 integrated circuits. A series of ten voltage comparators are used to drive the i.e.d. display, with each comparator driving one i.e.d. The inverting input of each comparator is fed with the buffered input signal, while the non-inverting inputs are fed with a series of reference voltages produced by a ten stage resistor network.

In normal use the lower end of the network (pin 4) is connected to earth and

the upper end (pin 6) is connected to the output of the internal 1.2 volt reference source. Each comparator has an output transistor which is switched on if the inverting input is at a higher voltage than the non-inverting input, or switched off if the comparative input levels are reversed. When switched on each output transistor switches on its l.e.d.

With zero input voltage all the output transistors will be switched off. Comparator 10 has the lowest reference voltage, and if the input potential is gradually increased the input voltage will eventually go above this reference level. The l.e.d. driven by comparator 10 is then activated. Comparator 9 has the next highest reference voltage, and when the input voltage exceeds this level the l.e.d. driven by this comparator would be activated. This process would continue until the input voltage exceeded 1.2 volts, at which point the tenth l.e.d. would be switched on. This gives a true bargraph display, with the number of l.e.d.s switched on depending on the input voltage.

## DOT MODE

The device contains some control logic that enables the "dot" mode to be selected instead, and in this mode no more than one l.e.d. is activated (the highest one that the input potential merits). In fact strictly speaking two l.e.d.s can be activated, since the LM3914/5 devices are designed so that in the dot mode one l.e.d. switches on before the next switches off as the transition is made from one threshold level to the next. This helps to avoid having an unstable display when the input voltage is close to a threshold level.

The 1.2 volt reference source forms part of a current generator circuit which controls the display l.e.d. current. A resistor between pins 7 and 8 is used to control this current, and the on current of each l.e.d. is about ten times the current through this resistor.

Returning to the circuit diagram, D11 to D20 are the display l.e.d.s, and in practice these are a proper bargraph display rather than ten individual l.e.d.s. R7 sets the l.e.d. current at about 8 milliamps. Pin 9 is coupled with pin 11 to set the device in the dot mode. This probably gives a slightly less clear display, but the bar mode would give an unacceptably high maximum l.e.d. current of some 80 milliamps and is not practical in this application.

IC3 is the comparator in the polarity indicator circuit, and D21 is the polarity l.e.d. C3, D22 and D23 rectify the output of IC3 and drive a.c. indicator l.e.d. D24 if an a.c. input signal is present.

The oscillator uses IC4 in a simple relaxation oscillator circuit, and TR1 plus TR2 are a complementary emitter-follower output stage which boost the output current capability of the oscillator. C5, D25, D26 and C6 rectify and smooth

the output of the oscillator to generate the negative supply rail.

The quiescent current consumption of the unit is approximately 12 milliamps, but this rises significantly when one or more l.e.d.s are activated.

## CONSTRUCTION

Details of the printed circuit board and wiring are provided in Fig. 4. IC1 and IC3 are MOS devices and should therefore be fitted in (8 pin d.i.l.) integrated circuit holders, as well as observing the other anti-static handling precautions. As IC2 is not one of the cheapest of devices it is advisable to use a socket for this one as well. It is essential to use a socket for the bargraph display as the holder is needed to raise the display to a suitable height above the surface of the

board. IC2 and the display require 18- and 20-pin sockets respectively.

Although the components are quite densely packed in parts of the board, con-



## COMPONENTS

### Resistors

R1	91k 0.4W 1%
R2	1M 0.4W 1%
R3,5	10k 0.4W 1% (2 off)
R4,6	10k (2 off)
R7	1k5
R8	1k
R9	470
R10,11,12,13	100k (4 off)
All 1/4W carbon 5% tolerance unless specified otherwise	

### Capacitors

C1,2,3	100µ 10V radial elect (3 off)
C4	1n carbonate
C5,6	47µ 16V radial elect (2 off)

### Semiconductors

IC1	CA3240E
IC2	LM3915N
IC3	CA3140E
IC4	741C
TR1	BC549
TR2	BC559
D1 to 10,	1N4148 (12 off)
22,23	10 l.e.d. bargraph display
D11 to 20	TIL209 (2 off)
D21,24	1N4002 (2 off)
D25,26	

### Miscellaneous

S1,2	d.p.d.t. miniature slider switches (2 off)
B1	9 volt (PP3 size) Plastic case about 120 x 65 x 40mm with four p.c.b. guide rail adaptors
25mm M3 screw and M3 fixing nut	
20 pin d.i.l. i.c. holder	
18 pin d.i.l. i.c. holder	
Three 8 pin d.i.l. i.c. holders	
Test prod (clip-on type) and lead	
Battery connector	
<b>Printed circuit board:</b> single-sided 100 x 62mm, EE PCB Service, code 8505-04	


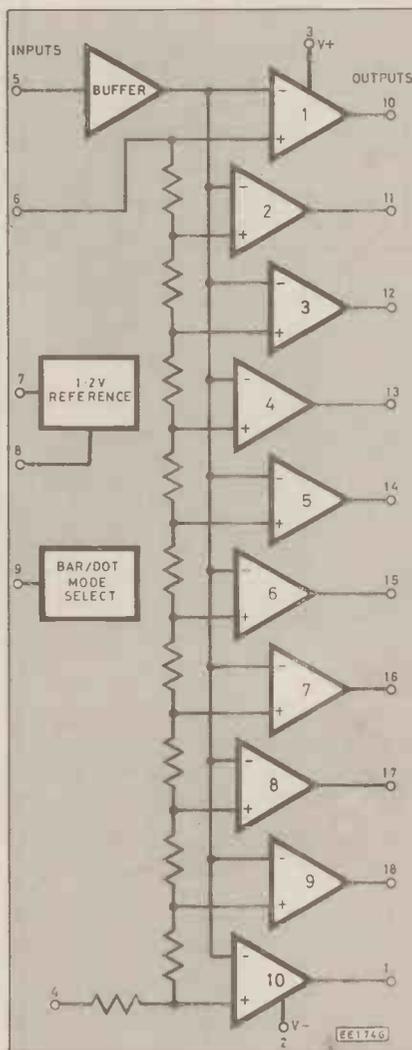


Fig. 3. Block diagram and pinning details of the LM3915N bargraph display integrated circuit.

Approx. cost  
Guidance only

**£14.50**

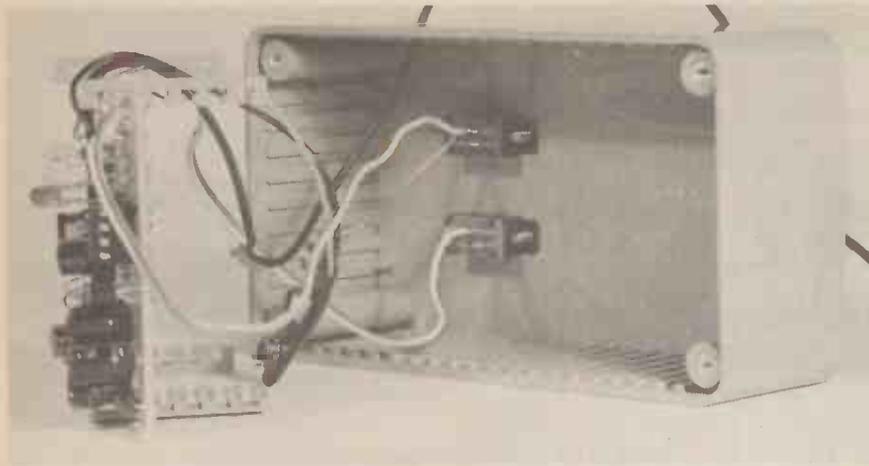

Circuit board slotted in the locating "pillars" prior to inserting in the case guide rails.


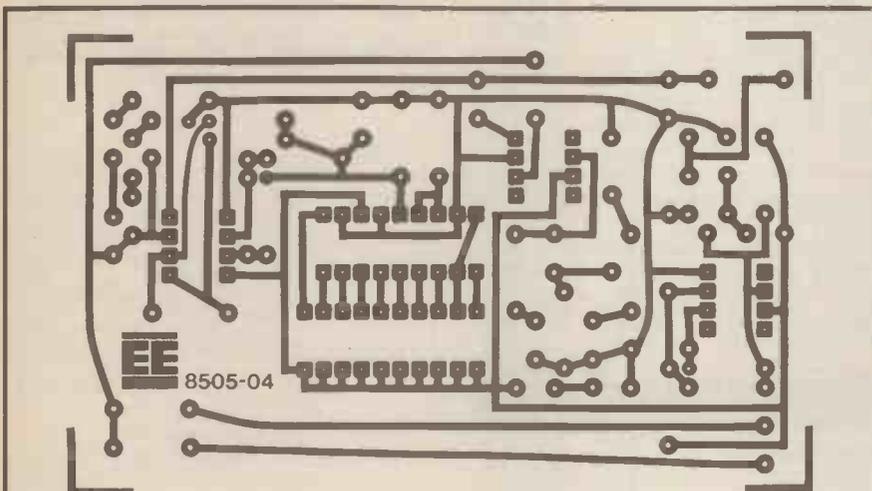


Fig. 4. Actual-size master pattern for the Voltage Probe. The component layout on the board topside and wiring to S1,S2,B1 and probe is shown below. This board is available from the EE PCB Service; order code 8505-04.

See  
**Shop  
Talk**  
page 256

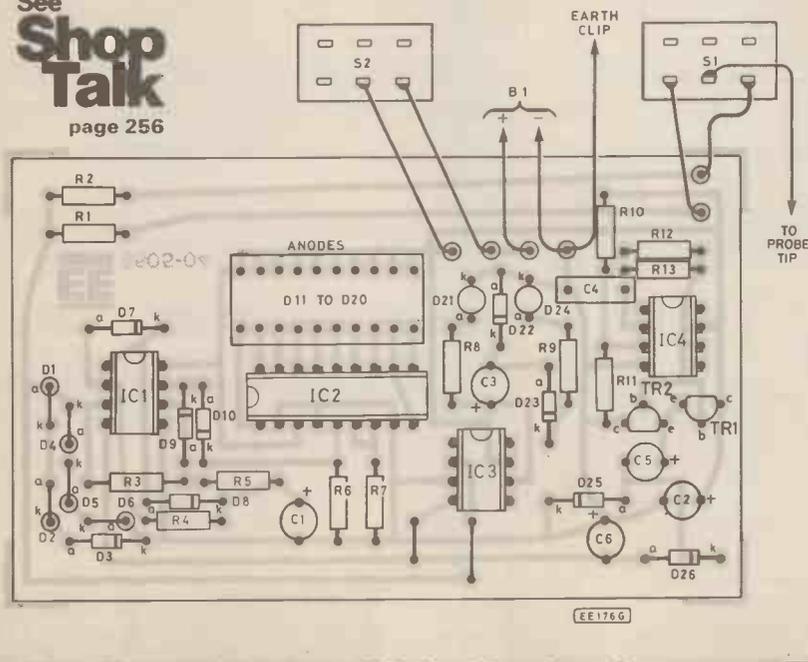

struction of the board should not be too difficult provided a soldering iron having a miniature bit is used, and the components are physically small types. In particular the capacitors must be printed circuit mounting types having a body length of no more than about 10 millimetres. L.e.d.s D21 and D24 are fitted on the board, and they should be mounted so that they protrude about 5 millimetres above the bargraph display.

### CASE DETAILS

A plastic case having approximate outside dimensions of 120 x 65 x 40 millimetres is used as the housing for this project. This is reasonably compact but is not so small that construction of the unit becomes excessively intricate and difficult. The printed circuit board is specifically designed to fit into this case, and it would be difficult to fit the unit into an alternative case without redesigning the printed circuit board. The case has moulded printed circuit guide rails, but the board is fitted to these via adaptors which may be supplied with the case, or might have to be purchased separately (depending on where the case is bought). The board is mounted well towards the top of the case, component side uppermost.

The lid of the case is drilled with two holes about 3.2mm to take D21 and D24. A rectangular cutout about 25 x 10 millimetres is also needed, and this acts as a display window. These must obviously be positioned accurately so that they properly match up with the l.e.d.s and display when the lid of the case is fitted in place. Probably the easiest way of making the rectangular cutout is to drill a hole about 8 millimetres in diameter and then file this out to the correct size using a miniature flat tapered file.

S1 and S2 are mounted on the rear panel of the case, and miniature slider switches are probably the neatest type to use in this application. A small exit hole for the lead to the earthing clip is drilled at any convenient point in the case. A probe tip of some kind is needed, and this can just consist of an M3 screw about 25 millimetres or more in length. This is mounted on the front panel of the case, and it is fitted with a soldertag on the inside of the case so that a connection can be easily made to it. A neater finish can be achieved by filing a round tip onto the screw, and by using a piece of PVC sleeving to insulate all but the tip.

When the completed unit is switched on it is likely that none of the l.e.d.s will light, although the polarity l.e.d. might do so since input might drift either side of the earth rail under no-input conditions. Connecting the unit to a few known voltages and trying both polarities in the case of d.c. sources, should confirm that it is functioning properly. When using the unit to gauge fairly high voltages, such as the mains supply, normal precautions to avoid electric shocks must, of course, be taken. □

# SHOP TALK



BY MIKE ABBOTT

## Aerosols!

This month, in our *Fault Finding* series we look at aerosols (among other things), so we have produced the accompanying chart as a guide to which vendors stock which aerosols.

The table is a generic guide to sprays, taking no account of specific brand names. The fire extinguishers are described as the types for use in kitchens and caravans. The Electro-value extinguisher contains 'arctons', and both aerosols featured in this guide are suitable for use on electrical fires once the power has been shut off.

Did you know that silicones travel? Thanks to investigations conducted by Electrolube in conjunction with British Telecom, evidence now exists to show that individual silicones, as used in household spray polishes, detach themselves and travel along surfaces over quite surprising distances. Once mobilised, they can get onto electrical contacts where arcing turns them into silicon carbide crystals. Result? Premature contact failure! The compass of

their mischief is greatly increased when they are airborne, so the moral of the story is: don't be too gung-ho with sprays containing silicones in the vicinity of open electrical contacts, such as relays and switches (sealed reed switches are safe). Even after the spray has settled silicones can travel.

In response to this discovery Electrolube produced a 'non-silicone' heat-sink paste, and is also looking at a formula for non-silicone polish. But alas it seems that glass and plastics just do not shine quite the same without those silicones. And as an Electrolube spokeswoman pointed out, even when people are made aware of the danger they prefer to take the risk, and go for a good shine. What do you clean your telephone with?

## CONSTRUCTIONAL PROJECTS

### Auto-Phaser

The *Auto-Phaser* comprises components available from general suppliers, such as **Magenta** and **Cricklewood**. A mechani-

cally robust switch should be chosen for S1. A suitable case is available in grey ABS plastic from **Magenta** (code ABS2), or in diecast alloy from **Maplin Electronics** (type M5005).

### Amstrad Amplifier

The Amstrad Amplifiers should present no buying difficulties. Different cases to the ones specified may be used, although in the smaller unit the p.c.b. is designed to slide in laterally. The mains switch on the larger unit need not be rotary, but a suitable rotary type can be purchased from **Cricklewood Electronics** (type RTYM). The **Maplin** 6VA transformer WB06G is ideal for T1, and the same supplier stocks dual log. 10k potentiometers (FX09K).

### Voltage Probe

The ten-stage bargraph display used in the *Voltage Probe* is available from **Maplin**, order code BY65V (red) or YG33L (green). There should be no problem obtaining components; suitable d.p.d.t. slide switches are found in the **Verospeed** catalogue.

### On Spec

The BPX65 photodiode featured in *On Spec* is available from **Watford Electronics** and costs £3.68. The 590KH temperature sensor is an RS Components device (No. 308 809), and may be obtained through **Ace Mailtronix Ltd.**, 26 Castle Rd., Wakefield, West Yorkshire WF2 7LZ. The VMOS f.e.t. VN66AF is available from **Rapid Electronics** and **Circuit** for around £1.25

### Caravan Indicator Control

The Caravan Indicator Control should not cause the constructor any component buying problems as there are no specialised parts involved.

Aerosol	Circuit	Electro-value	Green-weld	Maplin	Magenta	Marco Trading	Vero-speed
Antistatic (long term protection)		✓				✓	✓
Antistatic Dissipation Spray (water based)				✓			
Antistatic VDU Cleaner (harmless to antiglare coatings)				✓			
Contact Cleaner Lubricant (switch cleaner)	✓	✓	✓	✓		✓	✓
Contact Lubricant (high quality version)			✓	✓	✓		✓
Cleaner (p.c.b. flux remover)				✓			✓
Cleaner (video tape head)		✓		✓		✓	✓
Cleaner (tape drive equipment)				✓			✓
Cleaner (Ultracene is extra powerful, but will damage certain plastics)							✓
Contact Grease (extra adhesive for vertical surfaces)							✓
Conformal Coating (industry standard p.c.b. coating)							✓
Dry-Film Lubricant (colourless, non oily, ideal release agent)							✓
Electronic Cleaning/Degreasing Solvent (okay plastics/tape heads)	✓		✓	✓			✓
Freezer	✓	✓	✓	✓	✓	✓	✓
Foaming Cleaner (antistatic)	✓	✓	✓	✓		✓	✓
Fire Extinguisher (suitable electrical fires once power off)		✓	✓				
Graphite		✓	✓				
Lacquer (clear)	✓	✓		✓	✓	✓	✓
Moisture Repellent	✓	✓					✓
Oil (WD40 type)				✓			
Oil (clear, light, non-stain)				✓			✓
Polish				✓			
Silicone Compound (prevents arcing/leakage, and seals)	✓	✓		✓		✓	✓
Spray Duster (compressed inert gas)		✓		✓			
Silicone Lubricant (all materials)			✓				

# His weekdays are rewarding. His weekends even more so.

Working in telecommunications requires a great deal of skill and training and involves a lot of commitment.

Yet at the weekends some communications experts take on another equally demanding role. As Officers in the Territorial Army.

The training and selection processes are tough, but if you make the grade you'll have the satisfaction of applying your skills in a totally different field. As an Officer in the Royal Signals.

It's a serious undertaking.

The TA accounts for a third of the Army's strength, and in the event of war you would be commanding your men under battle

conditions alongside Regular Army units.

There's more than one way to earn a commission. Some people are selected to come in as potential Officers whilst others start as soldiers.

Your commitment will be at least 6 weekends and 2 weeks camp per year, plus some weekday evenings.

You'll be well paid for your time of course. But we think you'll find the real rewards lie in the camaraderie, team-work and sense of achievement that the TA experience gives you.

**Officer**  
**The Territorials** 



Find out more: If you are between 18 and 28 years of age and think you have the abilities we're looking for, complete the coupon and post it to Major Nigel Ley, (Dept. EEG), Duke of York's H.Q., Centre Block, Chelsea, SW3 4SG or contact your nearest TAVR Association. (We're in the phone book under 'Army').

Name \_\_\_\_\_  
Address \_\_\_\_\_  
Town \_\_\_\_\_ County \_\_\_\_\_ Age \_\_\_\_\_  
Educational Qualifications \_\_\_\_\_

# ON SPEC

*a regular feature for the Spectrum Owner...*

by Mike Tooley BA

LAST MONTH we showed how a simple input interface for the Spectrum could be built using only three commonly available TTL gates. This month we shall turn our attention to some practical applications of the interface in the field of monitoring light and temperature levels.

## Sensors

Light levels can be easily sensed using a simple photodiode/VMOS f.e.t. arrangement similar to that shown in Fig. 1a. Almost any type of photodiode can be used in this circuit; however, it should be noted that, as with most silicon photodetectors, the spectral response peaks in the infra-red region and thus such circuits may not appear to be particularly sensitive under low levels of room lighting.

In any event, a pre-set resistor, VR1, is provided as a means of adjusting the threshold of the sensor (i.e. the level of light at which the circuit changes the logical state of its output). The circuit can thus only differentiate between "light" and "dark"—its state being detected by simply reading the status of the appropriate input port.

In applications where only a single sensor is required, the output of the sensor may be connected to any one of the input channels of the input interface. In such cases, the remaining channels are simply left unconnected (in which case they will all revert to logic 1). A simple test routine for printing the status of a sensor connected to channel D is shown below:

```
100 REM Indicates whether a photosensor connected
105 REM to channel D is in light or darkness
```

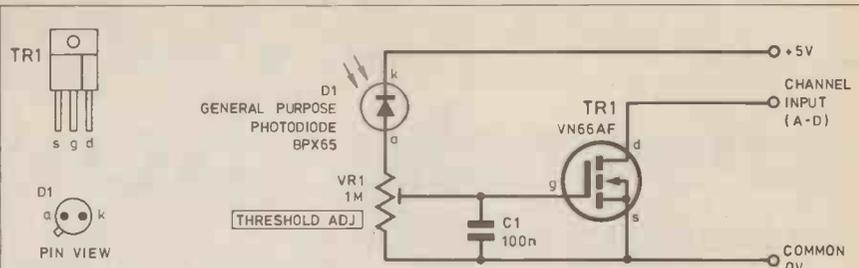


Fig. 1a. Circuit diagram of the light sensor.

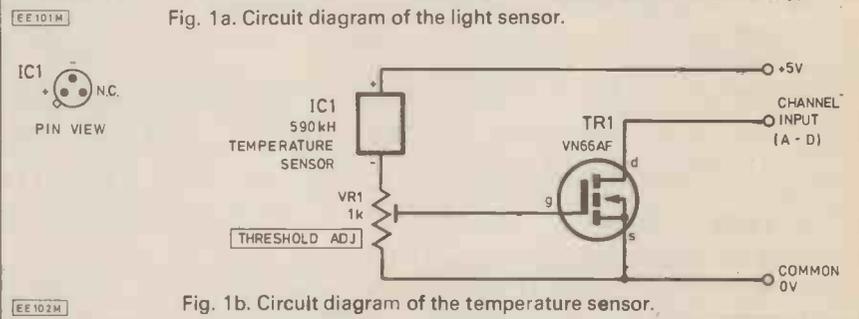


Fig. 1b. Circuit diagram of the temperature sensor.

```
110 PAUSE 10
120 LET d=IN 255
130 IF d=255 THEN PRINT AT 0,0;
"Dark "
140 IF d=254 THEN PRINT AT 0,0;
"Light"
150 GO TO 100
```

To provide an audible warning of darkness, line 130 should be modified as follows:

```
130 IF d=255 THEN PRINT AT 0,0;
"Dark ":BEEP 1,25
```

If it is necessary to provide several levels of light discrimination (e.g. "daylight", "twilight" and "darkness") it is, of course, possible to have more than one sensor, each connected to a different interface input channel. The threshold level of each circuit may then be adjusted for an appropriate level of illumination whilst the status of the input lines can be read and interpreted as a particular range of illumination.

A simple temperature sensing arrangement is shown in Fig. 1b. Here, a two terminal semiconductor temperature sensor is used to replace the photodetector of Fig. 1a. Note, however, that the value of the threshold adjusting potentiometer, VR1, should be changed from 1Mohm to 1kohm. Furthermore, the gate decoupling capacitor is no longer required.

Like its light sensing counterpart, this circuit can only discriminate between two levels of input (in this case "hot" and "cold"). Later we shall show how an analogue-to-digital converter interface can provide a somewhat more sophisticated means of measuring, displaying and recording both temperature and light levels.

## The Spectrum Signal Generator

To round of this month's instalment of *On Spec*, we are going to show how the Spectrum can, with some very simple software, be used as a programmable signal generator with an accuracy of typically better than 0.15 per cent. This provides a square wave output having a typical rise time of less than 1 microsecond over the range 10Hz to 10kHz in steps of 1Hz.

The frequency and number of output cycles must both be entered from the keyboard and these parameters are displayed together with the duration whilst the output signal is generated. Thereafter, the user is given the option of restarting with new parameters, repeating the same signal again, or exiting from the program.

The output signal is derived from the cassette port (marked "MIC") and

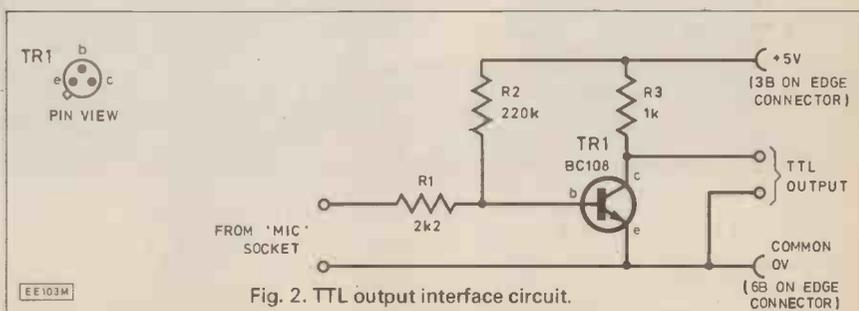


Fig. 2. TTL output interface circuit.

```

10 REM Signal generator
20 REM Everyday Electronics - April 1985
30:
40 REM Set up machine code
50:
60 CLEAR 32499: POKE 23658,8
70 DATA 237,91,244,126,42,246,126,205,181,3,201
80 FOR i=32504 TO 32514
90 READ xi
100 POKE i,xi
110 NEXT i
120:
130 REM Input prompts and calculations
140:
150 BORDER 1: CLS
160 PRINT AT 6,8; BRIGHT 1;"Signal Generator"
170 PRINT AT 17,6; FLASH 1;"Input desired values"
180 PRINT AT 18,6; FLASH 1;"followed by <ENTER>"
190 INPUT TAB 6;"Frequency ? ";frequency
200 IF frequency <10 OR frequency>10000 THEN BEEP .5,-20: GO TO 190
210 INPUT TAB 6;"Number of cycles ? ";nocycles
220 IF nocycles<1 OR nocycles>65535 THEN BEEP .5,-20: GO TO 210
230 LET tc=(1/frequency)-.000068
240 LET tn=(3500000#tc)/8
250 LET th=INT (tn/256)
260 LET tl=tn-(th#256)
270 LET dh=INT ((nocycles-1)/256)
280 LET dl=(nocycles-1)-(dh#256)
290:
300 REM Display parameters and call machine code routine
310:
320 PAPER 4: CLS
330 PRINT AT 4,2;"Frequency = ";frequency;" Hz"
340 PRINT AT 5,2;"Number of cycles = ";nocycles
350 PRINT AT 6,2;"Duration = ";(nocycles/frequency);" seconds"
360 POKE 32500,dl: POKE 32501,dh
370 POKE 32502,tl: POKE 32503,th
380 RANDOMIZE USR 32504
390 PRINT AT 18,4; FLASH 1;"Press any key to continue"
400 PAUSE 0
410:
420 REM Exit/again/re-start routine
430:
440 PAPER 5: CLS
450 PRINT AT 4,8;"<A> = again"
460 PRINT AT 5,8;"<R> = restart"
470 PRINT AT 6,8;"<E> = exit"
480 PRINT AT 18,8; FLASH 1;"Key your choice"
490 PAUSE 0
500 LET r%=INKEY%
510 IF r%="A" THEN GO TO 320
520 IF r%="R" THEN GO TO 130
530 IF r%="E" THEN NEW
540 GO TO 500

```

Signal generator program listing for use with 16k or 48k Spectrum.

All contributions to *On Spec* should be sent to the following address and not to the Editorial Offices:

Mike Tooley,  
Department of Technology,  
Brooklands Technical College,  
Heath Road, WEYBRIDGE,  
Surrey, KT13 8TT

appears a.c.-coupled as a square wave of approximately 3V p-p. This should be adequate for many purposes (including equipment calibration), it being simply necessary to connect the output to a 10k potentiometer in order to provide a means of adjustment of the output level. The output signal can also be heard from the Spectrum's own internal loudspeaker.

For driving TTL circuitry, the simple interface shown in Fig. 2 may be employed. This not only improves the shape of the square wave produced but also provides a fully TTL-compatible output of approximately 5V p-p. The transistor may conveniently derive its supply from the regulated 5V d.c. rail available at the expansion connector provided at the rear of the Spectrum.

The complete listing of our signal generator program is given, and this should be reasonably self-explanatory. However, the following points should be noted:

#### Line 60

First protects the area of memory in which the machine code module is placed and then forces upper case input from the keyboard.

#### Lines 70-110

Loads the machine code from the data statement of line 70.

#### Lines 150-220

Displays the title and then prompts the user for the required input parameters. Out of range inputs are detected and an audible warning is issued before the user is prompted again.

#### Lines 230-280

Calculates values to be "poked" into reserved memory for later use by the machine code module.

#### Lines 320-380

Displays the current parameters used by the program before calling the user routine. It should be noted that this routine, in turn, calls a routine which is resident in the Spectrum's ROM.

#### Lines 390 and 400

Awaits a key depression from the user before clearing the screen and re-displaying the menu.

#### Lines 440-540

Displays a menu inviting the user to select one of three options: providing the same signal again, restarting with new parameters, or exiting the program. This last option clears the program and variables from memory.

**NEXT MONTH: A simple four-channel output interface—see you then!**

# AUTO PHASE

R.A.PENFOLD



**M**OST phasers have either a foot pedal so that the effect can be controlled manually, or use an oscillator to provide a cyclic phasing effect. This unit does not use either of these methods, but instead uses an envelope following technique, so that the phasing effect varies in sympathy with volume of the processed signal. This gives an interesting variation on the more common phasing effects.

The unit was designed primarily for use with a synthesiser, but it should operate properly with practically any electric or electronic instrument. However, phasing effects are always most effective with a signal that contains a broad spectrum of frequencies, such as pulse and sawtooth waveforms, or a "fuzzed" guitar. It can be adjusted to accommodate a wide range of input signal levels. See block diagram of Fig. 1.

## OPERATION

The phasing effect is generated using a notch filter, or multiple notch filter, with the notch frequency or frequencies swept up and down the audio spectrum. There are two basic, and similar, methods commonly used to produce this effect. One is to use a delay line, with the delayed and non-delayed signals being mixed at the output of the circuit. The delay results in signals at some frequencies being in-phase, so that they add together to produce a strong output from the mixer, while at other frequencies they are out-of-phase, and have a cancelling effect on one another. If the signals are balanced at the mixer, at some frequencies the two signals will precisely cancel out one another to produce the required deep notches of attenuation. The slight peaks in the

## PHASE CONTROLLED BY AMPLITUDE

response caused by the in-phase signals adding together are not of great importance, and do not contribute significantly to the effect. Of course, the notches must be swept up and down in frequency, and this is achieved by varying the delay time (easily done with practical delay lines).

This system provides excellent results, but has the disadvantage of the relatively high cost of the delay line, plus the problems that are inherent in circuits of this type. Most phasers therefore use a slightly simplified arrangement where the delay line is replaced with a series of phase shift circuits. The circuit featured here is in this second category, and Fig. 1 shows the block diagram of the unit.

The buffer stage at the input is needed to ensure that the instrument connected to the input is loaded by a suitably high impedance, and that the subsequent stages of the phaser are fed from an adequately low source impedance. The two phase shifters each provide a phase shift that varies from 180 degrees at low frequencies to zero at high frequencies. The effect of the two in series is to provide a total phase shift that varies from 0 to 360 degrees. Therefore, at a certain frequency the phase shift will be 180 degrees, and

the circuit will invert the input signal. The mixer at the output combines the phase shifted and unprocessed signals, and at the frequency where the 180 degree phase shift is produced the two signals cancel one another out so that a notch is produced in the frequency response of the circuit.


For this system to operate properly it is essential to be able to vary the frequency at which the 180 degree phase shift occurs, and in practice the phase shifters are voltage controlled circuits so that the notch frequency can be varied by means of a control voltage. Two phase shifters provide just one notch, but more notches can be produced by using more phase shifters (two per notch are required). Phasers normally have two or three notches, but with the envelope following type of phaser featured here there was found to be little advantage in using more than one notch, and the final design is therefore of the single notch variety.

In order to produce the envelope following action some of the input signal is first amplified, and then fed to a rectifier and smoothing circuit. This gives a d.c. control voltage which is roughly proportional to the input signal level, and this is used as the control voltage for the phase shifters. The circuit is arranged so that the frequency of the notch rises and falls in sympathy with the amplitude of the input signal. This gives a better effect than the alternative of having the notch frequency fall as the input level rises.

## PHASE SHIFTER

The basic circuit of a phase shifter is shown in Fig. 2. At low frequencies C1 has a very high impedance, and can be ignored. The circuit then operates as a standard inverting mode operational amplifier stage with R1 and R2 setting the closed loop voltage gain, and R3 biasing the non-inverting input. The voltage gain

Fig. 1. Block diagram. Once switched on, phasing is controlled exclusively by signal amplitude.

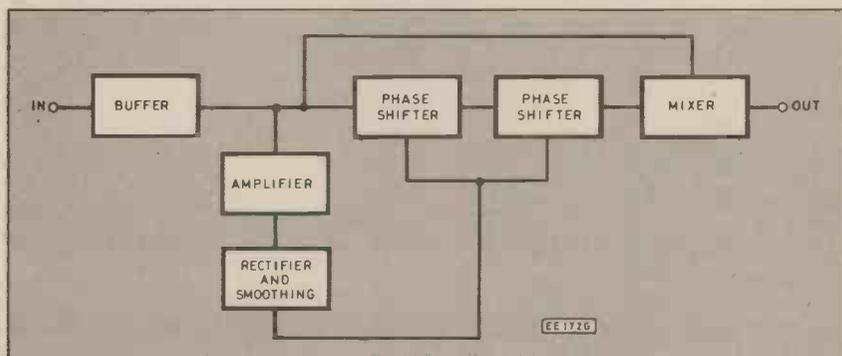

is equal to R2 divided by R1, and in this application these two resistors are made equal in value so that the circuit has unity voltage gain.

At high frequencies the impedance of C1 is negligible in comparison to the resistance of R3, and the input signal is coupled straight through to the non-inverting input of the operational amplifier, which consequently operates in the non-inverting mode. Normally, the voltage gain in this mode would be equal to R1 plus R2, divided by R2, or two times if R1 and R2 have the same value. However, the left-hand end of R1 would normally be connected to earth rather than the input signal, and this modified arrangement results in the circuit having unity voltage gain.

The circuit thus always has unity voltage gain, but gives a phase shift which varies from 180 degrees at low frequencies through to zero at high frequencies. Somewhere between these two extremes a 90 degree phase shift is obtained, which gives the required 180 degree phase shift from two of these circuits connected in series. The frequency at which the 90 degree shift occurs depends upon the relative values of C1 and R3, and this frequency can be varied by altering the value of either of these. In practice, it is much easier to vary the value of R3, which is replaced by a field effect transistor connected as a voltage controlled resistor.

IC1b and IC2a are used as the basis of the two phase shifters, and these use precisely the same configuration as the one described earlier. The field effect transistors used here as the voltage controlled resistors are n channel m.o.s.f.e.t.s from a CMOS 4007UBE device. This contains two complementary pairs plus an inverter, but in this case it is only the n channel m.o.s.f.e.t. of each complementary pair that is utilized, and the other parts of the device are ignored. These transistors are enhancement types, which means that they are normally switched off, and a forward bias is needed to bring them into conduction. This is the opposite of junction gate field effect transistors (such as the popular 2N3819, etc.), which are depletion mode devices. These are normally in the on state, and require a reverse gate bias in order to switch them off. In this application, enhancement mode f.e.t.s are slightly easier to use, and of more importance, they give more predictable results. R6 and R9 are needed to maintain a small bias to the non-inverting inputs of IC1b and IC2a when the m.o.s.f.e.t.s are switched off.

The mixer stage uses IC2b as a standard operational amplifier summing mode mixer. VR1 is adjusted to balance the two input signals to the mixer so that a deep notch and the strongest possible

effect are obtained. S1 can be used to switch out the phase shifted signal. The unit then acts as a simple buffer amplifier, and the phasing effect is switched off. In practice, S1 is a foot-operated switch so that the effect can be switched in and out while playing.



Some of the output from IC1a is coupled to variable attenuator VR3, and then to a high gain common emitter amplifier built around TR1. The output from TR1 is coupled by C9 to the rectifier and smoothing circuit. This has circuit values which give quite fast attack and decay times so that the filter accurately follows rises and falls in the input signal level. The positive d.c. signal produced by the rectifier/smoothing circuit is coupled direct to the gates of the two m.o.s.f.e.t.s. VR2 is adjusted so that under quiescent conditions the bias voltage fed to the m.o.s.f.e.t.s is just below the turn-on threshold so that the minimum filter frequency is obtained. The output from the smoothing circuit adds to this voltage so that the filter is swept up and down in frequency as the input signal rises and falls in volume, giving the required auto-phase effect. In practice, if desired, VR2 can be adjusted for a somewhat higher voltage so that the filter only operates over higher audio frequencies.

## THE CIRCUIT

The full circuit diagram of the *Auto Phase* unit is shown in Fig. 3.


The circuit is powered from a single 9 volt supply, but R1, R2 and C2 are used to give a centre tapping on the supply lines. IC1a is the input buffer stage, and this is a conventional operational amplifier non-inverting, unity voltage gain amplifier. R3 biases the non-inverting input of IC1a and sets the input impedance of the circuit at 100k.

Fig. 2. Typical phasing circuit.

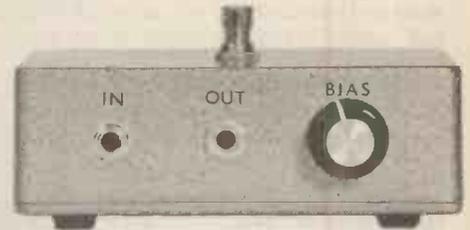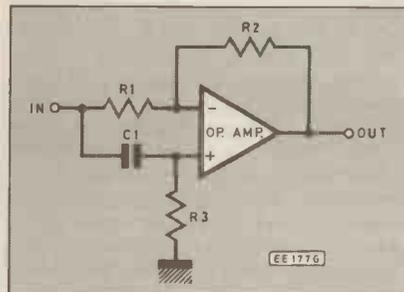

SET A MOBILE NOTCH LOOSE  
AMONG YOUR HARMONICS

Fig. 3. Circuit diagram. The inputs to IC3 (pins 3 and 6) are connected to each other and to R14.

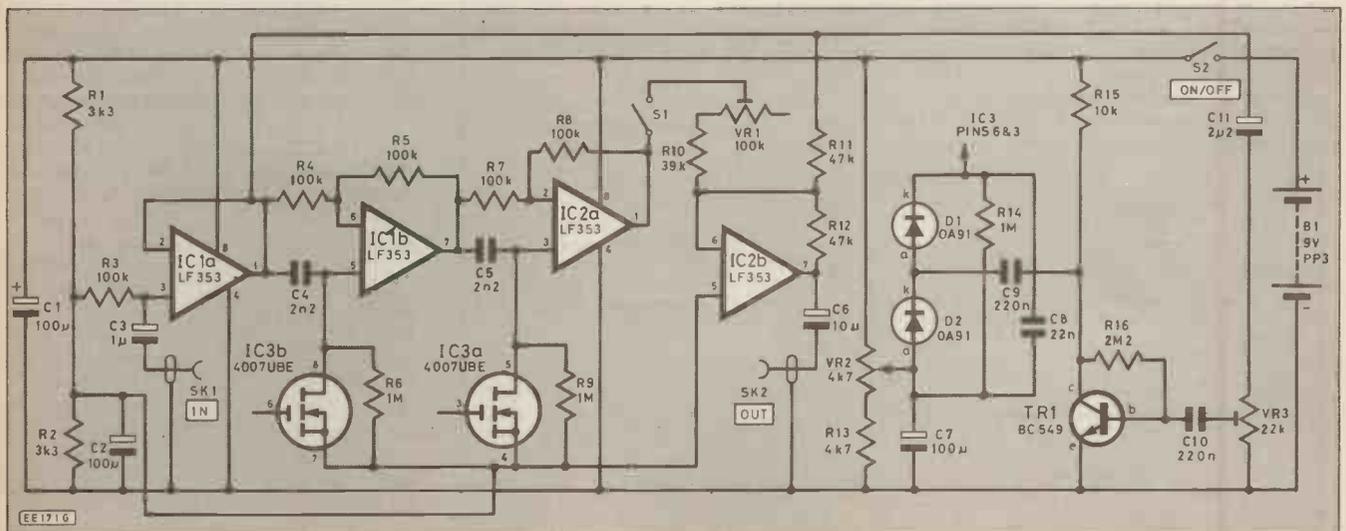

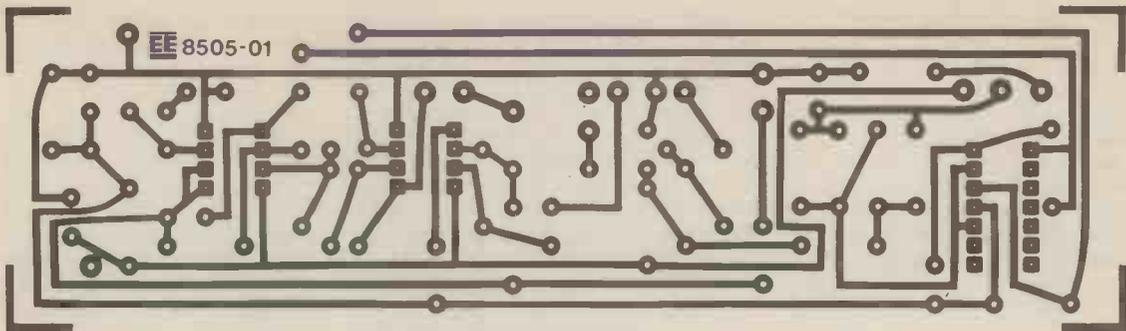


Fig. 4. P.c.b. layout.

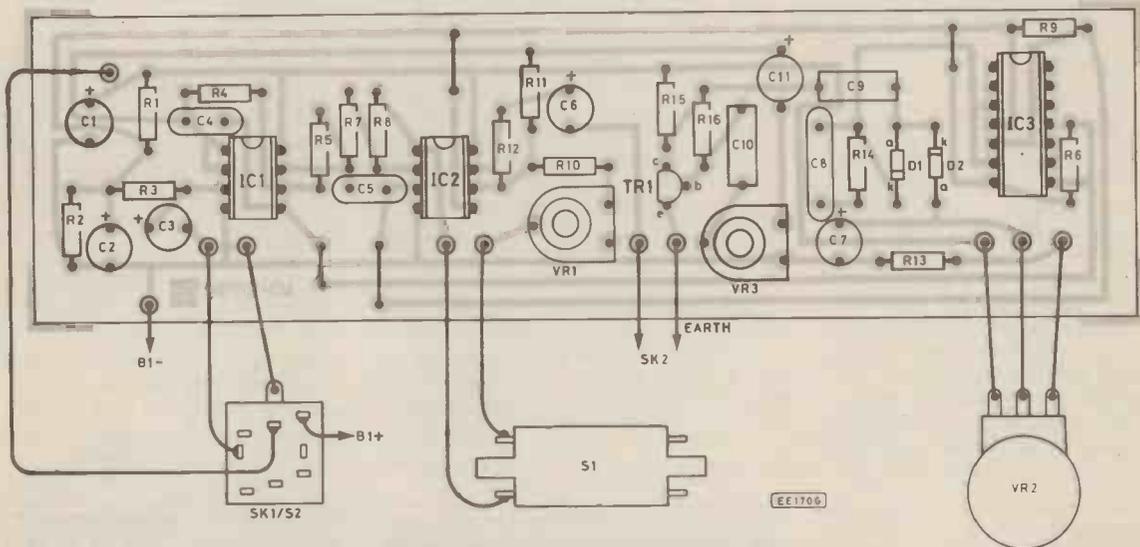


Fig. 5. Component layout of the Auto Phaser.

## COMPONENTS

Approx. cost  
Guidance only

£12

See  
**Shop  
Talk**  
page 256

### Resistors

R1,2	3k3 (2 off)
R3,4,5,7,8	100k (5 off)
R6,9,14	1M (3 off)
R10	39k
R11,12	47k (2 off)
R13	4k7
R15	10k
R16	2M2
All 0.25W 5% carbon film	

### Potentiometers

VR1	100k 0.1W horizontal preset
VR2	4k7 lin. pot
VR3	22k 0.1W horizontal preset

### Capacitors

C1,2,7	100µF 10V radial elect (3 off)
C3	1µF 63V radial elect

C4,5	2n2 mylar
C6	10µF 25V radial elect
C8	22nF polyester
C9,10	220nF carbonate
C11	2µ2 63V radial elect

### Semiconductors

IC1,2	LF353 (2 off)
IC3	4007BE
TR1	BC549
D1,2	OA91 (2 off)

### Miscellaneous

SK1	Standard jack with DPDT contacts
SK2	Standard jack
S1	Heavy duty push button switch
S2	Part of SK1
B1	9 volt (PP3 size)
Printed circuit board, control knob, diecast aluminium box about 150 x 80 x 50mm, two 8 pin d.i.l. sockets, 14 pin d.i.l. socket, PP3 battery connector, cabinet feet, Veropins, wire, solder	

## CONSTRUCTION

A diecast aluminium box measuring 150 by 80 by 50mm will comfortably accommodate all the components, and is suitably tough for this application. VR2 and the two sockets are mounted on the front panel, with S1 fitted on the lid of the case. S1 is a heavy-duty push-button type suitable for foot operation. S2 is a pair of make contacts on SK1 (which actually has d.p.d.t. contacts), so that the unit is automatically switched on and off when the jack plug is inserted in and removed from the input socket. This is a common way of providing on/off switching in musical effects units, but a separate on/off switch can, of course, be used if preferred.

Details of the printed circuit board and wiring are shown in Fig. 5. This is fairly easy to construct, but bear in mind that IC3 is a CMOS device. It should, therefore, be mounted in a (14-pin d.i.l.) i.c. socket, and the normal m.o.s. handling precautions should be taken. Do not overlook the four link wires. D1 and D2 are germanium diodes, and as such are more easily damaged by heat than the more familiar silicon devices. When connecting these, complete each soldered

joint as rapidly as possible so that overheating and damage to these components is avoided. Pins are fitted to the board at the places where leads from off-board components will eventually be connected.

The completed printed circuit board fits into the set of guide rails nearest the rear of the case, with the component side facing forward. The point-to-point wiring is then added, using ordinary multi-strand, p.v.c. insulated connecting wire.

## IN USE

It is essential for the three potentiometers to be set correctly if the unit is to function properly. VR1 should be set at almost minimum value (adjusted almost fully clockwise), and the unit should then give a reasonably deep notch and a strong effect. When the other two potentiometers have been adjusted properly, VR1 can be adjusted to optimise the effect.

With VR3 fully backed off (adjusted fully anti-clockwise) it should be possible to manually control the filter frequency using VR2. Set VR2 to place the notch at a fairly low audio frequency. Playing an instrument connected to the input of the unit, and then slowly advancing VR3 should gradually introduce the auto-phase effect. It is essential that VR3 is not advanced too far, or the sweeping of the filter will only occur at the very beginning



and end of each note, giving an effect that will probably be barely noticeable. The filter should only just be fully swept by a signal which achieves full volume at its peak level. When using an instrument that

has a high output level, VR3 will need to be almost fully backed-off. The unit will operate with lower level signals, such as the output from a low output guitar pick-up, with VR3 well advanced. □

# PREPARE FOR TOMORROW'S WORLD, TODAY!

An understanding of electronic and computer technology is fast becoming a vital part of today's living. Take out an annual subscription and have

**EVERYDAY ELECTRONICS & COMPUTER PROJECTS** delivered direct to your door every month...

## SUBSCRIPTION RATES

U.K. £12.00  
Overseas £15.00

**COMPLETE AND POST THIS ORDER FORM TODAY!**

## EVERYDAY ELECTRONICS and computer PROJECTS

## SUBSCRIPTION ORDER FORM

Annual Subscription Rates	
U.K.	£12.00
Overseas	£15.00
(Students: deduct £1 and quote Student number)	

Complete this form and post it, with payment or credit card authorisation to:  
**Everyday Electronics**  
Subscription Dept.  
Oakfield House,  
35 Perrymount Road,  
Haywards Heath,  
West Sussex RH16 3DH

POST COPIES TO:

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

POST CODE: \_\_\_\_\_

I enclose my cheque/P.O. payable to IPC Magazines Ltd. for £ \_\_\_\_\_  
Charge my credit card A/C at quoted rate



Card valid from: \_\_\_\_\_ to \_\_\_\_\_

Signature \_\_\_\_\_ **21**

# MULTIMETERS buyer's guide MULTIMETERS

**T**HE MULTIMETER is without doubt the most versatile and commonly used piece of test equipment available and, for the hobbyist, it usually represents the first major investment in serious electronic testing or construction.

There are hundreds of models available with a massive choice of specifications, prices and formats, so to help you through the 'multimeter jungle', we have compiled this guide. Obviously it is not a comprehensive coverage of all the models available but at least it will put you on the right road.

Before looking at specific models, we will take a look at various aspects, advantages and disadvantages of the different types and try to explain the meaning of manufacturers' specifications.

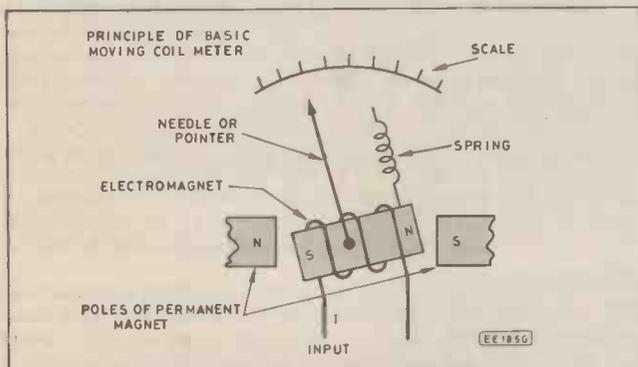


Fig. 1. The basic moving coil mechanism.

Modern multimeters, whatever their shape or size, all work on much the same principle. Whether electro-mechanical or electronic, digital or analogue, the heart of any meter is a voltage or current sensing device. This device together with a range selection circuit can be used to offer a wide range of measurements.

## TYPES OF METER AVAILABLE

Moving coil meters are still very common today despite increasing competition from low cost digital electronic meters. Indeed many engineers and technicians still prefer and 'trust' the traditional instruments which have been around for years.

The heart of the meter is a d'Arsonval movement or galvanometer which is an electromechanical device consisting of a coil of wire wrapped around an iron core, and mounted between the poles of a permanent magnet. A needle or pointer is attached to the coil, which is pivoted and free to rotate. Subsequently, when an electric current is

passed through the coil, the coil will rotate causing the needle to be displaced; the displacement being proportional to the current. (See Fig. 1.)

With a suitable scale placed adjacent to the pointer, the meter becomes an effective current meter and with modifications can be made to read a wide variety of ranges.

The forerunner of the modern electronic multimeter was the vacuum tube voltmeter (VTVM) which was essentially a valve amplifier circuit used to drive a moving coil meter. Of course in modern multimeters valves are replaced by transistors and integrated circuits to perform the sensing and amplifying function. Additionally analogue to digital converters are employed to drive alphanumeric digital displays rather than traditional moving coils. (See Fig. 2.)

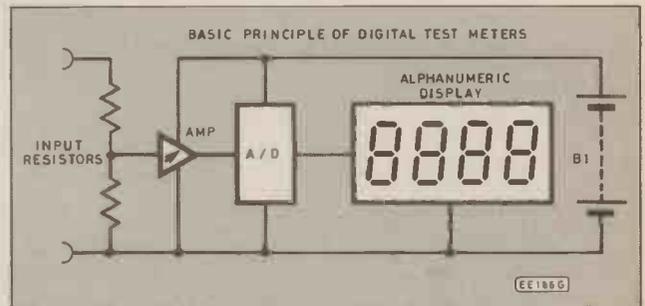


Fig. 2. Basic elements of a digital multimeter.

## SHUNTS AND MULTIPLIERS

As we have said, the basic meter can be expanded by the introduction of additional circuitry. Suppose for example a device will give a maximum reading when it detects a current flow of 1mA. In the case of the moving coil device a maximum reading occurs when the needle is deflected to its furthest position, full scale deflection (f.s.d.); in the case of a digital display (say four digits) then it would read 9999. Now if we want to measure a current of 10mA f.s.d., then a resistor is connected in parallel with the meter, the value of resistor being one ninth that of the meter. By application of Ohms law it can be seen that only one tenth of the total current would pass through the coil, whilst most of the current would pass through the SHUNT, as shown in Fig. 3.

To take voltage readings (Fig. 4) a series resistor can be connected in the meter circuit. Using the same example as before, we require only 1mA to give f.s.d. Thus if we, for example, wish to measure a voltage up to 10V, then by using Ohms law we can see that the series resistor (multiplier) should be:—

$$10V/10mA=1000\Omega$$

Because the resistance of the meter coil is negligible compared with that of the multiplier it can be ignored for these simple calculations, however in practical designs it must be accounted for.

For resistance measurements an independent power source is required which usually takes the form of one or more batteries. This is connected in series with the meter and the resistance to be measured completes the circuit. Obviously the current flow will be inversely proportional to the resistance and thus the resistance can be measured using a suitable scale. (See Fig. 5.)

Using these principles, a large number of resistance voltage and current measurements can be made with the aid of a switch and resistor

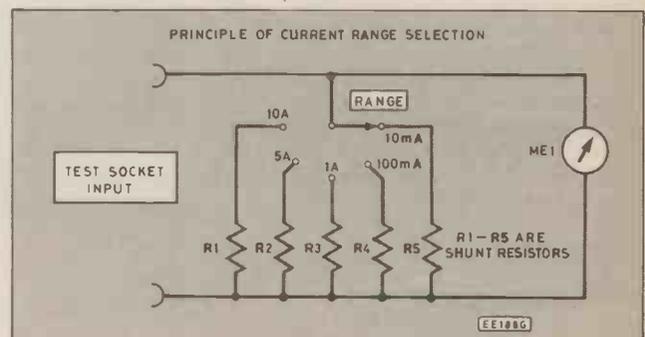


Fig. 3. Simple current measuring circuit.

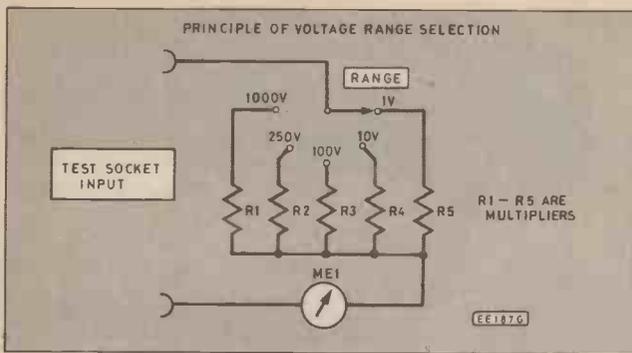


Fig. 4. Simple voltage measuring circuit.

network. For electronic multimeters different ranges are achieved using a combination of this type of network and an electronic circuit to provide amplification or attenuation of the measured signal.

### SENSITIVITY

Now that we have established the very basic principles of how multimeters work, we can start to look more deeply at manufacturers' specifications. One of the most important of these being the sensitivity or input impedance.

The sensitivity of a moving coil meter is given in terms of ohms per volt. In simple terms this figure refers to the resistance of the multiplier required to give an f.s.d. of one volt. Suppose the sensitivity is 1000 ohms per volt then to measure on a scale of 100 volts f.s.d., the input impedance would be 100k ohms.

It is desirable for the sensitivity of a meter to be very high to prevent a loading effect on the circuit under test. For example if we use a meter with a sensitivity of 10k ohms per volt to measure a voltage across a resistance of 1M ohm, then the actual meter reading will be incorrect.

Referring to Fig. 6 it can be seen that when the meter is connected in parallel with the 1M ohm resistor, then the effective resistance becomes less than 100k ohms. This will cause more current to be drawn from the circuit which in turn will cause a greater volt drop across  $R_x$ . From this it can be seen that the error caused by the loading effect will be decreased by an increase of sensitivity.

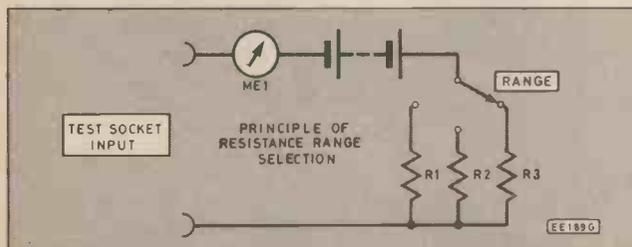


Fig. 5. Resistance measuring principles.

With normal moving coil meters the input impedance obviously varies depending on the scale. The higher the f.s.d., the higher the input impedance. However, with the electronic multimeters, the input impedance is often constant throughout the range, due to the nature of the input circuitry, which is usually a high impedance f.e.t. device.

Moving coil multimeters have a sensitivity of between about 1k ohm per volt to 100k ohms per volt whereas an electronic multimeter can have an input impedance of 10M ohm throughout the range.

Current measurements are also affected by sensitivity. It is desirable that the resistance of the meter be as small as possible when measuring current. If the resistance is high then a volt drop will be introduced into the circuit and the current will be limited by the meter resistance, and once again incorrect readings will be the result. If a meter has a large sensitivity then it also implies that the resistance when measuring current will be low.

### METER SCALES AND DISPLAYS

As was mentioned earlier many engineers and technicians still prefer moving coil displays. With these types it is possible to see fluctuations in voltage readings whereas in the case of digital displays a fluctuating

voltage may appear as a number of random voltages. This depends on the type of sampling circuit used in the meter and the frequency of the signal being measured.

The main advantage of digital displays is in the ease of reading and understanding the display. Digital meters usually have auto polarity sensing (it tells you when the test leads are the wrong way round), and a clear numerical reading together with the units indication. Most multi-range, moving coil instruments have several scales only one of which is relevant on a particular range. On top of this they have to be read from the correct angle or a parallax error will be caused. Also some of the scales on moving coil meters are not linear such as the resistance or decibel range.

### PROTECTION

Protection of the electronics or the moving coil is very important as they can be easily damaged by excess voltages or currents. For this reason many meters have overload protection of some kind, such as fused inputs, 'crowbar' or circuit breaker protection. These protection facilities are usually specified as maximum voltage or current ratings. Some meters have polarity reversal protection which is very useful as it is very easy to connect the leads the wrong way round.

As well as protecting the meter it is important to protect the user. As some meters are capable of testing thousands of volts or many amps, it is essential that good quality test leads are supplied with adequate insulation. The range selection switches and the casing should also be well insulated.

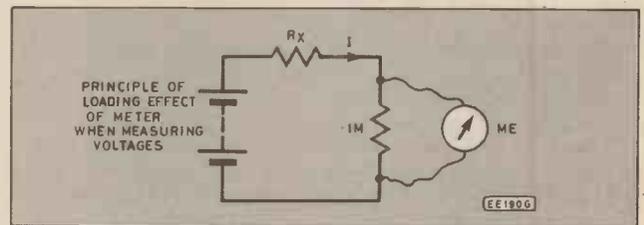


Fig. 6. Loading effects of the meter.

### CHOOSING A MULTIMETER

It would be impossible to describe every aspect of multimeters as it is such a vast subject and innovations are being introduced all the time. Many of the new models have features such as auto-ranging, capacitance inductance and decibel ranges, as well as a host of other 'goodies'. This is all well and good but if all you need is a basic multimeter then many of these functions may be surplus to requirements.

Like any other major purchase, you must first decide what your requirements and priorities are. If you need a meter to assist fault finding on car electrics then a resistance and low sensitivity low voltage scale is probably all you need. On the other hand for TV servicing you may need a high voltage and low current scale and sensitivity may be important.

Whilst bearing in mind the above points cost is likely to be an important factor. This is where this buyers' guide can really help. Each meter illustrated is accompanied by a brief description including the types of ranges and the input impedance. When these factors have been compared together with the price then it may help you to come to an acceptable compromise between performance and price. It could also save you a few pounds into the bargain.

## PLEASE NOTE

We would like to point out that readers buying from the guide are not protected by the Mail Order Protection Scheme unless the company concerned have advertised the product in a display advertisement in this issue.

This guide is an aid to the purchaser and makes no recommendations.



**Model:** TD 20. **Ranges:** 2V–500V a.c./d.c., 2k $\Omega$ –2M $\Omega$ . (9 ranges). **Impedance:** 11M $\Omega$ . **Special Features:** Continuity buzzer. **Price:** £42 + VAT. **Supplier:** House of Instruments, Raynham Rd., Bishop's Stortford, Herts. (0279 55155).



**Model:** BBC MA5D. 300mV–1kV a.c./d.c., 300 $\mu$ A–20A a.c./d.c., 3 $\Omega$ –20M $\Omega$ . (26 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Capacitance and decibel ranges. Built-in battery charger. **Price:** £320 + VAT. **Supplier:** House of Instruments, Raynham Rd, Bishop's Stortford, Herts. (0279 55155).



**Model:** Fluke 73, 75, 77. **Ranges:** 320mV–100V d.c., 3.2V–750V a.c., 10A a.c./d.c., 320 $\Omega$ –320M $\Omega$ . (10 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Diode and continuity tester. **Price:** 73–£65.00, 75–£75.00, 77–£95.00. **Supplier:** Fluke (GB) Ltd., Colonial Way, Watford, Herts. (0923 40511).



**Model:** Hung Chang HM101. **Ranges:** 10V–1kV a.c./d.c., 100mA d.c., 1M $\Omega$ . (12 ranges). **Model:** Hung Chang HM102. **Ranges:** 250mV–1kV d.c., 10V–1kV a.c., 50 $\mu$ A–500A, 6M $\Omega$ . (14 ranges). **Impedance:** Not known. **Price:** £14 + VAT. **Supplier:** Cirkit Holdings PLC, Park Lane, Broxbourne, Herts. (0992 444111).



**Model:** Keithley 175. **Ranges:** 200mV–1kV d.c., 200mV–750V a.c., 200 $\mu$ A–10A a.c./d.c., 200 $\Omega$ –20M $\Omega$ . (27 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Autoranging,  $\mu$ P operated with memory (100 readings). IEEE bus. **Price:** £449 + VAT. **Supplier:** Keithley Instruments Ltd., 1 Boulton Rd., Reading, Berkshire, RG2 0NL. (0734 861287).



**Model:** Micronta. **Ranges:** 2V-1kV a.c./d.c., 2mA-2A a.c./d.c., 20MΩ. (16 ranges). **Impedance:** Not known. **Special Features:** Diode test. **Price:** £44.95. **Supplier:** Tandy (stockists).




**Model:** Keithley 179A. **Ranges:** 200mV-1.2kV d.c., 200mV-1kV a.c., 200μA-20A a.c./d.c. 20MΩ. (26 ranges). **Impedance:** 10MΩ. **Special Features:** Autoranging. **Price:** £385 + VAT. **Supplier:** Keithley Instruments Ltd, 1 Boulton Rd., Reading, Berks. (0734 861287).



**Model:** TM11. **Ranges:** 150μV-500V d.c., 50μV-500V a.c., 150pA-500mA d.c., 50pA-500mA a.c., 1kΩ-10GΩ. **Impedance:** 100MΩ. **Special Features:** dB scale and 30 optional ranges. **Price:** £175 + VAT. **Supplier:** Levell Electronics Ltd., Moxon St., Bar-net, Herts., EN5 5SD. (01-440 8686).

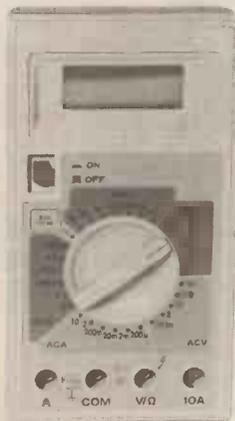**Model:** Hitachi VR3525. **Ranges:** 200mV-1kV d.c., 2V-750V a.c., 200μA-10A a.c./d.c., 200Ω-20MΩ. (20 ranges). **Impedance:** 10MΩ. **Special Features:** Autoranging. Diode test. Continuity buzzer. Temp. -20° to 700°C. **Price:** £120.75. **Supplier:** Reltech Instruments, New Rd., St. Ives, Huntingdon, Cambridgeshire. PE17 4BG. (0480 63570).




**Model:** Metex 3500. **Ranges:** 200mV-1kV d.c., 200mV-700V a.c., 200μA-10A a.c./d.c., 200Ω-20MΩ. (28 ranges). **Impedance:** 10MΩ. **Special Features:** Diode test facility and zero check. **Price:** £37.09 + VAT. **Supplier:** House of Instruments, Raynham Rd., Bishop's Stortford, Herts. (0279 55155).



**Model:** Fluke 8026B. **Ranges:** 200mV-1kV d.c., 200mV-750V a.c., 2mA-2A a.c./d.c. (19 ranges). **Impedance:** Not known. **Special Features:** Diode test. Conductance; 2mS-200nS. **Price:** £207. **Supplier:** Electroplan Ltd., PO Box 19, Orchard Rd., Royston, Herts., SG8 5HH. (0763 41171).



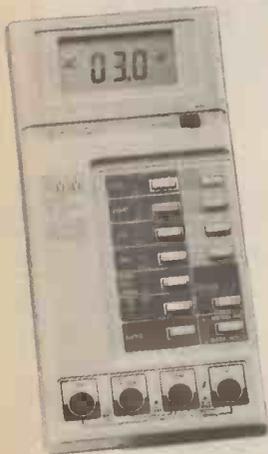**Model:** Pantec Zip. **Ranges:** 2V-500V a.c./d.c., 2kΩ-2MΩ. (8 ranges). **Special Features:** Auto-ranging and direct probe entry. **Price:** £49 + VAT. **Supplier:** Pantec, Carlo Gavazzi (UK) Ltd., 162-164 Upper Richmond Rd., Putney, London. (01-785 9022).



#### PLEASE NOTE:

Whilst every effort has been made to ensure that the information given in this guide is correct, we cannot be responsible for any price changes. Also specifications are subject to change without notice.

Where specifications have been listed, the number of ranges have been given together with the smallest and greatest full scale deflection readings available for each range. This information together with some special features mentioned should provide a rough guide to each instrument's capability.



**Model:** Microtest 80. **Ranges:** 100mV-1kV d.c., 1.5V-1kV a.c., 50μA-5A d.c., 250μA-2.5A a.c., 500Ω-5MΩ. (30 ranges). **Special Features:** Capacitance and Decibel ranges. **Price:** £27 + VAT. **Supplier:** Maplin Electronics.

**MULTIMETERS**  
**buyer's**  
**guide**  
**MULTIMETERS**



**Model: NK VF-3. Ranges:** 10–500V a.c./d.c., 0.5mA–250mA d.c., 1M $\Omega$ . (16 ranges). **Impedance:** 2k $\Omega$ /V a.c./d.c. **Price:** £7.95 + VAT. **Supplier:** Harris Electronics (London), 138 Grays Inn Road, WC1X 8AX. (01-837 7937).



**Model: BBC M2012. Ranges:** 200mV–650V a.c./d.c., 2mA–2A a.c./d.c., 2k $\Omega$ –2M $\Omega$ . (23 ranges). **Supplier:** House of Instruments. (0279 55155).



**Model: Maplin Pocket Multimeter. Ranges:** 10V–500V a.c./d.c., 0.5mA–250mA d.c., 1M $\Omega$ . (16 ranges). **Impedance:** 2k $\Omega$ /V a.c./d.c. **Price:** £6.95. **Supplier:** Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex, SS6 8LR. (0702 554155).



**Model: Beckman T90. Ranges:** 200mV–1kV d.c., 200mV–600V a.c., 200 $\mu$ A–2A d.c., 200 $\Omega$ –20M $\Omega$ . (18 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Diode test. **Price:** £59 + VAT. **Supplier:** Beckman Instruments Ltd., Mylen House, 11 Wagon Lane, Sheldon, Birmingham, B26 3DV. (021 742 7761).

**Model: AVO 1000. Ranges:** 300mV–1000V d.c., 10V–1000V a.c., 50 $\mu$ A–6A d.c., 10mA–6A a.c., 1 $\Omega$ –10M $\Omega$ . (23 ranges). **Impedance:** 20k $\Omega$ /V a.c., 2k $\Omega$ /V a.c. **Special Features:** Continuity buzzer. **Price:** £49.50 + VAT. **Supplier:** House of Instruments, Raynham Rd., Bishop's Stortford, Herts. (0279 55155).

**Model: ISI DM3350. Ranges:** 1kV d.c., 600V a.c., 10A a.c./d.c., 2M $\Omega$ . (15 ranges). **Special Features:** Autoranging. Continuity buzzer. **Price:** £49.35 + VAT. **Supplier:** Semiconductor Supplies International Ltd., Dawson House, 128/130 Carshalton Rd., Sutton, Surrey, SM1 4RS. (01-643 1126).



**Model: ALT/AI KD305. Ranges:** 2V–1kV d.c., 2V–750V a.c., 2mA–10A d.c., 200 $\Omega$ –20M $\Omega$ . (14 ranges). **Impedance:** 10M $\Omega$ . **Price:** £31.50 + VAT. **Supplier:** Semiconductor Supplies International Ltd., Dawson House, 128/130 Carshalton Rd., Sutton, Surrey, SM1 4RS (01-643 1126).



**Model: Miselco Electro Super. Ranges:** 100mV–1kV a.c./d.c., 100 $\mu$ A–6A a.c./d.c., 1M $\Omega$ . (20 ranges). **Impedance:** 20k $\Omega$ /V a.c./d.c. **Special Features:** dB scale. **Price:** £41 + VAT. **Supplier:** Alcon Instruments Ltd., 19 Mulberry Walk, London, SW3 6DZ. (01-352 1897).

# CHALLENGER

## A MULTIMETER FOR TODAY


Pantec's new Challenger analogue multimeter.

One of the new generation instruments from the electrical test and measurement specialists.

The Challenger 10 amps multimeter incorporates many advanced features including ● Diode tester ● Dry cell battery tester ● Built-in magnetic attachment ● Multi-position stand plus neck strap provision ● Practical design with ultra-clear display.

Send today for further details of the Multimeter for Today.

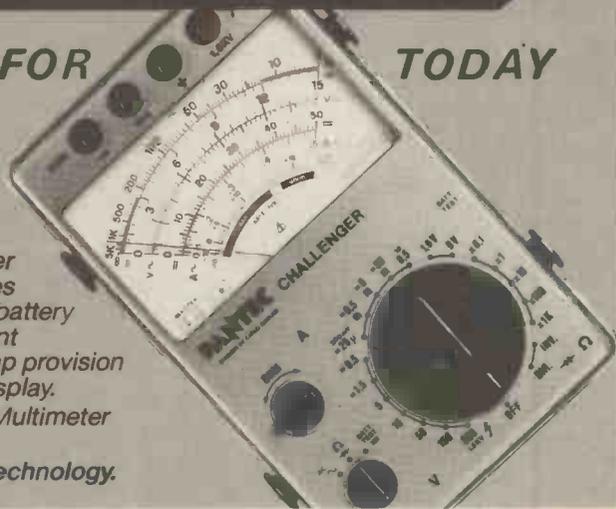Challenger - the best of Pantec technology.



Please send details of the new Pantec Challenger analogue multimeter.

Name

Company

Address

Tel:

# PANTEC

Pantec division of Carlo Gavazzi, 162/164 Upper Richmond Road, Putney, London SW15 2SL Tel: 01-785 9022 Telex: 8952493

## AFFORDABLE ACCURACY QUALITY MULTIMETERS FROM ARMON

### ANALOGUE

**HM-102BZ**  
10ADC Range, 20kΩ/VDC, Buzzer, Battery Test  
Scale..... **£13.00**  
19 measuring ranges

**HM-102R**  
Low end voltage & current ranges, Jack for  
Audio o/p Voltages..... **£11.00**  
20 measuring ranges

**HM-101S**  
Rugged, Pocket sized meter, for general  
purpose use..... **£7.50**  
16 measuring ranges  
Battery, Test Leads and Manual Included with  
each model.

### DIGITAL

**HC-6010** 0.5% Accuracy. Standard Model **£33.50**

**HC-5010T** 0.25% Accuracy. TR Test Facility **£39.50**

All models have full functions and ranges and  
feature:

3 1/2 digit 0.5" LED display  
Low battery indication  
Auto zero & Auto polarity  
ABS Plastic Casing & Tilt Stand  
DC AC 10amp Range  
Overload Protection on all ranges  
Battery, Spare Fuse, Test Leads and Manual

FULL DETAILS ON APPLICATION FROM:-

## ARMON ELECTRONICS LTD

DEPT S, HERON HOUSE, 109 WEMBLEY HILL ROAD, WEMBLEY, MIDDLESEX HA9 6AG


TELEPHONE 01-902 4321 TELEX 923985

PLEASE ADD 15% to your order for VAT. P&P Free of charge. Payment by cheque with order

Offer applicable to mainland UK only


Trade enquiries invited

Please allow 28 days for delivery

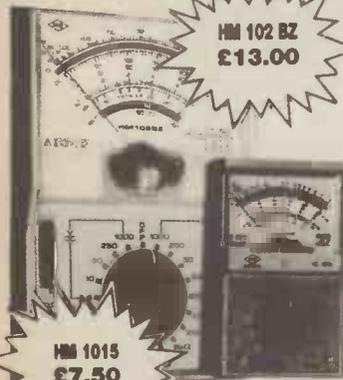

HM 102 BZ  
£13.00

HM 101 S  
£7.50

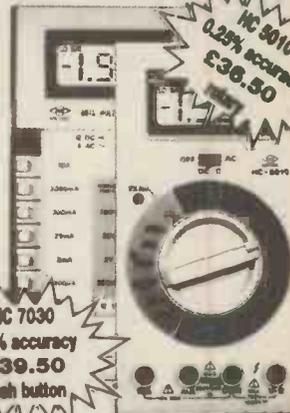

HC 6010  
0.25% accuracy  
£36.50

HC 7030  
0.1% accuracy  
£39.50  
push button

## GET YOUR FREE INFORMATION CARDS & SAMPLE COMPONENT PACK!

**COMPLETE SOLDERING KIT**  
(For the Hobbyist/Electronics Engineer)

**FOR LESS THAN £10!!**

Comprises of:-

- Antex Miniature 15W 240v AC Soldering Iron
- Antex Iron Stand c/w Sponge
- Desolder Pump
- 2 mtr Solder
- Desolder Braid
- 13A Plug

**LIMITED OFFER WHILE STOCKS LAST!**

**ONLY £9.85**

Please add 80p, P&P + 15% VAT

Call in and see our new counter now open  
9.00 - 5.00 Mon-Fri 9.00 - 12.00 Sat  
Too far to call? Don't worry, export/mail order is our speciality. Why not write and find out more.



24 hr answerphone for credit card orders  
Tel: 0244 536699



## SYSTEMS ELECTRONIQUE

(U.K.) LTD.

26 Engineer Park, Sandycroft, Deeside, Clwyd CH5 2QD.  
Tel: (0244) 536700.




FREE A4 SIZE PRICECARDS


We supply free cards containing kits and special offers information plus six basic component-cards. These cover the general ranges required by hobbyists, schools and colleges etc; they are Connectors, Passive components, Opto-electronics, Hardware and Semiconductors. Cards are automatically updated by post. Send now for your free cards and free SAMPLE COMPONENT PACK.



Iron Stand c/w Sponge

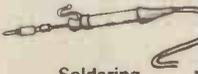

Soldering Iron

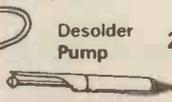

Desolder Pump

# QUASAR

## STEREO CASSETTE DECK

**SPECIAL OFFER PRICE**



From

**R T V C**

**£29.95**

INCLUDING VAT & CASE PLUS £2.75 P & P

For a special offer price of only £29.95 we're offering you this super Quasar Cassette Deck Kit. Including tape transport mechanism, n, ready punched and back printed quality circuit board and all electronic parts i.e. semi-conductors, resistors, capacitors, hardware, top cover, printed scale, mains transformer and a self assembly simulated wood cabinet. You only supply solder and hook-up wire.

**SPECIFICATIONS:**

Case size 285x260x90mm approx. Mechanism with-automatic stop and tape counter with reset button. Tape Speed: 4.76cm/sec (1 7/8 in/sec). Wow & Flutter: Typically 0.1%. Drive Motor: 12V d.c. with electrical governor. Play Torque: 40-75g/cm (DYNAMIC). Rewind & Fast Forward Torque: 60-140g/cm (STATIC). Rewind & Forward Time: Less than 100 sec. for C60 tapes. Bias/Erase Oscillator: Externally variable, frequency 60-100kHz. Output: (Adjustable) Up to 1 volt r.m.s. Mic. Sensitivity: 1mV @ 47k. DIN Sensitivity: 30mV @ 47k. Frequency Response: 30Hz-12.4kHz (-3dB). Signal to Noise Ratio. Noise reduction OFF-50dB. Noise reduction H.F. -56dB Noise reduction FLAT-70dB Cross Talk: Typically-50dB.

**CALLERS WELCOME: 323 EDGWARE RD., LONDON W2.**  
 - Open 6 days a week 9.00 - 5.30.  
 21 HIGH ST., ACTON LONDON W3 6NG  
 Tel: 01-992 8430 - Open 6 days a week 9.30 - 5.30  
 ½ day closing Wednesdays

To: RT-VC, 21A High St., Acton, London W3 6NG

Please send me  Kit/s

One deck kit costs £29.95 plus £2.75 p&p (£32.70)

I enclose PO/Cheque No. .... Value .....

Name .....

Address .....

Access 'phone orders 01-992 8430

To: RT-VC, 21A High Street, Acton, London W3 6NG



Mail order & shops:

441 PRINCES ROAD, DARTFORD, KENT DA1 1RB  
 Telephone: (0322) 91454

ORDERING INFORMATION: P/P 50p on orders less than £20 in value otherwise post free. All components full spec & guaranteed. Discounts available on orders over £50 — phone for details. For unlisted components phone for price. Goods normally despatched by return post.

**NEW CATALOGUE NOW AVAILABLE CONTAINING THOUSANDS OF LINES MANY ILLUSTRATED**

This incredible volume contains everything required by the home constructor, amateur radio and CB user and computer enthusiast.

We think the semiconductor section contains more types than have ever been offered to the hobbyist.

*Sections are headed as follows:*

- Aerials, Amplifiers, Audio Accessories, Batteries, Boxes, Bulbs, Capacitors, Crystals, Car Components, Car Audio, CB & Ham Equipment, Computer Connectors, Fuseware, Hardware, Headphones, Knobs, Lamps, Leads, Loudspeakers, Microphones, Meters, OPTO, PCB, Resistors, Semiconductors, Special Effect Equipment, Switches, Power Supplies, Test Equipment, Tools, Transformers, Wound Components.**

In addition to listed items we continue to provide a procurement service for obsolete and difficult to obtain types.

*How many suppliers do you have at the moment that offer a service like this?*

Please fill in coupon below and send with £1.25. Print clearly as coupon is used as address label.

Catalogue contains £2.50 discount order form — You make a profit straight away.

NAME .....

ADDRESS .....

POSTCODE .....



**Model:** Anders AMM301. **Ranges:** 6V–600V a.c., 60mV–300V d.c., 3V–1kV a.c., 50 $\mu$ A–10A d.c., 10mA–10A a.c., 200 $\Omega$ –200M $\Omega$ . (31 ranges). **Impedance:** 20k $\Omega$ /V d.c. **Special Features:** dB scale. **Price:** £25.50. **Supplier:** Anders Electronics Ltd., 48-56 Bayham Place, Bayham Street, London, NW1 0EV. (01-387 9092).



**Model:** Avometer DA116. **Ranges:** 200mV–1000V a.c./d.c., 200 $\mu$ A–10A a.c./d.c., 200 $\Omega$ –20M $\Omega$ . (31 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Diode test facility. **Price:** £152.10 + VAT. **Supplier:** House of Instruments, Raynham Rd., Bishop's Stortford, Herts. (0279 55155).



**Model:** M-2020S. **Ranges:** 100mV–1kV d.c., 10V–1kV a.c., 10 $\mu$ A–10A d.c., 2k $\Omega$ –20M $\Omega$ . (27 ranges). **Impedance:** 20k $\Omega$ /V d.c., 8k $\Omega$ /V a.c. **Special Features:** Transistor tester. **Price:** £19.95 + VAT. **Supplier:** Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex, SS6 8LR. (0702 554155).




**Model:** Avometer Eight, Mk. 6. **Ranges:** 100mV–1kV d.c., 3V–1kV a.c., 50 $\mu$ A–10A d.c., 10mA–10A a.c., 200 $\Omega$ –200M $\Omega$ . (31 ranges). **Impedance:** 20k $\Omega$ /V d.c. **Special Features:** Decibel and insulation resistance scales. **Price:** £138.70 + VAT. **Supplier:** House of Instruments.



**Model:** ALT/AI KD55C. **Ranges:** 200mV–1kV d.c., 200mV–750V a.c., 200 $\mu$ A–10A a.c./d.c., 200 $\Omega$ –20M $\Omega$ . (22 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Overload protection. **Price:** £44.10 + VAT. **Supplier:** Semiconductor Supplies International, Dawson House, 128/130 Carshalton Rd., Sutton, Surrey. (01-643 1126).




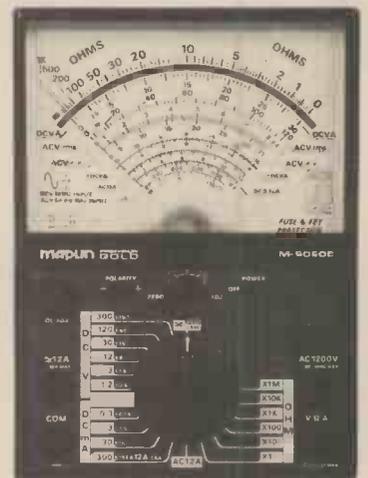**Model:** M-5050E. **Ranges:** 0.3V–1200V d.c., 3V–1200V a.c., 0.1 $\mu$ A–12A d.c., 12A a.c., 1–1G $\Omega$ . (53 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Polarity reversal switch. **Price:** £34.95 + VAT. **Supplier:** Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex, SS6 8LR. (0702 554155).



**Model:** Pantec PAN 2001. **Ranges:** 100 $\mu$ V–1kV a.c./d.c., 100mA–10A a.c./d.c., 0.1 $\Omega$ –20M $\Omega$ . (17 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Capacitance 1pF–20 $\mu$ F., Squarewave generator 15Hz–15kHz, Temp. –50°C to 150°C. **Price:** £99 + VAT. **Supplier:** Electronic & Computer Workshop Ltd., 171 Bloomfield Rd., Chelmsford, Essex, CM1 1RY. (0245 262149).



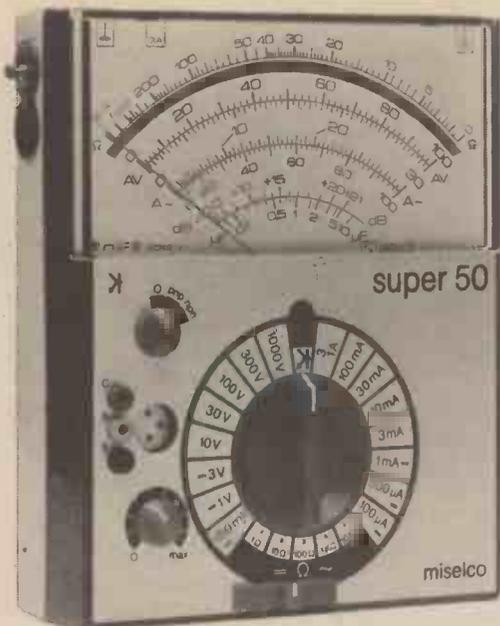

**Model:** Miselco Super 50. **Ranges:** 150mV-1kV a.c./d.c., 20 $\mu$ A-3A d.c., 3mA-3A a.c., 1 $\Omega$ -50M $\Omega$ . (34 ranges). **Impedance:** 50k $\Omega$ /V a.c./d.c. **Special Features:** dB -10 to +61 (5 ranges). Diode test. **Price:** £54.45 + VAT. **Supplier:** Alcon Instruments Ltd., 19 Mulberry Walk, London, SW3 6DZ. (01-352 1897).



**Model:** Pantec Explorer. **Ranges:** 3V-1kV d.c., 15V-1kV a.c., 3A-30A d.c./a.c., 5K $\Omega$ -500K $\Omega$ . (13 ranges). **Impedance:** 5k $\Omega$ /V d.c., 1k $\Omega$ /V a.c. **Special Features:** Metal detector. Phase detector. **Price:** £58 + VAT. **Supplier:** B.K. Electronics, Unit 5, Comet Way, Southend-on-Sea, Essex. (0702 527572).



**Model:** Pantec Challenger. **Ranges:** 0.25V-1kV d.c., 5V-1kV a.c., 25 $\mu$ A-10A d.c./0.5A-10A a.c., 500 $\Omega$ -5M $\Omega$ . (26 ranges). **Impedance:** 40k $\Omega$ /V a.c./d.c. **Special Features:** Shock proof case. Diode test. **Price:** £49 + VAT. **Supplier:** B.K. Electronics, Unit 5, Comet Way, Southend-on-Sea, Essex. (0702 527572).



**Model:** Hung Chang HC7030. **Ranges:** 100 $\mu$ V-1kV a.c./d.c., 0.1 $\mu$ A-10A a.c./d.c., 200 $\Omega$ -20M $\Omega$ . (17 ranges). **Impedance:** Not known. **Special Features:** Diode test. Overload protection. **Price:** £49.95. **Supplier:** Cirkit Holdings PLC, Park Lane, Bröxbourne, Herts. (0992 444111).



**Model:** Soar ME-531. **Ranges:** 200mW-1kV d.c., 2V-1kV a.c., 200mA-10A a.c./d.c., 200 $\Omega$ -2M $\Omega$  (18 ranges). **Impedance:** Not known. **Special Features:** Autoranging. Continuity buzzer. Diode test. **Price:** £63.95. **Supplier:** Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex, SS6 8LR. (0702 554155).

**Model:** Hitachi VR3510. **Ranges:** 200mV-1kV d.c., 200mV-600V a.c., 200 $\mu$ A-10A a.c./d.c., 200 $\Omega$ -20M $\Omega$ . (20 ranges). **Impedance:** Not known. **Special Features:** Continuity buzzer. Autoranging. Diode test. **Price:** £155.25. **Supplier:** Reltech Instruments, New Rd., St. Ives, Huntingdon, Cambridge, PE17 4BG. (0480 63570).



**Model:** ALT/AI KD25C. **Ranges:** 1kV d.c., 500V a.c., 200mA d.c., 2M $\Omega$ . (12 ranges). **Price:** £27.60. **Supplier:** Semiconductor Supplies International Ltd., Davison House, 128/130 Carshalton Rd., Sutton, Surrey, SM1 4RS. (01-643 1126).



**Model:** Trio DL-705. **Ranges:** 1mV-1kV a.c./d.c., 10 $\mu$ A-200mA a.c./d.c., 20M $\Omega$ . **Impedance:** Not known. **Special Features:** Semi-autoranging. Hi-lo option. **Price:** £123.91. **Supplier:** Supercat Electronics Ltd., PO Box 201, St. Albans, Herts. (0727 62171).



**Model:** HC 5010. **Ranges:** 200mV–100V d.c., 200mV–750V a.c., 20 $\mu$ A–10A a.c./d.c., 20 $\Omega$ –20M $\Omega$ . (31 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Selectable test voltage. **Price:** £36.50 + VAT. **Supplier:** Armon Electronics, Heron House, 109 Wembley Hill Rd., Middx., HA9 8AG. (01-902 4321).



**Model:** Beckman HD 100. **Ranges:** 200mV–1.5kV d.c., 200mV–1kV a.c., 200 $\mu$ A–2A a.c./d.c., 200 $\Omega$ –20M $\Omega$ . (21 ranges). **Impedance:** 22M $\Omega$  a.c./d.c. **Special Features:** Folding stand. **Price:** £129 + VAT. **Supplier:** STC Instrument Services, Edinburgh Way, Harlow, Essex, CM20 2DF.



**Model:** M-5010. **Ranges:** 200mV–1kV d.c., 200mV–750V a.c., 20 $\mu$ A–10A a.c./d.c., 20 $\Omega$ –20M $\Omega$ . (31 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Diode test facility. **Price:** £42.50 + VAT. **Supplier:** Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex, SS6 8LR. (0702 554155).



**Model:** ALT/AI KD615. **Ranges:** 200mV–1kV d.c., 200mV–750V a.c., 200 $\mu$ A–10A d.c., 200 $\Omega$ –20M $\Omega$ . (18 ranges). **Impedance:** 10M $\Omega$ . **Special Features:** Diode test. Overload protection. **Price:** £38.85 + VAT. **Supplier:** Semiconductor Supplies International, Dawson House, 128/130 Carshalton Rd., Sutton, Surrey. (01-643 1126).



**Model:** YN 360TR. **Ranges:** 250mV–1kV d.c., 10V–1kV a.c., 50 $\mu$ A–250mA d.c., 2k $\Omega$ –200k $\Omega$ . (19 ranges). **Impedance:** 20k $\Omega$ /V. **Special Features:** Fuse and diode protection, hfe range. **Price:** £17.98 inc. VAT. **Supplier:** Magenta Electronics Ltd, 135 Hunter St., Burton-on-Trent, Staffs, DE14 2ST. (0283 65435).



**Model:** M-102BZ. **Ranges:** 2.5V–1kV d.c., 10V–1kV a.c., 5mA–10A d.c., 10k $\Omega$ –1M $\Omega$ . (23 ranges). **Impedance:** 20k $\Omega$ /V d.c., 8k $\Omega$ /V a.c. **Special Features:** Continuity buzzer. **Price:** £14.95 + VAT. **Supplier:** Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex, SS6 8LR. (0702 554155).



## JAPANESE DEVELOPMENT GOES FLAT

THE Japanese have long been threatening to hit us with a revolutionary flat television/video screen that may be hung on the wall or even form part of the wall and be added to the "all mod cons" list circulated by house agents when offering a desirable property for sale!

This concept of the future has moved a step nearer with the announcement from Matsushita Electric Industrial of a new flat colour "panel" for all forms of media presentations and promotions.

The panel has been successfully used to develop a prototype of a truly "flat-screen" colour TV, featuring a diagonal 10-inch screen and a depth of only 9.9cm. The new set was put through its paces at *Tsukuba Expo '85 Show*, Japan, during March.

The colour panel features a square, completely flat screen, which, it is claimed, reproduces distortion-free images across the entire display area. Applications envisaged include office automation display and electronic services, such as; teletex, videotex, direct satellite broadcasts, high definition TV and cable/pay TV.

The new colour panel was developed using Matsushita's Matrix Drive and Deflection System. The screen consists of 3000 picture cells arranged in a matrix; 200 units horizontally and 15 vertically. Each picture cell is scanned by one electron beam which excites phosphor stripes. The prototype TV provides a resolution of 270 TV lines, a contrast ratio of more than 50, and a brightness of over 70fL.

### How It Works


The newly-developed Matrix Drive and Deflection System produces 3000 controlled beams by forming a matrix of 15 filament cathodes and 200 electron

beam control electrodes which cross cathodes at right angles. Each beam is horizontally deflected in six steps (two sets of R.G.B.) and vertically deflected in 32 steps (including the interlace) to form images consisting of 192,000 elements on the display panel. A complete picture is formed through the line-at-a-time method.


This deflection method also reduces the number of electrode terminals required to approximately one-seventh of the number used in the conventional matrix driving method.
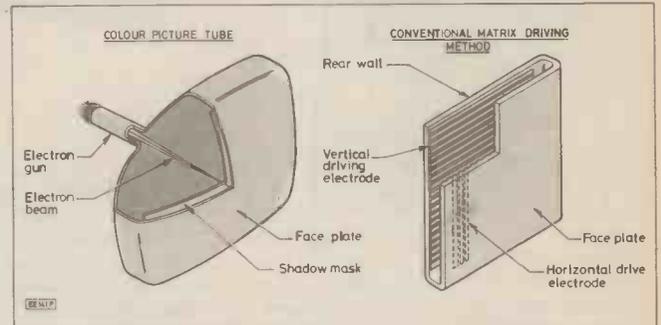
### Focusing

The system's lack of the shadow mask found in conven-



Conventional matrix driving method

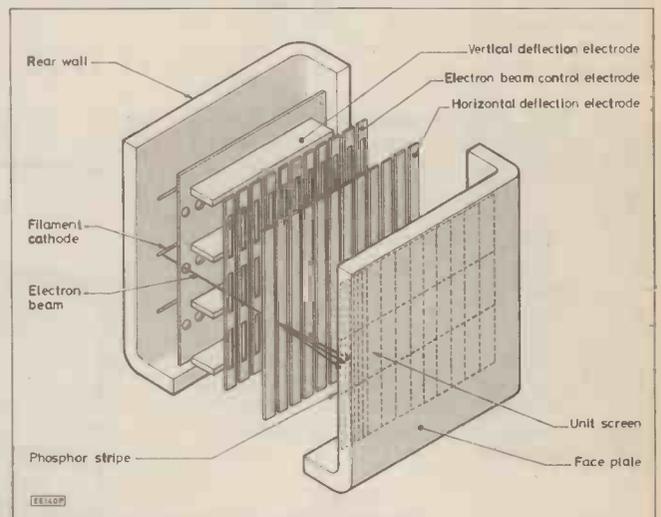

Matsushita matrix drive and deflection system

### Specifications . . .

	Colour Flat Panel	Flat Colour TV
Screen size:	200mm x 150mm	10 inch diagonal
Dimensions:	282mm (W) x 222mm (H) x 65mm (D)	370mm (W) x 355mm (H) x 99mm (D)
Weight:	7.5kg	14kg
Power consumption:	7 watts	70 watts
Brightness:	70fL	70fL
Resolution:	picture element pitch of 0.5mm	270 TV lines
Contrast:	More than 50	Gray scale: 64

tional colour picture tubes necessitates a fine electron beam of the same width as a phosphor stripe. They found the optimum electrode structure using the three-dimensional simulation technology previously developed by the company.

Separation of the horizontal and vertical lens systems to provide individual control of their focusings, has, it is claimed, resulted in improved resolution and colour reproduction. Of special importance to uniform display was the development of a cementing technology which evenly and alternately adheres 0.1mm grid electrodes with insulating plates.

### Digital Technology

Signal processing and driving are performed digitally and picture brightness is controlled by varying the pulse width which drives electron beams, thereby generating 64 steps in the gray scale. Colour reproduction is performed by digitizing the picture signal and alternately driving red, green and blue signals. Resolution is markedly improved by giving time differences in sampling each.

The use of a microcomputer for fine adjustment of the diameter and position of electron beams on the phosphor screen results in uniform brightness and high colour reproduction.

The Amstrad CPC464 home computer has been voted "Computer of the Year" by the Computer Traders Association. The award was made, at the *LET Show* trade exhibition, based on an independent poll of computer retailers.

## Money Matters

Total sales in the 12 months ended 31 December 1984 of £110.8 million (\$144.9M) was achieved by INMOS International plc. This is almost three times the level achieved in 1983. The company enjoyed its first profitable year producing profits of £14.4M (\$18.8M) against a loss of £13.5M in 1983.

In his statement accompanying their financial report, Mr. Harold Mourgue, Chairman of INMOS said:

"In 1984 INMOS invested over £28 million (\$32 million). The company plans substantial further investment in 1985. While much of the money is generated by INMOS operations, the board of Thorn EMI has indicated that it is prepared to commit the finance needed to ensure the company's continuing success . . ."

"We are therefore confident that INMOS will continue to grow and is significantly well placed to take advantage of a market recovery."

## BUSINESS LINK

The first small-dish transatlantic business satellite link exclusively for multi-national companies, provided by British Telecom International (BTI), has enabled the giant Massey-Ferguson group to establish its world-wide communications centre in the UK.

The key to the operation is BTI's SatStream North America small-dish satellite service using an Intelsat V satellite for high-speed computer traffic between Britain and North America.

The link allows dealers throughout Canada and the United States to place computerised orders via their own terminals for parts and machinery direct to the British factories.

Planning to make it an annual Spring Fair, the West of Scotland Amateur Radio Society is organising The Glasgow Amateur Radio Exhibition for 11 May at the Cardonald College, Glasgow.

More information may be obtained from the organising committee chairman, Tom Hughes GM3EDZ or Ian McGarvie GM4JDU.

## QUALITY FILM

A new film has been launched by the DTI's National Quality Campaign to promote the benefit of independent certification and thereby improve the quality and international competitiveness of UK industry.

In the film, "Getting Certified", business broadcaster and journalist, Brian Widlake talks to four key men who are concerned with quality systems. They describe the benefits of independent, third-party certification, as proof of a company's ability to manufacture to an agreed standard.

The 24 minute film is available on Free loan to industry and training and educational establishments from the Department of Trade and Industry. It can be obtained in 16mm film and video cassettes (VHS, Beta or U-matic format).

Anyone wishing to borrow the film should write, stating the format required, to: Standards and Quality Policy Unit, Department of Trade and Industry, Room 323, Ashdown House, 123 Victoria Street, London, SW1E 6RB.

The Right Honourable James Prior, M.P., Chairman of GEC and former Secretary of State for Northern Ireland, will officially open the first "British Electronics Week" at Olympia, London, on Tuesday, 30 April 1985.

## METER TAKE OFF

A major Ministry of Defence contract for the supply of handheld digital multimeters to the RAF has been won by Beckman Industrial.

The meters being supplied are standard heavy duty HD110 models which conform to NATO standards without modification. They were selected following a thorough evaluation of several

manufacturers' products by the Electrical Engineering Wing of the RAF Test Systems Flight.

Evan Steadman, Chairman of the Evan Steadman Communications Group and organiser of the "All Electronics/ECIF Show", has been named "Best exhibition organiser of 1984" in a worldwide readers' poll organised by the magazine *Conference & Exhibitions International*.

# Copyright Levy

The problem of unauthorised home taping of copyright material is discussed and possible solutions proposed in a HMSO document entitled "The Recording and Rental of Audio and Video Copyright Material" published by the Department of Trade and Industry. The Green Paper, which supplements one issued in 1981, also discusses the related issues of recording of broadcasts for educational purposes and the rental of pre-recorded copyright material.

"We have considered in detail the several hundred responses to that document (1981) and we intend to bring forward as soon as possible a comprehensive set of proposals for the reform of copyright and related laws," said Geoffrey Pattie, MP, Minister of State for Industry and Information Technology.

"On the issues of home and educational recording and on rental, the Government considers that a further opportunity for public comment is needed before a final decision can be taken."

The new Green Paper proposes that a levy be imposed on the sale of blank audio and video tape intended for domestic users who would in return be free to make, for personal use, video recording in general and audio recording of music. The size of levy to be subject to negotiation between beneficiaries and manufacturers/importers and to be statutorily limited to say 10 per cent of the retail price of audio tape and say 5 per cent of video tape. Audio tapes of less than 35 minutes total playing time to be exempt.

No realistic alternative to a levy scheme is seen, but there will be exemptions for certain categories of non-infringing user, for example the visually handicapped. It concludes that copyright owners are entitled to payment for the home taping of their material and that a levy is the only practicable way to providing such payment.

This latest document invites comments on the acceptability of a levy as a solution to the difficult problems posed by home taping. This is probably the last chance for readers to make their views known as all comments must be in by 30 April 1984. Proposals should be addressed to:

Industrial Property and Copyright Department, Department of Trade and Industry, State House, 66-71 High Holborn, London, WC1R 4TP.

# FAULT FINDING

## E.A. Rule Part 7

**D**URING this series, a number of servicing aids have been mentioned which can save time when locating a fault, and/or help clear the fault once found. The initial cost of these aids can be quickly recovered making them a good investment.

### AEROSOL SPRAYS

Some of the most useful are in aerosol spray form—a few general words about aerosol sprays may be helpful.

First, they should always be used in a vertical position. The expected shelf life is around two years with correct storage conditions, which are normally within the temperature range of 10°C to 40°C with absolute limits of 0°C and 50°C. Most service workshops or home construction locations will meet these conditions, but extra care is needed if your workshop is a shed outside, for example, as temperatures here could well exceed the limits. Aerosols must not be exposed to direct sunlight and *never* placed near a naked flame or high temperature object. The contents are highly pressurised and excessive heat can cause an explosion.

When using aerosol sprays be careful not to use the spray near to your eyes and remember that the spray can 'bounce' back from a surface or component. Always read the instructions and follow them; like so many things, aerosols are very safe when used correctly but if misused can be dangerous.

### FREEZER SPRAY

Another useful aerosol is the freezer spray, which provides a means of cooling components down to as low as minus 56°C in a very short time (frost can be seen on components in many cases). This rapid cooling will often show up a faulty component or help locate a cracked printed circuit board track. As the component or printed track is cooled it will contract and intermittent contacts will often be revealed because this contraction will part the connection. It can also be used as a heat shunt to maintain a low temperature near heat sensitive components while soldering their connections. Usage of the aerosol is similar to the switch cleaner with a small spout to localise the spray.

While on the subject of aerosols, although not a service aid as such, a fire extinguisher type is available which is



designed to be used on *small* electrical fires. These extinguishers contain liquified BCF gas, it is non-corrosive and harmless to electrical/electronic components.

### CONTACT CLEANER

One of the most useful aerosol sprays is the switch cleaner and this one is found in almost every service department. It contains a contact cleaner and a lubricant, this combination will clean off tarnish and corrosion from switch contacts and leave a thin film of lubricant to protect against further corrosion. This film of lubricant also helps maintain a low contact resistance which will reduce contact arcing or burning of switch contacts, prolonging their life. The solvent is inert and can be used on most surfaces safely. Some aerosols have a short flexible spout fitted which enables the spray to be directed onto a small area and avoids waste.
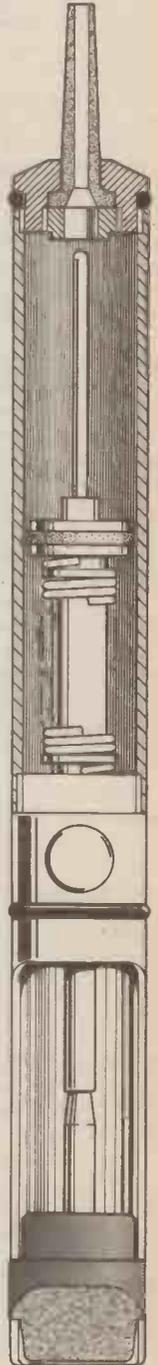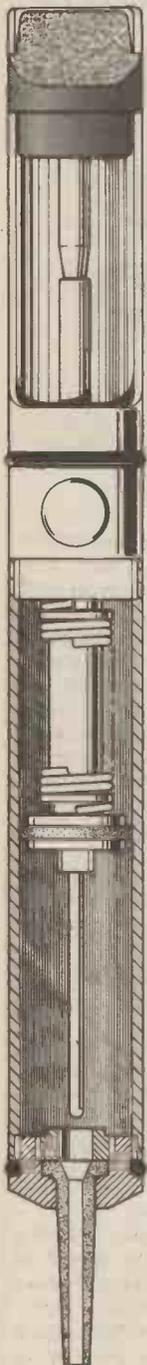
### DE-SOLDERING

A useful aid to removing components from a printed circuit board without damage is the de-soldering tool. There are a number of different types available, but perhaps the most popular are the ones that use suction to remove the solder. These are very effective and can be used with one hand while holding the soldering iron in the other. Basically, this device works like a bicycle pump in reverse mode. Instead of pushing the plunger (to force air out of the nozzle), the plunger is pulled (by a spring) so as to suck air up the nozzle; see illustrations. In practice, the tool is primed by pressing the plunger down into the main body against the spring. Then, while melting the solder with the soldering iron, the nozzle of the solder sucker is placed over the connection to be unsoldered and when the solder is molten the release button pressed. This releases the suction plunger and sucks the solder from the joint into the body of the solder sucker, leaving the connection completely free of solder after which the component can be removed without damage. After a period of use the nozzle can be unscrewed and the surplus solder cleaned out. These solder suckers can be used over and over again. The author is still using the same one after sixteen years, having periodically replaced the nozzle. With some of the multi-pin i.c.s, a solder sucker is the only way which will enable damage-free removal.



## MAG TAPE CLEANER

A video head cleaning fluid was mentioned last month regarding cleaning cassette recorder heads, etc. But the same fluid can also be used to degrease drive belts or idler wheels. Cleaning these with this fluid can give them a new lease of life and often a replacement will not be required. It is important to keep the container top screwed down tightly as these fluids evaporate very, very quickly.

## TWO FOR THE ROAD

An epoxy cement is another useful service aid. This adhesive can be used for most repair jobs, such as broken knobs, front panels, etc. It is important that the surfaces to be repaired are clean and free from grease and also with some plastics the surface should be roughened. Not all plastics can be repaired using epoxy cements, but it is effective in most cases. In one situation the use of such an adhesive proved to be the only suitable method to fix a multi-track professional recording head onto its mounting bracket; a method, I hasten to add, which was recommended by the manufacturers.

Last but not least is heat sink compound. Whenever a power semiconductor is changed it is important that a fresh application of a heat sink compound is applied between the semiconductor and heat sink. These compounds are normally a zinc oxide filled silicon and provide a good thermal conductor between semiconductor and heat sink, they also add extra electrical insulation when used with the normal (mica) washers.

There are many more service aids available and a look through a good components catalogue should reveal those most useful in your particular situation.

## FROM EXPERIENCE

Recently a cassette recorder was brought into the workshop with the complaint that the tape speed was too fast. Examination showed that the transistor used to stabilise the motor supply had become short circuited. A replacement



For a wide range of aerosol-aid stockists see *Shoptalk* page 256.

was fitted but the tape speed was now very erratic; a careful check of other components did not reveal any fault, but the output voltage was unstable. The actual cause was traced to an original manufacturing fault. During manufacture, a part of the printed circuit track was omitted—the test department had bridged this gap with solder! When the transistor was removed using the solder sucker tool, the solder bridge also was inadvertently removed, without even realising it was there in the first place. Only careful checking of the circuit against the manual revealed this one.

A common complaint received is that of noisy controls, mainly volume controls, but sometimes other types as well. The cause could be due to a leaky coupling capacitor allowing a small voltage to appear across the control, and this should be checked out, but often it is simply due to wear of the control track causing small particles of carbon dust to get between the wiper blade and track. Sometimes an application of the switch cleaner spray will effect a cure, but in the author's experience this may only effect a cure for a short time. The author has used a cure now for a number of years which is very effective, even with really bad controls. This is to use penetrating oil, such as *Three-in-one*. It is applied in very small quantities to the defective track and the control then operated a number of times. This application of penetrating oil direct to the track is almost 100 per cent effective, and careful tests over a number of years have not revealed any side effects. However, if used on the slider type of control it can make the mechanical operation feel rough, so it must be used very sparingly. Also keep the oil well away from other components.

This is the final part of this series on fault finding, and although limited to basic procedures the series should prove helpful. The photograph shows the equipment used by the author, and although it may look impressive, in fact most of the time the multimeter is the busiest piece of equipment—see page 264. □



# FOR YOUR ENTERTAINMENT

BY BARRY FOX

## Lasers Light the Way

The STC Laboratories out at Harlow get edgy when people talk about the company as being part of ITT. It was, until 1982, but then STC (Standard Telecommunications) hived off on its own with ITT owning just 24 per cent.

The original work on fibre optics was done at STL in Harlow in the 60s, by Hong Kong scientist Charles Kao. At that time it was all just mathematical prediction. He said that light could be channelled down a fibre of very pure glass.

Now STL has 800 scientists, of which a quarter work on fibre optics. Some of their laboratory experiments point where fibre optics will be leading towards the end of the century.

In a nutshell, the trend is towards longer light wavelengths, in the infra red band. This will open up all kinds of possibilities because in many applications it will no longer be necessary to convert light into electricity before carrying it to a processing system.

Today's optic fibres are made of silica glass. At certain fixed wavelengths there are "windows" in which light travels through it most efficiently. There is a window at the 1.3 micron wavelength and most of today's telecommunications use this. There is another window at 1.6 microns and this is where the next generation of systems will work.

Today's fibres are approaching their theoretical best with a loss of 0.1dB per kilometre. But if the wavelength is longer, as for infra-red light, the silica glass just absorbs it. So new glasses are needed. The best bet so far is a glass made from zirconium fluoride which has a theoretical absorption of as little as 0.01dB per kilometre. This opens the door to a submarine cable, a thousand kilometres long, without any booster repeaters along the route.

It looks likely that fluoride glass will be able to carry light of between 2 and 12 microns wavelength. This enables optic communication, for instance from a gas sensor or heat sensing camera. Light signals from the sensor could pass along an oil pipeline or through the wings of a military aircraft. At the moment the light must be converted to electricity.

Doctors use infra-red laser light, usually at 10.6 micron wavelength, for surgery. At the moment they need an articulated arm with mirrors to get it round corners. With fluoride glass it might be possible to pump watts, or even tens of watts, down a flexible fibre.

This wavelength incidentally is generated by the carbon dioxide lasers used for cutting steel. But in this case kilowatts of power are used and it is unlikely that this can ever be channelled down a fibre without frying it.

Of course nothing is for nothing. Fluoride glass transmits long wavelength infra-red because it has heavy atoms which can be thought of as weakly sprung. Unfortunately this makes the glass difficult to draw into

fibre. It melts at around 300°C instead of 2,000 degrees for silica, and crystallizes easily which means that it is fragile.

Fluoride glass is also very susceptible to water. If any gets into the glass it absorbs the light. The fundamental peak of water absorption is 2.9 microns. The other water absorption peaks which plague silica glass are weak harmonic overtones. So the worst risk of water absorption is in the infra-red band.

Fluoride glass has to be made in chambers where the air is so dry that only a few parts per million of water is able to get at the raw chemicals. Other odd mixes, for instance involving arsenic, in the chalcogenide group, may turn out to work well at the much longer wavelengths over 10 microns.

## Laser Sandwich

The light launched into a fibre usually comes from a laser. These aren't bulky gas lasers any more, they are solid state chips. A speck of active material, for instance gallium arsenide for wavelengths of around 0.85 microns or gallium indium arsenide phosphide for wavelengths of around 1.3 microns, is sandwiched between tiny reflectors in an integrated circuit.

Early solid state lasers had a short life, largely because they drew a high current and got hot. STL reckons it now has the world's lowest threshold current laser, for the 1.3 micron wavelength. The active light-emitting part measures just 1 micron in length and is 0.2 microns thick. As a reference, a human hair is 50 microns thick.

The chip starts to lase at a current threshold of 4.6 milliamps. So it runs very cool. Estimated working life is around 25 years which makes it safe to install in submarine cables. Obviously you can't send out a man with a screwdriver to replace lasers under the Atlantic.

Another new trick is to tune the laser output very tightly, because this means that the light pulses sent down a fibre do not spread. Before the chip lases, it emits a broad band of light, around 100 nanometres wide. It is now acting as an l.e.d. When it lases, through oscillation of the light between the reflectors, the bandwidth drops to a few hundred MHz which is under one nanometre. But there are still spikey lines in the spectrum, caused by standing waves in the resonant chamber between the mirrors.

## Optical Grating

The aim is to tune out all these lines except one. This is now done by building an optical grating into the laser chip. The grating ridges are one wavelength long and act as extra resonant chambers.

The grating works like a very sharp filter that kills off all but a single frequency in the laser output. So all the light travelling down the fibre is of exactly the same wavelength and frequency. So it travels at one speed and all arrives at the same time. So digital pulses do not spread and introduce errors into the signal.

Think for a moment about the difficulties of making such a grating, with a ridge spacing of 250 nanometres. The only way to do it is with an electron beam masking machine, which draws direct onto the silicon wafer with an accuracy down to 0.1 microns. This compares with an accuracy of one or two microns for the chips made with conventional photo lithographic techniques.

It will take several hours to trace each wafer by direct electron beam writing. But each wafer can produce up to 1,000 chips and even if only half these are usable it's worthwhile because telecommunication lasers of this type sell at thousands of pounds each.

## Electron Analysis

Finally, have you ever thought how you can check the electrical performance and continuity of a chip with circuit lines drawn down to a spacing of one or two microns, or even less? Early chips were tested with a mechanical probe. This is now impractical. The probe damages the chip.

One technique used at the STL Labs is to put power through the chip circuit and look at it under an infra-red microscope. Any faults show up as hot spots, because the fault areas generate more heat than the rest of the chip.

Another way is to put the chip inside an electron microscope and look at it while current is running through. Negative voltages show up as light tracks on the microscope picture and positive voltage shows up as dark tracks.

This is fine for d.c. but what about high frequency operations? Simple when you know how. The electron beam is switched on and off at the same frequency as the operating voltage, like a pop group strobe. That way it artificially freezes the dynamic performance of the chip. Magnification can be up to 100,000 times.

Electron beams can also be used to analyse the physical and chemical structure of the chip surface. When the beam hits the chip it produces X-rays and secondary electrons which have an energy pattern which is characteristic of the material which released them.


Computer software can give a direct readout of the material under the beam, down to a one micron spot. So if a chip doesn't work a lab technician with an electron microscope can look for a break in the voltage pattern and then do a spot analysis of that tiny area to identify any chemical blemish.

*This group of hair-thin strands of glass fibre cables are capable of carrying thousands of simultaneous telephone calls and digital information down each cable.*



# JUNE FEATURES...


## GRAPHIC EQUALISER

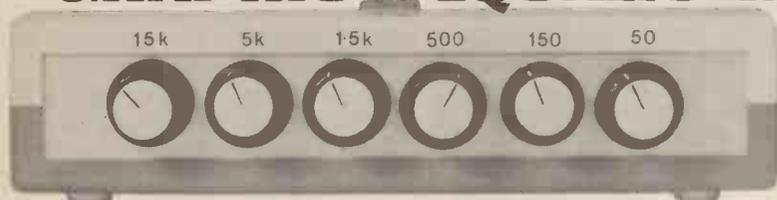

This low cost unit is an ideal add-on for electric guitars, providing a wide range of musical effects. The unit incorporates six graphic equaliser channels with centre frequencies between 50Hz and 15kHz.
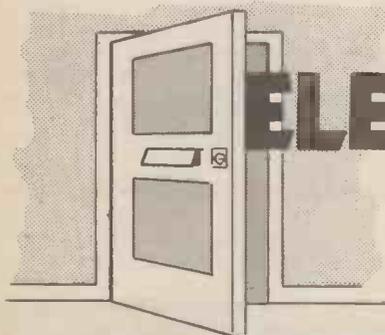
## COMPUTERISED SHUTTER TIMER

Use your microcomputer as a piece of photographic test equipment. This is a simple and inexpensive camera tester, yet will do what normally requires costly apparatus.



## ELECTRONIC DOORBELL

A doorbell with the ringing sound of a conventional electromechanical device, but taking advantage of the reliability and compactness of electronic techniques.

**Plus... Monostables - Bistables - Astables**

**EVERYDAY**  
**ELECTRONICS**  
and computer **PROJECTS**

JUNE 1985 ISSUE ON SALE FRIDAY, MAY 17

# DOWN TO EARTH

BY GEORGE HYLTON



THE DATA SHEET on an operational amplifier says that it will source 10mA and sink 15mA. Please explain.

Another case of jargon! "To source" is shorthand for "to act as the source of current". "To sink" means "to absorb current".

## CURRENT

Some simple examples (Fig. 1) illustrate the point. At (a) the boxed-in part is a source of current, which it supplies to a load  $R_L$ . The current rises when  $R_L$  is reduced, and its upper limit, when  $R_L = 0$ , is fixed by the internal resistance ( $100\Omega$ ) at 30mA. So 3V in series with  $100\Omega$  can source 30mA.

A current sink (b) can be just a resistance. If it's  $100\Omega$  as shown, then it can absorb up to 30mA when driven by 3V through a load  $R_L$  which may fall to zero.

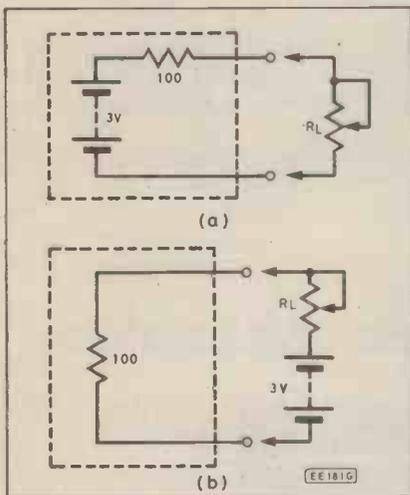


Fig. 1: in drawing (a), the current source is represented by a 3V battery with a 100 ohm internal resistance in series. In drawing (b), the 100 ohm load resistance is "sinking" up to 30mA via load resistor  $R_L$ , which is variable.

Obviously the amount of current which a circuit can source or sink must depend on the voltage available for driving it. In practical cases the voltage is often fixed by some other consideration. In logic circuits, for example, it may be fixed by a design requirement at, say, 5V.

In any case, the driving voltage can't be increased beyond a certain point, because any increase in current entails an increase in power dissipation. Every component or device has its safe dissipation limit, beyond which overheating may damage it. For this reason, sourcing and sinking ratings imply safety. A circuit which is forced to source or sink more current than its rating may overheat.

## OPERATING AMPLIFIER CURRENTS

"Source" and "sink" are really no more than brief terms for the ability of a circuit to deal with outward and inward current flows. But the terms have a certain handiness which guarantees their survival.

In the case of an operational amplifier with split d.c. supplies (Fig. 2) the circuit either sources current through the load  $R_L$ , or sinks it. The current really comes from the battery, of course. But if we take the battery for granted, the operational amplifier is seen to source or sink currents via  $R_L$  and "earth".

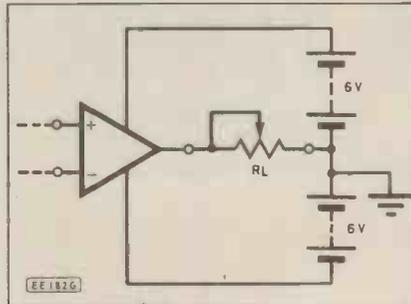


Fig. 2. The operational amplifier has a "split" supply, which means that the chip has both a positive and a negative power supply connection. In terms of sourcing and sinking current, the current flow (from the battery) can be considered as flowing from, or into, the operational amplifier, respectively.

$R_L$  may not be a physical resistor. It could be, for instance, the resistance of the operating coil of a relay. In this case, since a relay will only operate reliably when its coil passes enough current, the source or sink current rating can be very relevant. Quite often the two ratings differ. This can affect the way the operational amplifier is used.

Suppose, for example, that  $R_L$  is a relay coil whose operating current is 25mA. If the operational amplifier will source 20mA but sink 30mA then in this case the relay must be connected so that it is operated by the "sink" current.

An operational amplifier is arranged in Fig. 3 to switch on one of two l.e.d.s, one green, the other red. If the green l.e.d. needs more current than the red (for equal

brilliance) it may be necessary to pay attention to the source and sink ratings, and connect the l.e.d.s accordingly.

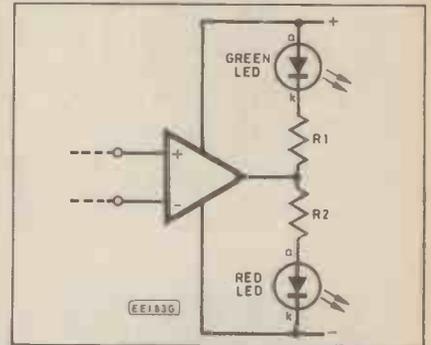


Fig. 3. When different l.e.d.s are connected in circuit, their current ratings will determine which l.e.d. is "sourced" current by the op-amp, and through which the op-amp "sinks" current.

If the current-sinking rating is the greater, then the arrangement shown may have to be used. (In many cases, of course, both sourcing and sinking capacities will be more than adequate, so either arrangement of l.e.d.s would do).

## SINKING ALONE

Many circuits can either source current, or sink it, but not both. Some integrated circuits have "open-collector" outputs; i.e., their last stage is a transistor with no collector load resistance. The user adds his own (see Fig. 4). If it takes the form of a relay or lamp you have to ensure that the current-sinking ability is adequate. Suppose, for example, a 6V, 300mW lamp has to be lit by a voltage comparator i.c. with open collector output. If the comparator will sink 100mA, is this enough?

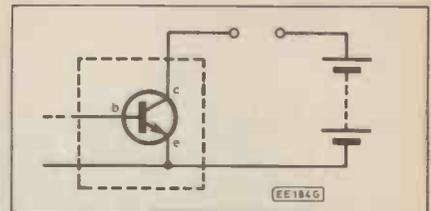


Fig. 4. The output stage of an integrated circuit which is "open-collector".

Since power (wattage) is the product of voltage across, and current flow through any device, it is easy to work out the current that the lamp will draw. We have  $0.3 \text{ (watts)} = 6 \text{ (volts)} \times I \text{ (amps)}$ . Hence  $I = \frac{0.3}{6} = 0.05A$ , or 50mA. The comparator is capable of sinking 100mA, so it can be used.

However, the designer must ensure that the supply voltage is correct for the job.

If a 6V supply is used, then the bulb needs the whole voltage, leaving nothing across the comparator output. If, when sinking 50mA, the comparator's output voltage is 3V, then the supply voltage will have to be increased in order to have enough for lamp and comparator output in series.

# COUNTER INTELLIGENCE

BY PAUL YOUNG

## Computer Weather

As much as I admire computers, and realise that life today would probably be intolerable without them, I still cannot resist a quiet smirk of satisfaction when one of them finishes up with egg on its monitor. This is most likely an age old instinct going back to the days when we were all savages and worshipped idols. Every now and again we would knock them down and chop them up, just to keep them in their place, so to speak.

This happened recently, I refer of course to the computers, not the idols. During the terrible spell of cold weather the BBC weather man explained they now had a wonderful new computer system, with which they could pinpoint any part of the country and tell us exactly what was going to happen. He then proceeded to tell those of us who lived in the South East, that next day we could expect an easterly blizzard and heavy snow, we were depressed but not surprised. To our relief and delight, the next day was sunny with a south westerly wind.

Perhaps it is a bit hard to blame the computer, because weather is less predictable than the fair sex. Fronts bringing rain occlude before they reach you, and a "Low"

which should have moved South East, shoots off in a North Easterly direction, causing the opposite of what was forecast, tantalizing isn't it?

## Common Market Shock

Something I have often wanted but doesn't exist, is a small neat two-way flex connector. The nearest thing to it was the old Bulgin range of "Domina" plugs and sockets.

Someone will no doubt howl that you must have an earth connection. My contention is, that if you are connecting a plastic clock, or a glass or porcelain table lamp or one of those appliances where the works are completely isolated there is no point. There must be countless occasions when you want to move a lamp around and you don't want a long lead, nor do you want a clumsy thirteen amp plug on the end.

Even if someone produced one, I have no doubt the bureaucrats in Brussels would jump on it. I well remember how they outlawed the Bulgin P70 series, because it was possible to unscrew the back with the mains on. They were all ignominiously derided to twelve volts d.c. despite the fact they had been in use for probably fifty years without harming anyone

What is so safe about the continental system, with its two pin plugs and no earth? This was understandable when they were using 110 volts, but now it is a standard 220/240 volts a.c.

I put this question to an electrical friend of mine. What happens if the metal part of the appliance becomes "Live" and you touch it? He explained that the current flowed via your body back to the switch box, which tripped a relay and switched off the power. He added, that of course you may be dead by then. It was not very reassuring. Was he having me on?

## Pirate Radio

I was sorry to learn that "Radio Jackie" had been closed down. They have been broadcasting for three or four years and were at one time customers of mine, buying high voltage capacitors for their transmitters. I remember at the time asking one of the partners how they got away with it and he told me that as they were practically non profit making, and carried out a large amount of work for charity, the Law kindly turned a blind eye.

From what I read about these events, I get the impression that the regulations governing these matters needs revising, to bring it into line with current needs. I remember many years ago, that popular witty saga of the *Wireless World* "Free Grid" bringing up the same point. He said according to the Act, it was illegal for one person to convey information to another by other means than the written or spoken word or telephonic communication.

In his usual humorous way, he added, that as far as he could see, it was an indictable offence to wink at a pretty girl. I hope he was joking.

all in your **JUNE** issue!

## CBM 64 MUSIC KEYBOARD

A stylus keyboard, a proper conventional keyboard or a synthesiser keyboard can be added to the CBM 64 using our design. Thus enabling the excellent music facilities of the machine to be fully exploited.

## modems

What is a modem? What does it look like? What can I do with it? How much does it cost? How does it work? How was it designed? How does it use the telephone system? What kind of databases can I access with it? What about microcomputer compatibility? Enough! Enough!!

The answers to all these questions can be found in a three part series which begins in the June issue. It will offer a wide insight into the expansive world of modems and open up new avenues of exploration into a world of privately and publicly accessible databases.

## 'RUR' HOBBY ROBOT

This new design is intended to form the basis of a mobile robot system that can be developed and expanded in a number of ways. The basic mobile unit carries a rack mounted c.p.u., rechargeable power source, tray and arm mounting facilities.

PRACTICAL

# ELECTRONICS


ROBOTICS · MICROS · ELECTRONICS · INTERFACING

JUNE ISSUE ON SALE FRIDAY, MAY 3

# DIGITAL ELECTRONICS

D.W. CRABTREE BSc Tech Eng (CEI)

## PART EIGHT

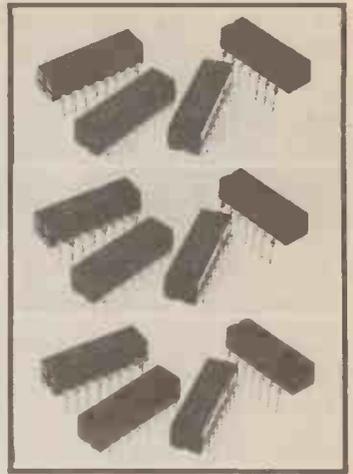

In the previous article in this series, we discussed microprocessor systems, their design and some of the decoding and memory mapping techniques that they employ.

In this, the final article of the series, we shall discuss the ways of using the information produced by the microprocessor (or by any other device).


### USE OF DATA

The data to which we now refer is the 8-bit (or 4-bit, 16-bit or 32-bit, dependent upon the type of system used) words produced by, say, a microprocessor system on the data lines. We shall not be discussing the application of these words within the system itself, since this is merely repeating what we have discussed earlier. We are, however, concerned with the use of controlling other devices using our data.

Some devices use the words directly from the data lines, whilst other devices require interface circuits connected either, via input/output ports or direct to the data lines. When devices are connected direct to the data lines it is generally necessary to provide decoding circuits in order to ensure that those devices are only "called" when required. Since we have already discussed decoding techniques in the previous article, there is no need for further explanation.

We shall only consider those devices which use a single bit of information, since, if they use more than one bit, the method is more than likely, simply repeated.


Suppose we are using an input/output port, which, although having the ability, as its name suggests, to either input or

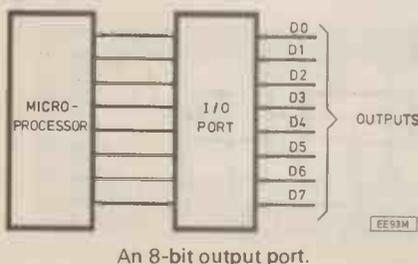

An 8-bit output port.

output information, is set to output data at the port only. This setting would be carried out using software control. We have, therefore, 8 bits of information being output from the system as shown in the diagram.


Now, we will assume that each of the 8 output lines contain information to control separate devices of some kind, which is quite likely and quite practical. The existence or not of data on the 8 lines is controlled by software commands, with, say, a "1" on the line being a request for the device to operate, whilst a "0" on the line is an instruction for the device not to operate. If devices are connected separately to the output lines, as we have suggested above, then we can operate none, one, or as many of the devices as we like, each independently of another, using program control. Hence we need only consider one of the lines, say output Do, as shown below.

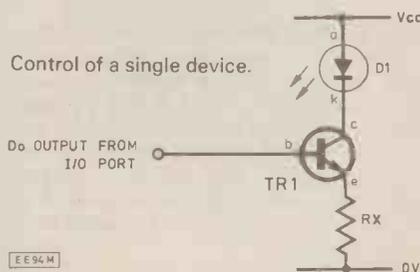

Now, suppose that only device that we need to operate is an l.e.d., that is we need to indicate whether or not our output line has a bit at logic 1. If it has, then we light the l.e.d., if not, the l.e.d. is not lit. Let us use the circuit shown, which is simply an l.e.d. driving circuit.

The output from the I/O port is fed into the transistor base. If the output is low, then the transistor will be switched off. If the output goes high, however, the transistor switches on and D1 is allowed to light, with the resistor Rx being the current limiting resistor for the device.

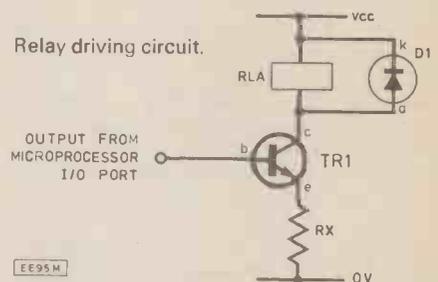Although the circuit is an analogue type, since a transistor is being used, which can be in any state between on and off, it should be remembered that here




only a high or low signal is available from the I/O port, with in-between states not permitted, therefore the transistor driving circuit will similarly only be working in either a high or a low state of conduction. In-between states will not exist.

Note also that the "Vcc" and "ground" connections shown on the circuit diagram may be the same as those used for the microprocessor system supply. Alternatively, another supply may be used for these functions, as long as the "ground" connection is attached to the microprocessor ground as a common.

Now, suppose we wanted to operate, say, a relay instead of an l.e.d. Then this is no problem, since we only have to put the relay in place of the l.e.d., with one or two other points considered. Firstly, the Vcc supply used should be a separate supply to that used by the microprocessor, but the ground connections should be made common as previously discussed. (The supply for the relay will probably need to be of a higher voltage anyway.) Secondly, since the relay is an inductive load to the circuit, a diode should be connected across the coil to protect the circuit from back e.m.f.s when switching takes place. Thirdly, the value of the resistor, to limit the current, and the type of transistor used, should both be carefully chosen. The circuit becomes that shown above.

If the devices to be operated involved the use of higher voltage supplies, say 50 volts d.c., then it may be necessary to use some other switching device, such as a VMOS device, which has the advantage of literally being able to dissipate any watts from only 1µA gate input. Shown opposite is a typical use of a VMOS, N-

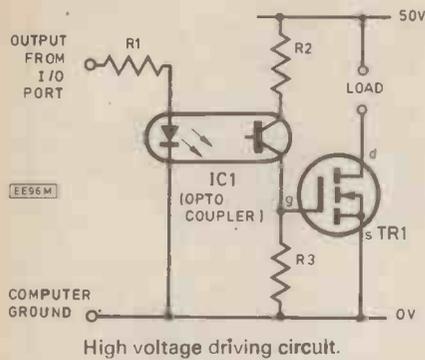
channel, device, as a drive to a 50V d.c. circuit.



Here, the output from the microprocessor I/O port is fed via a current-limiting resistor, R1, to an optocoupler which provides isolation between the TTL voltage levels and the higher voltage supply. Resistors, R2 and R3 provide a voltage-divider chain for the N-channel VMOS component, which drives the load as shown.

Above we have considered circuits which require d.c. supplies for the devices to be operated. If a.c. supplies are required, the triacs or other a.c. components should be considered as the driving device.

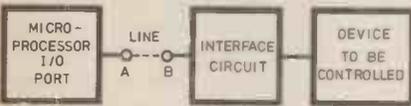We have now adequately provided background information to enable further research into interface circuits to be undertaken. Let us now consider the diagram below.



The basic interfacing format.

In our discussions above we have only considered the situation where the link between A and B, shown above, is a small distance. Then there is no problem here and the I/O port and the interface circuitry can be considered to be adjacent.

Now, however, suppose that the device to be operated is at some greater distance from the microprocessor I/O port, which is quite possibly the case when a remote control of the device is required. Suppose also that, instead of just one device being required to be operated, there are several controls to be sent to the remote location.

This gives us a problem, since, if we are working at TTL logic levels of 5 volts and 0 volts, then due to losses derived through cable resistances and/or wire resistances, there is a grave probability that the "high" levels output from the system cannot clearly be defined as "high" at the remote end of the system and malfunctions of the system would probably result.

We must therefore have some system which we can use to accept the outputs from the microprocessor I/O port and transmit to the remote end for control of


the devices there. This system performs the task of data transfer and the type of system utilised is dependent upon several factors:

**DATA FORMAT**—Is the data available in parallel or serial form? In the example above, the outputs from the I/O port will be in parallel form.

**DISTANCE OF THE TRANSMISSION**—Over very great distances, amplification may be required.

**REQUIRED SPEED OF THE TRANSMISSION**—Called the Data Rate, this need only be considered when overall speed of operation of a system is seen to be critical.

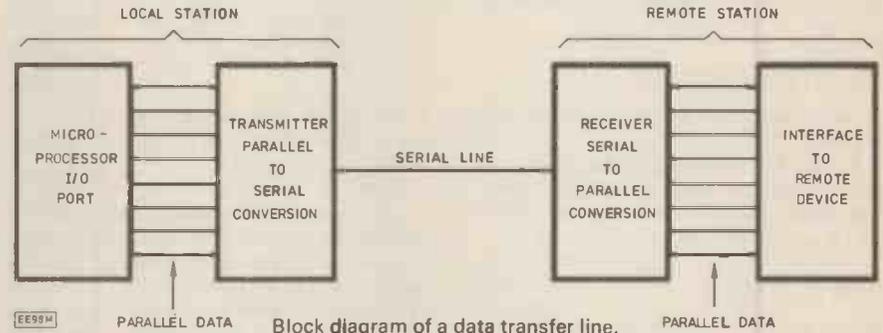**REQUIRED LEVEL OF INTEGRITY**—This is the accuracy required by the system in transmitting data



Block diagram of a data transfer line.

without any error in level detection at the remote end. Codes can be injected into the system to create a high level of integrity.

**SIGNAL TO NOISE PROBLEMS**—Any system suffers from electrical noise and, really, the greater the distance the data is to be transmitted, the greater the amount of noise picked up. We can, however, consider an ideal noise-free system here.

**CHANNEL CAPACITY AVAILABLE**—The transmission system used must have a limit to the number of channels available for transmission of data and this limit must be greater than the actual number of data channels required, or at least equal to that number. (In this latter case, there would be no allowance for any further channels to be added at a later date).

**TYPE (of transmission channel used).**

**DATA ENCODING**—Data can be encoded for transmission, this being generally essential, in some cases.


Generally, serial transmission of data is used for remote systems since only 2 wires (or a single fibre-optic link) would be required, hence a saving in cabling results. This system of transmission is shown below, in the block diagram.

It is seen, therefore, that we have a transmitter and a receiver at the local and remote ends respectively, with a parallel-to-serial and a serial-to-parallel conversion of data at the respective ends. Therefore, considering 8-bits of information produced at the microprocessor, bit 0 is transmitted first, followed by bit 1, bit 2, etc., until bit 7 has been transmitted, at which time bit 0 will be retransmitted and the cycle, or "scan" repeats. At the receiving end, the remote end, bit 0 will at first be received, then bit 1, etc.

To ensure correct operation a coding system is added to the transmitted data which is detected at the receiving end and this is used to ensure that the transmitter and the receiver are in phase so that bit 0 transmitted is detected as bit 0 and not as bit 4 say.
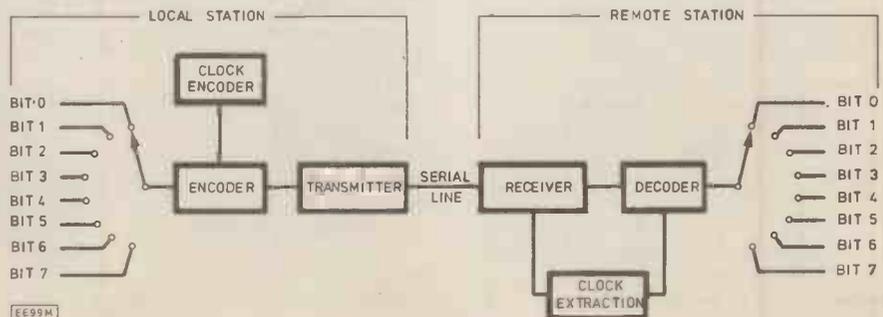
### TIME DIVISION MULTIPLEX

The basic type of transmission system is the T.D.M. or Time Division Multiplex system and gives operation similar to that described above. The name is derived from the task of splitting, or sharing, of a certain length of time between bits of information transmitted. In the simplest example, if 10 functions are to be transmitted in a time of 1 second then each function occupies 1/10th. second timespan. In practice, we are probably considering say, thousands of functions being transmitted in a 1/2 second timespan. Consider the diagram below, which shows the basic principle of the T.D.M. system.



The T.D.M. system.

Here, the 8 bits in our example are connected to a sequence switching system that takes each bit in turn and connects that bit to an encoder which gives a unique code for each bit. The encoded bit is then passed to the transmitter which puts the information out onto the serial link. At the receiver the information is decoded and the bit is output to the device relevant to that bit. Clock information is encoded at the transmitter end and extracted at the receiver end to ensure phases are the same at the two ends.

## DATA TRANSMISSION INTEGRITY

As previously mentioned, it is essential to check that the data transmitted is accurately received. Parity checking is one method used to prove integrity.


## PARITY CHECKING

Here we have a means of checking whether any one bit of a transmitted word is received in error. To do this, we always make sure that either an even number of bits (even parity) or an odd number of bits (odd parity) is transmitted.

A parity bit is generated at the transmitter and transmitted with the data. Let us consider even parity. Suppose we have the 7-bit word 1011101 to be transmitted. Then in this word there are 5 high bits. We must add a 1 to this to give an even number of high bits. This 1 to be added is the parity bit. Hence our word transmitted becomes 10111011. At the transmitter we have a parity generator and at the receiver we have a parity detector. Therefore, at the receiver we detect that the parity bit is 1 and, know-

ing that we are working with an even parity system, we know that, including the parity bit, there must be an even number of bits received that are "high". In this example, six "highs" are received so we know that the received word is correct. If only five "high" bits had been received then we would have detected an error and the word would have been rejected.

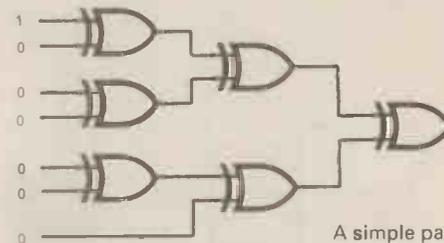Referring to the diagram below, a parity generator simply detects the number of 1's input and either gives a "1" or a "0" at the output, for even parity, to be used as the parity bit.



It is seen that the parity generator is a collection of EX-OR gates connected simply as shown. The parity receiver is similarly simply constructed.

The only disadvantage to parity checking is that, if an even number of bit errors occur, or indeed more than one bit error, then the parity check will not detect it, but the chance of two or more bit errors in an 8-bit word is very unlikely. For example:

7-bit word ..... 1000110  
 7-bit word + parity transmitted 10001101  
 7-bit word + parity received ... 10010101  
 receiver thinks 7-bit word is ... 1001010

..... wrong, but parity check does not discover any errors.

## HAMMING CODES

These are codes used for the detection and automatic correction of a single-bit error in a digital word. It is a repeated parity-checking procedure that checks the parity of one group of bits in the word, followed by another group, etc. By allowing overlapping of the groups, the actual position of the error can be detected and a correct bit generated. Instead of transmitting just 1 parity bit with, say, a 7-bit word, several Hamming bits are transmitted. The use of Hamming codes was developed in 1950 and the methods can be found to be aptly described in most books on data transmission. □

EE100M

*The above article concludes this series entitled Digital Electronics. In the series, I have tried to give an introduction to this subject for those who have little or no understanding of it. It would be impossible to go into very great detail on a widespread subject such as this in a short series of articles, such as this has been, however, we do hope that the series has been constructive and has provided a basis for further research into the subject.*

# PLEASE TAKE NOTE

## Sound Operated Flash (September 1984)


The stripboard and component layout on page 575 was incorrect and should be constructed as shown in the diagram opposite.

## Headlight Activated Switch (March 1985)

The earth lead to the light in Fig. 2 on page 137 should be common to the Mains In Earth, and *not* to the neutral as shown. Also, D3 cathode resistor (R12, 470) is not shown.

In Fig. 3, there should be a link between rows F and G, column 20.

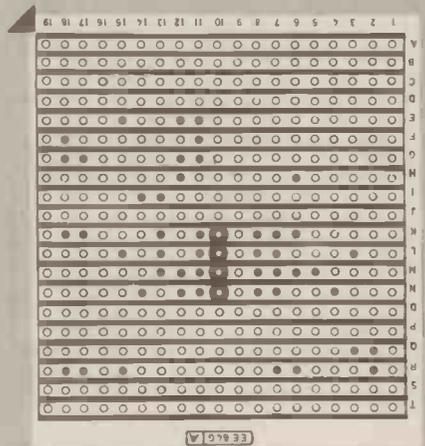
The wiring diagram, Fig. 5, should show row N connected to earth, and row B connected to JK1 input. They are transposed as published.


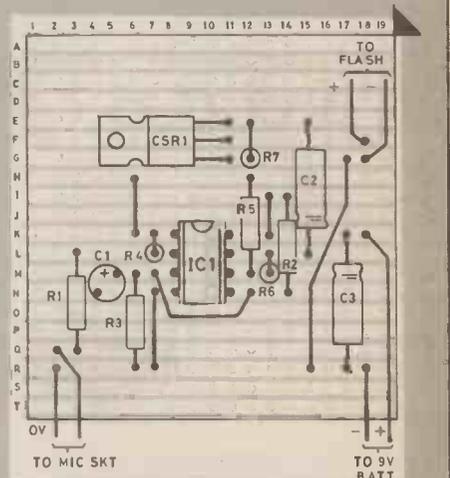
## Motorcycle Codelock—Circuit Exchange (February 1985)

Page 121. On the circuit diagram diode D1 is not an l.e.d.

In the last paragraph:  
 Line one; IC1c should read IC2a.  
 Line five; IC1d should read IC2b.  
 Line seven; IC1d should read IC2a.



## Digital Electronics—Part 5 (February 1985)

Pages 114 and 115. The two circuit diagrams of the Binary-Up and Binary-Down counters are transposed. Diagram EE60M should be in the place of EE58M and vice-versa.

## BAKERS DOZEN PARCELS

All the parcels listed below are brand new components. Price per parcel is £1.00, but if you order 12 you get one extra free.

- 1 - 5 13 amp ring main junction boxes
- 2 - 5 13 amp ring main spur boxes
- 3 - 25 13 amp fuses for ring mains
- 4 - 5 surface mounting switches suitable insulated for mains voltage
- 5 - 3 flush electrical switches intermediate type, will also replace 1 Or 2 way switches
- 6 - 5 in flex line switches
- 7 - 4 in flex line switches with neons
- 8 - 280 watt brass cased elements
- 9 - 2 mains transformers with 6v 1a secondaries
- 10 - 2 mains transformers with 12v 1/2a secondaries
- 11 - 1 extension speaker cabinet for 6 1/2" speaker
- 12 - 5 octal bases for relays or valves
- 13 - 12 glass reed switches
- 14 - 4 OCP 70 pico resistors
- 15 - 25 assorted germanium transistors OC45 etc
- 16 - 4 tape heads, 2 record, 2 erase
- 17 - 2 ultra sonic transmitters and 2 ditto receivers
- 18 - 2 15000 mfd computer grade electrolytics
- 19 - 2 light dependent resistors similar ORP12
- 20 - 5 diff micro switches
- 21 - 2 mains interference suppressors
- 22 - 2 25 watt crossover units
- 23 - 1 40 watt 3 way crossover unit
- 24 - 250 various screws and self tappers
- 25 - 1 of each wafer switches - 6p 2 way; 4p 3 way; 2p 6 way; 1p 12 way
- 26 - 2 tape deck counters
- 27 - 1 6 digit counter 12v
- 28 - 1 6 digit counter mains voltage
- 29 - 1 BOAC In Light stereo unit (second hand)
- 30 - 2 Nicad battery chargers
- 31 - 1 key switch with key
- 32 - 2 humidity switches
- 33 - 2 aerosol cans of ICI Dry Lubricant
- 34 - 96 x 1 metre lengths colour-coded connecting wires
- 35 - 4 battery operated model motors
- 36 - 2 air spaced 2 gang tuning condensers
- 37 - 2 solid dielectric 2 gang tuning condensers
- 38 - 10 compression trimmers
- 39 - Long and Medium wave tuner kit
- 40 - 4 x 465 KC IF transformers
- 41 - 8 Rocker Switches 10 amp Mains SPST
- 42 - 6 Rocker Switches 10 amp Mains SPDT
- 43 - 5 Rocker Switches 10 amp SP DT Centre Off
- 44 - 4 Rocker Switches 10 amp DPDT
- 45 - 1 24 hour time switch mains operated
- 46 - 1 6 hour clockwork timeswitch
- 47 - 2 lever switches 4 pole changeover up and ditto down
- 48 - 2 6v operated reed switch relays
- 49 - 10 neon valves - make good night lights
- 50 - 2 x 12v DC or 24V AC 4CO relays
- 51 - 1 x 12v 2C 0 very sensitive relay
- 52 - 1 x 12v 4C 0 relay
- 53 - 2 mains operated relays 3 x 8 amp changeovers (secondhand)
- 54 - 10 rows of 32 gold plated IC sockets (total 320 sockets)
- 55 - 1 locking mechanism with 2 keys
- 56 - Miniature Unselector with circuit for electric jigsaw puzzle
- 57 - 5 Dolls' House switches
- 58 - 2 telephone hand sets incorporating ear piece & mike (shand)
- 59 - 2 flat solenoids - ideal to make current transformer etc.
- 60 - 5 ferrite rods 4" x 5/16" diameter aerials
- 61 - 4 ferrite slab aerials with L & M wave coils
- 62 - 4 200 earpieces
- 63 - 1 Mullard Thyristor trigger module
- 64 - 10 assorted knobs & spindles

With most items quantity buyers get good discounts and save on postage costs.

## SOUND TO LIGHT UNIT



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form or £25.00 assembled and tested.

## MINI MONO AMP

on p.c.b., size 4" x 2" (app.) Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.



## The AMSTRAD Stereo Tuner.

This ready assembled unit is the ideal tuner for a music centre or an amplifier, it can also be quickly made into a personal stereo radio - easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 - 270 KHz, medium wave band 525 - 1850KHz, FM band 87 - 108MHz, mono, stereo & A.C. switchable, fully assembled and fully aligned. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial (note ferrite rod aerial is included for medium and long wave bands. All made up on very compact board Offered at a fraction of its cost: **only £6.00** + £1.50 post + insurance.

## 25w SPEAKER SYSTEMS

By Amstrad

25 watt RMS loading 8" woofer, 4" tweeter with crossover. £12.00 per pair + £4 post. New and unused but cabinets slightly damaged hence this low price, carry our normal guarantee.

## CAR STARTER/CHARGER KIT


Fiat Battery! Don't worry you will start your car in a few minutes with this unit - 250 watt transformer, 20 amp rectifiers, case and all parts with data £16.80 or without case £15.00, post paid.

## 4/5A BATTERY CHARGER

Transformer and rectifier £3.95 & £1 post, 3 kits £12 post paid.
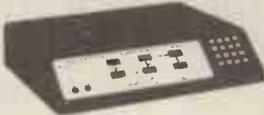
## PRESTEL UNITS

These are brand new and we understand tested, came with manufacturer's guarantee now void as the manufacturer no longer trades. These originally sold for over £150. We offer them complete, except for 7 plug in i.c.'s and price is only £14.95 less than the value of the modem included.



## STABILISED POWER SUPPLY (Mains Input)

By LAMDA (USA) - Ideal for computer aid-ons, d.c. output. Regulated for line volts and load current. Voltage regulation .1% with input variations up to 20% - load regulation 1% from no load to full load - or full load to no load. Complete in heavy duty case - Models available 5v - 9A £23. 12v - 1.5A £13.25. 15v - 1.2A £13.25. 24v - 2A £23.

## 25A ELECTRICAL PROGRAMMER

Learn in your sleep: Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £2.50.



## THIS MONTH'S SNIP

### TOP OF THE POPS LIGHTING if you use our disco switch

These have 12 x 10 amp changeover switches each rated at 10 amps so a whole street could easily be lit with one. Switches adjustable and could be set to give a running light, random flashes, etc. etc. 230 volts main operation. Brand new, made by Honeywell. Offered at approximately one third of cost. **ONLY £6.90**

## COMPUTER DESKS

Again available Computer desks - size approx 4' x 2' x 26" high - formica covered, cost over £100 each. Our price only from £9.50 - you must collect - hundreds supplied to schools.



## FROZEN PIPES.

Can be avoided by winding our heating cable around them - 15 mtrs connected to mains costs only about 10p per week to run. Hundreds of other uses as it is waterproof and very flexible. Resistance 60 ohms/metre, Price 28p/metre or 15m for £3.95

## FLEXIBLE EXTENSION LEAD

twin rubber 5mm ideal grass cutter etc. 250 metre coil £25.00. 50 metre coil £6.75

## 50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amp meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10kg parcel contains not less than 1,000 items - panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, 90% are unused components.

**YOURS FOR ONLY £11.50 plus £3.00 post.**

## REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Franco Company this is a very robust motor size approximately 7/8" long, 3/8" dia, 3/8" shaft Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

- 1 Franco motor with gear box
- 1 manual reversing & on/off switch
- 1 push to start switch
- 2 limit stop switches
- 1 circuit diag. of connections

£19.50 plus postage £2.50

## J. BULL (Electrical) Ltd.

(Dept EE) 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU

Established 30 YEARS

PRICES: All prices include VAT.

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £12 add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclay orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote. Shop open 9.00 - 5.30, Mon to Fri, not Saturday.

## VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95, without case, metal case - £2.95, adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30. Ex-Electricity Board. Guaranteed 12 months.



## EXTRACTOR FANS - MAINS OPERATED


- Woods extractor.
- 5" - £5.75, Post £1.25.
- 6" - £6.95, Post £1.25.
- 5" Planair extractor £6.50, Post £1.25.
- 4" x 4" Muffin 115v. £4.50, 230v. £5.75, Post 75p.

All the above ex-company, those below are unused.

4" x 4" £8.50, Post 75p.

9" American made £11.50, post £2.00.

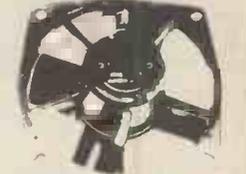Tangential Blower 10x3 air outlet, dual speed £4.60, Post £1.50.



## TANGENTIAL BLOW HEATER

by British Solartron, as used in best blow heaters. 3Kw £6.95 complete with 'cold' half and 'full' heat switch, safety cut out and connection diagram.



Please add Post £1.50 for 1 or 3 for £20 post paid 2.5 Kw KIT Still available: £4.95 + £1.50 post, or have 3 for £16 post paid

## ROCKER SWITCHES

Standard size 1ft 11.5 x 28 mm cut out. Single pole on/off - 15p each 1000 for £75. Single pole changeover 20p each - 1000 for £100. Single pole changeover with centre off - 25p each - 1000 for £125. Single pole on/off with neon - 36p - 1000 for £180.

## ROCKER SWITCH DP/DT

15 amp 250 volts suitable for motor reversing etc. - 46p - 100 for £34.50, 1000 for £230.

## MICRO SWITCHES

V3 type all 250 10 amp SpSt 20p 1000 - £100. Spdt 30p 1000 - £150, very low tongue Spdt. 40p 1000 for £200.

## EX-G.P.O. TELEPHONES

Black heavy type £5.50  
Lightweight 746 type £7.50  
Ex-G.P.O. plug £1.00  
Ex-G.P.O. socket £1.00

## WALL MOUNTING ROOM THERMOSTAT

By Danfoss has a really pretty two tone grey case with circular white scale and dial. Setting temperature from 0 - 30c - 13 amp 250v contacts. Price £4.60. - 10 for £40.

## BLEEPERS

6 or 12v battery or transformer operated, ideal for using in alarm circuits but particularly suitable for can and motor supply alarms. These give a loud shrill note. Price 69p. 1000 for £345. Jap made.

## MINIATURE WAFER SWITCHES

2 pole, 2 way - 4 pole, 2 way - 3 pole, 3 way - 4 pole, 3 way - 2 pole, 4 way - 3 pole, 4 way - 2 pole, 6 way - 1 pole, 12 way. All at 25p each or 10 for £2.00

## 12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/4" spindle - Price £3.45. Ditto, but double ended £4.25.

## MAINS MOTORS

We have very large stocks of motors from 2 watts to 1/2 hp. Most at a price well below cost, let us know your requirements.

## IONISER KIT


Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included. £11.95 plus £2.00 post.

## OTHER POPULAR PROJECTS

- R C Bridge Kit £9.95
- 3 Channel Sound to Light - with fully prepared metal case £14.95
- Big Ear, listen through walls £9.50
- Silent sentinel Ultra Sonic Transmitter and receiver £9.50
- Car Light 'left on' alarm £3.50
- Secret switch - fools friends and enemies alike £1.95
- 3 - 30v Variable Power Supply £13.80
- 2 Short & Medium wave Crystal Radio £3.99
- 3v to 16v Mains Power Supply Kit £1.95
- Radio stethoscope - fault finding aid £4.80
- Mug stop - emits piercing squawk £2.50
- Morse Trainer - complete with key £2.99
- Drill control kit £3.95
- Interrupted beam kit £2.50
- Transmitter surveillance kit £2.30
- Radio Mike £6.90
- F M receiver kit - for surveillance or normal F M £3.50
- Insulation Tester - electronic megger £7.95
- Battery shaver or fluorescent from 12v £6.90
- Matchbox Radio - receive Medium Wave £2.95
- 40 watt amp - hifi 20hz - 20kHz £9.50
- 115 Watt Amplifier 5Hz 25kHz £13.50
- Power supply for 115 watt amps £8.50

# FUNTRONICS WITH A/D/O CONTROL

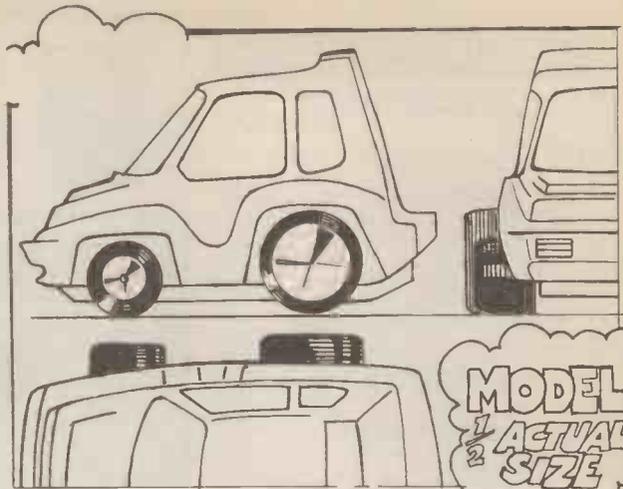
PART 2 (OF 3 PARTS) WILL LOOK AT THE RECEIVER (R&X FOR SHORT) COMPLETE COMPONENT LISTS WILL BE GIVEN IN PART 3



MODEL 1/2 ACTUAL SIZE
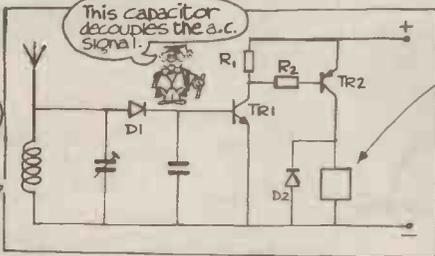
## DIODE CARRIER RECEIVER

This circuit is ideal for getting into a RC model quickly. It's very simple & cheap but has a short range.



Recognise the tuned circuit?

This box may be a relay or some other device. If it is a relay then Diode D2 is required to suppress the back emf developed in the relay winding.

### ABOUT the CIRCUIT

Normally (ie without signal) TR1 doesn't conduct nor does TR2

STARTS ARRIVES. D1 provides positive bias for NPN transistor TR1. Collector current passes through R1 moving the base of the PNP transistor TR2 to negative thus allowing TR2 to pass current. R2 limits base current

## INDUCTANCE



The simplest type of tuning coil is an OPEN winding of solid wire.

$$L(\text{inductance}) = \frac{N^2 \times \mu \times \pi \times R^2}{9R \times 10^9}$$


N = number of turns  
L = Length  
R = Radius

The above formula will give L (inductance) but note there are 3 variables and you must assume 2 values to find the 3rd.
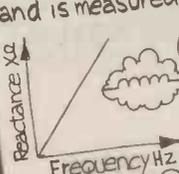
## PROF

To Fully understand the RECEIVER (and Transmitter) we must give close examination to the INDUCTOR & CAPACITOR. Let's have a look at the INDUCTOR & CAPACITOR together...

INDUCTORS & CAPACITORS offer a resistance to the flow of ALTERNATING CURRENT. Although it is not called RESISTANCE but REACTANCE (X) and is measured in OHMS



The reactance of an inductor INCREASES with frequency

The formula for this property is...

$$X_L = 2\pi f L$$

L is inductance in HENRIES

f is frequency in Hz

Spend some time studying these graphs



The reactance of a capacitor DECREASES with frequency

The formula for this property is...


$$X_C = \frac{1}{2\pi f C}$$

C is Capacitance in FARADS

It may be clear by now that INDUCTIVE & CAPACITIVE reactance are in ANTI-PHASE i.e. they have a phase difference of 180°. Let's have a look at how we arrive at the PHASOR sum of Inductance Capacitance... and resistance before looking at the tuned circuit.




### 1 G & L in series

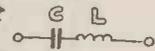


If  $X_L = 80 \Omega$   
 $X_C = 20 \Omega$   
then  $X = X_L - X_C$   
 $= 80 - 20$   
 $X = 60 \Omega$  (Inductive)

### 2 L & R in series

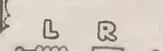


Here we must introduce IMPEDANCE (Z). Impedance is simply the TOTAL opposition to A.C. i.e. INDUCTIVE, CAPACITIVE & RESISTIVE. By applying Pythagoras we see that  $Z = \sqrt{X_L^2 + R^2}$

### 3 G & R in series

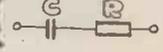


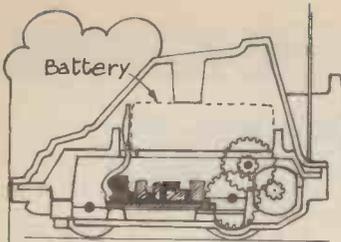And of course when a Capacitor is in series with a resistor we have  $Z = \sqrt{X_C^2 + R^2}$




Battery

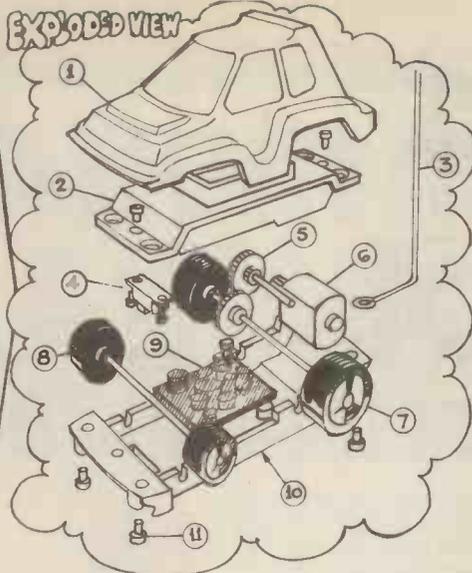- ① Body
- ② Battery house
- ③ Aerial
- ④ Switch
- ⑤ Intermediate gear (mounted in item 2)
- ⑥ motor
- ⑦ Rear wheels with gear
- ⑧ front wheels
- ⑨ Circuit
- ⑩ Base
- ⑪ Screws


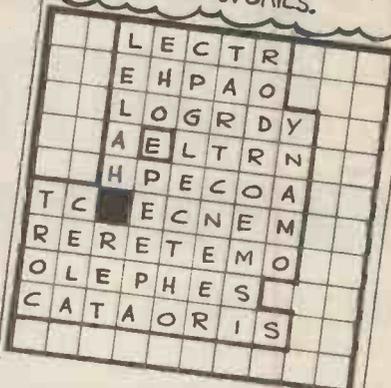
# BRAINBUSTER LINK-UP

Link-up the letters to form a chain of words related to electronics.



Start at **E** and find only 3 words.

- 1st word **GLUE** ...brain voltages...
- 2nd word ...produce a square law deflection...
- 3rd word ...ions through membrane.

## COLOUR CHANNELS

This is where the super-het receiver must be used. A coloured strip flying from the transmitter clearly indicates Tx & Rx frequency so avoiding interference with other transmitters. The Superhet is used because both Tx & Rx crystals must be changed.


colour	Tx	Rx
Black	26.970	26.515
Brown	26.995	26.540
Red	27.045	26.690
Orange	27.095	26.640
Yellow	27.145	26.690
Green	27.195	26.740
Blue	27.245	26.790
white	27.275	26.820

IF = 455KHz.


by Thakery

Solutions on page 290

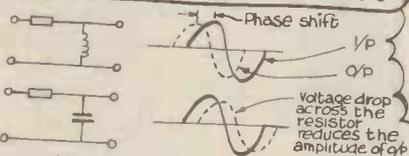Let's see what happens to an output when taken across the inductor and Capacitor in the RC & RL circuits




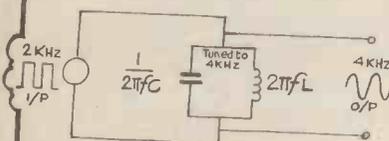NOW, let's have a look at the TUNED circuit...



The whole purpose of a TUNED circuit is to select a frequency (or harmonic) from the input.

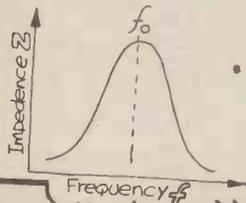This occurs at the **RESONANT** frequency ( $f_0$ ) or when...



This formula will give the frequency at which the circuit will resonate

$$2\pi f C = 2\pi f L$$

$$(2\pi f)^2 LC = 1$$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$\therefore f_0 = \frac{1}{2\pi\sqrt{LC}}$$

# RECEIVERS Rx

## ① the SUPERHET (crystal controlled)

This Receiver is popular because of its **STABILITY** & **SENSITIVITY**. It responds extremely well to the intended signal so that more than one model can be operated simultaneously and it is not **TOUGH** with regard to **POSITION** & **LENGTH** of **AERIAL**. SUPERHET is short for **SUPERHETERODYNE**. The incoming signal is **MIXED** with a locally generated signal to produce an **INTERMEDIATE** frequency which is then **AMPLIFIED** and then **DEMODULATED**.

## ② the SUPER REGENERATIVE

This is a much easier receiver to build than the Superhet. The Single regenerative **DETECTOR** replaces the **MIXER**, **OSCILLATOR**, **INTERMEDIATE FREQUENCY** Amplifier and **DEMODULATOR**. Of course it has certain disadvantages. It lacks the **CRYSTAL** controlled stability of the Superhet oscillator and so can respond to other transmitters.

## ③ the DIODE CARRIER RECEIVER

Now this is a very simple type and operates from the **UNMODULATED** carrier. We'll be looking at this type for the Receiver and Transmitter...

# CARAVAN INDICATOR CONTROL



T.R.de Vaux Balbirnie

**W**IRING the 7-pin socket for a caravan electrical system is a straightforward job. As many have found to their cost, however, it is unwise to connect the additional flashing indicator lights direct to the car system. At the very least this will cause a change in operating speed. At worst, the flasher unit will overheat and fail.

## ALTERNATIVE

The usual solution is to use a "heavy duty" flasher unit to replace the standard one. Alternatively, a *relay* may be used to relieve the existing unit of the extra load.

This project is a type of relay but without moving parts—the switching action is performed by *transistors*. If carefully constructed, it should give indefinite service. The Caravan Indicator Control meets UK Vehicle Lighting Regulations and, as described, is suitable for all trailers towed by negative-earth cars. By using alternative transistors it may be made for use with positive-earth vehicles.

## LAMP FAILURE

An important feature of this circuit is that a warning is given if a caravan indicator bulb fails as soon as this happens. Normally, a dashboard indicator light remains *off* until a turn is signalled—it then flashes in sympathy with the existing warning light. Should a filament fail, however, the new indicator will light immediately and glow continuously. If a spare bulb is carried, then the fault may be corrected before causing danger to other road users. Faulty wiring or poor earth connections will cause the warning light to flash intermittently.

## HAZARD OPERATION

If the towing vehicle has a "hazard" system whereby all four flashing indicators can be switched on together, the Caravan Indicator Control will operate both additional lights and all six will flash together. Although the dashboard indicator lamp will not operate under these conditions the existing hazard warning light gives a reminder that the system is switched on.

## CIRCUIT DESCRIPTION

The entire circuit for the Caravan Indicator Control is shown in Fig. 1. TR1 and TR3 drive power transistors TR2 and TR4 which have the caravan flashing indicator lamps, LP1 and LP2, connected in their emitter circuits. TR1 and TR2 are used for left turn signals while TR3 and TR4 are used for right ones. The appropriate transistors turn on when a small base current flows from the existing car system through R1 or R2 as appropriate. This current is so low as to have negligible effect on the flasher unit.

The rest of the circuit consisting of TR5, TR6 and associated components form a type of Exclusive-OR gate. There were problems with early circuits using integrated circuit gates and the present design is better suited to the "noisy" conditions of the car charging system. The gate is used to monitor voltage levels at the points A and B. In the following description, a voltage near to +12V is referred to as High, while near-zero voltage is called Low.

If either two Highs or two Lows are applied to the inputs of the gate (points A and B) then the warning indicator, LP3, will remain *off*. With one High and one Low input, it will switch *on*. When driving without the caravan, both inputs will be High (since they are connected to the battery positive through R3 and R4) and LP3 will be *off*. When a caravan is being

towed, the low-resistance filaments of LP1 and LP2 keep both inputs Low so, again, LP3 will be *off*. When a left turn is signalled point A will pulse between High and Low states while point B remains Low so LP3 will flash. For right turns a similar situation arises with Point B pulsing between the two states and point A remaining Low.

If either LP1 or LP2 should fail, then the appropriate point A or B will go High, causing LP3 to glow continuously. In "hazard" operation, both inputs pulse between High and Low states together so LP3 will remain *off*. Faulty indicator lamp connections will cause intermittent flashing of LP3.

## GATE

The gate works in the following way. Consider a left-hand turn signal—point A keeps pulsing High and turning on TR6. Current then flows through R7, LP3 and TR6. If a right turn is signalled current will flow through R8, LP3 and TR5. If TR5 and TR6 are both on or off together, then both terminals of LP3 will be at the same voltage and it will remain *off*.

Since LP3 derives current through R7 or R8, these components will become warm and must be adequately rated. Moreover, there will be 6V approximately "dropped" across the working resistor so LP3 must be a 6V lamp of the correct current rating (see components list). With

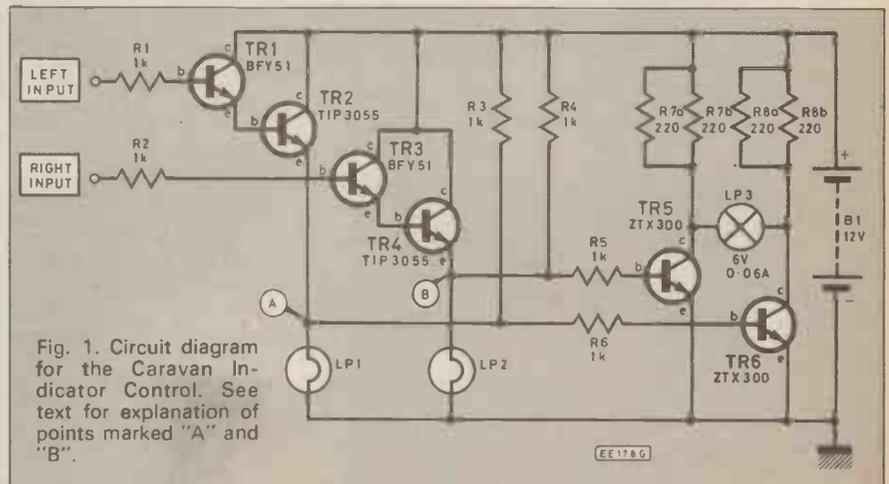


Fig. 1. Circuit diagram for the Caravan Indicator Control. See text for explanation of points marked "A" and "B".


the ignition switched *on* and no caravan in tow, both TR5 and TR6 will be *on* and current will flow through R7 and R8 continuously. The only consequence of this is that the case becomes slightly warm after a period of time.

## CONSTRUCTION

Note: an *aluminium* case must be used for this project—not a plastic one. Refer to Fig. 2 and construct the circuit panel using a piece of 0.1in. matrix stripboard size 12 strips by 22 holes. Drill the two fixing holes, make the breaks in the copper strips in the positions shown and follow by soldering the on-board components as indicated.

In the prototype, R7 and R8 each consisted of two off 220 ohm  $\frac{1}{2}$ W resistors connected in parallel. Alternatively, single 100 ohm 1W components could be used. Whichever method is employed, the resistors must be mounted well clear of the circuit panel and spaced away from one another to allow a free flow of air. When complete, the panel should be examined carefully for wiring errors and for accidental “bridging” between adjacent copper tracks. Solder connecting wires to strips A, D, E, F, G, H, I, J, K and L.

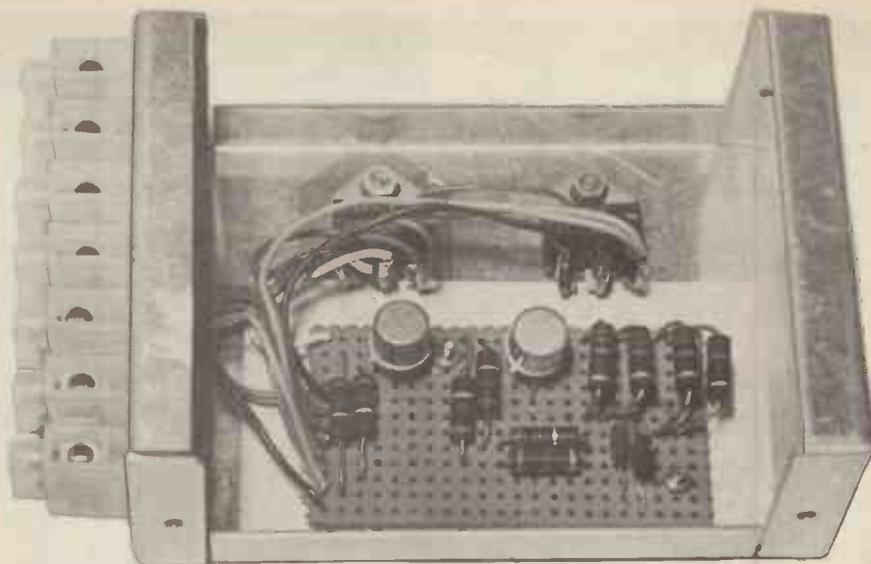Refer to the photograph and prepare the case to accept the panel. Drill a hole next to the terminal block position and fit a rubber grommet. This is to carry the wires passing through from the inside. Drill mounting holes to correspond with those already drilled in the panel. Secure the panel and the offboard components



noting that TR2 and TR4 require mounting kits so that they are *electrically isolated* from the case. A piece of thick cardboard should be placed between the underside of the panel and the case to provide insulation.

Make certain that there are no sharp protrusions which could penetrate the cardboard and cause short circuits. Check that R3 cannot short circuit to the upper panel fixing. In the prototype, the earth (battery negative) connection was made by means of a “flying lead”. Alternatively, an extra terminal on the block connector could be used.

## POSITIVE EARTH

Although a positive-earth prototype was not tested, there should be no problems if the alternative pnp transistors are used (see components list).

## INSTALLATION

Find a suitable place for the completed project. Behind a trim panel in the rear of the car is a good choice. Refer to Fig. 2 and make the terminal block connections. Begin by wiring the dashboard indicator light connections to terminals 6 and 7

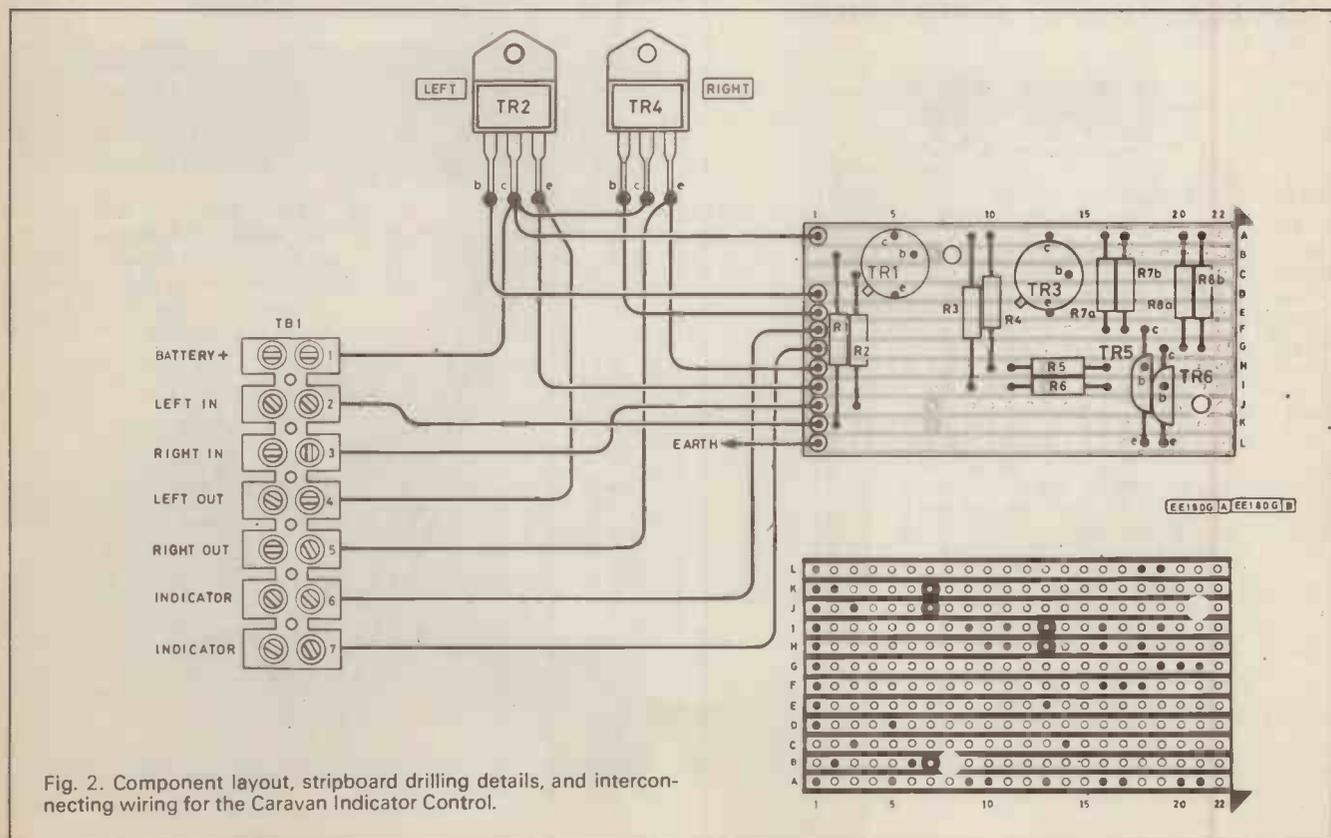


Fig. 2. Component layout, stripboard drilling details, and interconnecting wiring for the Caravan Indicator Control.

using light-duty twin wire—loudspeaker wire, for instance. Using stranded auto-type wire of 5A rating minimum connect terminals 4 and 5 respectively to the left and right-hand caravan flashing indicator circuits (pins 1 and 4 on the 7-pin socket). Connect terminals 2 and 3 respectively to the left and right-hand car direction indicator circuits using similar wire. Connectors are available from caravan accessory shops which enable this to be done without breaking the wires.

## FUSE

Connect terminal 1 to a fuse which is live only when the ignition is switched on. Use a small 12-volt bulb with one terminal earthed to a metal part to find a suitable fuse. Make sure that the correct side of the fuse is used—check by removing it that the test lamp goes off. Connect the flying lead to an existing earth point or, if one cannot be found nearby, drill a small hole and use an eyelet secured with a self tapping screw.

## TESTING

Connect the caravan plug to the 7-pin socket and switch the ignition on. Check that the direction indicators all work correctly with the dashboard light signalling the turns. Remove each caravan flashing indicator bulb in turn to simulate

# COMPONENTS

## Resistors

R1-R6 1k  $\frac{1}{2}$ W  $\pm 5\%$  (6 off)  
R7,R8 220  $\frac{1}{2}$ W (4 off) or  
100  $\frac{1}{2}$ W (2 off). See text.

## Semiconductors

TR1,TR3 BFY51 *nnp* silicon (2 off)  
TR2,TR4 TIP3055 *nnp* silicon (2 off)  
TR5,TR6 ZTX300 *nnp* silicon (2 off)

NOTE: for positive-earth cars the following alternative transistors should be used.

TR1,TR3 BC461 *pnp* silicon (2 off)  
TR2,TR4 TIP2955 *pnp* silicon (2 off)  
TR5,TR6 ZTX500 *pnp* silicon (2 off)

Approx. cost  
Guidance only

See  
**Shop  
Talk**

page 256

## Miscellaneous

AB9 aluminium box size 102 x 70 x 38mm.  
0.1in. matrix stripboard size 12 strips by 22 holes.  
5A terminal block—7 sections needed.  
Mounting kits for TR2 and TR4—2 off.  
Panel lampholder fitted with 6V 0.06A bulb.  
Light duty twin wire; 5A minimum stranded auto wire.  
Connectors, fixings, rubber grommet.

**£6.00**


failure of the filaments—the dashboard indicator should now light continuously. Check “hazard” operation—note that the ignition must be switched on for the caravan lights to work. If all is well, the

trim panel may be replaced and the unit forgotten. It should give years of reliable service, and the only time you should be aware of its presence is when the dashboard light signals a failed bulb.

## FUNTRONICS Solutions...
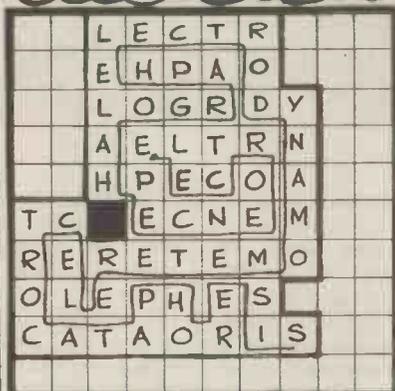
### LINK-UP

Link-up the letters to form a chain of words related to electronics.



1<sup>st</sup> ELECTROENCEPHALOGRAPH  
2<sup>nd</sup> ELECTRODYNAMOMETER  
3<sup>rd</sup> ELECTROCATAPHORESIS

## FOR QUALITY COMPONENTS BY MAIL ORDER

# ELECTROVALUE

**FREE**  
44 PAGE  
PRICED AND  
ILLUSTRATED  
CATALOGUE  
ON REQUEST

**FREE POSTAGE**  
GOOD DISCOUNTS  
GOOD SERVICE  
THOUSANDS OF  
STOCK ITEMS  
PHONE YOUR ORDER  
ACCESS OR  
BARCLAYCARD

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham,  
Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475  
North Branch, 680 Burnage Lane, Manchester M19 1NA  
Phone 061 432 4945

Please mention this publication when replying

# NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

## LIGHT PIPE

FOR use in those inaccessible corners, AEG-Telefunken (UK) have introduced a range of specially constructed l.e.d.s utilising a flexible optical guide to

## PRINTER INTERFACE

THE latest addition to the range of Eprom based Copy routines from Euroelectronics is

transmit light for distances up to 2 metres.

The "light pipe", which they claim offers the designer much more flexibility when designing equipment layouts, may be positioned on a printed circuit board and used to provide a visual front panel indication to a remote part of the equipment.

Available in standard 0.5, 1.0, 1.5 and 2.0 metre lengths, the light pipe may be cut and polished at any point in its length to suit the required application. The l.e.d. colours available include red, yellow and green.



The flexible transmission guide may also be fitted to a photosensitive detector to form one half of a matched pair for high voltage isolation applications. This would be ideal for many control and automation operations, including optical card/tape readers, counting and lighting control.

Further details may be obtained from:


**AEG-Telefunken (UK) Ltd.,**  
Dept EE, 217 Bath Road,  
Slough, Berks SL1 4AW.

## GOOD RECEPTION

THE release of a new TV aerial for mobile or static use, the subject of a provisional patent application, is announced by Maxview Aerials. Known as the Omnimax, it is claimed to take account of the fact that vehicles on the move will change their position relative to the siting of the transmitter, thus, in some cases, affecting the reception.

As its title implies, the aerial is claimed to overcome the directional problems by providing 360 degrees coverage. This is achieved by the use of a 12/24V d.c. High Gain Amplifier (22dB) and a novel "array" arrangement.

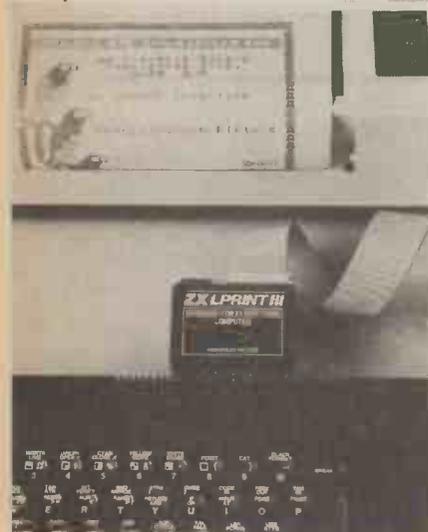Another feature is that it is "tuned" to cover the whole of the international u.h.f. television spectrum from 470 to 860MHz, channels 21 to 69. This makes it ideal for installing in sea craft, caravanettes and caravans when touring.



the ZXLPrint 111 printer interface for the Spectrum computer.

Full colour screen dumps can be carried out on Epson JX80 and Seikosha GP700 printers while four colour screen dumps for CGP115 and MCP40 are available as an option.

The ZXLPrint interface costs £34.95 and a cable—either Centronics or RS232—is available for the sum of £9.95. For further details and information on range of computer add-ons contact:

**Euroelectronics,**  
Dept EE, 26 Clarence Square,  
Cheltenham, Glos. GL50 2JP.

## SHURE SOUND

AT a time when there seems no end to the effects of the US dollar, it makes a welcome change to report that the world famous American Shure audio equipment specialists have launched a new product that slots at the lower price end of the market.

An ideal choice for the beginner whose budget cannot stretch to the headier heights of most Shure microphones, the new Shure Prologue line is an excellent

"starter" mic for vocalists, musicians or audio/video hobbyists.

There are three models, all available in high or low impedance versions and retail prices including VAT start at under £25. Each model is manufactured in diecast metal and features an on/off switch, XLR connector and is furnished with a swivel adaptor.

Further details and prices for the Shure Prologue range may be obtained from:

**HW International,**  
Dept EE, Efen Grove,  
London, N7 8EQ.

Designed for use on land or water vehicles, the Omnimax aerial sells, complete with amplifier, for the sum of £39.50 including VAT and comes complete with five metres of low-loss coaxial cable fitted with standard TV plugs at both ends. Two versions are available, for horizontal surface fixing or mast top fixing.

Further information may be obtained from:

**Maxview Aerials Ltd.,**  
Dept EE, Maxview Works,  
Setchley, King's Lynn,  
Norfolk, PE33 0AT.

# PRINTED CIRCUIT BOARD SERVICE

Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Black Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed here.

PROJECT TITLE	Order Code	Cost
— JULY '83 —		
User Port Input/Output <i>M.I.T. Part 1</i>	8307-01	£4.82
User Port Control <i>M.I.T. Part 1</i>	8307-02	£5.17
— AUGUST '83 —		
Storage Scope Interface, BBC Micro	8308-01	£3.20
Car Intruder Alarm	8308-02	£5.15
High Power Interface <i>M.I.T. Part 2</i>	8308-03	£5.08
Pedestrian Crossing Simulation <i>M.I.T. Part 2</i>	8308-04	£3.56
Electronic Die	8308-05	£4.56
— SEPTEMBER '83 —		
High Speed A-to-D Converter <i>M.I.T. Part 3</i>	8309-01	£4.53
Signal Conditioning Amplifier <i>M.I.T. Part 3</i>	8309-02	£4.48
Stylus Organ	8309-03	£6.84
Distress Beacon	*8309-04	£5.36
Distress Beacon Pocket Version	8309-05	£3.98
— OCTOBER '83 —		
D-to-A Converter <i>M.I.T. Part 4</i>	8310-01	£5.77
High Power DAC Driver <i>M.I.T. Part 4</i>	8310-02	£5.13
Electronic Pendulum	8310-03	£5.43
— NOVEMBER '83 —		
TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i>	8311-01	£5.46
Stepper Motor Manual Controller <i>M.I.T. Part 5</i>	8311-02	£5.70
Digital Gauss Meter	8311-03	£4.45
Speech Synthesiser for BBC Micro	8311-04	£3.93
Car On/Off Touch Switch	8311-05	£3.11
— DECEMBER '83 —		
4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i>	8312-01	£5.72
4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i>	8312-02	£5.29
TRS-80 Twin Cassette Interface	8312-03/09	£7.43
Touch Operated Die (Dot matrix)	8312-05/06	£4.34
Touch Operated Die (7-segment)	8312-05/07	£4.34
Continuity Tester	8312-08	£3.41
— JANUARY '84 —		
Central Heating Pump Delay	8401-01	£3.33
Biological Amplifier <i>M.I.T. Part 7</i>	8401-02	£6.27
Temp. Measure & Control for ZX Compr Analogue Thermometer Unit	8401-03	£2.35
Analogue-to-Digital Unit	8401-04	£2.56
Games Scoreboard	8401-06/07	£9.60

\*Complete set of boards. \*\*Calibrated with C1, VR1 and IC3 fitted.

*M.I.T.*—Microcomputer Interfacing Techniques, 12-Part Series.

— FEBRUARY '84 —		
Eprom Programmer/ROM Card for ZX81	**8402-01	£7.84
Oric Port Board <i>M.I.T. Part 8</i>	8402-02	£9.56
Negative Ion Generator	*8402-03	£8.95
Temp. Measure & Control for ZX Compr Relay Driver	8402-04	£3.52
— MARCH '84 —		
Latched Output Port <i>M.I.T. Part 9</i>	8403-01	£5.30
Buffered Input Port <i>M.I.T. Part 9</i>	8403-02	£4.80
VIC-20 Extension Port Con. <i>M.I.T. Part 9</i>	8403-03	£4.42
Com. 64 Extension Port Con. <i>M.I.T. Part 9</i>	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro	8403-05	£4.63
— APRIL '84 —		
Multipurpose Interface for Computers	8404-01	£5.72
Data Acquisition "Input" <i>M.I.T. Part 10</i>	8404-02	£5.20
Data Acquisition "Output" <i>M.I.T. Part 10</i>	8404-03	£5.20
Data Acquisition "PSU" <i>M.I.T. Part 10</i>	8404-04	£3.09
Timer Module	8404-05	£3.58
A.F. Sweep Generator	8404-06	£3.55
Quasi Stereo Adaptor	8404-07	£3.56
— MAY '84 —		
Simple Loop Burglar Alarm	8405-01	£3.07
Computer Controlled Buggy <i>M.I.T. Part 11</i> Interface/Motor Drive	8405-02	£5.17
Collision Sensing	8405-03	£3.20
Power Supply	8405-04	£4.93
— JUNE '84 —		
Infra-Red Alarm System	8406-01	£2.55
Spectrum Bench PSU	8406-02	£3.99
Speech Synthesiser <i>M.I.T. Part 12</i>	8406-03	£4.85
Train Wait	8406-04	£3.42
— JULY '84 —		
Ultrasonic Alarm System	8407-01	£4.72
Atom EPROM Simulator	8407-02	£3.08
Electronic Code Lock Main board	8407-03	£2.70
Keyboard	8407-04	£3.24
— AUGUST '84 —		
Microwave Alarm System	8408-01	£4.36
Temperature Interface—BBC Micro	8408-02	£2.24
— SEPTEMBER '84 —		
Op-Amp Power Supply	8409-01	£3.45
— OCTOBER '84 —		
Micro Memory Synthesiser	*8410-01	£8.20
Drill Speed Controller	8410-04	£1.60
— NOVEMBER '84 —		
BBC Audio Storage Scope Interface	8411-01	£2.90
Proximity Alarm	8411-02	£2.65
— DECEMBER '84 —		
TV Aerial Pre-Amp	*8412-01	£1.60
Digital Multimeter	*8412-02/03	£5.20
Mini Workshop Power Supply	8412-04	£2.78
— JANUARY '85 —		
Power Lighting Interface	8501-01	£8.23
Games Timer	8501-02	£1.86
Spectrum Amplifier	8501-03	£1.70
— FEBRUARY '85 —		
Solid State Reverb	8502-01	£3.68
Computerised Train Controller	8502-02	£3.38
— MARCH '85 —		
Model Railway Points Controller	8503-01	£2.78
— APRIL '85 —		
Insulation Tester	8504-02	£2.53
Fibre Alarm	8504-03	£3.89
— May '85 —		
Auto Phase	8505-01	£3.02
Amstrad CPC464 Amplifier		
Mains Unit	8505-02	£2.56
Micro Unit	8505-03	£2.71
Voltage Probe	8505-04	£2.67

# MARCO TRADING

LINEAR I.C.s	RESISTOR KITS	D CONNECTORS	DIODES	TRANSISTORS
CA3011 1.80	1/4W Pack 10 each value E12 10R-1M Total: 610 resistors <b>ONLY 4.80</b>	9 15 25 way way way	IN916 0.04 AA119 0.12	AC128 0.30 BF338 0.38
CA3012 1.75	1/4W Pack 5 each value E12 10R-1M Total: 305 resistors <b>ONLY 2.75</b>	Male Solder 75 100 1.50	IN4001 0.05 AA129 0.18	AC176 0.28 BFX26 0.28
CA3014 2.38	1/2W Pack 10 each value E12 10R-1M Total: 305 resistors <b>ONLY 5.25</b>	Angle 1.40 2.00 2.40	IN4004 0.06 AAY30 0.16	AF239 0.68 BFX84 0.24
CA3018 1.10	1/2W Pack 5 each value E12 2R2-2M2 Total: 365 resistors <b>ONLY 3.50</b>	Female Solder 1.00 1.45 1.85	IN4007 0.07 BY126 0.12	BC107 0.10 BFX85 0.26
CA3020 2.10	50V Ceramic Kit 5 ea. value 125 per Kit <b>£3.50 ea.</b>	Angle 1.50 2.00 2.40	IN4148 0.05 BY127 0.10	BC108 0.10 BFX87 0.26
CA3028A 1.30		Covers 80 80 80	IN4149 0.06 BY133 0.16	BC109 0.10 BFY50 0.21
CA3035 2.95			IN5400 0.12 BY184 0.40	A.B.C. 0.12 BFY52 0.21
CA3080E 1.80			IN5401 0.15 OA47 0.10	BC147 0.09 BFY90 0.90
CA3085 1.20			IN5402 0.15 OA90 0.08	BC182 0.09 BSX20 0.34
CA3086 0.68			IN5404 0.16 OA91 0.09	BC184 0.09 BU208 1.55
CA3090AQ 5.00			IN5406 0.18 OA95 0.18	BC184 0.09 BU407 1.65
CA3130E 1.40			IN5408 0.20 OA200 0.06	BC184L 0.09 MJ2955 0.90
CA3140E 0.60				BC212 0.09 OC45 0.58
HA1336W 3.15				BC212L 0.09 OC71 0.50
LM324N 0.55				BCY70 0.15 OC72 0.52
LM339 0.65				BD131/2 0.34 TIP31A 0.44
LM348 0.90				BD133 0.56 TIP32C 0.42
LM390 1.65				BD136 0.32 TIP33A 0.88
LM381N 1.45				BD136 0.36 TIP34A 0.72
LM382N 1.45				BF115 0.32 TIP295A 0.60
LM386 0.99				BF184 0.32 TIP3055 0.60
LM387 1.45				BF185 0.32 T1S43 0.88
LM389N 1.20				BF194 0.08 T1S88 0.40
LM3914N 2.55				BF196 0.10 2N3055 0.45
LM3915N 2.60				BF196 0.10 2SC1096 0.68
ML232B 2.10				BF197 0.10 2SC1173Y 0.82
555 0.35				BF200 0.38 2SC1306 0.92
C-mos555 0.88				BF224 0.20 2SC1307 0.40
741 0.25				BF244 0.26 2SC1307 0.76
SAS560S 1.85				BF244A 0.28 2SC2028 2.10
SAS570S 1.85				BF244B 0.26 2SC2029 0.73
SL901B 5.20				BF259 0.32 2SC2078 1.05
SL917B 6.25				BF262 0.30 2SC2166 1.20
TA7205AP 1.50				BF263 0.30 SK388 0.65
TA7222P 2.12				BF337 0.38 40673 0.80
TA1004 2.90				
TLO72 0.98				
TLO81 0.68				
TLO84 1.28				

**MARCO TRADING (DEPT EE5)**  
The Maltings  
High Street  
Wem, Shropshire SY4 5EN  
Tel: 0939 32763 Telex: 35565

ORDERING All components are brand new and to full specification. Please add 50p postage/packing (unless otherwise specified) to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges, etc, most welcome. (Do not forget to send for our 1985 catalogue - only 65p per copy. All orders despatched by return of mail. NEW RETAIL 1,000 sq ft shop now open Mon-Fri 9.00-5.00, Sat 9.00-12.00

**MARCO 85**  
Electronics Components Catalogue

Our latest 123 page catalogue over 4000 items fully illustrated. Send 65p now for your copy. FREE with orders over £5.00.

# Intruder Alarms and Accessories

**A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.**



contains:  
Control Unit  
Enclosure & mechanical fixings  
Key Switch & 2 keys  
L.E.O.s  
5" x 8" Horn Speaker  
4 high quality surface mounting Magnetic Switches

CA 1250  
HW 1250  
KS 3901  
LED 1  
HS 588  
MS 1025

**ALARM CONTROL UNIT CA 1250**  
Price £19.95+V.A.T.

The heart of any alarm system is the control unit. The CA 1250 offers every possible feature that is likely to be required when constructing a system: whether a highly sophisticated installation or simply controlling a single magnetic switch on the front door.

- \*Built-in electronic siren drives 2 loud speakers
- \*Provides exit and entrance delays together with fixed alarm time
- \*Battery back-up with recharge facility
- \*Operates with magnetic switches, pressure pads, ultrasonic or I.R. units
- \*Anti-tamper and panic facility
- \*Stabilised output voltage
- \*2 operating modes full alarm/anti tamper and panic facility
- \*Screw connections for ease of installation
- \*Separate relay contacts for external loads
- \*Test loop facility

**TIMER SWITCH & POWER SUPPLY MODULE DP 3570** Price £13.95 + V.A.T.

The DP 3570 consists of an adjustable timer switch and stabilised 12V power supply for use in a wide range of applications including security, lighting control and automatic switching.

The timer section of the module provides switching of loads up to 3A for preset times, the duration of which may be set by the user to between 10 seconds and 5 mins. The timed period may be triggered by the opening of a loop or the closing of external contacts, with the timed period commencing instantaneously or delayed to provide a form of entrance delay.

The power supply section of the module provides a 12V output of up to 250mA which is sufficient for most applications. The module operates from either 240V a.c. supply or a 12V battery for which in-line charge facilities are included. Connections to the module are by means of screw terminal connectors with no soldering needed.

For mounting the unit an attractive moulded enclosure is available.

ME 357 only £2.85 + V.A.T.

**EXTENDED SYSTEM CS 1480** Price £62.50 + V.A.T.

This system contains, in addition to the CS 1370, an ultrasonic detector type US 5063 in its enclosure, an additional horn speaker and a further 2 magnetic switches. This system represents outstanding value for money for the high level of security provided.

Order Code: CS 1480.

**HARDWARE KIT HW 1250**  
only £9.50 + V.A.T.

This attractive case is designed to house the control unit CA 1250, together with the appropriate LED indicators and key switch. Supplied with the necessary mounting pillars and punched front panel, the unit is given a professional appearance by an adhesive silk screened label. Size 200 x 180 x 70mm.

**INFRA-RED SYSTEM IR 1470** only £25.61+V.A.T.

Consisting of separate transmitter and receiver both of which are housed in attractive moulded cases, the system provides an invisible modulated beam over distances of up to 50M operating a relay when the beam is broken. Intended for use in security systems, but also ideal for photographic and measurement applications.

Size 80 x 50 x 35mm

**SELF-CONTAINED ULTRASONIC ALARM UNIT CK 5063** only £37.00 + V.A.T.

Requires no installation. Easily assembled using our professionally built and tested modules.

- \*Adjustable range up to 25ft
- \*Built-in entrance and exit delay
- \*Built-in timed alarm
- \*Key operated switch - Off, Test and Operate
- \*Provision for an extension speaker
- \*Fully self contained
- \*Uses US 5063, PSL 1865 Key Switch 3901
- \*3" Speaker 3516

Now you can assemble an really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house/flat. With a built-in LED indicator and test position the unit is easily set up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 90dbb of sound or even 110dbb with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm. Order as CK 5063.

**DIGITAL ULTRASONIC DETECTOR US 5063**  
only £13.95 + V.A.T.

- \*3 levels of discrimination against false alarms
- \*Crystal control for greater stability
- \*Adjustable range up to 25ft
- \*Built-in delays
- \*12V operation

This advanced module uses digital signal processing to provide the highest level of sensitivity whilst discriminating against potential false alarm conditions.

**ULTRASONIC MODULE ENCLOSURE**  
only £2.95 + V.A.T.

Suitable metal enclosure for housing an individual ultrasonic module type US 5063 or US 4012. Supplied with the necessary mounting pillars and screws etc. For US 5063 order SC 5063, for US 4012 order SC 4012.

**RISCOMP LIMITED**  
Dept EE29  
21 Duke Street,  
Princes Risborough,  
Bucks. HP17 0AT  
Princes Risborough (0844 4) 6326

**SIREN & POWER SUPPLY MODULE PSL 1865**  
only £9.95 + V.A.T.

A complete siren and power supply module which is capable of providing sound levels of 110dbb at 2 metres when used with a horn speaker. In addition, the unit provides a stabilised 12V output up to 100mA. A switching relay is also included so that the unit may be used in conjunction with the US 5063 to form a complete alarm.

**RISCOMP THE SECURITY SPECIALISTS!**

Add 15% VAT to all prices.  
Add 70p post and packing to all orders.  
Units on demonstration.  
Shop hours 9.00 to 5.30 p.m.  
Closed Wednesdays.  
Please allow 7 days for delivery.

Saturday 9.00 to 1.00 p.m.  
SAE with all enquiries.  
Order by telephone or post  
using your credit card.

**FULL RANGE OF ACCESSORIES STOCKED SEND SAE FOR DETAILS**

# EVERYDAY ELECTRONICS AT YOUR

## and computer PROJECTS

Reach effectively and economically to-days enthusiasts anxious to know of your through our semi-display and classified pages. Semi-display spaces may be booked at timetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word number 60p extra. All cheques, postal orders, etc., to be made payable to Everyday Electronics crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisement, should be sent to the Classified Advertisement Department, Everyday Electronics and 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone

### Receivers & Components

RESISTORS 1,000 mixed 1/8w, 1/4w, 1/2w, 2%, 5%, 10%, C. film £3.45 inc. P&P. D. J. HOOKER, Romney Marsh Electronics, Pennywood, Clark Road, Romney Marsh, Kent TN28 8PB.

FREE! PARCEL OF COMPONENTS worth £10. Send only 80p postage! D. HORSLEY, 113 Clare Road, Braintree, Essex.

VERY LARGE PACK OF MIXED COMPONENTS. Capacitors, transistors, resistors, diodes, boards, thyristors, multi-pin plugs & sockets and many more items £6.50p post & packing inclusive. G. EVANS, 7 Mendip Close, Pendine Park, Summerhill, Wrexham, Clwyd.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

### Books & Publications

OPTOELECTRONICS DATA BOOK from Texas Instruments £5.00 post free. SAE for full list of Texas and Intel data books at lowest prices. Agents for leading technical publications. Write or phone for quotation. MGBBooks, 24a Newgate, Barnard Castle, Co. Durham DL12 8NG. Tel. (0833) 31130.

### Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.

FULL SIZE TOP QUALITY Service Sheets £2.50 + L.s.a.e. CTV/Music centres £3.50 + L.s.a.e. Repair data almost any named TV/video £10.50 in circuits. L.s.a.e. brings any quite-free magazine/pricelists. TI-SEE, 76 Churches, Larkhall, Lanarkshire. Tel. 0698 883334.

### Software

#### ADVANCED COMPUTER TAPES FOR THE ZX SPECTRUM 48k

1. Dialogue tape uses a very modern artificial intelligence using specially developed codes which tie together over 2000 words.
2. Electronics design tape. Input is a basic specification in parts and output is a complete circuit diagram. Very adaptable.

Cost (inc p/p) is £10.00 each  
CWO to: N J Edwards, 68 Woodhill Rise,  
COSTESSEY, Norwich NR5 0DW

### Miscellaneous

SCHOOLS AND COLLEGES. Send now for our 1985 catalogue, top quality components at very competitive prices. Electron Electronics, 62 High Street, Croydon, Surrey.

### Miscellaneous Cont.

#### LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a Roden S-Dec.

This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experiments. Full instructions and 2 circuit diagrams with each S-Dec.

Send Cheque or P.O. to:  
Roden Products, Dep EE  
High March, Daventry,  
Northants, NN11 4DE.

**£5.25** including p & p



TO ADVERTISE  
ON THESE PAGES  
RING  
MANDI  
01-261 5846

### ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for ..... Insertions. I enclose Cheque/P.O. for £.....  
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


HEADING REQUIRED:

NAME .....

ADDRESS .....

#### EVERYDAY ELECTRONICS and COMPUTER PROJECTS

Classified Advertisement Dept, Room 2612,  
King's Reach Tower, Stamford Street, London SE1 9LS  
Telephone 01-261 5942

Rate:  
33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.


5/85


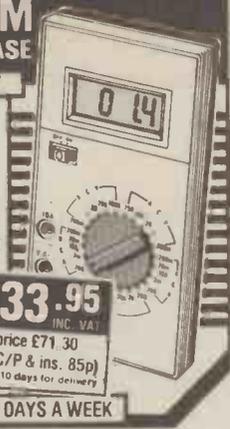
# 1/2 PRICE LCD DMM WITH CARRY CASE

EXCLUSIVE WHILE STOCKS LAST

- 3 1/2 DIGIT ■ 26 RANGE
- AUTO ZERO ■ AUTO POLARITY
- AC/DC 10 AMPS ■ TEST LEADS,
- CARRY CASE, BATTERY & INSTRUCTIONS
- 5 ranges AC/DC volts 5 ranges AC/DC current
- 6 ranges Resistance to 20 meg ohms
- Size: 161 x 87 x 25mm



**£33.95**  
INC. VAT  
List price £71.30  
(UK C/P & ins. 85p)  
Allow 10 days for delivery

## AUDIO ELECTRONICS

301 Edgware Road, London,  
W2 1BN 01-724 3564

ORDER BY POST OR PHONE OR CALL IN OPEN 6 DAYS A WEEK

# CRICKLEWOOD ELECTRONICS LTD

It's no secret!



... that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (for a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

**CRICKLEWOOD ELECTRONICS LTD.**

40 Cricklewood Broadway NW2 3ET.

01-450 0995 & 01-452 0161

ALL MAJOR CREDIT CARDS ACCEPTED  
Telex 914977 Phone or write today

EE6

\* GIVE YOUR PROJECT/PRODUCT A VERY PROFESSIONAL APPEARANCE WITH THIS VERSATILE TOUGH UNIT

## PLASTEK

HIGH QUALITY CONSOLE UNIT  
IN RIGID POLYURETHANE

UNIT EC21 **NEW**



Fully Finished in Grey/Black Spatter Textured paint, with brushed aluminium fascia—  
• Internal PCB mountings  
• Ventilation louvres  
• Cable entry plate  
• Rubber feet

**£29.90 inc. VAT**

Add P & P £1.50p

Discounts Available for Quantity/Trade Users

Complete low-cost Custom Enclosure

Moulding Service Available—Try us for a quotation

Send SAE or Telephone for Details

Send Cheque/PO to:

**B. & P. McBRIDE,**

Unit 1, The Midlands Ind. Estate,

Holt, Trowbridge, Wilts BA146RU

Telephone: (0225) 782872

\* NOT TO BE CONFUSED WITH A.B.S. or OTHER PLASTICS.

These Units are strong and finished to a very high standard.

BUY DIRECT FROM THE MANUFACTURER

## INDEX TO ADVERTISERS

AB Microsystems.....	244	ICS Intertext.....	242
AC/DC Electronics.....	295	Ideal Schools.....	295
American Inventors.....	295	London Electronics College.....	244
Armon Electronics.....	269	Magenta Electronics.....	246
Army.....	257	Maplin Electronics.....	Cover IV
Bi-Pak.....	Cover II	Marco Trading.....	293
BK Electronics.....	Cover III	M.J. Edwards.....	294
B.N.R.E.S.....	244	Pantec.....	269
B. & P. McBride.....	296	Radio Component Specialists.....	295
Bull, J.....	285	Rapid Electronics.....	245
Compytronics.....	295	Riscomp Ltd.....	293
Cricklewood Electronics.....	296	Roden Products.....	294
Electrovalue.....	290	R & TVC.....	270
Grandata Ltd.....	242	Skybridge Ltd.....	270
Greenweld.....	242	Systems Electronique.....	269
Henry's.....	296	T.K. Electronics.....	243

# WIN A FORD FIESTA XR2

Buy MOTORIST magazine and enter the 'Grand Prix' scratch game. Get your copy now! There are 100 BRITTOOL toolkits for the runners-up!

**SPECIAL FEATURES INCLUDE**

- \* **PORSCHE**—the team to beat
- \* **AUTO-SCHOOL No. 3**—the ignition system
- \* **STOP THE RUST PLUS ...**
- \* **ROAD & TRUCK TESTING THE GT's**

ASTRA versus GOLF versus COROLLA

# MOTORIST

Britain's No. 1 Practical Motoring Magazine

**May issue OUT NOW**





From a gentle purr to a mighty roar, the tightly controlled power of the beast is yours to command!

# All new in the 1985 Catalogue



## PROFESSIONAL QUALITY HIGH POWER LOUDSPEAKERS

A new range of superb quality loudspeakers.

- ★ Virtually indestructible high temperature voice-coil reinforced with glass-fibre
- ★ 100% heat overload tolerance
- ★ Advanced technology magnet system
- ★ Rigid cast alloy chassis
- ★ Linen or Plastiflex elastomer surrounds
- ★ 5-year guarantee (in addition to statutory rights)



Available in 5, 8, 10, 12, 15 and 18 inch models with 8Ω and some 16Ω impedances and with input powers ranging from 50W to 300W e.g.

- 5in. 50W 95dB 8Ω: XG39N / 16Ω: XG40T £17.95§
- 8in. 100W 98dB 8Ω: XG43W £29.95§
- 10in. 100W 100dB 8Ω: XG46A £29.95§
- 12in. 100W 101dB 8Ω: XG49D £29.95§
- 12in. Twin Cone 100W 100dB 8Ω: XG50E / 16Ω: XG51F £31.95§

Note - the output power doubles for each 3dB increase (ref 1W @ 1m).

## PRECISION GOLD MULTIMETERS



A new range of very high quality multimeters offering truly amazing quality at the price.

- Pocket Multimeter, 16 ranges, 2000Ω/V DC/AC £6.95§ (YJ06G)
- M-102BZ with Continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95§ (YJ07H)
- M-2020S with Transistor, Diode & LED tester and 10A DC range, 27 ranges, 20,000Ω/V DC £19.95§ (YJ08J)
- M-5050E Electronic Multimeter with very high impedance, FET input, 53 ranges including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95§ (YJ09K)
- M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated PCB for long-term reliability and consistent high accuracy (0.25% + 1 digit DCV) £42.50§ (YJ10L)

N.B. All our prices include VAT and Carriage. A 50p handling charge must be added if your total order is less than £5 on mail order (except catalogue).

### MAPLIN ELECTRONIC SUPPLIES LTD.

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 552911 SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
  - LONDON 159-161 King Street, Hammersmith, W6. Tel: 01-748 0926.
  - MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
  - SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 25831.
  - SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Tel: 0702-554000
- Shops closed all day Monday.

Our huge range of top quality electronic components at very competitive prices are all detailed in our catalogue, and with well over 600 new lines in our 1985 edition and many design improvements, it's well worth getting a copy. Here are just a few examples from the catalogue. (The items below are NOT kits).

- ★ Most phono and jack plugs now with integral strain relief sleeve - gold-plated types also available from 14p (gold from 70p)
- ★ Stereo Disco Mixer with cross-fade, talk-over, cue monitoring, aux input, slide controls. Only £58.95 (AF99H)



- ★ 10-Channel Stereo Graphic Equalisers - 3 models - basic; with peak level meter; and with spectrum analyser - from £77.95



- ★ Digital Delay Line permits Slap-back, Doubling, Flanging, Chorus and Echo. 11 controls. Only £195.00 (AF98G)
- ★ Video Enhancer improves picture quality when recording from one VTR to another, and with TV's with monitor input. Only 28.95 (XG59P)
- ★ Detailed descriptions of the exciting new 74HC range of IC's which combine the advantages of CMOS and TTL. From 46p
- ★ Keyboards: sloping keys, two-tone grey, mounted in steel frame, very smart cases (extra) available. 61 keys, only £33.95 (YJ12N) 79 keys, only £37.95 (YJ13P)
- ★ 1% Resistors now 50ppm/°C, 0.4W, only 2p each!
- ★ Auto transformers 120/240V 50VA, £10.75§ (YJ56L). 100VA £14.95§ (YJ57M). 150VA £16.95§ (YJ58N). 250VA £21.95§ (YJ59P).
- ★ Digital Clinical Thermometer. Only £13.95 (FK51F)



Check our 1985 Catalogue for all our other fascinating new lines.



☎ Phone before 2pm for same day despatch.

## 1985 CATALOGUE

Pick up a copy now at any branch of W.H. Smith or in one of our shops. The price is still just £1.35, or £1.75 by post from our Rayleigh address (quote CA02C).

Post this coupon now for your copy of the 1985 catalogue. Price £1.35 + 40p post and packing. If you live outside the U.K. send £2.40 or 11 International Reply Coupons. I enclose £1.75.

Name .....

Address .....

.....  
 .....

EE/5/85

§ Indicates that a lower price is available in our shops.

All offers subject to availability.

Prices firm until May 11th 1985.