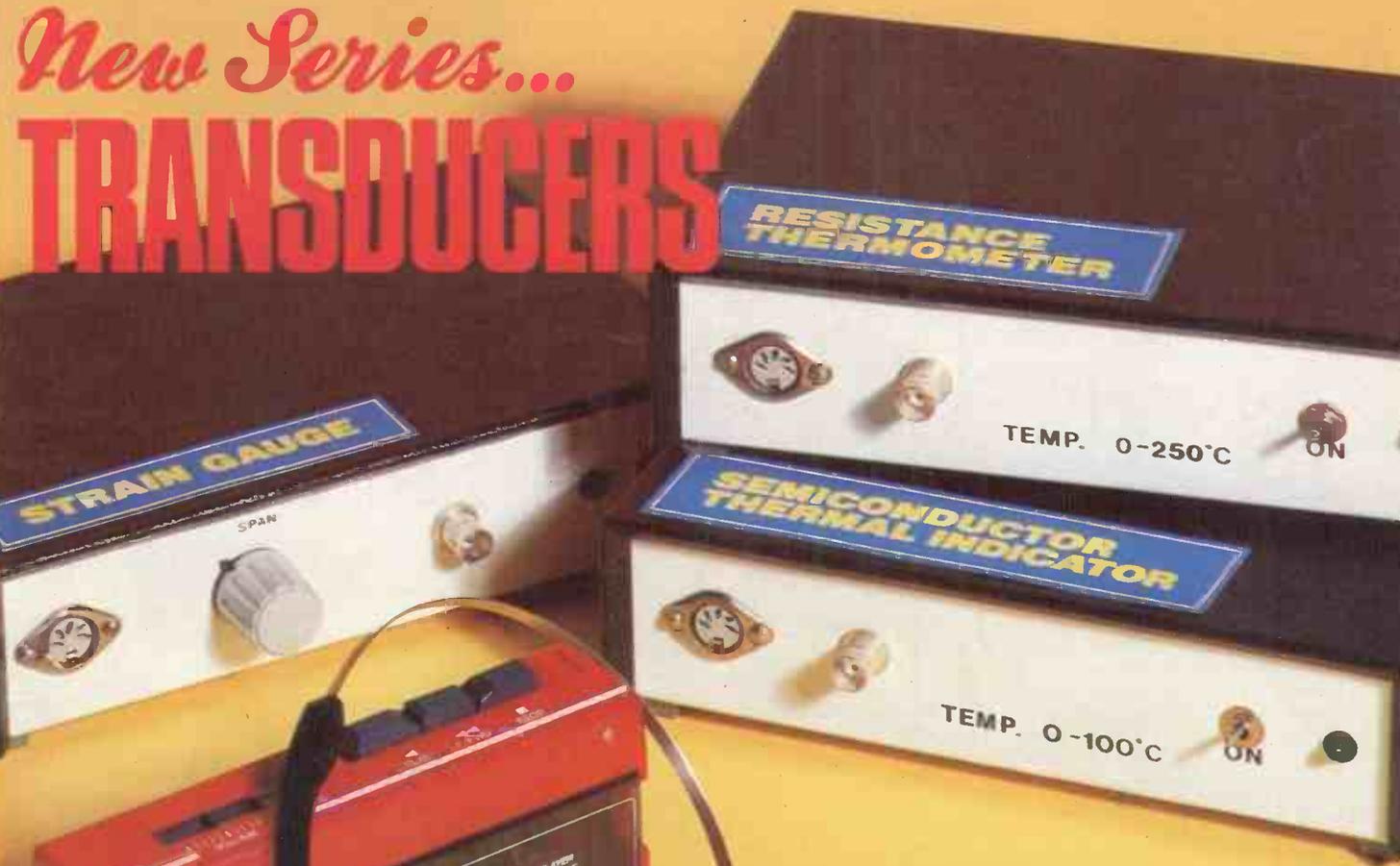


EVERYDAY ELECTRONICS and computer PROJECTS

SEPTEMBER 1985

£1.00

New Series... TRANSDUCERS



PERSONAL STEREO P.S.U

FRIDGE ALARM

ON SPEC - FUNTRONICS - ACTUALLY DOING IT - DOWN TO EARTH

Australia \$1.75 New Zealand \$1.95 Malaysia \$4.95

10548
AVE

SAVE EVEN MORE!

THE EVERYDAY ELECTRONICS FILM SERVICE

So many satisfied customers have been delighted with this award-winning film service that the economies made are now being passed on to you in the form of substantial price reductions. You can now save up to 75p on last year's prices. For 36 successful Superprints you pay only £2.95 inc. VAT. Compare this with last year's £3.70 and with the prices in the shops. Postage and packing is 30p extra as before. Here is the new price range – and remember, Superprints give you 30 per cent more picture area than standard prints at no extra charge.

No. of Superprints	Price (inc. VAT)	
12-15	£1.65	} PLUS P/P 30p extra
24	£2.20	
36	£2.95	

RELIABILITY AND QUALITY

All our colour prints are made on Kodak Luxury Lustre paper. Prints have square corners and are borderless to give you maximum picture area. All prints are checked at every processing stage for accurate colour reproduction in a laboratory which is the winner of five recent successive Kodak Gold Awards for Quality. No other processing laboratory has been able to match this record. After allowing for postal and peak-period delays, you should normally expect your prints after seven to ten days.

ALL YOU HAVE TO DO

Send any make of colour print film together with your cheque or postal order inside the Freepost envelope enclosed with this issue. Or fill in the coupon below and send together with your film and remittance in a strong envelope to: Everyday Electronics Film Service, FREEPOST, Watford WD1 8FP. Half-frame films are welcome, and these are charged at double the full-frame price.

PERSONALISED SERVICE

Readers know we care for their prints. If you have any queries, contact our service's ten-line switchboard: (01) 953 9911.



Approx. sizes of Superprints:
6" x 4" (35mm) 5¼" x 4" (110,
Disc and 135 Half Frame) 4" x 4" (126).



SPECIAL FILM OFFER

Films from the high-resolution emulsion 'ColorFast' range are available to all readers at highly competitive prices. And when you order three, you get another FREE.

110/24, 126/24, 135/24 £1.40 each OR 4 for price of 3—£4.20. Konica disc £1.60 OR 4 for price of 3—£4.80. 135/36 £1.80 OR 4 for price of 3—£5.40.

SPECIAL ALBUM OFFER

An attractive flip-type album, padded in black with gold embossing and holding 100 Supersize prints (in the shops £5.75) is offered to readers for only £3.99 inc. p&p.

All prices are correct at the time of going to press and are for UK readers only.

USE THIS LABEL IF YOU HAVE NO ENVELOPE, OR PASS TO A FRIEND.

To: Everyday Electronics Film Service, FREEPOST, Watford WD1 8FP.

From: Everyday Electronics Film Service,
FREEPOST, Watford WD1 8FP.

Name _____

Address _____

*Print my enclosed film

*Rush me _____ of 110/24, _____ of 126/24,
_____ of 135/24, _____ of 135/36, _____ of Disc/15 film _____

*Rush me _____ album(s)

for which I enclose cheque/PO payable to Everyday Electronics Film Service. £ _____

EES

Post Code _____



UNLESS YOU MAKE PRIOR ARRANGEMENTS WITH US we will only accept your film on the strict understanding that our liability in the case of loss or damage will not exceed the replacement cost of the unexposed film and the processing charges paid. NO CREDITS GIVEN FOR FAILURE PRINTS. This offer is limited to the U.K. Choice of materials at our discretion. The Everyday Electronics Film Service is operated in association with MFS Photographic Ltd., registered England 1835748. Registered Office: Stirling Way, Borehamwood, Herts. WD6 2AZ. Offer expires 31/3/86.

EVERYDAY ELECTRONICS and computer PROJECTS

VOL 14 N°9 SEPTEMBER '85

ISSN 0262-3617

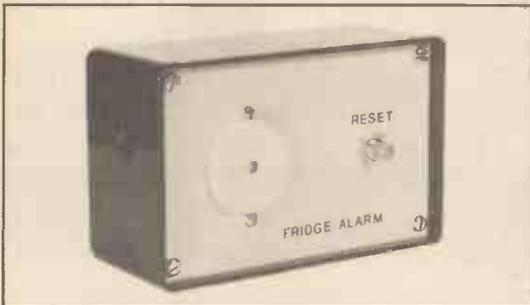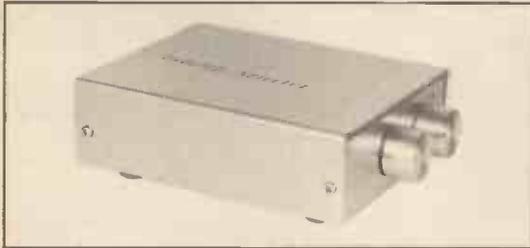PROJECTS... THEORY... NEWS...
COMMENT... POPULAR FEATURES...



TEACH IN '86

Don't miss the start of this important new series—See Pages 489 & 506

© IPC Magazines Limited 1985. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

PROJECTS

- UV EXPOSURE UNIT** by C. J. Bowes 472
Making light work of p.c.b.s
- VOLTAGE REGULATOR** 480
Keeping taps on your supply—Building Blocks project
- FRIDGE ALARM** by R. A. Penfold 482
Safe-guard the contents of the fridge
- PERSONAL STEREO PSU** by T. R. de Vaux Balbirnie 490
Save your batteries when using the "personal" in the home
- RESISTANCE THERMOMETER** 500
Simple measuring project using a platinum sensor—0–250°C
- SEMICONDUCTOR TEMPERATURE SENSOR** 502
Covers a range of 0 to 100°C
- CARAVAN ALARM** by T. R. de Vaux Balbirnie 504
Security system for caravanners
- RIAA PREAMPLIFIER INPUT SELECTOR** by R. A. Penfold 510
Improve the performance of your audio system with this stereo preamplifier

SERIES

- ELECTRONIC BUILDING BLOCKS** by Richard Barron 478
Part Two: A new look at electronic design—Voltage references
- FUNTRONICS** by Thakery 492
A light-hearted approach to electronics with quizzes
- TRANSDUCERS** by Mike Feather 499
Part One: Two projects for measuring temperature
- ACTUALLY DOING IT** by Robert Penfold 507
Component identification
- DOWN TO EARTH** by George Hylton 508
Neon lamps

FEATURES

- EDITORIAL** 471
- SHOPTALK** by Richard Barron 477
Product news and component buying
- CONSUMER ELECTRONICS SHOW CHICAGO** 486
by Rik Hooper
Latest trends in home entertainment
- ON SPEC** by Mike Tooley BA 494
Our regular Spectrum page: A digital-to-analogue converter
- EVERYDAY NEWS** 496
What's happening in the world of electronics
- FOR YOUR ENTERTAINMENT** by Barry Fox 498
No Call for DIY; Nightmare
- MAN BEHIND THE SYMBOL** by Morgan Bradshaw 514
Symbols, and the men they are named after, explained
- COUNTER INTELLIGENCE** by Paul Young 515
- NEW PRODUCTS** 516
Facts and photos of instruments, equipment and tools
- PRINTED CIRCUIT BOARD SERVICE** 517

Our October 1985 issue will be published on Friday, September 20.
See page 489 for details.

SUMMER SALE!!

All those people on the beach making Sandcastles – STOP – 'cos here are some really nice bargains. We're clearing stocks of last years offers at unbeatable prices . . . PLUS – all packs reduced . . . PLUS – a preview of new packs that will be featured later in the year!! All offers must end 31st August, so hurry hurry hurry!!! Minimum order value at these special sale prices is £10. Detail of all items can be found in earlier ads or send SAE for list.

PACKS

K524 Opto Pack **£3.95 £2.95**
 K525 Preser Pack **£6.75 £3.95**
 K528 Electrolytic Pack **£3.95 £3.20**
 K531 Precision resistors **£3.00 £2.50**
 K532 Relays **£6.00 £3.00**
 K517 Transistors **£2.75 £1.95**
 K523 Resistors **£2.50 £2.00**
 K520 Switches **£2.00 £1.70**
 K522 Copper clad board **£1.00 £0.70**
 K530 Polyester **£3.95 £2.95**
 K518 Disc Ceramics **£1.00 £0.70**
 K503 Wirewound Resistors **£2.00 £1.50**
 K505 Pots **£1.70 £1.40**
 W4700 Push button banks **£2.95 £2.00**
 K526 Heatsinks **£5.50 £4.00**
 K527 Hardware **£4.00 £3.00**

OTHER GOODS

"Crackshot" Joystick (Atari) **£8.50 £4.50**
 BBC Joystick **£9.50 £5.50**
 Analogue joystick **£9.85 £5.35**
 "The Sensible 64" book **£5.95 £2.00**
 Bimbox 6006 **£2.95 £2.00**
 LP11 compartment tray **£2.95 £2.00**
 Storage Bins **£3.95 £2.95**
 Ferric Chloride **£1.30 £0.99**
 SK1 Antex Kit **£11.38 £7.50**
 Veroboxes, two tone grey:
 825-21028 **£3.38 £2.50**
 825-21029 **£3.81 £2.95**
 825-21030 **£4.28 £3.30**
 825-21031 **£5.72 £4.50**
 Power/VU meter **£1.00 £0.60**
 4.8V PCB Ni-Cad **£0.99 £0.70**
 Single core Fibre. Optic 20m coil **£6.30 £3.50**
 Twin core Fibre Optic 20m coil **£11.00 £6.00**

NI-CAD CHARGER PANEL

177x114mm PCB with one massive Varta Deac 57x50mm Ø rated 7.2v 1000mAh and another smaller Deac 32x35mm Ø rated 3.6v 600mA. The price of these Ni-cad stacks new is over £20. Also on the panel is a mains input charger transformer with two separate secondaries wired via bridge rectifiers, smoothing capacitors and a relay to the output tags. The panel weighs 1kgm. All this for just **£6.00**.

1985 CATALOGUE

More components than ever before! With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just **£1.00!!**

"SENSING & CONTROL PROJECTS FOR THE BBC MICRO"

Have you ever wondered what all those plugs and sockets on the back of the BBC micro are for? This book assumes no previous electric knowledge and no soldering is required, but guides the reader (pupil or teacher) from basic connexions of the user sockets, to quite complex projects. The author, an experienced teacher in this field, has provided lots of practical experiments, with ideas on how to follow up the basic principles. A complete kit of parts for all the experiments is also available. Book, 245x185mm 120pp. Kit **£29.95**

Our shop has enormous stock of components and is open 9-5.30 Mon-Sat. Come and see us!!

GREENWELD

All prices include VAT; just add 60p P&P.
 Min Access order £10. Sale goods £10 min. CWO value.
 Official orders from schools etc. welcome – min invoice charge £10.



PANELS

Z914 1W mono amp panel **£1.50 £1.00**
 Z915 1W stereo amp panel **£3.50 £2.00**
 Z916 AM tuner panel **£1.50 £1.00**
 Z908 2xTDA1004 panel **£3.00 £1.50**
 Z912 IF Panel **£2.50 £1.50**
 Z910 RF/IF radio panel **£2.50 £1.50**
 "Simon" panel untested **£1.50**
 Z925 2 relays + triac **£1.90 £1.20**
 Z926 relay + triac + SCR **£1.85 £1.15**
 Z927 2x6V reeds **£0.60 £0.40**
 Z922 Panel with 36p3w switch **£9.50 £4.50**

NEW PACKS

K534 SLEEVE PACK – wide selections of types and sizes – PVC, rubber, silicone, heatshrink, etc. in boxes from 1mm to 18mm, lengths 9mm to 100mm. Approx. 100 **£1.00**
 K536 74 SERIES PACK – 'on board' chips for you to desolder – containing many LS and other types. Good mix. 40 **£1.85** 100 **£4.00**

K537 I.C. PACK – a mix of linear and logic chips, form 6 to 40 pin. All are new and marked, but some may not be full spec. 100 **£6.75** 250 **£14.00** *1000 **£45.00**
 *mostly in tubes

K538 DIODE PACK – untested small signal diodes like 1N4148 etc. at a price never before seen!! 1000 **£2.50** 10,000 **£20.00**

K539 LED PACK – not only round but many shaped leds in this pack in red, yellow, green, orange and clear. Fantastic mix. 100 **£5.95** 250 **£13.50**

K540 RESISTOR PACK – mostly 1/8, 1/4 and 1/2w, also some 1 & 2w in carbon, film, oxide etc. All have full length leads. Tolerances from 5 to 20%. Excellent range of values 500 **£2.50** 2500 **£11.00**

K535 SPRING PACK – approx 100 assorted compression, extension and torsion springs up to 22mm dia and 30mm long **£1.70**



MOTORIZED GEARBOX

The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx 50rpm. Data is supplied with the unit showing various options on driving the motors. Two new types of wheels can be supplied (the aluminium discs and smaller plastic wheels are now sold out). Type A has 7 spokes with a round black tyre and is 100mm dia. Type B is a solid heavy duty wheel 107mm dia with a flat rigid tyre 17mm wide.

PRICES: Gearbox with data sheets: **£5.95**
 Wheel type A: **£0.70 ea**
 Wheel type B: **£0.90 ea**

AUDIO MODULES AT THE LOWEST PRICES

Now Distributed by Riscomp

POWER AMPLIFIERS

AL 1030 (AL30) - Low cost general purpose 10W/8ohm module, supply voltage range 18-30V.



£3.30 + V.A.T.

AL 1540 - At 15W/8ohm medium power module incorporating over-load protection. Operating voltage range 20-40V.



£3.65 + V.A.T.

AL 2550 (AL60) - Compact 25W/8ohm module for domestic applications with a distortion figure of .06%, operating voltage range 28-50V.



£4.25 + V.A.T.

AL 5070 (AL120) - Top class 50W/8ohm module with self-contained heat sink and built-in protection circuitry, produces really 1st class sound with a distortion level at an incredible .02%.



£10.50 + V.A.T.

AL 12580 (AL250) - A rugged top of the range module providing output powers of up to 125W into 4ohms which employs 4 heavy duty output transistors to ensure a stable and reliable performance. Currently used in disco units, public address systems, juke boxes and even domestic Hi-Fi.



£14.70 + V.A.T.

PRE-AMPLIFIERS & MIXERS

PA 207 - A quality stereo pre-amplifier and tone control unit suitable for driving any of the above amplifiers. Operates from a supply rail of 40-70V.



£13.95 + V.A.T.

MM 100 - 3 input mixer featuring individual level controls, master volume, treble & base controls, with inputs for microphone, magnetic pick-up and tape or second pick-up (selectable). Operates from 45-70V.



£10.95 + V.A.T.

MM 100G - As MM 100 except inputs are for 2 guitar + microphone. **£10.95 + V.A.T.**

POWER SUPPLY

SPM90/45/55/65 - A stabiliser module available in 3 voltages, 45-55 & 65V providing a stabilised output of up to 2A and providing a superior performance especially with the higher power audio modules. (Requires an appropriate transformer + reservoir capacitor).



£5.75 + V.A.T.

★ All modules supplied with a comprehensive Data Sheet. ★

Order by post, order by phone Add 15% V.A.T. to all prices U.K. orders add 70p post and packing Export orders – post & packing at cost Please allow 7 days for delivery

RISCOMP LIMITED

Dept EE32,
 51 Poppy Road,
 Princes Risborough,
 Bucks, HP17 9DB,
 Princes Risborough
 (084 44) 6326

FREE CAREER BOOKLET

Train for success, for a better job, better pay!

Enjoy all the advantages of an ICS Diploma Course, training you ready for a new, higher paid, more exciting career.

Learn in your own home, in your own time, at your own pace, through ICS home study, used by over 8 million already!

Look at the wide range of opportunities awaiting you. Whatever your interest or skill, there's an ICS Diploma Course there for you to use.

Send for your FREE CAREER BOOKLET today – at no cost or obligation at all.

GCE		Choose from over 40 'O' and 'A' level subjects.	<input type="checkbox"/>
COMPUTER PROGRAMMING	<input type="checkbox"/>	CAR MECHANICS	<input type="checkbox"/>
BOOK-KEEPING & ACCOUNTANCY	<input type="checkbox"/>	INTERIOR DESIGN	<input type="checkbox"/>
POLICE ENTRANCE	<input type="checkbox"/>	HOTEL MANAGEMENT	<input type="checkbox"/>
ELECTRONICS	<input type="checkbox"/>	COMMERCIAL ART	<input type="checkbox"/>

Please send FREE DETAILS for the courses ticked above.

Name

Address

P. Code

ICS

Dept. ECS95, 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568/9 or 041-221 2926 (all hours)

The Rapid Electronics

MAIL ORDERS:
Unit 3, Hill Farm Industrial Estate,
Boxted, Colchester, Essex CO4 5RD.
Tel. Orders: Colchester (0206) 36412.
Telex: 987756.



**ACCESS AND
BARCLAYCARD
WELCOMED**

MIN. D CONNECTORS

Plugs solder lugs	55p	66p	90p	170p
Right angle	80p	135p	200p	350p
Sockets solder lugs	80p	100p	135p	200p
Right angle	120p	180p	290p	420p
Covers	100p	90p	100p	110p



SOLDERING IRONS

Antex CS 17W Soldering iron	43P
2.3 and 4.7mm bits to suit	85
Antex XS 25W soldering iron	43P
3.3 and 4.7mm bits to suit	85
Solder pump desoldering tool	48P
Spair nozzle for above	70P
10 metres 22 swg solder	100P
0.5kg 22 swg solder	750P

CONNECTORS

DIN Plug Skt Jack Plug Skt	
2 pin 9p 9p 2.5mm 10p 10p	
3 pin 12p 10p 3.5mm 10p 10p	
5 pin 13p 11p Standard 15p 20p	
Phono 10p 12p Stereo 24p 25p	
1mm 12p 13p 4mm 18p 17p	
UHF (CB) Connectors:	
PL259 Plug 40p, Rectifier 14p.	
SO239 Radio chassis skt 30p	
SO239S radio chassis skt 40p.	
IEC 3 pin 250V/6A.	
Plug chassis mounting	38p
Socket free hanging	60p
Socket with 2m lead	120p

VERO

Verobloc	395
Verobloc Size 0.1 in matrix	
2.5 x 1	26
2.5 x 3.75	125
3.75 x 5	90
7.5 x 17	455
V5 board	190
Veropins per 100:	
Single sided	55
Double sided	65
Spot face cutter	185
Pin insertion tool	160
Wiring pen	375
Spare spool 75p	6

MICRO

27128-250	650
6116P3	310
6264P15	850
4164-15	300
41256-15	2850
Z80A CPU 290	6850
Z80A CPU 320	6850
Z80A CTC 320	6875
Z80A 510	6880
Z80A DMA 880	6502

REGULATORS

78L05	30	79L05	45
78L12	30	79L12	45
78L15	30	79L15	45
7805	40	7905	45
7812	40	7912	45
7815	45	7915	45
LM317K	270	LM723	40
LM317T	90	78H05	550
LM723	420		

CABLES

20 metre pack single core connecting cable ten different colours	75p
Speaker cable	10p/m
Standard screened	16p/m
Twin screened	24p/m
2.5A 3 core mains	23p/m
10 way rainbow ribbon	26p/ft
20 way rainbow ribbon	47p/ft
10 way grey ribbon	14p/ft
20 way grey ribbon	28p/ft

HARDWARE

PP3 battery clips	6
Red or black crocodile clips	6
Black pointer control knob	15
Pr Ultrasonic transducers	350
P6V Electronic buzzer	65
P12V Electronic buzzer	75
PB270 Piezo transducer	75
P64mm 64 ohm speaker	70
P64mm 8 ohm speaker	70
20mm panel fuseholder	35
Red or black probe clip	25
4mm terminal	33
12 way 'chocolate' block	21
ultra-min. 6 or 12v rel. SPDT	130
ditto, but DPDT	195

CAPACITORS

Polyester, radial leads, 250V, C280	
type: 0.01, 0.015, 0.022, 0.033	
0.047, 0.068, 0.1, 0.15, 0.22	
0.33, 0.47, 0.68, 1.0, 1.5, 2.2	
3.3, 4.7, 6.8, 10, 15, 20, 30, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 6800, 10000, 15000, 22000, 33000, 47000, 68000, 100000, 150000, 220000, 330000, 470000, 680000, 1000000, 1500000, 2200000, 3300000, 4700000, 6800000, 10000000, 15000000, 22000000, 33000000, 47000000, 68000000, 100000000, 150000000, 220000000, 330000000, 470000000, 680000000, 1000000000, 1500000000, 2200000000, 3300000000, 4700000000, 6800000000, 10000000000, 15000000000, 22000000000, 33000000000, 47000000000, 68000000000, 100000000000, 150000000000, 220000000000, 330000000000, 470000000000, 680000000000, 1000000000000, 1500000000000, 2200000000000, 3300000000000, 4700000000000, 6800000000000, 10000000000000, 15000000000000, 22000000000000, 33000000000000, 47000000000000, 68000000000000, 100000000000000, 150000000000000, 220000000000000, 330000000000000, 470000000000000, 680000000000000, 1000000000000000, 1500000000000000, 2200000000000000, 3300000000000000, 4700000000000000, 6800000000000000, 10000000000000000, 15000000000000000, 22000000000000000, 33000000000000000, 47000000000000000, 68000000000000000, 100000000000000000, 150000000000000000, 220000000000000000, 330000000000000000, 470000000000000000, 680000000000000000, 1000000000000000000, 1500000000000000000, 2200000000000000000, 3300000000000000000, 4700000000000000000, 6800000000000000000, 10000000000000000000, 15000000000000000000, 22000000000000000000, 33000000000000000000, 47000000000000000000, 68000000000000000000, 100000000000000000000, 150000000000000000000, 220000000000000000000, 330000000000000000000, 470000000000000000000, 680000000000000000000, 1000000000000000000000, 1500000000000000000000, 2200000000000000000000, 3300000000000000000000, 4700000000000000000000, 6800000000000000000000, 10000000000000000000000, 15000000000000000000000, 22000000000000000000000, 33000000000000000000000, 47000000000000000000000, 68000000000000000000000, 100000000000000000000000, 150000000000000000000000, 220000000000000000000000, 330000000000000000000000, 470000000000000000000000, 680000000000000000000000, 1000000000000000000000000, 1500000000000000000000000, 2200000000000000000000000, 3300000000000000000000000, 4700000000000000000000000, 6800000000000000000000000, 10000000000000000000000000, 15000000000000000000000000, 22000000000000000000000000, 33000000000000000000000000, 47000000000000000000000000, 68000000000000000000000000, 100000000000000000000000000, 150000000000000000000000000, 220000000000000000000000000, 330000000000000000000000000, 470000000000000000000000000, 680000000000000000000000000, 1000000000000000000000000000, 1500000000000000000000000000, 2200000000000000000000000000, 3300000000000000000000000000, 4700000000000000000000000000, 6800000000000000000000000000, 10000000000000000000000000000, 15000000000000000000000000000, 22000000000000000000000000000, 33000000000000000000000000000, 47000000000000000000000000000, 68000000000000000000000000000, 100000000000000000000000000000, 150000000000000000000000000000, 220000000000000000000000000000, 330000000000000000000000000000, 470000000000000000000000000000, 680000000000000000000000000000, 1000000000000000000000000000000, 1500000000000000000000000000000, 2200000000000000000000000000000, 3300000000000000000000000000000, 4700000000000000000000000000000, 6800000000000000000000000000000, 10000000000000000000000000000000, 15000000000000000000000000000000, 22000000000000000000000000000000, 33000000000000000000000000000000, 47000000000000000000000000000000, 68000000000000000000000000000000, 100000000000000000000000000000000, 150000000000000000000000000000000, 220000000000000000000000000000000, 330000000000000000000000000000000, 470000000000000000000000000000000, 680000000000000000000000000000000, 1000000000000000000000000000000000, 1500000000000000000000000000000000, 2200000000000000000000000000000000, 3300000000000000000000000000000000, 4700000000000000000000000000000000, 6800000000000000000000000000000000, 10000000000000000000000000000000000, 15000000000000000000000000000000000, 22000000000000000000000000000000000, 33000000000000000000000000000000000, 47000000000000000000000000000000000, 68000000000000000000000000000000000, 100000000000000000000000000000000000, 150000000000000000000000000000000000, 220000000000000000000000000000000000, 330000000000000000000000000000000000, 470000000000000000000000000000000000, 680000000000000000000000000000000000, 1000000000000000000000000000000000000, 1500000000000000000000000000000000000, 2200000000000000000000000000000000000, 3300000000000000000000000000000000000, 4700000000000000000000000000000000000, 6800000000000000000000000000000000000, 10000000000000000000000000000000000000, 15000000000000000000000000000000000000, 22000000000000000000000000000000000000, 33000000000000000000000000000000000000, 47000000000000000000000000000000000000, 68000000000000000000000000000000000000, 100000000000000000000000000000000000000, 150000000000000000000000000000000000000, 220000000000000000000000000000000000000, 330000000000000000000000000000000000000, 470000000000000000000000000000000000000, 680000000000000000000000000000000000000, 1000000000000000000000000000000000000000, 1500000000000000000000000000000000000000, 2200000000000000000000000000000000000000, 3300000000000000000000000000000000000000, 4700000000000000000000000000000000000000, 6800000000000000000000000000000000000000, 100, 15000000000000000000000000000000000000000, 22000000000000000000000000000000000000000, 33000000000000000000000000000000000000000, 47000000000000000000000000000000000000000, 68000000000000000000000000000000000000000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47000, 68000, 1000, 1500, 2200, 3300, 4700, 6800, 100, 15000, 22000, 33000, 47	

OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof. **Supplied ready built and tested.**

OMP 100 MkII Amp. Module. 110w R.M.S. 4ohms 1/P Sens. 500mV - 10K. Size: 360 x 115 x 72mm. Price: £32.99 + £2.50 P&P.
 OMP/MF100 Mos-Fet. Very high spec 110w R.M.S. both 4 & 8ohms. 1/P Sens. 500mV - 10K. Size: 300 x 123 x 60mm. Price: £39.99 + £2.50 P&P.
 OMP/MF200 Mos-Fet. Very high spec 200w R.M.S. 4ohms 1/P Sens. 500mV - 10K. Size: 300 x 150 x 100mm. Price: £62.99 + £3.50 P&P.
 OMP/MF300 Mos-Fet. Very high spec 300w R.M.S. 4ohms 1/P Sens. 500mV - 10K. Size: 330 x 147 x 102mm. Price: £79.99 + £4.50 P&P.
 Vu Meter. 11 LED's. Plastic Case. Size: 84 x 27 x 45mm. Price: £8.50 + 50p P&P.

Full specifications available on request.

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order — Standard or P.A.

19" STEREO RACK AMPS

Professional 19" cased Mos-Fet stereo amps with twin Vu meters, twin toroidal power supplies, XLR connections MF600 Fan cooled. Three models (Ratings R.M.S. into 4ohms).
 MF200 (100 + 100W) £169.00
 MF400 (200 + 200W) £228.85
 MF600 (300 + 300W) £274.85

Securicor Delivery £10.00

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following:—
 3 Turntables (Mag). 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot. L & R Master Output controls. Output 775mV. Size 360 x 280 x 90mm.
 Price £134.99 — £3.00 P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres 57 x 46 x 14mm (9 volt). Price: £8.62 x 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.

3 watt FM Transmitter

POSTAL CHARGES PER ORDER £1.00 minimum.

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Sales Counter. ★

B. K. ELECTRONICS

LARGE (28p) S.A.E. FOR CURRENT LIST

PIEZO ELECTRIC TWEETERS — MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (each if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 40p P&P.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P.

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P

LOUDSPEAKERS

Cabinet fixing in stock. S.A.E. for details.

Loudspeakers 5" to 18". Up to 300W R.M.S. S.A.E. for full lists. McKenzie speakers at advantageous prices. All speakers listed 8 ohm imp.

POWER RANGE

8" 50 WATT R.M.S. Hi-Fi/Disco. 20 oz magnet 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq 40Hz. Freq. Resp. to 6KHz Sens. 92dB. PRICE £10.99 Available with black grille. £11.99 P&P £1.50 ea.

12" 100 WATT R.M.S. Hi-Fi/Disco. 50 oz magnet 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq.

25Hz Freq. Resp to 4KHz Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.

15" 100 WATT R.M.S. Hi-Fi/Disco. 50 oz magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 20Hz. Freq. Resp. to 2.5KHz. Sens. 97dB. PRICE £37.49 + £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone). 5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc. 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 + £1.00 P&P ea.

6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc. 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.

8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc. 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 + £1.50 P&P ea.

McKENZIE 12" 85 WATT R.M.S. C1285GP Lead guitar/keyboards/Disco. 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £24.99 + £3.00 P&P ea.

12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone. Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £24.99 + £3.00 P&P ea.

15" 150 WATT R.M.S. C15 Bass Guitar/Disco. 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £49.99 + £4.00 P&P ea.

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR. TEL 0702-527572



You can depend on

ELECTROVALUE

to supply the fine range of test & measurement gear by

thandar

Made in U.K.

- counters
- multimeters
- scopes
- signal generators etc.

FREE 44 PAGE PRICED AND ILLUSTRATED CATALOGUE ON REQUEST

● Over 6000 items stocked

ELECTROVALUE LTD 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB Phone Egham (0784) 33603. Telex 264475
 North Branch, 680 Burnage Lane, Manchester M19 1NA
 Telephone 061 432 4945
 Please mention this publication when replying

BRITAINS FOREMOST QUALITY COMPONENT SUPPLIERS

EVERYDAY ELECTRONICS KITS

GRAPHIC EQUALISER	JUNE 1985	£22.50
HIGH IMPEDANCE MULTIMETER	JUNE 1985	£26.35 — Case not included
ACROSS THE RIVER	JUNE 1985	£13.45
CARAVAN P.S.U.	JUNE 1985	£ 9.95 — 1/P&O/P Connectors not incl.
ELECTRONIC DOORBELL	JUNE 1985	£ 6.25
CONTINUITY TESTER	JULY 1985	£ 8.35
TRAIN SIGNAL CONTROLLER	JULY 1985	£10.45
EMERGENCY LIGHT FLASHER	JULY 1985	£ 6.50 — Tripod and bulbs not included

THIS MONTH'S PROJECTS — TELEPHONE OR S.A.E. FOR PRICES

All kits are complete (less batteries) unless otherwise specified including components, hardware, P.C.B. (or stripboard) case etc. Components are new and of good quality.
 Add 50p postage per order. Article reprint 60p. Cheque or Postal Order to:

C.P.L. ELECTRONICS

8 Southdean Close, Hemlington, Middlesbrough, Cleveland TS8 9HE.
 (MAIL ORDER ONLY)

UNIVERSAL NI-CAD CHARGER £5.99

To charge PP3, AA, C & D cells

NI-CAD RECHARGEABLE CELLS AA/HP7 500mA Hr. Pack of 4 £1.50 or 4 packs for only £5.00 (Ex-equipment, tested & guaranteed.)
 AA/HP7 NI-CAD CHARGER incl above pk of 4 cells + holder £4.99

BUTTON BATTERIES 1.5V for watches, calculators, cameras, lighters etc. 4 types any mix £1.50. AG13 11 58 x 5.4mm. AG10 11 58 x 3mm. AG12 11 58 x 4.2mm. AG3 7.87 x 3.6mm or any 8 for £2.50.

ELECTRET CONDENSER MICROPHONE Model EM109, a small mic, for cassette recorders etc. High output. Excellent quality. Fitted with 3.5mm jack plug. £4.50 or 2 for £8.00.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR — update 2. Over 20,000 USA, UK, European & Japanese Transistors with Electrical & Mechanical Specs., Manfcs & available substitutes. £5.95 (Rec. retail price £9.50).

SPEED CONTROL KIT FOR MINI-DRILLS includes completely assembled control unit in smart box with room for transformer. The only connections to make are 2 wires to a suitable transformer. The control unit will handle 2A continuous, 3A intermittent. £4.50.

TRANSFORMER for above 15V, 1A continuous (1.5A intermittent) for smaller type drill £2.90. (Brand new stock. The complete controller is advertised by major manufacturer for over £20!).

HIGH TORQUE MOTOR FOR MINI DRILLS 12V to 18V, 400W, 1000 rpm per volt. 5 pole rotor. Carbon brushes. 50 x 28mm dia. £2.90. (Fits into any 35mm plastic film container).

CHUCK & SET OF COLLETS to 2.5mm for above motor to make an inexpensive drill for PCB work. £2.00.

HSS DRILL BITS WITH SHANKS 1mm — 5 bits for £1.50 0.6mm or 0.8mm — 5 bits for £2.50 or 6 bits (2 of each size) £2.50. (Not recommended for glass fibre.)

All prices inclusive but please add 80p P&P per order.
 Many other items for callers or send s.a.e. for stock list. Goods normally sent by return.

CROYDON DISCOUNT ELECTRONICS

40 Lower Addiscombe Road, Croydon CR0 6AA. Tel. 01-688 2950

It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints.

If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code.


Then, if an advertisement bothers you, you'll be justified in bothering us. 
The Advertising Standards Authority.
 If an advertisement is wrong, we're here to put it right.

ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.

**PLEASE
 MENTION
 EVERYDAY
 ELECTRONICS
 WHEN REPLYING TO
 ADVERTISEMENTS**

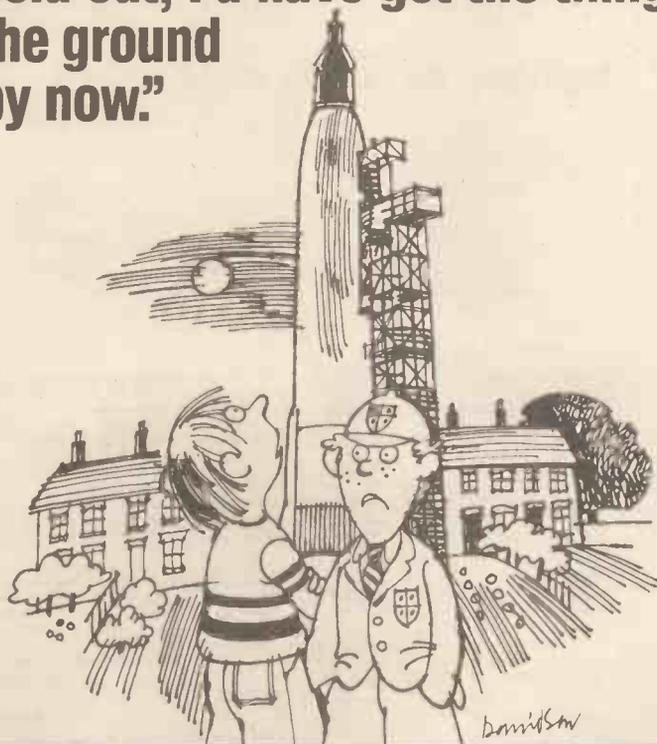"If last month's issue of EVERYDAY ELECTRONICS hadn't sold out, I'd have got the thing off the ground by now."



Sell-out disappointment can upset even the less ambitious reader! So why not take out a year's subscription and make sure of every issue, straight from the Publisher? Complete the order form below and post to EVERYDAY ELECTRONICS, Subscription Dept., Oakfield House, 35 Perrymount Road, Haywards Heath, West Sussex, RH16 3DH.

Annual subscription rates:
 UK £12 Overseas £15

EVERYDAY ELECTRONICS SUBSCRIPTION ORDER FORM

Annual subscription rates:
 UK £12 Overseas £15

To: Everyday Electronics, Subscription Dept., Oakfield House,
 35 Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Name _____

Address _____

I enclose payment of £_____ (cheque/PO payable to Everyday Electronics)

Charge my credit card account the amount of £_____

Card no. _____



Name of card _____ valid from _____ to _____

Signature _____

51

Full Kits Inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.
If you do not have the issue of E.E. which includes the project - you will need to order the instruction reprint as an extra - 70p each. Reprints available separately 70p each + p&p 60p.

THIS MONTH'S KITS


SAE or 'phone for prices

LOW COST POWER SUPPLY UNIT Aug 85	£16.72
TRI-STATE THERMOMETER (Batt) Aug 85	£6.05
TREMOLO/VIBRATO Aug 85	£34.48
STEPPER MOTOR INTERFACE FOR THE BBC COMPUTER less case Aug 85	£13.99
EMERGENCY LIGHTS FLASHER less lamps July 85	£6.39
CONTINUITY TESTER July 85	£5.37
TRAIN SIGNAL CONTROLLER July 85	£8.78
AMSTRAD USER PORT July 85	£15.33
1D35 STEPPER MOTOR EXTRA	£14.50
OPTIONAL POWER SUPPLY PARTS	£4.67
ACROSS THE RIVER June 85	£17.97
ELECTRONIC DOORBELL June 85	£6.55
COMPUTERISED SHUTTER TIMER June 85	£10.61
GRAPHIC EQUALISER June 85	£23.33
AMSTRAD CPC 464 May 85	£15.34
MAINS VERSION	£22.48
AUTO PHASE May 85	£16.39
INSULATION TESTER Apr. 85	£16.96
LOAD SIMPLIFIER Feb. 85	£16.98
SOLID STATE REVERB Feb. 85	£39.98
GAMES TIMER Jan. 85	£7.63
SPECTRUM AMPLIFIER Jan. 85	£5.98
TV AERIAL PRE-AMP Dec. 84	£12.36
Optional PSU 12V £2.03. 240V £9.86	
MINI WORKSHOP POWER SUPPLY Dec. 84	£34.98
DOOR CHIME Dec. 84	£14.91
BBC MICRO AUDIO STORAGE SCOPE INTERFACE Nov. 84	£28.77
PROXIMITY ALARM Nov. 84	£17.98
MAINS CABLE DETECTOR Oct. 84	£4.39
MICRO MEMORY SYNTHESIZER Oct. 84	£47.98
DRILL SPEED CONTROLLER Oct. 84	£6.89
GUITAR HEAD PHONE AMPLIFIER Sept. 84	£6.38
SOUND OPERATED FLASH less lead Sept. 84	£5.91
TEMPERATURE INTERFACE FOR BBC MICRO Aug. 84	£19.70
CAR RADIO BOOSTER Aug. 84	£13.87
CAR LIGHTS WARNING July 84	£7.99
VARICAP AM RADIO May 84	£10.43
EXPERIMENTAL POWER SUPPLY May 84	£18.72
SIMPLE LOOP BURGLAR ALARM May 84	£13.62
MASTERMIND TIMER May 84	£5.44
FUSE/DIODE CHECKER Apr. 84	£3.45
QUASI STEREO ADAPTOR Apr. 84	£10.90
DIGITAL MULTIMETER add on for BBC Micro Mar. 84	£24.98
NI-CAD BATTERY CHARGER Mar. 84	£9.85
REVERSING BLEEPER Mar. 84	£6.78
PIPE FINDER Mar. 84	£3.60
IONISER Feb. 84	£23.98
ZX81 EPROM PROGRAMMER Feb. 84	£14.48
SIGNAL TRACER Feb. 84	£14.89
CAR LIGHT WARNING Feb. 84	£3.76
GUITAR TUNER Jan. 84	£17.73
BIOLOGICAL AMPLIFIER Jan. 84	£19.16
CONTINUITY TESTER Dec. 83	£9.99
CHILDREN'S DISCO LIGHTS Dec. 83	£8.42
NOVEL EGG TIMER Dec. 83 inc. case	£10.24
SPEECH SYNTHESIZER FOR THE BBC MICRO Nov. 83 less cable + sockets	£21.98
MULTIMOD Nov. 83	£16.98
LONG RANGE CAMERA/FLASHGUN TRIGGER Nov. 83	£13.50
HOME INTERCOM less link wire Oct. 83	£14.38
DIGITAL TO ANALOGUE BOARD Oct. 83	£19.98
less cable, case & connector	

HIGH POWER DAC DRIVER BOARD Oct. 83 less case	£12.52
HIGH SPEED A TO D CONVERTER Sept. 83 less cable & connector	£27.98
SIGNAL CONDITIONING AMP Sept. 83 no case	£8.98
STORAGE 'SCOPE INTERFACE FOR BBC MICRO Aug. 83 less software	£15.38
PEDESTRIAN CROSSING SIMULATION BOARD Aug. 83 no case	£10.29
HIGH POWER INTERFACE BOARD Aug. 83 no case	£10.38
USER PORT I/O BOARD less cable + plug	£10.49
USER PORT CONTROL BOARD July. 83 less cable + plug + case	£25.14
GUITAR HEADPHONE AMPLIFIER May. 83	£7.92
MW PERSONAL RADIO less case, May. 83	£7.62
MOISTURE DETECTOR May. 83	£5.46
CAR RADIO POWER BOOSTER April. 83	£11.99
FUNCTION GENERATOR April. 83	£45.98
FLANGER SOUND EFFECTS April. 83	£24.17
NOVELTY EGG TIMER April. 83 less case	£5.48
DUAL POWER SUPPLY March. 83	£59.98
BUZZ OFF March. 83	£4.51
PUSH BIKE ALARM Feb. 83	£11.73
ZX TAPE CONTROL Nov. 82	£7.13
CONTINUITY CHECKER Sept. 82	£5.47
2-WAY INTERCOM July. 82 no case	£4.52
ELECTRONIC PITCH PIPE July. 82	£5.40
REFLEX TESTER July. 82	£7.77
SEAT BELT REMINDER Jun. 82	£4.10
EGG TIMER June. 82	£5.44
CAR LED VOLTMETER less case, May. 82	£3.18
V.C.O. SOUND EFFECTS UNIT Apr. 82	£12.71
CAMERA OR FLASH GUN TRIGGER Mar. 82	£13.65 less tripod bushes
POCKET TIMER Mar. 82	£4.10
GUITAR TUNER Mar. 82	£17.19
SIMPLE STABILISED POWER SUPPLY Jan. 82	£26.98
MINI EGG TIMER. Jan. 82.	£4.40
SIMPLE INFRA RED REMOTE CONTROL Nov. 81	£18.70
CAPACITANCE METER Oct. 81	£25.81
SUSTAIN UNIT Oct. 81	£13.99
TAPE NOISE LIMITER Oct. 81	£4.98
HEADS AND TAILS GAME Oct. 81	£2.75
CONTINUITY TESTER Oct. 81	£4.48
PHOTO FLASH SLAVE Oct. 81	£3.80
FUZZ BOX Oct. 81	£7.98
SOIL MOISTURE UNIT Oct. 81	£6.39
0-12V POWER SUPPLY Sept. 81	£19.48
COMBINATION LOCK July. 81 less case	£21.58
SOIL MOISTURE INDICATOR E.E. May. 81	£4.49
GUITAR HEADPHONE AMP E.E. May. 81	£4.66
PHONE BELL REPEATER/BABY ALARM May. 81	£6.15
INTERCOM April. 81	£24.43
MODULATED TONE DOORBELL Mar. 81	£7.35
2 NOTE DOOR CHIME Dec. 80	£11.35
UVI WIRE GAME Dec. 80	£12.87
GUITAR PRACTICE AMPLIFIER Nov. 80	£4.99
£14.10 less case. Standard case extra	
SOUND TO LIGHT Nov. 80 3 channel	£23.40
TRANSISTOR TESTER Nov. 80	£12.80
AUDIO EFFECTS UNIT FOR WEIRD SOUNDS Oct. 80	£14.40
IRON HEAT CONTROL Oct. 80	£6.30
MICRO MUSIC BOX Feb. 80	£17.86
Case extra	£3.60
SPRING LINE REVERB UNIT Jan. 80	£27.20
UNIBOARD BURGLAR ALARM Dec. 79	£6.70
DARKROOM TIMER July. 79	£3.20
MICROCHIME DOORBELL Feb. 79	£17.48
SOUND TO LIGHT Sept. 78	£9.20
CAR BATTERY STATE INDICATOR less case Sept. 78	£2.29
R.F. SIGNAL GENERATOR Sept. 78	£31.20
IN SITU TRANSISTOR TESTER Jun. 78	£7.50
WEIRD SOUND EFFECTS GENERATOR Mar. 78	£6.20
ELECTRONIC DICE Mar. 77	£4.96

TOOLS

ANTEX MODEL C IRON	£6.98
ANTEX X5 SOLDERING IRON 25W	£7.25
ST4 STAND FOR IRONS	£2.85
HEAT SINK TWEEZERS	45p
SOLDER HANDY SIZE 5	£1.39
SOLDER CARTON	£2.50
SOLDER REEL SIZE 10	£4.67
LOW COST PLIERS	£1.98
LOST COST CUTTERS	£1.99
BENT NOSE PLIERS	£1.89

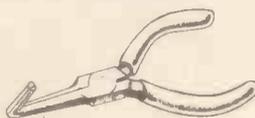

MINI DRILL 12V (MD1)	£8.38
MULTIMETER TYPE 1 100000pV	£6.98
MULTIMETER TYPE 2 20,0000pV	£17.98
MULTIMETER TYPE 3 30,0000pV	£27.98
MULTIMETER TYPE 4 10M DIGITAL	£39.98
DESOLDER PUMP	£5.48
SIGNAL INJECTOR	£2.98
CIRCUIT TESTER	79p
HELPING HANDS JIG & MAGNIFIER	£7.98
MINIATURE VICE (PLASTIC)	£1.85

FUN WITH ELECTRONICS

Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners - children and adults. Only basic tools needed. 64 full colour pages cover all aspects - soldering - fault finding - components (identification and how they work). Also full details of how to build 6 projects - burglar alarm, radio, games, etc. Requires soldering - 4 pages clearly show you how.

COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT. Supplied less batteries & cases. **FUN WITH ELECTRONICS, COMPONENT PACK £16.98 BOOK EXTRA £1.75.** Book available separately.



INTRODUCTION TO ELECTRONICS

An introduction to the basic principles of electronics. With lots of simple experiments. Uses soldering. Lots of full colour illustrations and simple explanations. A lovely book. Ideal for all ages.


INTRODUCTION TO ELECTRONICS COMPONENT PACK **£9.99**
BOOK EXTRA **£2.45**
Book also available separately.

TEACH IN 84

Full kit including 2 EBBO breadboards & a FREE copy of our catalogue. **TEACH IN 84 KIT £22.98 inc VAT.** Reprints 70p each (12 part series).

ROBOTS and MOTORS

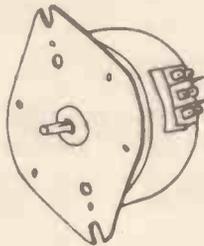DIY Robotics & Sensors Books - with the BBC £7.95; for the Commodore 64 £7.99. Components used in these books are in our catalogue/price list. Catalogue £1. Price list only 50p.
SAA1027 driver £5.99; 8 way darlington driver (ULN2803) £2.38; TL081 49p
EXPERIMENTS WITH YOUR COMPUTER £2.43. Suits BBC, CBM64 and Spectrum. Use your computer for experiments and to analyse information.



HOW TO MAKE COMPUTER CONTROLLED ROBOTS by Potter/Oxlade. BOOK £20. For BBC, Spectrum, C64 & VIC20.

Also similar to above HOW TO MAKE COMPUTER MODEL CONTROLLERS book £3.19.

PRACTICAL THINGS TO DO WITH A MICROCOMPUTER £2.19. Programs, information & electronic circuits.

ID35 Stepper Motor. 48 Steps. 12V. **£14.50**


BBC to ID35 Stepper Motor Interface Kit £13.99 Ref. EE. PCB, driver IC, components, connectors & leads included. Demonstration software listings, circuit diagram, pcb layout & construction details given. Requires unregulated 12Vdc power supply. Interface Kit £13.99; Optional Power Supply Parts £4.67

MOTOR - GEARBOX ASSEMBLIES

Miniature precision made. Complete with quality electric motor. Variable reduction ratios achieved by fitting from 1-6 gearwheels (supplied) as required. Operates from 1.5V to 4.5V. Small unit type MGS speed range 3rpm-2200rpm depending on voltage & gear ratio. Large unit type MGL (higher torque motor) 2rpm-1150rpm. Long 3mm dia output shafts. Ideal for robots and buggies.

Small Unit (MGS) £3.49. Large Unit (MGL) £3.98.

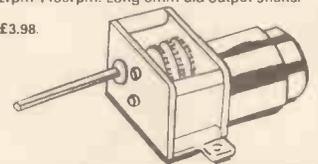Pulley wheels 3mm bore. Metal flange with brass hub. 10mm dia 85p. 20mm dia 98p. 30mm dia £1.21.
Metal collar with fixing screw, 3mm bore 24p. Flexible spring coupling 5mm. Length 31mm 68p
Flexible metal coupling (universal) 3mm £2.98



CATALOGUE

FULLY REVISED 1985 CATALOGUE. Brief details of each kit, our books, & illustrations of our range of tools & components. Also stepper motor, interface kit & simple robotics. Plus circuit ideas for you to build. If you read Everyday Electronics than you need a copy of the MAGENTA catalogue.

CATALOGUE & PRICE LIST - Send £1 in stamps etc. or add £1 to your order. Price list - 9x4 size

Catalogue FREE TO SCHOOLS/COLLEGES REQUESTED ON OFFICIAL LETTERHEAD.

ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £3.58. Component pack £20.98 less battery.

OUR PRICES INCLUDE VAT

MAGENTA ELECTRONICS LTD.

ADD 60P P&P TO ALL ORDERS. PRICES INCLUDE VAT. SAE ALL ENQUIRIES. OFFICIAL ORDERS WELCOME OVERSEAS: Payment must be sterling. IRISH REPUBLIC and BFPO: UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote. 24 hr Answerphone for credit card orders.



EVERYDAY ELECTRONICS and computer PROJECTS

VOL 14 No. 9 SEPT. '85

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

COMPONENT SUPPLIES

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

OLD PROJECTS

We advise readers to check that all parts are still available before commencing any project in a back-dated issue, as we cannot guarantee the indefinite availability of components used.

We regret that **we cannot provide data or answer queries on projects that are more than five years old.**

SUBSCRIPTIONS

Annual subscription for delivery direct to any address in the UK: £12.00. Overseas: £15.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.

BACK ISSUES & BINDERS

Certain back issues of EVERYDAY ELECTRONICS are available world-wide, price £1.00 inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

Binders to hold one volume (12 issues) are available from the above address for £5.50 inclusive of postage and packing worldwide.



ANOTHER ONE!

TEACH IN starts next month. That may not mean very much to our newer readers but to those that have taken EE for a few years it means another beginner's series in our highly rated manner. Teach In's started in the very first issue of EE (November 1971) and have been a part of the magazine every two years since that date. Many thousands of readers have used them to gain a basic understanding of electronics, to further their basic knowledge or to brush up on what might be getting a little outdated or simply forgotten.

Each Teach In has had its own style and presentation, each has employed a different method of practical demonstration, each in its own way has added to the general fund of data available. Many different and respected contributors have taken on the task of writing the series over the years—this year is no exception.

While EE readers may have seen the names of this year's Teach In contributors in our pages, one will be better known to them than the other. Mike Tooley now writes our regular *On Spec* feature and has produced some reviews of commercial products for us recently. David Whitfield has contributed to EE but at present is not a regular EE author. These two are however very well known to readers of our sister publication *Practical Electronics* where they have been regular contributors for many years. Writing as a team they have been responsible for many major constructional projects and a number of theoretical series and reviews. David Whitfield also writes the monthly *BBC Forum* page in PE.

They are both radio amateurs, regular constructors and authors. Mike is Principal Lecturer, Department of Technology at Brooklands Technical College and David is involved in computer software. Their experience and background admirably suit our needs and for *Teach In '86* we have the added advantage of back-up software for the BBC and Spectrum computers. Written by Mike and David, the software will help to reinforce the knowledge gained and keep a check on your understanding and progress.

Don't miss part one next month; copies will be in demand so place an order with your Newsagent now.

Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL, WESTOVER HOUSE,
WEST QUAY ROAD, POOLE, DORSET BH15 1JG

Phone: Poole (0202) 671191

We regret that lengthy technical enquiries cannot be answered over the telephone

Editor

MIKE KENWARD

Secretary

PAULINE MITCHELL
0202 671191 Ext 259

Advertisement Manager

NIGEL BELLWOOD 01-261 6882

Advertisement Sales Executive

RICHARD WILLETT 01-261 6745

Classified Supervisor

BARBARA BLAKE 01-261 5897

Advert Make-Up and Copy Department

JULIE FISH 01-261 6615

Advertisement Offices

EVERYDAY ELECTRONICS
ADVERTISEMENTS
KING'S REACH TOWER
STAMFORD STREET
LONDON SE1 9LS
Telex 915748 MAGDIV-G

UV EXPOSURE UNIT

C. J. BOWES

IT IS now possible for home constructors to buy all the materials needed to make professional quality printed circuit boards. One of the most useful techniques for manufacturing p.c.b.s is the photographic technique, by which prepared artwork is exposed onto sensitised glassfibre p.c.b. The major advantages of this technique are that the artwork is relatively easy to originate, and reasonably simple to correct if an error is detected. Once the master is proved to be correct, as many copies as are needed, can be simply produced rather than having to redraw the design directly onto the p.c.b. every time.

PCB PRODUCTION

Production of p.c.b.s by means of this technique require the sensitised boards to be exposed to ultra-violet (UV) light through the master artwork. This produces a latent image which is developed, either in a special proprietary developer or in sodium hydroxide solution. This produces a dye image on the board which is resistant to the etchant, usually ferric chloride solution, which is used to remove the unwanted copper from the board. This leaves the design originated on the artwork behind on the board. The process requires the use of a suitable light box in which the artwork and sensitised board are held in firm contact and exposed to the UV light.

The box should also screen the operator from the UV light, since prolonged exposure to the wavelengths suitable for exposing the sensitised board can cause irritation to the eyes. The process is also made easier if the light box is fitted with a timer to ensure accurate, and repeatable exposure times. Such light boxes are available from major component suppliers but they tend to be somewhat expensive.

SPECIFICATIONS

The unit described in this article is suitable for home construction and not only provides a suitable box in which to expose sensitised material but incorporates an electronic control system which allows any one of the six predetermined exposure times or a manual control to be selected. An audible warning device is incorporated which is triggered at the end of the preset exposure times, enabling the user to perform other tasks whilst waiting for the end of the exposure sequence to occur.

The construction of the outer case has been made as simple as possible, whilst

giving easy access to the interior components for servicing.

CIRCUIT DESCRIPTION

The circuit diagram of the unit is shown in Fig. 1. The system consists of two control circuits, one a monostable timer circuit and the other a standard flip-flop circuit. These are both triggered by an anti-bounce circuit and connected, via a transistor current amplifier, to a relay, which is used to control the mains voltage to the ultra-violet emitting fluorescent tubes and associated control gear.

STARTING CIRCUIT

A single pole, momentary action, change-over switch (S2) is used both to start the automatic timing circuit and to toggle the manual control circuit. Because of the nature of the 4027 flip-flop i.c. used in the manual control circuit it is necessary to take steps to avoid the problem of contact bounce causing spurious pulses. Suppression of these spurious pulses is achieved by the anti-bounce circuit comprising R8, R9, IC2b and IC2c.

This circuit produces a single pulse output irrespective of how many times the switch contacts may bounce on closing.

The positive going (changing from logic 0 to logic 1) output from the starting circuit is taken directly from the output of IC2c to the clock input of the flip-flop, IC3. The negative going output of the anti-bounce circuit is taken from the output of IC2b and is a.c. coupled to the trigger input of the monostable circuit via C4. R10 and D1 are included in this circuit to give a reliable trigger pulse.

MONOSTABLE TIMING DEVICE

Preset exposure timing is obtained by using half of a CMOS 556 timer i.c. (IC1a) connected as a monostable circuit. In this mode the output of the i.c. swings from 0V to the power supply voltage for a time (T) found by applying the formula:

$$T = 1.1 \times R \times C$$

(Where R = the resistor value in ohms and C = the capacitor value in Farrads.) In this case the capacitor value is that of C3 which is fixed at 100 μ and the value of the resistance is selected by S1a from the network of resistors comprising R1 to R6 and VR1 to VR6. R1 to R6 are wired as a chain of resistors which in combination with C3, provide a time delay of slightly less than that required for each of the preset



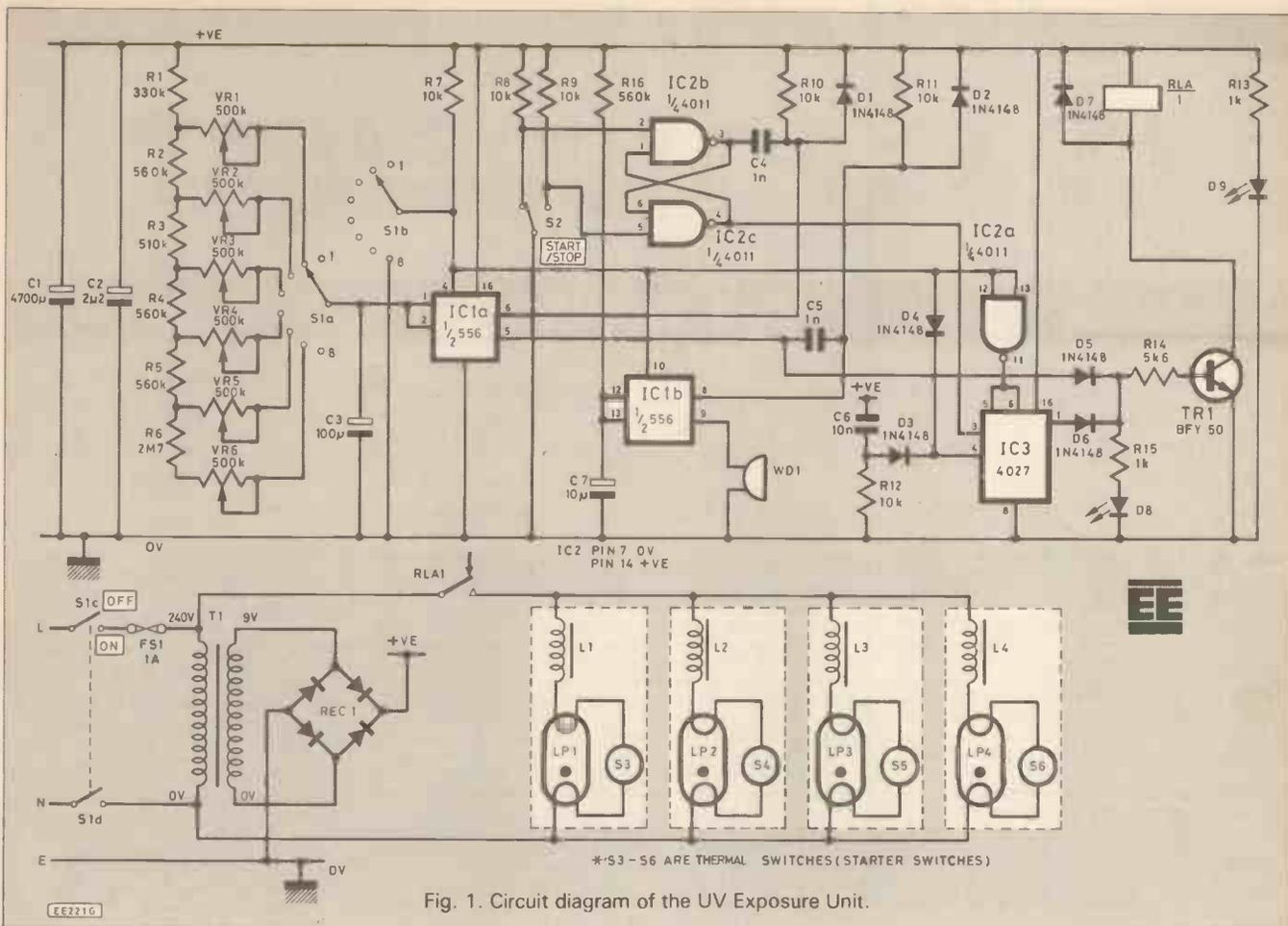


Fig. 1. Circuit diagram of the UV Exposure Unit.

timing intervals. S1a provides a means of adjusting the total value of resistance between V+ and C3. This enables the preset timings to be accurately set and overcomes the problems of tolerance within the timing components. The output from the monostable timer circuit is connected via D5 to the current amplifier which drives relay RLA.

MANUAL CONTROL CIRCUIT

Manual control of exposure time, using the start/stop switch S2, is achieved by means of a 4027 J-K flip-flop (IC3). The clock pulses produced by the anti-bounce circuit are used to toggle the output (Q) of IC3.

In order to ensure that the output from IC3 is at logic 0 when the unit is switched on, C6 and R12 are arranged so as to cause a short logic 1 pulse to be applied to the clear direct input (pin 4) of IC3 every time that power is initially connected to the power supply rails. D3 is used to avoid interference between this pulse and the voltage present at pin 4 of IC1a. In order to ensure that the output of the flip-flop circuit will automatically go to logic 0 when switching from manual to automatic control the clear direct input is also connected, via D4, to the wiper connection of S1b. This is so arranged that whilst automatic control is selected, the clear direct input remains at logic 1, forcing the output (Q) to remain at logic 0. The J

and K inputs are similarly connected, via the inverter formed by IC2a, to the wiper of S1b. This ensures that whilst the manual control option is not selected both the J and K inputs are at logic 0.

This inhibits the output of the i.c. from changing despite the presence of clock pulses at the input. Similarly S1b is used to short the end of R7 to ground. This is connected to the reset input (pin 4) of IC1a so that it is held at logic 0 whilst the manual control option is selected. This inhibits the output of a logic 1 signal by IC1a which would otherwise override the output from the manual control circuit.

The positive going pulses produced by the anti-bounce circuit are fed into the CK (clock) input (Pin 3) of IC3. When the manual control option is selected via S1 the J and K inputs are both a logic 1. Each pulse fed into the CK input causes the output (Q) to change state to the opposite logic state to that at which it currently is. This output is fed to the current amplifier circuit via D6.

UV TUBE CONTROL CIRCUIT

The mains operated UV tubes are controlled through RLA1. Insufficient current is available from the two control circuits to directly drive the relay. So TR1 is used as a current amplifier to boost this current to a sufficient level to operate the relay. The two diodes D5 and D6 act as a simple OR-gate

so that an output from either of the two i.c.s will be able to provide suitable bias current to cause TR1 to conduct through its collector-emitter junction. The relay is connected in series between the positive supply rail and the collector of TR1, thus the current flowing through the collector circuit also flows through the relay causing it to be energised. D8 is an l.e.d. which is illuminated by the output from the diode or gate to indicate that the fluorescent tubes are illuminated.

The unit uses four tubes, each of which is wired in series with a choke for power factor correction. Each fluorescent tube contains two heater filaments, one at each end. These are used to warm the tube up to the point at which electrons are emitted to produce a flow of charge through the gas inside the tube and cause the emission of light by electrons striking the coating inside the tube.

The heaters are initially connected in series until the charge flow is established, after which the circuit is broken to leave one of the filaments connected to Live through its choke and the other to Neutral. In order to achieve this control a Fluorescent Tube Starter is connected in series between the two filaments. The relay is connected so as to control the fluorescent tube circuits by completing the circuit between the mains power line and the chokes when it is energised.


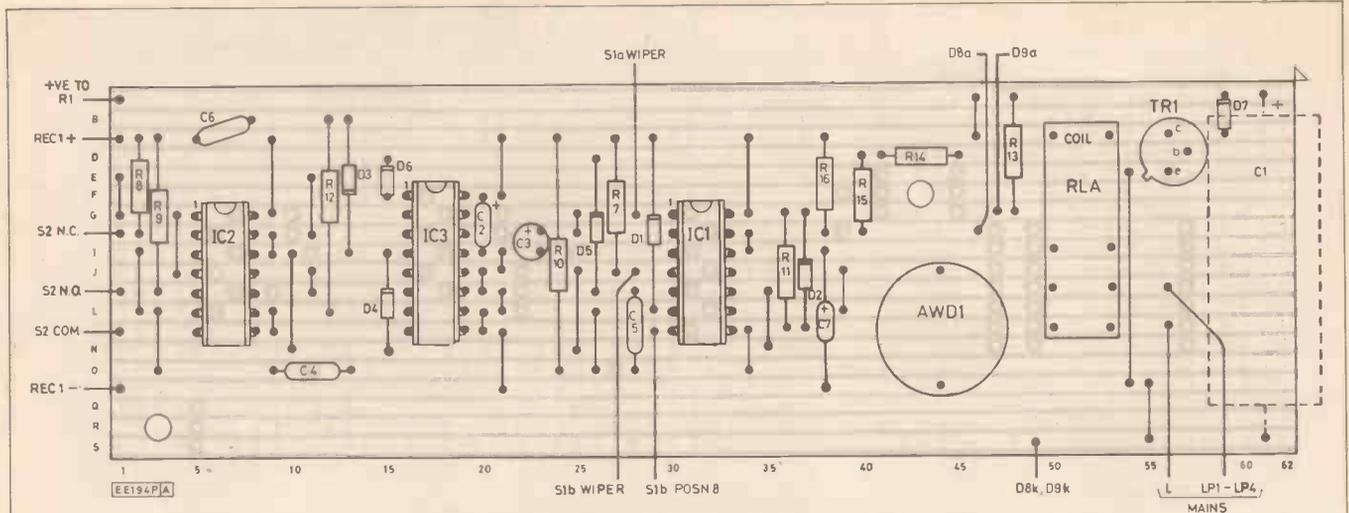


Fig. 2. Main stripboard layout and track details.

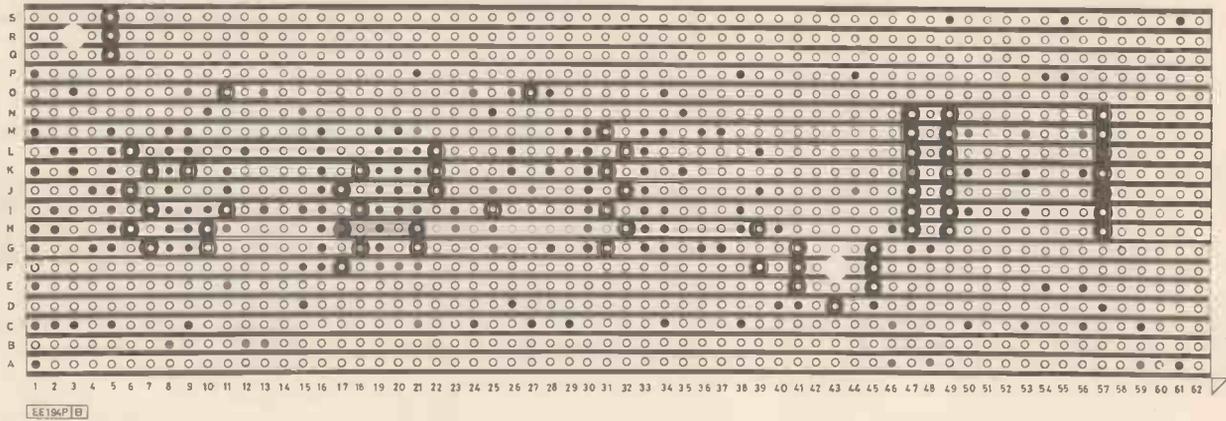

END OF EXPOSURE INDICATOR

An audible warning circuit is incorporated into the design to indicate the end of a preset timing period. The circuit uses the other half of the 556 timer i.c. connected as a monostable. The timing period for the circuit is set by means of R16 and C7 and, with the values given, produces an output of approximately six seconds duration. The circuit is triggered by being a.c. coupled to the output of IC1a. When the output of IC1a goes from the power supply rail voltage to 0 volts a short negative going pulse is produced by C5, D2 and R11. This is connected to the trigger input of IC1b and initiates the timing period. The reset input of this i.c. is connected to the wiper of S1b. This point is normally at logic 1 but the pull-up resistor, R7, is shorted out by S1b, giving a logic 0 state when the manual control option is selected. This inhibits the operation of the audible warning circuit when automatic timing is not selected. The output from IC1b is directly connected to WDI, which is a piezoelectric unit mounted directly onto the stripboard.

POWER SUPPLY

The power supply is conventional, consisting of a mains stepdown transformer, T1, which produces an output of 9V a.c. This is rectified by the diode bridge REC1 and smoothed by C1 to produce a 12V d.c.

output, which is connected across the power supply rails. C2 is a small decoupling capacitor, mounted in the centre of the stripboard.

ELECTRONIC CONSTRUCTION

Construction of the electronics for this project is fairly straightforward, with most components mounted on the main stripboard as shown in Fig. 2. The stripboard should first be prepared by breaking the tracks with a stripboard cutter as shown in Fig. 2. The board should then be turned over and the components mounted in the correct places.

Construction will be helped at this stage if the smaller components and wire links are positioned first and then soldered. These are followed by the next larger components and so on until the relay is positioned last. Note that D7 is located underneath C1 and should obviously be positioned and soldered before C1 is installed. Care should be taken to ensure that all polarity sensitive components, such as diodes, capacitors, the transistor and the i.c.s are correctly positioned. The wire connections to the stripboard should be connected last. Although the board has been arranged so that ribbon cables can be used, single wires can also be used for this purpose. Identification of the correct connections will be aided if wires of different colours are used.

The fixed and variable resistors associated with S1 are mounted on a smaller piece of stripboard and connected to the switch wafer by cable. The layout and track breaks are shown in Fig. 3.

After wiring up the two stripboards they should both be carefully checked for solder bridges, dry joints and incorrectly positioned components. The power supply should then be constructed and used to test out the two stripboards before any attempt is made to install them in the case. It is, however, best to leave calibration of the automatic timing system until after installation is completed, since there is a good possibility of the settings being disturbed during installation.

CASE CONSTRUCTION

This project requires the construction of a more complex case than is usual for most electronic projects. This is because of the need to ensure that the p.c.b. material is held in positive contact with the artwork and that both are correctly positioned over the UV tubes during exposure, as well as the usual function of holding the components safely inside the unit. The prototype was constructed of wood and is in two parts, an inner section which houses all the electronic parts and UV tubes, and an outer case into which the inner section fits. This design has

been chosen to aid installation and servicing. The sides and ends of the units are made of grooved timber which should be obtained as one piece. The groove must be wide enough to take the glass through which the exposure will be made. The sensitised board and artwork are held in position by means of a piece of foam plastics material glued to the underside of the lid. The case lid is hinged to the case and secured by means of two catches mounted on the opposite side of the case. (See photographs.)

INNER UNIT

The slide-in inner section is slightly more complex than the outer case and care must be taken in making it to ensure that it will be a secure fit within the outer case, whilst not requiring the use of excessive force when sliding it into position. The end piece and inner divider are made of the same timber as the outer case and sides and end, but the depth of these pieces is reduced by the thickness of the bases of both the outer case and the inner section. This is to ensure that the control panel slides into the grooves in the outer case when positioned in the grooves of the inner section's end and divider pieces. After these pieces have been cut accurately to size, the base of the inner section is positioned in the outer case and the position of the inner divider determined. This piece should be positioned so that the inner divider will be continuous with the edge of the lid when the latter is fitted. After marking the position of the divider on the base board the edge of the battens fixed to the outer case sides should also be marked before removing the inner base.

The holes through which the wires between the fluorescent tubes and the control circuits pass should be drilled and the divider can then be screwed and glued to the base. The end section can also be glued and screwed to the board at the same time. The support bearers for the UV tubes can also be positioned and glued to the base, care being taken to ensure that they do not protrude over the lines marked denoting the edge of the outer case bearers. Two screws, one each side, are required to hold the inner case in position in the outer case. The position of these can be marked and the holes drilled at this stage.

FINISHING

After the case has been completed it should be carefully checked to ensure that all the parts fit together. The case should then be sanded and painted. The inside of the light box section, including the part of the inner section divider which forms the fourth side of the light box, is painted matt white up to the level of the grooves into which the glass fits. The part of the inner section base which is not covered with the aluminium foil is also painted matt white. The lid, outside of the outer case, the edges and the inside of the case, down to the level of the grooves are painted to taste. Once the paint is dry foam plastic material can be glued to the inside of the lid and after the glue has dried the lid hinges can be fitted

COMPONENTS

Resistors

R1	330K
R2,R4,R5,	
R16,	560K (4 off)
R3	510K
R6	2M7
R7-12	10K (6 off)
R13-15	1K (2 off)
R14	5K6
VR1-VR6	500K $\frac{1}{4}$ W min. preset. (6 off)

Resistors (All $\frac{1}{4}$ watt high stability unless otherwise stated)

Capacitors

C1	4,700 μ 16V electrolytic
C2	2 μ 2 16V, tantalum
C3	100 μ 16V, electrolytic
C4,C5	1n disc (2 off)
C6	10n disc
C7	10 μ 16V, electrolytic

Semiconductors

REC 1	1A, 50V chassis mounting bridge rectifier
D1-D7	1N4148
D8	red 0.2in. l.e.d.
D9	green 0.2in. l.e.d.

TR1	BFY50
IC1	556 dual CMOS timer
IC2	4011B, quad two-input Nand Gate
IC3	4027B, dual J K flip-flop

See
**Shop
Talk**

page 477

Miscellaneous

S1 2 pole, 8 way rotary switch with mains switch (use 12 pole, 2 way); S2 s.p.d.t. momentary action push switch; 28mm knob for S1; 15mm knob for S2; RLA 12V p.c.b. mounting relay with mains contacts; T1 240V primary, 9V, 6 VA secondary transformer; FS1 20mm, 1A fuse and holder; S3-6 fluorescent tube starters and holders (4 off); LP1-LP4 8W fluorescent tube chokes (4 off); L1-L4 8W UV fluorescent tubes (N.B. the "Blacklight" tubes sold by disco shops are not suitable, use the replacement tubes sold by component suppliers); Mains lead and plug; P clip to accept Mains cable; Stripboard 19 strips x 62 holes, Stripboard 14 strips x 21 holes; 14 way d.i.l. socket (2 off), 16 way d.i.l. socket, 12V, p.c.b. mounting audible warning device; Materials for case.

Approx. cost
Guidance only **£45**


and the lid and its retaining catches can be fitted to the outside of the case.

CONTROL PANEL

The main control panel of the unit is designed to fit into the four grooves which surround the electronics compartment. The panel can be manufactured from any mate-

rial, or combination of materials, which have the same thickness as the glass. It can be painted, if necessary, and lettered with rub-down lettering secured by numerous coats of spray or clear varnish. Alternatively, the artwork can be transferred photographically, using the light box onto UV sensitive film which is then processed and stuck to the material of the panel.

Fig. 3. Timing stripboard and track details.

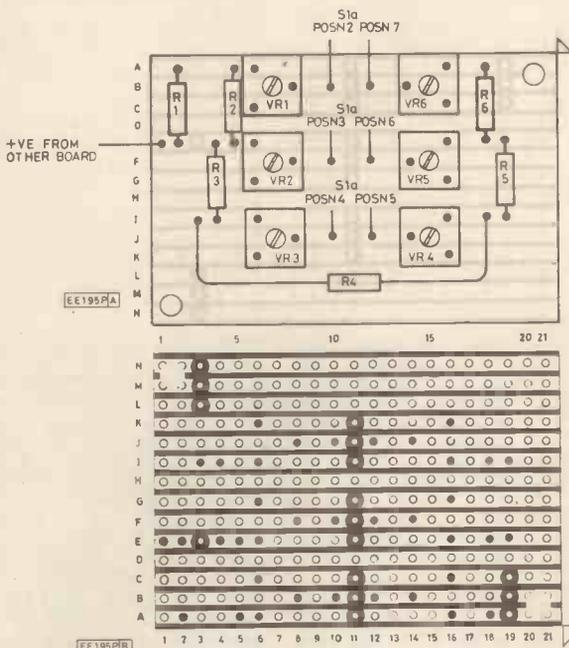



FINAL ASSEMBLY AND CALIBRATION


Once the box and the appropriate parts of the inner section have been completed the project can be assembled. All that is required to complete the case is to carefully slide the glass into the grooves. This should be done very gently with the hand pushing the glass wrapped securely in a thick towel. This is a vital safety precaution since the towel will protect the vulnerable arteries in the wrist from damage if the glass should fracture as a result of being pushed too hard.

The completion of the inner section consists of installing and connecting up the electronics. Firstly, the eight terry clips which are used to hold the UV tubes should be screwed to the bearers, so that the tubes will be evenly spaced.

The cables connecting the control circuitry to the ends of the fluorescent tubes farthest away from the electronics compartment should be glued to the base of the inner section with contact adhesive, care being taken to ensure that they lie flat on the base and pass neatly through the cut away undersides of the tube bearers. After the adhesive has dried the reflector, which is made from baking foil, should be cut to size and stuck to the base, over the top of the already installed cabling, with contact adhesive.

The stripboards, fluorescent tube control gear and power supply components are then installed as shown in the photographs and connected up to complete the circuit as shown in Fig. 1.

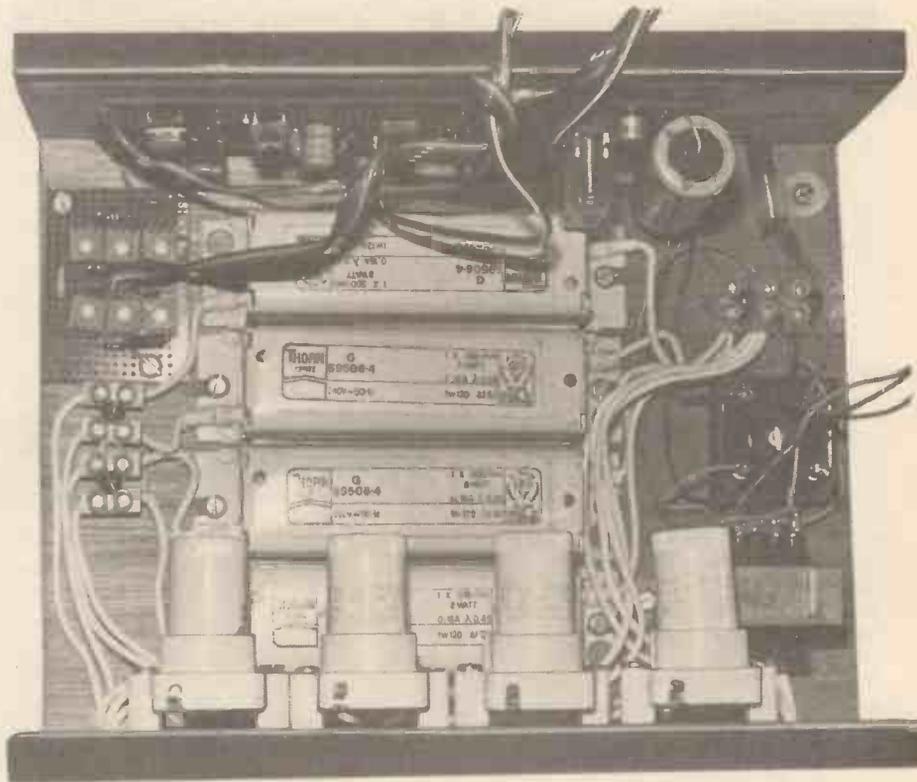The fluorescent tubes should then be fitted into their terry clips, connected up and then tested by switching S1 to the manual position and operating S2. The four tubes should individually strike and commence emitting light. They should also switch off on a subsequent operation of S2. It is advisable at this point to test the



Photographs illustrating the constructional details of the UV Exposure Unit.


operation of the circuit on the shortest automatic setting, to ensure that the striking of the tubes does not interfere with the timer circuit's operation.

The final task is to set the six presets (VR1 to VR6). This is best accomplished with all the fluorescent tubes except for that which strikes slowest, disconnected. The process is performed by selecting each of the auto time settings in turn with S1 and adjusting the appropriate preset until the

correct duration between the striking of the tube and its being extinguished at the end of the timing period is accurately achieved. If the time is too short, the preset should be adjusted to increase the resistance and vice-versa if the tube remains lit for too long then the preset should be adjusted so that the value of resistance should be reduced.

Once all the presets have been adjusted, the disconnected fluorescent tube leads, should be reconnected and the inner section

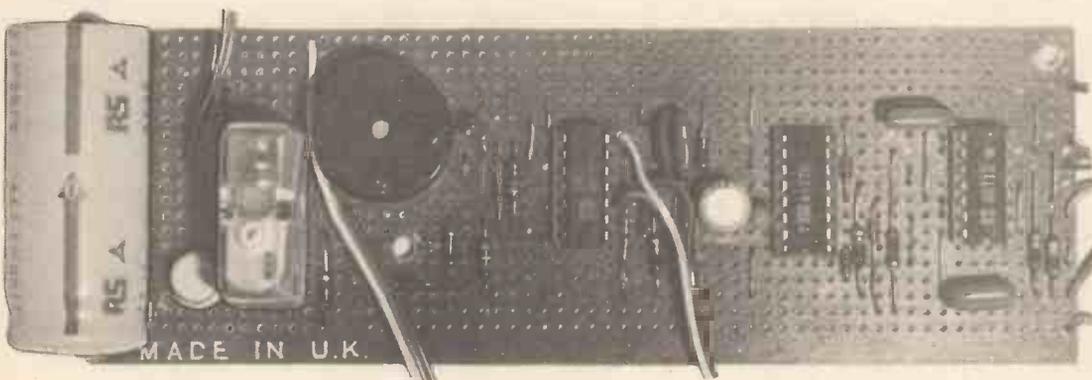slid into the outer case, taking care whilst so doing to carefully align the control panel in its grooves. The inner section is finally secured in place by screwing into position the two case fixing screws. □



Main stripboard layout showing the position of C1, the p.c.b. mounted relay and AWD1.

SHOP TALK



BY RICHARD BARRON

Catalogues Received

We have received the latest catalogue from **Greenweld** which replaces the 1984/85 edition (purple cover) and the winter supplement. It is priced at 70p but this can be recovered by making use of the discount vouchers on the back page of the catalogue. Up to £1 can be saved.

The catalogue contains a large and well illustrated range of components presented in alphabetic order. There is also a range of: kits, modules, test instruments and other miscellaneous items.

One section particularly worth a mention is the bargain list supplement which contains a good selection of very low-cost goodies such as: multimeters, power supplies and component packs.

More details are available from: **Greenweld Electronic Components, Dept. EE, 443, Millbank Rd., Southampton, SO1 0HX. ☎ (0703) 772501.**

Also this month, we received a late copy of the 1984/85 catalogue from **Marco Trading**. This contains a comprehensive list of components, audio products, cases, TV accessories, tools and electrical products.

Some of the product lines and prices in this catalogue may now be out of date but the 1985/86 catalogue will be available soon for around £1, and as usual will contain a bargain supplement.

For more details contact: **Marco Trading, Dept. EE, The Maltings, High St., Wem, Shropshire, SY4 5EN. ☎ (0903) 32763.**

The quarterly offering from **RS** is now available which covers their total product range for July to October. Unfortunately this catalogue is only available to trade customers. Despite this, some components for projects published in *EE* are specified as an **RS** part.

If you have trouble finding an equivalent then it is worth while getting in touch with a retail electronic components company who will often help; indeed they may even be able to supply the actual part you require.

Test Gear

Test gear is always of some interest to the hobbyist. We recently received the new short-form instruments catalogue from **Thandar**.

Some of the test instruments are a little expensive but there are a few oscilloscopes and multimeters which may be of

interest. Further details about these are available from: **Thandar Electronics Ltd., Dept. EE, London Rd., St. Ives, Huntingdon, Cambs., PE17 4HJ.**

Robots

Maplin Electronics, well known to the electronics hobbyist, is now set to become the major European supplier of non-industrial robots.

In order to better handle their expanding robot marketing and sales, Maplin have established a new Robot division. **Dave Snoad** who heads the Maplin robotic operations, believes that robots could before long become as popular as the home video or computer. Meanwhile, with the role of robots in industry continuing to expand, there is a considerable demand for training robots such as the "HERO"—the world's number one best seller.

Maplin are now developing interfaces for their highly competitively priced range of robots to such popular microcomputers as the Sinclair ZX81 and Spectrum, Commodore C-64 and the Acorn BBC-B.

Robot kits from Maplins come in a range of prices starting around £79.95 for the ZERO 2.

More details are available from: **Maplin Electronic Supplies Ltd, Dept. EE, PO Box 3, Rayleigh, Essex, SS6 8LR. ☎ (0702) 552911.**

On Spec For Spectrum Owners

If you are a Spectrum or Spectrum Plus owner, then our *On Spec* page is designed especially for you. It contains a host of useful tips and circuit ideas for making more use of your micro.

If you have any queries, or ideas which may be of interest to other Spectrum owners please write to:

Mike Tooley,
Department of Technology,
Brooklands Technical College,
Heath Road,
Weybridge,
Surrey KT13 8TT.

P.S. If you would like a copy of the latest "Spectrum Update" don't forget to include a stamped addressed envelope.

CONSTRUCTIONAL PROJECTS

Caravan Alarm

It is important to use the correct type of relay (RLA) for the *Caravan Alarm*, a suitable one being available from **Maplin Electronics**. The case used for the prototype of this project is also available from Maplin Electronic Supplies Ltd., Dept EE, PO Box 3, Rayleigh, Essex, SS6 8LR.

Fridge Alarm

The components for the *Fridge Alarm* project are readily available from many of the advertisers in *EE*. However, make sure that when you order the Quad 2-input CMOS NAND gate to specify the 4011UBE or the 4011BE as these are necessary to achieve very low quiescent current.

Personal Stereo PSU

The p.c.b. mounted transformer used on the prototype of the *Personal Stereo PSU* was supplied by **RS Components**. If there is any difficulty experienced in finding a similar transformer then a chassis mounted type may be used. Details of this are given in the article.

Resistance Thermometer (Transducers—1)

It is worth looking around at the various plugs and sockets available for the *Resistance Thermometer* as it may be worth using a cheaper alternative to the type used on the prototype. The platinum film probe for this project is available from **RS Components**, stock number 158-402.

RIAA Preamp/Input

The NE5534A i.c. specified for the *RIAA Preamp/Input* is a special low noise version but the LF351 or TL071 may be used as an alternative. The latter versions are cheaper but cause a loss of 10dB signal to noise ratio. The NE5534A is available from **Rapid Electronics, Dept. EE, Unit 3, Hill Farm Ind. Estate, Boxted, Colchester, Essex, CO4 5RD.**

Semiconductor Thermal Indicator (Transducers—1)

The programmable current source used in the *Semiconductor Thermal Indicator* is available from **Maplin Electronic Supplies**, order code WQ 32K.

UV Exposure Unit

The various "electrical" parts such as the starters and chokes for the *UV Exposure Unit* are available from many DIY electrical shops. The tubes may be a little harder to locate but are available from **RS** (stock no. 556-250). The other components are fairly common.

Voltage Regulator Unit (Building Blocks—2)

As was mentioned last month, the p.c.b. for this project is available from the **EE PCB Service** and is part of a set of four. This enables you to build four projects from one p.c.b. making each one very cheap.

ELECTRONIC BUILDING BLOCKS

PART TWO

RICHARD BARRON

BEFORE we continue this series, I must apologize for an error which appeared in Part One. The centre tap of the transformer should be connected to the 0V output track on the p.c.b. (Fig. 13) and not to C3 as shown.

Last month we took a close look at obtaining low voltage d.c. supplies derived from the mains. As we saw, that whilst being useful in some applications, an unregulated supply has many short-comings: only one voltage is available which is unstable when subjected to a wide range of load currents. Generally, as the current demand varies, the output voltage varies accordingly. Also, even with a constant load there will be a ripple content to the output voltage at a frequency of 100Hz (for full-wave rectified voltages derived from the mains. See Fig. 1).

The effect of this may be negligible for many loads such as d.c. motors or lamps, but it is almost certain to cause misoperation of loads incorporating i.c.s., especially digital circuits. Now we must consider some new *building blocks* which can be used to improve upon the simple supply.

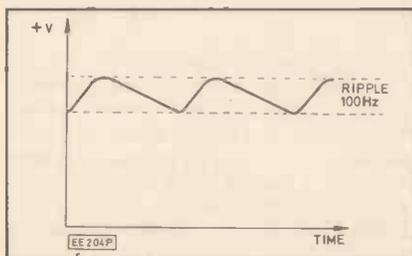


Fig. 1. 100Hz ripple.

CONSTANT VOLTAGE

The basic element of any regulated supply is a known voltage reference which can be relied on under a wide range of conditions. This reference usually relies on the characteristics of some form of semiconductor diode. We saw the basic characteristics of diodes in part one but now we must take a closer look at these devices which are used in many electronic circuits.

DIODES

The circuit symbol for the diode is shown in Fig. 2, together with a graph illustrating its general V-I characteristics. It can be seen that once the forward bias voltage threshold has been reached (usually around 0.6V for silicon diodes) the diode will pass a wide range of current with very little effect to the voltage across it. This characteristic can be utilised to provide a useful voltage reference.

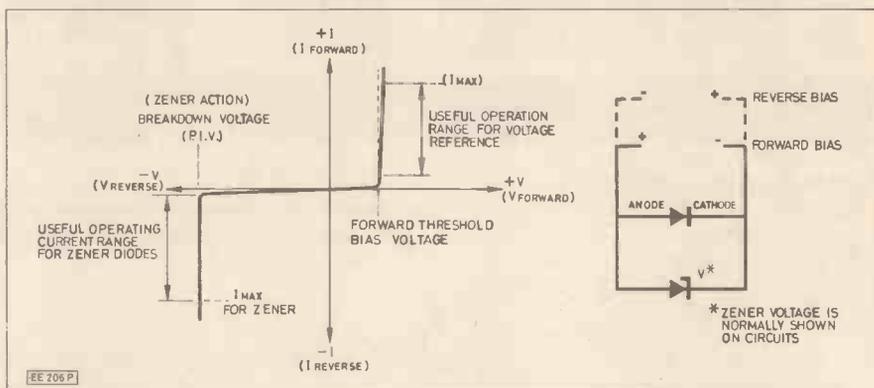


Fig. 2. Circuit symbols and diode characteristics.

Also shown in the graph is the diode reverse bias conditions. On ordinary diodes, once the peak inverse voltage has been exceeded, the diode will break down under the avalanche effect. If this occurs the diode is rendered useless. However there are certain diodes which can be used in the avalanche region, namely zener diodes.

ters can be influenced by other factors, particularly temperature. Typical limits are usually specified for a given working temperature (often 25 degrees C). Temperature variations caused by power dissipation or environmental conditions may cause these voltage and current parameters to change. The effects of this can be minimised by

ZENER DIODES

The action of the zener diode is similar to the standard diode except that providing the maximum reverse current is not exceeded, the diode will recover from the avalanche region. Since the zener diodes can be constructed to present different reverse voltage break-down levels, they provide very useful voltage references.

For our purposes, the characteristics outlined so far are the most important but it must be borne in mind that these param-

TYPE	IF MAX	PIV
IN4148	85mA	75V
IN4001	1A	50V
IN4002	1A	100V
OA202	80mA	150V
IN5401	3A	100V

Table 1a. Some common diodes.

TYPE	VOLTAGE RANGE	POWER
BZY88 SERIES	2.7-15V	500mW
BZX85 SERIES	2.7-6.8V	1.3W
BZX88 SERIES	7.5-72V	1.3W

Table 1b. Some common zeners.

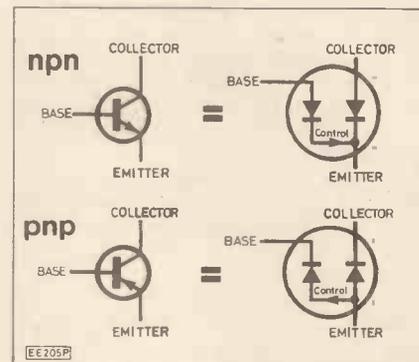


Fig. 3. Transistor action.

operating diodes well within the working limits especially the current limits. Table 1 lists the basic specifications of some common diodes.

Another semiconductor device used in regulator circuits is the transistor. These devices have a variety of applications which will be described in a forthcoming article in this series. In the mean time we will take a look at the basic characteristics of two types of transistor and try to explain their operation in terms of diode action.

Fig. 3 illustrates the circuit symbol and schematic constructional details of the bipolar *npn* and *pnp* transistor. To make use of these devices it is not necessary to have an in-depth understanding of their construction but merely to know their limits of operation.

For our purposes, transistors may be considered as two diodes connected anode-to-anode or cathode-to-cathode and these are called *pnp* and *npn* types respectively. This gives us three terminals: base, emitter and collector. If we consider the base-emitter diode as a control device for the collector-emitter diode then the operation should be fairly easy to grasp.

The base-emitter diode must be forward biased to allow the collector-emitter diode to pass current. Only a relatively small base current is required to allow a large collector current to flow. The relationship between these two currents is called the current gain (h_{fe}) of the transistor. In fact transistor characteristics are much more complicated than this but this explanation will do for now. Some typical transistor characteristics are shown in Table 2.

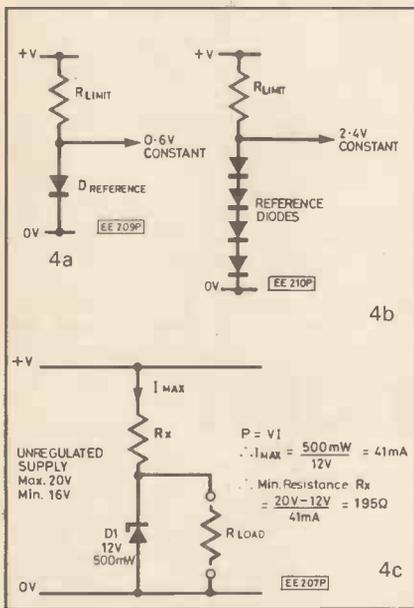


Fig. 4. Diode voltage references.

BUILDING

Now that some of the very basic concepts of semiconductors have been established we can now build on these to provide some practical designs for voltage reference *building blocks*.

Fig. 4 shows how diodes may be used to give us a fixed voltage which is tolerant to a wide range of supply voltages.

In Fig. 4a an ordinary diode is forward biased via a current limiting resistor to give a potential of 0.6V with respect to 0V. (Remember most silicon diodes require around 0.6V to conduct.) The limiting resistor should limit the current to well below the maximum forward current specified for the diode. Suppose the supply voltage is likely to vary from 8V to 12V then we would expect the voltage across the limiting resistor to vary between (12V-0.6V) and (8V-0.6V). This gives us between 11.4V and 7.4V across the resistor. Now if the diode had a maximum forward current of say 200mA then the resistor should be greater than: $11.4V/0.2A = 57$ ohms.

TYPE	CONSTRUCTION	Pt	Ic	Vce	Vcb	h_{fe}	Ft
BC107	npn	360mW	100mA	45V	50V	110-450	250MHz
BC108	npn	360mW	100mA	20V	30V	110-800	250MHz
BC109	npn	360mW	100mA	20V	30V	200-800	250MHz
BC212	pnnp	300mW	-200mA	-50V	-60V	60-300	200MHz
BC213	pnnp	300mW	-200mA	-30V	-45V	80-400	350MHz
BC478	pnnp	360mW	-150mA	-40V	-40V	110-800	150MHz
BFY51	nnp	800mW	1A	30V	60V	40	50MHz
2N3905	pnnp	310mW	-200mA	-40V	-40V	50+	150MHz

Pt=Total power which may be dissipated by the transistor
Ic=Maximum collector current
Vce=Maximum potential across collector-emitter junction
Vcb=Maximum potential across collector-base junction
hfe=Typical range of current gain
Ft=Maximum frequency of operation (switching)

Table 2. Some common transistor characteristics.

In Fig. 4b there are four diodes connected in series to provide a reference of around 2.4V. Any number of diodes may be connected this way to provide a range of references to suit. Obviously this may be impractical, but nevertheless useful to remember.

Fig. 4c shows a zener diode reverse biased to provide a 12V reference from a 20V unregulated supply. The principle of the calculations required to work out an appropriate limiting resistor value are exactly the same as for the ordinary diode.

However, as can be seen from Table 1, zener diodes are usually specified as having maximum power dissipations rather than maximum currents. So suppose a zener is described as a 6.3V device with a max power rating of 500mW. Then since power (P) = $V I$ watts, the maximum current is $500mW/6.3V = 79mA$. Therefore the limiting resistor for a 12V supply should be greater than $(12-6.3V)/0.079A = 81$ ohms.

CONSIDERING THE LOAD

The basic voltage references we have discussed so far are limited in use. This is due to the variations in load which we expect to operate. If we consider the circuit of Fig. 4c where a simple zener circuit is used to provide a constant supply of 12V then it is easy to show its limitations.

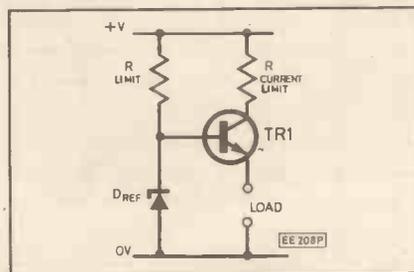


Fig. 5. Simple transistor regulator.

Suppose we have chosen a limiting resistor of 200 ohms and the load resistance requires a maximum current of 10mA at 12V. Now the limiting resistor has to pass current to keep the diode in its zener region plus 10mA to supply the load. In this case all is well as a current of 10mA through 200 ohms will only cause a voltage drop of 2V.

Even under worst case situations when the supply to the circuit has dropped to 16V there is still enough current to keep the diode biased to its zener region.

However, now let us consider the circuit has to supply a maximum current of 100mA. This will cause a drop across R_X of $0.1 \times 200 = 20V$. Obviously this is unacceptable as even under ideal conditions when the supply is at 20V the load cannot be operated.

INCREASING CURRENT CAPABILITY

To overcome the problem outlined above, a transistor can be introduced into the circuit which can supply the extra current and still maintain the correct voltage. The circuit of Fig. 5 shows how this may be achieved. A voltage reference is fed to the base of TR1 which causes the base-emitter junction to be forward biased when a load is connected. The base current need only be very small to maintain this condition as the collector-emitter "diode" will supply the necessary current to operate the load.

When using circuits of this type, a high gain transistor should be used which is of the correct current and power rating. Table 3 shows how transistors are normally specified in data sheets, giving various current limits such as collector current I_c , and voltage ratings such as base-emitter voltage, V_{be} . More of this will be explained when we look at our constructional project for this month.

INTEGRATED CIRCUITS

Although useful and indeed practical design ideas, the simple constant voltage regulators described so far are still less than adequate for supplying many circuits. Much more complicated configurations employing such techniques as spike rejection, overload protection and thermal compensation are available. In most cases however it is not necessary to design these types of circuits as they are available in integrated circuit form.

A few of the available voltage regulator i.c.s are listed in Table 3 and Fig. 6 shows

their pin-out details together with some standard methods of utilising them. It should be noted that most regulator i.c.s. require a heat sink to enable them to be used to their full capacity.

FORMULAE

Electronics can be a very complicated subject to study, but by applying some basic rules you should be able to make your way round many circuits without too much difficulty. From what we have discussed so far, you should be able to design some basic power supplies using only some very simple formulas. These are summarised in Table 4.

When applying these simple rules and formulae, remember to always consider "worstcase" situations, ie when is the current greatest or when is the volt-drop greatest.

From Ohms Law:

$$V = IR \quad ; \quad I = \frac{V}{R} \quad ; \quad R = \frac{V}{I}$$

The power dissipated in a d.c. circuit is given by:

$$P = VI \quad ; \quad V = \frac{P}{I} \quad ; \quad I = \frac{P}{V}$$

Table 4. Formulae.

TYPE	OUTPUT VOLTAGE	O/P SHORT CIRCUIT CURRENT	I/P VOLTAGE RANGE
7805	+5V	750mA	7-25V
7812	+12V	350mA	14.5-30V
7815	+15V	230mA	17.5-30V
7824	+24V	150mA	27-38V
7905	-5V	750mA	-7-25V
7912	-12V	350mA	-14.5-30V
7915	-15V	230mA	-17.5-30V
7924	-24V	150mA	-27-38V

Table 3. Voltage regulator characteristics (78 and 79 series).

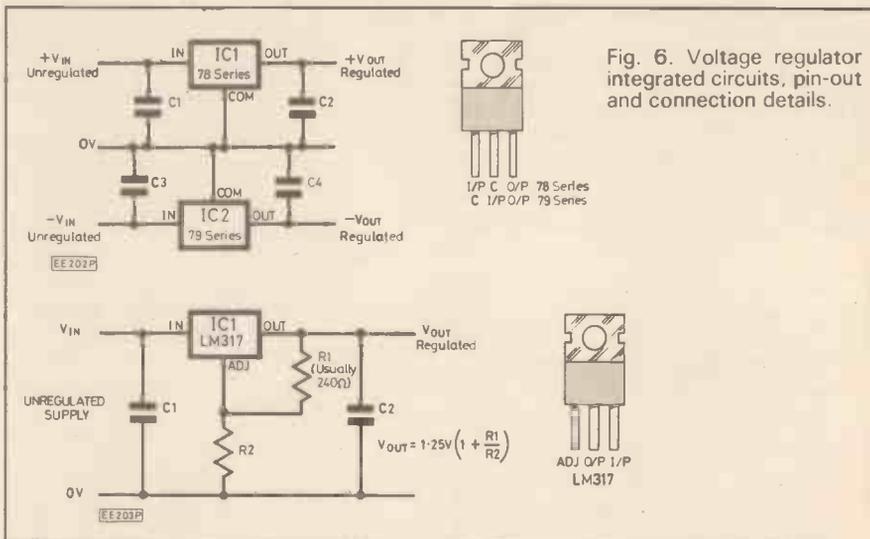


Fig. 6. Voltage regulator integrated circuits, pin-out and connection details.

VOLTAGE REGULATOR UNIT

This month's constructional project is a useful voltage regulator board which may be used in conjunction with last month's project to supply a range of voltages suitable for many other devices. Both discrete components and integrated circuits are used to give a variable plus and minus supply as well as a fixed 5V supply suitable for driving TTL and CMOS i.c.s.

CIRCUIT OPERATION

The circuit operation (Fig. 7) is fairly straightforward once the principles mentioned so far have been understood. The 5V supply uses a 7805 i.c. in its standard configuration and the positive variable supply uses a common LM317 i.c. The LM317 generates its own internal voltage reference which may be adjusted via a couple of external resistors, R1 and VR1.

The 7805, a fixed regulator, needs only a couple of external capacitors which help to provide added ripple protection and good regulation. Like the LM317 this i.c. is designed to provide internal overload, thermal and short circuit protection. These characteristics makes them both very easy and convenient to use. They are also both fairly inexpensive.

NEGATIVE SUPPLY

The negative voltage reference is obtained from a zener diode connected be-

tween 0V and the negative rail of the unregulated supply. A variable resistor, VR2, is connected across the voltage reference and its centre tap is used to provide a variable reference of between 0 and 7.3V which is fed to the base of TR1. TR1 and TR2 are connected in the Darlington configuration which produces a high current gain.

If a load is connected the emitter-collector junctions of the two transistors become forward biased and are able to supply sufficient current to drive the load. At all times the voltage at the emitter of TR2 remains constant as it is controlled by the volt drop across the base-emitter junctions of TR1 and TR2. In this case the output voltage will always be 1.2 (0.6 x 2) volts more positive than the voltage at the centre tap of VR2. R3 provides some degree of over current or short circuit protection.

DEVICE CONSIDERATION

IC1 and IC2 were chosen because of their proven reliability and ease of use. Both devices can safely supply an output current in excess of 500mA but under these conditions would require a heat sink due to the large power dissipation. Since this regulator board is only expected to supply around 300mA, heat sinks are not necessary.

In the variable output configuration used here the output voltage of the LM317 is given by:

$$V_{out} = 1.25V \left(1 + \frac{R2}{R1}\right) + I_{adj} R2$$

Using the values of R1 and R2 as shown, this would give an output voltage up to about 13V. However using the power supply from Part One limits this to around 8.5V in practice.

COMPONENTS

Resistors

R1	270
R2	100
R3	15 1 Watt

Capacitors

C1-C3	1µ tant. bead (3 off)
C4	10µ tant. bead

Semiconductors

D1	7V3 200mW zener
TR1	BC179
TR2	2N3905
IC1	LM317 voltage reg.
IC2	7805 voltage reg.

Miscellaneous

VR1	2k5 p.c.b. mounted pot.
VR2	10k p.c.b. mounted pot.
4mm sockets (4 off); wire; solder, etc.	

Approx. cost Guidance only **£4.50**

If this board is going to be used with other power supplies to provide a greater voltage and current range, then a heat sink may be required. In this case it is necessary to know the power likely to be dissipated by the regulator. This can be found by the formula: Power dissipation (P) = (V_{in} - V_{out}) × I_{out}.

POWER DISSIPATION

The zener diode used in this circuit is specified as being a 200mW, 7.3V device. Since the input to the regulator circuit is about 9V max, the voltage across R2 will be 1.7V max. This gives us a current of 17mA, therefore the power dissipated by D1 will be (7.3V × 17mA) 124mW maximum which is well within limits.

The output current from the zener reference will be small as it flows through a resistance of 10 kilohms (VR2). Although some current flows into the base of TR1 it can be ignored as it is negligible.

TR1 and TR2 are connected in the Darlington configuration to provide a large current gain (TR1 gain × TR2 gain). Whatever current is provided by this transistor pair, the output voltage remains the same, between 0V and 6.5V.

Most of the current to the output is supplied by TR2 which means that most of the power in this part of the circuit is dissipated by TR2. R3 is included to give some protection against over current conditions. It can be seen that if the output is say 6V then there will be about 2V dropped across R3. This will give a maximum current of (2V/15Ω) 133mA. If the circuit draws more current, the voltage drop across R3 will increase thus protecting the output transistor from being overheated.

The voltage and currents specified for TR2 are well within the limits of this circuit but a heat sink may be required.

CONSTRUCTION

All of the components for this circuit are mounted on a small p.c.b. which is shown in Fig. 9. This p.c.b. is obtainable from the EE p.c.b. service and is part of a single board (Fig. 8) containing four different circuits. All you have to do is carefully cut off the board you require. This idea means that the p.c.b. for each project in this series is very cheap.

As with all p.c.b. construction it is best to mount the smallest components first. The integrated circuits and transistors should be fitted last. All the input and output wires should be connected to p.c.b. pins to make a neater job. The outputs are terminated on 4mm sockets and should be labelled, 0V, 5V +V and -V.

VR1 and VR2 are p.c.b. mounted devices which makes it very

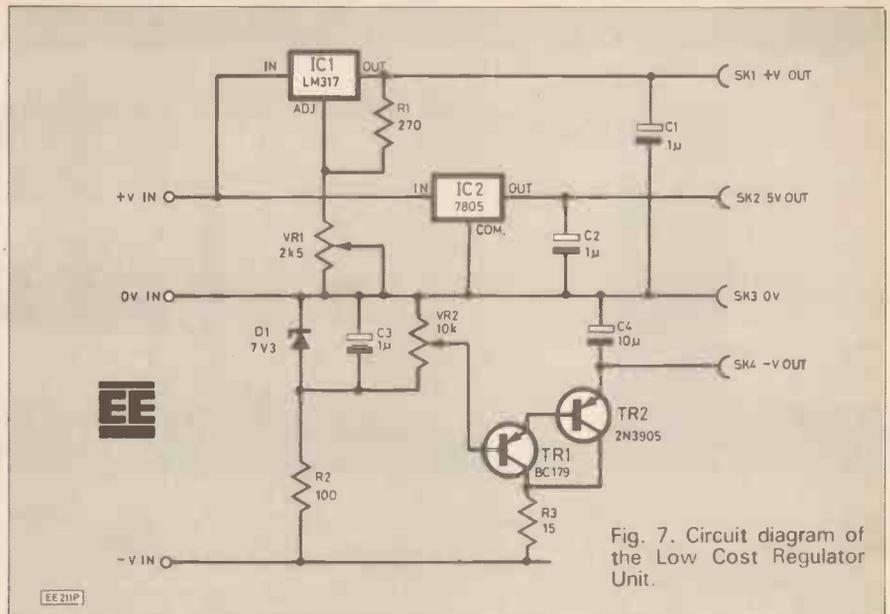


Fig. 7. Circuit diagram of the Low Cost Regulator Unit.

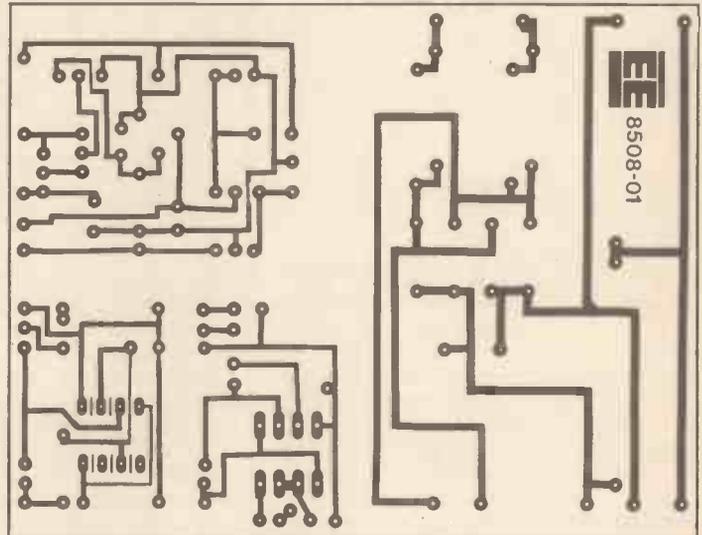


Fig. 8. P.c.b. design for four separate projects.

easy to mount the circuit in a suitable box. If you are using it in conjunction with the project from Part One there is plenty of room in the case for this and other circuits which will be described in other parts.


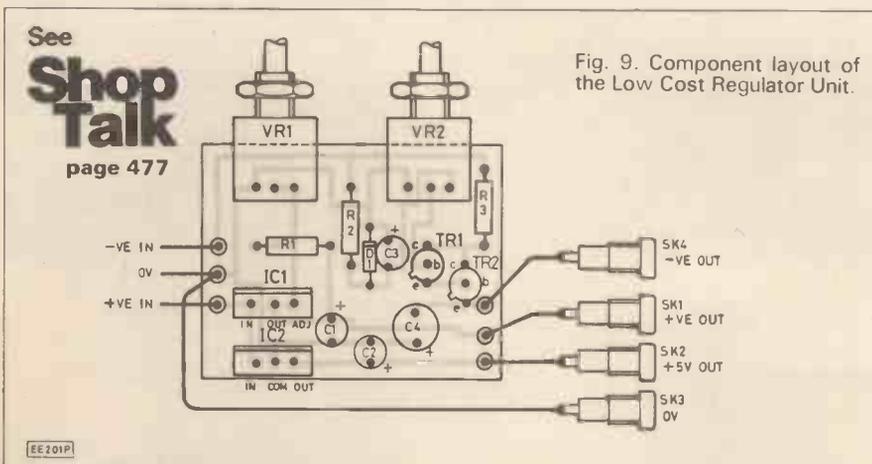


Fig. 9. Component layout of the Low Cost Regulator Unit.

Photo illustrating the Low Cost Regulator Unit p.c.b. assembly which may easily be added to the PSU of Part One.

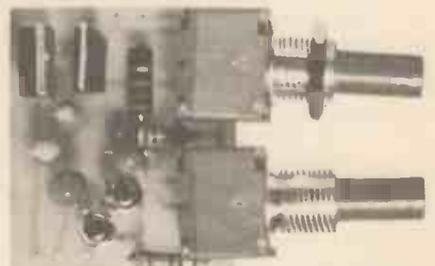

NEXT MONTH: We shall take a look at one of the most common building blocks used in electronics, the oscillator. The constructional project will be a simple audio signal generator.



FRIDGE ALARM

R.A. PENFOLD

MOST refrigerators have a form of door latch which usually fully closes the door once it is almost closed, but this does not always happen, and the door can sometimes be left slightly ajar. This results in wasted power as the refrigeration mechanism tries to cool the flow of air into the refrigerator, and of more importance, it can result in the interior temperature rising well above its normal level if the refrigeration mechanism is unable to cope with this inflow of air. This is not necessarily a disastrous situation, but it is certainly an undesirable one, especially if a long time passes before it is noticed and rectified.

This alarm is designed to prevent the door of a refrigerator from being accidentally left open for more than a minute or so. It is a form of light operated switch which is completely self contained and is merely placed in any convenient position inside the refrigerator. With the door closed the unit is in darkness and goes into its inactive state. In this mode the current consumption is extremely low, being typically only about one microamp. This is very important as the unit must operate continuously in a low temperature from a battery supply, and a negligible current consumption is essential if a reasonably long battery life is to be obtained. The battery should, in fact, have virtually its shelf life, and should only need to be replaced about two or three times a year.

The unit is activated by even quite low light levels. Many refrigerators have an internal light which is operated by a micro-switch and is automatically switched on when the door is open. This should provide considerably more than an adequate light level to activate the alarm, and the precise position of the unit within the refrigerator should not be too critical. Not all refrigera-

tors have an automatic light, and with those that do not the positioning of the alarm is somewhat more critical since there is only light entering the fridge through the partially open door to activate the unit. However, the high sensitivity of the light detector circuit helps to avoid having things excessively critical in this respect.

A straightforward light activated alarm would be usable, but it would have the disadvantage of triggering every time the refrigerator door was opened. This is avoided by incorporating a delay circuit which prevents the alarm from being sounded for around 1.5 minutes after the unit is activated. If the door is closed within this time the delay circuit is reset over a period of a minute or so, so that the full delay is obtained next time the door is opened. It might occasionally happen that the door will be intentionally left open for more than the delay period, and the alarm will obviously then be operated. The alarm can either be ignored and allowed to reset itself once the door is closed again, or to save on battery consumption (and one's nerves) the unit can be manually reset using the reset button. The alarm sound is a simple audio tone generated by a ceramic resonator, which should be perfectly satisfactory for this application.

SYSTEM OPERATION

The basic manner in which the unit functions is quite easy to understand, and the block diagram of Fig. 1 should help to explain the way in which it operates.

Obviously the first stage of the unit is a light detector, and as explained previously this must offer high sensitivity. One consequence of this high sensitivity is a high output impedance with inadequate drive current to operate the delay circuit properly. This is overcome by incorporating a buffer stage which gives a high level of current gain and enables the delay circuit to be driven properly even under quite low light levels. The delay circuit itself is just a CR type. This is used to operate an audio oscillator when the charge voltage exceeds a certain level. In order to ensure reliable gating of the oscillator a high gain amplifier is used to give a "sharper" control signal to the oscillator.

The oscillator does not have a high drive current available, and could not drive a normal loudspeaker properly (even a high impedance type). It is used to drive a ceramic resonator which generates a reasonably loud tone from the limited available drive current of only about two milliamps.

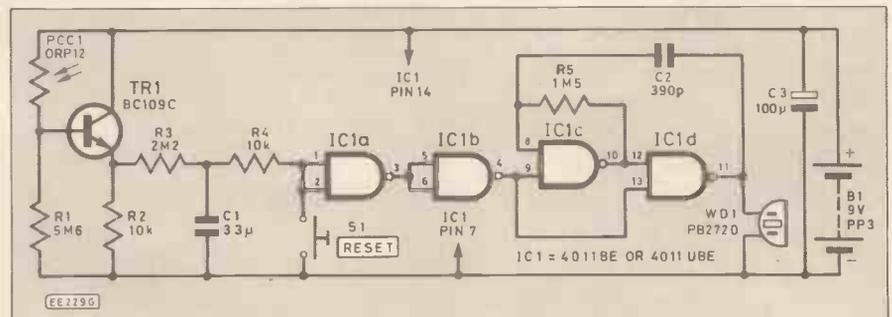


Fig. 2. Complete circuit diagram.

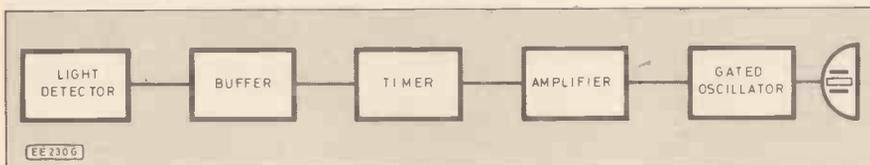


Fig. 1. Block diagram of the Fridge Alarm.

CIRCUIT OPERATION

The full circuit diagram of the unit is shown in Fig. 2; this is based on a CMOS 4011 quad two input NAND gate. Both the 4011BE (buffered) and 4011UBE (unbuffered) versions are suitable for this circuit.

Starting with the light detector circuit, a cadmium sulphide photoresistor PCC1 is connected to R1 to form a potential divider circuit. Under dark conditions PCC1 exhibits a resistance of many megohms, giving a very low output voltage from the potential divider circuit. The resistance of PCC1 falls in response to an increasing light level, and under a reasonable light level it will have a resistance of one megohm or less, giving an output voltage from the divider circuit which is something approaching the full supply potential. Resistor R1 has been given a high value in order to give the circuit good sensitivity.

The buffer amplifier consists of emitter follower TR1 and its load resistor R2. With PCC1 in darkness the input voltage to the base of TR1 will be so low that this device will be cut off, and only minute leakage currents will flow through it. This is an important point as it ensures that the buffer amplifier provides an insignificant contribution to the circuit's current consumption under stand-by conditions. The very high resistance through PCC1 and R1 results in

the light detector circuit also having an insignificant current consumption of only about one microamp.

Resistor R3 and C1 form the CR delay circuit. When the output from TR1 switches to the high state, C1 starts to charge via R3. The voltage across C1 rises exponentially rather than in a linear manner. In other words, as the voltage across C1 rises, the voltage across R1 decreases, giving a lower charge current and a slower rise in voltage.

It takes 5CR seconds for the charge voltage to reach more than 99 per cent of the input voltage, but only about 1CR seconds for it to reach approximately two thirds of the input voltage. In this case the charge voltage must reach typically a little under two thirds of the supply voltage in order to activate the alarm. With the specified values this results in a delay of about one minute or so, but in practice the precise delay obtained will vary somewhat from one unit to another due to component tolerances. Obviously the exact delay is not too important in this application, but if necessary it can be altered by using a different value for R3. The length of the delay is proportional to the value of this component.

It is necessary to use a tantalum bead capacitor for C1 as this type generally has a much lower leakage level than an ordinary electrolytic of the same value. A low leakage current is essential in this case as the charge current is very low. Anything other than a very low leakage level would result in all the charge current leaking away and a charge potential equal to the trigger voltage would never be reached.

Two gates of IC1 (IC1a and IC1b) connected in series are used as the amplifier.

Both gates have their two inputs connected together so that they function as simple inverters. The output of IC1b is normally low, but when the charge on C1 reaches the transition voltage of the inverters (about half to two thirds of the supply voltage) the output of IC1b changes from the low state

to the high one in just a fraction of a second. The high combined gain of IC1a and IC1b of around 2500 times ensures that a fast transition is obtained despite the very slow rate of change at the input. Resistor R4 is a protection resistor for the input of IC1a, and S1 is the reset switch. When operated, the latter discharges C1 by way of R4 which then protects S1 against an excessive current flow and contact sparking.

The oscillator is built around IC1c and IC1d, and this is virtually a conventional CMOS astable circuit. It differs from the standard configuration only in that a control signal is applied to one input of each gate, while the other input of each device is used to give an inverter action. The output of a NAND gate is low when both inputs are high, but is high if one or both of the inputs are low. This means that taking one input of each gate low ensures that the outputs must go high, and operation of the oscillator is blocked. However, when the control inputs are taken high, the output state of each gate is controlled by the other input, and oscillation is enabled. Thus the alarm sounds when the output of IC1b goes high.

The PB2720 ceramic resonator is a piezoelectric device which offers high efficiency at frequencies of around 2kHz to 4kHz. The alarm sound should be sufficiently loud for this application, but if desired the value of C2 can be altered to obtain the frequency which gives optimum efficiency and volume from WD1.

The choice of a CMOS device as the basis of this circuit was not an arbitrary one, CMOS devices have the advantage of a very low quiescent current consumption. In fact, the quiescent current drain of the 4011 is negligible. The current consumption will rise substantially when the refrigerator door is opened and the photocell circuit is activated, and it will rise further if the alarm switches on, but the current drain never exceeds more than about four milliamps.

CONSTRUCTION

Start construction by cutting out a 0-1in.

COMPONENTS

Resistors

R1	5M6
R2,4	10k (2 off)
R3	2M2
R5	1M5
All $\frac{1}{4}$ W 5% carbon film	

Capacitors

C1	33 μ 10V tantalum bead
C2	390p ceramic
C3	100 μ 10V axial elect.

Semiconductors

IC1	4011UBE or 4011BE CMOS quad 2 input NAND gate
TR1	BC109C


Miscellaneous

PCC1	ORP12 light dependent resistor
WD1	PB2720 ceramic resonator—available from Cirkit, 43-27203
B1	9 volt battery (PP3 size)
S1	Push to make/release to break switch

0.1 inch matrix stripboard, 26 holes by 13 copper strips; case about 107 by 66 by 39mm; battery connector; 14 pin d.i.l. i.c. holder; wire; solder; fixings; etc.

Approx. cost
Guidance only **£7.50**

See
**Shop
Talk**
page 477

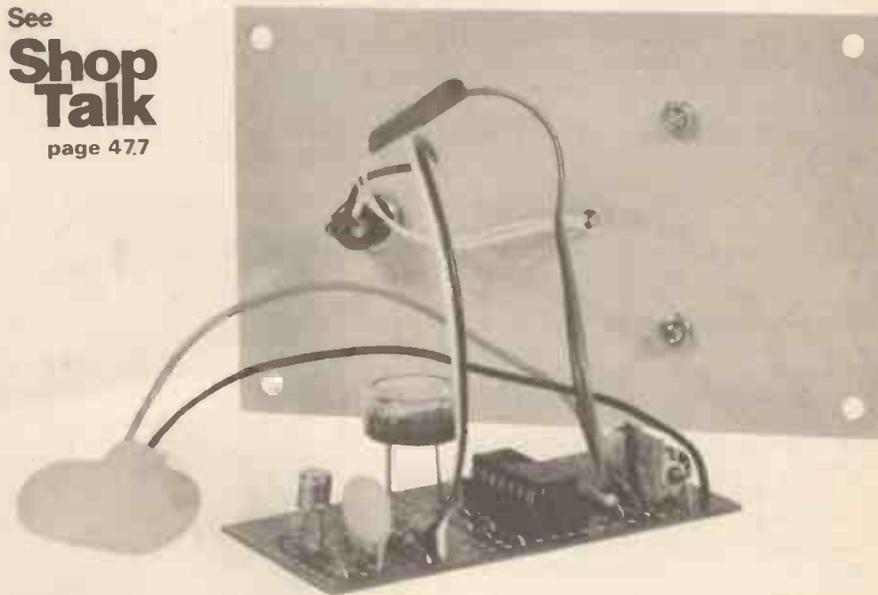

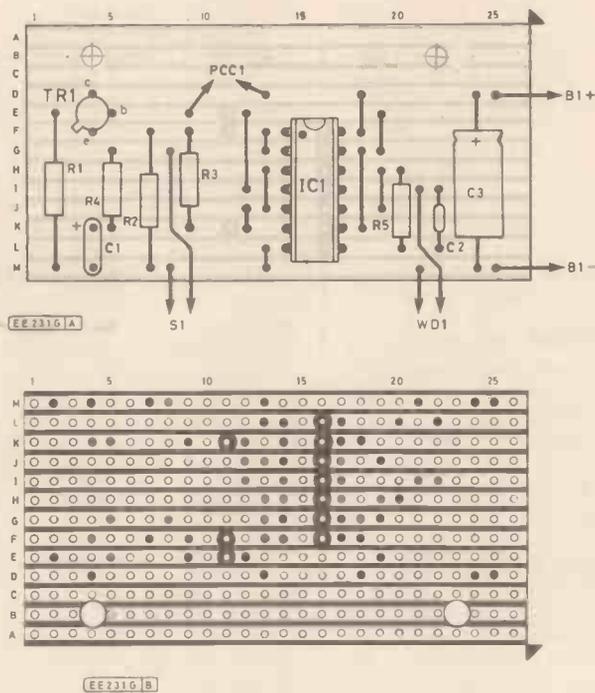


Fig. 3. Veroboard layout and wiring for the Fridge Alarm.

pitch stripboard having 26 holes by 13 copper strips. File any rough edges to a smooth finish and then make the cuts in the copper strips, as detailed in Fig. 3. The cuts can be made using either a special tool or a small hand-held drill bit. If the unit is not to be housed in the specified case the two 3.2 millimetre diameter mounting holes should also be drilled at this stage. These holes are not required if the board is fitted in the specified case.

As IC1 is a CMOS device it requires the normal antistatic handling precautions. It should be fitted in a 14 pin d.i.l. integrated circuit holder, but it should not be plugged into the holder until all the other components and the link wires have been soldered into place. It should be left in the antistatic packaging until then, and handled as little as possible when it is being plugged into the holder. Do not overlook any of the link wires—there are nine in all. Light dependent resistor PCC1 should be left with long leadout wires (about 20 millimetres long).

It is advisable to use the specified case for this project as it has printed circuit guide rails into which the component panel will slide. The case is a plastic type with a metal front panel and approximate outside dimensions of 107 by 66 by 39 millimetres. The component panel fits into the second set of vertical guide rails counting from the left hand end of the case. The component side of the board faces towards the left hand end of the case, and a hole about 10 to 12 millimetres in diameter is drilled adjacent to PCC1 to enable light to pass through to it. If a different case is used the component panel must be bolted in place using M3 or 6BA fixings. The board should be positioned so that PCC1 is close to the "window" drilled in the case.

Switch S1 and WD1 are mounted on the front panel, WD1 requires two short 8BA mounting bolts plus fixing nuts. Apart from the holes for these, a third small hole is needed in the front panel to enable the leadout wires of WD1 to pass through to the interior of the case. Alternatively, WD1 can be mounted behind the front panel, but this is a more difficult way of doing things as a large (30 millimetre diameter) cut out is then needed to accommodate the front plate of WD1.

The unit is completed by wiring S1, WD1, and the battery clip to the component panel, as shown in Fig. 3. It is likely that the leadout wires of WD1 will prove to be slightly too short, and extension leads must then be fitted. However, use some insulation tape or pieces of sleeving over the connections to make quite certain that they do not accidentally short circuit.

TESTING

As an initial test the unit can simply be

left in dimly lit room, and the alarm should operate after very roughly one minute. Placing the unit in darkness should result in the alarm cutting off again. Check the reset button by bringing the unit back into the light and pressing S1 once the alarm starts operating again.

It is a good idea to check that the quiescent current consumption of the unit (i.e. the current consumption with PCC1 in darkness) is no more than a few microamps. In the unlikely event of the current consumption being rather on the high side a cure should be effected by reducing the value of R1 to 1 megohm. This should only be done if an excessive stand-by current consumption is detected as it would otherwise unnecessarily reduce the sensitivity of the unit.

There should be no difficulty in finding a suitable position for the unit inside the refrigerator. In the case of one which does not have an interior light PCC1 must obviously be aimed towards the door opening. □




BAKERS DOZEN PARCELS

All the parcels listed below are brand new components. Price per parcel is £1.00, but if you order 12 you get one extra free, except those marked 's/h'.

- 1 — 5 13 amp ring main junction boxes
- 2 — 5 13 amp ring main outlet boxes
- 3 — 25 13 amp fuses for ring mains
- 4 — 5 surface mounting switches suitable insulated for mains voltage
- 5 — 3 flush electrical switches intermediate type, will also replace 1 or 2 way switches
- 6 — 5 in flex line switches
- 7 — 4 in flex line switches with neons
- 8 — 2 30 watt brass candle elements
- 9 — 2 mains transformers with 6v 1a secondaries
- 10 — 2 mains transformers with 12v 1/2a secondaries
- 11 — 1 extension speaker cabinet for 6 1/2" speaker
- 12 — 5 octal bases for relays or valves
- 13 — 12 glass reed switches
- 14 — 4 OCP 70 photo transistors
- 15 — 25 assorted germanium transistors OC45 etc
- 16 — 4 tape heads, 2 cassettes
- 17 — 2 ultra sonic transmitters and 2 ditto receivers
- 18 — 2 15000 mfd computer grade electrolytics
- 19 — 2 light dependent resistors similar DRP12
- 20 — 5 diff micro switches
- 21 — 2 mains interference suppressors
- 22 — 2 25 watt crossover units
- 23 — 1 40 watt 3 way crossover unit
- 24 — 250 various screws and self tappers
- 25 — 1 of each wafer switches — 6p 2 way; 4p 3 way; 2p 6 way; 1p 12 way
- 26 — 2 tape deck counters
- 27 — 1 6 digit counter 12v
- 28 — 1 6 digit counter mains voltage
- 29 — 1 BOAC in flight stereo unit (second hand)
- 30 — 2 Nicad battery chargers
- 31 — 1 key switch with key
- 32 — 2 humidity switches
- 33 — 2 aerosol cans ofICI Dry Lubricant
- 34 — 36 x 1 metre lengths colour-coded connecting wires
- 35 — 4 battery operated motor coils
- 36 — 2 air spaced 2 gang tuning condensers
- 37 — 2 solid dielectric 2 gang tuning condensers
- 38 — 10 compression trimmers
- 39 — Long and Medium wave tuner kit
- 40 — 4 x 485 KC IF transformer
- 41 — 8 Rocker Switches 10 amp Mains SPST
- 42 — 6 Rocker Switches 10 amp Mains SPDT
- 43 — 5 Rocker Switches 10 amp SPDT Centre Off
- 44 — 4 Rocker Switches 10 amp DPDT
- 45 — 1 24 hour time switch mains operated — (s/h.)
- 46 — 1 6 hour clockwork timeswitch
- 47 — 2 lever switches 4 pole changeover and ditto down
- 48 — 2 6v operated reed switch relays
- 49 — 10 neon valves — make good night lights
- 50 — 2 x 12v DC or 24V AC AC relay
- 51 — 1 x 12v 2C 0 very sensitive relay
- 52 — 1 x 12v 4C 0 relay
- 53 — 2 mains operated relays 3 x 8 amp changeovers (secondhand)
- 54 — 10 rows of 32 gold plated IC sockets (total 320 sockets)
- 55 — 1 locking mechanism with 2 keys
- 56 — Miniature Uniswitch with circuit for electric jigsaw puzzle
- 57 — 5 Oolits' House switches
- 58 — 2 telephone hand sets incorporating ear piece and mike (s/h)
- 59 — 2 flat solenoids — ideal to make current transformer etc.
- 60 — 5 ferrite rods 4" x 5/16" diameter aerials
- 61 — 4 ferrite slab aerials with L & M wave coils
- 62 — 4 200 ohm earpieces
- 63 — 1 Mullard Thyristor trigger and modules
- 64 — 10 assorted knobs 1/2 spindle
- 65 — 5 different thermostats, mainly bi-metal
- 66 — Magnetic brake — stops rotation instantly
- 67 — Low pressure 3 level switch
- 68 — Heavy duty 4 pole contactor — 24v coil
- 69 — 2 25 watt pots 8 ohm
- 70 — 2 25 watt pots 1000 ohm
- 71 — 4 wire wound pots — 18, 33, 50, and 100 ohm
- 72 — 1 1250 watt dimmer Ultra ref SE20
- 73 — 4 3 watt wire wound pots 50 ohm
- 74 — 50 1/3 watt carbon film resistors food spread 10 values
- 75 — 20 2 watt carbon resistors 10 values
- 76 — 30 1 watt carbon resistors 15 diff values
- 77 — 1 time reminder adjustable 1.60 mins
- 78 — 5.5 amp stud rectifiers 400V
- 79 — 4 2a bridge rectifiers 400V
- 80 — 2 10a bridge rectifiers 30V
- 81 — 2 30a panel mounting thyristor fuses
- 82 — 4 porcelain fuse holders and fuses
- 83 — 1 fluorescent choke — your choice — 15, 20, 30, 40 or 65w watt
- 84 — 10 — 1 mains voltage suppressor condensers
- 85 — 1 mains shaded pole motor 1/4" stack — 1/4 shaft
- 86 — 2 5" all fan blades fit 1/4" shaft
- 87 — 2 3" plastic fan blades fit 1/4" shaft
- 88 — Mains motor suitable for above blades
- 89 — 1 mains motor with gear box 1 rev per 24 hours
- 90 — 1 mains motor with gear box 1 rev per 12 hours
- 91 — 2 mains motor with gear box 16 rpm
- 92 — 4 fluorescent starters suit 4 — 80 w tubes
- 93 — 4 11 pin moulded bases for relays
- 94 — 5 B7C valve bases
- 95 — 4 skirted B9A valve bases
- 96 — 1 thermostat for fridge
- 97 — 1 infra red fire element 1000 watts
- 98 — 1 motorised stud switch (SH)
- 99 — 5 assorted ferrite shapes
- 100 — 3 ferrite magnets
- 101 — 1 2 1/2 hours delay switch
- 102 — 1 9v mains power supply unit
- 103 — 1 6v mains power supply unit
- 104 — 1 4 1/2v mains power supply unit
- 105 — 1 5 pin flex plug and panel socket
- 106 — 1 12v vibrating reed beepers
- 107 — 5" speaker size radio cabinet with handle
- 108 — 5 different multi medium croc clips
- 109 — 10 1/4" spindle type volume controls
- 110 — 10 slider type volume controls
- 111 — 2 musical boxes (less keys)
- 112 — 1 heating pad 200 watts
- 113 — 1 fm front end with tuning condenser and data
- 114 — 1 1w amplifier Mullard 1172
- 115 — Wall mounting thermostat 24v
- 116 — 3 pairs small 2prs. medium croc clips
- 117 — 4 pairs large (car size) crocodile clips
- 118 — Teak effect extension 5" speaker cabinet
- 119 — 1 log & 1 coal fibreglass fire fronts
- 120 — p.c.b. with 2 amp full wave and 4 other recs.
- 121 — 2 — 13 amp flush switched sockets
- 122 — 10 mtrs twin screened flex white p.v.c. outer
- 123 — 100 plastic with hardened pin flex clips
- 124 — 10 assorted slide switches

SOUND TO LIGHT UNIT

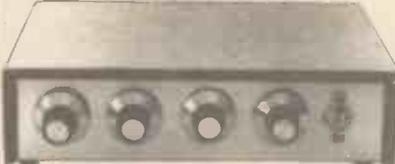

Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form.

CAR STARTER/CHARGER KIT Fiat Battery! Don't worry you will start your car in a few minutes with this unit — 250 watt transformer 20 amp rectifiers, case and all parts with data £16.50 or without case £15.00, post paid.

4/5A BATTERY CHARGER Transformer and rectifier £3.95 & £1 post, 3 kits £12.

WALL MOUNTING ROOM THERMOSTAT By Danfoss has a really pretty two tone grey case with circular white scale and dial. Setting temperature from 0 — 30 c — 13 amp 250v contacts. Price £4.60 — 10 for £40.

EX-G.P.O. TELEPHONES

Black heavy type	£5.50
Lightweight 746 type	£7.50
Ex-G.P.O. plug	£1.00
Ex-G.P.O. socket	£1.00

PRESTEL UNITS

These are brand new and we understand tested, came with manufacturer's guarantee now void as the manufacturer no longer trades. These originally sold for over £150. We offer them complete, except for 7 plug in r.c.'s and price is only £14.95 (less than the value of the modern included).

STABILISED POWER SUPPLY (Mains Input) By LAMOA (USA) Ideal for computer add-ons, d.c. output. Regulated for line volts and load current. Voltage regulation 1% with input variations up to 20%. Load regulation 1% from no load to full load — or full load to no load. Complete in heavy duty case. Models available 5v - 9A £23, 12v - 1.5A £13.25, 15v - 1.2A £13.25, 24v - 2A £23.

25A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you wake — switch on lights to ward off intruders — have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. Independent 60 minute memory jogger. A beautiful unit at £2.50.

THIS MONTH'S SNIP

TOP OF THE POPS LIGHTING
if you use our disco switch **ONLY £6.90**

These have 12 x 10 amp changeover switches each rated at 10 amps so a whole street could easily be lit with one. Switches adjustable and could be set to give a running light, random flashes, etc. 230 volts main operation. Brand new, made by Honeywell. Offered at approximately one third of cost.

COMPUTER DESKS

Again available. Computer desks — size approx 4' x 2' x 26" high formica covered, cost over £100 each. Our price only £9.50 — you must collect — hundreds supplied to schools.

50 THINGS YOU CAN MAKE

Things you can make include Multi range meter, Low ohms tester, A.C. amps meter, Alarm clock, Soldering iron minder, Two way telephone, Memory jogger, Live line tester, Continuity checker, etc. etc., and you will still have hundreds of parts for future projects. Our 10kg parcel contains not less than 1,000 items — panel meters, timers, thermal trips, relays, switches, motors, drills, taps, and dies, tools, thermostats, coils, condensers, resistors, neons, earphone/microphones, nicad charger, power unit, 90% are unused components.

YOURS FOR ONLY £11.50 plus £3.00 post.

REVERSIBLE MOTOR WITH CONTROL GEAR

Switch by the famous Framco Company this is a very robust motor size approximately 7 1/2" long, 3 1/2" dia. 3/8" shaft Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

1 Framco motor with gear box	1 push to start switch
1 manual reversing & on/off switch	2 limit stop switches
£19.50 plus postage £2.50	1 circuit diag. of connections

J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS; Cash, P.O. or cheque with order. Orders under £20 add £1 service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted day or night. Haywards Heath (0444) 454563. Bulk orders: phone for quote. Shop open 9.00 — 5.30, Mon to Fri, not Saturday.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95, without case, metal case - £2.95, adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

EXTRACTOR FANS — MAINS OPERATED

Woods extractor.
5" — £5.75, Post £1.25.
6" — £6.95, Post £1.25.
5" Planair extractor
£6.50, Post £1.25.
4" x 4" Muffin 115v.
£4.50, 230v.
£5.75, Post 75p.

All the above ex-computer, those below are unused.
4" x 4" £8.50, Post 75p.
9" American made
£11.50, post £2.00.
Tangential Blower 10x3
air outlet, dual speed
£4.60, Post £1.50.



TANGENTIAL BLOW HEATER

by British Solartron, as used in best blow heaters.
3Kw £6.95 complete with 'cold' half and 'full' heat switch, safety cut out and connection diagram.



Please add post £1.50 for 1 or 3 for £2
Still available: £4.95 + £1.50 post. or have 3 for £16 post paid

ROCKER SWITCHES Standard size fit 11.5 x 28 mm cut out. Single pole on/off — 15p each 1000 for £75. Single pole changeover 20p each — 1000 for £100. Single pole changeover with centre off — 25p each — 1000 for £125. Single pole on/off with neon — 36p — 1000 for £180.

ROCKER SWITCH DP/DT 15 amp 250 volts suitable for motor reversing etc. — 46p — 100 for £34.50, 1000 for £230.

MICRO SWITCHES V3 type all 250 10 amp SpSt 20p 1000 — £100 SpSt 30p 1000 — £150, very low tongue Spdt 40p 1000 for £200.

THE AMSTRAD STEREO TUNER

This ready assembled unit is the ideal tuner for a music centre or an amplifier. It can also be quickly made into a personal stereo radio — easy to carry about and which will give you superb reception.

Other uses are as a "get you to sleep radio", you could even take it with you to use in the lounge when the rest of the family want to view programmes in which you are not interested. You can listen to some music instead.

Some of the features are: long wave band 115 — 170 KHz, medium wave band 525 — 1650 KHz. FM band 87 — 108 MHz, mono, stereo & AFC switchable, fully assembled and fully adjusted. Full wiring up data showing you how to connect to amplifier or headphones and details of suitable FM aerial. Inert ferrite rod aerial is included for medium and long wave bands. All made up on your compact board

Offered at a fraction of its cost: only £5.75 + £1.50 post + insurance



MINIATURE WAFER SWITCHES

2 pole, 2 way — 4 pole, 2 way — 3 pole, 3 way — 4 pole, 3 way — 2 pole, 4 way — 3 pole, 4 way — 2 pole, 6 way — 1 pole, 12 way, All at 25p each or 10 for £2.00

12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/2" spindle —
1/10 hp £3.45
1/8 hp £5.75 1/6 hp £7.50



MAINS MOTORS

We have very large stocks of motors from 2 watts to 1/2 hp. Most at a price well below cost, let us know your requirements

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — a complete mains operated kit, case included.

£11.95 plus £2.00 post.

OTHER POPULAR PROJECTS

- | | |
|---|--------|
| R C Bridge Kit | £9.95 |
| 3 Channel Sound to Light — with fully prepared metal case | £14.95 |
| Big Ear, listen through walls | £9.50 |
| Silent sentinel Ultra Sonic Transmitter and receiver | £9.50 |
| Car Light 'left on' alarm | £3.50 |
| Secret switch — fools friends and enemies alike | £1.95 |
| 3 — 30v Variable Power Supply | £13.80 |
| 2 Short & Medium wave Crystal Radio | £3.99 |
| 3v to 16v Mains Power Supply Kit | £1.95 |
| Radio stethoscope — fault finding aid | £4.80 |
| Mug stop — emits piercing squawk | £2.50 |
| Morse Trainer — complete with key | £2.99 |
| Drill control kit | £3.95 |
| Interrupted beam kit | £2.50 |
| Transmitter surveillance kit | £2.30 |
| Radio Mike | £6.90 |
| F M receiver kit — for surveillance or normal F M | £3.50 |
| Insulation Tester — electronic megger | £7.95 |
| Battery shaver or fluorescent from 12v | £6.90 |
| Matchbox Radio — receives Medium Wave | £2.95 |
| 40 watt amp — hi-fi 20Hz — 20KHz | £9.50 |
| 115 Watt Amplifier 5Hz 25KHz | £13.50 |
| Power supply for 115 watt amps | £8.50 |

CONSUMER ELECTRONICS

SHOW *Chicago...*

*Rik Hooper takes a look behind the scenes
at one of America's foremost exhibitions.*



THE 1985 International Summer Consumer Electronics Show, held in Chicago from 2-5 June was the most heavily attended event in CES history. The summer show, like its winter counterpart in Las Vegas, is sponsored, produced and managed by the Electronic Industries Association's Consumer Electronics Group.

Over 1,300 exhibitors occupied more than 750,000 net square feet of floor space at McCormick Place, McCormick West, and the McCormick Center, Americana Congress and Blackstone Hotels. Exhibiting companies represented the full range of electronic categories; including audio equipment; video hardware, blank tape and prerecorded video; personal computer hardware and software for the home; telephones; satellite earth stations; accessories, and personal electronics items such as calculators and watches.

Attendance at the show was around 115,000 which eclipsed the 98,271 recorded last summer. Approximately two-thirds of these visitors were retailers who visited the giant exhibition to view the latest available technology, and make buying commitments for the remainder of the year.

PERSONAL CHOICE

As with past Consumer Electronics Shows, the computer companies were launching their latest products into the marketplace, and in particular computers for the 128K market.

On the opening day of the show Amstrad Consumer Electronics introduced its new 128K personal computer, which Chairman Alan Sugar predicted "will revitalise the home/office segment of the lagging personal computer market in the US, by offering true PC power and capability at a price the public can afford.

"Amstrad's CPC6128 has all the power of an Apple II, at as little as half the price," asserted Sugar, who was named as 1984 "Young Businessman of the Year" in the UK.

"Considering its power and low price, the CPC6128 fills a unique niche. It is the first personal computer with the capabilities for business, home, educational and entertainment use, at a price that makes sense to the consumer."

Amstrad brought out its first computer, the CPC464 in June 1984. Some 200,000 of these 64K machines were sold worldwide by

the year's end, paving the way for the CPC664 introduced last April, and the powerful new 128K model. According to Amstrad US, the 128K model will be released into the UK market in the early part of next year.

The CPC6128 comes in two package configurations. Both include 128K RAM memory, CP/M and AMDOS operating systems, Basic and Logo operating languages, a built-in 3-inch disc drive, and a bundled monitor—one system includes a high resolution 640 x 200 full colour RGB monitor, operating software, Amstrad's word processor, and entertainment software. The alternative system includes an 80-column monochrome green monitor with operating software and Wordstar word processor.

Commodore International displayed its full range of computer products and services now being marketed in dozens of countries around the globe. Commodore Business Machines, the US company, was showing the Commodore 128 personal computer, which it began shipping at the end of last month (July).

The 128 PC is a sophisticated system forecast to sell at £260. In addition, the 128 is fully compatible with peripherals and software

- ① *The Model Ku/C-6000 ten channel satellite receiver from Panasonic.*
- ② *The Sony WatchCam home security monitor system.*
- ③ *The new Amstrad CPC6128 128K personal computer, with built-in disc drive.*
- ④ *Latest audio/video amplifier, SA-V1160, and digital synthesiser audio/video receiver SX-V500, from Pioneer.*
- ⑤ *The Fisher ICS713S features a dual cassette deck and five band equaliser.*
- ⑥ *The 128K Commodore 128 PC is expandable to 512K and is shown here with separate disc drive, colour monitor and two-button mouse.*
- ⑦ *Home video system from Polaroid uses 8mm Super-color video cassettes.*



①



②



③



④



⑥



⑤

⑦



⑧



developed for the top selling Commodore 64, which is now owned by more than 4.5 million people worldwide.

The 128 PC incorporates two microprocessors, allowing it to run software in the 64 and 128K modes, in addition to the many programs written in CP/M language. This capability combined with 128's memory, expandable to 512K, allows the user to generate integrated business programs.

The contemporary styling of the Commodore 128 features a 92-key typewriter keyboard with a 14-key numeric pad for fast accurate number crunching. For added user friendliness, the 128 offers eight programmable function keys, six individual cursor keys for graphics and text manipulation, and a 'help' key that lists programming errors in reverse field.

AUDIO/VIDEO ROUND-UP

There was a strong showing by the audio/video manufacturers—spearheaded by Pioneer which introduced more than 60 new products. "This is by far the most exciting year ever for Pioneer," explained Jack Doyle, Pioneer's Chairman of the Board. "The scope and range of our new offerings demonstrate our commitment to providing the consumer with high-quality, high-value products that reflect the real needs of people today".

Two integrated amplifiers were unveiled by Pioneer, the high-end SA-V1160 and SA-960, rated at 100 and 70 watts per channel, respectively. The SA-V1160 is a Type 11, non-switching, low distortion amplifier featuring Pioneer's dynamic power supply. It has two video inputs, video dubbing capability, two r.f. inputs/outputs, two tape monitors and what is claimed to be a unique dynamic expansion circuit.

Matching the amplifiers are two new digital tuners, the state-of-the-art TX-V1160 featuring a m., f.m., and TV tuning sections. It offers 24 a.m./f.m. and 12 station presets, multichannel TV sound, separate audio program and remote control capability.

Reinforcing its leadership position in the compact disc revolution, Pioneer introduced four new players, three of which offer wireless remote control. Heading the line-up is the PD-5010, which incorporates Pioneer's linear servo system for error free tracking, 27-track programmability, 2-speed audible scanning and track search.

Fisher, the Californian audio equipment manufacturer presented a totally re-styled integrated component system line-up. Three models make-up the new line, the ICS-705, 713 and 735.

The ICS-705 features an a.m./f.m. stereo tuner, 3-band equaliser, turntable, cassette player/recorder and shelf size speakers. The ICS-713 adds a dual cassette deck with Dolby noise reduction, and a 5-band equaliser. The ICS-735 features a 15 watt per channel amplifier, a dual-deck with synchronous dubbing, sequential play, auto search function and Dolby. The Quartz PLL digital synthesiser tuner offers eight a.m./f.m. presets.

Toshiba America presented a complete range of electronic consumer goods including 12 new format colour television sets, a wide variety of hi-fi systems, compact disc players, radios, tape recorders, telephone answering machines, programmable coffee makers, and microwave ovens with numerous cooking features.

The company's main exhibit was the M-5400 VHS format video cassette recorder. This model, uses Toshiba's own integrated-circuit chips, is a 117-channel cable compatible VCR with four heads, 16-function wireless remote control and four event/seven day programmable timer.

Polaroid announced a Supercolor high grade hi-fi video cassette, formulated for optimal video and audio reproduction. Manufactured to strict specifications, the new tape meets the high standards required for true high-fidelity audio, recording and playback.

SATELLITE LAUNCHES

The satellite companies, once again, gave a strong showing of their products, with dish antennas mounted outside the main exhibition hall. At least 40 earth station manufacturers attended the

show, including the more well known companies such as Houston Satellite Systems, Interstat, Luxor, Panasonic and Uniden.

The Panasonic Industrial Company, a leading supplier of advanced electronics to the business and industrial marketplace, introduced a satellite receiver capable of receiving both Ku-band and C-band signals. The rugged Ku/C-band has ten channel capacity and features front panel push buttons for instant selection of channels.

Houston Satellite Systems introduced the Tracker System V—an antenna positioner that features u.h.f. wireless remote control and a Z-80 microprocessor system that memorizes satellite position, skew, and polarization. The user never has to manually change polarity when selecting various channels or moving from one satellite to another.

Channel selection is virtually instantaneous, and is performed by simply pressing the desired numbers or stepping up/down through the stations. The positioner has selective channel and satellite lockout capabilities where one may designate which channels can be viewed on any and all satellites. A particularly interesting feature is the satellite scan mode to rapidly move to the next programmed satellite without specifying the satellite name, and also a channel scan mode for initial system programming.

SHOW STOPPERS

Once again Sony Consumer Products Company produced the more novel and exciting products including Sony's first digital Trinitron XBR monitor receiver incorporating a digital memory which Sony calls the Home Management Helper System; and the Mini-8 ultra compact camcorder—the size of a paperback book—which promises to open up a whole new world to amateur movie makers with easy operation and two-hour recording capabilities.

Polaroid demonstrated their latest 8mm home video system including a lightweight, easy-to-operate, video camcorder, playback deck and pocket-sized 8mm video cassettes capable of 90 minutes or recording and playback on a home TV set.

The user simply inserts a Polaroid Supercolor 8mm video cassette in the camcorder (a combined camera and video recorder), tapes the action, then "docks" the camcorder in the playback machine for instant replay.

Probably one of the most original of all the products on display was the Sony WatchCam—a home security monitor system utilising the four-inch black and white flat picture tube of its popular Watchman personal TV series. In addition to a four-inch monitor, the system includes an ultra-compact B/W surveillance camera, a camera mount for easy installation in a standard door peephole, and a 67-foot connector cable.

The camera incorporates an ultra-sensitive saticon pickup tube capable of reproducing images in lowlight conditions. Weighing only six-ounces, it can easily be mounted on any standard door peephole to allow the user to see a visitor by simply switching on the monitor.

ISSUES AND ANSWERS

More than 150 of the year's most innovative products—selected by a panel of consumer electronics editors—were on display at the 10th annual *CES Design & Engineering Exhibition*, which was held on the Lobby level of McCormick Place. The products were judged on the basis of engineering and design superiority, and were selected from a field of more than 400 entries.

Over 35 hours of information conferences and workshop sessions were offered in four major product categories; video, audio, computer, and telephones and telecommunications. Each product category featured a focal conference called "Issues and Answers"; specialised, practical workshops; and informative business and retail operations seminars.

All conferences were videotaped and shown on large-screen TVs via "CES TV News", daily throughout the show and via cable in 15 major hotels. □

OCTOBER FEATURES...

**NEW
SIZE**

Understand Electronics **TEACH IN '86**

A new series in nine parts, designed to give a comprehensive background to modern electronics. The emphasis is on the *practical* rather than the theoretical. Many interesting exercises will be dealt with, giving the participant an excellent grounding in all aspects of our field, with the minimum of soldering. This course—with optional software—will be of interest to the complete newcomer as well as to those with some previous experience. A useful related project will also be featured every month (below).



PROJECT 1

Safe Power Supply Unit

This is a +9V/-9V d.c. unit designed for use with the *Teach-In '86* series (see above). It is the first of nine related projects, each relevant to that month's Teach-In notes. This unit is not essential for Teach-In participants (batteries can be used) but it will nevertheless always be a useful tool in its own right.

Soldering Buyer's Guide

Soldering is a vastly underrated business in the world of the electronics enthusiast, and its true importance cannot be too highly stressed. It is in reality a simple task 'when you know how' and the combination of a good soldering iron and capable hands will minimise dry joint problems and ensure a much higher rate of 'first time working projects'. This guide shows you how—it also features a wide range of currently available irons and equipment.

EVERYDAY
ELECTRONICS
and computer PROJECTS

OCTOBER 1985 ISSUE ON SALE FRIDAY, SEPTEMBER 20

ORDER YOUR COPY NOW—SEE PAGE 506

PERSONAL STEREO PSU

T.R.de Vaux Balbirnie



PERSONAL stereo systems may be seen everywhere—in streets, parks, buses and trains. Young people use them for pop music. Others play learning tapes—to help with a foreign language, for example. Since they use headphones rather than a loud-speaker, they are truly personal and do not disturb others who may not share the listener's tastes.

HOME USE

Personal stereos have sufficiently high quality to enjoy at home but prolonged use soon runs down the batteries. This project is a miniature mains power unit specially designed for these radios and cassette players—operating cost are then negligible. It seems that most models use either two or four AA type batteries for 3V or 6V operation. This unit will deliver up to 130mA at either voltage. This is sufficient for radios and most cassette players. The current requirement is sometimes overstated in the instructions so, if necessary, check with a multimeter. Be sure to fit new batteries before doing this. If more than 130mA is needed don't despair—read on! Check also that the equipment is fitted with a d.c. input socket of known polarity.

The output voltage is internally preset by a single resistor which may easily be replaced should the need for the alternative voltage arise. Although there are some mains connections to make, anyone competent with a soldering iron should, with care, be able to make a safe job.


CIRCUIT DESCRIPTION

The circuit for the Personal Stereo Power Unit is shown in Fig. 1. T1 is a transformer which reduces the mains input to a suitable low working voltage. Diodes D1 to D4 are connected as a full-wave rectifier and the resulting d.c. is smoothed by C1 and regulated by IC1. The output voltage is deter-

mined by R1 and R2. In this circuit, R2 is fixed in value and R1 chosen to provide the correct output—in fact, the voltages are made slightly low as a safety precaution. FS1 is a fuse in the positive output lead and LP1 is a neon (mains-on) indicator.

strips and connect the single link wire as indicated. Follow with soldered on-board components. When mounting R1, keep it clear of the circuit panel so that it is more easily replaced should the need arise.

Attach the Veropin for mains earth con-

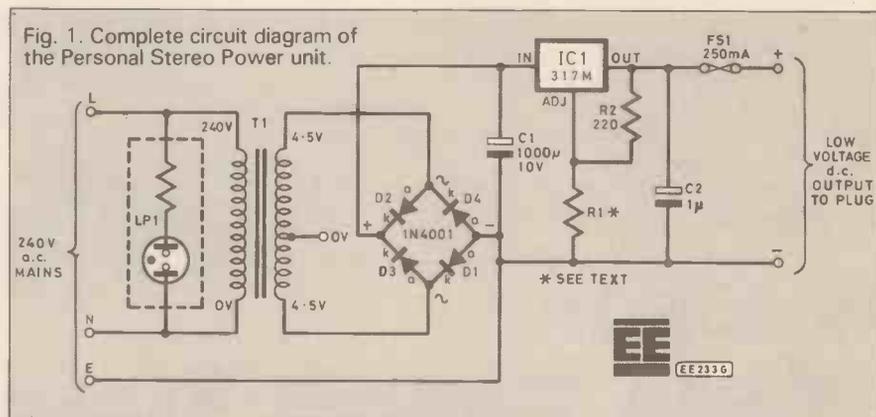

CONSTRUCTION

Refer to Fig. 2 and Fig. 3 for details of the circuit panel. This is based on a piece of 0.1in. matrix stripboard, 13 strips by 29 holes. The panel should be cut slightly large then filed to fit the runners of the plastic box securely. Make the breaks in the copper

nection. Note that with the circuit panel in position in the case, T1 rests on the base. Make a careful check on the double row of broken copper strips between the primary and secondary connections to T1. These must be broken completely to isolate the mains from the low-voltage section. Make a heat sink for IC1 using thin sheet alumin-

COMPONENTS

Resistors

R1* 270 for 3V output
820 for 6V output
R2 220
All resistors 0.4W ± 1%

Capacitors

C1 1000µ 10V electrolytic
C2 1µ 100V electrolytic

Semiconductors

D1-D4 1N4001 (4 off)
IC1 317M variable voltage regulator


Miscellaneous

Plastic box; 0.1in. matrix stripboard; 13 strips x 29 holes (for high-current circuit the board may be smaller); 20mm fuseholder and fuse; Veropin; 3A 3-way terminal block (for high-current only); solder tag (high current only); Small panel-mounting mains neon indicator; heatsink; 4.5-0-4.5V fully-encapsulated p.c.b. mounting mains transformer (R.S. stock no: 207-863).

* see text

See
**Shop
Talk**
page 477

Approx. cost
Guidance only **£9**

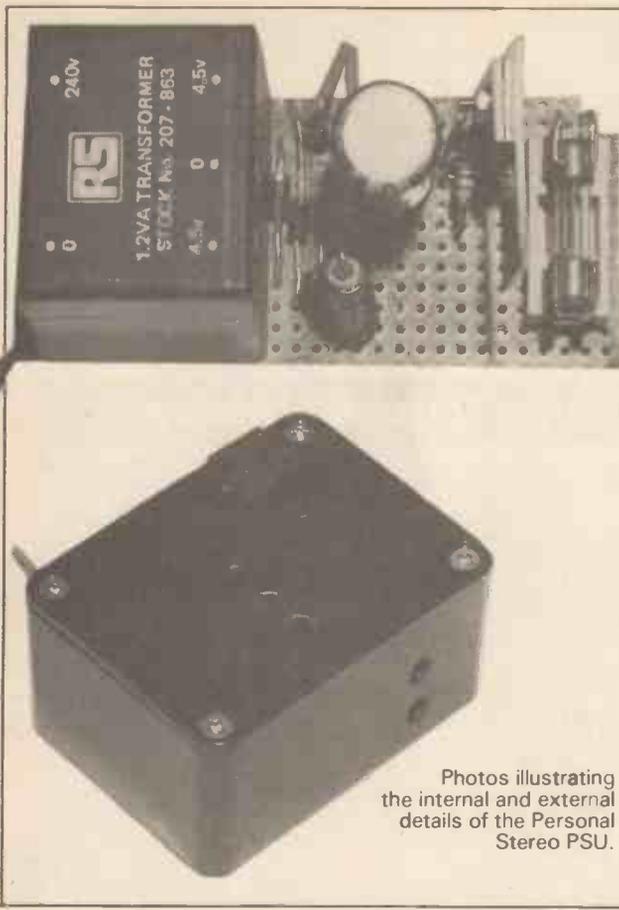

Photos illustrating the internal and external details of the Personal Stereo PSU.

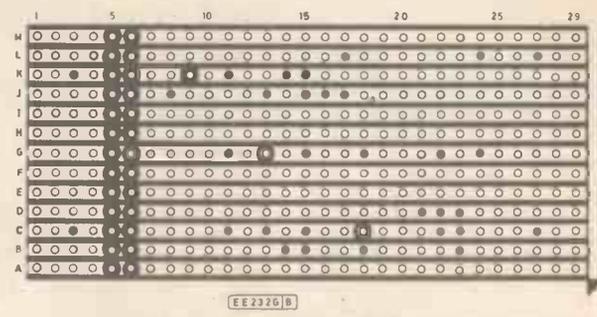


Fig. 2. Details of the stripboard layout including track cutting details.

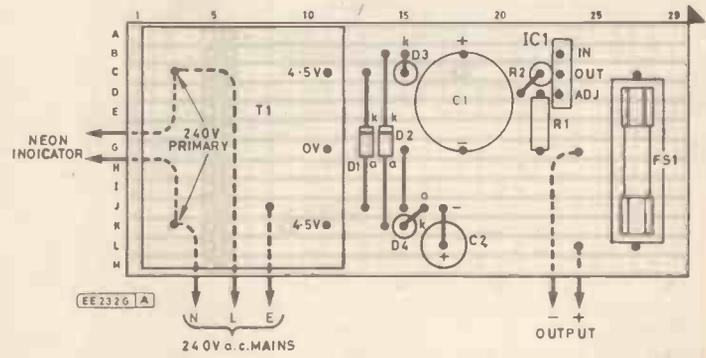


Fig. 3. Component layout of the Personal Stereo PSU.

ium, size 32 x 16mm. Drill a small hole in the corner and attach it to the i.c. noting that with the circuit panel in position, the heat sink rests in one of the slots in the box.

If currents in excess of 130mA are required then some modification to the above instructions is needed. Obtain an uprated chassis-mounting transformer appropriate to the current loading. This will determine the size of the case required. Construct the circuit panel from hole 10 onwards omitting the on-board transformer (Fig. 4.) Note that IC1 is suitable for loads up to 500mA.

PREPARING THE CASE

Begin by drilling the holes in the rear for the mains and low-voltage output leads. Drill the ventilation holes near T1 and a hole for LPI as shown in the photograph. The position of the latter is critical and care must be taken to ensure that LPI connections cannot touch the copper strips of the circuit panel. Use an insulating sleeve for added protection.

Measure pieces of 3A 3-core mains wire and light-duty twin wire for the output. Connect them to the underside of the circuit panel as indicated in Fig. 3. Connect the neon indicator. Fit both leads with strain relief bushes inside the case so that they cannot break free from the panel should they be pulled accidentally. Fit self-adhesive feet to the case, insert the fuse and attach the lid.

For the higher current circuit, mount T1 and the 3-way terminal block on the base of

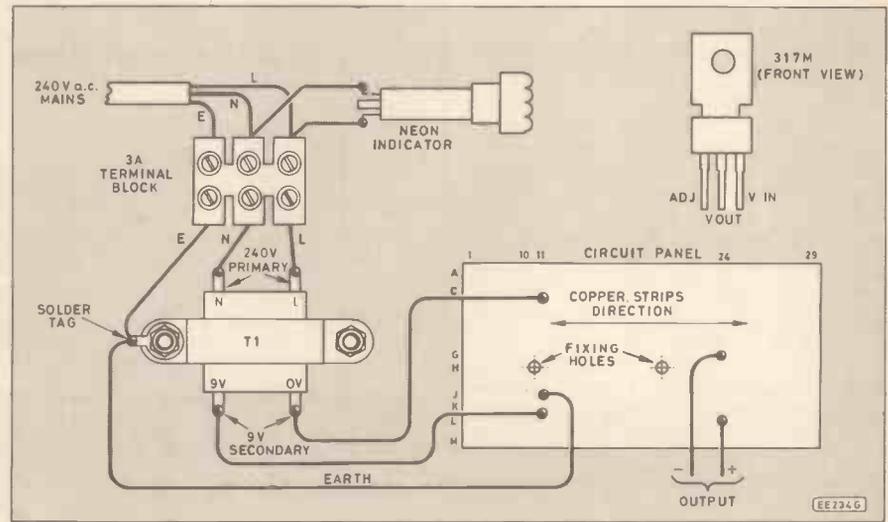


Fig. 4. Alternative transformer wiring details for the Personal Stereo PSU. The same stripboard is used.

the box. Include a solder tag beneath one T1 fixing. Mount the circuit panel nearby using two small fixings in strip H. Place small plastic stand-off insulators on the bolt shanks to hold the panel clear of the base of the box. Refer to Fig. 4 and complete the wiring. Note the mains earth connection to the T1 solder tag and from there to the negative supply line at the circuit panel. Double the area (at least) of the heat sink on the regulator, IC1.

TESTING

Attach the correct type of plug to the output lead making certain that the polarity has been correctly observed—interchanging positive and negative connections may damage the equipment. Fit the mains plug with a 3A fuse. Note that it is normal for T1 and IC1 to become quite hot in use and the case will therefore become warm in prolonged operation. □

FINTRONICS ON AERIALS



PROF


We've produced electric energy but how do we transmit it from its source to its user? Well, we can use this method for one



TRANSMISSION LINE

The transmission line is a high frequency signal to understand how it varies from its input and phase. To understand how to consider the cable to consist of Resistor, inductor, and capacitor the transmission line as shown.

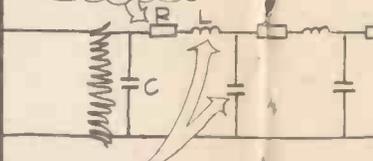The effect of the resistor is to AMPLITUDE (The amount of attenuation)




The effect of L&C is to shift the

In short the transmission line represents incoming signals, the value of which as well as length of cable.

(NB) At RADIO FREQUENCY a transmission line acts as a RESONANT CIRCUIT

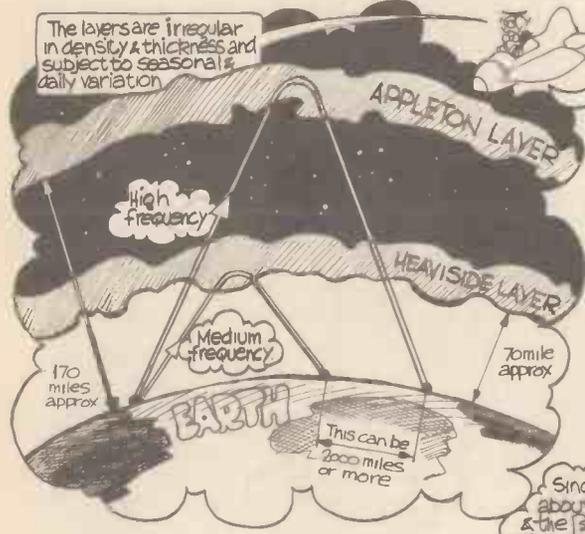The layers are irregular in density & thickness and subject to seasonal & daily variation



Let's take a much closer look At the IONIZED layers, yes, there's actually two, the APPLETON and KENNELLY-HEAVISIDE LAYER.


The electro-magnetic radiation consists of two parts - the GROUND WAVE and SKY WAVE. The GROUND WAVE (low frequency) tends to follow the earth's curvature to an extent. The Sky wave reaches the ionized layers. The effect of these depends, of course, upon the angle at which the wave meets and on its frequency.

WAVE

Since the layers are about 70 to 170 miles high & the gap is 8k dia, all sketches are NOT TO SCALE.

TRANSISTOR TEASER

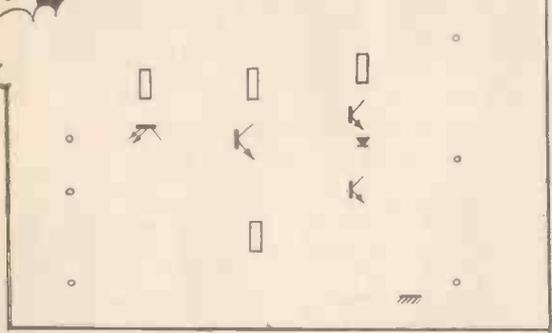Join up the components below to form a familiar circuit




Solutions on page 513



"Strange, we received your signals"

UNIDIRECTIONAL AERIALS

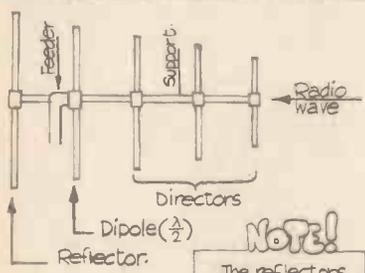


Transmission and reception are improved when 'director' and reflectors are added to the dipole. For transmitting aerials they have the effect of concentrating the radiation in one direction. For receiving aerials they have the effect of concentrating the strength of the received signal.

The function of the directors is very simple, they direct the radiation in the vicinity of the dipole and the function of the reflector is to reflect radio waves back to the dipole.

NOTE!

The reflectors and directors are not electrically connected to the dipole.

the LOADED AERIAL

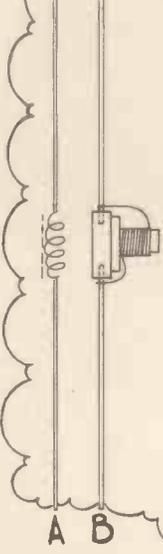


To match an aerial to a I.F. wave length particularly in a portable situation becomes impractical. Shorter aerials can be used by increasing the electrical length of the aerial by loading with a coil.

The coil in 'A' would double the field strength reading of say a 1 metre long aerial.

Sketch 'B' shows how this coil would be fitted. The coil would have about 30 turns of 28SWG enamelled wire on a 7mm dia former.

HALF WAVELENGTH DIPOLE

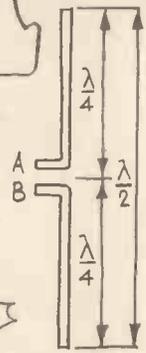The principle operation of a receiving aerial is that of a conductor. If the conductor (ie aerial) is placed in the path of electromagnetic radiation current is induced in the conductor.



For maximum radiated and received energy, the aerial has to be a optimum length, equal to half the wave length of the signal.

A & B connections are for the transmitter or receiver.


There is a very simple formula used to arrive at the optimum length.

$$\lambda = \frac{c}{f}$$

λ = wavelength
 c = speed of light
 f = frequency


transmission line in the form of cable is used to carry signals. Now, it's very important that its output signal is in both amplitude and phase. This comes about because we must use a very large number of capacitors distributed along the line below.

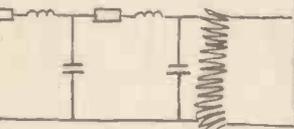to attenuate the signal (attenuation is the same regardless of frequency)



the phase at h.f. only presents an IMPEDANCE to which depends on frequency

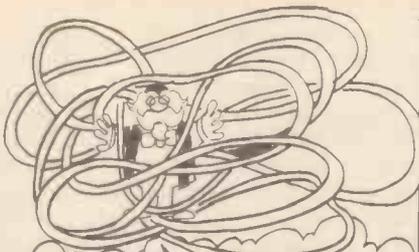transmission line may be used in a circuit




Let's consider a transmission line of infinite length. Looking at the transmitting end the line represents an impedance known as the characteristic impedance Z_0 . The value of Z_0 depends on the size of the conductor, the spacing, and insulation between live and earth.



But of course a transmission line cannot be of infinite length so let's look at the real world

TRANSMITTER

RECEIVER

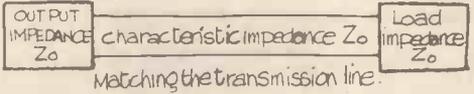


Let's consider a short line terminated by an impedance other than the characteristic impedance

The energy absorbed by the load (receiver) will be low because some energy is reflected by the terminating impedance and a **STANDING WAVE** is formed along the line. However, if we terminate the line with its characteristic impedance Z_0 , the transmitting energy wave sees an infinitely long line and reflection ceases. All the energy is thus absorbed by the load and the energy or power is transferred from the transmitter to load at a maximum. This is known as **MATCHING THE TRANSMISSION LINE**.



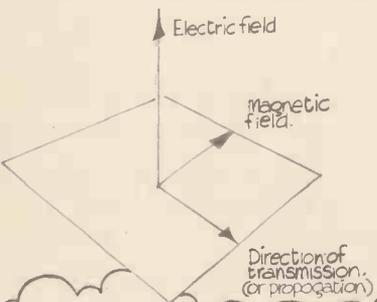You may be wondering what transmission lines have to do with **AERIALS** well not much but it's worth covering this method of transmitting a signal. As you will see both methods have their advantages & disadvantages



A vertical aerial creates a VERTICAL electric field and the radiation is said to be vertically polarised.

The electric field is at right angles to the magnetic field with the direction of propagation at right angles to both.

2-WORD LINK-UP

START	N	C		
↓	E	H		
I	Q	U	I	
T	S	G	N	
T	P	A		
E	H	G		

Make a chain of 2-words related to **ELECTRONICS** by joining the above letters

FUNDAMENTAL FACTS




Because the ionized layers are produced by the Sun's action, they are influenced by its seasonal movements and by daylight and dark produced by the earth's rotation. This causes seasonal and daily variations in density and height of the layers which means the radio engineer has to change the frequency of his transmitter and receiver twice daily to allow for the changes



"Alright, who told our new operator he had to physically follow the ionosphere?"

AERIAL POSITIONS

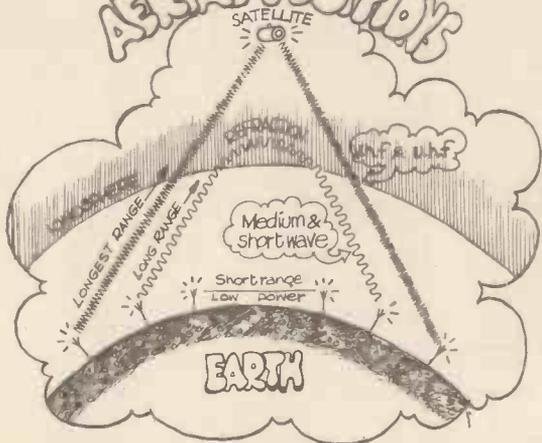

"FANTASTIC PICTURE! THAT LAST BIT OF FINE TUNING DID THE TRICK!"

by
Thakery

ON SPEC

a regular feature for the Spectrum Owner...

by Mike Tooley BA

THE QUESTION most often asked by readers of this column is: "Where can I get further information on Spectrum hardware and interfacing?" I shall, therefore, start this month's instalment of *On Spec* with a short "Recommended Reading List" for Spectrum hardware enthusiasts. The list is not exhaustive, being merely confined to those books which I have personally found useful.

Useful Reading

Almost certainly the cheapest of all publications covering Spectrum interfacing is Owen Bishop's "Easy Add-on Projects for Spectrum. ZX81 & Ace" (Pub. Bernard Babani ISBN 0-85934-099-6). This very modestly priced book describes a number of simple and often ingenious projects which are designed to operate in conjunction with a simple address-decoder module. This latter device can be put together from readily available components or can be purchased in kit form from Kelan Engineering (see August *EE*).

The "Spectrum Hardware Manual" by Adrian Dickens (Pub. Melbourne House, ISBN 0-86161-1115-2) describes the internal operation of the Spectrum and is liberally illustrated with useful photographs. It does, however, only cover Issues 1 and 2 of the Spectrum (there can't be very many Issue 1 Spectrums still going, can there?).

Several interface projects are described and these include a breadboard system (the photograph of this needs to be seen to be believed!), a reset switch, adding a Z80 PIO, a joystick/keyboard interface, and an eight channel analogue-to-digital converter. There is also a hand-drawn circuit diagram

of an Issue 2 Spectrum which, unfortunately, contains several errors!

Graham Bishop's "Spectrum Interfacing and Projects" (Pub. McGraw-Hill, ISBN 0-07-084702-9) contains a number of well-thought-out projects and interface designs, including analogue-to-digital and digital-to-analogue converters. The book also contains some fairly basic information on the Spectrum hardware configuration together with a brief introduction to machine code.

The "ZX Spectrum User's Handbook" by R. J. Simpson and T. J. Terrell (Pub. Newnes Microcomputer Books, ISBN 0-408-01323-0) deals with both hardware and software. The chapters on hardware and programming in machine code are particularly useful. A simple one-byte memory-mapped I/O interface is described but no constructional details are provided. This book is very comprehensive and contains all of the information that most Spectrum owners will ever require.

Now on to the project, which this month is a simple DAC, based on a standard and widely-available converter chip.

Digital-To-Analogue Converter

In simple control applications one often needs to provide an analogue, rather than digital, output. Whilst this can be achieved by networks of discrete "binary weighted" resistors (see Fig. 1) or by an R-2R ladder-network (see Fig. 2), several semiconductor manufacturers have come to our aid with

integrated circuits which will accept a digitally encoded input and provide a corresponding analogue output. Such devices contain the precision resistors matched to an accuracy which would be impossible to achieve using discrete component technology.

The complete circuit diagram of the digital-to-analogue converter is shown in Fig. 3. The circuit is based on the popular Ferranti ZN428E. This device is a monolithic 8-bit digital-to-analogue converter i.e. which uses an "R-2R" network and contains an 8-bit data input latch to facilitate byte up-dating from an 8-bit data bus. The chip also contains its own internal 2.5V reference.

Address decoding is provided by IC3. This provides a logic 0 output whenever all eight address lines go high (corresponding to a decimal address of 255). The output of IC3 is gated with \overline{IORQ} and \overline{WR} lines within IC4a and then inverted by IC4b in order to provide an active-low enable signal which allows data to be latched into IC1.

Depending upon other external hardware fitted, some readers may wish to change the port address. This can be achieved quite easily using the unused gate, IC4c. As an example, Fig. 4 shows the modification required for changing the port address to 191 decimal (i.e. avoiding the use of address line A6).

The analogue output appearing at pin 5 of IC1 is passed to an adjustable gain non-inverting buffer formed by the operational

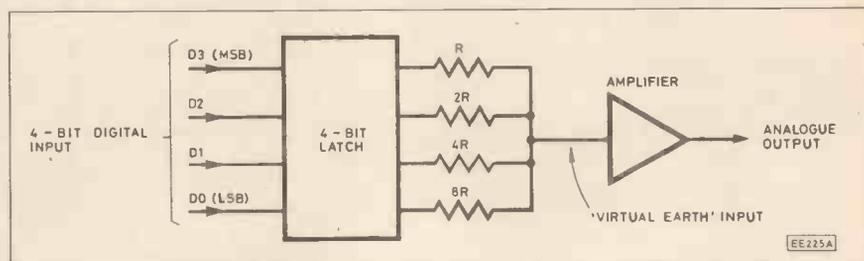


Fig. 1. Binary-weighted resistor network for D-to-A conversion.

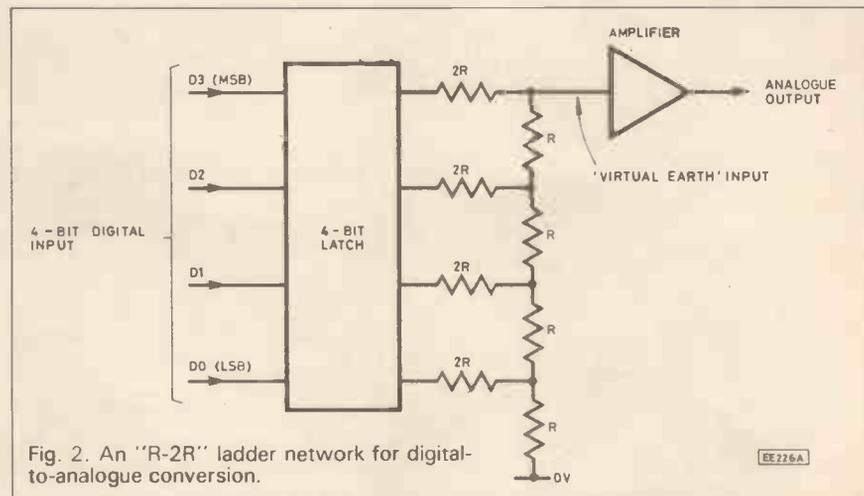


Fig. 2. An "R-2R" ladder network for digital-to-analogue conversion.

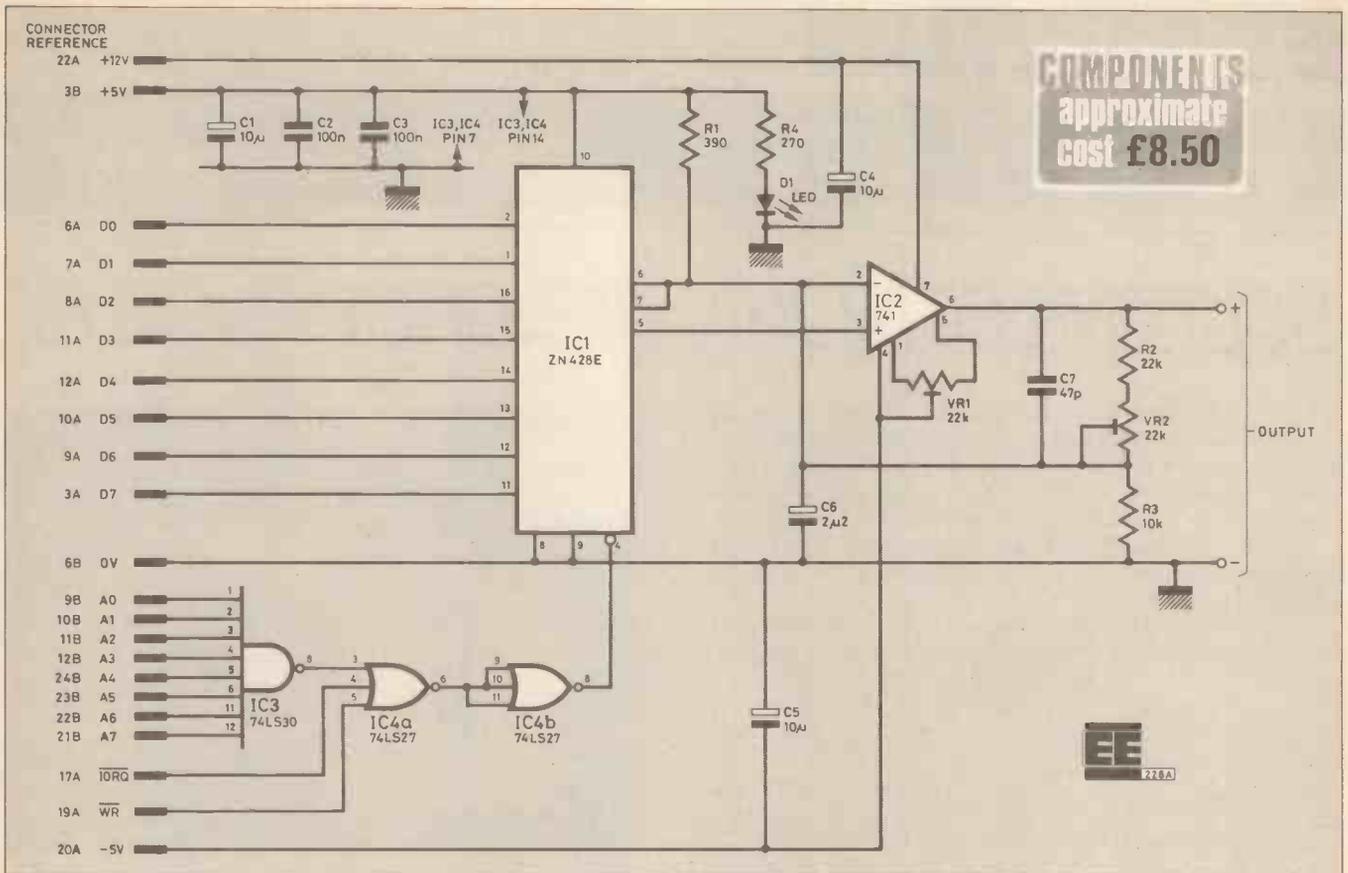


Fig. 3. Complete circuit diagram for the converter, using address 255 decimal.

amplifier, IC2. This stage provides a relatively low-impedance output which is substantially linear over the range 0V to 10V.

Construction

The digital-to-analogue converter is assembled on a piece of Veroboard measuring approximately 80mm x 100mm. As with previous projects, the precise dimensions of the board are not critical; however, it must have a minimum of 28 tracks aligned in the vertical plane so that a 28-way double-sided edge connector can be mounted along the bottom edge of the board.

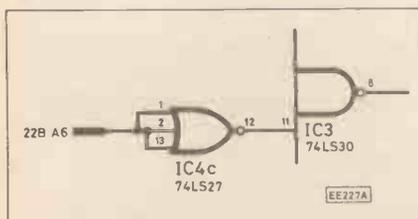


Fig. 4. Example of circuitry for decoding for port address 191 decimal.

This connector requires approximately five rows of holes across the full width of the stripboard and is arranged so that the board stands vertically when the connector is mated with the Spectrum.

Before soldering any of the components it is important to allow some clearance for the

rear "overhang" of the case. For the Spectrum this gap should correspond to 8 rows of holes (20mm approx.) whilst for the Spectrum Plus the gap should be increased to 12 rows of holes (30mm approx.).

Links on the underside of the board should make use of appropriate lengths of miniature insulated wire (of the type normally used for wire wrapping). Readers requiring further information on the connector should refer to *March On Spec* or send for our latest "Spectrum Up-Date".

When the stripboard wiring has been completed, the integrated circuits should be inserted into their sockets (taking care to ensure correct orientation) and the entire board should be carefully checked before connecting to the Spectrum. Note that the Spectrum should *always* be disconnected from its supply before either connecting or disconnecting any interface module. If all is well, when power is re-applied, the normal copyright message should appear. If not, disconnect the power, remove the interface and check again.

In October's *EE*, we shall deal with the DAC at greater length. In the meantime, please don't forget to let me have any comments for inclusion in *On Spec*.

NEXT MONTH: We shall deal with setting-up and practical applications of the converter, and some simple software for driving it.

COMPONENTS

Resistors

R1	390
R2	22k
R3	10k
R4	270
All	$\frac{1}{4}W \pm 5\%$

See
**Shop
Talk**

page 477

Potentiometers

VR1, VR2	22k (2 off)
----------	-------------

Capacitors

C1, C4, C5	10µ 16V electrolytic (3 off)
C2, C3	100n polyester (2 off)
C6	2µ2 25V tantalum bead
C7	47p ceramic

Semiconductors

D1	Red l.e.d.
IC1	ZN428E
IC2	741
IC3	74LS30
IC4	74LS27

Miscellaneous

14-pin d.i.l. sockets (2 off); 16-pin d.i.l. socket; 2-pin 2.54mm pitch p.c. mounting connector; 28-way open end double-sided 2.54mm pitch connector (e.g. Vero part number 838-24826A); 2.54mm hole pitch stripboard measuring approx. 80mm x 100mm (minimum 28 strips).

YOUNG ELECTRONIC DESIGNER AWARDS

THE final 37 aspiring young electronic designers, making up the teams in this year's *Young Electronic Designer Awards*, gathered anxiously in the Great Hall at the Westminster School, London (end of May), to see if all their hard work was to be rewarded with one of the top prizes.

This year the prize winners were announced by Miss Petula Clark and presented by His Royal Highness The Duke of Edinburgh.

The competition was divided into two age categories, senior (14 to 19) and junior (under 14). The prizes offered by the sponsors, Cirkit Holdings plc, were cash amounts of £500, £250, £100 and £50 in each age group. Also a special prize of a Texas Instruments Professional Computer was donated by Texas to the winning school in the senior section.

Of the original entries received the final was reduced to just eighteen projects divided across the two sections. Entries ranged from a "Granny" Buzzer to a Sequence Timer for Offshore Beacons and a Washday Alarm to a Interface Unit for the BBC Micro.



First place junior winner, Daniel Rodenhurst is pictured demonstrating his Egg Dipping Control Device project to HRH The Duke of Edinburgh, Miss Petula Clark, Alistair McDonald (3rd right) Chairman of Cirkit Holdings plc and Daniel's teacher Mr D. Morgan.

The judging panel for the grand finals was made up of the following: Professor John Eggleston, Chairman of the Department of Education, University of Warwick; Sir Robert Telford, President, The Marconi Co.; Sir Alec Morris, Divisional Executive—Equipment, British Aerospace Dynamics Group; Peter Van Cuylenburg, Managing Director, Texas Instruments Ltd.; Jonathan Burchell, Cirkit Holdings plc.

Final Results

After the opening ceremonies and speeches welcoming the distinguished guests, contestants, teachers and parents, the big



HRH The Duke of Edinburgh is pictured examining Jonathan Kempster's Audible Spirit Level which won first prize in the senior section of the Young Electronic Designer Awards competition.

moment arrived and the judges' final decisions were revealed.

WINNING DESIGNS

Senior

- 1st Ashcombe—£500
- 2nd Cavendish—£250
- 3rd Bishopshalt—£100
- 4th Bosworth College—£50

Junior

- 1st Maelor—£500
- 2nd Millfield High—£250
- 3rd Falmer High—£100
- 4th Bryn Offa—£50

The Audible Spirit Level, designed and built by Jonathan Kempster won the first prize of £500 in the senior section. His school Ashcombe School, Dorking are now the possessors of a Texas Professional Computer.

Second prize of £250 in this section was awarded to Paul Metcalf of the Cavendish School for his Pelican Crossing Model, a teaching aid for schools. An Infra-red Remote Control for use by the disabled to control equipment in the home won third prize of £100 for Russell Vowles of Bishopshalt School, Hillingdon.

Junior Winners

The £500 first prize in the junior section went to Daniel Rodenhurst of Maelor School, Wrexham for his Egg Dipping Device. Second prize (£250) was won by Paul Dunlow, Stephen Jenkins, Colin Knowles, Lee Taylor and Sean Taylor of Millfield High School, Cleveleys for their Caravan Reversing Aid. Third prize of £100 was awarded to Joanne Weeks, Angela Banfield and Rachel Sennett of Falmer High School, Brighton for their Washday Alarm.

All the participating finalists received consolation prizes of Texas TI-30 Galaxy Scientific calculators and packs of components.

First for TWA

First Computer has secured a major order for a combination of hardware, software and consultancy from the International division of TransWorld Airlines, one of the world's leading operators.

The order is to supply IBM XT business micro-computers for TWA's twelve international sites at major airport terminals in Europe, the Middle East and India. First Computer is also to provide a mix of "off the shelf" and custom written software. The systems will be used for TWA's personnel records, financial management and word processing needs at its international centres.

Mr Keith Riggs, TWA's Director of International Budgets and Controls said, "The factor that decided which company ultimately received the contract was the level of software development support that was available. First Computer are able to provide just the service TWA require."

Just the Ticket

Equipment to modernise fare and ticket collection procedures on London's underground is to be supplied and installed by Westinghouse Cubic under a contract worth £45 million awarded by London Underground Ltd. Westinghouse Cubic is the automatic fare collection and revenue systems specialist.

Passenger-operated ticket machines, booking office machinery and supervisory computers are to be supplied by the company, following the successful trials of new-style, passenger-operated ticket machines at Vauxhall station during 1983. The system will speed up ticket issue and reduce queueing by passengers. It will also provide the means of reducing the possibility of passenger fraud.

They will supply approximately 900 self-service ticket

machines of two types, which will issue new credit card-sized tickets including travelcards and season tickets. Coins of most denominations will be accepted by the machines and change will be given, while one machine type will also accept and give change from a £5 note.

Two types of machine are to be installed: "Few-fare" machines will be located at all but the quietest stations, issuing tickets to regular passengers aware of the correct fare to the ten most popular fare sectors from each station. "Multi-fare" machines will issue a complete range of tickets to all underground stations and selected BR stations by pressing a destination button.

Each station will have its own supervisory computer linked to the centralised computers at the Underground's control centre.

TOP GIRL

IF SHE did but know it, somewhere out there in industry is the 1985 Girl Technician of the Year busily getting on with her career in electrical or electronic engineering. The search is now on to find her.

Sponsored by The Caroline Haslett Memorial Trust and the Institution of Electronics Incorporated Engineers, *The Girl Technician Engineer of the Year Award* is intended to focus attention on electrical and electronic engineering as a worthwhile professional career for women. By selecting the most outstanding girl Technician Engineer it is hoped that she will, by her example, encourage more young girls to enter the electrical and electronic engineering profession.

Nominations for the 1985 Award, with its £250 prize, and for the newly announced Mary George Memorial Prize (£100), awarded to the most promising younger entrant, must be received by 8 October 1985.

For further details and copies of nomination forms, apply to: The Secretary, IEEIE, Dept EE, Savoy Hill House, Savoy Hill, London, WC2R 0BS.

The Radar Division of Thorn EMI Electronics has recently been awarded a £6M contract by the Ministry of Defence to develop and supply a colour display for the Searchwater ASW radars installed on RAF Nimrod MRS aircraft.

The new display is scheduled to enter service in 1987.

The Inland Revenue has ordered two performance and capacity management/modelling programs from BGS Systems for use in its computer centre at Worthing.

UNIVERSITY VENTURE

British Petroleum has committed £130,000 under its Venture Research ("Blue Skies") Programme to back the work of a three man team at Edinburgh University's Department of Computer Science. The expanding and unique Blue Skies Programme—currently running at £1.5 million per annum—exists to inject BP funding into challenging ideas drawn from across the whole range of experimental and theoretical research at universities and comparable institutions at home and abroad, in the belief that some of these could generate completely new types of industrial opportunity.


The £130,000 investment at Edinburgh goes to Professor Robin Milner and Dr Gordon Plotkin working in liaison with Professor Rod Burstall—all of the University's Department of Computer Science.

DESIGN SELECTION

CAMBRIDGE based TEK Marketing have just had two of their plug-in timer modules accepted by the Design Council for inclusion in the Design Centre Selection.

The TR31 is a precision electronic timeswitch which can be programmed for up to three on/off cycles during a 24 hour period. The T2R is a derivative of the T31 aimed exclusively at home security. It will switch a lamp or other appliance at random intervals during two user programmed periods.

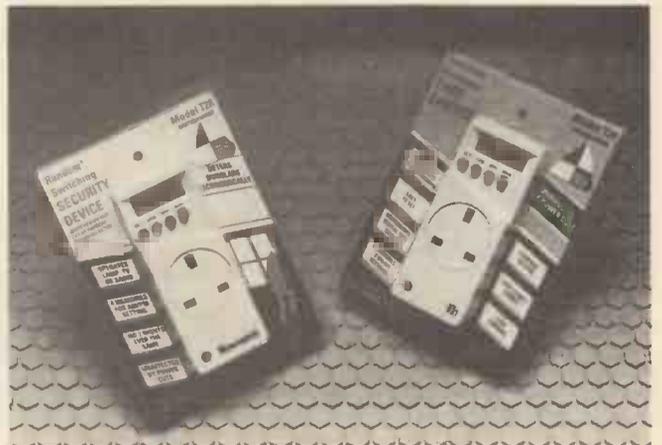Designed by TEK in 1983, it is claimed that they were the first products to enable the consumer to purchase a programmable electronic timeswitch, with battery back-up, suitable for plugging into a 13A mains socket.



FOR YOUR ENTERTAINMENT

BY BARRY FOX

No call for DIY

More and more shops are now selling DIY telephone wiring kits. You get some telephone wire, a standard BT socket and instructions on how to string it in parallel with an existing BT socket. Specialist shops, for instance in London's Edgware Road, sell the sockets on their own. Sometimes these have screw terminals, to make fitting easy.

Professional engineers don't like screws because they tend to work loose. They prefer friction-grip sockets which strip the insulation and bite into the metal as the wire is pushed in. The public can now buy the special tools needed to make a clean join with a friction socket.

Obviously, BT is not pleased about the sale of these sockets or kits: "They are not approved for connection to the public telephone network, only to a PBX private exchange. They should not be on sale to DIY installers.

"We don't approve of people adding extra sockets. The only thing we permit is the replacement of standard sockets with decorative ones. You can buy them, but they should still be installed by BT engineers."

With good reason, BT is getting worried. If DIY phone installers do not understand what they are doing, all kinds of odd things can happen. BT here is partly to blame. It has not publicized the technical pitfalls, so people just think BT is complaining out of commercial pique. Amateurs have a go at fitting by trial and error.

A recent booklet published by the government Office of Telecommunications, OFTEL, looked hopeful. It's entitled "Telecommunications Wiring in Business Premises and Homes." But it is only a run-down on the law and rules, written in the most awful civil service lingo. There is no technical meat. What the public needs is a booklet which spells out the electrical facts. It could well deter the bodgers who are worrying BT.

Electrically speaking, there is no limit on the number of sockets you can hang on a telephone line. The master socket contains a capacitor, but all the extension sockets are electrically inert.

Two wires (A,B) come into the house from the street. At the master socket a third wire, the bell wire, is added. The capacitor goes between the B wire and bell wire to let through the a.c. ringing signal, but block the d.c. speech and off-the-hook signalling current to the exchange.

There is an electrical limit on the number of phones you can plug in at any one time. It is the equivalent of four "standard" ringers or bells.

Every piece of authorised telephone equipment is marked with an REN, which is the Ringer Equivalent Number for the circuit. A ringer impedance of 4,000 ohms

has an REN of one or unity. If it has a lower impedance, and is current hungry, then its REN is higher than one. Unfortunately, the REN is often marked only on the box or booklet which few people read and most will throw away.

The theoretical limit for extension phones is 4 REN units. So you can safely connect four phones each with an REN of one. You could only connect three if they each had an REN of 1.33, and so on. Most phones now are unity, however. In practice, you can sometimes get away with a combination of phones that puts the REN at greater than 4, but don't rely on it.

Cross lines

Odd things can happen when you get over 4 REN. One phone may ring, but none of the rest. Or none of the phones may ring. Or they ring weakly. But the person calling hears a normal ringing tone.

The result can depend on the exchange. The ringing current originates locally, from your own exchange, but there may be several different ringing machines. City ringers may be better able to cope with odd loads, than rural systems.

Bear in mind, also, that although a computer modem does not put any impedance across the line (unless it is of the auto answer type) an answering machine has a REN just like a telephone. So plugging in or switching on an answering machine can upset the system balance.

Nightmare

As regular readers will know, I am certainly no computer buff. I have this quaint old-fashioned notion that computers should do a useful job, and save me time and money, not soak up time and money like a sponge while I learn to use them.

I have written about the miseries I suffered with the ACT Apricot, not because there is anything wrong with the machine, but because the instruction manuals (especially for the Xi hard disc version) are such a nightmare of jumbled jargon. After failing to stir the company into any real action through private correspondence I went into print and was immediately rewarded with a letter from a reader who said he was thrilled to find that he was not alone in being lost.

"The machine seems to have tremendous potential" he wrote "but there is little exaggeration in saying that the manuals explain nothing properly". He then threw up one of those nuggets of golden truth that describe a complicated situation in a few words. "The manuals are of the kind that you can only understand when you no longer need them."—I wish I'd thought of those words!

If you think we are exaggerating, try these simple tests. The Apricot Xi hard disc

Although approved phones all meet (or should meet) the 4,000 ohm REN specification, electronic phones with warble ringers may not have the same electrical characteristic as those with an electromechanical bell. Their impedance is a complicated mix of capacitance, inductance and resistance which gets even more complicated when several electronic phones are used in parallel.

It's just like hi-fi, where a loudspeaker rated at 8 ohms may well dip in impedance to only a couple of ohms when reproducing some music frequencies. This can upset an amplifier. Four electronic phones, each with an REN of one, may not ring reliably when all plugged in together, even though the REN total is on paper still only 4.

There can also be intermittent problems caused by dampness on the p.c.b.s inside the socket boxes. When the weather is wet, or the atmosphere humid, there may be tracking which lowers the d.c. isolation between the A and B wires. This can again stop the bells ringing.

For my money, the biggest single problem is lack of information. I know of no attempts by officialdom to explain the REN guidelines fully and in simple terms. The OFTEL booklet is a non-starter. BT feels unable to publish anything because it would be seen to encourage the DIY fitting which BT wants to stop.

If subscribers call out BT engineers and the trouble is a DIY socket, BT will disconnect it and charge £15 plus VAT for the visit. So people have an added incentive to bodge.

I checked a couple of phones recently (both approved) and neither had a clear REN marking. Under the circumstances, is it any wonder that people are running into technical troubles?

machine comes with all programs already stored on a Winchester. The instruction books tell you that you need to make safety backups. See if you can find where it tells you how to copy all the program tracks, and then the system tracks.

The Xi also offers path control so that it automatically searches out programs and files stored in sub directories. Try learning how to set a path from the instruction books. Also, try to create a simple command file, using Edlin. You would think, for instance, that it would make sense to start the description with the advice that you need to key "I" for insert, end with "E" for end and then "Q" for quit. You might think so, but you would be wrong.

Dixons and Tottenham Court Road shops are now selling Apricots at cut price alongside music centres and cameras. If you have a little spare time, try asking the sales staff about back-ups, Path and Edlin.

Every time I struggle with manuals like these I am left longing to get my hands on the man who wrote them so that I can shake him until he apologises for making simple logical things so infernally hard to comprehend. I also understand why the computer boom has crashed.

TRANSDUCERS

PART 1 GENERAL PRINCIPLES and TEMPERATURE MEASUREMENT... MIKE FEATHER BSc

WHAT is a transducer? Scientists and engineers are constantly involved with the task of measuring the sizes of physical quantities in the world around them. Common examples of such quantities might include temperature, pressure, or magnetic flux density.

GENERAL PRINCIPLES

Clearly, these measurements need to be accurate if they are to be of value and an equally important factor in the specification of a measuring instrument for them is that it should be easy to use.

Electrical quantities such as currents and voltage can be measured to a considerable degree of accuracy with relative ease by using, for example, a digital multimeter. More sophisticated systems might employ an analogue-to-digital converter to give a digital representation of the analogue electrical signal produced. This can then be processed by a microcomputer.

Most physical quantities are not, however, electrical in nature, and if we want to use the convenience of an electrical measurement technique to determine the size of such variables, it is first necessary to derive from them an electrical signal which is a representation of the size of the quantity. This is the function of the transducer.

Fig. 1.1 and Fig. 1.2 show typical arrangements of transducers and associated measuring techniques.

Many transducers produce an electrical signal which is proportional to the size of the quantity being measured. This is a generally desirable, but by no means essential, feature of a transducer.

Circuitry for non-linear transducers can be designed to produce an output which does vary linearly with the size of the parameter being measured: such circuits are often called "linearisers".

TRANSDUCERS FOR TEMPERATURE MEASUREMENT

The change in temperature of a material causes corresponding changes in a number of parameters associated with it. If these changes can be measured, we have the basis for a system of temperature measurement.

As an example, the expansion in volume of a small quantity of mercury with rise in temperature is used in the common mercury thermometer.

microprocessor data acquisition system described in the December 1983 issue of *EE*, the completed units can be used with a digital or analogue voltmeter.

TEMPERATURE MEASUREMENT USING RESISTANCE THERMOMETERS

The resistivity—or specific resistance—of a metallic conductor, unlike that of a semiconductor, shows an increase as the temperature of the conductor rises. For a particular length and diameter of wire then, the resistance will increase as its temperature rises.

The increase in resistance per K rise in temperature expressed as a fraction of the

Table 1.1: Measuring temperature change electronically

SYSTEM	ELECTRICAL QUANTITY	APPLICATION
Metallic conductor	Change in resistance	Platinum resistance thermometer
Semiconductor	Change in resistance	Thermistors and LM334
Thermocouple	Change in thermo e.m.f.	Thermocouples

For our purposes, we are interested in systems in which a change of temperature produces a corresponding change in some electrical quantity associated with the system. Some examples of these are given in Table 1.1.

In this article, we shall discuss the theory and the construction of two practical temperature measuring systems. Although originally intended for use with the

wire's resistance at 0°C varies according to the material of which the wire is made: this quantity is known as the *temperature coefficient of resistance* of the material. Its value does not differ very much for pure metals, but special alloy wires such as Constantan, or Eureka are specifically manufactured so as to possess small temperature coefficients. This means that the resistance of a length of such wire does



not vary much with its temperature, thus rendering the wire useful for the manufacture of standard and very high stability resistors.

Platinum, being a pure metal, possesses a relatively high temperature coefficient, which means that the resistance of a particular wire made of platinum will show an appreciable variation with its temperature; this forms the basis of resistance thermometry—a temperature measurement technique which is capable of high precision over a wide range.

A typical platinum resistance thermometer can measure temperatures in the range -50°C to $+250^{\circ}\text{C}$ with an accuracy of 0.1%.

The sensing element itself originally consisted of a fine platinum wire grid arrangement, but in modern devices, this has been replaced by a platinum track deposited on to an insulating substrate.

Temperature sensing elements of this type are available in an unshathed form and, if these are used, care should be taken when handling them as the arrangement is

rather delicate. A more robust sensor is available in which the platinum sensing element is housed in a stainless steel probe and provided with suitable connecting leads—see Fig. 1.4.

Determination of the resistance of the sensor generally utilises a bridge technique, with the sensor forming one arm of the bridge. Various bridge configurations exist, but the simple “quarter-bridge” circuit shown in Fig. 1.3 is adequate for many applications. When correctly adjusted, this circuit will produce an output voltage very close to $1\text{mV}/^{\circ}\text{C}$.

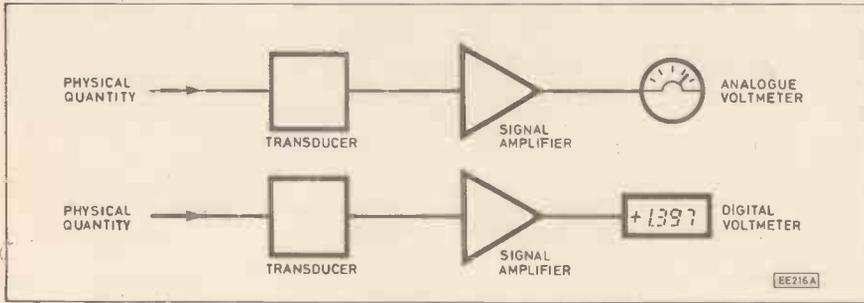


Fig. 1.1. Block diagrams for analogue and digital readouts.

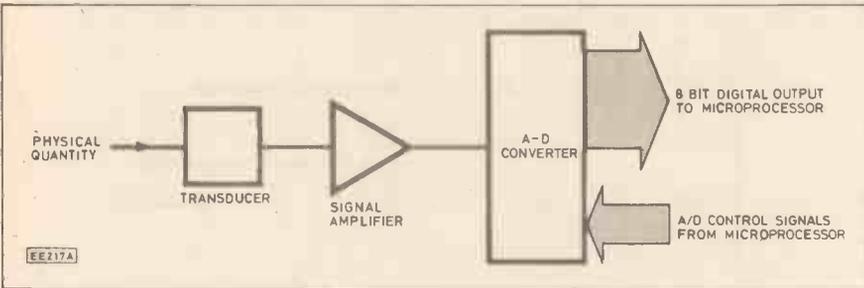


Fig. 1.2. Microprocessor interfacing using an A to D converter.

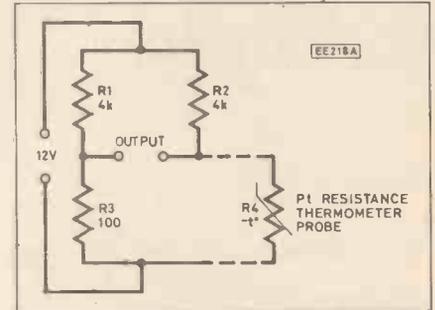


Fig. 1.3. Circuit diagram for a quarter bridge arrangement.

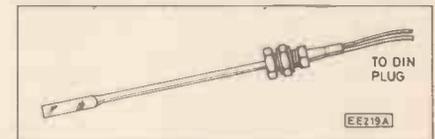


Fig. 1.4. Typical stainless steel probe housing the platinum sensing element.

Resistance Thermometer

THE PRACTICAL CIRCUIT

The practical circuit of the resistance thermometer is shown in Fig. 1.5. R1 and R2 form part of the ratio arm section of the bridge; VR1 completes this and provides a balance set facility.


All resistors should ideally be precision 0.1% types, but these are expensive and for many purposes, 1% types can be used. The bridge requires a stable voltage supply and the circuit includes the variable voltage regulator IC1 to provide this. The actual output voltage per unit change in the probe temperature depends on the bridge supply voltage and VR2 enables this to be varied for calibration purposes.

CONSTRUCTION

The construction of the circuit should present little difficulty, particularly if the p.c.b. pattern is used. See Fig. 1.6. Care should be exercised, however, when inserting and soldering in the fixed resistors. Their leads should not be bent too sharply at the ends as this can result in

mechanical stress and cracking of the resistive film. They should not be mounted in contact with the p.c.b., but two or three mm above it.

Fig. 1.5. Complete circuit diagram for the Resistance Thermometer.

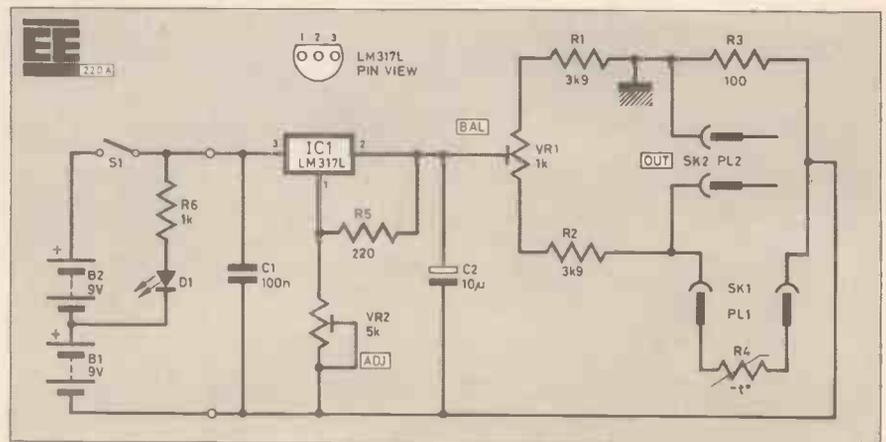

TESTING AND CALIBRATION

For acceptable accuracy, a digital voltmeter (3½ digits) is almost essential for calibrating the completed module. If a resistance decade box of range 0 to 199 ohms and a resolution of 0.1Ω is available, then this should be used and the following procedure adopted:

- (a) connect the DVM to the output of the bridge network and set it to its 200mV range

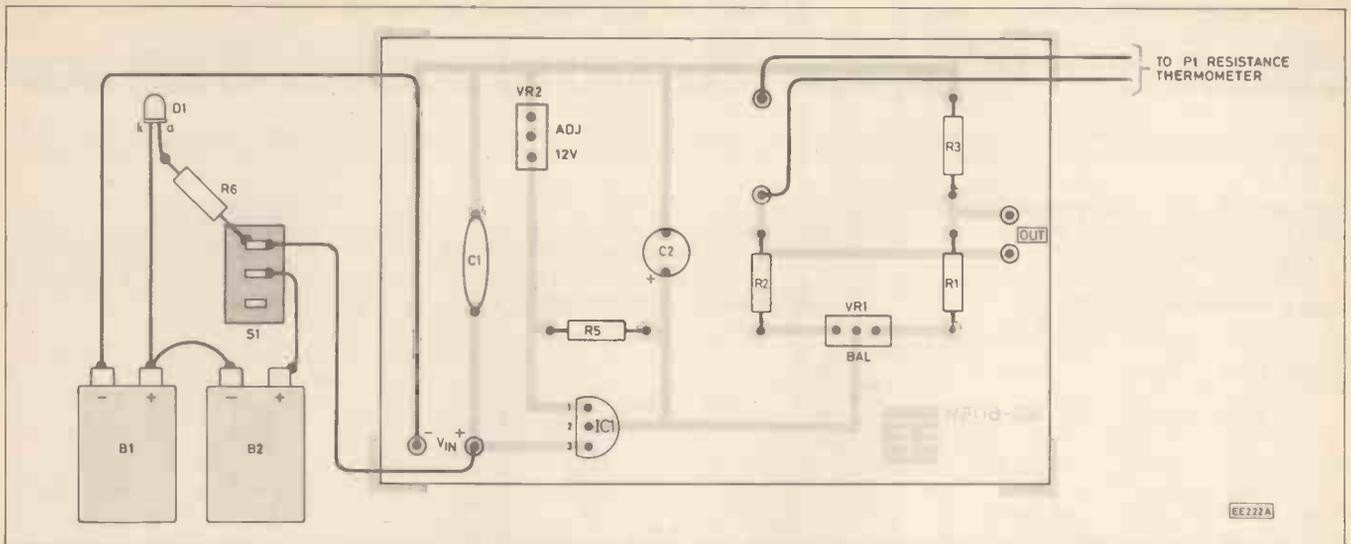


Fig. 1.6. Component layout and interwiring for the Resistance Thermometer.

COMPONENTS

See **Shop Talk** page 477

RESISTANCE THERMOMETER

Resistors

R1,R2	3k9 (2 off)
R3	100
R4	Platinum film probe
R5	220
R6	1k

All $\frac{1}{2}$ W 1% metal film (except R4—see text)

Potentiometers

VR1	1k, $\frac{3}{8}$ in. square. 25-turn cermet trimmer
VR2	5k, $\frac{3}{8}$ in. square. 25-turn cermet trimmer

Capacitors

C1	100n polyester
C2	10 μ elect., radial leads

Semiconductors

D1	green l.e.d.
IC1	LM317L voltage regulator

Miscellaneous

B1,B2	9V PP3 batteries (2 off)
PL1	5 pin DIN plug
PL2	BNC plug
S1	single-pole, sub-min. changeover switch
SK1	5 pin DIN socket
SK2	BNC socket

Case—203 x 127 x 51mm; printed circuit board, available from the *EE PCB Service*, order code 8509-03; stand-off mounting bushes for p.c.b.; battery connector clips; adhesive pads for batteries; adhesive feet for case.

Approx. cost Guidance only £32

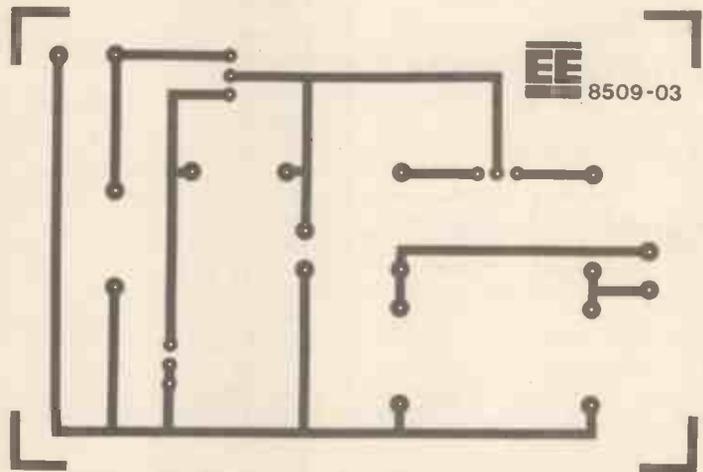


Fig. 1.7. Full size printed circuit board master for the Resistance Thermometer. This board is available from the *EE PCB Service*, order code: 8509-03.

(b) connect the decade box to the sensor terminals and set its resistance to 100.0 Ω (this is the resistance of the RS sensor at 0°C)

(c) adjust VR1 until a reading of zero is obtained on the DVM


(d) set the decade box to a resistance of 138.5 Ω (the resistance of the RS sensor at 100°C)

(e) adjust VR2 until the DVM reads exactly 100mV

The bridge is now calibrated and the platinum resistance sensor can be connected up instead of the decade box.

If a decade box is not available, then the bridge may be calibrated using the resistance sensor itself. It should be placed in an ice/water mixture and allowed to stand for several minutes and then step (c) carried out, in order to set the zero point.

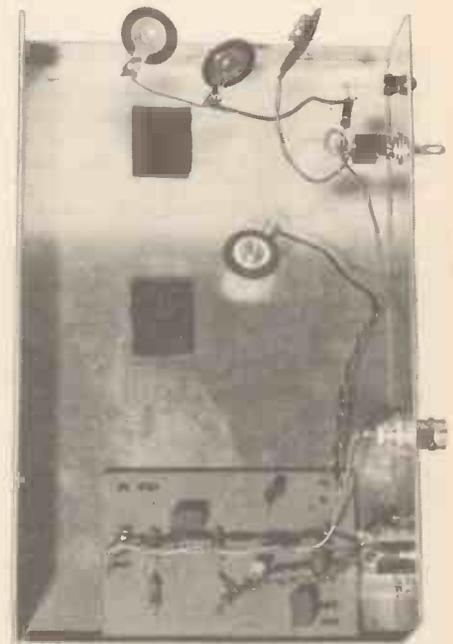Calibration at 100°C may be similarly achieved by placing the sensor in boiling water and adjusting VR2 for a 100mV output as in (e). Accuracy here depends upon the purity of the water and other conditions, but it should be adequate for most purposes.



Semiconductor Temperature Sensor

TEMPERATURE MEASUREMENT USING A SEMICONDUCTOR TEMPERATURE SENSOR

A NUMBER of semiconductor devices are available which produce an output current proportional to their absolute temperature. Commonly available are the LM334 and RS590 devices.

In the case of the LM334, a single resistor is used to set the current through the device to some value (the set current) which will then change linearly with the temperature at a rate of +0.33% per K rise in temperature. Fig. 1.8 shows a practical circuit for use with the LM334 to provide an output voltage of 0–100mV for a sensor temperature range of 0°–100°C, thus rendering it suitable for use with a DVM.

DESCRIPTION OF THE CIRCUIT

The LM334 is a three-terminal device, the current between V+ and V- (Pins 1 and 3) being dependent upon the value of R1 which, in this circuit, is chosen to be 220. This gives a set current which changes at a rate of 1µA per degree centigrade change in the temperature.

This temperature-dependent current is passed through the combination of R2/VR1 and develops across it a p.d. which varies linearly with the temperature of the LM334 sensor. VR1 provides a measure of trim so that the p.d. across R2/VR1 will increase at the required rate of 1mV per degree centigrade change in the temperature.

At 0°C (=273K), the current through the LM334 is, allowing for component tolerances, very nearly 273µA and this produces across R2/VR1 a p.d. of 273mV. When measuring centigrade temperatures in the range 0°C to 100°C we need the output from the circuit to be zero when the sensor is at 0°C. The R3/VR2 combination is used to provide a 273mV positive offset voltage for the negative terminal of the output.

For stable operation, a regulated supply is needed and IC1, a 78L05 voltage regulator, provides a steady +5V supply for both the LM334 and the offset voltage.

CONSTRUCTION OF THE CIRCUIT

This is a relatively straightforward matter if the p.c.b. approach is taken. Components should be inserted as shown in the overlay diagram of Fig. 1.9, noting carefully the orientation of the 78L05 regulator.

The LM334 itself is connected to the rest of the circuit by means of a short length of twin cored cable (it is convenient to locate R1 at the sensor itself rather than on the p.c.b.). The actual lead used can be of almost any length desired because of the very small current which flows in it.

Fig. 1.11 shows a possible "probe" arrangement for the LM334. The LM334 itself is housed in a T092 casing and it

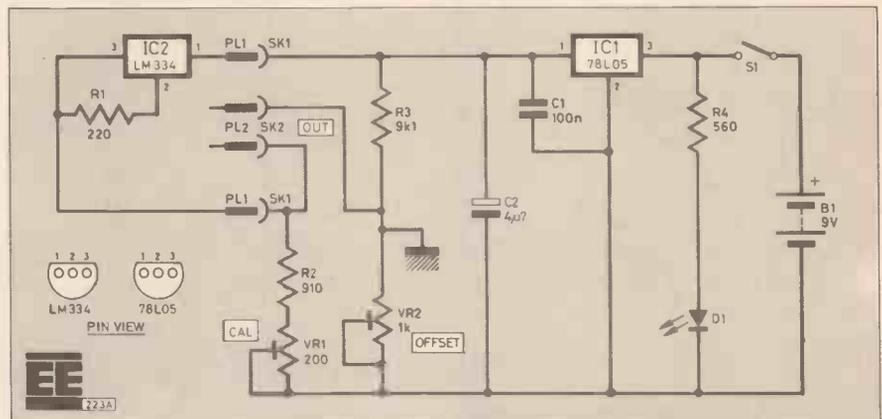


Fig. 1.8. Circuit diagram for the Semiconductor Temperature Sensor using the LM334.

resembles a small plastic-coated transistor. Its connections are shown in Fig. 1.8. In the assembly shown, the LM334 is mounted in a short aluminium tube which is closed at one end: the metal casing of an old OC82 transistor was used in the prototype. To ensure good thermal contact between the LM334 and the casing, a small quantity of heat sink compound was used.

The remainder of the probe consists of a length of rigid plastic tube (the case of an old felt-tip pen was used) and the 220 ohm current-setting resistor, R1, was contained in this. The twin lead terminates in a 5 pin DIN plug.


CALIBRATION OF THE COMPLETED TRANSDUCER

Calibration at 0°C and 100°C is necessary and the overall accuracy of temperature measurements will depend upon how accurately these temperatures can be reproduced. However, the linearity of the device does not warrant a precision of better than ±2°C, so melting ice and boiling water should provide adequate calibration points.

The following procedure should be followed:

- (1) connect up a DVM to the output terminals and switch on
- (2) set DVM to its 200mV range
- (3) place the LM334 sensor probe into an ice/water mixture which has stood for ten minutes or so and leave it to reach the temperature of the mixture
- (4) adjust the zero offset potentiometer VR2 until a reading of zero is obtained on the DVM
- (5) place the probe in boiling water and leave it to reach that temperature
- (6) adjust the sensitivity potentiometer VR1 until a reading of 100mV is obtained on the DVM
- (7) repeat steps 3, 4, 5 and 6 until no further adjustment of VR1 and VR2 is necessary.

The temperature transducer is now calibrated and ready for use. It is worth noting that it can, in fact, measure temperatures in the range of -50°C to +150°C although with slightly impaired accuracy outside the calibration range.

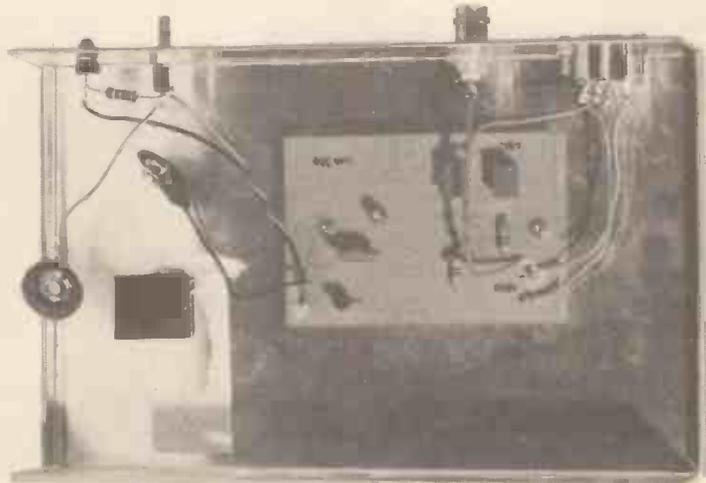

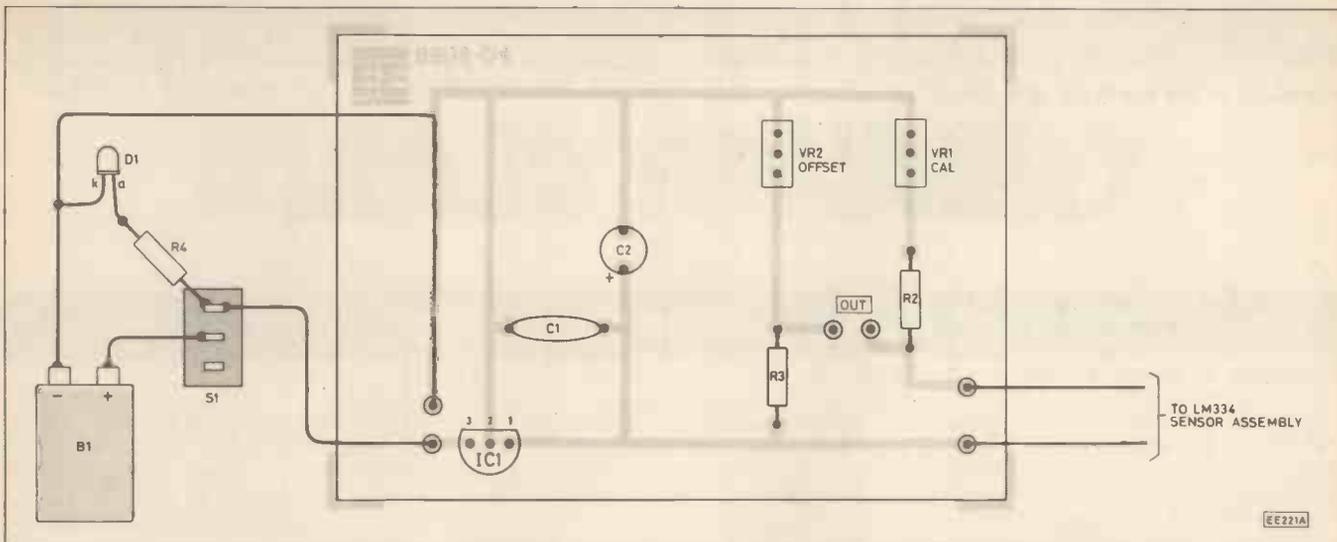


Fig. 1.9. Component layout and interwiring for the Semiconductor Temperature Sensor.

COMPONENTS

SEMICONDUCTOR TEMPERATURE SENSOR

Resistors

R1	220, 1%
R2	910, 2%
R3	9k1, 2%
R4	560, 5%
R1 to R3 $\frac{1}{2}$ W metal film/oxide. R4 carbon film. Tolerances as given	

Potentiometers

VR1	200, $\frac{1}{8}$ in. square. 25-turn cermet trimmer
VR2	1k, $\frac{1}{8}$ in. square. 25-turn cermet trimmer

Capacitors

C1	100n polyester
C2	4 μ 7 elect., radial leads

Semiconductors

D1	green l.e.d.
IC1	78L05 voltage regulator i.c.
IC2	LM334 programmable current source i.c.

Miscellaneous

B1	9V PP3 battery
PL1	5 pin DIN plug
PL2	BNC plug
S1	single-pole, sub-min. changeover switch
SK1	5 pin DIN socket
SK2	BNC socket
Case—203 x 127 x 51mm; printed circuit board, available from the <i>EE PCB Service</i> , order code 8509-04; stand-off mounting bushes for p.c.b.; battery connector clips; adhesive pads for battery; tube to house sensor i.c.; interconnecting wire; adhesive feet for case.	

Approx. cost
Guidance only

£18

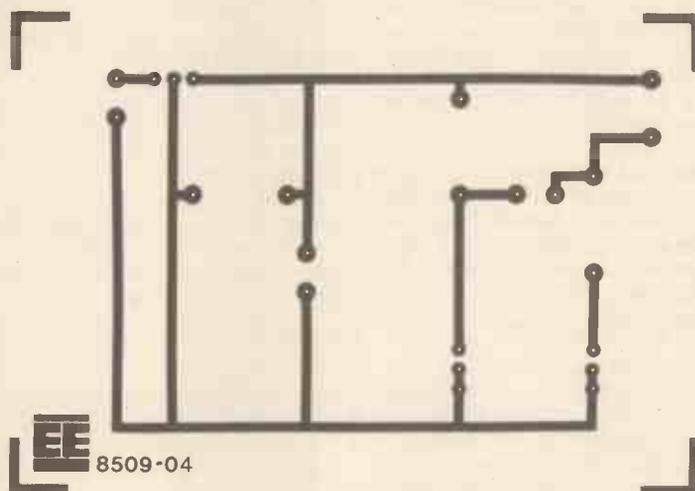


Fig. 1.10. Full size printed circuit board master for the Semiconductor Temperature Sensor. This board is available from the *EE PCB Service*, order code: 8509-04.

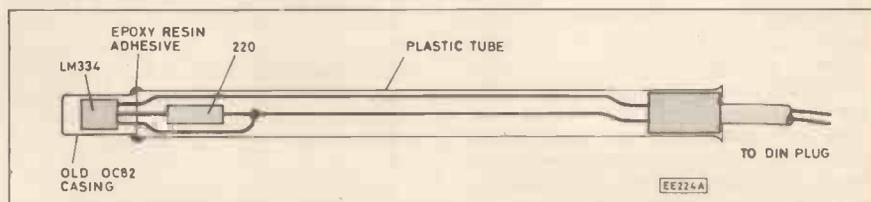


Fig. 1.11. Suggested probe assembly for the LM334.

NEXT MONTH: A strain gauge will be the subject of Part Two of this series.



CARAVAN ALARM

T. R. de Vaux Balbirnie

JUDGING from the large number of boats, bicycles and other valuables left unattended on organised caravan sites, outdoor enthusiasts must be among the world's most honest people.

There are times when the caravan is parked elsewhere, however, and it is here that the sneak-thief keeps a lookout for anything worthy of his attention. Fortunately, simple measures will deter all but the determined professional. This project will protect the caravan itself and also articles left inside and *outside*. In this last respect it is an improvement over existing alarms.

This alarm is only suitable for caravans having an independent 12 volt supply provided by a car battery. Such a system was described in the June, 1983, issue of *EE*. It could be used for other security applications not related to caravanning.

GENERAL DESCRIPTION

The Caravan Alarm is of the "link wire" type where breaking a continuous loop of wire triggers the warning device. On hearing this, the thief should beat a hasty retreat, leaving the goods where they are.

The system consists of a small control box at a secret place inside the caravan and a warning device (a car horn was used in the prototype) mounted underneath. Sockets inside and outside the caravan connect the link wires which pass through frames and handles of valuable articles—bicycles, gas cylinders, cameras, binoculars for example. A wire may be passed through a road wheel slot, effectively immobilising the caravan.

As well as plain link wires, microswitches, reed switches and mercury tilt-switches could all be made part of a comprehensive system. Link wires may be of any reasonable length and should be fitted with plugs and sockets at intervals to allow easy access for adding and removing items.

Once sounding, the alarm will not be silenced by re-connecting the link wire. It will operate for about half-a-minute, or some other preset time, then switch off. The alarm is then "locked out" and will not operate again until reset at the control box. The reason for this is that the thief, unlikely to re-connect the link wire, will not cause the battery to discharge by the circuit recycling and sounding the alarm continuously. This does mean that the system is insensitive to further attempted theft: the thief does not know this, however, and is unlikely to return. It is hoped that the alarm

will not be required to operate very often and it is assumed that the owner will check up periodically. An l.e.d. indicator on the unit signals the locked-out condition when the owner returns.

WARNING DEVICE

A car horn is suggested for giving the signal. The reason is that small audible warning devices are not loud enough for the purpose and more powerful devices are very expensive. Although the present circuit could operate any of these devices, car horns are readily available from car breakers' yards and are cheap, loud and weatherproof.

When choosing a used horn, buy a small modern one rather than a large metal-clad type from an old car. The latter consumes more current and could result in a short life for the relay contacts.

CIRCUIT DESCRIPTION


Referring to Fig. 1, it will be seen that TR1 and TR2 form a Darlington pair. The base of TR1 is kept at battery negative voltage as long as the link wire and any normally-closed switch contacts form a continuous circuit between points "A" and "B". This keeps both transistors off. If the link is broken, base current flows through R1 into TR1 via RLA1. The transistors now switch on, and the voltage across R2 rises. This triggers thyristor CSR1 and the warning device connected in its anode/cathode circuit sounds. If the loop is re-connected, the alarm will continue to sound since a thyristor, once conducting, will remain in this state until its anode/cathode current is interrupted.

Note that the collector current, and hence the gate current for CSR1, flows through the normally-closed contacts of relay RLA.

R1 has a very high value so that the continuous drain on the battery when the circuit is on "standby" is exceptionally low—about 6 μ A. A well-charged car battery can deliver such a current almost indefinitely—in fact, it would discharge by leakage far sooner.

With CSR1 conducting and the alarm sounding, current flows through D1, R5 and VR1. This charges C2 and the voltage across it gradually rises. After a time determined by the values of R5, VR1 and C2, the Darlington pair TR3 and TR4 switch on and the coil of RLA is energised. This component is fitted with a pair of change-over contacts. The normally-closed pair provides the flow of current in the anode/cathode circuit of CSR1. When the relay is energised by TR3/TR4, however, its contacts switch and interrupt the current flow through the thyristor, so silencing the alarm. At the same time, the collector current for TR1/TR2 and gate current to CSR1 stop flowing.

The normally-open contacts "latch" the relay by directing a continuous current through its coil. This is the "locked-out" condition. The l.e.d. (D3) connected in parallel with the coil signals this state. R7 limits the current through the l.e.d. and its value is higher than usual to reduce the current requirement yet allowing the l.e.d. to be sufficiently bright. D2 protects the transistors from possible damage due to the high back e.m.f. produced when the relay switches. C1 ensures reliable latching by providing current from the supply during the period when the moving contact of the relay travels from the normally-closed to normally-open position.

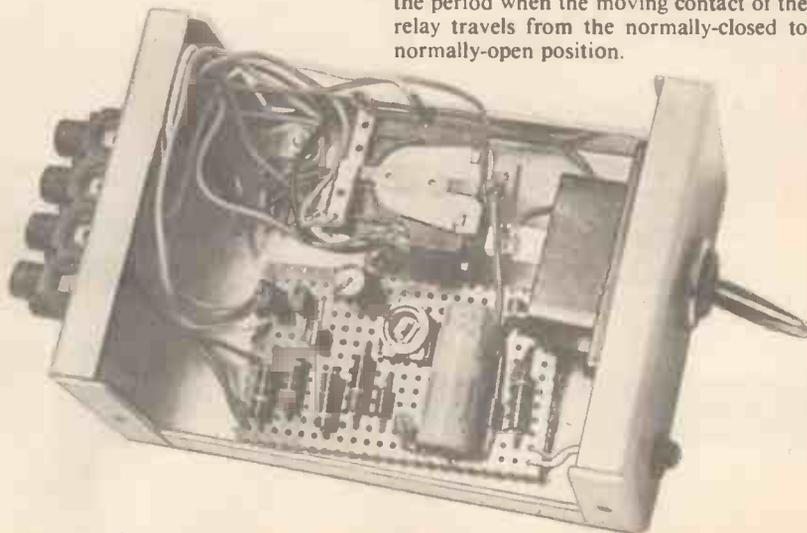

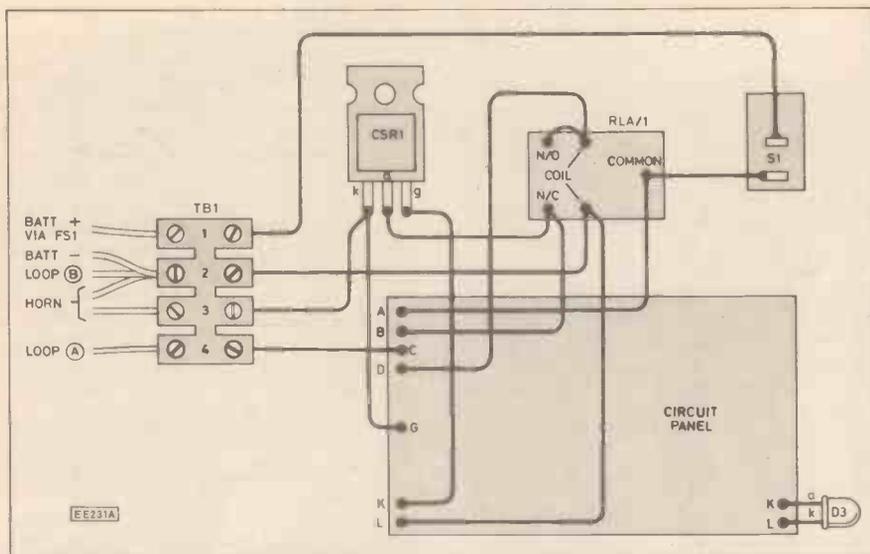


Fig. 3. Interwiring details for case mounted components. Note that the l.e.d. (D3) should be fixed using a plastic mounting clip.

finished alarm since any metallic contact between the case and the caravan body would result in a short circuit and FS1 would blow.

The circuit panel itself is attached using a further adhesive pad. Make certain that no soldered connections on the underside can penetrate the pad and cause a short circuit to the case. Check that, with the lid in position, all connections remain well clear of the metal work.

TESTING

It is kinder on the neighbours if testing is carried out using a lamp instead of the horn! Begin by adjusting VR1 to approximately mid-track position. With S1 off, make the connections to TB1. Include the line fuseholder carrying a 10A fuse in the positive battery lead. Use a short length of connecting wire to represent the link. Switch on and nothing should happen.

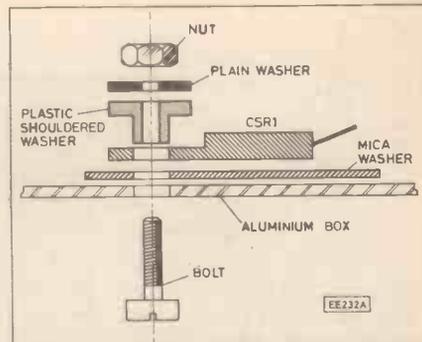


Fig. 4. Method of fixing the thyristor (CSR1) on the case using the mounting kit.

Now disconnect the link wire from TB1-4. The lamp should light and remain lit even if the link wire is re-connected. After a time, the lamp should go off and the l.e.d. will be seen to be glowing.


The circuit is reset by switching S1 off for a few seconds then on again. Adjust VR1 to give the desired delay time.

INSTALLATION

After a test with the horn, the circuit is ready for permanent installation. Another adhesive pad may be used to secure the box to the inside of the locker.

Do not omit the line fuse in the positive battery lead, as shown in Fig.1. With some horns, the negative connection is made through the vehicle chassis. In this case, simply connect TB1-2 to the chassis and omit the negative lead to the horn. □

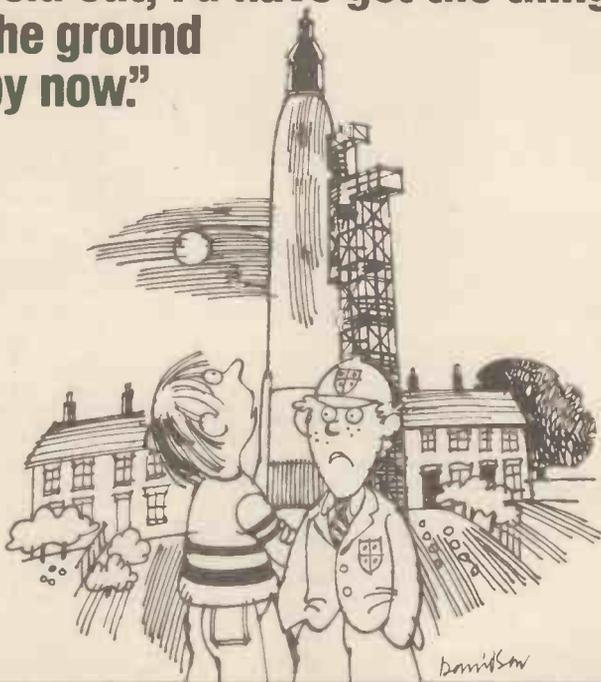"If last month's issue of EVERYDAY ELECTRONICS hadn't sold out, I'd have got the thing off the ground by now."



Sell-out disappointment can upset even the less ambitious reader! So why not take out a year's subscription and make sure of every issue, straight from the Publisher? Complete the order form below and post to EVERYDAY ELECTRONICS, Subscription Dept., Oakfield House, 35 Perrymount Road, Haywards Heath, West Sussex, RH16 3DH.

Annual subscription rates:
UK £12 Overseas £15

EVERYDAY ELECTRONICS SUBSCRIPTION ORDER FORM

Annual subscription rates:
UK £12 Overseas £15

To: Everyday Electronics, Subscription Dept., Oakfield House,
35 Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Name _____

Address _____

I enclose payment of £ _____ (cheque/PO payable to Everyday Electronics)

Charge my credit card account the amount of £ _____

Card no. _____

Name of card _____ valid from _____ to _____

Signature _____

Actually Doing it!!

IDENTIFYING component types is one thing, selecting the right value is another. It is easy enough to identify a resistor, but it is a little more difficult to distinguish between (say) a 2k2 resistor and a 10M type. This is due to the extensive use of colour codes to mark values on resistors, and to a certain extent on capacitors as well. The use of colour codes may seem to be an unnecessary complication, and from the beginner's point of view it is, but there are real advantages. The main one is that colour codes are less easily damaged to the point where they become unreadable than values that are marked using straightforward alpha-numeric characters. Another advantage is the ease with which the experienced user can pick out a component of the required value from a large batch of components. If the values are written on it, it is necessary to check through the components one-by-one until the required value is found.

Until recently the four band system was the only type of resistor colour coding in common use, but now a five band system receives a limited but significant level of use. Fig. 1 helps to explain these two very similar systems, but we will start with the four band coding. The first coloured band is the one which is marginally the nearest to one end of the resistor, and this gives the first digit of the value. Similarly, the second

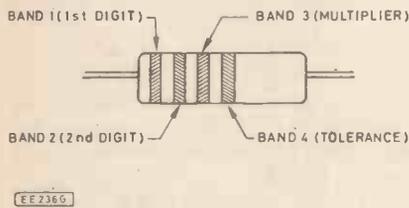



Fig. 1. Four and five band resistor colour codes. Do not assume that a resistor having a similar code to the one you require will have a similar value. If the "multiplier" is wrong the value will be wrong by a factor of at least ten.

band gives the second digit. For example, red and violet respectively represent 2 and 7 when they appear as the first or second band, as shown in the table in Fig. 1. The third band is the multiplier, and indicates the amount by which the first two digits are multiplied in order to give the value in ohms. Again taking a simple example, orange represents $\times 1000$, and a resistor having red, violet, and orange as its first three bands would have a value of 27000 ohms. A thousand ohms is usually abbreviated to a "kilohm" or "k", and a million

ohms is normally abbreviated to a "megohm" or just "M". A 27000 ohm resistor would therefore be shown as 27k on a circuit diagram or in a components list.

The fourth band indicates the tolerance of the resistor. This simply means the guaranteed maximum error in the value of the component, bearing in mind that no resistor has precisely its marked value. A 100 ohm resistor with silver (10%) as its fourth band would have a true value of anywhere between 90 and 110 ohms. It is perfectly alright (if a trifle extravagant) to use a resistor having superior tolerance to that called for in the components list, and a 1% type could be used instead of a 5% type, but it would be unwise to use a component having an inferior tolerance rating to the one specified.

The five band coding is normally only found on resistors having a tolerance of 1% or better, and it accommodates non-standard values which are not available to amateur users. The first three bands indicate the first three digits of the value, but the third one will almost invariably be black (0). The fourth and fifth bands indicate the multiplier and tolerance, as in the four band system. Orange, orange, black, red, brown therefore represents 33k ($3-3-0 \times 100=33000$ or 33k) with a tolerance of 1%. Probably the easiest way to tackle five band codes is to ignore the third band,

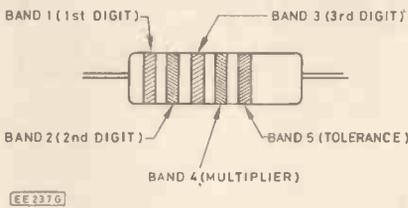

work out the value using the four band system, and then multiply this by ten to compensate for the ignored band.

Capacitor Codes

The Mullard C280 series and similar polyester capacitors are the only common types which use colour coding, although these days even these are not always colour coded. Fig. 2 shows the coding system used for this type of capacitor, and it is very similar to the four band resistor system. The first three bands give the value in exactly the same way, but it is in pico farads (pF) rather than ohms. Divide the value by 1000 to convert it to nano farads (nF) or 1000000 to convert it to micro farads (μF). If the first three bands were brown, black, and yellow, this would

Colour	Band Number			
	4 Band Codes		5 Band Codes	
	1	2	3	4
Silver	—	—	0-01	10%
Gold	—	—	0-1	5%
Black	0	0	0	1
Brown	1	1	1	10
Red	2	2	2	100
Orange	3	3	3	1000
Yellow	4	4	4	10000
Green	5	5	5	100000
Blue	6	6	6	1000000
Violet	7	7	7	—
Grey	8	8	8	—
White	9	9	9	—
None	—	—	—	20%

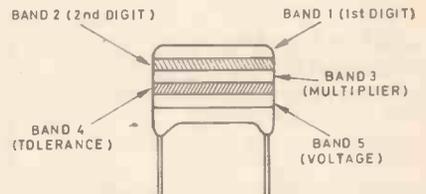


Fig. 2. C280 capacitor colour coding. This first three bands give the value (in pF) using the same system as for the four band resistor coding.

Colour	Band	
	4	5
Black	20%	—
White	10%	—
Green	5%	—
Orange	2-5%	—
Red	2%	250V
Brown	1%	—
Yellow	—	400V

indicate a value of 100000pF ($1-0 \times 10000=100000$). Pico farads are not normally used for large values, and 100000pF would be more likely to appear in the form 100nF or 0.1 μF .

The fourth band indicates the tolerance, and the fifth one shows the highest d.c. voltage to which the component should be subjected. Voltage ratings are often omitted from components lists, and this is simply because most types of capacitor have very high voltage ratings whereas modern circuits mostly operate at low voltages, giving no risk of exceeding the voltage ratings.

Robert Penfold

DOWN TO EARTH

BY GEORGE HYLTON

"I RECENTLY bought some neon lamps designed for 240V a.c. operation. The lamps are sealed into a translucent plastic enclosure, and it is not possible to see if a current-limiting resistor is incorporated. How can I find out if it is, without breaking open one of the lamps?"

NEON LAMP CHARACTERISTICS

An interesting question. The characteristic of a neon lamp is that it passes no current until a critical voltage is applied. Then it "strikes", passing a current which rises almost without limit, and is destroyed, unless sufficient resistance is included in the circuit. Generally speaking, neons strike at around 120V and then "run" at a lower voltage, around 70V.

In the usual circuit (Fig. 1) the current is limited by R1. The behaviour of the lamp is shown in Fig. 2, where the upper curve is the mains voltage. The shaded part is the voltage which appears across the lamp.

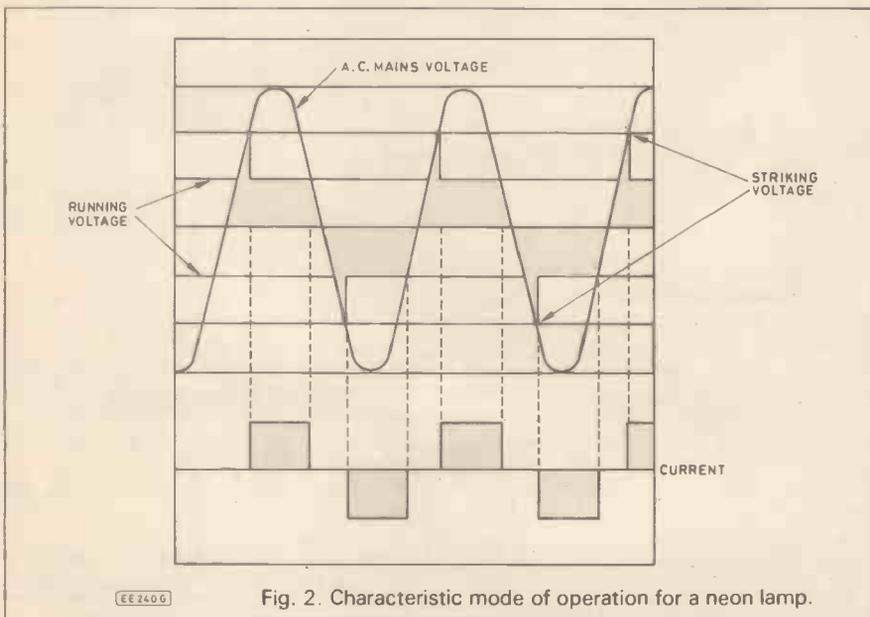


Fig. 2. Characteristic mode of operation for a neon lamp.

During each mains cycle this rises to the striking voltage (say 120V), falls instantly to the running voltage (say 70V), and then stays there, until the lamp goes out when the voltage falls too low to sustain the current. The voltage then follows the mains wave until the striking voltage is again reached during the next half cycle, when the process repeats.

Thus the lamp lights for a substantial portion of each half-cycle. For 50 Hz mains, this means that it lights 100 times a second. The current flows as shown in the lower graph.

To return to our problem: a typical current for a miniature neon of the type used in "mains on" indicators is 1mA. If the running voltage is 70V and the mains 240V this leaves 170V to be absorbed by R1. Of course the voltage changes over the mains cycle: 170V is an average. For a current of 1mA, R1 must be about 170k. Neon lamps are not precision components and the running voltage varies. So a likely standard-value resistance would in this case be 180k or 150k.

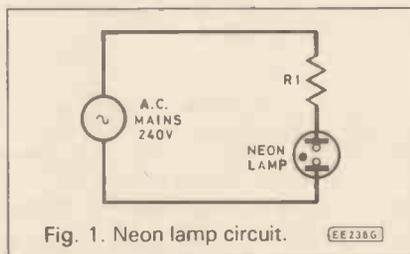


Fig. 1. Neon lamp circuit.

It's no use connecting an ohmmeter across the "unknown quantity" lamp, because the meter's internal battery voltage is far too low to make the lamp strike. So the resistance reading stays firmly at infinity.

The solution to the problem is to raise the voltage to well above the striking voltage, but make sure the current is limited. Perhaps the easiest way is to make use of the mains in a circuit with an

additional resistor, R2, and a voltmeter, as shown in Fig. 3. Here the dotted-round part is the lamp unit. At present we don't know what value R1 has—if there is no built-in resistor it is zero! So we choose R2 to limit the current. Neons can be run for short periods at greater than normal currents so we needn't be too fussy about the size of R2—a reasonable value is 100k. (When making the test remember that the mains can be *lethal* and take precautions against contact with the circuit).

CALCULATING RESISTOR VALUES

Suppose we connect up and the neon lights, and the voltmeter across R2 reads 100V. This leaves 140V across the lamp unit. This is so much greater than the running voltage that R1 must be present.

If there is no meter-loading error, i.e. if 100V is the true voltage, then the current must be $100V/100k=1mA$. If the neon runs at 70V then there must be 70V across R1 (since R1 and the neon together absorb 140V). It follows, since we have a current of 1mA through an unknown resistance which drops 70V, that R1 must be about 70k—in practice, probably larger.

When the lamp is operated normally, without R2, there must be about $240-70V=170V$ across R2 and the current must be $170/70000=2.4mA$ approximately.

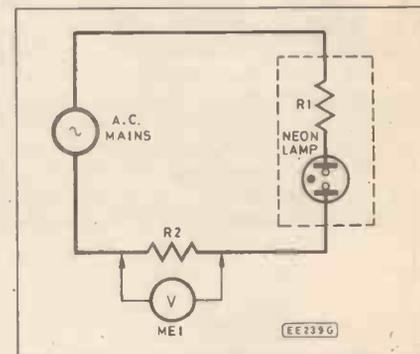


Fig. 3. Circuit for determining the approximate value of the ballast resistor.

BALLAST RESISTORS

The current limiting (or "ballast") resistor R1 must be adequately rated. For a 1mA neon the amount of power dissipated by R1 is quite small. Even if the full 240V appeared across a 100k resistor its dissipation would only be 240mW, so a "quarter-watt" component would just do.

However, resistors also have maximum voltage ratings. The voltage in this type of circuit might well exceed this rating in the case of some types of resistor. So if you find that a ballast resistor must be added, err on the side of making it too large (electrically or physically) rather than too small.

Neons emit some light even when the current through them is minute, which is why they are used (with large-value ballast resistors) in the "mains tester screwdrivers" used by electricians. A few microamps through the body is harmless.

CT1000K CLOCK/TIMER KIT
24hr Digital clock with presettable ON and OFF time for output. Ideal for use with tape recorders, lighting etc. **£14.90**

VERO

Mk1 THERMOSTAT KIT
will control 1kW heater. Ideal for greenhouse. **ONLY £4.60**

REGULATORS
78 Series **50p**
78L Series **30p**

ANTEX SOLDERING IRONS
15w **£5.60** ST4 stand **£1.90**

BT Phone
connectors starter pack **£9.50**

TRIACS

FREE 28 page catalogue. Send 9x6 SAE NOW!
Telephone orders - Access & Barclaycard **RING 01-567 8910 (24hrs)**

BOOKS
By Babani, TI and Elektor

MULTIMETERS
Analogue from **£6.50**
Digital from **£26.95**

DIGITAL LOCK KIT
operates from 5 to 18Vdc supply and gives 5040 combinations. 10 way keyboard supplied. 750mA output. Ideal for disabling car ignition or for door lock when used with 701 150 lock mechanism **£11.50**
701 150 **£14.95**

ULTRA SENSITIVE DVM/THERMOMETER KIT
3 1/2 Digit LCD design drawing a mere 150µA at 9v. 200 mV full scale or -20 to +150°C thermometer **£15.50**

LINEAR ICs
555 **21p**
CMOS 555 **55p**
741 **22p**
LM3914 **£2.65**
LS7225 **£2.60**
+ Lots lots more in our Cat.

BOXES
Plastic, diecast aluminium

LEDs
from **9p**

BEGINNERS PROJECT PACK
Build 10 fascinating projects including burglar alarm, intercom, thermostat etc on the solderless breadboard enclosed. Full circuit descriptions and layouts included **£12.50**

TOOLS
Side cutters **£2.10**
See Cat. for full range.

CMOS
4001 **18p**
4017 **39p**

3 NOTE XK102 DOOR CHIME
complete kit includes box & speaker **£5.50**

PANTEC KITS

VELLEMAN KITS

PLUS A WIDE RANGE OF PLUGS, SOCKETS, RESISTORS, POTS, CAPS, VERO etc etc

ELECTRONICS

13 BOSTON RD
LONDON W7 3SJ

Tel. Orders: 01-567 8910

Enquiries: 01-579 9794

Shop Hours: Mon-Fri. 9am-5pm
Sat. 10am-4pm. Closed Wednesday

ORDERING INFORMATION: ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.

LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
GOODS BY RETURN SUBJECT TO AVAILABILITY



MARCO TRADING



RESISTOR KITS

1/4W Pack 10 each value E12 10R-1M
Total: 610 resistors **ONLY 4.80**

1/4W Pack 5 each value E12 10R-1M
Total: 305 resistors **ONLY 2.75**

1/2W Pack 10 each value E12 2R2-2M2
Total: 730 resistors **ONLY 5.25**

1/2W Pack 5 each value E12 2R2-2M2
Total: 365 resistors **ONLY 3.50**

50v Ceramic Kit 5 each value
125 Per Kit **£3.50**

PRE-SETS

Vert + Horiz 100R to 1M 10p, 100 for **£6.50**

STANDARD CERAMIC CAPACITORS

All 50V. 1p to 10 nF 4p each, 100 for **£2.75**

COPPER WIRE

Tinned + Enamelled Copper Wire. 2oz reels:
14 to 30 swg **£1.00** per reel.

ZENER DIODE

400 mW 3v to 75v: 8p each, 100 for **£6.00**. 1 watt 3v3 to 200v: 15p each, 100 for **£12.50**

SWITCHES

Sub-Minature Toggle SPST 60p DPDT 63p DPDT 66p

Miniature Toggle SPDT 68p SPST DPDT Centre off 85p

Standard Toggle SPST On/Off Plate 48p DPDT On/Off Plate 58p

Miniature DPDT Slide Push-To-Make 15p Push-To-Break 20p

Rotary Switch 1 pole 12 way, 2 pole 6 way, 3 pole 4 way, 4 pole 3 way 50p

SOLDERING AIDS

Antex 15W iron 5.00
Antex 18W iron 5.00
Antex 25W iron 5.20
Antex Elements 2.00
Antex Bits 0.95
Antex stands 1.90
Desolder Tool 4.50
Spare nozzle 0.65
25W Kit-iron with 13A plug & stand **ONLY 7.20**

NI-CAD CHARGER

Universal charger to charge PP3, AA, C, D **PRICE 6.00**

SPEAKERS

4" Round 1.6W 4 Ohm **£1.50** pair
4" Round 1.6W 4 Ohm Plus Mounting Bracket. **£1.00** each
2 1/4" Round 0.4W 8 Ohm 85p each

EQUIPMENT WIRE

1/0 6.4 p/m **£2.75/100**
7/0 2.5 p/m **£3.50/100**
16/0 2.8 p/m **£5.35/100**
24/0 2.10 p/m **£7.50/100**

SERVICE AIDS

ALL SERVISOL PRODUCTS
Switch Cleaner 0.98
Circuit Freezer 1.14
Foam Cleanser 0.96
Aero Klene 0.90
Silicone Grease (Tubes) 1.64

DC MOTOR
6-12V **75p**
5 for **£3.00**

PLUG SOCKETS

Metal Co-ax Plug 0.18
Plastic Co-ax Plug 0.14
Metal Line Socket 0.50
Single Junc. Socket 0.30
Plastic Photo F.M. Plugs 0.20
PL259 Plugs 0.30
Reducer 0.15
Low loss splitter 1 m. 2 out 1.00
40 pin 0.34 3.10/10

BATTERY HOLDERS SNAPS

EH735/Take 2 AA Cells 17p
A302/Take 4 AA Cells 21p
A304/Take 6 AA Cells 32p
EH805/Take 8 AA Cells 40p
EH807/Take 10 AA Cells 46p
CX2/Take 2 C Cells 29p
B203/Take 4 C Cells 31p
DX2/Take 2 D Cells 29p
PP3 Battery Snap 7p, £5/100
PP9 Battery Snap 17p/pr £16/100

NI-CADS

PP3 **£4.45** 4/16.00
AA **£9.95** 10/30.00
HFII **£2.30** 4/9.50
C **£1.95** 4/8.75

WALKMAN TYPE SPEAKERS

Powered Stereo Speakers complete with carrying strap. Built-in Pre-amp. Needs to be heard to be believed. Uses 2 x D size batteries - not supplied. £3.50 each (plus additional postage £1 set).

CLOCK RADIO - VHF/LW/MW

Mains, digital display alarm clock/radio. Alarm control/Wake to music. Sleep control - 10 min. Snooze. Hour/Minute Time Setting. Brightness Control. £8.50 each (plus additional postage 75p per set).

PLASTIC BOXES

Dil to Dil 3 x 2 x 1" 0.25
3 x 2 1/2 x 2" 0.65
4 x 3 x 1 1/2" 0.80
6 x 4 x 2 1/2" 1.15
8 1/2 x 5 x 3 1/4" 2.15

Colour Black, all boxes with lids and screws.

L.E.D.s

RED: 3mm + 5mm 10p each, 100 for **£6.00**. YELLOW: 3mm + 5mm 13p each, 100 for **£10.00**. GREEN: 3mm + 5mm 13p each, 100 for **£10.00**. Prices include colouring clips.

SPECIAL OFFER

The complete set of three strip-fix plastic signs, containing over two thousand words. Transmitters, frequencies, dials, letters and symbols etc. Three for **£3.75**.

FUSEHOLDERS

20mm Panel Mounting 0.28
20mm Chassis Mounting 0.06
1 1/4in Panel Mounting 0.35
1 1/4in Chassis Mounting 0.34
Carline 1 1/4in Mounting 0.10

FUSES

OB 20mm 100mA to 6.3A 5p each, 100 for **£3.50**. Slow Blow 20mm 100mA to 200mA 12p, 100 for **£7.50**. 20mA to 800mA 12p, 100 for **£7.50**. 1A to 6.3A 10p, 100 for **£5.00**.

TELECOM EQUIP

BT Plug & 3M lead 1.25
BT MASTER SOCKET 2.85
BT Sec Skt 1.95
BT 4-core cable 1M 0.15
100M 12.00

ROTARY POTS

0.25W Carbon Log & Lin 1K-2M2 each 0.32
10 3.00
Any 100 28.99

SCREENED CABLES

Black - 3 core (2 metres extended) 75p
each **£0.00/10**

TRANSISTORS

AC126 0.30
AC176 0.28
AF239 0.68
BC107 0.10
BC108 0.10
BC109 0.10
A.B.C. 0.12
BC147 0.09
BC182 0.09
BC182L 0.09
BC184 0.09
BC184L 0.09
BC212 0.09
BC212L 0.09
BCY70 0.15
BD131/2 0.34
BD133 0.56
BD135 0.32
BD136 0.36
BF115 0.32
BF184 0.32
BF185 0.32
BF194 0.08
BF195 0.10
BF196 0.10
BF197 0.10
BF200 0.20
BF224 0.20
BF244 0.26
BF244A 0.28
BF244B 0.30
BF259 0.32
BF262 0.30
BF263 0.30
BF337 0.38

BF338 0.38
BFX26 0.28
BFX84 0.24
BFX85 0.26
BFX87 0.26
BFY50 0.21
BFY52 0.21
BFY90 0.90
BSX20 0.34
BUJ208 1.55
BUJ407 1.65
MJ2955 0.90
OC45 0.58
OC71 0.50
OC72 0.52
TIP31A 0.44
TIP32A 0.42
TIP33C 0.88
TIP34A 0.72
TIP2955 0.60
TIP3055 0.60
TIS43 0.88
TIS88 0.40
2N3055 0.45
2SC1096 0.68
2SC1173Y 0.82
2SC1306 0.92
2SC1307 0.40
2SC1957 0.76
2SC2028 0.73
2SC2029 2.10
2SC2078 1.05
2SC2166 1.20
2SK68 0.65
40673 0.80

DIODES

IN916 0.04
IN4001 0.05
IN4004 0.06
IN4005 0.06
IN4007 0.07
IN4148 0.05
IN4149 0.06
IN5400 0.12

AA119 0.12
AA129 0.18
AA330 0.16
BA100 0.24
BY126 0.12
BY127 0.10
BY133 0.16
BY184 0.40

74LS

LS00 28p
LS01 28p
LS02 28p
LS03 28p
LS03 32p
LS08 28p
LS09 28p
LS10 28p
LS11 28p
LS12 25p
LS13 33p
LS14 58p
LS15 25p
LS20 28p
LS21 28p
LS22 28p
LS30 30p
LS32 28p
LS37 23p
LS74 38p
LS122 70p
LS138 45p
LS139 68p
LS151 75p
LS155 50p
LS157 45p
LS158 58p
LS160 60p
LS161 70p
LS162 72p
LS163 80p
LS166 1.95
LS170 1.75
LS244 1.00
LS245 2.00
LS257 73p
LS393 1.15

MARCO TRADING (DEPT EE9)
The Maltings
High Street
Wem, Shropshire SY4 5EN
Tel: 0939 32763 Telex: 35565

ORDERING. All components are brand new and to full specification. Please add 50p postage/packing (unless otherwise specified) to all orders then add 15% VAT to the total. Either send cheque/cash/postal order or send/telephone your Access or Visa number. Official orders from schools, universities, colleges, etc, most welcome. (Do not forget to send for our 1985 catalogue - only 65p per copy. All orders despatched by return of mail.
NEW RETAIL 1,000 sq. ft. shop now open. Mon-Fri 9.00-5.00, Sat 9.00-12.00.



NEW 1985 CATALOGUE
WILL BE AVAILABLE AUGUST/SEPTEMBER
Range of components greatly increased - over 125 pages fully illustrated. Price £1.00 per copy. (Free upon request with orders over £15). Includes 50p Credit Note, Special Offer Sheets, Order Form and Pre-Paid Envelopes.

RIAA PREAMPLIFIER INPUT SELECTOR

R.A. PENFOLD

LIKE practically any branch of electronics, things in the audio world have changed steadily over the years. This can lead to a situation where a piece of equipment that has served its purpose well for several years becomes dated and lacking in certain respects. In the case of the author's tuner/amplifier the power amplifier section still offers a respectable level of performance, and in the lower to middle price range power amplifier designs have changed surprisingly little over the past few years. A point that is demonstrated by the fact that several popular amplifiers are still in production and selling well after four or five years.

At the front end things are a little different. A few years ago signal to noise ratios of about 60dB were common for magnetic pickup inputs, but these days a signal to noise ratio of over 70dB can be achieved using readily available components. Presumably due to deteriorating electrolytic smoothing capacitors, the level of mains "hum" from a magnetic pick-up preamplifier often increases over a period of years, and can become comparable or even slightly higher than the ordinary background "hiss". Another problem is simply that these days many people wish to use a variety of signal sources, such as different types of tape deck and a compact disc player. While most modern amplifiers and receivers are well equipped with input sockets, older types generally just have pick-up and tape inputs, plus a single auxiliary input.

This project is designed to overcome these shortcomings by providing three switched inputs that feed into the auxiliary input of the amplifier or receiver. A high quality, low noise magnetic pick-up preamplifier is included at one input, and this is used in place of the built-in preamplifier. The other two inputs just feed straight through to the auxiliary input, and are suitable for items of equipment such as a second tape deck and a compact disc player. In other words the unit effectively provides an extra auxiliary input and a high quality magnetic pick-up input.

EQUALISATION

A magnetic pick-up preamplifier must provide a fairly high voltage gain since the output from this type of pick-up is typically only around five millivolts r.m.s., whereas a power amplifier normally requires an input signal at about one hundred times this level. However, the preamplifier must also provide equalisation (tailoring of the frequency response) in order to give the system a flat overall response.

The equalisation during playback is needed to counteract the RIAA equalisation which is introduced during the recording process. The RIAA (recording) equalisation characteristic really consists of two separate sections. One of these is the pre-emphasis that is used in most broadcasting and recording systems. This consists of a certain amount of treble boost at the recording or transmission stage (the pre-emphasis), and

complementary treble cut at the receiver or playback equipment (de-emphasis). The result is an overall frequency response that is flat, but an improved signal to noise ratio due to the treble cut used during playback. This reduces background noise of the "hiss" variety which is an inherent part of any recording or transmission system.


The treble boost used during the recording process consists of a 6dB per octave boost at frequencies above 2120Hz. In more simple terms, a doubling in frequency above 2120Hz results in a doubling of the voltage gain. The preamplifier must therefore provide a 6dB per octave roll-off above 2120Hz (doubling in frequency giving a halving in the voltage gain).

The other part of the equalisation is a 6dB per octave roll-off at frequencies from 500Hz to 50Hz, and the preamplifier must therefore provide a boost of 6dB per octave over this frequency range. The purpose of this equalisation is to prevent excessive groove modulations. It has to be remembered here that the movement of the cutting head varies not just with the signal amplitude, but with frequency as well. The method of recording used for all normal records is the constant velocity type, where the speed at which the cutting head moves is controlled by the amplitude of the signal (the higher the amplitude the higher the velocity). The frequency of the signal is irrelevant. As a result of this, at high frequencies the cutting head has hardly started to move in one direction before the signal starts to decay, and then a change of polarity dictates a move in the opposite direction. This gives a large number of very small groove modulations.

With low frequencies a much longer time passes before the signal level starts to fall back to zero and change polarity, so that much larger but fewer groove modulations are produced. This is exactly the same effect that results in no perceptible movement of a loudspeaker cone if the unit is fed with a strong high frequency signal, whereas a low frequency signal of the same strength is sufficient to practically drive the diaphragm against the end stops.

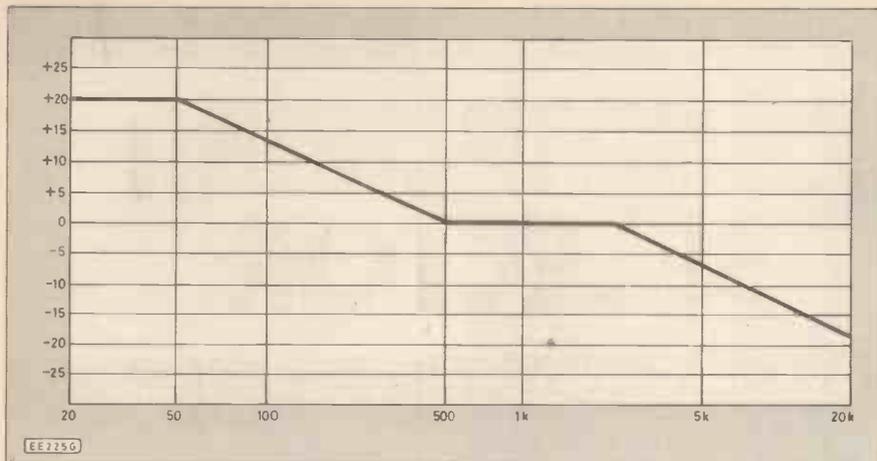In a disc recording context the effect of the large low frequency modulations would be to result in the grooves merging together, and the vertical movement of the cutting head could presumably result in holes being





cut right through the master disc. Obviously the problem could be overcome simply by reducing the amplitude of the whole signal, but this would give an unacceptable reduction in the signal to noise ratio of around 20dB. By only reducing the amplitude of low frequency signals the signal to noise ratio only deteriorates at these frequencies. While even this loss of performance is undesirable, it does not prevent excellent results from being obtained in practice.

The ideal playback response for an RIAA playback amplifier is shown in Fig 1. The sub-audio response is not shown, but this should be rolled off so that any sub-audio signals generated by record warps etc. are attenuated.

FEEDBACK

Frequency selective negative feedback is the normal way of providing RIAA equalisation, and most circuits are based on an operational amplifier working in the non-inverting mode, or an equivalent of this. Fig 2 shows the basic circuit for an operational amplifier in the non-inverting mode.

Three resistors are used to control the voltage gain and input impedance of the amplifier. Resistor R3 biases the non-inverting input to the 0V earth rail, and as an operational amplifier (in theory anyway) has an infinite input impedance, the input impedance of the amplifier is equal to the value of R3. In practice the input impedance will be slightly lower than R3, but the margin of error is normally too small to be of any consequence.

Resistors R1 and R2 are the negative feedback network which control the voltage gain of the circuit. In theory an operational amplifier has infinite voltage gain, and in practice it is extremely high at d.c. and low frequencies. The signal which is amplified is the voltage difference across the two inputs. As one would expect, a positive output is produced if the non-inverting (+) input is at the higher voltage, and a negative output is generated if the inverting (-) input is at the higher voltage. Due to the very high voltage gain of the operational amplifier only a very small voltage difference is required across the inputs in order to drive the output fully positive or fully negative.

The effect of R1 and R2 is to maintain a voltage balance at the two inputs of the operational amplifier. Thus, under quiescent conditions the output is maintained at precisely the same voltage as the non-inverting input, or at the earth rail potential in other words. This must be so, since a positive output potential would take the inverting input more positive due to the coupling via the potential divider formed by R1 and R2. This would unbalance the inputs, sending the output negative to restore the balance. A negative output potential would have a similar effect, but by taking the inverting input negative of the non-inverting one the output would be sent more positive, again restoring the balance.

If R2 is omitted, the output will be at the same potential as the inverting input since there will be no significant voltage drop through R1. The output is therefore maintained at the same voltage as the non-inverting input due to the balancing action, and the circuit acts as a unity voltage gain buffer stage. With R2 in circuit things are different, as R2 introduces losses through R1 by a normal potential divider action.

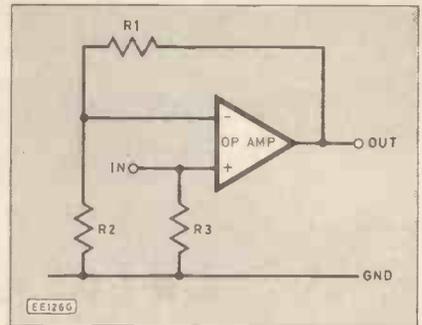


Fig. 2. Op.amp non-inverting mode configuration


Fig. 1. The Ideal RIAA playback characteristic

This necessitates a larger output voltage for a given input voltage in order to maintain the input balance, and the circuit provides voltage gain. In fact the voltage gain is equal to $(R1 + R2)/R2$. This is the "closed loop" gain (the gain of the circuit as a whole) which should not be confused with the "open loop" gain (the gain of the operational amplifier itself).

PRACTICAL CIRCUIT

The circuit diagram for one channel of the stereo preamplifier is shown in Fig 3. Most of the components are duplicated in the other channel, but exceptions are C1, C2, S2, and the batteries. Switch S1 is a three way four pole rotary switch, but in this circuit only two poles are used (one in each channel). In the components list and construction diagram the components in the second channel are ten higher than those in the first channel (e.g. the equivalent of C1 in the other channel is C11).

The circuit has dual balanced supplies, which is normal for operational amplifier circuits where the output may need to have

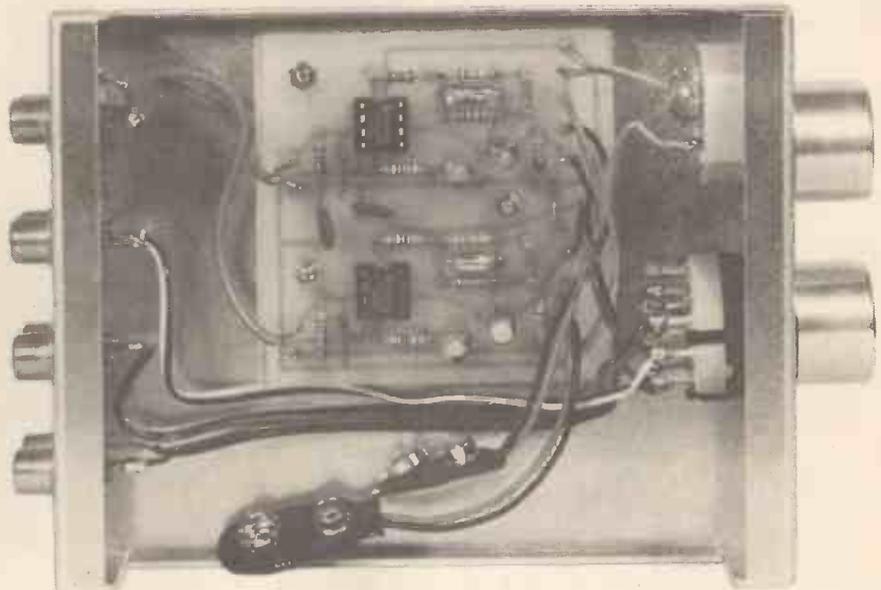

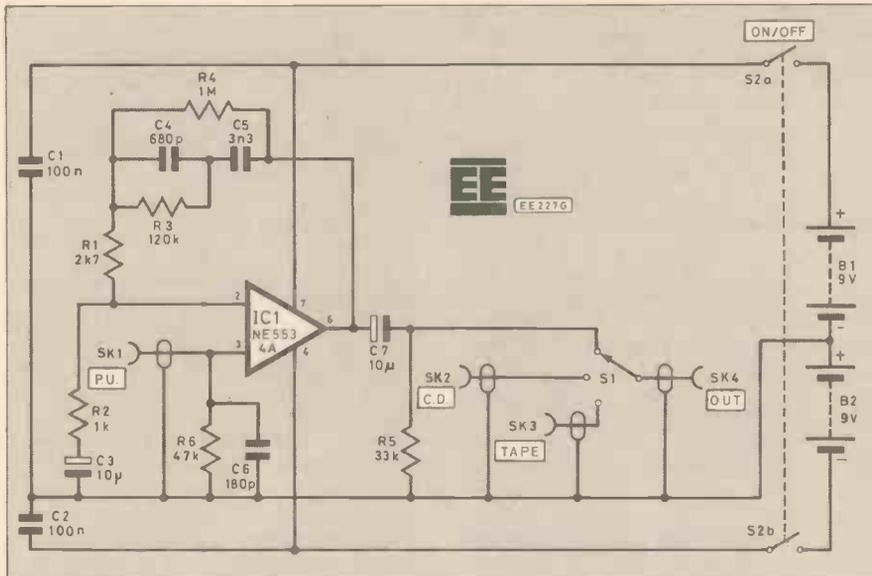


Fig. 3. Circuit for one channel of the RIAA Preamp Input Selector


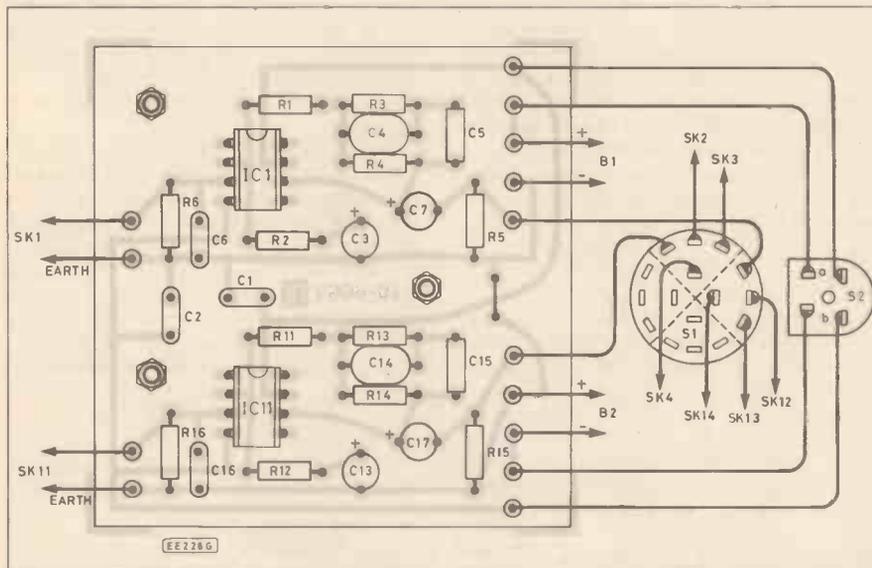
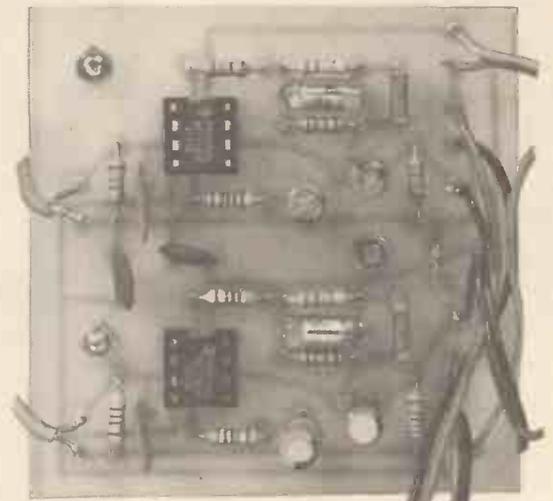


Fig. 4. Layout and wiring of the unit

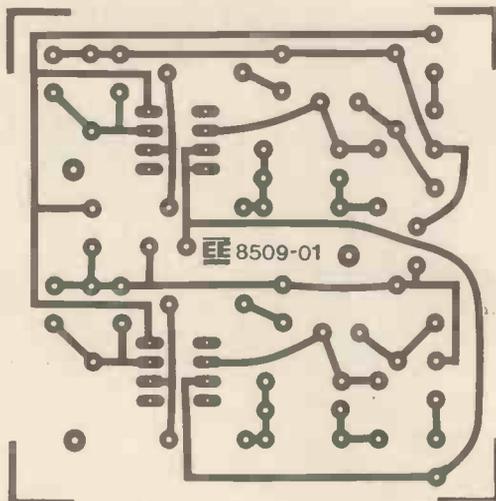

COMPONENTS

See
**Shop
Talk**

page 477

Resistors

R1,R11	2k7 (2 off)
R2,R12	1k (2 off)
R3,R13	120k (2 off)
R4,R14	1M (2 off)
R5,R15	33k (2 off)
R6,R16	47k (2 off)
All 1/4 W 5% carbon	

Capacitors

C1,C2	100n ceramic (2 off)
C3,C7, C13,C17	10u 25V radial elect. (4 off)
C4,C14	680p polystyrene (2 off)
C5,C15	3n3 carbonate (2 off)
C6,C16	180p ceramic plate (2 off)

Semiconductors

IC1,IC11	NE5534A (2 off) low noise op. amp.
----------	------------------------------------

Miscellaneous

S1	3 way 4 pole rotary switch
S2	Double pole rotary on/off switch
SK1 to SK14	Phono sockets (8 off)
B1,B2	9 volt PP3 size (2 off)
Printed circuit board, available from the EE PCB Service, order code 8509-01; two control knobs; aluminium case about 133 by 102 by 38mm; two 8 pin d.i.l. i.c. holders; two PP3 style battery connectors; wire, solder, etc.	

Approx. cost
Guidance only

£15.00

either polarity with respect to the earth rail. The unit could be powered from a mains power supply capable of providing between about plus and minus nine to 15 volts at a few milliamps, but care would have to be taken in order to avoid stray coupling of mains hum into the signal path. With a battery supply the hum level of the circuit is zero, and there is no problem with induced hum if the unit is positioned close to the pick-up.

Resistor R6 is the bias resistor for the non-inverting input of IC1, and a value of 47k is a suitable match for most pick-ups, but obviously a different value could be used here if necessary. Capacitor C6 serves two purposes; firstly it helps to prevent stray high frequency feedback from producing instability, it also helps to give a higher capacitance load for the cartridge, which usually gives a flatter frequency response. However, if the unit is used in conjunction with one of the few cartridges that are intended for low capacitance loads it might be beneficial to reduce the value of C6 and C16 to 47p.

The negative feedback circuit is more complex than just two resistors, and R1 in Fig 2 is replaced in the practical circuit with three resistors and two capacitors. The capacitors have an impedance that is frequency dependent. Their impedance reduces as the frequency is increased, and this property provides the equalisation. At low frequencies neither C4 nor C5 provide a low enough impedance to significantly affect the voltage gain of the circuit, and it is consequently set at about 60dB (1000 times) by the feedback resistors.

At higher frequencies C5 exhibits a lower impedance, and it effectively shunts R3 across R4 at frequencies above 500Hz, giving a voltage gain of about 40dB (100

times) and effectively producing the required bass boost. At frequencies of more than about 2kHz or so the impedance of C4 falls to a significant level and provides the treble cut. The equalisation curve obtained will not precisely match the ideal RIAA replay characteristic, but errors are normally within 1dB and are not significant.

Capacitor C3 provides the sub-audio roll-off part of the RIAA replay characteristic. It also provides d.c. blocking so that the d.c. voltage gain of the circuit is unity rather than 1000 times. This is important as practical operational amplifiers have small offset voltages, this results in the output drifting away from the earth potential, and a high d.c. voltage gain can multiply this effect to the point where the circuit fails to operate properly. Capacitor C7 and resistor R5 are used to eliminate any small d.c. offset that is present at the output of IC1.

The NE5534A specified for IC1 is a special very low noise and distortion type intended for critical audio applications. The circuit will work using less expensive operational amplifiers such as the LF351 and TL071, but these would provide a signal to noise ratio some 10dB or more higher. With the NE5534A the signal to noise ratio is typically about 75dB with reference to an output of two volts peak to peak. Incidentally, the standard NE5534 will also operate well in the circuit, but would give slightly inferior results.

Switch S1 is the input selector switch, and this merely couples the required signal source through to the output socket.

CONSTRUCTION

Details of the printed circuit board and wiring are shown in Fig 4. The printed circuit board is straightforward and easy to

construct or may be purchased from the EE PCB Service. The NE5534A is not a MOS integrated circuit, but as it is a fairly expensive device it is definitely still worthwhile fitting IC1 and IC11 in 8 pin d.i.l. i.c. holders. Printed circuit pins are used at the places where connections to off-board components will be made when the board is wired to the rest of the unit.

An aluminium box which measures approximately 133 by 102 by 38 millimetres is suitable as the housing for this project. Most other cases of about this size should also be suitable, but a metal case should be used so that the circuit board and wiring are screened from sources of electrical interference. Also, some earth connections are carried via the case which must therefore be of metal construction. The two controls are mounted on the front panel, the sockets are fitted on the rear panel, and the circuit board is mounted on the base panel of the case, leaving sufficient space for the batteries to one side of the board. Spacers are used over the mounting bolts to keep the connections on the underside of the board clear of the metal case.

To complete the unit the point to point wiring is added. It is a good idea (but not essential) to use screened leads to connect the board to SK1 and SK11, but ordinary hook-up wire can be used for the other leads.


In use the unit is connected to the rest of the system via normal twin screened phono leads. The unit must, of course, be switched on when the preamplifier is in use, but at other times it should be switched off to conserve the batteries. It is possible that with some combinations of cartridge and amplifier a higher level of gain will be needed. This can be accomplished by reducing the value of R2 and R12 to 560 ohms. □

FUNTRONICS


ANSWERS

TRANSISTOR TEASER

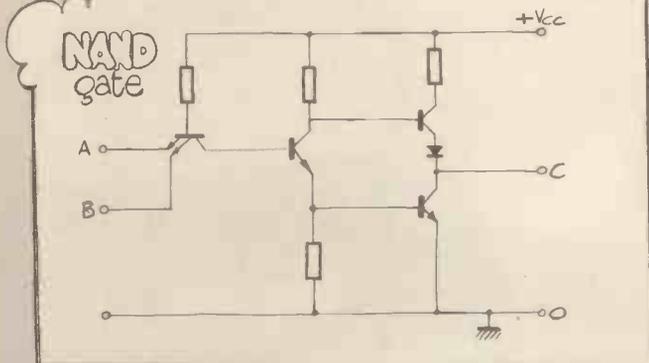Join up the components below to form a familiar circuit.



2-WORD LINK-UP

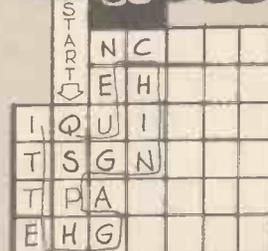

1st word: Quenching
2nd word: Spaghetti

The Man Behind the Symbol

Nº3 André Marie Ampère

by Morgan Bradshaw

WE HAVE seen how Volta's discovery enabled man to produce low electric power from batteries, but to obtain higher power he had to make magnets move. The man who did much to establish the relation between electricity and magnetism or, as he called it "electrodynamics", was the French mathematician and physicist Ampere who gave his name to the practical unit of electric current. (Table 1).

INFANT PRODIGY

Andre Marie Ampere was born on 22 January 1775, in the village of Polemieux, near Lyons, the son of a merchant, who was also the local Justice of the Peace.

Young Andre showed astonishing capabilities at a very early age. He had a phenomenal memory and it is said that he was calculating before he could read or write. He had read all the books in the family library by the age of eleven and written a treatise on conic sections by the age of 13.

His father took him to the Academy in Lyons to use the library, and young Andre discovered that he would have to learn Latin in order to study the great works of reference which were printed in that language. This he did in record time. He had already become an accomplished mathematician, and he had studied botany and

zoology, quite an achievement for a boy who had never been to school and who was completely self taught.

COMES THE REVOLUTION

Then in 1793 tragedy struck. Lyons had revolted against the tyranny of the French Revolution, the army of the Convention who hated all forms of authority captured the town and Andre's father was thrown into prison, and soon after taken to the Place Bellecour and publicly guillotined. Forced to watch, the shock was so great upon the mind of the eighteen year old Ampere that he remained in a state of apathy and near madness for almost three years.

Then in 1796 he met Julie Carron who gave him back his "zest for life". By this time he was short of money and, so that they could be married, Ampere started to give private lessons in mathematics and languages. On 2 August 1799 at the age of 24, he married his beloved Julie and one year later a son Jean Jacque (named after his grandfather) was born. Once again Andre was a happy man, he was now Professor of Physics and Chemistry in the town of Bourg, but after one year he accepted a senior post at the Academy at Lyons where he had astonished the professors with his capabilities when a child.

In 1804 tragedy struck Ampere a second blow, his wife to whom he was devoted, died of a chest disease. He did little for five years except to compose some tragic latin verse. Then in 1809 after publishing a thesis on the mathematical theory of gambling, he was recommended for the post of Professor of Mathematics at the Polytechnic in Paris.

He lived only for his work publishing many scientific papers, was elected to the Academy of Science in 1814, and made Inspector General of the French Universities, a post involving much travel.

OERSTED GETS THE NEEDLE

On 11 September 1820 the academy heard that the Dane, Hans Christian Oersted (who we will meet later), had discovered that a magnetic compass needle moved when placed near a wire carrying an electric current.

TABLE 1: THE AMP (A)

The flow of electric current is measured in amps. Just as we used the water pressure analogy for the volt (V), so we can compare electric current with the flow of water.

As a practical example the current which flows through a domestic chandelier holding four, 60-watt lamps when connected to a 240V mains supply would average one ampere (A).

Sir Charles Bright, the English telegraph engineer who supervised the laying of the first Atlantic cable, was one of the first to recognise the need for a practical unit of current with an internationally acceptable name and in 1881 the Ampere along with the Volt was adopted at the first meeting of the International Electrotechnical Commission.

The volt is the product of the ampere and the ohm.

The news of this discovery so excited Ampere that he worked night and day experimenting on the relationship of electricity and magnetism, and just one week

Photos:
Science
Museum,
London

Ampère's Apparatus



later on 18 September he presented to the academy the results of his experiments which showed that when electric current is passed through two parallel wires in the same direction they are attracted, and when the current flows in opposite directions they repulse.

He also proved that the force of attraction or repulsion is directly proportional to the strength of the currents, and inversely proportional to the square distance between them. This became known as *Ampere's rule*.

Ampere was now completely dedicated to the new source of power. His little workshop was crowded as he demonstrated his many experiments including one that showed the action of the earth's magnetic field on a wire in which current flows. His

discoveries led to many developments based upon magnets especially the electromagnet, the heart of the telegraph.

He gave many public demonstrations and one of his contemporaries reported "a gasp would go up from the audience as Ampere twisted insulated copper wire round an iron horseshoe joined the ends of the wire to Volta's battery, and showed how the horseshoe attracted a quantity of nails, and how it let them fall the moment the current from the battery was shut off".

Ampere died of pneumonia in Marseilles on 10 June 1836 and his death was transmitted to Paris by the Semaphore. Yet to come was the telegraph, telephone, and radio for which he had helped lay the groundwork.

COUNTER INTELLIGENCE

BY PAUL YOUNG

Young Tycoon

On the largest stand at a big electronics exhibition salesmen are talking in hushed whispers. "Here he comes," says one, and they fall back respectfully while the President of the company and six of his top executives advance to meet their distinguished visitor.

Who can it be you may wonder, a captain of industry, a leading electronic tycoon, the head of a large bank? No, it is none of these people, it is a thirteen-year-old schoolboy called, Rawson Stovall.

Rawson is an all-important figure in the electronic games industry. Months of research and the likelihood of success hangs on whether Rawson likes the end product. He is the right age and knows more about what the consumer wants in the games market than any of our experts, said one executive. When he talks, we listen.

As you probably will have guessed, this is happening in America, where at the moment the computer business is having a hard time. Since August last year 18,000 jobs in the industry have been lost. Regrettably we are not faring much better in the UK and quite recently I read that Mr. Robert Maxwell has had to rescue the wizard, Sir Clive Sinclair.

Super Battery

I suppose if anyone asked me what the shelf life of the average pen torch type of battery was, I would have said about eighteen months to two years. In the light of a recent experience I must now revise my estimate.

I have one of these cheap, maid-of-all-work multimeters that has a sensitivity of a thousand ohms per volt, will measure a.c. and d.c. voltage, limited d.c. current and with a fairly basic and not very accurate ohms range. I use it mainly for checking mains and making continuity tests.

The other day I was checking a suspect kettle element, when I noticed that the

meter needle was only just flickering. In a flash brilliant Young had worked out that the battery needed replacing. I began to wonder when I last changed the battery and I realised that this was the original battery supplied with the meter. Now for the surprise, I purchased this meter about thirty years ago!!

With a certain amount of trepidation I undid the case. What Leclanche miracle was I going to find? I removed the penlite battery. It was marked Number 555 and underneath in large letters were the words "FIVE RAMS". Above was the actual drawing of the five rams.

Having decided that four of them were dead and fifth very sick, I replaced the battery. I was also pleased to note that there was no sign of leakage of electrolyte. What did disappoint me was the bottom line. "Made in Hong Kong". All the same, I feel it would be inadvisable on the grounds of personal safety, to visit your local supplier and ask for a Five Rams battery.



★ BAKER ★

GROUP P.A. DISCO AMPLIFIERS post £2

150 watt Output, 4 input Mixer pre-amp. Illustrated £99
150 watt Output, Slave 500 mtr. Input 4+8+16 ohm £80
150+150 watt Stereo, 300 watt Mono Slave 500 mtr. Inputs £125
150 watt P.A. Vocal, 8 inputs. High/Low Mixer Echo Socket £129
100 watt Valve Model, 4 inputs, 5 Outputs. Heavy duty. £125
60 watt Mobile 240v AC and 12v DC. 4-8-16 ohm+100v line £89

MIKES Dual Imp £20, Floor Stand £13, Boom Stand £22, PP £2.

Reverb Unit for Microphone or Musical Instruments £35 PP £1.

Electronic Echo Machine for mic/etc. £85. Deluxe £95 PP £1.

H+H 1000w mono, 500w stereo quality amplifiers, model S500D, reconditioned, guaranteed £275 PP £5.

BAKER LOUDSPEAKERS		Post £2 each	
Type	Model	Size	Watts Ohms Price
P.A./Disco/Group	DG50/10	10	50 8/16 £18.00
Midrange	Mrd 100/10	10	100 8 £25.00
Hi-Fi	Plator	12in	30 4/8/16 £18.00
Hi-Fi	Superb	12in	30 8/16 £26.00
P.A./Disco/Group	DG45	12in	45 4/8/16 £18.00
Hi-Fi	Woolfer	12in	80 8 £25.00
Hi-Fi	Auditorium	15in	60 8/16 £39.00
P.A./Disco/Group	DG75	12in	75 4/8/16 £22.00
P.A./Disco/Group	DG100	12in	100 8/16 £26.00
P.A./Disco/Group	DG100/15	15in	100 8/16 £39.00

DISCO CONSOLE Twin Decks, mixer pre amp £145. Carr £10.
Ditto Powered 120 watt £199; or Complete Disco 120 watts £300.
150 watt £360; 360 watt £410. Carr £30.

DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2 ceramic tape, 1 mono mic channel, twin vtu meters, headphone monitor outlet, slider controls, panel or desk mounting, matt black fascia. Tape output facility. £59. Post £1.

DELUXE STEREO DISCO MIXER/EQUALISER as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. £129 PP £2

Headphone Monitor, Mike Talkover Switch
As above but 3 deck inputs, 4 line/aux inputs, 2 mic inputs, 2 headphone monitors £145.

P.A. CABINETS (empty) Single 12 £34; Double 12 £40. carr £10.

WITH SPEAKERS 45W £52; 75W £56; 90W £75; 150W £84.

200 Watt £100, 400 Watt £150.

300 WATT MID-TOP SYSTEM Complete £125 carr £12.

HORNBOXES 200 Watt £32, 300 Watt £38. Post £4.

WATERPROOF HORNS 8 ohms. 25 watt £20. 30 watt £23. 40 watt £29. 20V plus 100 volt line £38. Post £2.

MOTOROLA PIEZO ELECTRONIC HORN TWELFIER. 3 1/2in square £6
100 watts. No crossover required. 4-8-16 ohm, 7 1/2x3 1/2in. £10

CROSSOVERS. TWO-WAY 3000 c/s 30 watt £3. 60 watt £5. 100 watt £6.
3 way 350 c/s/3000 c/s. 40 watt rating. £4. 60 watt £6.50, 100 watt £10.

LOUDSPEAKER BARGAINS Please enquire many others in stock.

4 ohm 5in, 7x4in £2.50; 6 1/2in, 8x4in £3.8m; 8 1/2in, 6 1/2in, 25V £7.50.

8 ohm 2 1/2in, 3in. £2; 5x3in, 6x4in, 7x4in, 5in. £2.50; 6 1/2in, 8x5in £3; 8in £4.50; 10in, 15in, 12in. £6. 8in 25W £6.50. 8 in Twin Cone 60w £12.50.

15 ohm, 2 1/2in, 3 1/2in, 5x3in, 6x4in. £2.50. 6 1/2in 10W £5. 8in 10in. £7.

Famous Makes	Model	Size	Watts/Ohms	Price	Post
AUDAX	WOOFER	5 1/2in 25F	8	£10.00	£1
GOODMANS	HIFAX	7 1/2x4 1/4in	100 8	£34.00	£2
GOODMANS	HB WOOFER	8in.	60 8	£14.00	£1
WHARFEOALE	WOOFER	8in.	30 8	£9.00	£2
CELESTION	DISCO/Group	10in.	50 8/16	£21.00	£2
WEM	300	10in.	300 8	£36.00	£2
GOODMANS	PP12	12in.	75 15	£22.00	£2
WEM	300	12in.	300 8	£44.00	£2
GOODMANS	HPG/Group	12in.	120 8/15	£34.00	£2
GOODMANS	HPD/Disco	12in.	120 8/15	£34.00	£2
H+H	DISCO/BASS	15in.	100 4/8/16	£49.50	£3
GOODMANS	HPB/BASS	18in.	230 8	£71.00	£4
GOODMANS	HPD/BASS	18in.	230 8	£67.00	£4
GOODMANS	PP12	12in.	75 15	£22.00	£2

METAL GRILLES 8in £3, 10in £3.50, 12in £4, 15in £5.50, 18in £7.50.

R.C.S. DISCO LIGHTING EQUIPMENT

READY BUILT DELUXE 4 CHANNEL 4,000 WATT sound chaser + speed + programme controls £69. Mk2 16 programs, £89 PP £2.

PARTY LIGHT 4 coloured Flood Lamps Flashing to Music. Self-contained Sound to Light 410 x 196 x 115 £34.95 PP £2.

MAINS TRANSFORMERS Price Post

250-0-250V 80mA. 6.3V 3.5A. 6.3V 1A £7.00 £2

350-0-350V 250mA. 6.3V 6A CT £12.00 £2

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid

9V, 3A; 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A; 17-0-17V, 2A; 35V, 2A; 20-40-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 80V, 2A.

£8.50 post 50p MINI-MULTI TESTER

Pocket size instrument. A.C./D.C. volts, 15-150-500-1000.

DC current 0-150mA. Resistance 0-100K 1000 ohms p.v.

De-Luxe Range Doubler Meter, 50,000 o.p.v. 7 x 5 x 2 1/2in. Resistance 0.20 meg in 5 ranges. Current 50mA to 10A. Volts 0.25/1000V DC, 10v/1000V AC. £25.00 PP £1

PANEL METERS 50mA, 100mA, 500mA, 1mA, 5mA, 100mA, 500mA, 1 amp, 2 amp, 5 amp, 25 volt, VU 2 1/4x2 1/4in. £5.50 post 50p

ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1.80; 14 x 9in. £1.75; 6 x 4in. 55p; 12 x 8in. £1.30; 10 x 7in. 36p; 8 x 6in. 30p; 14 x 3in. 72p; 12 x 5in. 90p; 16 x 10in. £2.10; 16 x 6in. £1.30.

ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.

4 x 2 1/2 x 2 1/2in. £1.20; 3 x 2 x 1 1/2in. £1; 6 x 4 x 2in. £1.90; 8 x 6 x 3 in. £3; 12 x 5 x 3in. £3.60; 6 x 4 x 3in. £2.20; 10 x 7 x 3in. £3.60

HIGH VOLTAGE ELECTROLYTICS 32+32/500V £2

16/450V 50p 220/400V £2 32+32/350V £2

20/500V 75p 8+8/450V 75p 32+32+32/450V £1.50

32/350V 45p 20+20/350V 75p 16+32+32/500V £2

RECORD PLAYER DECKS. P&P £2.

Make Drive Model Cartridge Price

BSR Single Belt 12 volt Ceramic £22

BSR Single Rfm P207 Ceramic £22

AUTOCHANGER BSR Ceramic £22

AUTOCHANGER GARRARD Ceramic £24

Many others in stock. Phone for details.

DECCA TEAK VENEERED PLINTH space for small amplifier. Board cut for BSR or Garrard 18 1/4in. x 14 1/4in. x 4in. £5. Post £1

TINTED PLASTIC COVERS for Decks. £5 each Post £1

17 x 12 1/8 x 3 1/2in. 14 1/8 x 13 x 3 1/8 14 1/2 x 13 1/8 x 2 3/4in. 22 3/8 x 13 1/8 x 3in. 30 3/4 x 13 3/8 x 3 1/4in. 21 x 13 3/8 x 4 1/2in. 18 1/4 x 12 1/2 x 3in. 21 1/2 x 14 1/4 x 2 1/2in.

RADIO COMPONENT SPECIALISTS

Dept 4, 337, WHITEHORSE ROAD, CROYDON

SURREY, U.K. Tel: 01-684 1665

Post 5p Minimum. Callers Welcome. ACCESS VISA

Full Lists 34p Stamps Same day despatch Closed Wednesday

NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

DESIGNER'S KIT

A COMPREHENSIVE designer's kit for their family of 6301 microprocessors has been produced by Hitachi.

It is claimed that it will be particularly useful because of the versatility of the 6301 family which includes nine chips, three versions; 13 different operating modes; three speeds; four package styles and wide operating temperature versions.

The kit includes an EPROM on-chip CMOS microcomputer (HD63701XOC), an adaptor, a user's manual, datasheets and full support literature and is supplied for the sum of £80.

For further information contact:



*Hitachi Electronic Components (UK) Ltd.,
Dept EE, Hitec House,
221-225 Station Road,
Harrow, Middlesex,
HA1 2XL.*

SMALL WORLD

THE world's smallest and lightest portable compact disc player, is the claim being offered by Technics to describe their latest CD model SL-XP7. Small enough to fit in the palm of a hand, it measures only 126mm x 126mm x 31.9mm and weighs 520 grammes.

Slightly smaller than a CD jacket/cover, it features a newly developed fine focus single beam laser pick-up system and 15-step random access programming selection.

The development of the FF1, a miniaturised fine focus single beam laser pick-up has been the main factor contributing to the compact size and performance. This optical system which, it is claimed, has improved performance over other three beam

units, features a digitally controlled servo system using digital circuits to monitor laser tracking and focus accuracy.

The free floating mechanism of the optical deck is specially designed to resist physical shock, which is an important consideration in a portable system. The friction-free 4-wire suspension uses four special metallic wires to support the focus lens.

The 15-step random access programming facility allows the user to select tracks on the disc to be played in any order. The memory/recall key can also be used during play to obtain a recall display showing which tracks have been programmed.

For static or home use the unit is powered by an a.c. adaptor, but for total portability, an optional carrying case, with rechargeable battery pack is available.



ALIGNMENT TAPE

IF YOU are one of the 200,000 owners of the Amstrad CPC464 home computer, then you may be interested in the latest combined cassette cleaner and azimuth alignment tape system from Kiltdale.

Developed and manufactured by Kiltdale, it is claimed that the azimuth tape allows the user to effectively align his own recorder to assure virtual 100 per cent efficiency when loading software.

Azimuth misalignment occurs when the recording head is not exactly at right angles to the tape. Although cassette heads are correctly aligned at the factory, general wear and tear will cause misalignment and the associated difficulties in program loading.

After prolonged use dirt will build up in the head gaps causing the tape to lose contact with the head. Use of the head cleaner will gently polish the

head and remove the dirt at the same time.

The azimuth alignment is a process which requires the user to locate a small screw near the play/record head. By adjusting this screw and with the aid of the indicator arrow, it is claimed to take only a matter of seconds to complete the necessary adjustment.

The package, which retails for £4.99, includes a combined head cleaner and azimuth tape, a screwdriver, indicator arrow and full instructions. In addition to the Amstrad CPC464 and Sinclair Spectrum, Kiltdale will be introducing further packages for the BBC, Commodore 64 and Atari machines during the next few months.

*Kiltdale Ltd.,
Dept EE, Liddington Industrial
Estate, Leckhampton Road,
Cheltenham,
Gloucs, GL53 0DL.*



The SL-XP7 Stereo CD Player is due for release on the UK market in November and is expected to sell for less than £300.

*Technics/Panasonic UK Ltd.,
Dept EE, 300-318 Bath Road,
Slough, Berkshire, SL1 6JB.*

PCB SERVICE

Printed circuit boards for certain EE constructional projects are now available from the EE PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: EE PCB Service, Everyday Electronics Editorial Offices, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Cheques should be crossed and made payable to IPC Magazines Ltd.

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed in the latest issue.

PROJECT TITLE	Order Code	Cost
— JULY '83 —		
User Port Input/Output <i>M.I.T. Part 1</i>	8307-01	£4.82
User Port Control <i>M.I.T. Part 1</i>	8307-02	£5.17
— AUGUST '83 —		
Storage Scope Interface, BBC Micro	8308-01	£3.20
Car Intruder Alarm	8308-02	£5.15
High Power Interface <i>M.I.T. Part 2</i>	8308-03	£5.08
Pedestrian Crossing Simulation <i>M.I.T. Pt 2</i>	8308-04	£3.56
— SEPTEMBER '83 —		
High Speed A-to-D Converter <i>M.I.T. Pt 3</i>	8309-01	£4.53
Signal Conditioning Amplifier <i>M.I.T. Pt 3</i>	8309-02	£4.48
Stylus Organ	8309-03	£6.84
— OCTOBER '83 —		
D-to-A Converter <i>M.I.T. Part 4</i>	8310-01	£5.77
High Power DAC Driver <i>M.I.T. Part 4</i>	8310-02	£5.13
— NOVEMBER '83 —		
TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i>	8311-01	£5.46
Stepper Motor Manual Controller <i>M.I.T. Part 5</i>	8311-02	£5.70
Speech Synthesiser for BBC Micro	8311-04	£3.93
— DECEMBER '83 —		
4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i>	8312-01	£5.72
4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i>	8312-02	£5.29
Environmental Data Recorder	8312-04	£7.24
Continuity Tester	8312-08	£3.41
— JANUARY '84 —		
Biological Amplifier <i>M.I.T. Part 7</i>	8401-02	£6.27
Temp. Measure & Control for ZX Compr	8401-03	£2.35
Analogue Thermometer Unit	8401-04	£2.56
Analogue-to-Digital Unit	8401-06/07	£9.60
Games Scoreboard		
— FEBRUARY '84 —		
Oric Port Board <i>M.I.T. Part 8</i>	8402-02	£9.56
Negative Ion Generator	8402-03*	£8.95
Temp. Measure & Control for ZX Compr	8402-04	£3.52
Relay Driver		
— MARCH '84 —		
Latched Output Port <i>M.I.T. Part 9</i>	8403-01	£5.30
Buffered Input Port <i>M.I.T. Part 9</i>	8403-02	£4.80
VIC-20 Extension Port Con. <i>M.I.T. Part 9</i>	8403-03	£4.42
CBM 64 Extension Port Con. <i>M.I.T. Part 9</i>	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro	8403-05	£4.63

*Complete set of boards.

M.I.T.—Microcomputer Interfacing Techniques, 12-Part Series.

†Four separate circuits.

— APRIL '84 —		
Multipurpose Interface for Computers	8404-01	£5.72
Data Acquisition "Input" <i>M.I.T. Part 10</i>	8404-02	£5.20
Data Acquisition "Output" <i>M.I.T. Part 10</i>	8404-03	£5.20
Data Acquisition "PSU" <i>M.I.T. Part 10</i>	8404-04	£3.09
A.F. Sweep Generator	8404-06	£3.55
Quasi Stereo Adaptor	8404-07	£3.56
— MAY '84 —		
Simple Loop Burglar Alarm	8405-01	£3.07
Computer Controlled Buggy <i>M.I.T. Part 11</i>		
Interface/Motor Drive	8405-02	£5.17
Collision Sensing	8405-03	£3.20
Power Supply	8405-04	£4.93
— JUNE '84 —		
Infra-Red Alarm System	8406-01	£2.55
Spectrum Bench PSU	8406-02	£3.99
Speech Synthesiser <i>M.I.T. Part 12</i>	8406-03	£4.85
Train Wait	8406-04	£3.42
— JULY '84 —		
Ultrasonic Alarm System	8407-01	£4.72
Electronic Code Lock		
Main Board	8407-03	£2.70
Keyboard	8407-04	£3.24
— AUGUST '84 —		
Microwave Alarm System	8408-01	£4.36
Temperature Interface—BBC Micro	8408-02	£2.24
— SEPTEMBER '84 —		
Op-Amp Power Supply	8409-01	£3.45
— OCTOBER '84 —		
Micro Memory Synthesiser	8410-01*	£8.20
Drill Speed Controller	8410-04	£1.60
— NOVEMBER '84 —		
BBC Audio Storage Scope Interface	8411-01	£2.90
Proximity Alarm	8411-02	£2.65
— DECEMBER '84 —		
TV Aerial Pre-Amp	8412-01*	£1.60
Digital Multimeter	8412-02/03*	£5.20
Mini Workshop Power Supply	8412-04	£2.78
Power Lighting Interface	8501-01	£8.23
Games Timer	8501-02	£1.86
Spectrum Amplifier	8501-03	£1.70
— JAN '85 —		
Solid State Reverb	8502-01	£3.68
Computerised Train Controller	8502-02	£3.38
— FEB '85 —		
— MARCH '85 —		
Model Railway Points Controller,	8503-01	£2.78
— APRIL '85 —		
Insulation Tester	8504-02	£2.53
Fibrealarm	8504-03	£3.89
Auto Phase	8505-01	£3.02
Amstrad CPC464 Amplifier		
Mains Unit	8505-02	£2.56
Micro Unit	8505-03	£2.56
Voltage Probe	8505-04	£2.67
— MAY '85 —		
— JUNE '85 —		
Graphic Equaliser	8506-01	£3.21
Computerised Shutter Timer	8506-02	£2.09
Mono-Bi-Astables (Experimenters Test Bed)	8506-03	£2.45
Across The River	8506-04	£2.63
— JULY '85 —		
Amstrad User Port	8507-01	£3.17
Nascom Printer Handshake	8507-02	£1.90
— AUGUST '85 —		
Electronic Building Blocks—1 to 4†	8508-01	£2.98
Tremolo/Vibrato	8508-02	£4.03
Stepper Motor Interface	8508-03	£2.40
Drill Control Unit	8508-04	£2.90
— SEPTEMBER '85 —		
RIAA Preamp Input Selector	8509-01	£2.36
Transducers Resistance Thermometer	8509-03	£2.64
Transducers Semiconductor Temp. Sensor	8509-04	£2.72

EVERYDAY ELECTRONICS and computer PROJECTS

Reach effectively and economically today's enthusiasts anxious to know of your products and services through our semi-display and classified pages. Semi-display spaces may be booked at £7.80 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 33 pence per word (minimum 12 words), box number 60p extra. All cheques, postal orders, etc., to be made payable to Everyday Electronics and Computer Projects and crossed "Lloyds Bank Ltd." Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Department, Everyday Electronics and Computer Projects, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5846).

Receivers & Components

PRINTED CIRCUIT BOARDS made to own requirements, also some assembly work of boards undertaken. Send for details with requirements. B. M. ANSBRO, 38 Poynings Drive, Hove, Sussex.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-584188. Immediate settlement.

Service Sheets

BELL'S TELEVISION SERVICE for service sheets on Radio, TV etc. £1.50 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to: BTS, 190 King's Road, Harrogate, N. Yorkshire. Tel: 0423 55885.


SOLE SUPPLIERS TV/Video repair manuals/circuits. 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/M. centres/stereos £3.50 LSAE with every order/query please brings free pricelist/magazine inc s/sheet - or phone 0698 884585 (883334 outwith business hours) TIS(E) 76 Church Street Larkhall Lanarkshire.

Miscellaneous

FREE!! Electronic components plus catalogue. Send £1 p&p. E.C.P.S., 7, Harehill Crescent, Wingerworth, Chesterfield S42 6SS.

MAKE HYDROGEN GAS BALLOONS for flying aerals/weather experiments, etc. Kit £10.00 postage free. Note: you will need two one gallon demijohns to complete. Send to M. H. COUNSELL, 51 Kemp-ton Grove, F.G.L. Cheltenham, Gloucestershire.

LEARN
**ELECTRONICS WITHOUT
SOLDER**

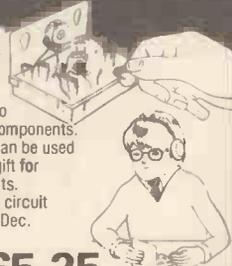

Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experiments. Full instructions and 2 circuit diagrams with each S-Dec.

Send Cheque or P.O. to:
Roden Products, Dep EE
High March, Coventry,
Northants, NN11 4DE

£5.25 including p & p

Tuition

IMPROVE YOUR PROSPECTS
With skills that are in demand. Learn the easy way with a Modern Home Study Course in:

ELECTRONICS

Train for a success in the fastest ever growing Industrial Sector. Course includes topics such as: Simplified Circuit Theory, Resonance, Transistor Amplifiers, Filters and Non-Linear Wave Shaping, Digital Circuits, Micro-Computers etc. (Use our course to help prepare for BTEC or C&G examinations.)

Write or telephone today for Free Prospectus - No Obligation
IDEAL SCHOOLS Ref: EE1
60 St. Enoch Square, Glasgow G1, UK.
or Tel: 041-248 5200

Software

Advanced Computer tapes for the ZX SPECTRUM 48k

1. Dialogue tape uses a very modern artificial intelligence using specially developed codes which tie together over 2000 words.
2. Electronics design tape. Input is a basic spec. Outputs Circuit diagram and PCB layout.

Cost inc. P/P is £10 each
CWO to **N. J. Edwards,**
68 Woodhill Rise, Costessey, Norwich, Norfolk NR5 0DW

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for Insertions. I enclose Cheque/P.O. for £.....
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)

HEADING REQUIRED:

NAME

ADDRESS

.....

.....

EVERYDAY ELECTRONICS and COMPUTER PROJECTS

Classified Advertisement Dept., H.H.,
King's Reach Tower, Stamford Street, London SE1 9LS
Telephone 01-261 5846

Rate: 33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

9/85

A COMPLETE SECURITY SYSTEM FOR ONLY £39.95 + V.A.T.

- Control Unit CA 1250
- Enclosure HW 1250
- Key Switch & 2 keys KS 3901
- L.E.D.'s LED 1
- 5 1/2" Horn Speaker HS 588
- 4 quality surface Magnetic Switches MS 1025



With only a few hours of your time it is possible to assemble and install an effective security system to protect your family and property, at the amazingly low cost of £39.95 + V.A.T. No compromises have been made and no corners have been cut. The outstanding value results from volume production and direct supply. Assembly is straight forward with the detailed instructions provided. When installed you can enjoy the peace of mind that results from a secure home. Should you wish to increase the level of security, the system may be extended at any time with additional magnetic switches, pressure pads or ultrasonic sensors. Don't wait until it's too late - order today. Order code CS 1370

- CA 1250 - 2 zone alarm control unit with built in alarm & power supply £19.95 + V.A.T.
- HW 1250 Enclosure & Hardware Kit for above £9.50 + V.A.T.
- LED 1 - Set of 4 l.e.d.'s in chrome bezels + Push Switch to fit HW 1250 £2.15 + V.A.T.
- KS 3901 - 3 position Key Switch £3.43 + V.A.T.
- HS 588 - 5 1/2" Horn Speaker, output of 110db's with CA 1250 or SL 157 £4.95 + V.A.T.
- US 5063 - advanced Digital Ultrasonic Detector, high sensitivity, with false alarm suppression £13.95 + V.A.T.
- SC 5063 - Enclosure for US 5063 £2.95 + V.A.T.
- IR 1470 - Infra-red system to provide 50' invisible beam, includes both transmitter and receiver £25.61 + V.A.T.
- SL 157 - Siren Module 12V £2.95 + V.A.T.

Wide range of modules and accessories, etc. Send S.A.E. for details.

Add 15% VAT to all prices
Add 70p post and packing to all orders
Units on demonstration
Shop hours 9.00 to 5.30 p.m.
Closed Wednesday
Please allow 7 days for delivery

Saturday 9.00 to 1.00 p.m.
S.A.E. with all enquiries
Order by telephone or post using your credit card

SELF-CONTAINED ULTRASONIC UNIT CK 5063



Requires no installation. Easily assembled using our professionally built and tested modules.

- Adjustable range up to 25 ft.
- Built-in entrance and exit delay
- Built-in timed alarm
- Key operated switch - Off, Test and Operate only
- Provision for an extension speaker
- Fully self-contained £37.00 + V.A.T.
- Uses US 5063, PSL 1865 Key Switch
- 3901, 3" Speaker 3515

Now you can assemble a really effective intruder alarm at this low price using tried and tested Riscomp modules. Supplied with full instructions, the kit contains everything necessary to provide an effective warning system for your house or flat. With a built-in LED indicator and test position the unit is easily set-up requiring no installation. It may simply be placed on a cupboard or desk. Movement within its range will then cause the built-in siren to produce a penetrating 900db's of sound, or even 110db's with an additional speaker. All parts included and supplied with full instructions for ease of assembly. Size 200 x 180 x 70mm Order as CK 5063

RISCOMP LIMITED

Dept EE32,
51 Poppy Road,
Princes Risborough,
Bucks. HP17 9DB
Princes Risborough (084 44) 6326



Cirkit Out Now! Out Now! Cirkit

ELECTRONIC COMPONENTS CATALOGUE

Over 4,000 different items

- ★ Available from leading newsagents throughout the country
- ★ Many new products including a range of computer add-ons, calculators, soldering irons, plus new tools, kits and modules.
- ★ Innovative new kits . . . Heart rate monitor . . . weather satellite receiver

BUY IT NOW!

Cirkit Holdings PLC Park Lane Broxbourne Hertfordshire EN10 7NQ Telephone: Hoddesdon (0992) 444111

TELEVISION/COMPUTER FULL-TIME TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN EDUCATION COUNCIL)

2 YEAR BTEC National Diploma (OND)

ELECTRONIC & COMMUNICATIONS ENGINEERING

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate (ONC)

ELECTRONIC EQUIPMENT SERVICING

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS

BTEC National Certificate (ONC)

COMPUTING TECHNOLOGY

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS

BTEC Higher National Certificate (HNC)

COMPUTING TECHNOLOGY & ROBOTICS

(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

SHORTENED COURSES OF FROM 3 TO 6 MONTHS CAN BE ARRANGED FOR APPLICANTS WITH PREVIOUS ELECTRONICS KNOWLEDGE

NEXT SESSION TO COMMENCE ON SEPTEMBER 16th

FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE (Dept EE)
20 PENYWERN ROAD, EARLS COURT,
LONDON SW5 9SU. Tel: 01-373 8721.

Master Electronics - Microprocessors - Now! The Practical Way!

- Electronics - Microprocessors - Computer Technology is the career and hobby of the future. We can train you at home in a simple, practical and interesting way.



- Recognise and handle all current electronic components and 'chips'.
- Carry out full programme of experimental work on electronic computer circuits including modern digital technology.
- Build an oscilloscope and master circuit diagram.
- Testing and servicing radio - T.V. - hi-fi and all types of electronic/computer/industrial equipment.

New Job? New Career? New Hobby?

SEND THIS COUPON NOW.

FREE! COLOUR BROCHURE

Please send your brochure without any obligation to

OR TELEPHONE US 062 67 6114
OR TELEX 22758 (24 HR SERVICE)



NAME _____ I am interested in

ADDRESS _____ ELECTRONICS

MICROPROCESSORS

RADIO AMATEUR LICENCE

CITY & GUILDS EXAMS

Other Subjects _____

British National Radio & Electronics School P.O. Box 7, Teignmouth, Devon, TQ14 0HS

CMOS	4095	580	74LS76	28p	74LS266	28p	PL95	140p	VOLTAGE REGULATORS	HA-1197	150p
4000	16p	4098	74LS78	34p	74LS273	72p	PL500	110p		HA-1306W	170p
4001	16p	4099	74LS83	46p	74LS279	46p	PL504	95p		HA-1319V	250p
4002	16p	4501	74LS85	50p	74LS280	140p	PL508	170p		HA-1339V	170p
4006	50p	4503	74LS90	30p	74LS290	30p	PL519	450p	7805	HA-1342	170p
4007	18p	4504	74LS91	75p	74LS293	30p	PV81	70p	7812	HA-1366WR	160p
4008	44p	4505	74LS92	46p	74LS296	44p	PY88	46p	7818	HA-1366	160p
4009	30p	4506	74LS93	40p	74LS299	43p	PY500A	150p	7824	HA-1377	220p
4010	32p	4507	74LS94	40p	74LS368	41p			7912	HA-1389	140p
4011	16p	4508	74LS95	52p	74LS373	68p			7915	HA-1392	230p
4012	16p	4510	74LS96	53p	74LS374	68p	7400		7918	HA-1397	250p
4013	20p	4511	74LS97	43p	74LS375	74p	7401		7924	HA-1398	240p
4014	40p	4512	74LS109	36p	74LS399	80p	7402		7815	HA-1201	85p
4015	40p	4513	74LS112	38p	74LS670	80p	7403		7816	LA-1352	120p
4016	27p	4515	74LS113	32p			7404		7817	LA-1365	140p
4017	40p	4516	74LS114	38p			7405		7818	LA-1365	120p
4019	33p	4517	74LS122	44p	DAF96	60p	7407		7819	LA-3301	120p
4020	50p	4518	74LS123	49p	EAB080	50p	7417		7824	LA-3361	115p
4021	50p	4519	74LS124	85p	DF96	50p	7428		7912	LA-4030	200p
4022	45p	4520	74LS125	36p	DF97	50p	7432		7915	LA-4031	140p
4023	16p	4521	74LS126	42p	DY802	45p	7414		LM309K	LA-4032	140p
4024	30p	4522	74LS132	44p	EAB080	50p	7417		LM317K	LA-4050	130p
4025	16p	4523	74LS133	34p	EB1	44p	7420		LM317T	LA-4051	160p
4026	58p	4527	74LS136	38p	EF80	26p	7421		LM322K	LA-4100	120p
4027	30p	4528	74LS138	38p	EF89	50p	7425		LM332	LA-4101	100p
4028	38p	4529	74LS139	40p	EC082	40p	7430		78H05KC	LA-4102SK	140p
4029	50p	4532	74LS145	53p	EC083	43p	7437		78G11C	LA-4112	250p
4030	78p	4551	74LS147	100p	EC084	45p	7442		78G11C	LA-4126	210p
4031	100p	4553	74LS148	110p	EC085	40p	7447		79H05K	LA-4140	70p
4032	54p	4555	74LS151	38p	EC081	49p	7450		79H05K	LA-4201	120p
4033	60p	4557	74LS154	100p	EC082	52p	7451		LA-4220	LA-4220	120p
4034	85p	4559	74LS155	51p	EC082	57p	7454		AN-214P	LA-4420	140p
4035	50p	4563	74LS156	49p	EC084	52p	7470		AN-240P	LA-4422	130p
4036	220p	4584	74LS157	35p	EC085	57p	7474		AN-360	LA-4430	130p
4037	60p	4585	74LS158	47p	EC086	49p	7475		AN-7110	LA-4460	170p
4038	50p	74LS160	52p	EF80	31p	7481		AN-7114	LA-4461	180p	
4039	220p	74LS161	56p	EF85	34p	7482		AN-7115	LA-5112	120p	
4040	42p	74LS162	50p	EF89	43p	7485		AN-7120	LM301	26p	
4041	38p	74LS163	45p	EF83	45p	7486		AV3-1270	LM311	35p	
4042	43p	74LS164	44p	EF184	53p	7489		AV3-1350	LM324	35p	
4043	40p	74LS165	65p	EL34	190p	7490		AV3-8910	LM325	45p	
4044	72p	74LS166	80p	EL36	60p	7492		AV3-8912	LM339	40p	
4045	49p	74LS168	56p	EL84	50p	7493		AV5-3800	LM348	50p	
4046	49p	74LS169	70p	EL95	50p	7495		CA270	LM380	100p	
4047	32p	74LS170	85p	EL500	80p	7497		CA3046	LM381	150p	
4048	26p	74LS171	40p	EL504	100p	74107		CA3048	LM382	130p	
4049	26p	74LS172	46p	EL505	31p	74111		CA3080	LM387	180p	
4050	42p	74LS173	59p	EL507	31p	74116		CA3080E	LM708 DIL	30p	
4051	40p	74LS174	55p	EL508	32p	74119		CA3086	LM723	40p	
4052	40p	74LS175	50p	EL509	45p	74122		CA3088E	LM741 DIL	18p	
4053	40p	74LS176	57p	EL510	50p	74123		CA3090A	LM741 MET	45p	
4054	58p	74LS177	57p	EL511	55p	74125		CA3130E	LM747	58p	
4055	58p	74LS178	56p	G234	180p	74126		CA3130S	LM748	35p	
4056	53p	74LS179	67p	PC97	100p	74132		CA3140E	LM1458	33p	
4057	57p	74LS180	62p	PC95	49p	74141		CA3189E	LM3900	30p	
4058	30p	74LS181	61p	PCF80	58p	74145		HA-1156W	M-5151JL	180p	
4059	160p	74LS182	62p	PCF200	135p	74153					
4060	15p	74LS183	60p	PCF801	110p	74155					
4061	16p	74LS184	70p	PCF802	57p	74157					
4071	16p	74LS185	64p	PCF806	115p	74160					
4072	16p	74LS186	64p	PCF200	106p	74164					
4073	16p	74LS187	78p	PCL81	54p	74167					
4074	16p	74LS188	50p	PCL82	53p	74173					
4076	50p	74LS189	50p	PCL84	50p	74174					
4077	16p	74LS190	92p	PCL85	55p	74175					
4078	16p	74LS191	30p	PCL86	55p	74176					
4081	16p	74LS192	59p	PCL805	59p	74180					
4082	16p	74LS193	65p	PFL200	85p	74182					
4085	42p	74LS194	48p	PL26	80p	74192					
4086	34p	74LS195	45p	PL82	45p	74196					
4089	30p	74LS196	52p	PL83	52p	74197					
4093	26p	74LS197	42p	PL84	50p	74353					

CRICKLEWOOD ELECTRONICS LTD

It's no secret!

that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LTD.
40 Cricklewood Broadway NW2 3ET.
01-450 0995 & 01-452 0161
ALL MAJOR CREDIT CARDS ACCEPTED
Telex 914977 Phone or write today

FREE Catalogue

NOW! SUMMER CATALOGUE

OVERSEAS ORDERS

Overseas readers are reminded that unless otherwise stated, postage and packing charges published in advertisements apply to the United Kingdom only.

Readers wishing to import goods from the United Kingdom are advised to first obtain from the advertiser(s) concerned an exact quotation of the cost of supplying their requirements carriage paid home.

LASER ALERT

CAR ALARM SYSTEM

Quick and easy to install, protect your car for as little as **£14.99** (inc. P+P)

with our simple security system.

Complete installation instructions

Cheques/Postal-orders to:-

Laser Alert
1, Noble Villas,
Sewardstone Road,
Waltham Abbey, Essex EN9

INDEX TO ADVERTISERS

B K Electronics	468
B.N.R.E.S.	519
Bull J.	485
Cirkit Holdings	519
C P L Electronics	468
Cricklewood Electronics	520
Croydon Discount Electronics	468
Edwards, N.J.	518
Electrovalve	468
Flight Electronics	I.B.C.
Grandata	520
Greenweld	466
ICS Intertext	466
Ideal Schools	518
London Electronics College	519
Magenta Electronics	470
Maplin Electronics	O.B.C.
Marco Trading	509
Portasol	520
Radio Components Specialists	515
Rapid Electronics	467
Riscomp Ltd	466 & 519
Roden Products	518
T.K. Electronics	509

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by McCorquodale Magazines Ltd., Andover, Hants. sole Agents for Australia and New Zealand - Gordon and Gotch (Asia) Ltd.; South Africa - Central News Agency Ltd. Subscriptions INLAND £13 and OVERSEAS £15 payable to IPC Magazines Ltd., "Everyday Electronics" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. EVERYDAY ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



The NEW educational product range from Flight Electronics Ltd, all of which may also be used as low cost development systems for engineers working on low budgets.

1 DT-01 Digital Trainer

For breadboarding, digital circuits, flip-flops and monostable multivibrators, counters, encoders, decoders, multiplexers, demultiplexers and sequencers, registers, LED and 7 SEGMENTS LED displays, memory devices, etc.

SPECIFICATION

AC ADAPTOR JACK: I/P DC +12V, 800mA.
 POWER SW: AC ADAPTOR.
 BATTERY, 1.5V x 4
 PULSE SW: Two bounce-free pushbuttons.
 LOGIC SW: Eight logic level switches in DIP type.
 DC O/P: DC +5V, 750mA for user.
 B-023 BREADBOARD: Solderless breadboard with 1580 interconnected tie points.
 CLIP TERMINAL: Logic probe clip terminal.
 BATTERY HOLDER: 1.5V x 4.
 LED DISPLAY: Eight LED buffered logic level indicators.
 BNC JACKS.
 SELECT SW: Clock range selection.
 LOW: 10 - 40 HZ.
 HIGH: 1K - 20K HZ.
 BANANA JACKS.
 CLOCK ADJ: Fine adj. of clock frequency.
 Includes Logic Probe.

2 MPF-1/88

SPECIFICATION

MICROPROCESSOR: 16 bit CPU, Intel 8088, 4.77 MHz version with an 8-bit data bus.
 RAM MEMORY: 4K standard RAM on two 2K byte RAM chips. Expandable to 24K by using three 8K byte RAM chips.
 ROM MEMORY: 16K standard ROM on two 8K byte ROM chips. Expandable to 48K by using three 16K byte ROM chips.
 ROM memory contains program code for the monitor, line assembler, and disassembler.
 DISPLAY SCREEN: 20 character x 2 line LCD display shows any 2 lines of a 20 character x 24 line logical screen.
 KEYBOARD: 59-key, full-size QWERTY keyboard.
 PRINTER INTERFACE: Centronics standard parallel interface with 16-pin connector.
 CASSETTE INTERFACE: Can be used with any monaural cassette recorder.
 RECORDING SPEED: 1000-2000 bits/second.
 BUS CONNECTOR: 62-pin IBM

3 MPF-1/65

SPECIFICATION

ADVANCED INTERACTIVE MONITOR: The heart of the MPF-1/65 software resides in 16K bytes of ROM.
 DISASSEMBLER: The built-in disassembler allows the user to list 6502 microprocessor instructions on both printer and video display.
 SCREEN EDITOR.
 TEXT EDITOR.
 TWO PASS ASSEMBLER.
 PRINTER DRIVER.
 DEBUGGING FEATURES.
 INPUTS AND OUTPUTS
 AUDIO SPEAKER.
 AUDIO CASSETTE INTERFACE: 1000-Baud
 PARALLEL PRINTER INTERFACE: Centronics/EPSON
 VIDEO MONITOR INTERFACE.
 COLOUR TV INTERFACE.
 SYSTEM EXPANSION CONNECTOR: 50 pin connector to provide interface with RS-232c or ROM cartridges.
 KEYBOARD: Standard calculator 49 key keyboard with 153 ASCII codes.
 PROFESSIONAL DOCUMENTATION: User's Manual and Monitor Source Code Listing Manual are standard.

4 MPF-1P

SPECIFICATION

Z80 CPU high performance microprocessor with 158 instructions.
 4K RAM, Battery Back-up circuits provided for the user to keep the contents of the RAMS.
 8K ROM, sophisticated monitor expandable to 16K.
 8K of sophisticated monitor, including text editor, two pass assembler, line assembler, break point, system initialization, keyboard scan, display scan, tape write and tape read, register and memory modification, insert, delete, move relation, fill and step execution.
 20 digits, 14-segment green phosphorescent display.
 49-key alphanumeric keyboard including editing and functional keys.
 Audio cassette interface: 165 baud average rate for data transfer between memory and cassette
 Extension connectors: all CPU buses usable for expansion.
 2.25" diameter speaker.
 9V, 1.0A adaptor provided.
 Three complete self-learning textbooks with experiments and applications.

5 MPF-1B

SPECIFICATION

CPU: Z80 CPU high performance microprocessor with 158 instructions.
 RAM: 2K bytes expandable to 4K bytes.
 ROM: 2K bytes of sophisticated monitor expandable to 8K bytes.
 INPUT/OUTPUT: 24 system I/O lines.
 MONITOR: 2K bytes of sophisticated monitor. Monitor includes system initialization, keyboard scan, display scan, tape write and tape read.
 DISPLAY: 6-digit, 0.5" red LED display.
 AUDIO CASSETTE INTERFACE: 165-Baud
 EXPANSION FACILITY: Z80-P10 16 uncommitted lines. Z80-CTC 4 uncommitted timer channels.
 USER AREA: Provides a 3.5" x 1.36" wire wrapping area for user's expansion.
 POWER REQUIREMENT: 9V, 1.0A adaptor is provided.
 KEYBOARD: 36 keys including 19 function keys, 16 hex digit keys, and 1 user-defined key.

Multitech

FLIGHT ELECTRONICS LTD

Flight House, Quayside Road, Bitterne Manor, Southampton, Hampshire SO2 4AD.
 Telephone (0703) 34003/227721. Telex 477793 KEMP SA G.

More This Month at Maplin

Colour-coded IDC cables

- 16-way (XR80B) ONLY 32p per metre.
- 20-way (XR81C) ONLY 40p per metre.
- 26-way (XR82D) ONLY 54p per metre.
- 34-way (XR83E) ONLY 70p per metre.
- 40-way (XR84F) ONLY 82p per metre.
- 50-way (XR85G) ONLY 99p per metre.

4-way flat flexible telephone lead (XR86T) ONLY 18p per metre.

Stepper motor 48 steps/rev, 12V 0.13A per phase, 4-phase unipolar, 57g, working torque 8mNm max. ONLY £9.95 (FT73G).

Driver chip for motor: SAA1027 ONLY £3.75 (QY76H).

★SAVE★ 1 Kit containing everything you need: motor, SAA1027, data sheet and passives ONLY £13.35 (LK76H).

Sounds Terrific



Professional Quality High Power Loudspeakers featuring:

- ★ Virtually indestructible high-temperature voice-coil reinforced with glass-fibre.
- ★ 100% heat overload tolerance.
- ★ Advanced technology magnet system.
- ★ Rigid cast alloy chassis.
- ★ Linen or Plastiflex elastomer surrounds.
- ★ 5-year guarantee (in addition to statutory rights).

Prices from £18.95.

Send S.A.E. for our free leaflet XH62S.

Top Ten Kits



THIS/LAST

MONTH	DESCRIPTION	CODE	PRICE	BOOK
1. (1)	Live-Wire Detector	LK63T	£2.95	14 XA14Q
2. (2)	75W Mosfet Amp.	LW51F	£15.95	Best E&MM
3. (3)	Car Burglar Alarm	LW78K	£7.49	4 XA04E
4. (4)	Partyline	LW93B	£10.95	Best E&MM
5. (5)	U/Sonic Intruder Dcttr	LW83E	£10.95	4 XA04E
6. (6)	8W Amplifier	LW36P	£4.95	Catalogue
7. (10)	Logic Probe	LK13P	£10.95	8 XA08J
8. (8)	Syntorm Drum Synth.	LW86T	£12.95	Best E&MM
9. (9)	Computadrum	LK52G	£9.95	12 XA12N
10. (7)	Light Pen	LK51F	£10.95	12 XA12N

Over 100 other kits also available. All kits supplied with instructions. The descriptions above are necessarily short. Please ensure you know exactly what the kit is and what it comprises before ordering, by checking the appropriate Project Book mentioned in the list above.

Is it a turtle? Is it a robot? Is it a buggy? Yes! it's Zero 2.



- May be used by any computer with RS232 facility.
- Stepper Motor controlled.
- Half millimetre/half degree resolution.
- Uses ordinary felt-tip pens.
- Built-in 2-tone horn, line-follower. LED indicators.

The Zero 2 Robot is the first truly micro robotic system available and remarkably it costs less than £80. Complete kit (only mechanical construction required) £79.95 (LK66W). Full details of power supply and simple interfacing for BBC, Commodore 64 and Spectrum, in Maplin Magazine 15 price 75p (XA15R).

MAPLIN

MAPLIN ELECTRONIC SUPPLIES LTD

Mail-order: P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 552911

SHOPS

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356-7292.
- LONDON 159-161 King Street, Hammersmith, W6. Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevoisy Valley Road. Tel: 0703-225831
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex. Telephone: 0702-554000. *Shops closed all day Monday.*

More Choice In Multimeters



A new range of very high quality multimeters offering truly amazing quality at the price.

Pocket Multimeter, 16 ranges, 2,000Ω/V DC/AC £6.95 (YJ06G)

M-102BZ with continuity buzzer, battery tester and 10A DC range, 23 ranges, 20,000Ω/V DC £14.95 (YJ07H)

M-2020S with transistor, diode and LED tester and 10A DC range, 27 ranges, 20,000Ω/V DC £19.95 (YJ08J)

M-5050E Electronic Multimeter with very high impedance FET input, 53 ranges, including peak-to-peak AC, centre-zero and 12A AC/DC ranges £34.95 (YJ09K)

M-5010 Digital Multimeter with 31 ranges including 20Ω and 20μA DC/AC FSD ranges, continuity buzzer, diode test, and gold-plated pcb for long-term reliability and consistent high accuracy (0.25% +1 digit DCV) £42.50 (YJ10L)



The Maplin Service

All in-stock goods despatched same day for all orders received before 2.00 pm.

All our prices include VAT and carriage (first class up to 750g).

A 50p handling charge must be added if your total order is less than £5.00 on mail-order (except catalogue).



☎ Phone before 2.00 p.m. for same day despatch

1985 CATALOGUE

Pick up a copy now at a branch of W.H. Smith* or in one of our shops. Price £1.35, or by post £1.75 from our Rayleigh address (quote CA02C).

*Some branches are now out of stock.

All offers subject to availability. Prices firm until 9th November 1985.

