

# EVERYDAY **ELECTRONICS** and **ELECTRONICS** MONTHLY

SEPTEMBER 1986

£1.10



**INFRA-RED  
BEAM ALARM**

---

**SCRATCH BLANKER**

---

**FREEZER FAILURE ALARM**

---

**SIMPLE PRINTER BUFFER**

---

**Newcomers Magazine for Electronic & Computer Projects**



## £1 BAKERS DOZEN PACKS

Price per pack is £1.00.\* Order 12 you may choose another free. Items marked (sh) are not new but guaranteed ok.

1. 5-13 amp ring main junction boxes
2. 5-13 amp ring main spur boxes
3. 5- surface mounting switches suitably insulated for mains voltage
4. electrical switches intermediate type, will also replace 1 or 2 way switches, white flush mounting
5. 4- in flex line switches with neons
6. 2- mains transformers with 6V 1A secondaries
7. 2- mains transformers with 12V 1A secondaries
8. 1- extension speaker cabinet for 8Ω speaker
9. 12- glass reed switches
10. 2- ultra transmitters and 2 receivers with circuit
11. 2- light dependent resistors
12. 4- wafer switches - 6p 2 way, 4p 3 way, 2p 6 way, 2p 5 way, 1p 12 way small one hold frong and good plating 1/2 spindle your choice
13. 1- 6 digit counter mains voltage
14. 2- Nicad battery chargers
15. 1- key switch with key
16. 2- aerosol cans of ICI Dry Lubricant
17. 96- 1 metre lengths colour-coded connecting wire
18. 1- long and medium wave radio fuses
19. 4- rocker switch 10 amp mains SPST
20. 1- 24 hour time switch mains operated (s.h.)
21. 2- 6V operated reed switches
22. 10- neon valves - make good night lights
23. 2- 12V DC or 24V AC, 3 CD relays
24. 1- 12V 2 CD miniature relay very sensitive
25. 1- 12V 4 CD miniature relay
26. 2- mains operated relays 3 x 6 amp changeover (s.h.)
27. 10- rows of 32 gold plated sockets (total 320 sockets)
28. 1- locking mechanism with 2 keys
29. 1- miniature unswitched with circuit for electric jigsaw puzzle
30. 5- ferrite rods 4" x 5/16" diameter aerials
31. 4- ferrite slab aerials with L & M wave coils
32. 1- Mullard thyristor trigger module
33. 10- assorted knobs & spindles
34. 5- different thermostats, mainly bi-metal types
35. 1- magnetic brake - stops rotation instantly
36. 1- low pressure 3 level switch can be mouth operated
37. 2- 25 watt pots 8 ohm
38. 2- 25 watt pots 1000 ohm
39. 7. 4- wire wound pots - 18, 33, 50 and 100 ohm your choice
40. 1- 1250 watt dimmer ultra ref SE20
41. 1- time reminder adjustable 1-60 mins clockwork
42. 2- 30A panel mounting 5 pin fuses
43. 2- mains shaded pole motor 1/3" stack - 1/2 shaft
44. 1- mains motor with gear box 1 rev per 24 hours
45. 2- mains motors with gear box 16 rpm
46. 1- thermostat for fridge
47. 1- motorised stud switch (s.h.)
48. 1- 2 1/2 hours delay switch
49. 1- mains power supply unit - 6V DC
50. 1- mains power supply unit - 4V DC
51. 1- 5 pin flex plug and panel socket
52. 1- 5" speaker 5Ω with 1/2" stack with handle
53. 10- slider type volume controls
54. 2- musical boxes (less keys)
55. 1- heating pad 200 watts mains
56. 1- FM front end with tuning condenser and data
57. 1- 1W amplifier Mullard type
58. 1- wall mounting thermostat 24V
59. 1- teak effect extension 5" speaker cabinet
60. 2- p.c. boards with 2 amp full wave and 17 other recs.
61. 4- push push switches for table lamps etc.
62. 10- mis-tune screwdriver flex white p.v.c. outer
63. 100- staples for thin flex
64. 25- clear plastic lenses 1 1/2 diameter
65. 4- pilot bulb lamp metal clip on type
66. 10- very fine drills for jobs etc.
67. 4- extra thin screw driver for instruments
68. 2- plastic boxes with windows, ideal for interrupted beam switch
69. 10- model aircraft motor - require no on/off switch, just spin to start
70. 2- car radio speakers 5" round 4 ohm made for Radiomobile
71. 1- 6 1/2" 4 ohm 10 watt speaker and 3" tweeter
72. 10- 4 BA spanner bits 25A 250V
73. 2- 4 reed relay kits 3V coil normally open or c/o if magnets added
74. 20- pilot bulbs 6.5V 3A Philips
75. 1- secret switch kit with data
76. 4- socket covers (protect inquisitive little fingers) for twin 13A
77. 1- air or gas shut off valve - inoperative test operated
78. 1- air or gas shut off valve - manual test operated
79. 1- 12V drip proof relay - ideal for car jobs
80. 3- varicap push button tuners with knobs
81. 5- 12 way connector blocks 2A 250V
82. 3- 12 way connector blocks 25A 250V
83. 1- 13A fused and switched spur for surface mounting or can be removed from box for flush mounting
84. 3- 13A sockets good British make but brown
85. 4- short wave air spaced trimmers 2-30"
86. 1- oscillating car kit with data - have fun with this
87. 10- 12V 6W bulbs Philips m.e.s.
88. 3- oblong amber indicators with 1/16" 12V
89. 6- round amber indicators with neons 240V
90. 100- p.v.c. grommets 1/4 hole size
91. 1- short wave tuning condenser 40 pf with 1/2" spindle
92. 1- three gang tuning condenser each section 500 pf with trimmers and good length 1/2" spindle
93. 1- plastic box stoping metal front, 18 x 95mm average depth 45mm
94. 2- double pole 20 amp 250V flush mounting switch - white
95. 6- B.C. lamp holder adaptors white
96. 5- 5 amp 3 pin flush sockets brown
97. 5- B.C. lampholders brown bakelite threaded entry
98. 1- in flex summerstat for electric blanket soldering iron etc.
99. 2- thermostats, spindle setting, adjustable range for ovens etc.
100. 1- mains operated solenoid with plunger 1" travel
101. 10- 10 digit switch pad for telephones etc
102. 6- computer keyboard switches with knobs, pcb or vero mounting
103. 20- 20 mtrs 80 ohm, standard type co-ax off lead
104. 1- electric clock mains driven, always night time - not cased
105. 2- stereo pre-amp Mullard EP9001
106. 2- 12V solenoids, small with plunger
107. 1- mains transformer 9V 1 amp secondary C core construction
108. 1- car door speaker (very flat) 8Ω 15 ohm made for Radiomobile
109. 2- speakers 6" x 4" 4 ohm 5 watt made for Radiomobile
110. 2- speakers 6" x 4" 16 ohm 5 watt made for Radiomobile
111. 1- mains motor with gear-box very small, toothed output 1 rpm
112. 4- standard size pots, 1 meg with dp switch
113. 1- 13A switched socket on double plate with fused spur for water heater
114. 1- mains transformer 2V 1A secondary split primary so ok also for 115V
115. 2- 15V transformers 15V 1A secondary p.c.b. mounting
116. 50 3.5V torch bulbs
117. 3 7" reel to reel tape spools
118. 1 ten turns 3 watt pot 1/2 spindle 100 ohm
119. 2 two plate brown bakelite calling roses
120. 50 silicon diodes mixed unmarked
121. 50 Germanium transistors mixed and unmarked
122. 10 round pointer knobs 1/2 spindle
123. 3 car cigar lighter socket plugs
124. 1 cover for 24hr time switch ref BD45
125. 2 15 amp round pin plugs brown bakelite
126. 1 mains solenoid with plunger compact type ceramic magnets Mullard 1" x 3/8 x 5/16
127. 1 12 pole 3 way ceramic wave charge switch
128. 1 stereo amp 1 watt per channel
129. 1 tubular dynamic microphone with desk rest
130. 1 module, speaker & battery to make musical card
131. 5 thermal fuses 15 amp woods metal
132. 1 T.V. turret tuner (black & white T.V.)
133. 12 adaptable legended knobs 1/2 spindle
134. 2 over thermostats
135. 1 Clare Elliot sealed relay 12V
136. 1 pressure pad switch 24 x 18 (Trigger Mat)
137. 5 sub miniature micro switches
138. 1 12" 8 watt min fluorescent tube white
139. 1 6" 4 watt min fluorescent tube white
140. 1 round pin kettle plug with moulded on lead

## MULLARD UNILEX AMPLIFIERS

We are probably the only firm in the country with these now in stock. Although only four watts per channel, these give superb reproduction. We now offer the 4 Mullard modules - i.e. Mains power unit (EP9002) Pre amp module (EP9001) and two amplifier modules (EP9000) all for £6.00 plus £2 postage. For prices of modules bought separately see TWO POUNDERS.

## CAR STARTER/CHARGER KIT

Flat Battery! Don't worry you will start your car in a few minutes with this unit - 250 watt transformer 20 amp rectifiers, case and all parts with data £16.50 or without case £15.00 post paid.

## VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95 without case, metal case - £2.95, adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

## SOUND TO LIGHT UNIT

Complete kit of parts of a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form.

## 12 volt MOTOR BY SMITHS

Made for use in cars, etc. these are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/2" spindle - 1/10 hp £3.45 1/8 hp £5.75 1/6 hp £7.50

## 25A ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake - switch on lights to ward off intruders - have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. A beautiful unit at £2.50

## THIS MONTH'S SNIP

is a Prestel Unit, brand new and complete except for some ICs, also we understand tested, so should work OK directly the missing chips are fitted. Supplied complete with handbook and keypad at only £5. It's a bargain that should not be missed, even if you don't want to use it for its original purpose. It has wonderful spares value; you will have a long low case, ideal if you plan to make something which has a lot of controls, such a case could easily cost you £5. You will have a modem; more and more telephone/computer operators are being performed and this modem could set you going. Price £5 plus £1 post.

## GOODS ARE ON APPROVAL

these notes are often heavily written and technical information sheets are seldom available about the items we have to describe, also advertisements sometimes go to press without our having a chance to correct any mistakes, however, everything we sell is supplied on the understanding that if it is not suitable for your project you may return it within 7 days for credit. If there was a definite error of description in our copy then we will pay postage. If not, then you pay the postage. Note this offer applies to kits, but only if construction is not started.

## FANS & BLOWERS

Woods extractors  
5" £5 + £1.25 post. 6" £6 + £1.50 post  
4" x 4" Muffin equipment cooling fan 115V £2.00  
4" x 4" Muffin equipment cooling fan 230/240V £5.95  
5" Planar extractor £5.50  
9" Extractor or blower 115V supplied with 230 to 115V adaptor £9.50 + £2 post.  
All above are ex computers but guaranteed 12 months.  
10" x 3" Tangential Blower. New. Very quiet - supplied with 230 to 115V adaptor on use two in series to give long blow £2.00 + £1.50 post or £4.00 + £2.00 post for two.

## IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder - a complete mains operated kit, case included. £11.95 plus £2.00 post.

## TELEPHONE BITS

Takes B.T. plug (has surge arrester - ringing condenser etc) and makes B.T. socket... £3.95  
Extension socket... £2.95  
Dual adaptors (2 from one socket)... £3.95  
Cord terminating with B.T. plug 3 metres... £2.95  
Kit for converting old entry terminal box to new B.T. master socket, complete with 4 core cable, cable clips and 2 BT extension sockets... £11.50

## MINI MONO AMP on p.c.b. size 4" x 2" (app.)

Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00

## J & N BULL ELECTRICAL

Dept. E.E., 128 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QL

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £20 add £1 service charge. Monthly account orders accepted from schools and public companies. Access & Board orders accepted. Brighton 0273 734648. Bulk orders: write for quote.

## OVER 400 GIFTS YOU CAN CHOOSE FROM

There is a total of over 400 packs in our Baker's dozen range and you become entitled to a free gift with each dozen pounds you spend on these packs. A classified list of these packs and our latest "News Letter" will be enclosed with your goods, and you will automatically receive our next news letters.

## TWO POUNDERS\*

- 2P2 - Wall mounting thermostat, high precision with mercury switch and thermometer
- 2P3 - Variable and reversible 8-12V psu for model control
- 2P4 - 24 volt psu with separate channels for stereo made for Mullard UNILEX
- 2P6 - 100W mains to 115V auto-transformer with voltage tappings
- 2P8 - Mains motor with gear box and variable speed selector. Series wound so suitable for further speed control
- 2P9 - Time and set switch. Boxed, glass fronted and with knobs. Controls up to 15 amps. Ideal to program electric heaters
- 2P10 - 12 volt 5 amp mains transformer - low volt winding on separate bobbin and easy to remove to convert to lower voltages for higher currents
- 2P11 - Power amp module Mullard Unilex EP9000 (note stereo pre-amp module Unilex 9001 is BD216)
- 2P12 - Disk or Tape projection motor - has balanced rotor and is reversible 230V mains operated 1500 rpm
- 2P14 - Mug Stop kit - when thrown emits piercing squawk
- 2P15 - Interrupted Beam kit for burglar alarms, counters, etc.
- 2P17 - 2 rev pr minute mains driven motor with gear box, ideal to operate mirror ball
- 2P18 - Liquid/gas shut off valve mains solenoid operated
- 2P19 - Disco switch motor drives 6 or more 10 amp change over micro switches supplied ready for mains operation
- 2P20 - 20 metres extension lead, 2 core - ideal most Black and Decker garden tools etc.
- 2P21 - 10 watt amplifier, Mullard module reference 1173
- 2P22 - Motor driven switch 20 secs on or off after push
- 2P23 - Counter resettable mains operated 3 digit
- 2P27 - Goodmans Sinker 6 inch round 8ohm 12 watt
- 2P28 - Drill Pump - always useful couples to any make portable drill
- 2P31 - 4 metres 98 way interconnecting wire easy to strip
- 2P32 - Hot Wire amp meter - 4 1/2 round surface mounting 0-10A - old but working and definitely a bit of history
- 2P34 - Solenoid Air Valve mains operated
- 2P35 - Battery charger kit comprising mains transformer, full wave rectifier and motor, suitable for charging 6v or 12v
- 2P38 - 200 R.P.M. Gearing Mains Motor 1" stack quite powerful, definitely large enough to drive a rotating aerial or a tumbler for polishing stones etc.
- 2P43 - Small type blower or extractor fan, motor inset so very compact, 230V
- 2P46 - Dur famous drill control kit complete and with prepared case.
- 2P49 - Fire Alarm break glass switch in heavy cast case
- 2P51 - Stereo Headphone amplifier, with pre-amp
- 2P55 - Mains motor, extra powerful has 1 1/2" stack and good length of spindle
- 2P62 - 1 pair Goodmans 15 ohm speakers for Unilex
- 2P63 - 1 5Kv 20 mA mains transformer ex-equipment
- 2P64 - 1 five bladed fan 6 1/2" with mains motor
- 2P66 - 1 2Kw tangential heater 115v easily convertible for 230V
- 2P67 - 1 12v-0-12v 2 amp mains transformer
- 2P68 - 1 15v-0-15v 2 amp mains transformer
- 2P69 - 1 250v-0-250v 60 mA & 86.3v 5A mains transformer + 50p post
- 2P70 - 1 E.M.I. tape motor two speed and reversible
- 2P72 - 1 115V Muffin fan 4" x 4" approx. (s.h.)
- 2P75 - 1 2 hour timer, plugs into 13A socket
- 2P76 - 1 auxid tweeter partner to 5P26 speaker
- 2P82 - 3v-0-3v 2 amp mains transformer
- 2P84 - Modem board with press keys for telephone redialler
- 2P85 - 20v-0-20v 1/2 A Mains transformer
- 2P88 - Sangamo 24 hr time switch 20 amp (s.h.)
- 2P89 - 120 min. time switch with knob
- 2P90 - 30 min. time switch with edgewise engraved controller
- 2P92 - Bailey & Mackey pressure switch 15 p.s.i.
- 2P94 - Telephone handset for EE home telephone circuit

## £5 POUNDERS\*

1. 12 volt submersible pump complete with a tap which when pushed brought over the basin switches on the pump and when pushed back switches off, an ideal caravan unit.
2. Sound to light kit complete in case suitable for up to 750 watts.
3. Silent sensitive ultra sonic transmitter and receiver kit, complete.
5. 250 watt isolating transformer to make your service bench safe, has voltage adj. taps, also as it has a 115V tapping it can be used to safely operate American or other 115V equipment which is often only insulated to 115V. Please add £3 postage if you can't collect as this is a heavy item.
6. 12V alarm bell with heavy 6" gong, suitable for outside if protected from direct rainfall. Ex GPO but in perfect order and guaranteed.
12. Equipment cooling fan - minin snail type mains operated.
13. Ping pong ball blower - or for any job that requires a powerful stream of air - ex computer. Collect or add £21 post.


- 5P15 - Uniselect 5 pole, 25 way 50 volt coil
- 5P18 - motor driven water pump as fitted to many washing machines
- 5P20 - 2 kits, matchbox size, surveillance transmitter and FM receiver
- 5P23 - miniature (appr. 2 1/2" wide) tangential blow heater, 1.2kw
- 5P24 - 1 hp motor, ex computer, 230V, mains operation 1450rpm. If not collect add £3 post
- 5P25 - special effects lighting switch. Up to 6 channels of lamps can be on or off for varying time periods
- 5P26 - Audax woofer 8" 8ohm 35 watt
- 5P27 - cartridge player 12V, has high quality stereo amplifier
- 5P28 - gear pump, mains motor driven with inlet and outlet pipe connectors
- 5P32 - large mains operated push or pull solenoid. Heavy so add £1.50 post
- 5P34 - 24V 5A toroidal mains transformer
- 5P35 - modem board from telephone auto dialler, complete with keypad and all ICs
- 5P37 - 24 hour time switch, 2 on/off's and clockwork reserve, ex Elec. Board loading up to 50A. Add £1 post
- 5P41 - 5" extractor fan, very quiet runner (s.h.), gntd 12 months
- 5P51 - 200 watt auto transformer, toroidal wound and encapsulated 230-115V
- 5P58 - Amstrad AM/FM stereo tuner with connection diagram

LIGHT CHASER KIT motor driven switch bank with connection diagram, used in connection with 4 sets of xmas lights makes a very eye catching display for home, shop or disco, only £5 ref 5P56.

VALVE PRE AMP described in the Aug E.T.I. it's a very interesting circuit if you intend trying it, we can supply many of the parts mains transformer 250-0-250 + 6.3V our ref 2P69 + £1 post  
89A valve bases 4 for £1 BD95  
Double tag strips 3 lengths £2 2P100  
Toggle switches dpst and 4p 4 way rotary switch BD394  
1 meg single gang pot 4 for £1 BD391  
100 + 100uf 320V electrolytic 2 for £1 BD392  
4uf 300V 4 for £1 BD393

ISSN 0262-3617

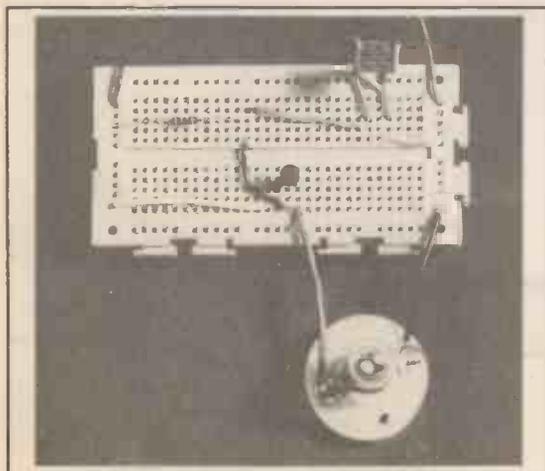PROJECTS ... THEORY ... NEWS ...  
COMMENT ... POPULAR FEATURES ...



© Wimborne Publishing Ltd 1986. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our October 1986 issue will be published on Friday, 19 September. See page 481 for details.

## Projects

<b>INFRA-RED BEAM ALARM</b> by R. A. Penfold	454
Protect your valuables with an invisible beam	
<b>CUSTOM JOYSTICK WITH AUTO FIRE</b>	460
Add rapid fire to your Spectrum	
<b>SIMPLE PRINTER BUFFER</b> by W. Hunter	464
Allows continuation of data entry whilst previous info is printed out	
<b>FREEZER FAILURE ALARM</b> by W. Hunter	474
Keep your assets frozen	
<b>ELECTRONIC CANDLE</b>	476
An "Exploring Electronics" project	
<b>CAR TIMER</b> by D. Butler	478
Can save you time and money	
<b>RESISTANCE/CAPACITANCE METER</b>	486
Auto-ranging test equipment using the BBC Micro	
<b>SCRATCH BLANKER</b> by R. A. Penfold	492
Bring your old records back to life	

## Series

<b>ON SPEC</b> by Mike Tooley BA	460
Readers' Spectrum Sinclair page	
<b>ROBOT ROUNDUP</b> by Nigel Clark	462
A new regular series that investigates the world of robotics	
<b>EXPLORING ELECTRONICS</b> by Owen Bishop	476
Part Three: More on using a transistor	
<b>AMATEUR RADIO</b> by Tony Smith G4FA 1	484
Aurora: Nice Day Out; Question Corner	
<b>BBC MICRO</b> by R. A. Penfold & J. W. Penfold	486
Regular spot for Beeb fanatics	
<b>ACTUALLY DOING IT</b> by Robert Penfold	498
What to look for if your project fails to work	

## Features

<b>EDITORIAL</b>	453
<b>FOR YOUR ENTERTAINMENT</b> by Barry Fox	459
Comdex; CD ROM	
<b>CIRCUIT EXCHANGE</b>	469
A forum for readers' circuit ideas	
<b>BOOK SERVICE</b>	470
Our own service for readers of EE	
<b>SEMICONDUCTORS IN PERSPECTIVE</b> by James Fowkes	472
The development of semiconductor devices	
<b>NEWS</b>	482
What's happening in the world of electronics	
<b>SHOPTALK</b> by David Barrington	485
Product news and component buying	
<b>DOWN TO EARTH</b> by George Hylton	490
Meter shunt calculator	
<b>MARKET PLACE</b>	491
Free readers' buy and sell spot	
<b>READERS' LETTERS</b>	499
Your news and views	
<b>PRINTED CIRCUIT BOARD SERVICE</b>	500
<b>SUBSCRIPTION SERVICE</b>	501

Readers' Services ● Editorial and Advertisement Departments

453

# DIY KIT SERVICE

## EFFECTS

Blow Box	SET 214	£24.83	£29.33
Chorus Flanger (PE*)	SET 235	£54.49	£59.99
Cybervox (EE*)	SET 228	£39.26	£44.76
Echo-Reverb (PE*)	SET 218	£52.16	£57.66
Flanger	SET 153	£23.95	£28.45
Frequency Doubler	SET 98	£10.80	£15.30
Fuzz (Smooth)	SET 209F	£15.08	£19.58
Guitar Modulo	SET 196	£19.06	£23.56
Guitar Overdrive	SET 56	£23.54	£29.04
Hand Clapper	SET 197	£22.19	£26.69
Multi-Processor	SET 189	£53.53	£61.33
Phaser (PE*)	SET 226	£36.86	£42.36
Reverb - Mono (EE*)	SET 232	£22.85	£27.35
Reverb - Stereo	SET 203	£32.04	£36.54
Rhythm Generator	SET 240	£54.49	£59.99
Ring Modulator (PE*)	SET 231	£40.08	£45.58
Thunder & L'ning (PE*)	SET 250T	£26.00	£29.50
Tom-Tom Synth	SET 190	£14.87	£19.37
Tremolo	SET 136	£11.12	£15.62
Wah (Auto & Manual)	SET 140	£18.86	£24.36
Wind & Rain Storm (PE*)	SET 250W	£26.00	£29.50

Unboxed Boxed

## GEIGER COUNTERS

PE Geiger, audio and meter output—Unit 264 with heavy duty box as published £69.50  
with normal black steel box £59.50  
without box £55.00  
EE Simple Geiger, audio only output—Unit 265 with steel box £49.50  
Unboxed £47.00

## CONTROLLERS

Bass Boost	SET 138B	£9.12	£13.62
Compander	SET 238	£18.49	£22.99
Disco Light Control	SET 245F	£57.00	£62.50
Envelope Shaper	SET 174	£20.70	£25.20
Fader (Voice Dp)	SET 107	£17.72	£22.22
Graphic Equaliser	SET 217	£20.83	£25.33
Rhythm Gen (Computer)	SET 173	£35.91	£41.41
Guitar To Synth	SET 156M	£13.57	£18.07
Headphone Amp Mono	SET 156S	£22.16	£26.66
Headphone Amp Stereo	SET 141	£12.31	£16.81
Mum Cut	SET 144	£10.43	£14.93
Microphone Pre-amp	SET 229M	£44.45	£49.95
Mixer 4ch Mono (PE*)	SET 256	£15.49	£19.99
Mixer 4ch Mono Simpl	SET 229S	£82.15	£89.95
Mixer 4ch Stereo (PE*)	SET 213	£19.87	£24.37
Mock Stereo	SET 227	£22.11	£26.61
Noise Gate (PE*)	SET 222	£20.81	£25.31
Sustain	SET 139	£15.51	£21.01
Tone Control	SET 138T	£9.12	£13.62
Treble Boost	SET 152	£72.15	£79.95
Vocoder	SET 155	£13.81	£18.31
Vodalek Robot Voice			

Unboxed Boxed

## FOOT PEDALS

Linkafex Chorus	SET 204	£37.26	£42.96
Linkafex Delay	SET 208	£36.39	£42.09
Linkafex Equaliser	SET 216	£19.73	£25.43
Linkafex Flanger	SET 207	£29.22	£34.92
Linkafex Fuzz	SET 209L	£17.54	£23.24
Linkafex Modulo	SET 211	£19.71	£25.41

## COMPUTER PROJECTS

'Scope Simulator (PE*)	SET 247	£39.00	£44.50
Dig Delay & Mcs (PE*)	SET 234	£162.00	£198.50
Mini Sampler (PE*)	SET 246	£69.50	£75.00
Rhythm Gen (Computer)	SET 185	£29.14	£34.64
Synth To Computer	SET 184	£21.65	£26.15
Chip Tester 24-pin (PE*)	SET 258F	£35.80	£39.30
Chip Tester 16-pin (PE*)	SET 258S	£29.00	£32.50
Mini Music Tuner (EE*)	SET 259	£19.00	£22.50

\* = Kit as Published

Boxes - Linkafex Robust Diecast, SET 234 19 inch steel rack, others Black Steel & Aluminium. All kits include PCBs, parts, instructions. Free wire & solder with boxed sets. Further details in Catalogue of over 70 kits - Send 9 x 4 S.A.E. (Overseas Catalogue send £1.00 or 5 IRCs). Mail order, GWO, CHO, PO, Access. Visa. Details correct at press, £80E.

Add 15% VAT. Add P&P - unboxed kits £1.00 each, SET 234 £3.50. Other boxed kits £1.50 each. Insurance 50p per £50. Overseas P&P in catalogue.

## PHONOSONICS, DEPT. EE69,

8 FINUCANE DRIVE, ORPINGTON, KENT BR5 4ED.  
Tel: ORPINGTON 37821 (STD 0689, LONDON 66)

# £1 BARGAIN PACKS

PK 1. 350 Assorted resistors. Full length leads.	PK 20. 2 Pairs D.C. plugs & sockets c/w leads & PP3 clip.
PK 2. 400 Assorted resistors. Pre-formed leads.	PK 21. 25 Assorted transistors. All new & coded.
PK 3. 60 Assorted resistors. Wire wound.	PK 22. 15 Assorted LC's. All new & coded.
PK 4. 200 Assorted capacitors.	PK 23. 50 Assorted unmarked & untested LC's.
PK 5. 200 Ceramic capacitors.	PK 24. 200 Assorted diodes.
PK 6. 60 Electrolytic capacitors.	PK 25. 20 E.H.T. diodes.
PK 7. 2 2200uf 100 volt capacitors.	PK 26. 3 Large power-fin heatsinks. T03
PK 8. 2 4700uf 30 volt capacitors.	PK 27. 1 4 section 7 segment L.e.d. clock display.
PK 9. 12 Assorted rotary potentiometers. Single.	PK 28. 20 Assorted neons. Panel mounting & wire ended.
PK 10. 6 Assorted rotary potentiometers. Dual.	PK 29. 1 Microphone c/w lead, switch, plugs & stand.
PK 11. 12 Assorted slider potentiometers.	PK 30. 3 Microphone inserts.
PK 12. 40 Assorted pre-set potentiometers.	PK 31. 3 Dynamic earpieces c/w lead & 3.5mm plug.
PK 13. 5 100K lin multitrans potentiometers.	PK 32. 2 Telescopic aerials.
PK 14. 5 1 meg lin multitrans potentiometers.	PK 33. 1 Stereo cassette tape head.
PK 15. 12 Assorted switches.	PK 34. 2 Small cassette motors.
PK 16. 1 bank 4-way push button switches c/w knobs.	PK 35. 1 Large cassette motor.
PK 17. 1 4 pole 5-way wafers switch.	PK 36. 1 Wire pack. Mains cable.
PK 18. 15 Assorted control knobs.	PK 37. 1 Wire pack. Screened signal cable.
PK 19. 20 Assorted plugs and sockets.	PK 38. 1 Wire pack. Connecting wire. Assorted.

Postal order or cheque with order. Please add £1 postage & packing per order. Shop open 9.30-6.00 Mon to Sat. Closed all day Thurs.

MJR WHOLESALE, 238 Waterside,  
Chesham, Bucks HP5 1PG. Tel: 0494 771033

## 'Scotlands newest components shop'

# OMNI ELECTRONICS

We stock a wide range of components:

transformers, switches, pots, ICs, capacitors, resistors, diodes, boxes, triacs, LEDs, cable, connectors, PCBs— in fact, all you need for your projects.

Send for our 21 page catalogue—20p + 12p postage or call at our shop Mon-Fri 9am-6pm, Sat 9am-5pm.

174 Dalkeith Road  
EDINBURGH EH16 5DX  
031-667 2611

**SEPTEMBER SPECIAL OFFER**

ONLY **£4.99** NORMALLY £6.20  
WITH ORDERS OF £10 OR OVER

**ABS BOXES**

MB1 85p	T3 50p
MB2 93p	PBL3
MB3 £1.15	68p
MB4 £2.90	BC3
MB5 £1.50	£2.99
MB6 £2.95	

**B.T. SOCKETS**

MASTER SOCKET	
2/A4	£2.85
SECONDARY SOCKET	
2/6A	£1.95
DUAL OUTLET	
LJ4	£4.80

**1/2 W. RESISTOR KITS**  
5 EACH PAIR (50)  
VALUE £1.00  
£1.95

**PORTABLE GAS SOLDERING IRON**

TOTALLY PORTABLE  
FILLS IN SECONDS  
WITH ORDINARY  
LIGHTER FUEL FOR  
UP TO 60 MINS  
CONTINUOUS USE.  
TIP TEMPERATURES  
TO MAX. 400°C.  
SMALL SIZE  
175 x 19mm




**£13.90**  
MEETS ALL  
SAFETY  
STANDARDS

SPARE TIPS—£4.50 each  
SIZES—2,4, 3,2 & 4-8mm

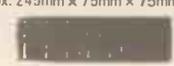**12V RECHARGEABLE UNIT**

A BANK OF 10 'D' TYPE NI-CADS  
ENCAPSULATED IN A BLACK PLASTIC BOX  
COMPLETE WITH INLET AND OUTLET  
SOCKETS (XLR TYPE) AND FUSE HOLDER.  
THIS GIVING 12V FROM A VERY NEAT AND  
TIDY UNIT.  
Approx. 245mm x 75mm x 75mm



**£5.99 + £1.85 P&P**  
+ 15% VAT

**74LS**

74LS00	24p
TO	
74LS12	33p
74LS13	48p
74LS14	24p
74LS19	44p

**C-MOS**

4000	24p
4001	24p
4002	68p
4006	24p
4008	59p
4009	44p

MANY MORE LISTED  
IN CATALOGUE

**NI-CAD BATTERY CHARGER**

THIS BATTERY CHARGER IS SUITABLE FOR  
AA, C, D & PP3 TYPE NI-CAD CHARGING AND  
CAN COPE WITH UP TO 4 OF EACH AA, C & D  
PLUS 1 x PP3 AT ANY ONE TIME.

**£4.50**  
NORMALLY £5.17 + 15% VAT

**RECHARGEABLE BATTERIES (NI-CADS)**

A RANGE OF NICKEL CADMIUM BATTERIES  
WHICH WILL REPLACE DRY BATTERIES. CAN  
BE QUICKLY AND EASILY RECHARGED USING  
THE ABOVE NI-CAD CHARGER.

AA — 95p each	10+ 85p each
C — £2.14 each	10+ £1.98 each
D — £2.30 each	10+ £2.10 each
PP3 — £3.75 each	10+ £3.65 each

**TRANSISTORS**

AC127	28p
AC128	30p
AC128K	34p
AC141	58p
AC141K	38p
AC142	56p
AC142K	38p
AC151	45p
AC152	45p
AC153	57p
AC153K	46p
AC176	30p
AC176K	28p
AC187	38p
AC187K	38p
AC189	28p
AC189K	38p
AC222	£1.50
AD142	88p
AD143	£1.10

MANY MORE LISTED  
IN CATALOGUE

**SWITCH CLEANING**

LUBRICANT **£1.24**  
226 gm AEROSOL TIN  
WITH APPLICATOR

ALL ORDERS + 65P P&P + 15% V.A.T.

**TEACH IN '86**

BASIC ITEMS		<b>£23.70</b>
Regulator Unit Kit	Project 1	<b>£17.95</b>
Universal Bridge Kit	Project 2	<b>£20.50</b>
Diode/Transistor Tester Kit	Project 3	<b>£12.45</b>
Audio Signal Tracer Kit	Project 4	<b>£9.80</b>
Audio Signal Generator Kit	Project 5	<b>£17.95</b>
R.F. Signal Generator Kit	Project 6	<b>£21.00</b>
F.E.T. Voltmeter	Project 7	<b>£16.45</b>
Digital Pulse Generator	Project 8	<b>£10.85</b>

**Save 5%. Order any two of the above kits, deduct 5% from total price. Article reprint 60p if required.**

**Extra Components - Part 1 70p, Part 2 £1, Part 3 £1.45, Part 4 £2, Part 5 £1.90, Part 6 £6.85, Part 7 45p, Part 8 £1.75, Part 9 25p.**

**SPECIAL PRICE FOR LATE STARTERS — ALL ABOVE ITEMS £155 plus £2.50 P & P**

**EVERYDAY ELECTRONICS KITS**

Graphic Equaliser	June '85	£22.50p
Across the River	June '85	£13.45p
Caravan PSU	June '85	£9.95p
Electronic Doorbell	June '85	£8.25p
High Z Multimeter (Exc. Case)	June '85	£26.35p
Community Tester	July '85	£8.35p
Train Signal Controller	July '85	£10.45p
Drill Control Unit (Exc. Case)	Aug. '85	£18.45p
Tremolo/Vibrato	Aug. '85	£31.00p
Fridge Alarm	Sept. '85	£7.45p
Caravan Alarm	Sept. '85	£15.00p
Strain Gauge Amplifier	Oct. '85	£24.95p
Oport	Jan. '86	£9.25p
One Chip Alarm	Jan. '86	£6.90p
Mains Delay Switch	Jan. '86	£17.85p

**TEACH IN COMPONENTS**

Case-Black ABS-213x142x57mm	£2.75p	
Veroboard-36 strips x50 holes	£1.35p	
Pot. Lin Carbon-1K, 4K7, 10K, 100K etc.	ea. 43p	
Pot. Lin Wirewound-1K etc.	ea. £2.20p	
Dual Pot. -5K etc.	ea. £1.45p	
Rotary Switches 2P6W, 3P4W, 4P3W, 1P12W etc	65p	
SPST Toggle Switch	55p	
Push to Make Switch	23p	
62Y88 Series Zener-All Voltages	10p	
Jack Socket - Standard Switched	28p	
Test Leads - 10 Leads with Croc Clips	£1.80p	
Terminal Posts - Various Colours	ea. 45p	
4mm Sockets - Various Colours	ea. 18p	
4mm Plugs - Various Colours	ea. 18p	
1mm Sockets	ea. 17p	
1mm Plugs	ea. 17p	
Adhesive Feet - Per 4	32p	
Edgewise Meter	£4.35p	
Knob Black/Red Cap	18p	
T03 Heatsink	87p	
T05 Heatsink	15p	
BC108.....14p	IN4001.....4p	7805.....43p
BC109.....14p	IN4148.....3p	555.....24p
BC461.....62p	0A47.....12p	LM317K. £2.85
BFY50.....32p	0A91.....8p	LM380N. £1.10
2N3053.....39p	W005.....24p	TL084.....£1.05p
2N3619.....42p	741.....23p	TL072.....

ALL KITS COMPLETE (LESS BATTERIES) UNLESS SPECIFIED. INCLUDE ALL COMPONENTS, PCB (OR VERO), CASE AND HARDWARE. ALL COMPONENTS NEW AND FULL SPEC. DO NOT ADD V.A.T. ADD 70p P&P PER ORDER & SEND CHEQUES OR POSTAL ORDERS TO:

**PRACTICAL WIRELESS KITS**

FET Dip Oscillator	Oct. '85	£19.90p
Capacitance Meter	Oct. '85	£23.90p
Meon-50MHz Transverter (+£1.50p&p)	Oct. '85	£49.50p
Two Tone Oscillator	Dec. '85	£22.45p
Crystal Calibrator	Jan. '86	£19.95p
RTTY/Morse Modem	Jan. '86	£35.85p

**C.P.L. ELECTRONICS**

8 Southdene Close, Hemlington, Middlesbrough,  
Cleveland TS8 9HE. Tel: 0642 591157

FREE PRICE LIST ON REQUEST

# RACK MOUNTING CABINET



★ Suitable for instruments, high quality amplifiers and many other purposes ★  
 Top, side and rear covers removable for access ★ Black anodised aluminium front panel ★ Separate front mounting plate ★ heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles ★ With ventilation slits and plastic feet ★ Rear box manufactured from steel painted in black ★ Aluminium version available (wholly made of black anodised aluminium sheets) ★ Different sizes ★ Comes in quick assembly flat package

Panel Size W H (inch)	Rear Box W H D	ME	AL
19x2.5	17x2.0x10	22.5	27.5
19x3.5	17x3.0x10	24.5	29.5
19x5.25	17x5.0x10	26.5	—
19x3.5	17x3.0x12	25.5	30.5
19x5.25	17x5.0x12	27.5	32.5
19x5.75	17x5.5x12	28.5	33.5
*17x2.5	15.5x2x9	16.5	20.5
*17x3.5	15.5x3x9	17.0	—
*19x3.0	17x2.5x10	—	20.5
*19x4.0	17x3.5x10	16.5	19.5
*19x4.0	17x3.5x12	19.5	22.5

\* Discontinued sizes, special price valid while stocks last. Please add £3.00 P&P for the first item and £1.50 for each additional item. Quantity discount available. To order send cheque/postal order, please allow up to 7 days despatch for cheque clearance. Customer who requires further information, please send S.A.E. Mail order only.

## T.J.A. DEVELOPMENTS

Dept. E.E., 53 Hartington Road,  
 London E17 8AS

### OSCILLOSCOPES

TELEQUIPMENT D75 Dual Trace 50MHz Delay Sweep ..... £350  
 COSSOR CDU150. Dual Trace 35MHz Solid State Portable 8 x 10cm display with manual ..... £200  
 GOLD OS255 Dual Trace 15MHz ..... £200  
 TELEQUIPMENT D61 Dual Trace 10MHz with Manual ..... £150  
 S.E. LABS SM111. Dual Trace 18MHz Solid State Portable AC or External DC operation 8 x 10cm display with manual ..... £150  
 TELEQUIPMENT D43. Dual Trace 15MHz. With manual ..... £100  
 TELEQUIPMENT SS4A. Single Trace 10MHz ..... Solid State. With manual ..... £110

### PHILIPS DIGITAL MULTIMETERS

4 digit, auto ranging. Complete with batteries and leads (p&p £5)  
 TYPE PM2517X (LCD) ..... £75

### MULTIMETERS

AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently). Complete with Batteries & Leads. £55  
 AVO 8 Mk2 Complete with Batteries & Leads £45  
 Above items in GOOD WORKING ORDER—appearance not A1 hence the price.  
 AVO TEST SET No 1 (Military version of AVO-8) Complete with batteries, leads & carrying case £65  
 AVO Model 7x. Complete with batteries, leads & carrying case ..... £40  
 AVO Model 73. Pocket Multimeter (Analogue). 30 ranges. Complete with batteries & leads ..... £18  
 AVO 72—Similar to above but no AC current range. With batteries & leads ..... £10

RACAL 32MHz Universal counter timer. Type 836 with manual ..... Only £50 ea

### STEPPING MOTORS

Type 1,200 Steps per rev. 4 Phase (5 wire) 12/24V. Torque 25oz inch (will run on 5V with reduced torque) ..... £15 ea  
 Type 2,6/12 Steps per rev. 3 Phase. 12/24 (will work on 5V) ..... £2 ea. 5 off £7.50  
 Type 3. NORTH AMERICAN PHILIPS 24 Steps per rev. 4 wire 5V 3-3Amps 0-250 rpm 0-200PPS £6 ea  
 Type 4,200 Steps per rev. 120V (3 wire) Torque 25oz inch ..... £4 ea  
 Type 7. WARNER 24 Steps per rev. 3 Phase (6 wire). 28V. Holding Torque 45oz inch ..... £5 ea

USED EQUIPMENT—WITH 30 DAYS GUARANTEE. MANUALS SUPPLIED IF POSSIBLE. This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £12. VAT to be added to Total Goods & Carriage.

## STEWART OF READING

Telephone: 0734 68041

110 WYKEHAM ROAD, READING, BERKS RG6 1PL

Callers welcome 9 a.m. to 5.30 p.m.

Mon-Fri (until 8pm Thurs)

### COMMUNICATION RECEIVERS

RACAL RA17L 500kHz-30MHz  
 only £140 each with manual  
 EDDYSTONE 730/4. 480kHz-30MHz.  
 only £110 each with manual

### PROFESSIONAL 9" GREEN SCREEN MONITORS

Made by KGM for Reuters. Gives quality 80 column x 24 line display. Composite Video In. Cased. Good Condition ..... New only £32 ea

### 5 1/4" FLOPPY DISK DRIVES

MP1 Double sided. Double density. 80 track. Un-used. £75 ea  
 DISK DRIVE PSU. 240V in 5V 1-6A & 12V 1-5A Out. Size W125mm. H75mm. D180mm. Cased. Un-used. ..... Only £10 ea (p&p £2)  
 QWERTY KEYBOARD (as in LYNX MICRO). Push to make. Cased ..... Only £5 ea (p&p £2)  
 LYNX MICRO—128K. No power. Supply available. Therefore ..... Only £50 ea (p&p £5)

AVO TRANSISTOR TESTER TT169  
 Handheld GO NOGO for in situ testing. Complete with batteries, leads & instructions. p&p £3. Now only £12

### ISOLATING TRANSFORMERS

240V IN—240V OUT 500VA £15 ea P&P £5  
 240V IN—240V OUT 200VA £8 P&P £3

### NEW EQUIPMENT

HAMEG OSCILLOSCOPE 605. Dual Trace 60MHz. Delay Sweep. Component Tester ..... £515  
 HAMEG OSCILLOSCOPE 203.5. Dual Trace 20MHz. Component Tester ..... £270  
 All other models available.  
 BLACK STAR FREQUENCY COUNTERS P&P £4  
 Meteor 100-100MHz ..... £99  
 Meteor 600-600MHz ..... £126  
 Meteor 1000-1GHz ..... £175  
 BLACK STAR JUPITER 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0-1Hz—500kHz. P&P £4 ..... £110  
 HUNG CHANG OMM 6010. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC Complete with batteries & leads. P&P £4 ..... £33.50  
 OSCILLOSCOPES PROBES. Switched x1; x10. P&P £2 ..... £11

For KITS & COMPONENTS  
 Choose the easy way — with

Send SAE now  
 for our FREE CATALOGUE  
 ORDERS: RING (01) 567 8910

### VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc.—details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits.  
 Supply. 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 8 x 4 x 2cms.  
 The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used.  
 MK12 IR Receiver (incl. transformer) £13.50  
 MK18 Transmitter £6.80  
 MK9 4-way Keyboard £1.90  
 MK10 16-way Keyboard £5.40  
 601133 Box for Transmitter £2.60

### TEN EXCITING PROJECTS FOR BEGINNERS

This kit has been specially designed for the beginner and contains a SOLDERLESS BREADBOARD, COMPONENTS, and a BOOKLET with instructions to enable the absolute novice to build TEN fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout program. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.  
 ORDER NO XK118 £12.50

### 405 207 AUTORANGING MULTIMETER

High quality AUTORANGING LCD multimeter with features normally found in meters costing much more such as DISPLAY HOLD, MEMORY, CONTINUITY BUZZER & 10A AC/DC current ranges. High accuracy with fully automatic operation makes this multimeter a must for the professional or serious hobbyist.

AC Volts: 0-2-20-200-500V.  
 DC Volts: 0-200m-2-20-200-1000V +0.8%.  
 AC Current: 0-20m-200mA +1.2%, 0-10A +2%.  
 DC Current: 0-20m-200mA +1.2%, 0-10A +1.5%.  
 Resistance: 0-200-2K-20K-200K-2M +1%  
 Continuity Buzzer sounds at <20R.  
 Dimensions: 127 x 69 x 25mm  
 £33.00

### DVM/ULTRA SENSITIVE THERMOMETER KIT

Based on the ICL 7128 and a 3 1/2 digit liquid crystal display, this kit will form the basis of a digital multimeter (only a few additional resistors and switches are required — details supplied), or a sensitive digital thermometer (—50°C to +150°C) reading 0.1°. The kit has a sensitivity of 200mV for a full-scale reading, automatic polarity and overload indication. Typical battery life of 2 years (PP3). £15.50

### DISCO LIGHTING KITS

DL1000K—This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. £15.95  
 DLZ1000K—A lower cost uni-directional version of the above. Zero switching to reduce interference. £8.95  
 Optional opto input allowing audio 'beat' / light response (DLA/1) 70p  
 DL3000K—3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. £12.95

### DL8000



The DL8000K is an 8-way sequencer kit with built-in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY—YES 80! different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300W output per channel.  
 And the best thing about it is the price: ONLY £28.50

### ELECTRONIC LOCK KIT

With hundreds of uses in doors, garages, car anti-theft devices, electronic equipment, etc. Only the correct easily changed four-digit code will open it! Requires a 5V to 15V DC supply. Output 750mA. Fits into standard electrical wall box. Complete kit (excl. front panel) XK101 £11.50  
 Electronic lock mechanism for use with the above kit. 70150 £14.95

### HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300W of lighting.  
 TDR300K Remote Control £14.95

Dimmer MK6 Transmitter for above £4.50  
 TD300K Touchdimmer £7.75  
 TS300K Touchswitch £7.75  
 TDE/K Extension kit for 2-way switching for TD300K £2.50



TH ELECTRONICS  
 13 BOSTON RD  
 LONDON W7 3SJ  
 Tel: 01-567 8910

SEND 9"x6" S.A.E. OR CALL AT SHOP MON-FRI 9-5pm SATURDAY 10-4pm

ORDERING INFORMATION:  
 ALL PRICES EXCLUDE VAT  
 FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.  
 LOCAL AUTHORITY AND EXPORT ORDERS WELCOME  
 GOODS BY RETURN SUBJECT TO AVAILABILITY

Full Kits Inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.  
If you do not have the issue of E.E. which includes the project — you will need to order the instruction reprint as an extra — 70p each. Reprints available separately 70p each + p&p 80p.

## THIS MONTH'S KITS SAE or 'phone for prices

BATTERY TESTER Aug 86	£6.85
TILT ALARM July 86	£7.45
HEADPHONE MIXER July 86	£27.69
CARAVAN BATTERY MONITOR July 86	£16.35
SQUEEKEE CONTINUITY TESTER July 86	£3.35
ELECTRONIC SCARECROW July 86	£8.45
VOX BOX AMP July 86	£12.73
EXPLORING ELECTRONICS 1/2	£9.99
PERCUSSION SYNTH June 86	£28.98
LIGHT PEN (less case) June 86	£5.80
PERSONAL RADIO June 86	£10.98
WATCHDOG June 86	£7.85
MINI STROBE May 86	£12.49
PA AMPLIFIER May 86	£23.77
LOGIC SWITCH May 86	£14.22
AUTO FIRING JOYSTICK May 86	£11.29
STEREO REVERB Apr 86	£23.98
VERSATILE PSU Apr 86	£22.39
CIRCLE CHASER Apr 86	£19.98
FRELOADER Apr 86	£7.70
STEPPER MOTOR DRIVER Apr 86	£4.66
88C MIDI INTERFACE Mar 86	£25.34
INTERVAL TIMER Mar 86	£17.11
STEREO HI-FI PRE-AMP	£44.62
MAINS TESTER & FUSE FINDER Mar 86	£7.98
FUNCTION GENERATOR Feb 86	£22.53
POWER SUPPLY FOR ABOVE	£7.26
TOUCH CONTROLLER Feb 86	£11.67
pH TRANSDUCER (less Probe) Feb 86	£22.01
LIGHT EFFECTS/GAMES UNIT Feb 86	£10.37
SPECTRUM OUTPUT PORT Feb 86	£10.21
HEADLIGHT ONE SHOT Feb 86	£10.69
OPORT Jan 86	£6.80
TACHOMETER Jan 86	£23.40
MAIN DELAY SWITCH left case Jan 86	£17.93
ONE CHIP ALARM Jan 86	£7.90
MUSICAL OODOR BELL Jan 86	£16.98
TTL LOGIC PROBE Dec 85	£8.59
DIGITAL CAPACITANCE METER Dec 85	£35.98
OIOOE/TRANSISTOR TESTER Dec 85	£15.98
UNIVERSAL LCR BRIDGE Nov 85	£23.49
FLUX DENSITY TRANSDUCER Nov 85	£26.15
FLASHING PUMPKIN less case Nov 85	£3.82
SQUEAKING BAT less case Nov 85	£8.63
SCREAMING MASK less case Nov 85	£9.98
STRAIN GAUGE AMPLIFIER Oct 85	£25.46
SIMPLE AUDIO GENERATOR Oct 85	£2.59
SOLDERING IRON POWER CONTROLLER Oct 85	£4.72
VOLTAGE REGULATOR Sept 85	£6.78
PERSONAL STEREO P.S.U. Sept 85	£8.99
R.I.A.A. PRE-AMP Sept 85	£14.49
CARAVAN ALARM Sept 85	£9.37
FRIDGE ALARM Sept 85	£6.82
SEMI-CONDUCTOR TEMP. SENSOR Sept 85	£18.93
RESISTANCE THERMOMETER Sept 85	£8.13
Probe	£18.83
PLATINUM PROBE Extra	£22.00
LOW COST POWER SUPPLY UNIT Aug 85	£16.72
TRI-STATE THERMOMETER (Batt) Aug 85	£6.05
TREMLOD/VIBRATO Aug 85	£34.48
STEPPER MOTOR INTERFACE FOR THE BBC COMPUTER less case Aug 85	£13.99
1035 STEPPER MOTOR EXTRA	£14.50
OPTIONAL POWER SUPPLY PARTS	£4.67
CONTINUITY TESTER July 85	£5.37
TRAIN SIGNAL CONTROLLER July 85	£8.78
AMSTRAID USER PORT July 85	£15.33
ACROSS THE RIVER July 85	£17.97
ELECTRONIC OODORBELL June 85	£6.55
GRAPHIC EQUALISER June 85	£23.33
AUTO PHASE May 85	£16.39
INSULATION TESTER Apr 85	£16.96
LOAD SIMPLIFIER Feb 85	£16.98
SOLID STATE REVERB Feb 85	£39.98
GAMES TIMER Jan 85	£7.63
SPECTRUM AMPLIFIER Jan 85	£5.98
TV AERIAL PRE-AMP Dec 84	£12.36
Optional PSU 12V £2.03	240V £9.86
MINI WORKSHOP POWER SUPPLY Dec 84	£34.98
OODOR CHIME Dec 84	£14.91
BBC MICRO AUDIO STORAGE SCOPE INTERFACE Nov 84	£28.77
PROXIMITY ALARM Nov 84	£17.98
MAINS CABLE DETECTOR Oct 84	£4.39
MICRO MEMORY SYNTHESIZER Oct 84	£47.98
DRILL SPEED CONTROLLER Oct 84	£6.89
GUITAR HEAD PHONE AMPLIFIER Sept 84	£6.38
SOUND OPERATED FLASH less lead Sept 84	£5.91
TEMPERATURE INTERFACE FOR BBC Aug 84	£19.70
CAR RADIO BOOSTER Aug 84	£13.87
CAR LIGHTS WARNING July 84	£7.99

VARICAP AM RADIO May 84	£10.43
EXPERIMENTAL POWER SUPPLY May 84	£18.72
SIMPLE LOOP BURGLAR ALARM May 84	£13.62
MASTERMIND TIMER May 84	£5.44
FUSE/DIODE CHECKER Apr 84	£3.45
QUASI STEREO ADAPTOR Apr 84	£10.90
DIGITAL MULTIMETER add on for BBC Micro Mar 84	£24.98
NI-CAD BATTERY CHARGER Mar 84	£9.85
REVERSING BLEEPER Mar 84	£6.78
PIPE FINDER Mar 84	£3.60
IONISER Feb 84	£23.98
ZX81 EPROM PROGRAMMER Feb 84	£14.48
SIGNAL TRACER Feb 84	£14.89
CAR LIGHT WARNING Feb 84	£3.76
GUITAR TUNER Jan 84	£17.73
BIOLOGICAL AMPLIFIER Jan 84	£19.16
CONTINUITY TESTER Dec 83	£9.99
CHILDREN'S OISCO LIGHTS Dec 83	£8.42
NOVEL EGG TIMER Dec 83 inc. case	£10.24
SPEECH SYNTHESIZER FOR THE BBC MICRO Nov 83 less cable + sockets	£21.98
MULTIMOD Nov 83	£16.98
LONG RANGE CAMERA/FLASHGUN TRIGGER Nov 83	£13.50
HOME INTERCOM less link wire Oct 83	£14.38
DIGITAL TO ANALOGUE BOARD Oct 83 less cable, case & connector	£19.98
HIGH POWER DAC DRIVER BOARD Oct 83 less case	£12.52
HIGH SPEED A TO D CONVERTER Sept 83 less cable & connector	£27.98
STORAGE SCOPE INTERFACE FOR BBC MICRO Aug 83 less software	£15.38
HIGH POWER INTERFACE BOARD Aug 83 no case	£10.38
USER PORT I/O BOARD less cable + plug	£10.49
USER PORT CONTROL BOARD July 83 less cable + plug + case	£25.14
GUITAR HEADPHONE AMPLIFIER May 83	£7.92
MW PERSONAL RADIO less case, May 83	£7.62
MOISTURE DETECTOR May 83	£5.46
CAR RADIO POWER BOOSTER Apr 83	£11.99
FUNCTION GENERATOR April 83	£48.98
FLANGER SOUND EFFECTS April 83	£24.17
NOVELTY EGG TIMER April 83 less case	£5.48
DUAL POWER SUPPLY March 83	£59.38
BUZZ OFF March 83	£4.51
PUSH BIKE ALARM Feb 83	£11.73
ZX TAPE CONTROL Nov 82	£7.13
CONTINUITY CHECKER Sept 82	£5.47
2-WAY INTERCOM July 82 no case	£4.52
ELECTRONIC PITCH PIPE July 82	£5.40
REFLEX TESTER July 82	£7.77
SEAT BELT REMINDER Jun 82	£4.10
EGG TIMER June 82	£5.44
CAR LEO VOLT METER less case May 82	£3.18
V.C.O. SOUND EFFECTS UNIT Apr 82	£12.71
CAMERA OR FLASH GUN TRIGGER Mar 82	£13.65
less tripod bushes	
POCKET TIMER Mar 82	£4.10
GUITAR TUNER Mar 82	£17.19
SIMPLE STABILISED POWER SUPPLY Jan 82	£26.98
MINI EGG TIMER Jan 82	£4.40
SIMPLE INFRA RED REMOTE CONTROL Nov 81	£18.70
CAPACITANCE METER Oct 81	£25.81
SUSTAIN UNIT Oct 81	£13.99
TAPE NOISE LIMITER Dec 81	£4.98
HEADS AND TAILS GAME Oct 81	£2.75
CONTINUITY TESTER Oct 81	£4.48
PHOTO FLASH SLAVE Oct 81	£3.80
FUZZ BOX Oct 81	£7.98
SOIL MOISTURE UNIT Oct 81	£6.39
0-12V POWER SUPPLY Sept 81	£19.48
COMBINATION LOCK July 81 less case	£21.58
SOIL MOISTURE INDICATOR E.E. May 81	£4.49
PHONE BELL REPEATER/BABY ALARM May 81	£6.15
INTERCOM April 81	£24.43
MODULATED TONE OODORBELL Mar 81	£7.35
2 NOTE OODOR CHIME Dec 80	£11.35
LIVE WIRE GAME Dec 80	£12.87
GUITAR PRACTICE AMPLIFIER Nov 80 £14.10 less case. Standard case extra	£4.99
SOUND TO LIGHT Nov. 80 3 channel	£23.40
TRANSISTOR TESTER Nov 80	£12.80
AUDIO EFFECTS UNIT FOR WEIRO SOUNDS Oct 80	£14.40
MICRO MUSIC BOX Feb 80	£17.86
Case extra	£3.60
SPRING LINE REVERB UNIT Jan 80	£27.20
UNIBOARD BURGLAR ALARM Dec 79	£6.70
DARKROOM TIMER July 79	£3.20
MICROCHIME OODORBELL Feb 79	£17.48
SOUND TO LIGHT Sept 78	£9.20
CAR BATTERY STATE INDICATOR LESS CASE Sept 78	£2.29
R.F. SIGNAL GENERATOR Sept 78	£31.20
IN SITU TRANSISTOR TESTER Jun 78	£7.50
WEIRO SOUND EFFECTS GENERATOR Mar 78	£6.20
ELECTRONIC DICE Mar 77	£4.96

## FUN WITH ELECTRONICS

Enjoyable introduction to electronics. Full of very clear full colour pictures and easy to follow text. Ideal for all beginners — children and adults. Only basic tools needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification and how they work). Also full details of how to build 6 projects — burglar alarm, radio, games, etc. Requires soldering — 4 pages clearly show you how.  
**COMPONENTS SUPPLIED ALLOW ALL PROJECTS TO BE BUILT AND KEPT.**  
Supplied less batteries & cases.  
**FUN WITH ELECTRONICS, COMPONENT PACK £16.98**  
**BOOK EXTRA £1.75.**  
Book available separately.

## INTRODUCTION TO ELECTRONICS

An introduction to the basic principles of electronics. With lots of simple experiments. Uses soldering. Lots of full colour illustrations and simple explanations. A lovely book. Ideal for all ages.  
**INTRODUCTION TO ELECTRONICS COMPONENT PACK £9.99**  
**BOOK EXTRA £2.45**  
Book also available separately.

## NEW BOOKS

Midi Projects. Penfold £2.95  
Getting The Most From Your Printer. Penfold £2.95  
More Advanced Electronic Music Projects. Penfold £2.95



## BOOKS

How to Get Your Electronic Projects Working. Penfold £2.15  
A practical Introduction to Microprocessors. Penfold £2.10  
Basic Electronics. Hodder & Stoughton £6.98  
Beginners Guide to Building Electronic Projects. Penfold £2.25  
DIY Robotics & Sensors Billingsley, BBC £7.95  
Commodore 64 £7.99  
Elementary Electronics. Sladdin £5.98  
Science Experiments with Your Computer £2.43  
How to Design & Make Your Own PCBs. BP121 £2.15  
How to Make Computer Controlled Robots. Potter £3.20  
How to Make Computer Model Controllers. Potter £3.19  
Interfacing to Microprocessors & Microcomputers £6.50  
Machine Code for Beginners. Osborne £2.45  
Micro Interfacing Circuits Book 1 £2.45  
Microprocessors for Hobbyists. Coles £4.98  
Practical Computer Experiments. Parr £1.95  
Practical Things to do With a Microcomputer. Osborne £2.19  
Questions & Answers — Electronics. Hickman £3.45  
Understanding the Micro. Osborne £1.95

• JUST A SMALL SELECTION. LOTS MORE IN OUR PRICE LIST •

## TEACH IN 86

**MULTIMETER TYPE M102BZ** as specified. Guaranteed Top quality. 20k/V, with battery check, continuity tester buzzer and fuse and diode protection. 10A dc range. Complete with leads, battery and manual. £13.98  
**VEROBLOC BREADBOARD, DESIGN PAD, MOUNTING PANEL AND 10 CROCODILE CLIP CONNECTING LEADS.** £6.98  
**REGULATOR UNIT FOR SAFE POWER SUPPLY.** All components including the specified case. Also the plugs, fuse and fuseholders to suit the EE mains adaptor. £10.78  
**COMPONENTS FOR PRACTICAL ASSIGNMENTS.** Parts 1 and 2 (Oct & Nov) £1.94. Part 3 (Dec) £1.37. Part 4 (Jan) £2.48. Part 5 (Feb) £2.22. Part 6 (Mar) £6.31. Parts 7, 8 & 9 (combined) £2.55.

## TEACH IN 86 PROJECTS

UNIVERSAL LCR BRIDGE Nov 85 £23.49  
DIDDE/TRANSISTOR TESTER Dec 85 £17.98  
USEFUL AUDIO SIGNAL TRACER Jan 86 £15.95  
AUDIO SIGNAL GENERATOR Feb 86 £24.96  
R.F. SIGNAL GENERATOR March 86 £23.32  
FET VOLT METER Apr 86 £20.46  
DIGITAL PULSE GENERATOR May 86 £15.89

## NEW

**MINI MODEL MOTORS**  
1½-3V, 2 TYPES. MM1—59p MM2—61p

## LEGO Technic Sets


TEACHERS WE ARE STOCKISTS OF THE WHOLE RANGE. CONTACT US FOR BROCHURES. VERY COMPETITIVE PRICES AND QUICK DELIVERIES.

## RECHARGE ORDINARY BATTERIES

Ordinary zinc carbon and 'Duracell' batteries can be recharged many times using our special charger. A designer-approved kit as featured in Practical Electronics, Aug 85 issue. Quickly pays for itself. PRICE £32.41 or send for details
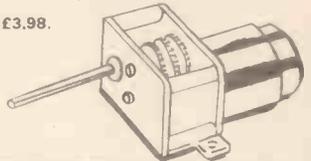
## MOTOR — GEARBOX ASSEMBLIES

Miniature precision made. Complete with quality electric motor. Variable reduction ratios achieved by fitting from 1-6 gearwheels (supplied) as required. Operates from 1.5V to 4.5V. Small unit type MGS speed range 3rpm-2200rpm depending on voltage & gear ratio. Large unit type MGL (higher torque motor) 2rpm-1150rpm. Long 3mm dia output shafts. Ideal for robots and buggies.  
**Small Unit (MGS) £3.49. Large Unit (MGL) £3.98.**  
Pulley wheels 3mm bore. Metal flange with brass hub. 10mm dia. £1.75. 20mm dia. £1.84. 30mm dia. £1.99.  
Metal collar with fixing screw, 3mm bore 24p. Flexible spring coupling 5mm. Length 31mm 68p.  
Flexible metal coupling (universal) 3mm £2.98.



## CATALOGUE

**FULLY REVISED CATALOGUE.** Brief details of each kit, our books, & illustrations of our range of tools & components. Also stepper motor, interface kit & simple robotics. Plus circuit ideas for you to build. If you read Everyday Electronics then you need a copy of the MAGENTA catalogue.

**CATALOGUE & PRICE LIST** — Send £1 in stamps etc. or add £1 to your order. Price list — 9x4 s.a.e.  
**Catalogue FREE TO SCHOOLS/COLLEGES REQUESTED ON OFFICIAL LETTERHEAD.**

## ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.  
Adventures with Electronics £3.58. Component pack £20.98 less battery.

★ • • SHOP • NOW • OPEN • • • • CALLERS • WELCOME • • • ★

## MAGENTA ELECTRONICS LTD.

EE44, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS, DE14 2ST.  
0283 65435, Mon-Fri 9-5.  
Access/Barclaycard (Visa) by phone or post.  
24 hr Answerphone for credit card orders.  
Our prices include VAT.

ADD 80P P&P TO ALL ORDERS. PRICES INCLUDE VAT. SAE ALL ENQUIRIES. OFFICIAL ORDERS WELCOME. OVERSEAS Payment must be sterling. IRISH REPUBLIC AND BFPO: UK PRICES EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote. SHOP HOURS: 9-5 MON-FRI.



PRICE LIST—FREE WITH ORDERS OR SEND SAE

## TOOLS

ANTEX MODEL C IRON	£5.98
ANTEX XS SOLDERING IRON 25W	£7.25
ST4 STAND FOR IRONS	£2.95
HEAT SINK TWEEZERS	45p
SOLDER HANDY SIZE 5	£1.39
SOLDER CARTON	£2.50
SOLDER REEL SIZE 10	£4.87
LOW COST PLIERS	£1.38
LOW COST CUTTERS	£1.99



BENT NOSE PLIERS	£1.89
MINI DRILL 12V (M01)	£8.38
MULTIMETER TYPE 1 100000pV	£6.98
MULTIMETER TYPE 2 20,00000pV	£17.38
MULTIMETER TYPE 3 30,00000pV	£27.98
DESOLDER PUMP	£39.98
SIGNAL INJECTOR	£5.48
CIRCUIT TESTER	78p
HELPING HANDS JIG & MAGNIFIER	£7.98
MINIATURE VICE (PLASTIC)	£1.85



# EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY

VOL 15 N99

SEPTEMBER '86

## NEW SERVICE

A NEW reader service will be introduced in EE next month—a service which will save you some money. With each issue from next month onwards we will include a special EE Reader Discount Scheme page giving information on advertisers' products that are available at special discount to EE readers. The page will also carry a special discount voucher that must be cut out and sent in with your order to claim the discount. Full details of how to order will be given and each participating advertiser will be given some editorial space to describe available products, etc.

We believe the scheme is breaking new ground; we hope it will be beneficial to you, to our advertisers and, through extra magazine sales, to us. EE already has the biggest UK sale of any of the monthly UK electronic hobby magazines (according to the latest Audit Bureau of Circulation figures) so our advertisers have the best vehicle in which to sell their product—we believe this scheme will enhance the benefits.

## OUTSERT

Next month's issue will carry a special yellow card affixed to the outside of the cover (called an outsert). The card will be the first voucher for the scheme and will also publicise the scheme. Because of this, the October issue is likely to be in great demand and we would suggest it is worth ordering your copy from your newsagent now. Last year our October issue also proved very popular and we sold out!

The design shown below will be used to identify the EE Reader Discount Scheme and you will find it on our special page, on the coupons and on advertisements and advertisement literature from participating advertisers. Watch out for it—it can save you money.



*Mike Kenward*



## BACK ISSUES & BINDERS

Certain back issues of EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY are available price £1.25 (£1.75 overseas surface mail) inclusive of postage and packing per copy. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. In the event of non-availability remittances will be returned. **Please allow 28 days for delivery. (We have now sold out of Oct. and Nov. 85 and April 86.)**

Binders to hold one volume (12 issues) are available from the above address for £5.50 (£6.25 overseas surface mail) inclusive of p&p. **Please allow 28 days for delivery.**

**Payment in £ sterling only please.**

## Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL,  
6 CHURCH STREET, WIMBORNE,  
DORSET BH21 1JH  
Phone: Wimborne (0202) 881749

See notes on **Readers' Enquiries** below—we regret that lengthy technical enquiries cannot be answered over the telephone.

## Advertisement Offices

EVERYDAY ELECTRONICS ADVERTISEMENTS  
4 NEASDEN AVE., CLACTON-ON-SEA, ESSEX  
CO16 7HG. Clacton (0255) 436471

**Editor** MIKE KENWARD

**Personal Assistant**  
PAULINE MITCHELL

**Assistant Editor/Production**  
DAVID BARRINGTON

**Assistant Editor/Projects**  
DAVID BRUNSKILL

**Editorial:** WIMBORNE (0202) 881749

**Advertisement Manager**  
PETER J. MEW Clacton (0255) 436471

**Classified Advertisements**  
Wimborne (0202) 881749

## READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply **must** be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

## COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

## OLD PROJECTS

We advise readers to check that all parts are still-available before commencing any project in a back-dated issue.

We regret that we cannot provide data or answer queries on projects that are more than five years old.

## ADVERTISEMENTS


Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should address them to the advertiser or should consult a local trading standards office, or a Citizen's Advice Bureau, or their own solicitor.

## SUBSCRIPTIONS

Annual subscription for delivery direct to any address in the UK: £13.00. Overseas: £15.00. Cheques or bank drafts (**in £ sterling only**) payable to Everyday Electronics and sent to EE Subscription Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. **Subscriptions can only start with the next available issue.** For back numbers see the note on the left.

# INFRA-RED BEAM ALARM

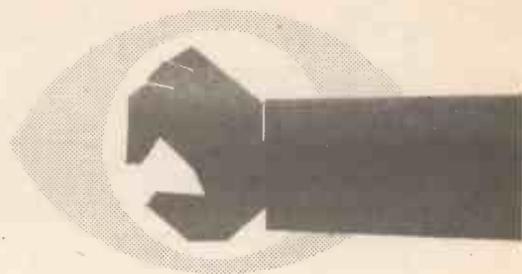

R.A. PENFOLD

## A simple alarm unit with various security applications

IN THE late sixties and early seventies broken beam infra-red alarms were popular in television spy series and the like, usually with the hero defeating the alarm by avoiding the beam or shining an infra-torch onto the receiving sensor. Infra-red alarms are no longer the technological marvels that they once were, and are now regarded as relatively mundane pieces of electronics. They have moved on from those early days though, and are no longer restricted to use over very short distances, such as across a corridor. It was this short operating range which made the early types so easy to defeat. Although an infra-red beam is invisible to the human eye, the transmitting and receiving devices are not, and can be difficult to conceal really effectively. Once an intruder has detected the presence of the beam it is not difficult to avoid it.

Using modern devices and techniques it is possible to produce designs which will operate over much longer distances. In fact systems of this type are no longer restricted to spanning a doorway, or even a room, and they can be used out-of-doors over quite long distances if desired. Units of this type are often referred to as "infra-red fences". The system described here is designed to operate in conjunction with an existing burglar alarm system, and it can be constructed at quite low cost. An operating range of at least ten metres is possible, and by simply modifying the value of one resistor in order to increase the output power of the transmitter it is possible to boost the range to 50 metres or more.

### OPERATING PRINCIPLE

The obvious arrangement for a broken beam alarm is to have a light source aimed at a suitable sensor, with a simple circuit to detect the presence or absence of any significant output from the sensor. In practice this does not work very well as it is difficult to provide a strong enough light beam to reliably switch the sensor between two distinct output levels. The infra-red beam tends to become swamped by the background infra-red level.

The easiest way around this problem is to use a set-up of the type outlined in the block diagram of Fig. 1. Instead of using a

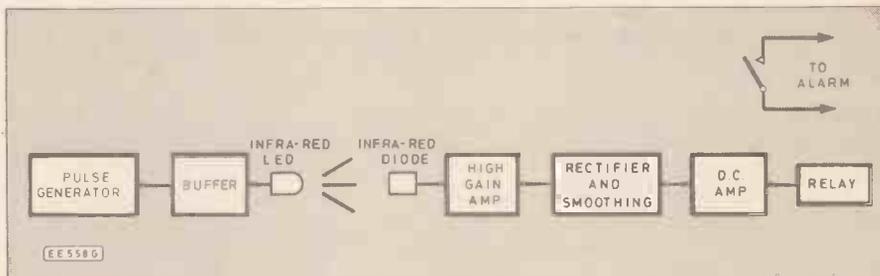


Fig. 1. Block diagram of the IR Beam Alarm.

continuous infra red beam, the special I.e.d. which generates the infra-red signal is pulsed on and off at a fairly high frequency (usually in the range 1 to 100kHz). The I.e.d. is driven from the pulse generator via a buffer stage which enables high I.e.d. currents to be provided. The drive signal is not usually a squarewave, but instead a short pulsed waveform is used. The general idea is to have the I.e.d. switched on for (say) ten per cent of the time so that a very high I.e.d. current can be used, but the average I.e.d. current is kept down to a safe level. For instance, with the I.e.d. pulsed at 500mA with a signal having a 1 to 9 mark-space ratio, the average I.e.d. current would only be 50mA (which is quite safe for a large I.e.d.).

There are several types of device which could be utilized as the sensor at the receiver, but the most common type for this application is a large area photodiode. These offer good sensitivity plus a reasonably wide bandwidth. This second factor is an important one as the received signal is not a continuous beam, but a series of narrow pulses. Although the pulses might be at a frequency of (say) 10kHz, the narrowness of the pulses results in most of the

component frequencies being at much higher frequencies, and the system must have a bandwidth of at least ten times the fundamental input frequency in order to respond to the input pulses properly and make full use of the power economy at the transmitter.

Although reasonably sensitive, the output signal from the sensor diode is not likely to be particularly strong, and it could well be less than a millivolt r.m.s. However, as it is a pulse signal it is easily amplified to a more suitable level using ordinary audio type amplifier stages. Because a.c. coupling can be used there is no problem with drift or changes in the ambient infra-red level causing spurious triggering of the unit.

The amplified signal is rectified and smoothed to produce a d.c. signal that is roughly proportional to the strength of the received signal. When the beam is not broken, the received signal is strong and a strong d.c. output is produced by this circuit. This signal is used to drive a d.c. amplifier which in turn activates a relay. If the beam is broken, the d.c. signal rapidly subsides and the relay switches off. A pair of normally open relay contacts are wired into the burglar alarm circuit. Although the



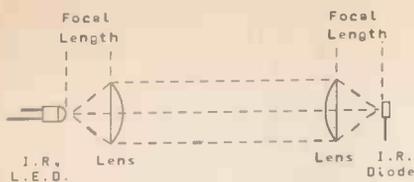


Fig. 2. Simple lens system.

contacts are called normally open types, in this circuit the relay is normally switched on, and it cuts off when the beam is broken. The relay contacts are thus effectively normally closed types, and are wired into the usual loop of normally closed switches in the main alarm circuit. This arrangement is fail-safe in that a failure in the alarm circuit will almost certainly result in the relay switching off, and the main alarm being activated.

## OPTICS

Although the range of a system of this type is much greater than a simple d.c. circuit, it is still difficult to obtain reliable operation at much more than two or three metres. It might be possible to refine the circuits to obtain some improvement, but a much better way of tackling the problem is to add an optical system. By focusing the output from the transmitter into a tight beam the usual fall off in strength as the range is increased is avoided. In practice there is some reduction in beam strength as range is increased due to imperfections in the focusing system and consequent spread of the beam, and the fact that air is not totally transparent. Even with quite a simple and inexpensive lens to focus the beam this can boost the range of the system by a factor of five or more. A lens at the receiver can be used to further boost the range by a similar factor.

Ordinary glass lenses, mirror lenses, or a combination of the two can be used in this application, but in its most basic (double-ended) form the lens system is as shown in Fig. 2.

At the transmitting end a plano-convex lens is used to focus the output from the l.e.d. into a narrow beam. Optically the receiving end of the system is just the opposite of the transmitter, with another plano-convex lens gathering up the output from the transmitter over a relatively large area, and then concentrating the received energy onto the infra-red sensor diode. For optimum results the l.e.d. and detector diode must be quite accurately aligned

behind their respective lenses, and they must be the correct distance from their lenses. The optimum spacing is equal to the focal length of the lens. You do not get something for nothing in the world of physics, and the price that has to be paid for the improvement in range is the highly directional nature of both the transmitter and the receiver. The practical result of this is that the system has to be carefully set up and mounted in a stable fashion if it is to function at all; but optical alignment of the equipment is not excessively difficult.

In the past there has been a problem for the home constructor with an arrangement such as this in that it has been difficult to obtain suitable lenses, and they have been quite expensive once located. Fortunately, suitable plastic lenses can now be obtained at low cost, making a project of this type perfectly feasible as a constructional project. Although in normal optical terms the quality of the lenses is, to say the least, extremely poor, image quality is unimportant in this context. The lenses need do nothing more than roughly focus the infra-red signal in order to give a large improvement in performance.

## TRANSMITTER CIRCUIT

The transmitter uses few components, as will be apparent from the circuit diagram which appears in Fig. 3.

IC1 forms the basis of the unit, and this is the low power CMOS version of the well known 555 timer. It operates here in a form of astable (oscillator) circuit, but it is not quite the standard configuration as steering diode D1 has been included. Normally this type of circuit operates by first charging timing capacitor C2 to two-thirds of the supply potential via both R1 and R2, and during this time the output at pin 3 goes high. C2 is then discharged by way of R2 and an internal switching transistor of the integrated circuit until the charge falls to one-third of the supply voltage. The cycle then starts again with C2 charging via R1 and R2. The output of IC1 goes low during the discharge period.

In Fig. 3, TR1 is a VMOS transistor, and it switches on the infra-red l.e.d. D2 when the output of IC1 goes high and forward biases TR1's gate. In the standard 555 astable circuit the period during which the output goes high is longer than the time it spends in the low state, since C2 charges via both R1 and R2, but only discharges through R2. This is the opposite of what we require, as it results in the l.e.d. being switched on for more than 50 per cent of the time, rather than the ten per cent or there-

abouts that is required. Diode D1 provides a simple solution by bypassing R2 during the charge portion of each cycle. The charge time is then controlled by R1, and the discharge time is determined by R2. By making R2 about ten times higher in value than R1 the required output waveform with a mark space ratio of about 1 to 10 is obtained. The oscillator operates at a frequency of about 3kHz.

Little current is consumed by the oscillator circuit, and TR1 requires no significant drive current. The current drawn from the battery supply is therefore little more than the average l.e.d. current, which comes to just over one milliamp. This low level of power consumption makes battery operation a practical proposition even if the unit is left operating for long periods of time, which is quite likely in a burglar alarm application. Each set of HP7 size cells should be capable of powering the unit continuously for well over a month, or using the unit around ten hours a day the batteries would only need replacement at approximately three monthly intervals.

## RECEIVER CIRCUIT

The full circuit diagram of the receiver unit is shown in Fig. 4. D3 is the detector diode, and this is reverse biased by R4. A small leakage current flows through D3, and the leakage level is dependent on the infra-red level received by D3. The pulses of infra-red energy from the transmitter therefore cause small pulses or current to flow through R4 and D3, generating small voltage variations which are coupled by C4 to the input of the high gain amplifier. The latter is a straightforward three stage common emitter circuit which has capacitive coupling between all three stages. The full gain of all three stages is not required, and R12 introduces a large amount of feedback to TR4 in order to reduce its voltage gain to a more suitable level. The voltage gain of the circuit is still well in excess of 80dB (10,000 times). The detector diode incorporates an infra-red filter which largely prevents problems with ambient light sources swamping the received signal. Tungsten lamps powered from the mains can generate a significant 100Hz infra-red signal, but the coupling capacitors in the amplifier have been given low values so that they provide some attenuation at 100Hz and reduce the risk of mains lighting holding the unit in the unactivated state.

Socket SK1 enables the output of the amplifier to be monitored using a crystal earphone or high impedance headphones. This is helpful when setting up the system as

Fig. 3. Transmitter circuit diagram.


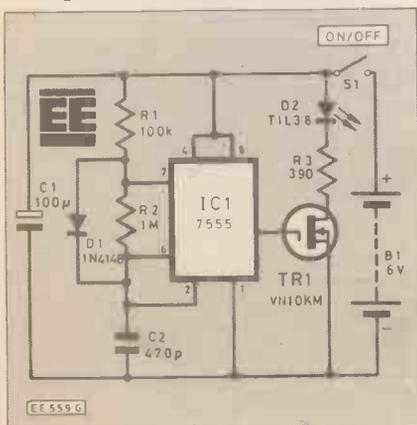


Fig. 4. Receiver circuit diagram.

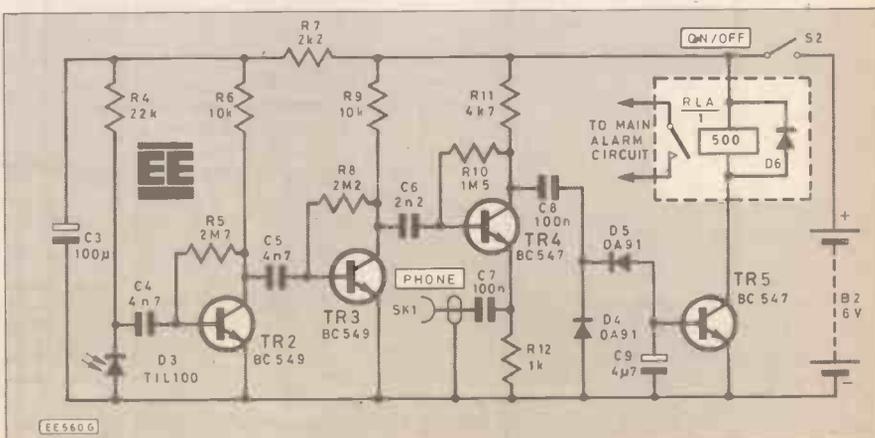

it enables the strength of the received signal to be gauged, making it much easier to set up the system for optimum reliability.

The output from TR4 is coupled to a conventional rectifier and smoothing circuit. The value of C9 controls the time taken for the d.c. signal to decay to the point where the relay cuts off once the beam has been broken, and this time must be kept to just a fraction of a second so that the relay always cuts off before the person breaking the beam moves on and the signal is restored. On the other hand, a very short decay time could reduce reliability and cause spurious triggering of the unit. A decay time of about 100ms seems to be a good compromise.

It is not possible to design the unit to have a very low stand-by current consumption as the relay will remain activated except for any brief occasions when the beam is

broken. However, a relay which has a very low current consumption can be used, and the fact that the voltage and current ratings of the contacts are very low is not a problem in this application where only minute power levels are involved. The total current consumption of the unit is about ten milliamps or so. This will give around 100 hours of operation from HP7 size batteries, and rechargeable Nicad cells probably represent the most practical power source. Alternatively, four HP2 size batteries would be capable of powering the unit continuously for about one month, or for over two months with around ten hours use per day. Of course, if preferred, either or both units can be powered from mains power supply units that supply a well smoothed output at around five to six volts.

Note that protection diode D6 is an integral part of the relay which is a mini-

## COMPONENTS

See  
**Shop  
Talk**  
page 485

### TRANSMITTER

#### Resistors

R1	100k
R2	1M
R3	390
All 0.25W 5% carbon	

#### Capacitors

C1	100µ radial elect. 10V
C2	470p ceramic plate

#### Semiconductors

IC1	ICM7555 CMOS timer
TR1	VN10KM VMOS transistor
D1	1N4148 silicon diode
D2	TIL38 5mm IR l.e.d.

#### Miscellaneous

S1	SPST miniature toggle switch
B1	6 volt (4 x HP7 size cells)

Plastic case about 150 x 100 x 60mm; Printed circuit board (available from the *EE PCB Service*, order code EE536); 30mm diameter lens with 80mm focal length (Maplin); 8 pin d.i.l. i.c. socket; battery holder for 4 x HP7 size cells; PP3 style battery connector; wire and solder

**COMPONENTS**  
approximate  
cost **£22.50**

### RECEIVER

#### Resistors

R4	22k
R5	2M7
R6,9	10k (2 off)
R7	2k2
R8	2M2
R10	1M5
R11	4k7
R12	1k
All 0.25W 5% carbon	

#### Capacitors

C3	100µ radial elect. 10V
C4,5	4n7 polyester layer (2 off)
C6	2n2 polyester layer
C7,8	100n polyester layer (2 off)
C9	4µ7 radial elect. 63V


#### Semiconductors

TR2,3	BC549 silicon npn (2 off)
TR4,5	BC547 silicon npn (2 off)
D3	TIL100 IR detector diode
D4,5	OA91 germanium diodes (2 off)
D6	Part of relay

#### Miscellaneous

S2	SPST miniature toggle switch
RLA1	5V, 500 ohm coil, 14 pin d.i.l. package with normally open contacts and protection diode.
SK1	3.5mm jack socket
B2	6 volt (4 x HP7 size cells)

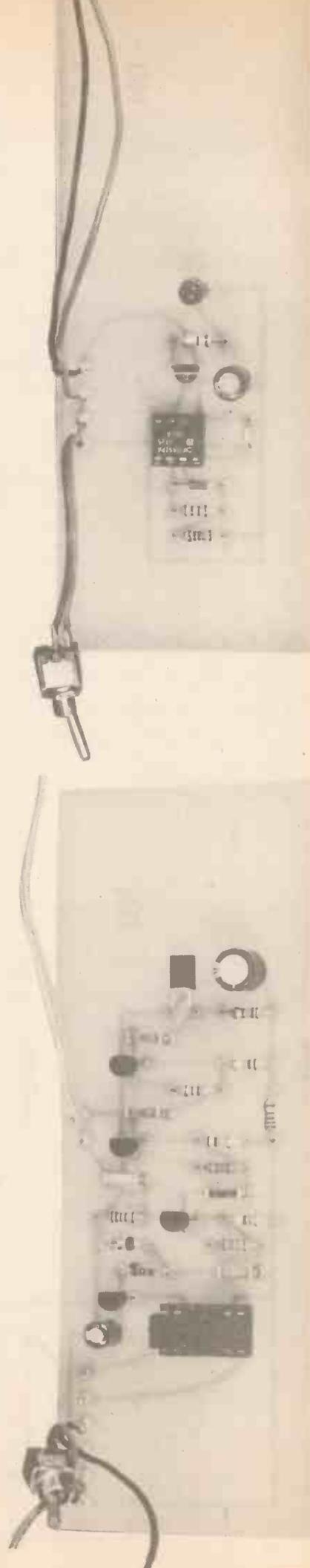Plastic case about 150 x 100 x 60mm; printed circuit board (available from the *EE PCB Service*, order code EE537); 30mm diameter lens with 80mm focal length; battery holder for 4 x HP7 size cells; PP3 style battery connector; 14 pin d.i.l. i.c. socket; wire and solder, etc.







ture type in a form of 14 pin d.i.l. encapsulation.

### CONSTRUCTION

Starting with construction of the transmitter, details of the printed circuit board are shown in Fig. 5. Although the board may

seem to be rather over-size, it is in fact designed to fit into the guide rails which are moulded into the specified case. It fits into the pair of rails nearest the back of the case with its component side facing forwards. Of course, there is plenty of space on the board for mounting holes, and if a different case is used there should be no difficulty in mounting the board satisfactorily.

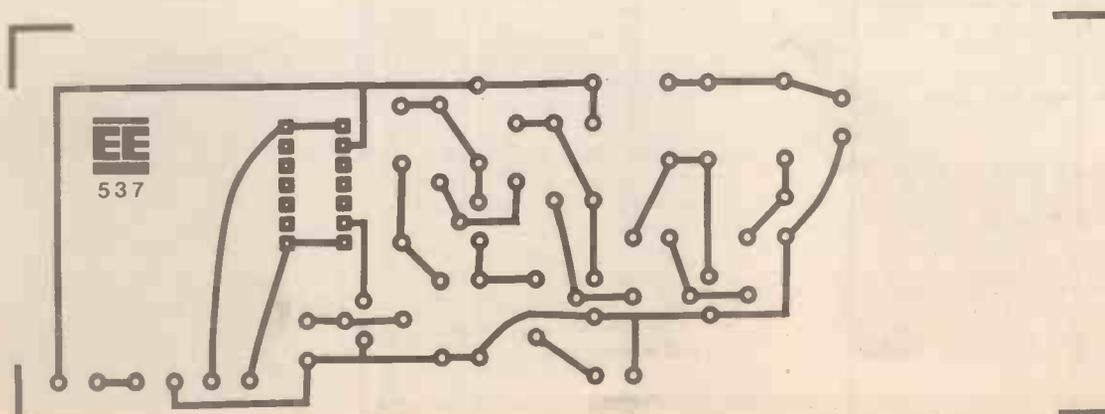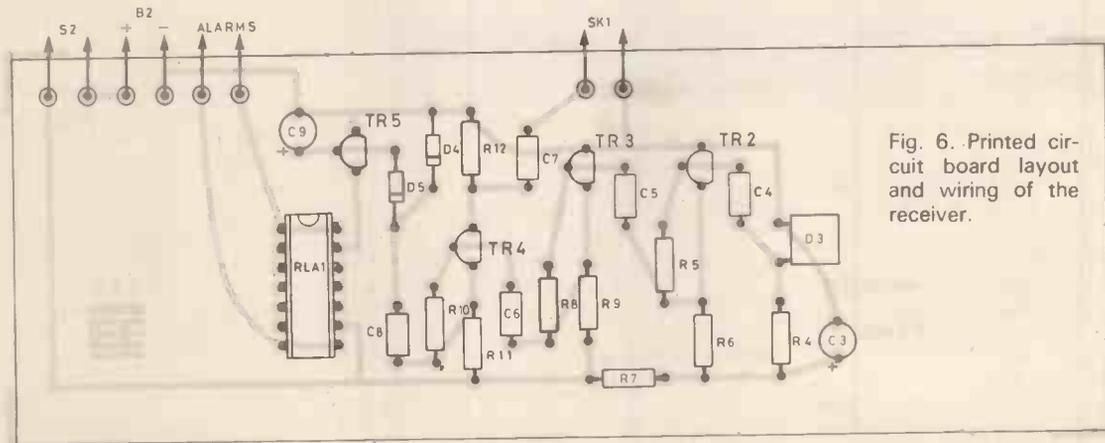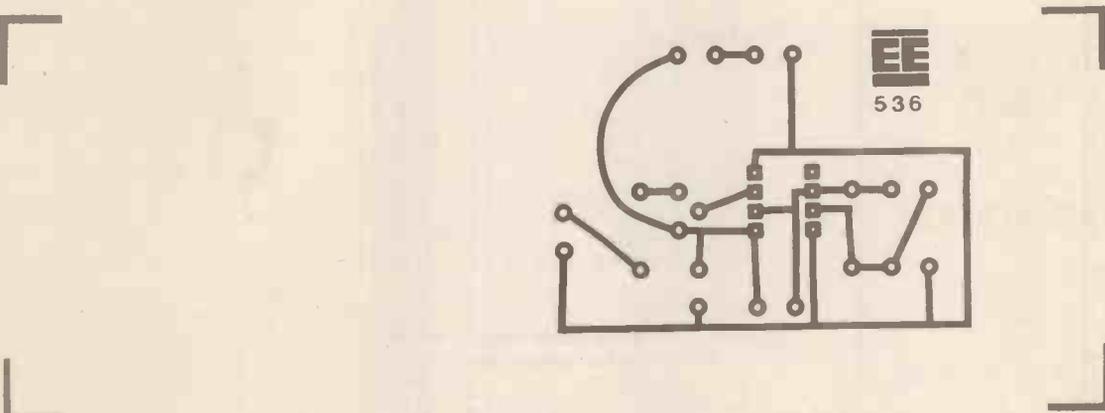
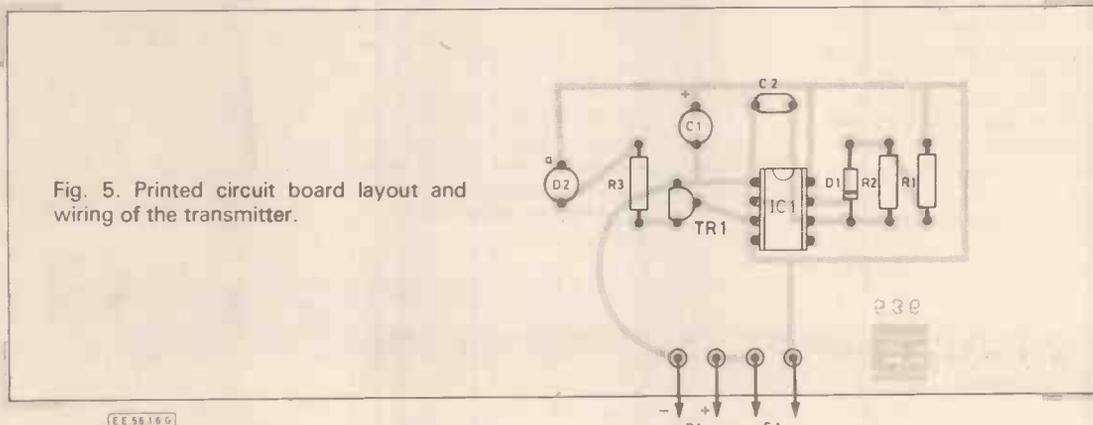
The board itself is easy to construct, and although IC1 is a CMOS device, it has built-in protection circuits which render the usual anti-static handling precautions unnecessary. It is, nevertheless, advisable to use a socket for IC1. The leads of D2 should be trimmed quite short so that it does not protrude too far above the board. This is important because the distance from the



lens to D2 will be inadequate if the leads are left too long, giving a mediocre level of performance.

The lens is mounted on the front of the case, and it must be accurately positioned directly in front of D2. A large offset would impair the performance of the system and would give a peak response that would be well away from a rightangle to the front panel, making it relatively difficult to set up the finished units properly. A 30 millimetre diameter cutout is required for the lens, and this can be produced by first drilling a central hole of around 10 millimetres in diameter and then enlarging it to the required size using a reamer.

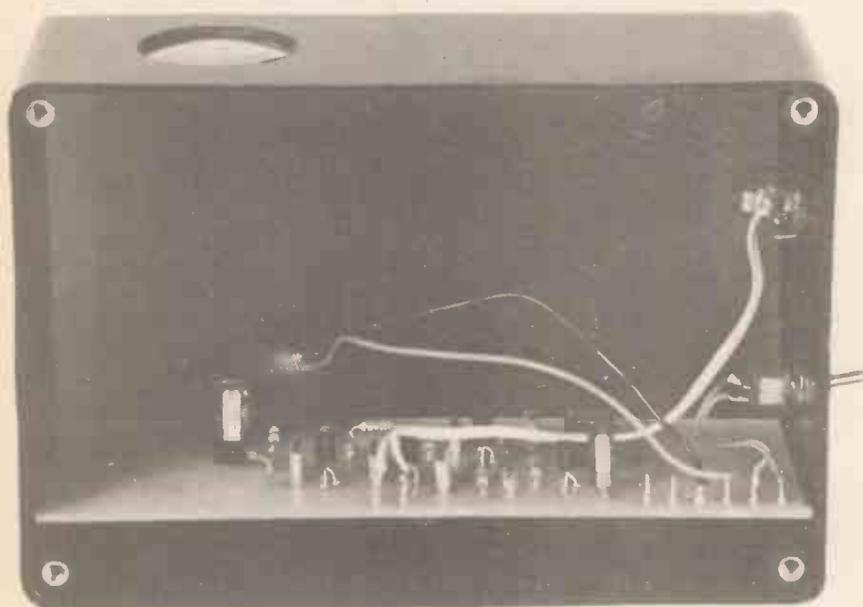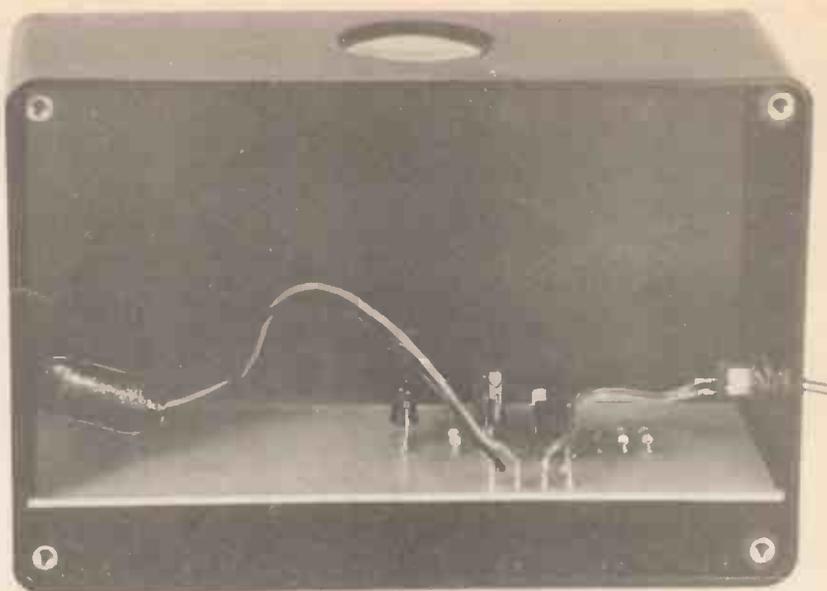The lens has a rim which enables it to be glued in place on the rear face of the front panel using any good general purpose adhesive, but be careful to avoid smearing adhesive over the main part of the lens. There is a slight problem in mounting the lens in that some of the printed circuit guide rails moulded into the case tend to get in the



way. These can be carefully cut away using a small modelling knife, or the lens can be mounted on the front surface of the case (which will not look as neat).

Switch S1 is mounted on one of the end panels, and then the unit is completed by wiring S1 to the board and adding the battery connector. If the unit is powered by four HP7 size cells fitted in a plastic battery holder, connection to the holder is via an ordinary PP3 type battery clip.

Construction of the receiver is along much the same lines as that of the transmitter. Details of the printed circuit board are shown in Fig. 6. The leadout wires of D3 are bent at right angles so that its sensitive surface (the large one which does not carry the type number) faces forwards towards the lens. The SFH205 is a suitable alternative to the TIL100, and the sensitive surface of this device is the curved one.

Diodes D4 and D5 are the germanium type, and these are much more vulnerable to damage by heat than silicon devices. Therefore, when soldering these in place the bit should not be kept on the joint for any longer than is absolutely necessary. The relay has a 14 pin d.i.l. encapsulation, but the middle three pins in each row are missing. The printed circuit board has all 14 holes drilled so that the relay can easily be mounted in a 14 pin d.i.l. socket if desired.


## IN USE

Initially the units should be tested at quite short range as they are then quite easily aligned. However, even at short range the system is still highly directional, and they will need to be aimed accurately in order to obtain proper operation. Things are very much easier if a crystal earphone is used to monitor the output from SK1, as the fairly high pitched tone from the receiver should be audible when the two units are even badly aligned, and adjustment of the receiver's orientation enables the volume of

the tone to be peaked. If the clipping level is reached there will be no further increases in volume if a stronger input signal is obtained, but there will be a noticeable drop in the background "hiss" level.

Setting up the system over a distance of several metres or more is a little more difficult, and the main problem is ensuring that the transmitter is aimed at the point where the receiver is situated. The receiver only has to be slightly outside the main beam in order to reduce the strength of the received signal to a totally inadequate level. The receiver can be used as a sort of field strength monitor to detect the precise direction of the beam, and the orientation of the transmitter can be adjusted by trial and error to home in the beam on the desired point. Alternatively, where possible it is easier if the transmitter can be aimed in the right general direction, and the receiver is then moved to a point within the beam. Try to get the units set up so that a strong signal is picked up at the receiver, as this gives optimum reliability.

The distance from each photocell to its lens is slightly less than the 80 millimetre optimum, but this only marginally reduces the maximum operating range, and has the advantage of making the system slightly less directional and easier to set up. A reliable operating range of 10 metres or more should be possible, and this can be considerably boosted by reducing the value of R3. This resistor can be made as low as  $4\Omega$  in value, giving a pulse current of around 500 milliamps. This will increase the current consumption of the transmitter though (to about 50 milliamps with R3 at  $4\Omega$ ), and R3 should not therefore be any lower in value than is really necessary. □

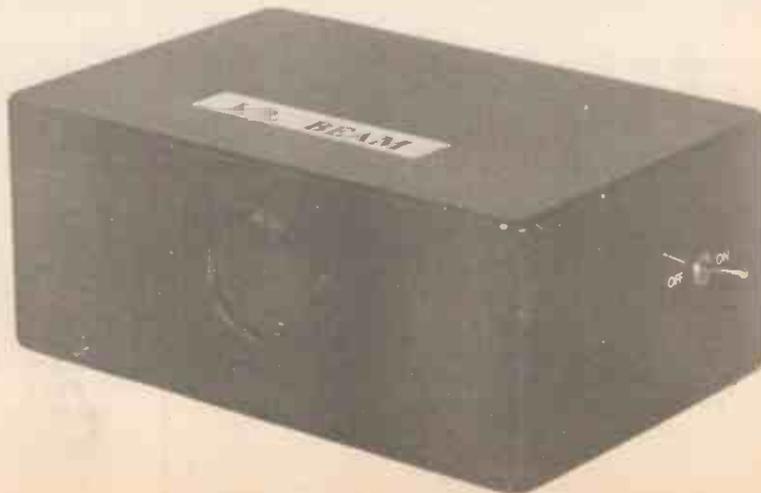

# FOR YOUR ENTERTAINMENT

BY BARRY FOX

## Comdex

I spent a few days in Georgia talking modems with Hayes; the privately owned US company which has quietly succeeded in bringing some order into the chaos of computer communications and electronic mail. The Hayes protocol has become a *de facto* standard. More on modems and Hayes protocol in a future month; it's a story on its own. While in Atlanta I visited Comdex, the computer trade's exhibition and conference held at the World Congress Centre. Some snippets are worth passing on.

Film company Polaroid has cleverly stolen a march on the US computer industry with an offer to recover data from floppy discs which have been damaged by misuse. Most magnetic media companies will replace a faulty floppy, but they balk if the disc has been mistreated. In any case you have still lost the data, which is usually far more valuable than the disc.

Polaroid now offers a Data Rescue Service in America. Anyone who has bought a Polaroid disc and damaged it can return it to the company. At no cost, and usually within 48 hours, Polaroid retrieves as much data as possible, copies it onto a new disc and posts it back to the owner.

Actually this isn't all that clever. Floppy discs are only circular sheets of magnetic tape. The trick is to find a solvent which will shift sticky materials from the disc surface but not break down the resin which binds the oxide to the plastics base film. Polaroid, who make the discs—or in the past has bought in from other manufacturers—is obviously in the best possible position to know the best solvent. As a publicity stunt Polaroid challenged the US computer press to try and find a way of contaminating a disc so that data was irretrievably lost. They tried everything from chilli sauce to ice cream. Polaroid cleaned it all off. The only loss was two per cent of data destroyed when one journalist made holes in the disc by stapling it to the sleeve. So far Polaroid isn't running the scheme in the UK.

## Big Blue Rules

Main impression at Comdex was that IBM rules the roost. Apple weren't there at all. Only Atari and Commodore, with the Amiga, were putting up a struggle against total domination of the PC industry by Big Blue.

The new IBM PC convertible lap-top, which will sell for 2000 dollars, used controversial new technology for the screen. IBM promises 8 hours operation from a single charge of the built-in nickel cadmium batteries. The only way to achieve this is with a passive screen of liquid crystal, which modifies reflected light instead of generating its own.

The PC convertible screen is a dot matrix display capable of resolving 25 lines of 80 characters each or a graphics image built up from 640 by 200 individual picture elements or pixels. All l.c.d.s suffer from the same problem; the image has low contrast, and the text appears as dark grey

on a light grey background. Room light reflects off the glass front of the screen and degrades contrast even further.

But IBM believes it has solved the problem of glare and stray reflections. Conventional screens use a sandwich of two glass or plastics sheets, a thin sheet to contain the liquid crystal fluid and a thick sheet to protect the thin under-layer. It is the air gap in between which causes odd reflection effects in ambient light. The IBM lap-top screen uses a single layer of transparent, flexible plastics. The l.c.d. fluid backs directly on to this, so the screen is soft to the touch. It deforms when pressed and the image disappears where it is touched. Although this does not matter, because there is normally no need to touch the screen, IBM acknowledges that if someone prods the screen with a sharp object the plastic will puncture and the l.c.d. material ooze out.

## CD ROM

Sony believes that CD ROM, the new technology which relies on a laser-read 12cm compact disc to store 600 megabytes of data instead of an hour of music, will be a consumer product by the end of the year. Sony began pressing CD ROMs at its US factory in Terre Haute, Indiana, in May. The company has also now started to sell CD ROM drives in bulk to other manufacturers for incorporation in home computers.

There are two types of Sony CD ROM drive. The CDU 5002 fits neatly into the slot in a computer which is normally used for a floppy disc drive. The CDU 100 is a stand-alone unit which plugs into the rear of a computer to offer an extra source of data. Sony is charging manufacturers a trade price of around 300 dollars for the CDU 5002 and 400 dollars for the CDU 100. An extra circuit board must be fitted inside the computer, but the extra cost to end user should still be well below 1000 dollars. For this premium on the price of a conventional computer, the customer will be able to read data from an optical disc as well as read and record with magnetic discs.

The stumbling block so far has been industry agreement on how a home computer will search through the data stored on a CD ROM. Although there is now a standard called CDI (CD Interactive Media) for the method of recording data on the disc so that it can be retrieved by any player, there is still no agreement on a protocol for searching through the retrieved data. In an effort to break the deadlock with market force and create a standard Sony has signed a joint venture deal with software company Knowledge-set of Monterey, California.

The joint venture, to be called Publishers Data Service Corporation, PDSC, will offer publishing companies a one-stop service. Sony's factory in Indiana will order and format the publisher's data, for instance, an encyclopaedia, and transfer it to digital tape. The same factory will then use this tape to produce a master disc from which CD ROMs are duplicated.

Knowledge-set will provide a retrieval program called KRS (Knowledge Retrieval System) so that a home or business computer can search through the data on the disc. KRS is compatible with any IBM PC. The joint venture promises a four week turnaround, from raw data to finished CD ROMs ready for sale. The Indiana plant can press up to 1-5 million discs a month. They can be either music or data discs.

## Towering Inferno

Finally a warning. If you ever visit a Comdex show, don't whatever you do mention the word "fire", let alone shout it.

When the MGM hotel in Las Vegas went up in flames it was during a Comdex show. This year at Atlanta in Georgia the delegates were getting decidedly twitchy by the time they left the peanut state.

Both the Omni and Marriott Marquis hotels in Atlanta have those scary glass lifts which run on vertical tracks up the outside of the walls. And this year both had fire scares. At the Omni hotel one of the lifts caught fire at 2am. When the fire alarms sounded no one took it seriously, until they started coughing on the kind of smoke which only a burning electric motor can generate.

At the Marquis the next day things were even more dramatic. All three of the lifts serving the 47 floors of bedrooms which overlook the biggest atrium in the world suddenly stopped dead. They then descended at high speed to the bottom floor.

Alarm bells rang on each landing and flashing lights told guests to use the stairs. Having heard about the Omni smoke they did, and weren't seen again for an hour. Later I pieced together what had happened.

Sensibly the hotel designers built smoke detectors into the lift system at engine room level, down in the basement. One whiff of smoke and the whole thing shuts down. Unfortunately, the hotel staff like to gather in the basement to puff on a few cigarettes, of one kind or another, and shoot the breeze about life in general.

"They aren't supposed to do it, but they do," a hotel receptionist confided, in between hoping I was having a nice day. Once the crafty smokers are caught, the lifts go up again. Unfortunately this is little consolation to anyone who has just started out on a 47 floor hike down the stairs. They do not have such a nice day. The Marquis management has not yet thought of a way of telling people on the stairs that the fire is out and the lifts are working. Maybe by next year's Comdex!

**Amiga can hook up to a video source with Genlock—but can it compete with IBM?**





*a regular feature for the Spectrum Owner...*

by Mike Tooley BA

## Alien zapping freaks! Build your own Custom Joystick

**T**HIS month we shall follow the theme introduced last month by taking a brief look at the RAM chips used in the Spectrum. We shall also be introducing another of the Spectrum's system variables and showing how readers can make their own "custom designed" joysticks.

### RAM chips

From last month's memory map, readers will see that the Spectrum's memory is divided into ROM (addresses from 0 to 16383 decimal) and RAM (addresses from 16384 to 65535 decimal). The latter address space is, in fact, populated by two types of dynamic RAM; the lower 16K being provided by eight 16K x 1 bit chips (4116, or equivalent) whilst the upper 32K is provided by eight 32K x 1 bit chips (4532, or equivalent).

The pin-outs for the Spectrum's RAM chips are shown in Fig. 1. Readers should note that the 4116 (which are now somewhat elderly) require no less than THREE separate supply rails! The 4532 devices are, thankfully, a little more up to date and only require a single +5V rail. The reason for the use of two different RAM types is simply that the Spectrum started life as a 16K machine and only later became available as (or expandable to) a full 64K machine.

At the time that the Issue 2 Spectrum emerged, full-specification 32K and 64K RAM devices were rather expensive. Doubtless it was for this reason that the RAM devices fitted in the upper 32K of the early 48K RAM machines were "failed" 64K devices in which just one half was "good"! These chips were coded with an "H" or an "L" and appropriate links provided on the p.c.b. Naturally, ALL chips in the 32K block MUST be of the same type; either all "H" or all "L"!

It seems likely that, on later issue Spectrums, the upper 32K may be populated by fully functional 64K RAM chips of which only half is actually put to use. With a little thought someone might even have managed to "page-in" the unused 32K. So, if you have had a go at this, why not drop me a line so that I can pass on the relevant information.

### REPDEL

This month we put the REPDEL system variable under the microscope. REPDEL is at a decimal address of 23561 and it contains the time delay (in fiftieths of a second) that a key must be held down before it begins to repeat. Whilst REPDEL is normally initialised to 35 (giving a delay of 35/50 sec) the value can be readily changed by simply poking a byte into 23561.

To produce a delay of exactly 1 second, for example, we would need to make the value in REPDEL equal to 50. This can be achieved by a statement of the form:

POKE 23561,50

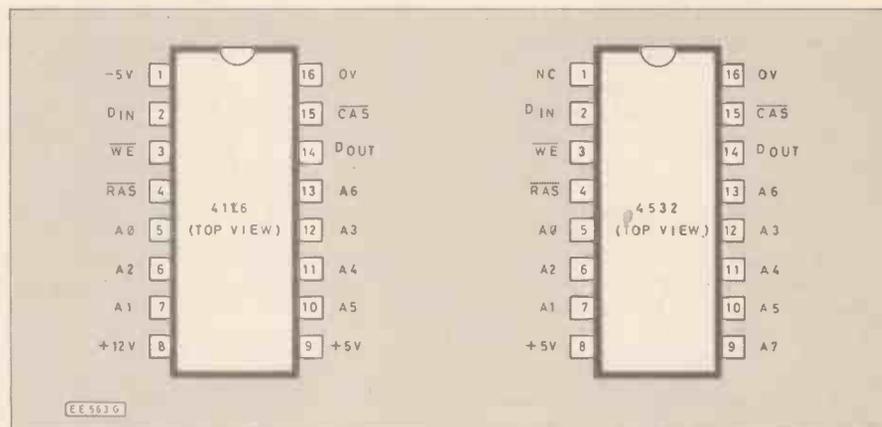


Fig. 1. Spectrum RAM pin connections for the 4116 and the 4532. Note that the 4116 requires three separate power supplies!

Readers would be forgiven for thinking that POKEing REPDEL with a value of zero would produce no delay at all. This, however, is not the case! Surprisingly, POKEing REPDEL with 0 results in the longest rather than the shortest possible delay. The reason for this apparent anomaly is simply that the Spectrum's operating system decrements the value contained in REPDEL until it reaches zero before exiting the key repeat delay loop. When POKEd with zero, REPDEL first decrements to 255 (i.e. -1) and thus the delay loop is repeated a total of 256 times.

### DIY Joystick

Several readers have accused me of taking a rather more serious approach to computing on the Spectrum than is really warranted by what has become accepted primarily as a "games" machine. To redress the balance here is a little project to warm the cockles of the hearts of all inveterate games players!

Most arcade games are greatly improved when using a good quality joystick. With this in mind, and having tried a number of commercially available joysticks with only moderate success, I recently set about producing my own "custom joystick".

Whilst hardened games addicts may disagree, my own preference is for a joystick

with very light but positive directional control used by the right hand with an entirely separate "fire" button operated by the left thumb. Furthermore, my "ideal" unit would be "hand-held" rather than having to rest on a flat surface.

### Circuit

The circuit diagram of the joystick is shown in Fig. 1. The four direction switches, S1 to S4, are microswitches mounted on a "professional" joystick assembly.

Figs. 2 and 3 respectively show the circuit and internal wiring of the joystick. The four direction switches, S1 to S4, are the microswitches. The switches provided on this unit are single-pole changeover types and, in this application, only the "make" (normally open) contacts are employed.

The exterior view of the prototype joystick, showing the control layout, is depicted in Fig. 4. Readers will doubtless wish to vary the layout to suit their own individual requirements. The Spectrum joystick connector (pin view) is shown in Fig. 5. This is

an "Atari standard" 9-pin D-connector in which pins 5, 7 and 9 are unused and simply left disconnected.

### Auto-fire unit

For "alien zapping freaks", Fig. 6 shows a further enhancement of the custom joystick which provides automatic operation of the fire button at a rate determined by the setting of VR1.

This circuit uses a 555 timer running in astable mode coupled to the joystick unit by means of an opto-isolator. This latter component is simply a standard single-transistor low-cost type housed in a conventional 6-pin d.i.l. plastic package.

The prototype auto-fire circuit was built in a separate plastic case (identical to that used for the joystick unit) and the supply derived from an internal PP3 9V battery. The prototype auto-fire unit was coupled to the joystick box using a short length of twin flex terminated with two 1mm plugs. Whilst this arrangement will prove quite satisfactory for occasional use, some constructors will undoubtedly want to mount the auto-fire unit within the joystick housing. This should not present too great a problem however, since space is very much at a premium, careful attention will have to be paid to layout. Good luck—and happy "zapping"!

# CUSTOM JOYSTICK WITH AUTO FIRE

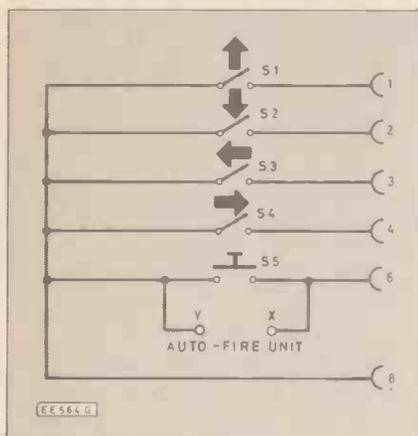


Fig. 2. Circuit diagram for the joystick.

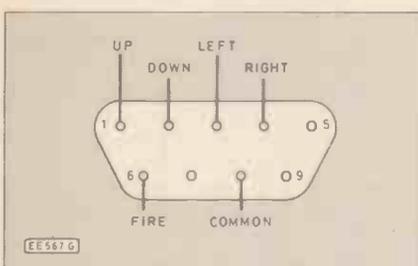


Fig. 5. Standard joystick interface connections (pin view).

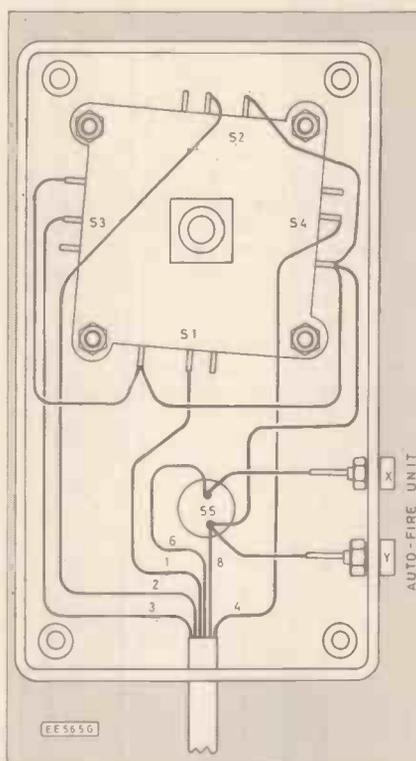


Fig. 3. Joystick internal construction and wiring.

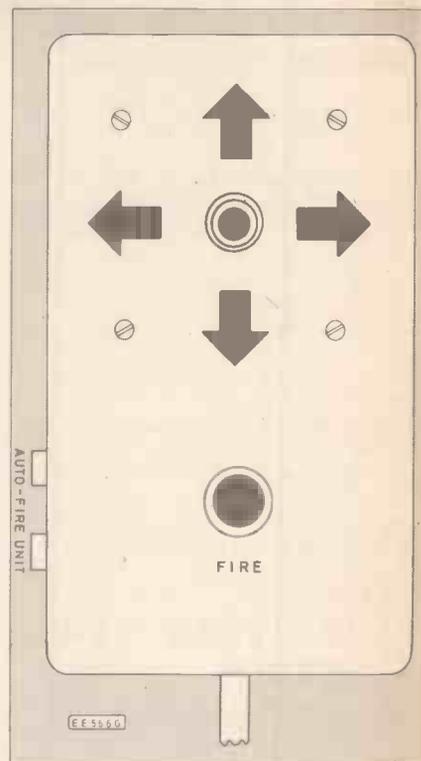


Fig. 4. Control layout of the joystick.

## COMPONENTS

### Joystick Components

Plastic case (approx. 110mm x 60mm x 30mm); joystick switch assembly (S1 to S4); momentary normally open push-button switch (S5); sockets (2 x 1mm); 9-way D-connector (to suit joystick interface); 6-way flexible cable (approx. 1m).

### Auto Fire Components

#### Resistors

R1 10k  
R2 10k  
R3 270  
All 0.25W ± 5%

See  
**Shop  
Talk**  
page 485

#### Potentiometer

VR1 100k linear carbon

#### Capacitors

C1 10µ p.c. elect. 16V  
C2 100µ p.c. elect. 16V

#### Semiconductors

IC1 555  
IC2 Opto-isolator (see text)

Approx. cost  
Guidance only

**£12**

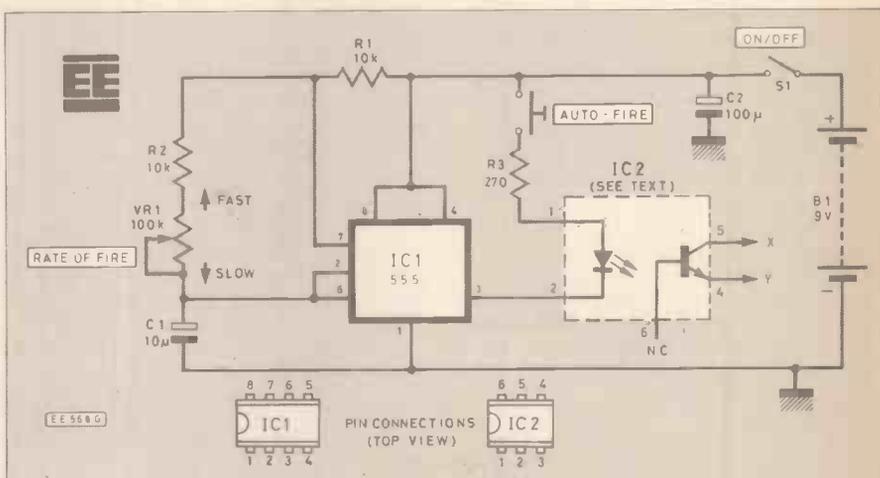


Fig. 6. Circuit diagram for the auto-fire unit.


If you have any comments or suggestions for inclusion in *On Spec*, please send them to:

Mike Tooley,  
Department of Technology,  
Brooklands Technical College,  
Heath Road,  
WEYBRIDGE,  
Surrey, KT13 8TT

P.S. Don't forget to include a large (A4 size) stamped addressed envelope if you would like to receive a copy of our "Update"!
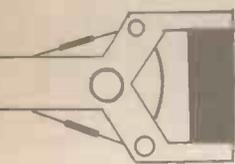
### Next Month

Next month we shall be reviewing some enhanced interpreters for the Spectrum and describing the construction of an "infallible" reset switch. This handy unit allows users to recover from BASIC and machine code program crashes without having to erase the entire contents of the Spectrum's memory. See you next month!



# Robot Roundup



NIGEL CLARK

## MECHANICAL SERVANT

THE DREAM of the mechanical servant has been around for a long time, fostered by growing automation in industry and the imagination of a large number of writers, particularly in science fiction. The difficulties encountered so far in making the dream reality have hardly dented the belief that it is possible to make a mechanical human.

For the majority of people anything that falls short of the ideal cannot be called a robot and expectations are high that it can be achieved with the might of the "miracle" microchip. A brief look at what can be achieved with the present technology and knowledge is sufficient to show that mechanical humans are a long way from becoming a fact. However, there is still a lot happening in the world of robots and the aim of this new regular feature is to reflect the trends in what is called the "personal" end of the market.

It is always useful to start with a definition of the area to be covered. Personal robots can be a problem in that everyone knows when they see one but trying to set down criteria can be difficult. This column will try to concentrate on devices which can be programmed either directly from an on-board processor or indirectly from a host computer. I use the term program loosely to include instructions given to toys, like *George Compurobot*, through a keypad.

A simpler way of finding out what will be covered here is to split the available machines into three categories—arms, bugs or turtles and toys.


## ARMS

Arms come in all shapes and sizes. Most are used in education and are usually smaller, cheaper versions of their industrial cousins with prices ranging to a maximum

of about £4,000. There are two types, articulated and Scara. The articulated are the dinosaur-like devices which operate in the vertical plane, whereas the Scara, which stands for Selective Compliance Assembly Robot Arm, works in the horizontal.

Within these two categories there are many different versions with prices usually depending on their complexity. The degrees of freedom, which govern their flexibility, vary from three to six with the usual number being five.

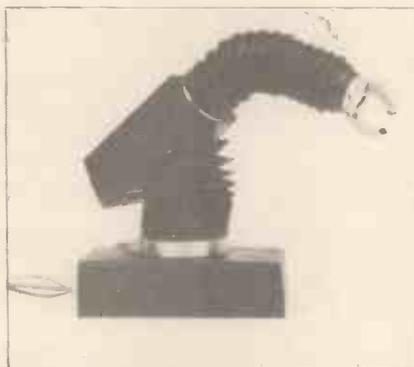In terms of the human body they are waist, shoulder, elbow and two wrist



The *Ogre* servo-assisted arm.

movements, rotation and up and down or pitch. The sixth degree is a sideways movement of the wrist or yaw. In addition there is an end effector, usually a gripper which is sometimes included in the number of degrees of freedom. Most grippers are two-fingered pinchers but there are three-fingered versions and some machines can take other devices.

The drive systems are equally, if not more, varied. The older models use stepper motors and nylon cord transmission

systems. Steppers have the advantage that they can be instructed to move a certain number of steps without feedback to assess when the required movement has been completed. They are slower, however, than the now more popular d.c. servos, which do need feedback.

Scaras, such as the *Cephek* from Reekie Technology or the *Ivax* from Feedback Instruments, are mostly powered by d.c. motors with a toothed belt drive, nylon cord having been found to slip. Articulated arms go in for more exotic systems such as the servo-driven screw drives of the *Ogre*, the servo powered screw-driven pistons of Remcon's Teachrobot or the oil hydraulic system of Feedback's HRA 933 and 934.

Positional feedback is usually obtained by optical encoders which use light reflecting from a disc on which there are black and white stripes.

Most can be obtained in kit form or fully built, the advantage of the kits, apart from their being cheaper, is that a detailed knowledge of the device can be obtained as it is built. They come complete with software for operating the system either by way of their own processors or from popular micros like the BBC B or increasingly the IBM PC.

Most manufacturers, like LJ Electronics, maker of the *Atlas*, or Cybernetic Applications, maker of among others the *Neptune* and *Serpent*, consider that their arms are only part of a total robot system and have built-up work cells to show how their arms can be used in a manufacturing environment. They include conveyor belts and sorting and storing systems. Cybernetic has recently gone a stage further by including a milling machine on which small items can be made which are then checked and sorted by the rest of the system.

Although there have been some problems in the market recently with Colne

Seymour Papert, reported to be the "father" of the turtle language—LOGO.



Even a child can teach a Neptune robot, when fitted with touch sensors.



Robotics being liquidated and Powertran Cybernetics assimilated into its parent company, Feedback Instruments, there are still a number of new developments.

Maker of the *Ogre*, L. W. Staines, is planning to launch a two-armed robot called *Troll*. It is based on the same robust technology as the *Ogre* and its two arms can perform tasks together. Recently a new name has appeared, *Spectravideo*. Already well-known for its computer peripherals, this company has announced a new low-cost four-axis arm with three clip-on end effectors.

## BUGGIES

Buggies or turtles are small mobile computer peripherals which initially were designed to help in education, particularly the teaching of maths where abstract concepts could be made physical. The turtle name came from the innovative work of an American, Seymour Papert, who wrote the language which they mostly use, LOGO, and used it to control small turtles on a screen before the mobiles were considered.

The devices are usually two wheeled, using stepper or servo motors, with a pen which can be raised or lowered to draw diagrams under the control of a computer.

There have been casualties here as well. *Valiant Designs* produced an infra-red controlled turtle which proved very popular but the company has since closed.

One of the earliest companies, however, is still around. *Jessop Micro Electronics* with its creatively-named *Jessop Turtle*, which looks like an upturned mixing bowl, is still selling steadily.

Here again manufacturers are finding that having a robot is not sufficient and two of the newer companies have developed a large amount of support material. *Clwyd Technics'* school-designed *Trekker* comes with programs and documentation for a range of school courses in which the mobile can assist learning and has been well received. *Zero* from IGR has bump and sound sensors and a line follower and the company is hoping to move out of education with some specially-written games.

## TOYS

At the cheaper end of the market are the "toys". Personal robots hit the headlines in this country about two years ago when *Androbot's Topo* was launched with the

expectation that RB Robot's RB5X would follow soon. Despite all the ballyhoo it quickly became apparent that they were little more than expensive, more than £1,000, toys and they failed to sell.

The companies which went for more reasonably-priced toys, like Tomy of the US, proved more successful. Tomy robots can, with some persuasion, react to speech, be programmed in a simple way and are mobile, like George, the Compurobot. The company is now importing the *Petster* range, which has similar capabilities, but instead of looking like miniature R2D2s they resemble furry toy cats, the ultimate in cuddly robots.

The three-way split, however, leaves out two areas which do not fit easily into any category, the Heros and kits. Lego, Fischertechnik and more recently Meccano, are providing packages which though appearing to be toys allow quite sophisticated devices to be constructed.

A buggy can be built from Lego which can be controlled by a switch panel or by a computer. *Fischertechnik* has recently expanded its range of computing kits to include a simple arm and Meccano has been assessing the market.

All have attracted interest from the education market because of their relatively low cost and flexibility and increasing amounts of software are being written for them.

There is also a set of kits from Milton Bradley which though they are more obviously aimed at the toy market their movements can be controlled by a simple keypad and can give an easy introduction to many robotic concepts.

The Heros are much more complex, being intended for higher levels of education. When *Topo* was receiving much attention *Hero 1* was also included as an example of how personal robots were developing, mainly because it was mobile and had a vaguely similar shape.

However, that was the end of the similarities. *Hero* had been designed with education in mind and had many more facilities than *Topo*. It had an on-board processor, with possibility of expansion, light, sound and movement sensors and a range-finder, a four-axis arm, speech and a comprehensive robotics course based around it.

Made in the US by Zenith/Heathkit it is imported by *Maplin Electronic Supplies* and is still selling for about £2,200 ready-built or £1,200 in kit. Recently its upgra-

ded version, the *Hero 2000* became available in this country with far larger ROM and RAM, improved speech and a five-axis arm selling for £2,200 plus VAT for the kit.

## THE CHALLENGE

Robots have a long way to go before they match the ultimate fantasy but developments are being made all the time. As BP discovered when it held two "Build-A-Robot" contests for schools and youth organisations, there is plenty of original thought around.

After its first contest, in which a block had to be found and collected in the shortest possible time, the organisers thought they would make the second one more difficult. A machine had to be built which would fetch a drink on request. It was thought this might prove too difficult, until the results were seen.

A similar "impossible" challenge has been set by Dr John Billingsley of Portsmouth Polytechnic—the building of a robot ping-pong player or *Robat*. That followed his *Micromouse* challenge which attracted interest from all over the world, lately in Japan.

The first prototype *Robat* machines have been seen and some have developed an efficient hand-eye co-ordination and been able to hit the ball. The next stage is to impart some direction to the resulting hit.

The big stumbling block to any form of "human" robot is the development of an intelligence. How to react quickly to all the inputs which can be received through a series of accurate sensors or spoken instructions is a limiting factor in all robots. There is plenty of work going on around the world in the area of artificial intelligence and Britain is one of the leaders in the field.


*The world of personal robots is wide-ranging and fascinating and I intend to cover it thoroughly. If you have any points you wish to make or any new products or developments which you think should have a wider audience I can be contacted through the magazine.*

*The Valiant infra red sensitive turtle—now defunct.*



*The now famous Hero 1 marketed in the UK by Maplin.*

# SIMPLE PRINTER BUFFER

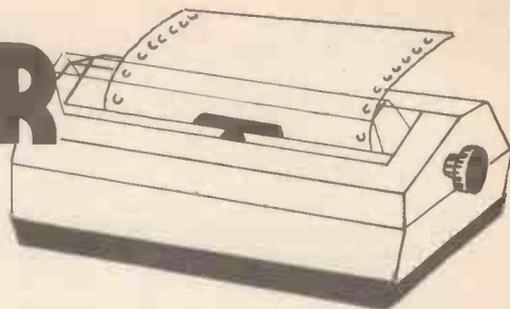

W. HUNTER

## An invaluable addition to any computer / printer set-up with a Centronics interface

A PRINTER buffer is one of those items which you will not miss until you've used one. Any serious computer user will find the circuit described here is really useful. (However we do not recommend this project to readers who have not built other projects successfully.) It allows the continuation of data or text entry whilst the previous letter, account, listing or what-have-you is printed out.

The commonest printer interface amongst cheaper printers and microcomputers is the Centronics Parallel Interface. It is available on the ubiquitous Epson range of printers, which can be driven by almost any computer. The printer buffer described in this article uses the Centronics Interface and has been designed for simplicity in construction and application. It fits between the printer cable from the computer and the printer itself. Whenever the computer wishes to send text to the printer, the buffer will accept the text as fast as the computer will transmit it, and then feed it slowly to the printer. The computer transmission will be at very high speed since the parallel interface is not constrained by a fixed Baud rate.

The buffer can accept text until its memory is full—that is 16K characters, at

which stage it signals to the computer to stop. Meanwhile the buffer is feeding text out to the printer at the printer's maximum acceptance rate. Depending on the printer it might be 100 characters per second (cps) for a matrix printer down to 12 cps for a daisy wheel printer. Very often, the buffer's 16K memory will be enough to accept all the computer's output at one go, freeing the computer for use in only a few seconds. The printer itself will be occupied for minutes as the buffer feeds out the full text at the printer's own speed. If the computer attempts to output more than the buffer can hold, it is halted at the moment the buffer is full. The buffer will then demand more text from the computer at the rate that the old text is sent to the printer.

### CIRCUIT

The heart of the buffer is the Motorola 6802 central processing unit (CPU) shown in Fig. 1. It is almost identical to the long-running 6800 but the 6802 offers the advantage of an on-board oscillator, simplifying the circuit. The CPU executes a program that is held in the 2716 which is a 2K byte EPROM. The 6802 CPU can access the computer and the printer through the 6821 parallel interface adaptor (PIA). This remarkably cheap device has its peripheral lines divided into two sets, known as Port A and Port B. Each set comprises eight data lines for either input or output, and two control lines for handshaking. In this design, port A is used as an input from the computer whilst port B is the output to the printer. The PIA must be configured correctly to perform the startup sequence at switch-on.



## COMPONENTS

See  
**Shop  
Talk**

page 485

### Resistors

R1,R6 10k (2 off)  
R2 to R5 4k7 (4 off)  
 $\frac{1}{4}W \pm 10\%$

### Capacitors

C1 47 $\mu$  elect. 12V  
C2,C3 33p (2 off)  
C4 10n  
C5 to C8 100n (4 off)  
C9 470 $\mu$  elect. 16V

### Semiconductors

IC1 MC6802 CPU  
IC2 MC6821 PIA  
IC3 2716 EPROM  
IC4,IC5 6264P RAM (2 off)  
IC6 74LS00 Quad  
NAND Gate  
IC7 74LS02 Quad NOR  
Gate  
IC8 7805 +5V  
regulator  
D1 OA202  
D2-D5 1A Rectifier bridge

### Miscellaneous

S1, S2 Miniature panel  
mounting push  
button switches (2  
off)  
T1 Mains transformer,  
3VA rating, 7 to 9  
volt output  
FS1 Mains fuse in  
fuseholder, panel  
mounting  
SK1 Centronics type 36  
way socket (IEEE-  
488)  
PL1 Centronics type 36  
way plug, cable or  
IDC.  
X1 4MHz crystal  
Case, minimum size approxi-  
mately 180 x 120 x 65mm;  
ribbon cable; double sided  
p.c.b. see Shop Talk; connec-  
tors, etc.

Approx. cost  
Guidance only

**£31**

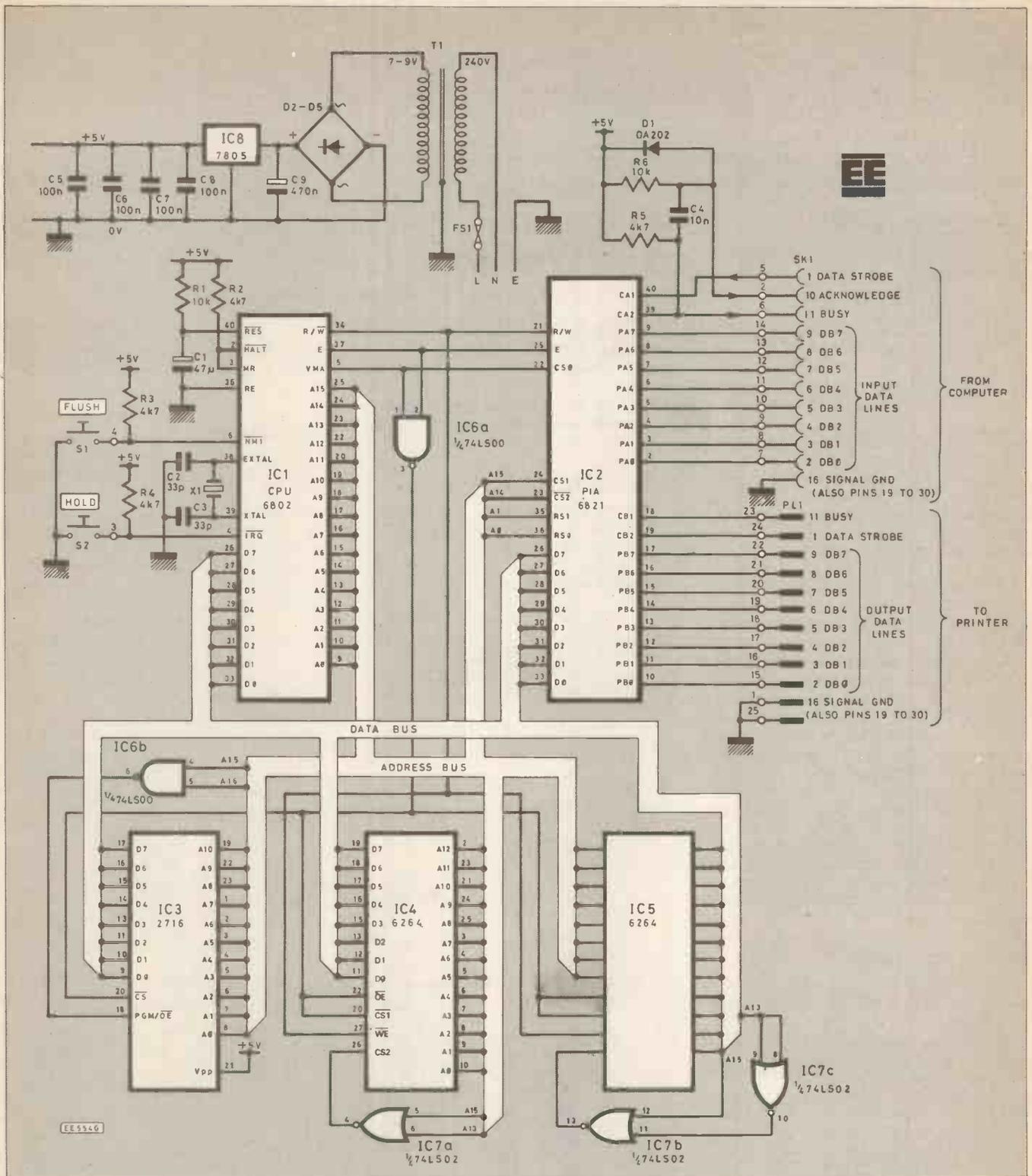


Fig. 1. Complete circuit diagram of the Printer Buffer.

Memory (i.e. RAM) is available in many different types of integrated circuits these days. The 6264 chips used in this design are part of the family known as "Byte-wide" memory chips, since they have eight parallel data lines. With these chips a byte of data can be read from one chip in one access cycle, making design simpler than with other types.

Each of the 6264 chips will hold 8K bytes, making a limit of 16K characters of text in the buffer. However the circuit and EPROM program are designed so that the buffer will run with only one memory chip if necessary, in case a constructor wishes to

keep the initial costs to a bare minimum.

The only remaining logic circuits are the NAND and NOR gates which are used for the decoding, shown in Fig. 2. In order to cover reset and interrupt vectors, the EPROM is decoded to the top of the memory map, occupying \$F800 to \$FFFF. The RAM is placed at the lowest addresses, the first (and possibly only) RAM chip being at \$0000 to \$1FFF, and the second at \$2000 to \$3FFF. This leaves plenty of space for the PIA, which only requires four addresses—these are available at \$8000 to \$8003. Those readers familiar with address decoding will realise that the locations

given are not the only locations which could be used. In fact the PIA occupies all addresses from \$8000 to \$BFFF, but there is no advantage in refining the decoding further for this project.

## HANDSHAKING

The Centronics parallel interface uses a system called "handshaking" in order to pass data from one device to another (see Fig. 3). Handshaking prevents the sending device (the source) from transmitting data too fast for the receiving device (the target) to deal with. At the start of transmission,

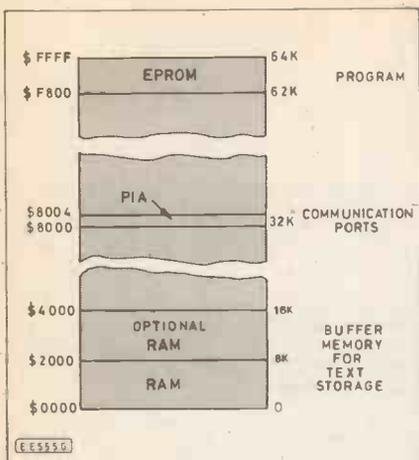


Fig. 2. Decoding of address space.

the source puts one byte of data on the eight parallel data lines. It then signals to the target that valid data is held on the lines, by sending a pulse called a strobe to the target. Since the data lines are all occupied, the strobe has to be sent on a separate line which is called the Strobe line. The source will now wait until the target has had time to read the data byte. The target signals that it has received the data, by putting a "high" voltage (i.e. 5V) on yet another line—the Busy line.

As soon as the source reads a high on the Busy line, it terminates its strobe pulse, if it hasn't already done so. The target now processes the data (i.e. prints or saves it) and then signals to the source that it is ready for another data byte. It does this by dropping the voltage on the Busy line back to zero. The Centronics interface provides for two types of target reply line. The Busy line can be replaced or assisted by an Acknowledge line. Some computers use only one or the other of these two lines. This design provides both, so it will interface with any computer with a Centronics interface.

### ACKNOWLEDGE

The Acknowledge line is held high normally, and when a byte of data has been read by the target, a short pulse to zero volts "acknowledges" the data. The source can then move on to the next byte. The width of the acknowledge pulse is not critical, and in this design a pulse of roughly 20 microseconds is produced. The pulse comes from a falling edge on the Busy line, through a 10 nanofarad capacitor, and signals that the buffer is ready to receive new data. If the buffer is full, the Busy line remains high and so there is no negative edge and no Acknowledge pulse, until space is available again.

Handshaking sounds complicated, but it achieves the fastest possible data transfer between variable speed machines. The interface needs two handshake lines (the Strobe and the Busy lines) to work, and these are just what the PIA provides. Port A and Port B each have two "control lines" in addition to the eight data lines. Remember that the PIA has to act as a target for the computer, and as a source for the printer. Control line CA1 is therefore a Strobe input, and CA2 is a Busy output for the target side of the PIA. Control line CB2 is a Strobe output and CB1 is a Busy input when the PIA is a source to the printer.

The beauty of the Centronics interface is

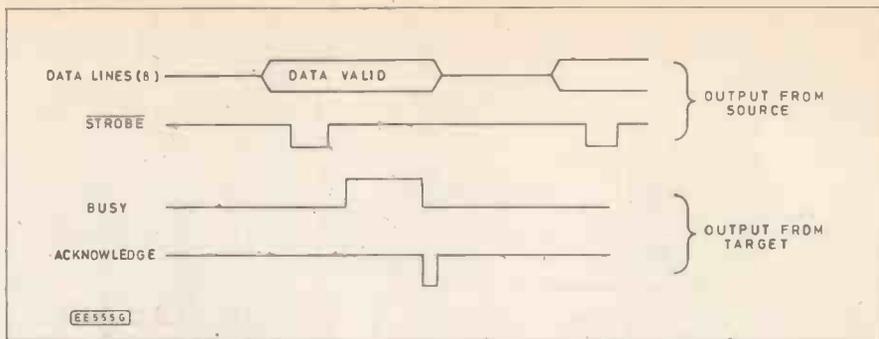


Fig. 3. Interface handshake timing diagram.

that when the buffer is temporarily full it can halt the computer's output, until space becomes available. This is achieved by holding the Busy line high. Similarly if the printer runs out of paper, it will halt output from the buffer in the same way.


### FUNCTION SWITCHES

Two function switches are provided—Hold and Flush. To keep the circuit simple, these switches are linked to the two interrupt lines of the CPU. A low on the Interrupt Request line (IRQ) will send the CPU off into a section of program which either suspends output to the printer, or resumes output if it is already suspended. The Non-Maskable Interrupt line (NMI) will divert the CPU to terminate output immediately and then reset its pointers to

effectively clear its memory. This is useful if printing needs to be stopped for some reason.

### PROGRAM

The program is held in EPROM and executed by the CPU. During normal operation, the program continually circulates through two routines, TRYIN and TRY-OUT. One acquires data from the computer and the other despatches data to the printer—subject always to the limitations of buffer memory size and printer speed. Two pointers are used by the routines, DATEND points to the byte most recently stored in memory and DATBEG points to the byte most recently output (the next higher address is the next byte for output, i.e. the Data Beginning).

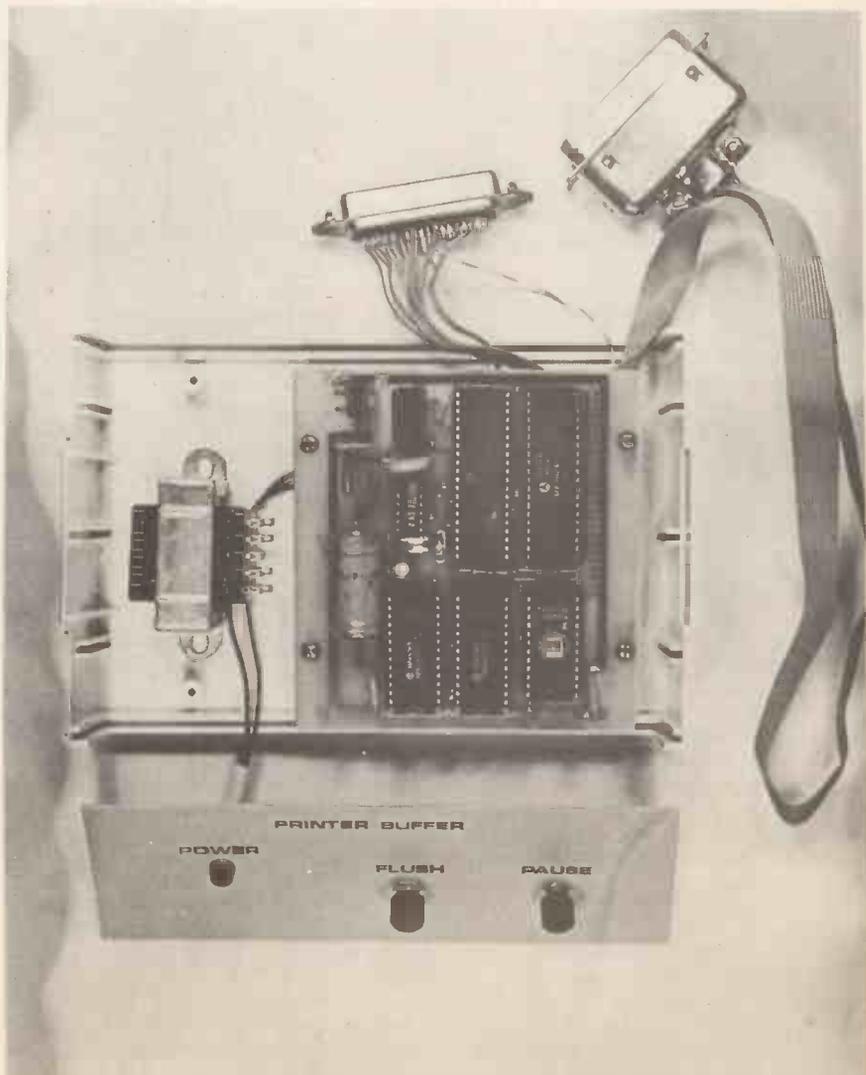

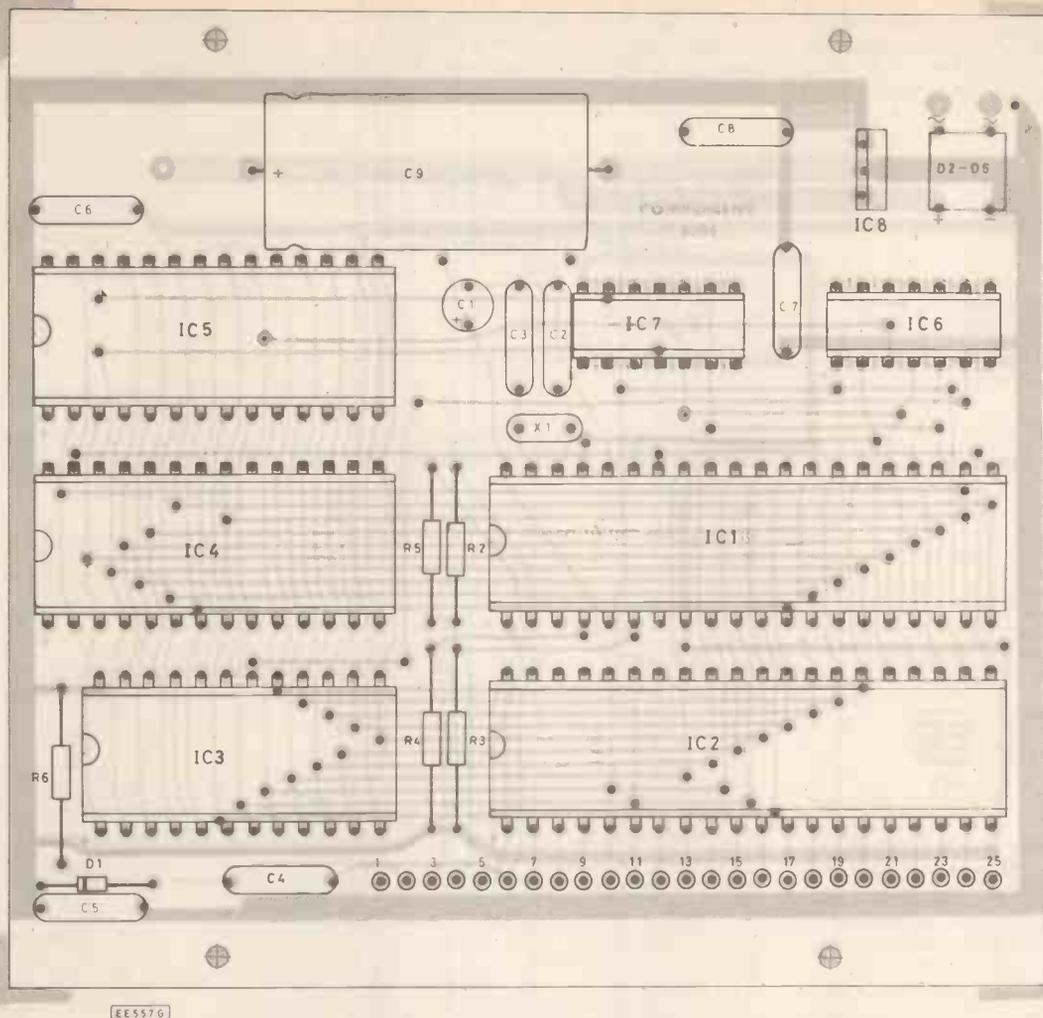


Fig. 4. Double-sided p.c.b. layout and wiring.

While TRYIN is executed, the index register (IXR) points to the next available storage location. Subroutine INDAT puts the Busy line low and checks the input port (at PIAIN) to see if a data strobe has latched the CA1 flag (bit 7 of PIAIN). If it has, the routine reads a data byte from the port and then puts the Busy line high again. TRYIN now stores the data byte, updates IXR and saves it in DATEND for the next round. Note that if no data strobe is detected or if memory is full, the pointer DATEND is not updated by IXR, so the current location is preserved for another try.

TRYOUT alternates with TRYIN and attempts to feed data to the printer. After loading the accumulator (A) with the next data byte (if there is data in memory), OUTDAT is called. This subroutine checks whether the previous output has been received and acknowledged by the printer (CB1, bit 7). If so, the new data is output via port B (PIAOUT). Finally the pointer DAT-BEG is updated. It can be seen that TRY-OUT will not send new data if there is none to send, or if the previous byte has not been acknowledged. This latter condition causes a slight hiccup for the first byte, since there was no previous byte to be acknowledged in this case. FLAG1 allows OUTDAT to circumvent the acknowledge condition for the first byte after power-on. The subroutine labelled STROBE provides the requisite handshaking pulses for OUTDAT.

When power is switched on, the reset line is held low for about 500ms by the resistor and capacitor on the line. The reset vector

takes the CPU to an initialisation routine. First the stack pointer is set to point to the top of the stack area, then the PIA is set up appropriately with port A as an input and port B as output. CA1 and CB1 are set up to trigger on negative edges for handshaking. The memory at \$2000 is tested to find if the second RAM chip is fitted and the appropriate value (\$2000 for 8K, \$4000 for 16K) is stored in MEMEND. The pointers DAT-BEG and DATEND are initialised to the start of buffer memory, above the stack at \$007F. Eventually the main loop of TRYIN—TRYOUT—TRYIN, etc is started.

The interrupt vectors NMI and IRQ are used by the control buttons for Hold and Flush. The NMI routine simply resets the stack then jumps into the initialisation routine beyond the PIA set up section. This is to avoid the possibility of an inadvertent strobe to the printer if the PIA was set up anew. An interrupt request (IRQ) can cause the processor to run one of two routines, since the Hold button has a toggle action. The routine which is to be run is pointed to by IRQV2. Initially this is the routine called IRQR1 and it is this routine that halts printing. The first action taken by IRQR1 is to put the Busy line high to stop output from the computer. It then goes into a 40ms delay to ensure that the Hold switch has stopped bouncing.

Although the processor sets an interrupt mask when it receives an interrupt request, it is possible for a second interrupt request to be latched and acted upon when the

interrupt mask is cleared. IRQR1 gets around this by indicating that the IRQ routine has been run by setting a flag IRQFLG. This allows it to ignore a second interrupt. Finally, IRQR1 adjusts IRQV2 to point to IRQR2 (the other interrupt request routine) and then enters the wait state. On the next press of the Hold button, the processor exits from the wait state and executes IRQR2. This allows printing to continue, by resuming the program at the point where it left off to service the first press of the Hold button. Thus no data can be lost by the Hold action.

## CONSTRUCTION

Construction of the printer buffer should present no problems. The power supply consists of a small transformer mounted separately in the case, driving a full wave bridge rectifier and smoothing capacitor. A fuse should be fitted in the mains input lead to the transformer, for safety. The d.c. supply is regulated at five volts by a 7805 positive regulator. Since current consumption is only 200mA, power loss in the regulator should not require a heat sink to be fitted unless the transformer produces excessive voltage. The power supply components are mounted on the printed circuit board (p.c.b.). It is suggested that all the integrated circuits (apart from the regulator) should be mounted in d.i.l. sockets. This not only protects against destruction by high soldering temperatures, but also assists greatly if a component is faulty.

Before mounting any components on the p.c.b. connect all the pin throughs and solder on both sides of the double sided board—there are 73 of these. A few components also require soldering on both sides

of the board. The p.c.b. track masters are not shown as this board is not recommended for home manufacture—see Shop Talk for a supplier. When the board has been constructed, the power supply regulation

can be checked before any expensive integrated circuits are plugged in. Connection to the computer is through a Centronics socket mounted on the back panel of the case. Separate wires or ribbon cable can be

## PRINTER BUFFER SOFTWARE

### \* SYSTEM EQUATES

```

$000 PIAIN EQU $8000 Input PIA
$002 PIAOUT EQU $8002 Output PIA
$080 MEMST EQU $0080 Start of buffer RAM
$07F STACK EQU MEMST-1 Top of stack

```

### \* SYSTEM VARIABLES

```

$0000 ORG $0
$0000 MEMEND RMB 2 Last available RAM address
$0002 DATBEG RMB 2 Address of data start
$0004 DATEND RMB 2 Address of data end
$0006 FLAG RMB 1 Data transferred flag
$0007 FLAG1 RMB 1 First data byte flag
$0008 IRQFLG RMB 1 Interrupt request flag
$0009 IRQV2 RMB 2 IRQ soft vector

```

### \* RESET AND INTERRUPT VECTORS

```

FFF8 ORG $FFF8
FFF8 F8 81 IRQV FDB IRQJMP
FFFA F8 B9 SWIV FDB SWIR
FFFC F8 B0 NMIR FDB NMIR
FFFE F8 00 RESET FDB START

```

\*\*\*\*\*

### \* PROGRAM STARTS HERE

```

F800 ORG $F800
F800 8E 00 7F START LDS #STACK
F803 BD F8 C1 JSR INIT
F806 0E START1 CLI

```

### \* MAIN ROUTINE

\* Check for data and output if any

```

F807 DE 02 TRYOUT LDX DATBEG Get address of start of data
F809 9C 04 CPX DATEND Any data in memory?
F80B 27 0F BEQ TRYIN Branch if none
F80D A6 00 LDA A 0,X Get data
F80F 8D F8 51 JSR OUTDAT Send data
F812 7D 00 06 TST FLAG Test if data sent
F815 27 05 BEQ TRYIN
F817 8D F8 78 JSR INCRX Update pointer
F81A DF 02 STX DATBEG Save it

```

\* Check buffer and input data if space available

```

F81C DE 04 TRYIN LDX DATEND Point to last data byte
F81E BD F8 78 JSR INCRX Update pointer
F821 9C 02 CPX DATBEG
F823 E7 E2 BEQ TRYOUT RAM full
F825 8D F8 28 JSR INDAT Look for input
F828 7D 00 05 TST FLAG Test if data input
F82B 27 DA BEQ TRYOUT
F82D DE 04 LDX DATEND
F82F A7 00 STA A 0,X Save data
F831 8D F8 78 JSR INCRX Update pointer
F834 DF 04 STX DATEND Save pointer
F836 20 CF BRA TRYOUT

```

\* READ INPUT PORT AND GET DATA IF ANY

```

F838 C6 34 INDAT LDA B #34
F83A F7 80 01 STA B PIAIN+1 Put IBZ lo
F83D 7F 0C 06 CLR FLAG
F840 7D 80 01 TST PIAIN+1 Check for strobe
F843 2A 08 BPL INDAT2
F845 7C 0C 0E INC FLAG Indicate data available
F848 E6 80 00 LDA A PIAIN Get data
F84B C6 3E LDA B #3C
F84D F7 8C 01 STA B PIAIN+1 Put IBZ hi
F850 39 INDATE RTS

```

### \* DATA OUTPUT ROUTINE

```

F851 7D 00 07 OUTDAT TST FLAG1 First byte since switch on?
F854 26 05 BNE OUTD1
F856 7D 80 03 TST PIAOUT+1 Check for printer acknowledge
F859 2A 0C BPL OUTD2 No acknowledge
F85E 7F 07 07 GLTD1 CLR FLAG1 Indicate first byte sent
F85E F6 80 02 LDA B PIAOUT Clear busy flag
F861 E7 80 02 STA A PIAOUT Send data
F864 7E F8 6E JMP STROBE Output STROBE pulse
F867 7F 00 06 OUTD2 CLR FLAG
F86A 39 RTS

```

### \* STROBE HANDSHAKE LINES

\* Strobe output port

```

F86B C6 34 STROBE LDA B #34
F86D F7 80 03 STA B PIAOUT+1 Put data strobe low
F870 C6 3C LDA B #3C
F872 F7 80 03 STA B PIAOUT+1 Put data strobe high
F875 D7 06 STA B FLAG
F877 39 RTS

```

\* INCREMENT X FOR LOOP MEMORY

```

F875 08 INCRX INX
F879 9C 00 CPX MEMEND REACHED END+1
F87B 26 03 BNE INCRX1
F87D CE 00 80 LDX #MEMST IF SO. START OVER
F880 39 INCRX1 RTS

```

### \* INTERRUPT ROUTINES

```

F881 DE 09 IRQJMP LDX IRQV2 Get address of IRQ routine
F883 6E 00 JMP 0,X Jump to it

```

\* Stop printing and wait

```

F885 C6 3C IRQR1 LDA B #3C
F887 F7 80 01 STA B PIAIN+1 Put IBZ hi
F88A 8D 2E BSR DELAY Delay for switch debounce
F88C 7D 00 08 TST IRQFLG This routine been done?
F88F 26 01 BNE IRQI1 Branch if not done
F891 38 RTI unwind second IRQ
F892 7F 00 08 IRQI1 CLR IRQFLG Flag routine done-print stopped
F895 0E CLI Enable next IRQ
F896 CE FB 9D LDX #IRQR2 Reset vectors to
F899 DF 09 STX IRQV2 point to other IRQ routine
F89B 3E WAI wait for interrupt
F89C 38 RTI Return to main prog

```

\* Restart printing

```

F89D 8D 1B IRQR2 BSR DELAY
F89F 7D 00 08 TST IRQFLG
F8A2 27 01 BEQ IRQI2
F8A4 38 RTI
F8A5 86 FF IRQI2 LDA A #FF Flag - printing restarted
F8A7 97 08 STA A IRQFLG
F8A9 0E CLI
F8AA CE FB 85 LDX #IRQR1
F8AD DF 09 STX IRQV2
F8AF 38 RTI

```

\* NON-MASKABLE INTERRUPT ROUTINE

```

F8B0 8E 00 7F NMIR LDS #STACK Restore stack
F8B3 BD F8 E0 JSR INIT Re-init RAM pointers
F8B6 7E FB 06 JMP START1 Begin again

```

\* SOFTWARE INTERRUPT ROUTINE

```

F8B9 38 SWIR RTI Not implemented

```

\* DELAY ROUTINE

```

F8BA CE 13 88 DELAY LDX #5000 40ms delay
F8BD 09 DEL1 DEX
F8BE 26 FD BNE DEL1
F8C0 39 RTS

```

\* INITIALISE PIA AND FIND MEMORY SIZE

```

F8C1 7F 80 01 INIT CLR PIAIN+1 Select DDR's
F8C4 7F 80 03 CLR PIAOUT+1
F8C7 7F 80 00 CLR PIAIN Make inputs
F8CA 86 FF LDA A #FF
F8CC B7 80 02 STA A PIAOUT Make outputs
F8CF 86 3C LDA A #3C
F8D1 87 80 03 STA A PIAOUT+1 Set up for handshake
F8D4 B7 80 01 STA A PIAIN+1
F8D7 E6 80 00 LDA A PIAIN Clear handshake flags
F8DA B6 80 02 LDA A PIAOUT
F8DD 8D FB F8 JSR TSTMEM Find memory size
F8E0 86 FF LDA A #FF
F8E2 97 07 STA A FLAG1 Set first byte flag
F8E4 97 08 STA A IRQFLG Set IRQ flag
F8E6 CE 00 80 LDX #MEMST
F8E9 DF 02 STX DATBEG Initialise data start pointer
F8EB DF 04 STX DATEND Initialise data end pointer
F8ED CE FB 85 LDX #IRQR1
F8F1 DF 09 STX IRQV2 Set up interrupt pointer
F8F2 86 34 LDA A #34
F8F4 B7 80 01 STA A PIAIN+1 Put IBZ low
F8F7 39 RTS

```

continued...

## PRINTER BUFFER SOFTWARE—continued

\* Find size of RAM available \*

F8F8 86 AA	TSTMEM	LDA	A	##2000	Last addr = #1 in first RAM
F8FA CE 20 00		LDX		##2000	Try storing data
F8FD A7 00		STA	A	0,X	Test if stored
F8FF A1 00		CHF	A	0,X	
F901 26 03		BNE	TSTM1		
F903 CE 40 00		LDX		##4000	Last address #1 in out RAM
F906 DF 00	TSTM1	STX		MEMEND	Save address
F908 39		RTS			

### SYMBOL TABLE

DATBED	0002	DATEND	0004	DEL1	F88D	DELAY	F88A	FLAG	0006
FLAG1	0007	INCRX	F87E	INCRX1	F890	INDAT	F888	INDAT2	F850
INIT	F8C1	INIT1	F8E0	IRQ11	F892	IRQ12	F8A5	IRGFLG	0008
IRGJMP	F881	IRGR1	F8E5	IRGR2	F89D	IRGV	FFFF	IRGV2	0009
MEMEND	0000	MEMST	0080	NMIF	F880	NMIV	FFFF	CJTD1	F85E
OUTD2	F867	OUTDAT	F851	PIA11	8000	PIAOUT	8002	RESET	FFFF
STACK	007F	START	F800	START1	F806	STRCBE	F8E6	SWIR	F8E9
SWIV	FFFA	TRYIN	F81C	TRYOUT	F807	TSTM1	F836	TSTMEM	F85E

used to connect this socket to pads on the p.c.b. Output from the buffer to the printer is through a ribbon cable soldered direct to pads on the p.c.b. at one end, and terminat-

ing in a Centronics plug at the other end. This plug should be either an insulation displacement type or soldered, with a cover. The ribbon cable to it should be clamped on

the back panel and lead out through a slot or recess. Two push button switches are mounted on the front panel for the Flush and Hold functions. □

# CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised. Payment is made for all circuits published in this feature. Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.

## CAR WARNING OF THINGS LEFT ON

EVERY car owner knows the horrible feeling; you find you have left something on, and return to the car to find a flat battery. This circuit overcomes that problem on my Volvo, and has done so for about two years.

Take a typical journey. Get in, switch on and start, stop, switch off, after having put the sidelights on during the journey. The result is a buzzer sounding and a pilot light on to say what's left on. Switch off the lights and all is well.

If you want to leave them on for parking, flip a toggle switch and the buzzer stops. Come back again after parking with lights on, switch on, and the buzzer sounds to remind you to put the switch back to the original position.

Diodes D1, D2, D3 and D4 form an OR gate. Any one of the sensed circuits switched on produces 12V to relay RLA and (via S1 in the SET position) the buzzer. If ignition is off, the buzzer and RLA have an "earth" return via lamp LP5; the buzzer sounds and the relay energises.

The relay contact RLA1 provides an earth return for indicators LP1, LP2, LP3,

and LP4 via diodes D5, D6, D7, and D8. The appropriate indicator lights up. Diodes D5, D6, D7, and D8 are needed to prevent incorrect indications via the low d.c. resistances to earth of other sensed circuits.

If ignition is on, neither the buzzer nor RLA sees an earth return, as IGN is at 12V. The buzzer is silent, and no indicators light up. In a "parking with lights" situation, IGN is an earth return via LP5, and the junction of D1, D2, D3, and D4 is at 12V. Relay RLA is energised, so the appropriate indicator is on.

Putting S1 to CANCEL silences the buzzer. When the car is started again, IGN becomes 12V; with S1 to CANCEL, this connects the buzzer between 12V and earth. It sounds, as a reminder to set S1 back to SET.

Lamp LP5 may not be necessary. All that is required is a permanent low-resistance connection between IGN and earth. On my Volvo, three added instrument illumination lamps provide this path.


Components are not critical. The circuit diagram shows suggested types. Indicators LP1, LP2, LP3, and LP4 are car accessory

shop 12V indicators, any colour you fancy. The diodes can be any 1A 400V type. The relay can be any small 12V component with a coil resistance over 1000 ohms. Don't use car accessory relays, they take too much coil current. The buzzer can be any small 12V type.

The indicators and the toggle switch are mounted on a small accessory panel. The rest goes on a small p.c.b. behind the dash. The IGN input comes from any live line fed via the ignition switch.

The sensed points can normally be picked up by "tee-in" car accessory connectors near the switches of the sensed circuits. I sense side lights, headlights, spot lights, and a rear screen heater which is not fed via the ignition switch. Sense what you like; the circuit can have as many OR gate diodes and indicator lamps as you like.

C. Waltham,  
Southampton.

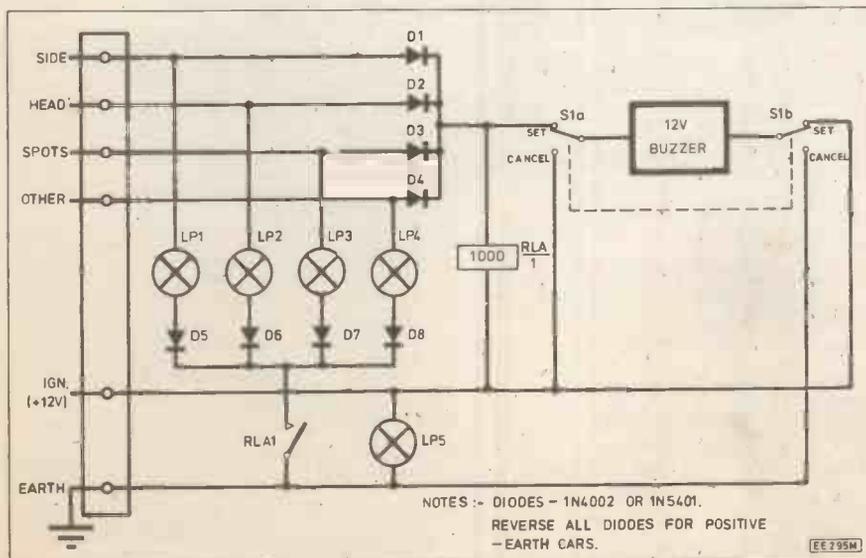

If you're a regular reader and have not yet submitted an idea for Circuit Exchange, why not have a go now? We will pay £40.00 per page for any article published.

We are looking for original ideas which may be simple or complex, but most importantly are useful and practical.

To help us to process articles which are offered for publication, all subject matter should conform to the usual practices of this journal. Special attention should be paid to circuit symbols and abbreviations and all diagrams should be on separate sheets, not in the text. Also manuscripts should be typed with wide margins and double line spacing or neatly hand written in the same fashion.

Just send in your idea to our editorial offices, together with a declaration to the effect that it has been tried and tested, is the original work of the undersigned and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proved by us.

# BOOK SERVICE

The books listed below have been selected as being of special interest to our readers, they are supplied from our editorial address (mail order only) direct to your door.

## DATA AND REFERENCE

### HOW TO IDENTIFY UNMARKED ICs

**K. H. Recor**  
Shows the reader how, with just a test-meter, to go about recording the particular signature of an unmarked i.c. which should enable the i.c. to then be identified with reference to manufacturers' or other data. An i.c. signature is a specially plotted chart produced by measuring the resistances between all terminal pairs of an i.c.  
*Chart* **Order code BP101 £0.95**

### RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

**B. B. Babani**  
Although this chart was first published in 1971 it provides basic information on many colour codes in use throughout the world, for most radio and electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers, etc. It is particularly useful for finding the values of old components.  
*Chart* **Order code BP7 £0.95**

### CHART OF RADIO, ELECTRONIC, SEMICONDUCTOR AND LOGIC SYMBOLS

**M. H. Babani, B.Sc.(Eng.)**  
Illustrates the common, and many of the not-so-common, radio, electronic, semiconductor and logic symbols that are used in books, magazines and instruction manuals, etc., in most countries throughout the world.  
*Chart* **Order code BP27 £0.95**

### TRANSISTOR RADIO FAULT-FINDING CHART

**C. E. Miller**  
Used properly, should enable the reader to trace most common faults reasonably quickly. Across the top of the chart will be found four rectangles containing brief description of these faults, viz—sound weak but undistorted, set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.  
*Chart* **Order code BP70 £0.95**

### DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS

**A. Michaels**  
Shows equivalents and pin connections of a popular selection of European, American and Japanese digital i.c.s. Also includes details of packaging, families, functions, manufacturer and country of origin.  
*256 pages* **Order code BP140 £4.95**

### LINEAR IC EQUIVALENTS AND PIN CONNECTIONS

**A. Michaels**  
Shows equivalents and pin connections of a popular selection of European, American and Japanese linear i.c.s. Also includes details of functions, manufacturer and country of origin.  
*320 pages* **Order code BP141 £4.95**

### INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

**A. Michaels**  
Helps the reader to find possible substitutes for a popular selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.  
*320 pages* **Order code BP85 £2.95**

### INTERNATIONAL DIODE EQUIVALENTS GUIDE

**A. Michaels**  
Designed to help the user in finding possible substitutes for a large selection of the many different types of diodes that are available. Besides simple rectifier diodes, also included are Zener diodes, i.e.d.s, diacs, triacs, thyristors, OCIs, photo and display diodes.  
*144 pages* **Order code BP108 £2.25**

## PROJECT CONSTRUCTION

### HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

**R. A. Penfold**  
We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.  
*96 pages* **Order code BP110 £1.95**

### HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

**R. A. Penfold**  
Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.  
*80 pages* **Order code BP121 £1.95**

### BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

**R. A. Penfold**  
Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also includes examples in the form of simple projects.  
*112 pages* **Order code No. 227 £1.95**

## CIRCUITS AND DESIGN

### MICRO INTERFACING CIRCUITS—BOOK 1

**R. A. Penfold**  
Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but p.c.b. layouts and other detailed constructional information are not included.

Book 1 is mainly concerned with getting signals in and out of the computer. Book 2 deals primarily with circuits for practical applications.  
**Book 1 112 pages Order code BP130 £2.25**  
**Book 2 112 pages Order code BP131 £2.25**

### A MICROPROCESSOR PRIMER

**E. A. Parr, B.Sc., C.Eng., M.I.E.E.**  
Starts by designing a small computer which, because of its simplicity and logical structure, enables the language to be easily learnt and understood. The shortcomings are then discussed and the reader is shown how these can be overcome by changes and additions to the instruction set. In this way, such ideas as relative addressing, index registers, etc., are developed.  
*96 pages* **Order code BP72 £1.75**

### PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 1

### PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 2

**R. A. Penfold**  
These books are designed to aid electronic enthusiasts who like to experiment with circuits and produce their own projects, rather than simply following published project designs.

**BOOK 1** contains: Oscillators—sinewave, triangular, squarewave, sawtooth, and pulse waveform generators operating at audio frequencies. Timers—simple monostable circuits using i.c.s, the 555 and 7555 devices, etc. Miscellaneous—noise generators, rectifiers, comparators and triggers, etc.

**BOOK 2** contains: Amplifiers—low level discrete and op-amp circuits, voltage and buffer amplifiers including d.c. types. Also low-noise audio and voltage controlled amplifiers. Filters—high-pass, low-pass, 6, 12, and 24dB per octave types. Miscellaneous—i.c. power amplifiers, mixers, voltage and current regulators, etc.

**BOOK 1 128 pages Order code BP117 £1.95**  
**BOOK 2 112 pages Order code BP118 £1.95**

### HOW TO DESIGN ELECTRONIC PROJECTS

**R. A. Penfold**  
The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics. Hints on designing circuit blocks to meet your special requirements are also provided.  
*128 pages* **Order code BP127 £2.25**

### POPULAR ELECTRONIC CIRCUITS—BOOK 1

### POPULAR ELECTRONIC CIRCUITS—BOOK 2

**R. A. Penfold**  
Each book provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed construction information. Any special setting-up procedures are described.

**BOOK 1 Temporarily out of print**  
**BOOK 2 160 pages Order code BP98 £2.25**

### A PRACTICAL INTRODUCTION TO MICROPROCESSORS

**R. A. Penfold**  
Provides an introduction which includes a very simple microprocessor circuit which can be constructed so that the reader can experiment and gain practical experience.  
*96 pages* **Order code BP123 £1.95**

### HOW TO USE OP-AMPS

**E. A. Parr**  
This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.  
*160 pages* **Order code BP88 £2.95**

## COMPUTING

### THE ART OF PROGRAMMING THE ZX SPECTRUM

**M. James, B.Sc., M.B.C.S.**  
It is one thing to have learnt how to use all the Spectrum's commands and functions, but a very different one to be able to combine them into programs that do exactly what you want them to. This is just what this book is all about—teaching you the art of effective programming with your Spectrum.  
*144 pages* **Order code BP119 £2.50**

### AN INTRODUCTION TO PROGRAMMING THE COMMODORE 16 & PLUS 4

**R. A. Penfold**  
Helps you to learn to use and program these two Commodore machines with the minimum of difficulty by expanding and complementing the information supplied in the manufacturer's own manuals.  
*128 pages* **Order code BP158 £2.50**

### AN INTRODUCTION TO PROGRAMMING THE BBC MODEL B MICRO

**R. A. & J. W. Penfold**  
Written for readers wanting to learn more about programming and how to make best use of the incredibly powerful model B's versatile features. Most aspects of the BBC micro are covered, the omissions being where little could usefully be added to the information provided by the manufacturer's own manual.  
*144 pages* **Order code BP139 £1.95**

### AN INTRODUCTION TO PROGRAMMING THE ACORN ELECTRON

**R. A. & J. W. Penfold**  
Designed to help the reader learn more about programming and to make best use of the Electron's many features. Adds considerably to the information already supplied in the manufacturer's own instruction manual.  
*144 pages* **Order code BP142 £1.95**

### AN INTRODUCTION TO PROGRAMMING THE ATARI 600/800 XL

**R. A. & J. W. Penfold**  
Especially written to supplement the manufacturer's own handbook. The information supplied will help the reader to master BASIC programming and to make best use of the Atari's many powerful features.  
*128 pages* **Order code BP143 £1.95**

### AN INTRODUCTION TO PROGRAMMING THE AMSTRAD CPC 464 AND 664

**R. A. & J. W. Penfold**  
The Amstrad CPC 464 or 664 running with Locomotive BASIC makes an extremely potent and versatile machine and this book is designed to help the reader get the most from this powerful combination. Written to complement rather than duplicate the information already given in the manufacturer's own manual. Also applicable to the CPC 6128.  
*144 pages* **Order Code BP153 £2.50**

### AN INTRODUCTION TO PROGRAMMING THE SINCLAIR QL

**R. A. & J. W. Penfold**  
Helps the reader to make best use of the fantastic Sinclair QL's almost unlimited range of features. Designed to complement the manufacturer's handbook.  
*112 pages* **Order code BP150 £1.95**

### AN INTRODUCTION TO Z80 MACHINE CODE

**R. A. & J. W. Penfold**  
Takes the reader through the basics of microprocessors and machine code programming with no previous knowledge of these being assumed. The Z80 is used in many popular home computers and simple programming examples are given for Z80-based machines including the Sinclair ZX-81 and Spectrum, Memotech and the Amstrad CPC 464. Also applicable to the Amstrad CPC 664 and 6128.  
*144 pages* **Order code BP152 £2.75**

### AN INTRODUCTION TO 6502 MACHINE CODE

**R. A. & J. W. Penfold**  
No previous knowledge of microprocessors or machine code is assumed. Topics covered are: assembly language and assemblers, the register set and memory, binary and hexadecimal numbering systems, addressing modes and the instruction set, and also mixing machine code with BASIC. Some simple programming examples are given for 6502-based home computers like the VIC-20, ORIC-1/Atmos, Electron, BBC and also the Commodore 64.  
*112 pages* **Order code BP147 £2.50**

### THE PRE-BASIC BOOK

**F. A. Wilson, C.G.I.A., C.ENG., F.I.E.E., F.I.E.R.E., F.B.I.M.**  
Another book on BASIC but with a difference. This one does not skip through the whole of the subject and thereby leave many would-be programmers floundering but instead concentrates on introducing the technique by looking in depth at the most frequently used and more easily understood computer instructions. For all new and potential micro users.  
*192 pages* **Order code BP146 £2.95**



## COMPUTING

continued

### HOW TO GET YOUR COMPUTER PROGRAMS RUNNING

J. W. Penfold

Have you ever written your own programs only to find that they did not work? Help is now at hand with this book which shows you how to go about looking for your errors, and helps you to avoid the common bugs and pitfalls of program writing. Applicable to all dialects of the BASIC language.

144 pages Order code BP169 £2.50

### AN INTRODUCTION TO COMPUTER COMMUNICATIONS

R. A. Penfold

Provides details of the various types of modem and their suitability for specific applications, plus details of connecting various computers to modems, and modems to the telephone system. Also information on common networking systems and RTTY.

96 pages Order code BP177 £2.95

### AN INTRODUCTION TO COMPUTER PERIPHERALS

J. W. Penfold

Covers such items as monitors, printers, disc drives, cassette recorders, modems, etc., explaining what they are, how to use them and the various types and standards. Helps you to make sure that the peripherals you buy will work with your computer.

80 pages Order code BP170 £2.50

### COMPUTER TERMINOLOGY EXPLAINED

I. D. Poole

Explains a wide range of terms that form the computer jargon used by enthusiasts. Includes a reference guide to the more commonly used BASIC commands.

96 pages Order code BP148 £1.95

### THE PRE-COMPUTER BOOK

F. A. Wilson

Aimed at the absolute beginner with no knowledge of computing. An entirely non-technical discussion of computer bits and pieces and programming.

96 pages Order code BP115 £1.95

## RADIO

### AN INTRODUCTION TO RADIO DXING

R. A. Penfold

Anyone can switch on a short wave receiver and play with the controls until they pick up something, but to find a particular station, country or type of broadcast and to receive it as clearly as possible requires a little more skill and knowledge. The object of this book is to help the reader to do just that, which in essence is the fascinating hobby of radio DXing.

112 pages Order code BP91 £1.95

### INTERNATIONAL RADIO STATIONS GUIDE

Completely revised and updated, this book is an invaluable aid in helping all those who have a radio receiver to obtain the maximum entertainment value and enjoyment from their sets.

Clearly shown are the station site, country, frequency and/or wavelength, as well as the effective radiation power of the transmitter.

128 pages Order code BP155 £2.95

## TO ORDER

Add 50p per order postage (overseas readers add £1, surface mail postage) and send a PO, cheque or international money order (£ sterling only) made payable to **Everyday Electronics** (quoting the order code and quantities required) to **EE & EM BOOKS SERVICE, 6 CHURCH STREET, WIMBORNE, DORSET. BH21 1JH.** (Mail order only.)

PLEASE ALLOW 28 DAYS FOR DELIVERY



# EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY

NOVEMBER 1986

£1.10

## NEW SERIES—DIGITAL TROUBLESHOOTING


**A**n outstanding new nine-part series by Mike Tooley BA (Principal Lecturer, Department of Technology at Brooklands Technical College). It will be aimed at those:

- Developing an interest in digital electronics as a logical extension of home computing activities;
- Requiring a practical introduction to the repair of digital equipment;
- Wishing to up-date their knowledge of electronics and wanting a practical introduction to modern digital devices and circuitry.

Each part is complemented by a project describing an item of test gear for use with the series. These projects are suitable for beginners but each item has a specification that matches commercially available instruments.

The first three items of test gear are: Regulated Bench PSU, Logic Probe and Logic Pulser.

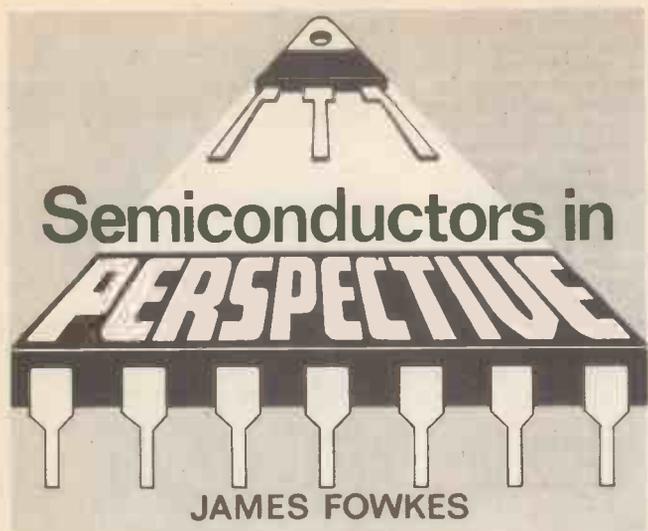**DON'T MISS THE START OF THIS NEW SERIES  
ONLY AVAILABLE IN EVERYDAY ELECTRONICS  
November issue on sale Friday, October 17. £1.10**



**T**HERE are still people who remember hearing "2LO calling" on a crystal and catswhisker radio. More correctly known as the crystal detector, it was one of a number of devices used to "rectify" an alternating current signal.

Other devices, in order of importance, were: The Coherer, the Electrolytic, and the Magnetic detector; The Thermionic Valve; and, much later, the Transistor.

Here we are only concerned with crystal detectors, the more common of which, again in historical format, are:

Bornite and Zincite  
Zincite and Tellurium  
Carborundum and Steel  
Galena and Tellurium  
Copper Pyrites and Tellurium  
Germanium and Copper  
Iron Pyrites and Silicon

Several others worthy of mention are:

Cassiterite, Graphite, Hertzite, Malachite, and Molebdenite; but the possibilities are endless.

Even a piece of common coal can rectify—or the inner and outer cones of a coal-gas flame.

Since only germanium and silicon appear to have survived common usage into the 20th century we will ignore all the others.

They possess a peculiar property where, when placed in contact with a foreign body, a current will flow much more easily in one direction than the other. This, in turn, changes a modulated pulse of radio-frequency voltage into a cumulative unidirectional current—which may be utilised to reproduce audio-frequencies from an earpiece or other electromechanism.

The property is only present where impurities exist in the crystal. Discovered by accident, it is variously described as rectification, detection, or demodulation. Potentiometric biasing may be used to select the straighter part of the characteristic curve; or a capacitor/resistor combination, so as to utilise the incoming signal.

The Greeks first spoke of "spirit" particles in 400BC and their electrostatic experiments with amber (Elektra) are well-known.

Experiments with rectifiers, however, did not begin until about 1835AD; then, around the turn of the century the silicon carbide rectifier was developed; commonly known as carborundum and catswhisker, this was the first use of silicon.

Shortly after the First World War, experiments began with silicon point-contact diodes. Ideal for u.h.f. detection, they were electrically similar to the thermionic valve, which was now fast replacing the crystal and catswhisker.

Germanium oxide can be obtained from the flue-ash resulting from burning common coal.

The advent of another war made miniaturisation a priority. Owing to material shortages, both germanium and silicon were used; the latter being less frequency-conscious.

## SIGNIFICANT DATES

**1835** Munck Roschenschold: Rectifying action in solids.

**1906** Carborundum and Catswhisker was developed.

**1924** Lossev Experiments with Point-Contacts and zincite with carborundum.

**1930** Wilson and Mott published *The Physical Theory of Conduction of Solids*.

**1945** J. Bardeen and W. H. Brittain began work on *Control of Surface Charge Density*, . . . and in . . .

**1948** published, *The Transistor, a Semiconductor Triode*.

**1949** Bell Telephone Laboratories announce the *p-n junction Transistor*.

(In Germany brass wire was substituted for the copper used in radios due to a shortage of the latter caused by allied bombardment.)

The instability of the catswhisker led to the study of "doping"—adding impurities to the junction—and conductivity was found to improve across the resultant alloy. Doping creates either a surplus or a deficiency of electrons in the crystal lattice. The former is referred to as the donor *n*, while the latter is called an acceptor *p*.

When *p* and *n* atoms bond together in a co-valent, or homogenous, union an energy exchange occurs as the two materials try to equalise, leaving a depleted area known as the "space-charge" region. An area of stress builds up in this region and is referred to as the *p-n* junction. "Forming" a junction is a continuous process, so that the junction may become a chemically "single" crystal.

Since each side of the junction is of opposite polarity, it follows that it must possess capacitance. The extent of this capacitance has considerable influence on determination of the upper frequency limits.

Negative electrons have to be "balanced" by positive holes. (A hole is an atom lacking an electron and, therefore, carrying a positive charge.) Where the electrons greatly outnumber positive holes the crystal is referred to as *n* type.

If positive holes predominate the structure is called *p* type.

The point-contact's catswhisker is pointed so as to concentrate the electric field. The same principle is applied to the lightning conductor.

Study concentrated on the effect of surface charges after the Second World War, and use of an electrolyte in contact with the surface of semiconductor material led to an additional electrode placed close to the first.

Soon afterwards, the Bell Laboratories announced the *p-n* junction transistor. (This was named after TRANSfer + reSISTOR = Transistor.) Which side of the junction the second contact is placed determines whether the resultant transistor will be *pnp* or *npn*.

The three transistor electrodes are called the emitter, the base, and the collector. Application of a forward bias between the emitter and base will cause holes (or electrons, depending on transistor type) to be emitted from the emitter into the space-charge region (the base). And a reverse bias applied from the collector to base will permit the collector to collect.

Direction of current flow has long been confused with the ambiguities of "current flow" and "electron flow"—the one in direct contradiction to the other.

With the arrival of crystal "chemistry"—a branch of quantum mechanics—new, and yet more confusing terms have evolved. Current flow by hole movement; forward current, reverse current, saturation current, leakage current, and now *p-n* or *n-p* junctions!

## INTEGRATED

Soon two or more transistors were to be found embodied in the same envelope. (This was no new event, for in the

wartime German "people's" set four thermionic valves shared the same glass case.)

Transistor-pairs soon followed; the "Darlington pair" and the "Super-alpha pair" soon led to logic blocks and gating circuits, and to diode-transistor combinations (DTL). Then, to obtain greater speed, the transistor-transistor (TTL) logic series evolved—and the integrated circuit was born.

Since the semiconductor industry concentrated on business processing and personal computers, integrated circuit development slowed down. Thermionic valves and other components were expensive in comparison with circuit wiring; whereas in semiconductors, chip area and wiring limit costs.

The advent of VLSI (very large scale integration) brought denser bulk memories, concentrating 256,000 ECL (emitter-coupled logic) devices onto a "chip" smaller than a baby's finger-nail, but with wide-ranging applications for solving design problems throughout the fields of physics and engineering.


The Government-sponsored Alvey directorate recently announced a £63 million, three year, research programme to a number of the larger manufacturers' research groups, to develop VLSI, which relies on a lithographic process. After the three years they move on to the next but one "chip" generation—up to 10 million components on a single chip. One project will be to develop an advanced 1.25 micron CMOS (CMOS stands for complementary metal-oxide semiconductor), using a double level metal process involving VLSI.

By applying the laws of quantum physics, computer study of molecules large enough to be of biological significance has produced stable silicon compounds, called "polysilenes", in which silicon atoms bond together. These silicon-silicon bonds form a "living" tissue which will make the "biological chip" possible. New laws, both social and ethical, will be needed then to govern its use.

Devices such as those proposed will make the home computer seem a simple mechanism compared even with the calculators in use today.

That simple crystal might well be termed our building block to the future . . .

A range of modern semiconductor diodes.

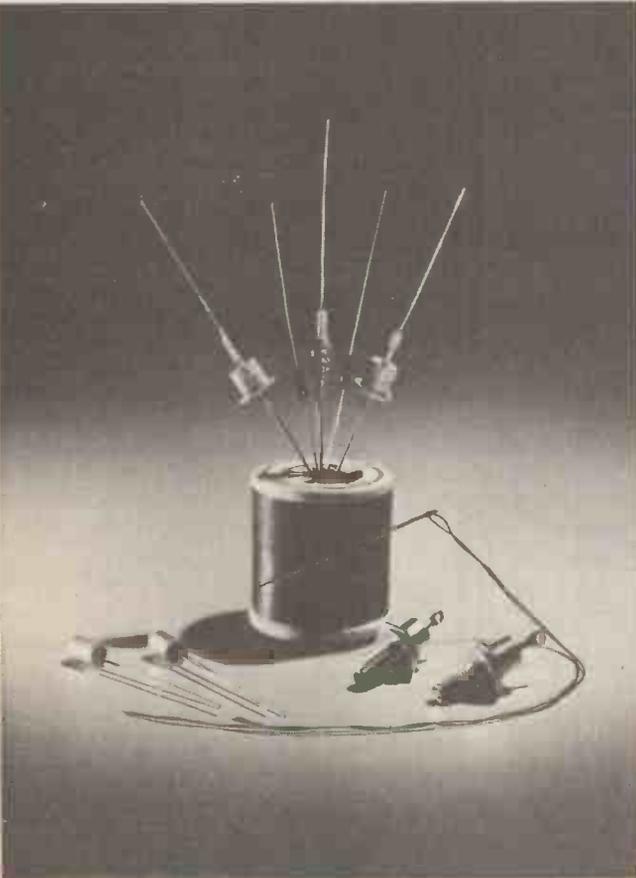

See last month's issue for details of SUMMER SALE OFFERS—ends Aug 31st.

#### COMPONENT PACKS

Greenweld are No. 1 in component packs—No. 1 for value and No. 1 for variety! We sell thousands of packs containing millions of components every year! They all offer incredible value for money—order some now and see how much you save over buying individual parts!

#### NEW FOR 1987 SEASON

K556 Fuseholders, single & twin, panel, chassis and line types 25 £2.00  
 K555 Fuses. Big selection of quick blow and ant surges types and sizes including 15mm, 20mm, 1" and 32mm 60mA-50A! 100 £3.95  
 K554 Thermistors. Mostly disc, rod and some valuable bead types. Identification/data sheet included. Big variety up to 40mm dial Catalogue value over £50 100 £8.00  
 K547 Zener Diodes. Glass & plastic, 250mW to 5W ranging from 3V to 180V. All readily identifiable. 100 £4.50  
 K548 Tantalum Capacitors. Wide range of values from 0.1 to 68µ, 3V to 50V. Includes both beads and valuable solid types. 100 £6.50  
 K549 Variable Capacitors. Mostly small trimmers, airspaced, mica and polyprop dielectrics, but also included are a few full size tuning caps. 25 £5.75  
 K544 Mullard Polyester Caps. Cosmetic imperfections, electrically OK. wide range of values from 0.01µ to 0.47µ in 100, 250 and 400V working. 200 £4.75  
 K545 Lumpy Diodes. Contains a wide selection of high current (up to 100A) rectifiers, bridges and SCR's, all marked full spec devices 25 £3.95  
 K546 Polystyrene/mica/ceramic capacitors. Lots of useful small value caps up to about 0.01 in voltages up to 8kV 100 £2.75

#### HARDWARE

K550 Self tapping screws, both pointed (AB) and blunt (B) in an assortment of sizes from 1/8"–1 1/4", No. 4 to No. 8, pozi & hex head. Excellent value 200 £1.00 1000 £4.00  
 K551 6BA screws in a variety of lengths & heads, from 3/8" to 20mm long. Steel 200 £2.00  
 K552 4BA screws in a variety of lengths and heads, from 1/2" to 1 1/2" long. Mostly steel, few brass 200 £2.40 1000 £9.60  
 K553 2BA screws in a variety of lengths and heads, from 3/8" to 2" long. Steel. 100 £2.00 1000 £8.00

#### ESTABLISHED FAVOURITES

K517 Transistor Pack—50 assorted full spec. marked plastic devices PNP NPN RF AF. Type numbers include BC114 117 172 182 183 198 239 251 214 255 320 BF 198 255 394 2N3904 etc., etc. Retail cost £7+. Special low price £2.75  
 K523 Resistor Pack—1000—yes, 1000 1/2 and 1/2 watt 5% hi-stab carbon film resistors with preformed leads for PCB mounting. Enormous range of preferred values from a few ohms to several megohms. Only £2.50 5000 £10 20 000 £36  
 K520 Switch Pack—20 different assorted switches—rocker, slide, push, rotary, toggle, micro etc. Amazing value at only £2.00  
 K522 Copper Clad Board—All pieces too small for our etching kits. Mostly double-sided fibreglass, 250g (approx. 110sq ins) for £1.00  
 K530 100 Assorted Polyester Caps—All new modern components, radial and axial leads. All values from 0.01 to 1µf at voltages from 63 to 1000V! Super value at £3.95  
 K518 200 Disc Ceramic Caps—Big variety of values and voltages from a few pF to 2.2µF; 3V to 3kV £1.00

K539 Led Pack—not only round but many shaped leds in this pack in red, yellow, green, orange and clear. Fantastic mix. 100 £5.95 250 £13.50  
 K540 Resistor Pack—mostly 1/2, 1/4 and 1/8W, also some 1 and 2W in carbon, film, oxide etc. All have full length leads. Tolerances from 5 to 20%. Excellent range of values. 500 £2.50 2500 £11.00

K503 100 Wirewound Resistors—From 1W to 12W, with a good range of values. £2.00  
 K535 Spring Pack—approx. 100 assorted compression, extension and torsion springs up to 22mm dia. and 30mm long £1.70  
 K505 20 Assorted Potentiometers—All types including single, ganged, rotary and slider £1.70  
 K528 Electrolytic Pack—All ready cropped for PCB mounting, this pack offers excellent value for money. Good range of values and voltages from 0.47µF to 1000µF, 6V to 100V. 100 £3.95 250 £8.95 1000 £32  
 W4700 Push Button Banks—An assortment of latching and independent switches on banks from 2 to 7 way, DPCO to 6PCO. A total of at least 40 switches for £2.95 100 £6.50 250 £14.00

K524 Opto Pack—A variety of single point and seven segment LEDs (incl. dual types) of various colours and sizes, opto isolators, numicators, multi digit gas discharge displays, photo transistors, infra red emitters and receivers. 25 assorted £3.95 100 £14.95 250 £35

K526 Heatsink Pack—Lots of different sizes and shapes of heatsink for most diode and transistor case styles. A pack of 25 assorted including several large finned types—total weight over 1 kg. £5.50 100 £19.50  
 K525 Preset Pack—Big, big variety of types and sizes—submin, min and std, MP slider, multiturn and cermets are all included. Wide range of values from 20R to 5M. 100 assorted £6.75 250 £12.95 1000 £48

K531 Precision Resistor Pack—High quality, close tolerance R's with an extremely varied selection of values mostly 1/2 and 1/4W tolerances from 0.1% to 2%—ideal for meters, test gear etc. 250 £3 1000 £10

#### 1986 CATALOGUE

Big 64 page catalogue packed with thousands of items from humble resistors to complex disco mixers. 8 page Bargain List + order form included, also Bulk Buyers List & £1.20 discount vouchers. All this for just £1.00 inc. post.

#### NEW SURPLUS LINES

Z469 AL30A amp. Panel 90 x 64mm. 10W RMS O/P with 30V supply. Popular audio amp module—these are equi-put but believed to be working. £2.50.

#### Z467 POWER SUPPLY BARGAIN

BRAND NEW Stabilized Supply in heavy duty ABS case with rubber feet. As used with the "Newbrain" Computer. Input 220/240V ac to heavy duty transformer via suppressor filter. Regulated DC outputs: 6.5V @ 1.2A; 13.5V @ 0.3A; -12V @ 0.05A. All components readily accessible for mods etc. Chunky heatsink has 2 x TIP31A. Mains lead (fitted with 2 pin continental plug) is 2m long. 4 core output lead 1.5m long fitted with 6 pole skt on 0.1" pitch. Overall size 165 x 75 x 72 mm. £5.95 10 for £40


Z475 TRIAC PANEL—240 x 165mm. 14 triacs 2N6346, TXAL1168 or sim. 200V 6-8A; 16 SCR's C106A1 4A 30V; 6 x 4099 in skts; 15 suppressors; 37 ZTX450; min 12V relay; R's C's plugs etc. Only £4.50

**GREENWELD**  
ELECTRONIC COMPONENTS

All prices include VAT; just add 60p P&P Min Access order £5. Official orders from schools etc. welcome—min invoice charge £10. Our shop has enormous stock of components and is open 9-5.30 Mon-Sat. Come and see us!

443D Millbrook Road, Southampton, SO1 0HX.  
Tel. (0703) 772501/783740

# FREEZER FAILURE ALARM

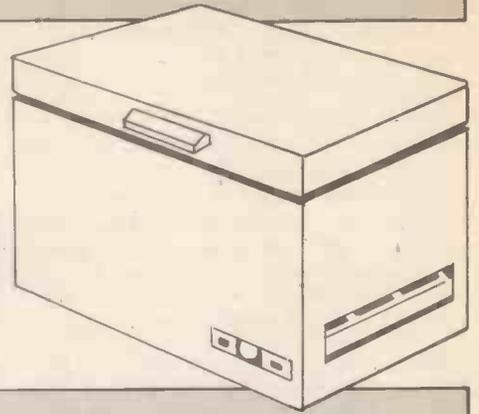

W. HUNTER

**Provides an audible warning of freezer failure**

A DOMESTIC freezer is a very reliable piece of household equipment and generally runs for many years with no trouble at all. If a fault occurs, then there is usually time to get the machine repaired before the food is spoiled, providing the freezer is kept shut and the repair man is called in immediately. But what happens if the freezer is in an out of the way place like the garage when the fault occurs, and it is not noticed for some time? This happened to the author recently and he was left with a large amount of thawing food which had to be used up quickly before it spoiled. This prompted the design and construction of the freezer failure alarm described in this article.

## BASIS OF OPERATION

The circuit described here uses a silicon diode as the temperature sensor, and measures the voltage across the diode which changes as the temperature of the diode changes. The forward voltage of a silicon signal diode will depend upon the particular diode type, but it is usually around 0.7 volts.

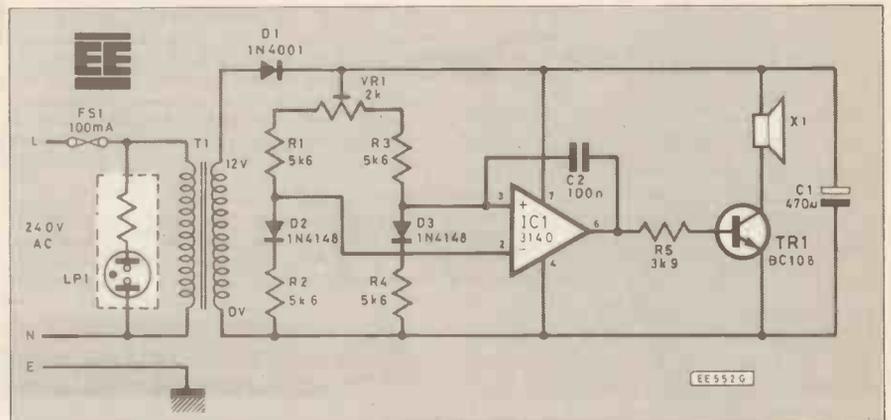


Fig. 2. Complete circuit diagram of the Freezer Failure Alarm.

This voltage falls by about 2mV for every Centigrade degree rise in temperature, and this is known as the temperature coefficient of the diode. Using this property, the diode can be used as a temperature measuring device. Fig. 1 shows the principle of the circuit used in the alarm.

The sensor diode D1 along with R2 forms one arm of a bridge circuit. The other arms are made up of R1, R3, and D2 plus R4. If all the resistors are of the same value, then the bridge will be in balance when the forward voltage drop of the two diodes is equal. Assuming that the two diodes have identical characteristics, then the bridge will be in balance if the two diodes are at the same temperature, and the voltmeter will read zero. If D1 is now cooled, then the voltage across it will increase by approximately 2mV for each Centigrade degree, the

bridge will be unbalanced, and the meter will show a positive reading.

## CIRCUIT

In Fig. 2 the circuit of the alarm is shown. The voltmeter is replaced by an op-amp which amplifies the difference in the voltage between the arms of the bridge. Because the amplifier has no d.c. feedback its gain is extremely high, and its output will switch from low to high with the slightest imbalance in the bridge. The output of the amplifier then drives the base of TR1 which in turn causes the audible warning device to sound. Variable resistor VR1 is used to balance the bridge when the sensor diode is at the required temperature. Capacitor C2 is required to make the amplifier switch on rapidly. It supplies positive feedback to a.c. signals so that as the output voltage begins


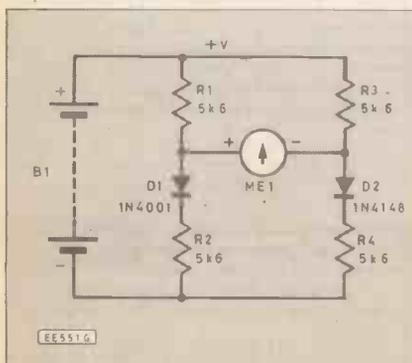


Fig. 1. Principle of operation.

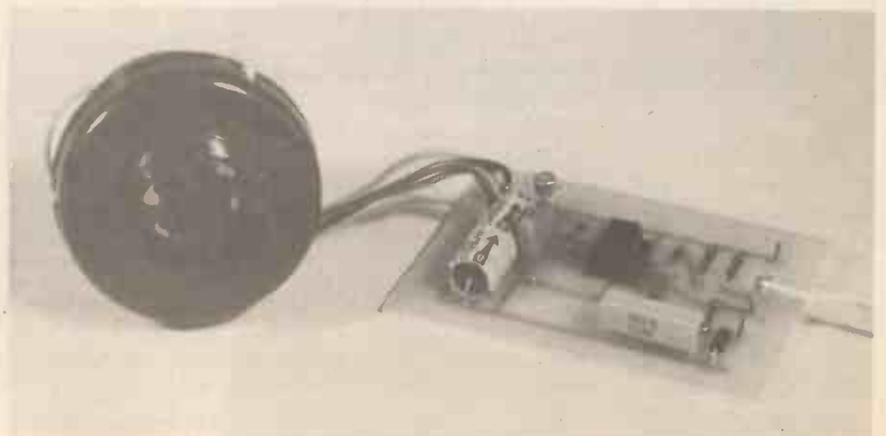

to change, this is fed back to the positive input and speeds up the transition. The circuit requires very little current, and is supplied by half-wave rectifying the 12V from the transformer and smoothing with capacitor C1.

## CONSTRUCTION

The circuit was built on a printed circuit board, the layout of which is shown in Fig. 3. The circuit board is mounted in a diecast box. All components are mounted on the board except the audible warning device—which is mounted on the outside of the box—and the sensor diode.

The diode is soldered to a pair of fine twisted wires and sleeved to protect the connections. The sleeve, which covers the diode itself, not only gives physical protection to the diode but also gives some thermal insulation, so that the diode does not warm up too quickly. This prevents the alarm from going off when the freezer door is opened, but will allow the diode to warm up sufficiently quickly if the freezer should fail.

The audible warning device (X1) was screwed onto the outside of the box in the author's alarm, but could be mounted remotely from the alarm and connected to the main unit with a long lead if required. The warning device uses a very small current, so there should be no appreciable voltage drop unless the connecting lead is very long or the wire is very thin. In the prototype X1 was a piezo ceramic device obtained from Verospeed (type SM2), but virtually any

# COMPONENTS

## Resistors

R1,R4	5k6 (4 off)
R5	3k9

## Capacitors

C1	470 $\mu$ elect. 40V
C2	100n

## Semiconductors

D1	1N4001
D2,D3	1N4148 (2 off)
IC1	3140 op. amp.
TR1	BC108

## Miscellaneous

X1	Audible warning device (15 to 20V operation)
T1	12V 1.5VA mains transformer
LP1	Mains neon indicator
FS1	20mm mains fuseholder and 100mA fuse

Diecast case, 113 x 63 x 31mm; p.c.b. available from the *EE PCB Service*, order code 534; connecting wire (see text), sleeving (see text), fixings, etc.

Approx. cost  
Guidance only

**£7.50**

See  
**Shop  
Talk**  
page 485

similar device could be used as long as it is rated for use at 15–20 volts.

## TESTING

Once the circuit has been built and checked, it can be tested. This is easily done by switching on with both diodes at room temperature, and adjusting VR1 until the alarm sounds, then back-off VR1 until the alarm just stops. If D2 is now warmed up by holding above a hot soldering iron (take care not to touch the diode with the iron or it may crack) the alarm should begin to sound. If VR1 does not have enough adjustment to either switch the alarm on or off then the bridge must be well off balance. This may be due to an error in construction or a component that is faulty. It is a simple matter to check the components with a meter to ascertain where the fault lies.

When the circuit has been tested, the sensor diode can be put in the freezer, and the connecting wires brought out over the door seal at a convenient point. If the wires are thin (use 7/0-1mm wire), then the seal of the freezer will not be impaired.

The diode should be left in the freezer for at least fifteen minutes to allow it and the sleeving to cool to the surrounding temperature before the alarm is adjusted. During this time the alarm should be switched on and the box lid closed to allow the diode in the other side of the bridge, D3, to reach its working temperature. This is necessary because the bridge circuit compares the voltages across the diodes, and cooling D3 has the same effect as warming D2. The potentiometer should, of course, be adjusted so that the alarm is not sounding during this wait. After this time the alarm can be adjusted in the same way as it was during testing. The alarm is now ready for use and the box can be closed up.

## RELIABILITY

Because of the simplicity of the circuit, it should be very reliable and should give no trouble, but for peace of mind it might be worthwhile testing the alarm once or twice a year. This may be done by removing the sensor from the freezer and checking that the alarm sounds after a small delay. This also provides an opportunity to check the calibration of the alarm. The author's alarm has been in use for more than six months and has given no trouble apart from a small recalibration when it was tested at four months. The adjustment required was very small and would not have caused any problem had the freezer failed. □


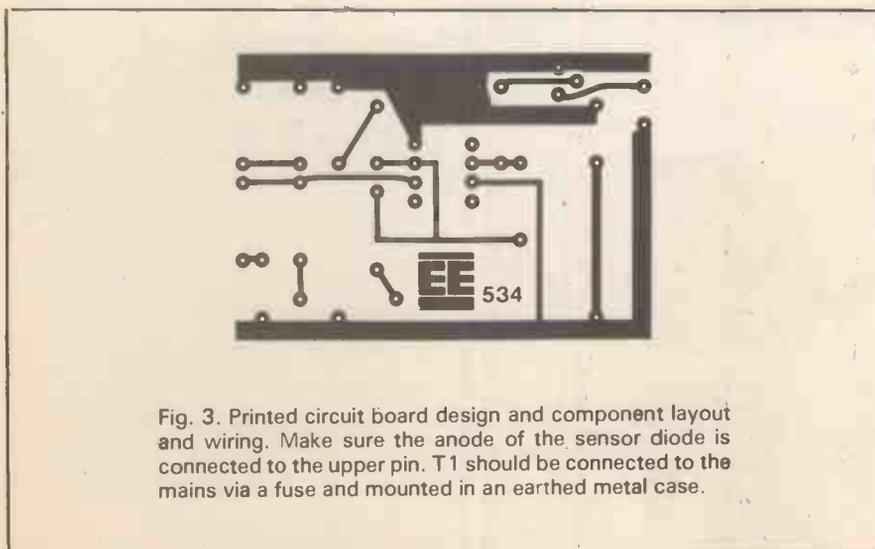


Fig. 3. Printed circuit board design and component layout and wiring. Make sure the anode of the sensor diode is connected to the upper pin. T1 should be connected to the mains via a fuse and mounted in an earthed metal case.

NEXT MONTH—WATCH  
OUT FOR THIS SYMBOL

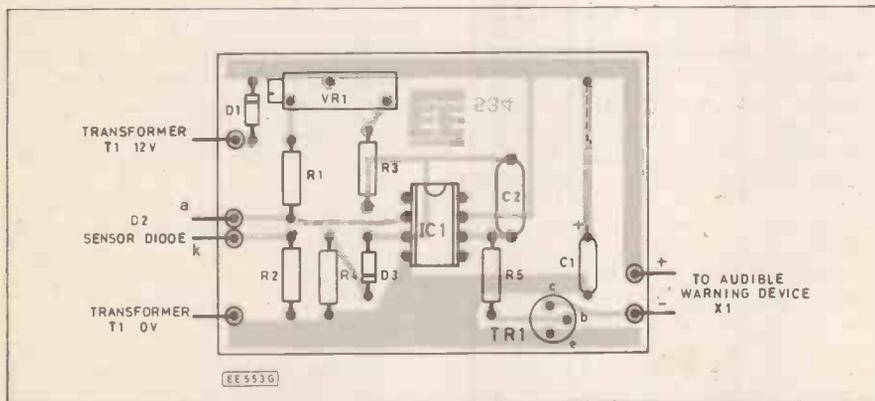

IT COULD SAVE  
YOU MONEY

# Exploring electronics

OWEN BISHOP

## Part 3 Another transistor switch

This series is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. There will not be masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

**T**HIS month we build another circuit based on a simple transistor switch. This circuit introduces you to ideas that are very important in circuit design—the idea of the *potential divider* and the idea of *feedback*. It also introduces another kind of semiconductor device, the *light-dependent resistor*.

### POTENTIAL DIVIDERS

Sum of resistors  $R_1$  and  $R_2 = R$  (Fig. 3.1a).

Potential across AC ( $V_{AC}$ ) is  $V_{AC} = IR = I(R_1 + R_2)$  so  $I = V_{AC}/R$

Potential across BC ( $V_{BC}$ ) is  $V_{BC} = IR_2$

$$= \frac{V_{AC}}{R} \times R_2 = V_{AC} \left( \frac{R_2}{R} \right)$$

The potential across AB is divided, and a fraction of it ( $R_2/R$ ) appears across BC.

This assumes that we draw no current from point B. If a small current is drawn, there will be little change, but if a large current is drawn the potential across BC may fall greatly.

In Fig. 3.1b  $V_{BC}$  can have *any* value between zero and  $V_{AC}$ , depending on the position of the wiper of the variable resistor, VR

### LIGHT DEPENDENT RESISTOR

The light dependent resistor (l.d.r.) is a resistor made from a semiconducting material such as cadmium sulphide. When light falls on it, the energy of the absorbed light causes additional electrons to be set free. This provides more

charge carriers, so current can flow more readily. The effect of this is that the resistance of the material decreases. The brighter the light, the lower the resistance. Its resistance may fall from 10 megohms in darkness to as low as 20 ohms in bright light.

The light dependent resistor (l.d.r.) is also known as a *photoconductive cell*.

### ELECTRONIC CANDLE

The electronic candle to be described is a novelty to amuse your family and friends. The "candle" has an electric lamp instead of a wick. When you strike a match and hold it close to the lamp, the lamp lights. When you blow, the lamp goes out. The candle works best in a dimly lit room.

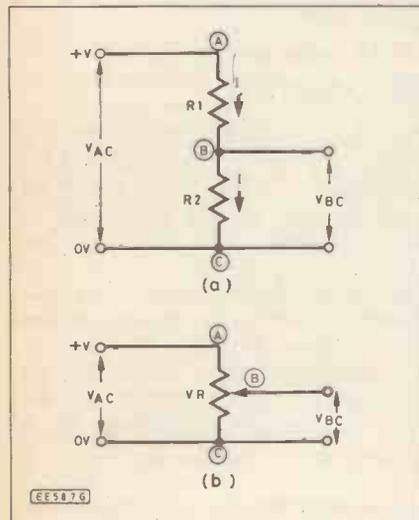


Fig. 3.1. Potential divider arrangements.



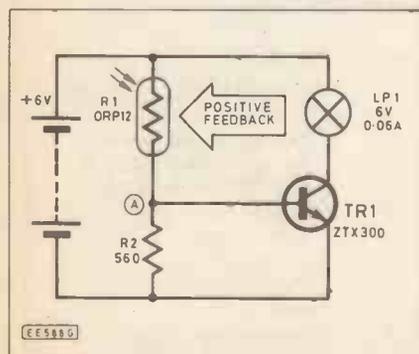


Fig. 3.2. Circuit diagram for an "Electronic Candle". The practical layout is shown opposite.

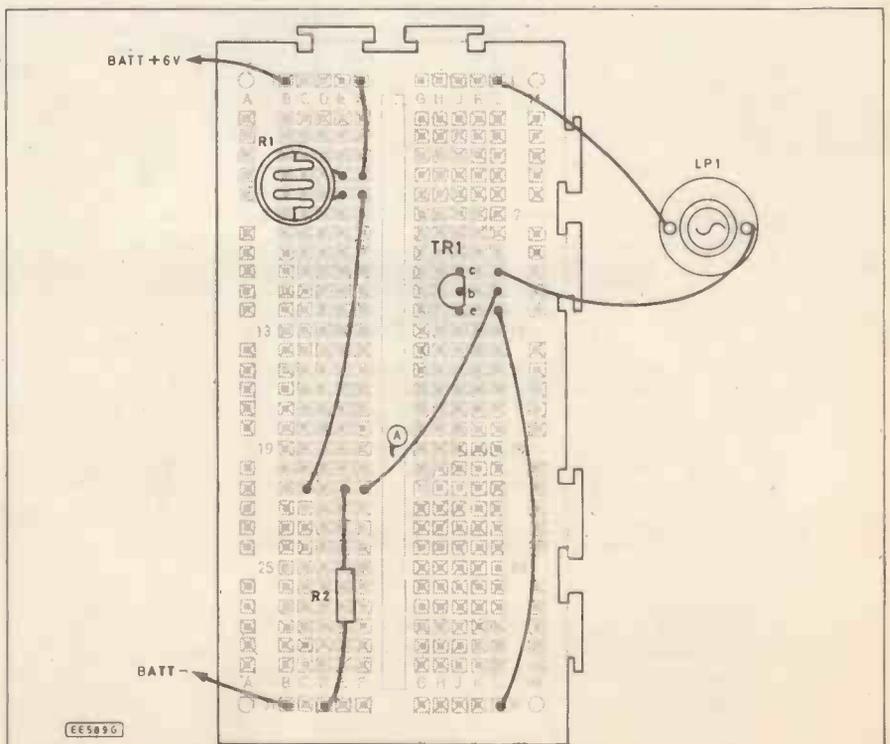

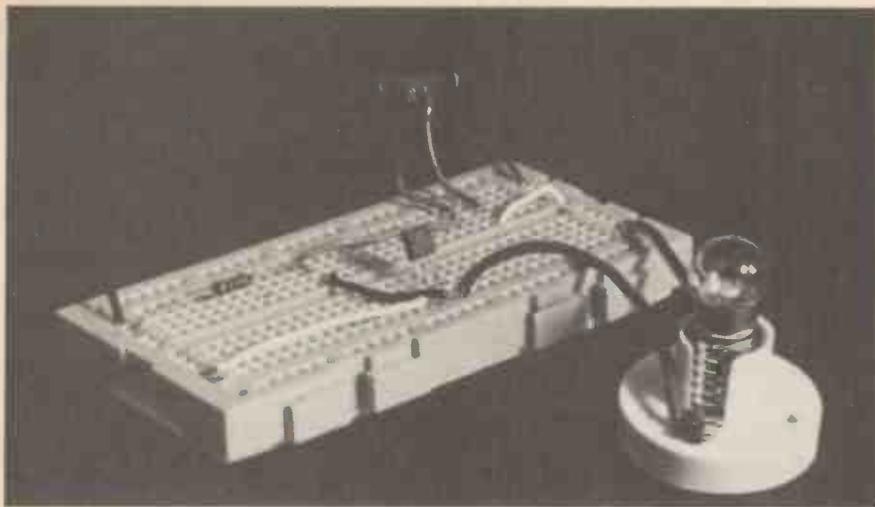

## Resistors

R1	MKY7C38E or ORP12 light- dependent resistor
R2	560

## Transistor

ZTX300 *n*pn junction transistor

## Miscellaneous

LP1 6V 0.06A lamp in holder;  
materials for making candle and  
concealing circuit if required;  
breadboard, e.g. Verobloc.

Approx. cost  
Guidance only

**£5**

## HOW IT WORKS

The lamp is turned on and off by a transistor used as a switch. The base current to the transistor comes from a *potential divider*. This is made up of R1 and R2 (Fig. 3.2). One of the resistors (R1) in the potential divider is a *light dependent resistor*. In the dark this has a resistance of several hundred kilohms. As the amount of light falling on it is increased, its resistance decreases. In bright light it has a resistance of only about 100 ohms. In the dark the potential at A is low, almost zero volts. No base current goes to TR1, so TR1 is off and the lamp is dark. If we shine a light on R1 (or hold a burning match near to it), its resistance falls. The potential at A rises and base current flows to TR1. The transistor is turned on, and the lamp lights. In the electronic candle, the lamp and l.d.r. (light dependent resistor) are close together. The light from the lamp keeps the resistance of R1 low, so once

turned on the lamp stays on. Even when we take the match away, the lamp stays on. To the uninitiated it appears that when we "light" the candle, using a match, it stays lit just like an ordinary candle. The "signal" from this circuit is the light coming from the lamp. Part of this signal is fed back to the l.d.r. The way the circuit is arranged ensures that light from the lamp keeps the lamp switched on. Conversely, absence of light from the lamp keeps the lamp switched off. This is positive feedback.

The electronic candle has a small shutter of card which rocks sideways and partly covers the l.d.r. when we blow on the candle. This partly breaks the beam of light between the lamp and l.d.r. As this happens the resistance of R1 increases sharply, the potential at A falls and TR1 is turned off. The lamp goes out. Now, even though we have stopped blowing, the amount of light reaching R1 from the surroundings is

not enough to turn on the lamp again. Just like an ordinary candle, it stays out when it has been blown out. The unit can be built up and tested as shown in Fig. 3.2.

## CONSTRUCTION

There is a lot of scope for your imagination in making this circuit look like a real candle. The drawing (Fig. 3.3) shows one way of doing it, but there are lots of other equally good ways.

## FEEDBACK

Most electronic circuits have some kind of *output signal*. The output signal may be sound, movement, electric current, or (as in this month's circuit) light. A small part of this signal may be taken and *fed back* to the circuit from which it came. The signal fed back is used to modify the output of the circuit.


Feedback may be positive or negative. If it is positive, an increase in the output signal leads to a further increase in output signal (until it reaches its maximum). If it is negative, an increase in output signal leads to a decrease in output signal (until it is zero or reaches a stable level).

This month's circuit shows positive feedback. We shall discuss negative feedback in later issues.


Next Month: Using a Thermistor.

## You will Need . . .

R1	Thermistor, type VA 1040 (or any similar type with a resistance of about 150 ohms at 25°C)
VR1	Variable resistor 1k
LP1	Filament lamp 6V 0.06A with holder
D1	TIL209 or similar light emitting diode
B1	Battery—box with four 1.5V cells
Breadboard (e.g. Verobloc); pointer-knob for VR1.	

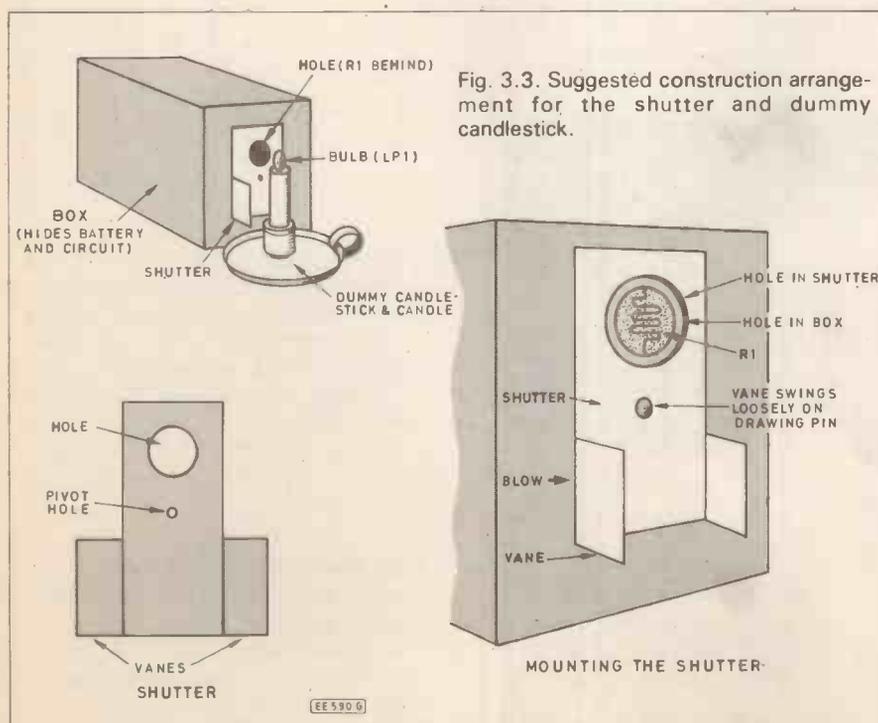

# CAR TIMER

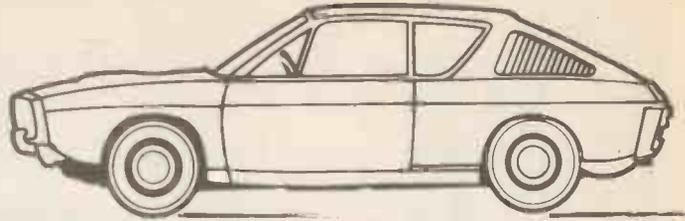

**D. BUTLER**

**Don't choke your car or collect parking tickets. The choice is yours!**

THE Car Timer project was originally designed as a "choke-on" reminder for cars which do not have any such indication. However, other applications can easily be found, as the circuit is a timer with an alarm. The timer is fully adjustable, as is the alarm note, it consumes little power and occupies a modest amount of space.

## CIRCUIT DESCRIPTION

The timer is formed around IC1 (Fig. 1), a 4060 14-stage ripple counter and oscillator. Components R1, R2 and C1 set the oscillator frequency, hence the timing period. The reset pin (pin 12) is provided with a pulse every time the supply is connected by the action of C2 and R3. In this way the timer is always initiated at the same point. The timer is activated by applying +12V to the supply line. Particular ways of achieving this will be considered later. The actual timing period is adjusted by connecting an oscillator output to the alarm circuit described below.

## PIEZOELECTRIC CIRCUIT

The alarm circuit produces a twin tone which may be modified by changing components C3, R5 and C4, R6. The transducer

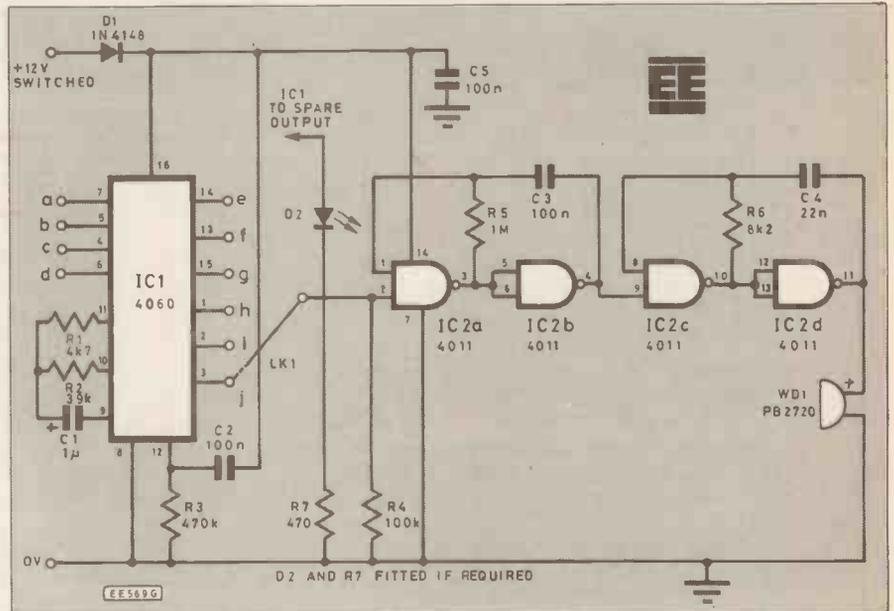


Fig. 1. Complete circuit diagram for the versatile Car Timer. Note timing link LK1.

(WD1) is a ceramic piezo-electric element which generates tones when a 3V peak square wave is applied. Rigid mounting methods ensure maximum volume levels, which is necessary in the environment of a car. The element has no moving parts, is robust and consumes little power.

A final mention should be made of diode D1, which protects the circuit from reversal of power connections.

**Table 1**

Connect LK1 to:	Approx. time
a	1/2 sec
b	1 sec
c	2 sec
d	4 sec
e	8 sec
f	18 sec
g	36 sec
h	2 min 23 sec
i	4 min 45 sec
j	9 min 30 sec

**NOTE:** The times given are also the "on" time of the alarm tone, e.g. LK1 to J. Alarm activates after 9 min 30 sec. Alarm turns off after 9 min 30 sec unless supply is removed first.


Figures quoted are for the following conditions:

R1 = 4k7 Supply voltage = 12  
 R2 = 39k  
 C1 = 1μ

## CURRENT CONSUMPTION

Based on the component values given above and 12V supply: Timer on = 0.75mA excluding l.e.d.; with alarm = 1.7mA. (Alarm tone alters current drawn from 1.5 to 3mA as frequency increases.)



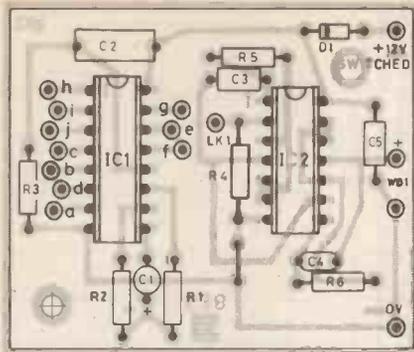

EE570G


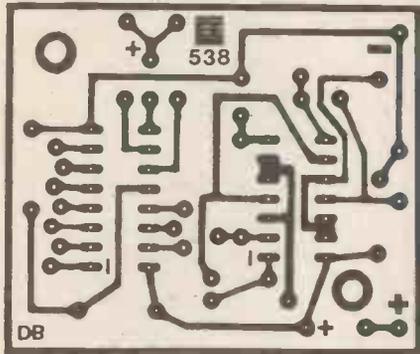
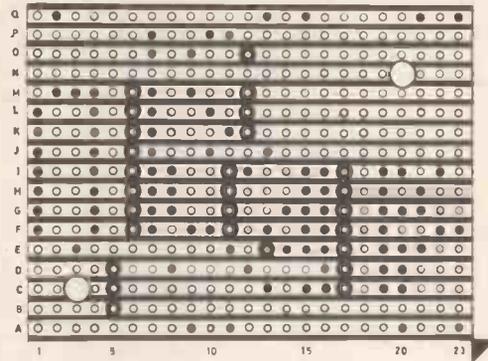


Fig. 2. Component layout and printed circuit master (full size), see EE PCB Service. Note a link wire should be attached to LK1 and one of the timing pins.

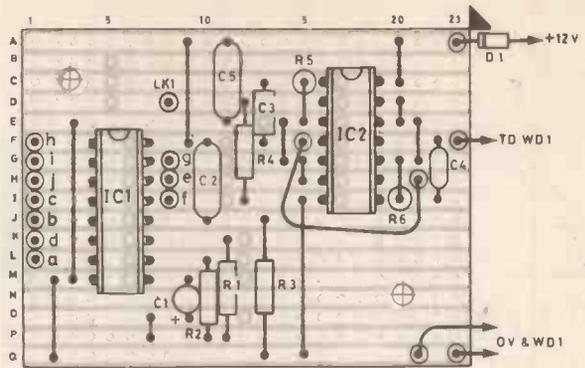

EE571G

Fig. 3. Component layout and details of breaks to be made in the underside copper strips of the stripboard version.

## COMPONENTS

### Resistors

R1	4k7
R2	39k
R3	470k
R4	100k
R5	1M
R6	8k2
R7	470 (if required)
$\frac{1}{4}$ W $\pm$ 5% carbon types	

See

**Shop  
Talk**  
page 485

### Capacitors

C1	1 $\mu$ 16V tant. bead
C2	100n polyester
C3	100n min. layer polyester
C4	22n min. layer polyester
C5	100n polyester


### Semiconductors

IC1	4060 ripple counter and oscillator
IC2	4011 dual input NAND gates
D1	1N4148 diode
D2	I.e.d. with mounting clip
WD1	piezo transducer PB2720

### Miscellaneous

Printed circuit board (available from the EE PCB Service Order Code 538) or Veroboard; case (if required) (Verobox part no. 202-21024B 71.5 x 49 x 24.5mm); mounting hardware; spade connectors; switch to activate timer, e.g. microswitch, mercury tilt, push button (see text).

COMPONENTS  
approximate  
cost **£5**

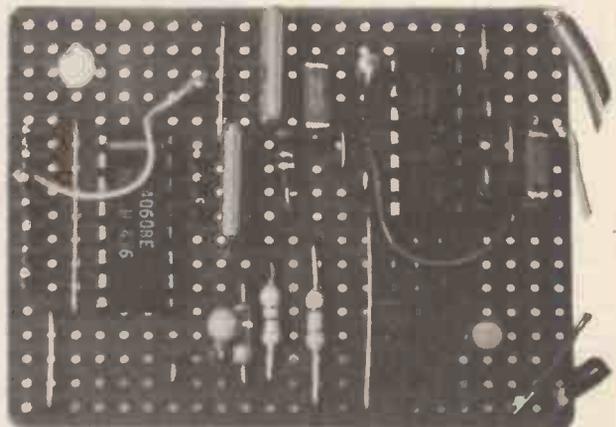

The completed stripboard version. Note the link wire (LK1) attached to one of the timing pins.

## CONSTRUCTION


The circuit may be constructed using the p.c.b. layout (Fig. 2) or the Veroboard layout (Fig. 3). No special construction techniques are used, except that care should be taken when soldering in IC1 and IC2 (sockets could be used). Remember to add a wire link from LK1 to one of the oscillator outputs using Table 1 for the intended timing period. If an I.e.d. indicator is used to show the timer is on, connect it to any

spare oscillator output via a 470 ohm current limiting resistor R7.

The piezo sounder should be firmly mounted to obtain maximum sound levels. Connection to the outside world, and the type of project case used depends largely on the application. The prototype was mounted in a small Verobox (part number 202-21024B) and connections made using spade terminals and "Scotch-block" break-in connectors.


SOME SUGGESTED APPLICATIONS ON NEXT PAGE

## SUGGESTED APPLICATIONS

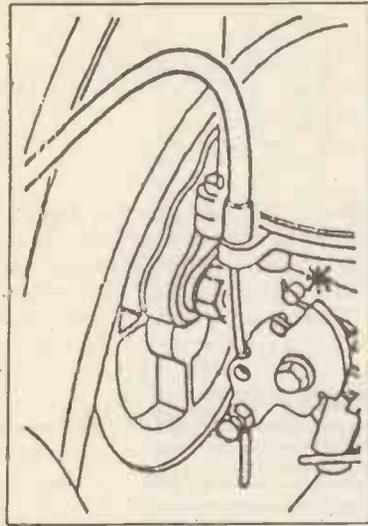

1

EE573G

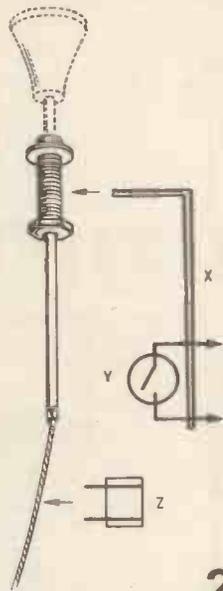

2

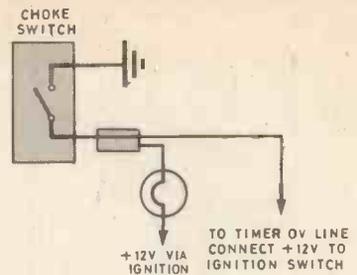


Fig. 4. Circuit of choke switch with warning light. The mechanical arrangement is shown left: 1 using microswitch and 2 using reed relay with magnet.

## APPLICATIONS

As mentioned earlier, the project was originally designed as a "choke-in" reminder and, therefore, the unit needs to be activated when the choke control is used. Obviously it is not possible to give detailed switching methods used on every type of car, but Figs. 4 to 6 illustrate several alternatives.

The timer may be activated easily if the choke control already has a switch included, usually for a dashboard warning lamp. In many cases this switch is connected to earth which means that the timer +12V should be permanently joined to +12V via the ignition. Using the choke cable is slightly more difficult, and sections (1) and (2) show switching methods.

(1) Shows the choke cam plate on the side of the carb. A miniature microswitch is mounted where indicated by "\*\*\*\*". The normally closed contacts are used as the microswitch lever will be released as the choke is turned on.

(2) Shows the choke cable near the control knob. A bracket (X) is attached to the control knob mounting thread, on which is a reed switch (Y). This is connected to +12V via ignition, and the +12V switched line of the timer. A small magnet is attached to the cable using twisted wire and insulation tape. The distance from the reed switch is judged by pulling the choke out and seeing whether the reed switch has engaged. Push the control back in and check that the switch has turned off. You may be surprised how far the magnet has to be fastened from the reed, as they are very sensitive. The reed and magnet method may be employed at either the control knob or carb end.

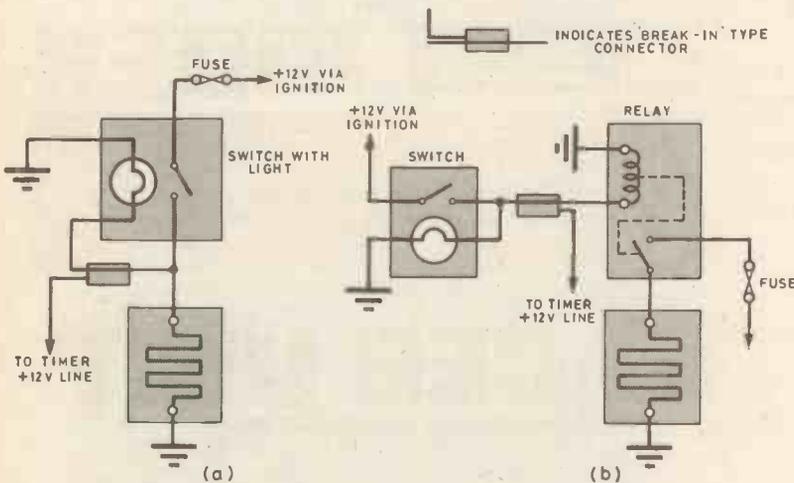


Fig. 5. Heated rear screen circuits, (a) without relay (b) with relay.

UPPER SECTION CONTAINS 9V BATTERY HELD IN PLACE BY SELF ADHESIVE PADS.

Fig. 6. Method of using circuit as a parking meter timer.

MATCHSTICKS USED TO JOIN TWO BOXES (LIDS NOT USED)

USE TOGGLE OR SLIDE SWITCH TO TURN TIMER ON

BUZZER MOUNTED UNDER CIRCUIT BOARD

EE573G

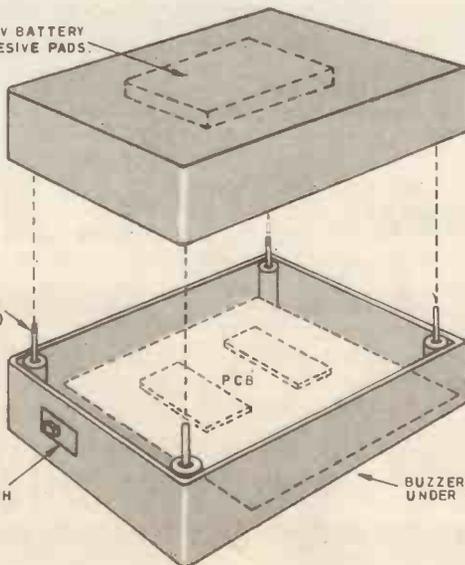


Fig. 5 also shows how the timer may be used on the heated rear screen. If the alarm goes off and the heater is still needed, just turn the switch off and then back on. The alarm will be cancelled for another time period. Finally Fig. 6 shows a parking meter and egg timer using two Veroboxes back to back.

Use two miniature Veroboxes without lids, fix lower sections using dowel, e.g. matchsticks. A 9V battery fits in top section, the circuit board in the lower section. Activate timer using an ultra-miniature toggle or slide switch. Adjust timing components to suit application, e.g. increase C2 to increase the time periods of the outputs.

# OCTOBER FEATURES...

## 10W AUDIO




## AMPLIFIER

Designed to be extremely versatile and useful, this amplifier provides 10 watts r.m.s. sine wave output power (20 watts peak) and will accept a wide variety of inputs. There are two "flat" inputs, one for dynamic and electret microphones, guitar pick-ups and other low signal sources. The other input accepts signals at standard "line" levels between 100mV and one volt. A third, completely independent input is provided with full disc RIAA equalisation for use with moving magnet pick up cartridges. The inputs can also be mixed to blend announcements with music, etc.

Three projects under one title—all simulations of the *Knight Rider* lights from the TV series. The three are: a lapel badge, using six l.e.d.s, a larger l.e.d. unit with 16 l.e.d.s and a mains version capable of driving six mains lamps totalling over 500 watts.

## LIGHT RIDER

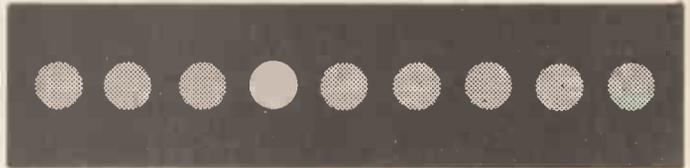

## MICROTRACER UNIT



The Micro-Tracer shows an interesting way in which a computer and two integrated circuits can be used as a signal injector and tracer. The software has been written for the BBC, C64 and PET series of computers.

**Feature**

## THE DIFFERENTIAL AMPLIFIER

EVERYDAY  
**ELECTRONICS**  
and **ELECTRONICS MONTHLY**

OCTOBER ISSUE ON SALE FRIDAY, SEPTEMBER 19

## YOUNG ELECTRONIC DESIGNER AWARDS

- ★ *Umpire's decision wins top prize, and a job!, for Stephen and Howard*
- ★ *Tim breaks sound barrier to win the Intermediate Class*
- ★ *Gareth "gets on his bike" to win the Junior Category*

Now in its second year, the *Young Electronics Designer Awards Scheme* is run by Cirkit Holdings in conjunction with co-sponsors Texas Instruments and Electronics Times—a trade magazine. The competition challenges students to design and construct an electronic device with a possible application in everyday life.

After the preliminary rounds, the final aspiring designers gathered in the Great Hall at the Westminster School, London, recently to hear whether they were to be amongst the prizes. The top prize in the Senior Category carried a reserved place in the Texas graduate intake—a job!

This year, the competition was divided into three sections, senior (19–25), intermediate (15–18) and junior (under 15). Texas also donated a business computer to the establishment sponsoring the winning entries in the older age groups and 30 TI calculators to the school sponsoring the winner in the junior class.

The 1986 winners were announced by Maggie Philbin, presenter of BBC's *Tomorrow's World*, and presented by the Rt. Rev. Michael Ashley Mann, The Dean of Windsor, and Dr. Robb Wilmott CBE, Chairman of European Silicon Structures.

### Final Results

After the opening ceremonies and speeches the big moment arrived and the judges' final decisions were revealed.

The winners in the senior category (19–25) went to Stephen Osborne (24) and Howard Mitchell (21) of Essex University for a Netball Umpire's Electronic Scorer. They received £500, £450 a year sponsorship to complete their studies, a vacation job and a



*Dr Robb Wilmot CBE and the Rt. Rev. Michael Ashley Mann congratulate Stephen and Howard on becoming the winners of the Senior Section.*

reserved place in TI's graduate intake; upon graduation.

Second place (£250) went to Michael Scott (21), David Boyd (20) and Douglas Mackay (20) from Thurso Technical College for their Robotic Rehabilitation Arm. Third position (£100) was awarded to Adrian Travis (23) for his entry Electronic Teaching Bricks.

### Intermediate Class

In the intermediate category, the winner was Tim Price who received £350 for his design of a Digital Audio Processor using a 16-bit processor and 128K of RAM.

The runner up in this section went to the only girl entrant, Rosemary Erskine (18) of Norwich High. Her Digital Anemometer won Rosemary £200. The £75 third prize went to James Lucy (16) for his BBC Micro Stage Lighting System.

### Junior Class

Winner of the junior class (£250) was Gareth Arthurs (13) for his novel Bicycle Lighting Unit. The unit switched the cycle lights between dynamo and battery according to the dynamo output, preventing them from being extinguished when the cycle stops at road junction, traffic lights or is parked.

Second spot (£150) went to David Marshall (14) for his Wheelchair Controller project and a Thermometer for the Blind or Partially Sighted won £50 for Jonathan Ibbotson (14).

For details of how to enter next year's competition, write to: Carla Sharyk, Young Electronic Designer Awards, Standard House, 16–22 Epworth Street, London, EC2A 4SX.



*(above) The Robotic Arm is demonstrated to Maggie Philbin (BBC) and Peter van Cuylenburgh (far right) of TI by Michael, Douglas and David.*

*(left) The Digital Audio Processor that won first prize for Tim Price in the Intermediate Category.*

*(right) Gareth (13) with his trophy and bicycle lighting unit that won top prize in the Junior Class.*



## INDUSTRY YEAR AWARDS

A £115,000 scheme to encourage closer links between industry and education has been announced by Minister of State for Industry, Peter Morrison.

Mr Morrison said: "I am pleased to announce that my department is launching the Industry Year Award to encourage collaboration between industry and institutions of further and higher education. We are offering £115,000 in cash prizes, to include one for the best example of collaboration with a small firm.

"Prizes will be given in three areas of collaboration: course development, training programmes and technology transfer. The winner in each section will receive £25,000, Runners-up £10,000 and a special prize of £10,000 will be offered for collaboration with a small firm."

## RADIO DATA

Radio Data System (RDS) is the new system, due to commence broadcasting in September, that will, it is claimed, make it easier for listeners to find their favourite radio programmes.

An inaudible signal will be added to v.h.f./f.m. transmitters which will enable a new generation of receivers to perform a variety of automatic functions. These range from advanced automatic tuning with a readout of the station name, a clock that is always accurate, instant switching to pick up traffic messages on other channels to the provision of a visual readout of music details of the concerto you are listening to.

The signals to control these functions are broadcast as digital codes in parallel with the main programme.

## Comet's New Dish

Comet became the first major national retailer to enter the satellite age when two complete satellite TV receiver packages went on sale at the end of last month (July).

A basic single satellite system, offering up to eight additional TV channels, is available for the sum of £890 and a multi-satellite system, offering 14 extra channels, is being offered at £1190. The prices include full installation, 12-month guarantee, and a "lifetime" satellite dish licence.

Pilot stores to carry stocks of the satellite packages are: Hull; Norwich; Leeds and Rochester. There is no extra charge for pre-site visits.

Sir George Jefferson, Chairman of British Telecom, announced that the group had achieved a profit of £1,828 million for the year ended March '86. This was 20 per cent up on the previous year.

Of this, £18 million was being allocated to the new employees' profit sharing scheme.

## FREE MODEMS

Following the purchase of substantial stocks of modems, Micronet have announced that they will be issuing them free to members subscribing for one full year in advance to both Micronet and Prestel.

Following the example of the French, they hope that this precedent for the UK will encourage Prestel to do likewise.

## Just Tandy

It has been reported that Tandy is to close half of its Computerworld stores because they are not making enough money. Instead certain areas will be covered by sales staff working from home, supported by their nearest centre.

Eight stores are affected and cover the areas of Bradford, Crawley, Croydon, Hull, Leicester, Liverpool, London's Victoria and Southampton. This move will leave around 40 staff to be redeployed, retrained or made redundant.

## The Watford Gap

One of the UK's leading mail order suppliers for BBC Micro accessories, Watford Electronics, is to break new ground by setting up a dealer network.

The move means that in future Watford's vast range of products comprising of hardware, software and peripherals will be available from selected dealers.

Commenting on this new venture, Watford's managing director Nazir Jessa said, "There are a lot of people who don't like to purchase via mail order and who would gladly pay a little extra if only they could buy from their local dealer."

## ROYAL SOCIETY FELLOWSHIPS

British Telecom has agreed to sponsor Royal Society Fellowships for Chinese scientific research workers to visit the UK to work in universities and research institutes. Awards will be made in fields of particular interest to BT, such as telecommunications and information technology.

Fellowships will normally be for periods of six months. Awards will cover living expenses in the UK, but not international fares which candidates will be expected to find from their home organisations.

Mr. David Pentecost is to be British Telecom's new Chief Executive, Procurement, in charge of the company's £1,900 million a year purchasing programme.

## CALLING OF THE CHURCH

Five flagpoles adorn the roof of Holy Cross Church in Knutsford, Cheshire, but only one is real. The others are aeriels which bring British Telecom's Cellnet cellular mobile radio network to this part of the north of England.

The church tower is one of the highest points on the local landscape, and an ideal location for the aeriels. Concerned not to spoil the view, BT decided to disguise them as flagpoles, complete with ropes and pulleys.

Pictured here, the Vicar of Holy Cross Church, the Reverend Paul Moulton, stands next to the real flagpole with the four Cellnet aeriels around him.

"I am pleased that the Church agreed to placing the aeriels here. They are absolutely out of the way and attract no attention—it's a good example of caring for the environment", he says.



# ...REPORTING AMATEUR RADIO...

TONY SMITH G4FAI

## AURORA

Many radio amateurs have rotatable antennas enabling them to transmit their signals in the direction of the station they wish to contact. Sometimes, however, it is more effective to beam in a completely different direction.

An example of this is auroral propagation, which becomes possible when a solar flare releases energy from the sun. Energetic charged particles are carried to earth by the solar wind, impinging on the upper atmosphere and ionizing the E layer in the auroral zones around the poles.

The resulting aurora act as reflecting layers, and by directing their VHF antennas northwards amateurs make contact with distant stations who are also beaming to the north. To take full advantage of the phenomenon, advance warning is necessary. Beacon stations nearest to the auroral zones can provide the first signals to be reflected to more southerly climes, and some enthusiasts have receivers monitoring beacon frequencies continuously for any sign of an auroral event.

Others tune to Leicester University's experimental auroral monitoring radar station at Wick, on 153.2MHz, and others to Scandinavian TV video carrier transmissions around 50MHz. Immediately signals are heard above a certain strength, warning networks are activated to alert others of possible aurora.

Events are sometimes repeated after 27 days, coinciding with the rotation period of the sun. Some amateurs keep a 27 day calendar to record occurrences and forecast future events. Aurora follow a seasonal pattern, peaking around March and September, although they can occur at any time throughout the year. When radio aurora occur at night in clear weather, there may also be visible aurora.

Amateurs in northern locations have the greatest success, but in major events stations in the south of England, and in Europe as far south as Italy, can participate. Signals received have a distinctive rough sounding note, and are slightly off frequency due to Doppler shift. This effect becomes more noticeable the higher the frequency of the signals, which are receivable up to 432MHz on occasions. Morse is the favoured mode of transmission, as weaker signals are easier to copy, but s.s.b. speech can be used, especially on 50MHz where Doppler shift is minimal.

Last February, despite the current low point in the solar cycle, there was an unexpected major aurora, causing great excitement among many amateurs.

British v.h.f. stations, even in the south, made exceptionally long distance contacts into eastern Europe, Scandinavia, and USSR call-areas. In the USA, the effect of the aurora reached nearly as far south as Florida, with record-breaking contacts of up to 1348 miles on two metres, and stations spread out across normally sparsely populated bands trying to find clear frequencies.

Auroral working is a fascinating activity, combining the possibility of outstanding success with some degree of uncertainty. Next time you hear on the news that the aurora borealis can be seen from your area, think of all the local amateurs rushing to their rigs. Better still, if you know anyone with amateur v.h.f. receiving facilities, get round there fast, and listen in to the action!

## NICE DAY OUT

In 1984, the Dunstable Downs Amateur Radio Club hit on the idea of holding a national amateur radio car boot sale, with few traders, just amateurs selling to amateurs at bargain prices. They held it at Old Warden Aerodrome, Biggleswade, Beds, home of the Shuttleworth collection of

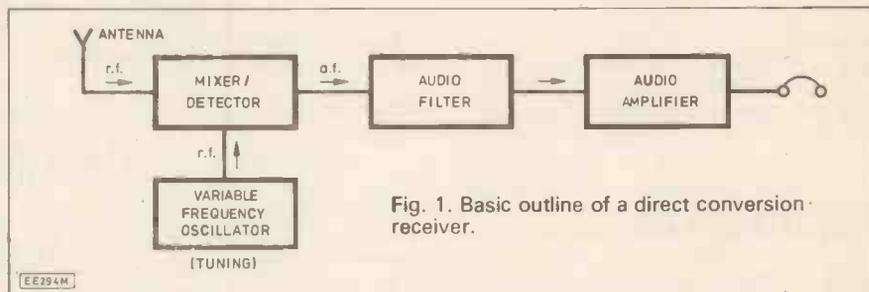


Fig. 1. Basic outline of a direct conversion receiver.

historic aircraft, and it was an instant success.

Last year the event was repeated, with over 100 car boots offering components, accessories, receivers, transceivers, computers, even household and motoring items. Now an annual event, this year's sale, on Sunday, 21st September, promises to be even bigger and better, and an outing for all the family.

The aircraft and motor museum is an attractive venue in its own right. Combine this with an opportunity to find out something about amateur radio at first hand, including a special-event talk-in station, GB4SC, visit the RSGB's bookstall and information stand, and pick up some useful components or other goodies for that next EE project, and you have a fine day out!

For 50p admission, deductible from the museum admission charge of £1.50, plus free car parking, it must also be one of the bargain outings of the year!

Apart from organising this event, the Dunstable club's activities include radio DF (direction finding) hunts; amateur TV; construction contests; and visits to places of interest. They participate in radio contests from a site on Dunstable Downs; provide the call-in station for the big RSGB rally at Woburn in August; and have a good programme of lectures throughout the year.

Newcomers to amateur radio are welcome in all these activities. Contact Phil Morris, G6EES, on Dunstable 607623, for further information, mentioning this column!

## QUESTION CORNER

**Q. Is there any type of simple receiver I can build to receive amateur transmission?**

A. Traditionally, the regenerative receiver has been recommended for beginners to listen to amateur signals. Simple designs using just one or two transistors have appeared in EE, and this type of circuit will receive single sideband speech, Morse, and a.m. transmissions surprisingly well.

In recent years there has been a lot of interest in direct conversion receivers which are equally easy to make, although there is a need for a stable variable frequency oscillator in the circuit. A simple receiver of this type is generally claimed to give better results than a regenerative circuit.

The diagram shows the basic idea. The wanted r.f. signal is mixed with the output of a local v.f.o. This oscillator is tuned slightly off the frequency of the incoming signal, and the difference between the two signals is at audio frequency, which can be filtered to provide any desired degree of receiver selectivity before audio amplification.

A disadvantage of d.c. receivers is that they provide double signal reception for Morse, as the sidebands of the wanted transmission can be resolved as audio signals on either side of zero-beat, the tuning point where the incoming signal and the local signal cancel each other out.

This turns to an advantage in receiving single sideband signals, when the appropriate sideband can be selected to give good reception. A.M. signals are resolved by tuning to zero-beat.

Obviously, the simpler a d.c. circuit is, the more its limitations, but even in its simplest form it can provide a useful introduction to amateur radio. Improvements can be made by using r.f. amplifiers/attenuators, improved detectors and audio filters, and by other means, and high quality performance then becomes possible.

A particular attraction of the d.c. receiver to amateurs is that the local oscillator can also serve as the v.f.o. for a low power transmitter. This arrangement is particularly popular for Morse transmission, and some of the QRP operators I have mentioned previously used transceivers of this type to extremely good effect.

# SHOP TALK



BY DAVID BARRINGTON

## Eureka!

Leading supplier to the BBC Micro market, **Watford Electronics** has unveiled a new RAM Expansion Card called the Eureka!

Announcing the latest addition to their range of BBC Micro expansion products, Mr. Nazir Jessa MD said "The Eureka Card would have made Archimedes jump out of his bath twice as quickly!"

Not only is the Eureka claimed to be cheaper than a Second Processor, but it also provides up to 14K more RAM than a 6502 Second Processor gives to the "Hi" versions of View Basic and Wordwise Plus. Shadow RAM is provided automatically.

The card fits into the processor socket of the BBC Micro and is controlled by software contained within a standard side-ways ROM. It is fully buffered, not only to the on-board RAM but also to the BBC Micro as well.

A new set of OSWORD calls are provided with the card to allow blocks of extra RAM to be written to and read from directly.

We hope to review the Eureka card in a future issue (we also hoped to include a photograph, but being so new Watford were unable to supply one). In the meantime further information and price may be obtained from: **Watford Electronics, Dept. EE, 250 High Street, Watford WD1 2AN.**

## Infra Red Beam Alarm

One or two items could cause purchasing problems for constructors of the *Infra Red Beam Alarm* project.

The lenses for focusing the infra red beam are stocked by Maplin. The l.e.d. type TIL38 and the detector diode TIL100 are currently listed by **Greenweld, TK Electronic, Maplin and Cricklewood Electronics.** The VMOS power f.e.t. transistor type VN10KM, called for in the transmitter, is stocked by Maplin and Cricklewood.

The relay used in this project is a low voltage, DIL package, "Reed" relay, with an internal diode connected across the coil. Other types of relay may be used provided they are able to operate down to about 4V and have a coil resistance of 500 ohms.

However, the layout of the printed circuit may have to be altered to accommodate other relays and a diode will have to be "hard wired" across the coil contacts. In case of difficulty in locating a suitable relay, the one used in the prototype was purchased from Maplin: code FX88V.

The printed circuit boards for this project may be purchased through our PCB Service: code EE536 and EE537.

## Freezer Failure Alarm

The MOS/FET operational amplifier and the warning device used in the *Freezer Failure Alarm* should be stocked by most of our advertisers.

The printed circuit board may be purchased from our PCB Service: code EE534.

## Car Timer

The "spade" connectors for the *Car Timer* project should be available from any good motorists' accessories shop.

The 4060 ripple-counter, with internal oscillator and the 4011 dual-input NAND gate devices are now fairly common and should not cause buying problems.

The printed circuit board may be purchased from our PCB Service: code EE538.

## Simple Printer Buffer

Ready programmed EPROMs (£8.50) and a double-sided printed circuit board (£9.75) for the *Simple Printer Buffer* are available from **Tayside Microsystems, Dept. EE, 55 Causewayend, Coupar Angus, Perthshire, Scotland, PH13 9DX.**

Most of the semiconductors and micro-processor crystal are also stocked by **Maplin, CMC Components and Cricklewood Electronics.** They can also supply the Centronics plug and socket.

## Spectrum Joystick

Looking through our collection of components catalogues, we cannot foresee any problems with locating a 6-pin optoisolator for the *Spectrum Joystick*—this months *On Spec* project. The D-connector and 6-way flexible cable should now be available from most of our advertisers.

The quoted price for this project is based on the RS "microswitch joystick mechanism". Of course, this sum may be reduced by obtaining this part from a local computer shop or you can make one up from separate microswitches.

## Exploring Electronics

A suitable "test bed" for the *Exploring Electronics* experiments would be the circuit block used in our *Teach In '86* series.

## Scratch Blanker

The delay line chip type TDA 1022 called for in the *Scratch Blanker* project should be available from most component suppliers, such as: **C.P.L. Electronics, Marco, TK Electronics, Greenweld and Cirkitt.**

The CMOS switch 4066BE is currently listed by **Maplin, Magenta and Cricklewood.** When specifying the 555 timer for IC9, be sure to order the low power, suffix L, or the CMOS ICM7555 device.

The printed circuit board may be ordered through the EE PCB Service: code EE539.

**★ BAKER ★**

**GROUP P.A. DISCO AMPLIFIERS post £2**

150 watt Output, 4 input. All purpose illustrated.....£99  
 150 watt Output, Slave 500 mv. Input 4-8-16 ohm. Outputs £80  
 150+150 watt Stereo, 300 watt Mono Slave 500 mv. Inputs £45  
 150 watt P.A. Vocal, 8 inputs. High/Low Mixer Echo Socket £149  
 60 watt Mobile 240v AC and 12v DC 4-8-16 ohm+100v line £89  
**MIKES Dual Imp £20, Floor Stand £13, Boom Stand £22, PPE2.**

Reverb Unit for Microphone or Musical Instruments £35 PP £1.  
 Electronic Echo Machine for mic/etc. E85, Deluxe £95 PP £1.  
 30 WATT COMBI 12ins Speaker Trins Bass, Treble Boost, Switch, Black Vinyl Finish, Carrying Handle £95 PP £5.  
**AMPLIFIER 20+20 watts suitable for small PA mike guitar or 40 watts mono. Wooden case. £65 PP £5.**

**DISCO CONSOLE** Twin Decks, mixer pre amp £145. Carr £10.  
 Ditto Powered 120 watt £195, or Complete Disco 120 watts £299. 300 watt £410. Carr £30.

**DISCO MIXER.** 240V, 4 stereo channels, 2 magnetic, 2 ceramic/tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, panel or desk mounting, matt black facia. **Tape output facility £59. Post £1.**

**DELUXE STEREO DISCO MIXER/EQUALISER** as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. **£129 PP £2**  
 As above but 3 deck inputs, 4 line/aux inputs, 2 mc inputs, 2 headphone monitors £145.

**DELUXE MIXER DESK.** 8 Channels, built in echo £250 PP £4.—  
 Phone, Microphone, Line, VU Meters, Stereo/Mono, Treble Bass & Slider Volume Controls.

**FAMOUS LOUDSPEAKERS—SPECIAL PRICES**

SIZE	POWER	OHMS	BLAZER	PHYSICAL SIZE IS NOMINAL	BLAZER FRAME DIMENSIONS	PRICE	POST
4 1/2 in	10	8	Audax	Hi Fi	10 1/2 x 10 1/2	£1	£1
5 in	10	8 or 16	Far East	Car Radio	10 1/2 x 10 1/2	£6	£1
5 1/2 in	80	8	Sound Lab	Hi Fi Twin Cone Full Range	10 1/2 x 10 1/2	£10	£1
5 1/2 in	25	8	Audax	Bestraeme Cone Woofer	10 1/2 x 10 1/2	£10.50	£1
6 1/2 in	25	4	Audax	Hi Fi Twin Cone Full Range	10 1/2 x 10 1/2	£7.50	£1
6 1/2 in	15	8 or 16	EMI	Woofer, Hi Fi	10 1/2 x 10 1/2	£7.50	£1
6 1/2 in	35	8	Audax	Bestraeme Cone Woofer	10 1/2 x 10 1/2	£17.50	£1
6 1/2 in	30	8	Goodmans	Twin Cone Hi Fi	10 1/2 x 10 1/2	£12	£2
6 in	20	8	Far East	Twin Cone, Hi Fi, Full Range	10 1/2 x 10 1/2	£5.95	£1
6 in	40	8	Audax	Hi Fi Woofer Bestraeme Cone	10 1/2 x 10 1/2	£18.50	£2
6 in	80	8	Sound Lab	Hi Fi Twin Cone Full Range	10 1/2 x 10 1/2	£14	£2
6 in	80	8	Goodmans	PA Hi Fi Woofer	10 1/2 x 10 1/2	£88	£3
6 in	60	8	Goodmans	Guitar PA Woofer	10 1/2 x 10 1/2	£16	£2
6 in	60	8	Goodmans	Disco-Guitar-PA	10 1/2 x 10 1/2	£18	£2
10 in	30	4 or 8	Far East	Bass Woofer, Hi Fi	10 1/2 x 10 1/2	£14	£2
10 in	15	8	SEAS	Hi Fi Woofer	10 1/2 x 10 1/2	£21	£2
10 in	15	8	Rigenda	General Purpose	10 1/2 x 10 1/2	£5	£1
10 in	50	8 or 16	Baker	Disco-Guitar-PA	10 1/2 x 10 1/2	£20	£2
10 in	80	8	Sound Lab	Twin Cone Full Range	10 1/2 x 10 1/2	£19.50	£2
10 in	30	8	WEH	Woofer Guitar PA	10 1/2 x 10 1/2	£42	£2
12 in	30	4 or 8 or 16	Baker	Twin Cone Full Range	10 1/2 x 10 1/2	£18	£2
12 in	45	4 or 8 or 16	Baker	Disco-Guitar-PA	10 1/2 x 10 1/2	£18	£2
12 in	80	8	Baker	Bass Woofer	10 1/2 x 10 1/2	£25	£2
12 in	80	8 or 16	Baker	Disco-Guitar-PA	10 1/2 x 10 1/2	£22	£2
12 in	120	8 or 16	Goodmans	Disco-Guitar-PA	10 1/2 x 10 1/2	£98	£2
12 in	100	8	H + H	PA	10 1/2 x 10 1/2	£39	£2
12 in	120	8 or 16	Baker	Disco-Guitar-PA	10 1/2 x 10 1/2	£42	£2
12 in	200	8	H + H	PA	10 1/2 x 10 1/2	£88	£3
12 in	300	8	WEH	Woofer	10 1/2 x 10 1/2	£49	£3
13x8	10	3	EMI (450)	Hi Fi with Tweeter	10 1/2 x 10 1/2	£5	£1
15 in	100	8 or 16	Baker	Disco-Guitar-PA	10 1/2 x 10 1/2	£39	£3
15 in	250	8 or 16 or 18	H + H	Hi Fi	10 1/2 x 10 1/2	£49.50	£1
15 in	250	8	Goodmans	Disco + Group	10 1/2 x 10 1/2	£74	£3
18 in	230	8	Goodmans	Disco + Group	10 1/2 x 10 1/2	£87	£4

**MID RANGE. POWER RATINGS ARE WITH CROSSOVER**

4 1/2 in	100	8	Seas	Hi Fi Cone	£14.50	£1
4 1/2 in	80	8	Alca	Hi Fi Dome	£12.50	£1
5 in	20	8	EMI	Hi Fi Cone	£4.50	£1
5 in	50	8	Far East	Hi Fi Cone	£10	£1
10 in	100	8	Baker	Hi-Fi-Disco-PA	£26	£2

P.A. CABINETS (empty) Single 12 £38; Double 12 £44. carr £10  
 WITH SPEAKERS 45W £56; 75W £60; 90W £80; 150W £88.  
**200 WATT COMPACT SYSTEM £115, 400 watt £165. carr £10.**  
**300 WATT MID-N-TOP SYSTEM Complete £125 carr £10**  
**TWEETER HORNBOSS 200 watt £32. PP £2.**  
**WATERPROOF HORN SPEAKERS 8 ohms. 25 watt £22. 30 watt £25. 40 watt £33. 20W plus 100 volt line £30. Post £2.**  
**MOTOROLA PIEZO ELECTRONIC HORN TWEETER, 3/4 in. square. £6 100 watts. No crossover required 4-8-16 ohm, 7 1/2 x 3 1/2 in £10**  
**METAL SPEAKER GRILLES 8 in £3, 10 in £3.50, 12 in £4.50, 15 in £6.50, 18 in £7.50. PP 65p each.**

**R.C.S. DISCO LIGHTING EQUIPMENT**  
**READY BUILT DELUXE 4 CHANNEL 4,000 WATT sound chaser + speed +4 programs £89. Deluxe Model £89 PP £2.**  
**PARTY LIGHT 4 coloured Flood Lamps Flashing to Music. Self-contained Sound to Light 410 x 196 x 115mm £34.95 PP £2.**

**FULL STOCK OF COMPONENTS, PLUGS, LEADS, ETC.**  
**MAINS TRANSFORMERS** Price Post  
 250-0-250V 50mA, 6.3V 3-5A, 6.3V 1A £1.00  
 350-0-350V 250mA, 6.3V 6A CT, £14. Shrouded £18.00  
 220V 25mA, 6V 1 Amp £3.00 220V 45mA, 6V 2 Amp £4.00  
**LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid**  
 9V, 3A; 12A; 16V, 2A; 20V, 1A; 30V, 1 1/2A; 30V, 5A + 7-0-7V, 2A; 30V, 6 x 4in; 55p; 12 x 8in; 12V, 2A; 12V, 2A; 20V, 1A; 20V, 2A.  
**LOW VOLTAGE TAPPED OUTPUTS AVAILABLE**  
 1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 volts £8.00 £2  
 Ditto 2 amp £10.50 3 amp £12.50 5 amp £18.00 £2  
 31-26-0-26-31 Volt 6 amp £14.00 £2

**MINI-MULTI TESTER £8.50 post 50p**  
 Pocket size instrument. AC/DC volts, 15-150-500-1000. DC current 0-150mA. Resistance 0-100K 1000 ohm v.v. De-Luxe Range Doubler Meter, 50,000 ohm v.v. 7 x 5 x 2in. Resistance 0/20 meg in 5 ranges. Current 50mA to 10A. Volts 0-25/1000v DC, 10v/1000v AC. £25.00 PP £1

**PANEL METERS 50mA, 100mA, 500mA, 1mA, 5mA, 100mA, 500mA, 1amp, 2 amp, 5 amp, 25 volt. VU 2 1/2 x 2 1/2 in. £5.50 post 50p**

**PROJECT CASES, Black Vinyl Covered Steel Top, All Base**  
 4 x 2 1/2 x 2 in. £3.00; 6 x 4 x 1 in. £4.00; 8 x 5 x 2 in. £4.50; 11 x 6 x 3 in. £6.00; 1 1/2 x 6 x 1 in. £10.00; 15 x 8 x 4 in. £13.50.  
**ALUMINIUM PANELS 18 s.w.g. 12 x 12 in. £2.00; 14 x 9 in. £2.00; 6 x 4 in. 65p; 12 x 8 in. £1.00; 12 x 12 in. £1.00; 16 x 9 in. £1.00; 14 x 3 in. 85p; 12 x 3 in. £1.00; 16 x 10 in. £2.35; 16 x 6 in. £1.50.**  
**ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK.**  
 4 x 2 1/2 x 2 in. £1.35; 3 x 2 x 1 in. 35p; 6 x 4 x 2 in. £2.00; 8 x 6 x 3 in. £3.40; 12 x 5 x 3 in. £4.00; 6 x 4 x 3 in. £2.50; 10 x 7 x 3 in. £3.40

**HIGH VOLTAGE ELECTROLYTICS**  
 20/500V.....75p 220/400V.....£2 32+32/500V.....£2  
 32+350V.....£2.95 18+18/450V.....£2 32+32/350V.....85p  
 47/350V.....75p 20+20/350V.....75p 80+40+20/350V.....95p

**RECORD PLAYER DECKS. P&P £2.**  
 Make Drive Model Cartridge Price  
 BSR Single Belt 240V Magnetic £30  
 BSR Single Rim 240V Ceramic £22  
 AUTO-CHANGER BSR Ceramic £7n. £18  
 Many others in stock. Phone for details.  
**DECCA TEAK VENEERED PLINTH space for small amplifier. Board cut for Garrard 18 in. x 14 in. x 4 in. £5. Post £2**

**RADIO COMPONENT SPECIALISTS**

**337 WHITEHORSE ROAD, CROYDON**  
**SURREY, U.K. Tel: 01-684 1665**  
 Post 65p Minimum. Callers Welcome.  
 7 days delivery Closed Wednesday Full Lists large s.a.e.

# ...Beeb...Beeb...Beeb...Bee

... auto-ranging resistance ... capacitance meter ...

ITEMS of test equipment that would once have been technically difficult and horrendously expensive to produce are now available at prices which are not beyond the means of dedicated electronics enthusiasts. This includes such things as digital multimeters, dual trace oscilloscopes, and auto-ranging capacitance meters. With a computer having the versatile interfacing capabilities of the BBC machines it is possible to produce sophisticated test gear with the aid of very inexpensive add-ons which make conventional budget priced equipment look positively expensive. The two simple add-ons described in this month's article demonstrate this point very well. Both use only a handful of inexpensive components, and one converts the Beeb into an auto-ranging resistance meter while the other converts it to an auto-ranging capacitance meter. In the previous article we consider ways of using the user port to enhance the capabilities of the analogue port, and these two add-ons both exploit this idea.

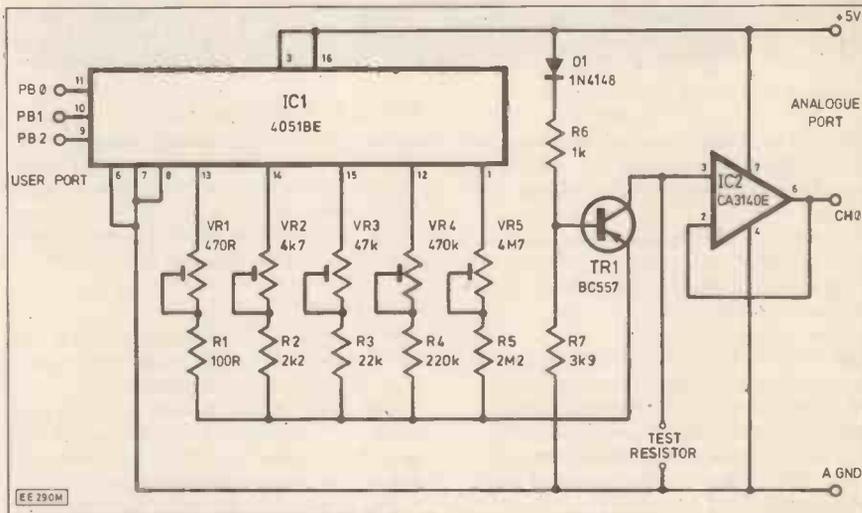


Fig. 2. Circuit diagram for the auto-ranging resistance meter.

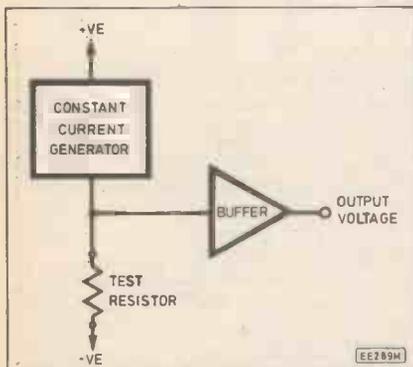


Fig. 1. Arrangement used for Resistance to Voltage conversion.

## R to V Conversion

The analogue port does, of course, measure voltage, and in order to measure any other commodity using the analogue inputs it must first be converted to a proportional voltage. Resistance is something that is quite easily converted to a proportional voltage, and there is actually more than one way of tackling the problem. The most commonly used approach, and the one which is probably best suited to our current requirements, is the simple set-up shown in Fig. 1.

A constant current is fed to the test resistor, and this produces a voltage across the resistor. Ohm's Law states that "voltage = current x resistance", and with the current at a fixed value the output voltage becomes proportional to the test resistance. For example, if you assume a current flow of one milliamp and work out the voltage produced with test resistance of 1k, 2k, 3k, etc., you will find that the answers are one

```

10 REM AUTO-RANGING
20 REM RESISTANCE METER
30 REM J.W.P. 6/86
40
50 ?&FE62=7
60 MODE 7
65 PROCSCREEN
70 REPEAT
80 PROC RANGE
90 PROC SHOW
95 FOR X=1 TO 1000:NEXT
100 UNTIL FALSE
110 END
1000 DEF PROC RANGE
1010 V%=-1
1020 REPEAT
1030 V%=V%+1
1040 ?&FE60=V%
1045 FOR X=1 TO 500:NEXT
1050 UNTIL ADVAL1 DIV 64<1023 OR V%>4
1060 ENDPROC
1070
2000 DEF PROC SCREEN
2010 PRINTTAB(5,5);CHR*(141);"RANGE"
2020 PRINTTAB(5,6);CHR*(141);"RANGE"
2030 PRINTTAB(11,12);CHR*(141)
2040 PRINTTAB(11,13);CHR*(141)
2050 ENDPROC
2060
3000 DEF PROC SHOW
3005 V%=STR*(V%+1);IF V%>4 THEN V%=""
3010 PRINTTAB(13,5);V%
3020 PRINTTAB(13,6);V%
3030 DISP*=FNREADING
3040 PRINTTAB(13,12);DISP*
3050 PRINTTAB(13,13);DISP*
3060 IF V%=0 THEN PRINTTAB(5,20)"Reading in OHMS. "
3070 IF V%=1 OR V%=2 OR V%=3 THEN PRINTTAB(5,20)"Reading in KILOHMS. "
3080 IF V%=4 THEN PRINTTAB(5,20)"Reading in MEGOHMS. "
3090 ENDPROC
3100
4000 DEF FNREADING
4005 IF V%>4 THEN R%="OVERLOAD":=R%
4010 R%=ADVAL1 DIV 64
4020 IF V%=0 OR V%=3 THEN D=1
4030 IF V%=1 OR V%=4 THEN D=100
4040 IF V%=2 THEN D=10
4050 R%=STR*(R/D)
4060 P=INSTR(R%,".")
4065 IF P=0 THEN P=LEN(R%)
4070 R%=LEFT*(R%,P+LOG(D))
4080 IF LEN(R%)<8 THEN R%=STRING$(8-LEN(R%),"")+R%
4090 =R%

```

## Listing 1: RESISTANCE METER

volt, two volts, three volts, etc. It is important that any device measuring the output voltage has a very high input resistance, as this resistance is in parallel with the test component and will impair the accuracy of the system if it has a significant shunting effect on the test resistance. The output voltage is therefore taken via a buffer stage having an ultra high input impedance.

In theory this arrangement has an infinite operating range, but in practice several measuring ranges have to be included in order to cover a wide resistance range with good accuracy. With (say) just one range going from 0 to 10 megohms, most resistors would give an insignificant output voltage which could not be measured accurately, especially when using a digital voltage measuring circuit with a strict limitation on its resolution. Several ranges can be covered simply by having a number of different current levels available. For instance, a tenfold increase in the test current reduces the full scale resistance value by a factor of ten—reducing the test current by a factor of ten increases the full scale resistance by the same factor.

### Resistance Meter Circuit

Fig. 2 shows the circuit diagram for a very simple but effective resistance meter add-on for the BBC machine, and with appropriate software this is capable of auto-ranging.

Transistor TR1 is at the heart of the system, and this is connected as a conventional constant current generator. The output current is controlled by the resistance

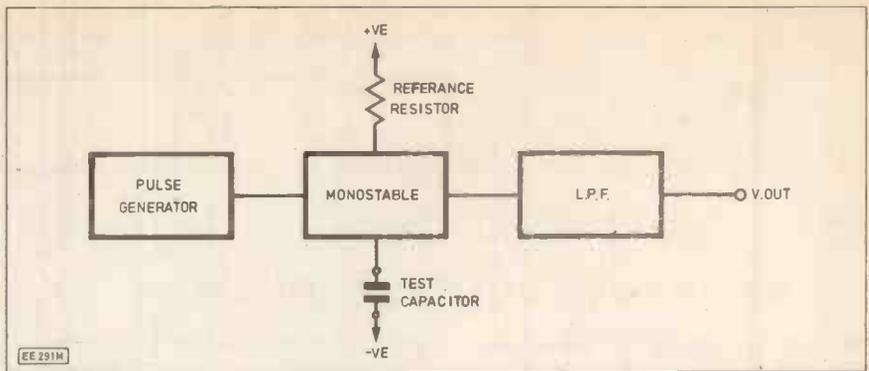


Fig. 3. A simple capacitance to voltage converter set-up.

between TR1's emitter and the positive supply rail. In this case there are five switched resistors giving the circuit five measuring ranges with full scale values of 1-023k, 10-23k, 102-3k, 1-023M, and 10-23M. This covers all the resistor values commonly used in electronics.

Each emitter resistance actually consists of a fixed resistor and a preset type wired in series. The preset resistors are adjusted to give good accuracy on each measuring range. Selection of the emitter resistance could be made by way of manual switching, but in order to achieve auto-ranging it is obviously necessary for range selection to be under the control of the computer. In this case the switching is provided by three lines of the user port and a 4051BE CMOS eight way analogue switch (ways "5" to "7" being

left unused). IC1 has a significant resistance of about 200 ohms through whichever switch is activated, and this resistance forms a large part of the emitter resistance on the lowest range. This is unfortunate as it does not aid good accuracy and stability on this range, but in practice results seem to be perfectly adequate in both respects.

IC2 is the output buffer stage, and this is a MOS input device which provides an input impedance of over a million megohms. It therefore ensures good linearity even on the 10-23 megohms range. On the face of it the buffer stage is unnecessary as the analogue inputs of the BBC computer have an extremely high input resistance anyway. Despite this it is often better to include a buffer in add-ons added to the analogue port so that signals in the connecting lead to the computer are at a low impedance and not a high impedance of several megohms. This avoids problems with excessive noise pick-up in the connecting cable.

### Software

Suitable software for the resistance meter add-on is given in Listing 1, and this supports auto-ranging. This facility operates in essentially the same manner as the auto-ranging voltmeter circuits described in the previous article, and a description of the process will not be repeated here. In order to calibrate the unit five test resistors are required, and these should be one per cent types having values which correspond to roughly half the full scale value of each range (e.g. 470, 4k7, 47k, 470k, and 4M7). Start with the preset resistors at about half resistance, then connect each resistor in turn and adjust the appropriate preset for the correct reading. The display indicates the range in use, and VR1 to VR5 operate on ranges 1 to 5 respectively.

### Capacitance Measurement

There are several ways of providing capacitance to voltage conversion, but these are mostly variations on the basic method of using a C-R timing network with the test capacitor as the capacitive element in this network. Fig. 3 shows the most simple type of converter, and this is the type which is used in this capacitance meter add-on.

The pulse generator produces a constant stream of pulses which are used to continuously trigger the monostable multivibrator. Each time it is triggered the latter provides an output pulse having a duration that is determined by the C-R timing network, and which is proportional to the value of the capacitor. With a small test capacitance the output from the monostable is a series of brief pulses, giving a low average output voltage. A high test capacitance gives a long

## Listing 2: CAPACITANCE METER

```

10REM AUTO-RANGING
20 REM CAPACITANCE METER
30REM J.W.P. 6/86
40
50?&FE62=7
60MODE 7
65 PROCSCREEN
70REPEAT
80PROCORANGE
90PROCSHOW
100UNTIL FALSE
110END
1000DEF PROCORANGE
1010 V%=-1
1020REPEAT
1030V%=V%+1
1040?&FE60=V%
1045 FOR X = 10 TO 2000:NEXT
1050UNTIL ADVAL1 DIV 64<1023 OR V%>4
1060ENDPROC
1070
2000DEF PROCSCREEN
2010PRINTTAB(5,5);CHR$(141);"RANGE"
2020PRINTTAB(5,6);CHR$(141);"RANGE"
2030PRINTTAB(11,12);CHR$(141)
2040PRINTTAB(11,13);CHR$(141)
2050ENDPROC
2060
3000DEF PROCSHOW
3005V%=STR$(V%+1):IF V%>4 THEN V%=""
3010PRINTTAB(13,5);V%
3020PRINTTAB(13,6);V%
3030DISP$=FNREADING
3040PRINTTAB(13,12);DISP$
3050PRINTTAB(13,13);DISP$
3060IF V%=0 THEN PRINTTAB(5,20)"Reading in PICO FARADS"
3070IF V%=1 OR V%=2 OR V%=3 THEN PRINTTAB(5,20)"Reading in NANOFARADS."
3080IF V%=4 THEN PRINTTAB(5,20)"Reading in MICROFARADS"
3090ENDPROC
3100
4000DEF FNREADING
4005IF V%>4 THEN R$="OVERLOAD":=R$
4010R=ADVAL1 DIV 64
4020IF V%=0 OR V%=3 THEN D=1
4030IF V%=1 OR V%=4 THEN D=100
4040IF V%=2 THEN D=10
4050R$=STR$(R/D)
4060P=INSTR(R$,".")
4065IF P=0 THEN P=LEN(R$)
4070R$=LEFT$(R$,P+LOG(D))
4080IF LEN(R$)<8 THEN R$=STRING$(8-LEN(R$),"")+R$
4090=R$

```

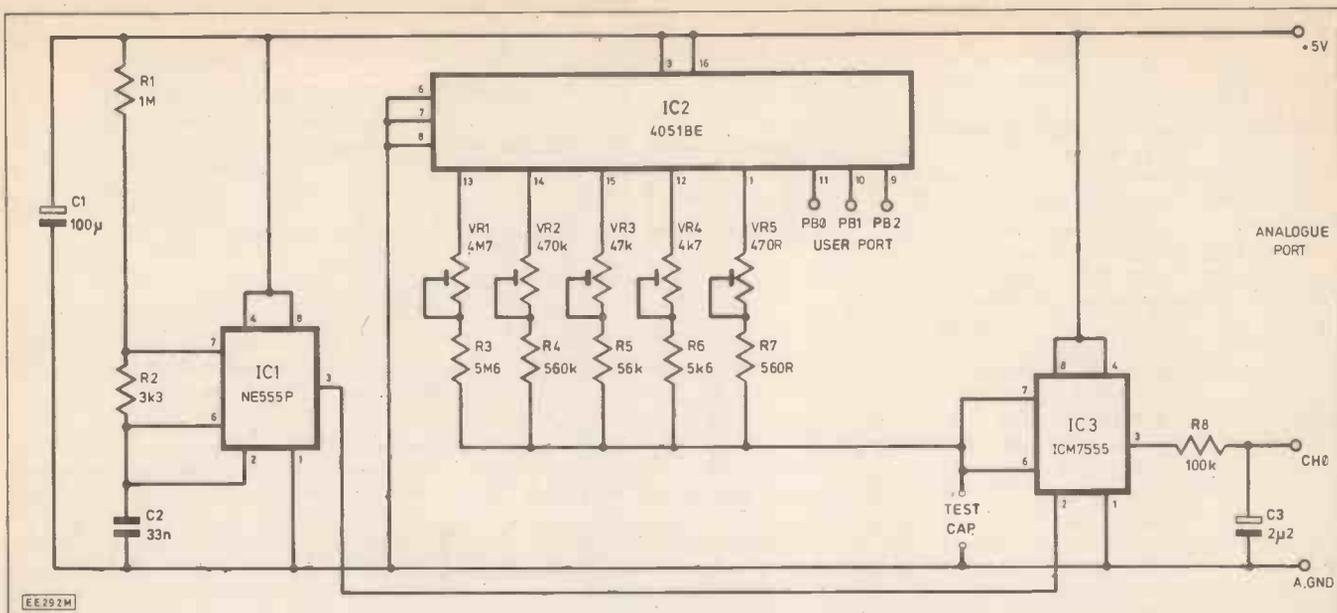


Fig. 4. Circuit diagram for the auto-ranging capacitance meter.

output pulse and a high average output voltage. In fact the average output voltage is proportional to the value of the component under test provided the value is not so high that new trigger pulses are received before each output pulse has finished (which would give a simple frequency divider action and a low output voltage).

Although the average output from the monostable is proportional to the test capacitance, the signal here is a series of pulses which the analogue converter in the BBC machine will read as zero, something beyond full scale value, or somewhere between these two extremes if a pulse starts or finishes during a conversion. This problem is easily overcome, though, and all that is required is a lowpass filter at the output of the monostable to integrate the pulses and provide a reasonably ripple free d.c. output signal.

### Circuit Operation

The full circuit diagram of the capacitance meter add-on is shown in Fig. 4. IC1 operates as the pulse generator, and this is a standard 555 astable circuit. The values of R1 and R2 have been arranged so that the output signal is a series of narrow negative pulses, which is the type of signal required for the correct triggering of the monostable. The monostable is based on IC3 which is another 555 device, but this time the low power CMOS (7555) version is specified. This is not a matter of reducing the current consumption, and the advantage of the 7555 in this case is its lower self capacitance. This gives improved accuracy with low value capacitors, but the self capacitance is still sufficient to boost very low readings and give poor accuracy. Values of a few tens of picofarads or less are little used,

and so this is not a major drawback, but to some extent it can be counteracted by deducting the self capacitance from readings on range one. The amount by which readings should be offset is the capacitance reading obtained on range one with no test capacitor connected.

Range switching is again accomplished by a 4051BE controlled by three user port lines. The five ranges have full scale values of 1.023nF, 10.23nF, 102.3nF, 1.023µF, and 10.23µF.

### Software

The program for use with the capacitance meter add-on is given in Listing 2, and this is just a slightly revamped version of the resistance meter program. Again, for calibration purposes close tolerance components having values roughly equal to half the full scale value of each range are required (e.g. 470pF, 4n7, 47nF, 470nF, and 4µ7). A compromise may have to be accepted on the highest range as a suitable calibration component might be difficult to obtain. As before, it is just a matter of connecting each calibration component and then adjusting the appropriate preset for the correct reading.

The circuits shown here and in the previous article should give some idea of the versatility available by using the analogue and user ports together. Those who like experimenting might like to try combining the circuits to produce an auto-ranging multimeter, and the basic techniques used in these designs can be applied to other measurement applications. Where possible electronic switching should be used as it offers high speed, low cost, and low power consumption. Its disadvantages are a lack of isolation between the control signal and the signal being switched, and what is likely to be of more relevance in this context, around 200 ohms resistance through each switch. Reed relays offer a better alternative where isolation and (or) low "on" resistance is needed.

*If you have any comments or ideas for inclusion in the Beeb Micro pages, please send them to: Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH.*

# TELEVISION/COMPUTER FULL-TIME TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN  
EDUCATION COUNCIL)

2 YEAR

**BTEC National Diploma (OND)**

**ELECTRONIC &**

**COMMUNICATIONS ENGINEERING**

(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

15 MONTHS

**BTEC National Certificate (ONC)**

**ELECTRONIC EQUIPMENT SERVICING**

(Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

15 MONTHS

**BTEC National Certificate (ONC)**

**COMPUTING TECHNOLOGY**

(Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

9 MONTHS

**BTEC Higher National Certificate (HNC)  
COMPUTING TECHNOLOGY & ROBOTICS**

(Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED  
PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

SHORTENED COURSES OF FROM 3 TO 6 MONTHS CAN BE ARRANGED FOR  
APPLICANTS WITH PREVIOUS ELECTRONICS KNOWLEDGE

NEXT SESSION TO COMMENCE  
ON SEPTEMBER 15th

H.N.C. SEPTEMBER 1986

FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE (Dept EE)**  
20 PENYVERN ROAD, EARLS COURT,  
LONDON SW5 9SU. Tel: 01-373 8721.

**TRAIN  
TODAY FOR  
A BETTER  
FUTURE**

Train for a new, more rewarding career with an ICS Home Study Course. Enjoy expert tuition in the comfort of your own home and study at the pace that suits you. ICS has over 90 years experience in home study courses and is the largest correspondence school in the world. Over the years we've helped nearly 9 million people to improve their job prospects.

Easy payment plans are available on all courses or you can pay by Access or Visa. Find out how we can help you. Simply post or phone today for your **FREE INFORMATION PACK** on the course of your choice. No obligation.

## WE'VE HELPED THEM

"My outlook has broadened tremendously as a result of this course and I am grateful for the inspiration it has given me."

Mr. L.N.S. (Leicester)

"Many, many thanks for your excellent courses. I cannot praise the tuition enough."

Ms. J.N. (Birmingham)

## NOW FIND OUT HOW WE CAN HELP YOU...

- GCE — Over 40 'O' & 'A' level subjects
- Book-keeping and Accountancy
- Electronics
- Police Entrance Examinations
- Interior Design
- Good English
- Car Mechanics
- Short Story Writing & Journalism
- Astronomy
- Radio, Audio & TV Servicing
- Computer Programming
- Hotel & Catering Management
- Catering & Gourmet Cooking
- Complete Gardening
- Carpentry & Joinery
- Running Your Own Business
- Royal Horticultural Society Exam
- Electrical Engineering
- Flower Arranging
- Electrical Contracting/Installations



**ICS**

Course of Interest

Name: \_\_\_\_\_

Address: \_\_\_\_\_

P. Code \_\_\_\_\_

International Correspondence Schools, Dept ECS96,  
312/314 High St., Sutton, Surrey SM1 1PR.  
Tel: 01-643 9568 or 041-221 2926 (both 24 hrs).



# JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.

**EC50 Mains Electronic Iron. £31.64**




proportional electronic temperature control inside the handle. Adjustable 280° to 400°C. Burn-proof 3-wire mains lead. Fitted 3.2mm Long-Life bit. 1.6, 2.4 and 4.7mm available. 240v a.c.

Features spike-free, solid state

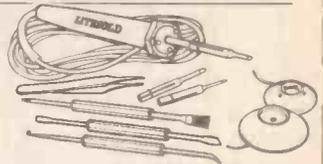**SK18 Soldering Kit. £16.36**

Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid. In PVC presentation wallet.



**ADAMIN Miniature Iron £7.08**




Possibly smallest mains iron in the world. Ideal for fine work. Slim

nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.

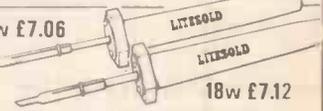**'L' Series Lightweight Irons. 12w £7.06**

High efficiency irons for all electronic hobby work. Non-roll handles with finger guards.

Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12



model, 12w, 2.4mm bit. LC 18 Model, 18w, 3.2mm bit. 240v Std - 12v available. Presentation wallet.

**Soldering Iron**

Stands 3&4

£5.66

No.5

£5.88



Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits. No 5 stand for EC50 iron No 4 stand for ADAMIN miniature Iron No 3 stand for LA12 and LC18 irons.

**Replacement Bits**

For all above irons. Non-stick designs, machined from special copper alloy, with Inconel retaining rings. Two types - Chromium plated with copper face (for economy and ease of use) and Iron plated with

Pre-tinned face (Long Life). State tip size, iron and type.

	Copper	UL
EC50	—	£1.64
Adamin 12 and	91p	£1.62
LA12	—	£1.01
LC18	—	£1.79

**BRADEWICK De-Solder Braid.**



£1.04 per Reel

For simple, safe and effective de-soldering of all types of joint, using a standard soldering iron. Handy colour-coded packs of 1.5 metres in 3 widths: Yellow - 1.5mm, Green - 2mm, Blue - 3mm.

**De-Solder Pumps £6.26**

High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy



thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

**Tool Sets**



Top quality Japanese metric hardened and tempered tools. Swivel-top chrome plated brass handles.

Fitted plastic cases. 113 set - 6 miniature screwdrivers 0.9 to 3.5mm £3.71

227 set 5 socket spanners 3 to 5mm £2.82

305 set 2 crosspoint and 3 hex wrenches

1.5 to 2.5mm £2.70

228 set 20 piece combination:


5 open, 5 skt spanners, 2 crosspoint, 3 hex

and 3 plain drivers, scribe, handle/holder £6.10

**Microcutters. £4.82** Light weight hardened and precision ground. Flush cutting. Screw joint, return spring, cushion-grip handles. Safety wire-retaining clip.



**Soldering Aids.**

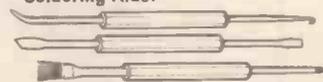

**Set of 3 £4.22**

Scraper/Knife, Hook/Probe, Brush/Fork. 3 useful double-ended aids to soldering/desoldering/assembly. In plastic wallet.



**ADAMIN Electric Stylus. £16.24**

Writes like a ballpoint in Gold, Silver, Copper or 6 colours, on card, plastics, leather etc. Personalise wallets, bags, albums, books,

models... Operates at 4.5v from its own plug-

transformer - totally safe. Supplied with coloured foils.



**SEND FOR OUR ORDER FORM TODAY  
AND JOIN UP WITH THE PROFESSIONALS**

Prices include p&p and VAT. Send order with Cheque/PO. Ring for Access/Visa sales, or ask for order forms.

**LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. EE,  
97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 01 689 0574**

# DOWN TO EARTH

BY GEORGE HYLTON

## METER SHUNT CALCULATOR

THE alignment chart, shown in Table 1, enables you to adapt a current meter to a higher current range. To do so, a resistance "shunt" must be connected across the meter terminals. By selecting the appropriate shunt resistance the current range can be multiplied by any desired factor.

To use the chart all you need to know is the internal resistance of the meter (usually marked on the dial) and the multiplication (M), see Fig. 1. A straight edge or thread stretched across the chart then gives the required shunt resistance.

**EXAMPLE:** A 0-10mA meter is required to read 0-30mA. This means that the multiplication factor is 3. If the meter resistance ( $R_m$ ) is 20Ω, what shunt resistance ( $R_s$ ) is needed?

As shown dotted on the chart, when  $M = 3$  is joined to  $R_m = 20$  the line cuts the  $R_s$  scale at 10Ω and this is the required value of shunt.


This kind of chart cannot be read reliably when the multiplication needed is large. For multiplications of more than 11 (where this chart runs out), calculate  $R_s$  from the formula:

$$R_s = R_m / (M - 1)$$

**EXAMPLE:** A 100μA meter with a resistance of 1k is to be adapted to read 100mA. In this case  $M = 1000$  and  $R_s = 1000/999 = 1.001\Omega$ .

In practice a 1Ω resistor could be used. Its tolerance should be as close as possible, preferably 1 per cent or better.

Fig. 1.

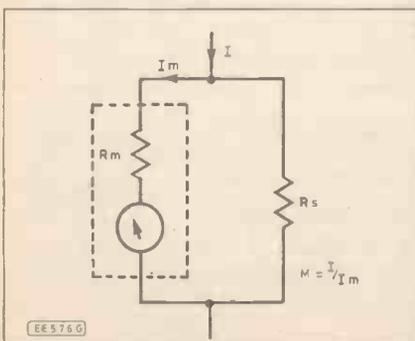

## MEASURING METER RESISTANCE

When  $R_m$  is not marked on the meter it can be measured. Ohmmeter measurement is not accurate enough (unless you have a digital meter) and may pass a damaging amount of current through the meter.

Some current meters are designed to drop a standard voltage (such as 100mV) when passing full-scale current. If this voltage is known, the resistance can be calculated. For a 100mV full-scale drop, a 1mA meter has a resistance of 100Ω; a 100μA meter 1k; a 10mA meter 10Ω; and so on. However, meter resistances vary, so if there is no dial indication of either the resistance or the full-scale voltage drop a measurement is needed.

The method shown in Fig. 2 may not be the last word in accuracy but it calls for the minimum of standards of comparison.

**WARNING: it only works on meters with linear scales!**

With S1 open, the meter current is adjusted by VR1 to produce a deflection at or near full scale. Note the reading carefully. Close switch S1 and connect close


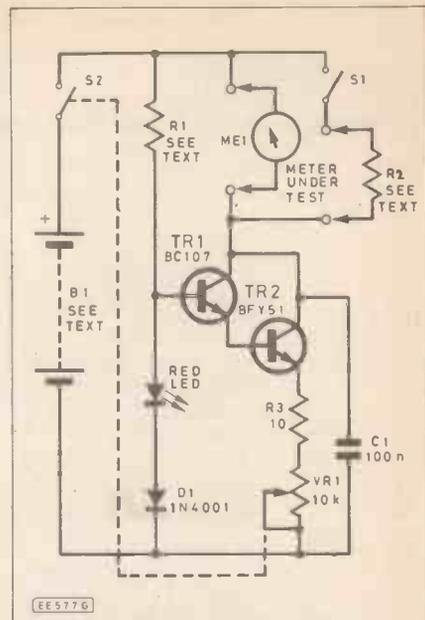


Fig. 2. Current meter resistance circuit.

Table 1:  
CURRENT METER RANGE EXTENSION CALCULATOR

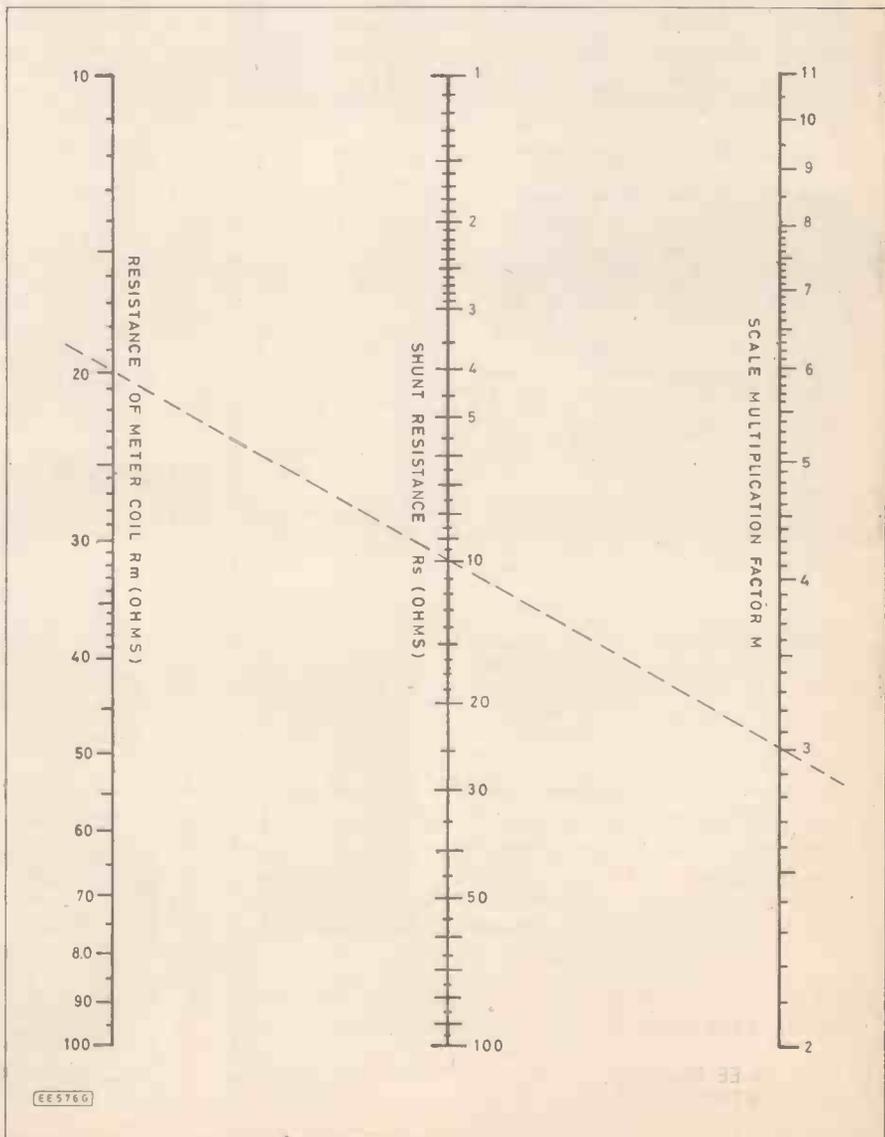

tolerance resistors R2 until you find one which reduces the reading by very roughly half. Note the new reading.

Divide the first reading by the second to give a number, M. Join this number on the M scale of the chart to the value of your R2 resistor on the central (Rs) scale. The line now cuts the Rm scale at the meter resistance.

### CIRCUIT VALUES

The meter test circuit will operate from any voltage above 3V. The only requirement is that this voltage should not change when the current changes. You can use fresh dry cells (U2 size), or a car battery, or a stabilised mains power unit.

Resistor R1 must be chosen to suit the voltage and the l.e.d. Red l.e.d.s drop about 1.6V when lit, and the silicon diode D1 drops about 0.7V. These voltages add up to about 2.3V and R1 receives the difference between 2.3V and B1.

So if B1 is 6V, the remaining 3.7V appears across R1. In this case, if the l.e.d. needs 10mA to light, R1 must be around 370Ω. (Use 330Ω or 390Ω.) For other voltages and l.e.d.s, calculate on the same lines.

The circuit will cope with meters up to about 100mA full scale. It is convenient to gang S2, the on/off switch, with potentiometer VR1. If VR1 is of the "inverse log." (reverse log.) type, meter current in-

creases with clockwise rotation. Single inverse log. potentiometers may be hard to find, but one section of a stereo balance pot is usually reverse log, or something like it.

### OSCILLATION

The purpose of capacitor C1 is to discourage h.f. oscillation, which can occur in this type of circuit, especially at high currents. If erratic results are obtained, this may indicate that the circuit is oscillating despite C1. Try a different value or put a second capacitor between base and collector of TR2.

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. EE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid "date corner"**. Ads. will not appear (or be returned) if these rules are broken.

# FREE! READERS' BUY & SELL SPOT EE MARKET PLACE

**Wanted:** replacement pick-up cartridge for Dynatron Espresso model GR5 record player. Good price paid. Rhydian Blackmore, Can-y-Lloer, Fformers, Llonwith, Dyfed, Wales. Tel: 05585 429.

**Advance** J3B signal generator sine/square wave, output 10Hz-100kHz. Includes cables and manual. Only £100. Richard Hind, 13 Cobwell Road, Retford, Notts. DN22 7BN. Tel: 0777 701040.

**DX200** Communication Receiver. Unused. £100. Aquarius computer. New. £40 o.n.o. Computer terminal keyboard. Excellent value £15. J. Howells, 118 Heritage Park, St. Mellons, Cardiff, S. Glam. Tel: 0222 797956.

**Hobbyist** has thousands spare components for disposal. New and used. Sell cheap or swap for W.H.Y. J. De-Almeida, 106, Thorney Park, Wroughton, Swindon, Wilts. SN4 0QT. Tel: 0793 812566/812291 ext. 252.

**EE (Dec.)** Digital Capacitance Meter in full working order with engraved front panel. Also pcb. Offers. Tel: 0248 722697.

**2532 EPROMS** £2 4116 50p. Rhythm Ace Electronic Drums £40. Commodore Plus 4 disk plotter—new, £250. J. Howells, 118 Heritage Park, St. Mellons, Cardiff, S. Glam. Tel: 0222 797956.

**Stepper Motors** 10V 4-phase 0.48A 7.5° per step £10 each. Harris digital data book (CMOS) £3. C. Orpin, 27 Cowleaze, Chinnor, Oxon. Tel: Kingston Blount 52405.

**Wanted:** Electronics Monthly December 1984, January 1985, February 1985 to buy or on loan. Tom Munnely, 16 Seabury Road, Malahide, Co. Dublin, Eire.

**Maplin** Frequency Counter 10Hz-500MHz. 8 digit variable time gate. Mains/battery operated. Fully calibrated £140 (o.n.o.). D. Pratt, 2 Slades Lane, Meltham, Huddersfield, W. Yorks. Tel: 0484 850327.

**Wanted:** Manual or circuit for video circuits V31A. Tube booster or anything for TV repairs. Peter Makin, 6 Fairisle Close, Clifton Estate, Nottingham. Tel: Nottingham 215460.

**Wanted:** Mullard E10-11GH CRT for Solatron scope. Also plug-in amps (CX-1270) if possible. Tel: Weybridge (0932) 44154.

**Complete** set Everyday Electronics November 1971 to May 1986. Three binders. £75. Tel: Brighton 562119.

**Transistor** tester logic probe plus many components, switches, leads etc. All unused. £25. Tel: Tunbridge Wells 29033.

**Discs:** 250 Datalife S/S D/D 80-track, used once. 50p each. 25 for £10. Minimum 10 discs. Cheque/P.O. P. Gordon, 32 Muirwood Drive, Currie, Lothian EH14 5EZ.

**200 P.W., P.E., E.E. Magazines** 1971-1977. Many complete years. All good condition. £50. Tel: 01-969 0073.

**Everyday Electronics** June 1981 to December 1985. Some missing. Individual sale. Reasonable offers considered. D. Strawn, 25 Stephens Drive, Inverkeithing, Fife KY11 1DD. Tel: 0383 417695 (after 5 p.m.).

**Wanted:** Philips 22RR522 Portable Radio-Recorder. Complete or the R/Rec. section switch p.c.b. board. Mr. R. Barlow, 55 Carolyn House, Durrington, Worthing, Sussex BN13.

**Wanted:** Any modern TV which has I.R. controls and multi-standard switching (two required if possible). Richard Shidhu, 115 Streatfield Road, Kenton, Middx. HA3 9BL. Tel: 01-204 4838.

**Newnes** Radio & Television books, servicing manuals, service sheets, magazines and books—send s.a.e. for list. Mr. F. D. Brown, 6 Ryan Close, Ferndown, Wimborne, Dorset BH22 9TP.

Please read the **RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no. Please publish the following small ad. **FREE** in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature ..... Date .....  
**COUPON VALID FOR POSTING BEFORE 19 SEPTEMBER, 1986** (One month later for overseas readers.)

**SEND TO:** EE MARKET PLACE, EVERYDAY ELECTRONICS, 6 CHURCH STREET, WIMBORNE, DORSET BH21 1JH.

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid "date corner"**

# SCRATCH BLANKER

R.A. PENFOLD

## Bring your old records back to life

THE compact disc, with its click-free reproduction, is rapidly gaining in popularity and looks likely to replace conventional discs in due course. This is cold comfort to anyone who owns a large collection of microgroove recordings, since the cost of replacing them with compact discs would be enormous and many recordings are never likely to be released on compact disc anyway. In fact compact discs are not totally immune to scratches, but except in very bad cases scratches fail to have any obvious effect on the audio output signal. This is due to error detection and correction circuits that are built into every player.

Somewhat similar techniques can be applied to ordinary discs, and so-called "click eliminators" can provide reasonable results from a badly scratched and otherwise useless record. There is a limit to the degree of improvement that can be produced using a relatively simple click eliminator circuit, and the problem is not so much eliminating the click as replacing it with something. In a simple click blanker it is replaced with a period of silence, and although the gap in the signal is too short to be heard as such, it is sufficiently long to produce an audible glitch. It is a very minor glitch when compared to the effect of a bad scratch, and in some cases it can actually be inaudible. In most cases though, it sounds like and is roughly analogous to tape drop-out.

## DESIGN

This design is for a reasonably simple and inexpensive scratch blanker which provides good results. It has to be pointed out that a blanker is inevitably much more complicated than a scratch filter circuit which simply provides top-cut filtering. This type of filter relies on the fact that surface scratches produce signals that are predominantly at high audio frequencies (about 7kHz or more). Severely attenuating these high frequencies gives a great reduction in the surface noise and leaves a passable standard of reproduction. Bad scratches can not be effectively combatted using filtering as they produce strong signals well down into the middle audio range, and an ordinary scratch filter would leave many of the frequency components unattenuated.

Using a lower cut-off frequency would give good attenuation of the scratch signal, but would result in a totally inadequate



bandwidth for music reproduction. Incidentally, a scratch blanker does not necessarily provide any reduction in audio bandwidth at all, and the unit featured here provides a full 20Hz to 20kHz bandwidth. The blanker connects between the preamplifier and the power amplifier, or it could be driven from the pick-up via a suitable preamplifier.


## BLANKING

In principle noise blanking is perfectly straightforward, and merely entails cutting the signal path for a short period when a noise spike is detected. The length of the blanking pulse depends on the application, but in the present context about three or four milliseconds is adequate. The problem is complicated by the need to blank the noise pulse before it starts to appear at the output of the circuit, and in practice this requires the use of a delay line. The basic arrangement is to feed the signal to the output via the delay line first and then the

electronic switch, but to drive the pulse detector circuit from the non-delayed signal. It takes the pulse detector under a millisecond to fully activate and break the signal path, and the delay line therefore only needs to provide a delay of about one millisecond in order to ensure that the noise pulse fails to reach the output.

Another slight complication is that of smoothing over the break in the signal. This is usually done using a sample and hold circuit, which is the method adopted in this design. A sample and hold circuit provides the effect shown in the waveform of Fig. 1(a). Here the signal is simply maintained at whatever voltage it happened to have at the instant the signal was cut off, and at the end of the blanking pulse it is immediately switched back to the current signal level. This does produce a slight glitch, in that at the instant the signal is switched on again the sample level and the signal level will usually be somewhat different. It is only a

Fig. 1(a). A sample and hold circuit is used to maintain the signal at a constant voltage during the blanking period. (b) Without the sample and hold circuit the blanking could make matters worse rather than better.

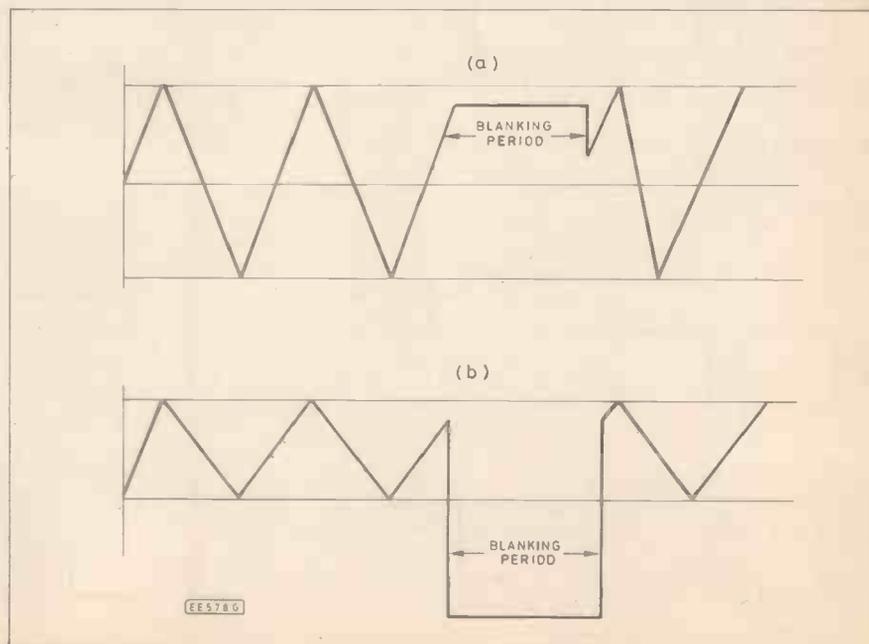

minor glitch though, and the switch in amplitude must always be below the peak to peak signal amplitude at the time. This ensures that under low signal conditions the glitch is always small and can never be dominant over the wanted signal.

What has to be avoided is a situation of the type shown in Fig. 1(b), where the signal is taken to a certain potential during the blanking period (or simply allowed to drift to any potential). This could produce a worse noise spike than the one which is being suppressed.

### SYSTEM OPERATION

The block diagram for the signal processing stages, is shown in Fig. 2 while Fig. 3 shows the block diagram for the blanking pulse generator circuit. Starting with the signal processing stages, there are two identical circuits, one for each stereo channel. An amplifier at each input provides buffering, plus a small amount of voltage gain (about 6dB). The voltage gain is needed as the input level to the delay line would otherwise be significantly less than that required for optimum noise performance. This voltage gain also compensates for small losses through the delay line, and the overall gain of the unit is little more than unity.

The delay line is a standard "bucket brigade" or CCD (charge coupled device) type. This consists of a series of capacitors and electronic switches which sample the input voltage, and pass the samples along the chain of charge storage capacitors through to the output of the device. There is obviously a delay between each sample being taken and it finally appearing at the output, and this delay depends on the number of capacitors in the line as well as

on the rate at which samples are passed from one capacitor to another. The rate of progress is controlled by a clock oscillator which is common to both channels, and it operates at a little over 200kHz. The delay line is a 512 stage type. The delay (in ms) is equal to the number of delaying stages divided by twice the clock frequency (in kHz), which works out at slightly more than one millisecond in this case.

### LOWPASS FILTER

A lowpass filter is needed at the input and output of each delay line. The input filters are needed to prevent any high frequency signals present on the input signal from entering the delay line where heterodyne tones could be generated by them interacting with the clock signal. In this case the clock frequency is well outside the audio range, and it is only radio frequency signals appearing on the input due to stray pick up that might cause problems. The output filters are needed to remove the clock signal. Apart from a slight clock breakthrough, the sampling process results in a stepped output signal, and the filtering is needed in order to smooth out the steps and give a proper output signal.

Each sample and hold circuit is really just an electronic switch feeding into a charge storage capacitor. The capacitor is normally driven from a low impedance source so that it has no significant effect on the circuit. However, when the switch breaks the signal path the capacitor retains whatever charge potential it happened to have at the instant the switch opened, giving the required "hold" action. A buffer amplifier ensures that there is no significant loading on the capacitor so that it is not discharged during the blanking period.

### BLANKING PULSES

Turning to the blanking pulse generator stages (Fig. 3), the first two stages are a unity gain inverting amplifier and a mixer. The right hand channel is fed direct to the mixer, but the left hand channel is inverted first. This gives a differential amplifier action with signals that are in-phase on the two channels tending to cancel out one another. Signals in antiphase on the two stereo channels are added together to give a strong output signal. Signals near the centre of the sound stage will be in-phase, and this results in the main signal being attenuated to some degree. On the other hand, the noise pulses will either be out of phase, or will only affect one channel, and in either case this results in a strong output from the mixer.

This does no more than slightly boost the noise spike in relation to the programme signal, and further processing is needed before strong noise pulses can be reliably distinguished from the main signal. This is achieved using a high slope highpass filter. The noise spikes have a strong high frequency content, whereas the main signal has relatively little signal content at these frequencies.

The filtered signal is amplified and then used to trigger a monostable multivibrator. The latter provides the blanking pulse to the sample and hold circuits, after its output signal has been inverted to give a pulse of the correct polarity for the sample and hold circuits.

As it stands, this arrangement seems to be capable of differentiating reliably between strong noise spikes and the main signal. However, if the sensitivity is adjusted to the point where relatively minor scratches are blanked, there is then a danger of sections of programme material which have a strong high frequency content activating the unit. This must not be allowed to occur as it would result in passages of music being virtually eliminated. There are no easy and totally effective solutions to this problem, but compromise solutions are possible. One would be to limit the blanker to just one operation in a given period of time. This would ensure that frequent spurious operations could not occur, and that sections of music could not be blanked out. Unfortunately it would also prevent the unit from blanking out the second noise spike where two occur in rapid succession.

### INHIBIT CIRCUIT

Another approach, and the one used in the final circuit, is to have an inhibit circuit which prevents the blanker from operating if a strong continuous output from the highpass filter is present. This is achieved by amplifying the filtered signal, then rectifying and smoothing it to produce a positive bias which drives a switching transistor. If the output from the filter is sufficiently strong, the transistor is biased into conduction and it effectively holds the output of the monostable in the low state, disabling the blanker action.

There may seem to be a flaw in this arrangement in that the inhibit circuit could be operated by the noise spikes, thus preventing them from being blanked. In practice this is avoided by having the attack time of the circuit just long enough to permit noise spikes to be blanked before the inhibit circuit becomes operational. This still leaves a real flaw in that the blanker is rendered inoperative during passages which have very strong high frequency content. This is not a major drawback though, since


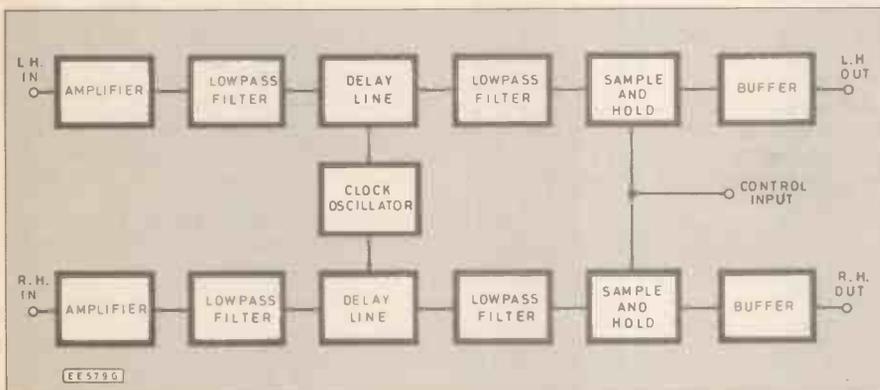


Fig. 2. Block diagram for the signal processing stages.

Fig. 3. The arrangement used to generate the blanking pulse.

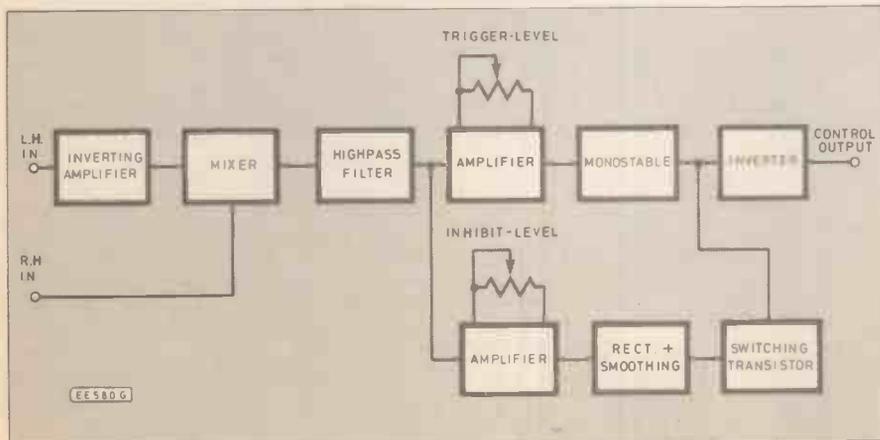

# COMPONENTS

Approx. cost  
Guidance only

£30

## Resistors

R1, 2, 33, 101, 102	4k7 (5 off)
R3, 15, 18, 19, 20, 21, 25, 26, 103	100k (9 off)
R4, 5, 10, 12, 13, 14, 16, 17, 27, 28, 29, 30, 104, 105, 112, 113, 114	10k (17 off)
R6, 7, 35, 106, 107	5k6 (5 off)
R8, 23, 108	15k (3 off)
R9, 109	1k (2 off)
R11, 31, 111	47k (3 off)
R22, 24	6k8 (2 off)
R32	39k
R34	1M5

All  $\frac{1}{2}$ W 5% carbon film

## Potentiometers

VR1, 101	22k sub-min horizontal preset (2 off)
VR2, 102	1k sub-min horizontal preset (2 off)
VR3	1M lin.
VR4	4k7 log.

## Capacitors

C1, 15, 101	4 $\mu$ 7 radial elect. 63V (3 off)
C2, 102	330nF carbonate (2 off)
C3, 26, 103	2 $\mu$ 2 radial elect. 63V (3 off)
C4, 8, 17, 18, 19, 20, 104, 108	2n2 carbonate (8 off)
C5, 7, 105, 107	1nF carbonate (4 off)
C6	100pF ceramic plate
C9, 109	150pF ceramic plate (2 off)
C10, 14, 16, 24, 110	47nF carbonate (5 off)
C11, 22, 111	10 $\mu$ F radial elect. 25V (3 off)
C21, 23, 25	100nF carbonate (3 off)
C12, 28, 29	100nF ceramic (3 off)
C13	100 $\mu$ F radial elect. 16V
C27	2200 $\mu$ F radial elect. 35V

## Semiconductors

IC1, 101	LF353 (2 off)	IC8	LF351
IC2, 102	TDA1022 (2 off)	IC9	L555CP or ICM7555
IC3	4047BE	IC10	uA7815
IC4, 6, 104	1458C (3 off)	TR1, 2	BC549 (2 off)
IC5	4066BE	D1, 2	1N4148 (2 off)
IC7	741C	D3, 4	1N4002 (2 off)

## Miscellaneous

SK1, 2, 101, 102	Phono sockets (4 off)
S1	Rotary mains on/off switch
FS1	500mA 20mm quick-blow fuse
T1	Mains primary, twin 15 volt 200mA secondaries

Case about 230 x 133 x 63mm; printed circuit board (available from the *EE PCB Service*, order code *EE539*); 20mm chassis mounting fuseholder; three control knobs; eight 8 pin d.i.l. i.c. holders; two 14 pin d.i.l. i.c. holders; two 16 pin d.i.l. i.c. holders; mains lead; Veropins; connecting wire; etc.

See  
**Shop  
Talk**  
page 485

of IC2. The TDA1022 only has 512 delaying stages, but there is a 513th stage which is used to maintain the output level while the 512th stage is taking a sample from the previous stage, and is unable to provide a valid output level. Preset VR2 is adjusted to minimise clock breakthrough, but most of the clock attenuation is provided by the third order (18dB per octave) filter based on IC4a.

The sample and hold circuit just consists of CMOS analogue switch IC5a and charge storage capacitor C10. The switches in the 4066BE device have low "on" resistances, especially when, as here, a 15 volt supply is used. Together with the low output impedance of IC4a this ensures that C10 does not introduce any significant high frequency roll-off. IC4b is the output buffer amplifier.

## UNITY GAIN

Moving on to Fig. 5, IC6a is the unity gain inverting amplifier, and IC6b functions as a summing mode mixer. The mixed signal is then fed to a fourth order (24dB per octave) highpass filter based on IC7. This has its cut-off frequency at approximately 10kHz, which seems to give about optimum results in practice. The next stage is an inverting amplifier built around IC8, and this has a voltage gain which is adjustable from about 100 times with VR3 at maximum resistance, to zero when it is at minimum resistance; VR3 is the trigger sensitivity control.

The monostable is a 555 type (IC9), but in this circuit a low power version (L555 or 7555) is used to ensure that noise spikes are not modulated onto supply lines, from where they could possibly break through to the output. Pin two of IC9 is the trigger input, and under quiescent conditions this is held at about half the supply voltage. To trigger IC9 pin two must be taken below one-third of the supply voltage, and scratches will produce a suitably strong input signal to do so on negative half cycles. IC9 then provides a positive output pulse which is set at approximately four milliseconds in duration by R32 and C23. It is a negative output pulse that is required, as the analogue switches are turned on by a "high" control signal, and switched off by a "low" control level. This problem is overcome by using one of the analogue switches (IC5c) as an inverter. The fourth switch in IC5 is left unused.

The inhibit circuit functions by switching on TR1 when there is a strong, sustained, high frequency input. TR1 then holds the control input of IC5a low, thus holding the two sample and hold circuits in the "pass" state. The control signal for TR1 is obtained by amplifying the output of IC7 using a high gain common emitter amplifier based on TR2. Its output is then rectified and smoothed by D1, D2 and C22 to give the positive d.c. control signal for TR1. VR4 is the inhibit sensitivity control.

## POWER SUPPLY

A well smoothed 15 volt supply is required, and this is provided by the mains power supply circuit shown in Fig. 6. This has T1 to provide isolation and voltage step-down, with push-pull rectification and a considerable amount of smoothing provided by D3, D4 and C27. A monolithic voltage regulator (IC10) then provides regulation and electronic smoothing. The total current consumption of the blanker circuit is around 60 milliamps.

scratches are relatively unimportant and not so noticeable during these passages. This system works well in practice, and enables the unit to be operated with a substantially higher level of trigger sensitivity than would otherwise be usable.

## CIRCUIT OPERATION

Refer to Fig. 4 for the circuit diagram of the signal processing stages, and to Fig. 5 for the blanking pulse generator circuit. Fig. 4 only shows the circuit for one channel, and most of the components are duplicated in the second stereo channel.

The input stage is an operational amplifier (IC1a) used in the non-inverting mode and having a voltage gain of two times. VR1 provides a variable bias voltage, and as the circuit is direct coupled from the input to the output this sets the bias level for all the subsequent stages as well. In practice it is set to obtain optimum large signal handling ability from the delay line circuit.


IC1b acts as the buffer amplifier in the input lowpass filter, which is 12dB per

octave type. Although delay lines often require very high slope filters at the input and output in order to obtain passable results, the high clock frequency used in this case enables excellent results to be obtained using relatively simple filters, and a 12dB per octave roll-off above 20kHz is more than adequate. The high clock frequency results in an excellent signal to noise ratio without the need for any form of noise reduction circuit.

The delay line chip is a TDA1022 (IC2) with its clock signal provided by IC3. The latter provides the clock signal for both channels incidentally. IC3 is a CMOS 4047BE astable/monostable device which operates in the free running astable mode in this circuit. The delay lines require a two-phase clock signal, but with its Q and  $\bar{Q}$  outputs the 4047BE can provide these without the need for an external inverter to the second phase.

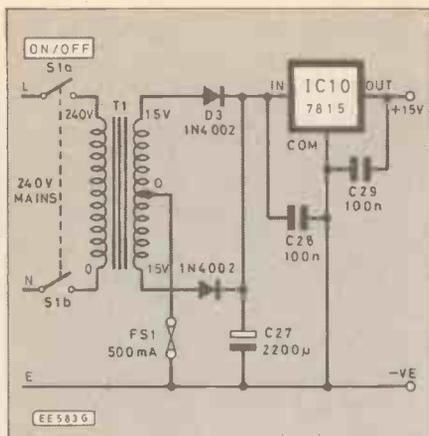Resistors R8 and R9 provide a bias signal to IC2, while VR2 acts as a simple mixer to combine the outputs of stages 512 and 513





## CONSTRUCTION

Construction is greatly simplified by the use of a single printed circuit board to accommodate all the components apart from the controls, sockets, fuseholder, and mains transformer. Details of the printed circuit board and wiring are shown in Fig. 7. This board is available from the *EE PCB Service*: code EE539.



The board is in most respects perfectly straightforward to construct, but there are a few points worthy of note. Firstly, in both Fig. 7 and the components list the components in the right hand channel have the same

identification numbers as those in the left hand channel, except that one hundred has been added to the number (e.g. C108 is the right hand channel equivalent of C8). A few components are common to both channels, and both channels are of course served by a single blanking pulse generator. There are a number of link wires, a dozen in fact, and these are made from 20 or 22 s.w.g. tinned copper wire. The two long link wires between IC2 and IC3 should be kept quite taut, or insulated if necessary, so that there is no risk of them short circuiting together.

Components IC2, IC3 and IC102 are MOS devices, and consequently require the standard antistatic handling precautions.

Fig. 6 (left). Circuit diagram of the mains power supply.

Fig. 7. Component layout and printed circuit board master (full size).

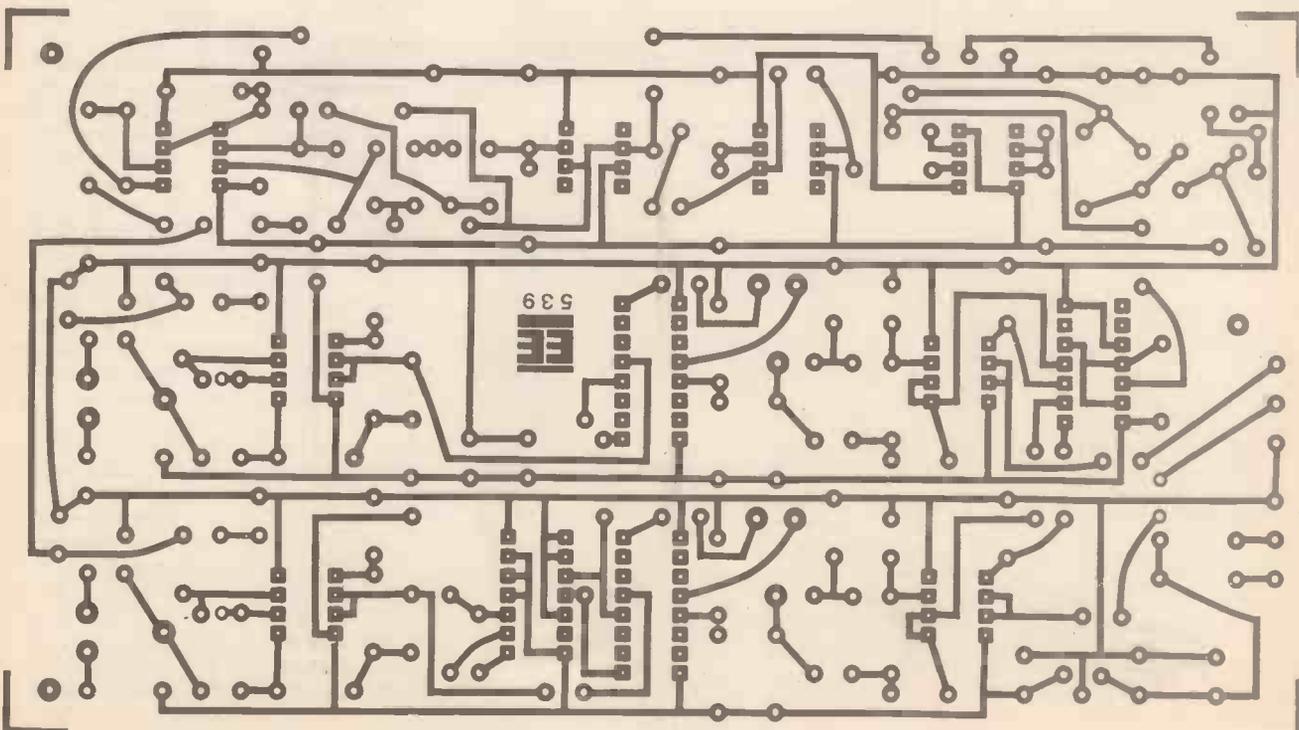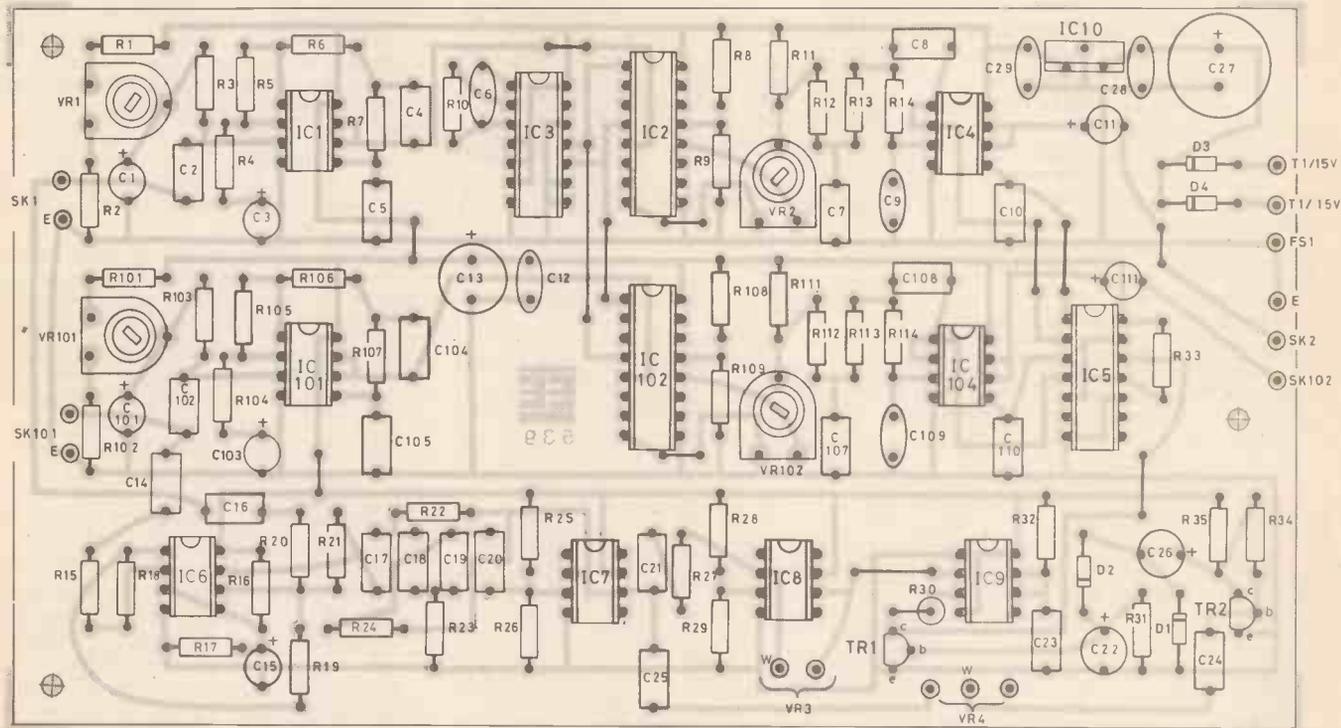

Although IC9 is also a MOS type, it has built-in protection circuits that render handling precautions totally unnecessary. IC10 will become quite hot in operation, and it is a good idea to fit it with a small aluminium fin to provide heatsinking and ensure that there is no risk of overheating. Most of the non-electrolytic capacitors are carbonate or miniature polyester types having a lead spacing of 7.5 millimetres, and it is essential that the correct type are used if they are to fit onto the board properly. Veropins are fitted to the board at all the points where connections to off-board components will be made.


## HOUSING

An instrument case having approximate outside dimensions of 230 by 133 millimetres is suitable as the housing for this project. Any case of about the same size should suffice, but do not choose one significantly smaller on any dimension. The sockets are mounted on the rear panel and phono types are probably the best choice for these, although a different type could obviously be used if this would be more convenient for use in your particular set-up. A hole for the mains lead is made in the rear panel, well towards the right hand end of the panel, and this should be fitted with a cable securing grommet.

The printed circuit board is mounted on the base panel using M3 or 6BA screws and fixing nuts. Spacers about 10 or 12 millimetres long are used to keep connections on the underside of the board well clear of the metal case. The board is fitted as far to the

left as possible, so as to leave space for T1 and the fuseholder at the right hand end of the base panel. A solder tag is fitted on one of T1's mounting bolts to provide a chassis connection point. For safety reasons the mains earth lead must connect to this tag, so that the case is earthed. The three controls are mounted on the front panel, and obviously on/off switch S1 should be fitted adjacent to T1, see Fig. 8 and photo.

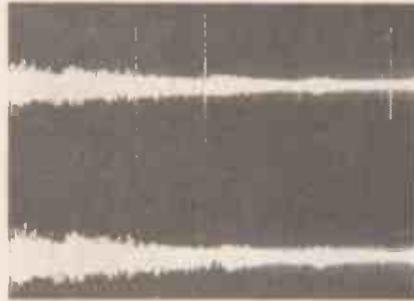To complete the unit the hard wiring is added, and as this is a mains powered project it is important to proceed carefully with this, and to thoroughly check the completed wiring.



Before and after oscillograph showing the effect of blanking.

## ADJUSTMENT AND USE

Presets VR2 and VR102 are adjusted for minimum clock breakthrough at the output of their respective channels, but due to the high clock frequency used in this circuit there is minimal clock breakthrough at any


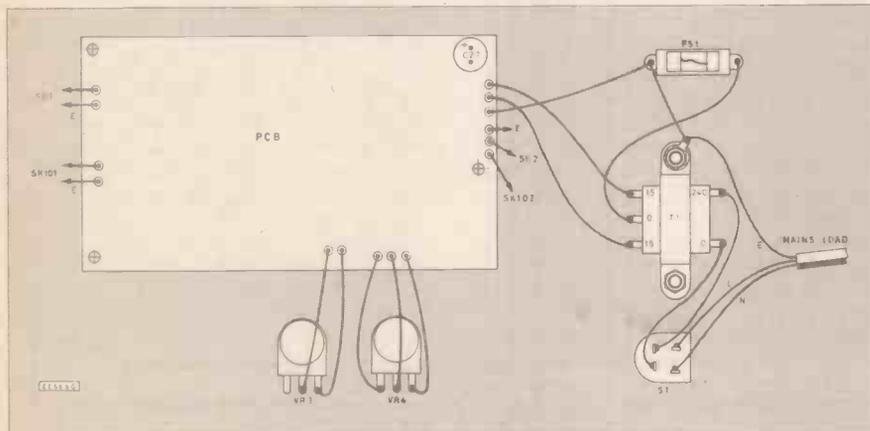


Fig. 8. Interwiring to the printed circuit board.

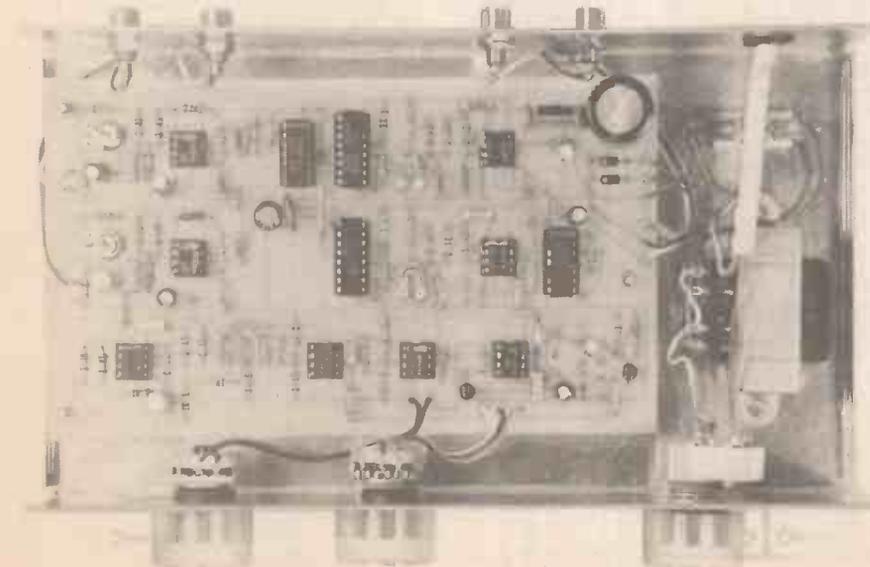

Completed Scratch Blanker showing interwiring to circuit board.

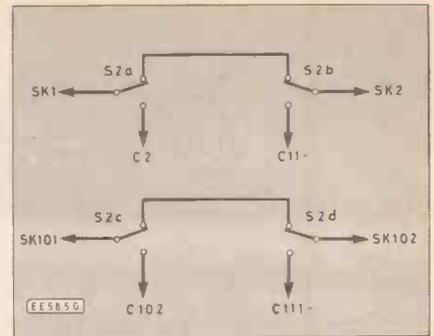


Fig. 9. Adding a bypass facility requires a 4-pole 2-way switch.

settings of these components. It is therefore quite in order to simply set these presets at a roughly mid-setting. If an audio signal generator and an oscilloscope are available, VR1 and VR101 are adjusted for symmetrical clipping on each channel. If suitable test gear is not to hand it is acceptable to simply adjust these to find any settings which give an output signal that is free from any obvious distortion. Provided the circuit is not overloaded it provides a typical total harmonic distortion level of well under one per cent.

Just where in the audio system the unit is connected depends on the facilities offered by the system concerned. If a tape monitor facility is available, this can provide a convenient way of selecting the unit or switching it out, as desired. With some amplifiers and receivers preamplifier outputs and power amplifier inputs are available, and the unit can then be connected between these. A bypass switch in the blanker unit would then be needed, and all that is required is a four pole changeover switch connected as shown in Fig. 9 (a three way four pole rotary switch with the end stop set for two way operation is suitable for S2). A third alternative is to feed the unit from the cartridge via a suitable preamplifier, and ready-made preamplifiers of the appropriate type are available if a home-constructed design can not be located. The output of the unit would feed into any high level input of the amplifier or receiver, such as a "Tape" or "Aux" input. With this method it would again be advisable to include the bypass switching.

If only very bad scratches are to be processed the trigger level control will not need to be advanced very far, and results will probably be perfectly adequate without needing to advance the inhibit sensitivity control at all. With the trigger level well advanced the unit will process relatively minor scratches, but the inhibit sensitivity control must also be well advanced or it is likely that some passages of music will be blanked out. However, this is something that depends on the nature of the recording, and it is really necessary to experiment a little with the settings of the two controls to determine what works best for a given recording.

The degree of attenuation applied to the scratch pulse is massive, and there is no significant breakthrough of this signal at all. As mentioned earlier, there may be a slight audible glitch when the blanker operates, or there may be no audible effect at all. This depends on the relative signal levels at the beginning and end of the blanking period, but there is never less than a very substantial improvement in the signal. The accompanying oscillograph shows "before" and "after" traces, which clearly show the effect of the blanking. □

# Actually Doing it!!

If you have followed this series thus far you should now be at the stage where you can build up projects, taking them through to a neat and fully finished article. Although one could reasonably be forgiven for thinking that this is the end of things, there is often one final stage on the way to success—getting the finished project to work. Had I been writing this series a few years ago I would have emphasized that the chances of getting a project to work first time, even for an experienced constructor, were not great. These days the situation is somewhat different, with the widespread use of ready-made printed circuit boards greatly reducing the risk of errors, and making first time operation much more likely. There are still plenty of things that can go wrong, though, and if on completing your first project it fails to operate you should not be too surprised or disappointed. In more than 90 per cent of cases where a newly constructed project fails to work the problem is a simple and straightforward one which can easily be rectified by someone with little technical knowledge and little or no test gear.

## THE OBVIOUS

Start by looking for obvious problems which are easily overlooked by one's eagerness to switch on and try out the new gadget. Is the battery fitted, and if it is, is it properly connected to the battery clip. The latter are a common cause of problems, and it is worthwhile gently pulling the two leads to ensure that one of them has not become detached from its press-stud. Sometimes one press-stud connects to the battery properly, but the other is a loose fit and power fails to get through to the circuit. In these cases the offending female press-stud can be crushed slightly with a pair of pliers to make it a reliable fit.

You should have thoroughly checked for errors such as integrated circuits fitted around the wrong way before switching on the unit, but probably few constructors are able to control their enthusiasm to test the new device, and most projects undergo little in the way of real checking prior to switch-on. Fortunately most modern components are very tolerant of abuse, and quite serious errors will often not result in any casualties. However, if at all possible it is obviously better to track down errors before switch-on rather than afterwards.

For one thing, if an error such as an integrated circuit fitted round the wrong way is not discovered until after the unit has been tried out, and on correcting the error the unit still fails to work, this introduces a strong element of uncertainty. It could be that there is another and unrelated error, or the integrated circuit might have been damaged. This means either spending a lot of time searching for a fault which might not exist, or replacing what might well be a perfectly good device. Some basic checking prior to switch-on

can save a lot of wasted time and money.

The hard wiring is where any errors are most likely to occur, and the most common causes of problems here were discussed in previous articles. If there is something in the wiring that you were not sure about when constructing the project, it would be a good idea to take another look at this to see if you might have misinterpreted something, and if it looks as though you might have done so, try the alternative method of connection.

## THE LESS OBVIOUS

More often than not a quick check over the unit will reveal some simple little error that is the cause of the problem, but some faults can be more difficult to spot. Printed circuit mounting capacitors of the carbonate or polyester layer varieties are a common cause of trouble. The standard fault is where the lead spacing is just fractionally narrower than the hole spacing in the board. On pushing the component down into place on the board one of the leads gets ripped away from the body of the component, but there may be little outward sign of this.

A close visual inspection will normally reveal this problem, though, as will gently pushing on the side of each component. If this fault is found it is often possible to solder the lead back in place, but this could affect the accuracy of the component as well as giving dubious long-term reliability. If this is done it is therefore best to regard it as only an interim measure, and to replace the component with a new type at the earliest opportunity, taking care not to give a repeat performance.

With projects constructed on stripboard the main hazard is accidental short circuits between copper tracks due to what are often quite small blobs of excess solder. With custom printed circuit boards this is less of a problem, but it can still happen, especially on areas of the board where there are a lot of connections in a small area (d.i.l. clusters etc.). Solder blobs and splashes (thin streaks of solder across the board) can be difficult to spot visually, and it is helpful to use a spirit-based cleaner to remove any excess flux from the board; a magnifying glass might also be very helpful.

## CONTINUITY CHECKER

I have often come across short circuits which defy visual detection even with close and detailed inspection, and my preferred way of doing things is to use a continuity tester to check for short circuits between adjacent tracks or pads which should not be connected. This really requires the use of a tester which will not respond to very low resistances or to forward biased semiconductor junctions, as otherwise a constant stream of misleading indications are likely to be obtained. Suitable continuity checker designs appear in *Everyday Electronics* from time to

time, or a multimeter set to a range having a full scale value of about 10 or 20k should suffice.

Do not be tempted into the classic mistake of building up a continuity tester from a torch battery and bulb wired in series. The problem with this arrangement is that it can force quite high currents through the circuit being tested, and this could result in the unit producing more faults than it locates. The simple continuity checker circuit of Fig. 1 is a sort of modern equivalent of the old torch bulb type, and the use of an ultra-bright l.e.d. enables the current to be kept to a suitably low level.

You may occasionally track down a short circuit with a continuity tester, but first yourself in the position of not being able to visually locate the offending piece of solder. Running the blade of a modelling knife between the two copper strips a few times over their entire length should cut through the solder and cure the fault.

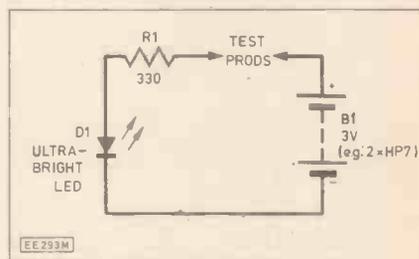


Fig. 1. Simple but safe continuity checker.

Soldering is a subject that has been covered in previous articles, and it is one which has to be mentioned again here since inadequate soldering is possibly the most common cause of projects failing to work. Good soldered joints on a circuit board should have a sort of mountain shape with a shiny surface to the solder. A rounded shape (often accompanied by a dull surface to the solder) usually indicates that the solder has not flowed over the track and lead properly. A dull and crazed finish to the surface of the solder indicates the lead has been moved as the solder solidified, causing numerous fractures in the solder.

Another problem that can occur is where a leadout wire has been trimmed slightly too short so that very little of the lead (or nothing at all) protrudes on the copper side of the board. This can result in a cap of solder over the leadout wire without it actually being soldered in place. Joints of this type can often be spotted because they are very much flatter than ordinary joints, with no sign of the leadout wire.

This is another case where a detailed visual inspection will often reveal the fault, but it can not be relied upon to do so. It is much better to use a continuity checker to test for a proper connection between each leadout wire and its copper track. Simply giving the components a firm pull will often reveal inadequate joints as the offending leadout wire may pull clear of the board, and it is worth giving this a quick try before spending a lot of time testing each connection with a continuity checker.

If a dry joint is located, do not simply try applying further solder to it. First clean off the original solder using a desoldering tool or solder wick, then make sure that both surfaces are clean and in a fit state for

soldering (with any excess flux being removed), and finally resolder the connection. It would be advisable to recheck the new joint with a continuity checker. If the problem was due to inadequate leadout protrusion, it might simply be a matter of applying the iron to the joint and pushing the component fully down and into place on the board. If the lead has been trimmed too short, one way around the problem is to solder a short piece of tinned copper wire in place, and then connect the leadout to this on the component side of the board. A neater solution is to simply replace the component. I have come across d.i.l. integrated circuit holders with very short pins that are barely a board's thickness in length. It can be very difficult to produce reliable connections with these, especially when using a fairly thick piece of board, and they are best avoided.

## COMPONENTS

Faulty components are quite rare these days, and unless you fail to take due care when connecting components it is extremely unlikely that a "dud" will be responsible for the problem. Therefore, if you are careful when constructing the unit and ensure that there are no faults of what could really be termed mechanical rather than electrical in nature (e.g. short circuits and integrated circuits fitted around the wrong way) the finished project is almost certain to work. It is useful to keep this in mind, and a positive approach to things gives a far better chance of success.

If a thorough check fails to reveal a fault the next step is to try checking the components, and at the very least a multimeter is needed for this. Even with the aid of a multimeter only fairly simple components

can be tested. As a quick initial check, ensure that the supply is getting through to the circuit board, and to all the integrated circuits, etc., that connect to one or other of the supplies. Broken printed circuit tracks are not a common fault, but they do occur.

Any multimeter should be capable of measuring over a wide resistance range, and testing the resistors should not be a problem. Do not overlook the fact that in-circuit checks may not be very accurate due to the presence of components connected in parallel with the one you are checking. What this means in practice is that some readings may be on the low side, but a higher than expected reading is certainly indicative of a fault. If a low reading is obtained, swapping the test prods over may give a more accurate one, but the only certain way of eliminating errors due to effect of other components is to temporarily disconnect one leadout wire so that the component is effectively isolated from the rest of the circuit.

A multimeter cannot thoroughly test inductors, but a broken wire will be indicated by a very high resistance through the winding. Similarly, capacitors cannot be properly tested, but the most common fault is a short circuit through the component, and a multimeter set to a resistance range will detect this. When first connecting the meter to the capacitor the needle might give a slight kick as the component charges up. The size of the kick depends on the value of the capacitor (higher values giving larger deflections), and this can be used as a rough guide to whether or not a component is functioning properly. However, very low values will not give a significant kick of the needle even with the

multimeter set to the highest resistance range, and this method is not applicable to digital multimeters.

Diodes are easily checked using a multimeter set to a resistance range. Connecting the test prods one way round should give a low reading, while a high reading should be obtained with the prods reversed. As a quick check of transistors, there should be a diode action between the base-emitter and base-collector leads, and a very high resistance across the collector-emitter leads with the test leads connected either way around. All these tests should ideally be carried out with one lead of the component under investigation disconnected from the board (or two leads in the case of transistors), and results are largely meaningless unless this is done.

Mistakes can occur in magazines (but very infrequently in *EE&EM*), and any corrections for errors in constructional articles normally appear an issue or two after the copy in which the project was published. If all else fails you can write into the magazine asking for help, but do try to include as much useful information as possible. Simply stating that a project has failed to work and asking why is very much a "how long is a piece of string?" type question. If the project does something, even something like a component getting warm, then give details of this. Even if it does nothing at all then this fact should be stated and might prove helpful. If you have a multimeter take a few voltage readings and include these. Most important of all, do not forget to include a stamped addressed envelope for the reply.

*Robert Penfold*

# LETTERS

## Spot on

Sir—In reply to David J. M. Lloyd's letter "Back to the beginning" (July '86 issue) I would like to say that as a beginner I find your magazine "spot on". My attention was first drawn to your magazine when I noticed a Waa-Waa Pedal project. I purchased my first small batch of components and completed the project in one day... all due, of course, to your easy to follow instructions and clear pictorial layout and diagrams. I was immediately hooked to electronics as a hobby.

I now have a regular order for your magazine. I am especially interested in your musical effects projects as I play electric guitar in a band. Car projects are of little interest to me as we do not own a car... we're a family of dedicated motorcyclists! "Home projects" like burglar alarms, intercoms and games are very interesting to build and useful to the whole family.

I learn something new about circuit layout and building with every project I complete. Learning from building projects and also from your "Teach In" series has helped me to gain a wealth of knowledge about electronic circuitry.

However, I do agree with Mr. Lloyd on the subject of computers. There are enough magazines covering technical information and "add-on" projects for computers. Anyway, most beginners would prefer building the more "conventional" projects rather than tackling the more difficult computer projects. That of course is just my opinion.

I disagree with Mr. Lloyd on the subject of formulae, calculations, etc. I find these of great interest and as I like to experiment with circuit design, formulae and calculations are a necessity.

Overall, I find *Everyday Electronics* and *Electronics Monthly* an excellent magazine for the beginner and not-so-beginner alike. I shall keep buying it... computer projects included... or not. Keep up the good work!

Billy McCoy,  
Newcastle West,  
Co. Limerick.

## No more please!

Sir—I read David Lloyd's letter (July 86 issue) with some interest.

The July issue was the first electronics magazine that I have bought for several years, although I have "pottered" with circuits during that time. I agree entirely with his views upon computers. The reason that I rejected the other magazines was that they were packed with computer circuits—no more please!

I would, however, like to see more articles on circuit design and applications

of popular i.c.s, how to actually make them work and tailor them to our own needs. A good example of this is the *Exploring Electronics* series—it shows us the principle of transmission, but, how would you build a modulator and r.f. amplifier??

Also, why not have more projects that can be built from readers' junk boxes? I'm sure there are thousands of us with 741s, 7400s, 4011s in our junk boxes, but unable to use them as they now seem to be "obsolete" and EE projects use only CA3240s etc., where a good ol' 741 could do the trick!

Just look at your readers' circuits. You'll see lots of 741s, BC109s etc. etc. Could it be they're trying to tell you something? Also let's have a bit of "boring" theory so we can design our own circuits—no, perhaps not—it might put you out of a job!

G. Finney,  
Pontypool,  
Gwent.

**EE** BOOK SERVICE  
**See Page 470**

# PCB SERVICE

Printed circuit boards for certain constructional projects are now available from the PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: The PCB Service, Everyday Electronics and Electronics Monthly Editorial Offices, 6 Church Street, Wimborne, Dorset BH21 1JH. Cheques should be crossed and made payable to Everyday Electronics. (Payment in £ sterling only.)

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

**NOTE: Please allow 28 days for delivery. We can only supply boards listed in the latest issue.**

PROJECT TITLE	Order Code	Cost
— JULY '83 —		
User Port Input/Output <i>M.I.T. Part 1</i>	8307-01	£4.82
User Port Control <i>M.I.T. Part 1</i>	8307-02	£5.17
— AUGUST '83 —		
Storage Scope Interface, BBC Micro	8308-01	£3.20
Car Intruder Alarm	8308-02	£5.15
High Power Interface <i>M.I.T. Part 2</i>	8308-03	£5.08
Pedestrian Crossing Simulation <i>M.I.T. Pt 2</i>	8308-04	£3.56
— SEPTEMBER '83 —		
High Speed A-to-D Converter <i>M.I.T. Pt 3</i>	8309-01	£4.53
Signal Conditioning Amplifier <i>M.I.T. Pt 3</i>	8309-02	£4.48
Stylus Organ	8309-03	£6.84
— OCTOBER '83 —		
D-to-A Converter <i>M.I.T. Part 4</i>	8310-01	£5.77
High Power DAC Driver <i>M.I.T. Part 4</i>	8310-02	£5.13
— NOVEMBER '83 —		
TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i>	8311-01	£5.46
Stepper Motor Manual Controller <i>M.I.T. Part 5</i>	8311-02	£5.70
Speech Synthesiser for BBC Micro	8311-04	£3.93
— DECEMBER '83 —		
4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i>	8312-01	£5.72
4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i>	8312-02	£5.29
Environmental Data Recorder	8312-04	£7.24
Continuity Tester	8312-08	£3.41
— JANUARY '84 —		
Biological Amplifier <i>M.I.T. Part 7</i>	8401-02	£6.27
Temp. Measure & Control for ZX Compr Analogue Thermometer Unit	8401-03	£2.35
Analogue-to-Digital Unit	8401-04	£2.56
Games Scoreboard	8401-06/07	£9.60
— FEBRUARY '84 —		
Oric Port Board <i>M.I.T. Part 8</i>	8402-02	£9.56
Negative Ion Generator	8402-03*	£8.95
Temp. Measure & Control for ZX Compr Relay Driver	8402-04	£3.52
— MARCH '84 —		
Latched Output Port <i>M.I.T. Part 9</i>	8403-01	£5.30
Buffered Input Port <i>M.I.T. Part 9</i>	8403-02	£4.80
VIC-20 Extension Port Con. <i>M.I.T. Part 9</i>	8403-03	£4.42
CBM 64 Extension Port Con. <i>M.I.T. Part 9</i>	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro	8403-05	£4.63
— APRIL '84 —		
Multipurpose Interface for Computers	8404-01	£5.72
Data Acquisition "Input" <i>M.I.T. Part 10</i>	8404-02	£5.20
Data Acquisition "Output" <i>M.I.T. Part 10</i>	8404-03	£5.20
Data Acquisition "PSU" <i>M.I.T. Part 10</i>	8404-04	£3.09
A.F. Sweep Generator	8404-06	£3.55
Quasi Stereo Adaptor	8404-07	£3.56

Simple Loop Burglar Alarm	8405-01	£3.07
Computer Controlled Buggy <i>M.I.T. Part 11</i>	8405-02	£5.17
Interface/Motor Drive	8405-03	£3.20
Collision Sensing — MAY '84 —	8405-04	£4.93
Power Supply		
— JUNE '84 —		
Infra-Red Alarm System	8406-01	£2.55
Spectrum Bench PSU	8406-02	£3.99
Speech Synthesiser <i>M.I.T. Part 12</i>	8406-03	£4.85
Train Wait	8406-04	£3.42
— JULY '84 —		
Ultrasonic Alarm System	8407-01	£4.72
Electronic Code Lock	8407-03	£2.70
Main Board	8407-04	£3.24
Keyboard		
— AUGUST '84 —		
Microwave Alarm System	8408-01	£4.36
Temperature Interface—BBC Micro	8408-02	£2.24
— SEPTEMBER '84 —		
Op-Amp Power Supply	8409-01	£3.45
— OCT '84 —		
Micro Memory Synthesiser	8410-01*	£8.20
Drill Speed Controller	8410-04	£1.60
— NOVEMBER '84 —		
BBC Audio Storage Scope Interface	8411-01	£2.90
Proximity Alarm	8411-02	£2.65
— DEC '84 —		
TV Aerial Pre-Amp	8412-01*	£1.60
Digital Multimeter	8412-02/03*	£5.20
Mini Workshop Power Supply	8412-04	£2.78
— JAN '85 —		
Power Lighting Interface	8501-01	£8.23
Games Timer	8501-02	£1.86
Spectrum Amplifier	8501-03	£1.70
— FEB '85 —		
Solid State Reverb	8502-01	£3.68
Computerised Train Controller	8502-02	£3.38
— MARCH '85 —		
Model Railway Points Controller	8503-01	£2.78
— APRIL '85 —		
Insulation Tester	8504-02	£2.53
Fibrealarm	8504-03	£3.89
— MAY '85 —		
Auto Phase	8505-01	£3.02
Amstrad CPC464 Amplifier	8505-02	£2.56
Mains Unit	8505-03	£2.56
Micro Unit	8505-04	£2.67
Voltage Probe		
— JUNE '85 —		
Graphic Equaliser	8506-01	£3.21
Computerised Shutter Timer	8506-02	£2.09
Mono-Bi-Astables (Experimenters Test Bed)	8506-03	£2.45
Across The River	8506-04	£2.63
— JULY '85 —		
Amstrad User Port	8507-01	£3.17
Nascom Printer Handshake	8507-02	£1.90
— AUGUST '85 —		
Electronic Building Blocks—1 to 4†	8508-01	£2.98
Tremolo/Vibrato	8508-02	£4.03
Stepper Motor Interface	8508-03	£2.40
Drill Control Unit	8508-04	£2.90
— SEPTEMBER '85 —		
RIAA Preamp Input Selector	8509-01	£2.36
Transducers Resistance Thermometer	8509-03	£2.64
Transducers Semiconductor Temp. Sensor	8509-04	£2.72
— OCT '85 —		
Transducers Strain Gauge	501	£2.87
Soldering Iron Power Controller	504	£2.09
— NOV '85 —		
Transducers—		
Magnetic Flux Density Amplifier	505	£3.93
Hallowe'en Projects (single board price)	506	£2.68
— DEC '85 —		
Electronic Building Blocks — 5 to 8†	508	£3.07
Opto Intensity Transducer	509	£2.70
Digital Capacitance Meter	512	£5.22
— JAN '86 —		
Mains Delay	503	£2.13
Musical Doorbell	507	£2.91
Tachometer—Transducers	513	£2.52
— FEB '86 —		
Touch Controller	510	£2.65
Function Generator	514	£3.10
Function Generator PSU Board	515	£2.09
pH Transducer	516	£2.75

\*Complete set of boards.

*M.I.T.*—Microcomputer Interfacing Techniques, 12-Part Series.

†Four separate circuits.

PROJECT TITLE	Order Code	Cost
Mains Tester & Fuse Finder	517	£2.27
BBC Midi Interface	518	£3.26
Stereo Hi Fi Preamp	519	£5.70
Interval Timer	520	£2.36
Stereo Reverb	521	£2.89
PA Amplifier	511	£2.67
Mini Strobe	522	£2.24
Auto Firing Joystick Adaptor	523	£2.73
Watchdog	524	£2.81
Percussion Synthesiser	525	£5.65
Personal Radio	526	£2.07
Tilt Alarm	527	£2.13
Electronic Scarecrow	528	£2.28
VOX Box Amplifier	529	£2.35
Headphone Mixer	530	£4.56
Solar Heating Controller	533	£3.32
Car Timer	538	£2.02
Freezer Failure Alarm	534	£1.90
Infra Red Beam Alarm (Trans)	536	£3.32
Infra Red Beam Alarm (Rec)	537	£3.32
Scratch Blanker	539	£5.43

Prices for **ELECTRONICS MONTHLY** PCBs are shown below.

PROJECT TITLE	Order Code	Cost
Cymbal Synth	EM/8412/2	£4.86
The Thing	EM/8412/4	£3.18
Speak Board	EM/8501/2	£3.97
Headphone Amp	EM/8502/1	£2.08
Intelligent Nicad Charger	EM/8502/2	£3.50
Anti Phaser	EM/8502/3	£4.56
Logical Lock	EM/8502/4	£3.58
Touch Dimmer	EM/8502/5	£3.29
Courtesy Light Extender	EM/8503/4	£3.29
Disco Light Chaser	EM/8503/5	£8.11

**EE PRINTED CIRCUIT BOARD SERVICE**  
**Please send me the following p.c.b.s.**  
 Make cheques/PO payable to: **Everyday Electronics**  
 (Payment in £ sterling only)

Order Code	Quantity	Price
.....	.....	.....
.....	.....	.....
.....	.....	.....

I enclose cheque/PO for £ .....

Name .....

Address .....

Make cheques/PO payable to: **Everyday Electronics**

Sound to Light Unit	EM/8504/1	£4.02
Car Audio Booster	EM/8504/2	£3.12
Short Wave Converter	EM/8504/3	£4.15
Car Burglar Alarm	EM/8505/3	£2.88
Metal Detector	EM/8506/1	£4.24
Power Supply Module	EM/8506/3	£3.20
Flanger	EM/8506/4	£4.29
EI Tom/EI Tom+	EM/8507/1	£4.10
EI Cymb	EM/8507/2	£4.10
Heartbeat Monitor	EM/8507/3	£3.98
Real Time Clock	EM/8507/4	£4.62
Intelligent Windscreen Wiper (incl. Terminal Board)	EM/8508/1/2	£4.12
HiFi Intercom (2 boards)	EM/8508/3	£2.92
Plug Power Supply	EM/8508/4	£2.28
Hot Water Alarm	EM/8508/5	£1.93
Sinewave Generator	EM/8509/1	£2.76
Household Battery Checker	EM/8509/2	£1.97
Audio Signal Generator	EM/8509/3	£3.65
Compressor Pedal	EM/8510/1	£2.87
Computer Cont Filter	EM/8510/2	£2.94
Spectrum MIDI Interface	EM/8510/3	£3.20

**"If last month's issue of EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY hadn't sold out, I'd have got the thing off the ground by now."**



Sell-out disappointment can upset even the less ambitious reader! So why not take out a year's subscription and make sure of every issue, straight from the Publisher? Complete the order form below and post to: **EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY**, Subscription Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. Tel. 0202 881749.

**Annual subscription rates:**  
**UK £13. Overseas £15 (£ sterling only)**

**EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY SUBSCRIPTION ORDER FORM**

Annual subscription rates:  
 UK £13. Overseas £15 (surface mail) £30 (air mail)

To: Everyday Electronics and Electronics Monthly,  
 Subscription Dept., 6 Church Street, Wimborne, Dorset  
 BH21 1JH.

Name .....

Address .....

.....

.....

I enclose payment of £..... (cheque/PO in £ sterling only payable to Everyday Electronics)

**Subscriptions can only start with the next available issue.** For back numbers see the Editorial page

# EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY

Reach effectively and economically today's enthusiasts anxious to know of your products and services through our semi-display and classified pages. The prepaid rate for semi-display spaces is £8.00 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 30 pence per word (minimum 12 words), box number 60p extra. VAT must be added. All cheques, postal orders, etc., to be made payable to Everyday Electronics. Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel.: 0202 881749.

## Components

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact **COLES HARDING & CO.**, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

## Switches

**SIMPLE SOUND OPERATED SWITCH.** Plans and PCB £2.50, from **HERRINGTON**, 63 Home-farm Road, London W7 1NL.

## Miscellaneous

**MAKE MONEY WITH YOUR MICRO.** Manual shows you how. Turn your games machine into a profitable business. Free details **Enterprise Books**, EE, 19 Margate Road, Preston, Lancs PR2 3TB.

## Printed Circuit Boards

PCBs made to own personal requirements with or without artwork. Send for details to: **B. M. ANSBRO**, 38 Poynings Drive, Hove, Sussex.

## Receivers & Components

**LEARN  
ELECTRONICS WITHOUT  
SOLDER**



Build electronic circuits without solder on a Roden S-Dec. This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experiments. Full instructions and 2 circuit diagrams with each S-Dec.

Send Cheque or P.O. to:  
Roden Products, Dep EE  
High March, Daventry,  
Northants, NN11 4DE.

**£5.25** including p & p

## ESR ELECTRONIC COMPONENTS

- Full range of components
- Motors & Servos
- Robot Arms & Interfaces
- Velleman Electronic Kits

Send for New Catalogue

60p inc. P&P

13A Station Rd, Cullercoats, North Shields,  
Tyne & Wear NE30 4PQ Tel. 091 251 4363

## Service Sheets

**SOLE SUPPLIERS** TV/Video repair manuals/circuits. 1000s s/manuals supplied by return. S/sheets £2.50 except CTV/M. centres/stereos £3.50 LSAE with every order/query please brings free pricelist/magazines inc s/sheet - or phone 0698 884585 (883334 out of business hours) TIS(EE) 76 Church Street, Larkhall, Lanarkshire.

Please mention  
**EVERYDAY ELECTRONICS**  
when replying to  
Classified Ads

### ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for ..... Insertions. I enclose Cheque/P.O. for £..... (Cheques and Postal Orders should be made payable to Everyday Electronics)


HEADING REQUIRED:

NAME .....

ADDRESS .....

.....

.....


**EVERYDAY ELECTRONICS**  
and **ELECTRONICS MONTHLY**  
Classified Advertisement Dept.,  
6 Church Street,  
Wimborne,  
Dorset BH21 1JH.  
Telephone 0202 881749

RATE: 30p per word, minimum 12 words. Box No. 60p extra. VAT must be added.

9/86

**WATCH OUT FOR**

# PROTEUS

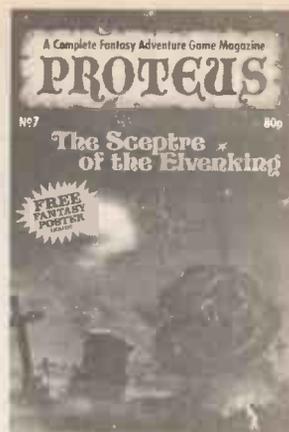

## Another Complete Fantasy Adventure Game

Another FREE poster



**More  
PERILS  
TO BRAVE**

# PROTEUS


## No. 7

At your  
newsagents  
now, only 80p

# CRICKLEWOOD

ELECTRONICS LTD

SUMMER  
ISSUE

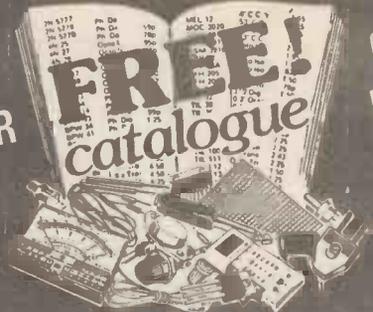

OUT  
NOW!

It's no secret!

... that there is a  
real difference at Cricklewood Electronics.

That's why you should never be without the **FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE**, for sheer variety, *competitive prices* and *service* from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your **FREE** copy now (no S.A.E. required). You have nothing to lose.

## CRICKLEWOOD ELECTRONICS LTD.

40 Cricklewood Broadway NW2 3ET

01-450 0995 & 01-452 0161

ALL MAJOR CREDIT CARDS ACCEPTED

Telex 914977

Phone or write today

## AFFORDABLE ACCURACY

Quality Multimeters from

# Cirkit



A  
comprehensive  
range of  
Analogue and  
(Pushbutton or  
Rotary  
Switched)  
Digital Models

### ANALOGUE

HM-102BZ — Illustrated above. 20kΩ/V DC.  
DC voltage range, 2.5-1000V; AC volts  
10-1000V; resistance, 10k-1MΩ; DC current,  
5-500mA + 10A; battery test and continuity  
buzzer ..... £12.50  
HM-1015 — Rugged, Pocket sized meter, for  
general purpose use ..... £7.50  
16 measuring ranges

Battery, Test Leads and Manual included with  
each model.

Please add 15%  
for VAT and  
70p for p&p

### DIGITAL

HC-7030  
0.1% Accuracy, Standard Model ..... £39.50  
HC-6010  
0.25% Accuracy, Standard Model ..... £33.50  
HC-5010T  
0.25% Accuracy, TR Test Facility ..... £39.50  
DM-105  
0.5% Accuracy, Pocketable ..... £21.50

All models have full functions and ranges and  
feature: 3½ digit 0.5" LCD display — low battery  
indication — auto zero & auto polarity — ABS  
plastic casing — DC AC 10amp range (not DM-  
105) — Overhead protection on all ranges —  
battery, spare fuse, test leads and manual.

Full details and specification from:

## Cirkit Distribution Ltd


Park Lane, Broxbourne, Herts, EN10 7NQ  
Telephone (0992) 441111 Telex 22478

TRADE ENQUIRIES WELCOME


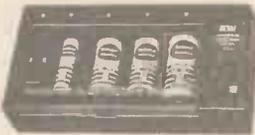
## UNIVERSAL NICAD CHARGER £6.95

WITH 4 RECHARGEABLE AA/HP7  
CELLS (TESTED & GUARANTEED)  
● CHARGES ANY COMBINATION  
PP3, AA, C & D CELLS



**NICADS**  
4 for £2 or 10 for £4.50

### BUTTON BATTERIES

AG3 7.87 x 3.6mm  
AG10 11.58 x 3mm  
AG12 11.58 x 4.2mm  
AG13 11.58 x 5.4mm  
4 for £1.60 or 10 for £3.

### SEALED LEAD ACID RECHARGEABLE BATTERY

6V 2.6A/Hr 132 x 60 x 32mm £9.95  
12V 2.6A/Hr £18.00

**DN/OFF OPTO-ISOLATOR** 20 Milli-second  
response, 6V 60mA lamp & cadmium photo-  
resistor housed in small metal can for PCB  
mounting. Will drive medium current relay.  
£1.20 each or 5 for £5.

**ULTRASONIC TRANSDUCERS**  
40kHz Matched pairs, transmitter/receiver. Per  
pair £4.20.

**BUZZER AND FLASHING LED ALARM** 12V  
housed in neat box with reset button. Used in  
car for belt-up or trafficator reminder etc., or  
anywhere a resettable alarm is required. High  
resistance trigger possible. £1.90 each or 5  
for £6.

### PCB KIT £5.95

4 pieces copper  
clad, circuit  
etchant, 2 pens,  
4 different  
sheet transfers,  
plastic tray  
& instructions.

Book 'How to Design &  
Make Your Own PCBs' £1.95



**ETCH RESIST PENS by STAEDTLER.**  
Fine tip 75p each or 2 for £1.20

### MINI-DRILL AND PRECISION TOOLS COMPLETE KIT—MAXICRAFT

Selection  
of buffer  
heads,  
abrasive  
discs,  
polishers  
& drills  
& chuck &  
collets  
42W, 18000 rpm, 9-16V, 1.5A. For model  
makers, engravers and electronic enthusiasts. In  
purpose made palette.  
£18.50



**NEON VOLTAGE TESTER/SCREWDRIVER**  
95p

**MAXICRAFT SOLDERING IRON** 10  
watt/12V ac/dc iron, specifically designed for  
fine circuit work and is capable of minimal use  
on average sized PCBs. The fine bit enables the  
user to delve into the most delicate of areas.  
£4.50. Replacement bits 70p each.

**TUNGSTEN CARBIDE BITS** 1mm ideal for  
glass fibre PCBs (¼" shanks) £1.20 each or 5  
for £5. Pack of 10 in case £8.95.

**SLOTTED OPTO-SWITCH**  
RS306-061 Infra-red source & sensor housed  
in slotted moulding. The 3.8mm slot permits  
beam to be broken, e.g. switching, counting,  
tape detection. Readily interfaced with TTL  
circuits. £1.90 each or 5 for £8.

ADD 80p p&p—GOODS SENT RETURN POST

## CROYDON DISCOUNT ELECTRONICS

40 Lower Addiscombe Road, Croydon CR0 6AA. Tel. 01-688 2950

## INDEX TO ADVERTISERS


B.K. ELECTRONICS.....	Cover III
BULL, J. & N. ....	Cover II
CIRKIT HOLDING .....	504
C.P.L. ELECTRONICS .....	450
CRICKLEWOOD ELECTRONICS .....	504
CROYDON DISCOUNT ELECTRONICS .....	504
ESR ELECTRONIC COMPONENTS .....	503
GREENWELD ELECTRONICS .....	473
I.C.S. INTERTEXT .....	489
LIGHT SOLDERING DEVELOPMENTS .....	489
LONDON ELECTRONICS COLLEGE .....	489
MAGENTA ELECTRONICS .....	452
MAPLIN ELECTRONICS .....	Cover IV
MARCO TRADING .....	450
M.J.R. WHOLESALE .....	450
OMNI ELECTRONICS .....	450
PHONOSONICS .....	450
RADIO COMPONENT SPECIALISTS .....	485
RODEN PRODUCTS .....	502
STEWART OF READING .....	451
T.J.A. DEVELOPMENTS .....	451
T.K. ELECTRONICS .....	451

# OMP POWER AMPLIFIER MODULES

\* PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE S.A.E. 28p STAMP FOR CURRENT LIST
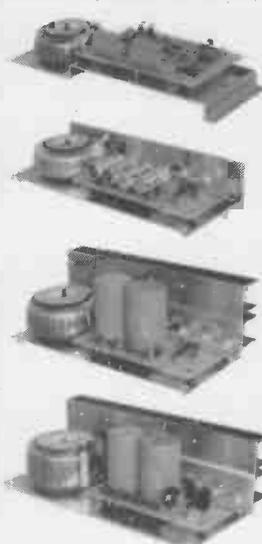
## OMP POWER AMPLIFIER MODULES

Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e. Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof. **Supplied ready built and tested.**



**OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 X 115 X 65mm. PRICE £33.99 + £3.00 P&P.**

**OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 X 123 X 60mm. PRICE PRICE £39.99 + £3.00 P&P.**

**OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 X 150 X 100mm. PRICE PRICE £62.99 + £3.50 P&P.**

**OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 X 147 X 102mm. PRICE PRICE £79.99 + £4.50 P&P.**

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.

**Vu METER** Compatible with any four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Forward biased logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 X 27 X 45mm. **PRICE £8.50 + 50p P&P.**

**LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.**



**POWER RANGE**  
**8" 50 WATT R.M.S. Hi-Fi/Disco.**  
 20 oz magnet. 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.  
**12" 100 WATT R.M.S. Hi-Fi/Disco**  
 50 oz. magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.

**McKENZIE**  
**12" 85 WATT R.M.S. C1285GP Lead Guitar/Keyboard/Disco.**  
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £29.99 + £3.00 P&P ea.  
**12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.**  
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £31.49 + £3.00 P&P ea.  
**15" 150 WATT R.M.S. C15 Bass Guitar/Disco.**  
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £57.87 + £4.00 P&P ea.  
**10" 60 WATT R.M.S. C1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.**  
 2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.99 + £2.00 P&P.  
**10" 200 WATT R.M.S. C10200GP Guitar/Keyboard/Disco.**  
 2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. PRICE £44.76 + £3.00 P&P.  
**15" 200 WATT R.M.S. C15200 High Power Bass.**  
 Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £62.41 + £4.00 P&P.  
**15" 400 WATT R.M.S. C15400 High Power Bass.**  
 Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £89.52 + £4.00 P&P.

**WEM**  
**5" 70 WATT R.M.S. Multiple Array Disco etc.**  
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £22.00 + £1.50 P&P. ea.  
**8" 150 WATT R.M.S. Multiple Array Disco etc.**  
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £32.00 + £1.50 P&P ea.  
**10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.**  
 1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £36.00 + £2.00 P&P ea.  
**12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.**  
 1" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £47.00 + £3.00 P&P ea.

**SOUNDLAB (Full Range Twin Cone)**  
**5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.**  
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 + £1.00 P&P ea.  
**6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.**  
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.  
**8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.**  
 1" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 + £1.50 P&P ea.  
**10" 60 WATT R.M.S. Hi-Fi/Disco etc.**  
 1 1/4" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. PRICE £16.49 + £2.00 P&P

## PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

**FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P.**  
**3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.**  
**SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.**



## BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. **FULLY GUARANTEED.**

**Control Unit** - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

**Indoor alarm** - Electronic swept freq. siren. 104dB output.

**Outdoor Alarm** - Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions. **SAVE £138.00** Usual Price £228.85

**BKE's PRICE £89.99 + £4.00 P&P**  
 ? Why buy a collection of self-assembly boards!

IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



## OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" X 15" X 12". Watts R.M.S. per cabinet. Sensitivity 1W. 1mtr. dB.

**OMP 12-100 Watts 100dB. Price £149.99 per pair.**  
**OMP 12-200 Watts 102dB. Price £199.99 per pair.**  
 Delivery: Securloc £8.00 per pair



## OMP 19" STEREO RACK AMPS



**Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. Three models (Ratings R.M.S. into 4ohms), Input Sensitivity 775mV**  
**MF200 (100 + 100)W. £169.00 Securicor**  
**MF400 (200 + 200)W. £228.85 Delivery**  
**MF600 (300 + 300)W. £299.99 £10.00**


## 1 K-WATT SLIDE DIMMER

- \* Control loads up to 1Kw
- \* Compact Size 4 3/4" X 1" X 2 1/2"
- \* Easy snap in fitting through panel/cabinet cut out
- \* Insulated plastic case
- \* Full wave control using 8 amp triac
- \* Conforms to BS800

\* Suitable for both resistive and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.  
**PRICE £13.99 + 75p P&P**
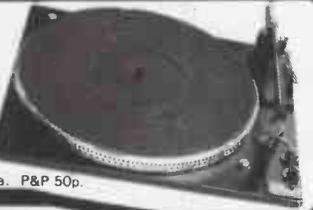
## BSR P295 ELECTRONIC TURNTABLE

\* Electronic speed control 45 & 33 1/3 r.p.m. \* Plus/Minus variable pitch control \* Belt driven \* Aluminium platter with strobed rim \* Cue lever \* Anti-skate (bias device) \* Adjustable counter balance \* Manual arm \* Standard 1/2" carriage fixings \* Supplied complete with cut out template \* D.C. Operation 9-14V D.C. 65mA  
**Price £36.99 - £3.00 P&P.**



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p.


## PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

**TYPE 'A' (KSN2036A) 3"** round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 40p P&P  
**TYPE 'B' (KSN1005A) 3 1/2"** super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P  
**TYPE 'C' (KSN6016A) 2" X 5"** wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P  
**TYPE 'D' (KSN1025A) 2" X 6"** wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P  
**TYPE 'E' (KSN1038A) 3 3/4"** horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P  
**LEVEL CONTROL** Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 X 85 mm. Price £3.99 + 40p P&P.
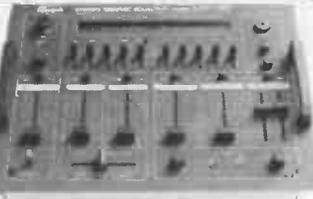
## STEREO DISCO MIXER


**STEREO DISCO MIXER** with 2 X 5 band L & R, graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following - 3 Turntables (Mag), 3 Mics, 4 Line, plus Mic with talk over switch. Headphone Monitor. Pan Pot. L & R. Master Output controls. Output 775mV. Size 360 X 280 X 90mm.  
**Price £134.99 - £3.00 P&P**



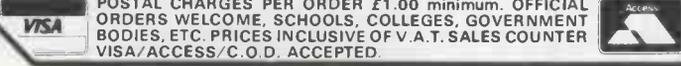
# B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.



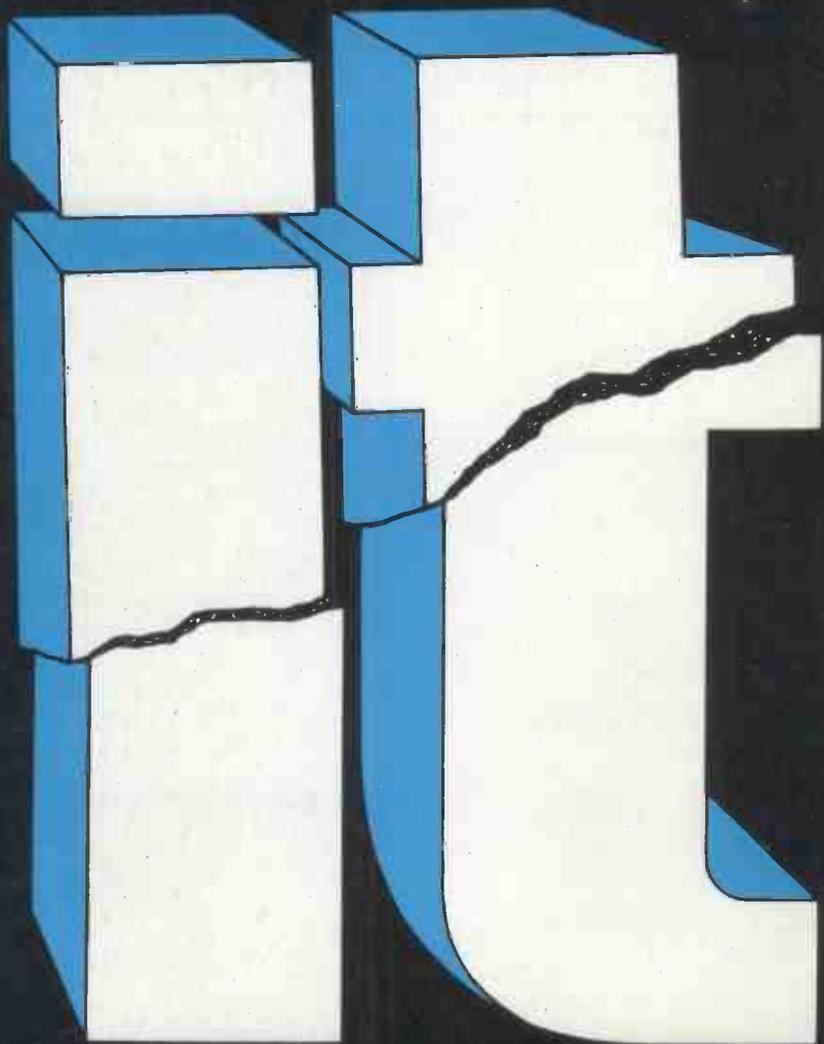**Lowest possible prices?  
Top quality components?  
Fast reliable service?  
Large range?**




**Maplin . . . . . We've cracked it.**

Pick up a copy of our new 1986 catalogue from most branches\* of W.H. Smith for just £1.45.  
Or post this coupon now, to receive your copy by post for just £1.45 + 40p p & p. If you live outside the U.K. send £2.50 or 11 International Reply Coupons. I enclose £1.85.

Name .....

Address .....

\*Some branches are now out of stock.

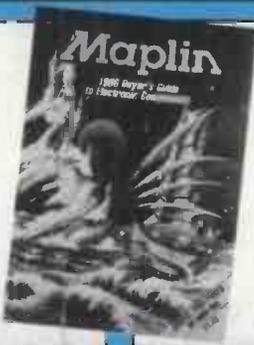

**MAPLIN ELECTRONIC SUPPLIES LTD.**

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: Southend (0702) 554161

**SHOPS**

- BIRMINGHAM Lynton Square, Perry Barr, Tel: 021-356 7292.
- LONDON 159-161 King Street, Hammersmith, W6.  
Telephone: 01-748 0926.
- MANCHESTER 8 Oxford Road, Tel: 061-236 0281.
- SOUTHAMPTON 46-48 Bevois Valley Road, Tel: 0703 225831.
- SOUTHEND 282-284 London Rd, Westcliff-on-Sea, Essex.  
Telephone: 0702-554000

*Shops closed all day Monday.*

EE/9/86