

EVERYDAY

SEPTEMBER 1987

ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

£1.20

Electronic Analogue/Digital Multimeter

**Personal Stereo
Amplifier**

**Car Overheating
Alarm**

**Burst Fire
Mains Controller**



Special Feature... Using a Multimeter

The Magazine for Electronic & Computer Projects

£1 BAKERS DOZEN PARCELS

Price per parcel is £1.00, but if you order 12 you get one extra free.
All the parcels listed below are brand new components. Unless marked s.h.

- 1 - 5 13 amp ring main junction boxes
- 2 - 5 13 amp ring main spur boxes
- 5 - 3 flush electrical switches
- 7 - 4 in flex line switches with neons
- 8 - 2 80 watt brass cased elements
- 9 - 2 mains transformers with 6V 1A secondaries
- 10 - 2 mains transformers with 12V 1/2A secondaries
- 11 - 1 extension speaker cabinet for 6 1/2" speaker
- 12 - 5 octal bases for relays or valves
- 13 - 12 glass reed switches
- 14 - 4 OCP 70 photo transistors
- 16 - 4 tape heads, 2 record, 2 erase
- 17 - 1 ultra sonic transmitters and 1 ditto receiver
- 18 - 2 15000 mfd computer grade electrolytics
- 19 - 2 light dependent resistors
- 20 - 5 different micro switches
- 21 - 2 mains interference suppressors
- 22 - 2 25 watt crossover units 2 way
- 23 - 1 40 watt 3 way crossover unit
- 28 - 1 6 digit counter mains voltage
- 30 - 2 Nicad battery chargers
- 31 - 1 key switch with key
- 32 - 2 humidity switches
- 33 - 2 aerosol cans of ICI Dry Lubricant
- 34 - 96 x 1 metre lengths colour-coded connecting wires
- 36 - 2 air spaced 2 gang tuning condensers
- 37 - 2 solid dielectric 2 gang tuning condensers
- 38 - 10 compression trimmers
- 41 - 6 Rocker Switches 10 amp mains SPST
- 43 - 5 Rocker Switches 10 amp SPDT Centre Off
- 44 - 4 Rocker Switches 10 amp DPDT
- 45 - 1 24 hour time switch mains operated (s.h.)
- 46 - 1 6 hour clock timeswitch
- 48 - 2 6V operated reed switch relays
- 49 - 10 neon valves - make good night lights
- 50 - 2 x 12V DC or 24V AC, 4 CO relays
- 51 - 1 x 12V 2C 0 very sensitive relay
- 52 - 1 12V 4C relay
- 53 - 2 mains operated relays 3 x 8 amp changeovers
- 55 - 1 locking mechanism with 2 keys
- 56 - Miniature Unselector with circuit for electric jigsaw
- 57 - 5 Dolls' House switches
- 60 - 5 ferrite rods 4" x 5/16" diameter aerials
- 61 - 4 ferrite slab aerials with L & M wave coils
- 62 - 4 200 ohm earpieces
- 63 - 1 Mullard thyristor trigger module
- 64 - 10 assorted knobs 1/2" spindles
- 65 - 5 different thermostats, mainly bi metal
- 66 - Magnetic brake - stops rotation instantly
- 67 - Low pressure 3 level switch
- 69 - 2 25 watt pots 8 ohm
- 70 - 2 25 watt pots 1000 ohm
- 71 - 4 wire wound pots - 18, 33, 50 and 100 ohm
- 73 - 4 3 watt wire wound pots 50 ohm
- 77 - 1 time reminder adjustable 1-60 mins
- 78 - 5.5 amp stud rectifiers 400V
- 85 - 1 mains shaded pole motor 1/2" stack - 1/2" shaft
- 86 - 2 5" ali fan blades fit 1/2" shaft
- 87 - 2 3" plastic fan blades fit 1/2" shaft
- 88 - Mains motor suitable for above blades
- 89 - 1 mains motor with gear box 1 rev per 24 hours
- 91 - 2 mains motors with gear box 16 rpm
- 93 - 4 11 pin moulded bases for relays
- 94 - 5 BTG valve bases
- 95 - 4 skirted B9A valve bases
- 96 - 1 thermostat for fridge
- 98 - 1 motorised stud switch (s.h.)
- 101 - 1 2 1/2 hours delay switch
- 103 - 1 16V mains power supply unit
- 104 - 1 14V mains power supply unit
- 105 - 1 5 pin flex plug and panel socket
- 107 - 1 5" speaker size radio cabinet with handle
- 109 - 10 1/2" spindle type volume controls
- 110 - 10 slider type volume controls
- 112 - 1 heating pad 200 watts mains
- 114 - 1 1W amplifier Mullard 1172
- 115 - Wall mounting thermostat 24V
- 118 - Teak effect extension 5" speaker cabinet
- 120 - p.c.b. with 2 amp full wave and 17 other recs
- 122 - 10 mtrs twin screened flex white p.v.c. outer
- 132 - 2 plastic boxes with windows, ideal for interrupted beam switch etc
- 155 - 3 varicap push button tuners with knobs
- 188 - 1 plastic box, sloping metal front, 16 x 95mm, average depth 45mm
- 241 - 1 car door speaker (very flat) 6 1/2" 15 ohm made for Radiomobile
- 243 - 2 speakers 6" x 4" 15 ohm 5 watt made for Radiomobile
- 266 - 2 mains transformer 9V 1/2A secondary split primary so OK also for 115V
- 267 - 1 mains transformers 15V 1A secondary p.c.b. mounting
- 330 - 2 6V 0.6V mains transformer .3A p.c.b. mounting
- 350 - 40 double pole leaf switches
- 365 - 1 700 660V 50hz metal cased condenser
- 453 - 2 2 1/2 in. 80ohm loudspeakers
- 454 - 2 2 1/2 in. 8ohm loudspeakers
- 463 - 1 mains operated relay with 2 sets c/o contacts
- 464 - 2 packets resin filler/sealer with cures
- 465 - 3 5A round 3 pin plugs will fit item 193
- 466 - 4 7 segment l.e.d. displays
- 470 - 4 pc boards for stripping, lots of valuable parts
- 473 - 1 5" 4ohm speaker with built in tweeter Radiomobile
- 480 - 1 3A double pole magnetic trip, saves repairing fuses
- 498 - 4 1000uf 25V axial electrolytic capacitors

TELEPHONE BITS

- Master socket (has surge arrester - ringing condenser etc) and takes B.T. plug £3.95
Extension socket £2.95
Dual adapters (2 from one socket) £3.95
Cord terminating with B.T. plug 3 metres £1
Kit for converting old entry terminal box to new B.T. master socket, complete with 4 core cable, cable clips and 2 BT extension sockets £11.50
100 mtrs 4 core telephone cable £8.50

COMPACT FLOPPY DISC DRIVE EME-101

The EME-101 drives a 3" disc of the new standard which despite its small size provides a capacity of 500k per disc, which is equivalent to the 3 1/2" and 5 1/4" discs. We supply the Operators Manual and other information showing how to use this with popular computers: BBC, Spectrum, Amstrad etc. All at a special snip price of £27.50 including post and VAT. Data available separately £2, refundable if you purchase the drive.

EVERLASTING BATTERIES!

Well not quite, but if you don't switch it on, the lithium battery has an almost indefinite shelf life, which makes it suitable for emergency, standby & similar applications, also for quartz clocks and instruments that draw only microscopic currents. The lithium battery we have is 3V and about as big and thick as 2p coin. Price 2 for £1 ref BD 558. Note these plug into DII socket our ref BD553.

3 POLE MODEL MOTOR

Will operate from as low as 1.5V and speed will increase steadily as the voltage is increased, at 9V however a governor takes over and the speed remains constant - and ideal motor for models. Size approx 28mm x 40mm easily reversible and with good length spindle 60p each our ref BM30.

CASSETTE STEREO TAPE HEADS

With mounting brackets and with tape guides pairs, one record/playback and the other erase £1 per ref BD541.

OPTO INTERRUPTER

Consists of a IR emitter mounted close to light dependent resistor when light or IR is interrupted the change of resistance can be made to switch or operate a relay - useful for counting, motor stopping etc. Price 2 for £1 ref BD545.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95 without case, metal case - £2.95, adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off's per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

Ex-Electricity Board
Guaranteed 12 months.

12 volt MOTORS BY SMITHS

Made for use in cars, etc. These are very powerful and easily reversible. Size 3 1/2" long by 3" dia. They have a good length of 1/2" spindle - 1/10 hp £3.45
1/8 hp £5.75 1/6 hp £7.50



SOUND TO LIGHT UNIT



Complete kit of parts for a three channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is pleasantly rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/2" sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £14.95 in kit form.

This Month's Snip

9" VDU OR MONITOR ideal to work with computer or video camera uses Philips black and white tube ref M24/308W. Which tube is implosion and X-ray radiation protected. VDU is brand new and has a time base and EHT circuitry. Requires only a 18V dc supply to set it going. It's made up in a lacquered metal framework but has open sides so should be cased (if you are handy with a drill and file you could make a case out of two of our 6 1/2" speaker cabinets). The VDU comes complete with circuit diagram and has been line tested and has our six months guarantee. Offered at a lot less than some firms are asking for the tube alone, only £18 plus £3 post. We also have some that failed the line test, again brand new but offered without guarantee at £8 plus £3 post. We do a kit for the 16V 2A psu to operate this monitor price is £3 our ref 3P26.

SLIDE SWITCHES

Sub miniature size only 10mm x 4mm single pole change over on/off. Price 5 for £1 ref BD553.

LOW VOLTAGE RELAY

OMRON 3.5V coil, plug in dill sockets, 5a c/o contacts. Brand new offered at a silly price 2 for £1 ref BD548.

POLARISED RELAY

Depending upon its direction of current as low 14 Ma makes this open circuit, so it could be used to protect delicate instruments or as an earth leakage, or reverse voltage trip etc. 2 for £1 ref BD549.

SLOTTED OPTO SWITCH

Infra red emitter and sensor mounted in slotted moulding, so that the emitter beam when broken makes a contactless switch, can be used in electronic ignition, speed sensing etc. etc. Price 2 for £1 ref BD545.

24hr TIME SWITCH

Beautifully made with West German precision. Just under 4" square with 15amp c/o contacts can be set anywhere around 24hr dial to the nearest 15 mins also with a override switch. Ref BP6 but hurry we have only 300. Price £8.

COMPUTERS

The Acorn "Electron" is used in many schools for games and serious jobs. Works into colour or Black and White TV. Proper price was £199, our Price, tested and working £45 + £3 post, tested but slightly faulty £36 + £3 post and lastly tested and not working £20 + £3 post. all are new and complete with: mains P.S.U., 300 page handbook, TV lead, and starter cassette. Full range of Software also in stock at very low prices.

TELEPHONE LEAD

3 mtrs long terminating one end with new BT, flat plug and the other end with 4 correctly coloured coded wires to fit to phone or appliance. Replaces the lead on old phone making it suitable for new BT socket. Price £1 ref BD552 or 3 for £2 ref 2P164.

POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, shop, work room etc. Makes you feel better and work harder - a complete mains operated kit, case included. £9.50 + £2 P&P.

J & N BULL ELECTRICAL
Dept. E.E., 250 PORTLAND ROAD, HOVE,
BRIGHTON, SUSSEX BN3 5QT

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £20 add £1 service charge. Monthly account orders accepted from schools and public companies. Access & B/card orders accepted. Brighton 0273 734648 or 203500.

NEW ITEMS

Some of the many described in our current list which you will receive with your parcel.

£2 POUNDERS*

- 2P120 - 1 combined clockwork switch and thermostat for boiler control
- 2P122 - 1 30a rotary switch, surface mounting with pointer knob
- 2P123 - 1 25a rotary switch, surface mounting, cover engraved, high, medium low and off
- 2P124 - 1 28kv .001mfd block condenser
- 2P127 - 1 30a bridge rectifier assembly on heat sinks
- 2P129 - 1 10amp motor 115V so supplied with adaptor for 230V
- 2P131 - 1 Crouzet motor 230V fits the Crouzet gearbox
- 2P132 - 1 ceiling heat-stak for fire warning or protection
- 2P133 - 1 Circuit breaker 20a, Crabtree ref C50
- 2P134 - 1 9V 500mA psu, plug into 13a socket
- 2P135 - 10m 10 conductor intercom cable
- 2P136 - 1 2 1/2kw element made for tangential blowers
- 2P137 - 1 Thermo couple, stainless steel tippec for measuring internal heat
- 2P138 - 1 Mains transformer 20V-0-20V 1a upright mounting
- 2P141 - 1 rechargeable battery D size (4 AH) solder tag ended
- 2P142 - 10m 4 pair intercom cable White PVC outer
- 2P144 - 1 mains operated relay with 4 x 8a c/o contacts
- 2P145 - 1 10,000 of 70V d.c. smoothing capacitor
- 2P146 - 1 7,800 of 150V d.c. smoothing capacitor
- 2P147 - 1 10w 100ohm live matching transformer
- 2P148 - 1 Technical information on 3" FDD refundable if you buy fdd
- 2P149 - 5 diff battery operated model motors
- 2P150 - 1 PSU chassis with all components for 24V 2A d.c. unregulated
- 2P151 - 1 Metal box 14 1/2" x 14" x 4" with lid add £2.00 post
- 2P152 - 1 Motor start capacitor 80uf 250V
- 2P153 - 1 Two station intercom unused but fits reject
- 2P154a - 1 Nicad charger - plug into 13a socket 5.2V 7UA output
- 2P154b - 1 Nicad charger - plug into 13a socket 6V 9VA output
- 2P155 - 1 Mains transformer giving 16, 17, 1E & 20V 60W
- 2P158 - 1 Oven thermostat with temp calibrated knob
- 2P159 - 1 9V 500mA cased with mains lead and output lead
- 2P160 - 1 13a plug adaptor fused takes 3 x 13a plugs
- 2P161 - 1 6" diagonal side cutters
- 2P162 - 1 Stereo Matrix PCB mounting deep/phasis K35
- 2P163 - 1 AC Working capacitor 12uf 60V AC or 1500V dc
- 2P163a - 1 AC Working capacitor 14uf 350V AC or 800V dc
- 2P164 - 3 Phone leads 3 mtrs long tags one end B.T. plug other end

£3 POUNDERS*

- 3P7 - 1 DC voltage, doubler or halver for 12V to 24V 12 to 6V 24 to 12V
- 3P8 - 1 24hr time switch Sangamo, new condition Guarantee 1 year
- 3P9 - 12V 500mA psu plugs in 13a socket
- 3P10 - 1 Mains transformer 50V 2A with 6.3 pilot light winding, upright mounting, fully shrouded
- 3P13 - 1 Noise filter to fit in mains lead of appliance up to 25a
- 3P15 - 1 waterproof case will take 200 watt transformer
- 3P16 - 1 signal box, 3 lamps on face plate of metal box size 5 1/2" x 3 1/2"
- 3P17 - 1 choke and starter to work 8" fluorescent tube at 125W
- 3P18 - 1 22V 3a mains transformer with bridge rect fitted on top panel
- 3P20 - 1 0-5a ammeter 3 1/2 ac/dc ex equipment
- 3P21 - 1 power factor correction condenser 35uf 350ac
- 3P22 - 1 200va - auto transformer 230 to 115V toroidal encapsulated £1.50 post
- 3P23 - 1 35V-0-35V tapped 20V-0-20V 100va
- 3P24 - 1 3" floppy disc for Amstrad etc.
- 3P25 - 1 7" Electricians pliers

£4 POUNDERS*

- 4P11 - 1 Car Radio aerial
- 4P12 - 50m low loss co-ax 75ohm + £1 post
- 4P13 - 3 Horsman time and set switches 15amp
- 4P14 - 1 150w mains transformer "C" core 43V 3.5A secondary
- 4P15 - 1 powerful motor 2" stack fitted with gearbox final speed 60rpm mains operated, could operate door opener etc.
- 4P17 - 1 Unselector 3 pole 25V, 50V coil standard size
- 4P18 - 1 Volt meter with digital display (DIGIMSOR)
- 4P19 - 1 12V dc motor will fit to gearbox 4P20
- 4P20 - 1 Gear train giving speed reduction

£5 POUNDERS*

- 5P86 - 1 Transformer upright mounting 230/240V primary 2 x 100 1a secondary
- 5P88 - 1 Transformer in waterproof metal box 24V 5A add £2 post
- 5P89 - 1 4 bank heating element each 2kw ideal contractor heater
- 5P90 - 1 18" long tangential blower with motor at one end
- 5P91 - 1 14" blower, motor in middle
- 5P92 - 10m Audio co-ax double screened 75ohm super low loss for TV
- 5P93 - 1 6" Alarm bell 24V dc or ac
- 5P94 - 1 Current transformer 14V out with 1a dc input
- 5P95 - 1 Vantage photo cell
- 5P97 - 1 Impedance matching transformer 0-4-5-8-160 ohm 100 add £150 post
- 5P98a - 1 0-90a ammeter for mounting outside control panel
- 5P98b - 1 0-180a ammeter for mounting outside control panel
- 5P99 - 1 Mains operated bi-polar centrifugal output size app. 5" x 1 1/2"
- 5P100 - 1 Mains splitter 45a switch 3 x 15a fused circuits
- 5P101 - 1 Model motor 1 rpm from 6V reversible

£7 POUNDERS*

- 7P1 - 1 Instant heat solder gun - mains with renewable tip and job light

£8 POUNDERS*

- 8P1 - 1 Charger transformer 10a upright mounting 230/240 primary 16v 10a secondary
- 8P2 - 1 6" underdome alarmbell suitable for a fire alarm or burglar alarm mains operated.
- 8P3 - 1 heat sink big powerful so ideal for power transmitter
- 8P5 - 1 1/2 hp motor 900 rpm capacitor run
- 8P6 - 1 24hr time switch - 2 on off 16a c/o contacts 3" x 3" x 1 1/2"
- 8P7 - 1 Silent sentinel invisible ray kit
- 8P8 - 1 Papst fan 3 1/2" x 3 1/2" x 1 1/2" 230V metal bodied

£10 POUNDERS*

- 10P13 - 1 reversible motor with gearbox 104rpm Parvalux
- 10P14 - 1 100a time switch 1 on/off per 24 hrs triggers ETI pair
- 10P15 - 1 Max demand meter 230 ac mains
- 10P16 - 1 powerful air mover 2 small type blowers with motor in middle
- 10P18 - 1 mains operated klaxon
- 10P19 - 1 12V 2A bell really loud, mains operated, in iron case + £5 post
- 10P21 - 1 super metal box size 19" x 20" x 7" deep lockable + £3 post
- 10P22 - 1 sensitive volt meter relay
- 10P23 - 1 fruit machine heart 3 fruit wheels each stepper motor operated
- 10P24 - 1 big panel meter face size 4 1/2" x 2 1/2" 200uA movement scaled 1-10
- 10P25 - 1 100W audio transformer 50-0-50V primary 8 ohm secondary
- 10P26 - 1 "Secretary" phone auto-dialler complete untested sold as such
- 10P29 - 1 12V engine cooling fan
- 10P30 - 1 instrument psu on pcb has 4 outputs. 12V/5V 6A/12V 5A/5V 5A
- 10P31 - 1 7 day time switch 16a c/o contacts sep switches for each day
- 10P32 - 1 68 rpm 1/6th hp motor reversible

£15 POUNDERS*

- 15P1 - 1 kit for 115V hi fi amp
- 15P2 - 1 kit for psu to supply one or two 15P1 amps
- 15P3 - 1 time switch battery or mains operated - 16a c/o contacts, 7 day programmable has 30hr reserve

£25 POUNDERS*

- 25P1 - 1 1500 PSI hydraulic pump 24V dc motor, made for operating aircraft under-carriage etc.

LIGHT CHASER KIT motor driven switch bank with connection diagram, used in connection with 4 sets of xmas lights makes a very eye catching display for home, shop or disco, only £5 ref 5P56.



EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

ABC





MEMBER OF THE ASSOCIATION OF PUBLISHERS

VOL 16 No.9 SEPTEMBER '87

The Magazine for Electronic & Computer Projects

ISSN 0262-3617

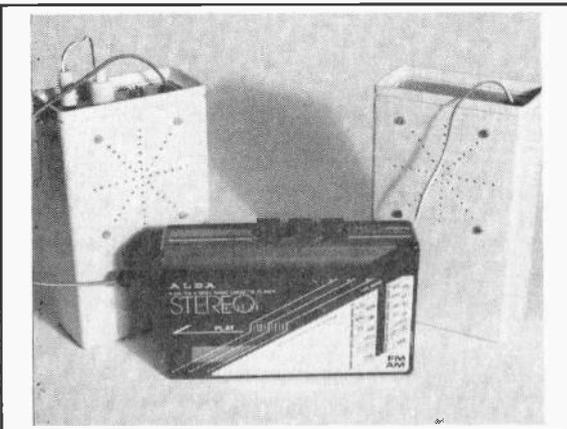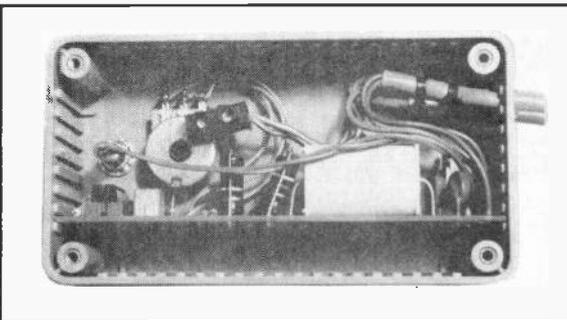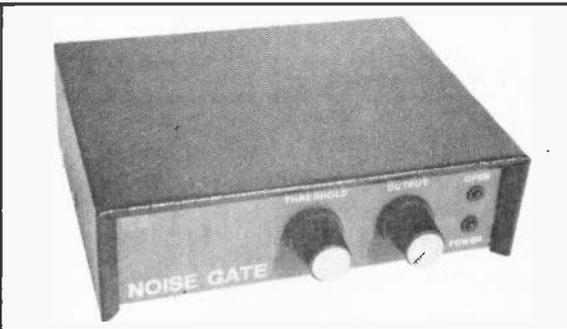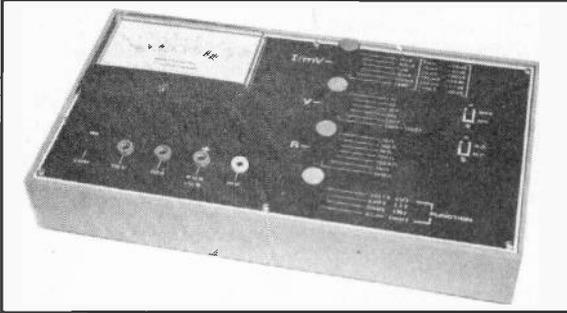PROJECTS... THEORY... NEWS...
COMMENT... POPULAR FEATURES...



© Wimborne Publishing Ltd 1987. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our October 1987 issue will be published on Friday, 18 September 1987. See page 469 for details.

Projects

- NOISE GATE** by Ian Coughlan 472
Amplify the sound not the noise
- PERSONAL STEREO AMPLIFIER** by Owen Bishop 476
Mobile mini amplifier for your personal player
- ELECTRONIC ANALOGUE/DIGITAL MULTIMETER** by Mark Stuart 490
Easy to build test meter for the workbench
- BURST FIRE MAINS CONTROLLER** by Andy Flind 500
Interference-free control of soldering irons, electric blankets and flashing lights
- SIMPLE NAND GATE AND FLIP-FLOP** 504
An "Exploring Electronics" project
- CAR OVERHEATING ALARM** by T. R. de Vaux-Balbirnie 508
You won't get overheated if you listen to this alarm
- LIGHT PEN** 512
Low-cost project for Beeb Micro owners

Series

- ROBOT ROUNDUP** by Nigel Clark 479
Investigating the world of robotics
- ON SPEC** by Mike Tooley BA 486
Readers Sinclair Spectrum page
- AMATEUR RADIO** by Tony Smith 488
New frequency allocations; Amateur Radio for the Handicapped
- ACTUALLY DOING IT** by R. A. Penfold 496
Making your own front panels
- EXPLORING ELECTRONICS** by Owen Bishop 504
Part Fifteen: Investigating logic circuits
- BBC MICRO** by R. A. & J. W. Penfold 512
Regular spot for Beeb fanatics

Features

- EDITORIAL** 471
- USING A MULTIMETER** by Mark Stuart 480
What to look for, its limitations and how to use it
- SHOPTALK** by David Barrington 484
Product news and component buying
- READERS' DISCOUNT SCHEME** 495
- NEWS** 498
What's happening in the world of electronics
- READERS' LETTERS** Your news and views 502
- MARKET PLACE** Free readers' buy and sell spot 506
- FOR YOUR ENTERTAINMENT** by Barry Fox 507
Time warp; Speak Easy; Bi-Grounding
- BOOK SERVICE** Our own service to readers of *EE* 514
- PRINTED CIRCUIT BOARD SERVICE** 516
- ADVERTISERS INDEX** 520
- SPECIAL OFFER** 489
Circular Movit R/C Kit

Readers' Services ● Editorial and Advertisement Departments

OMEGA ELECTRONICS

252A HIGH STREET, HARLESDEAN, LONDON NW14 4TD.
 TEL: 01-965 5748 MAIL ORDER & RETAIL SHOP
 TELEX: 265871 MONREF G Quoting 72: MAG31197

40008 CMOS	4068BP 0.13	4069UBP 0.13	7905 0.40	IC SOCKETS	8PIN 0.05
4001BP 0.13	4070BP 0.18	7912 0.40	14PIN 0.06	16PIN 0.08	18PIN 0.12
4002BP 0.13	4071BP 0.13	7915 0.40	20PIN 0.16	22PIN 0.17	24PIN 0.19
4006BP 0.28	4072BP 0.13	7918 0.40	28PIN 0.22	40PIN 0.25	
4007BP 0.13	4073BP 0.13	7924 0.40			
4008BP 0.28	4075BP 0.13	78L05 0.28			
4009BP 0.13	4076BP 0.37	78L08 0.28			
4010BP 0.16	4077BP 0.21	78L12 0.28			
4011BP 0.13	4078BP 0.13	78L15 0.28			
4012BP 0.13	4081BP 0.13	78L24 0.28			
4013BP 0.19	4082BP 0.13	78L05 0.40			
4014BP 0.28	4085BP 0.24	78L12 0.45	BRIDGE RECTIFIERS	W005 0.23	W01 0.26
4015BP 0.28	4088BP 1.00	7915 0.48	W02 0.32	W04 0.36	W06 0.41
4016BP 0.17	4093BP 0.16	LM317K 2.55	W08 0.45		
4017BP 0.27	4094BP 0.49	LM317T 1.50			
4018BP 0.27	4095BP 0.75				
4019BP 0.21	4096BP 0.65				
4020BP 0.29	4098BP 0.60				
4021BP 0.24	4099BP 0.37	ZENERS			
4022BP 0.29	4502BP 0.45	400MW BZ788 RANGE			
4023BP 0.13	4503BP 0.40	2V7 to 50V 0.5	TRANSISTORS	BC107 0.11	BC108 0.11
4024BP 0.23	4508BP 0.70	1.3W BZ785 RANGE	BC109 0.11	BC182 0.06	BC182L 0.06
4025BP 0.13	4510BP 0.30	3V3 50 75V 0.10	BC183 0.06	BC183L 0.06	BC184 0.06
4026BP 0.72	4511BP 0.45		BC184L 0.06	BC212 0.06	BC212L 0.06
4027BP 0.16	4512BP 0.34	COMPUTER IC'S	BC213 0.06	BC213L 0.06	BC214 0.08
4028BP 0.24	4514BP 0.61	4118 0.75	BC214L 0.06	BC237 0.10	BC238 0.10
4029BP 0.29	4515BP 0.61	4164 0.99	BC237 0.15	BC238 0.15	BC238L 0.10
4030BP 0.13	4516BP 0.34	41256 3.00	BC238L 0.15	BC246 0.10	BC547 0.10
4031BP 0.90	4518BP 0.34	41464 3.90	BC548 0.10	BC549 0.10	BC550 0.12
4035BP 0.90	4520BP 0.34	SPO256AL2 5.00			
4038BP 0.10	4522BP 0.62	Z80A CPW 1.80			
4040BP 0.30	4526BP 0.34	Z80A CTC 2.50			
4041BP 0.50	4528BP 0.30	Z80A DMA 7.50			
4042BP 0.23	4532BP 0.47	Z80A P10 2.50			
4043BP 0.31	4534BP 3.50	Z80A S10 5.00			
4044BP 0.31	4536BP 2.55				
4045BP 0.80	4538BP 0.39	RESISTORS 1/4 WATT			
4046BP 0.47	4539BP 0.36	IR-10M 0.01			
4047BP 0.39	4543BP 0.39				
4048BP 0.16	4555BP 0.31	MIN PRESETS			
4050BP 0.16	4556BP 0.40				
4051BP 0.31	4572BP 0.20	DIODES			
4052BP 0.31	4584BP 0.34	IN4001 0.03			
4053BP 0.31	4585BP 0.41	IN4002 0.03			
4054BP 0.52		IN4004 0.04			
4055BP 0.50	VOLTAGE REGULATORS	IN4006 0.06			
4056BP 0.55	7805 0.35	IN4007 0.06			
4060BP 0.51	7812 0.35	IN4148 0.02			
4063BP 0.55	7815 0.35				
4066BP 0.19	7818 0.35				
4067BP 1.00	7824 0.35				

PLEASE PHONE FOR UNLISTED ITEMS AS WE STOCK OVER 3000 ITEMS. PLEASE ADD 75p P&P + 15% VAT. OVERSEAS NO VAT ADD £2.00.



TOTAL ENERGY DISCHARGE ELECTRONIC IGNITION

IS YOUR CAR AS GOOD AS IT COULD BE ?

- ★ Is it **EASY TO START** in the cold and damp? Total Energy Discharge will give the most powerful spark and maintain full output even with a near flat battery.
- ★ Is it **ECONOMICAL** or does it "go off" between services as the ignition performance deteriorates? Total Energy Discharge gives much more output to fire lean fuel mixtures.
- ★ Has it **PEAK PERFORMANCE** or is it flat at high and low revs. where ignition output is marginal? Total Energy Discharge gives a more powerful spark from idle to the engines maximum (even with 8 cylinders).
- ★ Is the **PERFORMANCE SMOOTH**? The more powerful spark of Total Energy Discharge eliminates the near "misfires" whilst an electronic filter smoothes out the effects of contact bounce etc.
- ★ Do the **PLUGS AND POINTS** always need changing to bring the engine back to its best? Total Energy Discharge eliminates contact arcing and erosion by removing the heavy electrical load. The timing stays "spot on" and the contact condition does not affect the performance either. Larger plug gaps can be used, even wet or badly fouled plugs can be fired with this system.
- ★ **TOTAL ENERGY DISCHARGE** is a unique system and the most powerful on the market - 3.5 times the power of inductive systems - 3 times the energy and 3 times the duration of ordinary capacitive systems. Send for full technical details
- ★ **ALSO FEATURES** EASY FITTING, STANDARD/ELECTRONIC CHANGE-OVER SWITCH, STATIC TIMING LIGHT and DESIGNED IN RELIABILITY (14 years experience and a 3 year guarantee)
- ★ In **KIT FORM** it provides a top performance system at less than half the price of a comparable ready built unit. The kit includes: pre-drilled fibreglass PCB, pre-wound and varnished ferrite transformer, high quality 2µf discharge capacitor, case, easy to follow instructions, solder and everything you need to build and fit to your car. All you need is a soldering iron and a few basic tools.

TOTAL ENERGY DISCHARGE KIT £17.95 { Prices Include VAT
 ASSEMBLED READY TO FIT £23.90 { Add £1.00 P&P

ALSO AVAILABLE: Other Ignition systems and electronic car alarms

Order now or send for further details:

ELECTRONIZE DESIGN tel 021 308 5877
 2 Hillside Road, Four Oaks, Sutton Coldfield B74 4DQ

MULTIMETERS

BY **Cirkit**
Affordable Accuracy



DM105 £21.50

A meter to suit all pockets, including the one that holds the wallet! Full complement of ranges; 2V - 1kV DC, 200V-750V AC, 2mA-2A DC current and 2k-2M resistance range. Basic accuracy 0.5%.

A comprehensive range of quality Multimeters at very competitive prices

DIGITAL

All models feature full ranges, 3½ digit 0.5 in LCD, low battery indication, auto zero and auto polarity, strong ABS casing, 10 Amp range (except DM105), overload protection. Prices from £21.50 to £52.50. Battery, spare fuse, test leads and manual included with each model.

ANALOGUE

A choice of four meters with prices ranging from £5.50 to £21.00. All models include battery, test leads and manual.

Please add 15% VAT to all prices and 70p for post and packing.

Cirkit

Phone or write for full catalogue price £1.20 to
 Park Lane, Broxbourne, Herts EN10 7NQ.
 Telephone (0992) 444111.

Telex: 35565
 Tel: 0939-32763

MARCO TRADING

24 HOUR ANSWERING MACHINE

THE MALTINGS, HIGH STREET, WEM
 SHROPSHIRE, SY4 5EN.
 DEPT. EE9

ELECTRONIC COMPONENT MAIL ORDER COMPANY - ESTABLISHED 1972
 100+ PAGE CATALOGUE AVAILABLE - SEND £1 FOR YOUR COPY.

SEPTEMBER SPECIAL OFFER
HOBBY VICE ONLY £4.75 + 75p P&P + 15% VAT
 DIECAST ALUMINIUM WITH POLISHED JAWS.
 CAPACITY 50 MM.

STANDARD ABS BOXES

HIGH IMPACT ABS
 COLOUR: BLACK
 INTERNAL DIMENSIONS (MM)

A	B	C	1+	10
78	58	35	Box/MB1	£1.04 98p
95	71	35	Box/MB2	£1.14 £1.05
115	95	37	Box/MB3	£1.34 £1.24
140	90	55	Box/MB5	£1.98 £1.70
207	122	77	Box/MB4	£3.60 £3.40
213	142	57	Box/MB6	£2.70 £2.60

Twin Fluorescent Lamp
 12" Double Tube
 £5.50

ATTRACTIVE WHITE FITTING
 RUBBER FEET
 SPEX DIFFUSER ON/OFF SWITCH 3IN CABLE
 TRANSFORMERISED CIRCUITRY, KEYHOLE FIXING, 12V DC, 6W TUBE
 360 x 82 x 118MM

12V RECHARGEABLE UNIT
 10 x D SIZE NI-CADS (4 AH) ENCAPSULATED IN A BLACK PLASTIC CASE. FUSE HOLDER GIVES 12V OUTPUT CHARGED. EX-EQUIPMENT, FULLY GUARANTEED. 245 x 75 x 75mm
£5.99 + £1.85 P&P + 15% VAT

CHARGING UNIT FOR THE ABOVE 12V UNIT
 Manufactured by Saft, these chargers are available for the above battery packs (as advertised in the May issue of "What Video" - page 20). The chargers are stated as "fast charge units" but, by getting the life of the packs, we have modified them to a standard charging rate. Full charge of the packs is obtained after 10-12 hours (overnight) charging. Supplied complete with mains lead and charging lead fitted with a 4 pin plug (if plug version available upon request). Although in equipment, these chargers are fully repaired and guaranteed.
 Dimensions: 335 x 750 x 150mm.
 NI-PH £15 6-PH £18
 £1.85 P&P + 15% VAT

ELECTRONIC BUZZERS

MINIATURE 6V or 12V
 AUD/BUZ/6V - 75p
 AUD/BUZ/12V - 75p
 PIEZO ELECTRIC SUPER SLIM
 AUD/BUZ/P12 - 75p
 MUSICAL SEVEN AMERICAN TUNES
 AUD/BUZ/MUS/LMB7 - £2.30
 PIEZO ELECTRIC SIREN
 AUD/SIR/SP12 - £5.95

ELECTRONIC SIREN
 AUD/SIR/ELT - £7.50

ELECTRET MICROPHONE INSERT
 10MM DIAM 6.5MM THICK (3V-10V (5V TYP.))
 600 OHM 20-1200 HZ
 AUD/MIC/1 - 60p

PORTABLE GAS SOLDERING IRON
£14.50
 SPARE TIPS £4.50
 SIZE 2.4, 3.2 & 4.8mm

BATTERY CHARGER
 SUITABLE FOR AAA, AA, C, D AND PP3 NI-CAD BATTERY CHARGING. **£4.50**

NI-CAD BATTERIES
 AAA-£1.25 (10+ £1.20 each)
 AA-90p (10+ 85p each)
 C-£2.10 (10+ £1.90 each)
 D-£2.50 (10+ £2.20 each)
 PP3-£4.10 (10+ £3.30 each)

SUB-MINIATURE TOGGLE SWITCHES

HIGH QUALITY SOLDER TERMINALS. 240V 2A
 MOUNTING HOLE 5.2MM 1+ 10+
 SPST (2 TAGS) 8x5x7 55p 53p
 SPDT (3 TAGS) 8x5x7 80p 67p
 DPDT (6 TAGS) 8x7x7 65p 62p

MINIATURE TOGGLE SWITCHES
 SOLDER TERMINALS. 240V 1A MOUNTING HOLE 6.2MM
 SPST (2 TAGS) 13x9x8 50p 48p
 SPDT (3 TAGS) 13x9x8 55p 53p
 DPDT (6 TAGS) 13x9x12 55p 55p
 SPDT CENTRE OFF 13x9x8 60p 58p
 DPDT CENTRE OFF 13x9x12 66p 62p

SOLDER AT A RIDICULOUSLY LOW PRICE!
 A 500g REEL OF 22 SWG MULTI-CORE SOLDER 60% TIN 40% ALLOY. NON-CORROSIVE
ONLY £4.99 (10 + £3.75)

DESOLDERING PUMP
£2.99

ANTEX SOLDERING
 25W XS IRON £6.00
 18W CS IRON £5.90
 15W C IRON £5.70
 ST4 STAND £2.20
 SPARE BITS £1.20
 ELEMENTS FROM £3.20
 DIGITAL TEMPERATURE CONTROLLED STATION TCSV-DE72.50

GREENWELD

ELECTRONIC COMPONENTS

443D Millbrook Road, Southampton
SO1 0HX. Tel. (0703) 772501/783740

All prices include VAT; just add 60p P&P
(£2 sale items)
Min Access order £5. Official
orders from schools etc. wel-
come — min invoice charge £10.
Our shop has enormous stock of components and is open
9-5.30 Mon-Sat. Come and see us!!



1987 CATALOGUE

Out now!! Bigger and better than ever —
80 pages packed with components and
equipment, from humble resistors to high
tech scopes! Bargain List, Order Forms
and £1.50 Discount Vouchers all included
for just £1.00 inc. post.

ENTERPRISE

SIXTYFOUR


Although we have now sold out of the
complete computers and Z601 boards,
we do have the following:

Z657 As Z601 (see previous ads for
details) complete, but probably not fully
functional (customers returns). Supplied
with demo cassette, 2 booklets, + com-
prehensive data & cct..... **£12.00**
Z658 As above, but NICK or DAVE chip
and ROM missing..... **£9.00**

LOGIC PROBE

For TTL, CMOS etc. LED and sound
indication Pulse enlargement capability
allows pulse direction down to 25nsec.
Max f = 20 MHz 4-16V. I/P Z:1M £9.99

SOLDER SPECIAL!!!

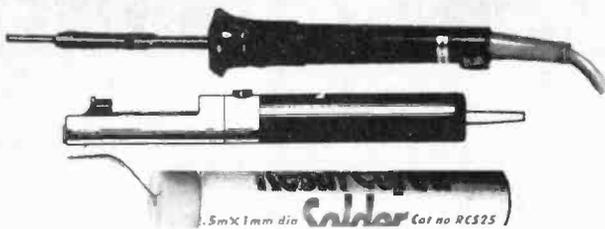

- ★ 15W 240Vac soldering iron
- ★ High power desolder pump
- ★ Large tube solder

ALL
FOR
£7.95

NEW THIS MONTH

CREAM DISPENSER

Z801 Coin operated machine for dis-
pensing hand cream. Cabinet 620 x 365
x 200mm, wt 10kg, contains coin mech,
PCB, counter, pump mech consisting of
high torque geared 6V motor driving cam
that pumps cream, and sensing compon-
ents, all powered by internal 6V 2.6A
rechargeable battery..... **£15 + £5 carr.**

SPEECH CHIP

Z733 SP0256A + index chip + ULA chip
as used in Currah micro-speech. Cct and
info for using SP0256 with Spectrum,
ZX81, BBC, VIC & C64. No info on other
2 chips. All 3 for..... **£3.00**

TELETEXT + PANELS

Z622 Teletext Unit. Keypad T100 man-
ufactured for the US market, hence 120V
ac supply (but Tx can easily be changed
for 240V model). Chassis with Rx/de-
coder circuitry, Mullard VM6700 module,
channel display, i/p & o/p skts. Believed
to be new & working, but no data. Size
410 x 250 x 60mm..... **£15.00**

Z620 68000 Panel. PCB 190 x 45 be-
lieved to be from ICL's 'One per Desk'

AUTO DIALLER

Sloping front case 240 x 145 x 90/50
contains 2 PCB's: One has 4 key-pads
(total 54 switches) + 14 digit LED display,
2 x ULN2004, ULN2033 & 4067; the
other has 12 chips + 4 power devices etc.
Case contains speaker. 8 core cable 2m
long with plug. For use with PABX. **£9.00**

COIN OPERATED MECHANISM

Made by Coin Controls, this will accept
various size coins by simple adjustment
of 4 screws. Incorporates various secu-
rity measures — magnet bent coin release
etc. Microswitch rated 5A 240V. Front
panel 115 x 64. Depth 130mm. Cost
£10.85..... Our price **£4.00**

computer containing MC68008P8 (8MHz
16/8 bit microprocessor, + 4 ROM's, all
in skts; TMP5220CNL, 74HCT245, 138,
LS08, 38 etc..... **£5.00**

Z625 32k Memory Board. PCB 170 x
170 with 16 2kx8 6116 static RAM's.
Also 3.6V 100mA memopack nicad, 13
other HC/LS devices, 96W edge plug, 8
way DIL switch, R's, C's etc..... **£4.80**

Details of other similar PCB's in latest list.

sinclair

MICROVISION

We have a quantity of these units in
varying states. From labels attached to
some of the PCB's it seems after assem-
bly on the production line they did not
function correctly. No attempt has been
made to repair them, though — instead
the following parts were removed:

- a) RF Tuner
- b) Vol control & switch
- c) ZN401E chip

Z666 2 PCB's in good condition + 2
CRT's + comprehensive data (replaces
Z555)..... **£6.95**
Z556 PCB in good condition with CRT
that has been removed, but maybe repair-
able. Conductive paint (15ml bottle
£3.45) will probably be needed to remake
contacts..... **£3.95**

Z558 CRT in 'as seen' condition —
possibly repairable..... **£2.00**
Z559 PCB in good condition without
CRT..... **£2.50**

Z560 Circuit diagram and notes: 7 pages
detailing tech. spec., description, cct op-
eration, fault diagnosis & repair, aid to
fault-finding chart, picture set up proce-
dure, PCB layout, info on the various
possibilities..... **£2.00**

RF Tuner **£6.95**; ZN401 chip **£9.95**;
Vol control + switch with knob **£1.00**

JUST ARRIVED!!

A major electronic distributors disconti-
nued lines, all being sold off at **LESS THAN**
1/2 PRICE!!—Boxes, cases, connectors,
LED's switches, DIP boards, cable ties
etc. All goods detailed in a 16 page
supplement available now **FREE**.

SPEAKERS

Z578 Sub-min speaker 30 x 30 x 3mm
thick by Fuji. 16R 0.4W. 60p ea; 10
£3.70; 25 £7; 100 **£22**; 1000 **£180**.
Z575 70 x 45mm 45R 0.5W 55p ea; 10
£3.30; 25 **£6**; 100 **£20**

SOLDER

500g reels resin cored. 18g..... **£5.95**
500g reels resin cored 22g..... **£7.95**

SUMMER SALE

MUST END SEPT 12th!!

SEND FOR YOUR FREE SALE LIST NOW!!

Up to 66% off our already low, low prices!!

Dozens of **half price** items!!

But stocks are limited, so it's first come, first served!

ORDER NOW to be sure of your share!!

Our SALE list and Bargain Lists are **FREE!!**

Our 80 page Catalogue costs just £1, with vouchers worth £1.50.

ALL BELOW ARE SALE ITEMS: MIN ORDER VALUE £10 + £2 POST

1/2 PRICE PANELS

Z914 1W Mono Amp.....	75p
Z915 1W Stereo Amp.....	£1.75
Z916 Am Tuner.....	75p
Z925 Relays.....	95p
Z926 Relay/Triac.....	92p
Z927 Reeds.....	30p
Z918 Inverter.....	£1.25
Z919 Inverter.....	£1.10
Z912 RF Panel.....	75p
Z910 RF Panel.....	75p
Z911 RF Panel.....	35p
Z913 RF Panel.....	35p
Z942 Joystick Interface.....	£1.00
Z974 Mixer Amp.....	£1.25
Z469 10W Amp Panel.....	£1.25
Z955 'Simon' Panel.....	50p
Z497 AM/FM Tuner.....	£6.45

7 SEG DISPLAYS—
MAN6740 40p; 10/£3.00
Others on P.78 of Cat. 30p; 10/£2.00;
100/£15.

FIBRE OPTICS—66% OFF!!

20m coils 1mm core—
single **£4.00** **£2.00**
twin **£6.00** **£2.00**

COMPUTER BOOKS—up to 90%

off!! **£9.95**, **£6.95**, **£5.95**
Now 10 for **£6!**

UHF Modulator 50% off!
Aztec UM1286 **£6.00** **£3.00**

1/2 PRICE PACKS

K547 Zener diodes.....	£4.50	£2.25
K544 Mullard polyesters...	£4.75	£2.35
K556 Fuseholders.....	£2.00	£1.00
K557 Terminal strips.....	£2.40	£1.20
Z525 Vero offcuts.....	£3.80	£1.90

25% OFF PACKS

K548 Tantalum caps.....	£6.50	£4.85
K549 Variable caps.....	£5.75	£4.30
K546 Mica/ps/cer caps.....	£2.75	£2.05
K554 Thermistors.....	£8.00	£6.00
K555 Fuses.....	£3.95	£2.95
K538 Diodes.....	£2.50	£1.85
K541 PCB Panels.....	£7.00	£5.25
K542 Reed Relays.....	£4.30	£3.20
K530 Polyesters.....	£3.95	£2.95
K518 Disc Ceramics.....	£1.00	75p
K503 Wirewound Resistors	£2.00	£1.50
K505 Pots.....	£1.70	£1.25
W4700 Push button banks	£2.95	£2.20
K526 Heatsinks.....	£5.50	£4.10
K527 Hardware.....	£4.00	£3.00
K534 Sleeve Pack.....	£1.00	75p
K536 74 Series Pack.....	£4.00	£3.00
K537 I.C. Pack.....	£6.75	£5.05
K538 Diode Pack.....	£2.50	£1.85
K539 L.e.d. Pack.....	£5.95	£4.45
K540 Resistor Pack.....	£2.50	£1.85
K535 Spring Pack.....	£1.70	£1.25
K524 Opto Pack.....	£3.95	£2.95
K525 Preset Pack.....	£6.75	£5.05
K528 Electrolytic Pack.....	£3.95	£2.95
K531 Precision resistors...	£3.00	£2.25

K532 Relays.....	£6.00	£4.50
K517 Transistors.....	£2.75	£2.05
K523 Resistors.....	£2.50	£1.85
K520 Switches.....	£2.00	£1.50

'NEWBRAIN' PANELS

Z494 Motherboard microprocessor
panel 265 x 155mm. Complete PCB for
computer. Z80, char EPROM, etc. 68
chips altogether + other associated com-
ponents, plugs, skts, etc. **£4.00**

Z495 RAM panel. PCB 230 x 78mm
with 14 x MM5290-2 (4116) (2 missing)
giving 28k of memory. Also 8 LS chips.
These panels have not been soldered, so
chips can easily be removed if
required. **£3.75**

Z679 Keyboard. 62 keys on ally chassis
260 x 90mm. No PCB **£6.50**

'NEWBRAIN' PSU

BRAND NEW Stabilized Supply in heavy
duty ABS case with rubber feet. Input
220/240V ac to heavy duty transformer
via suppressor filter. Regulated DC out-
puts: 6.5V @ 1-2A; 13.5V @ 0.3A; -12V
@ 0.05A. All components readily acces-
sible for mods etc. Chunky heatsink has 2
x TIP31A. Mains lead (fitted with 2 pin
continental plug) is 2m long. 4 core
output lead 1.5m long fitted with 6 pole
skt on 0-1" pitch. Overall size 165 x 75 x
72 mm.

£4.75 ea 10 for **£32**

SCOPES!
5% OFF
ALL MODELS

10% OFF
all ANTEX
PRODUCTS!!

10% OFF
all VERO
PRODUCTS!!

Full details of all sale items in
Catalogue/Bargain Lists

BI-PAK BARGAINS

RESISTORS

Pak No	Qty	Description	Price
VP1	300	Assorted Resistors mixed values & types	£1.00
VP2	300	Carbon Resistors 1/2, 1/4, 1/8 watt pre-formed, mixed	£1.00
VP3	200	1/8 watt Min. Carbon Resistors mixed values	£1.00
VP4	200	1/2-1 watt Resistors mixed values & types	£1.00
VP16	50	Wirewound Resistors mixed watt values	£1.00
VP112	1	Sub Resistance Box, 36 values 5ohms - 1Kohm	£4.75
VP140	50	Precision Resistors 1% Tol.	£1.00
VP181	100	1 and 2 watt Resistors, assorted values	£1.00

CAPACITORS

VP5	200	Assorted Capacitors, all types	£1.00
VP6	200	Ceramic Capacitors, Min. mixed values	£1.00
VP8	100	Mixed Ceramic Disc, 68pF-015pF	£1.00
VP9	100	Assorted Polyester/Polystyrene Capacitors	£1.00
VP10	50	C280 Capacitors, Metal foil, mixed values	£1.00
VP11	50	Electrolytics, all sorts	£1.00
VP12	40	Electrolytics 47mf-150mf mixed volts	£1.00
VP13	30	Electrolytics, 150mf-1000mf mixed volts	£1.00
VP15	25	.01/250V Min. Layer Metal Caps	£1.00
VP148	25	Solid Tantulum Caps. mixed values	£1.00
VP180	25	Tantulum Bead Caps. assorted values	£1.00
VP182	4	1000uf 50v Electrolytics	£1.00
VP182	30	Min. Electrolytics mixed values 47mf-1000mf 6-16v	£1.00
VP193	6	Sub Min. Electrolytics, 2x1000/2200/3300mf 10-16v	£1.00

74 SERIES SALE "ROCK BOTTOM" PRICES

VP223	50	Asst 74 TTL IC's "ALL GATES" new & coded our mix 7400-7453	£8.00
VP224	100	Asst 74 TTL IC's "ALL GATES" new & coded our mix 7400-7453	£10.00
VP7413	4	7413 Dual NAND Schmitt Trigger, 4 input	£1.00
VP7440	4	7440 Dual 4-Input, Positive-Nand Buffer	£1.00
VP7470	4	7470 And-gated Positive-edge-triggered Flip-Flop with preset	£1.00
VP7480	4	7480 Dated full Adder	£1.00
VP7481	4	7481 16-Bit Random Access memories	£1.00
VP7490	4	7490 Decade Counter	£1.00
VP7491	4	7491 8-Bit Shift Register	£1.00
VP7492	4	7492 Divide by 12 Counter	£1.00
VP7493	4	7493 4-Bit Binary Counter	£1.00
VP7494	4	7494 4-Bit Shift Register	£1.00

VP7495	4	7495 4-Bit Shift Register	£1.00
VP74111	4	74111 Quad J-K Master Slave, Flip-Flop	£1.00
VP74141	4	74141 BCD-Decimal Decoder/Driver	£1.00
VP74151	4	74151 1 of 8 Data Selectors/Multiplexers	£1.00
VP74153	4	74153 Dual 4 line to 1 line Data Selectors/Multiplexers	£1.00
VP74164	4	74164 8-Bit Parallel Output Serial Shift Registers	£1.00
VP74167	4	74167 Synchronous Decade Rate Multipliers	£1.00
VP74174	4	74174 Hex D-Type Flip-Flops	£1.00
VP74181	4	74181 Arithmetic Logic Units/Function Generators	£1.00
VP74193	4	74193 Sync. Up/Down Dual Clock Counters, Binary clear	£1.00
VP74279	4	74279 Quad S-R Latches	£1.00

BPX6 1 TTL Data Book 74 Series, including "LS". Complete with Pin out Diagrams, 7400-74870, TTL Interchangeability Guide, Function Selection Guide and Explanation of Function Tables. "ND VAT" .. £1.00

TOOLS

VP246	1	25 watt High Quality Low Cost Soldering Iron 240v AC Long life Element, 1.7m lead	£3.50
VP247	1	15 watt "Lightweight" High Quality Low Cost Soldering Iron 240v AC, 1.7m lead	£3.50
VP248	1	High Suction Desoldering Pump, teflon nozzle, Auto Eject, Heavy duty return spring	£4.00
VP249	1	High Quality Soldering Iron Stand, Cast iron base, Tip cleaning sponge	£4.00
VP250	1	Long Finger Grip, soldering aid, Heavy metal base, Serrated jaws with rev. tweezers action, ideal for holding small components, Fully adjustable	£3.00
VP251	1	Multi-tester, Pocket size, 18 ranges, 10000 ohms/VDC-4000 ohms/VAC, Fuse and diode protection, Mirrored scale, Leads with 2mm plugs, Batt. & instructions Inc.	£8.50
VP252	1	Multi-tester & Transistor Tester, 20000 ohms/V, 19 ranges Audio output, Test term. Fuse & Diode protection, Test leads & Transistor test leads, Batt. & Instructions, Mirrored scale, Size 147 x 97 x 45 mm	£18.80
VP253	1	Digital Multi-tester, 3 1/2 digit, Side switches for single-hand operation, High quality construction tough ABS body, Fully guaranteed, Overload protection, Input Imped. 10Mohms, 19 ranges Incl. 10ADC plus diode & transistor test, Accuracy 0.8%, Complete with leads, Batt. and manual, Size 145 x 70 x 31 mm	£35.00
VP254	1	250 grams Etchant Granules (Ferric chloride) makes 1 pint	£1.00
VP255	1	Etching Pen, Etch resistant, Spare tip, Blue	£1.00
VP256	1	PCB Mini Drill, Operating voltage 5-14V DC + 1mm twist drill and collar for .8 to 1.2mm drills and tommy bar Inc.	£1.00
VP257	1	Pack of 3 Twist Drills, 1, 1.5, 2mm for PCB Mini Drill	£1.00
VP258	1	Multicore Solder, 5m total, 18 and 22 S.W.G.	£1.00
VP259	1	PCB Holder, Fully adjustable from 0-320mm wide and to any angle, Complete with iron stand and sponge, Strong metal construction with rubber feet, Very High Quality	£15.00

MISC

VP223A	6	Tag Boards, 36 way Paxaline	£1.00
VP225	20	DIN Plugs, plastic 2-8 pin 180°/240°/360° mixed	£2.50
VP226	20	DIN Chassis Sockets, metal 2-8 pin 180°/240°/360° mixed	£2.50
VP227	18	DIN In-line Sockets, plastic 2-8 pin 180°/240°/360° mixed	£3.00
VP228	10	C15 Computer Cassette Tapes, leadless	£5.00
VP229	10	C80 Cassette Tapes, 2 x 30 min, low noise	£6.00
VP230	10	C90 Cassette Tapes, 2 x 45 min, low noise	£6.00
VP231	1	Cassette Head Cleaner Tape, non abrasive, in case	£1.00
VP232	1	Cassette Head Cleaner/Demagnetizer, in case	£2.00
VP233	1	Revolving Cassette Rack, holds 32, smoky perspex	£2.50
VP234	1	Demagnetizer Curved Probe, 240v AC	£3.00
VP235	1	VHS Video Head Cleaner Cassette, Wet type	£4.00
VP236	1	Betamax Video Head Cleaner Cassette, Wet type	£4.00
VP237	1	Universal Ni-Cad Battery Charger, AA-HP11-HP2-PP3	£6.00
VP238	4	AA Ni-Cad Batteries, 1.25v 500mAh C/R mA	£4.00
VP239	2	C-HP11 Ni-Cad Batteries, Rechargeable	£3.50
VP240	2	D-HP2 Ni-Cad Batteries, Rechargeable	£4.00
VP241	2	DRP12 Light Dependant Resistor	£1.50
VP242	4	Tri-colour LED's, 5mm Dia, 5mA, 2v R.G.Y.	£1.00
VP243	3	Tri-colour LED's, Rectangular 5mm R.G.Y.	£1.00
VP244	1	High Power Piezo Electric Siren, Emits Earpiercing warbling sound, Ideal alarms, White plastic body with mounting bracket, Power 12v DC 150mA, Output 100db (A) at 1m typ, Freq. 2.5KHz, Size 57 x 42 x 37 mm	£6.00
VP245	1	Automatic Lighting Switch, Photo electric, weatherproof, Switches lights or equipment "ON" at dusk "OFF" at dawn, Loads up to 3A at 240v AC, Size 50 x 45 mm	£5.00

SPEAKERS OFFER. SAVE UP TO 50%

VPL001	1	8 x 4" Elliptical 8 ohms 4W RMS Freq. Res. 135-10000 Hz General purpose Speaker, Gauss 7000	£2.50
VPL003	1	7 x 5" Elliptical 8 ohms 4W RMS Freq. Res. 90-10000 Hz Speaker, Centre HF cone, Gauss 7500	£3.00
VPL005	1	8 x 5" Elliptical 8 ohms 6W RMS Speaker, Freq. Res. 45-18000 Hz, Gauss 9000, Wide range Air suspension, sponge edge, Centre HF cone	£4.50
VPL006	1	9 x 6" Elliptical 8 ohms 10W RMS Speaker, Freq. Res. 60-10000 Hz, Gauss 10000, Centre HF cone	£4.50
VPL018	1	2 1/2" Transducer, Waterproof Speaker, Polyester film Diaphragm, Moisture res. 8 ohms 300mW RMS Freq. Res. 20-20000 Hz £1.00	£1.00
VPL018B	1	4" Round 8 ohms 1.2W RMS Freq. Res. 190-10K Hz, General purpose speaker, 100 x 100 x 35mm	£1.00
VPL022	1	5" Round 8 ohms 3W RMS Freq. Res. 90-9500 Hz, Car/General purpose Speaker, Gauss 7500, 133 x 42 mm	£3.00
VPL025	1	5 1/2" Round 8 ohms 15W RMS Wide range speaker, Freq. Res. 50-15000 Hz, Air suspension, Centre HF Cone	£7.00
VPL025A	1	6" Round 8 ohms 5W RMS Freq. Res. 70-2000 Hz, General purpose Speaker, Gauss 9000	£2.50
VPL029	1	8" Round 8 ohms 10W RMS Freq. Res. 45-16000 Hz, Wide Range Speaker, Centre HF cone	£4.00

BI-PAK

Send your orders to Dept EE BI-PAK PO BOX 6 WARE, HERTS

TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED, TEL 0763-48851, GIRO 388 7006, ADD 15% VAT AND £1.50 PER ORDER POSTAGE AND PACKING.



Use your credit card. Ring us on 0763 48851 NOW and get your order even faster. Goods normally sent 2nd Class Mail.




Remember you must add VAT at 15% to your order. Total Postage add £1.50 per Total order.

The Archer Z80 SBC

The SDS ARCHER - The Z80 based single board computer chosen by professionals and OEM users.

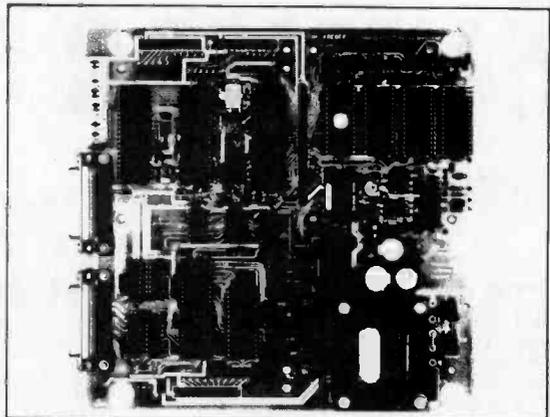
- ★ Top quality board with 4 parallel and 2 serial ports, counter-timers, power-fail interrupt, watchdog timer, EPROM & battery backed RAM.
- ★ **OPTIONS:** on board power supply, smart case, ROMable BASIC, Debug Monitor, wide range of I/O & memory extension cards.



The Bowman 68000 SBC

The SDS BOWMAN - The 68000 based single board computer for advanced high speed applications.

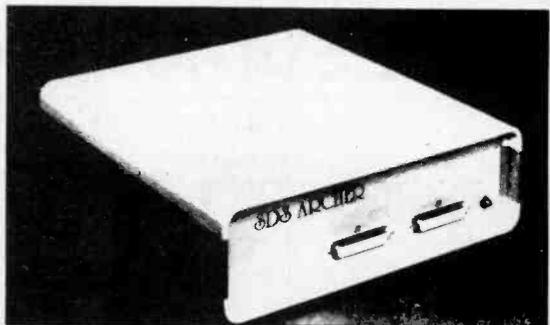- ★ Extended double Eurocard with 2 parallel & 2 serial ports, battery backed CMOS RAM, EPROM, 2 counter-timers, watchdog timer, powerfail interrupt, & an optional zero wait state half megabyte D-RAM.
- ★ Extended width versions with on board power supply and case.



Sherwood Data Systems Ltd

Sherwood House, The Avenue, Farnham Common, Slough SL2 3JX. Tel. 02814-5067

OCTOBER FEATURES...

INTRODUCING MICROPROCESSORS

by MIKE TOOLEY B.A.

EXCLUSIVE


City and Guilds Certificate Course

Over the next nine months this brand new series being published in Everyday Electronics magazine aims to provide readers with a thorough understanding of the principles and practice of microprocessors. More significantly, this series breaks new ground in the field of distance learning; it is the first to offer assessment and certification in conjunction with an internationally recognised examining body. We hope that you will follow this course for the next nine months and that many readers will complete the study programme which can lead to the award of a City and Guilds certificate in Introductory Microprocessors.

The Introduction, to be published next month, details the syllabus, explains how the course is set out, how and where to register for assessment, how the assessments are conducted, the microprocessors covered, cost, etc.

VIDEO CONTROLLER

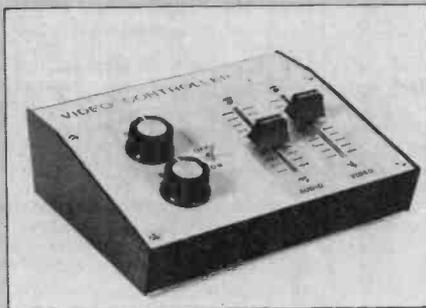Home video production takes on a new dimension with the use of this audio/video unit for mixing audio signals and fading video.



TRANSTEST

A simple but very useful "in circuit" transistor and diode tester. Much cheaper than commercial units.

SIMPLE STATIC MONITOR

"See" the static generated by stroking a cat or combing your hair. A simple project that could be useful in a school science lab or just use it for interest and entertainment.

EVERYDAY ELECTRONICS

OCTOBER ISSUE ON SALE FRIDAY, SEPTEMBER 18

Everyday Electronics, September 1987

Order Now!

We are already experiencing unprecedented interest in the City and Guilds series and anticipate that the October issue will be in great demand. We strongly advise you to make sure of your copy by placing an order with your Newsagent NOW (you can use the order form) or by taking out a subscription — see page 517. If you have not ordered a copy we cannot guarantee to be able to supply.

Please reserve/deliver a copy of Everyday Electronics for me each month.

Name

Address

E.E. PROJECT KITS

Full Kits inc. PCBs, or veroboard, hardware, electronics, cases (unless stated). Less batteries.
If you do not have the issue of E.E. which includes the project - you will need to order the instruction reprint as an extra - 80p each. Reprints available separately 80p each + p&p £1.00.

THIS MONTH'S KITS SAE or phone for prices

ELECTRONIC MULTIMETER Sept 87	£44.72
SUPER SOUND ADAPTOR Aug 87	£36.56
IMMERSION HEATER TIMER Aug 87	£17.99
3 BAND 1.6-30MHz RADIO Aug 87	£25.27
BUCCANEER I.B. METAL DETECTOR inc. coils and case, less handle and hardware July 87	£25.19
DIGITAL COUNTER/FREQ METER (10MHz) inc. case July 87	£67.07
MONOMIX July 87	£20.00
FERMOSTAT July 87	£11.56
VISUAL LIGHT TUNER Jun 87	£21.99
MINI DISCO JUN 87	£11.99
WINDSCREEN WASHER WARNING May 87	£4.88
FRIDGE ALARM May 87	£9.41
EQUALIZER (DISCISER) May 87	£14.79
ALARM THERMOMETER April 87	£25.98
BULB LIFE EXTENDER April 87 (less case)	£4.99
EXP. SPEECH RECOGNITION April 87	£19.98
COMPUTER BUFFER INTERFACE Mar 87	£11.96
ACTIVE 1/3 BURGLAR ALARM Mar 87	£33.95
VIDEO GUARD Feb 87	£7.99
MINI-AMP Feb 87	£14.99
CAR VOLTAGE MONITOR Feb 87	£11.98
SPECTRUM SPEECH SYNTH. (no case) Feb 87	£19.92
SPECTRUM 1/0 PORT less case. Feb 87	£8.99
STEPPING MOTOR BOOSTER (for above) Feb 87	£5.19
STEPPING MOTOR MD200 Feb 87	£16.80
HANDS-OFF INTERCOM (per station) inc. case Jan 87	£9.99
CAR ALARM Dec 86	£10.97
DUAL READING THERMOMETER (less case) Dec 86	£39.98
RANDOM NUMBER GENERATOR Dec 86	£14.97
8 CHANNEL A-D (SPECTRUM) CONVERTER Dec 86	£34.29
BBC 16K SIDEWAYS RAM Dec 86	£12.35
MODEM TONE DECODER Nov 86	£18.99
OPTICALLY ISOLATED SWITCH Nov 86	£11.99
CAR FLASHER WARNING Nov 86	£7.92
200MHz Dec. FREQUENCY METER Nov 86	£59.98
10 WATT AUDIO AMPLIFIER Oct 86	£34.95
LIGHT RIDER LABEL BADGE Oct 86	£9.71
LIGHT RIDER DISCO VERSION Oct 86	£18.59
LIGHT RIDER 16 LED VERSION Oct 86	£12.99
SCRATCH BLANKER Sept 86	£53.17
INFRA-RED BEAM ALARM Sept 86	£26.99
FREEZER FAILURE ALARM Sept 86	£14.76
CAR TIMER Sept 86	£8.30
BATTERY TESTER Aug 86	£6.85
HEADPHONE MIXER July 86	£7.45
CARAVAN BATTERY MONITOR July 86	£16.35
SQUEAKIE CONTINUITY TESTER July 86	£13.25
ELECTRONIC SCARECROW July 86	£8.45
VOX BOX AMP July 86	£12.73
PERCUSSION SYNTH June 86	£28.98
LIGHT PEN (less case) June 86	£5.80
PERSONAL RADIO June 86	£10.98
WATCHDOG June 86	£7.85
MINI STROBE May 86	£13.11
PA AMPLIFIER May 86	£24.95
LOGIC SWITCH May 86	£14.93
AUTO FIRING JOYSTICK May 86	£11.86
STEREO REVERB Apr 86	£25.18
VERSATILE PSU Apr 86	£23.51
CIRCLE CHASER Apr 86	£20.98
FREELADER Apr 86	£8.08
STEPPER MOTOR DRIVER Apr 86	£4.89
BBC MIDI INTERFACE Mar 86	£26.61
INTERNAL TIMER Mar 86	£17.97
STEREO HI-FI PRE-AMP Mar 86	£46.86
MAINS TESTER & FUSE FINDER Mar 86	£8.40
FUNCTION GENERATOR Feb 86	£23.66
POWER SUPPLY FOR ABOVE Feb 86	£7.82
TOUCH CONTROLLER Feb 86	£12.25
pH TRANSDUCER (less Probe) Feb 86	£23.11
SPECTRUM OUTPUT PORT Feb 86	£10.72
OPORT Jan 86	£7.14
TACHOMETER Jan 86	£24.57
MAIN DELAY SWITCH less case Jan 86	£18.83
ONE CHIP ALARM Jan 86	£8.29
MUSICAL DOOR BELL Jan 86	£17.83
TTL LOGIC PROBE Dec 85	£9.45
DIGITAL CAPACITANCE METER Dec 85	£39.57
FLUX DENSITY TRANSDUCER Nov 85	£28.72
FLASING PUMPKIN less case Nov 85	£4.20
SQUEAKING BAT less case Nov 85	£10.97
SCREAMING MASK less case Nov 85	£9.49
STRAIN GAUGE AMPLIFIER Oct 85	£28.00
SOLDERING IRON CONTROLLER Oct 85	£5.21
VOLTAGE REGULATOR Sept 85	£7.46
PERSONAL STEREO P.S.U. Sept 85	£9.89
R.I.A. PRE-AMP Sept 85	£15.94
CARAVAN ALARM Sept 85	£10.30
FRIDGE ALARM Sept 85	£7.50
SEMI-CONDUCTOR TEMP. SENSOR Sept 85	£20.82
RESISTANCE THERMOMETER Sept 85 less Probe	£20.71
PLATINUM PROBE Extra	£24.20

LOW COST POWER SUPPLY UNIT Aug 85	£18.39
TRI-STATE THERMOMETER (Batt) Aug 85	£6.66
TREMOLO/VIBRATO Aug 85	£37.92
STEPPER MOTOR INTERFACE FOR THE BBC COMPUTER less case Aug 85	£13.99
1035 STEPPER MOTOR EXTRA	£14.50
OPTIONAL POWER SUPPLY PARTS	£5.14
CONTINUITY TESTER July 85	£5.90
TRAIN SIGNAL CONTROLLER July 85	£9.66
AMSTRAO USER PORT July 85	£16.83
CROSS THE RIVER June 85	£19.77
ELECTRONIC DOORBELL June 85	£7.20
GRAPHIC EQUALISER June 85	£26.66
AUTO PHASE May 85	£17.98
INSULATION TESTER Apr 85	£18.65
LOAD SIMPLIFIER Feb 85	£18.68
GAMES TIMER Jan 85	£8.39
SPECTRUM AMPLIFIER Jan 85	£6.58
TV AERIAL PRE-AMP Dec 84	£14.83
Optional PSU 12V £2.44	240V £11.83
MINI WORKSHOP POWER SUPPLY Dec 84	£41.98
ODOR CHIME Dec 84	£17.89
99C MICRO AUDIO STORAGE SCOPE INTERFACE Nov 84	£34.52
PROXIMITY ALARM Nov 84	£21.58
MAINS CABLE DETECTOR Oct 84	£5.27
MICRO MEMORY SYNTHESIZER Oct 84	£57.87
DRILL SPEED CONTROLLER Oct 84	£8.27
GUITAR HEAD PHONE AMPLIFIER Sept 84	£7.66
SOUND OPERATED FLASH less lead Sept 84	£6.98
TEMPERATURE INTERFACE FOR BBC Aug 84	£23.64
CAR RADIO BOOSTER Aug 84	£16.64
CAR LIGHTS WARNING July 84	£9.58
VARICAP AM RADIO May 84	£12.52
EXPERIMENTAL POWER SUPPLY May 84	£22.46
SIMPLE LOOP BURGLAR ALARM May 84	£16.34
MASTERMIND TIMER May 84	£8.52
FUSE/DIODE CHECKER Apr 84	£4.14
QUASI STEREO ADAPTOR Apr 84	£13.08
DIGITAL MULTIMETER add on for BBC Micro Mar 84	£29.98
NI-CAO BATTERY CHARGER Mar 84	£11.82
REVERSING BLEEPER Mar 84	£8.14
PIPE FINDER Mar 84	£4.32
IGNISER Feb 84	£28.78
SIGNAL TRACER Feb 84	£17.88
CAR LIGHT WARNING Feb 84	£4.51
GUITAR TUNER Jan 84	£21.28
BIOLOGICAL AMPLIFIER Jan 84	£22.99
CONTINUITY TESTER Dec 83	£11.99
CHILDREN'S DISCO LIGHTS Dec 83	£9.42
NOVEL EGG TIMER Dec 83 inc. case	£12.29
SPEECH SYNTHESIZER FOR THE BBC MICRO Nov 83 less cable + sockets	£26.38
MULTIMOD Nov 83	£20.38
HOME INTERCOM less link wire Oct 83	£17.26
STORAGE SCOPE INTERFACE FOR BBC MICRO Aug 83 less software	£18.42
HIGH POWER INTERFACE BOARD Aug 83 no case	£12.45
USER PORT 1/0 BOARD less cable + plug	£12.59
USER PORT CONTROL BOARD July 83 less cable + plug + case	£30.16
MW PERSONAL RADIO less case, May 83	£9.14
MOISTURE DETECTOR May 83	£6.95
NOVELTY EGG TIMER April 83 less case	£6.58
DUAL POWER SUPPLY March 83	£59.48
BUZZ OFF March 83	£5.41
PUSH BIKE ALARM Feb 83	£14.07
ZX TAP CONTROL Nov 82	£9.55
2-WAY INTERCOM July 82 no case	£5.42
REFLEX TESTER July 82	£9.32
SEAT BELT REMINDER Jun 82	£4.92
EGG TIMER June 82	£6.53
CAR LED VOLT METER less case, May 82	£3.81
V.C.O. SOUND EFFECTS UNIT Apr 82	£15.25
CAMERA OR FLASH GUN TRIGGER Mar 82 less tripod bushes	£16.38
POCKET TIMER Mar 82	£4.92
SIMPLE STABILISED POWER SUPPLY Jan 82	£32.37
MINI EGG TIMER Jan 82	£5.28
SIMPLE INFRA RED REMOTE CONTROL Nov 81	£22.44
SUSTAIN UNIT Oct 81	£16.79
TAPE NOISE LIMITER Oct 81	£5.97
HEADS AND TAILS GAME Oct 81	£3.30
PHOTO FLASH SLAVE Oct 81	£4.56
FUZZ BOX Oct 81	£9.87
SOIL MOISTURE UNIT Oct 81	£7.66
0-12V POWER SUPPLY Sept 81	£23.38
COMBINATION LOCK July 81 less case	£25.89
SOIL MOISTURE INDICATOR E.E. May 81	£5.39
PHONE BELL REPEATER/BABY ALARM May 81	£7.38
MODULATED TONE DOORBELL Mar 81	£8.82
2 NOTE DOOR CHIME Dec 80	£13.62
LIVE WIRE GAME Dec 80	£15.44
GUITAR PRACTICE AMPLIFIER Nov 80 £14.10 less case. Standard case extra	£5.98
SOUND TO LIGHT Nov. 80 3 channel	£28.08
AUDIO EFFECTS UNIT FOR WEIRO SOUNDS Oct 80	£17.28
SPRING LINE REVERB UNIT Jan 80	£32.64
UNIBOARD BURGLAR ALARM Dec 79	£7.98
DARKROOM TIMER July 79	£3.84
MICROCHIME DOORBELL Feb 79	£20.98
SOUND TO LIGHT Sept 78	£10.89
R.F. SIGNAL GENERATOR Sept 78	£37.44
IN SITU TRANSDUCER TESTER Jun 78	£9.00
WEIRO SOUND EFFECTS GENERATOR Mar 78	£7.44
ELECTRONIC DICE Mar 77	£5.97

MAGENTA

DIGITAL TROUBLESHOOTING

Top quality kits & parts for this new series. Our excellent technical back-up service helps to ensure that your projects succeed every time.
PART 1 BENCH POWER SUPPLY—Full kit £24.98.
LOGIC PROBE—£7.58 including case.
LOGIC PULSER—£7.48 including case.
VERSATILE PULSE GENERATOR—£29.98 including case.
DIGITAL I.C. TESTER—£29.21 (case different).
CURRENT TRACER—£20.56.
AUDIO LOGIC TRACER—£8.99.

EXPLORING ELECTRONICS

A full set of parts including the Verobloc breadboard to follow the series right up to Nov. issue. £14.87. Dec parts £4.99. Jan parts £4.99. Feb parts £4.29. March parts £8.99. April parts £4.44. May parts £3.98. June parts £4.40. July parts £4.79. Aug parts £3.85.

INTRODUCTION TO ELECTRONICS

An introduction to the basic principles of electronics. With lots of simple experiments. Uses soldering. Lots of full colour illustrations and simple explanations. A lovely book. Ideal for all ages.
INTRODUCTION TO ELECTRONICS COMPONENT PACK £10.99
BOOK EXTRA £2.45
Book also available separately.

NEW BOOKS

Modern Opto Device Projects £2.95
Electronic Circuits for the Control of Model Railways £2.95
A T.V.-DIXERS Handbook BP176 £5.95
Midi Projects. Penfold £2.95
Getting The Most From Your Printer. Penfold £2.95
More Advanced Electronic Music Projects. Penfold £2.95



BOOKS

How to Get Your Electronic Projects Working. Penfold £2.15
A practical Introduction to Microprocessors. Penfold £2.10
Basic Electronics. Hodder & Stoughton £8.98
Beginners Guide to Building Electronic Projects. Penfold £2.25
DIY Robotics & Sensors Billingsley. BBC £7.95
Commodore 84 £7.99
Elementary Electronics. Sladdin £5.98
Science Experiments with Your Computer £2.43
How to Design & Make Your Own PCBs. BP121 £2.15
How to Make Computer Controlled Robots. Potter £3.20
How to Make Computer Model Controllers. Potter £3.19
Interfacing to Microprocessors & Microcomputers £6.50
Machine Code for Beginners. Usborne £2.45
Micro Interfacing Circuits Book 1 £2.45
Microprocessors for Hobbyists. Coles £4.98
Practical Computer Experiments. Parr £1.95
Practical Things to do With a Microcomputer. Usborne £2.19
Questions & Answers — Electronics. Hickman £3.45
Understanding the Micro. Usborne £1.95

* JUST A SMALL SELECTION. LOTS MORE IN OUR PRICE LIST *

TEACH IN 86

MULTIMETER TYPE M102BZ as specified. Guaranteed. Top quality. 20kV, with battery check, continuity tester buzzer and fuse and diode protection. 10A dc range. £14.98
Complete with leads, battery and manual.
VEROBLOC BREADBOARD, DESIGN PAD, MOUNTING PANEL AND 10 CROCODILE CLIP CONNECTING LEADS. £6.98
REGULATOR UNIT FOR SAFE POWER SUPPLY. All components including the specified case. Also the plugs, fuse and fuseholders to suit the EE mains adaptor. £16.78
COMPONENTS FOR PRACTICAL ASSIGNMENTS. Parts 1 and 2 (Oct & Nov) £1.94. Part 3 (Dec) £1.37. Part 4 (Jan) £2.48. Part 5 (Feb) £2.22. Part 6 (Mar) £6.31. Parts 7, 8 & 9 (combined) £2.55.

TEACH IN 86 PROJECTS

UNIVERSAL ICR BRIDGE Nov 85 £25.83
DIODE/TRANSISTOR TESTER Dec 85 £18.89
USEFUL AUDIO SIGNAL TRACER Jan 86 £16.75
AUDIO SIGNAL GENERATOR Feb 86 £26.21
R.F. SIGNAL GENERATOR March 86 £24.48
FET VOLT METER Apr 86 £21.48
DIGITAL PULSE GENERATOR May 86 £16.68

NEW
MINI MODEL MOTORS
1 1/2-3V, 2 TYPES. MM1—59p MM2—61p

LEGO Technic Sets

TEACHERS WE ARE STOCKISTS OF THE WHOLE RANGE. CONTACT US FOR BROCHURES. VERY COMPETITIVE PRICES AND QUICK DELIVERIES.


STEPPING MOTORS 12 VOLT

NEW
48 STEPS | 200 STEPS
ID35 | MD200
£14.80 | £16.80



MOTOR — GEARBOX ASSEMBLIES

Miniature precision made. Complete with quality electric motor. Variable reduction ratios achieved by fitting from 1-6 gearwheels (supplied) as required. Operates from 1.5V to 4.5V. Small unit type MGS speed range 3rpm-2200rpm depending on voltage & gear ratio. Large unit type MGL (higher torque motor) 2rpm-1150rpm. Long 3mm dia output shafts. Ideal for robots and buggies.
Small Unit (MGS) £3.49. Large Unit (MGL) £3.98.

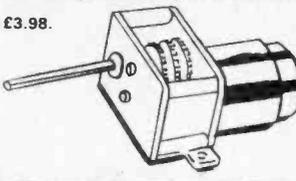

1987 CATALOGUE

Brief details of our range kit, our books, & illustrations of our range of tools & components. Also stepper motor, interface kit & simple robotics. Plus circuit ideas for you to build. If you read Everyday Electronics then you need a copy of the MAGENTA catalogue.

CATALOGUE & PRICE LIST — Send £1 in stamps etc. or add £1 to your order. Price list — 9x4 size. Catalogue FREE TO SCHOOLS/COLLEGES REQUESTED ON OFFICIAL LETTERHEAD.


ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec Breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.
Adventures with Electronics £3.58. Component pack £20.98 less battery.

TOOLS

ANTEX MODEL C IRON £6.98
ANTEX X5 SOLDERING IRON 25W £7.25
ST4 STAND FOR IRONS £2.85
HEAT SINK TWEEZERS £4.5p
SOLDER HANDY SIZE 5 £1.39
SOLDER CARTON £2.50
SOLDER REEL SIZE 10 £4.67
LOW COST PLIERS £1.98
LOW COST CUTTERS £1.99

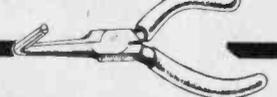BENT NOSE PLIERS £1.89
MINI DRILL 12V (MD1) £8.38
MULTIMETER TYPE 1 100000v £6.98
MULTIMETER TYPE 2 20.0000v £17.98
MULTIMETER TYPE 3 30.0000v £27.98
MULTIMETER TYPE 4 10M DIGITAL £39.98
DESOLDER PUMP £5.48
SIGNAL INJECTOR £2.98
CIRCUIT TRACER 78p
HELPING HANDS JIG & MAGNIFIER £7.98
MINIATURE VICE (PLASTIC) £1.85



MAGENTA ELECTRONICS LTD. SHOP NOW OPEN—CALLERS WELCOME
E656, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS. DE14 2ST.
Access/Barclaycard (Visa) by phone or post.
24 hr Answerphone for credit card orders.
Our prices include VAT.

ADD £1 P&P TO ALL ORDERS. PRICES INCLUDE VAT. SAE ALL ENQUIRIES. OFFICIAL ORDERS WELCOME. OVERSEAS: Payment must be sterling. IRISH REPUBLICAN AND BFPO. UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote. SHOP HOURS: 9-5 MON-FRI.

PRICE LIST—FREE WITH ORDERS OR SEND SAE

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

The Magazine for Electronic & Computer Projects

VOL 16 N°9

September '87

Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL,
6 CHURCH STREET, WIMBORNE,
DORSET BH21 1JH
Phone: Wimborne (0202) 881749

See notes on **Readers' Enquiries** below—we regret that lengthy technical enquiries cannot be answered over the telephone

Advertisement Offices

EVERYDAY ELECTRONICS ADVERTISEMENTS
4 NEASDEN AVE., CLACTON-ON-SEA, ESSEX
CO16 7HG. Clacton (0255) 436471

CITY & GUILDS

AS MENTIONED a couple of months ago, our new series *Introducing Microprocessors* starts next month. The series can lead to the award of a City & Guilds certificate (Introductory Microprocessors) and we believe this is a first for any UK monthly magazine. It is also exclusive to EE.

Make sure you get next month's issue—it carries the introduction to the series with all the details of how to register for assessment, centres, cost etc. We are already experiencing unprecedented interest in this series and I strongly recommend that you make sure of your copy by either ordering it from your newsagent or by taking out a subscription—see pages 468 and 517.

If you do not have a copy on order we cannot guarantee to be able to supply!

The course should provide all readers with a thorough understanding of the principles and practice of microprocessors. Even if you do not wish to try to gain a C&G certificate, *Introducing Microprocessors* will be well worth following. For those who are interested in the qualification you may like to know that you do not have to take the assessments within any given period. The study can thus be spread over a couple of years if you so wish. As I said, don't miss next month's issue—order now!

PCBs

I would like to warn all readers that we are about to rationalise our *EE PCB Service*. The number of boards available will be reduced from next month when virtually all boards over two years old will be dropped from the list.

We have found that after two years the very low requirement for p.c.b.s makes the service uneconomical. It will also be necessary to increase the price of some boards. So if you want a p.c.b.—particularly if it is an old one—get your order in now. You have been warned!

Many of our p.c.b. prices have never been raised and with the rising cost of materials and labour, we now have to increase the price to cover these. I assure you our p.c.b.s will still be good value for money and competitive with other suppliers.




BACK ISSUES & BINDERS

Certain back issues of EVERYDAY ELECTRONICS and ELECTRONICS MONTHLY are available price £1.50 (£2.00 overseas surface mail) inclusive of postage and packing per copy. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. In the event of non-availability remittances will be returned. **Please allow 28 days for delivery. (We have sold out of Oct. & Nov. 85, April, May & Dec 86.)**

Binders to hold one volume (12 issues) are available from the above address for £4.95 (£9.00 overseas surface mail) inclusive of p&p. **Please allow 28 days for delivery.**

Payment in £ sterling only please.

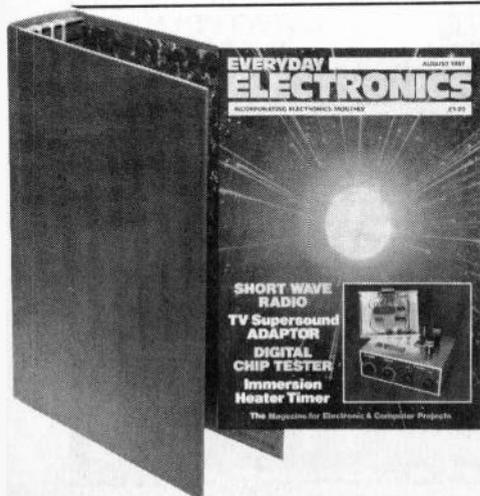

Editor MIKE KENWARD

Personal Assistant
PAULINE MITCHELL

Assistant Editor/Production
DAVID BARRINGTON

Assistant Editor/Projects
DAVID BRUNSKILL

Editorial: WIMBORNE (0202) 881749

Advertisement Manager
PETER J. MEW Clacton (0255) 436471

Classified Advertisements
Wimborne (0202) 881749

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply **must** be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

OLD PROJECTS

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that **we cannot provide data or answer queries on projects that are more than five years old.**

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.


The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should address them to the advertiser or should consult a local trading standards office, or a Citizen's Advice Bureau, or a solicitor.

SUBSCRIPTIONS

Annual subscription for delivery direct to any address in the UK: £14.00. Overseas: £17.00 (£33 airmail). Cheques or bank drafts (**in £ sterling only**) payable to Everyday Electronics and sent to EE Subscription Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. **Subscriptions can only start with the next available issue.** For back numbers see the note on the left.

NOISE GATE

IAN COUGHLAN

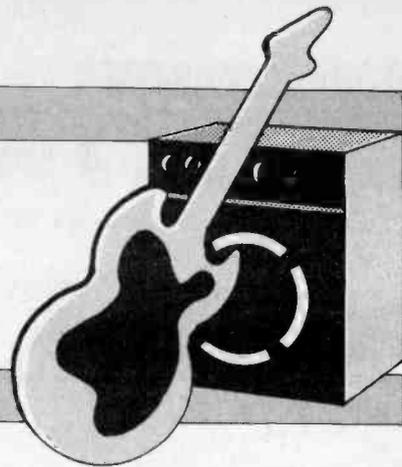

Ideal project for the musician who wants to create the right sounds, without the noise

OVER the last few years the popularity of electronics effects units for musicians has grown dramatically particularly those using time-delay techniques. These include flangers, choruses, echo, reverbs, and so on. While these effects offer the musician new and interesting sounds, they often suffer from a poor signal-to-noise ratio; that is, the amount of noise produced relative to the maximum signal level that the system can handle. This noise is normally masked by the music, but stop playing and the same noise becomes quite objectionable, manifesting itself in the form of hisses, whistles, crackles, whoops, etc.

Using more than one effect-box simply makes matters worse, as do noisy leads and jack-connectors. One solution would be to turn the amplifier's volume control down whenever playing stops, but that is obviously impractical. The Noise-Gate offers a neat and simple answer to the problem. Connected immediately before the input to the amplifier—and therefore after any effect-boxes in use—it constantly monitors the signal level. If the signal is below a certain level, then the Noise-Gate will "close" and prevent the signal from reaching the amplifier. Start playing and the signal rises, causing the Noise-Gate to "open", allowing the signal to get through to the amplifier. So when there is music, the signal gets through; when there is only noise, it doesn't.

The signal level at which the Noise-Gate will open is called the "threshold", and a control is provided so that it may be adjusted. The threshold should be set just above the level of the noise (the so-called "noise floor"), so that any signal above the threshold, and therefore above the noise floor, will open the Noise-Gate. Note the terminology used: *open* means the signal is allowed to pass through, *closed* means it is not. Don't think in terms of a switch: think in terms of a gate (hence the name "noise-gate").

The Noise-Gate should open as quickly as possible in response to an increase in the input level, so that little of the music is lost. In this design, the response time is around a couple of milliseconds. Obviously, the same does not hold true when the input level falls below the threshold, otherwise the Noise-Gate would close with every gap in the music of more than a millisecond or two. This design will remain open for about half a second after the music stops. These times

are not externally adjustable, but the experimenter may wish to try altering the values of the relative components, to lengthen or shorten either or both times.

There is also a control for adjusting the gain of the Noise-Gate. Normally this would be set to unity (output = input), but can be set anywhere between 0.02 and 5 (or -34dB to +14dB gain). A switch on the rear allows the user to open the Noise-Gate regardless of the signal level, this is handy for tuning-up instruments; and an l.e.d. on the front panel displays the status of the Noise-Gate.

CIRCUIT DESCRIPTION

Integrated circuit IC3 (Fig. 1) is a quad CMOS switch, and IC3a, is the "gate" in noise-gate. For the input signal to reach the output, it must first pass through IC3a, and

the state of this switch is controlled by the voltage on IC3 pin 13. When this voltage is high, the switch allows the signal to pass; and when it is low, the signal is blocked. IC1b, wired as a variable gain stage, boosts or attenuates the gated signal, and provides a low output impedance suitable for driving virtually any amplifier or tape-recorder input stage.

For the Noise-Gate to open, about six volts peak-peak is required at IC2a pin three. This is much larger than can be provided by musical instruments, so the input signal is boosted considerably by IC1a, another variable gain stage, whose gain is adjustable between 23 and 73, giving a threshold that can be set from about 85mV peak-peak, to 250mV peak-peak. IC2a pin two is biased by R10 and R12 to

COMPONENTS

Resistors

R1,R12,R15,R16,R18,R19	1M (6 off)	R8,R10	330k (2 off)
R2	200k	R11,R17	10k (2 off)
R3,R4	470k (2 off)	R13	5k 1
R5,R9	4k7 (2 off)	R14	33k
R6	100	R22,R23	3k9 (2 off)
R7,R20,R21	100k (3 off)		

All 0.25 watt 5% carbon

Potentiometers

VR1	1M log. carbon
VR2	10K log. carbon

Capacitors

C1	330n miniature layer polyester 100V
C2,C3,C4,C7	10µ miniature radial elect. 16V (4 off)
C5	100µ miniature radial elect. 16V
C6	22p polystyrene 160V
C8,C10	100n miniature layer polyester 100V (2 off)
C9	470n miniature layer polyester 100V

Semiconductors

IC1	TL072 dual low-noise op-amp
IC2	TL082 dual op-amp
IC3	4066B quad switch
IC4	78L12 +12V voltage regulator
D1,D2,D3,D4	1N4001 1A 50V rectifier diode (4 off)
D5	1N4148 small signal diode
D6,D7	3mm red light emitting diode (2 off)

Miscellaneous

S1	s.p.s.t. miniature toggle switch
SK1,SK2	6.3mm jack sockets (2 off)
FS1	500mA fuse and 20mm panel mounting fuse holder
T1	1.2VA mains transformer with 12V secondary

Printed circuit board available from the EE PCB Service, order code 577; case 154mm x 120mm x 45mm; p.c.b. mounting pillars (4 off); l.e.d. mounting clip (2 off); 7/02 wire; miniature screened cable; 3-core 3A mains cable; cable grommet and clamp for mains cable; control knobs (2 off); primer and paint; instant lettering; solder tag; screws for p.c.b. pillars; 1mm rubber sleeving; p.v.c. insulating tape.

Approx. cost

Guidance only

£17 (plus case)

See
**Shop
Talk**
page 484

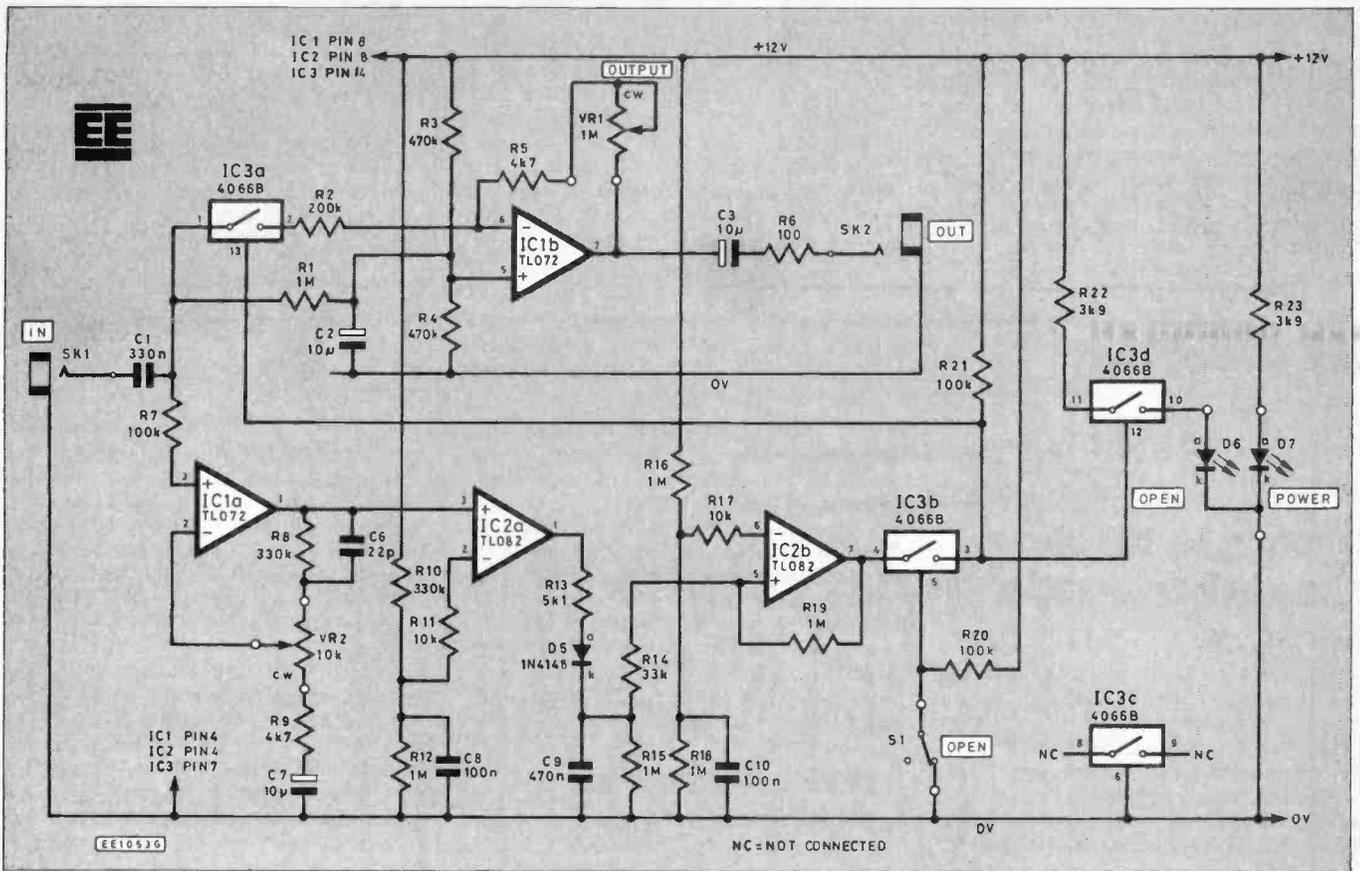



Fig. 1. Complete circuit diagram for the Noise-Gate. The 12V power supply section is shown below.

about 9V. With no input signal present, IC2a pin three is at 6V. Therefore, for IC2a, which is the threshold detector, to operate, IC2a pin three must exceed 3V peak (or 6V peak-peak). When the threshold is reached, IC2a pin one will go high, charging C9 via R13 and D5. R13 and C9 determine the time taken for the Noise-Gate to open. When the voltage on C9 exceeds about 6.2V, so the voltage on IC2b pin five will exceed that on pin six (6V), and will cause IC2b pin seven to go high. Without R19, IC2b would tend to oscillate as the voltages on pins five and six approached each other.

When the input level drops below the threshold, so C9 will no longer be getting charged from IC2a pin one, and will discharge through R15. R15 sets the time taken for the Noise-Gate to close. This resistor may be decreased for shorter hold times, but must not be increased, otherwise the Noise-Gate will not function.

Switch S1, when closed, pulls IC3b pin five to 0V, causing IC3b to open, and allowing IC3 pins 12 and 13 to be pulled high via R21. IC3a will therefore close, allowing the input signal to reach the amplifier stage, as described above, and IC3d will close, causing D6, an l.e.d. to light, indicating that the Noise-Gate is open. Since IC3b is open, the voltage on IC2b will have no effect on the status of the Noise-Gate: i.e., the 'Gate will be open regardless of the input signal. When S1 is open, IC3b pin five will be pulled high by R20. IC3b will then be closed, and the state of IC3a and IC3d, and therefore the status of the Noise-Gate, will depend on the voltage on IC2b pin seven, and this in turn depends on the input signal level.

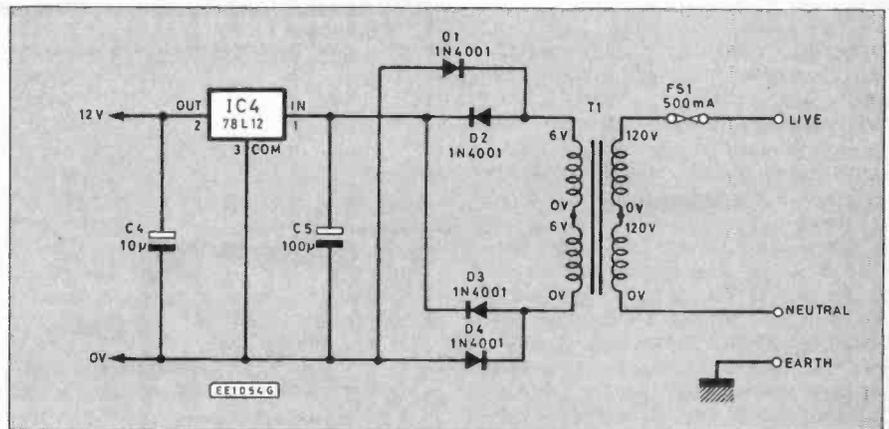Power is supplied by transformer T1, and regulated by IC4, a 78L12 voltage regulator, see Fig. 1.



CONSTRUCTION

Construction of the Noise-Gate is fairly straightforward and is built on a single printed circuit board. Because the mains transformer is also mounted on the board **extreme care must be taken when testing.**

The component layout and printed circuit board foil master pattern is shown in Fig. 2. This board is available from the *EE*

PCB Service, code 577.

Begin by checking the bare printed-circuit board for shorts. Veropins should be inserted into the p.c.b. from the foil side. These can be gently tapped into place with a hammer, and then soldered. Fix the resistors to the p.c.b., followed by the capacitors and the link-wire. If using d.i.l. sockets for the i.c.s, fit these next, then the fuse-clips,

IC4, and the diodes. Turn the p.c.b. over, and connect insulated wire between the points shown in Fig. 2. Lastly, fix the transformer to the board, and fit the i.c.s in their sockets.

If using the same box as the prototype, drill it as shown in the photographs. De-burr the holes, and rub-down the surfaces to be painted (the front and the rear), prime

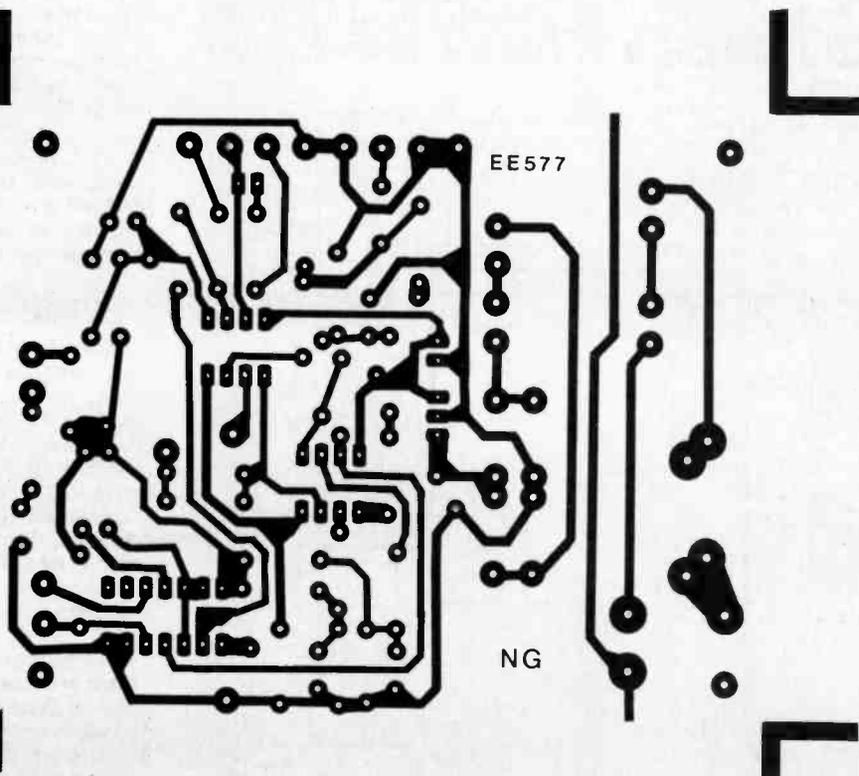
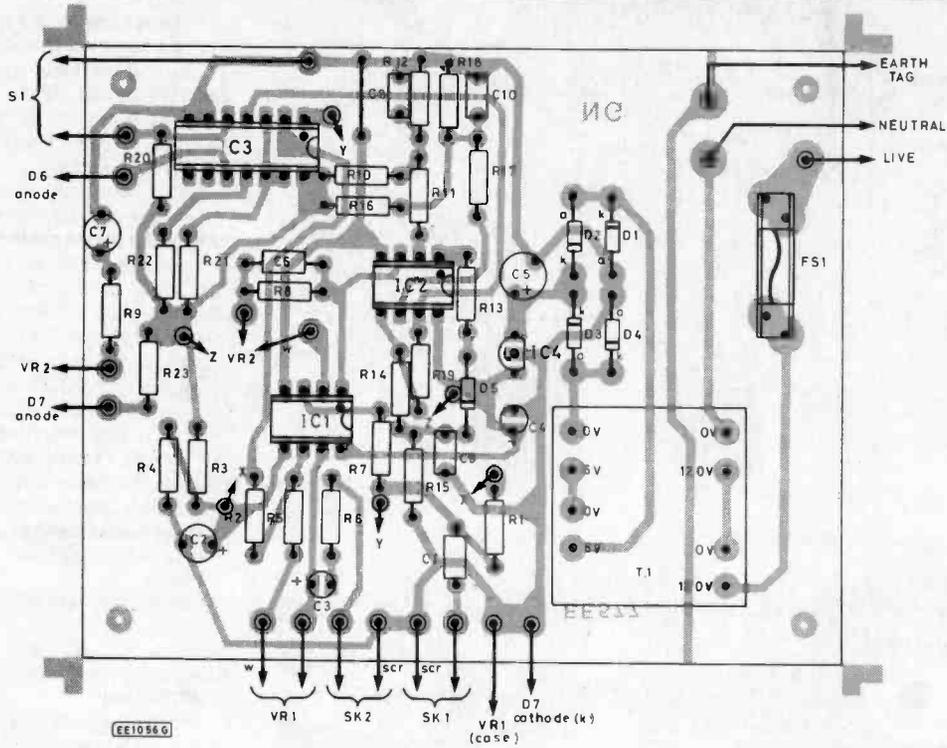


Fig. 2. Component layout and full size printed circuit foil master pattern for the Noise-Gate. Note that the wires terminated with single letters should be a single sleeved link, i.e. x to x, y to y etc, and be soldered on the underside.


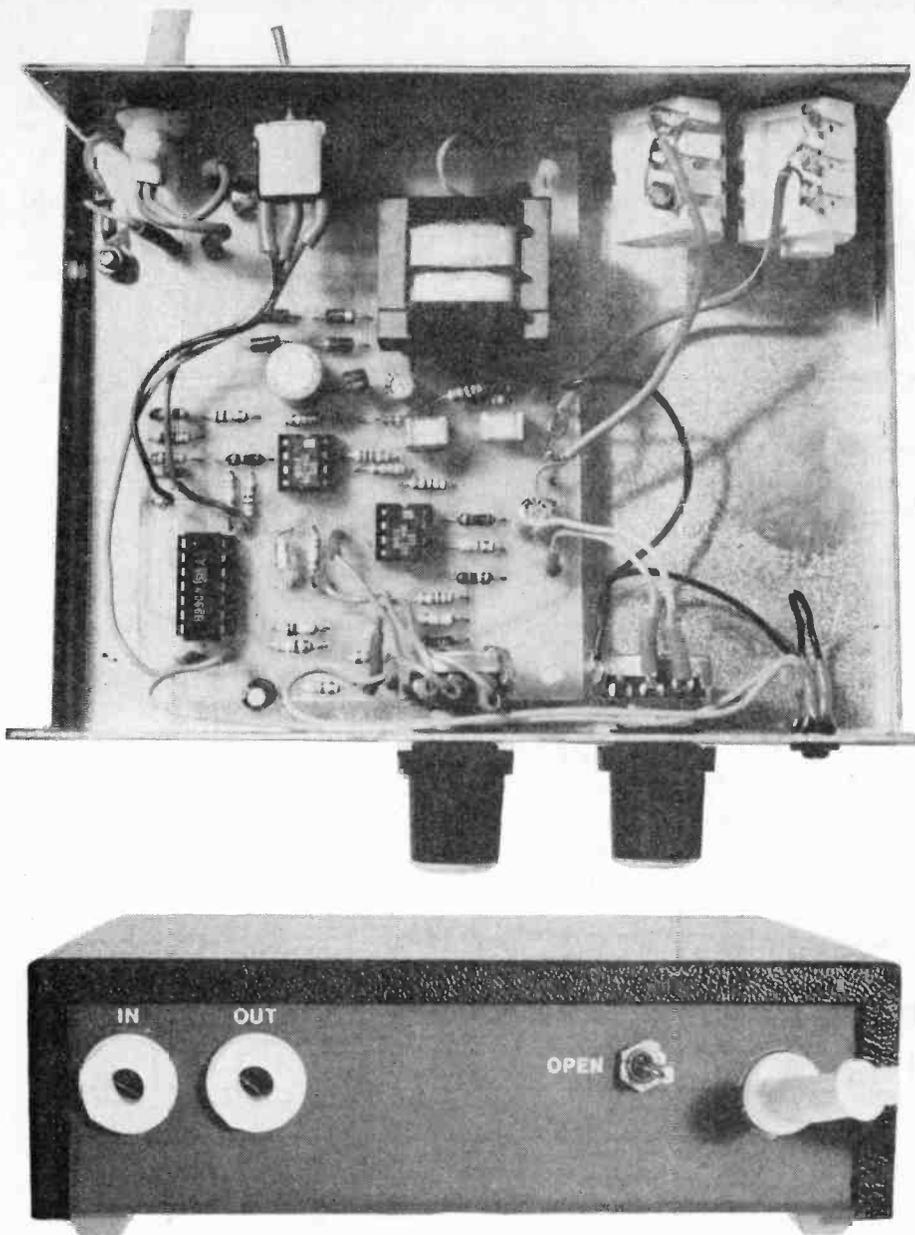


Fig. 3. Front and rear panel wiring and connections to the p.c.b. The internal wiring, board positioning and rear mounted components are shown in the photographs above.

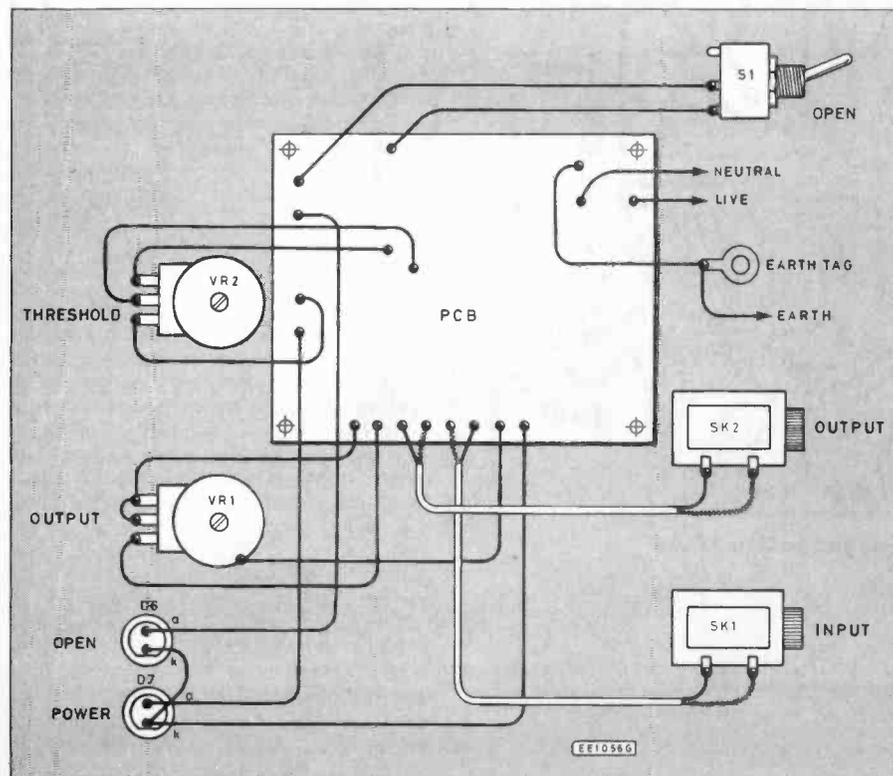

them, and paint them. When the paint is dry, lettering can be applied, using Letraset or Mecanorma dry-transfers, which should then be protected with a light coat of varnish. Fix the earthing-point and the p.c.b. mounting pillars to the base of the box. As a safety measure, apply a few lengths of p.v.c. adhesive insulating tape to the inside of the box, underneath those areas of the p.c.b. that carry mains voltages. Fix the p.c.b. to the four mounting pillars.

INTERWIRING

Connect the mains cable (not forgetting the grommet and a cable clamp) to the p.c.b., and the earth conductor to the earth tag, which should be connected to the earthing point on the box. At this point it may be worth checking that the power supply is operating.

Fit a 500mA fuse, and check the resistance between the live and neutral conductors of the mains cable (this should be a few tens of ohms). Next, check that the earth conductor is connected to the case, and that the resistance between the earth conductor and the live and neutral conductors is very high (it ought to be immeasurably high on a normal multimeter—in other words, check for an open circuit). Next, check for a similarly high resistance between the live and neutral conductors and the 6V windings of the transformer. If all is well, then the mains can be applied. **Take extreme care, as mains voltages are potentially lethal.** Check across pins seven and 14 of IC3 for 12 volts.

If the 12 volts is not present, then disconnect the mains before attempting to find out why. If the 12 volt supply is correct, disconnect the mains before continuing the construction.


Fix the two sockets, the switch, the two potentiometers, and the two l.e.d.s to the box. Connect these components as shown in Fig. 3, using 7/02 connecting wire and miniature screened cable. Make a quick visual check over the p.c.b. to ensure nothing has been missed out or fitted the wrong way round. Fix the lid on the box, and connect the mains supply. The Power l.e.d. should light. The Open l.e.d. may also be lit, depending on the position of the switch on the rear of the noise-gate: position the switch so that the l.e.d. goes out.

TESTING

Connect the noise-gate between an instrument and the amplifier. If using effects boxes, the noise-gate should be connected between the last of these and the amplifier. As the instrument is played, the Open l.e.d. should light, and the signal from the instrument should reach the amplifier. The Open l.e.d. should go out as playing stops: if it does not, then rotate the threshold control until it does. The Output control should be set to provide an output level suitable for whatever amplifier or tape-recorder is being used.

Flangers and choruses are among the worst producers of noise, so, if using one or both of these effects, switch them on, and adjust them for their worst output (that is, for maximum noise). Adjust the threshold control until the Open l.e.d. just lights, and then rotate it in the opposite direction until it goes back out. Playing the instrument should now open the gate, and the gate should close about half a second or so after playing stops. Construction and testing is now complete. □

PERSONAL STEREO AMPLIFIER

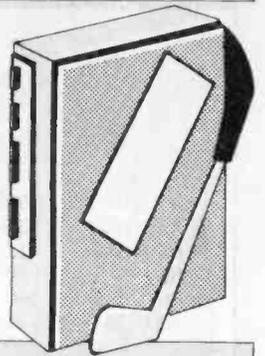

OWEN BISHOP

Turn your personal stereo player into a portable mini hi fi system

ONE person's music is another person's cacophony! Owners of personal tape players avoid this situation by keeping their music to themselves. Their favourite melodies may be reproduced with high fidelity anywhere in the world. Yet this will not petrify the passing pedestrian or Pukeka (depending on location) with that bane of civilization—other peoples' music! On the other hand, there are occasions for sharing the enjoyment of music with friends or loved ones (subject to their consent, of course) and this is the reason for presenting this project.

It is possible to buy stereo amplifiers designed to operate with certain makes of

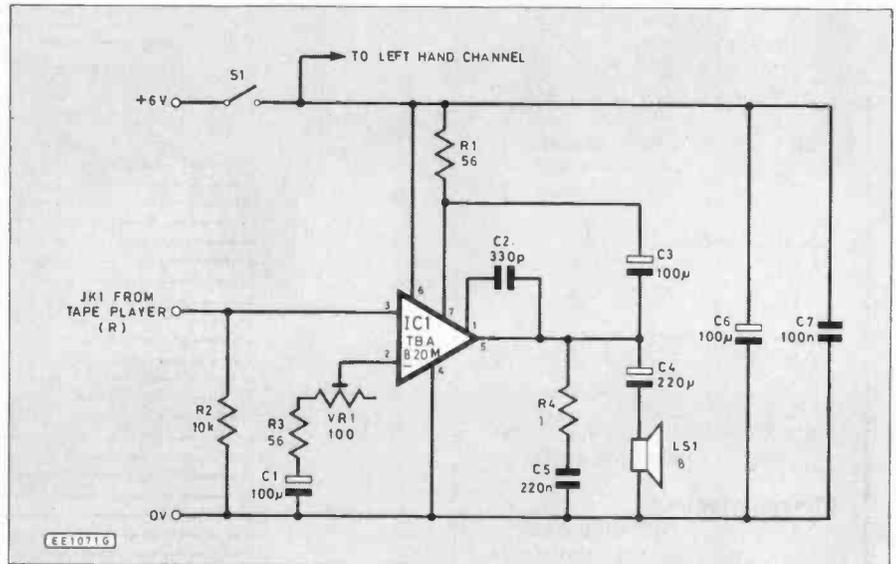



Fig. 1. Circuit of the right hand channel of the amplifier. In the left hand channel VR1 and R3 are replaced by R5. Capacitors C6 and C7 are common to both channels, all other components are duplicated.

personal tape player. But these are usually expensive and are not available for all players. The amplifier described here has been designed to connect to the Sony Walkman. It also works with the Grundig Beat Boy and has been successfully tested with many other tape players. The design features small size, light weight, robust construction and low battery consumption. In short, it is intended to be complementary to the personal tape-player. In addition, being based on a pair of readily available i.c.s, the amplifier is inexpensive and is simple to construct.

THE CIRCUIT

The circuit (Fig. 1) consists of two virtually identical amplifiers each built around a TBA 820M audio amplifier i.c. The special features of this i.c. are that it can operate on a supply voltage as low as 3V, and that it has a low quiescent current (about 3mA). Its maximum output is only 2W but, since the amplifier is to be powered by M1 500 cells, it is not realistic to demand more. The amplifier will play for several hours before the cells become discharged and the sound quality deteriorates. The lower the output volume, the cheaper the running costs!

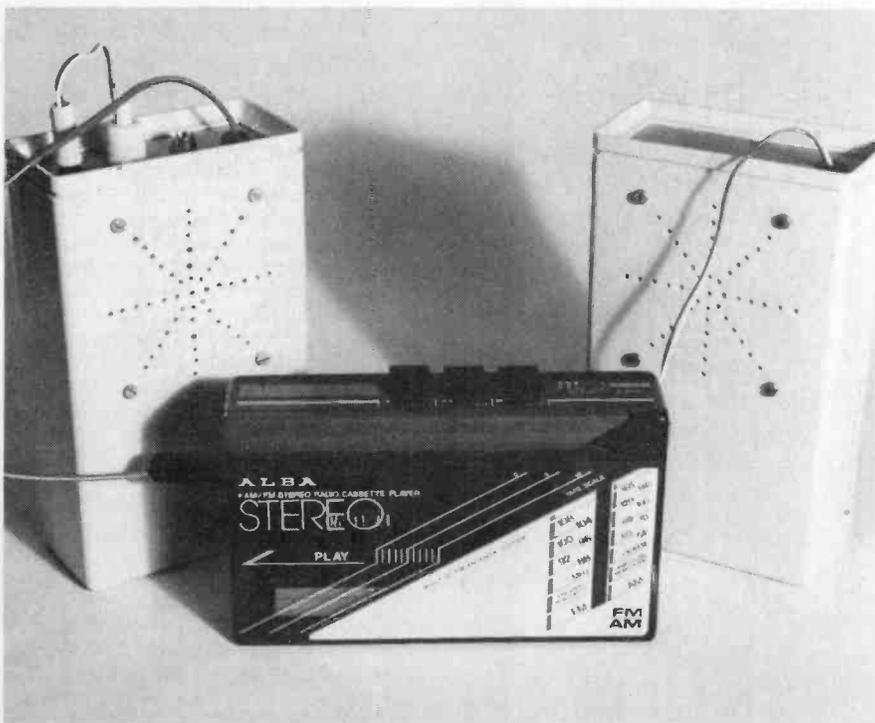The diagram (Fig. 1) shows the circuit of the right channel amplifier, left hand component numbers are plus 100. Input from the right channel of the tape player is fed to pin three of IC1. The gain of the amplifier is set by adjusting the setting of VR1. The purpose of this is to allow the user to



COMPONENTS

See
**Shop
Talk**
page 484

Resistors

R1,R101,R3 56 (3 off)
R2,R102 10k (2 off)
R4,R104 1 (2 off)
R5 120
R6 150
All 0.25W, 5% carbon

Capacitors

C1,C101,C6 100 μ axial elect.
10V (3 off)
C2,C102 330p, polystyrene
(2 off)
C3,C103 100 μ radial elect.
10V (2 off)
C4,C104 220 μ , elect. 10V (2
off)
C5,C105 220n polyester (2
off)
C7 100n polyester

Potentiometer

VR1 100 horizontal
preset

Semiconductors

D1 Light emitting diode, recessed in
bezel
IC1,IC101 TBA820M, audio
amplifier (2 off)

Miscellaneous

S1 Push-on-push-off
button switch or
s.p.s.t. slide switch
JK1 Stereo jack plug to
fit tape player
LS1,LS101 8 ohm loudspeakers, 75mm diam. (2
off)

SK1, mono jack socket, with
mono jack plug to fit; plastic instrument case approx 90mm x
155mm x 45mm with end panel
and battery compartment (2 off);
stripboard approx 77mm x
62mm (24 strips x 30 holes);
1mm terminal pins (7 off); 8-pin
d.i.l. sockets (2 off); 4BA bolts,
each with nut and solder tag (4
off), four self-tapping screws or
other fixings; small grommet;
light duty two-core screened
cable; single stranded and multi-
stranded connecting wire.

Approx. cost **£12 (plus cases)**
Guidance only

equalise the gains of the two amplifiers to produce a satisfactory stereophonic output. The *variable* output of the right channel amplifier is set to match the *fixed* output level of the left channel amplifier. The output volume of the system as a whole is more simply controlled by adjusting the volume control of the player itself.

The circuit is powered by four M1500 alkaline dry cells connected as a 6V battery. Although the i.c.s are able to operate at 3V, the sound quality tends to be inferior at this supply voltage.


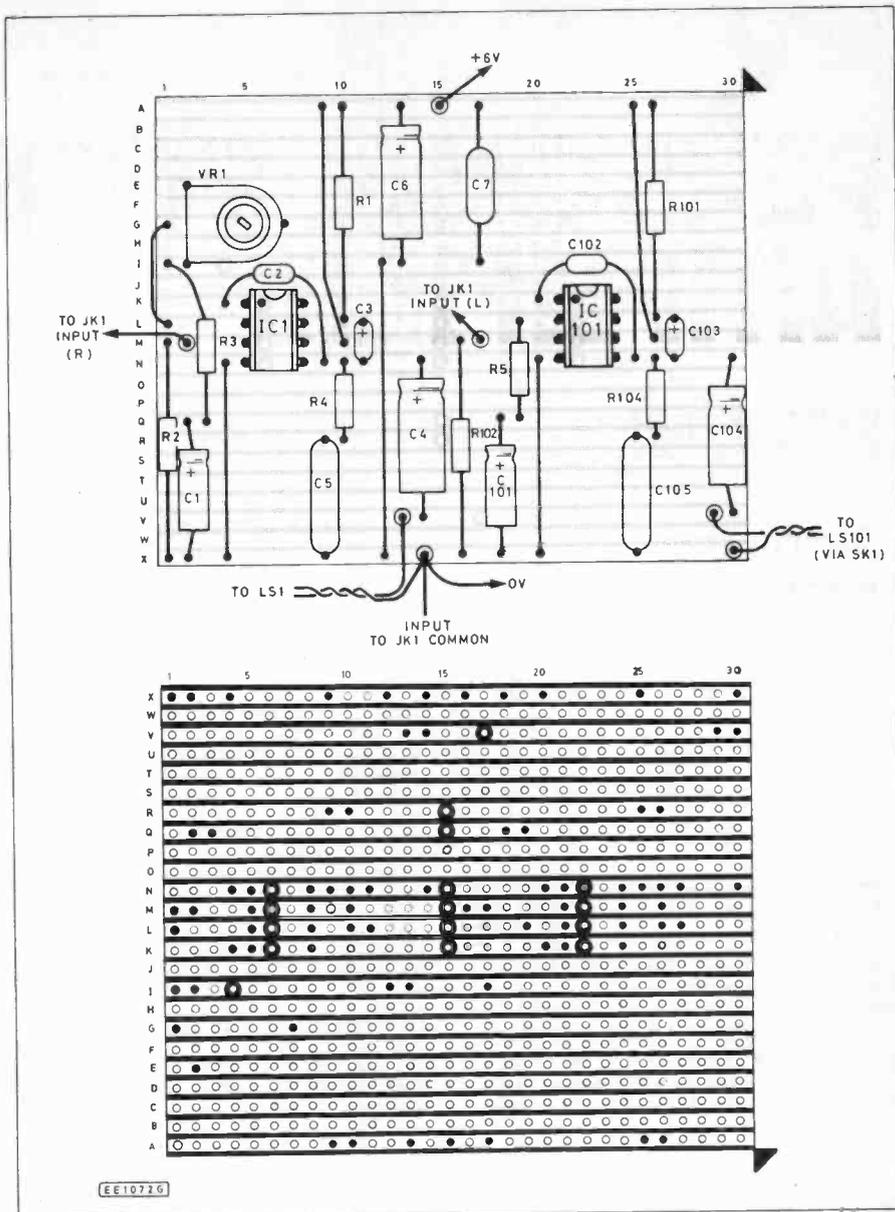


Fig. 2. Components layout and wiring.

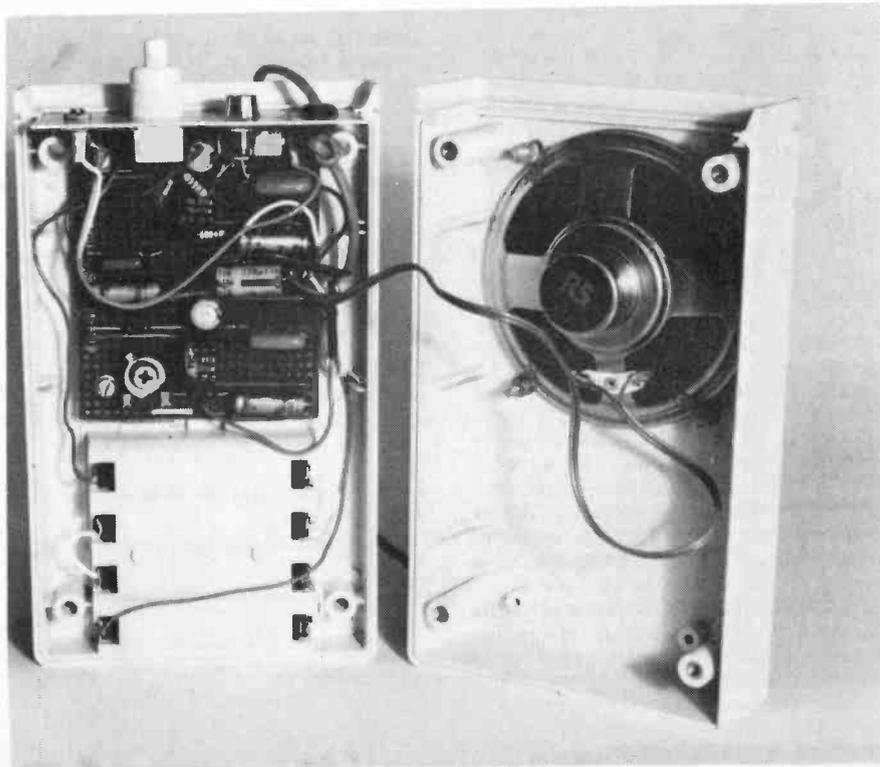

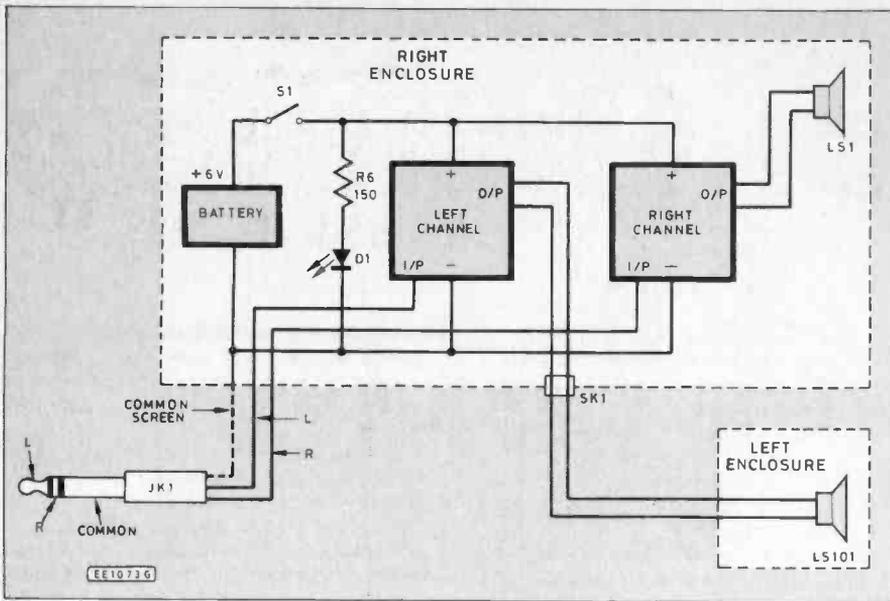


Fig. 3. Interconnection of the various parts of the amplifier system.

CONSTRUCTION

The circuit may be accommodated on a small piece of strip-board as shown in Fig. 2. Before beginning assembly, check that the board will fit neatly into the intended enclosure (see later). Take note of points at which holes will need to be made through the board for mounting screws or bolts. It may be necessary to adapt the component layout slightly to allow for these.

First cut the copper strips beneath the board at the locations shown in Fig 2. Then solder in the connecting wires, followed by the resistors. Finally mount the other components, taking care to observe the correct polarity of the electrolytic capacitors.

The off-board connections are shown in Fig 3. Wiring up the connections depends on the type of case used for the enclosure. In the prototype an enclosure with a built-in battery compartment was used. The spring contacts for the individual cells were not already connected, so it was necessary to solder short wires so as to join the cells to form a 6V battery (Fig 4). The enclosure had a panel at one end. This was drilled for mounting the sockets and controls as shown in the photographs.

A push-on-push-off switch was used for S1, as this type is cheap and simply needs a circular hole for mounting. However, in a tightly packed suitcase or backpack, such a switch can be turned on by jolting or accidental pressure during the course of a journey. This could soon result in the cells becoming discharged. If you are concerned that this may happen, fit a slide switch instead. The light-emitting diode is not strictly necessary. It consumes about 10mA but, since it acts as a warning that the power supply is on, it probably saves current in the long run. Fig 3 shows the connection to the tape player. The stereo jack plug JK1 is connected by a two-core screened lead to the circuit board. This lead passes through a grommeted aperture in the front panel.

Before mounting the circuit board in its case, check the circuit carefully against the diagrams. Make sure all joints are properly soldered, and that there are no solder bridges between adjacent copper strips. It is worth while to inspect the underside of the circuit board using a hand lens at this stage

as even the finest "hair" of solder can prevent a circuit from working.

The case used for the prototype had four conveniently placed mounting pillars on the bottom half. The circuit board was drilled to match these, and self-tapping screws used to fix the board to the case. If the case you are using does not have such pillars, the board may be fixed in place with bolts, or with "sticky fixers".

SPEAKER ENCLOSURES

The speakers can be mounted in any type of enclosure, depending on the preference of the reader. It would be possible to use two existing speakers from a stereo system. For the prototype, which was intended to be a highly portable system, two identical cases just large enough to hold the miniature speakers were used, and (in one of them) the circuit board and cells were also mounted. Although it is slightly uneconomical to use a case with battery compartment for the left channel speaker, it is preferable to have matching cases. The battery compartment of the left-channel enclosure is a handy place for storing spare cells.

Before mounting the speakers in the lids of the cases, mark the inside of the lids to show where the speakers are to be located. When deciding where to place the speakers take account of the positions of the battery compartment, the circuit board and other

Fig. 4. Battery connections.

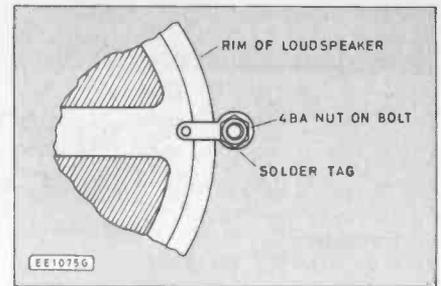
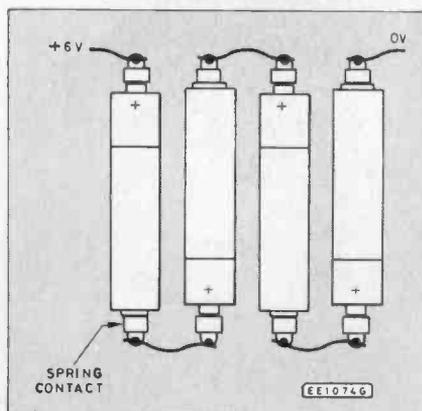


Fig. 5. Loudspeaker mounting.

components in the other half of the case. A radial pattern of holes drilled through the lid of the case with a 1mm bit, make a robust "grille".

Four holes suited to 4BA bolts are drilled just outside the edge of the loudspeaker area. The four bolts each have a solder tag, and a nut threaded on them. The solder tags are turned inward to overlap the rim of the speaker (Fig. 5). The nuts are then tightened, so that the rim of the speaker is gripped firmly by the tags.

With all components mounted, the various connections are made as in Fig 3, using multistranded connecting wire. The pair of wires from the left channel speaker should be about one to three metres long and terminate in a mono jack plug to fit the socket on the panel of the right channel enclosure. Next, place the lids on the cases. Inspect carefully as you place the lid on the right channel case to ensure that the speaker does not come into contact with the circuit board or any other components. The lid of the left channel case may be bolted in place, but leave the other lid off until the system has been tested.

TESTING

Put four cells into the battery compartment, arranging them as Fig 4. Set VR1 to about the middle of its track. Insert the stereo jack plug into the earphone socket of a tape player. Insert the mono jack plug of the left channel speaker into the correct socket on the panel of the right channel case. Set up the two cases on the bench with speakers a metre or two apart and facing toward you. Switch on. The l.e.d. should glow and there should be a slight crackle from the speakers as the switch is operated. If there is no light, no crackle, or there is continuous whistling or crackling etc, switch off and re-examine the circuit board and other connections.

Assuming that all appears to be well. Place a tape in the player, turn the volume setting of the player well down (the amplifiers have high gain), and start the player. Turn the tape-player volume up to the required level. Check that sound is coming from both speakers. Now adjust VR1 until an equal volume of sound is obtained from each speaker and a realistic stereo effect is obtained. The resistance values quoted for VR1 and R3 are such that it should be possible to make the right channel sound either louder or softer than the left channel. If the right channel sounds louder than the left no matter what the setting of VR1, then replace R3 with a resistor of higher resistance, such as 100 ohms. Conversely, if the volume on the right channel is always too low, replace R3 with a resistor of smaller value, such as 27 ohms.

Having established the correct setting of VR1, switch off, replace the lid on the right channel enclosure and bolt it in place. The stereo tape amplifier is now ready for use. □

Robot Roundup

NIGEL CLARK

COCKROACH

The dream of a mechanical cockroach is fast becoming reality. It is complete mechanically and is in the process of having its software developed further to allow it to perform as well as intended in the original specification.

Dr John Billingsley, of the Electronic and Electrical Engineering Department of Portsmouth Polytechnic, and leader of the project said that the software for the first phase was now complete and work had begun on the second phase. At the moment the central processor was telling each of the legs what to do and when but it was intended that the central system would only issue general commands leaving the legs to work out how to achieve them.

This however is no toy mechanical insect. It is a serious attempt by a team at the polytechnic to create a new type of walking robot. The idea to model the device on a cockroach came from Arthur Collie, one of the members of the team. Cockroaches do not have central nervous systems and so cannot control their movements centrally as most creatures do. The legs work independently moving one step in response to a stimulus with obstacles sensed by the inability to go through with a step. When the concept first came to Collie about ten years ago it was not feasible to have six independent legs because of the size and cost of the individual controllers. The microprocessor changed that. Now with the help of grants from the Royal Society, the Science and Engineering Research Council and a little help from the armed forces unmanned vehicle programme Collie has taken two years off from his job to work on the idea.

Billingsley said that the present software was quite sophisticated with constant checks being carried out to see if the instructions were being followed. However, it was still a system of big brother giving orders from the centre.

'Each of the legs is being told to go through a set procedure of picking up, moving forward and putting down again. We want the only instruction to be to walk with a particular combination of legs, it would then be up to the legs how that was achieved.'

When the project began Billingsley said he was searching for a cantering, rather than a walking, robot. That was a reference to the intention for the device to mimic the movement of humans who while walking are dynamically stable but statically unstable. They are permanently off balance while moving and although they are stable, if they come to a sudden halt they will fall over as when being tripped up. Existing walking robots remain stable throughout their movement. While they gain in steadiness they lose on speed and fluency of motion.

The most usual form of movement by the cockroach is based on stable triangles. While the first and third legs of one side and the middle leg of the other remain steady, supporting the machine, the others move. With the weight towards the front of the device the centre of gravity, during movement, does not yet move in front of lines between the first and middle legs of each side, thus keeping it stable at all times. Human-like movement is being planned.

At the moment the movement is force driven to ensure that each leg continues

moving until it finds something solid to stand on. However, the robot is still a little wobbly because of some software problems.

Each leg has joints at the hip and knee. The thigh is powered by two pneumatic cylinders working in opposite directions so that movement is always achieved by a cylinder pulling rather than pushing, with a double acting cylinder for the hip. Feedback is obtained from pressure sensors on the cylinders and angle sensors on the joints.

MOUSE AND ROBOT


Two of Billingsley's other interests are progressing during the summer. On September 15 in Portsmouth the European finals of the Robot contest this year are taking place as part of the EuroMicro Conference. And the Institution of Electrical Engineers is hosting the World Finals of the Micromouse competition.

Billingsley is hoping that the Robot event goes better than last year's European finals in Venice when Britain's John Knight was the only person to achieve a hit of the ball with the bat. The Finnish team could not get their machine through customs and the Belgian device did not work. There were also problems with the table and running repairs were required necessitating the finding of a hardware shop in Venice (with no knowledge of the Italian for the relevant items!). Portsmouth may not be as exotic but it should enable a better contest to take place.

Billingsley is also hoping that some new entrants will take part. The British heats were held by the IEE in July and some enquiries had been received from newcomers but at the time of writing it was not known if there were any new faces to challenge Knight and Dr John Marr. In addition sponsors are being sought to help with prizes and the costs of holding the event. Anyone who would like to help should contact Billingsley at Portsmouth Polytechnic.

The MicroMouse contest, which has been taken over by the IEE, was also held in July. It was given the grand title of World Finals because the Americans are holding the event next year and said that they were going to designate them the world finals. However it was thought unlikely that the Japanese would be appearing because of the cost, this, despite beating all European opposition when a contest was held in Tokyo last year.

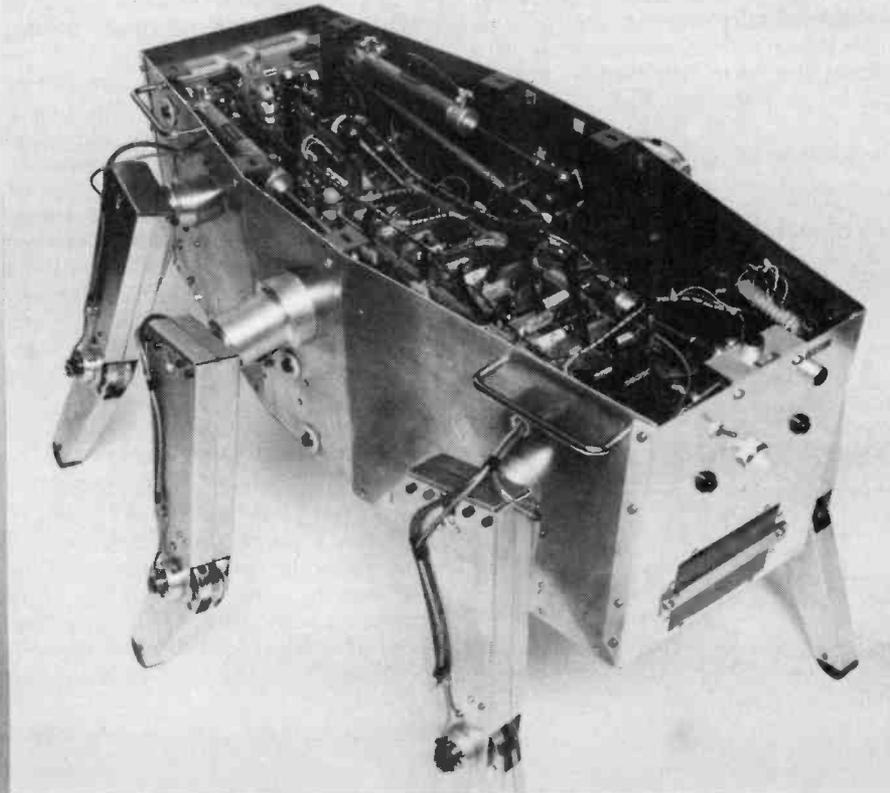By using what was considered by most of the regular competitors as an out-of-date design they managed to reach the centre of the maze far more quickly than the more "sophisticated" models. The Japanese were still using stepper motors instead of the faster d.c. motors but by staying with a basic design and continually making improvements they had developed some very efficient machines.



USING A

MULTIMETER

Mark Stuart

What to look for, its limitations and how to use one of the most versatile of test instruments.

LIKE most electronics enthusiasts my tool kit started with a screwdriver, a pair of pliers and a soldering iron. The first "measurements" that I needed to make were simple and crude. There were three very common questions to answer:

Is the battery flat?

Has the fuse blown?

Is the "power" getting through?

Without knowing it I was asking about the three basic electrical units — **voltage**, **resistance** and **current**. With the aid of a battery and a bulb I was able to get some indication of all three, using the methods shown in Fig. 1.

With experience I was able to judge voltage and current by the brightness of the bulb, and by using the fuse checking arrangement I was able to test some low value resistors as well as fuses. I got by using these methods for quite some time until the great day arrived and I carefully unpacked my first multimeter. With this prized possession I was able to measure voltage, resistance and current accurately over wide ranges. The real beauty of it

though, was that I could use it in exactly the same way as my battery and bulb. The principles were exactly the same, only the quality of the equipment had changed.

As my electronics knowledge advanced I learned that my multimeter also had some shortcomings. Just as the battery and bulb method had its limitations, so too did the multimeter. The multimeter of course got much nearer to telling me exactly what was happening, but it wasn't always telling me everything, and sometimes it could be quite a long way from the truth. In fact, I had a good deal more to learn about electrical and electronic measurements as the rest of this article shows.

VOLTAGE MEASUREMENTS



In Fig. 1a the basic principle of voltage measurement is shown. Voltage appears *across* components in a circuit and so is measured by putting the meter leads one each end of the component, that is, in parallel. To illustrate some typical measurements

the circuit of the *Active Infra-Red Burglar Alarm project* (March '87 EE) is reproduced in Fig. 2.

The most common measurement made in circuits of this kind are voltage measurements. The reason for this is that unlike currents, voltages can be read without breaking the circuit. For example, the first sensible check on a circuit is to measure the supply voltage. A simple multimeter set to the 25 volt d.c. range could be used with the negative probe (usually black) connected to point (a) and the positive probe (red) to point (b).


The next check would be to move the positive probe to point (n) to read the Zener stabilised supply voltage across D2. To measure the collector voltage of TR1, the positive probe is moved on to point (d) still keeping the negative probe connected to point (a). A great deal can be learned about a circuit by voltage measurements made in this way.

With most circuits all of the voltage measurements are made from a common point (in this case point (a)) usually the negative supply point. The voltage at points (b), (n), and (e) are said to be measured "with respect to negative". Voltages may be measured with respect to any suitable point in a circuit or across individual components. For example the voltage across R11 is measured by putting the negative probe on point (r) and the positive probe on point (p).

OHMS PER VOLT

So far the voltages measured have all been from "low impedance" points in the circuit and will read accurately. If the meter is connected to read the voltages at points (c) and (g) (with respect to negative) the readings will be low. The reason for this, is best ex-

Fig. 1. First attempts at "measuring" Voltage, Resistance and Current with a battery and bulb.

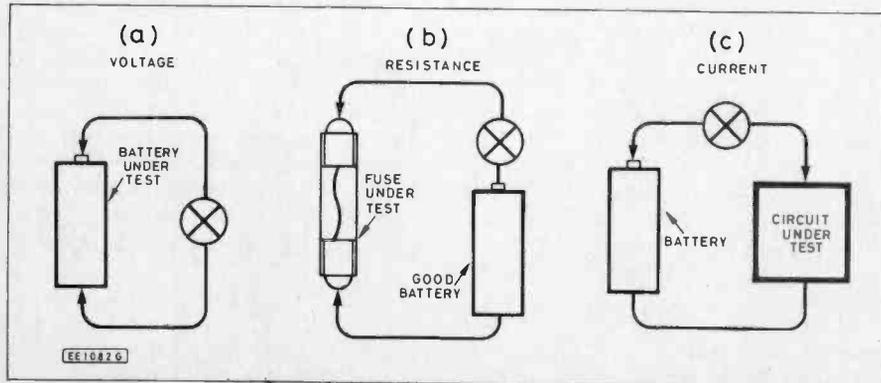

plained by reference to Fig. 3 which shows the internal circuit of a multimeter when set to its voltage ranges. The meter movement is essentially a current measuring device, the construction and operation of which has been described elsewhere.

To convert a basic 50 microamps meter movement into a voltmeter, a series resistor is used. The value of a resistor is calculated from Ohms law so that it passes 50 microamps at the required full scale voltage. For example a 10 volt range needs a resistor of 10 volts divided by 50 microamps that is $10/0.00005$ ohms = 200,000 or 200k. The other ranges are calculated in a similar way, giving 500k for 25V and 2M for 100V. A value of 50 microamps has been chosen as this is an extremely common value for standard multimeters.

The expression "ohms per volt" which appears in multimeter specifications is derived by working out the series resistor that would be required

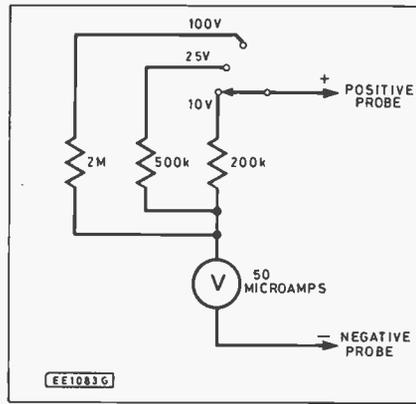


Fig. 3. Circuit diagram of multimeter Voltage ranges—10V; 25V and 100V.

the current flowing through R6 and into the base of TR1 is two microamps. If the multimeter is set to the 10 volt range its resistance is 200k. At 0.6 volts 200k draws a current of $0.6/200,000$ or

where there are high value resistors, voltages will read lower than they really are.

AVERAGE READING

Another situation where a multimeter doesn't tell the whole truth is when the voltage at point (j) is measured (with respect to negative). At point (j) there is not a steady voltage, but one which varies one hundred times a second from approximately 14 volts to 16 volts. The meter will try to follow the voltage, but fail, because it can't move quickly enough. The result is an average reading of 15 volts. For most purposes an average reading is adequate, but it gives no indication of the ripple voltage. This is simply a job that a multimeter can't do. The best instrument for this is an oscilloscope.

Other points in the circuit will also give misleading readings. For example, point (h) oscillates between 0V and +10V, spending half of its time in each state. The meter will read the average

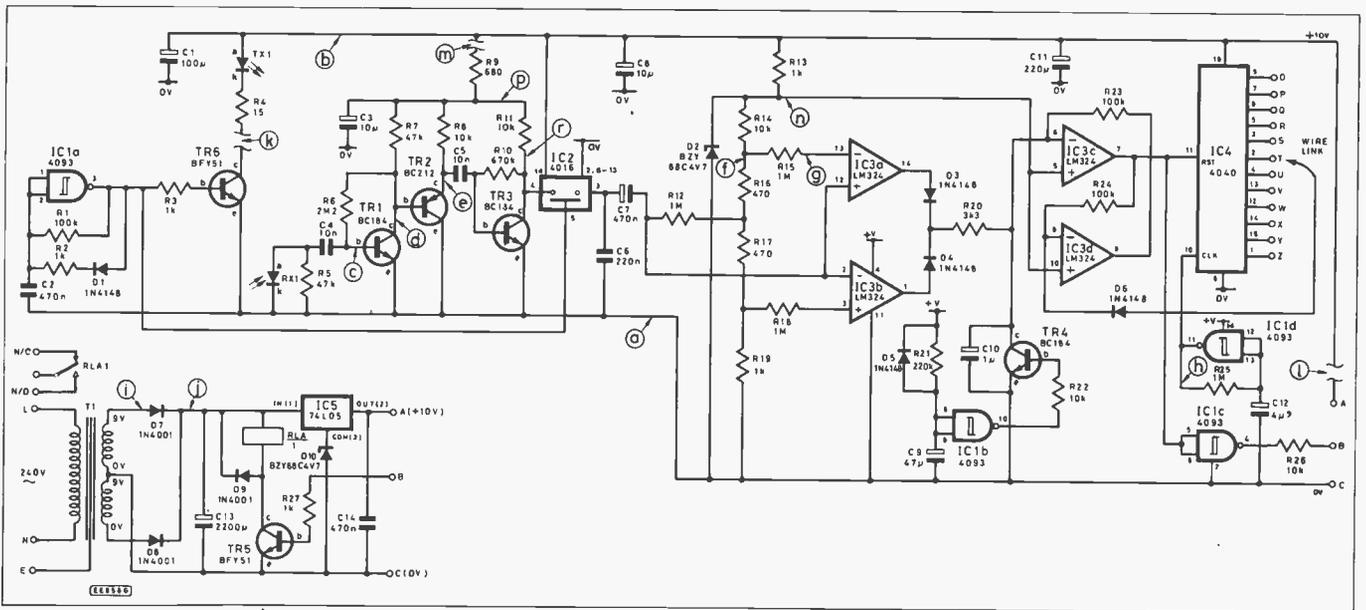


Fig. 2. Some typical measurement "test points" in a working circuit for an Active Infra Red Burglar Alarm (EE Mar '87). Points k, l, and m indicate where current measurements are made.

to give a full scale voltage of one volt. For a 50 microamp meter, it is $1/0.00005 = 20k$. A multimeter with a 50 microamp meter is therefore a "20 kilohms per volt" type. The best (most sensitive) analogue multimeters are based on a $10\mu A$ movement and so have a sensitivity of $1/0.00001$ or 100k per volt.

How this affects the circuit under test depends upon how easily the circuit can supply the 10 or 50 microamps that the meter requires. Power supply points such as (b) and (n) can supply an extra 50 microamps without any difficulty, but to sensitive parts of the circuit such as points (c) and (g) 50 microamps represents a heavy current drain that substantially affects circuit operation.

In the case of point (c) the actual voltage in the circuit is 0.6 volts and

three microamps. Since this is more than the current already flowing in the circuit there is not enough current to drive the meter properly and so the meter reads low.

Similarly when the voltage at point (g) is measured the current required by the meter is drawn from point (f) via R15. As the voltage here is approximately one volt the meter requires five microamps on the 10 volt range which must be drawn through R15. Now, to get five microamps through one megohm takes five volts (Ohms law again). As there is only one volt available it is obvious that the meter will read very low. In fact the meter will read 0.2 volts which is miles away from the true voltage.

If all the arithmetic here is a bit too much, don't worry, the principle is simply that at points in the circuit

voltage which is five volts, but give no indication of the oscillation.

The voltage at points (d), (e) and (r) will give one reading when the infra-red beam is being received, and another reading when it is not. In many circuits voltage differences such as this do occur and sometimes service sheets or manuals give two sets of voltage readings. The "quiescent" voltages are usually those found when the circuit is operating normally but without an input signal, and are the most commonly quoted ones.

Despite these imperfections, voltages measured with a multimeter are still the simplest and most effective "first approach" to circuit testing. The number of voltage measurements made using multimeters each day must exceed the numbers of all other electrical measurements put together.

RESISTANCE MEASUREMENTS



The measurement of resistance is much more straightforward than voltage measurement but the meter circuit is slightly more complicated. Fig. 4 shows a simplified standard multimeter circuit for resistance measurement. Resistors R1, VR1, and R2 are simply to make the 50μA meter movement into a voltmeter reading 0 to 3 volts. The variable resistor (VR1) allows the sensitivity to be varied slightly so that full scale deflection can still be achieved when the battery voltage falls to 2.5V. The three range resistors R3, R4, and R5 are selected individually by the range switch S1.

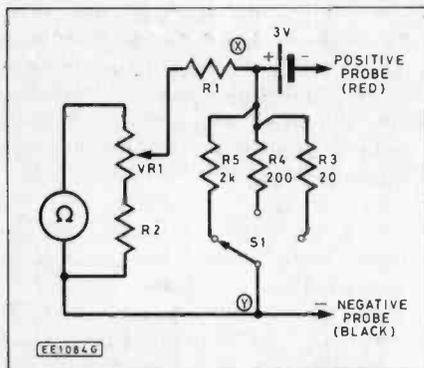


Fig. 4. Circuit diagram of multimeter Ohms ranges—20 ohms; 200 ohms and 2 kilohms (2k).

When the probes are touched together the full battery voltage is connected across whichever range resistor is in circuit and the meter reads full scale. If necessary, adjustment of VR1

can be made for exactly full scale. When the probes are separated the battery negative terminal is no longer connected anywhere and there is no deflection of the meter. These two extremes represent zero resistance (or short-circuit) and infinite resistance (or open-circuit) respectively. The scale of the meter reads backwards because zero resistance corresponds to full scale deflection and infinite resistance to no deflection.

When an unknown resistance is connected across the meter terminals, the battery is no longer connected directly across the range resistor. Instead, it is connected to the range resistor via the unknown resistor. If the unknown resistor is equal to the range resistor, half of the battery voltage will appear across each, and the meter will read centre scale deflection. So with the three range resistors given, centre scale is obtained by measuring resistors of 20ohms, 200ohms and 2k. For those who want to do the arithmetic the deflection for other values of resistance is given by dividing R (Range) by (Range) plus R_X where R_X is the unknown resistor.

For the 20ohm range this gives a deflection on the 50 microamp meter corresponding to nine microamps for 200ohms, 33 microamps for 10ohms, 25 microamps (centre scale) for 20ohms and a tiny deflection of one microamp for 2k ohms. A glance at any multimeter resistance scale will show that this is non-linear, and is especially cramped at the high resistance end.

If there are sufficient ranges (usually four or five) however, it is possible to get satisfactory readings from one ohm

to one megohm. Higher resistance readings can also be obtained but it is necessary to have a higher voltage battery. Some multimeters have provision for two batteries, the higher one being switched into circuit when the highest resistance range is selected.

Apart from measuring resistance, one of the other uses of the k ohms ranges is to make simple checks for continuity, and to test diodes.

DIODES

When testing diodes it is essential to bear in mind this very important fact: The RED Probe is NEGATIVE and the BLACK Probe is POSITIVE.

This comes about because of the need to keep the negative terminal of the meter movement permanently connected to the negative probe. The construction of the meter and the switching arrangements are made much simpler by this means. Referring to Fig. 4 should help to make it plain. Over the years this polarity reversal has been accepted as "standard" and all conventional analogue multimeters are the same. Digital meters and electronic meters, however, have more complicated switching arrangements and, as if to add to the confusion, have their positive output on the red probe for ohms measurement. If in doubt the best way is to keep a known diode handy. Usually resistor values are measured by first removing the resistor from circuit.


In-situ measurements can be made but often the readings will be low because of other components forming parallel paths. This is particularly so in circuits with transistors and i.c.s. For example the value of R7 in Fig. 2 could be measured in theory by connecting the probe between points (p) and (d).

With the black probe on (d) and the red probe on (p) a correct reading could be obtained, but with the probes reversed a parallel path via R8 and the base-emitter junction of TR2 is introduced leading to a reading nearer to 15k.

In a situation like this where one way the resistance is lower than the other way, it is always true that the higher value is nearer to the correct reading.

If the resistance reads the same in both directions it is probable that the value is correct, but by no means certain, because there could be purely resistive parallel paths in existence.

A final note on resistance ranges: Make sure that the circuit is switched off whenever resistance measurements are made. A glance at Fig. 4 shows that on the resistance ranges all that exists between the probes is a battery and the range resistor. Connecting a power supply across this unlucky combination is a frequent source of smoke as the range resistor is destroyed. Luckily the meter movement itself is usually adequately protected by R1, but it's better not to put it to the test.

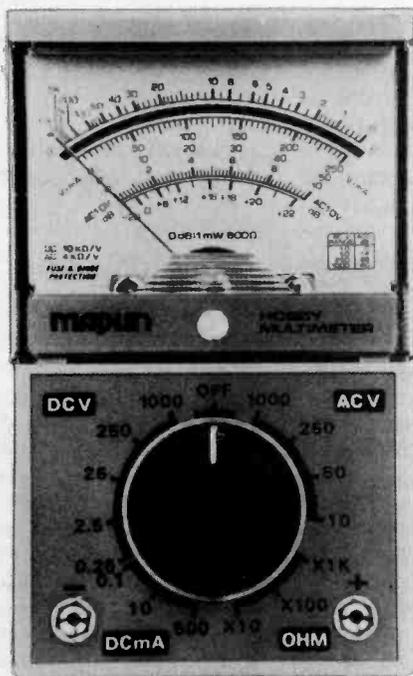

The Hobby Multimeter from Maplin has 10k/V d.c. and 4k/V a.c. sensitivities. The meter also features a clear, easy to read, mirrored scale for accurate reading.—Maplin Supplies ☎ 0702 552911



The HM-102BZ multimeter from Cikit is protected against accidental overload, has a continuity test buzzer and a jack socket for measuring audio output voltages. The meter is rated at 20k/V d.c. and 8k/V a.c.—Cikit ☎ 0992 444111



The general purpose Miselco Mini 20 from Alcon Instruments boasts an easy to read mirrored scale, single knob switching and sensitivities of 20k/V d.c. and 4k/V a.c.—Alcon Instruments ☎ 01-352 1897

CURRENT MEASUREMENTS

(A)

Current measurements are made by breaking the circuit and inserting the meter. Whilst voltage is measured across components current passes through them.

The multimeter current ranges circuits are shown in Fig. 5. As with the voltage circuit the current circuit is very straightforward. The three resistors are known as shunts because that is their function.

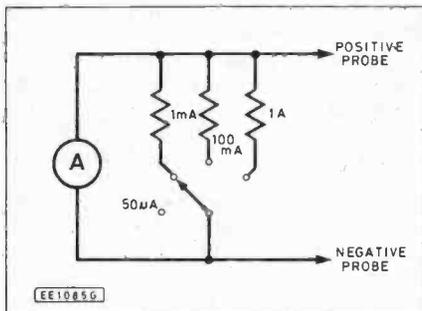


Fig. 5. Circuit diagram of multimeter Current ranges—1A; 100mA and 1mA.

For example on the 1mA range 950 microamps flow through the shunt resistor whilst 50 microamps flow through the meter. On the one amp and 100mA ranges the same principle applies, with all but 50 microamps flowing in the shunt resistors. To calculate the value of the shunt resistors (here comes some more arithmetic) the meter movement resistance needs to be known. In the case of most standard 50 microamps meters this is 2k. The value of the current that must flow in the shunt if first calculated e.g. for 1mA the shunt current is 1mA minus 50 microamps which equals 950 microamps. The shunt value can then be worked out as follows: Shunt value = meter movement current times meter resistance divided by shunt current.

For 1mA this gives: 0.00005 times 2000 divided by 0.000950 which gives

105 ohms. The other shunt values are one ohm and 0.1 ohm for the 100mA and 1A ranges respectively.

The measurement of the power supply current of the Infra-Red alarm in Fig. 2 is taken by breaking the circuit at point (1) and inserting the meter. When measuring an unknown current it is wise to start with the highest range (in this case one amp) so that the meter is not overloaded. The range switch can then be advanced until the best range is reached. The alarm circuit takes approximately 20mA so is best measured on the 100mA range.

SERIES RESISTANCE

When the meter is put into the circuit it adds another series resistance which has some effect on the current being measured. In this instance when set to the 100mA range the meter shunt resistance one ohm is added to the circuit. With 20mA flowing a resistance of one ohm produces a voltage drop of 20 millivolts. This is not significant in 10 volts, but there are sometimes situations where the extra voltage drop of a meter can have a significant effect. An example of where meter resistance begins to cause problems is given when measuring the current in the Infra-Red emitter circuit (point (2)). The current is not continuous but instead is a series of pulses of approximately 0.5 amps with a mark-space ratio of 100 to 1. The average current is therefore 0.5 divided by 100 or 5mA.

Connecting the meter into circuit adds an extra one ohm to the 15ohms already present (R4) and so the pulse current is reduced. The average current reading will be lowered from 5mA and will read one part in 15 lower than the true value.

Another problem encountered when inserting a multimeter into power supply circuits is that sometimes even a small extra resistance can cause severe

instability and violent circuit oscillation. In these conditions the meter reading will be quite different from the true circuit current. In general, current measurements are relatively trouble-free and accurate, without the huge errors that can occur when making voltage measurements.

A.C. MEASUREMENTS

(B)


So far the voltage and current measurements made have all been in d.c. circuits. Another essential requirement is to be able to measure alternating currents and voltages, particularly at mains frequency. The usual way to achieve a.c. measurements is simply to put a diode in series with the meter. The meter is thus fed with a half wave rectified signal which it averages to produce a constant reading. A separate set of series resistors and current shunts are required so that the meter reads correctly.

In most meters it is assumed that the a.c. signals being measured will be sine waves and that the frequency is in between 10Hz and 5kHz. Some better meters give a wider frequency range. In general the meter manufacturers take some liberties with a.c. measurements, particularly a.c. current, based on the fact that the main use of such ranges is to measure power supply voltages and currents where an error of up to ten per cent can be acceptable. High quality expensive multimeters have elaborate a.c. ranges often using special transformers to step up the voltage so that the rectifier circuits can work to their very best.

The main problem encountered when taking a.c. measurements is that any departure from a sine wave signal will produce inaccurate readings. A square wave and a pulse waveform will both give strange readings, and as the waveform is not usually known to the meter user it is very hard indeed to get meaningful results. It is safest to stick to reading mains frequency sinewave signals, and leave the rest until an oscilloscope is available.


CONCLUSION

Having spent most of this article discussing the drawbacks and limitations of multimeters I think I should say that I find my multimeter to be indispensable. There are very few circuits that can't be examined or repaired with its aid. My toolkit is now much more extensive than 25 years ago when that first multimeter arrived, and in those years the changes in electronics have been incredible. Sadly I no longer have the original meter—I dropped it downstairs some time ago, and before that I blew the 20 ohm range resistor by trying to measure a power supply voltage with the meter set to k ohms. □

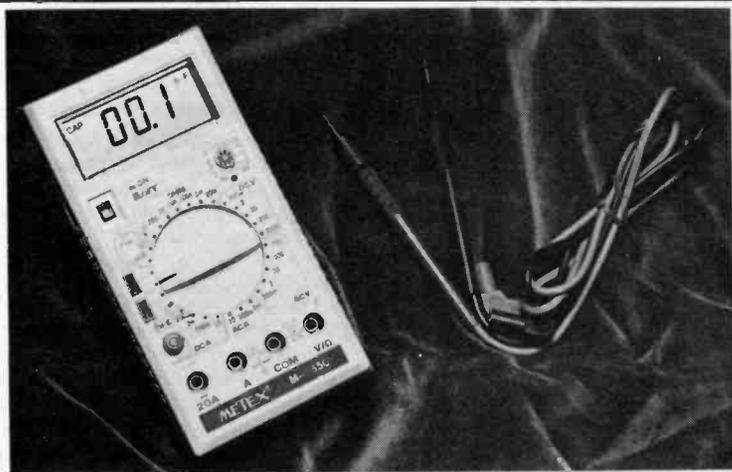

The new breed of multimeters now boast ranges with digital displays. The very latest Metex M-3650 from Crotech also has special facilities for testing transistor hFE, measuring capacitors (2000pF to 20µF) and for taking frequency measurements up to 200kHz
—Crotech Instruments ☎ 0480 301818

SHOP TALK

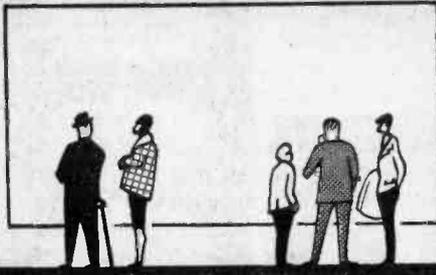

BY DAVID BARRINGTON

Catalogue Received

With the possible call on the stocks of one of Europe's largest component suppliers, they claim to carry a bank of over 30,000 parts, Smith Electronics have issued a 100-page "International Electronic Catalogue" entitled *Electronic Actuell*.

With items ranging from circuit boards to complete kits, the catalogue is fully illustrated and contains special "buy line" panels. It also lists test equipment and computer peripherals.

Although all descriptions are in English, the prices are given in Deutsch Marks. Even so, the catalogue is free to EE readers and is well worth adding to the book library. To obtain a copy, send a large (A4) stamped, addressed envelope to: **Smith Electronics, Dept EE, 157 Chapel Street, Leigh, Lancs WN7 2AL.** (☎ 0942 606674).

Kits and Modules

Knowing the amount of interest we received when, a few years ago, we published a design for a *Digital Rule* working on "doppler shift principles", readers might like to explore the possibilities of the latest "Distance Measuring Instrument" from **Xen-Electronics** of the Isle of Wight.

The *EE Rule* was only capable of measuring fairly short distances whereas the Xen module, working on similar principles, is claimed to be capable of distances, between two parallel objects, of up to 26ft. With the addition of an optional display board the unit will give a digital readout of distance measured.

By adding a low cost (£2.95) parabolic reflector it is claimed that distances up to 65ft have been achieved.

Ideal for DIY enthusiasts for measuring a room for either wallpapering or carpeting, the Xen instrument could also be used for robotics, height gauge or even vehicle reversing applications. Another application that springs to mind, is that by using several "reflectors" strategically placed around a room or valuables it might form the basis of an intruder alarm.

The basic kit, comprising printed circuit board, components and ultrasonic transducer, costs £22.95 plus VAT (built and tested £34.95 +VAT). The kit price for the l.c.d. Display Board is £13.95 plus VAT (£17.95 +VAT ready-built). The Parabolic Reflector costs £2.95 plus VAT. A postage and packing charge of £1.15 per order must also be added.


For further details of the Distance Measuring Instrument contact: **Xen-Electronics, Dept EE, Unit 4, Samuel Whites Estate, Medina Road, Cowes, Isle of Wight PO31 7LP.** (☎ 9083 292847).

One of the latest excellent bargain modules from **Greenweld Electronics** is a low voltage power supply claimed to be

capable of operating at up to 2A output.

The Astec type AA7271 is a six transistor, "switched mode" power supply module built on a neat, 50mm square, printed circuit board. The circuit will accept low voltage inputs up to 24V d.c. and give a stable 5V d.c. output at up to 2A. The circuit also incorporates current overload protection, thermal cutout and excellent filtering.

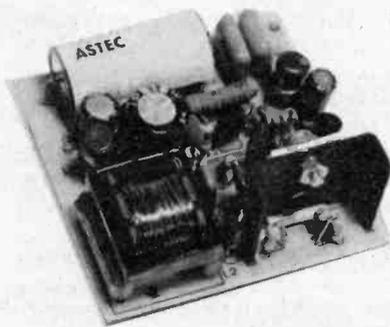The Astec AA7271 switched mode power supply module is being offered at an all inclusive price of just £5. For further details of their many other "summer specials" contact **Greenweld Electronics, Dept EE, 443 Millbrook Road, Southampton, SO1 0HX.** (☎ 0703 772501).



CONSTRUCTIONAL PROJECTS

Electronics Analogue/Digital Multimeter

The low noise diodes used in the prototype *Electronic Analogue/Digital Multimeter* were types BAS45. Provided that they are "classed" as low noise, almost any general-purpose or signal diodes should work in this circuit. However, there may be slight variations in meter performance from device to device.

Digital panel meter modules are now stocked by quite a few companies and, provided they will operate from a 9V supply, readers should not experience any difficulties in selecting a suitable display module. The module used by the designer was a 3½ digit LCD type, with 10mm display digits, stocked by Magenta.

A complete kit (£44.72), including the printed circuit board, is available from **Magenta Electronics, Dept EE, 135 Hunter Street, Burton on Trent, Staffs DE14 2ST.** Add £1 for p&p per order. The printed circuit board is available from the *EE PCB Service*, code EE579 (see page 516).

Car Overheating Alarm

Most of the parts required for the *Car Overheating Alarm* appear to be standard components and should be available, "off-the-shelf", from most of our advertisers.

However, a couple of items may possibly cause local sourcing problems.

The glass bead thermistor type GL16 used in the prototype is currently listed by Maplin, code WH23A. This thermistor has a resistance of 1Megohm at 20°C and a maximum operating temperature of 300°C. The GL16 seems to be rather expensive at £4.95 and other bead thermistors may be used, provided they are capable of operating within the range of the above characteristics.

Finally, be sure to use the light-duty automobile type cable and connectors were specified. These items should be available from most car spares shops.

Burst Fire Mains Controller

We cannot foresee any component buying problems when ordering parts for the *Burst Fire Mains Controller*. Note that the capacitor C1 is a 250V a.c. suppression type and it is important to point this out when ordering.

The mains transient suppressor VDR1 should be available from most component stockists and should not prove difficult to purchase. The one in the author's model was purchased from Maplin. Also, be sure to ask for a potentiometer with a plastic spindle when ordering VR1.

The printed circuit board is available separately through the *EE PCB Service*, code 578 (see page 516).

Noise Gate

A couple of items need special attention when ordering components for the *Noise Gate*.

When ordering the front panel mounted potentiometers, VR1 and VR2, be sure to specify "logarithmic" types. Also, note that the working voltage rating of the capacitors is a *minimum* rating and should not be less than that specified, particularly C6. It is quite in order to use types which have a higher working voltage rating.

Some readers may experience difficulty in locating a suitable p.c.b. mounting mains transformer for this project. The one used in author's prototype is a Colne type (code 3543) and was purchased from MS Components Ltd., (tel: 01-670 4466) Cat No. 700. Although it may need to be "hard wired" to the p.c.b., it should be possible to use one of the many excellent mains transformers stocked by advertisers, such as **Barrie Electronics** (01-555 0228).

The printed circuit board for this project is available through the *EE PCB Service*, code EE577 (see page 516).

Personal Stereo Amplifier

All components for the *Personal Stereo Amplifier* are standard items and should not cause any purchasing problems. The 2W power amplifier i.c., type TBA820M, is a fairly popular device and is listed or stocked by practically all of our advertisers.

The loudspeakers can be mounted in almost any type of enclosure, the prototype use two plastic instrument cases with battery compartments, and the final choice is left to the individual constructor. The case should have enough room to take the circuit board and speaker. Existing enclosures can be used if they are rated at 8 ohms.

We do not expect readers to experience any component buying problems for the *Exploring Electronics* project or the *Light Pen*—this month's *On Spec* project.

For KITS & COMPONENTS -
Choose the easy way - with *refundable with first order*

Send **50p* & SAE**
for CATALOGUE

ORDERS: RING (01) 567 8910 - 24 HRS.

NEW ELECTRONIC GUARD DOG KIT



One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need is a mains supply, intruder detector and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.

XK125 Complete kit of parts £21.95


DISCO LIGHTING KITS

DL1000K - This value-for-money 4-way chaser features bi-directional sequence and dimming. 1kW per channel. **£17.50**
OLZ1000K - A lower cost uni-directional version of the above. Zero switching to reduce interference. **£9.85**
OLA/1 (for DL & OLZ1000K) Optional opto input allowing audio 'beat' /light response. **70p**
OL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel **£14.25**

The **DL8000K** is an 8-way sequencer kit with built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80! different sequences including standard flashing and chase routines. The kit includes full instructions and all components (even the PCB connectors) and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light LED and a 300 W output per channel.

And the best thing about it is the price.

ONLY £28.50

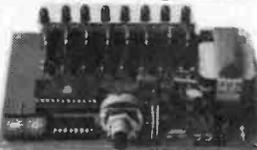

TEN EXCITING PROJECTS FOR BEGINNERS

This Kit has been specially designed for the beginner and contains a **SOLDERLESS BREADBOARD**, **COMPONENTS**, and a **BOOKLET** with instructions to enable the absolute novice to build **TEN** fascinating projects including a light operated switch, intercom, burglar alarm, and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.

ORDER NO XK118 £13.75

XK102-3-NOTE DOOR CHIME

Based on the **SAB0600 1C** the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a **PP3 9V** battery and push-switch to complete.

AN IDEAL PROJECT FOR BEGINNERS £6.00

XK113 MW RADIO KIT

Based on **ZN414 IC**, kit includes PCB, wound aerial and crystal earpiece and all components to make a sensitive miniature radio. Size: 5.5 x 2.7 x 2cms. Requires **PP3 9V** battery.

IDEAL FOR BEGINNERS £6.00

VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (excluding transformer) 9 x 4 x 2 cms. The companion transmitter is the **MK18** which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available—**MK9** (4-way) and **MK10** (16-way), depending on the number of outputs to be used.

MK12 IR Receiver (incl. transformer) £14.85
MK18 Transmitter £7.50
MK9 4-Way Keyboard £2.00
MK10 16-Way Keyboard £5.95
601 133 Box for Transmitter £2.60

HOME LIGHTING KITS

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300W of lighting.

TDR300K Remote Control Dimmer £18.45
MK6 Transmitter for above £4.95
TD300K Touchdimmer £8.50
TS300K Touchswitch £8.50
TDE/K Extension kit for 2-way switching for TD300K £2.70
LD 300K Light Dimmer £4.35

NEW POWER STROBE KIT

Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5Ws strobe tube and full assembly instructions. Supply: 240V ac. Size: 80 x 50 x 45.

XK124 STROBOSCOPE KIT £12.50

NEW HIGH SECURITY LOCK KIT

Designed for use with our lock mechanism (701 150) this kit will operate from a 9V to 15V supply drawing a standby current of only 50µA. There are over 5000 possible 4-digit combinations and the sequence can be easily changed. To make things even more difficult for an unauthorised user an alarm can be sounded after 3 to 9 incorrect entries—selectable by means of a link. The alarm can sound for a few seconds to over 3 minutes during which time the keyboard is disabled preventing further entries. A latched or momentary output is available making the unit ideal for door locks, burglar alarms, car immobilisers, etc. A membrane keyboard or pushbutton switches may be used and a beep sounds when a key is depressed. Kit includes high quality PCB, all components, connectors, high power piezo buzzer and full assembly and user instructions.

XK121 LOCK KIT £15.95
350 118 Set of Keyboard Switches £4.00
701 150 Electric Lock Mechanism 12 volt £16.50

PROPORTIONAL TEMPERATURE CONTROLLER KIT

Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max. load 3kw (240V ac) Temp. range up to 90°C. Size: 7x4x2.5cms.
MK4 £7.10

PACK A
 650 x 25W Resistors 47R to 10M
£4.25

PACK B
 60 x Electrolytics 1µf x 1000V
£3.25

PACK C
 35 x Polyester Capacitors 10µf-1µf
£4.50

PACK D
 35 Horizontal Presets 1K to 1M
£3.00

PACK E
 30 x IC Sockets 8, 14 & 16 pin
£2.00

PACK F
 25 Red LEDs 5mm
£1.75

PACK G
 25 Green LEDs 5mm
£2.00

PACK H
 30 x 5mm LEDs Red, Green, Yellow
£2.50

PACK J
 50 x 1M4148 Si. Diodes
£1.00

PACK K
 40 x NPN/PPN Transistors BC107/210 General Purpose
£2.25

SPECIAL OFFER
 10% OFF if you buy ALL TEN PACKS

TOOLS ★ TOOLS ★ TOOLS



Good quality tools selected to offer outstanding value for money.

650 004 6in mini. Snipe Nose Pliers. Serrated jaws and return spring. **£2.10**
650 005 6in lap jointed side cutters. Insulated handles and return spring. **£2.10**
650 008 Light duty cutters. Cutting capacity 0.2-1.2mm copper wire. **£1.60**
TOOL KIT - Contains: side cutters, snipe nose pliers, wire strippers, flat blade screwdriver, philips screwdriver in black textured, reinforced and padded case which when opened out measures 240x205mm **£6.80**



650 007 Self-adjustable automatic wire stripper with built-in cable cutter. **£3.95**
650 012 Watchmakers Screwdriver Set. 1.0/1.4/2.0/2.4/3.0/3.8mm **£1.75**
650 019 Set of 4 Stainless Steel Tweezers. Straight nosed, straight nosed-reverse action, bent nosed, flat nosed. 110mm long. **£3.65**
650 502 Reliant 9-12V dc Drill. **£6.90**
650 500 Titan 12V dc Drill. **£10.25**
650 570 Saturn Mains Drill. **£16.50**
WE ALSO STOCK ANTEX IRONS AND ACCESSORIES

LOGIC PROBE



A MUST for working with TTL & CMOS devices. Displays logic levels and pulses down to 25ns with LEDs and sound. Comprehensive instruction booklet supplied. Working voltage 4-16V dc Input Impedance 1M Max. i/p frequency 20MHz

ONLY £9.50

RECHARGEABLE SOLDERING IRON

Powerful cordless iron complete with table-top/wall-mounting charging bracket. Reaches soldering temperature in 10 seconds. Includes lamp which lights when soldering. Comes with mains charging unit and 12V car battery adaptor. **£17.95**

HELPING HANDS

Magnifier and crocodile clips on ball and socket joints mounted on a heavy base. Ideal for holding and inspecting PCBs during soldering, fault finding, etc. **(650 035) £3.95**



MW RADIO

SCOOP PURCHASE ONLY £19.95!!!
 Comprises ready-built AM Tuner module (superhet), separate audio amp with volume control and miniature speaker. All you have to do is connect these three items to a 9V battery. Full instructions supplied. AVAILABLE WHILE STOCKS LAST.

HANDY MULTIMETER

An ideal multimeter for the hobbyist featuring 20kV input impedance, 19 ranges including 10A d.c., battery checker and continuity buzzer. Supplied complete with test leads, battery and instruction manual. As recommended for the EE "Teach In" series. Dimensions: 135mm x 89mm x 40cm. AC Volts: 0-50-250-1kV (5%). DC Volts: 0-2.5-10-50-250-1k DC Current: 0-5-10-500mA-10A Resistance: 10k-100k-10M dBs: -20dB to +62dB

Part no. 405104 **£12.95**

P.C.B. ETCHING KIT

Ideal starter pack. 2 pieces Copper Laminated, Circuit Etchant, Etch Resist Pen, 7 Assorted Transfer Sheets and Tray. Full and comprehensive instructions on laying out and etching your own PCB designs. **£5.20**

SOLAR POWERED NICAD CHARGER

Takes up to 4 x AA size. Charges 2 batteries in 4-8 hrs., 4 in 10-14 hrs. depending on strength of sunlight. Ideal for boating, caravanning, modelers, etc. **£5.95**

VELLEMAN KITS

We stock the full range of Velleman Kits. Why not try one of these!
K1771 Miniature FM TRANSMITTER (50mW). 9-12V DC. Frequency: 100-108MHz. Ideal for babyphone, etc. **£6.50**
K2572 STEREO PRE-AMPLIFIER **£7.93**
K2583 HEATING CONTROLLER. Enables four temperatures to be set and maintained for set periods in a day. Display shows time or temperature. **£75.76**
K2638 CAR ALARM. Easy to mount. No false alarms. Adjustable entry/exit times. Automatic reset prevents discharging of battery. **£16.80**
K2603 YEAR TIMER. Standard memory - 40 steps expandable to 240 steps. Non-volatile memory holds program without any power source. Auto-start after power failure. Two programmable "sleep" times. 4 relay outputs - one relay (3A/240V) supplied with kit. Extra relays (K2632). Membrane keyboard and housing included. (Transformer not included.) Size: 241x118x59mm. **£132.30**
K2632 Hardware extension kit **£19.20**
TR2603 Transformer for K2603 **£8.40**
 Send see 12" x 9" for full catalogue.

TR ELECTRONICS
 13 BOSTON RD
 LONDON W7 3SJ
 Tel: 01-567 8910

SEND 9"x6" S.A.E. & 50p FOR CATALOGUE OR CALL AT SHOP MON-FRI 9-5pm SATURDAY 10-4pm

ORDERING INFORMATION: ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P: Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002.

LOCAL AUTHORITY AND EXPORT ORDERS WELCOME GOODS BY RETURN SUBJECT TO AVAILABILITY





a regular feature for the Spectrum Owner...

by Mike Tooley BA

THIS month's constructional project provides users with a simple five-key keypad which can be used for control applications and also makes an excellent alternative to a conventional joystick for fast moving games by providing "fingertip" rather than "lever yanking" control! We begin, however, by describing some simple software routines and interface circuitry for use with the five channel optically isolated input interface described last month.

Five-bit Input Interface Software

In last month's *On Spec* I glibly mentioned that the state of the five input channels of the optically isolated interface can be more easily sampled from machine code than from BASIC. The reason for this is simply that the Z80 instruction set contains a number of useful "bit test" instructions. These instructions allow the programmer to examine the state of individual bits within the CPU registers. Subsequent code can then branch depending upon the outcome of the bit test.

Alternatively we can simply flag the results of our bit test back to BASIC using a value returned in the BC register pair. We shall briefly examine both of these techniques but first, it is worth briefly outlining the method used to read the joystick port from machine code.

Reading the Joystick Port

The joystick port can be easily read using the following code:

```
0E FE joyread LD C,#FE;Read the keyboard with
06 EF LD B,#EF;A0 and A12 low and the
ED 78 IN A,(C); address in BC, then return
C9 RET to the ;calling routine
```

The single line address decoding employed in the Spectrum ULA associates address line A0 with the keyboard such that, when both the A0 and input/output request (IORQ) lines are taken low, the state of the keyboard is placed on the data bus. The keyboard thus has binary, decimal and hexadecimal addresses of 11111110, 254, and FE respectively. Joystick 1 corresponds to the row of keys extending from "6" to "0" which is decoded from the keyboard

matrix by taking address line twelve (A12) low (whilst all of the other upper eight address lines remain high).

To accomplish this task in BASIC we can simply use IN 61438 (A0 and A12 will both be low) but in machine code we must use the BC register pair (either loading B and C separately as in the example above or, saving one byte of code, by loading the BC register pair with EFFE in one go!). In either case we can then read the state of the port by executing an IN A,(C) instruction. Note that the contents of the B register will appear on the upper eight address lines when the IN A,(C) instruction is executed and hence the data from the relevant keyboard row is then transferred into the accumulator. The five least significant accumulator bits represent the five joystick switches according to the following table:

Bit	Joystick
0	fire
1	up
2	down
3	right
4	left

Bit Testing

Now, to return to the main theme, we can examine the state of each individual channel of the five channel optically-isolated input interface we can test the state of the channel(s) in which we are currently interested by using the Z80 BIT instruction. Suppose that we have an application in which channels 1 and 2 (corresponding to bits 0 and 1) are to be repeatedly sensed and, depending upon which channel is active we wish to make the Spectrum's border colour either red (channel 1 active) or green (channel 2 active). Furthermore, we will assume that channel 1 is to have precedence and that, if neither channel is currently active, the border should be black.

```
inport EQU #EFFE ; input port address
border EQU #229B; ROM border routine
red EQU 2
green EQU 4
black EQU 0
ORG #A000; Relocatable
01 FE EF readin LD BC, inport; Get ready for input
ED 78 IN A, (C) ; fetch current port status.
CB 47 BIT 0,A ; Is channel 1 active ?
28 0A JR Z,redon ; If so, act on it!
CB 4F BIT 1,A ; Is channel 2 active?
28 0C JR Z,greenon; If so, act on it!
3E 00 LD A,black ; Neither is active
CD 9B 22 CALL border; so make it black and
C9 RET ; go back
3E 02 redon LD A, red ; Channel 1 is active
CD 9B 22 CALL border; so make it red and
C9 RET ; go back
3E 04 greenon LD A,green ; Channel 2 is active
CD 9B 22 CALL border; so make it green and
C9 RET ; go back
```

The above code is not particularly elegant but has been presented in a form which, hopefully, most readers will be able to understand. Those familiar with machine code may have spotted that there is a much simpler solution to this particular problem which does not involve using the bit test instructions. For the benefit of the curious here it is;

```
inport EQU #EFFE ; Input port address
border EQU #229B; ROM border routine
ORG #A000; Relocatable
01 FE EF readin LD BC,inport; Get ready for input,
ED 78 IN A, (C) ; fetch current port status
07 RLCA ; Shift left and
2F CPL ; invert the result then
CD 9B 22 CALL border; drop into the ROM
before
C9 RET ; going back
```

The second program does almost the same as the first program and readers wanting a challenge are invited to suggest what the difference is and why it occurs!

Both demonstration routines may be tested using an assembler (e.g. Hisoft's DEV-PAC) however those not having access to an assembler need not despair. Both routines have been given with the resulting object code given in hexadecimal form. To enter the code into your Spectrum all that is required is our *On Spec* hexloader (available in the current *On Spec* package). All you will need then do is to choose a suitable start address for the code (e.g. A000 hex, or 40960) and enter the hex bytes from the left hand column of the listings. Then save the program for future use before exiting to BASIC for testing. A suitable BASIC program for calling the routine would be as follows:

```
10 REM Five channel input port demo.
20 RANDOMISE USR 40960
30 GOTO 20
```

The alternative method of flagging the outcome of a bit test back to BASIC is also quite straightforward as witnessed by the following example which produces a low pitched BEEP if channel 1 is active and a high pitched BEEP if channel 2 is active. Channel 1 again has precedence and no BEEP is produced if neither channel is active:

```
inport EQU #EFFE ; Input port address
ORG #A000; Relocatable
01 FE EF readin LD BC,inport; Get ready for input and
ED 78 IN A, (C) ; fetch current port status.
CB 47 BIT 0,A ; Is channel 1 active?
28 08 JR Z,lobeep ; If so, branch ...
CB 4F BIT 1,A ; Is channel 2 active?
28 08 JR Z,hibeep ; If so, branch ...
01 00 00 LD BC, 0 ; Neither is active so flag
C9 RET ; a zero and return
01 01 00 lobeepLD BC,1 ; Channel 1 is active so
C9 RET ; return with 1
01 0A 00 hibeepLD BC,10 ; Channel 2 is active so
C9 RET ; return with 10
```

A suitable BASIC test program would then take the following form:

```
10 LET z=USR 40960
20 IF z<>0 THEN BEEP 0.1,z
30 GO TO 10
```

Finally, it is worth mentioning that you don't need to have a completed five channel optically isolated input interface to hand in order to test any of these routines! For those who just want to try out the code, both programs can be tested using the "0" and "9" keys to simulate inputs on channels 1 and 2 respectively. In the case of the first two programs, if you hold the "0" key down when the code is running you should be rewarded with a red border. Holding the "9" key down, on the other hand, should produce a green border and, when neither key is held down, the border should revert to black. In the case of the last program,

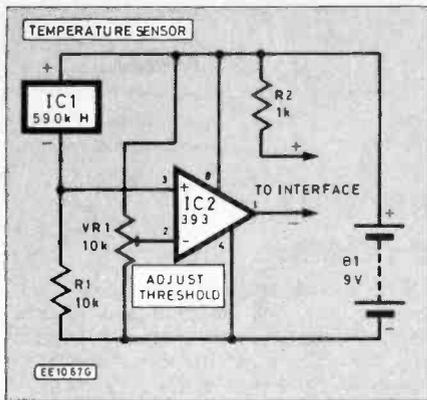


Fig. 1. Temperature sensor signal conditioning (NB: No series limiting resistor need be used within the interface).

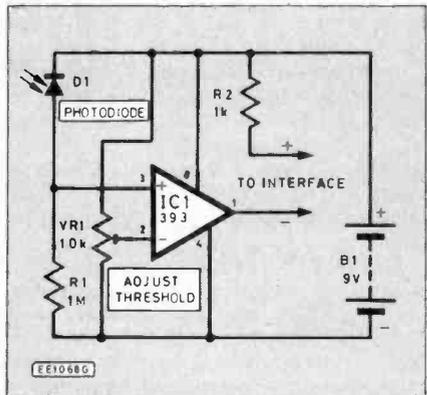


Fig. 2. Light level sensor signal conditioning (NB: No series limiting resistor need be used within the interface).

pressing the "0" key should result in a low frequency BEEP whilst pressing the "9" key should produce a high frequency BEEP. When neither key is held down, no sound should be emitted.

Temperature and Light Level Sensing

With the aid of suitable transducers and a single comparator chip, the five channel interface circuitry can easily be extended to permit sensing of temperature and light

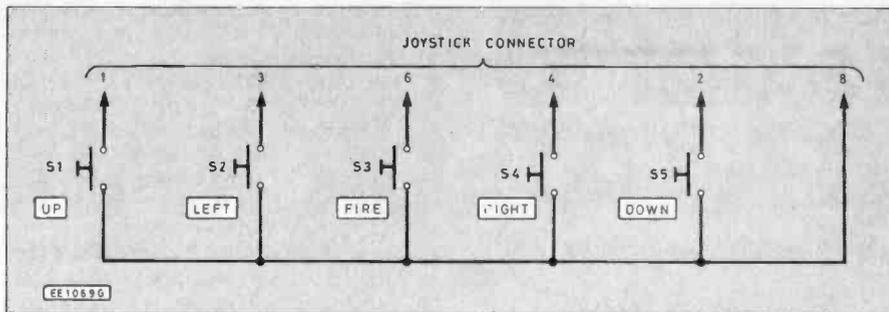


Fig. 3. Keypad circuitry (NB: See July EE for Spectrum Plus Two joystick connections).

levels on a simple "high"/"low" or "above"/"below" basis. Typical additional circuitry is shown in Fig. 1 and 2. Neither of these circuits is at all critical as regards layout, component tolerances, or adjustment and a wide range of commonly available temperature and light level sensors will operate successfully in this configuration.

Five-key keypad

The five-key keypad is designed to replace the five switches fitted to a standard joystick. The minimal circuitry of the five-key keypad is shown in Fig. 3. The switches are low profile p.c.b. mounting types which are fitted to a small piece of 0.1inch matrix stripboard following the layout shown in Fig. 4. The keys should be arranged so that they fit comfortably below the user's fingers and the spacing should be adjusted accordingly.

The matrix board assembly should be mounted in a small plastic case (that used in the prototype measured 112mm x 62mm x 31mm). The switches are connected to the joystick interface by a length of multi-core cable terminated with a female nine-way D connector (connections given in July's instalment of E.E. or send for our Update).

If you have any comments or suggestions or would just like a copy of our *On Spec Update*, please drop me a line enclosing a large (at least 250m x 300mm!) stamped addressed envelope. Mike Tooley, Department of Technology, Brooklands Technical College, Heath Road, Weybridge, Surrey KT13 8TT.

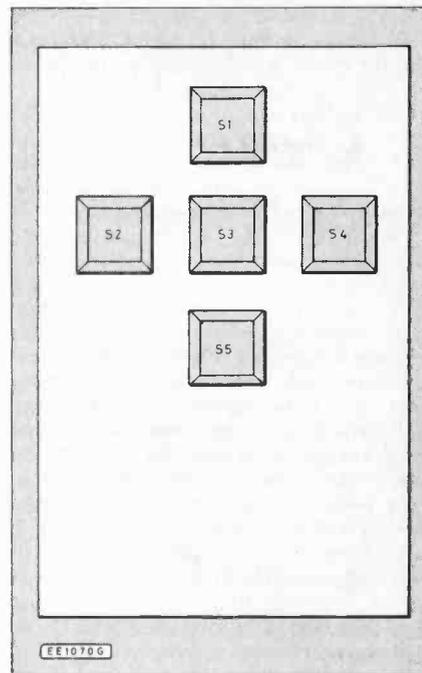


Fig. 4. Suggest keypad layout using low profile p.c.b. mounting switches.

Next month we shall be describing a versatile counter/timer interface based on the Z80-CTC. We shall also have some further notes for those wishing to incorporate machine code routines within their own programs.

PROTEUS

The Shadow of Shargan

—No13 OUT NOW

PROTEUS—THE BEST SOLO ROLE PLAYING GAME
MAGAZINE AVAILABLE
ON SALE AT YOUR NEWSAGENTS NOW—85p

FREE
FANTASY
POSTER
INSIDE



...REPORTING AMATEUR RADIO...

TONY SMITH G4FAI



NEW FREQUENCY ALLOCATIONS

Despite my gloomy prognosis last month on the possibility of the future reductions in the amount of radio spectrum allocated to radio amateurs—arising from the DTI sponsored report "Deregulation of the Radio Spectrum in the UK"—there is some good news for the moment.

The DTI has announced that as from 1st June, 1987, both the 50MHz and the 70MHz amateur allocations are expanded and, even better, these bands are now available for use by class B licensees.

The 50MHz band, covering 50-000 to 50-500MHz was made available to amateurs from 1st February, 1986, following a trial period with a limited number of authorised stations, as was reported in this column in February and April, 1986. Now the band has been expanded to cover 50-000 to 52-000MHz, although there are still restrictions on the power and the type (and height) of antenna to be used, to avoid interference to television transmitters which are still operating on these frequencies in Europe.

UK amateurs have "primary" status on 50-000 to 51-000MHz and "secondary" status on 51-000 to 52-000MHz, meaning that operation in the latter is subject to not causing interference with other services. A further relaxation is that portable (/P) or temporary premises (/A) operation is now permissible, although mobile (/M) is still not allowed on this band.

The 70MHz band was previously 70-025 to 70-500MHz, and is now expanded to 70-000 to 70-500, remaining unchanged as a secondary allocation.

ENTER THE "B" LICENSEES

While the extra spectrum allocation is good news, the big news from the amateur point of view is that class B licensees, representing nearly half of all licensed amateurs in the UK, who were previously restricted to frequencies above 144MHz, can now use these two lower frequency bands.

Class B operators now have the opportunity to obtain long distance (DX) contacts far more often than they have on the v.h.f. bands previously available to them. Many countries of the world have amateur allocations at 50MHz, although there are not many in Europe. Even in low sun-spot conditions there are occasional "openings" permitting contacts with the USA and Canada, and as conditions improve during the new sunspot cycle B licensees previously delighted with the occasional "lift" conditions across Europe on two metres, will enjoy rare and exotic DX around the world.

On 70MHz, the situation is different. It has never been a popular band with A licensees except for contests, because only the UK, Gibraltar, and Eire have regular allocations.

Many B licensees may find, however, that they get better inter-UK results than

on two metres, covering greater distances with lower powers and more modest antennas. This could now become quite a popular band, with increased activity attracting even those who previously spurned it.

TIME-BOMB!

So its good news all round this month, and the Radio Society of Great Britain is to be congratulated on obtaining these valuable new concessions for amateur radio. But in the midst of their euphoria they would do well not to ignore the time-bomb quietly ticking away in the corner—the recommendation to the government by management consultants (reported last month) that far from amateurs having additional spectrum allocations, they should have less. At the risk of being called a misery-bags, I can't help wondering how long it will be before I find myself reporting not additions, but reductions in amateur frequency allocations!

AMATEUR RADIO FOR THE HANDICAPPED

Sometimes when I work other amateurs on the air they will mention in passing that they are "white stick" (i.e. blind) operators, or that their equipment has been modified to help them overcome some form of handicap.

Quite often, local amateurs will have helped them study for and pass the Radio Amateurs Examination (RAE), erect their antennas, and instal their equipment. They sometimes go on to say just how much amateur radio has expanded their immediate horizons, and how helpful they find it.

They need not have told me any of this, and if they hadn't I would probably have never known their situation. This is the great advantage of amateur radio for the handicapped—in most cases they can meet other amateurs over the air on equal terms. Whatever their disability, means can usually be found for them to put out signals sounding no different to anyone else's.

Although such operators rarely need help to actually operate their stations, they do need help or advice in setting them up in the first place. To this end, The Radio Amateur Invalid and Blind Club (RAIBC) was founded in 1954 as a self-help organisation to enable blind and handicapped people to pool their knowledge and skills, and to benefit from each other's experience.

HELP AVAILABLE

The range of assistance to help with particular disabilities is wide. For those studying for the RAE, cassettes of textbooks are available for the visually handicapped, and special arrangements are made for those who are blind, or unable to travel or write, to take the RAE orally (or to take the Morse test) in their own homes.

Once they have their licences, devices are available to help those with limited sight, for instance, to tune their equipment aurally instead of visually. Other disabilities can be overcome—even deafness—by adapting standard equipment to suit needs of most individuals, and when speech itself is difficult Morse code operating, sometimes with special keying arrangements, comes into its own.

Members of RAIBC keep in touch with each other through the Club's magazine *Radial*, and through regular "nets" on the air. The magazine gives news of members and their activities, future events, details of equipment for sale or wanted, and other relevant information for handicapped amateurs.

There are Club nets on the air every day of the week, including an international one on 14-290MHz on Thursdays at 1400 hours and Saturdays at 0730. Apart from licensed amateurs there are many listeners to these nets, often also handicapped in some way, and the exchange of news and views which takes place is widely disseminated to an appreciative audience.

While members help each other and undertake a good deal of fund-raising themselves, the RAIBC also receives valuable support from non-handicapped amateurs. Clubs and other organisations donate money, some regularly, while individuals act as helpers to members in preparing for their examinations, installing, modifying or repairing equipment, and providing general support and encouragement where needed.

There is a continuing need for such help, which is always much appreciated. If you feel you could assist in any way, even if you are not a licensed amateur, please contact RAIBC, 9 Conigre, Chinnor, Oxon.

Members operating a special event station during an RAIBC "open day" at the Wedgwood Electrical Collection, in Christchurch, Dorset, last year.



SPECIAL OFFER...



CIRCULAR RADIO CONTROL MOVIT KIT

£16.95
including VAT and
postage


This fascinating unit will provide hours of interest and pleasure. The Circular Movit consists of two large wheels each independently driven by an electric motor and gear train; these are housed in discs between the wheels. A battery pack and the control electronics are housed in plastic domes fitted to the outside of each wheel. The whole unit is controlled from a hand held radio control transmitter.

The Movit comes as a kit of parts plus full instructions for assembly — the electronic control units are supplied built and tested. Enjoy building it, be fascinated by operating it!

EE Movit Offer, Commotion Ltd., 241 Green Street, Enfield, Middlesex EN3 7TD. Tel: 01-804 1378.

Please supply		Value
Quantity	Circular Movit @ £16.95	
Overseas readers add £3.00 postage		Total £
Please make cheques payable to Commotion Ltd.		
Visa/Access or Cheque No.....		
Signature.....		
Name.....		
Address.....		
.....		
.....		
OFFER CLOSES Friday, October 23, 1987		
Name.....		
Address.....		
.....		
.....		
Post to: EE Movit Offer, Commotion Ltd., 241 Green Street, Enfield, Middlesex EN3 7TD Telephone orders: 01-804 1378		

BLOCK CAPITALS PLEASE

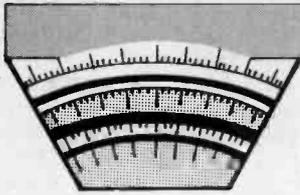

1.999

ELECTRONIC ANALOGUE/DIGITAL MULTIMETER

MARK STUART

A versatile test instrument for the workshop

THE DESIGN of an Electronic Analogue/Digital Multimeter was a very interesting exercise in compromise. During the course of its development a great deal of respect was gained for the designers of what were considered to be "ordinary" commercial instruments.

The basic electronic circuit for Voltage, Current, Resistance, and A.C. Measurements are fairly easy to deal with when taken individually, but combining them into a compact hand-held unit with a single range switch is another matter.

After some thought, it was concluded that the only solution suitable for home construction would be a "bench" meter and to incorporate a number of separate range switches. The idea of a single multi-pole multi-way switch was considered, but the price, and the complicated wiring that would be necessary completely ruled this out.

Two advantages of using separate range switches are that the switches can be printed circuit board mounting types—so eliminating wiring and wiring error and that parts of

the circuit can be built separately and used individually in other applications.

The "indicating device" specified is a panel meter with a 100 μ A sensitivity. This is modified by means of a series resistor to read 0-1V. Almost any standard panel meter can be used, or instead one of the new digital panel meter modules could be added.

The overall performance of the meter is very good, its frequency range when measuring a.c. voltages and currents is good up to 50kHz and the input impedance of 10 Megohms on all voltage ranges gives good accuracy in high impedance circuits where a normal analogue multimeter would be useless.

In addition to the standard range the meter has an "A.C. Millivolts" circuit which allows audio frequency measurements from 3mV r.m.s. up to 1V and is very useful for testing amplifier signal levels, microphone and pick-up outputs, frequency responses and general signal tracing.

The resistance ranges have the benefit of a linear scale that reads from left to right instead of the usual non-linear, reverse reading scales, also the probes are correctly polarised—that is red is positive—when making Ohms checks. All resistance measurements are made at a maximum of 100mV so in-situ measurements will not be affected by transistors, i.c.s and diodes in the circuit.

Other features are that the meter is protected from overloading by a fuse and electronically, and measurements up to 1000V and 10A a.c. and d.c. are possible. The meter is built in a fully insulated case for safety.

CIRCUIT DESCRIPTION

The full circuit diagram for the Electronic Analogue/Digital Multimeter is shown in Fig. 1. For clarity each section will be described separately.

VOLTAGE

Inputs for voltage measurements are applied to the voltage divider chain made up of resistors R2 to R7. Voltage ranges are selected by S1a, which taps off a proportion of the input voltage from the divider chain and passes it to IC1, the input amplifier circuit.

On the 1kV range an extra resistor (R1) is added to the top of the divider. To avoid having high voltages on the circuit board this resistor is made up from a series combination of values which are sleeved and mounted in the lead to the 1kV terminal (SK3).

The input impedance of the circuit is set by the total combined value of R2 to R7 which is 10 Megohms. In order to make accurate measurements on all ranges it is essential that the input amplifier circuit has an impedance which is in excess of 50 Megohms.

Use of a f.e.t. input amplifier i.c., TL071, and careful board layout ensures that this is achieved. IC1 does not have any gain, but it acts as a buffer circuit with a very high input impedance and a low output impedance.

From IC1 the signal passes to a second amplifier stage IC2 via resistor R32. S1b switches resistor R33 in and out of circuit on alternate ranges to give the 3V, 30V, and 300V ranges.

The combination of resistors R32 and R33 is such that the signal is reduced by 3 to 1 on each of these ranges but remains unaltered on the 1V, 10V, and 100V ranges. The amplifier IC2 has a gain of 10 and its output is applied to the meter movement via switch S5 when d.c. measurements are selected.

A.C. VOLTAGE

The circuit as far as the output of IC2 is identical for A.C. and D.C. ranges. Capaciti-



tors C1, C2, C3, C4, and C5 correct for the effects of stray capacitance and maintain a level frequency response to above 50kHz.

When a.c. measurements are made the meter is connected via switch S5 to the output of the rectifier circuit IC5. This circuit takes its input from IC2 and produces a half-wave rectified output which is averaged by the meter movement to give a steady d.c. reading.

Diodes D3 and D4 in the feedback loop around IC3 are connected so that on negative half-cycles the output stays at 0V, but positive half-cycles are passed normally with a gain of just over 2.

The value of gain is selected so that the meter reads the average value of the incoming signal and indicates the correct (r.m.s.) voltage. As with all meters the accuracy of a.c. readings depends on the signal waveform. Sine waves are the most frequently encountered and so the meter is set to read correctly for these.

Diodes D7 and D8 across the meter protect it from being overdriven when switching ranges etc. Diodes D1 and D2 provide similar protection for IC1.

CURRENT

On the Current range the shunt resistors R8 to R13 are connected in circuit by S3a and the voltage across them read by the standard voltage circuits. S2a selects the value of shunt resistor and S3b makes the connection between the shunt resistors and the input of IC1.

The values of the shunt resistors are selected to drop 100mV at the full scale current. A shunt of one ohm will give full scale reading on the meter when a current of 100mA is passing and so on.

For the 10A range a shunt value of 0.01 ohm is required. This is made from a length of wire connected directly between the 10A socket (SK4) and the negative (Common) socket SK2. This is necessary because the

range switch is only rated at 1A, and the p.c.b. copper tracks would have to be huge to carry 10A comfortably.

The a.c. and d.c. current measurements are treated by the amplifier section in exactly the same way as voltages. The current ranges increase in direct decades ($\times 10$) so that the use of S1b is not involved. Switch S3c ensures that this is switched out of circuit on all ranges except voltage.

RESISTANCE

Resistance is measured by passing a known constant current through the resistor under test and measuring the voltage drop across it using the standard voltage circuits.

The current source consists of IC4, transistor TR1, and associated components.

A reference voltage of 5.6V from Zener diode D5 is connected to the non-inverting input of IC4. Negative feedback around IC4 via TR1 and resistor R42 works in such a way that the emitter voltage of TR1 is made

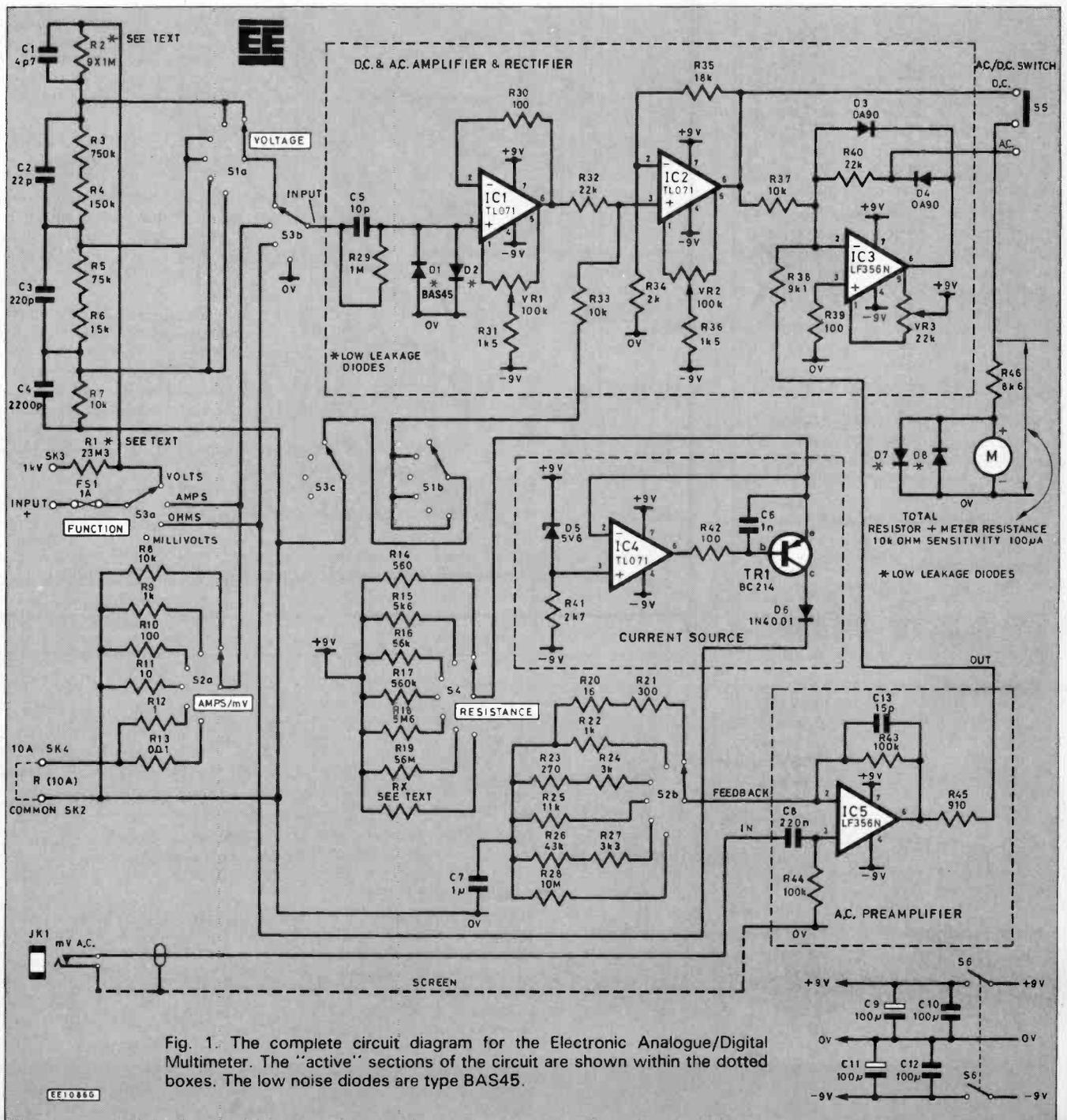


Fig. 1. The complete circuit diagram for the Electronic Analogue/Digital Multimeter. The "active" sections of the circuit are shown within the dotted boxes. The low noise diodes are type BAS45.

COMPONENTS

Resistors

R1	23·3M (2 × 10M + 1 × 3M3 in series 5 per cent)
R2	9 × 1M (in series—see text)
R3	750K
R4	150K
R5	75K
R6	15K
R7,8,33,37	10K
R9,22	1K
R10,30,42	100
R11	10
R12	1
R13	0·1
R14	560
R15	5K6
R16	56K
R17	560K
R18	5M6
R19	56M (series combination—see text)
R20	16
R21	300
R23	270
R24	3K
R25	11k
R26	43K
R27	3K3
R28	10M
R43,44	100K
R29	1M
R31,36	1K5
R32	22K
R34	2K
R35	18K
R38	9K1
R39	100
R40	22K
R41	2K7
R45	910
R46	8K6 (or value to suit meter—see text)
R(10A)	0·01 Ohm made from resistance wire (see text)

See
**Shop
Talk**
page 484

All 0·25W carbon except where stated

Potentiometers

VR1,VR2	100K Horizontal Preset (2 off)
VR3	22K Horizontal Preset

Capacitors

C1	4·7p axial 500V
C2	22p ceramic 50V
C3	220p ceramic
C4	2,200p polystyrene
C5	10p ceramic
C6	1n ceramic
C7	1μ min layer 100V
C8	0·22μ 100V
C9,C11	100n disc ceramic 50V (2 off)
C10,C12	15p ceramic
C13	

Semiconductors

D1,D2,D7,D8	BAS45 low leakage diodes (4 off)
D3,D4	low leakage diodes (4 off)
D5	0A90 (2 off)
D6	5V6 Zener diode
D7	1N4001
TR1	BC214

IC1,IC2,IC4	TL071 (3 off)
IC3,IC5	LF356N (2 off)

Switches

S1,S2	2-pole 6-way, make-before-break (2 off)
S3	3-pole 4-way
S4	1-pole 12-way, make-before-break
S5,S6	DPDT Min. slide switches (2 off)

Miscellaneous

100μA Panel meter 1·4k resistance (see text); 8-pin i.c. sockets, 5 off; fuse, 1A Q.B.; 20mm chassis fuseholder; knobs, four with coloured caps; case, with insulated front panel; 4mm sockets, 4 off; insulated jack socket (with N/C switch); test leads and probes, 2 off; PP3 battery clips, 6 × AA battery holders, 2 off. Printed circuit board, available from EE PCB Service—Code EE579 (see page 516).

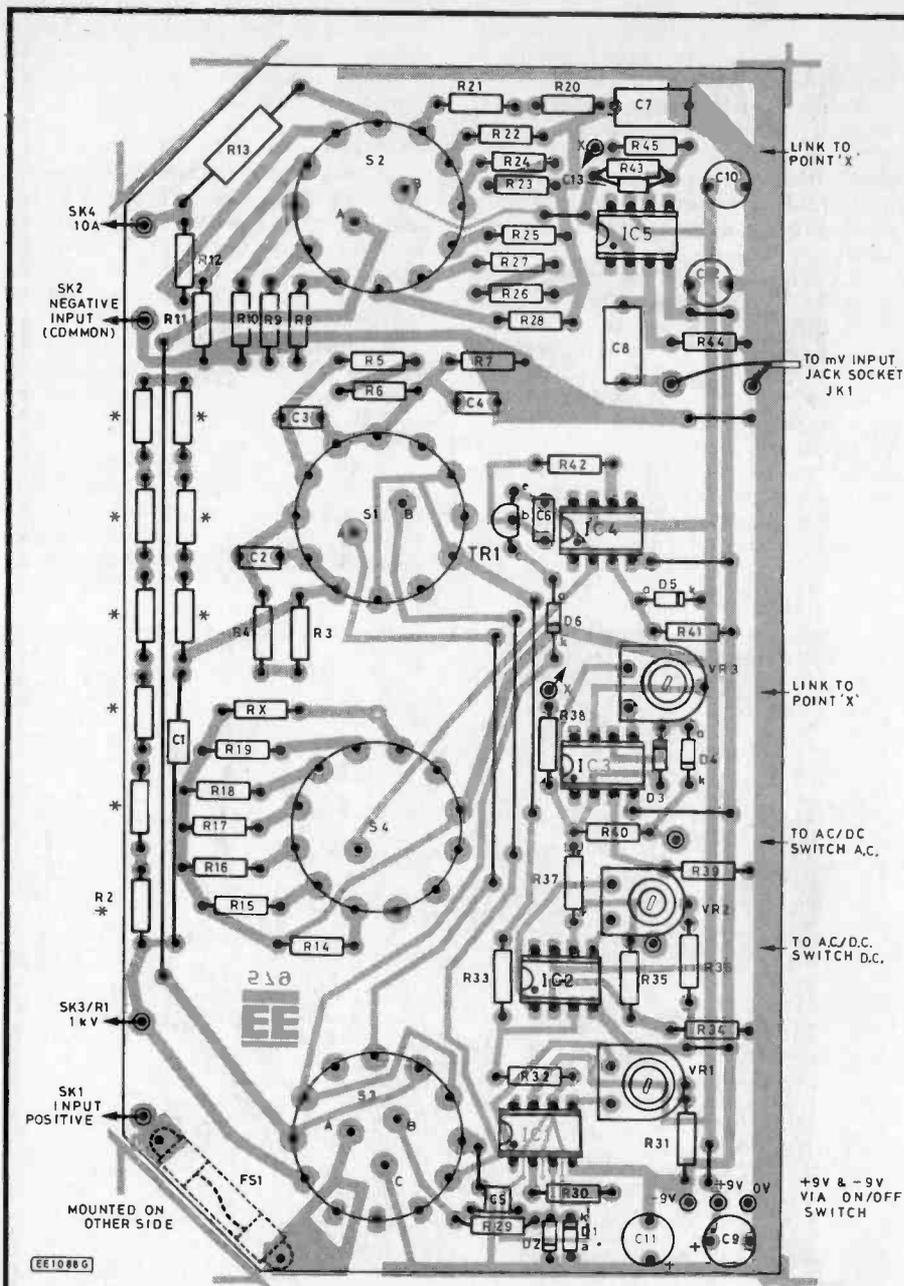


Fig. 2. Component layout on the printed circuit board. Note that the long link wires should be made with plastic insulated connecting wire, see photographs.

Approx. cost
Guidance only **£45** (excluding Test Leads)


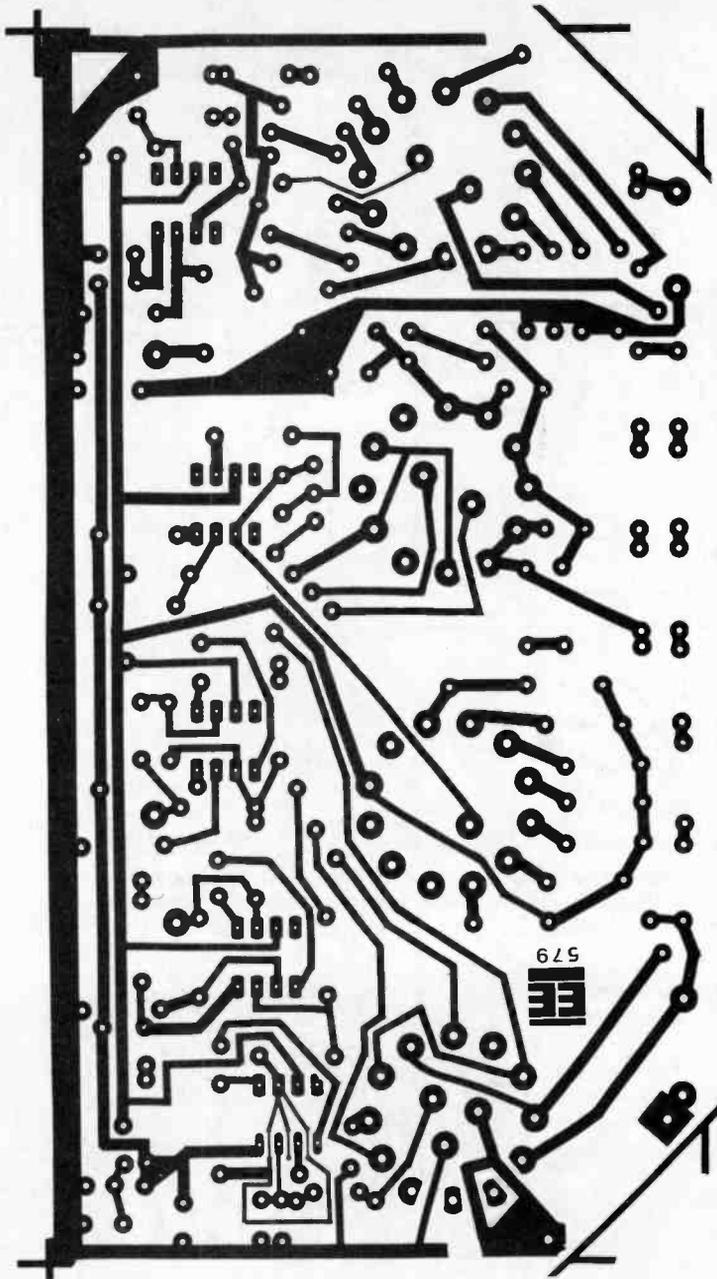


Fig. 3. Full size printed circuit board foil master pattern. This board is available from the EE PCB Service.

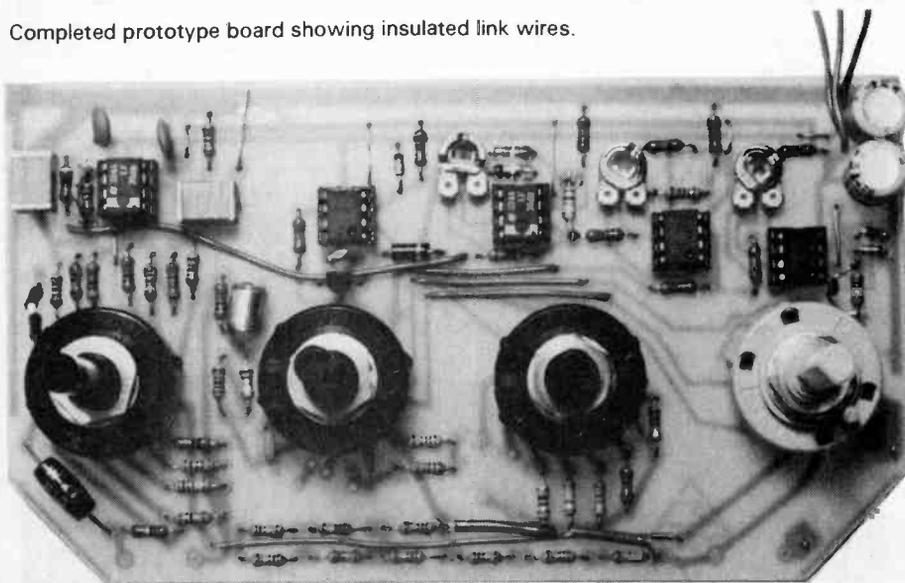Completed prototype board showing insulated link wires.



equal to this reference voltage. This means that 5.6V appears across whichever emitter resistor is selected by S4.

This constant reference voltage across a fixed resistance value gives a constant current output at the collector of TR1. As the reference voltage is 5.6V a 5k Ω range resistor gives a current of 1mA. The standard voltage circuit, which is connected via S3b, gives full scale deflection for 100mV. A range current of 1mA thus gives a full scale reading of 100 ohms. Low value resistors drop less voltage and so the reading is directly proportional to the resistor value.

On the higher resistance ranges the current becomes rather too small for comfort. For example on the 100k range a current of only 1 μ A is required. The 1M and 10M ranges require 0.1 μ A and 0.01 μ A respectively. A current of 0.1 μ A is just about the limit of the circuit, so readings on this range will not be too accurate, and a 10M range is impractical.

The middle resistance ranges are accurate and linear, and much easier to use than a standard meter. No compensation has been made for wiring and test lead resistance, so on the lower ranges 100 ohm and 10 ohm, an offset zero will be present when the test leads are short circuited. This value should be subtracted from any measured resistance value to give the true reading.

A.C. MILLIVOLTS

The measurement of A.C. Millivolts is made by first amplifying the input to 1V and using the standard rectifier circuit IC3.

The A.C. Pre-Amplifier, IC5, is connected to IC3 via resistors R45 and R38. The gain of IC5 is set by the feedback resistor R43 and the range resistor selected by S2b. The values of resistors R20 to R28 are chosen to given ranges of 1V 300mV, 100mV, 30mV, 10mV and 3mV. The frequency response is level up to 100kHz except on the 3mV range where it is slightly lower.

When making measurements on the mV range the input of IC1 is connected to 0V by S3b so that stray inputs do not interfere. In a similar way the input of the mV range is shorted out when the input lead is disconnected by use of a switched jack socket (JK1).

The input impedance on this range is set to 100 kilohms by the input resistor R44.

POWER SUPPLIES

The Multimeter circuit consumes very low current, but as meters tend to be used frequently it is recommended that two sets of six AA cells are used. These can be standard or re-chargeable types, and should give very long life.

Mains derived power supplies can also be used, but take care to use double insulated circuits *without* an earth on the output side as this could cause all sorts of problems with earth loops.

CONSTRUCTION

As the circuit is all built on a single printed circuit board the assembly is fairly straightforward. Fig. 2 shows the component layout and Fig. 3 the printed circuit board track pattern, full size. This board is available from the EE PCB Service, code EE579 (see page 516),

Begin assembly by fitting the wire links as shown. The longer links should be made with insulated wire whilst the shorter ones can be made from offcut resistor leads.

As there are rather a lot of resistors and most of them carry the five-band one per cent colour code system it is necessary to be rather careful to get the correct values in the right places. Any errors will give "odd" ranges which may not be easy to spot as the meter may appear to be working perfectly.

Sockets should be used for all i.c.s. The rotary switches are usually supplied with loop tags for direct wiring and these must be cut off leaving as much of the straight stems of the tags as possible.

Switches S1, S2, and S3 will fit more than one way round, so take care to set them fully anticlockwise and use the "flat" of the shaft as a guide to get them right. Remember that the pointer on the knob is exactly opposite the flat on the spindle. If you get it wrong and don't want to unsolder the switch, screw fix knobs are a good alternative way out.

Capacitor C1 is mounted between two distant points—its leads must be sleeved and may need extending to fit the board centres. Make sure that all diodes, and capacitors C9 and C11 are the right way round.

The final component to be fitted to the board is the fuseholder which is fitted to the track side to keep easy access to the fuse. Once the board assembly is complete connect the necessary wires to the board. The mV input should use screened cable, the other input socket connections should be made with 16/0-2 wire.

Resistors for the 1KV socket should be fitted in a length of sleeving between the board and the input socket. The 10A shunt is made from a 71cm length of 18s.w.g. enamelled wire connected directly between the 10A socket and the negative (Com) socket SK2. The wire can be loosely wound on a flat piece of insulating material (e.g. Paxolin).

The wiring diagram Fig. 4 shows how the shunt can be fitted and the wiring to the other parts of the board from the sockets.

TESTING AND SETTING UP

The thorough testing of a meter of this type presents quite a problem. The wide range of accurate voltages and currents necessary to check each range fully is not likely to be available even in electronics workshops. The best way is to make comparisons with other meters using whatever sources of voltage and current are available. It is possible that a local training centre, school or college will be able to help, so ask around.

Fine tuning of capacitor values C1, C2, C3, C4, and C5 may be undertaken by those determined to extract the very best from the meter. These components affect the frequency response on the A.C. Voltage ranges. Capacitors C1 and C5 in particular have a large effect and should be changed only if a good reliable sine wave source of 0-100kHz or more is available.

If no test gear is available it is safe to say that the meter should work accurately first time provided no errors are made in assembly.

There are three presets that must be set up to remove the zero offsets of IC1, IC2 and IC3. To do this, set the A.C./D.C. switch S5 to D.C. and the Range switch to mV. Link pin 3 of IC2 to 0V and if necessary adjust VR2 to zero the meter. Remove the link and if necessary adjust VR1 for zero. These two are now correctly set.




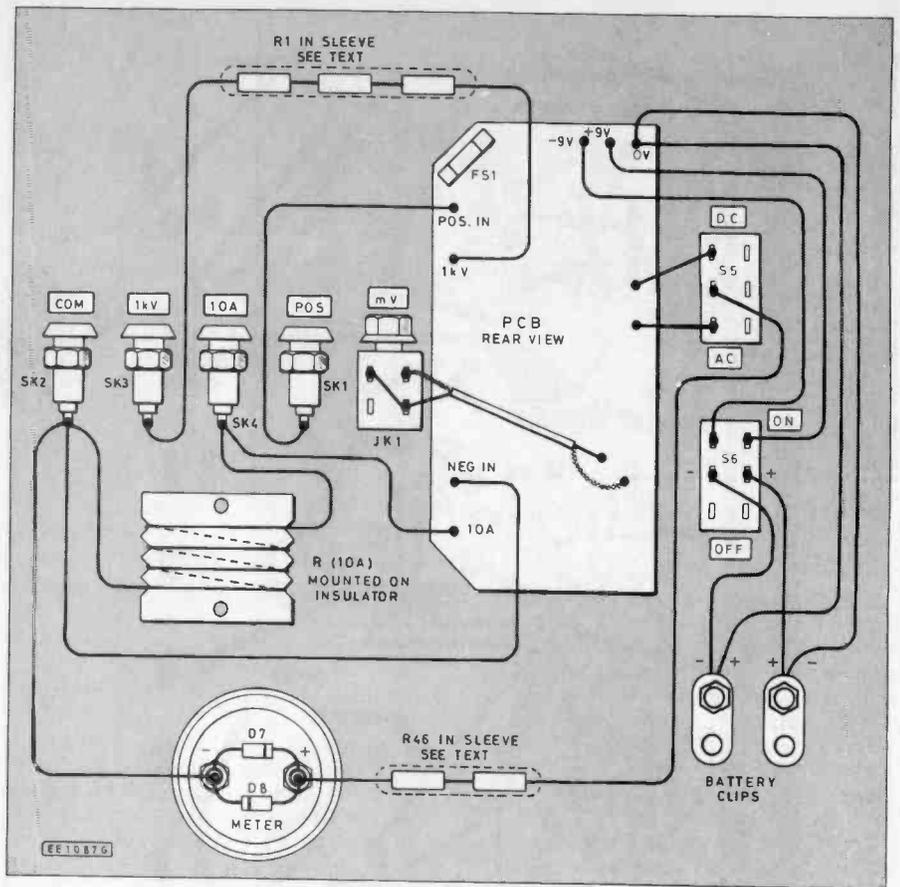


Fig. 4. Interwiring details for the off-board components. The circuit board and components are all mounted on the rear of the front panel. Note the resistors "encased" in plastic sleeving, see photo opposite page.

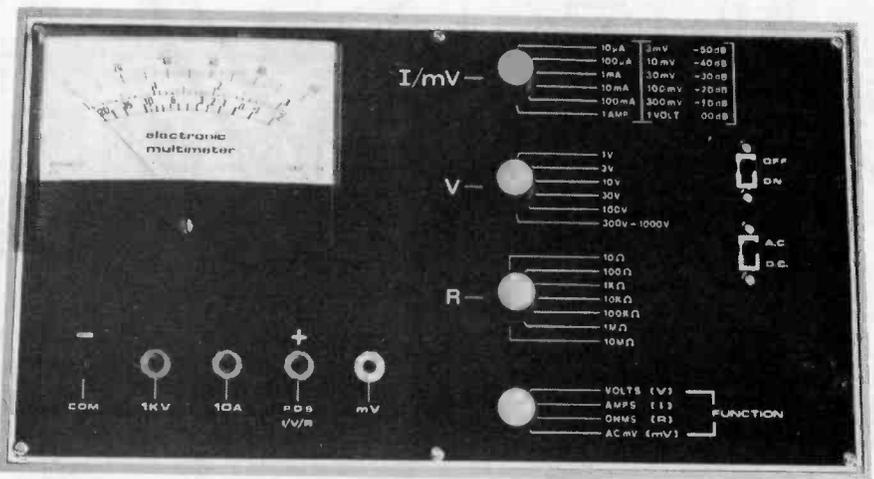


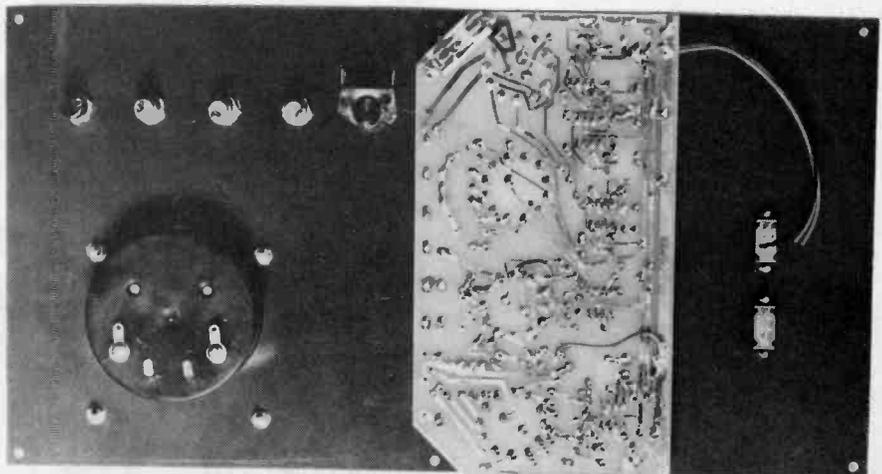Front panel layout and lettering. The positioning of the p.c.b. and other components is shown below.



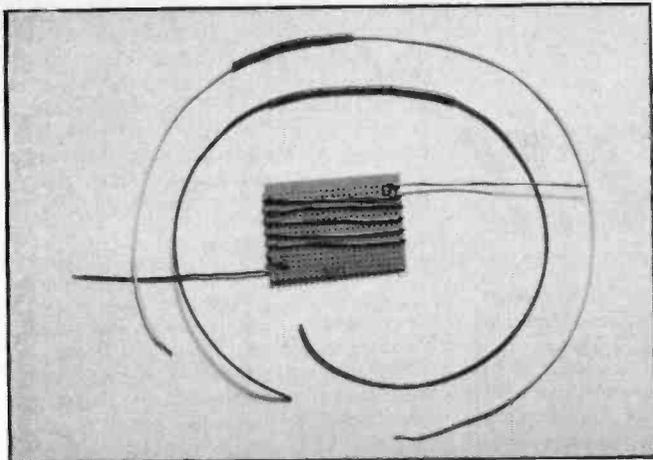

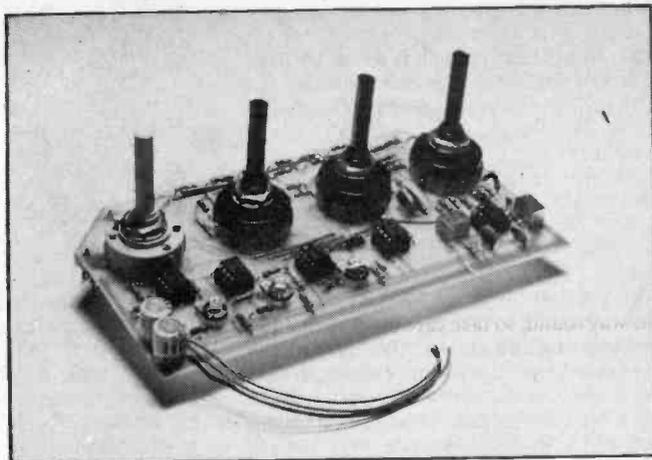The 10A "shunt resistor" wound around some plain board. Also shown are the two resistor leads, R1 and R46.



The completed printed circuit board ready for mounting on the rear of the front panel. The board is held in place by the potentiometer fixing nuts.

Next set the A.C./D.C. switch to A.C. and turn VR3 until the meter deflects to the right. Back of the setting of VR3 to the point where the meter just touches zero and the settings are complete.

The accuracy of the Ohms range depends on the Zener diode D5 which is specified as a five per cent component. More accurate voltage references can be obtained and substituted if required.

The value of resistor R46 depends on the meter being used. Its value can be calculated easily as its function is to make the meter resistance value up to 10 kilohms. A meter of four kilohms resistance thus requires a six kilohms resistor and so on.

It is also possible to use meters of other current ratings, all that is necessary is to set

the meter and series resistor so that 1V gives a full scale deflection (f.s.d.). Thus a 1mA meter would need a combined meter plus series resistor value of one kilohm. A 50 μ A meter, 20 kilohms; a 500 μ A meter, 2 kilohms etc.

On A.C. ranges the "averaging" effect of some types of meter may be affected by the diode (D4) in the drive circuit. A 1k resistor from D4 cathode to 0V line overcomes this and allows any type of meter to be used.

SAFETY

For complete safety an *INSULATED* case is *ESSENTIAL* where high voltage readings are to be made. It is also necessary to add some screening to the meter electronics.

The best way to combine these two functions is to use a plastic case with a metal front panel overlaid with a Paxolin insulating panel. The metal panel should be connected to the 0V point in the circuit.

DECIBEL RANGES

The dB Range on the meter is set to be accurate on the A.C. mV Ranges. On the 1V A.C. Range (mV) the 0dB point represents the universal 1mW in 600 ohms. Each range down from this subtracts exactly 10dB so relative measurements are easy.

The use of dB scales is a difficult subject for beginners and it is not intended to go into details here. Hopefully, a further article explaining their meaning and use will be published shortly. □



READERS DISCOUNT SCHEME



Readers—you can obtain a 5% discount on goods from the advertisers listed using coupons cut from EE, provided you follow the rules below:

GREENWELD ELECTRONICS LTD.

A full range of components at our shop in Southampton; open 9-5.30 Mon-Sat, as well as many surplus lines, all available by mail order. Bargain List free with our Catalogue. Send for your copy today, only £1 inc. post. Now even better value with EE Discount Vouchers!

RADIO COMPONENT SPECIALISTS

Amplifiers—(PA, disco, music), audio leads all types, components, capacitors, potentiometers, resistors, disco lighting, sound to light units, disco decks, disco consoles, disco mixers, echo chambers, fuzz lights. Multimeters, mains transformers, microphones, stands, leads, goose necks, speakers with or without cabinets, tweeters, mid range units, 100V line matching audio transformers, etc.

TK ELECTRONICS stock a wide range of components including triacs, ICs & opto together with other accessories (switches, tools, multimeters, buzzers, crystals, Antex, Velleman and Vero products, etc.). We specialise in kits for timers, disco and home lighting, remote control kits for beginners. Send s.a.e. and 50p (refundable on first order) for catalogue.

OMNI ELECTRONICS are willing to give a 5% discount on all orders over £10.00, excluding VAT, if a valid voucher is enclosed. We stock a wide range of components—ideal for the hobbyist. Goods listed in our catalogue are generally in stock, orders will be sent by return post. Why wait?

RULES

1. Discounts are available from advertisers listed on this page.
2. Unless otherwise stated by the advertiser, discounts are only available on orders over £20 in value.
3. Unless otherwise stated by the advertiser, one voucher is required for each £50 value of the order placed (i.e. for orders between £20 and £50 send one voucher, between £50 and £100 send two vouchers, etc.)
4. Cut out vouchers (not photostats) must be sent when claiming the discount.
5. Each voucher sent must be valid on the day of posting (i.e. it cannot be used after its expiry date).
6. Discount is not available on "sale" or "special offer" items.
7. You must indicate on your order that the 5% EE Readers Discount has been deducted from the payment sent.
8. All advertisers reserve the right to refuse this discount on any item supplied.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★ ★

EVERYDAY ELECTRONICS

ONE COUPON

VALID UNTIL END OF AUGUST 1987

Entitles EE readers to discount from listed advertisers when used according to the scheme rules as set out in EVERYDAY ELECTRONICS

BECKER-PHONOSONICS, established 1972. Designers and suppliers of a wide range of kits for projects published in *Everyday Electronics* and other leading periodicals. Range includes musical and audio effects, computer controlled circuits and Geiger counters. EE discount scheme applies to all full kits over £30 goods value, excluding Geiger counters.

Actually Doing it!!

ADDDING panel legends to a project using rub-on transfers, provided it is done reasonably skillfully, can certainly make the finished unit look much more professional. Even well finished projects tend to have a home-made look about them though. Unfortunately, rub-on transfers rub off almost as easily as they can be applied, and cannot easily be given a really effective protective covering. There are alternative methods of panel labelling which can give much more professional results, and are good enough to fool many people into thinking that a home constructed project is the "real thing". On a more practical level, these alternatives give much more durable labels. In fact they give such a tough finish that the lettering is virtually impossible to damage, and it will not show any signs of wear even after the project has been subjected to many years of hard use.

It is only fair to point out from the start that these advanced systems of labelling are much more involved than applying a few rub-on transfers. Perhaps of more importance to most constructors, they are quite expensive. Some of the more sophisticated systems (particularly the brushed aluminium effect types) are so expensive as to be something that few of us can seriously consider, even for the occasional project. It could even cost more for the front panel than for the rest of the project! However, there are much cheaper labelling systems, and it is these that we will consider in this article.

MASTERING THE TECHNIQUE

The panel labels under discussion here are the type that are produced by a simple photographic process. The films are not ordinary daylight types, but are ultra-violet sensitive films that can be exposed to daylight for short periods without any risk of fogging. Little special equipment is required in order to produce an exposure, but ideally an ultra-violet light box should be available. Failing that it is possible to use some other source of ultra-violet, such as a sun-ray lamp or even strong direct sunlight.

Before an exposure can be made it is necessary to have a "master" artwork from which the photographic copy can be made. It is possible to make up individual labels for the controls, etc., but it is generally easier to make up a large label that covers the entire panel. This also gives much neater results. The first stage in making up the master artwork is to draw out the panel design onto paper. This does not need to be an exact representation of the required front panel design, and basically all that is needed are lines to indicate the perimeter of the panel, plus base lines for the legends. It is also more than a little helpful to mark the centre of each word using a short vertical line beneath the base line.

This drawing is taped to a drawing board (which can just be the kitchen table or a

piece of faced chipboard) and then a piece of tracing paper or drafting film is taped in place over it. The required design is then marked onto the film or tracing paper, including corner markings which can simply be drawn on with pencil. The lettering is produced using rub-on transfers, and these are readily available in a number of sizes and letter styles. They can be obtained from stationers, graphics art suppliers, and some of the larger electronic component retailers. A useful range are available from shops in the W.H. Smiths chain. Some useful symbols and other panel markings are available from a few sources.

Both tracing paper and drafting film provide a surface to which the transfers will adhere well. An old ballpoint pen or something of this nature can be used as the rub-on tool, but I have always found it much easier to use the correct "spatula" tool which is available from a few suppliers of the transfers. Reasonable care needs to be taken when applying the transfers, and making a neat job of this is not too difficult provided due care is taken and the job is not rushed.

The base lines on the paper pattern make it easy to get the vertical alignment of the letters right, but more care needs to be taken with the spacing. With a little experience this can be done accurately by eye, and some transfer systems include some form of aid to accurate spacing. For the finished panel to look reasonably neat it is essential that the legends are centred properly. This is basically just a matter of counting the number of letters in each word, and then starting with the middle letter over the centre line. If the word has an even number of letters, the middle two letters should be positioned just either side of the centre mark. This does not actually guarantee perfect results since some letters are wider than others. Initially it might be as well to ignore this fact, but with experience you can learn to compensate for narrow letters (particularly the letter "i") and wide letters such as "W".

COMPUTER GRAPHICS

These days there is the alternative of using a computer and some form of drawing or graphics programme to generate the panel design. This will only give usable results though, if the output can be produced accurately to scale, and in really

opaque ink on some form of transparent or translucent medium. There is unlikely to be any problem if the output device is a plotter, but using a dot matrix printer some form of processing will be needed in order to give a usable master artwork. For example, the design can be printed onto ordinary paper, and with a suitable copier, then photocopied into translucent film.

EXPOSURE

The materials I have used have been the "Permasign" type, and the film can be handled in ordinary daylight without any risk of it being fogged. However, it should be stored in total darkness and should not be exposed to bright sunlight. It is cut to size prior to making an exposure, but take great care not to damage the emulsion side (the dull surface). Try not to touch this surface either, as finger marks seem to be reproduced on the developed film.

If an ultra-violet lightbox is available, the exposure is made in the manner shown in Fig. 1. It is probably not worthwhile buying a lightbox just for producing a few photographic front panels, but it is a more viable proposition if you will also use it when producing your own printed circuit boards. A lightbox is something that is not too difficult to build yourself, but at least two tubes are needed to give even illumination over even a fairly small area of around 150 by 250 millimetres. More tubes give a stronger light source and shorter exposure times. An essential feature is the foam pad which presses the film down onto the artwork so that a "crisp" image is obtained on the film. There is often a tendency for the film and artwork to shift slightly when the lid of the box is closed. To avoid this tape the artwork onto the glass panel, and then tape the film in place over the artwork. Make quite sure that the master has the transfer side facing upwards, and that the film has its shiny side facing upwards.

The manufacturer's recommended exposure times are 45 seconds for a 120 watt lightbox, and 90 seconds for 32 watt type. I find an exposure time of five minutes gives good results with my 16 watt lightbox. It is worthwhile experimenting with some small pieces of film to find an exposure time that gives good results with the particular box you are using.

If a lightbox is not available the alternative set up of Fig. 2 can be adopted. The base board needs to be something that has a smooth, flat surface, and a piece of good quality faced chipboard is ideal. The sheet of glass is used to press the master and film flat against one another, and the glass must not be a type which gives high absorption of ultra-violet rays. As the film is against the baseboard and its emulsion side up it is not feasible to tape it in place unless some double-sided tape fixed to the underside is used. However, with this set

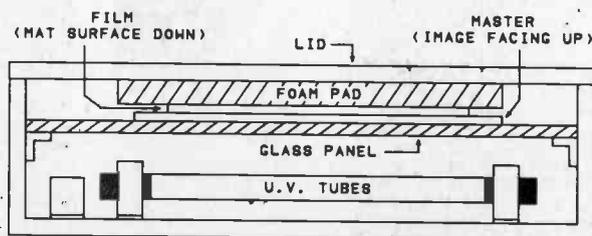


Fig. 1. The set up when using a lightbox to make the exposure.

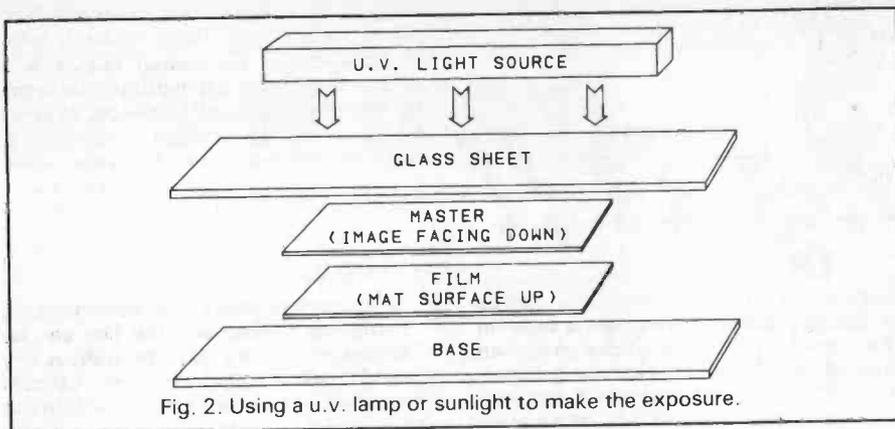


Fig. 2. Using a u.v. lamp or sunlight to make the exposure.

up it is not too difficult to get everything properly aligned and to then carefully place the glass in position. Take care not to disturb anything during the exposure. For reasons of safety, the edges of the glass plate should be ground to a smooth finish, or given a protective covering of some kind.

The exposure time can only be determined by trial and error, and with direct sunlight it may be difficult to obtain consistent results as the strength of the light will inevitably vary somewhat from one time to the next. An exposure time of around five to ten minutes will probably be needed. It is unlikely that satisfactory results will be obtained using daylight on an overcast day. The correct exposure time could be very long indeed, and could vary enormously from one exposure to the next. Provided the artwork is of high quality with really opaque lettering it is better to err on the long side with exposure times.

Things should be much easier using a sun-ray lamp, and consistent exposures should be obtained provided the lamp to film distance is always the same. It will still be necessary to determine the best exposure time by empirical means. Bear in mind that ultra-violet light can be harmful to one's eye-sight, and observe the lamp manufacturer's recommendations. This basically means keeping yourself and any

other living matter (plants and pets) out of the ultra-violet light while the exposure is being made.

DEVELOPMENT

A flat-bottomed dish of adequate size is needed for development of the film. Dishes sold for photographic use or for etching printed circuit boards are suitable. Sufficient developer to fully immerse the film is poured into the dish, and then the film is placed into the developer for about ten seconds. Then remove the film and place it emulsion side uppermost on the worktop. Use photographic tongs to remove the film, or only handle it by the edges. The emulsion is very easily damaged at this stage.

Next a developer pad is soaked in developer, and is carefully wiped across the film to remove the areas of softened emulsion. Note that it is the areas of film that were not exposed to ultraviolet (i.e. the lettering) that are removed. The film is then rinsed in water and wiped gently some more in order to remove any residues. Once it has been allowed to dry or has been dried with a paper towel it is ready for inspection. There will often be minor damage to the emulsion, and any minor holes or scratches will probably not show up on the finished panel. However, any serious blemishes can be repaired using some-

thing like a technical pen or an overhead transparency pen, filling in the affected areas on the emulsion side of the film. Any blemishes must be repaired at this stage and cannot be fixed later on.

FIXING

The film is fixed in place on the front panel of the project using special double-sided self-adhesive cards. These cards are white on one side, and are available in a variety of colours on the other side. It is just a matter of removing the backing paper and fixing one side of the card to the front panel, and then removing the second piece of release paper so that the film can be fixed in place.

The film has its adhesive surface towards the adhesive, which should result in a panel with right-way-round lettering if the exposure has been made correctly. The panel is black with lettering in whatever colour shows through from the card. Clear material is available where something like the silver colour from an aluminium panel must show through on the letters. It is, of course, possible to have black letters on a coloured panel. This requires a negative master artwork though, and producing one of these could be difficult.


Front panels of this type are very tough due to the fact that the emulsion side of the film is facing towards the front panel. The exposed surface is the blank side of the film, and this can be cleaned and polished without any risk of damaging the lettering. The finished panels certainly look very neat and professional, and justify the extra time and expense involved in their production.

Next month we will continue in a similar vein, and will consider photographically reproduced printed circuit boards.

Robert Penfold

Developer, transfers, film, developer pads and double-sided adhesive cards.

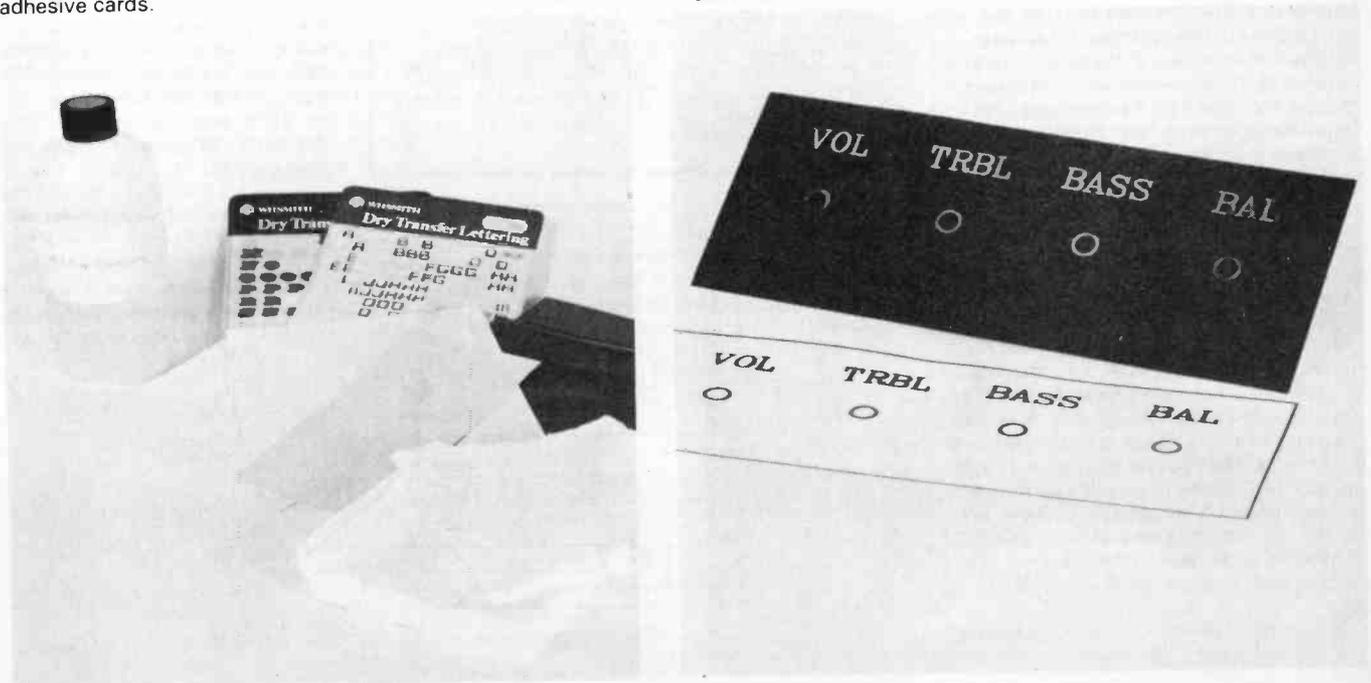The master artwork and finished panel produced by the method described.



YOUNG ELECTRONIC DESIGNER AWARDS

Neil and Jonathan tread softly and walk off with £10,000 computer.

TWENTY FIVE enthusiastic young electronic designers, ranging from 12 to 21 years of age and representing sixteen different education institutions took part in this year's finals of the "1987 Young Electronic Designer Awards" contest at the Institution of Civil Engineers, London, last month (July). The competition challenges students to design and construct an electronic device with a possible application in everyday life.

Organised under the auspices of the YEDA Trust, a registered charity, the annual contest is sponsored by Cirkit Holdings plc and Texas Instruments Ltd. Winning finalists were awarded trophies, cash and certificates which could launch them on rewarding careers in the electronics industry.

Top prize in the Senior Class carried a reserved place in the Texas graduate intake (upon graduation)—a job! In addition it carries TI sponsorship for the remainder of his/her course, at the rate of £450 per annum, and a vacation job during the summer of 1987.

The educational institution whose entrant's project was adjudged to have the most commercial potential was awarded a Texas Instruments Business-Pro computer valued at over £10,000. In addition, TI donated a "Personal Consultant Plus" development package and a week's training course in its use and operation.

Final Results

After the opening ceremonies the big moment arrived and the judges' final decisions were revealed.

Winner of the £500 first prize in the senior category went to Douglas Mackay (21) of Robert Gordon's Institute, Aberdeen for his Robotic Functional Arm. Robert was in a team from Thurso Technical College that took second place in this category last year.

Second place (£250) went to Stephen Morrison (21), Carl Gibson (18) and Paul Briggs (19) from Brunel University for their Wheelchair Controller. Third position (£100) was awarded to Morgan Metters (21) and Tim Mottershead (20) from Hatfield Poly. for their Speech Synthesiser entry.

Paul and Roger from Cheltenham College receive their awards and congratulations from Sir John Egan, Chairman of Jaguar Cars.



Watched by their teacher Mr. L. Haywood (left), Ken Sanders (second left), MD Texas Instruments and TI Engineer Philip Hutson (second right), junior winners Neil (seated) and Jonathan of Wilford Meadows School get to grips with the School Prize of a TI Business-Pro computer. Their Digital Tyre Pressure Gauge project was considered to have the most commercial potential.

Intermediate Class

Intermediate category winner went to Paul Dagley-Morris (16) and Roger Lucas (15) of Cheltenham College and received £350 for their Animal Stress Meter.

Runner up in this section and £200 went to Jonathan Ackland (15) and William Meere (15), Cheltenham College for their Saucepan for the Blind. The £75 third prize went to David Earle (17) of Brentwood School for his Colour Recognition System.

Junior Class

Winners of the junior class (£250) were Neil Motson (14) and Jonathan Cragg from Wilford Meadows School for their Digital Tyre Pressure Gauge.

Second spot (£150) went to Ian Levy from Allerton High School for his Ladder Safety Device. The £50 third prize went to the only girl finalist, Sophia Ballarini of Hayfield Comp. School for her Water Level Indicator and Alarm project.

Judging Panel

The 1987 awards were presented by Sir John Egan, Chairman of Jaguar plc, who is a YEDA Trustee and the members of the judging panel were Professor John Eggleston of Warwick University; Sir Alec Morris, British Aerospace; John Wesley, Investors in Industry PLC; Richard Reisz, Editor BBC 'Tomorrow's World'.


Jeffrey Archer, a special guest at the event, made a final address following the announcement of the results.

School Prize

The project adjudged to have the best commercial potential was the Digital Tyre Pressure Gauge submitted by Neil Motson and Jonathan Cragg. Their design won a TI Business-Pro Computer, worth over £10,000, for the Wilford Meadows School, Nottingham.

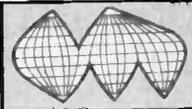Senior winner, Douglas of Robert Gordon's Institute demonstrates his Robotic Arm project to Richard Bulgin, Chief Executive of Cirkit Holdings.





TUBE INVESTMENT

An investment of some £15 million in its television tube assembly plant at Durham to make it the main European production centre for high-resolution data graphic (DGD) has been announced by Mullard tubes. Part of the investment will also go into Durham's sister tube components plant at Simonstone, near Burnley.

Initially production will concentrate on 90 degree 14-in. colour DGD tubes and by the end of 1988 is expected to reach an annual level of around a quarter of a million tubes. High-resolution DGD colour tubes are used in VDUs and work stations produced by the world's leading manufacturers of computer hardware.

At present all European based manufacturers of VDUs rely on imported DGD tubes—mainly from Japan. An indigenous source of tubes not only reduces imports but also opens up a valuable and growing export market which in Europe alone stands at around £100 million.

Data graphic colour display tubes differ from conventional colour TV picture tubes in that they are required to display a much higher-resolution picture. This is achieved by using a shadowmask with a finer pitch (0.3 compared with 0.6 for a TV tube), an extremely high-precision electron gun, tighter controls on all glass tolerances and a specially designed deflection coil assembly.

Solar Power

Mitsubishi Electric Corporation of Japan, has developed the world's highest performance gallium arsenide (GaAs) solar cell for space use with average photoelectric conversion efficiency of more than 20 per cent.

The cell, measuring 2 centimetres by 2 centimetres, employs metal organic chemical vapor deposition (MOCVD) technology and features maximum conversion efficiency of 21.9 per cent under air mass zero condition and less deterioration under radiation in outer space. Even after 10 years of use in space, 82 per cent of its original output will be maintained.

MOCVD technology allows simultaneous uniform growth of many GaAs crystals. Based on this, Mitsubishi have established the mass production

Europe Calling

British Telecom is to play a major role in the development of a Pan-European digital cellular radio network. This follows an agreement made in Bonn between the United Kingdom, France, West Germany and Italy.

The four countries have now agreed to work towards a commercial service on the new network by 1991. This will allow customers to use their phones wherever they are in each of the four countries.

BT also welcomed assurances that the proposed Pan-European digital cellular radio system would not be jeopardised by the decision to allocate, on a temporary basis, 40 additional channels to Racal-Vodafone. The channels have been allocated on the understanding that they be returned by the end of December 1987.

Innovation Award

The Scottish Business in the Community award for innovation (SCOTBIC) has been won by East Kilbride based Fern Developments for their development work on "High-Tec" digital filters.

The award, sponsored by the National Girobank, Scotland, was presented, together with a cheque for £1,000, by HRH The Prince of Wales to Fern's Managing Director Murdo Mackay at a special ceremony in Glasgow recently.

technology to manufacture 120 such GaAs solar cells at a time.

A superlattice structure of thin aluminium gallium arsenide and GaAs layers inserted under the active portion of the solar cell allowed improvement in conversion efficiency with layer thickness of less than half of the conventional cell to reduce film making cost. To minimize characteristic deterioration as a result of exposure to radiation in outer space, they also developed the technology to decrease the depth of P-n junction from 0.5 to 0.3 micron.

GaAs solar cells have higher photoelectric conversion efficiency and less efficiency deterioration under exposure to radiation and high temperature compared with silicon solar cells which have so far been used in satellites.

ON COURSE

A listing of some forthcoming study courses:

- Name:** Radio Amateurs Course
Location: North Trafford College of Further Education
Date (Enrol.): September 2-4, 1987
Info.: North Trafford College, Tel: 061 872 3731
- Name:** Amateur Radio (C&G No. 765)
Location: Addington High School, Croydon.
Date (Enrol.): September 19 (9a.m.-12.30p.m.)
Info.: Addington, Tel: 0689 41461
- Name:** Radio Amateurs Exam (C&G No. 765)
Location: Hendon College, Colindale NW9.
Date (Enrol.): September 9 (7.30p.m.-9.30p.m.)
Info.: Hendon College, Tel: 01-200 8300
- Name:** Morse Classes and Radio Amateur Exam
Location: Croydon College
Date (Enrol.): September (7p.m.-9.30p.m.)
Info.: Tom G3EUU, Tel: 01-668 1725

London Electronics College

The LEC new series of up-dated one year full-time BTEC National Certificate courses starts from September 21. Selection of subjects available include: Equipment Servicing (TV, VCR & CCTV)—Computing Technology—Information Technology—Software Engineering.

These courses are for those wishing to update or re-train, either with Employer sponsorship (up to £1000 ATS grant aid) or for those recently taking redundancy.

Details and Prospectus: The London Electronic College, Tel: 01-373 8721.

YOUNG SCIENTISTS TRIUMPH IN EUROPE

THREE young British scientists won major recognition in the "19th European Philips Competition for Young Scientists and Inventors" held in Paris recently.

From a total of 27 entrants from 14 nations, Peter Badger, aged 19, from West Bridgeford School, Nottingham, won an award of 14,000FF (£1,424) for his computer based design for improving table tennis skills. Placed third overall, Peter's invention was praised by judges drawn from seven countries for its thoroughness in design and its commercial potential.

Youngest contestants of the competition, Andrew Sutton and Nicholas Porter, both aged 14, of Aylestone School, Hereford, won Certificates of Distinction, worth 4,000FF (£407) for their practical device to measure accurately extremely slow speeds of wire drawing in an annealing process, for Messrs Wiggins Alloys of Hereford.

(left to right) Andrew, Nicholas and Peter with their commendations.



BURST FIRE MAINS CONTROLLER

ANDY FLIND

An inexpensive controller for soldering irons, and other low power heating devices—also useful as a lamp flasher.

THE idea for this project arose when a new soldering iron was purchased for the author's workshop. The old iron was a fifteen-watt model, perfectly adequate for light electronic work, but sadly unequal to the occasional heavier task. It was decided that the replacement should be a twenty-five watt iron, especially as a very popular version just happened to be on "special offer" at the time.

The extra power is sometimes useful, but for lighter day-to-day work it soon proved to be an embarrassment. The bit (an iron-coated type) continually oxidised and refused to tin properly; eventually it turned blue and started to warp! Joints made with it took ages to solidify and displayed the typical appearance of overheating... in short, something had to be done.

BURST FIRE

The usual method of controlling light loads is by variable phase control, as used in lamp dimmers. Even when well suppressed though, these create a lot of radio frequency interference at close range, especially unwelcome where sensitive electronic equipment is being tested. As a soldering iron has a fair degree of thermal inertia, some form of "burst fire" controller seemed the best solution, as these are inherently interference-free.

Since the mains supply alternates between positive and negative peak voltages at fifty hertz, it follows that it must pass through zero a hundred times a second. If the load can be switched on and off at, or very close to, these zero points, the switching device will not make or break any heavy currents so the interference generated will in consequence be negligible. "Burst fire" controllers switch loads on and off at regular intervals, the switching taking place at zero crossings. The net power delivered depends on the ratio between the "on" and "off" times.

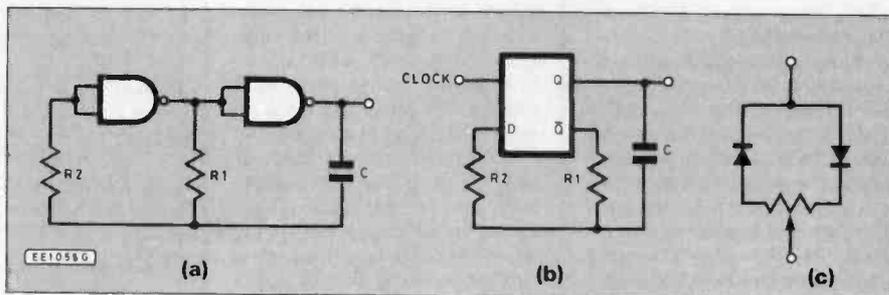


Fig. 1a. CMOS NAND gate oscillator. Fig. 1b. Oscillator built with a "D" type flip-flop. Fig. 1c. Substitute for R1 to obtain variable mark to space output.


Switching "off" at the right moment is easy. If the drive is removed from a triac gate it will continue to conduct until the current passing through it falls to a low level, which of course coincides with the low voltage point (for a resistive load). Thus the correct "off" point is selected automatically. Switching on is slightly more difficult; the right point has to be sensed in some way and drive applied to the triac at that exact moment.

Custom chips are available for the job, but are not really suited to light loads. The reason for this is that they usually fire the triac with a very short pulse to the gate, then rely on the "on" condition being maintained by the load current. With a small load such as a twenty-five watt iron this is likely to be insufficient at the point where the gate pulse ends; for such applications a continuous gate drive is better. Fortunately

it is possible to construct an extremely simple circuit around a "D" type flip-flop which will not only generate the required variable mark-space timing function, but can be synchronised to the zero crossings through its clock input.

A common oscillator circuit that can be built with the two inverting logic gates is shown in Fig. 1a. Positive feedback is applied right around the circuit via capacitor C and R2, ensuring clean and positive switching. However, after each switching action, negative feedback from R1 gradually pulls the input towards the opposite polarity until another change of state takes place. R2, by the way, prevents the gate's input protection from loading the timing circuit.

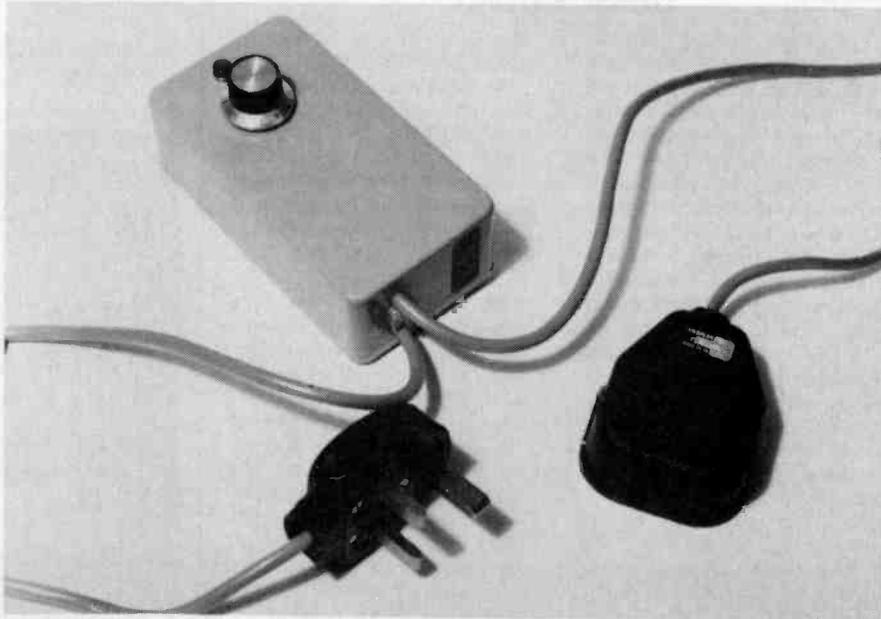In Fig. 1b the same circuit is shown built with a "D" type flip-flop. With this type of device, the "Q" output will assume the state



present on the "D" input, whilst the "Q" output will take up the opposite state. We thus have an input and two opposing outputs, so an oscillator circuit can be constructed exactly as before. However, changes of input are only transferred to the outputs when the "clock" input changes state, so this can be used to synchronize output changes to another input signal.


As shown, the output will have equal "on" and "off" periods, but with some simple additions these can be altered as desired. If a linear pot is used for R1 with a couple of steering diodes, the output will have a constant frequency but the ratio between high and low states will be directly proportional to the pot setting.

CIRCUIT

The full circuit appears in Fig. 2. A low voltage supply for the electronics is derived from the mains through a series capacitor, C1, together with diodes D1, D2 and Zener D3. C2 stores and smoothes the output. With capacitive mains droppers there is always a slight risk of catastrophic failure should the capacitor fail, but in the author's experience this is uncommon, especially where protection against high voltage transients (VDR1) is provided. Capacitors are much cheaper and easier to mount on p.c.b.s than transformers!

To generate the clock signal, current flowing through R2 is passed through the transistor's base-emitter junction during positive half-cycles, turning it on. During the negative periods it flows through D4, and the transistor turns off. A logic signal synchronised to the mains can thus be taken from its collector. The i.c. used, a CMOS 4013B, actually contains two "D" type flip-flops. The first of these is used as described, the output switching at about 1Hz, with the on-off ratio being adjustable through VR1.

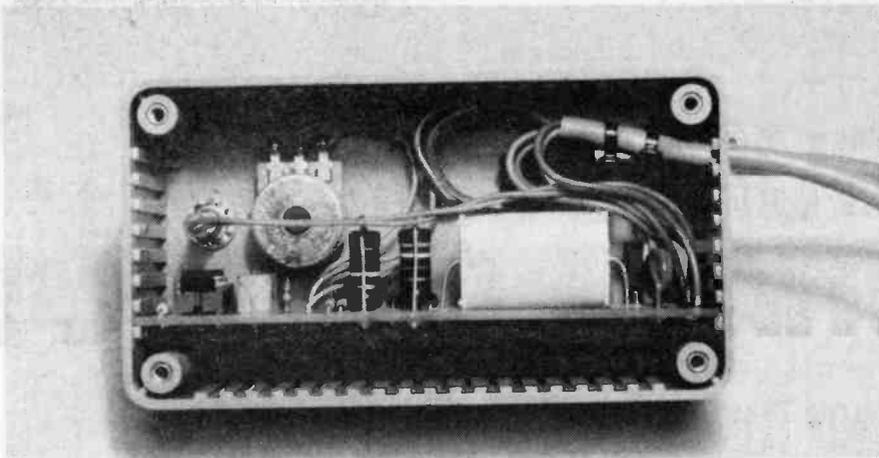The flip-flops in the 4013 are also provided with "set" and "reset" inputs, which can be used to drive the outputs directly regardless of the "D" and the "clock" inputs. In the first stage these are not used so they are connected to ground. The second flip-flop is used simply as a follower to buffer the output before it drives the triac. Its "set" and "reset" inputs are driven from the "Q"



and "Q" outputs of the first stage, and the unused "D" and "clock" inputs are grounded.

The triac is a C206D, chosen for this project as it is readily available and requires less gate current than most other types. The neon lamp is optional; it provides indication that the unit is operating correctly and if, like the author, you're in the habit of forgetting to switch off the iron after a long day at the bench, the flashing will serve as a useful reminder!

CONSTRUCTION


Construction of this project is quite straightforward, so little needs to be said about it. Since live testing is difficult and a faulty component in some areas could result in a fair degree of destruction, it is a good idea to check some of the parts before insertion, in particular diodes D1 to D4. Zener D3 can be tested with a suitable voltage source, say a couple of nine volt batteries, and a series resistor of 1k or so (R6 will suffice for this), then measure the voltage across the diode—it should be 12V. Fig. 3 shows the positions of all the components; take care to ensure that the diodes are fitted the correct way round.

TESTING

Testing, of course, must be carried out with due regard for the fact that all of the

circuit will be connected directly to the mains and **MUST therefore be treated as "live"**. It is suggested that a socket is used for IC1, and initially the unit should be plugged in without this i.c. It is a good idea to connect the meter probes to the points indicated before plugging in, to eliminate the risk of making contact with live parts. Begin with

Fig. 2. Complete circuit of the Burst Fire Mains Controller.

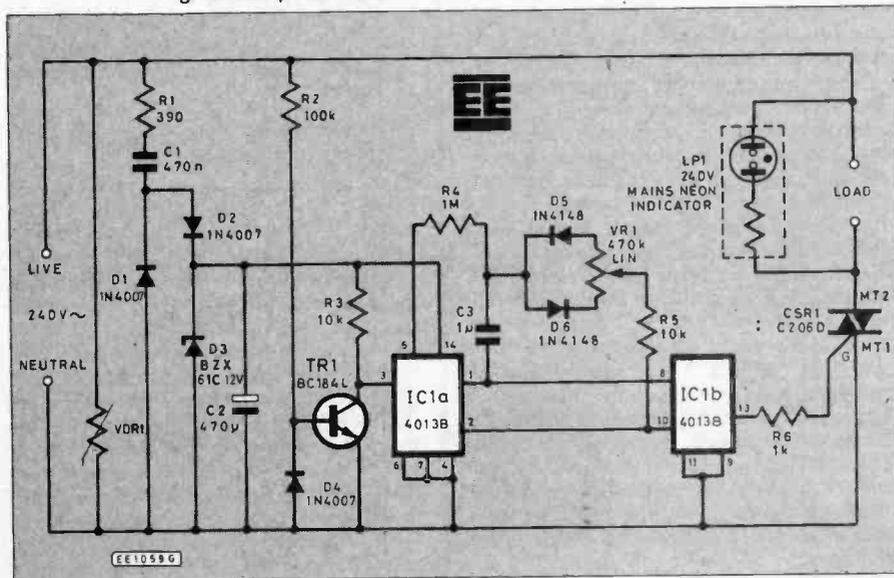

COMPONENTS

See
**Shop
Talk**
page 484

Resistors

R1	390 1 watt
R2	100k 1 watt
R3,5	10k (2 off)
R4	1M
R6	1k
All 0.5W types except R1 and R2	

Potentiometer

VR1	470k lin. carbon with nylon or plastic spindle
-----	--

Capacitors

C1	0.47μ 250V r.m.s. a.c. suppression type
C2	470μ axial lead elect. 25V
C3	1μ polyester layer

Semiconductors

IC1	CMOS 4013B dual "D" type flip-flop
TR1	BC184L
D1,D2,D4	1N4007 (3 off)
D3	BZX61C12V 12volt Zener
D5,D6	1N4148 (2 off)
CSR1	C206D triac

Miscellaneous

VDR1 mains transient suppressor; printed circuit board available from the EE PCB Service, order code 578; ABS box, 120 x 65 x 40mm; plastic control knob; 240V mains neon indicator (with integral resistor); 8-pin d.i.l. socket; connecting wire; fixings etc.

Approx. cost
Guidance only

£10

LETTERS

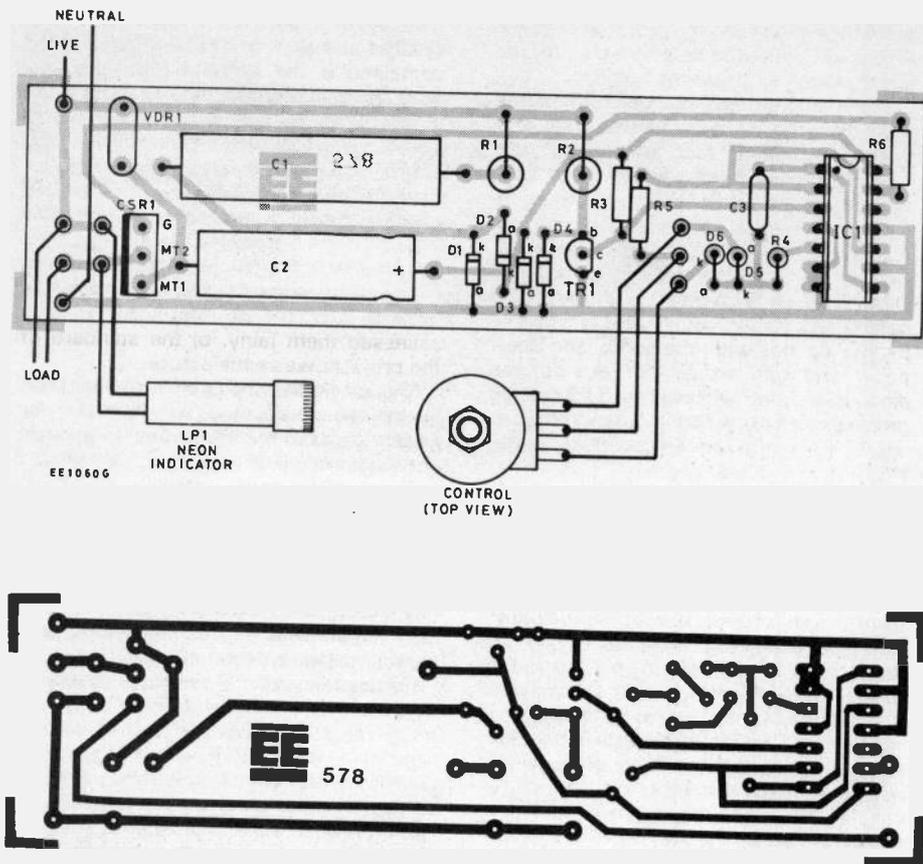


Fig. 3. Layout and wiring of the controller. The earth wires from the mains input and to the load should be connected together with a screw connector—see photo.

the meter connected across the 470μ capacitor C2, set to a range covering up to 250 volts d.c. This will protect your meter if a fault is present.

Plug in, and if there is scarcely any reading, reduce the meter range until you can see the voltage on C2, which should be around 11.5 to 12 volts. If this seems correct, unplug and reconnect the meter between negative and the bottom end of R3 (collector of TR1), which should read around five volts when plugged in again. This is an average reading, indicating that TR1 is switching properly. Ignore any reading present when the unit is unplugged, which will be due to charge stored in C2. If all appears well, it remains only to insert IC1 and plug in again; the neon indicator should begin to flash at about 1Hz, and adjustment of VR1 should vary the flashes from so brief they're just visible to so long they're very nearly continuous.

FINAL ASSEMBLY

The layout of the unit in its case is shown in Fig. 4. The "cord-grip" arrangement is a little unusual; since the unit is rather compact, there isn't space for most of the available types of cable clamp. The solution is to place a nylon screw between the two cable entry holes and tie the cables firmly to it with a couple of nylon cable-ties. This provides a compact, cheap and effective fixing for both leads. No metal parts should be exposed on the outside of the case. A potentiometer with a nylon shaft and a plastic knob must be used. The unit must be connected to the mains via a fused (3A) plug.

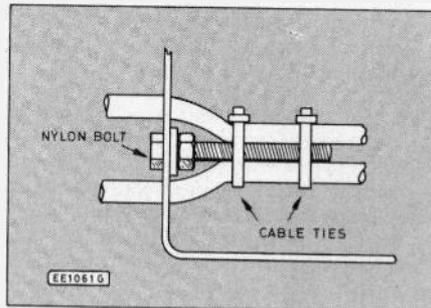


Fig. 4. Method of securing the mains leads.

IN USE

Though designed to control a soldering iron, this simple unit could be used or adopted for a host of other applications. It can be employed anywhere where a low-power interference-free controller is required, for instance with an electric blanket. The specified triac is rated at three amps, permitting safe use with loads up to about 500 watts (though a small heatsink may be required above a couple of hundred watts).

Alternatively it could be used to operate flashing displays of various kinds, disco lights, Christmas tree lights, and so forth. The flash rate can easily be altered or made variable just by changing the pot connections and the value of C3. Two pots would allow independent adjustment of the "on" and "off" periods. C3 of course must be non-polarised: in practice this means that larger values should be made from two electrolytics placed back-to-back. Low-leakage types such as tantalums are preferable for this. The prototype has been tested with two 10μ tantalum beads giving a flash rate of around five seconds, with no problems at all. □

Improving

Sir—I have been reading EE ever since the very first issue (November 1971 and I still have it!), through the years the magazine has been featuring transistor only projects, then onto i.c. projects and now to computer projects. The magazine has improved ever since and is improving even more as the years go on, who knows we might see a project using fibre optics instead of connecting wires.

I read S. Hudman's letter in the EE July issue and agree with him that there are very limited projects for the Commodore 64/128, I would like to buy an EPROM Programmer to interface with my computer but alas they are too expensive, I would like to see this as a future project in EE but, I'm good at building projects but not designing them so this is a hint to any project designer.

I noticed that there are two features in the magazine for Spectrum and the BBC computers but none for the humble Commodore. So how about it Mr Kenward, will there be a page or half a page for us Commodore owners? I'm sure that after S. Hudman's letter was printed it will now create a flood of letters from other Commodore owners . . .

Alan Smith
Aberdeen

The Fibrealarm (EE April 85) used an optic fibre as part of a loop alarm system—another project using fibre optics is now being designed.

The "flood" of letters is now about six.

Electronics on the Curriculum

Sir—I have noticed with interest the recent correspondence about electronics in schools. As someone closely involved in teaching and examining electronics at both "O" and "A" level perhaps I could be allowed to make a few points.

(1) Electronics is most usually found in schools as modules within other subjects (e.g. Physics or CDT), only rarely is it taught as a separate subject. Whether this picture will change significantly remains to be seen.

(2) While the systems approach, where pupils of 12–13–14 assemble working electronic systems from prebuilt modular boards, is excellent for making children aware of what electronic systems are capable of and giving them some "design" experience, albeit somewhat constrained by resources, there comes a time when to progress further pupils have to be shown how to design with electronics at the "naked chip" level. Unfortunately most modular courses do not get heavily into this area which is a pity since it is only here that pupils begin to feel "in control" of what they are doing. There is always some mystery about modular boards which able pupils are unhappy with. At the naked chip level concepts such as the potential divider, voltage and current requirements of

inputs and outputs, loading effects and interfacing come to dominate and need teaching and practical experience.

(3) At this school we have been fortunate to be able to assemble classes for fully blown courses at "O" and "A" level and most students appear to enjoy the work. It has been interesting to note that a high proportion of those taking the senior course have decided to undertake electronics related courses at University, some with considerable distinction. I am told that they would not normally have considered electronics as a career had they not experienced it in a practical sense in the lower part of the school. This backs up your point about the need for coherent courses pre 16.

(4) Hobbyists do not rule OK. The days are long since past when the supply of electronics engineers could come mainly from those who have discovered it as a hobby during their teenage years. One could claim that such people have taken up electronics in spite of their school experience. What we need now are coherent courses of real substance within which young people can discover that the subject is interesting, challenging and useful regardless of hobby interest. Being a girl's school none of our pupils would normally have electronics as a hobby nor would they call into WH Smiths to buy an electronics magazine, yet given experience of the work in school some are indeed prepared to base a career on it. Such courses already exist but many schools find it difficult to fit them into a school week. We are here up against not just the old arts/science divide of C. P. Snow but the updated tripartite divide of arts/science/technik. Electronics is of course part of technik—a concept weak in English culture and education.

(5) Physics as a discipline is in no way essential to the study of electronics and many science teachers fail to realize this. How many pupils who say "I would like to be an electronics engineer" are told "Oh—you will need strong Physics then". Whether the Universities or Colleges ask for it or not this is simply not true. Some mathematical facility is of course important but having Physics is a bonus, not an essential.

(6) Do not base your case for teaching electronics on its economic value alone. Its educational virtues lie in its systems orientated thinking and the problem solving approach, together with the global applicability of concepts such as feedback and stability. If examples are needed consider the effect of opinion polls on an election outcome or the importance of systems ideas to ecological problems. We would wish to teach electronics whether there were jobs at the end of it or not. In fact I am very cynical about the current attempts to attract more women into electronics. This has only occurred because there is a shortage and not through altruism and ideas of natural equality. Should the shortage disappear will there still be the cries to encourage women?—I think not. A certain critical mass of women in the engineering professions may significantly change the tasks engineering applies itself to. Are the men in the profession ready for this? This brings me to my final point.

(7) To obtain a "good press" amongst school students electronics as a discipline must decouple itself from the arms and

weaponry industries and the issue of technologically caused unemployment. It is not just a case of emphasising medical, caring, conservationist and humanly orientated applications in publicity but actually emphasising them in fact. Having half our working engineers connected to the "nasty" end of the business is nothing to be proud of even if the most alluring or complex technology is to be found there. Do we need an Engineering Hippocratic Oath? One could claim that Physics had committed suicide by its association in people's minds with 'the bomb' and Chernobyl and one would not like to see electronics and Information Technology go the same way. At the moment the latter appear to have a relatively neutral image. Will things stay that way?

We were warned nearly two decades ago about the social strains electronics developments would bring to society and the schools are now feeling some of them. I do assure you that we are doing our best to cope while trying to serve many masters. A large infusion of directly targetted money to go to all secondary schools to buy equipment and teacher preparation time would go a long way towards improving the numbers taking up electronics. (We have yet to see the effects of the TVEI schemes.) As a discipline in schools it is capable of selling itself given sufficient equipment and knowledgeable staff. What other suggestions do people have for getting electronics a decent slice of the curriculum.

Your own efforts to champion this cause are to be applauded.

Paul Stevenson
Physics/Electronics Dept
Norwich High School for Girls
Norwich

Teaching Experience

Sir—Although I have only subscribed to your magazine since last September, your editorial in the May 1987 issue has prompted me to write and inform you of my experience of teaching electronics.

I am a teacher of Maths and Physics at The British School in The Netherlands and have taught there since 1975. Two years ago, due to a change in our Physics syllabus at "O" level, I was faced with the task of teaching a small amount of electronics to the fifth form. This was a topic about which, even as a Physics teacher, I knew absolutely nothing. In order to educate myself I decided to run a CEE (Certificate of Extended Education) course for a small group of sixth formers first, with the idea that we could learn together and then I would be able to teach my fifth formers properly. I used Robert Penfold's book *Electronics—build and learn* as a main guide and any other electronics book I could get my hands on.

In the beginning it was incredibly difficult, perhaps you cannot imagine it but I still remember the problems. Here are a few examples: I did not know of the existence of "S Dec" or "Breadboard" (in fact I still don't know what breadboard really means). I did not know what I.e.d. stood for, nor what a "seven segment display" was. Transistor numbers were very confusing, ZTX300 sounds a lot different to BC109. What is the difference between a bistable, a multivibrator and a flip flop... etc.

However I pressed on with the CEE syllabus as it appeared to be suitable and it contained a fair emphasis on practical work. Being inexperienced and also unable to visit other schools to see how to run such a course, I wrote to the Examining Board for advice. I received from them a copy of their detailed syllabus notes. I did not find these notes at all helpful. My letters to the Examining Board regarding the standard of my pupils' practical project were not answered: I had to assess the projects but still do not know if, a) I assessed them fairly, b) the standard of the projects was satisfactory.

My point is that the Examining Board will award the certificates but they do not appear to have the resources to provide adequate advice or teaching material for anyone wishing to run the courses! If, at the same time as using their wisdom to compile a syllabus they prepared detailed, structured notes and a suggested teaching plan, together with a list of available equipment, then teachers like me would not find the task so daunting and would certainly make a better job of it!

Fortunately, last September (1986) I came across your magazine. Owen Bishop's *Exploring Electronics* series is really excellent and pitched just at the right level for my pupils. I myself find it very enlightening and I look forward to trying out the circuits each month. It contains just the sort of information I would have appreciated from the Examining Board and it provides an interesting and stimulating course. I will certainly use it in my teaching next year.

I too would like more students to be able to move into employment in the field of electronics but how do I guide them? Perhaps you can help me—I have two requests for information.

Firstly, as the CEE will cease to exist soon, can you tell me what "certificate" courses are commonly recognised in the UK and could you recommend one in particular (roughly which is equivalent to the CEE?)

Secondly, I see advertisements for "Teach In" courses in your magazine but I do not know exactly what they are. Is it possible to buy a complete course as a package, including the computer software, or is it necessary to buy back issues (now sold out) of EE from October '85 to June '86? Would the software be any use on its own? I would very much appreciate any information you could send me on this matter. We have BBC computers here at school and if "Teach In" is at all suitable, I would like to get it organised as soon as possible.

Chris Davis
The British School in The Netherlands
"Breadboard" is derived from one form of construction of prototypes used in the early days of radio. This consisted of a wooden board into which were hammered panel pins; the circuit was then constructed on this base. Modern plug in "breadboards" are of course much neater and re-usable.

We believe the City & Guilds courses will be of interest to you in place of CEE—see our new series starting next month.

Our various Teach-In series are aimed at teaching beginners the basics of electronics. They have been running since 1971. Teach In '86 will be republished as a book in the very near future—price around £2. The Teach-In '86 tapes are useful on their own as they are in the form of questions and answers on electronics theory.

Exploring electronics

OWEN BISHOP

This series is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. There will not be masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

Part 15 Investigating logic circuits

AS THEIR name implies, logic circuits carry out a logical operation. Such a circuit may have one or more *input* terminals and one *output* terminal.

The state of the output is determined by the state of the inputs, depending on a logical rule. What the rule is depends on the "wiring" of the circuit.

Logical circuits can be built up from diodes, transistors and other components but ready-made integrated circuits give better performance at lower cost. The i.c. chosen for these investigations is the 7400 i.c. It contains four separate and identical logic gates, see Fig 15.1.

A logic gate is the logical unit out of which more complicated logic circuits can be built. Each gate of the 7400 has two inputs and performs the NAND operation. We will not try to understand "how it works", but simply to find out "What It Does".

INVESTIGATION ONE

We shall commence our investigation of logic circuits by taking a look at the operation of just *one* NAND gate as shown in Fig. 15.2. The i.c. needs a power supply through pins 7 and 14. Pin 14 is connected to the positive supply and pin 7 to 0V ("ground"), as shown in the demonstration bread-board layout in Fig 15.3. This supply feeds all four gates.

Note that the 7400 series of logic i.c.s, to which the 7400 i.c. belongs, is designed to work on a 5V supply. A 6V supply may be used, but *never* use anything higher than 6V.

The output of the gate is indicated by the light emitting diode (l.e.d.), D1. This lights when output is "high", and is off when output is "low".

There are *two* inputs to which we attach flying leads, *A* and *B*. Try connecting them both to 0V (both low), then one to low and one to 6V (high), and finally connect both to high. Check that the behaviour of the output agrees with the Truth Table for NAND as described in the next section.


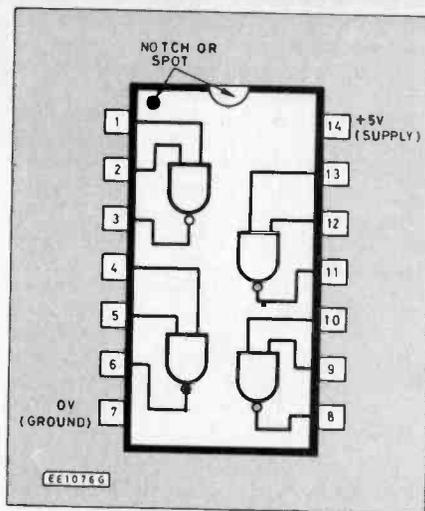


Fig. 15.1. The 7400 i.c. showing the pin connections for its four NAND gates.

LOGIC GATES

Inputs and outputs may be either "high" (for example +6V) or "low" (=0V). For convenience, we represent a high input or output by "1" and a low input or output by "0". The way a logic gate behaves depends on the logical operation it is designed to perform.

Fig. 15.2. Investigating the action of a NAND gate. The numbers by the gate terminals are the i.c. pin numbers.

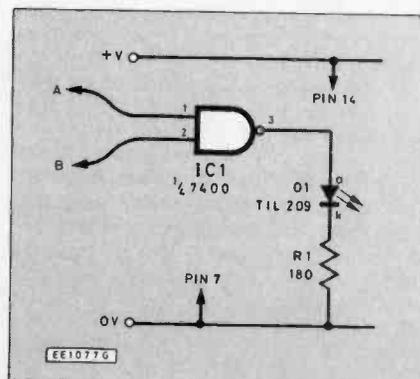

There are three main logical operations:


NOT (also called INVERT): There is only one input. The output is the opposite of the input. If the input is "1", output is "0". If the input is "0", output is "1".

OR: There are two or more inputs. If any one or *more* inputs are high, the output is high. So output is low only if *all* inputs are low.

AND: There are two or more inputs. If *all* inputs are high, then output is also high. But if any one or more inputs are low, output is low.

The action of these gates can be summarised in the following truth tables:

Fig. 15.3. Demonstration component layout for the NAND gate.

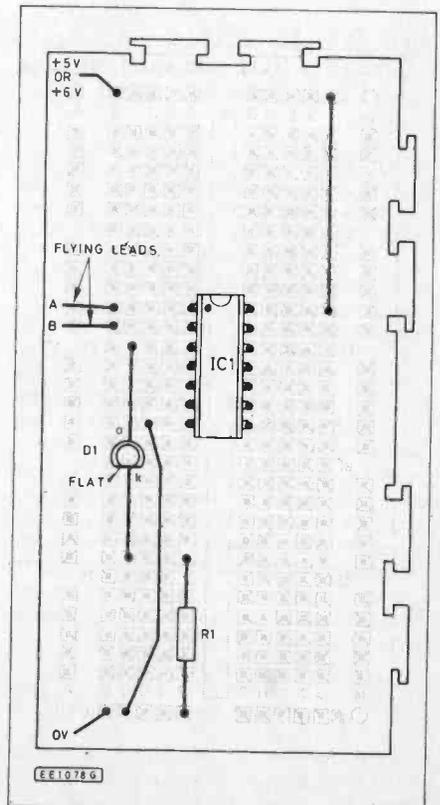

See
**Shop
Talk**
page 484

Resistors

R1, R2 180 ohm (2 off)
All 0.25W 5% carbon

Semiconductors


D1, D2, TIL 209 or similar light-emitting diode
IC1 7400 quadruple NAND gate

Miscellaneous

Breadboard (e.g. Verobloc); connecting wire and 5V to 6V supply.

Approx. cost
Guidance only,

£5

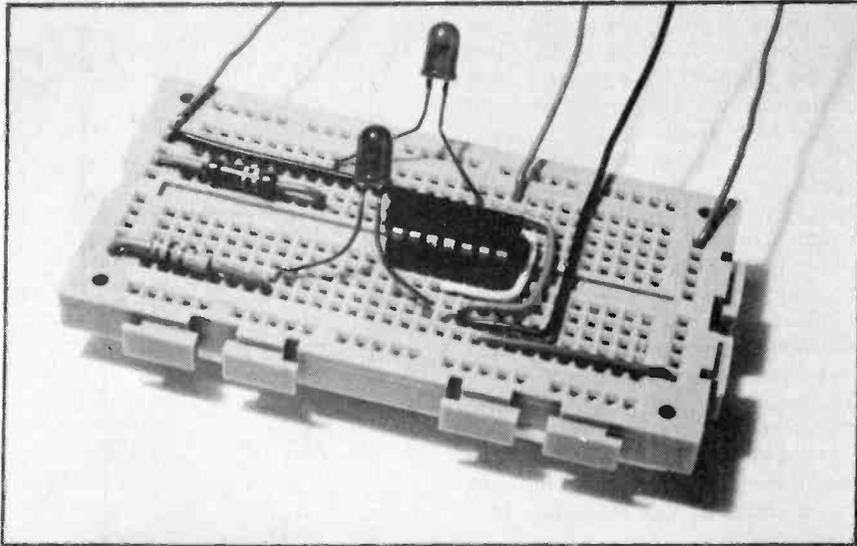

NOT		OR			AND		
Input	Output	Inputs	Output		Inputs	Output	
		A	B		A	B	
0	1	0	0	0	0	0	0
1	0	0	1	1	0	1	0
		1	0	1	1	0	0
		1	1	1	1	1	1

Although the diagrams and tables above show only two inputs, remember that OR and AND gates can have more than two inputs.

MORE LOGIC GATES

Three other kinds of logic gate are often used:

NOR: which is short for NOT-OR. It is equivalent to an OR gate followed by a NOT gate, so its output is the opposite of that of an OR gate.

NAND: which is short for NOT-AND. It is equivalent to an AND gate followed by a NOT gate, so its output is the opposite of that of an AND gate.

EXCLUSIVE-OR: there are two inputs. Output is high when one OR the other BUT NOT BOTH of the inputs are high. When both inputs are low or both are high, output is low.

The action of the gates is summarised in the following Truth Tables:

NOR			NAND			EXCLUSIVE-OR		
Inputs	Outputs		Inputs	Outputs		Inputs	Outputs	
A	B		A	B		A	B	
0	0	1	0	0	1	0	0	0
0	1	0	0	1	1	0	1	1
1	0	0	1	0	1	1	0	1
1	1	0	1	1	0	1	1	0

INVESTIGATION TWO

Try the effect of joining both inputs of the NAND gate together as shown in Fig 15.4. Work out what you think will happen when the flying lead A is touched to (i) low and (ii) high. Try it and see. *What is the name given to this logical operation?* (answer p.506).

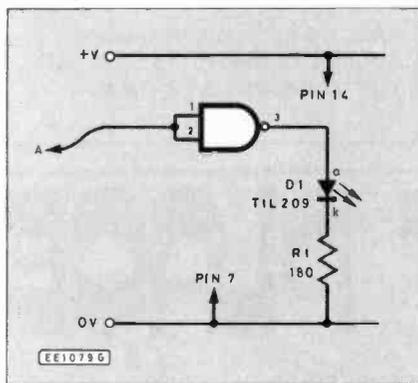


Fig. 15.4. Another way of using a 2-input NAND gate.

Next, using your breadboard, layout and connect up the circuit of Fig 15.5(a). Try to work out what will happen when A and B are touched (i)


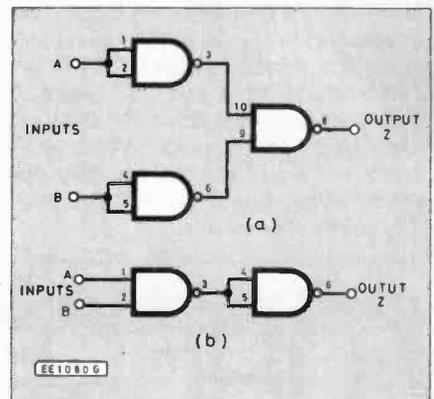


Fig. 15.5. Two more ways of connecting NAND gates.

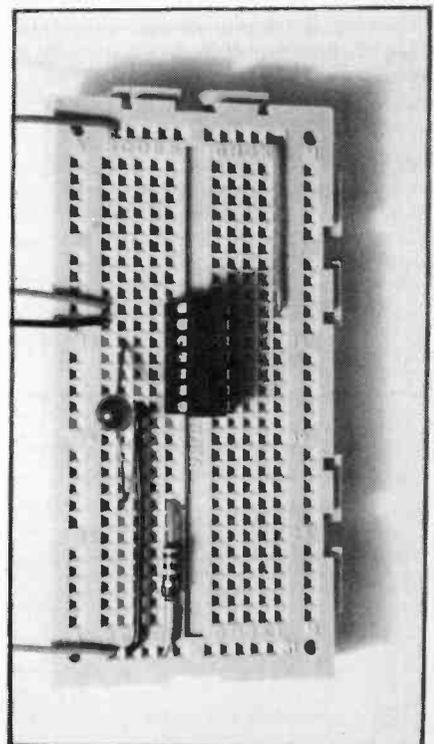

both to low, (ii) one to high and one low, and finally (iii) both to high. Try it.

Check the Truth Tables to see which logical operation these three gates are performing. (answer p.000) Repeat for the circuit of Fig 15.5(b). *How could you build a NOR gate, using NAND gates?*

INVESTIGATION THREE

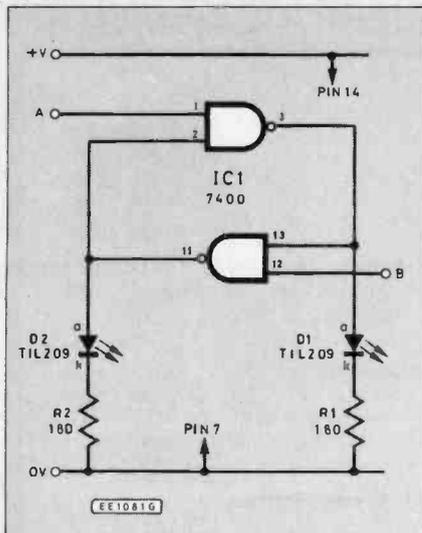


Fig. 15.6. A "flip-flop" circuit using NAND gates.

Connect up two gates as shown in the circuit diagram Fig 15.6 and the "test bed" component layout Fig. 15.7. In your previous experiments, you may have noticed that, when an input is not connected to anything, it behaves as if it was connected to high.

The two inputs *A* and *B* are both high when unconnected, as in the diagram. Now touch one of them to low. What happens? Now take it away from low again. What happens?—Maybe nothing has happened so far.

Now touch the other input to low. What happens now? Remove it from low, then touch it to low again. Does anything happen? Play around with this circuit until you have found out just how it behaves.

This circuit has the properties of a *bistable* or "flip-flop", like the one described in Part 7 of *EVERYDAY ELECTRONICS* January 1987. It is much easier to build. It can remember which input was the last one to be made low. Bistables similar to this are used by the thousand in the memory i.c.s of pocket calculators and computers.

Try any other ways of joining gates that you can think of: try to work out what should happen, then find out if it does. You can join two or more input pins together; you can feed an output

ANSWERS

Fig 15.4 is equivalent to a NOT gate.

Fig 15.5a is equivalent to an OR gate.

Fig 15.5b is equivalent to an AND gate.

Make a NOR gate by feeding the output of Fig 15.5a to a NOT gate, made as in Fig 15.4.

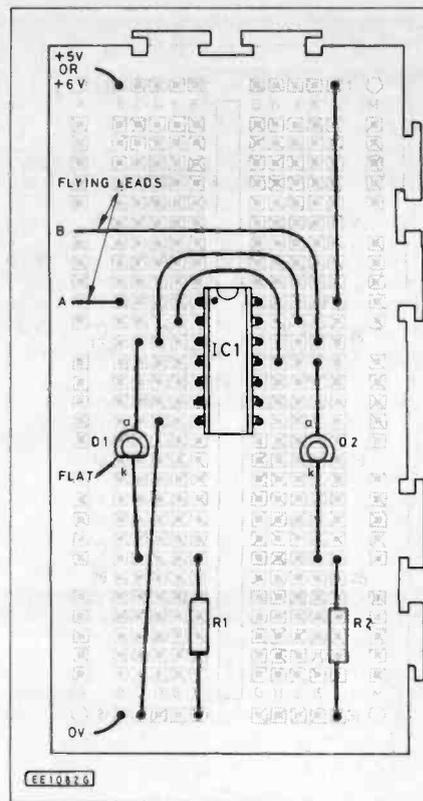


Fig. 15.7. Test-bed component layout for demonstrating the action of the "flip-flop" circuit.

to up to eight inputs: but you can *NOT* wire two or more *outputs* together. Next Month: Oscillators using logic i.c.s.

MARKET PLACE

MICRO Ammeters, Voltmeters, ISOL-trans, 3phs motor, wattmeter, PSU, 50 volt trans. £10 the lot. Blackburn, 57 Friern Watch Avenue, Nth. Finchley, London N12 9NY. Tel: 01-445 6997.

FOR SALE: Two Centronics 101 printers with manuals and spare parts £280. ono. Tel: Haddenham (0844) 291993.

WANTED Elan Enterprise 164 basic cartridge or complete computer, cheaply. Mr. J.D. Crossley, "The White House", Limpenhoe, Norfolk NR13 3AL. Tel: Gt. Yarmouth 700332.

EPROMS 2716 2K blanked and fully working £1 each. David Keene, 3 Trelawny Road, Exhall, Coventry CV7 9FB. Tel: (0203) 490050 (evenings).

WANTED: Newbrain A/AD computer circuit diagram, also operating manual. S. Coppin, 3 St. Pauls Road, Honiton, Devon EX14 8BR.

WANTED: Panel meters with scales of 0-20V f.s.d. and 0-1A must be unscratched and same size. S. G. Phelan, 47 Doothorpe, O.P.E., Hull HU5 9HA. Tel: 0482 851244.

PRESENT address of Teleton Electronics Audio Co. or circuit of Teleton Amplifier 54Q-307. Tel: Accrington (0254) 35672.

JUPITER Ace User Domain Resource Centre hardware and software projects for free. For details contact: Ian Jones, 21 Dene Street, Pallion, Sunderland, Tyne & Wear.

FREE READERS ADS.

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. EE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a **cut-out valid "date corner"**. Ads. will not appear (or be returned) if these rules are broken.

COMPONENTS, resistors, capacitors, transistors, diodes, pots, switches, cable. £10. M. Topping, Tree Court A, Owens Park, Fallowfield, Manchester M14 6HD.

WANTED: Sinclair ZX81 computer in good working order preferably with instruction and/or accessories. C. C. Fowler, 32 Joselin Close, Earls Colne, Essex CO6 2SE.

Name & Address:			

BLOCK CAPITALS PLEASE

Please read the **RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no. Please publish the following small ad. **FREE** in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature..... Date.....
COUPON VALID FOR POSTING BEFORE 18 SEPT., 1987
 (One month later for overseas readers.)

SEND TO: EE MARKET PLACE, EVERYDAY ELECTRONICS, 6 CHURCH STREET, WIMBORNE, DORSET BH21 1JH.

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid "date corner"**

EE MARKET PLACE
 SEPT. '87

FOR YOUR ENTERTAINMENT

BY BARRY FOX

Time Warp

We all know the old adage GIGO; garbage in, garbage out. If you give a computer poor information, it will give you poor answers. We also all know the other old adage; computers don't make mistakes, it's the people who use them.

Not always. Sometimes the people who use computers are trapped by the mistakes made by others—Try these two.

Recently owners of Apricot computers wondered why their files were coming up with the wrong date and accounting systems were going up the spout. Closer examination showed that the date stored in their computer's calendar memory was 40 days and 40 nights out of step.

This can put the wrong dates on test, letters and invoices. Apricot discovered that the fault lies in the Basic Input/Output System, or BIOS, which was for several years supplied with all Apricots.

The BIOS is software which interfaces the computer's electrical circuits with the operating system software controlling all its vital functions. A battery-backed clock inside the computer is controlled by the BIOS and is supposed to keep a permanent running check on the time and date, with allowance for leap years.

For several years the Apricot clock worked properly. Then, at the beginning of March 1987, it went wrong by 40 days and will stay wrong for the next full year.

Apricot has been trying to salvage the situation by offering owners an updated version of the BIOS software. But replacing the old BIOS with the new version requires a degree of computer skill well beyond most business users. Worse still, some programs tailored to the BIOS will not work properly with the new BIOS. The keyboard is different and the screen layout changes for some programs. Some "utility" programs just aren't usable.

For these people Apricot is offering an extra program, which, when loaded into the computer, automatically back-dates the clock by 40 days every time the computer is switched on. But installing this program also requires a fair knowledge of how computers work. Fine for readers of EE but not so fine for businesses which regard computers as glorified typewriters.

Reserved Word

The MS-DOS operating system from Microsoft has now become the *de facto* standard for home and personal computers. So all over the world people are using MS-DOS machines as word processors.

Let's suppose you are writing an article, as I was recently, about electrical connections. When the text was written I went to save it on disc as a file named *Con*. The word processing program automatically put a *.doc* label on the end.

The word processor immediately told me that there was already a file named *Con.doc* on the disc. I knew there wasn't but did a directory check. This confirmed that there was no such file on the disc. So I tried to save again and the computer asked me if I wanted to overwrite what it said was already there, but I knew wasn't.

All right, I thought, if you think there is something there called *Con.doc*, go ahead and overwrite it. So I entered the command. Immediately the system threw up its hands in horror and crashed.

Subsequently I found that something similar is likely to happen with other short words like "aux" and "com", file names you might perhaps use when writing an article about auxiliary power supplies or common ground connections.

"O' yes", said a computer-wise friend, "they are reserved words. MS-DOS uses them as basic commands, so you can't use them as file names for wordprocessing, or spreadsheets or databases."

I phoned Microsoft, authors of MS-DOS. "O' yes, it's a well known fact", said Microsoft. "We've never had any reports of problems. Any good programmer should write the wordprocessing software round it, to warn the user".

I asked Microsoft what their own word processing program WORD did when someone tries to save a file with a reserved name. It gives a "disc full" error message, Microsoft told me.

Why not a more useful message like "You cannot use this file name, it is one of our reserved words"?

"It's a well known fact etc etc", came back Microsoft. "It always has been and it always will be. No-one uses those words for files" Not true. / did.

So here's what I am going to do. The next time I am at a trade or public computer show, with the opportunity to get my hands on equipment, I am going to go round every stand that is running a word processor program, type in a couple of words and try to save them as a test file with the file name *Con*. Then we'll see whether "it's a well known fact".

Speak Easy

Hi fi buffs lie awake at night, not dreaming of music, but worrying about the latest development and whether they should have it.

Over recent years loudspeaker cables have been a major source of hi fi worry. Few people dispute that it makes poor sense to use thin bell wire to carry the heavy currents at low voltage with which modern amplifiers drive modern loudspeakers.

The currents are high because modern loudspeakers are inefficient at converting electrical energy into sound. This is the penalty we pay for higher fidelity and good bass response from a small cabinet.

Effectively the speaker system has to throw away some energy in the middle and upper frequency range so that the low frequency sound energy can be of matching level.

If the speaker connecting cables are thin wires of high resistance, then some of the expensive audio energy from the amplifier is converted into useless heat before it even gets to the loudspeakers.

There is a wide choice now of specialist loudspeaker cables, made from thick, low resistance copper. Sometimes the copper is braided and sometimes it is formed by a

process which aligns the crystals and minimises the amount of oxygen impurity. All this is supposed to improve the sound.

Whether linear oxygen free copper cable (LOFC) really makes a difference, or whether the difference is heard only by people who have paid extra for their cables and want to hear a difference, is a moot point. But certainly there is a lot to be said for using thick copper wires.

The cheapest way of buying thick copper wire is to go to an electricians' shop—not a hi fi dealer—and buy 15A or even 30A mains wiring cable. The copper cores are thick and has very low resistance.

Although mains cable is expensive, it is far cheaper than fancy hi fi cable. The only problem is that when you buy heavy mains wire, it comes as 3-core cable, not 2-core. So you are paying heavily for an extra core which serves no useful purpose. Now, there *is* a purpose for this extra core.

Bi-Grounding

Marantz, once an American hi fi company but now a Japanese operation with a majority shareholding owned by Philips, has come up with an idea called "bi-grounding". The original proposal came from Marantz engineer Ken Ishiwata who is Japanese but works in Europe. His design for a loudspeaker which uses three wires instead of two is now being made in England for the European market by Goodmans of Havant—*A cosmopolitan idea!*

Hi fi loudspeakers contain at least two separate transducers, one designed to handle only low frequencies ("woofers") and the other only high frequencies ("tweeters"). In the most expensive hi fi systems these transducers are individually powered by separate amplifiers connected by separate pairs of wires. In less expensive systems the loudspeaker is fed from a single amplifier by a single pair of wires, and the separate transducers inside the loudspeaker are joined together by an electric circuit called a "crossover". This separates the high and low frequency signals and feeds only low frequency signals to one transducer and only high frequency signals to the other.

Ken Ishiwata's idea is to provide a halfway stage between these two, expensive and cheap, approaches. He believes that there is unwanted electrical interaction between the two transducers if they share the same "negative earth" wire to the amplifier.

This is because all transducers produce spurious signals (back e.m.f.) and if these feed back into the crossover, low frequency signals will reach the high frequency transducer. By using separate "earth" wires back to the amplifier there is less chance of interaction in the crossover.

As supplied, the Marantz loudspeaker has a short bridging wire between two of the terminals, so that owners can connect it in conventional manner with an ordinary pair of wires running to a pair of terminals on a hi fi amplifier. Adventurous hi fi enthusiasts, however, can remove the bridging wire and try connecting the loudspeaker to their amplifier using 3-core cable instead of 2-core cable. This, claims Marantz, gives a marked improvement in sound quality.

By subcontracting manufacture to UK company Goodmans, Marantz has kept the cost down to under £200 a stereo pair of loudspeakers. It is easy for people to try the bi-ground connection if they want, by using the third, unused, core of mains cable.

CAR OVERHEATING ALARM



T. R. de VAUX-BALBIRNIE

An audible bleep warning of car overheating

THIS circuit was designed with caravanning in mind since the engines of many tow cars tend to overheat especially in mountainous areas. It could also be useful to non-caravanning readers who experience overheating problems with any car. It is suitable for both positive and negative-earth systems.

AUDIBLE WARNING

Although the car may be fitted with a water temperature gauge, the reading on this is easily missed and an *audible* warning is more effective in attracting attention. Some designs produce a continuous signal in the event of overheating. This is unnecessary and causes undue annoyance especially since it may take several minutes for the engine to cool to normal operating temperature again. In the present system, a short bleep (of nominally one second duration) is given each half-minute. This gives excellent warning without being obtrusive.

The entire circuit, apart from the engine-mounted temperature sensor, is housed in a plastic box with an audible warning device mounted on top. A terminal block connects the sensor and car electrical supply. The sensor is attached with adhesive so, although firmly mounted on the engine, it may be removed should the need arise.

CIRCUIT DESCRIPTION

The circuit of the Overheating Alarm is shown in Fig. 1; IC1 is an operational amplifier used in comparator mode. It switches on when the temperature of the sensor, R1, rises above some preset value—nominally 95 degrees C. The potential divider, R3/R4, applies a fixed reference voltage to IC1 non-inverting input (pin three). A second potential divider is formed between R2 and VR1 in the upper section and R1 in the lower one. Since R1 is a negative temperature coefficient device, its resistance falls as its temperature rises. Thus, the voltage applied to the inverting input falls with rising temperature.

With correct adjustment of VR1, the inverting input voltage will fall below the non-inverting one at the required tempera-

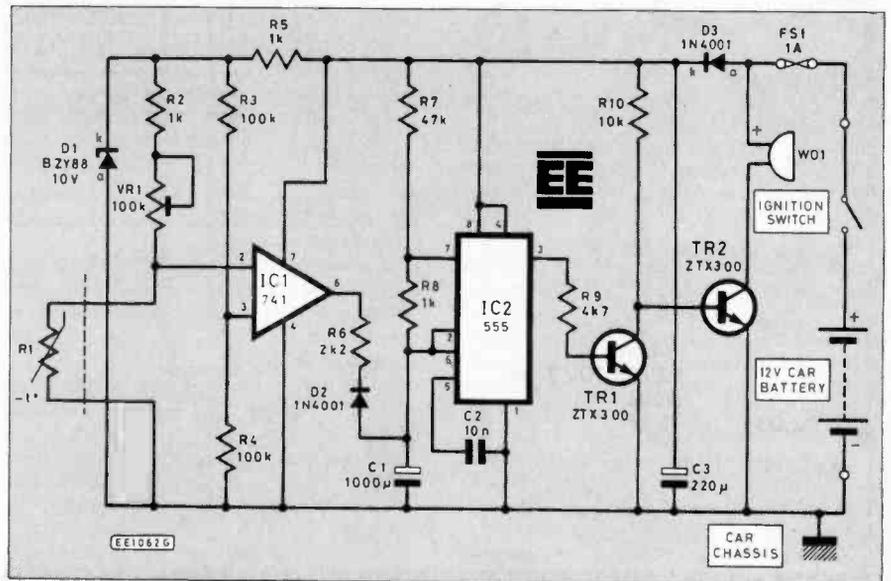



Fig. 1 Circuit diagram of the Car Overheating Alarm.

ture. IC1 output (pin six) then goes high (positive supply voltage). This allows no current to flow through R6 and D2 since D2 is reverse-biased. There is therefore no effect on IC2 which functions as a free-running multivibrator producing a train of positive-going pulses from its output (pin three). With the values of C1, R7 and R8 used in the prototype, each pulse will be high for 30 seconds and low for one second approximately.

Transistors TR1 and TR2 invert the pulses to give short high and low states (see

Fig. 2). This happens in the following way. With IC2 pin three high, current flows through R9 to the base of TR1 so turning it on. TR1 collector is then low so TR2 is off. With IC2 pin three low, TR1 is off with its collector high. TR2 is then switched on and the audible warning device, WD1, in its collector circuit operates. The inverting effect causes WD1 to bleep for one second each 30 seconds approximately. With R1 below the operating temperature, IC1 is off with pin six low. This makes IC2 pins two and six low also, resulting in IC2 output

Fig. 2 IC2 output and WD1 drive waveforms.

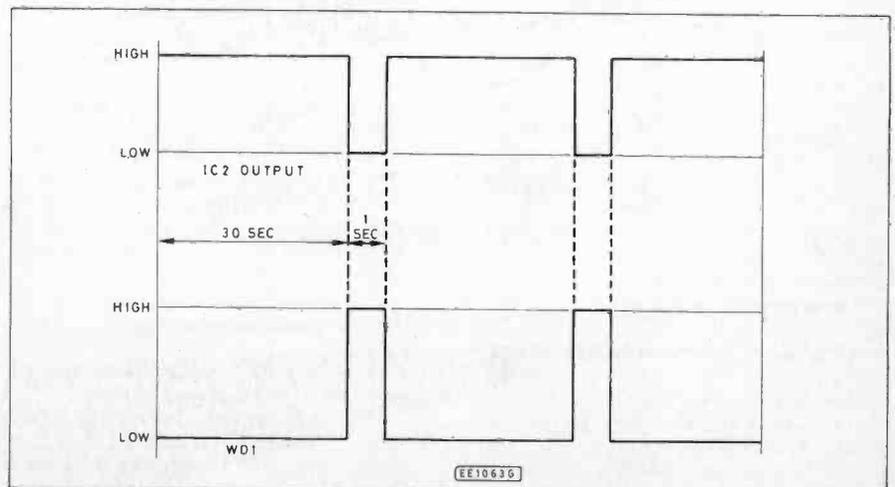

COMPONENTS

See
**Shop
Talk**
page 484

Resistors

- R1 GL16 bead thermistor
resistance at 20°C 1M
R2,R5,R8 1k (3 off)
R3,R4 100k (2 off)
R6 2k2
R7 47k
R9 4k7
R10 10k
All 0.25W carbon, except R1

Potentiometer

- VR1 100k miniature vertical preset

Capacitors

- C1 1000µ p.c.b. elect. 16V
C2 10n
C3 220µ p.c.b. elect. 16V

Semiconductors

- IC1 741 op. amp.
IC2 555 timer
TR1,TR2 ZTX300 npn silicon
D1 BZY88 10V Zener diode
D2,D3 1N4001

Miscellaneous

- WD1 12V solid-state buzzer (480 ohms impedance).

Approx. cost
Guidance only

£13.50

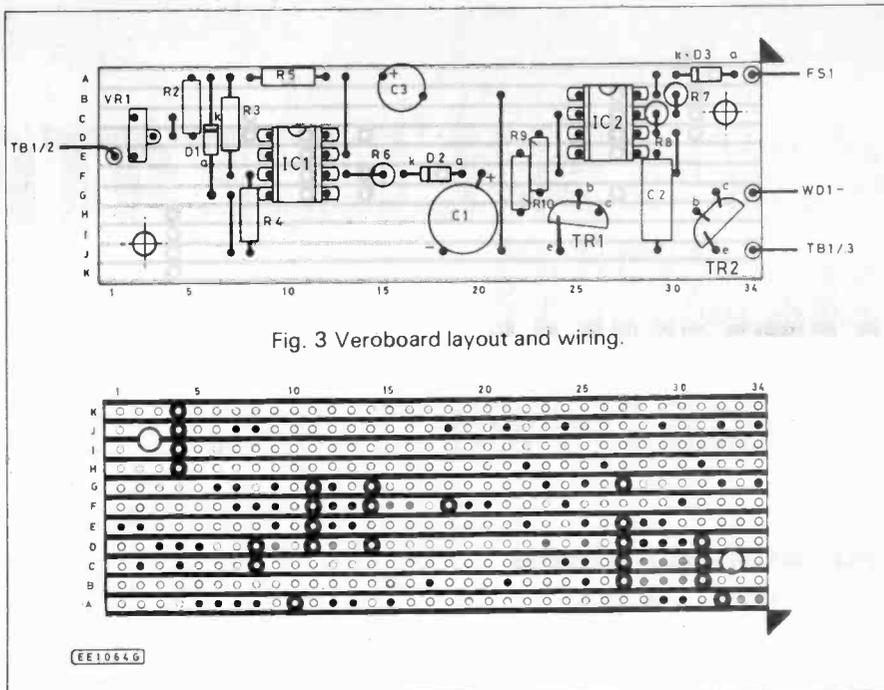


Fig. 3 Veroboard layout and wiring.

FS1 20mm chassis fuseholder with 1A fuse.

TB1 3A terminal block—three sections.


Eight pin d.i.l. i.c. sockets (2 off); plastic box approx 120 x 65 x 40mm; 0.1 inch matric stripboard size 11 strips x 34 holes; stranded wire; auto-type wire; connectors; fixings; materials for sensor (see text).



being high continuously. After inversion, WD1 remains off.

The purpose of R5 and Zener diode, D1, is to stabilise the supply to the op-amp inputs for precise operation. D3 and C3 smooth the fluctuations produced by the car generator. FS1 is a fuse which protects the system from accidental short-circuits.

CONSTRUCTION

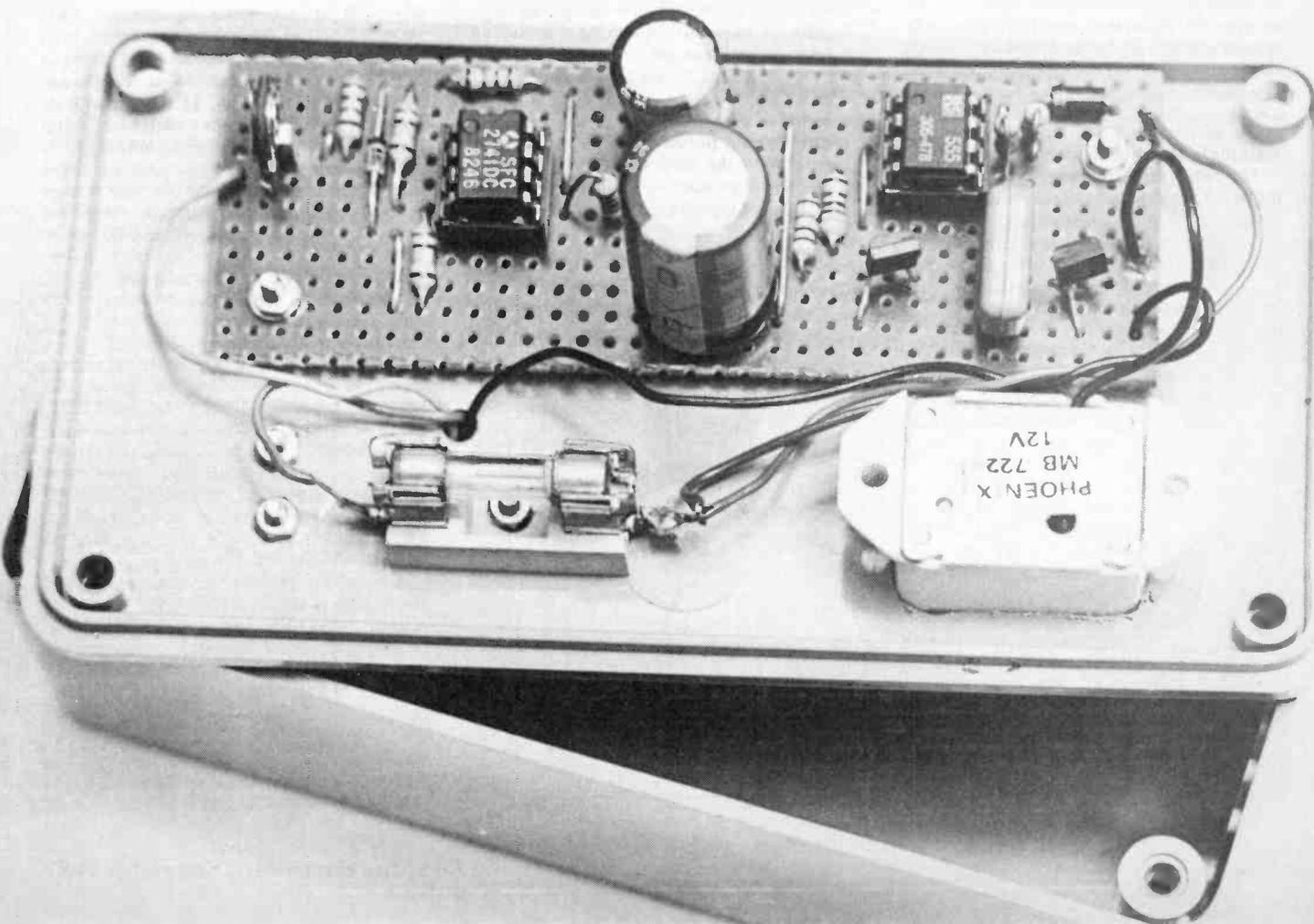Construction is based on a circuit panel made from a piece of 0.1 inch matrix stripboard size 11 strips by 34 holes. Refer to Fig. 3. Drill the two mounting holes and make all breaks and inter-strip links. Use a spot-face cutter or a small drill to make the



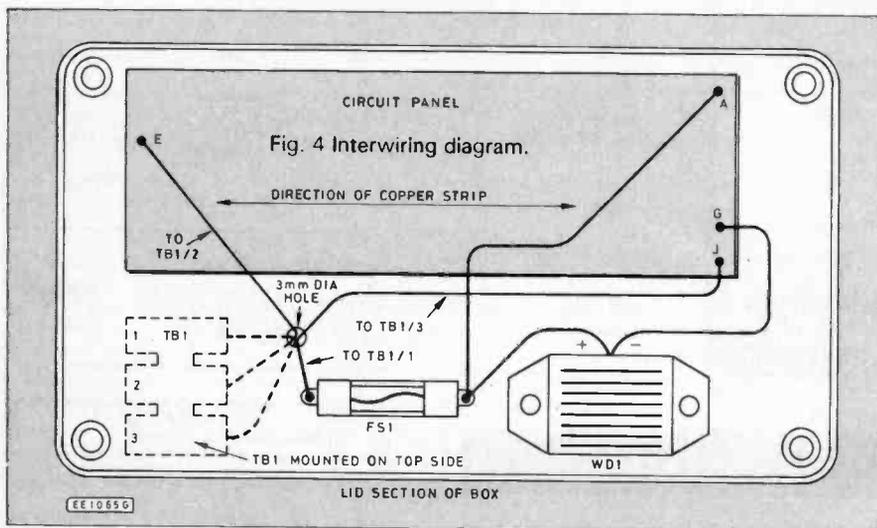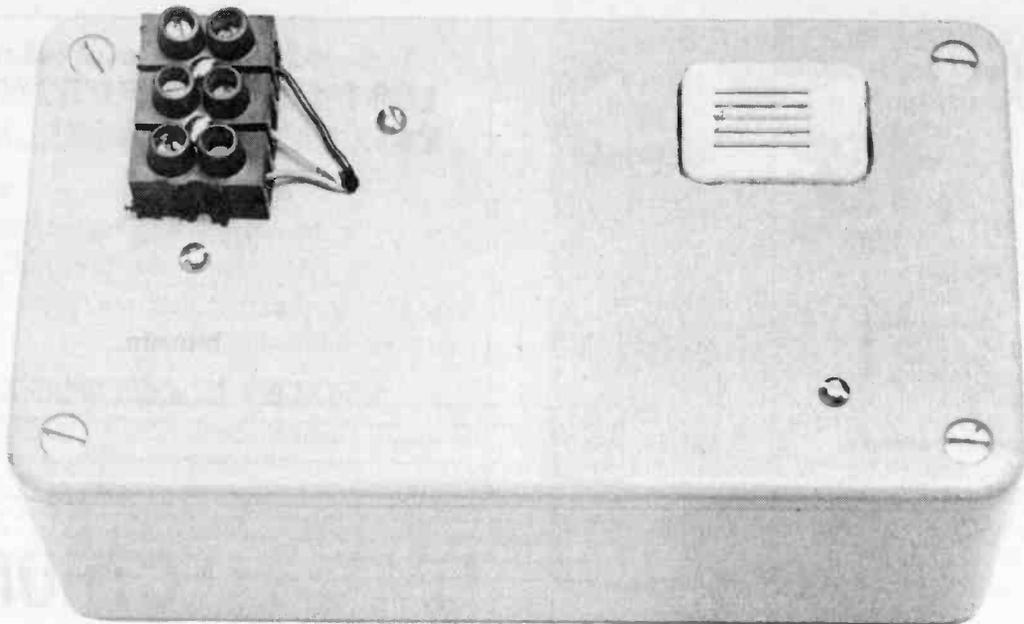

breaks and check that these are complete. Follow with the soldered on-board components. Note that C1, C3 and the diodes must be connected the correct way round. Solder

lengths of light-duty stranded connecting wire to strip E on the left-hand side and strips A and J on the right-hand side of the circuit panel.


Refer to Fig. 4 and mount WD1 (using a little glue around the rim), FS1 and TB1 on the lid of the case (see photograph). WD1 could be direct surface-mounted if desired. Drill a 3 mm diameter hole near TB1 for the wires passing through from inside. Complete all wiring and mount the circuit panel on the lid of the box using the holes drilled for the purpose. Drill a hole in the side of the case so that VR1 may be adjusted using a small screwdriver when the lid is in position. Leave VR1 adjusted to approximately mid-track position, insert the fuse and fit the lid checking for trapped wires.

SENSOR

The bead thermistor used for the sensor is delicate and needs good protection. Fig. 5 shows how this was achieved in the prototype. The sensor should be attached to a *sheltered* part of the engine where it will not be subject to the effect of cool moving air—make a small shield if necessary. Choose a part of the engine which becomes hot in operation and is clear of moving parts. Clean this part carefully and roughen the surface with carborundum paper. Treat the attachment surface of the sensor in a similar fashion. Bond the sensor in position using a thin film of quick-setting epoxy resin adhesive.

Use light-duty auto type wire for all connections—where it passes through any hole in metal use a rubber grommet. For a negative-earth car, connect the sensor wires to TB1/2 and TB1/3. Find a suitable fuse which is live only when the ignition is switched on and connect this to TB1/1. Make sure that the correct side has been used—when the fuse is removed the circuit should not work. Connect TB1/3 to an earth point (car chassis). For a positive-earth vehicle, make the sensor connections to TB1/2 and TB1/3. Connect the fuse to TB1/3 and TB1/1 to the earth point.

Adjust VR1 over a trial period so that the alarm *just* remains off with the engine at normal operating temperature. Clockwise rotation of the sliding contact increases the operating temperature and vice-versa. Once adjusted, the unit may be hidden behind the car dashboard. If the alarm tends to operate when the car is travelling slowly but not at higher speeds, this usually means that the sensor is badly sited and needs additional shielding from moving air. □

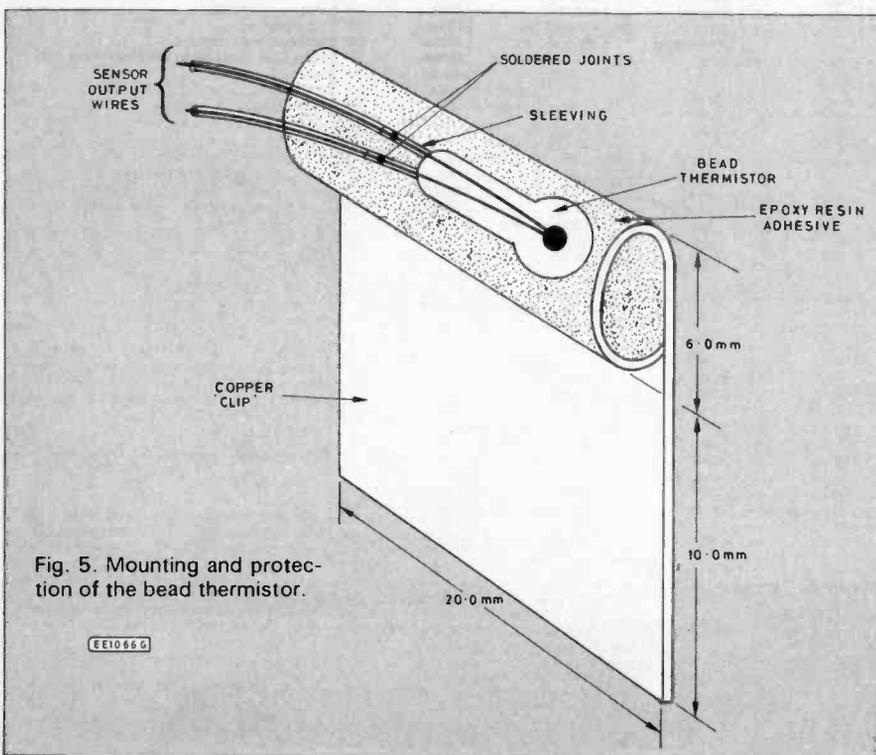

Beeb...Beeb...Beeb...Beeb...Beeb

... Simple Light pen ...

THERE are few aspects of the BBC Ports which have not been covered at least briefly in previous "BEEB Micro" articles, but one notable exception is the Light Pen input. This is actually a terminal on the analogue port rather than a separate input port, and it operates in conjunction with circuitry included in the machine's 6845 c.r.t. controller chip.

Light pens are perhaps less popular than they once were, having been to some extent eclipsed by Mice and other pointing devices. Despite this they still represent an interesting and practical approach to cursor control etc., and can be home constructed for a few pounds.

Scanning

The term "light pen" tends to give the impression that the device produces light, but this is actually the opposite of its function. A light pen is really just a simple light detector circuit, but in order to function properly it must have a high operating speed and a narrow angle of view.

Some light pens operate in a very simple manner, and can only indicate whether the pen is aimed at a light or dark area of a screen. Most can be used to indicate to a computer (with reasonable resolution) the point on the screen at which the pen is aimed. The BBC Light Pen input and internal circuit enables quite accurate pointing of this type.

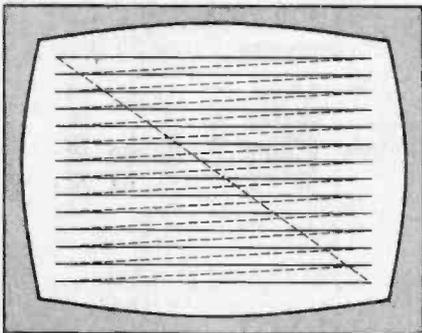


Fig. 1. Computer/television display is produced using this scanning system (dotted lines represent the flyback periods).

To act as an accurate pointing device a light pen relies on the scanning process used to produce the display on the television or monitor. This operates in the manner shown in Fig. 1, with the electron beam being scanned across the screen in a series of horizontal lines, starting at the top of the screen and working downwards.

The dotted lines represent the "flyback" periods, and during these the beam is moved much faster. The beam is normally switched off during the flyback periods as well.

The electron beam produces a spot of light at the point where it strikes the phosphor coating of the screen, but the spot is so fast to be perceived as such by the

human eye. Instead, the display appears to be a series of closely spaced lines across the screen (with a real display having hundreds of lines, and not just the dozen or so shown in Fig. 1). At normal viewing distances the lines are not apparent, but they can be seen quite clearly if you look at any television or monitor display.

Of course, to produce an image of some kind the intensity of the electron beam (and thus also the brightness of the spot of light) are modulated in the appropriate manner. With television displays and some computer displays a system of interlacing is used.

With this method only every other line is covered by the first scan, and then the remaining lines are covered by the next scan. Two frames (scans) are then needed to produce each complete picture, but there are fifty frames per second, giving the same picture rate of twenty five per second for both systems.

Whichever method of scanning is used, the timing signals are generated by circuits in the computer. The light pen must produce an output pulse as the spot of light passes in front of it, and from the time in each scan that this pulse occurs the circuits of the c.r.t. (cathode ray tube) controller can deduce the position of the pen. With some c.r.t. controllers the light pen position is read from two registers, with these giving X and Y co-ordinates.

The system used in the 6845 c.r.t. controller is a little less convenient, and although there are two light pen registers, these provide figures that must be combined to form one large value, rather than taken as X and Y values. The two most significant bits of the most significant byte are unused, giving a 14-bit number. The light pen value is at a minimum in the top left hand corner of the screen, and increases as the pen is moved to the right and down the screen.

In order to derive X and Y co-ordinate values it is first necessary to deduct the large offset value (i.e. value obtained with the pen in the top left hand corner of the screen). If values are then divided by the appropriate amount, the integer part of the result gives the Y co-ordinate, and the remainder is the X co-ordinate.

Light Pen Circuit

Light pen circuits can be very simple indeed, and can in fact consist of just a

single component (an integrated circuit having a photo-diode driving a Schmitt trigger). Suitable components for this ultra-simple approach tend to be relatively expensive and difficult to obtain, and the alternative approach used in the circuit of Fig. 2 has its merits.

The light pen proper is formed by the photo-transistor TR1 and the first of the inverting Schmitt triggers, IC1a. The circuit is very simple in operation, and normally the input of the trigger drifts to the high state. This gives a low output level from the circuit under quiescent conditions.

When photo-transistor TR1 detects the passing spot of light it changes from having the very low leakage level associated with silicon transistors, to a much higher leakage level of a few milliamps. This is sufficient to pull the input of the trigger low, so that its output switches to the high state.

It is this low to high transition that activates the light pen circuitry in the 6845 c.r.t. controller, and it is essential that the light pen provides positive output pulses. A high operating speed is obviously imperative if the pen is to accurately and consistently indicate the correct screen position, and this combination of a photo-transistor and a Schmitt trigger seems to be perfectly adequate in this respect.

With virtually any practical light pen application there is a need for the computer to have some means of determining when the pen has been positioned on the screen and a reading should be taken. Some light pens incorporate a micro-switch that is automatically operated when the pen is placed against the screen, and some have a built-in switch for manual operation. Neither of these methods are very easy to implement in a home constructed pen, and simply using the computer's keyboard for manual indication is a more practical method.

A more sophisticated alternative is to use some additional circuitry to provide a means of automatic indication. In this design the second Schmitt trigger (IC1b) acts as a buffer stage which drives a smoothing and rectifier network based on diodes D1 and D2.

When the pen is in position on the screen the rectifier network is fed with a 50Hz signal that produces a positive output signal from the smoothing circuit. This switches on transistor TR2 and pulls a digital input on the analogue port (PB0) to the low state. Automatic indication can therefore be ob-

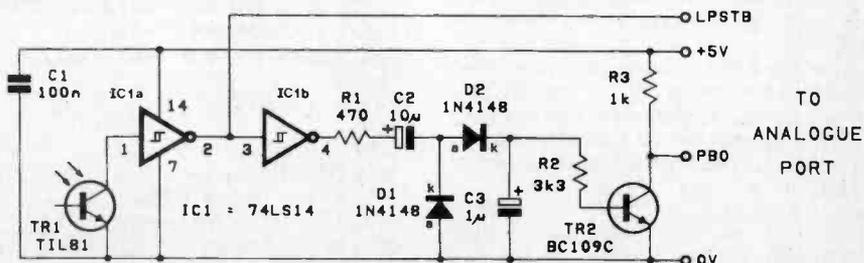


Fig. 2. The light pen circuit diagram.

tained by monitoring PBO, or manual indication via the keyboard can still be used if preferred.

Construction

The Light Pen can be built with transistor TR1 as a remote sensor, but in the interests of optimum speed and reliability it is better if the whole circuit is built into the "pen". There are few components in the unit and it can be made quite small without any real difficulty. In order to be usable it does need to be made quite small, otherwise there will be a tendency for the unit to severely obstruct your view of the screen.

Although a TIL81 photo-transistor is specified for the TR1 position, some other photo-transistors with built-in lenses will also work in the circuit (the BPX25 for example). However, the TIL81 is relatively cheap, readily available, and has the very narrow angle of view needed for good results in this application. Consequently, it is probably only worthwhile trying an alternative if you happen to have a likely component in the spares box.

IC1 should be the LS version of the 7414, and I would not recommend the use of any other version. Connections to the analogue port are made via a 15-way "D" plug, and connection details are shown in Fig. 3.

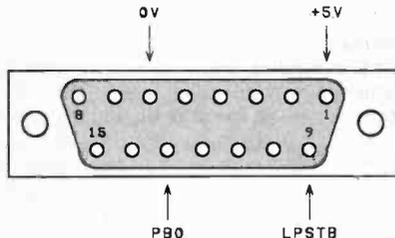


Fig. 3. Rear view of D-plug.

Software

The 6845 c.r.t. controller is at addresses &FE00 and &FE01. Data is written to and read from the device at the higher address, but this address is shared by some eighteen registers!

The required register is selected by writing the appropriate value (from 0 to 17) to the lower address. The light pen registers are registers 16 (high byte) and 17 (low byte).

To read the light pen it is a matter of first writing a value 16 to &FE00, then reading &FE01. Then 17 is written to &FE00 and another reading is taken from &FE01.

Multiplying the first reading by 256 and adding it to the second reading gives the basic light pen value. For optimum reliability the light pen registers should be read using an assembly language routine.

The offset to be removed from the raw light pen value depends on the mode in use, and also to a smaller extent on the characteristics of the light pen itself. The pen will detect the spot less than instantly, and a delay of only a few microseconds enables the spot to move on by a few cursor positions.

The list below gives approximate offset values, but it should only be regarded as a rough guide, and some fine tuning of the offsets will probably be needed in order to get the cursor and pen positions to accurately match:

Modes 0, 1 and 2	1548
Mode 3	2060
Modes 4 and 5	2826
Mode 6	3082
Mode 7	10254

The MOD and DIV functions provide convenient methods of producing the X and Y cursor positions.

PBO is one of the fire-button inputs of the Joystick Port, and as such can be read using the ADVAL function. An alternative is to read the appropriate input line directly, and this is bit 4 at address &FE40. ANDing the value read from this address will give an answer of 16 if the pen is not in position, or 0 if it is.

The accompanying listing will permit testing of the pen, and it simply places a cross at the pen position. It demonstrates the basic method of reading the pen and using the values, and could serve as a basis for your own programs.

A feature of every light pen I have ever encountered, including this one, is a lack of stability with the indicated position tending to jump around slightly. The standard approach to combatting this is to take several readings and then average them, or something of this nature.

It can also be useful to include a routine to remove any readings that are well removed from the average, and then to recalculate the average. With error correction of this type it is generally possible to obtain very stable results.

When using the pen (and writing software for it), bear in mind that it will only work if it is aimed at a fairly bright part of the screen. Also, it must be held close to the screen and held steady if stable results are to be obtained.

One final point is that scrolling of the screen changes the correct offset value, and the software should therefore be written to avoid any scrolling of the screen.

LIGHT PEN Listing

```

10 REM Lightpen Program
20 REM makes a + follow pen
30 MODE 1
40 COLOUR 0:COLOUR 130
50 DIM P% 25
60 [PENCODE
70 LDA £16
80 STA &FE00
90 LDX &FE01
100 LDA £17
110 STA &FE00
120 LDY &FE01
130 STX &70
140 STY &71
150 RTS:]
160 CLS
170 REPEAT
180 PROCpen(2)
190 PROCspot
200 FOR X=1 TO 100:NEXT
210 UNTIL FALSE
220
230
240 DEF PROCpen (scale_factor)
250 offset=1548
260 CALL PENCODE
270 penval=(?&70*256+?&71)-offset
280 ypen%=penval DIV 80
290 xpen%=(penval MOD 80)/scale_factor
300 ENDPROC
310
320
330 DEF PROCspot
340 PRINTTAB (X%,Y%); " ";
350 X%=xpen%:Y%=ypen%
360 IF ?&FE40 AND 16 ENDPROC
370 PRINTTAB (X%,Y%); "4";
380 ENDPROC

```

NATIONAL COMPONENT CLUB

All our packs are brand new, no manufacturers rejects, faulty or unmarked components. If you are anything less than delighted with your order please send it back for a full money refund within seven days of purchase.

ALL PACKS ONLY £1 EACH

- Pk1 300 ASSORTED RESISTORS Values from 1 ohm to 1M all full length leads.
- Pk2 50 WIRE WOUND RESISTORS All high wattage, lots of different values.
- Pk3 25 POTS AND PRESETS Sliders, multiturn, multigang, cermet, carbon etc.
- Pk4 70 ASSORTED CAPACITORS All different types values up to 4700uf, voltages to 250V.
- Pk5 20 LARGE ELECTROLYTICS Values like 4700uf, 2200uf at voltages up to 250V.
- Pk6 1 25,000uf Electrolytic capacitor.
- Pk7 20 ASSORTED IC'S TTL, Linear etc all brand new and fully marked.
- Pk8 60 ASSORTED DIODES Zeners, signals like the IN4148, rectifiers from the IN4000 series.
- Pk9 10 18 WAY IC SOCKETS Low profile.
- Pk10 1 PROJECT BOX 153mm x 83mm x 48mm complete with lid and screws.
- Pk11 1 4 DIGIT DISPLAY Seven segment, multiplexed with data sheets.
- Pk12 1 9V 105db SIREN 120mA electro mechanical.
- Pk13 10 ASSORTED SWITCHES micro-switches, highpower rockers etc.
- Pk14 5 MICRO-SWITCHES all different.
- Pk15 MYSTERY PACK Our best selling pack last month.
- Pk16 75 ASSORTED HARDWARE Rubber feet, cable ties, bolts, grommets, sleeving, PCB mounts etc.
- Pk17 5 FUSE HOLDERS 20mm new style complete with protective boots.
- Pk18 15 PP3 BATTERY CLIPS With 100mm red and black leads.

Please send your order together with cheque or postal order to:

DEPT. EE, WOODSIDE, DOWSETT LANE,
RAMSDEN HEATH, Nr BILLERICAY, ESSEX, CM11 1JL.

Please add 75p towards P & P.
All prices include VAT at 15%.

★ BAKER ★

GROUP P.A. DISCO
AMPLIFIERS post £4

150 watt Output, 4 Input Mixer pre-amp. Illustrated.....	£99
150 watt Output, 3 Input 3 Speaker Outputs.....	£89
150 + 150 watts Stereo, 300 watt Mono Slave Mossfast.....	£145
150 watt P.A. Vocal, 8 Inputs, High/Low Mixer Echo Socket.....	£149
60 watt Mobile 240V AC and 12V DC, 4-8-16 ohm + 100v line.....	£89
Compact P.A. amp 20 + 20 Stereo or 40 watts Mono.....	£59
30 watt Guitar/P.A. Amplifier, 2 inputs.....	£55
30 watt COMBI, 12in. Speaker, Treble, Base etc.....	£95
500 watt Heavy Duty Mono Slave Amplifier Fan coded.....	£275

FAMOUS LOUDSPEAKERS		FULLY GUARANTEED	
Make	Model	Size	Watts Ohms Price Post
GOODMANS	HIFAX	7 1/2 x 4 1/2 in	100 8 £38 £2
GOODMANS	HR WOOFER	8in.	60 8 £16 £1
BAKER	DISCO/GROUP	10in.	60 8/16 £22 £2
BAKER	MID-RANGE	10in.	100 8 £30 £2
BAKER	DISCO/GROUP	12in.	120 8/16 £35 £2
WEN	WOOFER	12in.	300 8 £55 £2
GOODMANS	DISCO/GROUP	2in.	320 8/15 £39 £2
BAKER	DISCO/GROUP	15in.	100 8/16 £44 £4
H + H	DISCO/GROUP	15in.	100 4/8/16 £54 £4
H + H	DISCO/GROUP	15in.	200 8/16 £89 £4
GOODMANS	HP/BASS	18in.	250 8 £92 £4
GOODMANS	HPD/BASS	18in.	230 8 £92 £4

COMPACT FULL RANGE SPEAKER SYSTEMS size 24 x 17 x 12in.
120 watts £100, 200 watts £130, 400 watts £180 each. Carr. £10.
MID-N-TOP 300 watts add on system complete £140 each. Carr £10.

DISCO CONSOLE Twin Decks, mixer pre amp £149. Carr £10.
Ditto Powered 120 watt £199; or Complete Disco £299. Carr £30.

MAINS TRANSFORMERS VALVE TYPE 240V PRIMARY		Price Post
250-0-250V 80mA, 6V 3A, 0-5, 6V 1A		£10 £2
350-0-350V 250mA, 6.3V 6A CT		£16 £2
220V 25mA, 6V 1 Amp, £3.00	220V 45mA, 6V 2 Amp	£4
STEP-UP STEP-DOWN 240V-120V 150W £9, 250W £12, 500W £15 £2		

LOW VOLTAGE MAINS TRANSFORMERS £5.50 each post paid
9V, 3A; 12V, 3A; 16V, 2A; 20V, 1A; 30V, 1A; 30V, 5A + 17-0-17V, 2A; 35V, 2A; 20-40-60V, 1A; 12-0-12V, 2A; 20-0-20V, 1A; 0-12-27V, 2A.

RECORD DECKS. P&P £2. Many others in stock. Phone for details.				
Make	Drive	Supply	Cartridge	Price
JAP Single	Belt	12V DC	Magnetic	£30
BSR Single	Belt	240V	Magnetic	£30
BSR Single	Rim	240V	Ceramic	£22
BSR Auto	Rim	240V	Ceramic	£18
Garrard Auto	Rim	240V	Ceramic	£24

PROJECT CASES. Black Vinyl Covered Steel Top. All Base
4 x 2 1/2 x 2 1/2 in. £3.00; 6 x 4 x 1 1/2 in. £4.00; 8 x 5 x 2 in. £4.50 p.p. £1;
11 x 6 x 3 in. £6.00; 11 1/2 x 6 x 5 in. £10.00; 15 x 8 x 4 in. £13.50 p.p. £2.
ALUMINIUM PANELS 18 x w.g. 12 x 12 in. £2.50; 14 x 9 in. £2.40; 6 x 4 in.
6 5/8; 12 x 8 in. £1.80; 10 x 7 in. £1.50; 8 x 6 in. £1.00; 14 x 3 in. £1;
12 x 5 in. £1.15; 16 x 10 in. £2.70; 16 x 6 in. £1.80 p.p. 6 5/8 each.
ALUMINIUM BOXES. MANY OTHER SIZES IN STOCK
4 x 2 1/2 x 2 in. £1.35; 3 x 2 x 1 in. £1.15; 6 x 4 x 2 in. £2.00; 8 x 6 x 3 in. £3.40;
12 x 5 x 3 in. £4.00; 6 x 4 x 3 in. £2.50; 10 x 7 x 3 in. £4.00 p.p. £1.

HIGH VOLTAGE ELECTROLYTICS Many others in stock			
20/500V.....	£1	220/400V.....	£2
32/350V.....	50p	8x8/450V.....	£1
47/350V.....	£1	20+20/350V.....	75p

AIR SPACED TWIN GANGS 365 + 365 + 25 + 25p £2.00.
REVERSE VERNIER cord drive 90p. Spindle Extender £1.50.
VERNIER DIALS, 0-100, 36mm, £3.00, 50mm £3.50.

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 01-684 1665
Post 65p Minimum. Callers Welcome

ACCESS
VISA

List. Large S.A.E. Delivery 7 days Closed Wednesday

BOOK SERVICE

The books listed below have been selected as being of special interest to our readers, they are supplied from our editorial address direct to your door.

DATA AND REFERENCE

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.
Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias—tedious and higher mathematics have been avoided where possible and many tables have been included.
The book is divided into six basic sections: Units and Constants, Direct-current Circuits, Passive Components, Alternating-current Circuits, Networks and Theorems, Measurements.
256 pages **Order Code BP53 £2.95**

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST

G. T. Rubarow, T.Eng (C.E.I.), Assoc.I.E.R.E.
The object of this book is to supply the hobbyist with a background knowledge tailored to meet his or her specific requirements and the author has brought together the relevant material and presented it in a readable manner with minimum recourse to mathematics.
128 pages **Order Code 228 £2.50**

MICROPROCESSING SYSTEMS AND CIRCUITS

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.
A truly comprehensive guide to the elements of micro-processing systems which really starts at the beginning. Teaches the reader the essential fundamentals that are so important for a sound understanding of the subject.
256 pages **Order Code BP77 £2.95**

COMMUNICATION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.
A look at the electronic fundamentals over the whole of the communication scene. This book aims to teach the important elements of each branch of the subject in a style as interesting and practical as possible. While not getting involved in the more complicated theory and mathematics, most of the modern transmission system techniques are examined including line, microwave, submarine, satellite and digital multiplex systems, radio and telegraphy. To assist in understanding these more thoroughly, chapters on signal processing, the electromagnetic wave, networks and transmissions assessment are included, finally a short chapter on optical transmission.
256 pages **Order Code BP89 £2.95**

AUDIO

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.
Analysis of the sound wave and an explanation of acoustical quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapter on audio systems—amplifiers, oscillators, disc and magnetic recording and electronic music.
320 pages **Order Code BP111 £3.50**

HOW TO IDENTIFY UNMARKED ICs

K. H. Recorr
Shows the reader how, with just a test-meter, to go about recording the particular signature of an unmarked i.c. which should enable the i.c. to then be identified with reference to manufacturers' or other data. An i.c. signature is a specially plotted chart produced by measuring the resistances between all terminal pairs of an i.c.
Chart **Order code BP101 £0.95**

RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

B. B. Babani
Although this chart was first published in 1971 it provides basic information on many colour codes in use throughout the world, for most radio and electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers, etc. It is particularly useful for finding the values of old components.
Chart **Order code BP7 £0.95**

CHART OF RADIO, ELECTRONIC, SEMICONDUCTOR AND LOGIC SYMBOLS

M. H. Banani, B.Sc.(Eng.)
Illustrates the common, and many of the not-so-common, radio, electronic, semiconductor and logic symbols that are used in books, magazines and instruction manuals, etc., in most countries throughout the world.
Chart **Order Code BP27 £0.95**

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

A. Michaels
Helps the reader to find possible substitutes for a popular selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.
320 pages **Order code BP85 £2.95**

TRANSISTOR RADIO FAULT-FINDING CHART

C. E. Miller
Used properly, should enable the reader to trace most common faults reasonably quickly. Across the top of the chart will be found four rectangles containing brief description of these faults, viz—sound weak but undistorted, set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.
Chart **Order code BP70 £0.95**

DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS

A. Michaels
Shows equivalents and pin connections of a popular selection of European, American and Japanese digital i.c.s. Also includes details of packaging, families, functions, manufacturer and country of origin.
256 pages **Order code BP140 £4.95**

LINEAR IC EQUIVALENTS AND PIN CONNECTIONS

A. Michaels
Shows equivalents and pin connections of a popular selection of European, American and Japanese linear i.c.s. Also includes details of functions, manufacturer and country of origin.
320 pages **Order code BP141 £4.95**

INTERNATIONAL DIODE EQUIVALENTS GUIDE

A. Michaels
Designed to help the user in finding possible substitutes for a large selection of the many different types of diodes that are available. Besides simple rectifier diodes, also included are Zener diodes, i.e.d.s, diacs, triacs, thyristors, OCIs, photo and display diodes.
144 pages **Order code BP108 £2.25**

NEWNES ELECTRONICS POCKET BOOK

E. A. Parr
Newnes Electronics Pocket Book has been in print for over twenty years and has covered the development of electronics from valve to semiconductor technology and from transistors to LSI integrated circuits and micro-processors. To keep up to date with the rapidly changing world of electronics, continuous revision has been necessary. This new Fifth Edition takes account of recent changes and includes material suggested by readers of previous editions. New descriptions of op.amp. applications and the design of digital circuits have been added, along with a totally new chapter on computing, plus other revisions throughout.
315 pages (hard cover) **Order Code NE02 £8.95**

CIRCUITS AND DESIGN

ELECTRONICS SIMPLIFIED—CRYSTAL SET CONSTRUCTION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.
Especially written for those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day one can read intelligently and handle simple tools.
80 pages **Order Code BP92 £1.75**

50 CIRCUITS USING GERMANIUM SILICON AND ZENER DIODES

R. N. Soar
Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most simple and inexpensive of components—the diode. Includes the use of germanium and silicon signal diodes, silicon rectifier diodes and Zener diodes, etc.
64 pages **Order Code BP36 £1.50**

50 SIMPLE LED CIRCUITS

R. N. Soar
Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components—the light-emitting diode (LED). Also includes circuits for the 707 common anode display.
64 pages **Order Code BP42 £1.95**

COIL DESIGN AND CONSTRUCTION MANUAL

B. B. Babani
A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now rather old, with the exception of torroids and pulse transformers little has changed in coil design since it was written.
96 pages **Order Code 160 £2.50**

MICRO INTERFACING CIRCUITS—BOOK 1

MICRO INTERFACING CIRCUITS—BOOK 2
R. A. Penfold
Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but p.c.b. layouts and other detailed constructional information are not included.
Book 1 is mainly concerned with getting signals in and out of the computer; Book 2 deals primarily with circuits for practical applications.
Book 1 112 pages **Order code BP130 £2.25**
Book 2 112 pages **Order code BP131 £2.25**

A MICROPROCESSOR PRIMER

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
Starts by designing a small computer which, because of its simplicity and logical structure, enables the language to be easily learnt and understood. The shortcomings are then discussed and the reader is shown how these can be overcome by changes and additions to the instruction set. In this way, such ideas as relative addressing, index registers, etc., are developed.
96 pages **Order code BP72 £1.75**

A PRACTICAL INTRODUCTION TO MICROPROCESSORS

R. A. Penfold
Provides an introduction which includes a very simple microprocessor circuit which can be constructed so that the reader can experiment and gain practical experience.
96 pages **Order code BP123 £1.95**

HOW TO USE OP-AMPS

E. A. Parr
This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.
160 pages **Order code BP88 £2.95**

PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 1

PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 2
R. A. Penfold
These books are designed to aid electronic enthusiasts who like to experiment with circuits and produce their own projects, rather than simply following published project designs.

BOOK 1 contains: Oscillators—sinewave, triangular, squarewave, sawtooth, and pulse waveform generators operating at audio frequencies. Timers—simple monostable circuits using i.c.s. the 555 and 7555 devices, etc. Miscellaneous—noise generators, rectifiers, comparators and triggers, etc.

BOOK 2 contains: Amplifiers—low level discrete and op-amp circuits, voltage and buffer amplifiers including d.c. types. Also low-noise audio and voltage controlled amplifiers. Filters—high-pass, low-pass, 6, 12, and 24dB per octave types. Miscellaneous—i.c. power amplifiers, mixers, voltage and current regulators, etc.

BOOK 1 128 pages **Order code BP117 £1.95**
BOOK 2 112 pages **Order code BP118 £1.95**

HOW TO DESIGN ELECTRONIC PROJECTS

R. A. Penfold
The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics. Hints on designing circuit blocks to meet your special requirements are also provided.
128 pages **Order code BP127 £2.25**

POPULAR ELECTRONIC CIRCUITS

—BOOK 1
POPULAR ELECTRONIC CIRCUITS
—BOOK 2
R. A. Penfold
Each book provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed construction information. Any special setting-up procedures are described.
BOOK 1 Temporarily out of print
BOOK 2 160 pages **Order code BP98 £2.25**

GETTING THE MOST FROM YOUR PRINTER

J. W. Penfold
Details how to use all the features provided on most dot-matrix printers from programs and popular word processor packages like Wordwise, Visawrite and Quill, etc. Shows exactly what must be typed in to achieve a given effect.
96 pages **Order Code BP181 £2.95**

A Z80 WORKSHOP MANUAL

E. A. Parr, B.Sc., C.Eng., M.I.E.E.
This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z80 based computer.
192 pages **Order Code BP112 £3.50**

AN INTRODUCTION TO 68000 ASSEMBLY LANGUAGE

R. A. & J. W. Penfold
Obtain a vast increase in running speed by writing programs for 68000 based micros such as the Commodore Amiga, Atari ST range or Apple Macintosh range etc., in assembly language. It is not as difficult as one might think and this book covers the fundamentals.
172 pages **Order Code BP184 £2.95**

THE ART OF PROGRAMMING THE ZX SPECTRUM

M. James, B.Sc., M.B.C.S.
It is one thing to have learnt how to use all the Spectrum's commands and functions, but a very different one to be able to combine them into programs that do exactly what you want them to. This is just what this book is all about—teaching you the art of effective programming with your Spectrum.
144 pages **Order code BP119 £2.50**

AN INTRODUCTION TO PROGRAMMING THE COMMODORE 16 & PLUS 4

R. A. Penfold
Helps you to learn to use and program these two Commodore machines with the minimum of difficulty by expanding and complementing the information supplied in the manufacturer's own manuals.
128 pages **Order code BP158 £2.50**

AN INTRODUCTION TO PROGRAMMING THE BBC MODEL B MICRO

R. A. & J. W. Penfold
Written for readers wanting to learn more about programming and how to make best use of the incredibly powerful model B's versatile features. Most aspects of the BBC micro are covered, the omissions being where little could usefully be added to the information provided by the manufacturer's own manual.
144 pages **Order code BP139 £1.95**

AN INTRODUCTION TO PROGRAMMING THE ACORN ELECTRON

R. A. & J. W. Penfold
Designed to help the reader learn more about programming and to make best use of the Electron's many features. Adds considerably to the information already supplied in the manufacturer's own instruction manual.
144 pages **Order code BP142 £1.95**

AN INTRODUCTION TO PROGRAMMING THE ATARI 600/800 XL

R. A. & J. W. Penfold
Especially written to supplement the manufacturer's own handbook. The information supplied will help the reader to master BASIC programming and to make best use of the Atari's many powerful features.
128 pages **Order code BP143 £1.95**

AN INTRODUCTION TO PROGRAMMING THE AMSTRAD CPC 464 AND 664

R. A. & J. W. Penfold
The Amstrad CPC 464 or 664 running with Locomotive BASIC makes an extremely potent and versatile machine and this book is designed to help the reader get the most from this powerful combination. Written to complement rather than duplicate the information already given in the manufacturer's own manual. Also applicable to the CPC 612B.
144 pages **Order Code BP153 £2.50**

AN INTRODUCTION TO PROGRAMMING THE SINCLAIR QL

R. A. & J. W. Penfold
Helps the reader to make best use of the fantastic Sinclair QL's almost unlimited range of features. Designed to complement the manufacturer's handbook.
112 pages **Order code BP150 £1.95**

AN INTRODUCTION TO Z80 MACHINE CODE

R. A. & J. W. Penfold
Takes the reader through the basics of microprocessors and machine code programming with no previous knowledge of these being assumed. The Z80 is used in many popular home computers and simple programming examples are given for Z80-based machines including the Sinclair ZX-81 and Spectrum, Memotech and the Amstrad CPC 464. Also applicable to the Amstrad CPC 664 and 612B.
144 pages **Order code BP152 £2.75**

AN INTRODUCTION TO 6502 MACHINE CODE

R. A. & J. W. Penfold
No previous knowledge of microprocessors or machine code is assumed. Topics covered are: assembly language and assemblers, the register set and memory, binary and hexadecimal numbering systems, addressing modes and the instruction set, and also mixing machine code with BASIC. Some simple programming examples are given for 6502-based home computers like the VIC-20, ORIC-1/Atmos, Electron, BCC and also the Commodore 64.
112 pages **Order code BP147 £2.50**

THE PRE-BASIC BOOK

F. A. Wilson, C.G.I.A., C.ENG., F.I.E.E., F.I.E.R.E., F.B.I.M.
Another book on BASIC but with a difference. This one does not skip through the whole of the subject and thereby leave many would-be programmers floundering but instead concentrates on introducing the technique by looking in depth at the most frequently used and more easily understood computer instructions. For all new and potential micro users.
192 pages **Order code BP146 £2.95**

HOW TO GET YOUR COMPUTER PROGRAMS RUNNING

J. W. Penfold
Have you ever written your own programs only to find that they did not work! Help is now at hand with this book which shows you how to go about looking for your errors, and helps you to avoid the common bugs and pitfalls of program writing. Applicable to all dialects of the BASIC language.
144 pages **Order code BP189 £2.50**

AN INTRODUCTION TO COMPUTER COMMUNICATIONS

R. A. Penfold
Provides details of the various types of modem and their suitability for specific applications, plus details of connecting various computers to modems, and modems to the telephone system. Also information on common networking systems and RTTY.
96 pages **Order code BP177 £2.95**

AN INTRODUCTION TO COMPUTER PERIPHERALS

J. W. Penfold
Covers such items as monitors, printers, disc drives, cassette recorders, modems, etc., explaining what they are, how to use them and the various types and standards. Helps you to make sure that the peripherals you buy will work with your computer.
80 pages **Order code BP170 £2.50**

COMPUTER TERMINOLOGY EXPLAINED

I. D. Poole
Explains a wide range of terms that form the computer jargon used by enthusiasts. Includes a reference guide to the more commonly used BASIC commands.
96 pages **Order code BP148 £1.95**

THE PRE-COMPUTER BOOK

F. A. Wilson
Aimed at the absolute beginner with no knowledge of computing. An entirely non-technical discussion of computer bits and pieces and programming.
96 pages **Order code BP115 £1.95**
prehensive specifications of over 1400 devices.

NEWNES COMPUTER ENGINEER'S

POCKETBOOK
Michael Tooley
An invaluable compendium of facts, figures, circuits and data, indispensable to the designer, student, service engineer and all those interested in computer and microcomputer systems. It will appeal equally to the hardware or software specialist and to the new band of "software engineers". This first edition covers a vast range of subjects at a practical level, with the necessary explanatory text. The data is presented in a succinct and rapidly accessible form so that the book can become part of an everyday toolkit.
205 pages (hard cover) **Order code NE01 £8.95**

PROJECT CONSTRUCTION

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold
We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.
96 pages **Order code BP110 £1.95**

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold
Deals with the simple methods of copying printed circuit

board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.
80 pages **Order code BP121 £1.95**

BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold
Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also includes examples in the form of simple projects.
112 pages **Order code No. 227 £1.95**

RADIO

AN INTRODUCTION TO RADIO DXING

R. A. Penfold
Anyone can switch on a short wave receiver and play with the controls until they pick up something, but to find a particular station, country or type of broadcast and to receive it as clearly as possible requires a little more skill and knowledge. The object of this book is to help the reader to do just that, which in essence is the fascinating hobby of radio DXing.
112 pages **Order code BP91 £1.95**

INTERNATIONAL RADIO STATIONS GUIDE

Completely revised and updated, this book is an invaluable aid in helping all those who have a radio receiver to obtain the maximum entertainment value and enjoyment from their sets.
Clearly shown are the station site, country, frequency and/or wavelength, as well as the effective radiation power of the transmitter.
128 pages **Order code BP155 £2.95**

NEW RELEASE

TRANSISTOR SELECTOR GUIDE

Prepared using the latest computerised techniques, from a vast database of electronic component specifications, this unique guide offers a range of selection tables compiled so as to be of maximum use to all electronics engineers, designers and hobbyists.
Section 1: Covers component markings, codings and standards, as well as explaining the symbols used and how the tables are arranged.
Section 2: Tabulates in alpha-numeric sequence the comprehensive specifications of over 1400 devices.
Section 3: Tabulates the devices in a similar fashion to the previous section but this time they are arranged by case type.
Section 4: Considers particular limits to the electrical parameters when compiling the tables and it is subdivided as follows: Darlingtons transistors; devices that can handle voltages upwards of 300V; devices that can handle currents upwards of 5A; devices that can handle powers upwards of 5W; radio frequency devices that operate upwards of 30MHz; FETs.
Section 5: Illustrates package outlines and leadouts.
Section 6: Consists of a surface mounting device markings conversion list.
192 pages **Order code BP234 £4.95**

EE BOOK SERVICE

TO ORDER

Please check the latest issue for price and availability.

Add 50p per order postage (overseas readers add £1, surface mail postage) and send a PO, cheque or international money order (£ sterling only) made payable to **Everyday Electronics** (quoting the order code and quantities required) to **EE BOOK SERVICE, 6 CHURCH STREET, WIMBORNE, DORSET. BH21 1JH.**

Although books are normally sent within seven days of receipt of your order please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.



PCB SERVICE

Printed circuit boards for certain constructional projects are now available from the PCB Service, see list. These are fabricated in glass-fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to: The PCB Service, Everyday Electronics Editorial Offices, 6 Church Street, Wimborne, Dorset BH21 1JH. Cheques should be crossed and made payable to Everyday Electronics. (Payment in £ sterling only.)

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps. Do not send any other correspondence with your order.

Readers are advised to check with prices appearing in the current issue before ordering.

NOTE: Please allow 28 days for delivery. We can only supply boards listed in the latest issue. Boards can only be supplied by mail order and on a payment with order basis.

PROJECT TITLE	Order Code	Cost
— JULY '83 —		
User Port Input/Output <i>M.I.T. Part 1</i>	8307-01	£4.82
User Port Control <i>M.I.T. Part 1</i>	8307-02	£5.17
— AUGUST '83 —		
Storage 'Scope Interface, BBC Micro	8308-01	£3.20
Car Intruder Alarm	8308-02	£5.15
High Power Interface <i>M.I.T. Part 2</i>	8308-03	£5.08
Pedestrian Crossing Simulation <i>M.I.T. Pt 2</i>	8308-04	£3.56
— SEPTEMBER '83 —		
High Speed A-to-D Converter <i>M.I.T. Pt 3</i>	8309-01	£4.53
Signal Conditioning Amplifier <i>M.I.T. Pt 3</i>	8309-02	£4.48
Stylus Organ	8309-03	£6.84
— OCTOBER '83 —		
D-to-A Converter <i>M.I.T. Part 4</i>	8310-01	£5.77
High Power DAC Driver <i>M.I.T. Part 4</i>	8310-02	£5.13
— NOVEMBER '83 —		
TTL/Power Interface for Stepper Motor <i>M.I.T. Part 5</i>	8311-01	£5.46
Stepper Motor Manual Controller <i>M.I.T. Part 5</i>	8311-02	£5.70
Speech Synthesiser for BBC Micro	8311-04	£3.93
— DECEMBER '83 —		
4-Channel High Speed ADC (Analogue) <i>M.I.T. Part 6</i>	8312-01	£5.72
4-Channel High Speed ADC (Digital) <i>M.I.T. Part 6</i>	8312-02	£5.29
Environmental Data Recorder	8312-04	£7.24
Continuity Tester	8312-08	£3.41
— JANUARY '84 —		
Biological Amplifier <i>M.I.T. Part 7</i>	8401-02	£6.27
Temp. Measure & Control for ZX Compr Analogue Thermometer Unit	8401-03	£2.40
Analogue-to-Digital Unit	8401-04	£2.56
Games Scoreboard	8401-06/07	£9.60
— FEBRUARY '84 —		
Oric Port Board <i>M.I.T. Part 8</i>	8402-02	£9.56
Negative Ion Generator	8402-03*	£8.95
Temp. Measure & Control for ZX Compr Relay Driver	8402-04	£3.52
— MARCH '84 —		
Latched Output Port <i>M.I.T. Part 9</i>	8403-01	£5.30
Buffered Input Port <i>M.I.T. Part 9</i>	8403-02	£4.80
VIC-20 Extension Port Con. <i>M.I.T. Part 9</i>	8403-03	£4.42
CBM 64 Extension Port Con. <i>M.I.T. Part 9</i>	8403-04	£4.71
Digital Multimeter Add-On for BBC Micro	8403-05	£4.63
— APRIL '84 —		
Multipurpose Interface for Computers	8404-01	£5.72
Data Acquisition "Input" <i>M.I.T. Part 10</i>	8404-02	£5.20
Data Acquisition "Output" <i>M.I.T. Part 10</i>	8404-03	£5.20
Data Acquisition "PSU" <i>M.I.T. Part 10</i>	8404-04	£3.09
A.F. Sweep Generator	8404-06	£3.55
Quasi Stereo Adaptor	8404-07	£3.56

Simple Loop Burglar Alarm	8405-01	£3.07
Computer Controlled Buggy <i>M.I.T. Part 11</i>	8405-02	£5.17
Interface/Motor Drive	8405-03	£3.20
Collision Sensing — MAY '84 —	8405-04	£4.93
Power Supply		
— JUNE '84 —		
Infra-Red Alarm System	8406-01	£2.55
Spectrum Bench PSU	8406-02	£3.99
Speech Synthesiser <i>M.I.T. Part 12</i>	8406-03	£4.85
Train Wait	8406-04	£3.42
— JULY '84 —		
Ultrasonic Alarm System	8407-01	£4.72
Electronic Code Lock	8407-03	£2.70
Main Board	8407-04	£3.24
Keyboard		
— AUGUST '84 —		
Microwave Alarm System	8408-01	£4.36
Temperature Interface—BBC Micro	8408-02	£2.40
— SEPTEMBER '84 —		
Op-Amp Power Supply	8409-01	£3.45
— OCT '84 —		
Micro Memory Synthesiser	8410-01*	£8.20
Drill Speed Controller	8410-04	£2.40
— NOVEMBER '84 —		
BBC Audio Storage Scope Interface	8411-01	£2.90
Proximity Alarm	8411-02	£2.65
— DEC '84 —		
TV Aerial Pre-Amp	8412-01*	£2.40
Digital Multimeter	8412-02/03*	£5.20
Mini Workshop Power Supply	8412-04	£2.78
— JAN '85 —		
Power Lighting Interface	8501-01	£8.23
Games Timer	8501-02	£2.40
Spectrum Amplifier	8501-03	£2.40
— FEB '85 —		
Solid State Reverb	8502-01	£3.68
Computerised Train Controller	8502-02	£3.38
— MARCH '85 —		
Model Railway Points Controller	8503-01	£2.78
— APRIL '85 —		
Insulation Tester	8504-02	£2.53
Fibrealarm	8504-03	£3.89
— MAY '85 —		
Auto Phase	8505-01	£3.02
Amstrad CPC464 Amplifier	8505-02	£2.56
Mains Unit	8505-03	£2.56
Micro Unit	8505-04	£2.67
Voltage Probe		
— JUNE '85 —		
Graphic Equaliser	8506-01	£3.21
Computerised Shutter Timer	8506-02	£2.40
Mono-Bi-Astables (Experimenters Test Bed)	8506-03	£2.45
Across The River	8506-04	£2.63
— JULY '85 —		
Amstrad User Port	8507-01	£3.17
Nascom Printer Handshake	8507-02	£2.40
— AUGUST '85 —		
Electronic Building Blocks—1 to 4†	8508-01	£2.98
Tremolo/Vibrato	8508-02	£4.03
Stepper Motor Interface	8508-03	£2.40
Drill Control Unit	8508-04	£2.90
— SEPTEMBER '85 —		
RIAA Preamp Input Selector	8509-01	£2.40
Transducers Resistance Thermometer	8509-03	£2.64
Transducers Semiconductor Temp. Sensor	8509-04	£2.72
— OCT '85 —		
Transducers Strain Gauge	501	£2.87
Soldering Iron Power Controller	504	£2.40
— NOV '85 —		
Transducers—	505	£3.93
Magnetic Flux Density Amplifier	506	£2.68
Hallowe'en Projects (single board price)		
— DEC '85 —		
Electronic Building Blocks — 5 to 8†	508	£3.07
Opto Intensity Transducer	509	£2.70
Digital Capacitance Meter	512	£5.22
— JAN '86 —		
Mains Delay	503	£2.40
Musical Doorbell	507	£2.91
Tachometer—Transducers	513	£2.52
— FEB '86 —		
Touch Controller	510	£2.65
Function Generator	514	£3.10
Function Generator PSU Board	515	£2.40
pH Transducer	516	£2.75

*Complete set of boards.

M.I.T.—Microcomputer Interfacing Techniques, 12-Part Series.

†Four separate circuits.

PROJECT TITLE	Order Code	Cost
Mains Tester & Fuse Finder	517	£2.40
BBC Midi Interface	518	£3.26
Stereo Hi Fi Preamp	519	£5.70
Interval Timer	520	£2.40
Stereo Reverb	521	£2.89
PA Amplifier	511	£2.67
Mini Strobe	522	£2.40
Auto Firing Joystick Adaptor	523	£2.73
Watchdog	524	£2.81
Percussion Synthesiser	525	£5.65
Personal Radio	526	£2.40
Tilt Alarm	527	£2.40
Electronic Scarecrow	528	£2.40
VOX Box Amplifier	529	£2.40
Headphone Mixer	530	£4.56
Solar Heating Controller	533	£3.32
Car Timer	538	£2.40
Freezer Failure Alarm	534	£2.40
Infra Red Beam Alarm (Trans)	536	£3.32
Infra Red Beam Alarm (Rec)	537	£3.32
Scratch Blanker	539	£5.43
10W Audio Amp (Power Amp)	543	£2.58
(Pre-Amp) £4.78 Pair	544	£3.18
Light Rider—Lapel Badge	540 & 541	£2.70
—Disco Lights	542	£4.55
—Chaser Light	546	£3.23
Modem Tone Decoder	547	£2.76
200MHz Digital Frequency Meter	548	£4.12
Dual Reading Thermometer	549	£5.87
Automatic Car Alarm	550	£2.40
BBC 16K Sideways RAM	551	£2.40
(Software Cassette)	551S	£4.95
Random Light Unit	552	£4.70
Car Voltage Monitor	553	£2.40
Mini Amp.	554 & 555	£4.55
Video Guard	556	£3.05
Spectrum I/O	557	£3.78
Spectrum Speech Synthesiser	558	£3.88
Computer Buffer/Interface	560	£2.66
Infra Red Alarm: Sensor head	561	£3.35
PSU/Relay Driver	562	£3.60
Alarm Thermometer	559	£2.40
Experimental Speech Recognition	563	£3.80
Bulb Life Extender	564	£2.40
Fridge Alarm	565	£2.40
EE Equaliser—Ioniser	566	£3.28
Mini Disco Light	567	£2.40
Visual Guitar/Instrument Tuner	568	£3.18
Fermostat	569	£2.67
EE Buccaneer	570	£3.28
Metal Detector	571	£3.80
Monomix	571	£3.80
Super Sound Adaptor, Main Board	572	£3.37
PSU Board	573	£2.65
Simple Shortwave Radio, Tuner	575	£2.51
Amplifier	576	£2.40
Noise Gate	577	£4.41
Burst Fire Mains Controller	578	£3.31
Electronic Analogue/Digital Multimeter	579	£6.40

TEACH-IN-SOFTWARE

To complement each published part of the Teach-In series (Oct. '85 to June '86), we have produced an accompanying computer program. The Teach-In Software is available for both the BBC Microcomputer (Model B) and the Sinclair Spectrum (48k) or Spectrum-Plus. The programs are designed to reinforce and consolidate important concepts and principles introduced in the series. The software also allows readers to monitor their progress by means of a series of multi-choice tests, with scores at the end.

Tape 1 (Teach-In parts 1, 2 and 3), Tape 2 (parts 3, 4 and 5) and Tape 3 (parts 6, 7, 8 and 9) are available for £4.95 each (inclusive of VAT and postage) from Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. **IMPORTANT** State BBC or Spectrum; add 50 pence for overseas orders; allow 28 days for delivery.

PLEASE TAKE NOTE

Warning to readers: From next month we will be dropping a number of older p.c.b.s from our service, these will mainly be those over two years old—if you want one or likely to want one order NOW! The price of some other p.c.b.s will also be increased.

EE PRINTED CIRCUIT BOARD SERVICE

Please send me the following p.c.b.s.

Make cheques/PO payable to: **Everyday Electronics**
(Payment in £ sterling only)

BLOCK CAPITALS PLEASE

Order Code	Quantity	Price
.....
.....
.....

I enclose cheque/PO for £

Name

Address

Please allow 28 days for delivery

NEWSAGENT ORDER FORM

Please reserve/deliver a copy of **Everyday Electronics** for me each month.

Signed

Name & Address

(BLOCK CAPITALS PLEASE)

Everyday Electronics is published on the third Friday of each month and distributed by Seymour.

Make sure of your copy of EE each month—cut out this form, fill it in and hand it to your newsagent.

SUBSCRIPTIONS

Sell-out disappointment can upset any reader! So why not take out a year's subscription and make sure of every issue, by post, straight from the Publisher? Complete the order form below and post to:

EVERYDAY ELECTRONICS, Subscription Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. Tel. 0202 881749.

Annual subscription rates:

UK £14. Overseas £17 (£ sterling only)
Overseas air mail £33 (£ sterling only)

EVERYDAY ELECTRONICS SUBSCRIPTION ORDER FORM

Annual subscription rates:
UK £14. Overseas £17 (surface mail) £33 (air mail)

To: Everyday Electronics,
Subscription Dept., 6 Church Street, Wimborne, Dorset BH21 1JH.

Name

Address

I enclose payment of £..... (cheque/PO in £ sterling only payable to Everyday Electronics)

Subscriptions can only start with the next available issue. For back numbers see the Editorial page

EVERYDAY ELECTRONICS

Reach effectively and economically today's enthusiasts anxious to know of your products and services through our semi-display and classified pages. The prepaid rate for semi-display spaces is £8.00 per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 30 pence per word (minimum 12 words), box number 60p extra. All cheques, postal orders, etc., to be made payable to Everyday Electronics VAT must be added. Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: 0202 881749.

Electronic Components

RESISTORS (metal film, full length leads): mixed (1, 2, 5%) 1000 off £6.50, 100 off £1.10. Mixed (1%) 70 off £1, (2%, 1/2W) 70 off £1, (1W) 35 off £1, (2W) 30 off £1. Enclosed miniature cermet trim-pots (assorted): 10 off £1.50, 50 off £5. Ten turn wirewound potentiometers: 5 assorted £1.60. Low profile turned pin d.i.l. sockets: 8 off 24 pin £2.30, 40 pin 60p each. Postage and packing 70p. SAE for full list. Milner Electronics, 2 Elgarth Drive, Wokingham, Berkshire RG11 4HH.

MICRO TRANSMITTER KIT, 500m range, tunable 88-115MHz, sensitive microphone, £3.95. Cheques/PO to: Quantum Electronics (EE), 267 Rednal Road, Kings Norton, Birmingham B38 8EB.

DELUXE WALKIE TALKIES long range, 49MHz £24.99/pair (normally £31.49). Satisfaction or refund. Send £3 now, pay balance upon receipt. 48 hrs. delivery. Xenon (Dept EE9), 24 Wharnccliffe Street, Barnsley, Yorkshire.

TECH-SUPPLY. Variable power supply 3-30V 1.5 amp, fully tested, guaranteed. With meter £45.50 inclusive. Without meter £38.50 inclusive. Cheque/PO payable to: Tech Supply, 1 Holland House, Bolton Road, Radcliffe, Manchester M26 0GW. Allow 14 to 21 days delivery.

Bargain Bags

BARGAIN BAGS. Resistors, tuners, panels, speakers, caps, presets etc. Bargain at £10 + £2 p&p. Cheque payable to K. Pendlebury, 43 Cowpe Road, Waterfoot, Rossendale, Lancs BB4 7DQ.

ROCK BOTTOM PRICES FOR QUALITY COMPONENTS

Turntable belts Tape heads Multimeters
Soldering irons Styli Speakers Aerials
Crossovers Video copy kits Plugs Leads
SEND OR PHONE FOR FREE LISTS
STRACHAN ELECTRONICS,
9 CROALL PLACE, EDINBURGH EH7 4LT
Tel: 031-556 9549

TURN YOUR SURPLUS

ICS transistors etc into cash, immediate settlement. We also welcome the opportunity to quote for complete factory clearance.
Contact **COLES-HARDING & CO,**
103 South Brink, Wisbech, Cambs.
ESTABLISHED OVER 10 YEARS
Tel: 0945 584188

PLEASE MENTION EVERYDAY ELECTRONICS WHEN REPLYING TO ADVERTISEMENTS

Services

ELECTRONIC repairs and rebuild service. All projects undertaken. Tel: D.G. Electronics, Chelmsford (0245) 266160.

Service Manuals

SERVICE SHEETS from £2.50/1sae ctv/music/combis £3.50/1sae. Sae Newnes & TV Technic Books in stock. Thousands Service & Repair Manuals. SAE Free Review/pricelists. TIS (EE), 76 Church St, Larkhall (0698 883334), Lanarkshire.

WORKSHOP SERVICE MANUALS

Thousands stocked, most makes, models, types, audio, TV, video, test, amateur etc. LSAE enquiries/quotation and FREE Review/price lists with details of our Unique Repair and Data Guides, from Valves to Videos.

MAURITRON (EE), 8 CHERRY TREE ROAD, CHINNOR, OXON OX9 4QY.

Printed Circuit Boards

PRINTED CIRCUIT BOARDS produced to own personal requirements. Please send sae for details: Mr. B. M. Ansbro, 38 Poynings Drive, Hove, Sussex.

Special Offers

FREE MEMBERSHIP to a new national electronics club. For details and a free pack of components worth over £10 send only £1 p&p to Dept. EE, Woodside, Dowsett Lane, Ramsden Heath, Billericay, Essex CM11 1JL.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of **Everyday Electronics** for Insertions. I enclose Cheque/P.O. for £ (Cheques and Postal Orders should be made payable to Everyday Electronics)

HEADING REQUIRED:

NAME

ADDRESS

EVERYDAY ELECTRONICS
and **ELECTRONICS MONTHLY**
Classified Advertisement Dept.,
6 Church Street,
Wimborne,
Dorset BH21 1JH.
Telephone 0202 881749

RATE: 30p per word, minimum 12 words. Box No. 60p extra. VAT must be added.

9/87

£1 BARGAIN PACKS

Buy 10 packs ... get one free (your choice)

PK 1. 350 Assorted resistors. Full length leads.
 PK 2. 400 Assorted resistors. Pre-formed leads.
 PK 3. 60 Assorted resistors. Wire wound.
 PK 4. 200 Assorted mixed capacitors.
 PK 5. 200 Assorted ceramic capacitors.
 PK 6. 60 Electrolytic capacitors.
 PK 7. 2 2200µf 100 volt capacitors.
 PK 8. 2 4700µf 30 volt capacitors.
 PK 9. 12 Assorted rotary potentiometers. Single gang.
 PK 10. 6 Assorted rotary potentiometers. Dual gang.
 PK 11. 12 Assorted slider potentiometers.
 PK 12. 40 Assorted pre-set potentiometers.
 PK 13. 5 100K lin multiturn potentiometers.
 PK 14. 5 1 meg lin multiturn potentiometers.
 PK 15. 12 Assorted switches.
 PK 16. 1 bank 4-way push button switches c/w knobs.
 PK 17. 1 4 pole 5-way waler switch.
 PK 18. 15 Assorted control knobs.
 PK 19. 20 Assorted plugs and sockets.
 PK 20. 2 Pairs D.C. plugs & sockets c/w leads & PP3 clip.
 PK 21. 25 Assorted transistors. All new & coded.

PK 22. 15 Assorted I.C.'s. All new & coded.
 PK 23. 50 Assorted unmarked & untested I.C.'s.
 PK 24. 100 Assorted diodes.
 PK 25. 20 E.H.T. diodes.
 PK 26. 3 Large power-lin heatsinks. T03.
 PK 27. 1 4 section 7 segment i.e.d. clock display.
 PK 28. 20 Assorted neons. Panel mounting & wire ended.
 PK 29. 1 Microphone c/w lead, switch, plugs & stand.
 PK 31. 3 Dynamic earpieces c/w lead & 3.5mm plug.
 PK 32. 2 Telescopic aerials.
 PK 35. 1 Large cassette motor.
 PK 36. 1 Wire pack. Mains cable.
 PK 38. 1 Wire pack. Connecting wire. Assorted colours.
 PK 39. 300 Assorted resistors. 1/2W or less. F.L. leads.
 PK 40. 200 Assorted Polyester capacitors.
 PK 41. 12 Push to make switches. pcb mounting.
 PK 42. 12 Push on-Push off switches.
 PK 43. 4 Assorted toaster elements.
 PK 44. 3 Assorted record player spilt.
 PK 45. 50 Assorted I.F. and tuning coils.
 PK 46. 35 Assorted resistors 1% tolerance.

Postal order or cheque with order. Please add £1 postage & packing per order.
 Access and Barclaycard orders welcome, minimum £10. Please phone orders before 4pm.
 Electronics magazines, we have an extensive range of back issues. 50p for current lists.

**MJR WHOLESALE, Unit 3, 238 Waterside,
 Chesham, Bucks HP5 1PG. ☎ 0494 771033**


MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your FREE INFORMATION PACK on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	Radio, Audio and TV Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds)	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCE over 40 'O' and 'A' level subjects			<input type="checkbox"/>



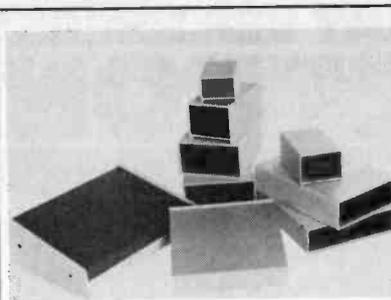Name _____ P. Code _____
 Address _____
 International Correspondence Schools, Dept ECS97, 312/314 High St.,
 Sutton, Surrey SM1 1PR. Tel: 01-643 9568 or 041-221 2926 (24 hrs).



**BOXING PROBLEMS??
 LOOK NO FURTHER!!**

Choose from our standard range below, or if you are looking for a specific size, then we can produce YOUR OWN CUSTOM BOX WITHOUT ANY TOOLING COSTS, with all holes, slots, PCB grooves, etc, already machined in, ready to assemble.

H	W	D		CONSOLE BOXES
C1: 30	50	80*	D10: 50 x 100 x 110*	
C2: 40	60	90*	D20: 35 x 145 x 170*	PRG1: 20/60 x 130 x 160*
C3: 50	70	110*	D30: 40 x 120 x 170*	PRG2: 35/70 x 230 x 160*
			D40: 70 x 110 x 145*	PRG3: 35/77 x 290 x 190
			D50: 60 x 160 x 170	
			D60: 100 x 180 x 210	
BA4: 20	85	120	D70: 70 x 200 x 215	All sizes are in millimetres, and are internal.
			GA1: 93 x 280 x 160	
			GA2: 140 x 400 x 205	

All made from high impact resistant plastic which is easily drilled or cut.

Boxes marked * are available through Cirkit Distribution Ltd., Park Lane, Broxbourne, Herts.

For other sizes and details of Custom Service contact us at the address below.

Distributor enquiries welcome.

BAFBOX LTD.

Unit A, Park End Works, Croughton,
 BRACKLEY NN13 5LX
 Telephone: 0869 810830

ELECTRONICS TECHNICIAN FULL-TIME TRAINING

(FULL TIME COURSES APPROVED BY THE BUSINESS & TECHNICIAN EDUCATION COUNCIL)

2 YEAR
 BTEC National Diploma (OND)
ELECTRONIC & COMMUNICATIONS ENGINEERING
 (Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

1 YEAR
 BTEC National Certificate (ONC)
INFORMATION TECHNOLOGY
 (Electronics, Satellite TV, CD, Networks, Telecomms)

ELECTRONIC EQUIPMENT SERVICING
 (Electronics, Television, Video Cassette Recorders, CCTV, Testing & Fault Diagnosis)

SOFTWARE ENGINEERING
 (Electronics, Assembler, BASIC, PASCAL, CAD/CAM)

COMPUTING TECHNOLOGY
 (Electronics, Computing Software/Hardware, Microelectronic Testing Methods)

10 MONTHS
 BTEC Higher National Certificate (HNC)
COMPUTING TECHNOLOGY & ROBOTICS
 (Microprocessor Based Systems, Fault Diagnosis, ATE, Robotics)

THESE COURSES INCLUDE A HIGH PERCENTAGE OF COLLEGE BASED PRACTICAL WORK TO ENHANCE FUTURE EMPLOYMENT PROSPECTS

NO ADDITIONAL FEES FOR OVERSEAS STUDENTS

SHORTENED COURSES OF FROM 3 TO 6 MONTHS CAN BE ARRANGED FOR APPLICANTS WITH PREVIOUS ELECTRONICS KNOWLEDGE

O.N.C. 21st September 1987
 FULL PROSPECTUS FROM

**LONDON ELECTRONICS COLLEGE (Dept EE)
 20 PENYWERN ROAD, EARLS COURT,
 LONDON SW5 9SU. Tel: 01-373 8721.**

Zenith Electronics.®

Kits - Modules - Hardware

NEW

★ High quality TOUCH DIMMER R/Built. finished in white plastic and Brass touch plate. £12.99 inc. VAT & P&P.

The following are examples of our proven product designs in kit form:

- ★ 10 Channel Variable Speed Running Light; Drives LEDs or mains lamps. Kit £14.97
- ★ 3 Note Electronic Door Chime unit; 9 volt operation, 3 melodious tones; variable frequency. Kit £9.83
- ★ Miniature FM Transmitter; 60-145MHz. Kit £6.95
 R/Built £8.95
- ★ 3 Watt FM Transmitter, 80-108MHz. Kit £13.99
 R/Built £18.99
- ★ 300 Watt Light Dimmer unit for 240 volt mains lights. Kit £6.95
- ★ 4 Code Digital Code unit plus Key Pad—select own code; 9 volt. Kit £15.95
- ★ 5-100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit £11.11
- ★ VU Meter 10 LED indicator; -5 to +12dB range. Kit £12.59
- ★ Automatic light controller; automatically turns on and off lights at pre-set times and triggered by darkness. Kit £25.08
- ★ Mains Wiring and Metal Detector. R/Built £11.00
- ★ Digital Clock module; 12-24 hour timing; LED type £17.49
 or LCD type £22.80
- ★ Amplifier Power Meter; 10 LED indicator from 0-25-100 Watt Input—9 volt operation. Kit £9.52
- ★ Light sensitive relay unit; variable sensitivity trigger control; senses light or dark—selectable. Kit £8.45


ALL KITS CONTAIN FULL INSTRUCTIONS. P.C.B.s AND COMPONENTS.
 ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.
 OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.
 PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.

S.A.E. For
 -FREE-
 Data Pack

Zenith Electronics, 14 Cortlandt Business Centre,
 Hailsham, E. Sussex, U.K. BN27 1AE.
 Tel: 0323 847973

INDEX TO ADVERTISERS

AUDIOKITS	520
BAFBOX	519
BI-PAK	468
B.K. ELECTRONICS	Cover III
BULL, J. & N.	Cover II
CIRKIT DISTRIBUTION	466
COLES-HARDING	518
C-SCOPE	511
ELECTRONIZE DESIGN	466
GREENWELD ELECTRONICS	467
I.C.S.	519
LONDON ELECTRONICS COLLEGE	519
MAGENTA ELECTRONICS	470
MAPLIN ELECTRONIC SUPPLIES	Cover IV
MARCO TRADING	466
MAURITRON	518
M.J.R. WHOLESALE	519
NATIONAL COMPONENT CLUB	513
OMEGA ELECTRONICS	466
OMNI ELECTRONICS	511
PHONOSONICS	520
RADIO COMPONENT SPECIALISTS	513
SHERWOOD DATA SYSTEMS	468
SMITH ELECTRONICS	511
STRACHAN ELECTRONICS	518
T.K. ELECTRONICS	485
XEN-ELECTRONICS	511
ZENITH ELECTRONICS	519

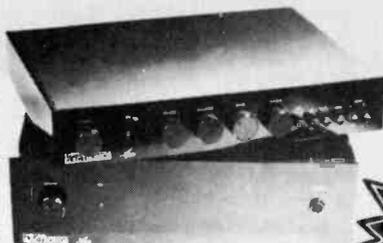

The EE APEX PREAMP AND POWER AMP KITS

Build this superb preamp and power amp kit and enjoy high fidelity sound at a fraction of the cost of comparable ready built amplifiers.

Complete kits as described in March-June issues of Everyday Electronics including high current transformers and attractively styled cases with high quality components.

Preamp	£192.50
Power amp-stereo	£192.50

Or build it with the very best components available including IAR Wonder caps, Extended foil polystyrene capacitors, bulk foil resistors, Holco precision resistors, silver plated switches, gold plated phono sockets and Kimber cable for internal wiring.

Preamp	£410
Stereo Power amp	£310
Mono Power amp	£232

All components including PCBs available separately

For full parts price list of the EE Apex preamp and details of **AUDIOKITS** audiophile components and kits,

please send 9" x 4" SAE to:

AUDIOKITS Precision Components

6 MILL CLOSE, BORROWASH, DERBY DE7 3GU. Tel: 0332 674929

CONSTRUCTIONAL

KIT CATALOGUE


PHONOSONICS

FASCINATING ELECTRONIC PROJECTS

- ★ BE KIT CREATIVE
- ★ RAISE YOUR SKILLS
- ★ LEARN BY BUILDING
- ★ ENJOY BY USING




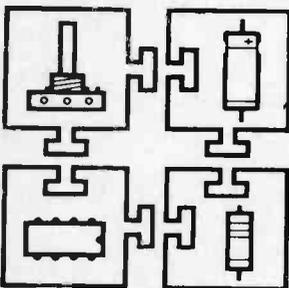THROUGH
ELECTRONICS
UNDERSTAND
ESSENTIAL
TECHNOLOGY



- ★ MUSIC MODULES
- ★ GEIGER COUNTERS

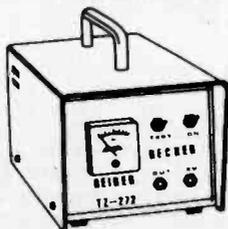- ★ DIGITAL INTERFACES
- ★ MANY MORE FINE DESIGNS



POPULAR PROJECTS FROM
A LEADING AUTHOR

KITS THAT FIT

MUSIC AND EFFECTS

A-D-A Interface*	Set 251	61.00
Chip Test 16-Pin*	Set 258S	32.50
Chip Test 24-Pin*	Set 258F	39.30
Chorus Flanger Dual	Set 235	59.99
Compander	Set 238	22.99
Cybervox Voice FX	Set 228	44.76
Digital Delay & MCS	Set 234RK	198.50
Disco Light Control	Set 245F	62.50
Echo-Reverb Stereo	Set 218	57.66
Equaliser 3-Chan	Set 217	25.33
Event Counter	Set 278	39.50
Flanger (Mono)	Set 153	28.45
Guitar Modulo	Set 196	23.56
Micro-Scope*	Set 247	44.50
Micro-Trace*	Set 261	19.50
Mini-Sampler	Set 246	75.00
Mixer 4-Ch Stereo	Set 229S	89.95
Mixer Simple 4 Chan	Set 256	19.99
Mock Stereo	Set 213	24.37
Morse Decoder*	Set 269	22.16
Noise Gate	Set 227	26.61
Phaser-Enhanced	Set 226	42.36
Polywhatsit! FX	Set 252	122.69
Rhythm Gen*	Set 185	34.64
Ring Modulator	Set 231	45.58
Storm Wind & Rain	Set 250W	29.50
Thunder & Lightning	Set 250T	29.50
Tuner-Micro*	Set 257	55.32
Tuner-Simple*	Set 259	22.50
Vodalek Voice FX	Set 155	18.31

* Computer controlled (BBC, C64, PET)
Most PCBs available separately

Send A4 SAE for detailed catalogue, and with all enquiries (overseas send £1.00 or 51.R.C.'s).
Add 15% VAT. Add P&P - Sets over £50 add £2.50. Others add £1.50. Overseas P&P in catalogue. Text photocopies - Geiger & DDL Texts £1.50 each, others 50p, plus 50p post or large SAE. Insurance 50p per £50. Mail order, CWO, CHQ, PO, Access, Visa.

**PHONOSONICS, DEPT EE79, 8 FINUCANE DRIVE,
ORPINGTON, KENT BR5 4ED. Tel: 0689 37821**

LOW COST GEIGER COUNTERS



NUCLEAR FREE ZONES?
CHECK THEM OUT -
GET A GEIGER

THE PE GEIGER WAS
SHOWN ON BBC TV
"TAKE NOBODY'S WORD
FOR IT" PROGRAM

Detectors for environmental and geological monitoring - know your background! You'd be amazed at the quantities sold since Chernobyl.

METERED GEIGER (PE MK2)

Built-in probe, speaker, meter, digital output. Detector tube options - ZP1310 for normal sensitivity, ZP1320 for extrasensitivity.

Kit-form - SET 264 - (ZP1310) £59.50, (ZP1320) £78.50

Ready-built - T2272 - (ZP1310) £75.50, (ZP1320) £94.50

AUDIO GEIGER (EE MK2)

Built-in probe (ZP1310), speaker, digital output. Kit-form SET 265 MK2 £49.50. Ready-built T2274 £65.00

GEIGER-MITE SET 271 £39.50

Miniature geiger with ZP 1310 tube. LED displays radiation impacts. Socket for headphones or digital monitoring. Kit-form only.

OMP POWER AMPLIFIER MODULES

OMP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi, etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

Supplied ready built and tested.



OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens. for Max. output 500mV at 10K, Size 355 X 115 X 65mm. PRICE £33.99 + £3.00 P&P.

OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 X 123 X 60mm. PRICE PRICE £39.99 + £3.00 P&P.

OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 X 150 X 100mm. PRICE PRICE £62.99 + £3.50 P&P.

OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 X 147 X 102mm. PRICE PRICE £79.99 + £4.50 P&P.

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV). Order - Standard or P.A.

Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 X 27 X 45mm. PRICE £8.50 + 50p P&P.



LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.



POWER RANGE
 8" 50 WATT R.M.S. Hi-Fi/Disco.
 20 oz. magnet. 1 1/2" ally voice coil. Ground ally fixing escutcheon. Res. Freq. 40Hz. Freq. Resp. to 6KHz. Sens. 92dB. PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea.
 12" 100 WATT R.M.S. Hi-Fi/Disco
 50 oz. magnet. 2" ally voice coil. Ground ally fixing escutcheon. Die-cast chassis. White cone. Res. Freq. 25Hz. Freq. Resp. to 4KHz. Sens. 95dB. PRICE £28.60 + £3.00 P&P ea.

McKENZIE
 12" 85 WATT R.M.S. C1285GP Lead Guitar/Keyboard/Disco.
 2" ally voice coil. Ally centre dome. Res. Freq. 45Hz. Freq. Resp. to 6.5KHz. Sens. 98dB. PRICE £29.99 + £3.00 P&P ea.
 12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
 Res. Freq. 45Hz. Freq. Resp. to 14KHz. PRICE £31.49 + £3.00 P&P ea.
 15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
 3" ally voice coil. Die-cast chassis. Res. Freq. 40Hz. Freq. Resp. to 4KHz. PRICE £57.87 + £4.00 P&P ea.
 10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.
 2" voice coil. Res. Freq. 75Hz. Freq. Resp. to 7.5KHz. Sens. 99dB. PRICE £19.99 + £2.00 P&P.
 10" 200 WATT R.M.S. C10200GP Guitar/Keyboard/Disco.
 2" voice coil. Res. Freq. 45Hz. Freq. Resp. to 7KHz. Sens. 101dB. PRICE £44.76 + £3.00 P&P.
 15" 200 WATT R.M.S. C15200 High Power Bass.
 Res. Freq. 40Hz. Freq. Resp. to 5KHz. Sens. 101dB. PRICE £62.41 + £4.00 P&P.
 15" 400 WATT R.M.S. C15400 High Power Bass.
 Res. Freq. 40Hz. Freq. Resp. to 4KHz. Sens. 102dB. PRICE £89.52 + £4.00 P&P.

WEM
 5" 70 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 52Hz. Freq. Resp. to 5KHz. Sens. 89dB. PRICE £22.00 + £1.50 P&P ea.
 8" 150 WATT R.M.S. Multiple Array Disco etc.
 1" voice coil. Res. Freq. 48Hz. Freq. Resp. to 5KHz. Sens. 92dB. PRICE £32.00 + £1.50 P&P ea.
 10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 92dB. PRICE £36.00 + £2.00 P&P ea.
 12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 4KHz. Sens. 94dB. PRICE £47.00 + £3.00 P&P ea.

SOUNDLAB (Full Range Twin Cone)
 5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 63Hz. Freq. Resp. to 20KHz. Sens. 86dB. PRICE £9.99 + £1.00 P&P ea.
 6 1/2" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1" voice coil. Res. Freq. 56Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £10.99 + £1.50 P&P ea.
 8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
 1 1/2" voice coil. Res. Freq. 38Hz. Freq. Resp. to 20KHz. Sens. 89dB. PRICE £12.99 - £1.50 P&P ea.
 10" 60 WATT R.M.S. Hi-Fi/Disco etc.
 1 1/2" voice coil. Res. Freq. 35Hz. Freq. Resp. to 15KHz. Sens. 89dB. PRICE £16.49 + £2.00 P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt) Price: £8.62 + 75p P&P.
3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.
SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 90 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.



PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

BURGLAR ALARM

Better to be 'Alarmed' than terrified. Thandar's famous 'Minder' Burglar Alarm System. Superior microwave principle. Supplied as three units, complete with interconnection cable. FULLY GUARANTEED.

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.
Indoor alarm - Electronic swept freq. siren. 104dB output.
Outdoor Alarm - Electronic swept freq. siren. 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00 Usual Price £228.85
BKE's PRICE £89.99 + £4.00 P&P
 ? Why buy a collection of self-assembly boards!

IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms. Full range 45Hz - 20KHz. Size 20" X 15" X 12". Watts R.M.S. per cabinet. Sensitivity 1W. 1mtr. dB.

OMP 12-100 Watts 100dB. Price £149.99 per pair.
OMP 12-200 Watts 102dB. Price £199.99 per pair.
 Delivery Securicor £8.00 per pair



OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies, XLR connections. MF600 Fan cooled. Three models (Ratings R.M.S. into 4ohms). Input Sensitivity 775mV

MF200 (100 + 100)W. £171.35 Securicor
MF400 (200 + 200)W. £228.85 Delivery
MF600 (300 + 300)W. £322.00 £10.00

1 K-WATT SLIDE DIMMER

- * Control loads up to 1Kw
- * Compact Size 4 1/2" X 1" X 2 1/2"
- * Easy snap in fixing through panel/cabinet cut out
- * Insulated plastic case
- * Full wave control using 8 amp triac
- * Conforms to BS800

* Suitable for both resistive and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.

PRICE £13.99 + 75p P&P

BSR P295 ELECTRONIC TURNTABLE


- * Electronic speed control 45 & 33 1/2 r.p.m. * Plus/Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1/2" cartridge fixings * Operation 9-14v D.C. 65mA



ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p.

PIEZO ELECTRIC TWEETERS MOTOROLA

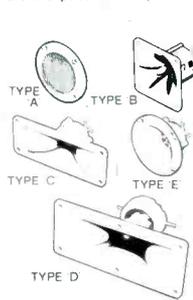Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 40p P&P
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P
TYPE 'C' (KSN6016A) 2" X 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 40p P&P
TYPE 'D' (KSN1025A) 2" X 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 40p P&P
TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 40p P&P
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 X 85 mm. Price £3.99 + 40p P&P

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 X 5 band L. & R. graphic equalisers and twin 10 segment L.E.D Vu Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following -
 3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot. L. & R. Master Output controls. Output 775mV. Size 360 X 280 X 90mm.
 Price £134.99 - £3.00 P&P



B. K. ELECTRONICS

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME, SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS C.O.D. ACCEPTED.



APACHE



The Apache

A superb ready-built scale-model off-road racer complete with a 2-CHANNEL DIGITAL PROPORTIONAL RADIO CONTROL SYSTEM - for the price of the RC system alone! All this is included in the price:
 Ready-built 1/4 scale model car (overall size 325 x 186 x 130mm, 12.8 x 7.3 x 5.1in.)
 Front and rear low-profile semi-pneumatic rubber tyres.
 Front wheel independent suspension.
 High or low gear selection.
 Sealed box with differential gearing.
 Powerful motor gives scale speeds up to 140 mph.

COMPLETE* SYSTEM ONLY
£49.95!
 (YP25C)

Front and rear coil-spring shock absorbers.
 2-channel digital proportional radio control transmitter (and receiver).
 (Standard 27MHz AM - no licence required in UK)
 Servo-controlled proportional steering.
 Proportional motor speed control in forward and reverse.

*Batteries and ni-cad charger not included. Car requires 8 AA cells (ni-cad recommended YG00A £1.35 each).
 Transmitter requires 6 AA cells, (alkaline FK64U 55p each or ni-cad as above). NB - and if you have a collision at 100mph or more, you'll be pleased to hear that spare parts are available.



Please rush me my Apache model racer, with 2 channel digital proportional radio control system. I wish to receive:

	Code	Qty	Price
Apache model racer	YP25C		
AA ni-cad battery	YG00A		
AA alkaline battery	FK64U		
		Total	

All prices include VAT. Please add 50p towards postage.
 If order below £5.00, please add 50p handling.
 I enclose cheque postal order made payable to Maplin Electronic Supplies Ltd., or see credit card details.
 Here are my personal details:
 Customer Number

Name

Address

Post Code

I authorise you to debit my Credit Card account for the cost of goods despatched.

Credit Card Number

Access/American Express/Mapcard/Visa Delete as required

Note: Goods will be despatched only if the address given is the cardholder's address.
 If ordering by Credit Card please sign.

Signature

Expiry Date

EE/9/87

Maplin Maplin Electronic Supplies Ltd.
 P.O. Box 3, Rayleigh, Essex, SS6 8LR. Telephone, Credit Card Sales (0702) 554161. Enquiries (0702) 552911
 Shops at: Sutton New Road, Erdington, Birmingham. Tel: 021-364 8411, 155-161, King Street, Hammersmith, London, W6. Tel: 01-748 0926
 8 Oxford Rd., Marlow, Bucks. Tel: 061-236 0281, 46-48, Bevons Valley Rd., Southampton. Tel: 0703 23851.
 292-294 London Rd., Westcliff-on-sea, Essex. Tel: 0702-854000.