

EVERYDAY

OCTOBER 1989

ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

£1.40

FREE INSIDE!

**MARCO
32 PAGE
CATALOGUE**



SEISMOGRAPH

**New Series
LOGO LEGO &
THE SPECTRUM**

CAR IGNITION SYSTEMS

The Magazine for Electronic & Computer Projects



No. 3 LIST BAKERS DOZEN PACKS

All packs are £1 each, if you order 12 then you are entitled to another free. Please state which one you want. Note the figure on the extreme left is the pack ref number and the next figures are the quantity of items in the pack, finally a short description.



- BD152 1 Gas or liquid shut off valve, clockwork dial, setting can be on for up to 12 hours.
- BD153 1 Same as BD152 but thermostatically operated.
- BD154 1 12v operated drip proof relay, ideal for outdoor or in-car operation.
- BD158 4 12 way 5 amp screw down polythene bodied connector strips. Used to be called choc blocks when made of Bakelite.
- BD159 2 12 way 25 amp connector blocks
- BD160 1pr Plug together 12 way connector blocks, ideal for quick joins in leads.
- BD168 2 Component mounting tag strips each with 50 stand up tags.
- BD169 4 Short wave air spaced trimmers 3-30pf. Screw driver operated.
- BD170 4 Assorted neon type numicator tubes made by HIVAC.
- BD175 1 2 watt mains motor driving gearbox, final speed 200rpm.
- BD177 5 12v Lilliput bulbs.
- BD178 3 Panel mounting slim line indicator lights with amber lens. These take Lilliput bulbs.
- BD179 3 Oblong mains neon indicator lights, approx 1in x 1/2in. PVC grommets for insulation through 3/8th hole.
- BD181 100 25pf air spaced tuning capacitor, small hole fixing with 1/4in spindle.
- BD189 1 20 amp double pole switch on flush plate which fits standard 3x3 electrical box, illuminated when on.
- BD190 1 20 amp dp switch but surface mounting, oblong shape.
- BD191 6 Lamp holder adaptors which take two pin plug, also supplied.
- BD200 1 10 digit switch pad, telephone type.
- BD205 1 Very small 12v operated relay with one pair change-over contacts.
- BD212 1 Mains transformer 230v primary and two 8v 1/2 amp secondaries.
- BD213 2 5 core curly leads, tinsel wire for phones, etc.
- BD214 2 Sub-min toggle switches double pole double throw.
- BD215 4 Mini dpdt slide switches with chrome dolly instead of the usual plastic toggle.
- BD217 100 Standard wire ending push-ons for standard 1/4in tags.
- BD218 100 Ditto, but right angled.
- BD219 100 Soldercon tags. With these you can make your own sockets for ICs etc.
- BD223 4 1200 watt fire spirals, bright nickel chrome wire.
- BD224 1 Battery operated motor made for 9v cassette players but speed controllable by lowering voltage.
- BD227 4 50k quad pots. Standard 1/4in spindle single hole fixing.
- BD228 1 Ice stat thermostat. Ideal for controlling water pipe antifreeze coils.
- BD229 1 Instrument buzzer, variable low, medium or soft.
- BD233 2 Eagle educational kits. One makes chemical balance with weights and the other has electricals for experiments.
- BD234 4 500µf + 500µf 50v electrolytics.
- BD236 1 Mains transformer with 9v 750mA secondary.
- BD237 1 Computer grade electrolytic 3150µf at 40v.
- BD243 2 8x4 16 ohm loudspeakers permanent magnet, 5 watts.
- BD246 4 Standard size 1/2meg with 1/4in spindle and dp switch
- BD247 1 The medium wave permeability tuner, couple this to a ZN414 and you have a radio.
- BD248 1 A noise suppressor/mains filter
- BD249 1 13A socket on plate with spur, fits normal electrical box.
- BD253 1 Oven thermometer — bimetal type, reads 200-500°F.

There are over 1,000 items in our Bakers Dozen List. If you want a complete copy please request this when ordering.

CAMERAS. Three cameras, all by famous makers, Kodak etc. One disk, one 35mm and one instamatic. All in first class condition, believed to be in perfect working order, but sold as untested. You can have the three for £10 including VAT, which must be a bargain — if only for the lenses, flash gear etc. Our ref 10P5B.

EQUIPMENT WALL MOUNT It is a multi-adjustable metal bracket that could be used for mounting flood light, loudspeaker, TV camera, even a fan and on almost any sort of wall or ceiling even between wall and ceiling. The main fixing brackets rotate so that an inward or an outward corner can be accommodated. Front panel also tilts upward or downwards to a reasonable angle and can be easily removed separately for wiring. A very useful bracket. Regular price would be around £6 each. Our price only £3. Our ref 3P72. Or 2 for £5. Our ref 5P152.

MICROPHONE LEADS 6m twin screened wire terminating one end with a standard 1/4in mono jack plug and the other end with the usual screwed on microphone connector. With coiled spring for lead protection. Price £1. Our ref BD174.

EXTRA SPECIAL CROC CLIPS Medium size, just right for most hook-ups. Normally sell for around 10p to 15p each. These are insulated and have a length of wire connected to them but this is very easy to snip off if you do not need it. 20 for £1. Our ref BD117A.

DON'T MISS THAT IMPORTANT CALL Fit an extension lead and take your phone in the other room with you. 5m long, one end has the standard flat BT socket and the other the standard flat BT phone plug so you don't have to interfere with the house wiring, you simply plug it in. Price £3. Our ref 3P70.

COPPER CLAD PANEL For making PCB. Size approx 12in long x 8 1/2in wide. Double-sided on fibreglass middle which is quite thick (about 1/8 in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref BD633.

3 VOLT MOTOR Very low current so should be very suitable for working with solar cells. £1 each. Our ref BD681.

STEREO HEADPHONE AMPLIFIER Very sensitive. A magnetic cartridge or tape head will drive it. Has volume control and socket for stereo headphones. 3v battery operated. £1 each. Our ref BD680.

FET CAPACITOR MICROPHONE EAGLE CI.200 Output equivalent to a high class dynamic microphone while retaining the characteristics of a capacitor microphone. Price £1. Our ref BD646.

SUB-MAN TOGGLE SWITCH Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 3 for 1.00. Order ref BD649.

POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, workroom etc. Makes you feel better and work harder — a complete mains operated kit, case included. £12.50 + £2 P&P. Our ref 12P51.

LINEAR RECORD PLAYER Made by BSR, their ref VL315. Hailed as the most sophisticated of record players, is completely electronically controlled. Due to cancelled export order we are now able to offer these brand new, complete with cartridge and diamond stylus at only £15 plus £2 post. This is a 12v DC operated unit. Our ref 15P25. Two or more post free.

VIDEO TAPES These are three hour tapes of superior quality, made under licence from the famous JVC company. Offered at only £3 each. Our ref 3P63. Or 5 for £11. Our ref 11P3. Or for the really big user 10 for £20. Our ref 20P20.



ELECTRONIC SPACESHIP.

Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the components on the pcb. Complete kit £8. Our ref 8P30.

THERE IS GOING TO BE A BURIAL! For several years now we have been offering mains operated clocks at only £1 each. These are cooker clocks which in addition to telling you the time would also switch things on and off at pre-set times. However, despite this silly price these have been very slow sellers and as we have still almost 10,000 of them in store which we have to clear we are making one even sillier final offer before burying them. You can have 16 brand new clocks still in original packing for only £5. Our ref 5P151. Add £3 post if not collecting.

BUSH RADIO MIDI SPEAKERS Stereo pair. BASS reflex system, using a full range 4in driver of 40hms impedance. Mounted in very nicely made black fronted walnut finish cabinets. Cabinet size approx 8 1/2in wide, 14in high and 3 1/2in deep. Fitted with a good length of speaker flex and terminating with a normal audio plug. Price £5 the pair plus £1 post. Our ref 5P141.

3 1/2in FLOPPY DRIVES We still have two models in stock: Single sided, 80 track, by Chinon. This is in the manufacturers metal case with leads and IDC connectors. Price £40, reference 40P1. Also a double sided, 80 track, by NEC. This is uncase. Price £59.50, reference 60P2. Both are brand new. Insured delivery £3 on each or both.



ATARI 65XE COMPUTER

At 64K this is most powerful and suitable for home and business. Complete with PSU, TV lead, owner's manual and six games. Can be yours for only £45 plus £3 insured delivery.

REMOTE CONTROL FOR YOUR 65XE COMPUTER With this outfit you can be as much as 20 feet away as you will have a joystick that can transmit and a receiver to plug into and operate your computer and TV. This is also just right if you want to use it with a big screen TV. The joystick has two fire buttons and is of a really superior quality, with four suction cups for additional control and one handed play. Price £15 for the radio controlled pair. Our ref 15P27.

AGAIN AVAILABLE: ASTEC PSU. Mains operated switch mode, so very compact. Outputs +12V 2.5A, +5V 6A, +5V .5A, ±12V 5A. Size: 7 1/2in long x 4 1/4 in wide x 2 1/4 in high. Cased ready for use. Brand new. Normal price £30+, our price only £10. Our ref 10P34 plus £1 postage.

VERY POWERFUL 12 VOLT MOTORS. 1/3rd Horsepower. Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20 plus £2 postage. Our ref. 20P22.

PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe as long as you do not look directly into the beam when eye damage could result. Brand new, full spec. £30 plus £3 insured delivery. Mains operated power supply for this tube gives 8kv striking and 1.25kv at 5mA running. Complete kit with case £15. As above for 12V battery. Also £15. Our ref 15P22.

ORGAN MASTER Is a three octave musical keyboard. It is beautifully made, has full size (piano size) keys, has gold plated contacts and is complete with ribbon cable and edge connector. Can be used with many computers, request information sheet. Brand new, only £15 plus £3 postage. Our ref 15P15.

FULL RANGE OF COMPONENTS at very keen prices are available from our associate company SCS COMPONENTS. You may already have their catalogue, if not request one and we will send it FOC with your goods.

A REAL AIR MOVER Circular axial fan. It moves 205cu ft per minute which is about twice as much as our standard 4 1/2in. square fans. Low noise, mains operated, 6 1/2 in diameter. Ex computers. Regular price over £30 but yours for £10 if you order quickly. Our ref 10P71A.

HIGH RESOLUTION MONITOR. 9in black and white. used Philips tube M24-306W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new. £16 plus £5 post. Our ref 16P1.

12 VOLT BRUSHLESS FAN. Japanese made. The popular square shape (4 1/2in x 4 1/2in x 1 1/4in). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26.

FDD BARGAIN

3 1/2in made by Chinon of Japan. Single sided, 80 track, Shugart compatible interface, interchangeable with most other 3 1/2in and 5 1/4in drives. Completely cased with 4 pin power lead and 34 pin computer lead £40 plus £3 insured delivery. Our ref 40P1.

MINI MONO AMP on p.c.b. size 4" x 2" (app.) Fitted Volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00.



J & N BULL ELECTRICAL

Dept. EE 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5DT.

MAIL ORDER TERMS: Cash, PO or cheque with order. Orders under £20 add £1.50 service charge. Monthly account orders accepted from schools and public companies. Access and Bcard orders also. — minimum £5. Phone (0273) 734648 or 203500.

POPULAR ITEMS — MANY NEW THIS MONTH

Some of the many items described in our current list which you will receive if you request it

POPULAR ITEM AGAIN AVAILABLE Twin 0005 tuning capacitor with normal 1/4in spindle now listed by many firms at over £10 each. We have htmr brand new and in perfect condition at £2 each. our ref 2P40.

SUB-MIN PUSH SWITCHES Not much bigger than a plastic transistor but double pole. PCB mounting. Three for £1. Our ref BD688.

CARTRIDGES for the Double Microdrive. Price 4 for £5. Our ref 5P146.

NICAD CHARGER UNIT Metal pronged, plastic case contains mains transformer and rectifiers with output lead and plug — made to charge two cells but no doubt adaptable or wonderful spares value. Only 50p each, two for £1. Our ref BP385.

EDGEWISE PANEL METER If you are short of panel space then this may be the answer. It has a FSD of 100µA and a nice full vision scale. It fits through a hole approx 1 1/4in x 1/2in. Another feature is that it has an indicator lamp behind the scale which you could light up, it would then serve as an on/off indicator. Price £1. Our ref BD700.

AA CELLS Probably the most popular of the rechargeable NICAD types. 4 for £4. Our ref 4P44.

COMPUTER SPECIAL. The Perex 16meg Byte tape streamer. These are brand new and really an exceptional bargain. A few only so hurry. Only £15. Our ref 15P29.

20 WATT 40HM SPEAKER With built in tweeter. Really well made unit which has the power and the quality for hi-fi reproduction. 6 1/2in diameter. Price £5. Our ref 5P155. It is heavy so please add £1 to cover postage if not collecting.

MINI RADIO MODULE Only about 2in square with ferrite aerial and solid dia tuner with its own knob. It is a superhet and it operates from PP3 battery and would drive a crystal headphone direct but be better with our mini mono amp. Price £1. Our ref BD716.

BULGIN MAINS PLUG AND SOCKET The old faithful 3 pin with screw terminals. The socket mounts through a 1 1/2in hole and the mains is brought in by the insulated plug. Used to be quite expensive but you can have 2 pairs for £1 or 4 of either plug or socket for £1. You could make yourself a neat and compact bench panel with these. Our ref BD715, BD7155 or BD715P.

MICROPHONE If you want a low cost microphone then just arrived we have a very small hand-held dynamic mic with on/off switch in the handle, its lead terminates with one 3.5 plug and the other a 2.5 plug for remote control. Price only £1. Our ref BD711.

EXTENSION CABLE WITH A DIFFERENCE It is flat on one side making it easy to fix and to look tidy. It is 4 core so suitable for telephone, bell, burglar alarms, etc. 50 yard coil for £5. Our ref 5P153.

MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES 140v 100w pair made by the famous Hitachi Company. Reference 25K413 and its component 25J118. Only £4 the pair. Our ref 4P42.

BATTERY OPERATED TRAVEL MECHANISM On a plastic panel measuring approx. 9in x 3 1/2in. Is driven by a reversible 12v battery motor, fitted with a pulley and belt which rotates through a threaded rod and causes a platform to travel backwards and forwards through a distance of approx. 5in. Price £5. Our ref 5P140.

MAINS OPERATED WATER VALVE with hose connection for inlet and outlet suitable for low pressure. Auto plant watering, etc. Only £1 each. Our ref BD370.

20 VOLT 4 AMP MAINS TRANSFORMER Upright mounting with fixing feet. Price £3. 3P59.

16 OHM PM SPEAKERS Approx. 7in x 4in. 5 watts. Offered at a very low price so you can use two in parallel to give you 10 watts at 8 ohms. £1 for the two. Our ref BD684.

EHT TRANSFORMER 4kv 2mA Ex-unused equipment. £5. Our ref 5P139

4 CORE TINSEL COPPER LEAD As fitted to telephones, terminating with flat BT plug. 2 for £1. Our ref BD639.

EHT TRANSFORMER 8kv 3mA. £10. Our ref 10P56

VERY USEFUL MAGNETS Flat, about 1in long, 1/2in wide and 1/4in thick. Very powerful. 6 for £1. Our ref BD274(a).

ACORN COMPUTER DATA RECORDER REF ALF03. Made for the Electron or BBC computers but suitable for most others. Complete with mains adaptor, leads and handbook. £10.00. Ref 10P44. Add £2 special packing.

SOLAR CELLS Will give good current (depending on size) from sunlight or bright daylight. Module A gives 100mA. Price £1. Our ref BD631. Model C gives 400mA. Price £2. Our ref 2P199. Model D gives 700mA. Price £3. Our ref 3P42.

SOLAR POWERED NI-CAD CHARGER 4 Ni-Cad batteries AA (HP7) charged in eight hours or two in only 4 hours. It is complete, boxed ready to use unit. Price £6. Our ref 6P3.

METAL PROJECT BOX Ideal for battery charger, power supply etc., sprayed grey, size 8 1/4" x 4" high, ends are louvred for ventilation other sides are flat and undrilled. Price £3. Order ref 3P75.

13A PLUGS Good British make complete with fuse, parcel of 5 for £2. Order ref 2P186.

13A ADAPTERS Takes 2 13A plugs, packet of 3 for £2. Order ref 2P187. 20v-0-20v. Mains transformers 2 1/2 amp (100 watt) loading, tapped primary, 200-245 upright mountings £4. Order ref 4P24.

CAPACITOR BARGAIN Axial ended — 4700µf at 25v. Jap made. Normally 50p each, but you will get 4 for £1. Ref 613.

SINGLE SCREENED FLEX 7.02 copper conductors, pvc insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m for £1. Our ref BD668.

3 CORE FLEX BARGAIN No. 1 Core size 5mm so ideal for long extension leads carrying up to 5 amps or short leads up to 10 amps. 15m £2. Ref 1P189

3 CORE FLEX BARGAIN No. 2 Core size 1.25mm so ideal for long extension leads carrying up to 13 amps or short leads up to 25A. 10m for £2. Order ref 2P190

ALPHA-NUMERIC KEYBOARD This keyboard has 73 keys with contactless capacitance switches giving long trouble free life and no contact bounce. The keys are arranged in two groups, the main area field is a QWERTY array and on the right is a 15 key number pad, board size is approx. 13" x 4" — brand new but offered at only a fraction of its cost namely £3 plus £1 post. Ref 3P27.

1/8 HORSEPOWER 12 VOLT MOTOR Made by Smiths, the body length of this is approximately 3in., the diameter 3in, and the spindle 3/16th of an inch diameter. It has a centre flange for fixing or can be fixed from the end by means of 2 nuts. A very powerful little motor which revs at 3,000rpm. We have a large quantity of them so if you have any projects in mind then you could rely on supplies for at least two years. Price £6. Our ref 6P1. discount for quantities of 10 or more.

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

ABC



MEMBER OF THE BPP GROUP
PUBLISHERS OF PRACTICAL

VOL 18 No 10 OCTOBER 1989

The Magazine for Electronic & Computer Projects

ISSN 0262-3617

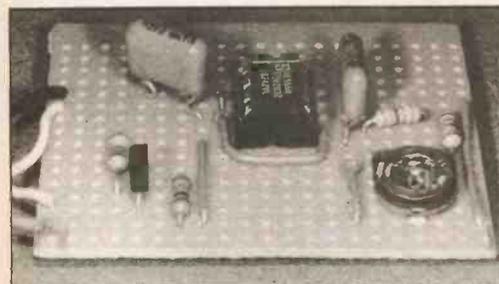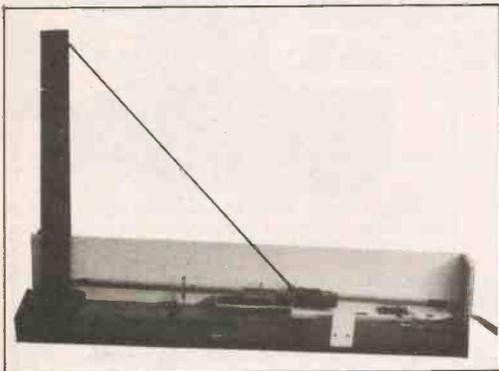PROJECTS... THEORY... NEWS...
COMMENT... POPULAR FEATURES...



© Wimborne Publishing Ltd 1989. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our November '89 Issue will be published on Friday, 6 October 1989. See page 619 for details.

Projects

- EE SEISMOGRAPH** by Tony Hopwood and Andy Flind **626**
Watch for earthquakes and nuclear tests around the world.
- I.C. SOUND GENERATOR** by Chris Bowes **632**
An easy to build, low cost unit that uses the popular 555 timer.
- VARIABLE STABILIZED POWER SUPPLY** **650**
by Steve Knight
Fully variable from 0V to 30V at 1A.
- LEGO, LOGO and SPECTRUM** by Alan Harper **653**
Introduce your Spectrum to the world of robotics.
- MUSIC ON HOLD** by David Butler **662**
Keep your caller amused.
- SIMPLE L.E.D. TIMER** By Chris Bowes **668**
Low cost unit that can be adapted to many timing applications.

Series

- AMATEUR RADIO** by Tony Smith **644**
More Primary Bands; Power Levels; Skeletons.
- STABILIZED POWER SUPPLIES** by Steve Knight **646**
Part Four: Variable supplies.
- INTRODUCING DIGITAL ELECTRONICS** **658**
Answers to Part 12
- ON SPEC** By Mike Tooley **666**
Readers' Sinclair Spectrum page.
- BBC MICRO** by R. A. Penfold & J. W. Penfold **673**
Regular spot for Beeb fanatics.
- ROBOT ROUNDUP** by Nigel Clark **676**
Investigating the world of robotics.

Features

- EDITORIAL** **625**
- SHOPTALK** by David Barrington **636**
Product news and component buying.
- CAR ELECTRONIC IGNITION SYSTEMS** **638**
by Stewart Robertson
Brief summary of the application of electronics to car ignitions.
- FOR YOUR ENTERTAINMENT** by Barry Fox **660**
Airvision; Skyview; Sound Systems.
- DOWN TO EARTH** by George Hylton **678**
Skin Effect; Reducing Resistance.
- MARKET PLACE** Free readers buy and sell spot. **679**
- DIRECT BOOK SERVICE** Special service to EE readers **680**
- PRINTED CIRCUIT BOARD SERVICE** **684**
- ADVERTISERS INDEX** **688**

FREE

Marco 32-page catalogue

between pages 652/653

Readers' Services • Editorial and Advertisement Departments

625

THE RTC MONITOR II

100 WATT SPEAKER KIT £60.00 + £3.50 P&P (pair)

RESPONSE: 55Hz-20kHz

BASS POLYMER CONE D: 22cm

DOVE TWEETER: 14mm

OVERALL SIZE
(HWD): 382,252,204mm

RECOMMENDED AMP POWER:

10-100 watts per channel

The performance standard achieved in this compact design is distinctively superior to anything else available at the price. The drive units used are of sophisticated design and have been carefully integrated with a Complex Crossover.

Stereo performance is exceptionally good with a well focussed sound stage and sharp resolution of detail. Distortion throughout the frequency range is low even at quite high power input and this gives a great sense of dynamic range and openness especially when used in bi-wired mode.

Supplied with:— 2 READY CUT BAFFLES, ALL CROSSOVER COMPONENTS, 2 BASS MID-RANGE, 2 DOME TWEETERS, HOOK UP WIRE, GRILLE CLOTH, SCREW TERMINALS AND SCREWS.

CROSSOVER KIT. To build 2 sets of crossovers £11+£1.75 post. (Featured in *Everyday Electronics*—May 1989 issue). Reprint Free with Kits



AMPHONIC 125+ 125 POWER AMPLIFIER



125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.

Output power 125W RMS max. per channel

Output impedance 4 to 16 ohms

(max. power into 4 ohms)

Sensitivity 450V at 22K ohms

Protection Electronic short-circuit and fuses

Power 220-240V a.c. 50Hz

Chassis dim 435x125x280mm

Weight 10kg approx

£124.99 + £7.00 p&p



J.B.L. BOLIVAR COMPONENT SPEAKERS

10" HI-FI BASS UNIT WITH 1" VOICE COIL, HIGH COMPLIANT, RE-INFORCED MOLDED PAPER CONE, ROLLED FOAM EDGE WITH A BIG 4 1/2" MAGNET 6Ω IMPEDANCE £18.73

4 1/2" 100W HI-FI MID RANGE 1" VOICE COIL, PAPER CONED AND DOTTED CERAMIC EDGE FITTED WITH A 3 1/2" MAGNET. 6Ω IMPEDANCE £5.33

4 1/2" HI-FI TWEETER 3/4" VOICE COIL, 1 3/4" CONE WITH FOAM EDGE 6Ω MAGNET, 6Ω IMPEDANCE £6.33
POSTAGE £4.70 PER ORDER

52W 2-WAY COMPONENT SPEAKER SYSTEM £3.95

Comprises 8in rolled surround bass unit and 2 1/4in tweeter for In-Car or Hi-Fi use. 4 ohm. Made by Sanyo.

8 OHM HI-FI COMPONENT SPEAKER £4.95

6 1/2in. Audax 60w. Res freq. 45Hz bass-mid

8in SOUND LAB 60W £12.95

Res freq. 38Hz full range

12in DANTEX 100W £21.75

Res freq. 23Hz bass unit

Postage £3.20 each order

★ SPECIAL PURCHASE

Batteries C size NiCad 2.2 Ah EVERY-READY AN220

£1.98 each

£1 BARGAIN PACKS BUY 10 GET 1 FREE

Please state pack(s) required
No = Order No. Qty = Quantity per pack

No	Qty	Description
BP010	2	6 1/2" Speaker 8Ω 10 watt
BP012	2	6 1/2" Speaker 4Ω 10 watt
BP013	3	8" x 5" Speaker 4Ω 6 watt made by E.M.I.
BP015A	1	5 1/2" full range 12 watt 4Ω speaker with matching grill. For small p.a. or in car use.
BP015B	1	30 watt, dome tweeter. Size 90x66mmil JAPAN made
BP016	6	2200µf can type Electrolytic 25V d.c. computer grade made in UK by PHILIPS
BP017	3	33000µf 16V d.c. electrolytic high quality computer grade UK made
BP018	3	2000µf 50V d.c. electrolytic high quality computer grade made in USA
BP019	20	20 ceramic trimmers
BP020	4	Tuning capacitors, 2 gang dielectric a.m. type
BP021	10	3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA
BP022	5	Push-button switches, push on push off, 2 pole change over. PC mount JAPAN made
BP023	6	2 pole 2 way rotary switch
BP024	2	Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch UK made by LORLIN
BP025	4	3 pole, 3 way miniature rotary switch with one extra position off (open frame YAXLEY type)
BP026	4	4 pole, 2 way rotary switch UK made by LORLIN
BP027	30	Mixed control knobs
BP028	10	Slide potentiometers (popular values)
BP029	6	Stereo rotary potentiometers
BP030	2	100k wire wound double precision potentiometers UK made
BP031	6	Single 100k multitune pots, ideal for varicap tuners UK made by PHILIPS
BP032	4	UHF varicap tuner heads, unboxed and untested UK made by PHILIPS
BP033	2	FM stereo decoder modules with diagram UK made by PHILIPS
BP034	3	AM IF modules with diagram UK made by PHILIPS
BP034A	2	AM-FM tuner head modules. UK made by MULLARD
BP034B	1	Hi-Fi stereo pre-amp module inputs for CD, tuner tape, magnetic cartridge with diagram. UK made by MULLARD
BP035	6	All metal co-axial aerial plugs
BP036	6	Fuse holders, panel mounting 20mm type JAPAN made
BP037	6	In line fuse holders 20mm type UK made by BULGIN
BP038	20	5 pin din, 180° chassis socket
BP039	6	Double phono sockets, Paxolin mounted
BP041	3	2.8m lengths of 3 core 5 amp mains flex
BP042	2	Large VU meters JAPAN made
BP043	30	4V miniature bulbs, wire ended, new untested
BP044	2	Sonotone stereo crystal cartridge with 78 and LP styli JAPAN made
BP045	2	Stereo cassette record and play heads JAPAN made
BP046	4	6-0-6 4VA mains transformers, P.C. mount UK made
BP047	1	24V 750mA mains power supply. Brand new boxed UK made by MULLARD
BP049	10	OC4A transistors. Remove paint from top and it becomes a photo-electric cell (or P12) UK made by MULLARD
BP050	30	Low signal transistors n.p.n., p.n.p. types
BP051	6	14 watt output transistors. 3 complimentary pairs in T066 case (ideal replacement for AD161 and 162s)
BP052A	1	Tape deck pre-amp IC with record/replay switching No LM1818 with diagram
BP053	5	5 watt audio ICs. No TBA800 (ATEZ)
BP054	10	Motor speed control ICs, as used with most cassette and record player motors
BP055	1	Digital DVM meter I.C. made by PLESSEY as used by THANDAR with diagram
BP056	4	7 segment 0.3 LED display (R.E.D.)
BP057	8	Bridge rectifiers, 1 amp, 24V
BP058	200	Assorted carbon resistors
BP059	1	Power supply PCB with 30V 4V/A transformer. MC7818CT IC & bridge rectifier: Size 4" x 2 1/4"
BP060	1	Transcription record player motor 1500rpm 240V a.c.
BP061	5	6.35mm Mono jack plugs
BP063	5	6.35mm stereo switched jack sockets
BP064	12	Coax chassis mount sockets
BP065	1	3mtr Euro-mains lead with a matching chassis socket

MULTIBAND RADIO

VHF 54-176 MHz + AM CB BANDS 1-80

Listen to: AIR TRAFFIC CONTROL,

AIRCRAFT, RADAR

PUBLIC UTILITIES AND

RADIO AMATEURS AND

MANY MANY MORE

£15.95

POSTAGE £2.85

SQUELCH CONTROL

"RUBBER DUCK AERIAL"



RADIO and TV COMPONENTS ACTON LTD

21 HIGH STREET, ACTON LONDON W3 6NG

MAIL ORDER TERMS. POSTAL ORDERS and or CHEQUES

with orders. Orders under £20 add £3.00 service charge. Nett


monthly accounts to Schools, Colleges and P.L.C. only

ACCESS: VISA. Phone orders between 9.30 & 12pm please

Phone: 01-723 8432 or 01-992 8430

Callers 323 Edgware Road, London W2

30+30 WATT AMPLIFIER KIT

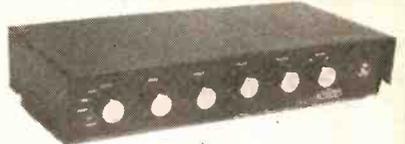

An easy to build amplifier with a good specification. All the components are mounted on the single P.C.B. which is already punched and backprinted.

■ 30W x 2 (DIN 4 ohm)

■ CD/Aux, tape I, tape II, tuner and phono inputs.

■ Separate treble and bass

■ Headphone jack

Size (H.W.D.) 75 x 400 x 195mm

Kit enclosed: case, P.C.B., all components, scale and knobs £36.80. post £3.50

(Featured project in *Everyday Electronics* April 1989 issue). Reprint Free with kit.

TV SOUND TUNER



In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are quite common and that really is quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact independent TV tuner that connects direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 5 pre-selected tuning controls. It can also be used in conjunction with your video recorder.


£29.50 + £2.50 p&p

As above but with built-in stereo headphone amplifier for the hard of hearing

You can tune into the TV channel you want while still receiving the picture on your TV set. In fact it is rather like a second television, but without the screen. So that the ordinary TV can be placed for everyone to see, and the volume on it can be comfortable for others, while the sound tuner can be placed where you can control it. You will need to plug in one of your own listening aids such as headphones or an induction loop to hear the sound. The tuner is mains operated, has 5 pre-selected tuning controls and can be used in conjunction with a video recorder.

Size: 270 x 192 x 65mm. £35.90 + £2.50 p&p

A.M. F.M. STEREO TUNER KIT

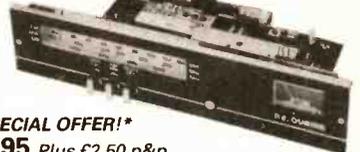

SPECIAL OFFER!

£8.95 Plus £2.50 p&p

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics

For ease of construction and alignment it incorporates three Mullard modules and an I.C. I.F. System.

FEATURES: VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM-Ferrite rod, FM-75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to strict P.E. specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

Hi-Fi stereo cassette deck transport mechanism, complete with 3 digit rev counter and tape heads, 12V d.c. operation. Unused manufacturers surplus JAPAN made

£6.20 + £1.50 P&P 2 for £10 + £2.50 P&P

EXTRACTABLE HOUSING FOR YOUR CAR STEREO + SIZE DIN E * HANDLE INCLUDED * SPACE FOR MEMORY BATTERY * 4 OR 2 SPEAKER SYSTEM.

ENABLES YOU TO REMOVE YOUR VALUED STEREO FROM YOUR CAR (WITHOUT THE AID OF A HAMMER AND CHISEL, CHAINSAW ETC). £9.95 postage £2.50


FREE

WITH THIS ISSUE OF **EE**
GREENWELD
ELECTRONICS COMPONENTS CATALOGUE

132
PAGES OF
BARGAINS

WORTH
£1.50

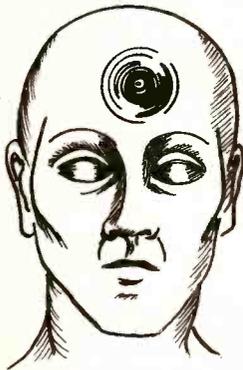Once again *EE* is proud to be able to give away the full Greenweld catalogue. It comes *FREE*, banded with every copy next month.



EEG BIOFEEDBACK MONITOR

*Would you like to listen to the rhythms of your mind?
You don't have to be a master of Zen and Yoga to learn how to relax after a stressful day!
The brain produces various frequencies of electrical or "brain-wave" activity, the best known being Alpha, Beta and Theta. Scientists believe the control of these "waves" is one of the secrets of relaxing.*


Build the EEG Biofeedback Monitor and all will be revealed.

IRON-ON REMINDER

Forgetting about a switched-on soldering iron can have results varying from pitted bit to a fire hazard, especially if left overnight. So, for constructors who habitually nod off, or wander away to watch their favourite TV programme, this circuit is a must.

VARIABLE POWER SUPPLY

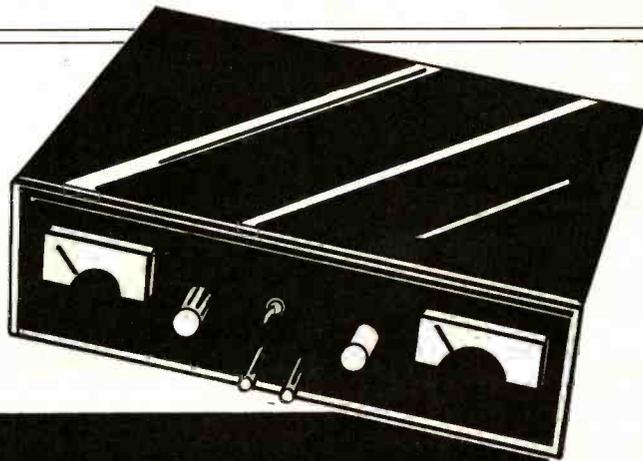A powerful, fully variable 0-30V 2A output power supply that will prove invaluable in the workshop.



EVERYDAY
ELECTRONICS

NOVEMBER ISSUE ON SALE OCTOBER 6 1989

NEW COMPONENT PACKS

New components, lots of new packs, and a better selection than ever in the old favourites. If you haven't yet sampled these delicious component assortments, you just don't know what you're missing! All the packs are **£1 (+VAT)** each, but if you order five packs you can select an extra one **FREE**. Order ten packs and you can have three extra packs **FREE**. Go for it!

PASSIVE COMPONENTS

- PACK 1 - 200 RESISTORS. Finest carbon film, with lots of E12 values and a few precision.
- PACK 2 - 100 CAPACITORS. Polystyrene, ceramics, metallised film. A fine selection!
- PACK 3 - 30 ELECTROLYTICS. Values to 470µF.
- PACK 4 - 15 LARGE ELECTROLYTICS. Values to 4,700µF.
- PACK 5 - 10 TANTALUM CAPACITORS. Values from 0.1µF to 68µF!
- PACK 6 - 20 HIGH VALUE POLYESTER CAPACITORS. Values to at least 3µ3.
- PACK 7 - 15 DIL RESISTOR NETWORKS. Lots of values.
- PACK 8 - 50 POWER RESISTORS. 1W and above.
- PACK 9 - 30 SUB-MINIATURE CAPACITORS. Look like diodes!

OPTO ELECTRONICS & DISPLAYS

- PACK 11 - 10 5mm LEDs: 4 red, 2 yellow, 2 orange, 2 green.
- PACK 12 - 10 3mm LEDs: 4 red, 2 yellow, 2 orange, 2 green.
- PACK 13 - 10 Rectangular LEDs. Mixed red and green.
- PACK 14 - 10 Mixed LEDs. All shapes, sizes, colours.
- PACK 15 - 2 DUAL 0.3" CA 7-seg displays (panel type).
- PACK 16 - 1 DUAL 0.5" CC 7-seg display (panel type).
- PACK 17 - 1 QUAD 0.3" CA 7-seg display (panel type).
- PACK 18 - 2 INFRA-RED COMPONENTS. Emitter and receiver.
- PACK 20 - 1 CALCULATOR DISPLAY, eight digits.
- PACK 23 - 2 PHOTOTRANSISTORS. Respond to visible and IR light.

SEMICONDUCTORS

- PACK 26 - 3 TAG136D MAINS TRIACS (400V, 4A).
- PACK 27 - 30 IN4000-SERIES RECTIFIERS.
- PACK 28 - 30 MIXED SEMICONDUCTORS. Diodes, transistors, ICs, triacs, all sorts.
- PACK 29 - 20 ASSORTED ICs. CMOS, TTL, linear, memory, as available. Changes daily!
- PACK 30 - 20 TRANSISTORS. High grade general purpose NPN.
- PACK 31 - 12 BC912 TRANSISTORS. High grade general purpose PNP.
- PACK 32 - 12 BC213 TRANSISTORS. High grade general purpose PNP.
- PACK 33 - 3 DUAL OP-AMPS MC1458. With data.
- PACK 35 - 20 RECTIFIERS. Studs, high current, glass bead, top hat, IN4000, etc.
- PACK 36 - 50 DIODES 1N4148. The most popular type for projects!
- PACK 39 - 10 SURFACE MOUNT AND LCC ICs. Special hi-tech pack!

MISCELLANEOUS

- PACK 41 - 4 POWER MICROSWITCHES. Push to break.
- PACK 42 - 8 SPST STANDARD MICROSWITCHES (V3).
- PACK 43 - 5 SPST ROLLER-OPERATED MICROSWITCHES (V3).
- PACK 44 - 1 MINI BIO-FEEDBACK KIT. With PCB, components and instructions.
- PACK 45 - 1 MINI DREAM-MACHINE KIT. With PCB, components and instructions.
- PACK 46 - 1 MINI BURGLAR ALARM KIT. With PCB, components and instructions.
- PACK 47 - 6 AUDIO TRANSFORMERS.
- PACK 48 - 200 CABLE CLIPS to attach alarm or doorbell wires to wall.
- PACK 51 - 1 CRYSTAL OSCILLATOR MODULE, 19,6608MHZ.
- PACK 52 - 12 PP3 BATTERY CLIPS.
- PACK 53 - 2 PIEZO TRANSDUCERS. Use as microphone or speaker.
- PACK 60 - 100 MYSTERY PACK of at least 100 components. The most popular pack of all!

AUTUMN COLLECTION

Buzz like a butterfly, hoot like a bee; the computer you pay for, but the switches are free! Match this famous quotation with our equally famous sound effects computer, and you could be on your way to a fortnight's holiday in the Canary Islands. On the other hand, you're much more likely to be sitting in your front room. But you never can tell where people read their electronics mags, can you?



SOUND EFFECTS COMPUTER

Take a powerful PIC655A single chip computer, mask program it to produce the most outrageously realistic sound effects, add an audio amplifier to bring them up to loudspeaker level, and you have the Highgrade Sound Effects Computer. How about a motor rally, complete with gear changes? Or a ship hooting its mournful way through the fog? Or a fly so realistic it'll have you running for the swat! Sirens, helicopters, steam trains, aliens - you name it, it's in there. The

computer is easily programmed with the thirteen switches supplied. In one mode you can even play it like a synthesizer! I have to admit, it's my favourite project of the moment. With your computer we also give you: a battery connector, a loudspeaker, thirteen switches, and a wiring diagram and programming instructions. You add a PP3 battery, a length of connecting wire and ten minutes of your time to connect it all together.

SOUND EFFECTS COMPUTER KIT **£12.80!** (+VAT)



LCD DISPLAY MODULES

On one side of the PCB is an LCD which displays two lines of text and symbols. On the back there's a powerful surface-mount drive IC to take in data, store it, and drive the display. Interface is through an eight-way connector for the power supply and data signals. We supply full data on the IC, which should be enough for you to get it up and running!

LCD DISPLAY MODULE **£6.60** (+VAT) 10 DISPLAYS **£54!** (+VAT)

LED DISPLAYS

TYPE 1: DUAL 0.56" COMMON ANODE

Large, high brightness digits for displays that have to be visible at some distance. Each display has two digits, but the connections to each are entirely separate. They can be butted up to each other to make a display as long as you choose! And just look at the price.

10 0.56" DUAL CA DISPLAYS **£4.80!** (+VAT) 50 DISPLAYS FOR **£22!** (+VAT)



TYPE 2: 1 1/2 DIGIT 0.5" COMMON CATHODE

Another two digit display, with the left-hand one lighting up as ±1. Once again, connections to the two digits are entirely separate.

PACK OF 10 1 1/2 DIGIT 0.5" CC DISPLAYS **£3.80!** (+VAT) 50 DISPLAYS FOR **£17!** (+VAT)

BAR-GRAPH LED MODULE

Eleven rectangular green LEDs assembled as a bar graph display. The central LED is turned edge-on to indicate the 'normal' position, or for centre-zero or tuning indicator displays. All LED leads are individually available at the rear of the assembly.

BAR GRAPH MODULE **£1.40** (+VAT) 10 MODULES **£11.80!** (+VAT)



LEDs

Rectangular LEDs in a tasteful shade of green, or a violent primary red. Bring some colour into your life! The prices ARE genuine.

PACK OF 100 RED, GREEN OR MIXED (you choose) RECTANGULAR LEDs **£3!** (+VAT)

PACK OF 500 RED, GREEN OR MIXED LED'S **£14!** (+VAT)



BUFFER AMP

Elantec EL2033 damn fast (100MHz) buffer amplifiers. Equivalent to National LH0033C. Current list price is **£28.50** each, I kid you not. With data.

EL2033 100MHz BUFFER AMP **£2.80!** (+VAT)

KEYBOARDS

Full size QWERTY keyboard units with separate numeric pad and function keys. Exactly 100 keys in all. Must be good value just for the switches!

COMPUTER KEYBOARD **£4.80!** (+VAT)

POWER METERS

Meter movement scaled 0-10 with red pointer against a green scale which can be back lit for glowing effect. Full scale approx. 1mA.

POWER METER **£1.80!** (+VAT) 5 METERS **£7.80** (+VAT)

MONSTER PARCELS

PARCEL 3 Lots and lots of ICs. Who knows what might turn up? Into the parcel go all the remainders from past lists, ICs we haven't got enough of to advertise separately, all the CMOS and TTL, and lots more. Some IC's will be common and familiar, some won't. Some have data and some don't. Some you'll recognise at once, others you'll have to do some detective work on. A fascinating mixture with lots of nice surprises for you if you know your ICs.

PARCEL 3A: 100 ICs for **£12!** (+VAT) PARCEL 3B: 500 ICs for **£49!** (+VAT)

PARCEL 4 Tants. So much nicer than common old electrolytics, I always think 'An excellent range of values, now reaching as high as 68µF (all parcels) and up to 100µF if you're lucky!

PARCEL 4A: 100 TANTS FOR **£6.80!** (+VAT) PARCEL 4B: 500 TANTS FOR **£29!** (+VAT)


PARCEL 6 Transistors. A useful selection of general purpose types, with a few exotics to keep you on your toes. Lots of BC212s, BC548s, and other common types.

PARCEL 6A: 200 TRANSISTORS for **£7.80!** (+VAT)

PARCEL 7 LEDs! All kinds of shapes, sizes, styles and colours. How about making an LED garden? During the day, flowers. At night, a spectacular display of coloured LEDs!

PARCEL 7A: 100 LEDs for **£5.90!** (+VAT)

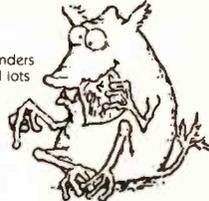PARCEL 7B: 500 LEDs for **£24.90!** (+VAT)




UK Orders: Please add £1 postage and packing and 15% VAT to the total (including postage).
Europe and Eire: Please add £2.50 carriage and insurance. No VAT.
Outside Europe: Please add £4.80 carriage and insurance. No VAT.
Access Orders Please phone 0600 3715 for immediate attention to your order.

HIGHGRADE COMPONENTS LTD UNIT 111, 8 Woburn Road, Eastville, Bristol BS5 6TT.

0/11/89 2770

SURGICAL TOOLS

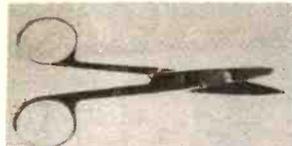

Another parcel of precision made stainless steel high grade surgical tools, made by Rocket of London. All these tools have minor surface faults (very difficult to find on many!!)

TWEEZERS

A wide variety of sizes and styles, from a small 86mm tweezer to a robust 205mm pair for heavy duty work. Sold in sets as described below at a substantial saving over the individual price; typically £6 per pair!

Z4191 Pack of 11 all different, featuring both straight and curved ends, serrated and plain varying in length from 86mm to 205mm. List price is around £100. **£12.95.**

Z4192 Pack of 6 pairs (over 130mm) **£7.95.**

Z4193 Pack of 6 small pairs (up to 150mm) **£6.95.**

Z4194 Pack of 6 selected pairs across the range. **£7.50.**


SCISSORS

Superb quality instruments with pointed, rounded and flat ends. Again these are sold in sets to give excellent value.

Z4195 Pack of 10 assorted pairs from 100 to 140mm long, with both pointed and rounded ends, straight and curved cutting blades. Everything from extremely fine points to general purpose. All 10 pairs for just **£13.95.**

Z4196 Pack of 5 asst. pairs across the range **£7.95.**

BREADBOARDS

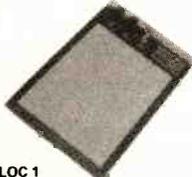

PROTOBLOC 1

G708 Protobloc 1 has a total of 400 tie points consisting of two sets of 30 rows of 5 interconnected sockets plus 4 rows of interconnect sockets running alongside, suitable for use as power supply rails. All contact positions are clearly defined on an alphanumeric grid. ABS polymer board mounted on an adhesive foam base. Will accommodate up to three 16 pin devices. An ideal introduction to solderless circuit development systems. Size 80x60mm **£2.50**

PHOTOBLOC 2

G711 Photobloc 2 has a total of 840 tie points consisting of two sets of 64 rows of 5 interconnected contact sockets plus 4 rows of 50 interconnected sockets running alongside, suitable for use as power supply rails. All contact positions are clearly defined on an alphanumeric grid. ABS polymer board mounted on an adhesive foam base. Will accommodate up to seven 16 pin devices. Size 172x64mm **£3.95**

PHOTOBLOC 2A

G712 As above, but the ABS polymer board is mounted onto a rigid base plate complete with three 4mm terminals in red, black and green for power connections. A mounting bracket which clips into the base is also provided to accept a variety of components including switches and potentiometers, etc. Price **£6.95**

PROJECT BOARD GL24

G724 2 of type G711 mounted onto a rigid baseplate with 3 coloured terminals, for power connections. Over-all size 225x150mm **£13.95**

PROJECT BOARD GL36

G736 3 of type G711 and an additional strip of 100 tie points mounted onto a rigid base plate with 4 coloured terminals. Overall size 242x195mm **£19.95**

POWER SUPPLIES



0-24V DC 3A

A112 Variable stabilized power supply with overload protection. Meter reads voltage or current (switched). Two voltage ranges; 0-12V and 12-24Vd.c. Ideal for laboratory use.

Input voltage:- 240V a.c. 50Hz
Output voltage:- 0-24V d.c. (2 ranges)
Stability:- 0.2%
Ripple:- 2.5mV
Dims:- 180 x 110 x 180mm
Price **£64.50**

0-24V DC 5A


A113 Variable stabilized power supply with overload protection. Meter reads voltage or current (switched). Two voltage ranges; 0-12V and 12-24Vd.c. Ideal for laboratory use.

Input voltage:- 240V a.c. 50Hz
Output voltage:- 0-24V d.c. (2 ranges)
Stability:- 0.2%
Ripple:- 4mV
Dims:- 180 x 180 x 110mm
Price **£85.00**

1990 CATALOGUE

128 PAGES OF ELECTRONIC COMPONENTS AND EQUIPMENT. HUGE RANGE! AMAZING VALUE! DON'T MISS OUT — RESERVE YOUR COPY NOW — ONLY £1.50 POST FREE!! PUBLISHED ON 1st OCTOBER 1989

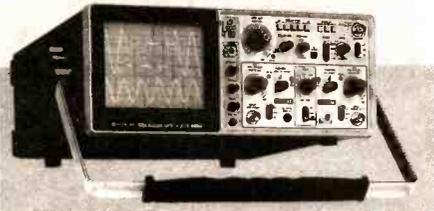HITACHI OSCILLOSCOPES FOR QUALITY AND VALUE



VZ23 DC-20MHz, dual Channel, single time base delayed sweep, DC offset, alternate magnifier, 6in screen, 5mV/div. vest. sensitivity 0.2µs/div-0.2s/div sweep time. Complete with 2 probes, manual, mains lead. **£475**

Other models from **£339** — full details in catalogue.

SWITCH MODE POWER SUPPLIES



ASTEC Model AA12531

I/P: 115/230V ac 50/60Hz
O/P: V1 + 5v 5A
V2 + 12v 0.15A
Size: 160 x 104 x 45mm
Partially enclosed panel with fixing holes in steel case on 120 x 125mm centres.
Inputs and Outputs are on colour coded leads; there is also an EEC socket on a flying lead **£6.95.**

ASTEC Model AC9231

I/P: 115/230V ac 50/60Hz
O/P: 50Watt max:
V1 + 12v 2.5A
V2 + 5v 6.0A
V3 12v 0.5A (+ or -)
V4 5v 0.5A (+ or -)
Size: 203 x 112 x 60mm
Fully enclosed case with built in tapped mounting holes.
Inputs and Output pins on edge of panel **£12.95.**

CAR SPEAKERS



New range of high power, high quality 'Soundlab' speakers.

Specially designed for in-car use at powers up to 240W! All are 4Ω impedance.

Chassis mounting models, complete with leads, grilles and all necessary fixings:
RTS410 2x50W, 4in, 100-18,000Hz **£12.95**
RTS520 2x50W, 5in+1 3/4in, 80-18,000Hz **£15.95**
RTS630 2x100W, 6 1/2in+2in+1in, 60-20,000Hz **£29.95**
PODS — Sophisticated 3-speaker systems:
RTS300 2x75W, 5in, 2in & 1in units, 80-18,000Hz **£27.95**
RTS400 2x120W, 4in, 2in & 1in units, 60-20,000Hz **£39.95**

METEX METERS

8 different models in our catalogue!!

- ★ 4 1/2 digit 12mm LCD display
 - ★ 30 ranges including 20A ac/dc
 - ★ Frequency counter
 - ★ Capacitance test with zero adjust
 - ★ Data hold switch
 - ★ Transistor test
 - ★ Diode test
 - ★ Continuity test
 - ★ Test leads with 4mm plugs
 - ★ Rugged yellow case
 - ★ Carrying case
- Battery and instruction manual included.
AC volts 0-200m-2-20-200-750Vac ±0.5%
DC volts 0-200m-2-20-200-1000Vdc ±0.5%
AC current 0-2m-200m-20Aac ±1.0%
DC current 0-200µ-2m-200m-20Adc ±0.5%
Resistance 0-200-2k-20k-200k-2M-20MΩ ±0.15%
Capacitance 0-20p-200n-20µF ±2.0%
Frequency 0-20k-200kHz ±2.0%
Transistor hFE 0-1000 NPN/PNP
Dims 176 x 90 x 36mm




M4650 £94.00



All prices include VAT; P&P £2.00 per order. Min Credit Card £5. No CWO min. Official Orders from Education welcome — min invoice charge £10.00
Our shop has enormous stocks of components and is open from 9-5.30 from Mon-Sat. Come and see us!
HOW TO CONTACT GREENWELD: By Post: Use the address below. By Phone: (0703) 772501/783740 (landphone out of business hours). By Fax: (0703) 787555. By E-Mail: 72-MAG36026. By Telex: 9312131093 (GW G). Payment is accepted by cheque postal order/cash inc foreign currency bank notes/book tokens.

443D MILLBROOK ROAD, SOUTHAMPTON, SO1 0HX.

GREEN SCREEN HI-RES 12in MONITOR CHASSIS

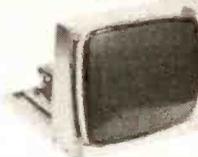

Brand new and complete except for case, the super high definition (1000 lines at centre) makes this monitor ideal for computer applications. Operates from 12V d.c. at 1.1A. Supplied complete with circuit diagram and 2 pots for brilliance/contrast, plus connecting instructions. Standard input from IBM machines, slight mod (details included) for other computers **Only £24.95**

DISK DRIVE PSU KIT

Ideal for powering single 3 1/2in or 5 1/4in drive. Mains input, stabilized smoothed outputs, 5V at 1A + 12V at 1A. Simple, easy to assemble kit with all parts and full instructions. **£4.95**

FREE SOFTWARE!!

To introduce our NEW software service, featuring all the best public domain and shareware, we're giving away, absolutely free, a 5 1/4in disk containing a complete catalogue of over 500 programs together with 2 FREE games.

To obtain your free copy, simply add to your order "FREE DISK". Don't forget to add £2.00 post, even if you order nothing else! Please note all available software, plus this free disk is only for IBM PC compatible machines using MS.DOS. The catalogue on disk contains brief information on all software available.

BIB ACCESSORIES

BCC11 Liquid Static Eliminator. A spray can of special formula liquid giving long term neutralisation of all harmful static charges from all glass and plastic surfaces. Comes complete with cloth. **£1.**

BCC8 Computer terminal maintenance kit for screen, keyboard and printer. Contents: Soft brush for keyboard and stiff brush for printer and print cleaning fluid. Aerosol can of air-blast. Kleen-Screen, an antistatic liquid; cleaning cloths. All this is contained in a presentation pack for just **£2.95.**

VE13 Lens Care Kit — High quality brush with dust protector, a bottle of antistatic lens cleaning fluid and a super soft lint free cleaning cloth, all contained in a handy storage wallet. Ideal for all still and movie/video camras — plus of course, spectacles. Offered at the exceptionally low price of just **£1.50.**

ANTEX SOLDERING EQUIPMENT

We stock the full range of Antex Soldering Irons, all at discounted prices.


Model C Popular basic 15 watt model. Price **£7.95.**

Model CS 17 watt model with leakage less than 2µA **£7.95.**

Model XS 25 watt general purpose iron, with a wide range of bits available. Price **£7.95.**

Model MLXS For car/boat/caravan, this 12V model with large clips to connect on battery is rated 25 watts **£10.95.**

STEREO VIDEO SOUND MIXER

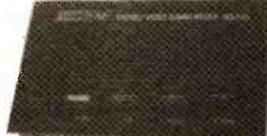

MX300 This versatile mixer is an essential part of editing videotapes. It allows audio inputs from camcorder or second video recorder (phono), cassette recorder or other music source (phono), and 2 microphones (3.5mm). The original soundtrack can be monitored and there is a master output (phono) to the VCR. Power can be a PP3 battery of an external 9V source. Smartly styled in a sloping front case with a matt black finish the overall dimensions are 175 x 110 x 55mm **£19.95.**

MAGENTA ELECTRONICS LTD

135 Hunter Street,
Burton-on-Trent,
Staffs. DE14 2ST
Tel: 0283 65435
Fax: 0283 46932

All prices include VAT
Shop open 9-5 Mon-Fri;
9-2 Saturday
Official orders welcome

Add £1
p&p to
all orders

EDUCATIONAL BOOKS & BOOK PROJECTS

INTRODUCTION TO ELECTRONICS

An introduction to the basic principles of electronics using a book and a set of components. Lots of simple experiments with full colour illustrations, diagrams and explanations. A lovely book, ideal for all ages. Based on Verobloc, requires soldering.

INTRODUCTION TO ELECTRONICS Book £3.50
COMPONENT PACK (less book) £11.70

ADVENTURES WITH ELECTRONICS

The classic Easy to Follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-DEC breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-DEC breadboard and all the components for the series.

ADVENTURES WITH ELECTRONICS £4.75
COMPONENT PACK (less book) £22.35

FUN WITH ELECTRONICS

From the USBORNE Pocket Scientist series — An enjoyable introduction to electronics. Full of very clear full colour pictures accompanied by easy to follow text. Ideal for all beginners — children and adults. Only basic tools are needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification & how they work). Also full details of how to build 6 projects — burglar alarm, radio, game, etc. Requires soldering — 4 pages clearly show you how.

The components supplied in our pack allows all the projects to be built and kept. The book is available separately.
FUN WITH ELECTRONICS Book £2.25
COMPONENT PACK (less book) £17.55

30 SOLDERLESS BREADBOARD PROJECTS

A book of projects by R. A. Penfold covering a wide range of interests. All projects are built on a Verobloc breadboard. Full layout drawings and component identification diagrams enable the projects to be built by beginners. Each circuit can be dismantled and rebuilt several times using the same components. The component pack allows all projects in the book to be built one at a time.

Projects covered include amplifiers, light actuated switches, timers, metronome, touch switch, sound activated switch, moisture detector, M.W. Radio, Fuzz unit, etc.

30 SOLDERLESS BREADBOARD PROJECTS Book 1 £2.95
COMPONENT PACK £27.15
VEROBLOC £7.49

ENJOYING ELECTRONICS

A more advanced book which introduces some arithmetic and calculations to electronic circuits. 48 chapters covering elements of electronics such as current, transistor switches, flip-flops, oscillators, charge, pulses, etc. An excellent follow-up to Teach-in or any other of our series. Extremely well explained by Owen Bishop who has written many excellent beginners' articles in numerous electronics magazines.

ENJOYING ELECTRONICS Book £3.60
COMPONENT PACK £14.31
VEROBLOC £7.49
Note — A simple multimeter is needed to fully follow this book. The M102 BZ is ideal. £13.98

A FIRST ELECTRONICS COURSE

A copiously illustrated book that explains the principles of electronics by relating them to everyday objects. At the end of each chapter a set of questions and word puzzles allow progress to be checked in an entertaining way. An S-DEC breadboard is used for this series — soldering is not required.

A FIRST ELECTRONIC COURSE BOOK £3.75
PACK £22.35

Supplying Electronics for Education, Robotics, Music, Computing and much, much more!

Send NOW for our

illustrated CATALOGUE

Only £1.00!

STEPPING MOTORS

A range of top quality stepping motors suitable for driving a wide range of mechanisms under computer control using simple interfacing techniques.


ID35 PERMANENT MAGNET MOTOR — 48 steps per rev. £16.50

MD200 HYBRID MOTOR — 200 steps per rev. £16.80

MD35 ¼ PERMANENT MAGNET MOTOR — 48 steps per rev. £12.70

MD38 PERMANENT MAGNET MOTOR — 48 steps per rev. £8.95

D.C. MOTOR GEARBOXES

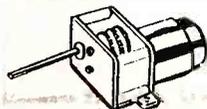

Ideal for Robots and Buggies. A miniature plastic reduction gearbox coupled with a 1.5-4.5 Volt mini motor. Variable gearbox reduction ratios are obtained by fitting from 1 to 6 gearwheels (supplied). Two types available:

SMALL UNIT TYPE MGS

Speed range 3-2200 rpm. Size 37x43x25mm

£3.99

LARGE UNIT TYPE MGL

Speed range 2-1150 rpm. Size 57x43x29mm

£4.55

TOOTHED BELTS & PULLEYS

Glass fibre reinforced belts with nylon coating. Width ¼", Pitch ½". Available in a range of lengths from 6"—26" £1.68-£2.60

Matching pulleys 8 tooth, 12, 25 + 40 £1.48, £1.70, £2.80, £2.99

EVERYDAY ELECTRONICS KIT PROJECTS

Ref	Price	Ref	Price
815 EE TREASURE HUNTER Aug 89	Full Kit £39.95	578 SPECTRUM I/O PORT less case Feb 87	£10.05
814 BAT DETECTOR Jun 89	£19.98	569 CAR ALARM Dec 86	£13.24
812 ULTRASONIC PET SCARER May 89	£13.80	563 200MHz DIG. FREQUENCY METER Nov 86	£67.98
807 MINI PSU Feb 89	£22.71	561 LIGHT RIDER LABEL BADGE Oct 86	£10.86
806 CONTINUITY TESTER Feb 89	£10.28	560 LIGHT RIDER DISCO VERSION	£20.89
803 REACTION TIMER Dec 88	£31.93	559 LIGHT RIDER 16 LED VERSION	£14.52
801 DOWNBEAT METRONOME Dec 88	£18.71	556 INFRA-RED BEAM ALARM Sept 86	£30.19
800 SPECTRUM EPROM PROGRAMMER Dec 88	£28.72	544 TILT ALARM July 86	£8.33
796 SEASHELL SYNTHESIZER Nov 88	£26.61	542 PERSONAL RADIO June 86	£12.28
795 I. R. OBJECT COUNTER Nov 88	£31.56	528 PA AMPLIFIER May 86	£28.70
790 EPROM ERASER Oct 88	£26.57	523 STEREO REVERB Apr 86	£28.16
786 UNIVERSAL NICAD CHARGER July 88	£7.44	513 BBC MIDI INTERFACE Mar 86	£29.76
780 CABLE & PIPE LOCATOR April 88	£16.35	512 MAINS TESTER & FUSE FINDER Mar 86	£9.39
775 ENVELOPE SHAPER Mar 88	£15.96	497 MUSICAL DOOR BELL Jan 86	£19.95
769 VARIABLE 25V-2A BENCH POWER SUPPLY Feb 88	£52.95	493 DIGITAL CAPACITANCE METER Dec 85	£44.25
763 AUDIO SIGNAL GENERATOR Dec 87	£14.53	481 SOLDERING IRON CONTROLLER Oct 85	£5.83
739 ACCENTED BEAT METRONOME Nov 87	£22.31	464 STEPPER MOTOR INTERFACE FOR THE BBC COMPUTER less case Aug 85	£8.95
740 ACCOUSTIC PROBE Nov 87 (less bolt & probe)	£18.85	1D35 STEPPER MOTOR EXTRA	£8.95
744 VIDEO CONTROLLER Oct 87	£31.03	OPTIONAL POWER SUPPLY PARTS	£5.47
745 TRANSTEST Oct 87	£10.33	461 CONTINUITY TESTER July 85	£6.60
734 AUTOMATIC PORCH LIGHT Oct 87	£18.29	455 ELECTRONIC DOORBELL June 85	£8.05
736 STATIC MONITOR Oct 87	£9.22	453 GRAPHIC EQUALISER June 85	£26.89
723 ELECTRONIC MULTIMETER Sept 87	£50.01	444 INSULATION TESTER Apr 85	£20.85
728 PERSONAL STEREO AMP Sept 87	£15.24	430 SPECTRUM AMPLIFIER Jan 85	£7.36
730 BURST-FIRE MAINS CONTROLLER Sept 87	£14.45	392 BBC MICRO AUDIO STORAGE SCOPE INTERFACE Nov 84	£38.61
724 SUPER SOUND ADAPTOR Aug 87	£40.89	387 MAINS CABLE DETECTOR Oct 84	£5.89
718 3 BAND 1.6-300MHz RADIO Aug 87	£28.25	386 DRILL SPEED CONTROLLER Oct 84	£9.24
719 BUCCANEER I.B. METAL DETECTOR inc. coils and case, less handle and hardware July 87	£28.17	362 VARICAP AM RADIO May 84	£14.00
720 DIGITAL COUNTER/FREQ METER (10MHz) inc. case July 87	£71.43	337 BIOLOGICAL AMPLIFIER Jan 84	£25.71
722 FERMOSTAT July 87	£12.93	263 BUZZ OFF Mar 83	£6.05
711 VISUAL GUITAR TUNER Jun 87	£24.48	242 INTERCOM no case July 82	£6.06
715 MINI DISCO LIGHT Jun 87	£13.41	240 EGG TIMER June 82	£7.31
707 EQUALIZER (IONISER) May 87	£16.54	205 SUSTAIN UNIT Oct 81	£18.78
700 ACTIVE I/R BURGLAR ALARM Mar 87	£37.97	108 IN SITU TRANSISTOR TESTER June 78	£10.03
581 VIDEO GUARD Feb 87	£8.94	106 WEIRD SOUND EFFECTS GEN Mar 78	£8.33
584 SPECTRUM SPEECH SYNTH. (no case) Feb 87	£22.28	101 ELECTRONIC DICE Mar 77	£6.67

INSULATION TESTER

EE APRIL '85

A reliable electronic tester which checks insulation resistance of wiring appliances etc., at 500 volts. The unit is battery powered simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. One of our own designs and extremely popular.

KIT REF 444

£20.85



PET SCARER

EE MAY '89

Produces high power ultrasound pulses. L.E.D. flashes to indicate power out-put and level. Battery powered (9V-12V or via Mains Adaptor).

KIT REF 812

Mains Adaptor £1.98

£13.80

DIGITAL CAPACITANCE METER

EE DEC '85

Simple and accurate (1%) measurement of capacitors from a few pF up to 1,000 μ F. Clear 5-digit LED display indicates exact value. Three ranges - pF, nF, and μ F. Just connect the capacitor, press the button and read the value.

KIT REF 493

£44.25


3 BAND SHORT WAVE RADIO

EE AUG '87

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

KIT REF 718

£28.25

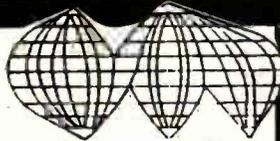

DIGITAL FREQUENCY 200 MHz METER

EE NOV '86

An 8 digit meter reading from AF up to 200 MHz in two ranges. Large 0.5" Red LED display. Ideal for AF and RF measurements. Amateur and C.B. frequencies.

KIT REF 563

£62.98

MOSFET VARIABLE BENCH 25V 2.5A POWER SUPPLY

EE FEB '88

A superb design giving 0.25V and 0-2.5A. Twin panel meters indicate Voltage and Current. Voltage is variable from zero to 25V. A Toroidal transformer MOSFET power output device, and Quad op-amp IC design give excellent performance.

KIT REF 769

£52.96



MINI STROBE

EE MAY '86

A hand held stroboscope which uses 6 "ultra bright" LEDs as the light source. Designed to demonstrate the principles of stroboscope examination, the unit is also suitable for measuring the speed of moving shafts etc. The flash rate control covers 170-20,000 RPM in two ranges.

KIT REF 529

£14.76

ACOUSTIC PROBE

EE NOV '87

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers and nosey parkers!

KIT REF 740

£18.65



MAINS TESTER & FUSE FINDER

EE MARCH '86

A handy unit which sounds an audible warning when the mains supply is disconnected and gives visual indication on three neon lamps of the connections to mains sockets. Designed for checking correct connections of mains wiring and for tracing which socket connects to which fuse in fusebox. Can detect no live, no neutral, no earth, L/N reversal, L/E reversal.

KIT REF 512

£9.39


EE EQUALISER

EE MAY '87

A mains powered ioniser with an output of negative ions that give a refreshing feeling to the surrounding atmosphere. Negligible current consumption and all-insulated construction ensure that the unit is safe and economical in use. Easy to build on a simple PCB.

KIT REF 707

£16.54

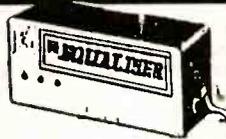

MUSICAL DOORBELL

EE JAN '86

This project uses a special I.C. pre-programmed with 25 tunes and 3 chimes. A Magenta design, the circuit is battery powered and only draws current whilst producing sounds. Two rotary switches select the tune required. Provision is made for three bell pushes, each of which sounds a different tune, so that three points of entry can be identified.

KIT REF 497

£19.95


VISUAL GUITAR INSTRUMENT TUNER

EE JUNE '87

Magenta designed with Quartz accuracy from a built in crystal. The guitar string frequency is compared with the reference to produce an output in the form of "rotating" circle of LEDs. Speed and direction of rotation indicates how far out of tune. Possible to tune other instruments by simple circuit modification.

KIT REF 711

£24.48

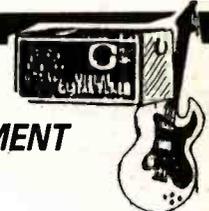

LIGHT RIDERS

EE OCT '86

Three projects under one title - all simulations of the Knight Rider lights from the TV series. The three are a lapel badge using six LEDs, a larger LED unit with 16 LEDs and a mains version capable of driving six main lamps totalling over 500 watts.

KIT REF 559 CHASER LIGHT

£14.52

KIT REF 560 DISCO LIGHTS

£20.89

KIT REF 561 LAPEL BADGE

£10.86

EE TREASURE HUNTER

EE AUG '89

A sensitive pulse induction Metal Detector. Picks up coins and rings etc., up to 20cms deep. Low "ground effect". Can be used with search-head underwater. Easy to use and build, kit includes search-head, handle, case, PCB and all parts as shown.

KIT REF 815

Headphones

£39.95

£1.99



STEPPING MOTOR INTERFACE

EE JULY '85

This interface enables 4 phase unpolar stepping motors to be driven from four output lines of any computer user port. The circuit is especially suitable for the ID35 motor and our MD200 which are commonly used in buggies and robot arms. Supplied complete with ribbon cable and connector for the BBC user port.

KIT REF 464

£8.95

KITS & COMPONENTS

ELECTRONIC GUARD DOG



One of the best burglar deterrents is a guard dog and this kit provides the barking. Can be connected to a doorbell, pressure mat or any other intruder detector and produces random threatening barks. All you need is a mains supply, intruder detector and a little time.

XX125 £24.00

DISCO LIGHTING KITS



DL8000K 8-way sequencer kit with built-in opto-isolated sound to light input. Only requires a box and control knob to complete. £34.60

DL1000K 4-way chaser features bi-directional sequence and dimming 1kW per channel. £21.00

DL21000K Uni-directional version of the above. Zero switching to reduce interference. £11.80

DLA/1 (for DL & DL21000K) Optional opto input allowing audio 'beat' / light response. 80p

DL3000K 3-channel sound to light kit, zero voltage switching, automatic level control and built-in mic. 1kW per channel. £17.00


POWER STROBE KIT

Produces an intense light pulse at a variable frequency of 1 to 15Hz. Includes high quality PCB, components, connectors, SWs strobe tube and assembly instructions. Supply: 240V ac. Size: 80x50x45.



XX124 STROBOSCOPE KIT. £15.00

VOICE RECORD/PLAYBACK KIT

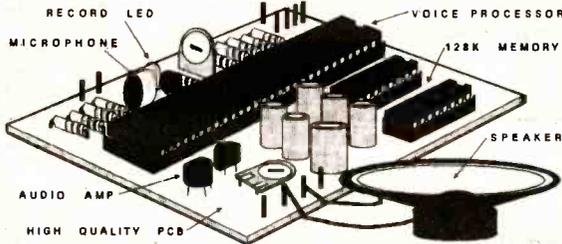

This simple to construct and even simpler to operate kit will record and playback short messages or tunes. It has many uses - seatbelt or lights reminder in the car, welcome messages to visitors at home or at work, warning messages in factories and public places, in fact anywhere where a spoken message is announced and which needs to be changed from time to time. Also suitable for toys - why not convert your daughter's £8 doll to an £80 talking doll!!

Size 78x60x15 mm
Message time 1-5 secs normal speed, 2-10 secs slow speed

XX129 £22.50

TEN EXCITING PROJECTS FOR BEGINNERS

This kit contains a solderless breadboard, components and a booklet with instructions to enable the absolute novice to build ten fascinating projects including a light operated switch, intercom, burglar alarm and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section on component identification and function is included, enabling the beginner to build the circuits with confidence.

XX118 £15.00

MULTIMETER BARGAINS

A high accuracy Autoranging meter with Display Hold, Memory features.

AC volts 0-2-200-750 1.2%

DC volts 0-0.2-2-200-1000 0.8%

AC current 0-2m-200mA 1.2% 0-10A 2%

DC current as for AC

Resistance. 0-200-2K-20K-200K-2M 1%

Continuity. Buzzer sounds at /20 ohms

Size 127x69x25mm

405 207 £31.75

A 15 range Autoranging multimeter with


4AC, 5DC and 6 resistance ranges. Only

8x55x108mm. Complete with wallet.

405 206 £19.50

Ask for a leaflet on our range of meters


ELECTRONIC WEIGHING SCALES

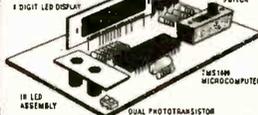

Kit contains a single chip microprocessor, PCB, displays and all electronics to produce a digital LED readout of weight in Kgs or Sts/lbs. A PCB link selects the scale - bathroom / two types of kitchen scales. A low cost digital ruler could also be made.

ES1 £7.20

SUPER-SENSITIVE MICROBUG

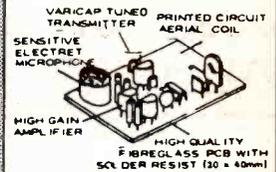

Only 45x25x15mm, including built-in mic. 88-100MHz (standard FM radio). Range approx. 300m depending on terrain. Powered by 9V PP3 (7mA). Ideal for surveillance, baby alarm etc. £5.50

VERSATILE REMOTE CONTROL KIT



Includes all components (+transformer) for a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can switch up to 16 items of equipment on or off remotely. Outputs may be latched to the last received code or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size (exc. transformer) 9x4x2 cms. Companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available - MK9 (4-way) and MK10 (16-way).

MK12 IR Receiver £17.00

MK18 Transmitter £7.80

MK9 4-way Keyboard £2.40

MK10 16-way Keyboard £7.00

601133 Box for Transmitter £2.60

SIMPLE KITS FOR BEGINNERS

Kits include all components (inc. speaker where used) and full instructions.

SK1 DOOR CHIME play a tune when activated by a pushbutton. £3.90

SK2 WHISTLE SWITCH switches a relay on and off in response to whistle command. £3.90

SK3 SOUND GENERATOR produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun. £3.90

SPECIAL OFFERS ON KITS FOR SCHOOLS AND TRAINING CENTRES - contact Sales Office for discounts and samples

ELECTRONIC LOCK KIT



Don't lock yourself out! This high security lock kit will secure doors to sheds, garages or your front door and the built-in alarm will deter would be prowlers. Scores of uses including area access preventing unauthorised use of machinery or even disabling your car. One correct 4 digit code (out of 5000) will open the lock. Incorrect entries sound the alarm and disable the keyboard for up to 3 mins. Kit includes 12-way keypad, and operates from 9 to 15V (50uA) supply. Will drive relay or 701 150 lock mechanism.

XX121
£15.95

MICROPROCESSOR TIMER

Kit controls 4 outputs independently switching on /off at 18 preset times over a 7-day cycle. LED display of time/day easily programmed. Includes box.

CT6000K £49.50

XX114 Relay kit for CT6000 includes PCB, connectors and one relay. Will accept up to 4 relays. 3A/240V c/o contacts £4.75

701115 Additional relays. £1.80

TK ELECTRONICS
13 Boston Road
London W7 3SJ
Tel: 01-567 8910
Fax: 01-566 1916

ORDERING INFORMATION All prices exclude VAT. Free p&p on orders over £50 (UK only), otherwise add £1+VAT. Overseas p&p: Europe £3.50 elsewhere £10.00. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 529314002. Local authority and export orders welcome. Goods by return subject to availability.



ORDERS: 01-5678910 24 HOURS

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

The Magazine for Electronic & Computer Projects
VOL. 18 No. 10 October '89

THE SEASON

This issue marks the start of another "season" of electronics. The schools and colleges are back, hobbyists are getting down to earnest construction work after the summer "sunshine" lay-off and many training schools and companies are launching a new set of recruits on their future careers.

It is always a busy time for us and a time when issues are bursting with extras. This year is no exception with the *Marco* catalogue free inside this issue and *Greenweld's* free with next month's issue. December will carry a free circuit board, together with a couple of projects you can build on it, and all these issues will have a bumper crop of projects, etc.

SNAPPED UP

I am sure all readers will find the catalogue particularly useful so please make sure your copy is ordered from your newsagent. It is inevitable that issues with catalogues and other extras are snapped up quickly and while we do print extras to meet the demand there can still be shortages in some areas.

If you do have difficulty in getting a copy please let us know, we can usually get our distributors to investigate. Our circulation is steadily rising and that can sometimes go unnoticed by newsagents who find themselves with a shortfall.

TEACH-IN

Another *Teach-In* book - No. 3 - is about to be published. This one is the complete *Exploring Electronics* series that appeared in *Everyday Electronics* some time ago. The 28 parts have been collected together into a single publication costing just £2.45. For anyone interested in "learning by doing" this publication is a must - watch out for it on the bookstalls on 22nd September.



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £15.70. Overseas: £19.00 (£36 airmail). Cheques or bank drafts (in £ sterling only) payable to Everyday Electronics and sent to EE Subscriptions Dept., 6 Church Street, Wimborne, Dorset BH21 1JH.



Subscriptions can only start with the next available issue. For back numbers see below.

BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS are available price £1.50 (£2.00 overseas surface mail—£ sterling only please) inclusive of postage and packing per copy. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. In the event of non-availability remittance will be returned. *Please allow 28 days for delivery. We have sold out of Sept. Oct. & Dec. 85, April, May, Oct. & Dec. 86, April, May & Nov. 87, Jan., March, April, June & Oct. 88.*

BINDERS

Binders to hold one volume (12 issues) are available from the above address for £4.95 (£6.95 to European countries and £9.00 to other countries, surface mail) inclusive of postage and packing. *Please allow 28 days for delivery. Payment in £ sterling only please.*

Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL,
6 CHURCH STREET, WIMBORNE,
DORSET BH21 1JH

Phone: Wimborne (0202) 881749

FAX: (0202) 841692

See notes on **Readers' Enquiries** below—we regret that lengthy technical enquiries cannot be answered over the telephone

Advertisement Offices

EVERYDAY ELECTRONICS ADVERTISEMENTS
HOLLAND WOOD HOUSE, CHURCH LANE,
GREAT HOLLAND, ESSEX CO13 0JS.
Frinton (0255) 850596

Editor MIKE KENWARD

Secretary PAMELA BROWN

Deputy Editor

DAVID BARRINGTON

Business Manager

DAVID J. LEAVER

Editorial: WIMBORNE (0202) 881749

Advertisement Manager

PETER J. MEW Frinton (0255) 850596.

Classified Advertisements

Wimborne (0202) 881749

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply **must** be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that **we cannot provide data or answer queries on projects that are more than five years old.**

ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should address them to the advertiser or should consult a local trading standards office, or a Citizen's Advice Bureau, or a solicitor.

TRANSMITTERS/BUGS/ TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the U.K. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.

EE SEISMOGRAPH



TONY HOPWOOD and ANDY FLIND Part One

Is this the first homebrew Seismograph? Watch for earthquakes and nuclear tests around the world.

QUITE A FEW months ago it was decided to build a seismograph and the following is the fruit of this dedicated labour.

There are few books on the subject, so building one turned out to be a voyage of discovery in a little travelled scientific backwater.

The theory is simple enough. A freely suspended mass will tend to remain still as the earth trembles under it, and the relative motion between the support frame and mass can be detected and recorded by mechanical or electronic means to give the profile of a seismic event.

There are two basic types of seismometer. Portable "velocity type" instruments designed to respond to vertical or transverse waves shorter than two seconds period, and longer period fixed instruments. The most spectacular traces are recorded by long period instruments which can detect the surface waves arriving from earthquakes anywhere on the planet, so that's what I built.

A seismometer tuned to over six seconds period has the big advantage of discriminating against short wave local disturbances like traffic, while still able to detect

the short sharp transients that signify the onset of a distant earthquake.

It was decided to build a "garden gate" type — a horizontal pendulum tuned to an eight second period, with the beam set North/South to be most sensitive to East/West transverse waves.

Short period instruments are usually electrodynamic with a moving magnetic mass exciting a fixed coil to convert seismic motion into voltage. As the period increases, this gets more difficult, and involves coils with thousands of turns of fine wire to give adequate signal as well as precision temperature compensated spring suspensions.

A simpler way is to use electronics to sense the deviation of a long period seismic beam from its mechanical null — so with the help of Andy Flind, an electronic pickoff system was developed which gave high sensitivity and stability without needing any precision mechanical fitting.

Construction is split between electronics and mechanics (to be described next month) and can be tackled in any order, although some thought should be given to the siting of what is rather a large instrument before final construction is started!

ELECTRONICS

The electronics of this project are designed to sense tiny movements of the Seismograph's main beam whilst imposing practically no friction. As well as being sensitive, the circuit needs good long-term stability, a feature not often required of d.i.y. circuits.

There are various transducers capable of detecting movement. The best known, the variable resistor, is unsuitable because of its high level of friction. Various optical and capacitive sensors, often used in industry, were rejected because they involve electro-mechanical "follower" mechanisms that would be difficult to make. Linear Hall-effect devices were considered, but they are expensive, their long-term drift characteristics were unclear, and they draw a fairly high operating current. The possibility of battery operation was considered desirable for this project.

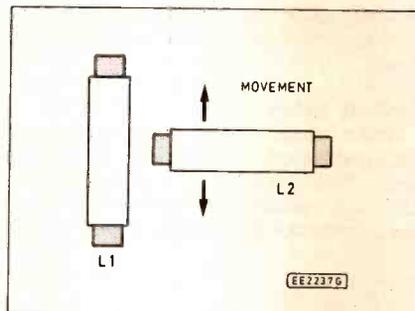


Fig. 1. Coil position and movement.


The system chosen uses two coils wound on short lengths of ferrite rod. One of these is energised with a sinewave current. The other is placed at right-angles about five to ten millimetres away from it, as shown in Fig. 1. If the coil positions are carefully adjusted, it is possible to find a "null" point where induced voltages in the second coil cancel to zero. Small displacements then result in output voltages, which are amplified and detected to indicate the movement.

As a bonus, the phase of the induced output depends on the direction of movement away from null. In one direction it is in phase with the energising signal, in the other, opposite to it. If a synchronous detector is used, driven by the oscillator, the direction of movement will be indicated by positive or negative output.

BLOCK DIAGRAM

A block diagram of the system is shown in Fig. 2. An oscillator drives one coil and a

Fig. 2. The electronics system block diagram for the EE Seismograph.

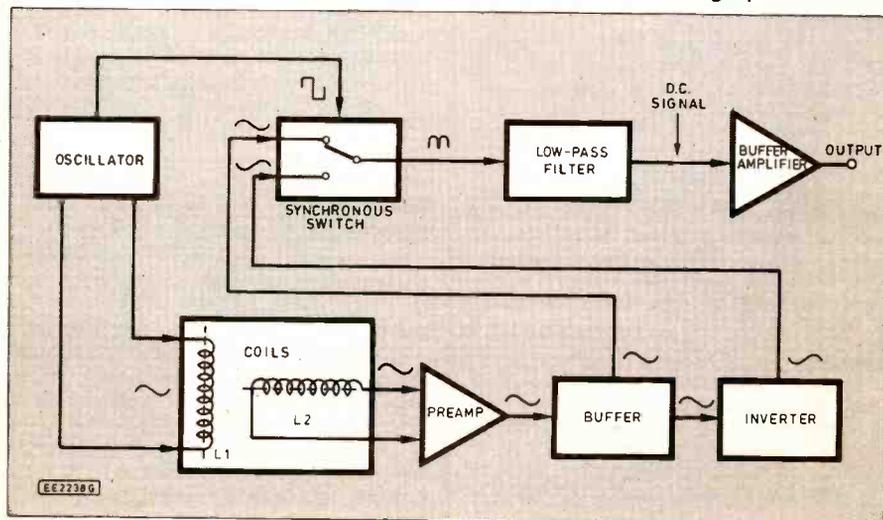

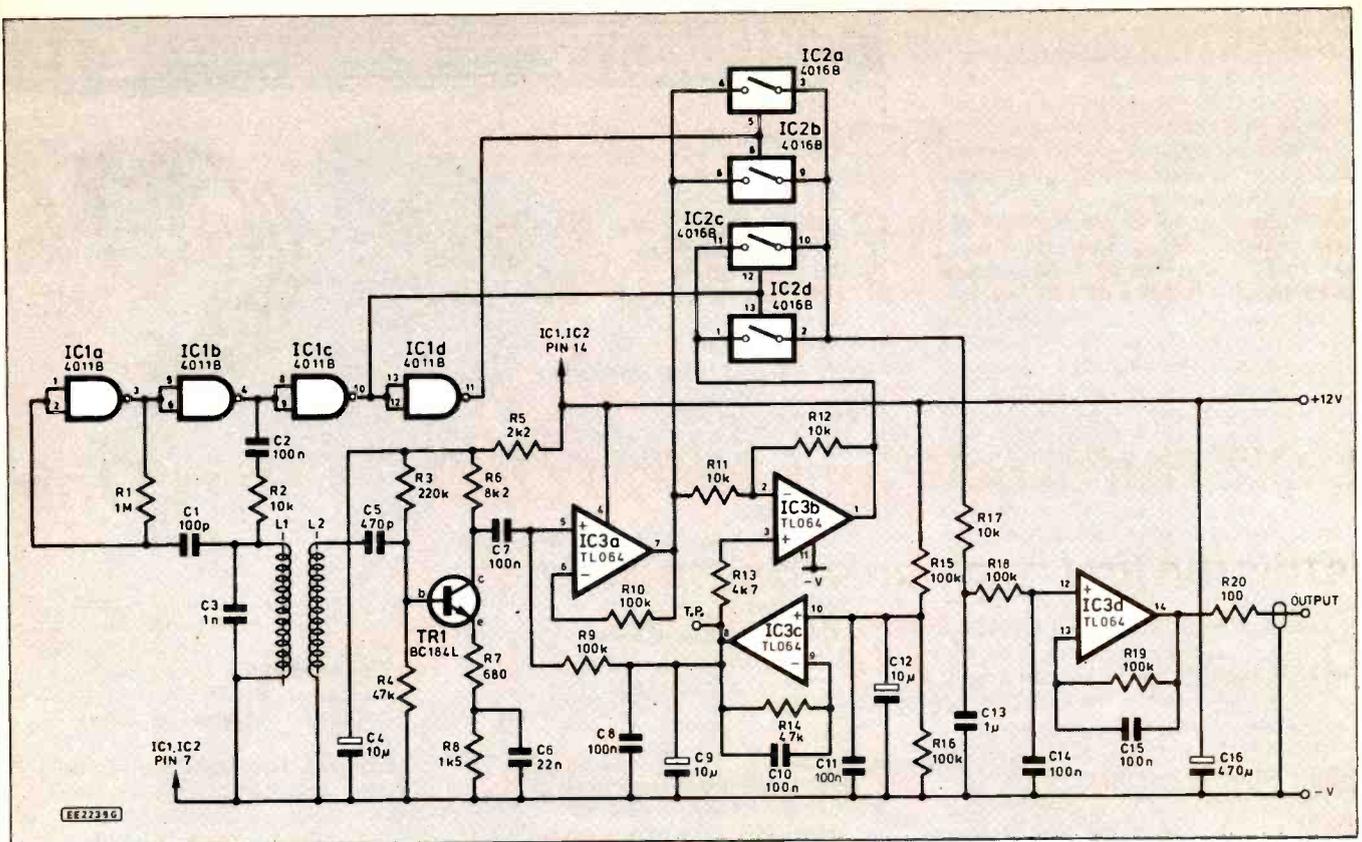


Fig. 3. Circuit diagram for the detector stage of the Seismograph. The coils L1, L2 are wound on ferrite rod and are interchangeable.

synchronous electronic switch. The output from the second coil is amplified, buffered and inverted before going to the switch.

The various signal waveforms in the circuit are shown, and it will be seen that the switch output is similar to that from a full-wave rectifier. The remaining a.c. component in this is removed by passive low-pass filtering, and a d.c. amplifier and buffer complete the circuit.

Whilst the effect is not completely linear it is good enough over the range of movement needed for the EE Siesmograph. It takes only a small energising current from a simple oscillator, is extremely sensitive, yet is easy to mount and set up. Careful design of the electronics provides good long-term stability. Additionally, it's cheap and easy to make.

Disadvantages? Well, the coil on the beam needs two wires to energise it, but these, if thin and placed close to the fulcrum, do not impair performance.

PRACTICALITIES

An instrument of this type is often sited some distance from occupied buildings to minimise disturbance and vibration from human activities. However, it would be useful to have the output available in the workshop or laboratory. With this in mind, the circuit is split into two sections, a "Detector" board for the Seismometer itself, and a "Control" unit, containing the power supply and output processing circuitry.

Connections between the two units consist of a single-ended low voltage supply, and one low-impedance signal lead that uses the negative supply as "common". This arrangement means that connections between the two can normally be made using the cheapest three-core cable available; screening and similar precautions are unlikely to be necessary.

CIRCUIT

In the detector circuit diagram, Fig. 3, the coil L1 is driven by a simple oscillator formed by two NAND gates IC1a and IC1b. The coils each have an inductance of about 2.5mH, so with C3, 1nF, the frequency is about 100kHz. This is low enough for simple processing but high enough for the characteristics of the ferrite. With L2 positioned as described, an output only appears when it moves away from the "null".


As the small movements to be detected produce small signals, TR1 provides voltage amplification of about ten. Its collec-

tor output is buffered and inverted by IC3a and IC3b. The two anti-phase signals from these go to an electronic two-way switch formed from IC2, a CMOS 4016B quad analogue switch, and the remaining two gates of IC1. The switch output is similar to that of a full-wave rectifier, but is positive or negative depending upon the phase of the input relative to that of the driving oscillator.

A d.c. reference of half the supply voltage is required for the op-amp stages of the circuit, this is supplied by IC3c and appears superimposed on the switch output. Simple low-pass filtering, R17, R18 and C13, C14, removes the high frequency component of the signal, leaving a d.c. output that is nominally half the supply but swings positive or negative with coil movements. This is buffered by IC3d for transmission to the control unit.

STABILITY

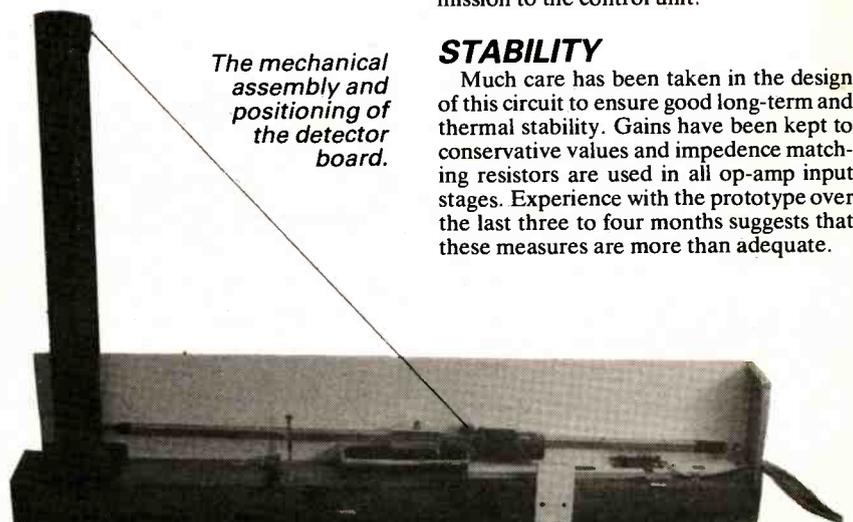Much care has been taken in the design of this circuit to ensure good long-term and thermal stability. Gains have been kept to conservative values and impedance matching resistors are used in all op-amp input stages. Experience with the prototype over the last three to four months suggests that these measures are more than adequate.



The mechanical assembly and positioning of the detector board.

SUPPLY

The "Control" part of the circuit, Fig. 4, provides a regulated supply for the detector and processes its output. A 12-0-12 volt 100mA transformer and bridge rectifier produces two supplies, positive and negative. These are regulated with three-terminal 100mA regulators IC1 and IC2 to give +12 volts and -5 volts relative to the "common rail". This rail is also the negative supply and common for the detector, and is intended to be earthed.

The purpose of the negative supply is to enable the output to swing below as well as above the earthed "common", since many chart recorders require such a signal. The signal processing part of the circuit begins with low-pass filter R9 and C11, which removes any noise induced in the connecting lead between the units, although the low output impedance of the detector unit should minimise such interference. The signal is then amplified by IC3b, a non-inverting amplifier with a voltage gain set at about two.

The other half of IC3 (IC3a) provides a reference voltage controlled by VR1 and VR2, "coarse" and "fine" zero adjusters. It will be recalled that the input is a voltage that varies about a nominal value of six volts; the effect of R7 is to shift the output downwards by six volts to swing about the "common" rail.


CONSTRUCTION

Construction can start with the Control unit, since the 12V supply will be needed for testing the detector. After ensuring that the board fits the slots of the moulded case, the transformer should be mounted on it. The holes for this are not provided as their spacing will vary with different makes of transformer. Its position can be seen from the layout Fig. 5, and the mounting screws should connect its metalwork to the large earthed area of copper on the p.c.b.

The bridge rectifier and 470 μ F capacitors C1 and C5 should be fitted, taking care with polarity, and the unit powered up. Since this implies connection to live mains, the usual precautions should be taken to avoid inadvertent personal contact!

A check should now reveal about 17

Fig. 4. Circuit diagram for the control stage of the Seismograph.

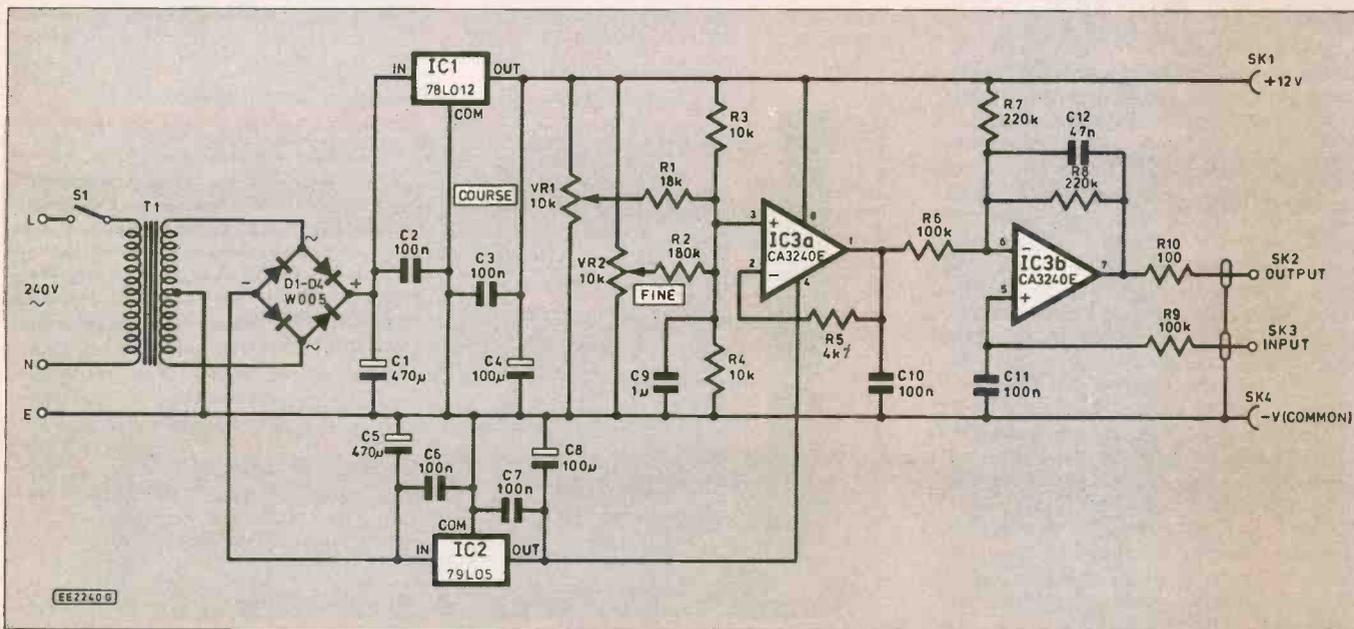

COMPONENTS

Approx. cost
Guidance only

£15

Control Unit

Resistors

R1	18k
R2	180k
R3, R4	10k (2 off)
R5	4.7k
R6, R9	100k (2 off)
R7, R8	220k (2 off)
R10	100

All 0.6W \pm 1% metal film type.

Potentiometers

VR1	10k lin. carbon
VR2	10k lin. carbon


Capacitors

C1, C5	470 μ radial elect. 35V (2 off)
C2, C3	100n polyester (6 off)
C6, C7	
C10, C11	
C4, C8	100 μ radial elect 25V (2 off)
C9	1 μ polyester
C12	47n polyester

Polyesters are miniature layer type.

Semiconductors

D1 to D4	W005 bridge rectifier, 50V 1.5A
IC1	78L012 12 volt 100mA positive regulator
IC2	79L05 5 volt 100mA negative regulator
IC3	CA3240E, dual op-amp, MOSFET inputs

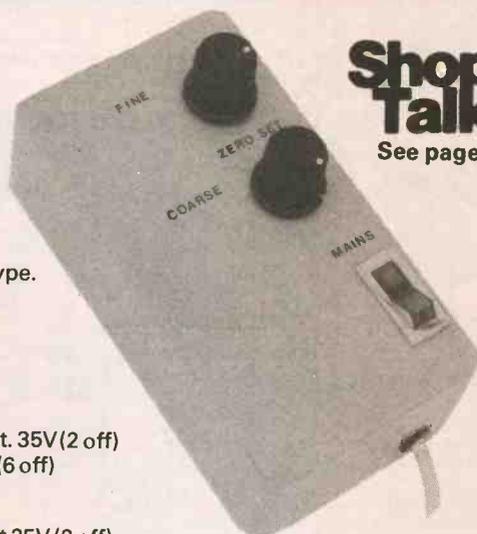

Shop
Talk

See page 636

Miscellaneous

SK1	4mm socket red.
SK2	4mm socket black.
SK3, SK4	phono sockets (2 off)
T1	Mains transformer 12-0-12V 100mA sec.
S1	SPST 240V toggle switch

Printed circuit board, available from the *EE PCB Service*, order code EE658; 8-pin d.i.l. socket; case, ABS plastic, 150 x 80 x 50mm; control knobs (2 off)

volts across each capacitor. If this seems OK, C2, C3, C4 and C6, C7, C8 should be added (with the power disconnected of course), with the regulators IC1 and IC2. Check the polarity of the two 100 μ F capacitors. If the unit is energised again, the 12 volt positive supply should now appear across C4 and the 5 volt negative across C8.

With the power supplies operating correctly, the remaining components can be fitted. A socket is recommended for IC3;

these cost only pence and make troubleshooting far simpler.

Resistors R1 and R2 are not mounted on the p.c.b. R6 sets the circuit gain. If it is desired to experiment with this, R6 may be mounted on Veropins for easy access, or even replaced by a variable component. The stage gain is given by R8/R6. With the value given, the sensitivity of the prototype was about 50mV per thou. (of an inch!) of movement when the coils were 5mm apart, half this at 10mm apart.



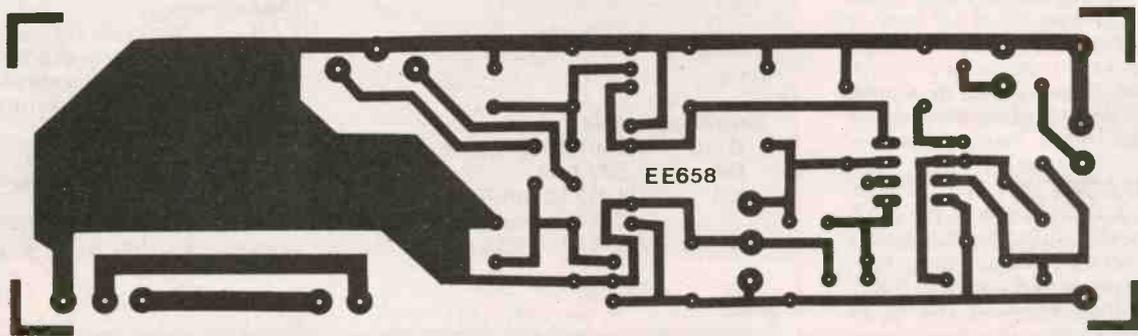
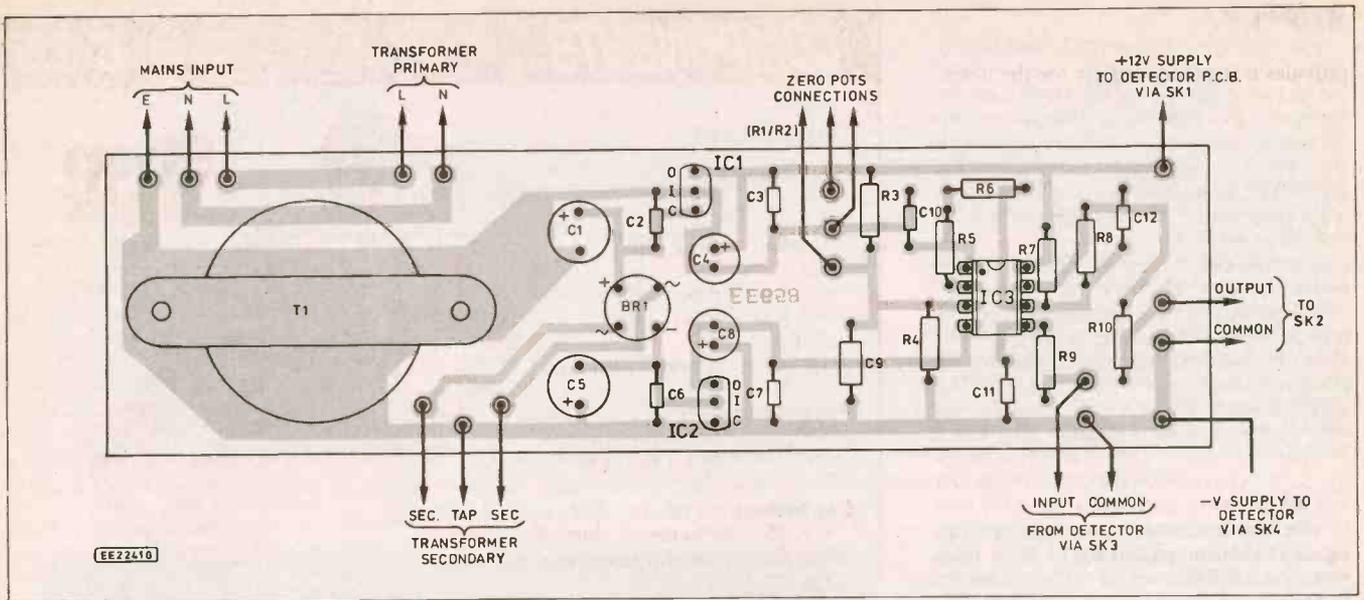
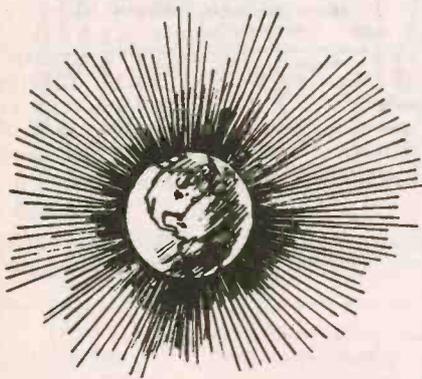


Fig. 5. Control unit printed circuit board component layout and full size copper foil master pattern. This board is available through the EE PCB Service, code EE658.

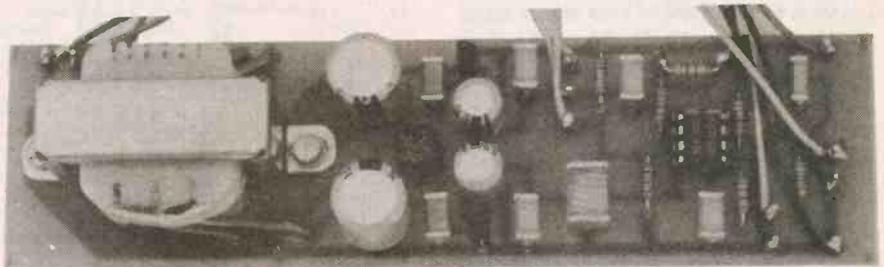


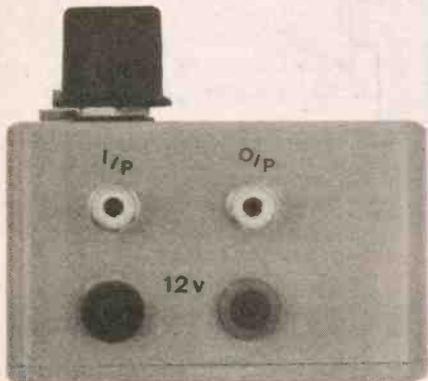The four input/output sockets on the side of the case.



Completed circuit board for the control unit.

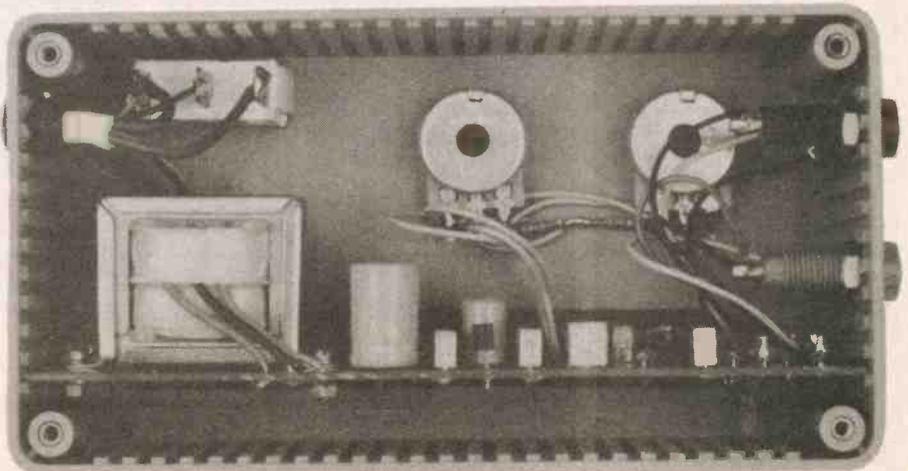The completed board slotted into the plastic case. Note the two resistors (R1, R2) wired directly to the two controls.



TESTING

The board is now ready for final testing. Two 10k resistors should be connected from the supply rails to the input as shown in Fig. 6., and one pot and the 18k resistor to the zero-setting connections. IC3 should be inserted. If the unit is energised and the output monitored, the pot should provide output adjustment of plus and minus 2.5 to 3.0 volts (2.8 on prototype).

A "wet finger" across one of the 10k resistors should produce movement in the appropriate direction and the 180k resistor across either should cause a shift of about 0.7 volt. A quick retest of the supply volts, +12V and -5V, and a check that nothing is overheating completes the job. The transformer and IC2 run slightly warm; this is normal.

COILS

The coils are needed to test the detector p.c.b., so these can be wound next. Each consists of 250 turns of 32 s.w.g. enamelled copper wire, layer-wound over 4cm of a 5cm length of ferrite rod. The ferrite is cut to length by notching around it with a fine-toothed file and snapping it. A layer of insulation tape keeps the wire from touching the ferrite.

Once wound, the wire must be secured to prevent movement, which would affect stability in this project. There are various ways to do this; for the prototype heat-shrink sleeving over each coil provided both security and protection to the windings, but a dip in potting resin might be even better. None of the coil dimensions is critical in any way, as only one coil is resonant and the frequency only has to be approximately correct.

DETECTOR BOARD

Construction of the detector board begins with the fitting of all components as shown in Fig. 7, save the three i.c.'s. Sockets should be used for these; they should not be inserted yet.

Following a careful physical check, including correct electrolytic polarity, the board can be powered with a 12 volt supply, still without i.c.'s. Following the usual electrolytic charging surge the supply current should settle to 0.6 to 0.7mA. Any significant variation from this value should be investigated before proceeding. Assuming it is correct, the voltage at TR1 collector should be about 6 volts above the negative

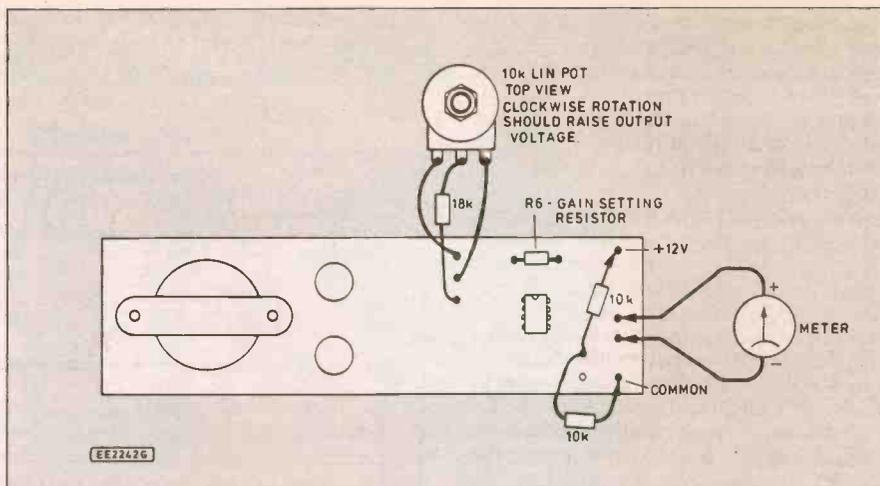


Fig. 6. Set-up for testing the control board.


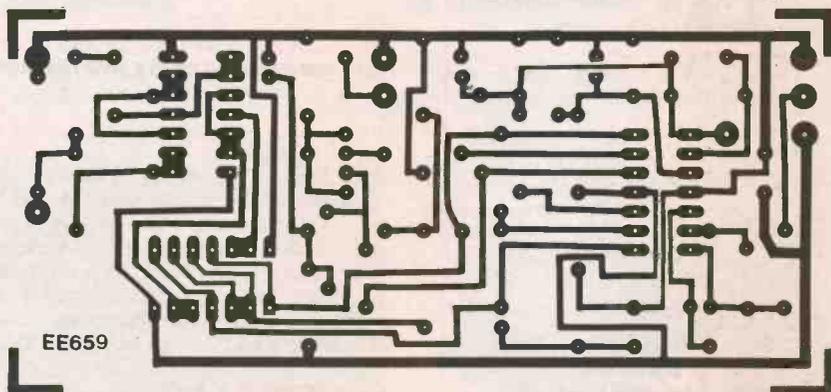
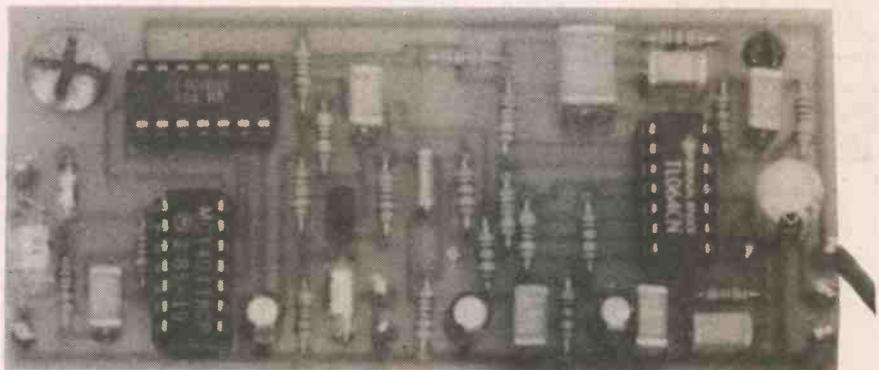


Fig. 7. Printed circuit board component layout and full size copper foil master pattern for the detector board. The completed board is shown in the photograph above.

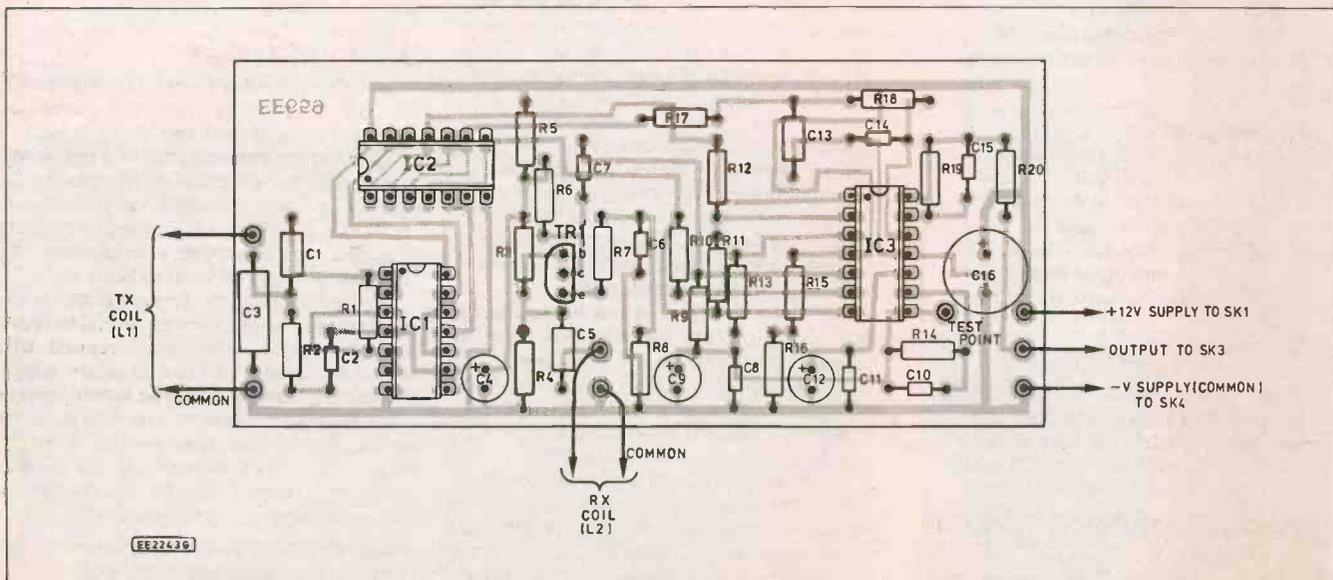

(common) supply. If so, IC1 should be inserted and the TX coil connected. This will push the supply current to around 1mA and the four output pins of IC1, pins 3, 4, 10 and 11, should appear to be at about 6 volts d.c. although in reality they will be switching from rail to rail at the operating frequency.

Next insert IC3. This will raise the supply current to about 1.8mA. The first three outputs, pins 1, 7 and 8, and the "test point" (driven from pin 8), should all be at 6 volts, set by divider R15 and R16. If so, IC2 can be inserted and the receiver coil L2 connected. The output should be monitored and the coils placed at right angles to each other, 5mm to 10mm apart. Careful adjustment of their relative positioning should locate a 6 volt output point, the "null".

Alternatively, the meter can be connected between the test point and output, where the null will give an output of zero volts with movement to either polarity. If the coils are around 5mm apart, a sideways

COMPONENTS

Detector Board

Resistors

R1	1M
R2, R11	10k (4 off)
R12, R17,	
R3	200k
R4, R14	47k (2 off)
R5	2k2
R6	8k2
R7	680
R8	1k5
R9, R10,	100k (6 off)
R15, R16,	
R18, R19	
R13	4k7
R20	100

All 0.6W \pm 1% metal film

Capacitors

C1	100p polystyrene
C2, C7	
C8, C10,	
C11, C14,	
C15	100n polyester (7 off)
C3	1n polystyrene
C4, C9,	10 μ radial elect. 50V
C12	(3 off)
C5	470p polystyrene
C6	22n polyester
C13	1 μ polyester
C16	470 μ radial elect. 16V

Polystyrenes are miniature layer type.

Semiconductors

TR1	BC184L npn silicon transistor
IC1	4011B CMOS quad NAND gate
IC2	4016B CMOS quad analogue switch
IC3	TL064 quad op-amp.

Miscellaneous

14-pin d.i.l. sockets (3 off); Vero pins; 8mm ferrite rod, 10cm length; 32 s.w.g. enamelled copper wire; heatshrink sleeve (see text); p.c.b. available from the EE PCB Service, order code EE659.

Approx. cost guidance only

£12

Shop Talk

See page 636

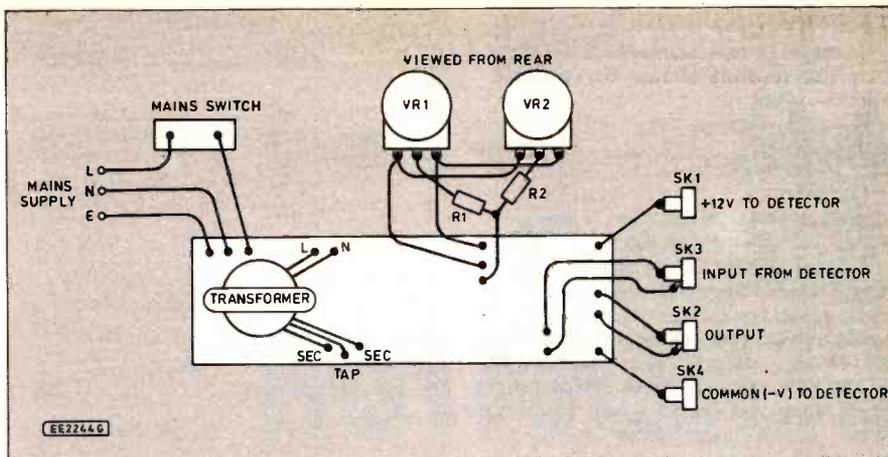


Fig. 8. Interwiring from the board to case mounted components.

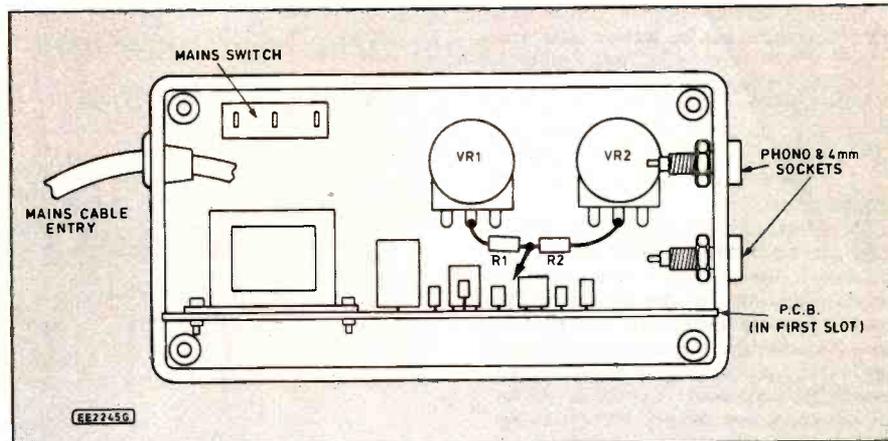


Fig. 9. Layout of components inside the control unit plastic case. Note the lead from the junction of the two resistors to the board.

movement of 2mm to 3mm should cause an output change of one volt, with polarity depending upon direction. The final current drain will vary slightly but should be about 1.8 to 1.9mA. This low supply current will allow long-term use from batteries if necessary, especially if the p.s.u. board is replaced with a circuit incorporating one of the new C-MOS micropower regulators such as the RS LP2951 or MAX666CPA.

HOUSING AND MOUNTING

The control and output board is housed in a 150x80x50 mm ABS plastic box with internal slots for the p.c.b. Input and output connections are made through phono sockets, whilst the 12 volt supply is available from red and black 4mm sockets. The "coarse" and "fine" zero adjusters and the mains switch are situated on top of the box. Wiring between these components is shown in Fig. 8. The prototype was not fitted with a mains fuse, it being felt that a 2amp plug fuse was sufficient. However a 100mA cartridge fuse could be incorporated into the case if preferred.

The detector board is not housed as in most cases it will be incorporated into the equipment with which it is to be used.

Setting up and use of the detector is straightforward as it is very tolerant of misalignment, much of which can be compensated for with the "zero" adjustment. The coils are not too sensitive to nearby metal, though obviously they should not be mounted hard against large structural metal components. In particular, any form of mounting that involves a complete metal

loop around either of the coils must be avoided as this would act as a "shorted turn" drawing much energy from the system. If twists of wire are used, they must be of insulated wires. Nylon cable ties would be fine, or perhaps glue.

For the Seismograph installation, it is best to install the transmitter coil L1 on the moving beam, with a twisted pair of thin wires connecting it to the p.c.b., with the flexing portion of these wires as close to the beam's fulcrum as possible. At this point it will have the least influence on the beam action. The receiver coil is best connected to the board with screened lead, kept as short as possible.

ADJUSTMENT

For correct adjustment a meter should be used to set up the detector, connected between output and the "test point". It should have a range of plus and minus one volt, and the coils should be adjusted for an output as close to zero as possible. If desired a 100-0-100 μ A meter can be fitted together with as suitable series resistor, say 10k, for continuous local indication.

In areas of high interference it may prove necessary to screen the signal lead between the two units. Two-core screened wire could be used, with the negative supply (common) connected to the screen and the 12 volt positive supply and signal to the cores. In most installations this shouldn't prove necessary though, simple 3-core cable or telephone wire, etc. should be adequate even over long distances.

Next Month: Mechanical assembly, setting-up and seismic recording.

I.C. SOUND GENERATOR

CHRIS BOWES



A very simple, low cost unit that uses the popular 555 timer i.c. and a single transistor for audio sound generation

THIS MONTH we introduce a simple I.C. Sound Generator circuit, which can be used either on its own or incorporated with other circuits in this series to provide an audible addition to a control or alarm circuit. Like all of the circuits in this series it can be operated from a single nine volt battery and may be mounted inside a case if this is desired.

The generator circuit uses a 555 timer in the standard astable mode. The basic circuit for this is shown in Fig. 1a. In this arrangement the i.c. produces an output at pin 3 (the i.c.s output connection) which repeatedly switches on and off in a timed sequence as shown in Fig. 1b. The duration of the on and off periods is governed by the values of R_A , R_B and C in the manner shown in Fig. 1b.

The output current from the 555 timer is not sufficiently high to enable the circuit to directly drive a loudspeaker so a single transistor is used as an emitter follower to provide the necessary current handling capacity.

CIRCUIT DESCRIPTION

The full circuit diagram for the I.C. Sound Generator is shown in Fig. 2. Basically the circuit consists of the 555 timer astable circuit shown in Fig. 1, with preset VR1 and resistor R1 taking the place of R_A and resistor R2 taking the place of R_B . Preset VR1 is included to enable the frequency of the output oscillation of IC1 to be adjusted so as to give the desired output tone and resistor R1 is included to provide a minimum resistance in the circuit and to prevent damage to the i.c. which would otherwise occur should VR1 be accidentally set to its zero value.

The frequency of the circuit's operation is determined by the values of VR1, R1, R2 and capacitor C1. With the components specified the operating frequency will be at approximately 1kHz. Capacitor C2 is required by the bipolar timer i.c. to set the control voltage level at pin 5 of IC1. If you use the CMOS version of the 555 timer then C2 may be omitted.

A simple emitter follower amplifier, formed by transistor TR1 and resistors R3, R4, is used to provide the current gain needed to drive the loudspeaker LS1.

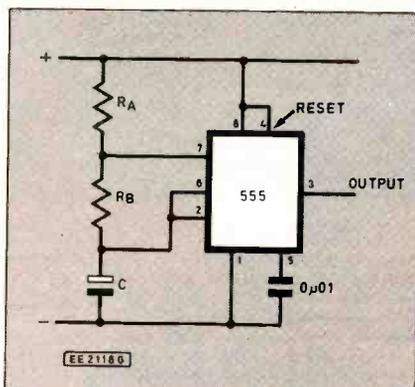


Fig. 1a. Using the 55 timer in the astable mode.

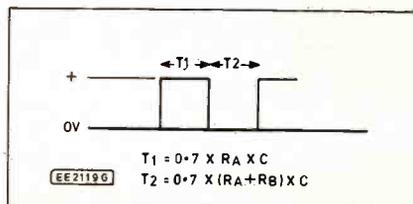


Fig. 1b. 555 timer astable timing diagram.

When a current flows through the base-emitter circuit of the transistor this allows a much higher current to flow through the collector-emitter circuit.

The emitter follower circuit makes use of the fact that the transistor's construction is such that the voltage between the base and emitter is maintained at 0.7V. When the voltage at the output (pin 3) of IC1 is at the 0V level then no current flows through TR1. When the voltage at pin 3 rises to the battery voltage then a current flows through the base-emitter circuit.

In order to maintain the base-emitter voltage at 0.7V the voltage across the loudspeaker consequently rises to approximately 0.7V less than the battery voltage. As the output from IC1 is constantly being switched on and off this causes the voltage across the loudspeaker to be switched on and off at the same frequency.

Resistor R3 is included in the base circuit of TR1 to ensure that the current flowing

through the base-emitter of the transistor is kept to a safe level. Similarly, resistor R4 is included in the collector of TR1 to restrict the maximum current flowing through the loudspeaker to a level which will prevent damage occurring.

CONSTRUCTION


The first task when commencing the construction of the I.C. Sound Generator is to cut a piece of stripboard 13 strips deep and 20 holes wide. If you are going to mount the project into a box by using p.c.b. stand-offs you will need to allow an extra six holes width (three each side) on the board for case mounting holes using a 4mm drill, make these mounting holes at the four corners of the board before starting to construct the circuit.

The component layout and details of breaks required on the underside copper tracks is shown in Fig. 3. It is important that these track breaks are made completely so that not even the merest sliver of copper remains to bridge across the track break.

Once the board has been prepared you can start the electronic construction. To help with this the strips and holes have been numbered and lettered, see Fig. 3.

Although it does not make any difference to the operation of the circuit which order you insert the components into the

Fig. 2. Complete circuit diagram for the I.C. Sound Generator.

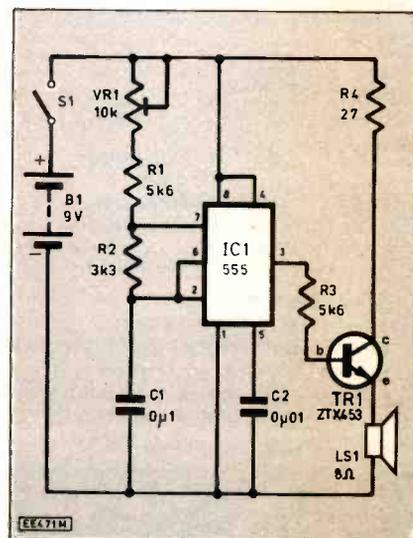

stripboard you will find it easier to construct the circuit if the components are inserted in ascending order of size. Commence by inserting and soldering the five link wires into place, as shown in Fig. 3. The wire links are made with insulated single-core wire and after soldering in place cut off any excess wire protruding on the underside of the board with your cutters.

The next task is to put the resistors in their correct places by first bending the wires of the resistor at right angles to the body of the component so that they will fit through the holes, as shown in Fig. 3. Counting across and down the board, using the numbers and letters as a guide, put all of the remaining resistors into their correct position and solder them into place. Also fit and solder preset VR1 into place.

The next item to be inserted into position is the i.c. holder. Although it is possible to solder the i.c. directly into place, using a socket will both make the construction simpler and make for easier replacement if a

The final step, prior to connecting the battery, is to insert IC1 into its holder making sure that the notch on the i.c. corresponds with the notch on the i.c. holder. Some versions of the 555 timer do not have a notch in one end but have a slight, circular dent near pin one. In this case the end with the indentation goes nearest to the edge of the i.c. holder which has the notch.

CASE

Although the project can be easily used as it stands or be incorporated into another project, you may wish to mount it into its own case. The easiest way to do this is to use self adhesive p.c.b. mounting strips as shown in the photographs.

Alternatively, you may use stand-offs in the position of the mounting holes previously drilled in the stripboard before making the circuit up. The requisite holes should be carefully marked on the body of the case and the appropriate stand-offs mounted in suitable positions to support

COMPONENTS

**Shop
Talk**

See page 636

Resistors

R1	5k.6
R2	3k.3
R3	1k
R4	27

All 0.25W 5% carbon

Potentiometer

VR1	250k min. skeleton preset, horiz.
-----	-----------------------------------

Capacitors

C1	0 μ 1 Mylar 16V
C2	0 μ 01 Mylar 16V

Semiconductors

TR1	ZTX453 npn silicon
IC1	NE555 bipolar timer

Miscellaneous

LS1	8 ohm loudspeaker
S1	Min. toggle switch (optional)
SK1	3.5mm switched jack socket (optional)
B1	9V (PP3 or equivalent) battery

Stripboard, 0.1in matrix 13 strips \times 20 holes (see text); plastic case to suit (optional); 8-pin i.c. socket; battery connector; connecting wire; solder etc.

Approx. cost
Guidance only

£7

the stripboard. Similarly suitable mounting holes must be drilled to accommodate the switch S1 and loudspeaker LS1.

In the version of this project shown in the photographs the loudspeaker is not provided with mounting holes so it was necessary to hold the loudspeaker against the case lid by means of a strip of material which spans the width of the loudspeaker and is held in place with two bolts which are accommodated in suitable holes drilled in

The completed board mounted in its case.

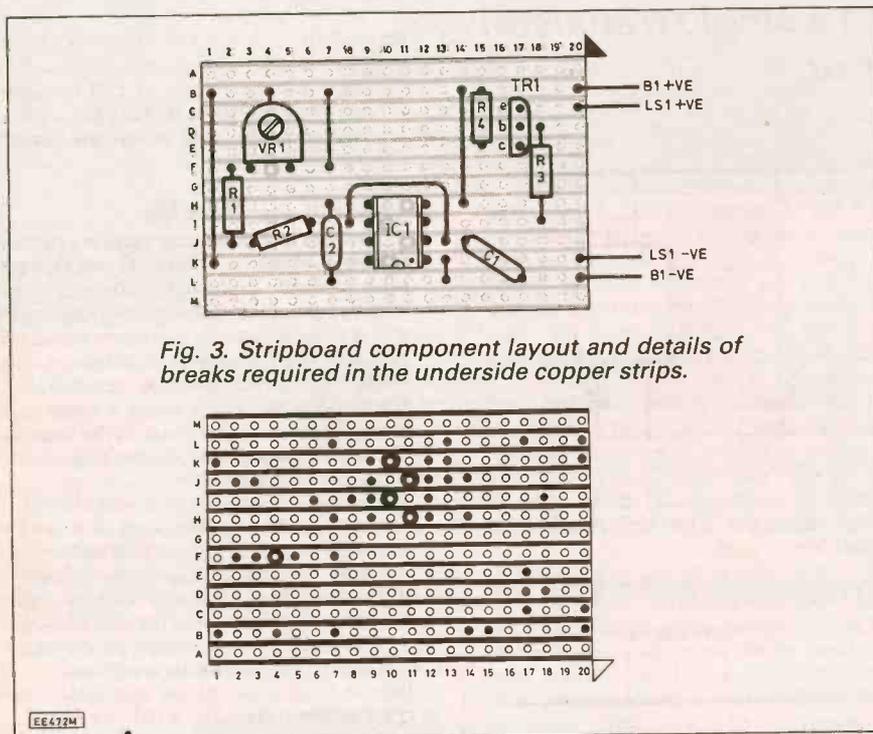


Fig. 3. Stripboard component layout and details of breaks required in the underside copper strips.


fault should occur. It is important that you take care to make sure that the notch on the i.c. holder is facing towards the bottom of the stripboard as this will help you when inserting the 555 timer into place.

Next come the capacitors which are both non polarised types so it does not matter which way round they are inserted. Finally insert transistor TR1 into the correct holes, making sure that it is orientated as shown in Fig. 3, and soldered into place.

INTERWIRING

The connecting wires to the battery can now be soldered into place on the board. The black wire from the battery connector goes to the point on the stripboard shown as B1 -V and the red wire of the battery connector goes to one tag of the on/off switch S1. Another red wire is then connected between the other switch terminal and the B1+V connection on the stripboard.

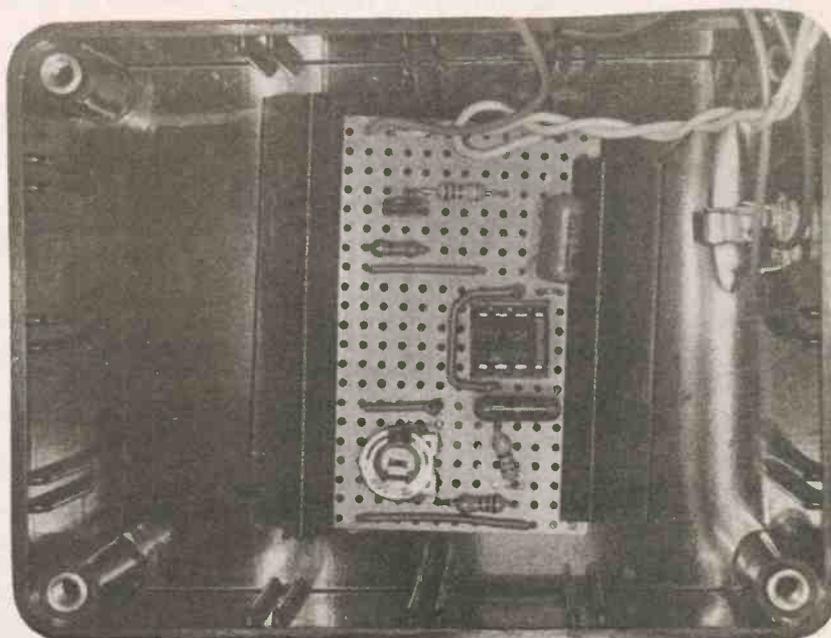Two wires should also be soldered to the loudspeaker and connected to the LS1+ and LS1- connection points on the stripboard.



the case. It will also be necessary to drill a matrix of holes in the lid to allow the sound from the loudspeaker to be transmitted.

In order to provide remote switching the case can be fitted with a small switched jack socket, which is mounted in the side of the case and wired in series with the battery and switch S1. If desired the switched socket can be wired in such a way that when the jack plug is removed the socket is shorted out — thus allowing the circuit to be controlled solely by S1 until the jack plug is inserted, when the circuit can then be controlled from the end of the cable connected to the jack plug.

When preparing the case all of the holes required should be drilled before installing the circuitry. Similarly if the case is to be painted or lettered this should be completed before the circuitry is installed.

TESTING

Before connecting the battery and testing the circuit you should carefully examine the stripboard to make sure that all of the components are inserted into their correct places, are the correct way round and that there are no blobs of solder shorting out the tracks.

If the circuit does not operate correctly it will be necessary to check for faults. In this project the only components which will cause problems if they are connected the wrong way round are IC1 and TR1.

If no mechanical problems are found then it will be necessary to check the circuit through to see whether there is a faulty component or not. You will probably find that you will need to use a test meter to perform this stage of the process.

Because of the high frequency of operation of this circuit fault finding with a test meter can be somewhat difficult. However, the process can be made easier by temporarily connecting a capacitor of between 22 μ F and 100 μ F in parallel with capacitor C1. This will cause the output frequency of the circuit to be slowed down to a level where the operation of the circuit can be easily measured. Fault finding then becomes much easier.

You should be able to measure the battery voltage between any 0 volt connection and both pins 8 and 4 of IC1 as well as between the Battery+ connection to the board and pin 1 of IC1. If these voltages are not present this will indicate faulty wiring up of the stripboard.

The next step is to check the voltage at the output (pin 3) of IC1. If the circuit is

working correctly this voltage should be regularly switching between 0 volts and the battery voltage.

If this does not occur and the output is locked permanently at a fixed voltage then you should remove the i.c. from its socket and check the voltage at the pin 3 connection again. If the voltage persists with IC1 removed then the fault does not lie with IC1 but most possibly with the wiring associated with the i.c. and the output or its associated wiring.

Replace the i.c. and check the voltages at pins 2, 6 and 7. The voltage at pin 7 should be fluctuating around a value which is roughly $\frac{2}{3}$ of the battery voltage. The voltages at pins 2 and 6 should be identical (because these two pins are connected together by a wire link) and these should also be fluctuating in a similar manner, but at a voltage slightly less than that found at pin 7.

If neither or only one of these voltages are present then the most likely cause is that the circuit from the positive voltage rail, through preset VR1, resistors R1 and R2 is not correctly made. This is best checked by measuring the voltage present between 0V and each junction in the component chain through VR1, R1, R2 and capacitor C1 and investigating at the point where no voltage is measured.


If a voltage is present between 0V and pin 7 but no voltage, or only a very small voltage, is measured between the 0V rail and pins 2 or 6 of IC1 then you should check that the resistance between pins 7 and 6 of IC1 is roughly equal that of resistor R2. If this is correct then check the resistance of capacitor C1 with the resistance range of your meter.

If the resistance is very low (less than about 500 ohms) then you should replace capacitor C1. If there is no voltage measurable between pins 6 and 2 of IC1 then this could be caused by a short circuit between the connections of C1 or by a short circuit within C1.

OUTPUT STAGE

If the voltage switching described above is taking place then the i.c. and its associated components are working correctly and the fault will most probably lie in the area of transistor TR1 and its associated components. The first point to check is the junction of resistor R3 and the base of TR1.

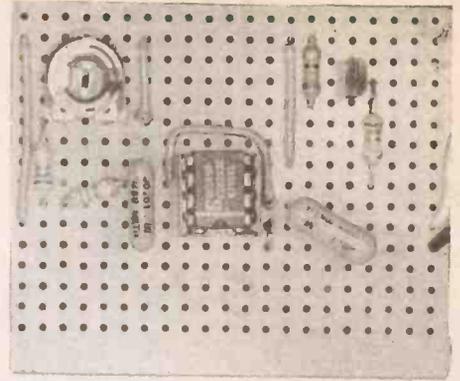The voltage at this point should fluctuate between 0 volts and almost full battery vol-



The completed circuit board showing the five link wires.

tage, in time with the fluctuations in the output of IC1. If this is happening then you should be able to measure a similar voltage change at the junction of the emitter of TR1 and the loudspeaker LS1.

The voltages between 0V and the emitter and collector of TR1 should both be measured. The voltage at the emitter should rise and fall, following the fluctuations of the output from IC1. If the voltage at the emitter does not rise and fall but stays at 0V then the connections to the loudspeaker should be checked out.


If the voltage remains locked at a level approaching the battery voltage, then the transistor should be checked for correct function by removing it from the circuit and measuring the resistance between the base and emitter and the base and collector. It is important to measure these resistances with *both* polarities of the meter current.

Because of the construction of the transistor a high resistance should be measurable between the base and the other connections, with the base connected to one of the meter leads, and a low resistance should be measurable between the base and the emitter or collector, with the base of the transistor connected to the other lead of the meter. If the resistances measured do not match the expected results then the transistor should be substituted for a new one.


SETTING UP



Once construction and testing are complete the circuit can be very easily set up by installing the battery, switching the circuit on and adjusting preset VR1 until a sound at the desired pitch is heard. □

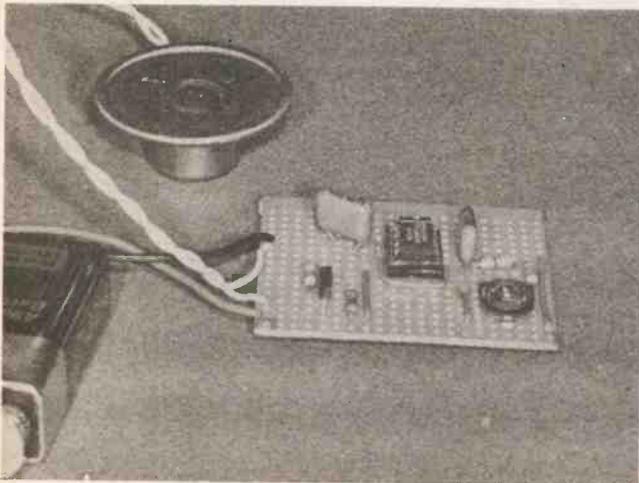The completed board wired to the loudspeaker and battery prior to mounting in the case.



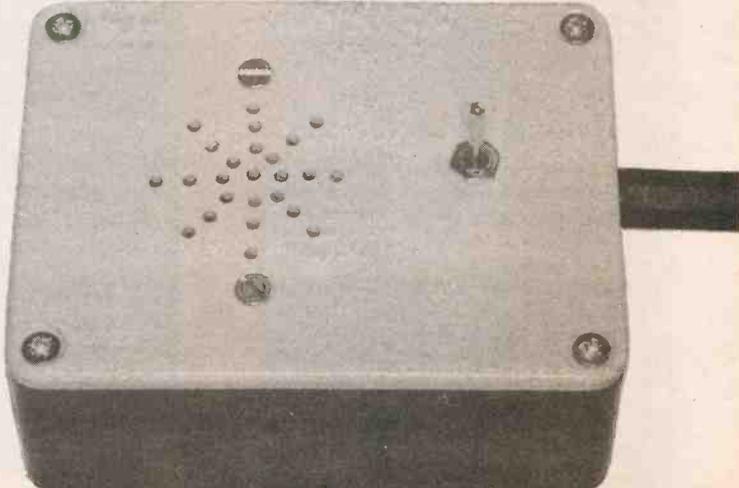The completed unit showing the matrix of holes above the speaker, the optional switch and jack plug.



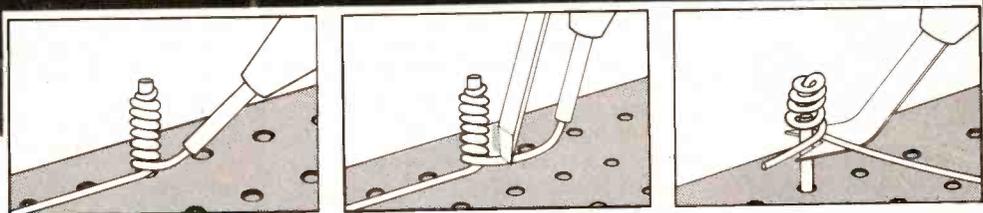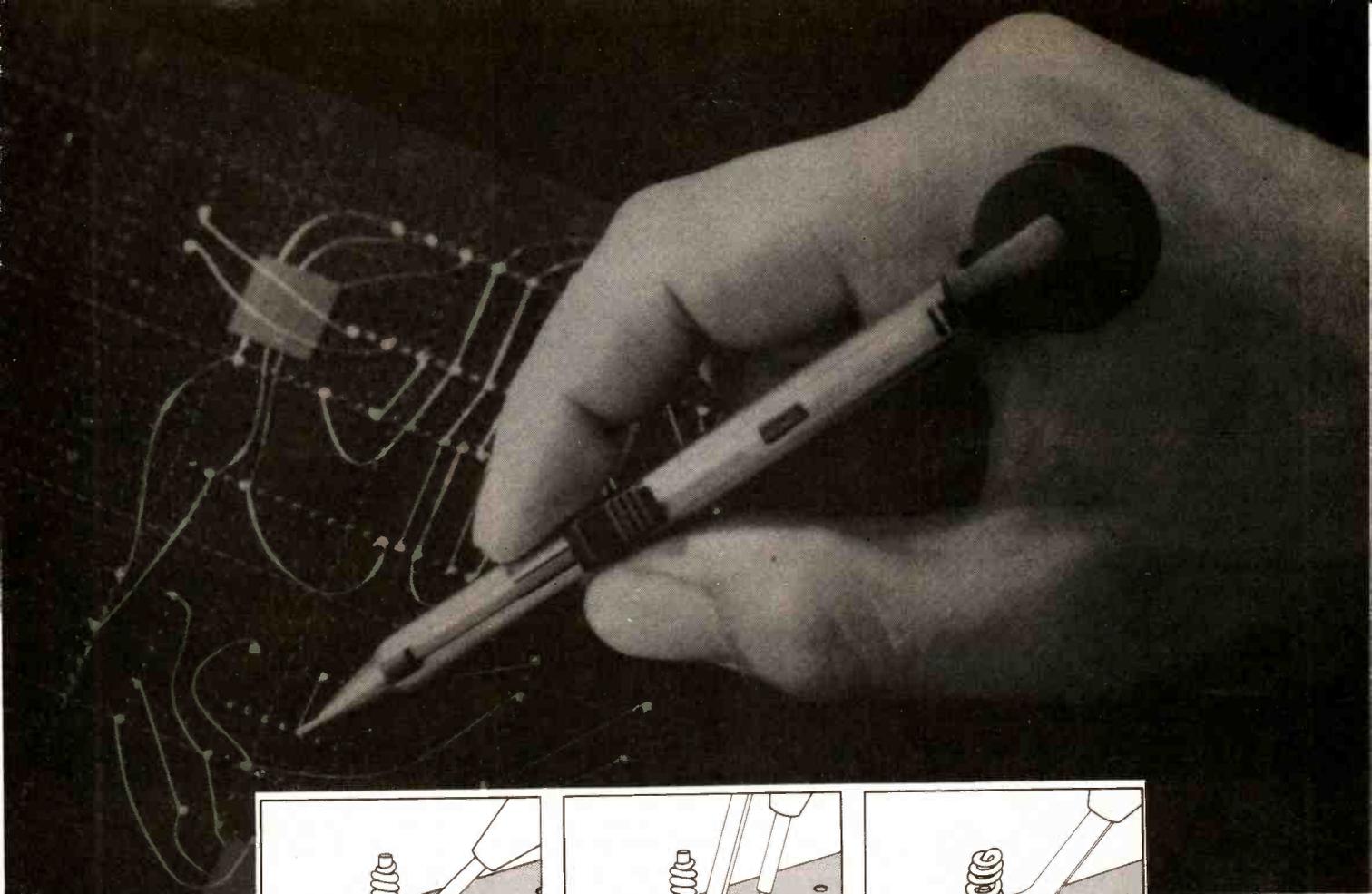

EASIWIRE

Circuit construction the easy way.

Solderless, quick and easy to learn. That's Circuigraph Easiwire from BICC-VERO. From now on you'll wonder why you ever used solder to construct your electronic circuits!

Consider the benefits Easiwire offers:

- You need no solder, no chemicals
- You simply wind the circuit wire around the pins
- You can re-use components
- It's easy to change
- The cost is low

What's more, Easiwire is ideal for circuit repairs. In kit form, Easiwire comes complete with everything you need to construct circuits. That includes a wiring pen with integral cutter, two reels of wire, a component positioning and removal tool – and an instruction book. Of course kit items are available separately too.



Take advantage of the special offer price now. Complete the coupon below and send it to:

BICC-VERO Electronics Limited,
Flanders Road,
Hedge End,
Southampton, SO3 3LG.

or phone 0489 788774 now with your credit card number (24-hour answering service)



Please rush me.....Easiwire kits.
Special offer price £15. – (includes p & p and VAT).
I enclose cheque/postal order for
made payable to BICC-VERO Electronics Limited.

Card number

Expiry date


Name

Address

.....Postcode

Signature.....Date

SHOP TALK

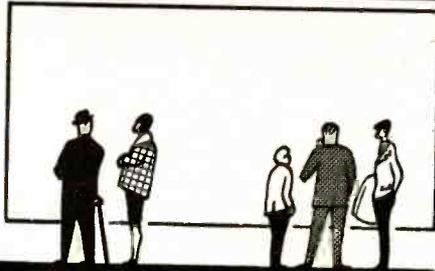

BY DAVID BARRINGTON

Newcomer

With the new season now in full swing, it is time to take stock and replenish the "component store". One item that often gets overlooked, but should be considered a top priority is updating the collection of components catalogues.

One catalogue that should be added to the list is the latest from **Jidenco**. Calling upon their vast experience in selling to the trade, their first venture into Mail Order for the constructor contains over 100-pages, is printed on top quality paper and is lavishly illustrated with photographs of stock items.

The stock of opto-devices, including i.e.d.s and seven-segment displays is quite extensive. The relay section is also fairly far ranging. Amongst other items that caught the eye, is a range of surface mount devices (SMD's).

Copies of the catalogue cost £1.50 and is available direct from Jidenco. The catalogue contains discount vouchers redeemable as follows: 50p off £5 plus orders; £1 off £10 plus orders; £5 off £50 plus orders. **Jidenco CD, Jidenco House, Dept EE, Vale Road, Windsor, Berks, SL4 5JW.**

EE Seismograph

Readers should not experience too many difficulties when purchasing components for the "electronics" section of the *EE Seismograph*. The "hardware" or mechanical requirements for the project will be highlighted next month.

The ferrite rod required for the "detector" coils seems to come in various diameters and lengths and may prove a little difficult to source locally. The range varies from about 8mm to 12mm diameter and 100mm to 200mm length.

It is quite feasible that the "null point" can be pinpointed on all the various combinations of ferrite rod and the most popular size stocked appears to be the 10mm diameter by approximately 140mm length. Ferrite rods are currently listed by **Magenta, Maplin, Cirket, Omni, TK Electronics and Greenweld.**

If you have to cut down the length of a rod, be extremely careful as ferrite is very brittle. It is suggested that readers follow the details for cutting the rod, contained in the article, to the letter.

Logo Lego and Spectrum

The 74LS series of i.c.s called for in the *Logo Lego and Spectrum* project are very common devices and should not

present any purchasing problems. Most of the other components for this project are also standard off-the-shelf items.

However, the 6V miniature relays may prove a little difficult to locate locally. The ones in the prototype model were ordered through Maplin and are listed under their "Ultra Miniature" range, code FM91Y (Ult-Mn Relay 6V SPDT).

Other relays can be used provided they have contacts rated at 2A and a coil resistance of about 100 ohms. The contact ratings will, of course, depend upon the type of load and application required.

The Spectrum edge connector and the Darlington driver, type ULN2803A, are now quite common devices and stocked by most component advertisers. The printed circuit board for this project is available from the *EE PCB Service*, code EE660.

Readers experiencing any difficulty in obtaining Lego kits can contact them direct at **Lego UK Ltd., Dept EE, Wrexham, Clwyd, LL13 7TQ.** We also understand that **Magenta Electronics** (☎0283 65435) are a recognised stockist of Lego kits and should be able to obtain most parts.

Stabilized Power Supplies

Of the components required for the 700mA version of the *Variable Stabilized Power Supply*, the mains transformer selected by the designer was specially wound by the **Trent Coil Winding Co.** Quote order code 00493 (£10.25 plus £2.55 post and packing).

Many of our advertisers now supply special transformer kits for making up your own mains transformers. With these kits you just select the secondary requirements and, referring to a table, wind on the necessary number of turns. Alternatively, specialist transformer suppliers such as **Jaytee Electronic Services** should be able to come up with a suitable unit.

The printed circuit board for the 700mA version is available from the *EE PCB Service*, code EE656 (see page 684).

Turning our attention to the 1A 30V *Variable Stabilized Power Supply*, the author has again selected from the Trent mains transformers. The one specified is the 00494 (£10.25 plus £2.55 p&p) used in a previous project and can be obtained from Trent Coil Winding Co., Dept EE, 26 Derby Road, Long Eaton, Notts.

The only source to date that we have been able to locate for the large, moving

coil, panel meter (110mm x 83mm) used in the prototype models is from **Maplin**. This is listed under their "Large Meters" section, code RX54J (50µA Large Pan Meter). The Q-type quoted by the designer was the listing title adopted by Electrovalue, however we have been informed that all their stocks of the Q45 are exhausted and not likely to be replaced (i.e. discontinued).

The smaller T-type alternative meter suggested is also an Electrovalue designation. But, in this case, the 60mm x 46mm is stocked by most of our component supplier advertisers. The meter resistance does differ and you will have to recalculate the meter resistors accordingly.

As there are numerous equipment cases on the market, the final choice is left to the individual constructor. It should be an all metal type and be able to take the weight of the mains transformer and have plenty of room for the heatsink/circuit board.

The printed circuit board for the 30V Variable Stabilized Power Supply is obtainable through the *EE PCB Service*, code EE657 (see page 684).

Music on Hold

The melodies generator chip UM34811A appears to be the only item that could possibly cause sourcing problems to constructors of the *Music on Hold* project. This is a 16-pin multi-instrument melody i.c. which has a 512-note memory and is capable of generating up to 16 tunes.

Looking through our library of components catalogues, this device appears to be only listed by Maplin. This should be ordered as code, UJ44X (UM34811A).

Be sure to specify the lever type when ordering the microswitch. The small printed circuit board is available from the *EE PCB Service*, code EE646 (see page 684).

Simple L.E.D. Timer

We do not expect any component buying problems for readers undertaking the *Simple L.E.D. Timer*, one of this month's pocket money projects.

There are two popular CMOS versions of the standard 555 timer i.c. stocked by practically all our component advertisers and either of these should work in this circuit. The two devices in question are designated IC7555 and TLC555C and are completely pin for pin compatible with the bipolar 555 timer.

The bargraph type i.e.d. display is now quite a common unit and should be stocked by most good component suppliers, although it may prove a bit cheaper to purchase individual standard i.e.d.s. The 6V-12V solid state buzzer is another item that is stocked, in many versions, by most advertisers.

I.C. Sound Generator

We cannot foresee any component sourcing problems for readers constructing the *I.C. Sound Generator*, this month's "pocket money" project.

The self-adhesive stand-off insulator strips or "feet" for mounting the circuit board in the case should be generally available. No doubt readers will have their own ideas about mounting the board in the case.

HART

HART AUDIO KITS

— YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI



Yes, you too can afford the very best in real Hi-fi equipment by building a HART kit. With a HART kit you can avoid the hilarious prices and magical claims of the 'oxygen free grain oriented copper' brigade and the flashy exterior and mundane interior of the mass market products. With every HART kit you get the benefit of circuit design by world leaders in their field, men of the calibre of John Linsley Hood for instance who has been in the forefront of audio design for many years. This circuit expertise is harnessed to realise its full potential by HART engineering standards which have been famous in the kit field since 1961. The HART approach is simply to give you the best value in Hi-fi by combining the best circuit concepts with the latest and best components within a unit carefully designed to bring out your hidden skills as an equipment builder.

Units in the HART audio range are carefully designed to form matched stacks of identically sized cases, in many cases even the control pitches are also lined up from unit to unit for a cohesive look to your customised ensemble.

Flagship of our range, and the ideal powerhouse for your ultimate system is the new AUDIO DESIGN 80 WATT POWER AMPLIFIER, described in the May issue of 'Electronics Today International'. This complete stereo power amplifier has so many features that you really need our list to browse through them all. Glossing over its technical merits, which its pedigree guarantees anyway, it is a power amp with the extra versatility of a built-in passive input stage giving three switched inputs, volume and balance controls. Tape or CD players may, therefore, be directly connected along with a standard pre-amp output, indeed your system may not need a preamp at all with the well balanced output of competent CD players.

Send for our new FREE Spring '89 List. It has full information on this new amplifier as well as details of improvements to other kits in our range.

Our 300 SERIES amplifiers for instance now feature optional Phono input sockets and double size LCR power supply capacitors. The 400 SERIES John Linsley Hood Audiophile Tuner range now incorporates the very latest updated stereo decoder circuit which can also be retro-fitted to existing tuners with our 'Tuner Enhancement Package'.

Also listed are many exciting new products for the serious audiophile such as our Gold plated phono and XLR plugs and sockets and ultimate quality connection leads for CD audio or digital signals.

ALPS PRECISION LOW-NOISE STEREO POTS

Just arrived in stock. Exciting new range of precision audio pots in values to cover most quality amplifier applications. All in 2-gang stereo format, with 20mm long 6mm dia. steel shafts.


Throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability.

Values available are 10K and 100K Log, 100K lin and 10K Special Balance. (Zero loss in centre position). Our prices are incredibly low for pots of this quality due to large purchases for our quality kits.

2-Gang Lin £6.30
2-Gang Log £7.20
2-Gang Special Balance, zero crosstalk and zero centre loss £7.80

We are so impressed with these new controls that we will include them in the passive input stage of our new 80 watt power amplifier kits AT NO EXTRA CHARGE until November 1989.

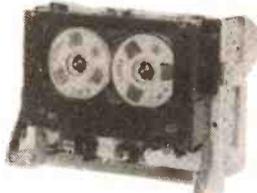SOLENOID CONTROLLED FRONT LOAD CASSETTE DECK TN3600



High quality (0.08%W&F) successor to our very popular SF925F. A very useful high quality cassette mechanism for domestic or industrial use. Offers all standard facilities plus cue and revue modes all under remote, logic or software control. The power and control requirements are very simple with 12V solenoids and 12V Motor with built in speed control. Deck is supplied as standard fitted with a very nice 10kHz R/P head and a 1.5mH erase head.

TN3600 Deck with stereo head £48.53
INF340 Full manufacturers data £2.90

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HS16 Sendust Alloy Stereo Head. High quality head with excellent frequency response and hyperbolic face for good tape contact. £17.86
HC40 NEW RANGE High Beta Permalloy Stereo head. Modern space saver design gives excellent high-frequency response with easy fitting and lower cost. Suitable for chrome, metal and ferric tapes, truly a universal replacement head, with ample quality for Hi Fi decks and cheap enough for car players! £6.65
HX100 Special Offer Stereo Permalloy Head £2.86
HRP373 Downstream Monitor Stereo Combination Head £44.39
HQ551 4-Track Record & Play Permalloy Head for auto-reverse car players or quadraphonic recording £16.79
HS24 Standard Erase Head £2.59
SM166 2/2 AC Erase Head, Standard Mount £12.60
HS9510 2/4 Stereo DC Erase Head £8.70
HQ751E 4/4 AC Erase Head, tracks compatible with HQ551 £57.06
We can supply card reader heads for OEMs at very keen prices.

REEL TO REEL HEADS

999R 2/4 Record/Play 110mH. Suits Stuart tape Circuits £13.34
998E 2/4 Erase Head 1mH. Universal Mount. Suits Stuart £11.96

TAPE RECORDER CARE PRODUCTS

HART TC1 TEST CASSETTE Our famous triple purpose test cassette. Sets tape azimuth, VU level and tape speed £5.36
DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation £4.08
DEM115 Electronic, Cassette Type, demagnetizer £8.61
Our new SPRING '89 List is FREE. Send for your copy now. Overseas customers welcome, please send 2 IRCs to cover surface post, or 5 for Airmail.

Please add part cost of carriage and insurance as follows:-

INLAND
Orders up to £10—£1
Orders £10 to £49—£1.50
Orders over £50—£2.50
Express Courier—£9

OVERSEAS
Please see
the ordering
information
with our lists.

QUALITY AUDIO KITS

24hr SALES LINE
(0691) 652894

ALL PRICES INCLUDE VAT

HART
HART ELECTRONIC KITS LTD
6 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 9AF

CONQUERING NEW HEIGHTS



CROTECH 3133

- ★ Component Comparator
- ★ Variable Hold Off
- ★ Triple DC Source
- ★ DC - 25 MHz
- ★ 40ns/div
- ★ 2mV/div
- ★ Low Cost *

Full 2 Year Warranty

£299*

To scale the heights, just call us for your FREE copy of our catalogue



*(Ex VAT & Delivery)

Crotech Instruments Limited

2 Stephenson Road, St. Ives, Huntingdon, Cambs. PE17 4WJ
Telephone: (0480) 301818

Yes its 25MHz for £299

CAR ELECTRONIC IGNITION SYSTEMS

STEWART ROBERTSON



“You know about electronics what’s up with my car?” You reply, “Well, er, you see” pregnant pause, “I don’t know—gulp—in fact I don’t know anything about electronic ignitions.” How embarrassing. Well it was when it happened to the author. Having read *Everyday Electronics* religiously every month, he still didn’t know the answers.

THE FOLLOWING article sets out to redress the balance in the reader’s favour. You’ll need something in your favour because there are very few cars made these days with standard ignition systems. So let’s start at the beginning.

INDUCTANCE

If you apply a voltage to an inductor the current doesn’t instantaneously rise to a maximum but grows relatively slowly. The actual rate of growth is dependant on the applied voltage and the resistance and inductance of the circuit.

What happens is the growth of current is resisted by a voltage (called back e.m.f.) which is induced in the inductor. Similarly when a steady current is switched off the inductor opposes that change by producing an e.m.f. which tries to maintain the flow of current.

Now e.m.f.s are voltages, so by getting current to flow through a coil and then switching the current off we can generate a voltage. Which if the inductance is large the resistance low and the rate of switch-off quick can be quite a high voltage.

TRANSFORMERS

This high voltage can be stepped up to say 40kV if we use the transformer action by winding another coil of many turns around the inductor. This is essentially the action of a *coil* in a conventional ignition system.

The current is switched on and off by the contact breaker points in the distributor. The rotor arm and distributor cap are used to direct the high voltage to the correct spark plug. See Fig. 1.

HOW IT WORKS

Let’s just go over the circuit in case we have to find any faults in it. The source of supply is the car battery which, by a heavy duty cable, normally connects to the starter solenoid. The solenoid terminal is used to feed current to the ignition switch, which in turn feeds the coil positive (+) terminal.

Current flows to Earth (car chassis) through the coil if the contact breaker points are closed. When the points open a high voltage is induced and there is a capacitor connected across the points to reduce arcing and enhance the effect.

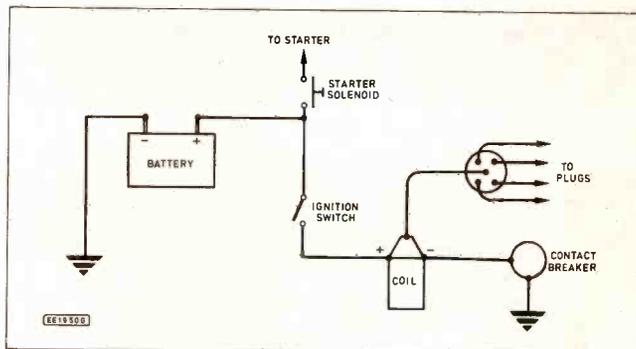


Fig. 1a. Conventional c.b. ignition system.

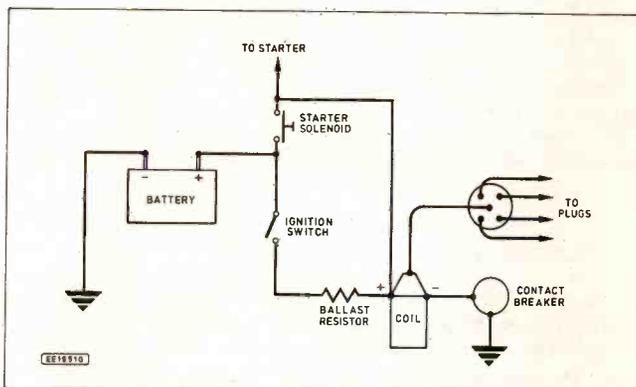


Fig. 1b. Conventional ignition system with an in-circuit current limiting “ballast” resistor.

High voltages leave the coil by the thick lead (lots of insulation) which goes to the distributor. Typical coil primary resistance is three ohms and maximum current in the region of four amps.

This system is called the "Kettering" system after Charles Kettering who invented it. It works O.K. provided the spark is made to occur when the respective cylinder is just before-top-dead-centre (BTDC). This can usually be adjusted by rotating the distributor in its mounting and is called "timing" the ignition.

SPARK ADVANCE SYSTEMS

Unfortunately there are some mechanical add-ons to enhance performance (anything mechanical is unfortunate). One of these add-ons is to advance the spark so that it occurs earlier at high engine revolutions.

This is known as the "centrifugal advance system" and is a quaint collection of bob weights and springs buried in the bottom of the distributor. As the revs increase it rotates the cam of the contact breaker points a few degrees in the direction of rotation, thus the spark occurs earlier.

Similarly the base plate is rotated by another system which advances the spark only on light throttle openings. This is an economy device which is activated by a vacuum capsule on the side of the distributor.

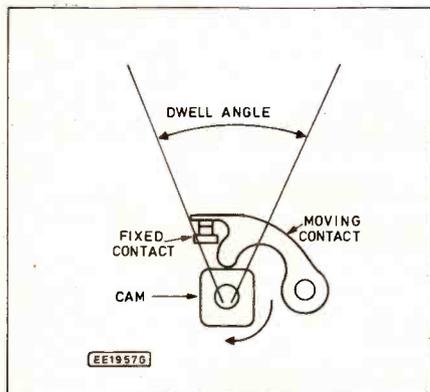


Fig. 2. Dwell angle or "dwell time" is the period the contacts are closed.

LIMITATIONS

The Contact Breaker system was invented by Charles Kettering in 1908. Although he was undoubtedly a far-seeing man (he later became head of General Motors) it is not surprising that we are now able to improve on his invention.

The areas most in need of improvement are to be found in the low voltage section of the distributor.

Points

The points are a switch which when closed allows current to flow in the coil. The size of the voltage that is generated by the coil is directly proportional to the SPEED that the points open and the AMOUNT of current that the coil carries.

Both speed and amount of current are limited by the size of the points set. A large set could carry more current but would not open so quickly or alternatively a small set would open quickly but not be able to carry the current. A modern points set is a compromise.

Dwell

The time that the coil has to store energy is determined by the time the points are closed and is known as the "dwell time". At high engine speeds the dwell time is very short and can become inadequate leading to misfiring and certainly to inadequate combustion and loss of power and economy. This occurs because the dwell time is controlled by a fixed dwell angle of cam rotation. See Fig. 2.

Maintenance

Arcing at the points surface erodes the metal and adjustment is lost. The cam follower also wears and contributes to loss of gap.

Adequate gap to prevent arcing and maintain dwell angle is gradually lost and needs to be restored every 5000 miles or so. If emissions and economy are to be maintained even more frequent adjustment is called for.

Timing

All timing operations are controlled mechanically. They are therefore subject to friction, wear and general lack of accuracy. Low emission, high performance and good economy all rely upon accurate timing.

C.B. IGNITION ENHANCEMENTS

Ballast Resistor

The current carried by the coil is forced through by the voltage applied by the battery. Unfortunately, when cranking from cold the battery does not provide as high a voltage. A solution is to provide a coil which has a resistance of only 1.5 ohm so that at the reduced voltage it will still draw about 4A of current.

However, when the engine is running, 12V to 14V will be available and so an extra resistance ("ballast resistor") is connected into the circuit to limit the current to the 4A required. See Fig. 1b. This system aids starting.

Sliding Points

When the points arc, they are eroded; if the arcing can be spread over a larger area it will take longer to erode the points and service intervals can be extended. The more recent Minis have an example of how to achieve this.

As the points open the base plate and cam follower are arranged so that the points surfaces slide across each other and spread the

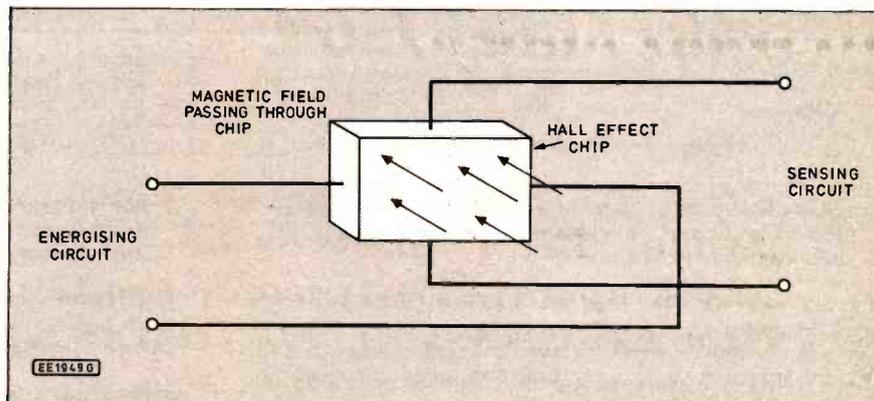


Fig. 3. Basic action of the Hall effect device. A magnetic field from a magnet is broken by a rotating disc and induces an energising pulse in the device.

erosion over a greater area. This is claimed to increase service intervals to 12,000 miles.

TRANSISTOR ASSISTED IGNITION

So far in our view of ignition systems it's implied that the improvements have been to increase the maintenance period and improve economy. But there is now an even greater pressure on the manufacturers to reduce emissions. Rich mixtures of fuel and air produce a lot of nasty by-products but they do ignite easily. Modern engines run on lean mixtures—some very lean indeed.

To make sure the air/fuel mixture ignites properly it requires a high energy spark and a high voltage. The ordinary C.B. ignition systems are not always able to manage this, particularly at high engine speeds, so transistor assisted systems were introduced.

The energy stored in a coil is equal to $\frac{1}{2}LI^2$ where L =the inductance and I =the current. It is clear that if the current is doubled the energy available is four fold. Unfortunately the points are already over burdened—if they were made larger to carry more current they would have too much inertia to handle the revs.

But by the use of transistors (usually a Darlington Pair) large currents can be controlled quite easily and additionally the current can be switched very fast and with no arcing. Triggering of the transistors can be by contact breaker points or by some device which requires less maintenance.

ADVANTAGES

Large currents mean high energy, similarly fast switching speeds mean high voltage generation—this gives reliable firing when cranking and at high engine speeds. Dwell angle is less critical. Points sets, if used, carry only small currents and therefore last longer without adjustment.

Switching is clean, no arcing, so timing is more accurate. Also the effects of points bounce can be eliminated which ensures more accurate timing.

Overall the result is a car which starts more reliably, produces more power and is more drivable when cold and needs less choke. This is bound to improve emissions and fuel economy.

HOW TO RECOGNISE

This type of system has now been superseded but was normally housed in a module attached to the side of the distributor or

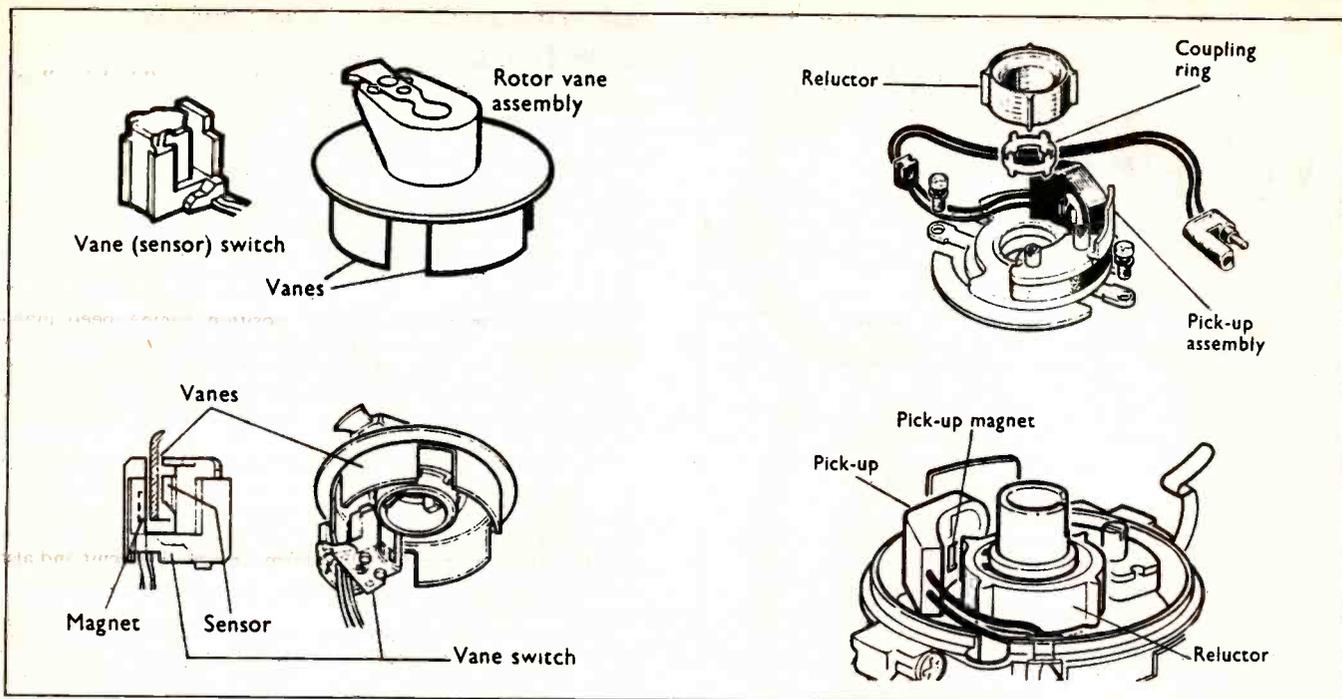


Fig. 4. Hall effect arrangement. (a) Vane switch (or sensor) and rotor vane assembly. (b) Interaction of rotor vane and vane sensor.

Fig. 5. Early distributor reluctor system arrangement. (a) Reluctor and pick-up assembly. (b) Reluctor tooth and pick-up alignment.

attached to the coil. The coils have a low primary resistance of about three-quarters of an ohm.

Any system which is electronic but still uses the points is likely to be of this type. The modules are commonly called "amplifiers" or "igniters".

IGNITION TRIGGERING SYSTEMS

Contact points are mechanical switches; because they are mechanical they wear and need regular adjustment. They also bounce when they open and close at high speed, this can affect the accuracy of their timing.

ALTERNATIVES

With transistor ignition systems it is no longer necessary to rely on the points to perform the triggering function. With only a little more circuitry it is possible to trigger them with sensors which have no moving parts.

Early systems sometimes used photo-electric light sensors which produced a pulse when masked from a light source by a revolving disc. These were perfectly satisfactory but modern practice is to use a magnetic sensor and two systems now predominate.

Hall Effect

Modern semi-conductor technology has produced a device which when placed in a magnetic field deflects an electric current and is called a "Hall Effect" device. See Fig. 3.

The actual arrangement is to fix a Hall Effect chip in a distributor so that a flanged disc rotating on the distributor shaft masks it from a magnet. Slots in the flange allow the magnetism to reach the Hall Effect device when the trigger pulse is required.

The Hall Effect chip is supplied with current and at the correct moment a trigger pulse appears on the output connection which is fed to the control module. No adjustment should ever be required. See Fig. 4.

Reluctor Systems

When a magnetic circuit is broken any coil in that circuit will experience an induced voltage. This voltage can be used to trigger a transistor ignition system. If a toothed wheel is part of the magnetic circuit then the circuit will be interrupted when a tooth is not in alignment with a pole piece.

An early method was to put the toothed wheel into a distributor and this has the advantage of being able to utilise the centrifugal advance and the vacuum advance systems. The disadvantages are that distributor bearings wear, gear backlash and the mechanical advance systems still produce some inaccuracy. See Fig. 5.

A more recent method is to put the toothed wheel on the flywheel where there is no backlash or possibility of drive gear wear. Additionally extra teeth can be provided so that engine

speed can be sensed by the same sensor. However, alternative systems are then required to replace the vacuum and centrifugal advance. See Fig. 2.

ADVANTAGES

Accurate ignition timing from a no-maintenance system which once set should not need adjustment.

CONSTANT ENERGY IGNITION

It takes time between each spark for the current and hence the magnetic field in the coil to grow to its maximum. If the coil does not reach full capacity it will not generate its full output and will be unable to ignite weak mixtures and misfiring can occur.

Certainly incomplete combustion leading to poor power and high emissions do occur. This is particularly the case with high revving engines and 6, 8 and 12 cylinder units.

There are numerous solutions to this problem but because electronics are relatively cheap it is common to find combined systems. The commonest are described below:

Electronic Dwell Control

Dwell period is related to the angle that the cam in the distributor rotates through while the points are closed. This is called "dwell angle" and is usually about 50 degrees on a contact breaker system (see Fig. 2).

If dwell angle is increased at high revs, there will be an increase in dwell *period* compared with a fixed dwell angle system. This is easy to arrange if electronic triggering is in use. The increased period allows the coil time to reach its maximum current flow and hence maximum energy storage.

The reduced dwell at low revs, reduces current consumption and heating of the coil.

Constant Current Operation

With constant current operation the coil resistance is made so low (0.80 ohm) that the coil current rises to its maximum even in the short time available at high revs. The constant current circuitry prevents it from rising too high in the longer periods available at low revs.

STATIONARY ENGINE CUT-OFF

Both the above systems employ a circuit which cuts off current to the coil when the engine is stationary. This is essential as otherwise the coil would overheat with the high current (as high as about 18A) which could flow if the ignition were left on.

These systems optimise the ignition system so that regardless of engine speed, battery voltage, starting or high revs, the engine is provided with a powerful and consistently timed spark. And yet at low revs, or when stationary, components are protected from excessive heat and power is not wasted.

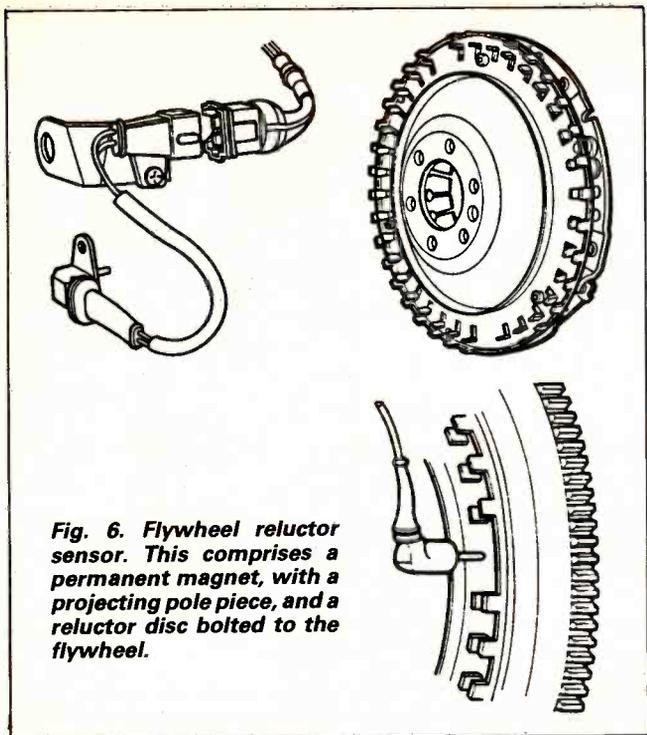


Fig. 6. Flywheel reluctor sensor. This comprises a permanent magnet, with a projecting pole piece, and a reluctor disc bolted to the flywheel.

HOW TO RECOGNISE

Most modular electronic ignition systems now incorporate all or some of the previously mentioned techniques. These systems are usually housed in packs which are attached to the side of distributors or on the bulkhead with the coil.

However, note they still use the mechanical vacuum and centrifugal advance mechanisms so there is still a distributor-like casing driven by the cam-belt or camshaft. Only in the programmed ignition systems is the distributor eliminated (except for cap and rotor arm).

PROGRAMMED IGNITION

Transistor ignition systems with a conventional distributor using centrifugal advance and vacuum advance do not completely meet the requirements of modern engines in modern operating environments.

Distributor systems sense engine load by the use of manifold depression. This is arranged to mechanically vary the rotation of the distributor. Apart from the usual difficulties associated with mechanical control systems such as friction, wear and backlash; there is a limitation in the range of different amounts of advance which can be accommodated. See Fig. 7.

Similarly centrifugal (bob weight) advance systems mentioned previously have all the mechanical disadvantages mentioned and can provide only two stages of advance. Finally mechanical systems have no facility for the input of additional information such as engine temperature.

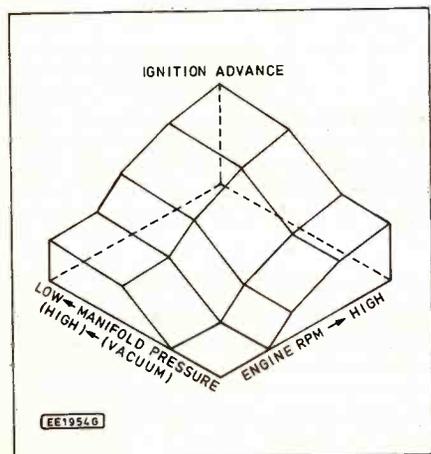


Fig. 7. Ignition or "engine" map using the distributor system.

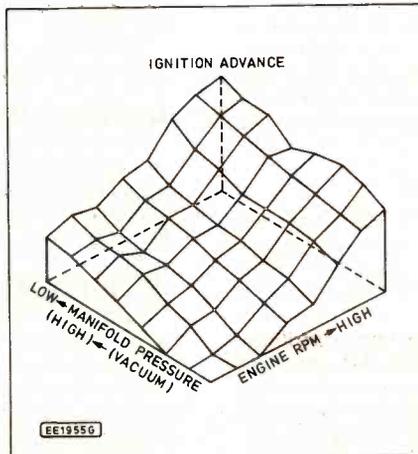


Fig. 8. Engine map using the programmed ignition system.

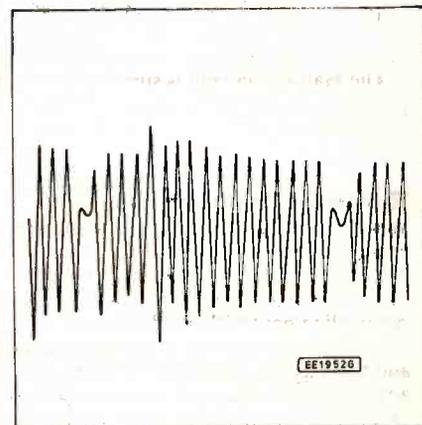


Fig. 9. Typical waveform to be expected from a reluctor sensor output.

MICROPROCESSOR IGNITION CONTROL

Programmed Ignition comes in the ubiquitous "black box" called an ECU (Electronic Control Unit). It makes use of a ROM i.c. to store information about a particular engine's advance requirement under all load and speed conditions. In operation this is then read by a *microprocessor* and further modified by additional inputs such as coolant temperature and engine knocking ("pinking") to provide the optimum ignition advance.

The stored information called an engine "map", is worked out by the engine manufacturer on an engine test bed (see Fig. 8). Even the most rudimentary programmed ignition system will require the following inputs: engine position; engine speed; manifold depression; battery voltage and coolant temperature.

Engine position and speed are often taken from a flywheel reluctor sensor, (see Fig. 6) which comprises a permanent magnet with a projecting pole piece and a reluctor disc which is bolted to the flywheel.

The disc has pairs of lugs projecting at 10 degree intervals around the circumference. The sensor is mounted in such a way on the engine that as the flywheel rotates the pairs of lugs pass each side of the projecting pole piece. Thus for an instant at 10 degree intervals the sensor and the lugs form a magnetic circuit and also pulses are generated, their frequency indicating the speed of rotation of the engine.

However, at Top-Dead-Centre (TDC) for cylinders 1 and 4 and at 180 degrees further round thus TDC for cylinders 2 and 3 there are pairs of lugs missing. There will therefore be pulses missing at these points and the ECU can thus detect TDC for the appropriate cylinders (see Fig. 9). In this way engine speed and position is passed to the ECU.

ENGINE LOAD

Engine load is the other important parameter and this is related to manifold depression. In other words if the throttle is wide open (full load) manifold depression will hardly exist as the manifold will be at virtually atmospheric pressure. If on the other hand the car is descending a hill on a trailing throttle (no load) there will be a large vacuum or high manifold depression.

On light loads the engine runs much more economically if the ignition is advanced. You may recall that a vacuum capsule is fitted to distributor type ignition systems to achieve this. With programmed ignition the manifold pressure passes up a pipe to the ECU where it is measured with a pressure transducer.

ADDITIONAL INPUTS

Engine temperature is a useful input to include in an ignition system in that retarding of the timing can lead to better drivability from cold and speedier warm-up. A coolant sensor is already available on most cars anyway (for the temperature gauge) and so this is relatively cheap to implement.

Temperature sensors are made from a negative temperature coefficient semiconductor, encapsulated in a brass housing and screwed into the engine block or thermostat housing. Their resistance varies from about 10 kilohms at -10°C to about 300 ohms at engine running temperature.

KNOCK SENSOR

A significant addition with programmed ignition is the "knock sensor"! Engines are more economical, more powerful and produce less harmful emissions if run at maximum advance.

In the past the standard setting always had to allow a margin for error because the consequences of an *over-advanced* engine are dire; broken pistons and burnt valves to name a couple. But with a microprocessor looking after the ignition it could run the engine at maximum safe advance and it could sense the onset of "knocking", "pinking" (or whatever you call it) it could then retard the ignition until the unwanted condition ceased.

This "feedback" scheme of things is exactly what is implemented and what is more the relatively high speed of a microprocessor allows it to differentiate between different cylinders and only retard the ignition on the cylinder required. Being a feedback system there is also the possibility that this can compensate for the age of the vehicle or the wrong fuel.

The knock sensor is a piezo electric accelerometer and is screwed into the block. The name belies a simple construction of a piezo crystal which is clamped between the block and a weight (i.e., a thick washer). See Fig. 10.

Vibration of the engine thus squeezes the crystal and produces a signal. The tricky bit is then to sort out which signal is the one which indicates knocking. Inside the ECU you can imagine there are bandpass filters and other bits of jiggery pokery (sorry signal processing).

A typical algorithm for the microprocessor is: At the fourth ignition pulse after the knock has occurred the timing is retarded in steps of 1.25 degrees until the knock disappears. The ignition is then advanced by 0.625 degrees every 32 engine revs until the advance agrees with the figure in the ROM (Read Only Memory) or the knock occurs again.

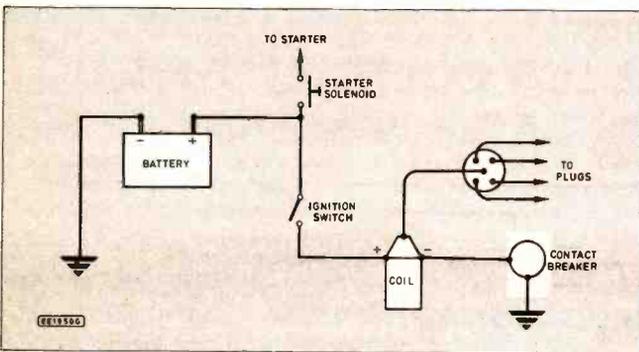


Fig. 10. Mechanical arrangement for the piezoelectric transducer "knock sensor" and examples of output waveforms. The sensor is screwed into the engine block.

PROGRAMMED IGNITION ADVANTAGES

The advantages of the programmed ignition are: Better drivability; easier starting; smoother running; improved economy and power and automatic adjustment for the age of vehicle. Additional inputs can be added to give traction control, smooth idle, smoothed auto gear change, turbo boost control and exhaust gas recirculation. Inter-connection with a fuel management system is also possible which enhances the effect of both systems.

HOW TO RECOGNISE

Apart from the rotor arm and distributor cap all the other functions of a distributor have been replaced by an Electronic Control Unit (ECU). The ECU is a box, often black, it has a finned section and apart from a multiplug has a vacuum pipe from the inlet manifold leading into it. It is often mounted on the bulkhead or suspension turret.

FAULT-FINDING

Both programmed ignition and the simpler module type ignition system are easy to fault find as long as you remember that their function is to replace the contact breaker. Have a look at the diagram of the basic system (Fig. 1 and Fig. 11) and visualise the ECU in place of the contact breaker and ignore all the sensors.

Clearly a bulb connected across the two coil terminals should flash when the engine is cranked, if not then check for battery voltage from the coil all the way back to the battery. You should also find battery voltage on the coil negative with the engine stationary—due to "stationary engine cut-off" referred to earlier.

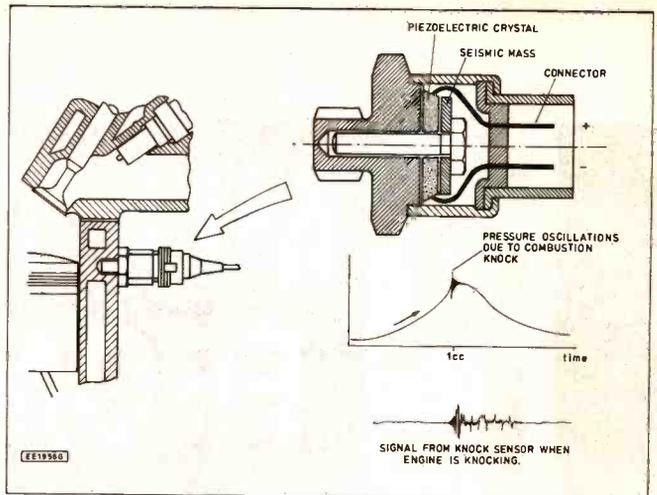


Fig. 11. Block diagram showing the Electronic Control Unit (ECU) superimposed on the conventional c.b. system. (See also Fig. 1.).

If the test bulb still does not flash then it has to be the feed to the module or ECU which is often taken from the coil positive terminal or direct from the ignition switch.

If the car still does not start, and assuming it is the ignition, then it must be the high tension circuit. *A word of caution is due here: electronic ignition circuits produce quite a kick, so be careful!*

High tension circuits must be tested in such a way that you always provide an "Earth" path. If you don't it'll find one of its own and do some damage on the way. The best check is to dive in the middle. Remove the lead to the centre of the distributor cap and rest it on the engine in such a way that a spark can jump to the block. When cranking if you don't get a healthy spark which will jump across 1/4 in. then you've got problems with the coil. If you have a spark then the fault must be in the distributor cap or rotor arm.

With a Programmed Ignition the sensors can cause a problem. Obviously if the TDC sensor has failed the system will not function. Check out with a multimeter, retractor coils have a resistance in the couple of hundred to three or four kilohms bracket. Failed ones are open circuit or short circuit.

Similarly with coolant temperature sensors, open or short. Good ones range from 10 kilohms when cold down to 300 ohms at 100°C. Hall Effect sensors are difficult but try your multimeter switched to a.c. volts on the output lead. With the engine cranking any reading probably means O.K.

POOR PERFORMANCE

Apart from tired components like plugs and leads poor performance can only be caused by bad timing, so with the module type of ignition check it and also check the operation of the vacuum and centrifugal advance systems.

Programmed ignition cannot get its ignition timing wrong except if it thinks the engine is cold so check out the coolant temperature sensor. The only other problem could be "pinking" and this points the finger at the knock sensor.

Incidentally, correct function of this component can be verified by tapping the engine block close to the sensor quite hard and repeatedly with a spanner. If the engine is ticking over at hot idle speed you will detect a drop in speed which indicates the timing has been retarded. However, some cars have a stepper motor controlling the idle speed so this will have to be disconnected first.

IN CONCLUSION


We have purposely not attempted to explain the workings of the inside of "black boxes" found in the ignition systems on cars. Nobody in their right mind is going to attempt to fix one of them at the side of the road.

The guts of the ECU's however are very interesting and will perhaps be considered at a later date. What we have attempted to do is show that although sophisticated, these systems are quite easy to understand at the block diagram level and give enough, we hope, information to quickly resolve any problem associated with them.

Do please look before you leap — like any electrical device in the hostile environment of a car engine compartment — most faults are caused by poor connections. □

MICRONTA[®]

MULTIMETERS FROM TANDY[®]

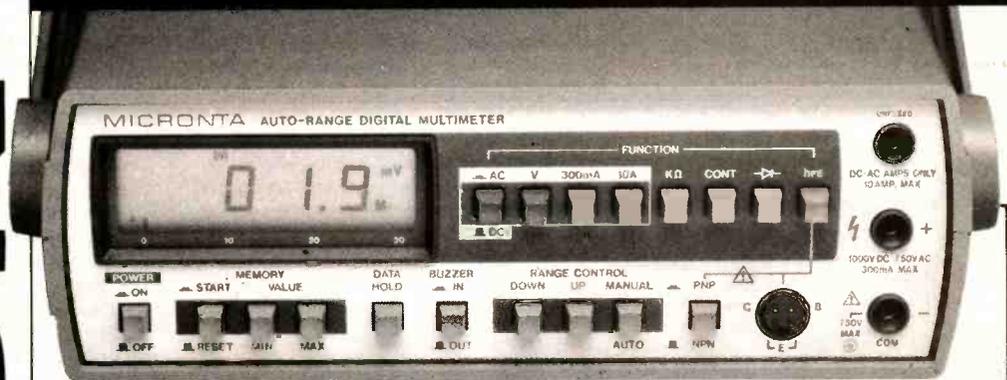

BENCHTOP DIGITAL LCD MULTIMETER £79⁹⁵

- Measures AC/DC Volts, Current And Resistance
- Manual Or Autoranging Facility

22-195

POCKET AUTORANGING MULTIMETER £19⁹⁵


- Measures To 400V AC/DC
- Includes Mini Probes And Folding Case

22-171

PROBE-STYLE MULTIMETER £29⁹⁵

22-165

- Fully Automatic Range And Polarity

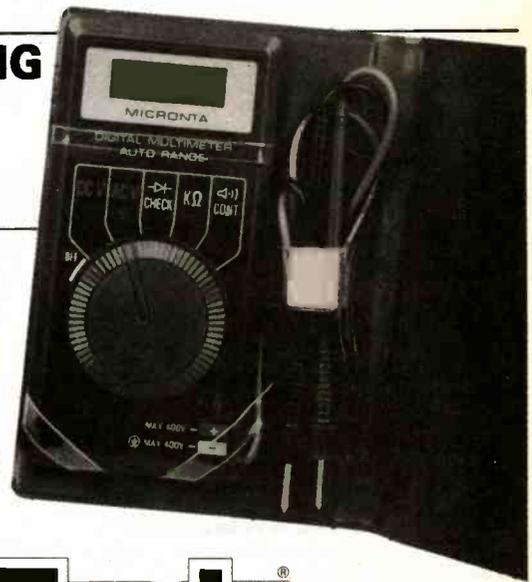

Tandy[®]

For The Best In High Quality Electronics

Over 400 Tandy Stores And Dealerships Nationwide.
See Yellow Pages For Address Of Store Nearest You.

InterTAN U.K. Ltd., Tandy Centre, Leamore Lane,
Walsall, West Midlands. WS2 7PS Tel: 0922 710000

...REPORTING AMATEUR RADIO...

TONY SMITH G4FAI

MORE PRIMARY BANDS

Although there is apprehension about pressures on amateur radio frequency allocations at the next World Administrative Radio Conference it is heartening to be able to report some gains at the present time.

The WARC held in 1979 agreed that the 18.068 to 18.168 and 24.890 to 24.990MHz bands should be transferred to the amateur service on a primary basis. In order to protect existing users, while replacement frequencies were being found for them, the bands were made available to Class A amateurs initially on a restricted basis only.

These restrictions involved limitations on type of transmission, maximum power and antenna characteristics, and a requirement that no interference be caused to other services. Only Morse transmissions were allowed with a maximum power of about 10 watts, and antennas were limited to horizontal polarisation with no greater gain than that of a half-wave dipole.

The original services have since been moved to other frequencies and, as from 1st July 1989, the two bands are now available to amateurs on a primary basis, using all permitted modes of transmission at the normal power levels applying to the amateur h.f. bands.

Apart from Morse, stations can also operate with telephony, radio teletype (RTTY), data, facsimile, and slow-scan TV, with power limits of 100W carrier or 400W PEP (peak envelope power) for emissions with suppressed or reduced carrier, e.g. single-sideband (SSB). There is no restriction on the performance of antennas so beams can be erected to provide better long distance (DX) performance.

Despite the restrictions a good number of amateurs have been using these bands for the last few years. New h.f. transceivers nowadays include facilities for the "new WARC bands", and the dropping of the Morse only rule will undoubtedly make the bands interesting for many more operators.

POWER LEVELS

I have quoted "maximum power" in watts, which is how the amateur licence used to specify power. The present licence however sets out power limits in dBW, which is a way of expressing power levels relative to a fixed amount of power, in this case one watt.

Using this system, 1W is written as 0dBW. Doubling the figure in watts adds 3 to the dBW figure so, for example, 2W equals 3dBW and 4W equals 6dBW.

In the amateur licence, therefore, the 100 watts and 400 watts I mentioned above are defined as 20 and 26dBW respectively. The definition was changed in 1982, but most amateurs I

know find it confusing and still talk about "watts" when referring to the power of their transmitters. No doubt that is why advertisements for the latest "state-of-the-art" rigs also still describe power levels in the old-fashioned way.

EARLY COMMUNICATIONS

Edinburgh's Museum of Communication will be displaying some interesting items from its collection in the Upper Library, Bo'ness over the weekend 16th to 18th September. On show will be examples of early spark transmission, telegraph and telephone mechanisms, early single and multi-valve receivers, services communication receivers and transmitters, clandestine radios, early domestic wireless sets, gramophones, horn speakers, and more.

These are just a few of the things collected over the years by the museum's curator, Harry Matthews. He is continually adding to the collection and is always pleased to hear from anyone having interesting items which need a "good home" where they can be preserved for posterity.

Harry is always involved in interesting activities. In *Morsum Magnificat*, Summer 1987, there was a description of one of his projects—"tidying-up", photographing, and drawing the circuits of a historic WW2 spy-set for Leith Police who were setting up their own museum.

The set had an interesting story. It was in the luggage of Werner Walthi, arrested at Waverley Station, Edinburgh, in September 1940, and subsequently hanged as a spy. A code used by the Germans was found in Walthi's luggage and decoy messages were transmitted with the radio giving false information on the movement of British shipping, resulting in a number of U-boats being destroyed.

Further particulars about the museum, and the special exhibition at Bo'ness, can be obtained from Harry Matthews, 22 Kinglass Avenue, Bo'ness, West Lothian, EH51 9QA.

Incidentally, Bo'ness is the home of the Kinneil and Bo'ness Steam Railway. Over the weekend of the museum's exhibition trains will be operating on the 7 mile return journey to the Birkhill Clay Mine, newly opened to the public this year by the Bo'ness Heritage Trust.

SKELETON IN THE CUPBOARD

Most of the time in this column I extol the attractions of amateur radio as an enjoyable and satisfying scientific hobby covering many fields often on an international scale. It has social, adventurous and experimental aspects, plus worthwhile opportunities for public service, all at the choice of the individual. My message, as ever, is "come and join us".

But nothing is perfect and there is one area of activity within amateur radio

where problems have existed for years, and no-one seems to know how to deal with it. This is the disruptive behaviour of a small section of operators using v.h.f. repeaters.

Talk-through repeater stations are installed by clubs or groups at favourable high sites to enable amateurs operating mobile stations, usually from their cars, etc., to contact other stations over greater distances than is normally possible by direct transmission. The repeaters receive signals on one frequency and re-transmit them on another, and because they are used by many different stations there is need for good operating discipline.

Unfortunately, some operators pay no regard to these needs, hogging the repeaters for normal base-station, rather than mobile, operation; making new users of repeaters unwelcome; interrupting on-going QSO's (contacts) with foul language, abuse, or illegal transmissions of music and generally blocking access for other users.

It all started in the early '70s when repeaters were first introduced and I remember it being said then that nothing could be done by the authorities unless the culprits were actually heard by them and could be identified. There were apocryphal tales of the "boys" going out at night in their cars with direction-finding equipment to find the culprits, but what happened when they did I cannot say!

Nowadays there are some 250 repeaters throughout the country and while some areas seem to have less trouble than others, the problem still exists. The licensee for all UK repeaters is the Radio Society of Great Britain while the various groups are franchised to run the repeaters on the Society's behalf.

Following complaints by over 70 amateurs about the misuse of one repeater last year the repeater group concerned declared that although it was responsible for the technical side of the installation it could not censor the users. In response to this the RSGB's Repeater Management Group emphasised that the group as franchise holder was responsible for the way the repeater was used, adding that in a similar case the DTI had requested a shut down.

Occasionally one hears that an amateur has been prosecuted for repeater offences, both in the UK and in other countries. It seems a pity though that the only other solution is the shut down of a repeater since that surely represents a victory for the few saboteurs over the majority of decent users.

Many people listening to amateur radio for the first time, perhaps in a friend's shack, hear repeaters in action and judge the hobby from what they hear. I can assure them that if they listen on other frequencies they will get a completely different impression.

TEACH-IN SERIES

TWO SPECIAL PUBLICATIONS

FROM EVERYDAY ELECTRONICS



SEE DIRECT BOOK SERVICE pages—for full ordering details

THE FIRST "TEACH-IN" BOOK

ONLY £1.95 plus P & P

By Michael Tooley BA and David Whitfield MA MSc CEng MIEE

A comprehensive background to modern electronics including test gear projects. This 104 page, A4 size book forms a complete course in basic electronics; designed for the complete newcomer it will, however, also be of value to those with some previous experience of electronics. Wherever possible the course is related to "real life" working circuits and each part includes a set of detailed practical assignments.

This book is an excellent companion for anyone interested in electronics and will be invaluable for those taking G.C.S.E. or B.T.E.C. electronics courses.

ORDER CODE: EE/T-1

TEACH-IN 88/89 BOOK

£2.45 plus P & P

A complete City and Guilds Certificate Course for 726/303 Introductory Microprocessors

Written by Mike Tooley BA this course can lead successful readers to a City and Guilds Certificate. Everything you need to know is included—even pre-test papers, etc.

From Terminology, Integrated Circuits and Logic Families in Part One, the course progresses in easy stages up to High- and Low-level Languages, Flow Charts and Assembly Language. Also featured is a range of eight Data Pages giving information on popular microprocessor chips. A comprehensive index is included, making this a valuable reference manual.

ORDER CODE: TI 88/89

ELECTRONICS
TEACH-IN No: 3
£2.45

EXPLORING ELECTRONICS

- Explains the workings of components and circuits by involving the reader in inexpensive experiments.
- Assumes no previous knowledge
- Split into 29 easily digestible sections
- Contains many useful projects

From the Publishers of
EVERYDAY ELECTRONICS

ON SALE — 22 SEPT

EXPLORING ELECTRONICS

From the Publishers of
EVERYDAY ELECTRONICS

NEWSAGENT ORDER FORM

Please reserve/deliver a copy for me.

Signed

Name and Address
(BLOCK CAPITALS PLEASE)

.....
.....

Make sure of your copy—cut out this form, fill it in and hand it to your newsagent. (distributed by Seymour.)

SEE YOUR NEWSAGENT NOW!

STABILIZED POWER SUPPLIES



STEVE KNIGHT Part Four

Apart from delving into the basic theory of p.s.u. design and potential problems, this short five part series will introduce three practical projects which are fairly simple to build and have reasonably good specifications.

The three stabilized units are: Variable 0V to 12V 1.5A; Variable 0V to 25V 1A; Variable 1.5V to 25V, with switched current limits of 0.5A, 1A, 1.5A and 2A.

TWO REGULATED power supplies with current limiting, one providing 0 to 25V at 700mA and the other 0 to 30V at 1.0A, are our subjects this month. Before getting on with the constructional details, however, a few words about the meters used on these projects won't be out of place.

The addition of a voltmeter/ammeter indicator to any power unit, although not strictly necessary, really completes the job and gives it a more professional finish. Of course, it is always possible to calibrate the voltage control knob on the panel with voltage markers, and since for a stabilized supply there is negligible variation in the output voltage within the specified current range, this is an inexpensive alternative. If cost is also in mind, a single voltmeter can be fitted; this will indicate gross current overloads by either falling to zero on short-circuited loads or failing to increase when the normal current has been exceeded.

The thing to try and avoid is rescaling a meter which has a scale marked in a completely different fashion from what is actually wanted. This *can* be done and the author has rescaled many, but it is a job that requires some skill and a whole lot of patience in removing an existing scale without damaging the instrument itself and some reasonable artistry in marking the new scale to its proper divisions.

METER

In both this month's designs, a 50 μ A meter, type Q45, has been used. This is a large meter measuring 110mm \times 83mm and the scale, as provided, is marked (naturally!) 0-50 μ A.

The scale changes needed are fairly simple to carry out, but *do NOT* under any circumstances do this on a dirty bench top or anywhere else where there are iron filings or other pieces of eager minutiae waiting to get into the moving-coil mechanism and jam everything solid. Find yourself a dust free corner away from the wife, kids and the dog; then carefully remove the plastic covering and put it to one side.

Equally carefully remove the two scale fixing screws and *slide* the scale from beneath the pointer. Now put the meter and the two screws inside the plastic cover and put the lot in a safe place.

METER SCALE

The first of this month's projects needs a scale reading 0-25V and 0-1A, and Fig. 4.1a and Fig. 4.1b shows the scale before modification and afterwards. You need a packet of rub-off lettering with figures which reasonably match those already in the scale.

The existing μ A marking and scale figures have now to be removed; this is best done by *gently* scraping them with a used razor blade, keeping the blade at right angles to the surface and avoiding "digging in" the corner of the blade. This sounds as though we are going to end up with a patchy surface but with the necessary pati-

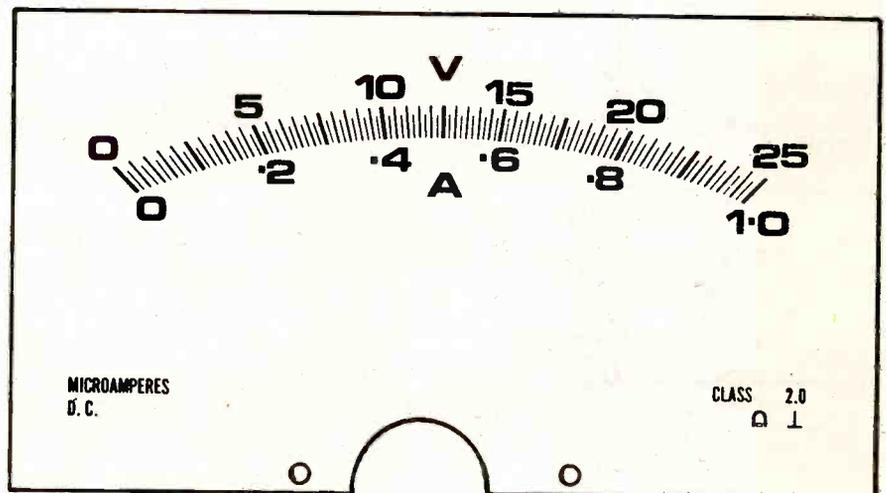
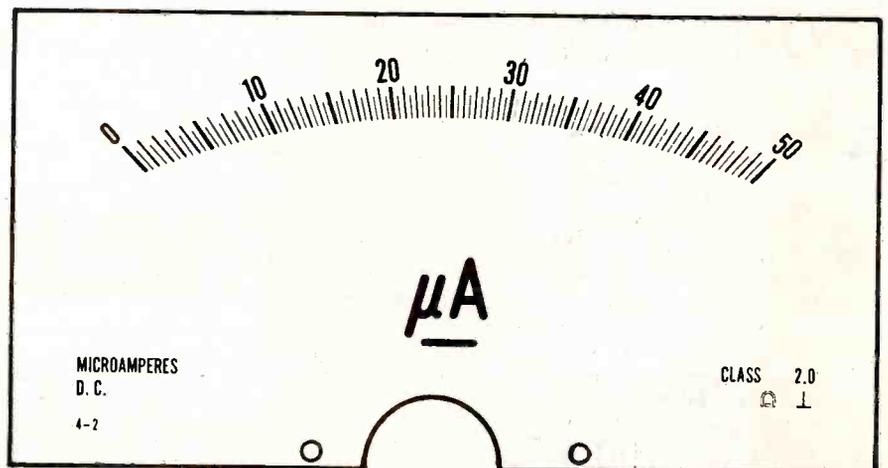


Fig. 4.1. Meter scaling before (a) and after (b) modification. The top figures are removed as well as the μ A marking.

ence the scale print will come off and leave the underlying white surface undisturbed.

Practice on the small unimportant printing at the foot of the scale first. Then get rid of all the dust and add the V and A lettering and the additional numbering as shown in Fig. 4.1b. You then have a scale reading 0-25V and 0-1A.

For the second project we need a scale reading 0-30V and 0-1A. Here the voltage scale doesn't fit readily into the existing divisions, so we leave the 0-50 markings as they are and add only the current figures 0-1A in exactly the same way as before. True, we shall only be using three-fifths of the scale length for our 30V output, but these scales are quite large and easily read so this is no great hardship.

Reassemble the scale on to the meter, taking care that the screws don't fall into the works, and snap the cover back into place. Do this at the bottom first so that the zeroing button engages properly. It should do this without adjustment if you haven't disturbed it.

You can if you wish use a smaller 50 μ A version of this meter, the type T21 (see Shoptalk), and modify the scale in the same way. If you don't fancy rescaling meters in this way, use separate meters for voltage and current. The 1A type T30 and the 30V type T43 are suitable.

Constructional Project

VARIABLE STABILIZED POWER SUPPLY

0-25V at 700mA maximum, ripple less than 3mV r.m.s.

THE COMPLETE circuit diagram for the 0-25V Stabilized Power Supply is shown in Fig. 4.3. This design will provide a highly stabilized output adjustable from 0 to 25V at a maximum current of 700mA and with a ripple of less than 3mV r.m.s at full load. The output impedance is one ohm, D.C. to 80kHz.

The power input is derived from transformer T1 which has two secondary windings, one of 28V at a current rating of 1.5A and the other of 12V at a rating of 100mA. Both of these supplies are rectified by bridge rectifiers REC1 and REC2 respectively. After smoothing by capacitor C1, the positive supply line from REC1 goes on

those obtainable from integrated systems. Also, few external components are saved by their use and additional circuitry is nearly always required to get the output voltage range from i.c. regulators down to zero. We will be coming to an example of integrated design with these additions in next month's project.

Both circuits operate on the principles shown in the block diagram of Fig. 4.2 where the various parts covered in Part 1 of this series are now brought together in practical form.

through the series regulator transistor TR1, a 2N3055 (or a 2N3771 may be used), and the current sense resistor R9 to the positive supply output terminal.

The output from bridge rectifier REC2 provides, after smoothing by capacitor C2, a negative line which supplies the zener reference diode D3 and also biases the emitter of the error detector TR3 in conjunction with the diodes D1, D2, to approximately -0.7V. This arrangement allows the output voltage to be taken down to zero.

The series regulator transistor TR1 carries the whole of the output current and acts as an automatic resistance. Its base current is controlled by the error amplifier

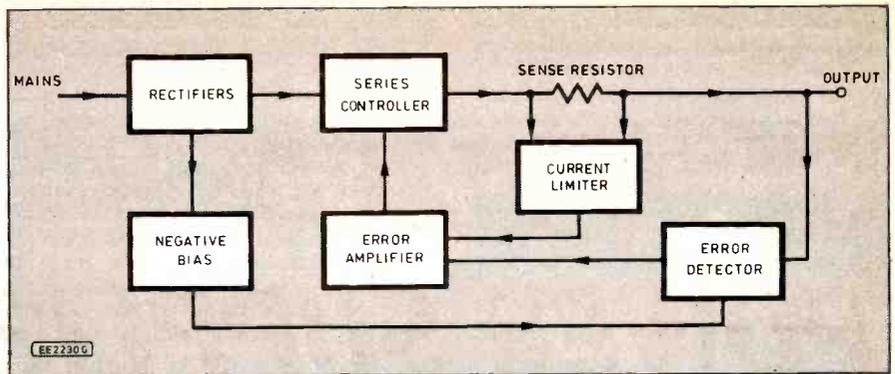



Fig. 4.2. The general block diagram for the two stabilized supplies described.

REGULATED SUPPLIES

Both projects to be described are very similar in construction and apart from a few minor details, the assembly instructions which follow can apply equally to both designs. Both circuits use discrete transistors, four in the case of the 25V unit and six in the case of the 30V unit.

Some might think that the circuits are retrograde in that they are not using integrated packages, but apart from fairly expensive regulator i.c.'s, the performance figures for these designs are better than

Fig. 4.3. Complete circuit diagram for the 25V 700mR Variable Stabilized Supply. Capacitor C8 is mounted across the output terminals.

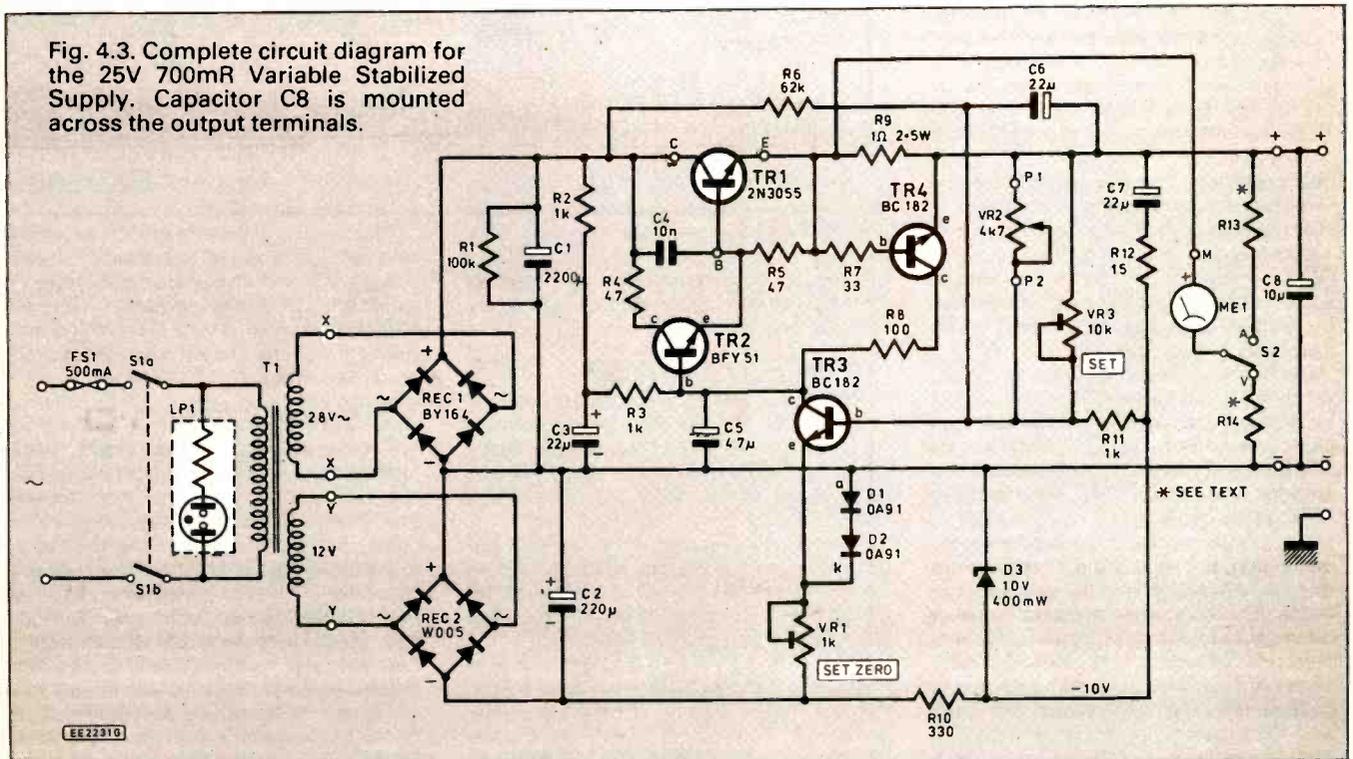

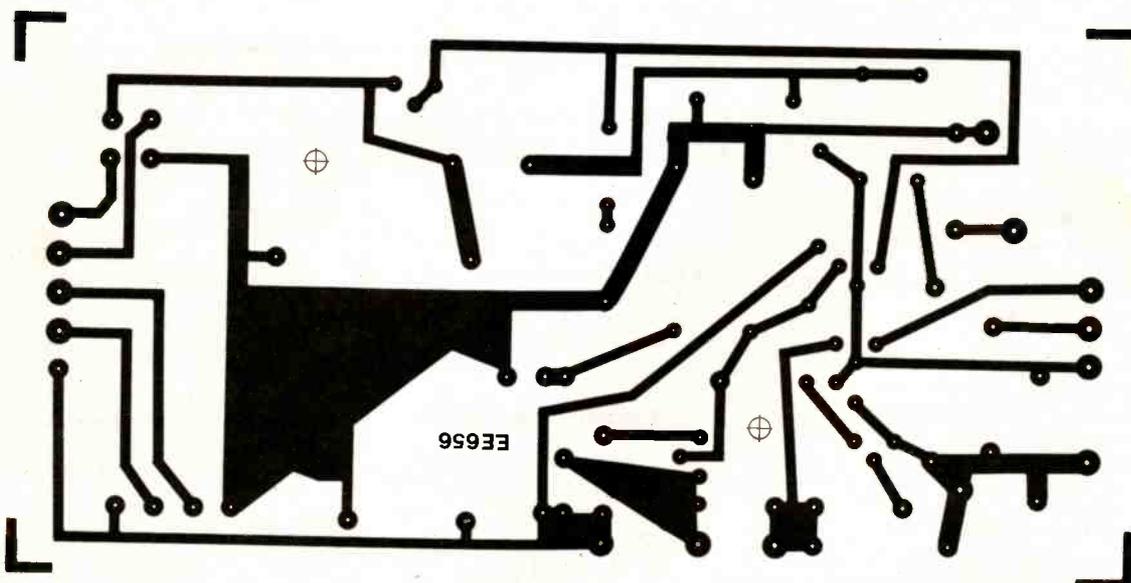
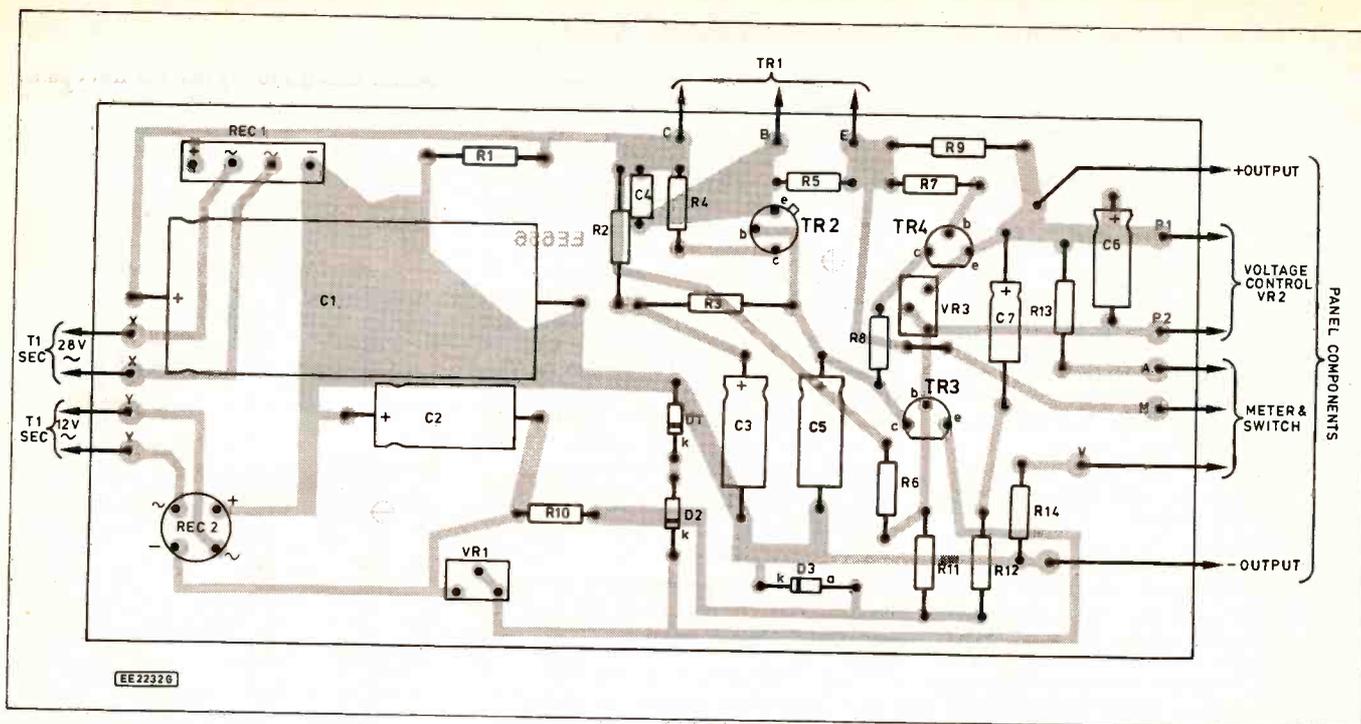


Fig. 4.4. Printed circuit board component layout and full size copper foil master pattern. Drill fixing centres marked "F" to suit mounting spacers.

TR2 which amplifies the output from the error detector TR3 to a level sufficient to drive the base of TR1.

Base bias for TR1 and collector bias for TR2 are provided by resistor R4. Hence, whatever happens at the base of TR3 has the effect of adjusting the effective series resistance of TR1.

The base of TR3 connects to the voltage adjusting potentiometer VR2. This control sets the required output voltage to anything between 0V and 25V. Once this is set, any unwanted variation in the output level is passed to the base of TR3 and initiates the feedback to TR1.

Suppose the output tends to fall slightly. The voltage at the base of TR3 falls and its collector current (derived through resistors R2-R3) also falls. This increases the base voltage of TR2 which, being in emitter-follower configuration, increases the base current of TR1. This reduces the resistance of TR1 and the output fall is compensated.

This regulation also acts to reduce the output ripple voltage; any ripple on the

rectifier side of transistor TR1 is passed by way of resistor R6 to the base of the error detector (TR3), and this, together with capacitor C6 effectively bypassing VR2 to a.c. ripple components in the output, enables the feedback to treat the ripple as an unwanted variation.

CURRENT LIMITER

Transistor TR4 serves as the current limiter. Its base-emitter bias is derived from the voltage developed across the series resistor R9. Providing that this voltage is less than about 0.7V, TR4 remains switched off.

The value of resistor R9 is one ohm and when the output current reaches 700mA, the voltage drop is 0.7V. This then switches transistor TR4 on and takes control away from the error detector TR3.

The base of TR2 consequently moves negative and TR1 is biased back to the point where a 700mA current cannot be exceeded. In actual practice, the current limit may lie between 650 and 750mA,

depending upon the tolerances of resistor R9 and transistor TR3.

The output is monitored by the switch selected Voltmeter/Ammeter already described and finally smoothed by capacitor C8. Preset controls VR1 and VR3 are used to set up the voltage limit readings on the meter when the unit is ready for testing.

CONSTRUCTION

Everything except the mains transformer, the meter and its switching, and the voltage adjust control, goes on to a printed circuit board (p.c.b.). In turn, this p.c.b. screws on to a simple aluminium heatsink which carries the series regulator transistor TR1. The same heatsink is used in the second project to be described, and what is said here about the various mountings will apply equally well to the later design.

The circuit board component layout and full-size copper foil master pattern is shown in Fig. 4.4. A ready-drilled printed circuit

board is available from the *EE PCB Service*, code EE000.

When assembling this board the only precautions to be taken are, the usual ones of getting the rectifiers, electrolytics and diodes the right way round. More care is needed for bridge rectifier REC2 than for REC1. Bridge REC1 can only go in one of two ways but REC2 can go in any one of four!

Check very carefully, and take care with the soldering, in particular around the transistor connections. Transistor TR2 must have a corrugated type heatsink pushed on to it, and wirewound resistor R9 should be spaced away from the surface of the board by at least 3mm. There is a short link needed immediately below the position of VR3, don't overlook this or the meter won't work, although everything else will.

AMMETER/VOLTMETER

Resistors R13 and R14 need a few words. These convert the basic $50\mu\text{A}$ meter movement into an ammeter (A) and a voltmeter (V) respectively. Resistor R14 is switched in series with the meter on the voltage range; since the meter has to read 25V full scale deflection (f.s.d) and its own internal resistance is stated to be 1700ohms, we have to restrict the current through it to $50\mu\text{A}$ when 25V is applied to it and R14 in series. By Ohm's law we get: $R14 = 25 / (50 \times 10^{-6}) = 500\text{k}\Omega$, less 1700 $\Omega = 498,300\Omega$.

Well, we aren't going to pick that off the shelf, and the and the best we can do is to use a 510k Ω , 1 per cent resistor. This will tend to make the reading slightly on the low side but this is compensated for by the fact that the voltage is actually being measured on the higher potential side of resistor R9 and what appears at the terminals is always slightly less than this.

For the current reading, the f.s.d. is 1A. What we are now effectively reading is the voltage drop across R9 interpreted in terms of current.

If 1A flowed through R9 it would drop 1V, hence we want the meter to provide f.s.d. when 1V is applied to it and the series resistor R13. Hence $R13 = 1 / (50 \times 10^{-6}) = 20\text{k}\Omega$, less 1700 $\Omega = 18.3\text{k}\Omega$. An 18k Ω , 1 per cent resistor will do here.

If, of course, you use any alternative meter, you will need to recalculate these values.

HEATSINK

We now have to fit the circuit board to the heatsink which carries the 2N3055 series controller transistor (TR1), and we do this in the same way as we did for last month's project. Bend a piece of 16s.w.g. aluminium (you can use 14s.w.g. if you wish) to the dimensions shown in Fig. 4.5.

Place the board on the heatsink, away from the "bend" side, and mark through the two fixing holes indicated by "F" on the board. The board will be screwed to the aluminium sink at these points using $\frac{1}{2}$ in. spacers.

Let the bottom edge of the board be a quarter inch or so above the foot of the aluminium. There is nothing critical about the actual positioning.

Spray the heatsink black if possible and mount TR1 at its centre, insulating the transistor TO3 case from direct contact with the aluminium with the usual insulating kit. A silicone rubber washer is preferable to mica here, but if you use the latter, give both sides of it a thin smear of heat transfer compound before mounting.

Solder three differently coloured flexible leads to the emitter, base and collector (case) of transistor TR1 long enough to reach to the E, B and C solder pads at the top edge of the board after it has been screwed to the heatsink. It is easier if you have soldered Vero pins to these points, and the same, if you wish, to the other out-pads.

When the board has been screwed to the heatsink, it should look something like Fig. 4.6; TR1 leads looping neatly over the top edge of the board and soldered to the appropriate pins. The spacers may be either metal or plastic types, 6BA or 4BA threaded. If you use metal types, ensure that they are not fouling the board wiring tracks. Their length is not critical, but $\frac{1}{2}$ in should be considered a minimum.

This completes the board and heatsink assembly.

BOXING UP

We have not specified any particular case for this project (or for the next one


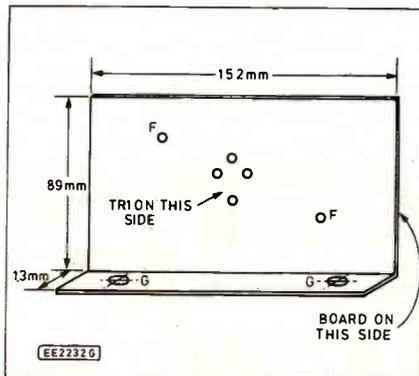


Fig. 4.5. Heatsink (16 or 14s.w.g.) drilling details. Holes at "F" to match board and two holes "G" 4BA clear. Centre group to suit TO3 transistor outline.

Fig. 4.6. Circuit board mounted on heatsink.

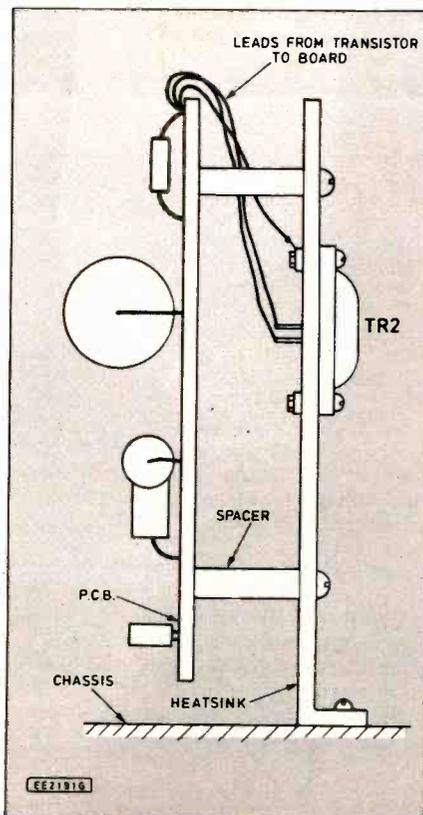

come to that) because there is a vast range of suitable cases available at a vast range of prices. Enough to say that the front panel shouldn't measure less than about 229mm (9in) wide by 127mm (5in) high, and you will need a depth of 102mm (4in) minimum.

COMPONENTS

Shop Talk

See page 636

25V UNIT

Resistors

R1	100k
R2, R3	1k 0.5W (2 off)
R4, R5	47 (2 off)
R6	62k
R7	33
R8	100
R9	1 2.5W wirewound
R10	330
R11	1K
R12	15
R13	18K 1% see
R14	510k 1% text

Potentiometers

VR1	1k min. skeleton preset, vert.
VR2	4k7 rotary carbon, lin.
VR3	10k min. skeleton preset, vert.

Capacitors

C1	2200 μ axial elec. 63V
C2	220 μ axial elec. 25V
C3, C6, C7	22 μ axial elec. 25V
C4	10n metal film
C5	47 μ axial elec. 25V
C8	10 μ tantalum 35V

Semiconductors

REC1	BY164 1.4A bridge rectifier
REC2	W005 1.5A bridge rectifier
D1, D2	OA91 (2 off)
D3	10V. 400mW Zener
TR1	2N3055 npn silicon power
TR2	BFY51
TR3, TR4	BC182 (2 off)

Miscellaneous

S1	2-pole 250V. 1A toggle (or slide)
S2	s.p.c.o. miniature toggle
LP1	220-250V neon indicator
T1	Mains transformer, 28V and 12V secs. (Trent type 00493)
ME1	50 μ A moving coil meter

Printed circuit board, available from *EE PCB Service*, code EE656; case to choice, front panel minimum of 229x127mm; 16s.w.g. aluminium heatsinks corrugated TO heatsink; terminals, 4mm type 1 black, 1 red; 500mA fuse; connecting wire, solder etc.

Approx. cost **£30**
Guidance only

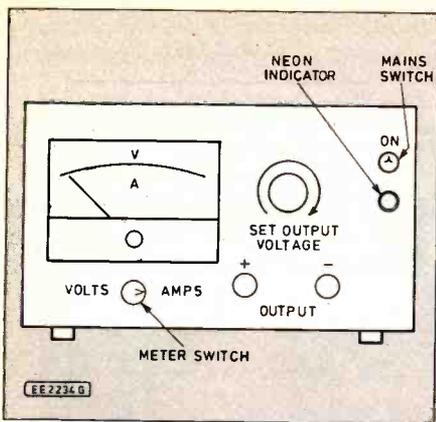


Fig. 4.7. Suggested front panel layout.

This panel size will allow room for the specified meter, the meter switch, the voltage adjust potentiometer, the mains switch and indicator neon and the output terminals. The mains lead can come in at the rear where the fuse can also be mounted. A suggested layout is shown in Fig. 4.7, with the lettering carried out in rub-down letters before the components are fitted.

Inside the box, mount the mains transformer and the heatsink and board panel. The wiring from the board to the external parts is fairly self-explanatory from the circuit diagram: there are two pairs of leads

from the XX, YY points to the mains transformer T1 secondary windings (make sure you put them to the right windings) and three leads to the meter switch from points A, M and V.

There are two leads, positive and negative respectively, to the output terminals (note that capacitor C8 is soldered directly across these), and two leads from points P1, P2 to the voltage adjust potentiometer VR2.

Just one point about this last component; the maximum output voltage corresponds to the control resistance being all in, i.e. connect P1 to the slider or wiper (w) terminal and P2 to the terminal representing the fully anticlockwise position of the slider as viewed from the front. If you do get it wrong, no harm will be done, the output will just decrease instead of increasing as you advance the control clockwise.

TESTING

Before switching on and testing the unit, carry out the following adjustments: set preset control VR3 fully anticlockwise i.e. all in circuit. Also preset VR1 to mid-position and the voltage adjust control VR2 fully anticlockwise (minimum output).

Put the meter switch S2 into the VOLTAGE (V) position. Switch on and carefully advance the voltage control on the front panel; if all is well, the voltmeter should read an increasing output.

If this does not happen, it may be that the meter switch has been wired the wrong way

round, so switch over to the "amps" side as a quick check. If the meter now reads, reverse the switch wiring.

As the maximum of 25V is approached, adjust the voltage control VR2 in conjunction with preset VR3 so that, by the time the voltage control has reached its maximum position, the voltmeter just reads 25V f.s.d. (full scale deflection). Preset VR3 is simply in parallel with VR2 and adjusts the total resistance to give the output level we want.

Now reduce the voltage control to its minimum setting and adjust preset VR1 so that the meter reads exactly zero. Return to maximum voltage and readjust VR3 if necessary to restore the output to 25V. This completes the voltage setting up.

To check on the current side of things and to ensure that the current limiter is working, switch over to CURRENT (A) on the meter switch S2 and short circuit the output. The ammeter should read somewhere about 700mA (0.7A).

This checks the limiting and also the current metering. Remove the short circuit and if by now nothing has started to complain, the power unit is ready for use.

Keep in mind when using this power unit, that once the current limit is reached, the voltage output will stay put and cannot be further increased. For example, suppose you have a load resistance of 30Ω, then the greatest voltage you can get before 0.7A is reached is 21V. The voltmeter will not, therefore, go past the 21V position.

Constructional Project

VARIABLE STABILIZED POWER SUPPLY

WE NOW turn to the second of this month's offerings, a 0-30V regulated supply which will provide us with a maximum current of 1A. The complete circuit diagram for the 0-30V Stabilized Power Supply is shown in Fig. 4.8.


In most respects this circuit is similar to the one we have already discussed, as a glance at Fig. 4.8 will show. A mains transformer T1 with twin secondary windings provides a positive and a negative supply by way of the two bridge rectifiers and


appropriate smoothing and there is the familiar series controller transistor TR1 with its driver TR2.

The error detector this time consists of a "long tailed pair", transistors TR5 and TR6 in a differential circuit. This gives an advantage over the previous supply in that stabilization against temperature changes is provided by this form of circuit. Only the difference between the two bases is amplified and temperature variations will tend to move both bases in the same direction.

The output from the collector of TR5 goes to the error amplifier TR4 which in


Fig. 4.8. Complete circuit diagram for the 30V 1A Stabilized Power Supply.

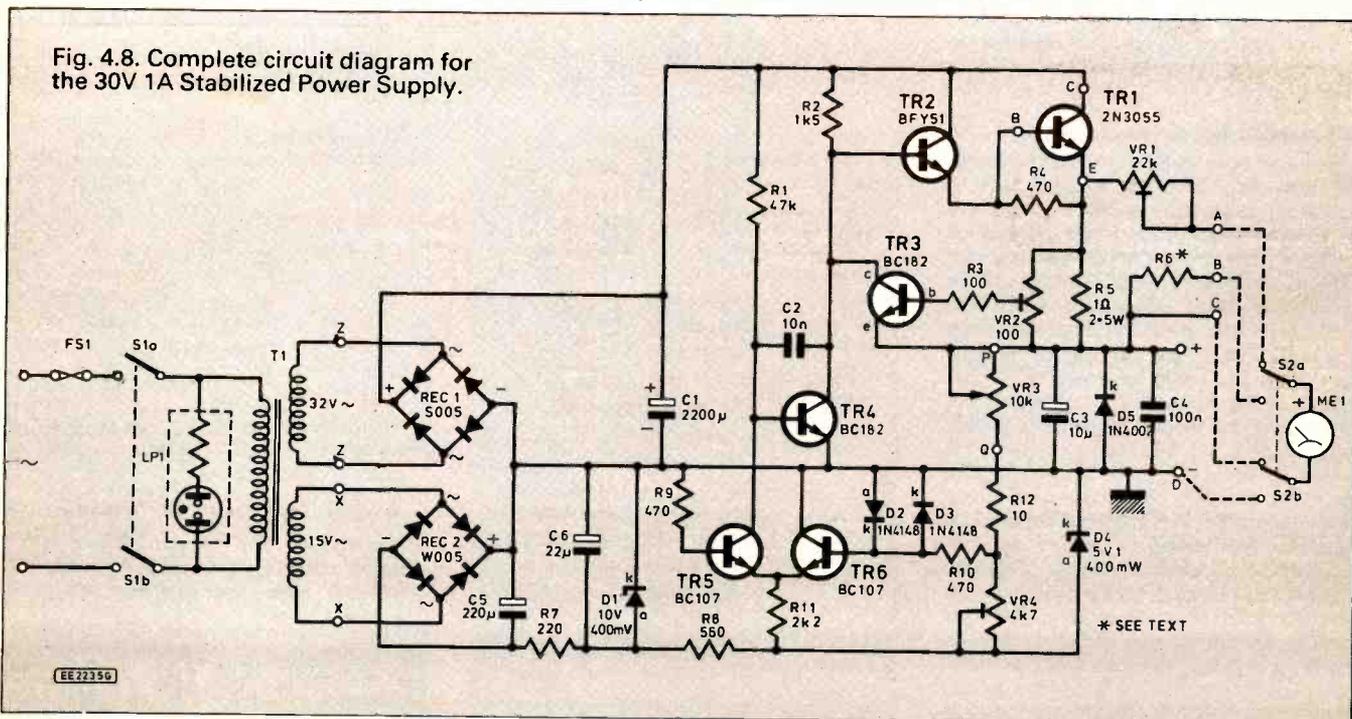

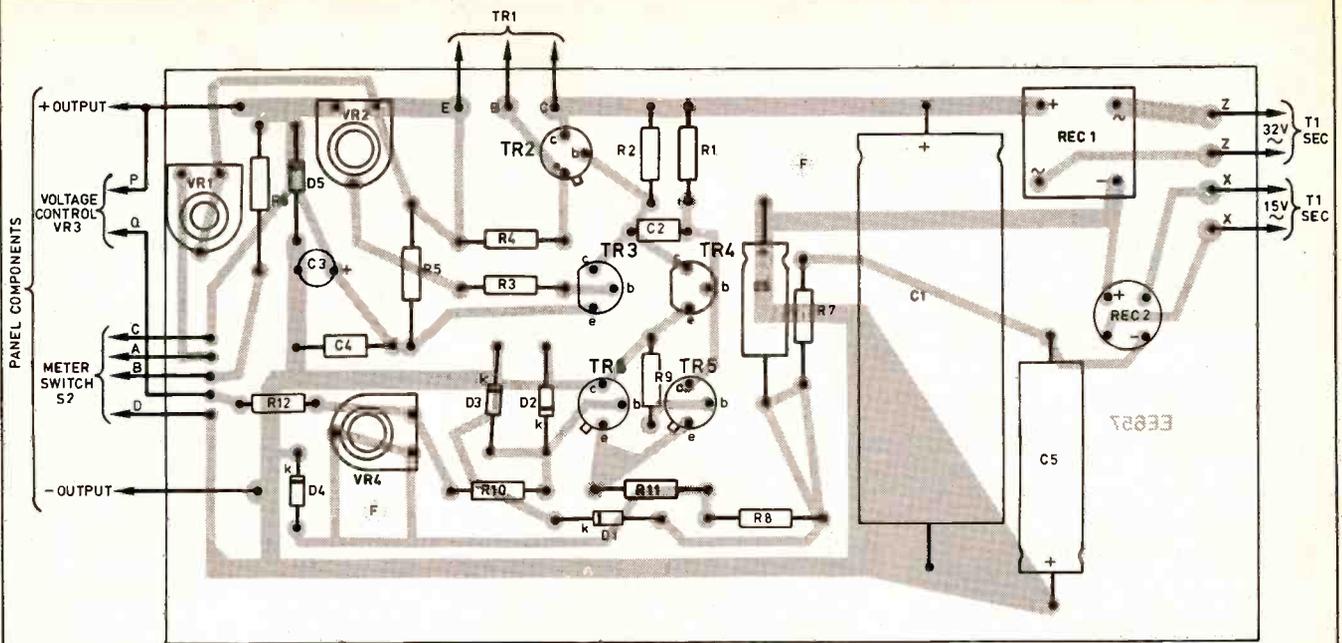

EE2238B

Fig. 4.9. Printed circuit board component layout and full size copper foil master pattern.

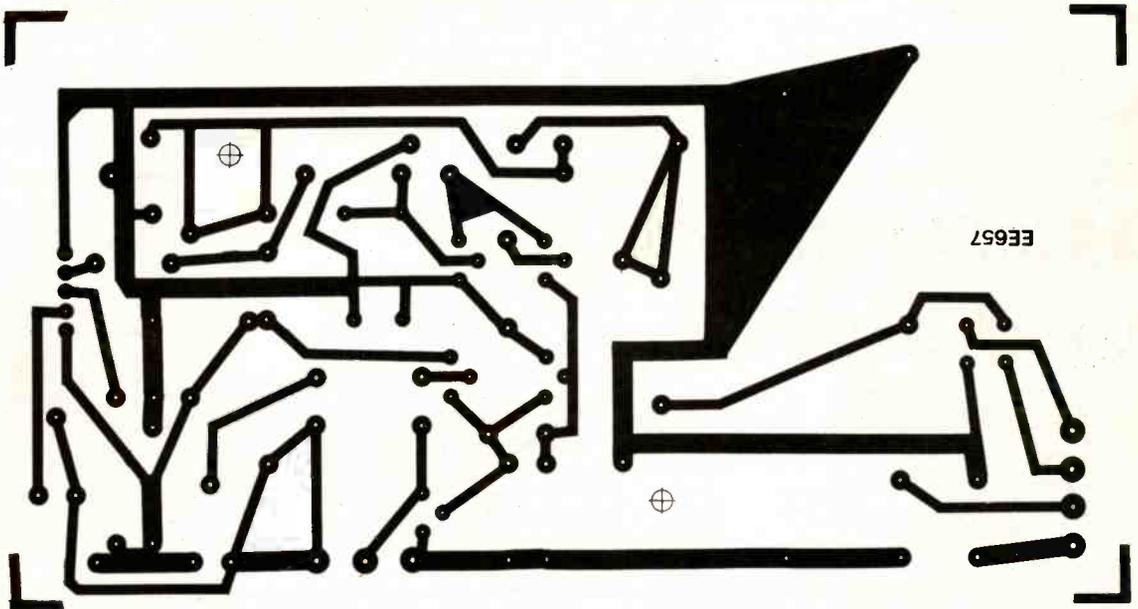

COMPONENTS

30V UNIT

**Shop
Talk**

See page 636

Resistors

R1	47k
R2	1.5k 0.5W
R3	100
R4, R9,	
R10	470 (3 off)
R5	10 2.5W wirewound
R6	300k 1%
	(2 off — see text)
R7	220
R8	560
R11	2k2
R12	10

All 0.3W carbon film, except where stated

Potentiometers

VR1	22k skeleton preset, horiz.
VR2	100 skeleton preset, horiz.
VR4	4k7 skeleton preset, horiz.
VR3	10k rotary carbon, lin.

Capacitors

C1	2200 μ axial elec. 63V
C2	10n metal film
C3	10 μ tantalum 35V
C4	100n metal film
C5	220 μ axial elec. 25V
C6	22 μ axial elec. 25V

Semiconductors

REC1	S005 2A bridge rectifier
REC2	W005 1.5A bridge rectifier
D1	10V 400mW Zener
D2, D3	1N4148 signal diode (2 off)
D4	5.1V 400mW Zener
D5	1N4002 1A 100V rec. diode
TR1	2N3055 npn silicon power

TR2	BFY51 npn silicon
TR3, TR4	BC182 npn silicon (2 off)
TR5, TR6	BC107 npn silicon (2 off)

Miscellaneous

S1	2-pole 250V, 1A toggle (or slide)
S2	d.p.c.o. miniature toggle
T1	Mains transformer, 32V and 15V secs. (Trent type 00494)


ME1 50 μ A moving coil meter
Printed circuit board, available from EE PCB Service, code EE657; case to choice, see text, 16s.w.g. aluminium heatsink; corrugated TO heatsink; terminals, 4mm type 1 black, 1 red; 500mA fuse; connecting wire, solder etc.

Approx. cost
Guidance only

£32



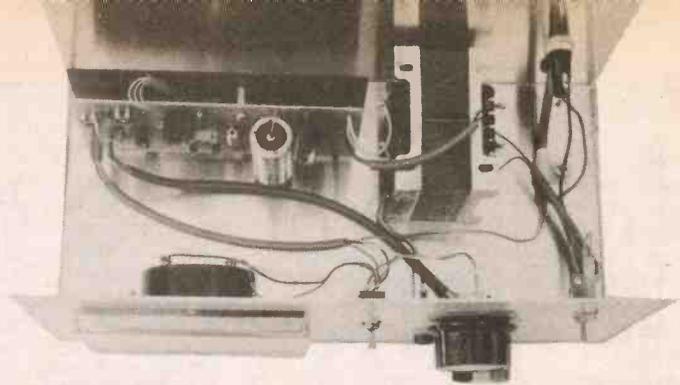Completed early prototype showing relettered panel meter.



Close-up showing mounting of heatsink/circuit board.

turn drives the base of TR2. This, along with series controller TR1, forms a Darlington pair which controls the effective resistance of TR1 and so regulates the output against unwanted variations in the manner already described.

The current limiter this time is TR3 which senses the voltage developed across resistor R5, a part of which is tapped off by way of preset VR2. In this way the maximum output current can be set to 1A, or anything smaller if you so desire. The output is smoothed by capacitor C3 and protected against reverse input transients by diode D5.

CONSTRUCTION

The 0-30V unit is built in exactly the same way as the previous project. All components except the mains transformer T1, the voltage adjust potentiometer VR3, the meter and the meter switch S2 are assembled on a printed circuit board. This board is also available ready-drilled from the *EE PCB Service*, code EE000.

The component layout and full size copper foil master pattern is shown in Fig. 4.9 and should, by now, need little explanation. All the important points to watch are identical with those mentioned earlier. The meter multiplier resistor R6 is made up from two 300k Ω , 1 per cent resistors in series — if you are using the specified meter that is.

Interwiring from the circuit board to off-board components can be carried out by referring to Fig. 4.9 and the photographs. Two pairs of leads from the points Z-Z and X-X go to the mains transformer secondary windings of 32V and 15V respectively.

Four leads from points A, B, C and D on the board go to the meter switch S2, which this time is a double-pole changeover miniature toggle (or you may use a slide type if you wish); two leads are taken to the voltage adjust potentiometer VR3, one of which is common to the output positive lead; and the positive and negative outputs themselves. Use at least 16/0.2mm flexible wire for the transformer connections and the output leads.

After completing the board and drilling the two fixing holes marked F, mark these through on to the heatsink, and drill these and the TO3 case fitting holes for TR1 in the same way as was described previously. Transistor TR1 should now be fitted to the heatsink, and the board screwed in place, using 1/2in spacers; refer back to Fig. 4.6. Three coloured leads from points C, B and E should be soldered to TR1 pins.

The assembly, together with the various other components can then be fitted into a suitable case and the panel layout can again follow that suggested in Fig. 4.7. The meter this time, of course, is calibrated 0-50V, 0-1A (see "Meter Scale" Section).

TESTING

Set preset VR1 and rotary control VR3 fully anticlockwise (all in), presets VR2 and VR4 to mid-position. Note that VR3, the front panel voltage control, is wired so that all the track resistance is in circuit with the wiper fully anticlockwise viewed from the front.

Set the meter switch S2 to VOLTAGE and after switching on, advance the voltage control carefully. The voltage output should rise and when the control is fully clockwise, preset VR4 should be adjusted until the meter reads exactly 30V f.s.d.

To calibrate the current reading, switch to CURRENT on the meter switch and connect a load resistor in series with an ammeter across the output terminals. Adjust VR1 until the panel meter reads identically to the external ammeter.

(right) completed power supply showing interwiring and positioning of components.

(below) Layout of components on completed printed circuit board.

If you don't have another ammeter as a checker, connect a known resistance (say 10 Ω , 3W) across the output terminals and advance the voltage control to provide, say, 5V output (as seen on the voltmeter). The current will now be 0.5A, so switch over to CURRENT and adjust VR1 accordingly. If you don't fancy all this, just replace VR1 with an 18k Ω , 1 per cent resistor (0.5W) and the current reading will be sufficiently accurate not to lose any sleep over.



CURRENT LIMIT

The current limit of 1A now has to be set. Turn the voltage control to minimum, switch over to CURRENT, and put a short-circuit across the output. Advance the voltage control so that the meter goes over to f.s.d. or thereabouts, then adjust VR2 until the current is just below the 1A reading.

What you aim for is a f.s.d. reading of 1A when the output is shorted — nothing more. If the meter cracks over, you haven't adjusted VR2 properly.

You can, if you wish, set the current limit to any value less than 1A; simply adjust VR2 to give you that limit when the output is short circuited. Like the previous design, the voltage will then not increase above the point at which the current has reached its limiting value.

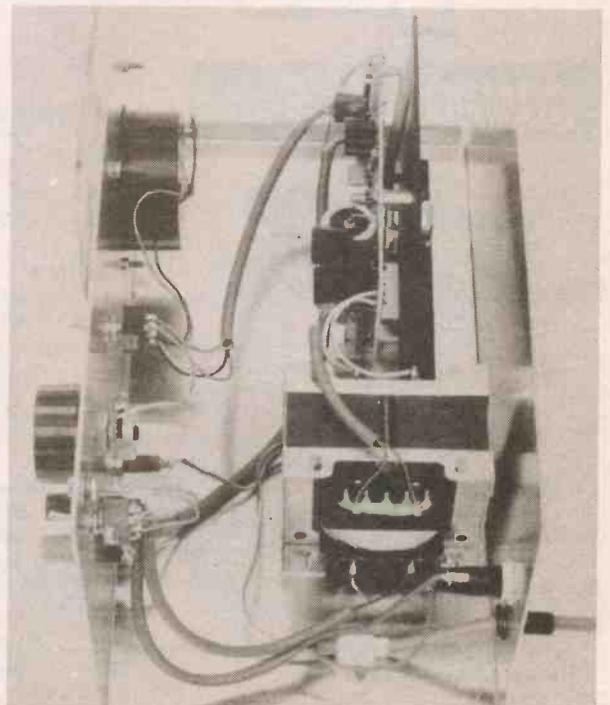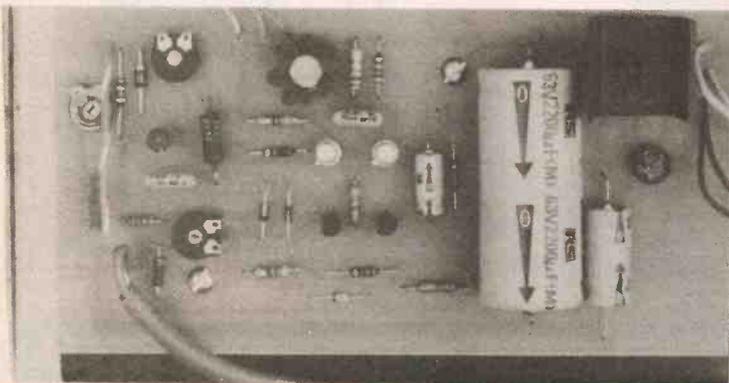Next Month: A Variable Stabilized Power Supply, with four switched current limits up to 2A will be described.



New Series


LOGO, LEGO

AND

THE SPECTRUM

ALAN HARPER

Part 1

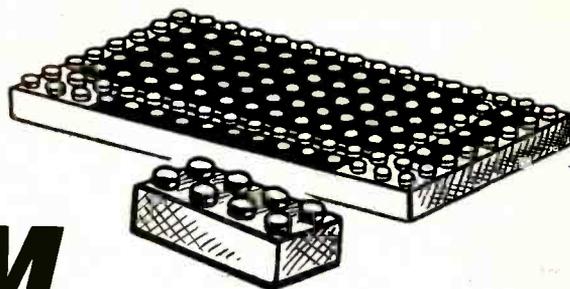

Build this interface card and introduce your Spectrum to the excitement of Legoland

THE objective of the project described below was to provide an environment for experimentation in simple robotics which would enable my three children (and myself) to extend the experience in the turtle graphics language LOGO which the children had begun in school.

To meet this objective an interface was constructed to enable our Spectrum computer to control robots constructed from Technical Lego. The interface is a simple 8 bit latch/buffer configuration which drives up to eight relays and can receive inputs from up to eight mechanical switches. As the equipment is intended for unsupervised use by youngsters the mechanical and electrical robustness formed a key element of the overall design.

The construction of viable robots from Technical Lego requires an elementary appreciation of the principles of gears and levers. This is dealt with briefly later in the article. Several simple LOGO procedures are described which enable LOGO to swiitch the Lego motors via the relays and read the states of the switches which can be configured, for example, as collision indicators.

Though configured for a Spectrum and the LOGO language the interface described below could easily be adapted for any home computer. All that is required is appropriate address decoding. In addition to LOGO this article also includes some simple BASIC routines which are useful for quick tests on the interface.

MOTIVATION - THE LOGO LANGUAGE

In many schools the first and sometimes only computer language that students use is the turtle graphics language LOGO. The LOGO language, at its most elementary level, allows the student to "drive" a turtle around the screen. The commands are simple and are entered in a direct mode.

For example:

> FD 10 LT 90

This will cause the turtle to move forward ten units and turn left (anti-clockwise) through a right angle. (">" is the prompt.)

> REPEAT 4 [FD 10 LT 90]

This will draw a square of side ten units.

In addition new instructions can be defined.

> TO SQ :X

> REPEAT 4 [FD :X LT 90]

> END

This defines a new procedure which draws a square of side "X" units. You enter > SQ 20 to draw a twenty unit square.

The language is totally procedural. (No line numbers/no GOTO's.) In most school configurations the instructions may also be given to a floor turtle in which a retractable pen is mounted so that the output can be drawn on large sheets of paper.

The advocates of LOGO claim that it teaches good structured programming from the outset but more importantly, in a teaching environment, it provides concrete experience rather than abstract mathematical ideas. By working in small groups students learn to communicate with each other using the language of mathematics rather than mathematics being an isolated activity.

If LOGO achieves half these broad objectives it will be well worth the effort involved. To continue this worthwhile activity within the home we bought the LOGO language as soon as it was released for the Spectrum. Even though the school uses BBC and Commodore computers most releases of LOGO are very similar. Any variations are in general extensions to the common core of functions.

Initially we used LOGO in a screen turtle mode. Clearly the next move had to be the extension to the outside world. After some thought it was decided to construct a simple latch/buffer interface driving relays and reading switches which could control robots constructed from Technical Lego of which a large supply was readily available. By this means it is hoped to extend the boundaries of LOGO in a manner consistent with the basic principles of learning by involvement and experimentation.


Initially it is envisaged that the students involvement will be at a software level as with the standard system though the turtle may have changed its shape and tasks capabilities significantly (e.g. a wandering robot with a gripper) however the use of Lego and the configuration of the interface permits the students' involvement to easily extend into the electro-mechanical aspects of the robot construction and motor wiring.

THE INTERFACE - OVERALL DESIGN

The system block diagram is shown in Fig. 1. The computer control and address buses are input to address decoding logic. The decoding logic produces two enable signals which control a latch and a tri-state buffer. The latch and buffer are connected to the computer data bus.

The outputs of the latch and the inputs to the buffer are electrically isolated from the remaining circuitry using optical isolators. This prevents any subsequent mis-wiring of the robot motors and collision detection switches from damaging the computer. The latch/optical isolator is followed by a relay driver and eight relays which control the supply of power to the Lego motors. Since the inputs to the buffer originate from mechanical switches they are first passed through a de-bounce circuit.

Fig. 1. System block diagram.

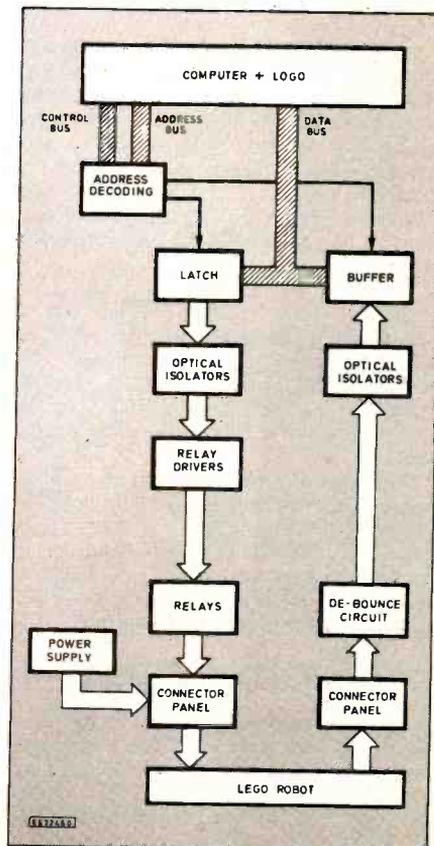

The output which becomes low is in fact the decimal value of the three bit binary word ($A_2+A_1+A_0$). For example $A_2=1$, $A_1=1$, $A_0=0$ give $(4+2+0)=6$, hence Y6 (Pin 9) goes low.

For this project only one output line from each decoder is required. However, this configuration provides effective decoding of all read/write requests in the upper half of the input/output map. In my own configuration the remaining signals are routed via the edge connector to the spare lines on the motherboard. This will make further address decoding for subsequent projects trivial.

Latch/Buffer

IC5 (74LS244) is a tri-state buffer. The chip has two independent sections. However for this application this feature is ignored and the enable low signal is connected to both pins 1 and 19. When the enable signal from the decoder output is low the eight inputs are connected through to the Spectrum data bus.

IC6 (74LS373) is Octal D-type Latch. This device requires a positive enable pulse at pin 11 to latch the data bus signals into the output ports. This was obtained by using one element of IC4 (74LS00—four 2-input NANDS). For clarity, Fig. 3 shows the connections to one element of the data bus—DO. Connections to D1-D7 follow logically to the remaining pins of each device.

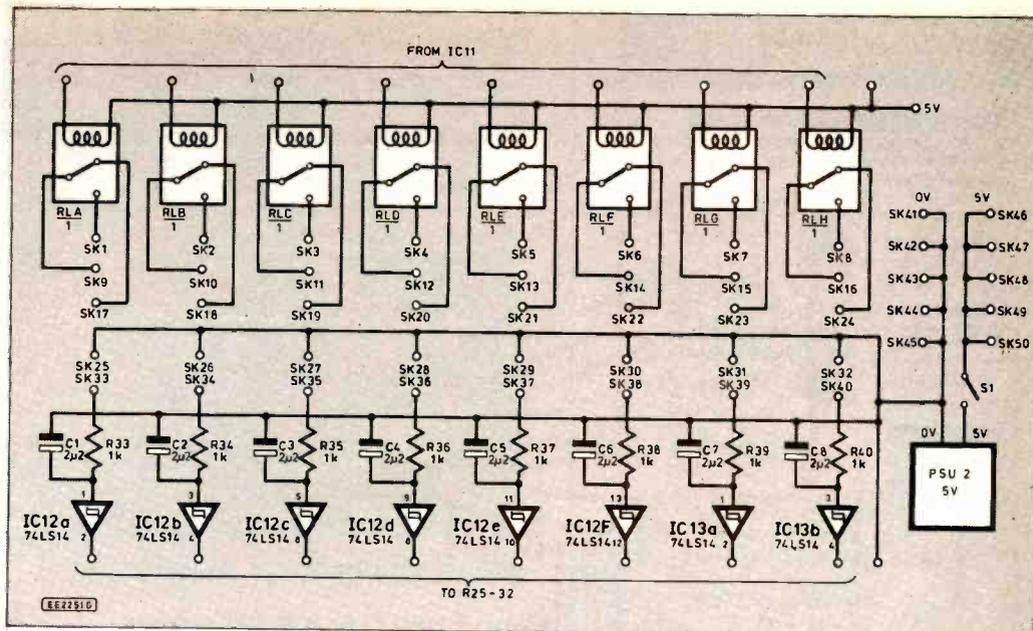


Fig. 5. Circuit diagram for the interface box.

minature p.c.b. mounting relays. The device used is 6V s.p.d.t. as shown in Fig. 3. The operating voltage range is 4.5V to 7.8V. Clearly these relays provide a further level of electrical isolation.

The eight relay outputs connect to a matrix of 3×8 1mm sockets mounted on the top of the interface box.

De-bounce circuits

Mechanical switches do not always make and break "cleanly". They can suffer "contact bounce" which produces a series of

directly from the computer 5V rail available at the edge connector. Alternatively if this supply is becoming stretched an auxiliary 5V stabilised source is recommended.

The other p.s.u. (PSU2) must power the right hand sections of IC7 to IC10, IC11 to IC13, the coils of the eight relays and all the Lego motors (four or five perhaps). The i.c.'s need a stabilised 5V, the relay coil will operate from 5V and, although the Lego motors usually use $3 \times 1.5V$ (4.5V), they work without any problems at 5V. Hence a stabilised 5V supply meets all the requirements.

The elements of PSU 2 are shown in Fig. 4. This is a common basic design though any design for a 5V 1A p.s.u. would be suitable. If an auxiliary supply is also required for PSU 1 an identical design could be used. It is suggested that these supplies are built to the design shown last month in the *Stabilized Power Supplies* series—see page 584 Sept. 89 EE. A 12V 1A mains transformer can be used for each 5V supply. The p.c.b. is available from the EE PCB Service.

CONNECTIONS

The array of 1mm sockets on the surface of the interface box (SK1 to SK50) is shown in Fig. 5. SK1 to SK24 are the connections to the relays. They are arranged in a 3×8 array. The least significant bit on the data bus switches RLA. When RLA is switched the connection of SK9 toggles between SK1 and SK17.

The inputs are connected to SK25 to SK40. Joining SK25 to SK33 together by a switch such as a collision detector will cause 5V (a "1") to appear on the least significant bit of the data bus.

SK41 to SK50 provide power for the Lego motors. By routing the 5V supply to the motors via the relays the signals on the data bus may be used to control the action of the motors. Some ideas for motor/relay wiring are given later.

A panic button (S1) which switches off power to the motors is included. This is particularly useful when the software crashes since without such a switch it can leave a robot heading for the top of the stairs with no quick way of stopping it.

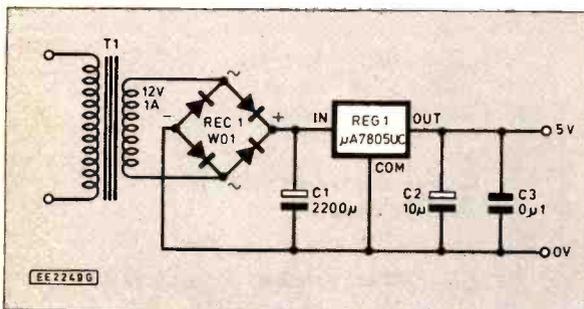


fig. 4. Suggested circuit diagram for the two power supply units (P.S.U.'s).

Optical Isolators

The outputs of the latch (IC6) and the inputs to the buffer (IC5) are electrically isolated from the subsequent circuitry by optical isolators. These ensure that no damage can be done to Spectrum by any incorrect wiring at the interface box sockets. The device used contains four isolators in a 16 pin d.i.l. package.

Relay Driver and Relays

The optically isolated latch outputs from IC9 and IC10 are connected to a relay driver IC11 (ULN2803A). This device provides eight outputs which can each supply up to 500mA at up to 50V. The device includes internal diodes to prevent the back e.m.f. of inductive loads damaging any preceding circuitry. This specification makes this device particularly suitable as a relay driver for this application.

Some relays can be somewhat bulky. To avoid this problem use was made of ultra-

noise spikes which can cause problems in digital systems. The problems will depend on how quickly the inputs are read and how these signals are interpreted by the software.

To avoid any possible problems a de-bounce circuit was included in the input lines. The resistor/capacitor network (R33/C1 etc) smooths the input signal which results from closing a switch between SK25 and SK33. The smoothing eliminates some of the noise. Further protection is provided by the hysteresis of IC12 (74LS14) which is a Schmitt trigger. (There are six Schmitt triggers in each 74LS14 so two devices are required for the eight inputs).

5V POWER SUPPLY

Two separate power supply units (p.s.u.s) are required.

One p.s.u. (PSU1) powers IC1 to IC6 and the left hand sections (see Fig. 3) of IC7 to IC10. This can be derived either

COMPONENTS

Interface Card and Interface Box

Resistors

R1 to R8 100 (8 off)
R9 to R24 1k (16 off)
R25 to R32 100 (8 off)
R33 to R40 1k (8 off)

Potentiometers

VR1, VR2 102W cermet type mounted adjacent to Lego motors (2 off)

Capacitors

C1 to C8 2.µ2 elect. 63V (8 off)

Semiconductors

IC1 74LS30 eight input NAND gate
IC2, IC3 74LS138 3 to 8 line decoders (2 off)
IC4 74LS00 quad 2-input NAND gate
IC5 74LS244 octal buffer
IC6 74LS373 octal D-type latch
IC7 to IC10 quad opto-isolator (4 off)
IC11 ULN2803A octal Darlington driver array
IC12, IC13 74LS14 Hex Schmitt trigger inverter (2 off)

Relays

RLA to RLH6V ultra-miniature relay (Maplin FM91Y or similar)

Sockets

SK1 to SK8 1mm black (8 off)
SK9 to SK16 1mm red (8 off)
SK17 to SK24 1mm black (8 off)
SK25 to SK45 1mm black (21 off)
SK46 to SK50 1mm red (5 off)
Plus 10 black and red 1mm plugs (you may need more eventually).

Miscellaneous

Suitable case; S1 s.p.s.t. toggle switch; ribbon cable (20 way); 2x10 way p.c.b. ribbon cable connectors; p.c.b. available from the *EE PCB Service*, order code EE660; 2x28 way Spectrum edge connector; i.c. sockets; connecting wire, etc.

Approx. cost
Guidance only

£60


INTERFACE CARD CONSTRUCTION

As indicated earlier the project is split into two separate sections. The interface card was constructed as a home made p.c.b. and carries IC1 to IC11 as indicated in Fig. 6. The board is available from the *EE PCB Service*, Order Code EEXXX.

Address decoding could have been achieved using CMOS chips. However, since for test purposes the board required repeated handling after insertion of the address decoding logic this option was rejected.

When constructing a project of this complexity much time and frustration can be saved by a policy of progressive testing during construction. I firmly believe that provision for testing should form part of the basic circuit design.

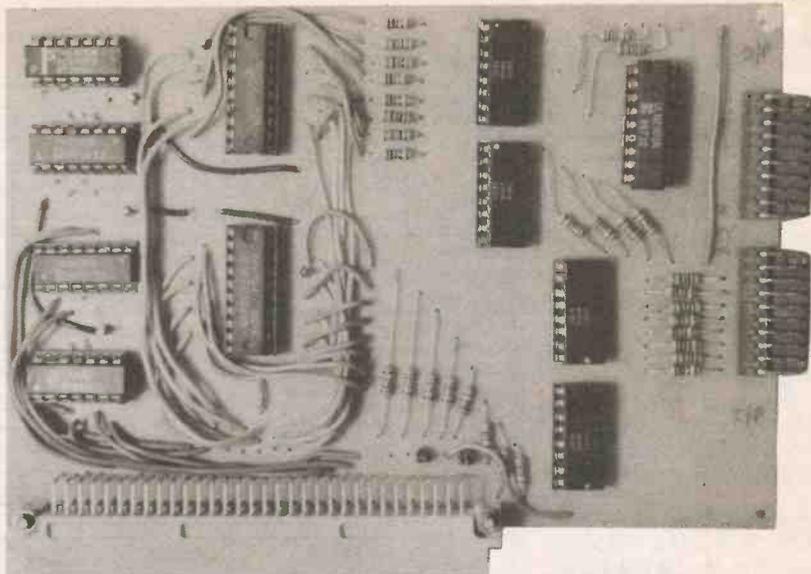Construction proceeded as follows: test all p.c.b. tracks for continuity. Then insert



Interface Card PCB notes

- 1) The p.c.b. layout connects power to all chips.
- 2) The data bus is re-arranged (by wire links) into numeric order prior to connection to IC5 and IC6.
- 3) Wire links.

The board contains many cross track wire links on the component side of the p.c.b. Some of these are shown on the diagram. However, to prevent confusion a wiring plan for the 2x28 way Spectrum edge connector and the latch and buffer chips (IC5 and IC6) is given in tabular form below.

Edge

Connector Name	to IC Pin	Pin and IC	Pin	Comments
D0	6A 5	3 6	3	IC5=LS244-Input Buffer
D1	7A 5	5 6	4	IC6=LS373-Output Latch
D2	8A 5	7 6	7	
D3	11A 5	9 6	8	Connections are made via the "unscrambled" data bus pads.
D4	12A 5	12 6	13	
D5	10A 5	14 6	14	
D6	9A 5	16 6	17	
D7	3A 5	18 6	18	
A0	9B 1	1 1		IC1=LS30 -NAND gate
A1	10B 1	2 2		IC2=LS138-Decoder
A2	11b 1	3 3		IC3=LS138-Decoder
A3	12B 1	4 4		
A4	24B 1	5 5		
A5	23B 2	2 3	2	Connections are made first to IC3 then to IC2
A6	22B 2	3 3	3	
A7	21B 1	6 6		
IORQ	17A (5	2) 5	3	Connection to IC2 is via a p.c.b. track
RD	18A 4	3 3		Be certain to get these two the right way round.
WR	19A 4	2 2		
0V	6/7B			Provision is made on the p.c.b. for the power to be provided from either the Spectrum or an auxiliary p.s.u. by connection to p.c.b. pins. Do not mix up these connections - this is an expensive area for errors.
5V	3B			

4) Inputs to and outputs from IC5 (Buffer) and IC6 (Latch).

The data bus connections to IC5 and IC6 are given above. The path through these chips is indicated below. The pins given in brackets are the pins to which the edge connector is connected as defined in section 3 above.

	IC5 - Buffer Pin		IC6 - Latch Pin
D0	(3) - 17	(3)	- 2
D1	(5) - 15	(4)	- 5
D2	(7) - 13	(7)	- 6
D3	(9) - 11	(8)	- 9
D4	(12) - 8	(13)	- 12
D5	(14) - 6	(14)	- 15
D6	(16) - 4	(17)	- 16
D7	(18) - 2	(18)	- 19

Wire link connections to the optical isolators and relay drivers follow logically and are visually obvious.


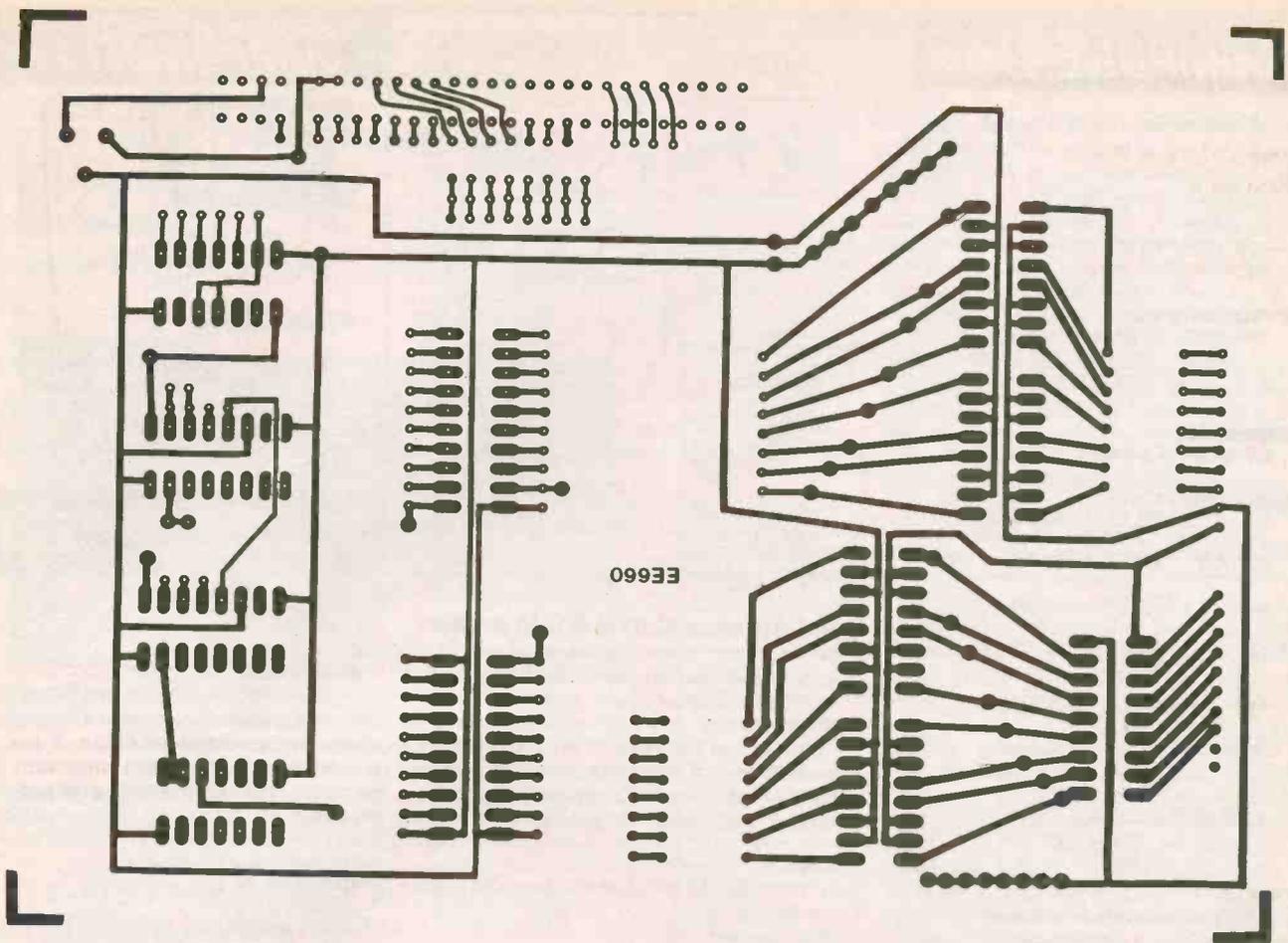


Fig. 6. Component layout and full size printed circuit board copper foil master for the Interface Card.

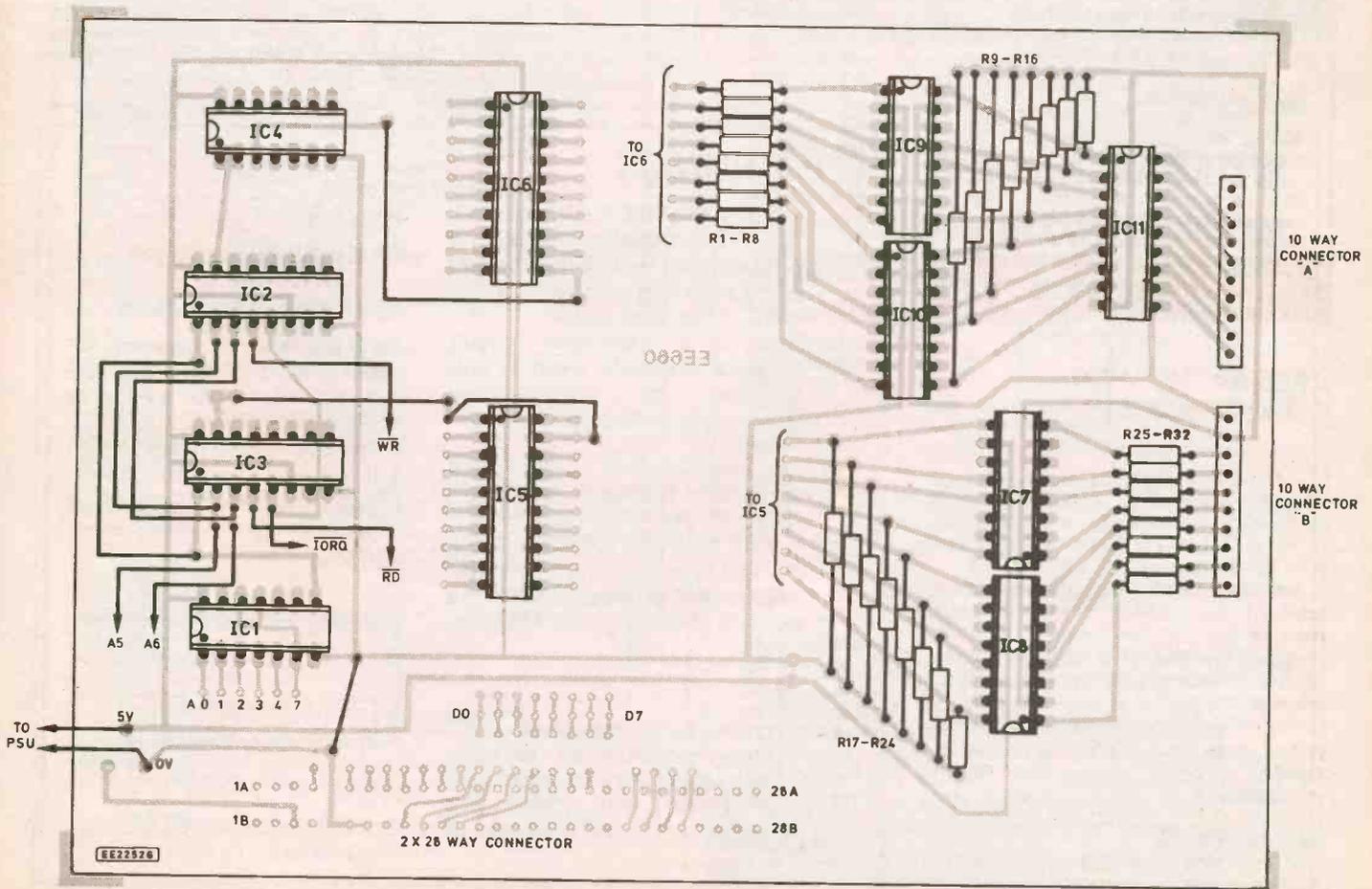

APPENDIX A PULSE DETECTOR

When testing circuits which produce single very short positive or negative pulses a simple pulse detector is an invaluable tool. (I'm surprised they are not included in the standard multimeter.) A suitable design is shown in Fig. A1. Essentially it is a flip-flop which is reset by S2. This brings the l.e.d. on. SK1 and SK2 are connected to the power rails of the circuit under test.

To detect a low pulse connect S1 to SK3 and connect SK3 to the chip output which is expected to produce a low pulse. When the low pulse occurs the l.e.d. will go off. To detect a high pulse S1 is connected to the pin 8 of IC1d and SK2 is connected to chip output which is expected to produce a high pulse. (IC1d just inverts the high pulse.)

This unit can either be built on some scrap Veroboard or housed in a small box

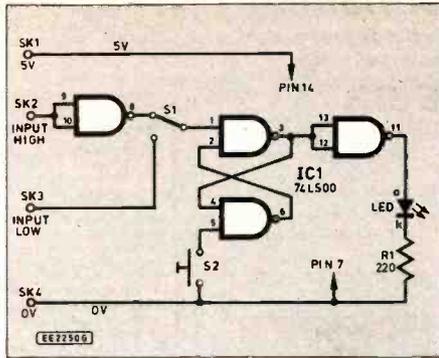


Fig. A1. Circuit diagram for a Simple Pulse Detector.

with smart terminals and probes. If the latter solution is adopted the cost will be about four pounds.

COMPONENTS

PULSE DETECTOR

Resistor

R1 220

Semiconductors

IC1 74LS00 quad 2-Input NAND
LED1 light emitting diode (red)

Miscellaneous

S1 s.p.s.t. toggle switch
S2 push to make switch
SK1 to SK4 4mm sockets (4 off)
Suitable case and probes (if required); small piece of Veroboard; i.c. socket; connecting wire, etc.

Approx. cost
Guidance only

£4

all i.c. sockets, edge connectors and cross track wiring. Test continuity throughout. This is your last chance to find those simple dry joints or broken wires before they cause a frustrating array of peculiar faults (I write from bitter experience!).

Check and insert all resistors. Check again. Check capacitors, this can be crudely done by charging them up with a battery and then testing with a voltmeter. Then insert the capacitors.

Insert the decoding chips IC1, IC2, IC3, and IC4. To test the decoding logic it is necessary to first connect the interface card to the Spectrum. Ensure the Spectrum is switched off first. If this precaution is ignored it is possible by a half space misalignment to effectively connect all the expansion socket connections together! **This can virtually destroy the Spectrum.**

When the BASIC instruction OUT 159,255 is executed pin 15 of IC2 should go briefly to 0V. We now meet the first problem. The length of the low enable pulse is too short to detect with a voltmeter. If an

oscilloscope is available then it could be used. Alternatively, if you cannot spare the money for an oscilloscope I recommend my "poor mans' oscilloscope" shown in the Appendix. This is a pulse detector which can be built at very little cost using some Veroboard and an 74LS00. See the Appendix for details. This instrument will indicate a low or high pulse by the switching off of an l.e.d. This device can also be used to test for a low enable pulse at pin 15 of IC3 which should occur when the instruction LET X= IN 159 is executed. Once this test is complete disconnect the interface card from the Spectrum.

Insert Optical Isolators IC7 to IC10 and test. This requires two power supplies for testing purposes (4.5V batteries will do). When power is applied to the end of resistor R1 check that the correct voltage appears at pin 16 of IC9. Similar checks can be conducted on all isolators. Insert IC11. Repeat the above tests through to the output of IC11. Insert the latch and buffer IC5 and IC6. Re-connect to the Spectrum. Test

the latch IC6 as follows:

10 INPUT NN
20 OUT 159,NN
30 GOTO 10

Try NN=1,2,4,8,16,32,64,128 in turn and check that the appropriate voltages appear at the outputs of IC's 6, 9, and 11. For this test the Spectrum will power half the board. PSU 2 can now be used to power the other half. Be careful of the mains wires if they are still exposed. To test the tri-state buffer enter the programme,

10 PRINT IN 159
20 GOTO 10


Apply 5V to the input ends of R25 to R32 in turn and check that the PRINT on the screen reads 1,2,4,8,16,32,64,128 in turn.

Stage by stage testing is tedious. However, by following something like the system indicated above it is possible to construct a reasonably complex circuit with a good degree of confidence in the final product. It can save much time at a later date. **Next Month:** Interface box, final assembly and software routines.


INTRODUCING DIGITAL ELECTRONICS

Answers to Part 12

1.

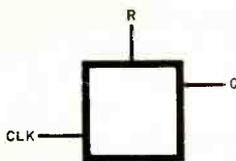

2.

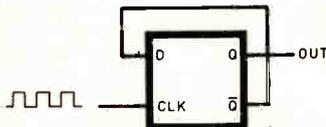

3. Combinational logic devices lack memory, they are the primitive logic elements which, by the application of feedback, can be configured to form sequential logic functions.

4. Input data at the D input is transferred to the Q output after receipt of a pulse at the CLK input.

For both the CMOS 4013 and TTL 7474 flip-flop devices the bit on D is transferred to Q on the positive going edge (the low to high transition) of the clock pulse.

- This is a sequential circuit because it contains memory and operates by automatically sequencing through a number of states.
- The arrangements in sets 1, 2, 3 and 4 form the basic gates NOT, AND, OR and EXOR respectively. NAND, NOR and EXNOR may be derived by connecting an inverter (e.g. a set 1 arrangement) to the outputs of sets 2, 3 and 4 respectively.

Note.


The City and Guilds objectives in Section 9 of the logbook, those relating to health and safety, must be completed in addition to the work done in this series at your local Assessment Centre.

PLEASE TAKE NOTE

Part Eleven (August 1989)

Page 523. In the "Appendix N" panel the i.c. pinout information for the 7400 device is shown incorrectly.

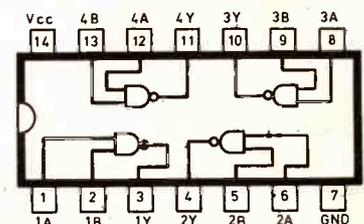The two NAND gates at pins 8-10 and 11-13 have been transposed. The correct outline is shown below:




QUAD 2 INPUT NAND GATES
TTL 7400 (CMOS 4011)

Need an extra pair of hands?

It's often the case that conventional methods just won't do. Fortunately there is now an alternative with the

MULTI-PURPOSE JIG

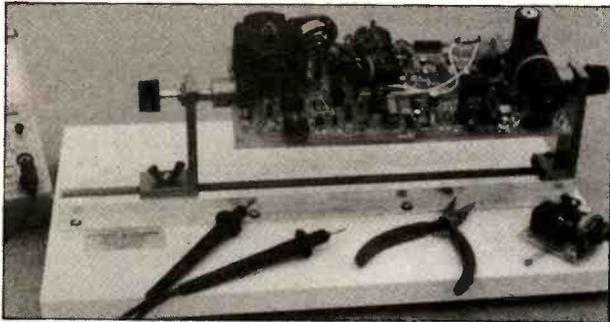It will hold a circuit board steady for assembly and wiring—It can hold things while glue sets—It can hold models for painting and repair—All its interchangeable heads rotate through 360 degrees so you can position your workpiece to best advantage—no need to take it out to turn it over either—just rotate it to where you want it. Precision spring loaded head for holding pressures of up to 5.5lbs.



Each jig is hand built for a lifetime of use. Supplied with circuit board assembly head, 12.5mm rubber faced heads and static discharge lead. Other heads and accessories available.

Standard jig takes items up to 310 x 145mm **£19.50**
Mini jig takes items up to 148 x 85mm **£16.50**

inc. VAT and carriage

Local authority, school and college orders welcome
EVERETT WORKSHOP ACCESSORIES
5 Railway Terrace, Henllan, Llandyssul,
Dyfed SA44 5TH Tel: 0559 371226

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60 OUTPUT 0-280V
200W 0.1 amp max £24.00 p&p £3.00 (£31.05 inc VAT)
0.5KVA 2.5 amp max £26.50 £3.75 (£34.79 inc VAT)
1KVA 5 amp max £34.00 £4.25 (£43.99 inc VAT)
2KVA 10 amp max £49.00 £5.50 (£62.88 inc VAT)
3KVA 15 amp max £65.00 £6.25 (£81.94 inc VAT)
5KVA 25 amp max £115.00
Carriage on request



VOLTAGE CHANGING TRANSFORMER

1250 Watt auto. Tapped 0-90V, 100, 110, 115, 120, twice to obtain voltages between 90 and 240V. Fitted in heavy duty (toured) metal case. Fused input. Price incl VAT & p&p £39.50.

COMPREHENSIVE RANGE OF TRANSFORMERS-INSULATION & AUTO (110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES
4ft 40 watt £10.44 (£12.00 inc VAT) Caller only (£9.99 inc VAT)
2ft 20 watt £7.44 + £1.25 p&p (£7.53 inc VAT)
13in 10 watt £5.80 + 75p p&p (£6.38 inc VAT)
12in 8 watt £4.80 + 75p p&p (£5.12 inc VAT)
9in 6 watt £3.60 + 50p p&p (£3.60 inc VAT)
6in 4 watt £3.60 + 50p p&p (£3.60 inc VAT)

230V AC BALLAST KIT for either 6in, 9in or 12in tubes £5.50 + 55p p&p (£6.36 inc VAT)
For 13in tubes £6.00 + 75p p&p (£7.75 inc VAT)

400 WATT UV LAMP

Only £28.00 + £2.50 p&p (£35.08 inc VAT)

175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS

Available with BC or ES fitting. Price incl VAT & p&p £19.84.

12 VOLT BILGE PUMPS

Buy direct from the importers

500 GPH 15ft head 3 amp £16.00 inc.

1750 GPH 15ft head 9 amp £19.25 + £2.00 p&p (£25.00 inc VAT)

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit pair of bi-pin leads neon indicator on/off switch safety microswitch and circuit £14.00 + £2.00 p&p (£18.40 inc VAT)

SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical users etc. Approx 16 joules. Adjustable speed £48.00 + £2.00 p&p (£57.50 inc. VAT)

Case and reflector £22.00 + £2.00 p&p (£27.60 inc VAT) SAE for further details including Hy-Light and Industrial Strobe Kits.

Ample Parking Space

Showroom open Monday/Friday

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

01-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquires

WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled can be used for a variety of purposes. Inlets 1 1/2 ins. Outlet 1 inch. Price including p&p and VAT — £10.95 or 2 for £20 including p&p and VAT.

SPECIAL OFFER AC CAPACITORS

1.5 MFD 440V £2.00 5 MFD 440V £4.00
2 MFD 440V £2.50 5.4 MFD 280V £2.00
4.1 MFD 440V £3.50 5 MFD 660V £3.00
12 MFD 400 £4.00
p+p 50p per unit plus VAT to be added to total.

TORIN CENTRIFUGAL BLOWER

230V ac 2,800 RPM 0.9amp 130mm diameter impeller outlet 63 x 37mm overall size 195 x 160 x 150mm long. Price £1750 + £2.50 p&p (£23 inc. VAT)

SHADED POLE GEAR MOTORS

In the following sizes:
9 RPM 12 RPM 80 RPM 160 RPM 110V AC or 240V AC with capacitors (supplied). Price incl VAT & p&p £12.65

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price incl VAT & p&p £33.00.

12 V DC COOLER EXTRACTOR FAN

New brushless motor 92mm sq. Price incl VAT & p&p £11.50.

SOLID STATE EHT UNIT

Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £1.00 p&p (£10.93 inc VAT) NMS

COOLING FANS-BRAND NEW!

200/400V AC American Boxer 'Peewee' 7-bladed high efficiency cooling unit 80mm sq x 40mm deep 40c/m approx. Price incl VAT & p&p £10.35.

EX-EQUIPMENT FANS 120mm sq x 38mm deep in either 115V or 230V AC Tested and guaranteed. Price incl VAT & p&p £7.76.

Large selection of various speed geared motors from stock. Phone or write for details.

From stock at prices that defy competition
C/F Blowers Program Timers
Microswitches Synch Motors
write/phone your enquires

NMS = NEW MANUF SURPLUS
R&T = RECONDITIONED AND TESTED

Carbon Film resistors 1/4W 5% E24 series 0.51R to 10M0	1p
100 off per value—75p, even hundreds per value totalling 1000	£6.00
Metal Film resistors 1/4W 10R to 1M0 5% E12 series—2p, 1% E24 series	3p
Mixed metal/carbon film resistors 1/4W E24 series 1R0 to 10M0	11/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 4M7 E6 series	7p
Miniature polyester capacitors 250V working for vertical mounting	
015, 022, 033, 047, 068-4p, 0.1-5p, 0.12, 0.15, 0.22-6p, 0.47-8p, 0.68-8p, 1.0-12p	
Mylar (polyester) capacitors 100V working E12 series vertical mounting	
1000p to 8200p - 3p, .01 to .068 - 4p, 0.1 - 5p, 0.12, 0.15, 0.22-6p, 0.47/50V-8p	
Submin ceramic plate capacitors 100V wkg vertical mountings. E12 series	
2% 1.8pf to 47pf - 3p, 2% 56 pf to 330pf - 4p, 10% 390p - 4700p	4p
Disc/plate ceramics 50V E12 series 1PO to 1000P, E6 Series 1500P to 47000P	2p
Polystyrene capacitors 63V working E12 series long axial wires	
10pf to 820pf - 3p, 1000 pf to 10,000pf - 4p, 12,000 pf	5p
741 Op Amp - 20p, 555 Timer	22p
cmos 4001 - 20p, 4011 - 22p, 4017	40p
ALUMINIUM ELECTROLYTICS (Mids/Volts)	
1/50, 2.2/50, 4.7/50, 10/25, 10/50	5p
22/16, 22/25, 22/50, 47/16, 47/25, 47/50	6p
100/16, 100/25 7p; 100/50 12p; 100/100	14p
220/16 8p; 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
Submin, tantalum bead electrolytics (Mids/Volts)	
0.1/35, 0.22/35, 0.47/35, 1.0/35, 3.3/16, 4.7/16	14p
2.2/35, 4.7/25, 4.7/35, 6.8/16 15p; 10/16, 22/16	20p
33/10, 47/6, 22/16 30p; 47/10 35p; 47/16 60p; 47/35	80p
VOLTAGE REGULATORS	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V	55p
DIODES (piv/amps)	
75/25mA 1N4148 2p, 800/1A 1N4006 6p, 400/3A 1N5404 14p, 115/15mA OA91	6p
100/1A 1N4002 4p, 1000/1A 1N4007 7p, 60/1.5A 51M1 5p, 100/1A bridge	25p
400/1A 1N 4004 5p, 1250/1A BY127 10p, 30/1.5A OA47	8p
Zener diodes E24 series 3V3 to 33V 400 mW - 8p, 1 watt	12p
Battery snaps for PP3 - 6p for PP9	12p
L.E.D.'s 3mm, & 5mm, Red, Green, Yellow - 10p, Grommets 3mm - 2p, 5mm	2p
Red flashing L.E.D.'s require 5V supply only	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A Q/blow 5p, A/surge 8p, Holders pc or chassis	5p
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0mm - 30p, Machines 12V dc	£7.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£3.50p
AA/HP7 Nicad rechargeable cells 80p each. Universal charger unit	£6.50p
Glass reed switches with single pole make contacts - 8p, Magnets	12p
TRANSISTORS	
BC107/8/9-12p, BC555/8/9-8p, BC182L4L-10p, BC183, 183L-10p, BC212, 212L-10p, BC327, 337, 337L-12p, BC727, 737-12p, BD135/6/7/8/9/-25p, BCY70-15p, BFY50, 52-20p, BFX88-15p, 2N3055-50p, TIP31, 32-30p, TIP41, 42-40p, BU208A-£1.20, BF195, 197-12p	

THE CR SUPPLY CO

127 Chesterfield Rd, Sheffield S8 0RN

Return posting

JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.

SK18 Soldering Kit. £18.34

Build or repair any electronic project.

LC18 240v 18w iron with 3.2, 2.4,

and 1.6mm bits. Pack of 18 swg

flux-cored 60/40 solder. Tweezers,

3 soldering aids. Reel of De-Solder

brander. In PVC presentation wallet.



ADAMIN Miniature Iron £8.58

Possibly smallest mains iron in the world. Ideal for fine work. Slim

nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.

'L' Series Lightweight Irons. 12w £8.57

High efficiency irons for all electronic hobby work. Non-roll handles with finger guards.

Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12

18w £8.64
model, 12w, 2.4mm bit. LC 18 Model, 18w, 3.2mm bit. 240v Std - 12v available. Presentation wallet.


Soldering Iron Stands 3&4 £6.65

Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits. No 5 stand for EC50 iron No 4 stand for ADAMIN miniature Iron No 3 stand for LA12 and LC18 irons.



De-Solder Pumps £7.75

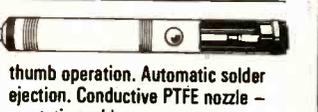High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.



Prices include p&p and VAT. Send order with Cheque/PO. Ring for Access/Visa sales

LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. EE
97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 01 689 0574

FOR YOUR ENTERTAINMENT

BY BARRY FOX

Airvision

Until recently, Brits only got the chance to enjoy in-flight entertainment if they went on long haul flights to America or further afield. Now things are changing. Like airlines in Japan and the US, airlines in Europe, are now starting to get in-flight entertainment on short haul flights.

On long haul flights you get a selection of audio entertainment, on headphones, and either one or two films, usually projected on a screen at the front of the cabin.

Projection used to be from Super 8 film, now it's from video, usually Beta format because Sony has close ties with systems supplier Trans Com of California — in fact Sony now owns the company, having bought it from parent company Sundstrand. Standard Beta tapes give better pictures than standard VHS tapes, and with Beta now failed as a domestic format, there is less risk of tape pilferage.

Some airlines install TV monitors in the passenger cabin, either instead of a video projector and screen, or they use monitors to fill in "blind" areas of the cabin where passengers cannot get a good view. The latest trend is to give passengers individual screens.

British Airways has been testing *Airvision*, a personal viewing system jointly developed by Philips and Warner Brothers. A small l.c.d. (liquid crystal display) colour screen is built into the back of each seat and a push button control panel lets passengers choose between six video programmes simultaneously sourced from six VHS recorders. BA is testing *Airvision* in tourist class for a very good reason — in club or first class passengers have more leg room, so the seat in front is too far away for the small l.c.d. screen.

It's unlikely *Airvision* will catch on, because the cost of providing every seat with an l.c.d. screen and control panel is very high compared with the cost of installing one video projector or several monitor sets.

Skyview

British Airways is also testing two other personal video systems, this time for first class passengers. *Skyview* from Fieldtech, and a similar system from Avicom. Both rely on an l.c.d. screen which is mounted on an adjustable arm fixed to the seat armrest. The armrest houses an 8mm video playback unit and passengers are offered a choice of 8mm cassettes to watch during the flight.

Both systems use American NTSC Video 8 hardware, rather than European PAL. Fieldtech hit on the clever idea of buying unsold stock from Kodak, who had previously contracted Matsushita (Panasonic) in Japan to produce domestic Video 8 equipment for sale in the USA.

Kodak's venture failed and the company flopped off remaining hardware

at cut prices. It will be interesting to see how much Fieldtech has to pay for further supplies direct from Matsushita, if BA places a big order — especially as Matsushita is itself expanding its own in-flight interests.

A different approach to personal video is adopted by Virgin. Each top class passenger gets to borrow one of Sony's Video Walkman units for the duration of the flight. Again the cabin crew comes round with a selection of 8mm video cassettes.

Inevitably pilferage will be a problem with these personal systems. The fact that someone flies first class does not necessarily mean that they are honest and can resist the chance of an easy theft.

Some airlines use VHS cassettes, even though they are larger than Beta or Video 8. Usually this is for political reasons, for instance because the system has been installed by Matsushita's Avionics division. Matsushita, of course, is the parent company of JVC, developer of the VHS system.

It is most likely that VHS users will probably soon upgrade to the new Super VHS format, which gives better picture quality. Already Sony is upgrading the latest Trans Com systems to Hi-8, the improved quality variation of Video 8.

In-flight developments all ride on the top of domestic video developments. The in-flight market is too small to encourage bottom-up innovation.

Despite all this emphasis on new technology, I have to say (as someone who does a lot of long haul flying, e.g. visiting factories and going to seminars and exhibitions round the world) that a lot of the benefits never seem to reach the customer. On a Virgin flight recently, tourist class, I was put in a seat where it was quite impossible to see the screen. Video projectors are often badly aligned, so that the picture suffers from colour fringing.

Japanese short haul, internal, flights show golfing films, and often have a video camera at the front of the plane to give passengers a pilot's view of take-off and landing. So do some American airlines.

Plenty of flights around Europe, either to holiday locations or business city centres, are quite long enough for a few short films. Apart from anything else, many airlines now put the compulsory safety instructions on video, instead of having the crew demonstrate how to use life jackets etc.

Sound Systems

The sound is always relayed to passengers through headphones. These used to be awful acoustic stethoscopes, which pipe sound up plastic tubes from tiny loudspeakers hidden inside the seat rest. Stethoscopes are not only uncomfortable, they reproduce no sound over around 10kHz and give virtually no bass response.

Many airlines have now gone over to electromagnetic head-sets, often made by German company Sennheiser — with non-standard plugs to discourage people from pinching them. Unbelievably, TWA still provides stethoscope head-sets even to passengers in first class.

Even if short haul flights in Europe do not introduce video entertainment, they are likely to offer passengers the chance to listen to music — hopefully through electromagnetic headphones.

The first sound system used a clumsy endless loop cartridge developed by Trans Com — rather like a bulky metal version of the old eight-track car cartridge. These loops of tape ran for an hour, with four audio tracks.

The cartridges, which cost around \$500 each, had to be sent back to Trans Com for re-recording and needed internal lubrication. The lubrication used to shed, clogging the heads and trimming treble response. When the lubrication failed, the tape suffered from wow and they finally jammed.

There was also a system that used a cartridge with 1in tape that shuttled backwards and forwards past a playback head. The tape held 32 tracks and the 16-track head switched sideways at the end of each shuttle, rather like an auto-reverse cassette recorder, to give 16 tracks at any one time. These could be allocated to eight stereo programmes, 16 mono, or a mix of both.

Around five years ago Matsushita introduced a new system, which uses standard Philips cassettes, albeit with a slightly modified track format. The tape has four equal sized tracks running in the same direction, whereas with conventional cassettes there is a guard band in the middle between two track pairs, which run in opposite directions for flip-over playing.

It is probably no coincidence that Matsushita launched this system when the Philips patents on the original cassette ran out, and the company could no longer control the tape track standard through royalty free licences.

The surprisingly small Matsushita playback unit has six drives, arranged in back to back pairs. As three drives play a total of twelve channels, the three other drives re-wind their tapes. Tones at 30Hz control switching, with phase comparison tricks to prevent the music misleading the machine.

With C-120 cassettes, the system can give listeners a choice of 12 two hour audio channels, either 12 mono programmes, 6 stereo or a mix of both. Audio quality is improved by the use of BDX noise reduction.

Hell Ride

Trans Com has now gone one stage further, using compact disc players as well as Philips cassettes.


The latest plan is to provide passengers with word processors, a telex, fax and telephone link. The idea is that long haul flyers will be able to take messages from the office back home, telling them to work all night.

Personally, it's my idea of hell. I regard a long haul flight as one of the few times I can get away from the telephone and catch up on reading while listening to music and watching films I never have time to see back home.

TRANSFORMERS FROM JAYTEE

The UK Distributor for Standard Toroidal Transformers

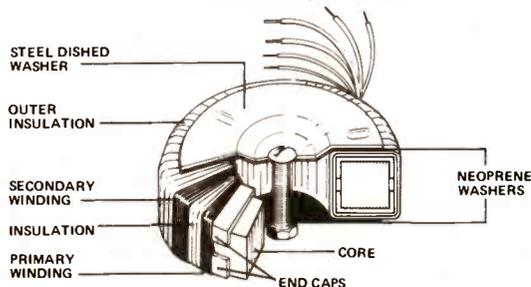- * 106 types available from stock
- * Sizes from 15VA to 625VA
- * Dual 120v primaries allowing 110/120v or 220/240v operation



TYPE	SERIES NO.	SEC VOLTS	RMS CURRENT	TYPE	SERIES NO.	SEC VOLTS	RMS CURRENT
15VA £9.30	03010	6+6	1.25	160VA £16.85	53011	9+9	8.89
	03011	9+9	0.83		53012	12+12	6.66
	03012	12+12	0.63		53013	15+15	5.33
	03013	15+15	0.50		53014	18+18	4.44
	03014	18+18	0.42		53015	22+22	3.63
	03015	22+22	0.34		53016	25+25	3.20
	03016	25+25	0.30		53017	30+30	2.66
	03017	30+30	0.25		53018	35+35	2.28
30VA £10.60	13010	6+6	2.50	53026	40+40	2.00	
	13011	9+9	1.66	53028	110	1.45	
	13012	12+12	1.25	53029	220	0.72	
	13013	15+15	1.00	53030	240	0.66	
	13014	18+18	0.83	225VA	63012	12+12	9.38
	13015	22+22	0.68	63013	15+15	7.50	
	13016	25+25	0.60	63014	18+18	6.25	
	13017	30+30	0.50	63015	22+22	5.11	
50VA £12.20	23010	6+6	4.16	63016	25+25	4.50	
	23011	9+9	2.77	63017	30+30	3.75	
	23012	12+12	2.08	63018	35+35	3.21	
	23013	15+15	1.66	63026	40+40	2.81	
	23014	18+18	1.38	63025	45+45	2.50	
	23015	22+22	1.13	63033	50+50	2.25	
	23016	25+25	1.00	63028	110	2.04	
	23017	30+30	0.83	63029	220	1.02	
	23028	110	0.45	63030	240	0.93	
	23029	220	0.22	300VA	73013	15+15	10.00
80VA £13.50	23030	240	0.20	73014	18+18	8.33	
	33010	6+6	6.66	73015	22+22	6.82	
	33011	9+9	4.44	73016	25+25	6.00	
	33012	12+12	3.33	73017	30+30	5.00	
	33013	15+15	2.66	73018	35+35	4.28	
	33014	18+18	2.22	73026	40+40	3.75	
	33015	22+22	1.81	73025	45+45	3.33	
	33016	25+25	1.60	73033	50+50	3.00	
	33017	30+30	1.33	73028	110	2.72	
	33028	110	0.72	73029	220	1.36	
120VA £14.35	33029	220	0.36	73030	240	1.25	
	33030	240	0.33	500VA	83016	25+25	10.00
	43010	6+6	10.00	83017	30+30	8.33	
	43011	9+9	6.66	83018	35+35	7.14	
	43012	12+12	5.00	83026	40+40	6.25	
	43013	15+15	4.00	83025	45+45	5.55	
	43014	18+18	3.33	83033	50+50	5.00	
	43015	22+22	2.72	83042	55+55	4.54	
	43016	25+25	2.40	83028	110	4.54	
	43017	30+30	2.00	83029	220	2.27	
	43018	35+35	1.71	83030	240	2.08	
	43028	110	1.09	625VA	93017	30+30	10.41
43029	220	0.54	93018	35+35	8.92		
43030	240	0.50	93026	40+40	7.81		
			93025	45+45	6.94		
			93033	50+50	6.25		
			93042	55+55	5.68		
			93028	110	5.68		
			93029	220	2.84		
			93030	240	2.60		

Prices include VAT and carriage


Quantity prices available on request
Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT66PL
Telephone: (0227) 375254 Fax: 0227 365104

PUBLIC ADDRESS AND DISCO EQUIPMENT

YOU PAY TRADE PRICES!

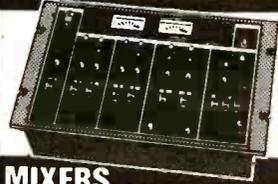

MIXERS

Choose from 25 models ■ Mixers for home use, disco's, public address and studio use ■ From 4 to 16 channels ■ Also 6 and 8 ch midi systems ■ Equalizer mixers MRT60 and many more.



DECKS

3 models heavy duty top quality with plinth/cover.
■ DLP1 belt drive quick start.
■ DLP2 direct drive system.
■ DLP3 quartz controlled quickstart direct drive.



ECHO'S

■ VC1 analogue ■ 6040 stereo amplifier ■ 8040 digital echo ■ Also mini echo's.

DIGITAL DELAY/REVERB

■ 19" rack systems ■ Digital reverb with 63 user programs ■ Digital delay up to infinite repeat ■ Also multi-effects programmable unit.

GRAPHICS

■ 19" rack systems ■ 31 band single channel ■ 2 x 15 band two channel, and 2 x 31 band two channel.

CHASSIS SPEAKERS/CABINETS

■ PA speakers 5 1/2" to 12" ■ Twin cone from 40 to 100 Watts ■ Various models disco/group speakers 10" to 18" various types ■ Bass speakers ■ Bass mids and mids ■ Also Rexine cabinets 10", 12" & 15" ■ Plus range of cabinet fittings and portable speaker stands and brackets.

PIEZO TWEETERS

■ 10 models stocked from £2.95 to £7.95 ■ Square piezo £4.95.

PUBLIC ADDRESS SPEAKERS

■ For PA and background music system with and without 100 volt line
■ OUTDOOR. Range of weatherproof systems at various power ratings
■ INDOOR. Columns for speech, columns for music ceiling speakers, suspension speakers, corridor speakers, wall speakers, music speakers - various sizes and types.

POWER AMPLIFIERS

■ Power boosters single channel: 100W, 175W and 2kW. 2-ch/stereo: 135 + 135W, 160 + 160 Watt and 1500 + 1500 Watt.

AMPLIFIERS

■ With preamps ■ 240V AC models and 12V DC/240V AC or 24V DC/240V AC ■ From 15 Watts up to 175 Watts ■ Also background music tape amplifiers and paging amplifiers. ■ Plus range of mixer-amplifiers. ■ Choose from 25 models.

MOBILE AMPLIFIERS

■ Range of 12 volt amplifiers up to 100 Watts ■ Also portable megaphones stocked and 12 volt power boosters.

MICROPHONES/STANDS

■ XLR/Jack etc ■ Mics for disco, public address and Hi-Fi ■ Good quality at low cost ■ Also stands, booms etc. and wireless microphone system

OUTDOOR HORNS

■ Various models up to 12" with or without 100 volt line with drivers
■ Also range of horns with choice of drive units.
■ Accessories: Leads ■ Plugs
■ Adaptors ■ Transformers etc. for all PA requirements.

HORN/CROSSOVERS

■ 100 Watt midrange and tweeter horns ■ Also matching crossovers and filters up to 300 Watts.

CALL IN OR PHONE FOR BEST PRICES
OPEN 6 DAYS A WEEK



AUDIO ELECTRONICS

301 Edgware Road, London, W2 1BN

Tel: 01-724 3564 Fax: 01-724 0322

SALES OFFICE 01-258 1831

Also at HENRY'S 404 Edgware Road, W2

TRADE/EDUCATION ORDERS ACCEPTED

PA - DISCO CATALOGUE WITH DISCOUNT VOUCHERS Ref PAI
Send A4 SAE (£1.00 UK) or £2 UK, full products catalogue

MUSIC ON HOLD



DAVID BUTLER

Prevents telephone from picking up unwanted background conversations. Indicates to caller that he/she has not been forgotten! No direct electrical connection to telephone.

THE MAIN reason for this project was discovered while making telephone calls at work. While waiting for people to come to the phone the receiver is usually just left on the desk where it does a fine job of relaying all conversations around the office back down the line.

On several occasions the retort of "Oh no, not him ringing again!" was heard. It certainly is remarkable how well the phone can pick up these unwanted comments, and on a more serious note, those which may be of commercial interest.

This project blocks out this unintentional "eavesdropping", whilst on hold, by simply playing a series of tunes to the caller. It also reassures the caller that someone is

about to attend to them and not forgotten that the handset is lying on the desk.

The electronics consist of a melody generator i.c. and a l.e.d. flasher, all operating from a single 1.5V battery. The construction is reasonably straightforward, the only critical part being the mechanical arrangement for resting the telephone handset on the microswitch above the loudspeaker.

CIRCUIT DESCRIPTION


The full circuit diagram for the *Musical On-Hold* unit is shown in Fig. 1. The heart of this circuit is built around IC2, the multi-tune chip type UM34811A.

This device requires very few external components to provide a 16-tune repertoire, see Table 1. The tunes are pre-programmed to produce one of three instrument sounds, namely: piano, mandolin or organ.

Table 1: Tune Selection

- 1 Twinkle, Twinkle Little Star
- 2 Cuckoo Waltz
- 3 Eency Weency Spider
- 4 Lullaby
- 5 Santa Lucia
- 6 Oh My Darling Clementine
- 7 Are You Sleeping
- 8 Rock-a-Bye Baby
- 9 London Bridge is Falling Down
- 10 Little Brown Jug
- 11 Butterfly
- 12 Long Long Ago
- 13 Cuckoo Waltz
- 14 Mary Had A Little Lamb
- 15 The Train Is Running Fast
- 16 Dream of Home and Mother

Fig. 1. Complete circuit diagram for the Music On-Hold.

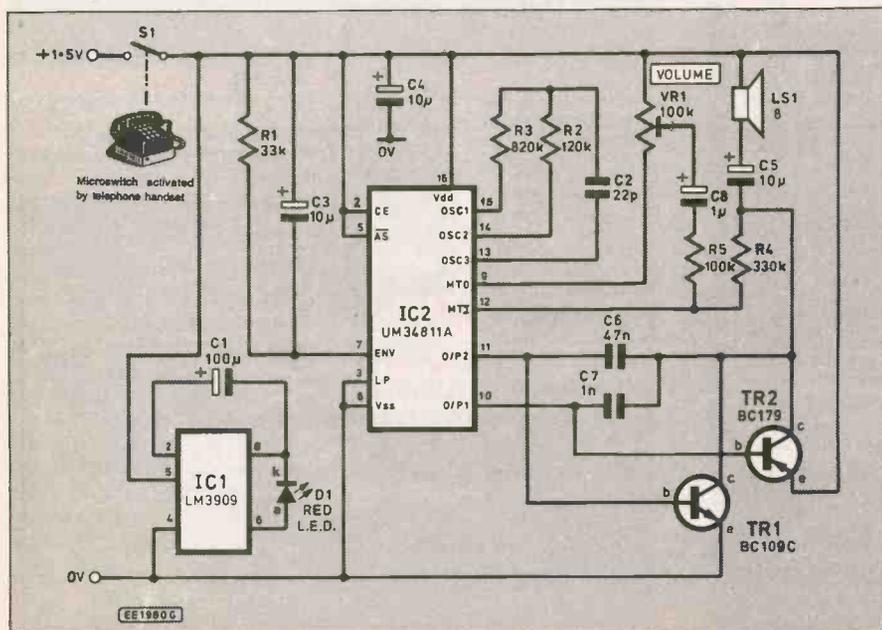

The tempo and tones of the tunes are defined by capacitor C2 and resistors R2 and R3. These are connected to the three oscillator pins 13, 14 and 15 of IC2. The resistor R2 and capacitor C2 set the internal oscillator, whilst resistor R3 from pin 15 to the junction of R2/C2 makes the oscillator less susceptible to supply voltage fluctuations.

The decay between notes or "envelope" is set by resistor R1 and capacitor C3, connected to IC2 pin 7. Changing the values of these components alters the charge/discharge time of the internal pre-programmed envelope circuit.

The circuit, as it stands, is programmed to play all tunes in sequence, but this can be changed to single tune and stop by altering the connections to pins 3 and 5 as follows:

- | Pin | Function |
|-----|--|
| 3 | Connected to positive supply line (V_{dd}); plays ONE tune only. |
| 4 | Connected to negative supply (V_{ss}); plays ALL tunes. |
| 5 | Connected to positive supply line (V_{dd}); tunes REPEAT continuously. |
| 6 | Connected negative (0V) supply; tunes STOP at end. |

The internal preamplifier outputs from pins 10 and 11 are fed to transistors TR1 and TR2. These transistors are arranged as a push-pull output stage for driving the miniature 8 ohm loudspeaker LS1.

The output volume of the unit is controlled by potentiometer VR1. This control may be an on-board miniature preset or a case mounted rotary type.

Finally IC1, an LM3909 i.e.d. flasher/oscillator, and D1, a red i.e.d., are employed to indicate that the unit is in use. Capacitor C1 sets the oscillator rate which in turn flashes the i.e.d.

Both i.c.s consume little current (IC1 < 0.5mA, IC2 < 12µA standby) and so the project may be powered from a single AA or D size 1.5 battery.

CONSTRUCTION

Construction of the *Musical On-Hold* project is mostly straightforward and can be built on a printed circuit board or Veroboard. The only real problems likely to occur may be the mounting of the micro-switch S1 and the miniature loudspeaker LS1.

COMPONENTS

Resistors

R1	33k
R2	120k
R3	820k
R4	330k
R5	100k

All 0.6W 5% carbon.

Potentiometer

VR1 100k enclosed preset, vert.

Capacitors

C1	100µ elec. 10V
C2	22p ceramic
C3	10µ elec. 10V
C4	10µ elec. 10V
C5	10µ elec. 10V
C6	47n polyester
C7	1n ceramic
C8	1µ elec. 10V

Semiconductors

D1	3mm red i.e.d.
TR1	BC109C npn silicon
TR2	BC179 pnp silicon
IC1	LM3909 i.e.d. flasher/oscillator
IC2	UM34811A melodies generator

Miscellaneous

LS1	8 ohm miniature loudspeaker 40mm dia.
S1	miniature microswitch, with operating lever
B1	1.5V battery, AA or D size
Printed circuit board	(EE PCB Service, code EE646) or 0.1in. matrix Veroboard (approx. 28 strips×25 holes); case, diecast aluminium 120mm×95×30mm; 8-pin d.i.l. socket; 16-pin d.i.l. socket; battery holder (AA size); plastics strips, approx 90mm × 30mm×15mm; i.e.d. clip; metal brackets (3 off); wire mesh; card; connecting wire; solder; nuts and bolts, etc.

Approx. cost
Guidance only

£18

**Shop
Talk**
See page 636

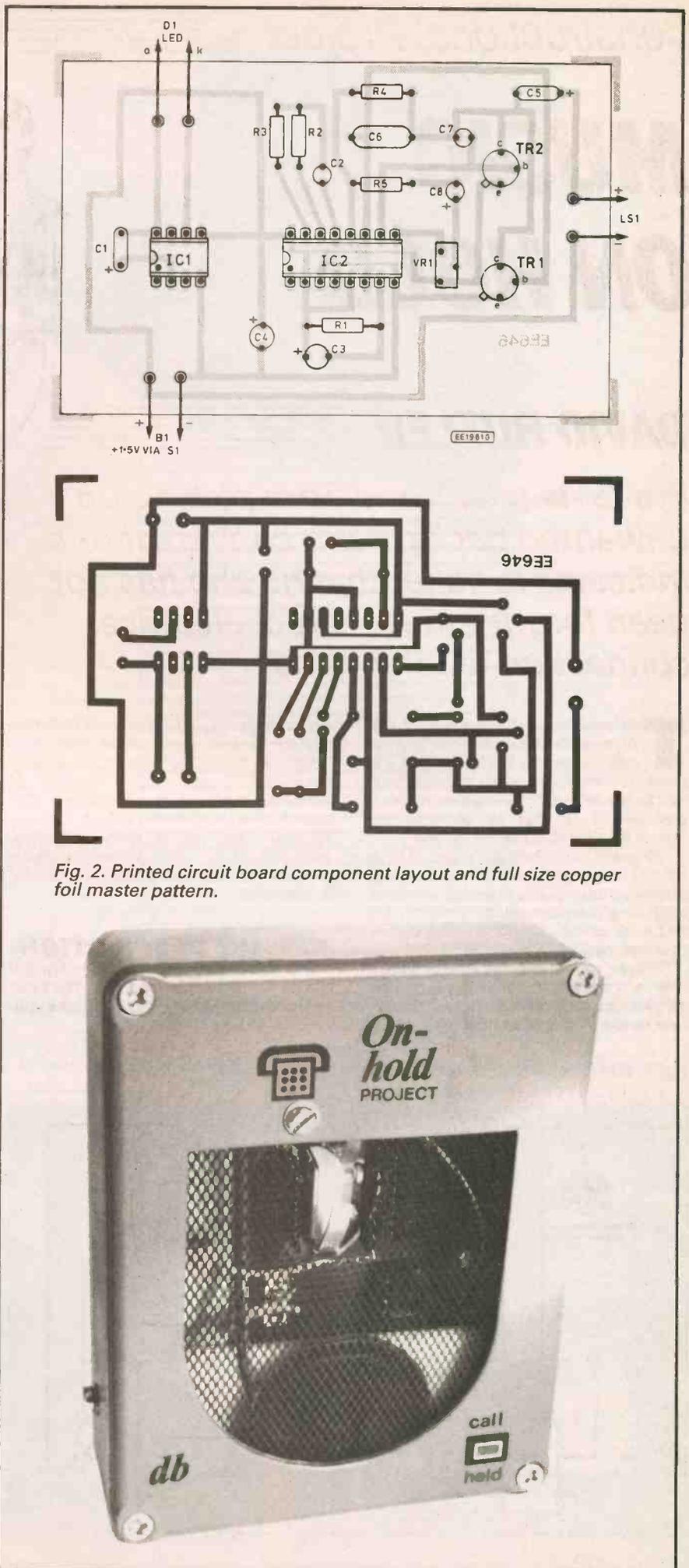


Fig. 2. Printed circuit board component layout and full size copper foil master pattern.


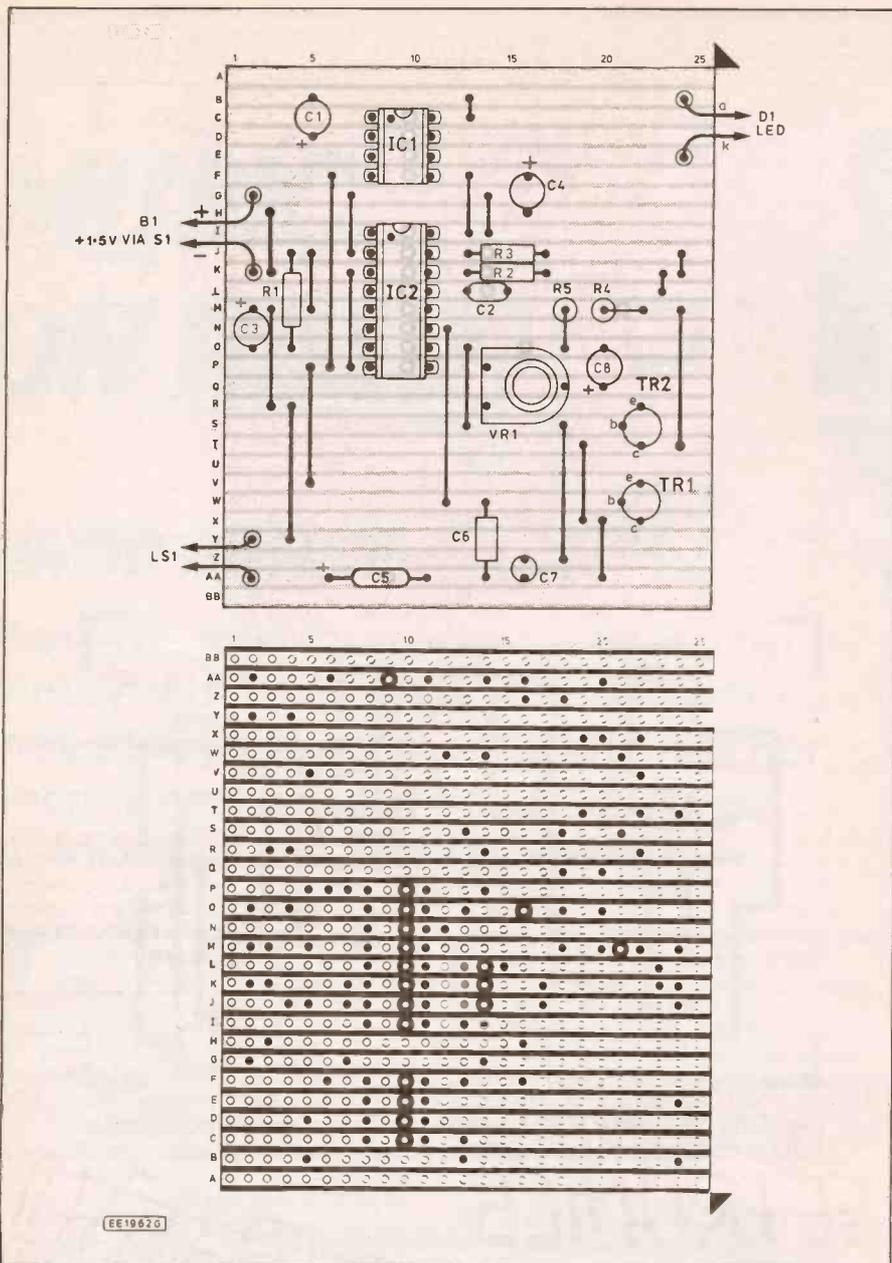


Fig. 3. Component layout and details of breaks required in the underside copper strips for the Veroboard version.

Layout of components inside the case.

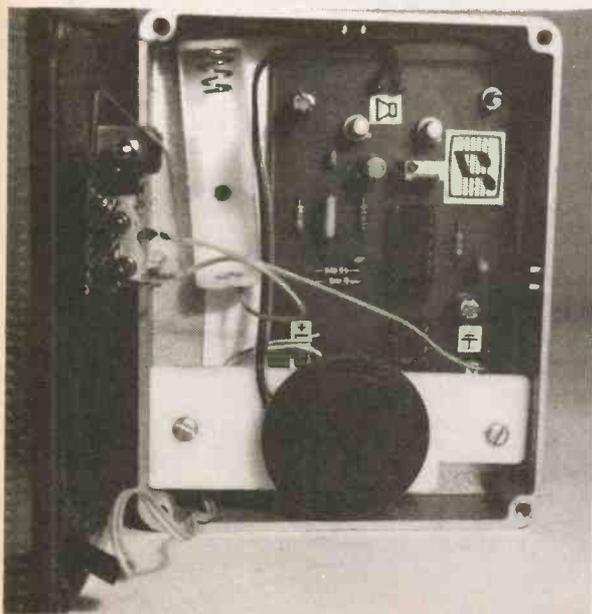

Mounting the microswitch on the lid using a plastics strip and metal bracket.

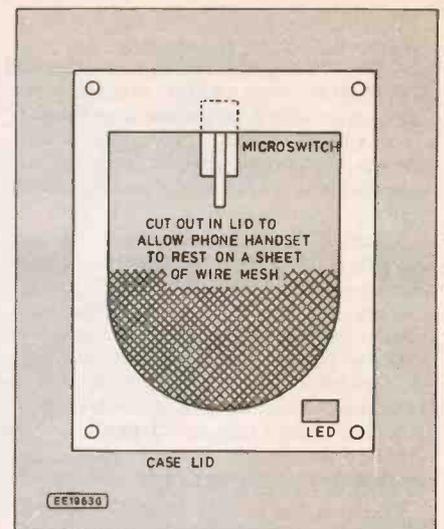
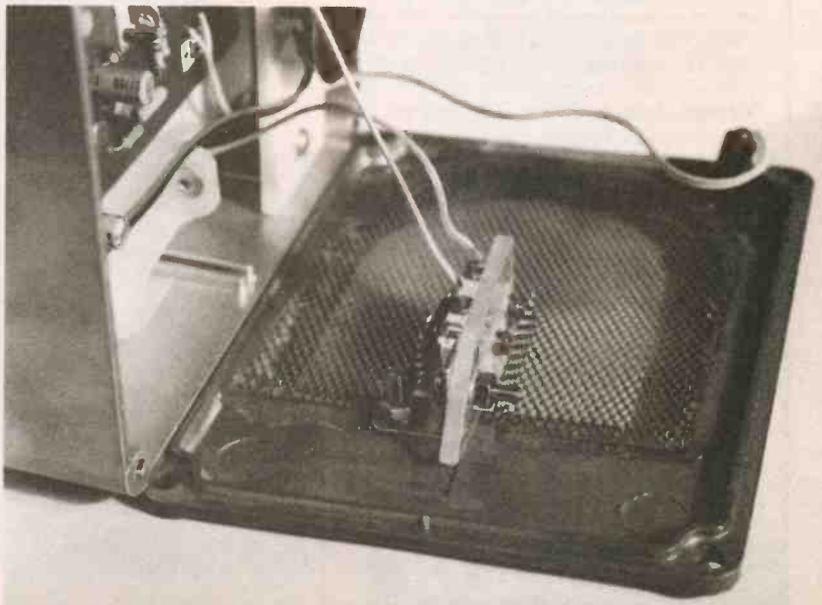


Fig. 4. Suggested layout and cutout details for the case lid.

Commence construction by first selecting either the p.c.b. or the Veroboard version. The component layout and full size copper foil master pattern for the p.c.b. version is shown in Fig. 2. (This board is available from the *EE PCB Service*, code EE646). The Veroboard component layout and details of breaks required in the underside copper tracks is shown in Fig. 3.

Mount and solder the two i.c. holders and the four solder pins in position. Do NOT at this stage insert IC1 and IC2 in their respective holders, leave these until last.

Next solder all resistors in place followed by the preset VR1, capacitors and the two transistors TR1 and TR2. Take particular care to ensure that the electrolytic capacitors and the transistors are inserted correctly. Finally, attach lengths (approx. 150mm) of connecting wires to the four solder pins and also to the l.e.d. pads on the circuit board.

Those building the circuit on Veroboard should double-check that all 18 breaks in the copper strips have been made. Also confirm that there are 19 wire links on the board.

CASE

Once the circuit board has been checked out it should be put to one side and a suitable case should be prepared to take the loudspeaker, battery holder and micro-switch. The prototype model used a shallow metal diecast case (to withstand daily office life!) with a cutout in the lid to take the telephone handset, see Fig. 4.

The cutout is covered with a wire mesh glued to the underside of the lid and sits above the loudspeaker. The microswitch is also mounted on the lid using a metal bracket and plastics strip.


The microswitch is arranged so that the operating lever just protrudes through the wire mesh and any object placed on the mesh will automatically operate the switch. The only other component mounted on the lid is the red l.e.d. which should be positioned in one corner, see photographs.

A piece of card, about 110mm x 76mm, should be placed in the bottom of the case to one side. This card sits under the p.c.b. and stops the board's copper tracks from shorting out.

The board is held in place by two sets of nuts and countersunk bolts. A single AA size battery holder should now be fixed in position to one side of the board.

A piece of 90mm x 30mm plastics strip, with a small 20mm diameter hole cut in it to "cradle" the loudspeaker, is mounted above the circuit board at one end. The strip also has a small corner cut out at one end to allow the l.e.d. to pass when closing the lid.

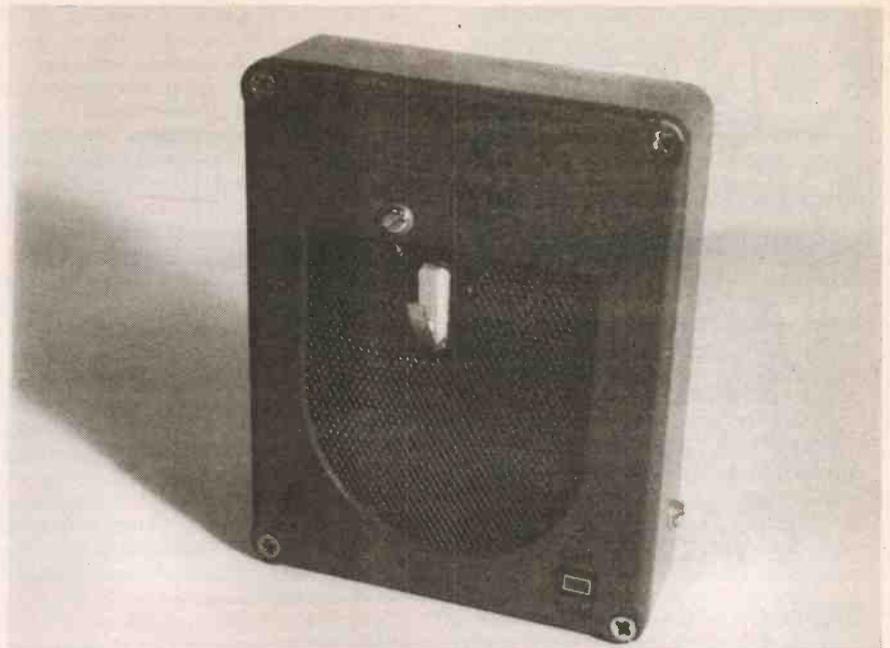Once all the components have been mounted in the case the lengths of connect-



Completed unit showing the microswitch lever protruding through the wire mesh.

ing wires should be soldered to the battery holder, loudspeaker, l.e.d. and micro-switch.

The two i.c.s should now be pressed into their holders and the battery inserted into the holder. Before closing the lid the unit can be checked for operation by pressing the microswitch lever. The close packing of components may necessitate some slight adjustments before the lid will close up, the

position of the microswitch is particularly important in this respect.

IN USE

When the phone is placed on the box the l.e.d. should start to flash, along with the start of the tunes. The volume control preset VR1 should be adjusted to a comfortable level to avoid any possible damaging effect to the ears of the caller. □

NOW FREE
WHILE
STOCKS LAST

CRICKLEWOOD ELECTRONICS

1989 100 PAGE COMPONENT CATALOGUE

SEND OFF FOR YOUR COPY TODAY...

- WE STOCK AN UNRIVALLED RANGE
- ALL OUR COMPONENTS ARE FIRST CLASS BRANDED ITEMS
- WE OFFER A SAME DAY SERVICE ON ALL STOCK ITEMS
- NO MINIMUM ORDER — IF YOU NEED ONE COMPONENT WE CAN SUPPLY ONE COMPONENT
- WE HAVE ADOPTED A NEW LOWER PRICING POLICY + QUANTITY DISCOUNTS

JUST FILL IN THE COUPON OPPOSITE OR PHONE US ON 01-452 0161 FOR YOUR FREE COPY!

CRICKLEWOOD ELECTRONICS LTD
40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
TEL: 01-450 0995/452 0161
FAX: 01-208 1441
TELEX: 914977

SEND OFF FOR YOUR FREE CATALOGUE AND VOUCHERS TODAY

I WOULD LIKE TO RECEIVE COPY (COPIES) OF
THE 1989 CRICKLEWOOD ELECTRONICS
COMPONENT CATALOGUE.

NAME.....

ADDRESS.....

I WOULD LIKE TO RECEIVE A FREE COPY OF YOUR
1989 CATALOGUE.

E



a regular feature for the Spectrum Owner...

by Mike Tooley BA

THIS month, in preparation for some forthcoming constructional projects, we shall be taking a detailed look at the hardware of MGT's exciting new SAM COUPE. We also have details of a new electronic drawing package from BESoft which will appeal to any electronics enthusiast who needs to produce neatly drawn circuit diagrams. We begin by opening up an old topic which may be of interest to those who own Issue 2 Spectrums.

Extra RAM

N. Allen writes from Alcester with some further information concerning the potential extra 32K of RAM present within the early "16K" versions of the Spectrum. Mr. Allen writes:

"Your article on RAM chips (May 1989) intrigues me. My Spectrum is an Issue 2 so I thought the potential extra 32K worth investigating. The link to select the upper or lower half of the 64K chips (the 4532's located in two rows of four just below centre on the board) is between the ULA (the large i.c. next to the modulator) and the upper left hand 74LS157. The link restricts the RAMs to a 7x8 matrix instead of the possible 8x8 address bits (giving 32K).

Before continuing, both halves of the 4532s can be checked by first POKeing an address into the top 32K (such as 40000) with zero, then PEEKing the address. Now try POKeing 255 and PEEKing. A return of the POKEd number indicates that at least half of all eight RAMs is working (one chip for each bit). Now turn the link round and repeat the PEEKs and POKEs.

I have replaced the link with a pull-up resistor of 47k and taken the central hole of the three to pin 4A of the edge connector (pending future developments such as using an output port to switch a 74LS373 to page the extra memory in or out)."

Although I have not personally tried Mr. Allen's suggested modification, I do know of several other Spectrum users who have successfully made use of the unused 32K RAM in Issue 2 machines by similar means. It is, however, worth pointing out that only the later Issue 2 Spectrums may have been fitted with fully functional 32K RAM chips.

Early models are quite likely to have chips which have defective memory cells

(in one half of the matrix). This does not, of course, preclude users from making the modification and then identifying and replacing the faulty chip (or chips). For those who wish to follow this route, a simple method for checking and identifying suspect RAM devices was described in the May 1989 instalment of *On Spec*.

Hardware Expansion and the SAM COUPE

Version 1.1 of MGT's SAM COUPE manual recently dropped through my letter box. The document contains much of interest to both hardware and software developers and, by studying its contents, one can at last begin to form a realistic impression of what MGT's new machine will be capable of. The COUPE provides a number of sophisticated I/O facilities not previously found on Sinclair/Amstrad Spectrum machines and all connections to the COUPE (with the exception of the removable internal disk drives) are made via the rear panel.

Bus expansion

A standard 64-way Euroconnector (with rows A-C fitted) provides access to the principal bus signals. With a few notable differences, this connector provides a similar function to that associated with the Spectrum edge connector. The usual data and address bus signals are available as are the control bus signals; RD, WR, INT, NMI, HALT, RESET, IOREQ, MREQ, BUSREQ, and BUSACK.

Also present are two ROM chip selects, AUDIO LEFT and AUDIO RIGHT, RED, GREEN and BLUE, CSYNC, VSYNC, and MIC/EAR. This last named signal is also available from a single 3.5mm jack connector. We shall include further details of the particular connector in a further instalment of *On Spec*.

Cassette jack

A 3.5mm (mono) jack socket provides the combined MIC/EAR signal. The signal is bi-directional; output is via the cassette recorder's MIC socket when SAVEing data whilst input is via the unit's EAR socket when LOADing. It makes no difference to the COUPE if EAR and MIC are connected together but readers should note that not all cassette tape recorders will tolerate this!

SCART

The 21-way SCART connector provides both RGB and composite video signals together with left and right audio outputs. This connector will thus facilitate connection of a wide range of video monitors, both analogue and digital. The pin connections are as follows:

Pin	Signal	Pin	Signal
1	AUDIO RH	2	SPEN
3	AUDIO LH	4	AUDIO GND
5	BLUE GND	6	BLUE TTL
7	BLUE LIN	8	RED TTL
9	GREEN GND	10	GREEN TTL
11	GREEN LIN	12	BRIGHT TTL
13	RED GND	14	CSYNC GND
15	RED LIN	16	CSYNC
17	C. VID GND	18	POWER IN
19	C. VID	20	POWER IN
21	GND		

Light pen

The light pen connector is a standard 5-pin DIN socket. The connector has a dual function; not only does it provide a light

pen (or light gun) input but it also provides stereo audio output for connection to a domestic Hi-Fi system (via an AUX input). The pin connections are as follows:

Pin	Signal
1	0V
2	AUDIO LEFT
3	SPEN INPUT
4	AUDIO RIGHT
5	+5V

Joystick

The joystick connector is a standard 9-pin D-connector. The connector follows the Atari convention except that an extra strobe line is available for a second joystick together with a line carrying +5V. MGT intend to facilitate dual joystick operation by means of a second joystick fitted with a special plug-socket connector. The joystick is read by the keyboard port (port address 254 decimal) and overlays numeric keys 1 to 5 for the second joystick and 6 to 0 for the first joystick. The joystick connector is wired as follows:

Pin	Signal
1	UP
2	DOWN
3	LEFT
4	RIGHT
5	0V
6	FIRE
7	+5V
8	STROBEL 1
9	STROBEL 2

Mouse

The mouse interface employs a standard 8-pin DIN connector. MGT's three button mouse interrupts the CPU to request a read of its X and Y signal lines. The software driver is contained within the ROM and overlays the cursor keys. The mouse input can be read from the keyboard port (address 254 decimal) with address lines A8 to A15 set high. The mouse connector is wired as follows:

Pin	Signal
1	LEFT
2	UP
3	RIGHT
4	MSE INT
5	RDMSEL
6	0V
7	+5V
8	DOWN

MIDI INPUT

MIDI input is via a 7-pin DIN connector. The input is serial data at 31.25Kbaud which is fed via an opto-isolator to a serial-parallel convertor. The MIDI interface interrupts the CPU when a data byte has been assembled within the MIDI-IN register (address 253 decimal). This INPUT can also be read by bit-7 of the VMPP (address 252 decimal) and is also used by the NETWORK. The connections are as follows:

Pin	Signal
1	NET-LOOP
2	not connected
3	NET+LOOP
4	MIDI+IN
5	MIDI-IN
6	NET-LOOP
7	NET+LOOP

MIDI OUTPUT

MIDI output also employs a 7-pin DIN connector. By writing a data byte to address 253 decimal (the MIDI-OUT register) the MIDI interface outputs a current of

7.5mA at 31.25Kbaud. When transmitting, bit-4 of the STATUS register (address 249 decimal) is set. This OUTPUT can also be driven by bit-7 of the VMPR (address 252 decimal). An internal through connection is made from MIDI IN to MIDI OUT by setting bit-6 (THROM—through MIDI) of the BORDER register (address 254 decimal). MIDI OUTPUT is also used by the NETWORK. The connections are as follows:

Pin	Signal
1	NET-LOOP
2	GND
3	NET+LOOP
4	MIDI+OUT
5	MIDI-OUT
6	NET-LOOP
7	NET+LOOP

ELECTRODRAW

In May's *On Spec*, I reviewed the ingenious PCB Designer package from Kemsoft. The popular computer press often refers to packages of this type as "productivity software"; a very apt title for programs which can be instrumental in saving the user many hours of toil! I was, therefore, interested to learn of another package which puts the Spectrum to excellent use serving the needs of the electronics enthusiast. This program is from a relatively new company, BESoft, and is entitled ELECTRODRAW.

ELECTRODRAW is a versatile electronic drawing aid which allows users to draw, edit, store, and print electronic circuit diagrams. The program is available in either tape or microdrive versions, the latter having obvious advantages when storing and retrieving diagrams.

ELECTRODRAW contains a number of features which make it easy to use. The program has symbol, label, line and box drawing facilities and includes a magnifier which produces a four-times normal size image of the area around the cursor for precise alignment of symbols and conductors. Symbol editing and creation can be carried out from within the main program and a "symbol merge" facility allows symbols from one diagram to be transferred to another. All microdrive functions (except MOVE#) are supported from within the main program.

ELECTRODRAW runs on any 48K or 128K Spectrum (including the Plus-2 in 48K mode without any add-ons (but some facilities require a printer and some require a microdrive). The following printer interface options are supported: ZX or Alphacom-32, Centronics interface, and Sinclair Interface One RS-232 output.

The program comprises 11K of pure machine code (there is no BASIC loader).

It is important to note that, although the cassette version supports all the microdrive facilities, the program itself cannot be transferred to microdrive. The cassette version can, however, be exchanged for a microdrive version for a small fee. Owners of the cassette are asked to return the cassette version with payment.

The software is supplied with a 12-page A5 format manual. The manual is neatly presented and includes sections entitled "Getting Started", "The Main Menu Options", "The Drawing Process", "The Symbol Design Routine", "Tape/Microdrive Options", and "Handling Very Long Diagrams".

Symbols

Successful use of any technically oriented drawing package depends very largely on the availability of an adequate library of commonly used symbols. Drawing packages should, ideally, be supplied with a number of symbols libraries (one for each application) and should also allow the user to define his or her own personalised set of symbols. ELECTRODRAW contains a library of fifty electronic symbols which are immediately available whenever the program is loaded. These symbols (which can be mirrored and rotated) will be adequate for most drawings, however, there will be occasions when additional symbols will undoubtedly be required.

Symbol definition is straightforward within ELECTRODRAW. The program allows approximately 17Kbytes of memory for symbol definition. This space is sufficient for about 500 symbols of 2x2 character squares. The fifty symbols supplied with the package take about 2.5Kbytes and this leaves over 14Kbytes free for the user's own symbol library (sufficient for approximately 400 symbols of average size!).

In use

I tested the cassette version of ELECTRODRAW in conjunction with a Spectrum Plus and Epson printer. In order to speed up loading of the program, I also took a "snapshot" of the program (and drawings) using the 48K snapshot facility of MGT's Plus-D interface. No problems were encountered in using the software when transferred to disk. However, since the software transferred was from tape (rather than microdrive), all storage operations reverted to cassette. BESoft are, hopefully, investigating the viability of producing a version of the program from Disciple and Plus-D users.

My overall impression of ELECTRODRAW is that it is a pleasure to use; most of the operations are quite intuitive, the cursor control is good, and the mirror and

rotate facilities are excellent. I did find it necessary to re-draw a few of the symbols, though this was simply a matter of personal preference rather than reflecting any serious shortcomings of the symbol library.

Since ELECTRODRAW is clearly intended for low-cost applications, the program does not support output to a plotter. The quality of printed output is, however, perfectly adequate for many applications. Furthermore, subject to the usual constraints associated with dot-matrix printers, the output proved to be comparable (though not superior) to that produced by much more expensive packages (e.g. GFA Draft on the Atari-ST when using a dot-matrix printer as an output device).

In Conclusion

Fully blown "professional" CAD packages can cost many hundreds (if not thousands) of pounds. ELECTRODRAW is not in the same league as these highly sophisticated packages but, for those who require a simple package for straightforward electronic drawing and don't require fancy features (such as scaling or multiple layer drawing), ELECTRODRAW is in a class of its own.

The quality of the artwork produced is perfectly adequate for most purposes and the program should be instrumental in dramatically improving the presentation of such things as project reports, equipment handbooks, and manuscripts. At less than £20 this particular "productivity package" must be considered a real bargain!

ELECTRODRAW costs £17.50 (cassette version) or £19.00 (microdrive version) including postage and packing. BESoft are at 20, Ashville Road, Leytonstone, London, E11 4DT. Tel: 01-558-3469 (evenings only).

Next month: I shall be dealing with a bumper crop of queries together with some more hints and tips received from readers. We also have details of Andy Wright's SAM BASIC (Andy will be well known to many readers as the author of Beta BASIC) and will be delving into the memory map of the SAM. In the meantime, if you would like a set of our Update sheets, please drop me a line enclosing a large (250mmx300mm) and adequately stamped (currently 42p for UK postage) and addressed envelope. Please note that I can no longer provide individual replies to queries but instead will do my best to provide answers in future instalments of *On Spec*.

Mike Tooley, Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey, KT13 8TT.

kitmaster

ELECTRONIC CONSTRUCTION KITS SECOND TO NONE

Our FM MINI TRANSMITTER (BUG) is rather exceptional, measuring only 2x1/2 in. It has two transistors, one power output. Varicap controlled. High quality condenser, electret insert plus ready wound coil. About one mile range. Glass PCB. MKIII version. 9V DC. Complete kit £4.75

Exclusive to us our FM RADIO MICROPHONE measures just 2x1/4 in. It has F.E.T. circuitry and is designed to function from only 1 1/2V DC with one 18 inch trailing lead for its aerial. Varicap controlled and built to the same high quality as the above. Complete kit £6.75

MANY OTHER QUALITY KITS AVAILABLE. SAE PLEASE.

ALL PRICES ARE COMPLETELY INCLUSIVE.

RETURN POSTING DETAILS OF ALL KITS SENT WITH ALL ORDERS.

CHEQUES P.O. TO:

KITMASTER PRECISION TIME
65 Roseland Road, Waunarlwydd, Swansea SA5 4ST

CAMBRIDGE COMPUTER SCIENCE LIMITED

Just In — Reconditioned 10MB Winchesters only £42.00 each

☆ 5.25" Disk Drives, 80 Tk, DSDD	£34.00 each
☆ 3" Disk Drives, 40 Tk, SSDD	£28.00 each
☆ 5.25" Disk Drives, 80 Tk, DSDD Used, No Wty	£15.00 each
☆ 5.25" Disks, 48 Tpi, boxes of 10	£3.00 box
☆ Dual Disk Drive Power Supply	£20.00 each
☆ Lead to connect one drive to psu	£2.00 each
☆ 50W PSU 5V 6A, 12V 2.5A, -5V 0.5A, -12V 0.5A	£15.00 each
☆ Gould PSU 0-30V @6A — Limited quantity only at	£45.00 each
☆ Single Data lead (BBC Micro to Disk Drive)	£2.00 each
☆ Dual Data lead (BBC Micro to 2 Disk Drives)	£4.00 each
☆ Power lead (BBC Micro to Disk Drive)	£1.00 each
☆ Dual leads (BBC Micro to 2 Disk Drives)	£2.00 each
☆ 68000 CPUs (The first orders get 10MHz chips)	£3.50 each
☆ 74LS TTL assortments, 10 different devices	£1.20 pack
☆ 8K Byte NV ram chips	£3.00 each £10.00 four
☆ 20 pin dit low profile IC sockets	£0.50/10 £4.00/100
☆ 40 pin dit low profile IC sockets	£0.60/10 £5.00/100
☆ Keyboard, 100 keys on board LCD & micro i/f	£8.00 each
☆ Toroidal mains transformer, 12V 4A & 0.4A, 12-0-12 .1A & .2A, 9-0-9 .2A	£4.00/1 £6.00/2 £8.00/3

All items new unless stated. Add 15% VAT to all prices. Prices include postage. Add 50p to orders below £5.00

Send an SAE for our latest list or for more info.
Dept EE, 374 Milton Road, Cambridge, CB4 1SU
Tel: 0223 424602

SIMPLE L.E.D. TIMER

CHRIS BOWES



A low cost, easy-build unit that can be adapted to many simple timing applications

THIS PROJECT is essentially a variation on the chaser circuit, featured last month, in which a series of l.e.d.s are made to come on in sequence. This display format has been adapted to provide an indicating function which is used to show an elapsed preset time period. An audible output is triggered when the last l.e.d. is illuminated and the circuit is latched so that the alarm continues to sound until the circuit is turned off.

Although the component values have been chosen to suit a timing period of about four minutes, the circuit can be easily adapted so that the period is altered to suit other applications. The author uses his model as an audio/visual egg timer.

As with all of the circuits in the "Pocket Money" series, the design is intended to operate from a standard 9 volt battery. The circuit shown includes a buzzer but this can be replaced with any of the audible output circuits featured in this series, although it may be necessary to alter the transistor to one of a higher power to ensure that correct operation occurs.

HOW IT WORKS

The circuit really contains three standard circuit building blocks, some of which we have already met in this series.

The first standard circuit block is the 555 timer astable circuit which is used, in this case, to provide a series of pulses which are used to "clock" the rest of the circuit through. The standard layout of the 555 timer astable is shown in Fig. 1a and in this configuration produces an output waveform as shown in Fig. 1b.

The duration and interval between pulses produced by this circuit are determined by the values of R_A , R_B and C as shown by the two formulae given in Fig. 1b. By altering the values of the components in accordance with the given formulae the timer can be adapted to suit other applications.

The second building block is a standard "chaser" circuit using a 4017 Johnson Counter i.c. This very useful i.c. provides a sequential series of outputs, which are used to drive the indicator l.e.d.s, which change

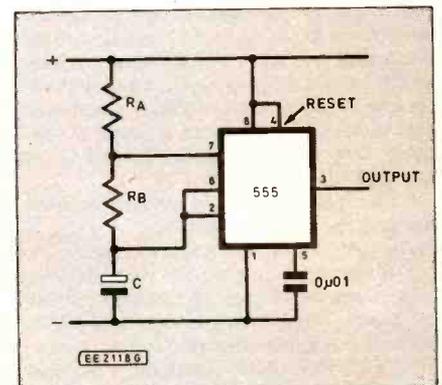


Fig. 1a. Using the 555 timer in the astable mode.


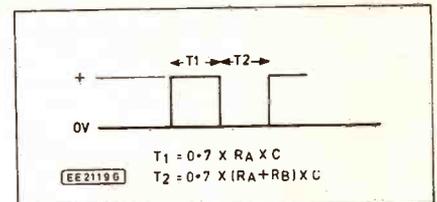


Fig. 1b. 555 timer astable timing diagram.

Fig. 2. Complete circuit diagram for the Simple L.E.D. Timer. The diodes D1 to D10 are contained in a ten-way l.e.d. module.

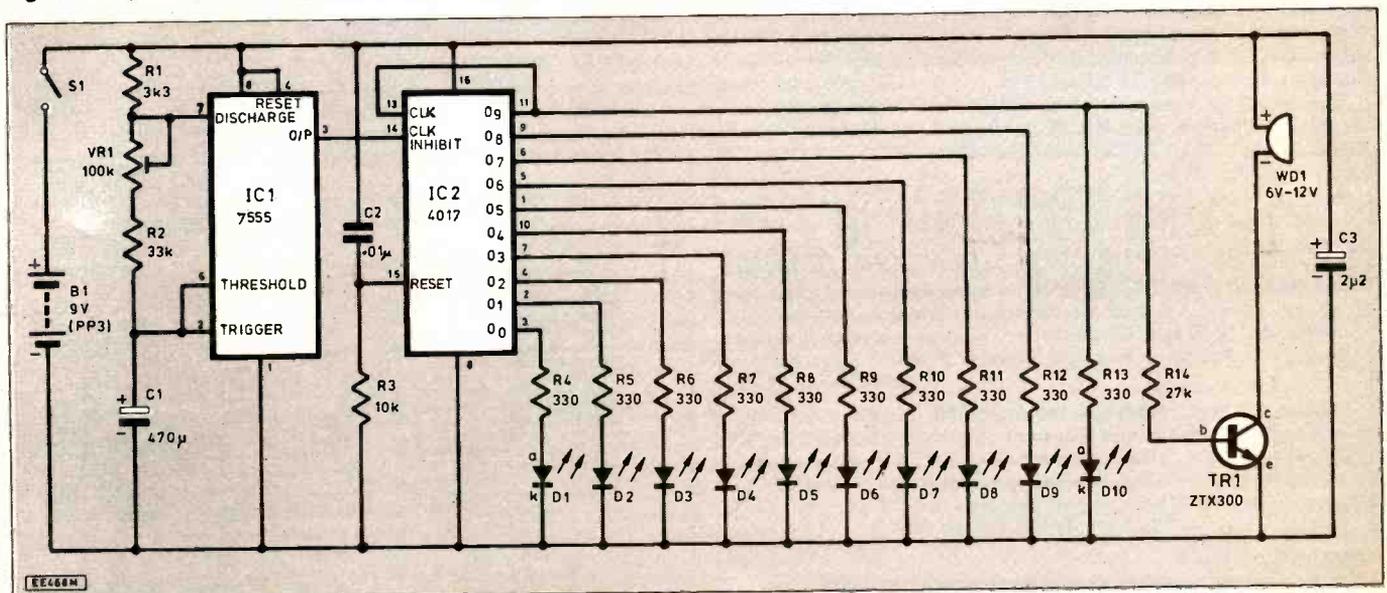

every time a clock pulse is received from the astable circuit.

The i.c. is provided with a "clock enable" input which is connected to the last output so that when this output is energised the clock is "locked". This provides a latching function which is used to keep the last building block (the alarm) operating until the circuit is switched off.

The final building block is a simple, single transistor current amplifier which is used to provide the current needed to drive the output buzzer, which requires more current than could be provided by the Johnson counter.

CIRCUIT DESCRIPTION

The complete circuit diagram for the Simple l.e.d. Timer is shown in Fig. 2. The clock pulse required to advance the "chaser" circuit is provided by IC1, R1, R2, VR1 and C1. This is virtually the same as that shown in Fig. 1a with the combination of preset VR1 plus resistor R2 taking the place of R_B. The addition of VR1 to the fixed resistor enables the time between the clock pulses to be adjusted, for instance, if used as an egg timer it can be calibrated to give exactly the correct time period which is in fact spread over the nine pulses required for the sequence.

Because IC2 is a CMOS device, the bipolar 555 timer can *not* be used in this project and IC1 *MUST* be the CMOS version, i.e. ICM7555 or TLC555C. There is however, some gain in the fact that the CMOS timer does not require the connection of a capacitor between the 0V power supply rail and pin 5.

The "chaser" function for the display is provided by IC2, which is a 4017 Johnson Counter. This i.c. has two inputs which can be configured in different ways so as to provide a number of different functions.

In this circuit the output from the IC1 is connected to pin 14 (one of the clock inputs) of IC2, and pin 13 (used in this case as a clock enable input) is connected to output 0₉ (pin 11) of IC2. Whilst 0₉ is at the logic 0 (0 volts) level, pin 13 is also held at logic 0.


In this condition the outputs 0₀ to 0₉ of the 4017 each go to the logic 1 (battery voltage) state in turn, changing every time that the clock pulse at pin 14 changes from the logic 0 state to the logic 1 state (the change going from logic 1 to logic 0 state is ignored) for as long as pin 13 is in the logic 0 state. This continues until 0₉ (pin 11) is energised going to the logic 1 state. Because this output is connected to pin 13, which acts as a clock enable input this is also forced to the Logic 1 state, causing IC2 to latch in its existing state, keeping pin 11 in the energised state and causing all further pulses at pin 14 to be ignored.

Capacitor C1 and resistor R3 form a very simple pulse circuit which makes the Master Reset input (pin 15) go momentarily to the logic 1 state. This causes the 4017 to be reset so that output 0₀ (pin 3) is energised, as soon as the timer is turned on.

DISPLAY

The ten outputs from the 4017 are each connected to an indicator l.e.d. (D1 to D10) through a 330 ohm dropping resistor (R4 to R13). The l.e.d.s work in the same way as ordinary diodes, by allowing a current to flow through in one direction, but not in the other. When a current flows through the l.e.d. it glows.

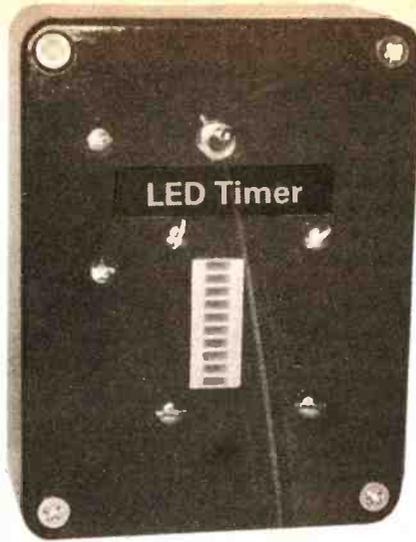It is important that the l.e.d. is not subjected to excessive current and the dropping resistors are included to restrict the



current flowing through the l.e.d. to a safe level. The l.e.d.s are made to illuminate in turn as each of the outputs of IC2 goes to the logic 1 state

CURRENT AMPLIFIER

Output 0₉ from IC2 is also connected via resistor R14 to the base of TR1. This transistor is used as a simple current amplifier to energise the audible warning device, WD1. When a current is allowed to flow through the base/emitter junction of TR1 it causes a larger current to be drawn through WD1 and the collector/emitter circuit of TR1, causing the buzzer to sound.

Capacitor C3 is a tantalum capacitor which is used to provide smoothing (decoupling) of the power supply rails in all CMOS circuits. This component is necessary to ensure correct operation of the circuit.

CONSTRUCTION

The timer project is easily made up using two stripboards as shown in the photographs and in Fig. 3 and Fig. 4. You will probably find it helpful to look at those whilst you make up the circuit.

The first task is to cut two pieces of stripboard to the correct size. You will need one piece, used for the main circuit board, which is 16 strips deep and 29 holes wide and another, used for the display, which is 16 strips deep by 14 holes wide. The sizes allow for drilling 4mm mounting holes in the positions shown, before starting to construct the circuit.

Similarly, before any components are mounted on the stripboards, you will need to break the copper tracks, as shown Fig.3 and Fig. 4. It is important that these track breaks are made completely so that not even the merest sliver of copper remains to bridge any tracks.

Although it does not make any difference to the operation of the circuit which order you make up the two boards or which order you insert the components into the boards you will probably find it best to make up and test the display board first and then go on to the main circuit board. The making up of both boards is easier to do if the components are inserted and soldered in ascending order of size.

DISPLAY BOARD

The display board is the simpler of the two boards to make up. The prototype of this project used a ten-way l.e.d. module as the display but there is no reason why you should not make use of ten single l.e.d.s instead if you prefer. The first stage of making up this board is to connect the wire links shown in Fig. 3.

COMPONENTS

Resistors

R1	3.k3
R2	33k
R3	10k
R4 to R13	330 (10 off)
R14	27k

All 0.25W 5% carbon

**Shop
Talk**

See page 636

Potentiometer

VR1	100k min. skeleton preset, horizontal
-----	---------------------------------------

Capacitors

C1	470μ p.c.b. elec. 10V
C2	0μ01 Mylar 16V
C3	2μ2 tantalum 10V

Semiconductors

D1-D10	10-way bar l.e.d. array (or 10X single l.e.d.s)
TR1	ZTX300 npn silicon
IC1	CMOS 7555 timer
IC2	4017 10-stage Johnson counter

Miscellaneous

S1	s.p.s.t. switch
WD1	6V-12V solid state buzzer
B1	9V battery (PP3 type)

Stripboards, 17 strips×29 holes (main board) and 16 strips×14 holes (display); 16-pin i.c. socket; 8-pin i.c. socket; plastic case; self adhesive stand-offs (7 off); battery connector; connecting wire; solder, etc.

Approx. cost **£ 10.50**
Guidance only



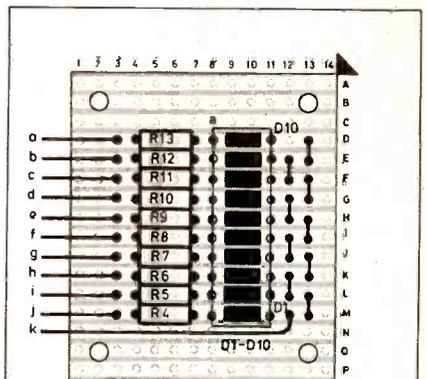


Fig. 3. Display board component layout and details of copper track cuts.

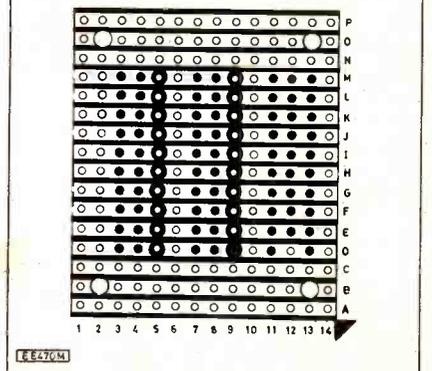

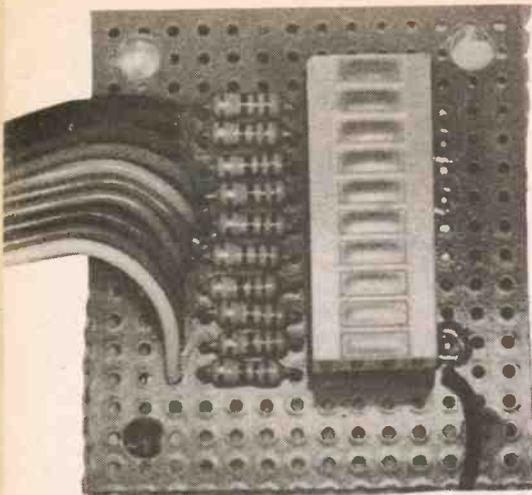

Completed display board showing the 10-way I.e.d. module.

There are a number of wire links required to make the common 0V connection to the I.e.d. cathodes (k) and you may prefer to make these connections by means of a single bare wire soldered to the underside of the stripboard.

The next stage is to insert the d.i.l. socket used for the I.e.d. display, followed by the display itself. If discrete I.e.d.s are being used, insert them into their correct places and solder them in place. These I.e.d.s are polarity sensitive so it is important to ensure that they are connected the correct way round, or else they won't work.

Also at this stage the wires linking the two boards together can be attached to the display board. Although the board has been designed so that ribbon cable can be used stranded, single-core wire can also be used successfully. If single wires are used then construction will be made easier if different coloured wires are used for this purpose.

Testing and fault finding of the timer should be carried out prior to inserting the boards in a suitable case.

DISPLAY BOARD TESTING


It is advisable to test the display board separately *before connecting it to the main driver board*. This is simply done by connecting the negative of the battery to the common connection on the board and touching *each* of the wires connected to the anodes (a) of the I.e.d.s, via the associated dropping resistors to the positive connection of the battery in turn.

Each I.e.d. should light up as the connection is made. If none of the I.e.d.s light up then the most likely causes are either that the 10-way I.e.d. module (if you are using one) is inserted into its holder the wrong way round or that there is a faulty connection in the common wire connecting all the cathodes (k) to the battery negative.

The first fault can be cured by rotating the module through 180 degrees. The second fault will have to be traced by testing the continuity (using the meter's "ohms" range) between the battery end of the common wire and its connections on the board.

If some of the I.e.d.s light but not all then it will be first necessary to check whether there is a pattern as to which diodes light and which do not. If there is a point in the sequence up to which they light and then the rest do not then it is likely that there is a break in the links joining the commoned cathodes together. This can be traced as described above.

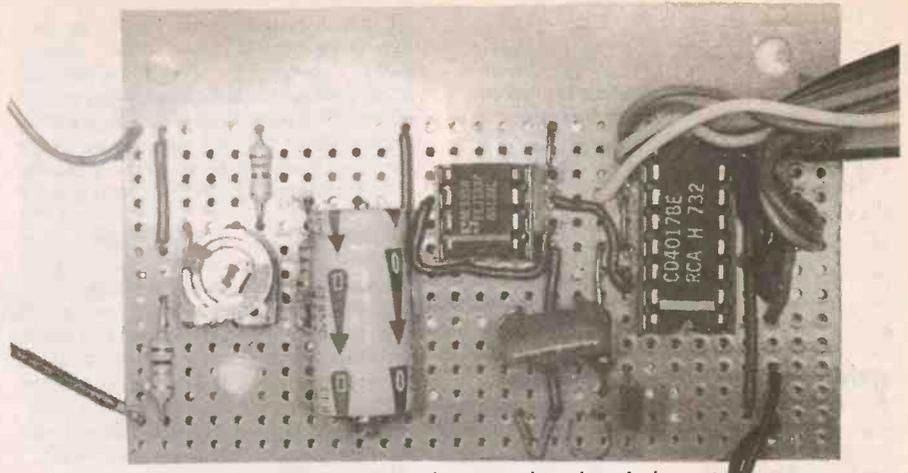If there is no pattern as to which I.e.d.s light and which do not then it is most likely



Layout of components on the completed main board.

that there are individual faults in each of the circuits leading to the anodes of the I.e.d.s, via the associated series resistor. The complete circuit, from the wire leading to the main board, through the series resistor and the connection to the anode's should be thoroughly checked with a meter to ensure complete continuity of the circuit. If neither of these checks reveal any explanation as to why a correctly installed I.e.d. does not light then it must be assumed that it is faulty and should be replaced.

MAIN BOARD

After the display board has been made and checked it is now time to construct the main board, starting by inserting the wire links as shown in Fig. 4.

The next task is to put the resistors in their correct places by first bending the wires of the resistor at right angles to the body of the component, so that they will fit

through the holes, as shown in Fig. 4. Also fit preset VR1 into the correct position and solder it into place.

The next item to be inserted into position is the I.C. holder. Although it is possible to solder the I.C. directly into place using a socket will both make the construction simpler and make for easier replacement if a fault should occur. It is important that you take care to make sure that the notch on the IC holder is facing towards the bottom of the stripboard as this will help you when inserting the ICs into place.

Next come the capacitors. C2 is a non polarised capacitor so it does not matter which way round it is inserted but C1 and C3 are electrolytic capacitors so it is important that they (the -ve connection usually marked on the component case - see photographs) are connected as shown in Fig. 3. Similarly care must be taken when mounting the transistor to ensure that its orientation corresponds with that shown in Fig. 3. and the photographs.

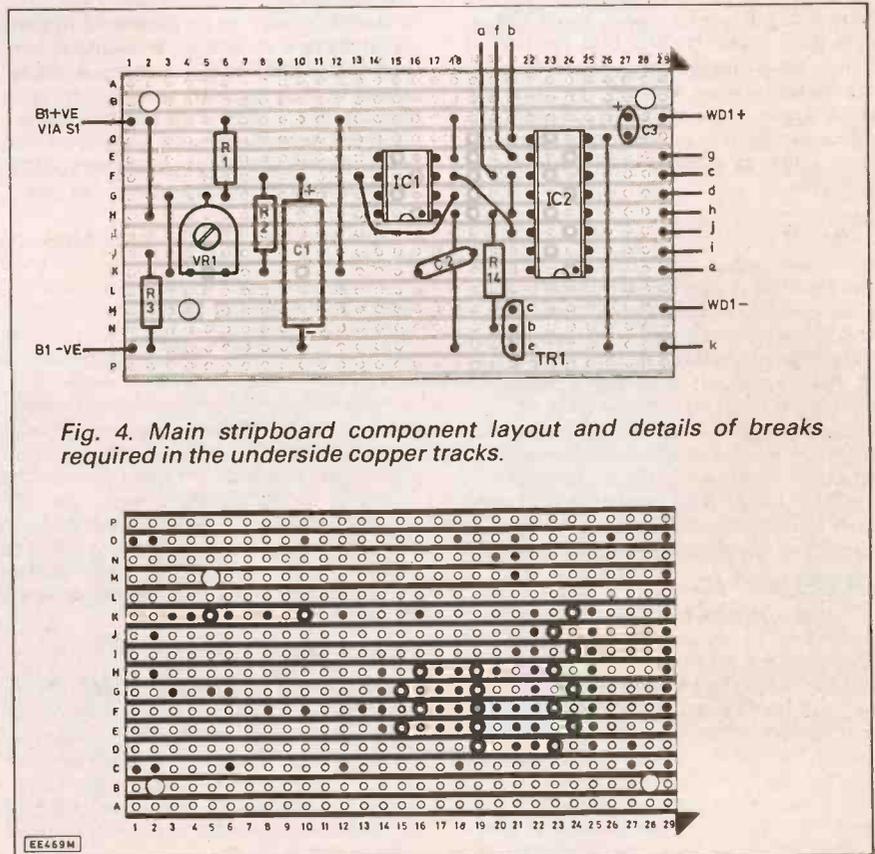


Fig. 4. Main stripboard component layout and details of breaks required in the underside copper tracks.

The final component to be mounted is the buzzer or other audible warning device. This device is often polarity sensitive so care must be taken, if the device is marked with polarities on the case or by means of red and black coloured wires, to make the connections with the correct polarity.

The wires connecting the battery to the circuit board can then be tinned and soldered into place. The black wire from the battery connector goes to the point on the stripboard and the battery connector's red wire will need to go to one of the switch terminals. Another wire is connected between the other switch terminal and the B1+V connection on the stripboard. The tested display board can now be connected to the main board taking care to ensure that the connections match exactly those shown in the board layouts.

The final step is to insert the i.c.s into their holders, making sure that the notch or indentation on the i.c. corresponds with the notch on the i.c. holder. Some i.c.s do not have a notch in one end but have a slight, circular dent near pin one.

MAIN BOARD TESTING

Before connecting the battery and testing the circuit you should carefully examine the stripboard to make sure that all of the components are inserted into the correct places, are the correct way round and that there are no blobs of solder shorting out the tracks. Once the board has been checked then the battery should be connected and you should be able to see the l.e.d.s turning on in turn and be able to set the rate of this by adjusting VR1.

If the circuit does not operate correctly it will be necessary to check for faults. You will probably find that you will need the aid of a multimeter to perform this stage of the process.

CLOCK GENERATOR

Check that the clock generator circuit, comprising R1, VR1, R2, C1 and IC1, is operating correctly. The best method of doing this is to use a voltmeter to measure the output voltage at pin 3 of IC1. If the clock circuit is operating correctly then the meter needle should be seen to register a slow pulse at approximately 30 second intervals.

If this does not happen then the next stage is to perform some basic voltage checks. You should be able to measure the battery voltage between any 0 volt connection and both pins 8 and 4 of IC1 as well as between the Battery + connection to the board and pin 1. If these voltages are not present this will indicate faulty wiring up of the stripboard.

If this does not produce a satisfactory solution then the output voltage at pin 3 of IC1 should be checked. If this is locked permanently at a fixed voltage then you should remove the i.c. from its socket and check the voltage at pin 3 connection again. If the voltage persists with IC1 removed then the fault does not lie with IC1 but most possibly with the wiring associated with the i.c. and the output to IC2 or its associated wiring.

The next step is to replace the i.c. and check the voltages at pins 2, 6 and 7. The voltage at pin 7 should be fluctuating slowly around a value which is roughly between $\frac{1}{3}$ rd and $\frac{2}{3}$ rds of the battery voltage. The voltages at pins 2 and 6 should be identical (because these two pins are connected together by a wire link) and these should also be fluctuating but at a voltage slightly less than that found at pin 7.

If both of these voltages are not present then the most likely cause is that the circuit from the + voltage rail, through VR1, R1 and R2 is not correctly made. This is best checked by measuring the voltage present between 0 volts and each of the points in the component chain through VR1, R1, R2 and C1 and investigating at the junction where no voltage is measured.

If a voltage is present between 0 volts and pin 7 but no voltage, or only a very small voltage, is measured between the 0 volts rail and pins 2 or 6 of IC1 then you should check that the resistance between pins 7 and 6 of IC1 is roughly equal that of resistor R2. If this is correct then check the resistance of capacitor C1 with the resistance range of your meter.

If the resistance is very low (less than about 500 ohms) then you should replace C1. If there is no voltage measurable between pins 6 and 2 of IC1 then this could be caused by a short circuit between the connections of C1 or by a short circuit within C1 or its connections to the stripboard.

If voltage is present at pins 2 and 6 of IC1 but it does not fluctuate then the likely

causes are that C1 is not correctly connected, is faulty or that IC1 is faulty. To check C1 you should touch connect another capacitor of similar value across the connections to see if this cures the fault. If this does not cure the fault check that the connection between the positive connection of C1 and pins 2 and 6 of IC1 is correctly made.

COUNTER

If voltage switching is taking place at the output of IC1 then the i.c. is working correctly and the fault is most likely to lie in the area of IC2 and its associated components. The first stage is to check that the power supply is correctly connected to pins 8 and 16. In case this voltage cannot be measured then you should check the connections to pin 8 and 16 and ensure that the wire links have been correctly made.

The next stage is to check that the clock pulses from pin 3 of IC1 are being correctly received at pin 14 of IC2. As these pulses are somewhat slow you may find it helpful to replace capacitor C1 with a lower value capacitor at this stage.


If the clock pulses are being correctly received at pin 14 of IC2 then it is necessary to check that pin 15, the master reset input, is at logic 0. If a logic 1 state exists at this point the circuit will be locked with output 0 permanently in the high state. If a logic 1 state is found at pin 13 then you should check very carefully for solder bridges between pins 15 and 16 of IC2.

If the clock pulses are being received at pin 14 and pin 15 is in the logic 0 state, then the counter should advance by one for every clock pulse received, provided that pin 13 (the count enable input) is in the logic 0 state. Because this pin is connected to pin 11 of IC2 then the counter should advance until pin 11 is forced to the logic 1 state.

Now check the Logic state of pin 3, which should be at logic 0 (0 volts). If the logic state at pin 13, is logic 1 or an indeterminate logic state then the connections between pins 13 and 11 (which is a wire link) should be carefully checked.

If this connection is correct, with no accidental connection between either of these pins and the battery supply line, then the states of the output pins of IC2 should be checked. You should find that only one of the outputs (pins 1, 2, 3, 4, 5, 6, 7, 9, 10 and

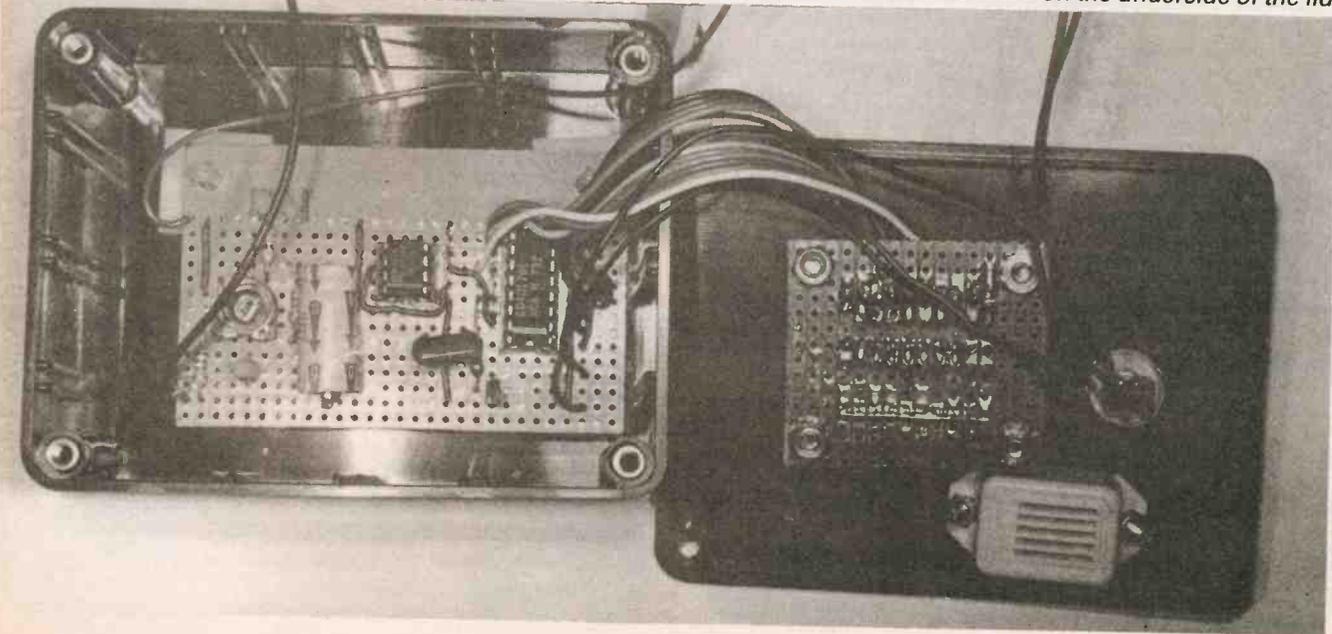The two circuit boards mounted inside the case and case lid. Note the audio buzzer mounted on the underside of the lid.



11) should be in the logic 1 state and all other outputs should be in the logic 0 state.

Immediately the device is switched on pin 3 should be at the logic 1 state. If this is not the case then the problem may possibly be that the master reset input (pin 15) is not receiving a quick reset pulse from the circuitry made up of capacitor C2 and resistor R3. The connection between the battery supply rails and these two components as well as that between the junction of R3 and C2 and pin 15 of IC2 should be checked.

If more than one of the outputs is in the logic 1 state then one must suspect that IC1 is faulty and must be replaced. Assuming that the l.e.d. display board has been checked and connected up to the main board beforehand then the states of these outputs may be monitored by observing the illumination of the l.e.d.s on the display board to the main board. If more than one l.e.d. lights at the same time then the connections between the ribbon cable joining the display to the main stripboard should be carefully checked to ensure that there are no solder bridges between adjacent tracks.

ALARM

The final part of the project to check is the alarm. This is very simple since it comprises a resistor, a transistor and an audible warning device. If the audible warning device does not sound when the last l.e.d. is illuminated then the circuitry associated with TR1 should be checked.

An initial test is to short out the emitter and collector of TR1, with a small piece of wire, and see whether the audible warning device sounds. If this produces no effect

then WD1 should be inspected to ensure that it has not been connected with the wrong polarity. If the polarity is correct, the connections from the positive power supply rail to WD1 and from the warning device to the collector of TR1 and from the emitter of TR1 to the strip carrying the battery negative connection should be checked.

If the audible warning device is working correctly then the operation of the transistor can be checked by making a temporary link, with IC2 removed from its socket, between pins 16 and 11 of IC2. This should produce a battery voltage measurable between the end of resistor R14 furthest away from the base of TR1 and 0 volts. If this does not occur then the connection between pin 11 and the i.c. end of R14 should be investigated.

With a battery voltage present at the junction of resistor R14 and pin 11 of IC2, a voltage of approximately 0.7V should be measurable between the base and the emitter of transistor TR1. If no voltage is measurable here then the resistance of R14 should be measured to ensure that it is actually acting as a resistor and not an open circuit. If this does not produce a resistance reading, close to the value specified for R14 and TR1 is connected the correct way round, then TR1 must be suspected of being faulty and should be replaced.

CASE

This project has been designed to fit inside a case. The first stage of preparation of the case is to cut, carefully, a hole in the case lid, the correct size to accommodate the l.e.d. display. This should be carefully measured, taking into account the need to

allow for stand-offs into which the mounting holes on the stripboard containing the display will fit. For this reason the positioning of the display should be done with some care. It is also necessary to drill a hole in the case lid to accommodate switch S1. Once the necessary holes have been drilled in the case lid it can then be lettered and the lettering protected with several layers of clear, spray on varnish.

Self adhesive stand-offs should be mounted on the component side of the display board and the board offered up to the inside of the case lid. When the display is correctly seated in the hole cut for it then the pads may be pressed firmly into place to hold the board in the correct position.

Self adhesive stand-offs can also be fitted to the main board (with the pads on the track side this time). The main board can be offered into place and the self adhesive pads pressed firmly onto the bottom of the case to hold the stripboard into the correct position. The battery can now be replaced in the battery clips, the circuit tested and preset VR1 adjusted to give the correct timing period before finally screwing down the case lid.

IN USE

The timer is very simple to use. All that is necessary to do is to operate switch S1, at which point D1 will come on. The remaining l.e.d.s will then come on in order, at approximately half minute intervals, until D10 is illuminated at the time that you have preset by adjusting VR1. When D10 comes on the audible warning device will sound and will continue to sound until S1 is switched off. □

SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. Build up service available if required.

MTX. Micro-miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range	£12.95
VT500. Hi-power audio transmitter. 250mW output. 20mm x 40mm 9-12V operation. 2-3000m range	£15.95
VOX75. Voice activated transmitter. Variable sensitivity. 30mm x 40mm. 9V operation. 1000m range	£18.95
CTX900. Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm. 9V operation. 1000m range	£21.95
DSX900. Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm. 9-12V operation	£21.95
HVX400. Mains powered audio transmitter. Connects directly to 240V AC supply. 30mm x 35mm. 500m range	£18.95
XT89. Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 28mm. 9V operation. 2-3000m range	£36.95
TX900. Tracker/Bleeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm. 9V operation. 2-3000m range	£21.95
ATR2. Micro size telephone recording interface. Connects between telephone line (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line 10mm x 35mm	£12.95
TLX700. Micro miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line 1000m range	£12.95
XML900. RF bug detector. Variable sensitivity. Triggers LED and bleeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation	£26.95
XL7000. Professional bug detector/locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate bleeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation	£54.95


UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Full catalogue available on receipt of 28p stamp. Trade enquiries welcome.

**SOMA
DESIGNS**

The Workshops, 95 Main Rd
Baxterley, Nr. Atherstone
Warks CV9 2LE

VISA
AMEX
0827 714476

NEW CATALOGUE OUT NOW!

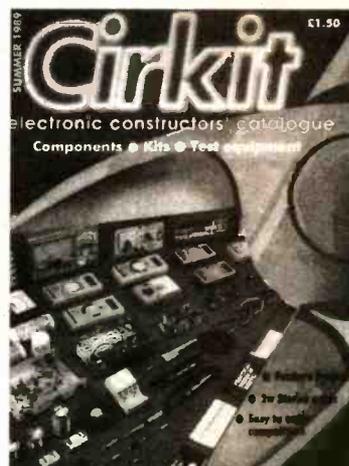

Over 3,000 product lines feature in the Summer 1989 edition of the Cirkitt Constructors' Catalogue, available from most larger newsagents or direct from the company priced at £1.50. The latest books, an RF frequency meter, two new PSU designs, a 3.5MHz converter and a 2 Watt stereo amplifier are among the innovative new kits this issue. In the test equipment section there's a whole new range of multimeters, a bench DVM and a triple output PSU.

For eagle-eyed readers there is the opportunity of winning an audio signal generator worth more than £180.00 in the latest fiendish competition. All prices now include VAT for quicker, easier ordering; and Cirkitt's same-day despatch of all orders, combined with value-for-money discount vouchers, makes the line-up even more attractive.

ONLY
£1.50

Cirkitt



Cirkitt Distribution Ltd.
Park Lane, Broxbourne, Herts EN10 7NQ.
Telephone (0992) 444111.

Beeb...Beeb...Beeb...Beeb...Be

... Disk Interfacing ... Disk Interfacing ... Disk Interfacing ... Disk Interfacing

THINK it is true to say that the BBC computer has one of the better cassette interfaces. Having used many home computers with a variety of cassette recorders, the only computer in my experience that gives more reliable results is the Dragon 32 (and the short lived Dragon 64 that followed it). An excellent but little copied feature of the BBC cassette interface is that when searching for a file it tells you what files it has found, and it gives a progress report as it goes through each file.

Once loading, if an error should occur you only need to wind the tape back a little and try again, rather than having to start from scratch. This makes loading programs and data from cassette about as painless as it possibly could be.

Disk Drive

Despite the BBC computer's good cassette storage system, a disk drive is still a tremendous advantage. Apart from the increased convenience, a lot of the more sophisticated BBC software is only usable on a disk based system.

This is usually due to memory restrictions necessitating the use of overlays. This is where only part of the program is ever in memory. If you call up a program function and the relevant part of the program is not in memory, it is automatically loaded from disk and executed. Any overlay already in that part of memory is over-written, and must be reloaded from disk if it is needed again.

This system is far from fast, with the same program sections often being loaded from disk time and time again. Its saving grace is that it enables the computer to run software of a complexity and sophistication that would otherwise be out of the question.

Such a system is not really practical with a cassette based system since locating and loading the overlays would take far too long. A disk system can quickly locate and load a file on the disk. The serial nature of a cassette system, plus its low loading/saving speed, render it far less versatile.

Slipped Disks

I must admit to having had my BBC model B computer for a number of years before I eventually fitted it with a disk interface and hooked on a twin disk drive. It was one of those things I had always meant to do, but considerable slippage occurred because I had gained the impression that it was a major job that required the removal of the main p.c.b. plus a lot of intricate soldering.

In fact the board can be left in-situ, and no soldering is involved. The disk interface socket is (of course) already present on the board, and it seems that the passive components are also ready-fitted, as are holders for the integrated circuits. Fitting a disk interface is basically just a matter of taking off the computer's lid and plugging in the eleven missing integrated circuits.

It is a little more difficult than this in that the integrated circuit holders are mostly tucked away beneath the keyboard and behind the keyboard cable and connector. You therefore need to remove the three nuts and bolts that hold the keyboard in place so that it can be removed to give easy access to the holders.

The eleven integrated circuits are as follows:—

IC78	8271
IC79, IC80	7438 (2 off)
IC81, IC86	74LS393 (2 off)
IC82	74LS10
IC83, IC84	4013BE (2 off)
IC85	4020BE
IC87	74LS123

Acorn DFS ROM (fit in any sideways ROM socket).

The integrated circuit holder indicates the correct orientation for each device (they are all fitted with pin 1 towards the rear of the computer). These integrated circuits are standard types apart from the 8271 disk controller and the Acorn DFS ROM.

The 8271 is actually obsolete and has not been manufactured for some years, but it is still available. Like all disk controller chips it is a complex device, and is not exactly cheap. In fact this component accounts for what is probably about 75 per cent of the disk interface's cost! The Acorn DFS ROM seems to be available from the usual stockists of Beeb bits and pieces.

There are actually alternative DFS ROMs that can be used, such as the popular Watford type (which is the type I fitted). The real Acorn ROM is the safest option though, and all disk software should run without difficulty using this chip. Comparing the prices of sets of components bought individually with the cost of complete DFS kits, a kit represents a more convenient way of buying the components, and could be cheaper as well.

Complications

In order to get the disk interface to operate properly there are one or two minor details to be attended to. Just what you need to do depends on the issue number of the board in your computer. My Beeb has an issue 4 board, which is probably the most common type. On issue 4 (or higher) types you only need to locate and cut link S9 on the board. This link is about 2.5cm to the left of pin 1 on the 8271 chip (IC78).

On issue 1, 2, and 3 boards matters are slightly less straightforward. The track running from IC27 pin 9 to the right hand pad of link S9 has to be cut. Then pin 9 of IC27 has to be cut as close to the board as possible, and lifted upwards slightly so that it is clear of the board. Thin insulated connecting wire is then used to connect IC27 pin 9 to the right hand pad of link S9! This may sound a bit odd, but I am assured that this is

the correct procedure. Presumably this process gets rid of one or two unwanted connections to IC27 pin 9.

Note that this modification assumes that the computer is a model B (not a model A) and that it is fitted with a series 1 operating system. Model A and early model B computers require a small amount of updating before they can take this modification. If you have one of the few machines in these categories it would probably be as well to get an authorised dealer to fit the disk interface and check that everything is as it should be.

Incidentally, this upgrade equips the computer with the standard (single density) DFS, not the more advanced ADFS type. However, for most purposes the DFS interface should be perfectly satisfactory.

Optimising

On the BBC keyboard p.c.b., about 5cm to the right of the spacebar, there is provision for an octal d.i.p. switch or link wires to be fitted. These control a few start-up options, one of which pertains to the disk drives.

Switch 1 selects the master filing system if the DNFS ROM is fitted. Normally this switch is set to the open position, but closing it selects the econet system (if fitted). Switch 2 is unused.

Switches 3 and 4 are used to select a DFS operating speed to match the disk drives. The table below shows the effect of the four switch setting combinations.

Switch 3	Switch 4	Head Settle Time	Head Step Time	Head Load Delay
Closed	Closed	16	4	0
Closed	Open	16	6	0
Open	Closed	50	6	32
Open	Open	20	24	64

The original Acorn drives were quite slow, and require the default setting of both switches/links open. Most modern drives, including the popular Mitsubishi and current Tandon drives, require the fastest speed (both switches/links closed).

If in doubt, using the default settings seems to give satisfactory results with fast or slow drives, but will give less than optimum performance with fast drives. A little trial and error is perhaps the best way of finding the best settings in the absence of any definite information on your drive or drives.

An auto-boot option is provided by switch 5. This is not normally needed, and this switch is usually set to the open position. Pressing SHIFT-BREAK then produces an auto-boot. Switches 6, 7, and 8 select the initial screen mode. All switches closed selects mode 0, running through to mode 7 with all switches open. Note that all these functions are under software control

via the *FX255 operating system command.

Connections

One reason for the success of the BBC computers is that, unlike many home computers of the early eighties, they use mainly standard interfaces. The disk interface is of the standard type, with a 34-way IDC socket at the computer end which connects to a 34-way edge connector at the disk drive. There are a lot of BBC compatible drives available, including some inexpensive types suitable for the DIY enthusiast. 5.25 inch drives are probably the best choice as most BBC disk software is on disks of this size.

The BBC computer will work with 40 or 80-track drives, single or double sided. Double sided 40-track drives are a safe option and are quite abundant. If you get 80-track drives it is advisable to buy a type that can be switched to 40-track operation so that they can read any software supplied only in 40-track format.

Using a 34-way IDC connector, a 34-way (2 x 17 way 0.1 inch pitch) IDC edge connector, and about 0.6 metres of 34-way ribbon cable it is not too difficult to put together your own cable. The main point to watch is that you do not get the connections crossed over. Pin 1 of the BBC computer's disk connector is at the top left hand corner when looking onto this port from the front of the computer. Pin 1 should be marked on the male edge connector of the disk drive.

For a twin drive system two edge connectors must be fitted to the cable. The first is fitted at the end of the cable in the usual way, while the second is fitted the same way round and about 100 millimetres in from the end of the cable. This assumes that the two drives will be fitted in the same case stacked one above the other. Different mounting arrangements could require greater separation between the two edge connectors.

Power

The power port of the BBC computer is designed primarily for powering a disk drive, although many users prefer disk drives which have their own mains power supply. This leaves the computer with plenty of spare capacity to power other add-ons and add-ins. Also, the power port of the computer is only guaranteed to be

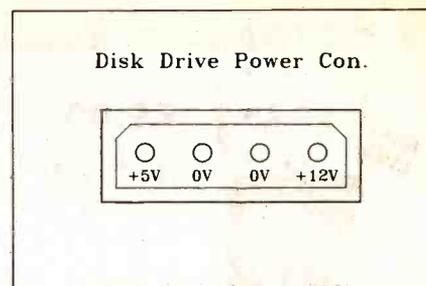
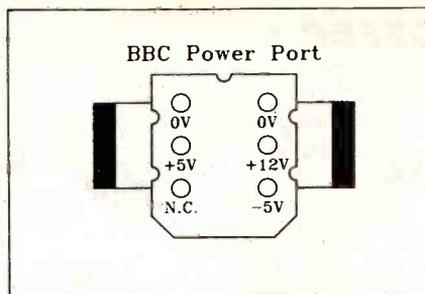


Fig. 1. Details of the BBC's power port and the standard five-way connector used on disk drives.

able to power one disk drive, but many users wish to fit two drives (the power port can in fact power twin drives, but only if they are both low consumption types).

Anyway, Fig. 1 gives details of the BBC computer's power port and the standard five way connector used on disk drives. Unfortunately, both types of plug are difficult to obtain, but you might be able to obtain them from one of the larger Acorn stockists. Alternatively, ready made BBC disk drive power cables are readily available, as are the main disk drive cables.

Drive Settings

In books and articles on disk drives it is normal to refer readers to the information leaflet for their drives in order to get information on the correct settings for the jumper leads. I have bought about half a dozen "bare" drives over the years, and in my experience disk drives are simply not supplied with any technical information. With luck you might be able to squeeze some out of your supplier.

The main thing to get right is the drive number setting. Usually there are jumper terminals marked something like "DS0", "DS1", "DS2", and "DS3", which are the drive select terminals. If you only have one drive, then this should have the "DS0" terminals linked with a jumper. If it is a double sided drive, then its two sides are effectively drives 0 and 2.

If a second drive is fitted, this should have the "DS1" terminals linked. It then effectively drives 1 and 3 if it is a double sided type. If you are using single-sided drives, it is possible to have four of them

acting as drives 0 to 3 by linking a different set of drive select terminals on each drive.

Other terminals that are usually found on a disk drive are the "MUX" (or just "MX"), "MS", and "HM" types. The "MUX" (multiplex) terminals are linked if only a single drive is used. "HM" (head motor) are always left open, and "HS" (head select) are always fitted with a jumper. There may well be several other pairs of terminals, but you can usually get away with simply leaving these at their default settings.

Termination Resistors

One further complication is that disk drives are fitted with termination resistors of about 150 ohms in value that can be switched in or out of circuit (or fitted/unplugged in some cases). The idea is that these resistors should only be in-circuit on the drive at the end of the cable. With a single drive, these resistors should therefore be in-circuit. With a twin drive system they should be in-circuit on the drive at the end of the cable, and out of circuit on the other drive.

On my Mitsubishi drives these resistors are in the form of an octal 150 ohm resistor in a standard 16 pin d.i.l. encapsulation. This is fitted in its socket or unplugged, as required.

I must admit that I only recently learned about the use of termination resistors in disk drives. I have been using twin drives with both of them fitted with the termination resistors. Although technically incorrect, the drives have worked faultlessly for about four years!

EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

NEWSAGENT ORDER FORM

Please reserve/deliver a copy of **Everyday Electronics** for me each month.

Signed

Name and Address
(BLOCK CAPITALS PLEASE)

Everyday Electronics is published on the first Friday of each month and distributed by Seymour.

Make sure of your copy of EE each month—cut out this form, fill it in and hand it to your newsagent.

EVERYDAY ELECTRONICS

SUBSCRIPTION ORDER FORM

Annual subscription rates (1989): UK £15.70. Overseas £19 (surface mail) £36 (air mail)
To: Everyday Electronics, Subs. Dept., 6 Church Street, Wimborne, Dorset BH21 1JH.

Name

Address

I enclose payment of £..... (cheque/PO in £ sterling—only payable to Everyday Electronics)  
Access or Barclaycard/Visa No.

Signature..... Card Ex. Date.....

Please supply name and address of card-holder if different from the subscription address shown above.

Subscriptions can only start with the next available issue. For back numbers see the Editorial page.

★ OCTOBER SPECIAL OFFER ★



£9.99

BATTERY TESTER

A compact dry cell battery tester capable of testing 15 voltage/battery types from 1.35V hearing aid batteries to 22.5V batteries. Test leads store in rear of case. Packed on attractive display card. Dims.: 105x64x32mm



THE MALTINGS, HIGH STREET, WEM, SHROPSHIRE SY4 5EN, DEPT EE10

Tel: 0939 32763 Telex 35565 Fax 33800

Electronic Component Mail Order Company — Established 1972
217 PAGE CATALOGUE AVAILABLE — SEND £1 FOR YOUR COPY
Including Discount Tickets — 50p off £5+ order; £1 off £10+ order; £5 off £50+ order.

★ Please add £1.00 postage and packing to all orders unless stated. ★

FM TRANSMITTER

Very High Quality MINI-BUG — Ideal for Baby Alarms etc.!!
A very good range is obtainable — we have obtained over 1/2 mile, but it does depend on conditions. Simply remove the cover — insert battery — and you're ready to go. Reception can be obtained on any F.M. radio. Frequency: 105-108 MHz F.M.
Power: PP3 9V Battery (not included)
Dimensions: 4.25" x 2.25" x 0.75"
Order Code — SQ034

£9.98



SOLDER 60/40

A 500g reel of 22 swg multicore solder 60% tin, 40% alloy non-corrosive.

£5.75

ALSO 18swg



OSCILLOSCOPES

TEKTRONIX D755 — 50 meg solid state
Kartridge £10.00

Price incl. VAT £295

VIDEO LEAD KIT A

1 lead BNC to phono (1 metre in length), 1 lead 5 pin DIN 180° to phono (1 metre in length). Originally intended for Fern. 3V23, 3V29, 3V30, JVC HR 7700E etc. etc. Many other applications.
Price: £1.99 each
10+ £1.50 each

LOGIC PROBE

Simple to use — good quality — logic probe. Displays the logic state of each gate of TTL, C-MOS, etc. devices. Logic state displayed in light and sound. Pulse enlargement capability allows pulse detection down to 25ns.
Supplied complete with comprehensive instruction manual.
Specification:
Working voltage — 4-16dc.
Thresholds: HI - 70%; LO - 30%Vcc
Input Impedance: 1 Mohm
Max. input frequency: 20MHz
Order Code — TEST/LOGIC

Price **£9.90**

VERO — VERO — VERO

17 9" x 33 4" £6.75
33 4" x 33 4" £2.36
5" x 33 4" £1.99
Easiwire Kit £15.00
Verobloc £6.71
ATTENTION RETAILERS — Trade prices available on full Vero range — minimum order £25

12V RECHARGEABLE UNIT

10 x D x Size Ni-Cads (4 ah) encapsulated in a black case. Fuse holder. Gives 12 volt output when charged. Ex-equipment. Fully guaranteed. Dimensions: 245 x 75 x 75mm.
£9.19 each + P&P £1.85
£8.34 for 10 + P&P £4.50
CHARGER FOR 12V UNIT £11.50 + P&P £2.12

MARCO TRADING'S LATEST 217 PAGE CATALOGUE NOW READY ONLY £1

FULL OF CMOS, TRANSISTORS, LS, ICs, DIODES, BRIDGES, VALVES, RESISTORS, BOXES, BOOKS, SOLDERING TOOLS, TEST GEAR, METERS, CABLE, KITS, SPEAKERS, AERIALS, AUDIO ETC. ETC. AND INCLUDING £6.50 OFF IN DISCOUNT TICKETS WITH SPECIAL OFFER LIST, PREPAID ENVELOPE AND ORDER FORM.

VISIT OUR RETAIL SHOPS

WEM (MARCO), The Maltings, High St., (0939) 32763
WOLVERHAMPTON (WALTONS), 55A Worcester St. (0902) 22039
BIRMINGHAM (SUPERTRONICS), 65 Hurst Street (021) 666 6504

NI-CAD BATTERY CHARGER

Universal 1+ £4.99 each
10+ £4.75 each
4x AA Charger £4.95 each

NI-CAD RECHARGEABLE BATTERIES

	1 off	10 off
AAA	£1.50	£1.30
AA	95p	85p
C	£1.95	£1.80
D	£2.00	£1.85
PP3	£3.90	£3.20

SPECIAL PRICE ON VARTA NI-CAD PP3
£3.50 each, 3 for £10
WHILE STOCKS LAST

"CLOSED-CIRCUIT" TELEVISION SYSTEM

PRICES **£160** COMPRISING:
1x CAMERA 1x MONITOR 1x CAMERA BRACKET




(Plus £12.00 carriage)

● ALSO NEW EQUIPMENT AVAILABLE

12V Twin Fluorescent lamp 12" Double Tubes

IDEAL FOR BOATS, CARAVANS, VANS, ETC

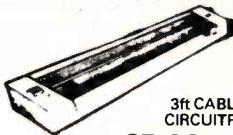

£5.99 EACH

ATTRACTIVE WHITE FITTING, RIBBED PERSPEX DIFFUSER, ON/OFF SWITCH, 3ft CABLE, TRANSISTORISED CIRCUITRY, KEYHOLE FIXING, 12V D.C. 8W TUBES 368x67x43mm

QUARTZ-HALOGEN SPOTLIGHT




£5.99

★ LEARN BY BUILDING ★ ENJOY BY USING ★

PROJECT KITS

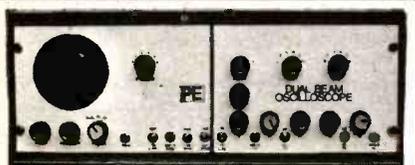★ BE CREATIVE ★ RAISE YOUR SKILLS ★ GET KITTED! ★



DUAL BEAM OSCILLOSCOPE

2Y-amps, 6 ranges, variable level, DC to over 1MHz. 4 modes — Y1, Y2, Y1 & Y2, Y1 & Y2 to X. Time base variable from 0.05Hz to 20KHz. Variable sync level, polarity and source. Separate bright-line, brilliance and focus controls. Independent trace deflection controls. Details in catalogue.

BURGLAR ALARM CONTROLLERS

MULTIZONE CONTROL SET280

£23.90

Two entry-zones, anti-tamper loop, personal attack, entry-exit timing, timed duration, automatic resetting, latching LED monitors.

SINGLE ZONE CONTROL SET279

£10.50

With timed duration control and latching LED monitor. Both units can be used with any standard detection devices, such as contact or magnetic switches, pressure pads, tremblers, ultrasonics, infrared etc., and will activate standard bells, strobes or sirens.

COMPUTER KITS

The software listings published with the computer kit projects are for use with C64, PET and BBC computers.

CHIP TESTER SET258F £41.50

Computer controlled logic and chip analyser.

EPROM PROGRAMMER SET277 £26.20

Computer controlled unit for 4K Eproms.

MICRO-CHAT SET276 £69.50

Computer controlled speech synthesiser.

MICRO-SCOPE SET247 £49.50

Turns a computer into an oscilloscope.

MICRO-TUNER SET257 £57.40

Computer controlled, tuning aid and freq counter.

MORSE DECODER SET269 £26.70

Computer controlled morse code-decoder.

MORE KITS IN CATALOGUE
SEND MEDIUM S.A.E. FOR CATALOGUE AND WITH ALL ENQUIRIES
(OVERSEAS SEND £1.00 TO COVER POSTAGE)

VARIOUS

VOICE SCRAMBLER SET287 £49.50

32 switchable channels to keep your communications confidential.

STORMS! £35.50 each unit

Raw nature under panel control! Wind & Rain SET250W.

Thunder & Lightning SET250T.

DISCO-LIGHTS SET245F £69.50

3 chan sound to light, chasers, auto level.

EVENT COUNTER SET278 £36.60

4-digit display counting for any logic source.

PE FREQUENCY COUNTER AND GENERATOR

DETAILS IN CATALOGUE

ENVIRONMENT

SIDEREAL CLOCK SET295 £54.50

Dual purpose star-time and solar-time digital clock with alarm.

WEATHER CENTRE

Keep the Met Office in check and monitor the wind speed and direction, rain, temperature, soil moisture and sunny days.

Six detector circuits — KIT 275.1 **£18.50**

Automatic metered control monitor — KIT 275.2

Optional computer control circuit — KIT 275.3 **£15.50**

ELECTRONIC BAROMETER SET285

£41.20

Computer controlled unit for monitoring atmospheric pressure.

GEIGER COUNTER SET264 £65.50

A nuclear radiation detector for environmental and geological monitoring. With built in speaker, meter and digital output. This project was demonstrated on BBC TV.


ORDERING

Add 15% VAT. Add P&P — Sets over £50 add £3.00. Others add £2.00. Overseas P&P in catalogue. Text photocopies — Oscilloscope £3.00, Geiger £3.00, Weather £2.00, others £1.00, plus 50p post or large SAE. Insurance 50p per £50. MAIL ORDER, CWO, CHG, PO, ACCESS VISA. Telephone orders: Mon-Fri, 9am — 6pm. 0689 37821. (Usually answering machine).


MORE KITS IN CATALOGUE

PHONOSONICS, DEPT EE90, 8 FINUCANE DRIVE, ORPINGTON, KENT, BR5 4ED.

MAIL ORDER

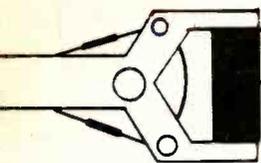

Robot Roundup

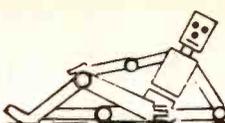

NIGEL CLARK

With the start of a new school term it is again time to see what is on the market. As usual every effort is made to ensure that the information is accurate but the prices (quoted ex-VAT) are approximate and most companies offer education discounts so it is best to check with suppliers for exact prices.

ARMS

Armdroid HS 1B (Hasfield Systems) 5-axis plus gripper, servo-driven with steel-reinforced belt transmission. Lift 250gms. Control by BBCs, Commodores and IBM. £750.

Alfred (Research Development Associates) 5-axis plus gripper, servo-driven with toothed belts, lift 170gms. Has work cell. Between £200 and £250.

Atlas II (LJ Technical Systems) 5-axis plus gripper, stepper driven with toothed belts. Lift 1kg. On-board micro and teach pendant for stand-alone system. Wide range of operating software. Controllable from BBC and IBM compatible machines. Work cell available. Arm costs £3,300, IBM interface £350.

Beasty Plus arm (Commotion) 3-axis plus gripper, servo-driven, lift 75gms. Supplied with kit and instructions on how to build four different configurations and comprehensive user guide. Kit costs £120 and £35 for interface.

Cyber 310 (Computer Voice) 5-axis plus gripper, stepper driven with belt and cable transmission. Lift 250gms. Software for all usual micros. Staged a recovery in last year and now has a work cell. £700.

ESA 1010 (Feedback Instruments) 4-axis plus gripper. Updated version of Powertran's Armatrol. Only machine able to work off the ZX81 as well as most of the other micros. £1,100.

EMU (LJ Technical Systems) 4-axis plus gripper, servo-driven with direct mechanical linkages, lift 100gms, software for BBC and LJ's Emma. £425, workcell extra.

HRA 934 (Feedback Instruments) 5-axis plus gripper, hydraulically powered.

Lift 2.5kgs. On-board processor and can be controlled by BBC, Apple, C64. £3,200.

MA 2000 (Tecquipment) 6-axis plus gripper, servo-driven with toothed belt transmission, pneumatic gripper. Lift 1kg. Software for BBC and Open University's Hektor, was developed for Open University courses. Gripper is fitted to take pneumatic tools and wired for sensors. Can be linked with the MA 3000 more robust industrial version. Sells at £5,500 for export including basis software, discounts available for UK.

MA 3000 (Tecquipment) 5-axis arm plus gripper. Larger but simpler version of MA 2000. Can be linked with MA 2000 as part of system. £10,750.

MARS (Research Development Associates) Also known as Modular Automation Robot System. Modules can be fitted together in a number of ways including normal 5-axis arm and SCARA. Servo-driven can lift 1kg. Uses same on-board processor as Alfred and can be controlled by most of the popular micros except Atari. £2,400. Larger industrial version developed recently costing £4,000.

Mentor (Cybernetic Applications) 5-axis plus gripper. Servo-driven, lift 1kg. Can be controlled by small-scale model simulator. Software for BBC, IBM and Apple. Can be networked with up to three other Cybernetic machines and work cell. £900.

Naiad (Cybernetic Applications) 5-axis plus gripper, lift 500gms, powered by hydraulics (water). All axes driven by different kinds of hydraulic piston, all cylinders made of see-through plastic. Gripper can be powered by hydraulic system or pneumatic piston for which supply provided at extra cost.

As with Mentor can be controlled by simulator and networked with up to three other Cybernetic machines and work cell. Software for BBC, IBM and Apple. £1,750.

Neptune I (Cybernetic Applications) 5-axis arm plus gripper. Electro-hy-

draulically powered (water) lift 2.5kgs. Software for BBC, IBM and Apple and on-board processor. As with Mentor can be controlled by simulator and networked with up to three other Cybernetic machines and work cell. £4,040.

Neptune II (Cybernetic Applications) 6-axis plus gripper. Rest of specifications same as for Neptune I with addition that it can be controlled by touch sensors on all axes. £5,490.

Robotarm (Logotron and Resource) 5-axis plus gripper, bucket or magnet pick up, servo-driven, battery-powered and has two standard Atari joystick ports for control. Sold as educational package with interface for BBC. £99.95.

Teach robot (Remcon Microelectronic) 5-axis plus gripper, lift 200gms. Four of axes driven by linear rams, feedback by shaft encoders on motors. Available with software and interface for IBM and compatibles. £995.

SCARA ARMS

IVAX 901 (Feedback Instruments) 4-axis plus pneumatic gripper, servo-driven, lift 500gms, software for on-board processor, IBM, BBC and Apple. Work cell available. £3,600.

PW801 (Feedback Instruments) 4-axis plus gripper, servos on all axes except end rotation which has a stepper motor, lift 2kgs. Software for IBM and Apricot. Work cell available, interchangeable gripper jaws. £7,350.

RTX (UMI) 6-axis plus gripper, servo-driven, lift 4kgs, software for IBM. £7,480.

RTX 100 (UMI) More robust version of RTX, intended for light industry. £9,100.

Serpent I (Cybernetic Applications) 4-axis plus gripper, servo-driven with pneumatic power for vertical movement of gripper, height of arm set manually, software for BBC, IBM and Apple. Can be networked with up to three other Cybernetic machines and work cell. £2,700.

Serpent II (Cybernetic Applications). Same as above except that it has longer reach. £2,735.

Others


Kestrel (Cybernetic Applications). Gantry supported arm with 4-axes plus gripper, stepper driven, works in x, y and z co-ordinates, lift 2kgs, vacuum or two-fingered pneumatic gripper. Software for IBM, can network with up to three other Cybernetic machines and work cell. £4,250.

MOBILES


Jessop Turtle (Jessop Microelectronics) also known as the Edinburgh Turtle, it looks like an upturned mixing bowl, one of the earliest turtles controlled by a version of Logo. Powered by servos with optical encoders, includes pen. Linked to computer by umbilical cord. Software for BBC, Apple RML and IBM. £220.

Lego Buggy (Lego and Resource) Two-wheeled servo-driven, built from

Kestrel from Cybernetic

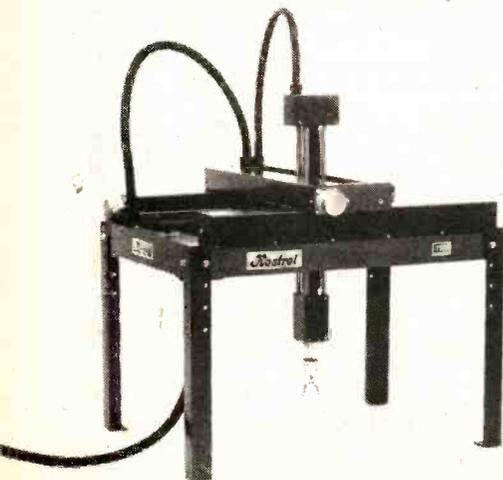

Hasfield Armdroid HS1B

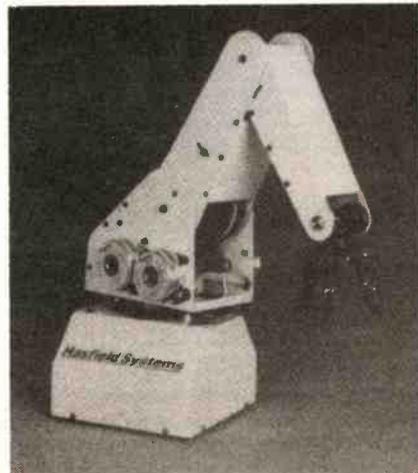

Lego kit with Resource control board attached. Maze following, detecting obstacles, speed control and bar code reading can be done. Software in Buggy Basic, Control and Control IT. £30 for buggy alone, £50 for control board.

Roamer (Valiant Technology) Two-wheeled, servo-driven, stand-alone mobile, uses Logo-like language with instructions entered by keypad on top of the Smartie-shaped machine. Pen holder. Can be customised with the kits supplied. £90 retail, £70 educational.

Trekker (Clywd Technics) Two-wheeled servo-driven. Developed by children at North Wales secondary school and given extensive in-house testing before being put on market with substantial software and documentation. Software for BBC and Commodores and extension pack for junior schools. £180.

Valiant Turtle (Valiant Technology). Two-wheeled servo-driven with pen, remote-controlled via infra-red link, designed to resemble a turtle. Uses version of Logo and software for BBC, Apple, IBM. Microworlds being created in which it can be used. £300 retail, £250 educational.

HEROS

Hero 2000 (Maplin Professional Supplies) is the only one left of the range which used to include Hero I and Hero Junior. Large mobile. Has light, sound and motion detectors, rangefinder and speech. 5-axis arm driven by stepper motors, lift 1lb. Gripper has touch sensor to adjust gripping force. Easily built and dismantled to show how it works. £2,500 in kit.

ADDRESSES

Clywd Technics, Antelope Industrial Estate, Rhydynwyn near Mold, Clywd.
Commotion, 241 Green Street, Enfield, Middlesex EN3 7TD
Computer Voice, Cherry Trees, Milwich, Stafford ST18 0EG.
Cybernetic Applications, West Portway Industrial Estate, Andover, Hampshire SP10 3LF.
Feedback Instruments, Park Road, Crowborough, East Sussex TN6 2QR.
Hasfield Systems, The Old Rectory Stables, Hasfield, Gloucester GL19 4LG.
Jessop Microelectronics, Unit 6A, 3 Long Street, London E2 8HJ.
Logotron, Dales Brewery, Gwydir Street, Cambridge.
LJ Technical Systems, Francis Way, Bowthorpe Industrial Estate, Norwich.

Maplin Professional Systems, PO Box 77, Rayleigh, Essex.
Remcon Microelectronic, PO Box 81, Chislehurst, Kent BR7 6LP.
Research Development Associates, BTC, Bessemer Drive, Stevenage, Hertfordshire.
Resource, Exeter Road, off Coventry Grove, Doncaster DN2 4PY.
Stevenage Adventure Workpacks, 29 Lytton Fields, Knebworth, Herts SG3 6BA.
Tecqupment, Bonsall Street, Long Eaton, Nottingham NG10 2AN.
Tribotics, 27 Crawley Mill Industrial Estate, Witney, Oxfordshire.
UMI, UMI House, 9-15 St James Road, Surbiton, Surrey.
Valiant Technology, Gulf House, 370 York Road, Wandsworth, London SW18 1SP.

KITS

Numerous suppliers provide collections of components including motors which can be used to build robotic models. However, only **Fischertechnik**, **Lego**, **Tribotics** and **Stevenage Adventure Workpacks** provide kits which can be linked to a computer.

Fischertechnik was first in the market with its computing kits including d.c. motors, potentiometers, switches plus a large collection of parts for a variety of models including plans for two arms. The plans have been recently expanded to include a number of other models including a simulation of a welder.

Lego with Technic series includes kits from which an arm, a plotter and a

buggy can be made. Servos with optical encoders are available as are programs and an interface for the BBC and a battery-powered controller. Special kits and packages for schools.

Tribotics provides a larger-scale series of models based around drain-piping. Variety of devices including an arm, mobile with caterpillar tracks and walking robot.

Stevenage Workpacks provide kits of varying complexity. Some only include the electronics and mechanics with templates from which the wooden components can be made. £500.

Prices of all the kits vary and it is best to enquire what each pack contains at the different price levels.

PCB DESIGNER


FOR THE 48K ZX SPECTRUM

Now you can produce high quality printed circuit boards/circuit diagrams/component layouts on your 48K ZX Spectrum. If you don't own one it's worth getting one just for this suite of programs! Comprehensive manual included with getting started tutorial.

FULL SUITE FOR ONLY £30.00 INC.


PCB LAYOUT:

Produce quality printed circuits directly from your EPSON RX/FX or compatible dot matrix printer using a dense 1:1 printout on positive photoresist coated board. Or super quality using x2 printout and photoreduction. Many features such as 15 track widths; 15 pad sizes; 16 transistor/corners; 20 connectors; large multiscreen WYSIWYG display gives a clear uncluttered view of pads, tracks and drill holes; 0.1in. grid on/off; Block move; copy; mirror; rotate; erase; area fill (ideal for earth plane); preview; undo; dimensionally accurate printer routine with quick print; 1:1 or 2:1 dumps. Custom pad design and library.

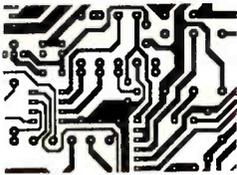

COMPONENT LAYOUT

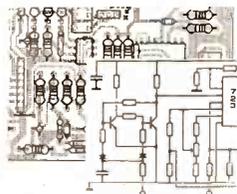Draw component layouts directly or from existing pcb layouts using a unique track reducing facility. The following components are provided: resistors, capacitors, ics, diodes, transistors, line drawing, printout and block commands as above.



CIRCUIT DIAGRAMS

Features similar to the above programs with a library of electronic symbols including resistors, capacitors, diodes, transistors, fets, op amp, switches, inductors, logic gates.

ABOVE LAYOUTS ACTUALLY PRODUCED ON THIS PACKAGE

Version now available for EE Centronics Interface - see Jan issue. State version required from: Disciple/+D; Discovery; +3; Microdrive & Tape. Important! Tape and Microdrive users please state Centronics interface in use.

An exceptional package which can be very highly recommended. Offers many of the features which would be expected of packages which cost ten times the price.

—EVERYDAY ELECTRONICS

KEMSOFT THE WOODLANDS, KEMPSEY, WORCESTER WR5 3NB. Tel. 0905 821088 after 6 p.m.

74HC series ICs

74HC00 19p	74HC02 19p	74HC03 19p
74HC04 19p	74HC08 19p	74HC10 19p
74HC11 26p	74HC14 39p	74HC20 19p
74HC27 31p	74HC30 35p	74HC74 39p
74HC86 29p	74HC107 36p	74HC138 41p
74HC161 48p	74HC175 52p	74HC393 69p

74LS series ICs

74LS00 20p	74LS02 20p	74LS05 20p
74LS30 20p	74LS32 20p	74LS51 20p
74LS90 30p	74LS93 30p	74LS107 23p
74LS112 23p	74LS138 35p	74LS139 35p
74LS151 38p	74LS164 38p	74LS193 55p
74LS245 58p	74LS374 52p	74LS375 64p

74F series ICs

74F00 32p	74F02 32p	74F64 32p
74F174 77p	74F251 64p	74F353 64p
74F373 91p	74F398 96p	74F399 96p

ECL series ICs

10101 1.15	10102 1.15	10103 1.15
10104 1.15	10124 3.68	10125 3.68

A wide range of components and TTL, CMOS and ECL ICs are available. We also supply PC, XT and AT spares at LOW PRICES. Write or phone for our FREE catalogue.

Resistors at bulk prices *Your Mix*
 Carbon film, 0.25W, 5% 1p each or 45p for 50
 Metal film, 0.25W, 1% 3p each or £1.35 for 50

VC sockets, solder type (pin:price)
 14:10p, 16:11p, 20:14p, 24(0.6 or 0.3):16p.

VC sockets with 0.1uF decoupler
 14:60p, 16:65p.

Prototyping boards (Vero)
 IBM XT £45.00, IBM AT £52.00

ACCESS welcome by post or phone. Callers by appointment please. VAT INCLUDED. Please add 50p for post and packing. Catalogue free. No minimum order charge.

BLACKMORE ELECTRONICS LTD.
 FREEPOST, Blandford Forum
 Dorset DT11 7BR

LOW PRICES!

☎ 0258 451347 (24hr answerphone)

NEW PRODUCT!

If YOU WANT A PC BUT CAN'T AFFORD ONE, or perhaps you want to upgrade yours but don't know how, send for our NEW book "PC-DIY" which explains all about how to build, upgrade and fault-find PC XT and AT computers at LOW COST. PC-DIY suits beginners and is a valuable reference for experts too! We feature all the parts you need, suggest sources of supply and give detailed descriptions of how to assemble a PC XT or AT to your specification. With PC-DIY it's easier than you might think!
 To Blackmore Electronics or phone out 24 hour hotline with your Access card details. Available only from us! Order today!

SPECIAL OFFER!

COMPUTER BITS

Special offer! Floppy drive cleaning kits only 2.70 postage included. (State 5 1/4 or 3 1/2). We also sell masters, pens, labels, binders, spares etc. etc.



DOWN TO EARTH

BY GEORGE HYLTON

SKIN EFFECT

AT THE instant when an electrical circuit is energised, does current begin to flow through the centres of the wires, or do the outside layers of the wire conduct first, or does the entire mass of metal in the wire carry current right from the start?

The question may seem purely academic. I have to admit that, when I first came across it, I was reminded of medieval theologians asking how many angels can dance on the point of a pin. However, the pioneer electrical engineers who asked it had good reason to want to know. They realised that it had a bearing on the behaviour of telegraph lines and cables.

The answer is that current starts to flow in the first outer layers of the wire. I can't remember who first produced convincing reasons for thinking so, and as I write this I'm far from home or libraries, but I have a feeling it may have been Heaviside.

Whoever it was, the consequences for the radio engineer are anything but academic. Because the current starts on the outside and works its way inwards, the resistance of the wire is not constant but increases with frequency.

The reason for this stems from the fact that when two conductors are parallel, a change in current in one of them tries to cause a current to flow in the other. If it can actually flow, this induced current is in the opposite direction to the primary current.

A solid wire can be thought of as made up of many smaller parallel wires. A change of current in any of these tends to create an opposing current in its neighbours. In Fig. 1, if A is the outermost layer of a conductor and carries a current in the direction shown, any change in current tries to force an opposing current through the next inner layer B. Switching on a current is itself a change, so the effect occurs even in d.c. circuits.

In time, the temporary opposition is overcome, and A and B conduct in the same direction. This combined current tries to produce a reverse flow in layer C. When this opposition dies away, layer D replaces C, and so on, layer by layer until, in the end, all layers conduct in the same way.

This process of filling up the wire with current is very rapid. But it is not instantaneous. It takes time to complete. In an a.c. circuit, the current keeps reversing. So there may not be time. Reversal may take place before the middle of a wire is fully conducting. The higher the frequency the less complete is the conduction. At extremely high frequencies current never penetrates deeper than the outermost layers, the "skin" of the wire. For this reason the behaviour is called skin effect.

SKIN DEPTH

If only the skin conducts, the rest of the wire may as well not be there. At high frequencies a hollow tube would be just as good as a solid wire. The effective resistance of the solid wire is the resistance of the tube, which is clearly higher than the d.c. resistance of the wire since there's less metal to act as a conductor. The high-frequency resistance of a wire is greater than the low-frequency resistance.


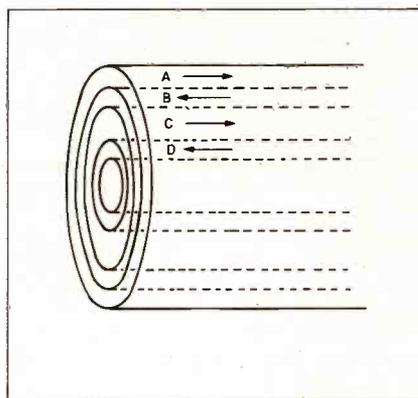


Fig. 1. Cross section through wire. When current starts to flow in A as shown an induced current tends to flow in the opposite direction in layer B, and so on.

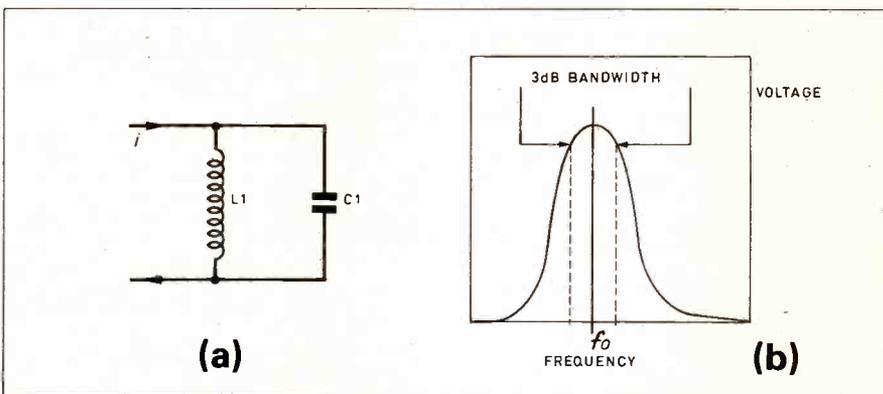

Of course, a solid wire isn't really made up of separate layers, so the skin effect is not clear-cut but blurred. High-frequency current doesn't just penetrate to a fixed depth beyond which no current flows at all. What happens in real life is that as you move from the outside towards the centre of a wire you encounter less and less high frequency current, though there's always some current, even right at the centre. When radio engineers talk of the "skin depth", they mean the depth at which the current has fallen to a particular

fraction of the outer current (actually to $1/e$ of the outer current where e is the same number as the base of natural logarithms).

REDUCING RESISTANCE

Skin effect is important to the design of inductors. In radio, the goodness of an inductor is often expressed as a quality factor or Q-factor for short. When the inductor is used in a parallel-tuned LC circuit (Fig. 2a) the selectivity is high when the Q-factor is high. The usual yardstick for selectivity is the 3dB bandwidth (Fig. 2b) that is the interval between the two frequencies where the response falls by 3dB (by about 30 per cent). Obviously, 3dB isn't much of a reduction, but it gives an easily computed figure. If the peak frequency is f_0 , then the 3dB bandwidth is f_0/Q . So if an LC circuit tuned to 450kHz has a Q of 45 then 3dB bandwidth is 10kHz.

Now, Q goes down as the h.f. resistance goes up. If one coil has a resistance of 1 ohm and another, otherwise identical coil has a resistance of 10

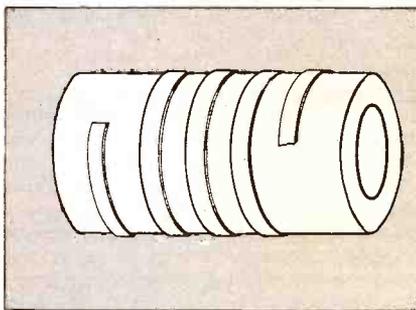


Fig. 3. Tape-wound inductor.

Fig. 2 (below). Parallel-tuned LC circuit (a). Frequency response (b). The bandwidth between points where the response has fallen by 3dB is f_0/Q .

ohms, the Q of the 1 ohm coil is 10 times the Q of the 10 ohm coil.

One way of fighting skin effect is to use, instead of one thick wire a number of thin wires in parallel, all insulated from one another. The insulation puts space between the small wires and allows each one to act on its own. This kind of stranded-insulated wire is called litz wire (from its German name, Litzendraht).

Parallel wires, even when insulated, are still not completely isolated from one another. They interact electromag-

netically like the layers of a solid wire. As the frequency is raised, the effect gets worse. This reduces the value of stranding and at really high frequencies solid wire is just as good.

Designers of h.f. inductors know that the current in one turn affects the current distribution in an adjacent turn, reducing the Q. Interaction can be reduced by spacing out the turns. However, more turns are then needed and the resulting increase in length of conductor itself gives increased resistance. There is a broad optimum spacing which gives the highest Q at a particular frequency.

Another strategy is to use flat tape instead of round wires (Fig. 3). This reduces resistance but also inductance, so it's only useful where a low inductance is sufficient.

SILVER-PLATE

A third ploy is to use a conductor material which has less resistance than the usual copper. The only useful material is silver, which is expensive. However, silver-plated conductors improve Q at extremely high frequencies where the skin depth is so low that even a very thin layer of high-conductivity material brings benefits.

Microwave components are often silver-plated.

You might think that the ultimate answer would be to wind coils using superconductive wire with no resistance at all. There are several snags. One is that at present all known superconductors must be kept very cold. Another is that the higher the conductivity the greater the skin effect.

In a superconductor, alternating currents are confined to a very thin surface layer. The current density in this layer is high, and the resulting high magnetic field strength may itself destroy the superconductivity.

MARKET PLACE

SWAP 210 components including transistors, cap's, resistors, for any multimeter working or not. Don't pay p & p. Trevor Page, 12 Ffordd Cadfan, Tywyn, Gwynedd LL36 9EE.

ELECTRONIC BUFF to design legal special purpose secure telecommunications recording type equipment. Will pay. T. Austin, Tel. 021 783 3385.

ZX81 SINCLAIR with power pack and two manuals. Working. Good condition. Price £12+£2 postage. Mr. Holdway, 20 Wherwell Road, Guildford, Surrey, GU2 5JR.

PAIR CODAN 7727 s.s.b. transceivers 6 channel h.f. 12V supply. Offers Mr. C. Meikle, 123B Pepsy Road, New Cross, S.E. 14. Tel: 01-732 8437.

WANTED instruction manual for Seiksha SP-1200 AI Printer — especially details of escape codes. Will pay photocopy/postage. C. Richardson, 18 Ounsdale Crescent, Wombourn, Wolverhampton, WV5 9HU. Tel. 0902 896162.

WANTED CB radio information; circuit diagram and anything else to do with CB and amateur radio equipment. K. Brandon, 28 Mendip Way, Sundon Park, Luton, Bedfordshire, LU3 3JL.

WANTED exchange service sheet Ekco car radio model CR948 for Radiomobile No. 320. Mr. J. A. Caldwell, 31 Neston Green, Gt. Sutton, Ellesmere Port, South Wirral, L66 3NY.

LASER TUBES brand new 2mW helium-neon with information. Only £50. Telephone weekends and evenings. 0332-515205.

WANTED user manual Heathkit transistor tester model IM36. E. H. Downer, 1 Twitten Way, Worthing BN14 7JU. Tel. 0903-206384

MICROPROCESSOR BUS analyser for 8 bit PCs. Tests for memory, I/O and track shorts, etc. £250. Tel. 0455-557143.

WANTED BUY circuit diagram Omega 9054 double cassette stereo audio recorder. Tel. 552-7045 after 6 p.m.

FLUKE digital meter £50. Small AVO £20. Clamp meter £15. Tel. 01-554-2913 6-8 p.m.

WANTED book Programming Programmable Calculators by Harold S. Engelsson. Condition and price to F. Hill, 061-973 3559.

WANTED CROTECH 3036 or 3031. Will pay up to £100. Must be in full working order. Mr. C. R. Day, 20 Sandford Way, Tuffley, Gloucester GL4 0TR.

MARCONI transistor tester TF.2703+book v.g.c. Offers, cash, cameras, clocks, shotguns — anything considered. Details reply interested. Mr. H. Cranford Evans, 120 Manchester Road, Southport, Lancashire PR9 9BH.

MICROTRANSMITTER ENTHUSIAST would like to hear from anybody who has bought Suma kits especially the VOX75. Contact Julian Cox Tel. 091-2851728.

CB CIRCUITS manual £5.00. Military circuits manual £8.50. Valve wireless servicing book £4.00. Post+packing £1.00. S. J. Austin, 8 Greenwood Avenue, Chinnor, Oxford OX9 4HN.

PIR INTRUDER DETECTOR, p.c.b. relays £1 each, d.p.t.d. key switches £1.50 each with data. Equip, not seconds. s.a.e. to D. Lintern, 290 Stanstead Road, Hoddesdon, Herts. EN11 0RX.

SPECTRA physics 262 argon laser with variable current supply and 2.2VA, TF multiline optics, good tube £1200. John Spang, 47 Carleton Road, Chorley, Lancs. DR6 8JQ. Phone 02572-75831.

OHIO SUPERBOARD computer, mint condition in metal case with integral power supply £25 buyer collects York. G. S. Houghton Tel. 0423 330620.

BACK ISSUES Everyday Electronics and other magazines for sale. s.a.e. lists. M. Small, 157, Hatchett Road, Bedford, Middlesex.

25M 50 core signal cable (RS cat) cost £35 offers? Also transformer 250/2500V ex laser p.s. £10. Martin, 0705-269485.

EVERYDAY ELECTRONICS unique collection 1975-1989 complete plus many earlier including issue one. Good condition. Sensible offers. David Griffin, 62 Buckshaft Road, Ruspidge, Cinderford, Glos. GL14 3AX. Tel. 0594-24109.

SPECTRUM +2 OWNER wishes to contact same with view to learning assembly language and machine code. P. Morris, 6, Burnell Street, Brimington, Chesterfield, Derbyshire S43 1HW. Tel. 0246-207765.

WANTED SCANNER with frequency read out. Phone Sheffield 326126.

FREE READERS ADS.

RULES Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Pen pals or items related to electronics only. No computer software. EE cannot accept responsibility for the accuracy of ads, or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut-out valid "date corner". Ads. will not appear (or be returned) if these rules are broken.

SMALL STROBOSCOPE 4 Joules frequency 2 to 20Hz. Fully cased £25. Tel. 061-494 1887.

URGENTLY WANTED information and/or chips by Curtis Electromusic Specialities. Especially CEM 3310, CEM 3320, CEM 3330, CEM 3340, Contact Mr. N. Gallacher, 23, Stratheden Park, By Cupar, Fife, Scotland KY15 5RP — (0334) 56507.

DESPERATELY WANTED valve amp theory books/circuits also o/t for single EL84 valve amp. Will pay. Richard Vernon, 319 Archway Road, Highgate, London N.6.

FOR SALE 4 channel 4 program lighting controller five available. Bargain £30 ea. more information on request. The Ultimate Roadshow, 8 Woodland Avenue, Congleton, Cheshire CW12 1LN.

WANTED intro board to go with the book Introducing Microelectronics by David Thompson. Stephen Lawrence, 4 Dale Park Rise, Leeds, LS16 7PP. Tel. Leeds (0532) 677423.

WANTED October 1988 to May 1989 editions of Everyday Electronics. Offers around £10. Mike Payne, 10 Lawns Park, Selsley Road, North Woodchester, Stroud, Glos GL5 5PP.

I AM LOOKING for pen pals interested in digital and analogue electronics. Reza, 180 Bushy Hill Drive, Merrow, Guildford, Surrey GU1 2UG. Tel. 574700.

GOULD switch mode power supply model EXT 90/12 2764 Eproms few logic chips. Phone after 11 a.m. Mr. J. Battersby, 4 Stork Cottages, off Pole Lane, Darwen, Lancashire BB3 3LQ. Tel. 0254 76127.

WANTED Repair manual for Sinclair ZX Spectrum also series on Spectrum repairs from T.V. Engineer trade magazine. Alister Stewart, 3 Fife Street, Banff, Scotland AB4 1JB.

AUDIO WATTMETER AW10 by Heath £15 o.n.o. Dawe Stroboscope model 1214 £25. D. K. R. Russell, 9 South Beach Road, Ardrossan, Ayrshire KA22 8AX. Tel. 0294 64144.

Name & Address:			

BLOCK CAPITALS PLEASE

Please read the **RULES** then write your advertisement here—one word to each box. Add your name, address and/or phone no. Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a **cut-out valid** date corner.

Signature Date

COUPON VALID FOR POSTING BEFORE 6 OCTOBER '89

(One month later for overseas readers)


SEND TO: EE MARKET PLACE, EVERYDAY ELECTRONICS, 6 CHURCH STREET, WIMBORNE, DORSET BH21 1JH.

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a **cut-out valid** "date corner"

DIRECT BOOK SERVICE

The books listed have been selected as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full details are given on the last book page.

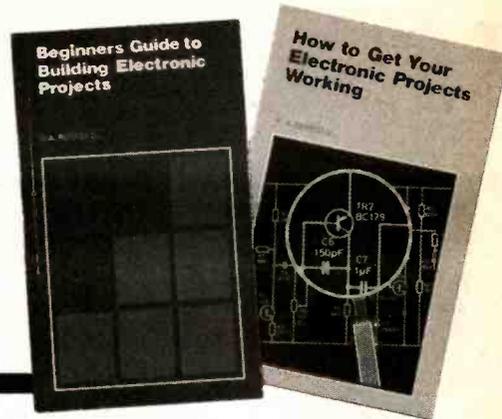For another selection of books see next month's issue.



MORE BOOKS NEXT MONTH—MORE BOOKS NEXT MONTH

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

96 pages Order code BP110 £2.50

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

Deals with the simple methods of copying printed circuit

board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.
80 pages Order code BP121 £2.50

BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also includes examples in the form of simple projects.

112 pages Order code No. 227 £2.25

ELECTRONIC SCIENCE PROJECTS

O. Bishop

These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained.

144 pages Order code BP104 £2.95

CIRCUITS & DESIGN

PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 1 PRACTICAL ELECTRONIC BUILDING BLOCKS—BOOK 2

R. A. Penfold

These books are designed to aid electronic enthusiasts who like to experiment with circuits and produce their own projects, rather than simply following published project designs.

BOOK 1 contains: Oscillators—sinewave, triangular, squarewave, sawtooth, and pulse waveform generators operating at audio frequencies. Timers—simple monostable circuits using i.c.s, the 555 and 7555 devices, etc. Miscellaneous—noise generators, rectifiers, comparators and triggers, etc.

BOOK 2 contains: Amplifiers—low level discrete and op-amp circuits, voltage and buffer amplifiers including d.c. types. Also low-noise audio and voltage controlled amplifiers. Filters—high-pass, low-pass, 6, 12, and 24dB per octave types. Miscellaneous—i.c. power amplifiers, mixers, voltage and current regulators, etc.

BOOK 1 128 pages Order code BP117 £1.95
BOOK 2 112 pages Order code BP118 £1.95

ELECTRONIC ALARM CIRCUITS MANUAL

R. M. Marston

One hundred and forty useful alarm circuits, of a variety of types, are shown in this volume. The operating principle of each one is explained in concise but comprehensive terms, and brief construction notes are given where necessary.

Aimed at the practical design engineer, technician and experimenter, as well as the electronics student and amateur.

124 pages Order code NE11 £9.95

DESIGNING DC POWER SUPPLIES

G. C. Loveday C.Eng MIERE

Covers all aspects of the design of regulated power units, using discretes, i.c. regulators and switched units. It also covers protection circuits and reference supplies. Many design examples and exercises all with fully worked solutions are given.

131 pages Order code BM2 £6.95

MODERN OPTO DEVICE PROJECTS

R.A. Penfold

In recent years, the range of opto devices available to the home constructor has expanded and changed radically. These devices now represent one of the more interesting areas of modern electronics for the hobbyist to experiment in, and many of these devices have useful practical applications as well. This book provides a number of practical designs which utilize a range of modern opto-electric devices, including such things as fibre optics, ultra bright l.e.d.s and passive IR detectors etc. While many of these designs are not in the "dead simple" category, they should be within the capabilities of anyone with a reasonable amount of experience in electronics construction and some of the more simple designs are suitable for beginners.

104 pages Order code BP194 £2.95

DIGITAL LOGIC GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning. This is not a constructor's book in the sense of presenting circuits to build and use, it is for the user who wants to design and troubleshoot digital circuitry with considerably more understanding of principles.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages Order code PC106 £8.95

HOW TO USE OP-AMPS

E. A. Parr

This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

160 pages Order code BP88 £2.95

MICRO INTERFACING CIRCUITS—BOOK 1 MICRO INTERFACING CIRCUITS—BOOK 2

R. A. Penfold

Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but p.c.b. layouts and other detailed constructional information are not included.

Book 1 is mainly concerned with getting signals in and out of the computer; Book 2 deals primarily with circuits for practical applications.

Book 1 112 pages Order code BP130 £2.25
Book 2 112 pages Order code BP131 £2.75

SENSORS AND TRANSDUCERS

Keith Brindley

There are a considerable number of transducers. Look through any electronic components catalogue and you'll find a wide variety of types, and each type has many versions. It's not easy to choose a transducer correctly for a particular function. In many specifications, terms and procedures are referred to which might deter you from using one that is, in fact, the best for the job. Yet, opting to use a transducer merely because it is easier to interface into the measuring system is not the answer. A greater knowledge of all types of transducers capable of doing the task is the ideal, and only then can a totally satisfactory decision be made to use one in particular.

176 pages Order code NE17 £12.95

ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

Robert Penfold

Robots and robotics offer one of the most interesting areas for the electronics hobbyist to experiment in. Today the mechanical side of robots is not too difficult, as there are robotics kits and a wide range of mechanical components available. The micro controller is not too much of a problem either, since the software need not be terribly complex and many inexpensive home computers are well suited to the task.

The main stumbling block for most would-be robot builders is the electronics to interface the computer to the motors, and the sensors which provide feedback from the robot to the computer. The purpose of this book is to explain and provide some relatively simple electronic circuits which bridge this gap.

92 pages Order code BP179 £2.95

50 SIMPLE LED CIRCUITS

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components—the light-emitting diode (LED). Also includes circuits for the 707 common anode display.


64 pages Order code BP42 £1.95
BOOK 2 50 more l.e.d. circuits Order code BP87 £1.35

ELECTRONICS SIMPLIFIED—CRYSTAL SET CONSTRUCTION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Especially written for those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day one can read intelligently and handle simple tools.

80 pages Order Code BP92 £1.75

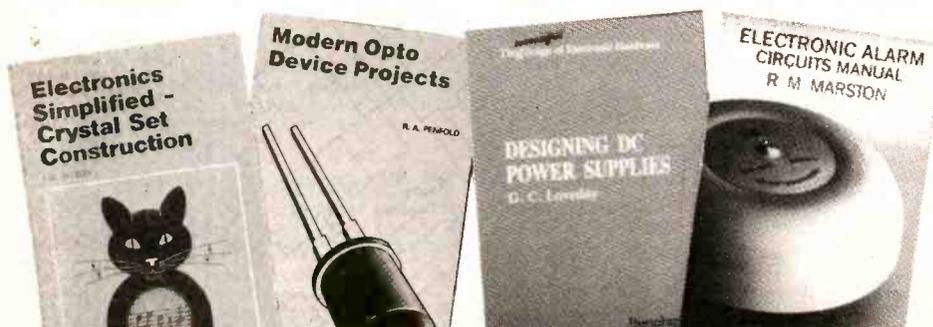



RECOMMENDED READING

FOR INTRODUCING DIGITAL ELECTRONICS

ELECTRONICS—A "MADE SIMPLE" BOOK
G. H. Olsen
 This book provides excellent background reading for our *Introducing Digital Electronics* series and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity.
 330 pages Order code NE10 £4.95

ELECTRONIC HOBBYISTS HANDBOOK
R. A. Penfold
 Provides an inexpensive single source of easily located information that the amateur electronics enthusiast is likely to need for the day-to-day pursuance of this fascinating hobby. Covers common component colour codes. Details the characteristics and pinouts of many popular semiconductor devices, including various types of logic ICs, operational amplifiers, transistors, FETs, unijunctions, diodes, rectifiers, SCRs, diacs, triacs, regulators and SMDS, etc. Illustrates many useful types of circuits, such as timers and oscillators, audio amplifiers and filters, as well as including a separate section on power supplies. Also contains a multitude of other useful data.
 88 pages Order code BP233 £4.95

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST
G. T. Rubaroe, T. Eng (C.E.I.), Assoc. I.E.R.E.
 The object of this book is to supply the hobbyist with a background knowledge tailored to meet his or her specific requirements and the author has brought together the relevant material and presented it in a readable manner with minimum recourse to mathematics.
 128 pages Order Code 228 £2.50

PRACTICAL DIGITAL ELECTRONICS HANDBOOK
Mike Tooley (Published in association with Everyday Electronics)
 The vast majority of modern electronic systems rely heavily on the application of digital electronics, and the *Practical Digital Electronics Handbook* aims to provide readers with a practically based introduction to this subject. The book will prove invaluable to anyone involved with the design, manufacture or servicing of digital circuitry, as well as to those wishing to update their knowledge of modern digital devices and techniques. Contents: Introduction to integrated circuits; basic logic gates; monostable and bistable devices; timers; microprocessors; memories; input and output devices; interfaces; microprocessor buses. Appendix 1: Data. Appendix 2: Digital test gear projects; tools and test equipment; regulated bench power supply; logic probe; logic pulser; versatile pulse generator; digital IC tester; current tracer; audio logic tracer; RS-232C breakout box; versatile digital counter/frequency meter. Appendix 3: The oscilloscope. Appendix 4: Suggested reading. Appendix 5: Further study.
 208 pages Order code PC100 £6.95


ELECTRONICS TEACH-IN
Michael Tooley BA and David Whitfield MA MSc
CEng MSEE (published by Everyday Electronics)
 This value for money *EE* book provides a comprehensive background to modern electronics including test gear projects. A complete course in basic electronics; designed for the complete newcomer it will however also be of value to those with some previous experience of electronics. Wherever possible the course is related to "real life" working circuits and each part includes a set of detailed practical assignments. Includes details of eight items of related test gear giving full constructional information and diagrams for each one. They are: Safe Power Supply; Universal LCR Bridge; Diode/Transistor Tester; Audio Signal Tracer; Audio Signal Generator; RF Signal Generator; FET Voltmeter; Pulse Generator. An excellent companion for anyone interested in electronics and invaluable for those taking G.C.S.E. and BTEC electronics courses.
 104 pages (A4 size) Order code EE/T-1 £1.95

FROM ATOMS TO AMPERES
F. A. Wilson
 Explains in crystal clear terms the absolute fundamentals behind electricity and electronics. Really helps you to discover and understand the subject, perhaps for the first time ever. Have you ever: Wondered about the true link between electricity and magnetism? Felt you could never understand the work of Einstein, Newton, Boltzmann, Planck and other early scientists? Just accepted that an electron is like a little black ball? Got mixed up with e.m.f. and p.d.? Thought the idea of holes in semiconductors is a bit much? Then help is at hand with this inexpensive book, in as simple a way as possible and without too much complex mathematics and formulae.
 244 pages Order code BP254 £3.50

BEGINNERS GUIDE TO MICROPROCESSORS
E. A. Parr
 An excellent grounding in microprocessors, this book is broadly relevant to the whole of our *Introducing Microprocessors* course. It is easy to read and well illustrated.
 224 pages Order code NE03 £5.95

ELECTRONICS TEACH-IN 88/89—INTRODUCING MICROPROCESSORS
Mike Tooley BA (published by Everyday Electronics)
 A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.
 80 pages (A4 size) Order code TI-88/89 £2.45

NEWNES ELECTRONICS POCKET BOOK
E. A. Parr
 Newnes Electronics Pocket Book has been in print for over twenty years and has covered the development of electronics from valve to semiconductor technology and from transistors to LSI integrated circuits and microprocessors. To keep up to date with the rapidly changing world of electronics, continuous revision has been necessary. This new Fifth Edition takes account of recent changes and includes material suggested by readers of previous editions. New descriptions of op. amp. applications and the design of digital circuits have been added, along with a totally new chapter on computing, plus other revisions throughout.
 315 pages (hard cover) Order Code NE02 £9.95

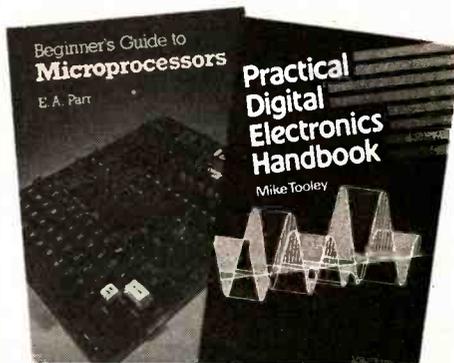

COMPUTING

NEWNES COMPUTER ENGINEER'S POCKETBOOK
Michael Tooley
 An invaluable compendium of facts, figures, circuits and data, indispensable to the designer, student, service engineer and all those interested in computer and microcomputer systems. It will appeal equally to the hardware or software specialist and to the new band of "software engineers". This first edition covers a vast range of subjects at a practical level, with the necessary explanatory text. The data is presented in a succinct and rapidly accessible form so that the book can become part of an everyday toolkit.
 205 pages (hard cover) Order code NE01 £8.95

GETTING THE MOST FROM YOUR PRINTER
J. W. Penfold
 Details how to use all the features provided on most dot-matrix printers from programs and popular word processor packages like Wordwise, Visawrite and Quill, etc. Shows exactly what must be typed in to achieve a given effect.
 96 pages Order Code BP181 £2.95

AN INTRODUCTION TO Z80 MACHINE CODE
R. A. & J. W. Penfold
 Takes the reader through the basics of microprocessors and machine code programming with no previous knowledge of these being assumed. The Z80 is used in many popular home computers and simple programming examples are given for Z80-based machines including the Sinclair ZX-81 and Spectrum, Memotech and the Amstrad CPC 464. Also applicable to the Amstrad CPC 664 and 6128.
 144 pages Order code BP152 £2.75

AN INTRODUCTION TO PROGRAMMING THE ACORN ELECTRON
R. A. & J. W. Penfold
 Designed to help the reader learn more about programming and to make best use of the Electron's many features. Adds considerably to the information already supplied in the manufacturer's own instruction manual.
 144 pages Order code BP142 £1.95

AN INTRODUCTION TO PROGRAMMING THE ATARI 600/800 XL
R. A. & J. W. Penfold
 Especially written to supplement the manufacturer's own handbook. The information supplied will help the reader to master BASIC programming and to make best use of the Atari's many powerful features.
 128 pages Order code BP143 £1.95

AN INTRODUCTION TO PROGRAMMING THE SINCLAIR QL
R. A. & J. W. Penfold
 Helps the reader to make best use of the fantastic Sinclair QL's almost unlimited range of features. Designed to complement the manufacturer's handbook.
 112 pages Order code BP150 £1.95

A Z80 WORKSHOP MANUAL
E. A. Parr, B.Sc., C.Eng., M.I.E.E.
 This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z80 based computer.
 192 pages Order Code BP112 £3.50

A CONCISE INTRODUCTION TO MS-DOS
N. Kantaris
 This guide is written with the non-expert, busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the guide is also designed to be circular, which means that you don't have to start at the beginning and go to the end. The more experienced user can start from any section. The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and other manufacturers of "compatible" microcomputers, including the AMSTRAD PC's. It covers both floppy disc-based systems and hard disc-based systems.
 64 pages Order code BP232 £2.95

AN INTRODUCTION TO 68000 ASSEMBLY LANGUAGE
R. A. & J. W. Penfold
 Obtain a vast increase in running speed by writing programs for 68000 based micros such as the Commodore Amiga, Atari ST range or Apple Macintosh range etc., in assembly language. It is not as difficult as one might think and this book covers the fundamentals.
 112 pages Order code BP184 £2.95

THE ART OF PROGRAMMING THE ZX SPECTRUM
M. James, B.Sc., M.B.C.S.
 It is one thing to have learnt how to use all the Spectrum's commands and functions, but a very different one to be able to combine them into programs that do exactly what you want them to. This is just what this book is all about—teaching you the art of effective programming with your Spectrum.
 144 pages Order code BP119 £2.50

BEGINNER'S GUIDE TO HI-FI

Ian Sinclair
The *Beginner's Guide to Hi-Fi* will appeal to the audio enthusiast, whether newly won over by advances in technology or well established and wondering whether to update equipment. The book deals with the sound from its sources in the studio to its ultimate end in your ears, and shows what sound is, how it is recorded and how it is reproduced.
Every aspect of Hi-Fi, from pickup cartridges to loudspeakers, has been covered, and the emphasis has been on explaining design aims. Cassette systems have been given considerable prominence, including the more modern Dolby C and dbx noise reduction systems. The CD record has been covered in detail so that you can find out just why this system of sound reproduction is so superior.
194 pages Temporarily out of print.

DATA & COMPONENT IDENTIFICATION

HOW TO IDENTIFY UNMARKED ICs

K. H. Recorr
Shows the reader how, with just a test-meter, to go about recording the particular signature of an unmarked i.c. which should enable the i.c. to then be identified with reference to manufacturers' or other data. An i.c. signature is a specially plotted chart produced by measuring the resistances between all terminal pairs of an i.c.
Chart Order code BP101 £0.95

INTERNATIONAL DIODE EQUIVALENTS GUIDE


A. Michaels
Designed to help the user in finding possible substitutes for a large selection of the many different types of diodes that are available. Besides simple rectifier diodes, also included are Zener diodes, i.e.d.s, diacs, triacs, thyristors, OCIs, photo and display diodes.
144 pages Order code BP108 £2.25

LINEAR IC EQUIVALENTS AND PIN CONNECTIONS

A. Michaels
Shows equivalents and pin connections of a popular selection of European, American and Japanese linear i.c.s. Also includes details of functions, manufacturer and country of origin.
320 pages Temporarily out of print

RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

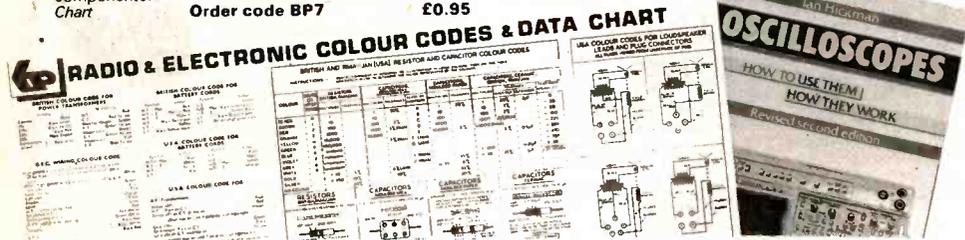B. B. Babani
Although this chart was first published in 1971 it provides basic information on many colour codes in use throughout the world, for most radio and electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers, etc. It is particularly useful for finding the values of old components.
Chart Order code BP7 £0.95



RADIO, TV, SATELLITE

INTERNATIONAL RADIO STATIONS GUIDE

P. Shore
Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around the ever more complex radio bands. This new edition has been completely revised and rewritten and incorporates much more information which is divided into the following sections:
Listening to Short Wave Radio; ITU Country Codes; World-wide Short Wave Radio Stations; European, Middle East and North African Long Wave Radio Stations; European, Near East and North African Medium Wave Radio Stations; Canadian Medium Wave Radio Stations; USA Medium Wave Radio Stations; Broadcasts in English; Programmes for DXers and Short Wave Listeners; UK FM Radio Stations; Time differences from GMT; Abbreviations; Wavelength/Frequency Conversion.
320 pages Order code BP255 £4.95

AERIAL PROJECTS

R. A. Penfold
The subject of aerials is vast but in this book the author has considered practical aerial designs, including active, loop and ferrite aerials which give good performances and are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.
Also included are constructional details of a number of aerial accessories including a pre-selector, attenuator, filters and tuning unit.
96 pages Order code BP105 £2.50

AN INTRODUCTION TO LOUDSPEAKERS AND ENCLOSURE DESIGN

V. Capel
This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally, there is a step-by-step description of the construction of the *Kapellmeister* loudspeaker enclosure.
148 pages Order Code BP256 £2.95

MUSICAL APPLICATIONS OF THE ATARI ST's

R. A. Penfold
The Atari ST's are now firmly established as the computers to use for electronic music applications. The range and sophistication of these applications are much greater than most people may realise, but there are still a lot of misconceptions about just what can and cannot be achieved. This book will help you sort out the fact from the fallacy and to get the most musically from the ST's.
A wide selection of topics are covered, including the internal sound chip; MIDI; applications programs such as sequencing and score writing, etc; simple but useful add-on projects and MIDI programming.
90 pages Order code BP246 £5.95

TESTING & TEST GEAR

TRANSISTOR RADIO FAULT-FINDING CHART

C. E. Miller
Used properly, should enable the reader to trace most common faults reasonably quickly. Across the top of the chart will be found four rectangles containing brief description of these faults, viz—sound weak but undistorted, set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.
Chart Order code BP70 £0.95

OSCILLOSCOPES: HOW TO USE THEM—HOW THEY WORK

Ian Hickman
Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models is available. But which is the right 'scope for a particular application? Which features are essential, which not so important? What techniques will get the best out of the instrument?
Ian Hickman, experienced in both professional and hobbyist electronics, has revised this well-established book to help all oscilloscope users—and potential users.
133 pages Order code NE09 £6.95

AN INTRODUCTION TO SATELLITE TELEVISION

F.A. Wilson
As a definitive introduction to the subject this book is presented on two levels. For the absolute beginner or anyone thinking about purchasing or hiring a satellite TV system, the story is told as simply as such a complex one can be in the main text.
For the professional engineer, electronics enthusiast, student or others with technical backgrounds, there are numerous appendices backing up the main text with additional technical and scientific detail formulae, calculations, tables etc.
There is also plenty for the DIY enthusiast with practical advice on choosing and installing the most problematic part of the system—the dish antenna.
104 pages Order Code BP195 £5.95

COMMUNICATION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.
A look at the electronic fundamentals over the whole of the communication scene. This book aims to teach the important elements of each branch of the subject in a style as interesting and practical as possible. While not getting involved in the more complicated theory and mathematics, most of the modern transmission system techniques are examined including line, microwave, submarine, satellite and digital multiplex systems, radio and telegraphy. To assist in understanding these more thoroughly, chapters on signal processing, the electromagnetic wave, networks and transmissions assessment are included, finally a short chapter on optical transmission.
256 pages Order Code BP89 £2.95

PRACTICAL MIDI HANDBOOK

R.A. Penfold
The Musical Instrument Digital Interface (MIDI) is surrounded by a great deal of misunderstanding, and many of the user manuals that accompany MIDI equipment are quite incomprehensible to the reader.
The Practical MIDI Handbook is aimed primarily at musicians, enthusiasts and technicians who want to exploit the vast capabilities of MIDI, but who have no previous knowledge of electronics or computing. The majority of the book is devoted to an explanation of what MIDI can do and how to exploit it to the full, with practical advice on connecting up a MIDI system and getting it to work, as well as deciphering the technical information in those equipment manuals.
128 pages Order code PC101 £5.95

MORE BOOKS NEXT MONTH

DIRECT BOOK SERVICE

(A Division of Wimborne Publishing Ltd.)

TO ORDER

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.00 for all countries outside Europe, surface mail postage) and send a PO, cheque or international money order (£ sterling only) made payable to **Direct Book Service** quoting your name and address, the order code and quantities required to **DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET, BH21 1RW** (mail order only).

See next month's issue for another three page selection of books.

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of *Everyday Electronics*) before ordering from old lists.

Note—our postage charge is the same for one book or one hundred books!

MORE BOOKS NEXT MONTH

POWER CONDITIONER

FEATURED IN ETI
JANUARY 1988

The ultimate mains purifier. Intended mainly for lowering the noise floor and improving the analytical qualities of top-light audio equipment.


The massive filter section contains thirteen capacitors and two current balanced inductors. Together with a bank of six VDRs, to remove every last trace of impulsive and RF interference. A ten LED logarithmic display gives a second by second indication of the amount of interference removed.

Our approved parts set consists of case, PCB, all components (including high permeability toroidal cores, ICs, transistors, class X and Y suppression capacitors, VDRs, etc.) and full instructions.

PARTS SET £29.80 + VAT

A low cost (but high performance) mains conditioner is also available.

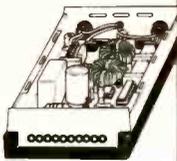MAINS CONDITIONER PARTS SET £5.40 + VAT
RUGGED PLASTIC CASE £1.80 + VAT



KNIGHT RAIDER

FEATURED IN ETI JULY 1987

The ultimate in lighting effects for your Lamborghini, Maserati, BMW (or any other car, for that matter). Picture this: eight powerful lights in line along the front and eight along the rear. You flick a switch on the dashboard control box and a point of light moves lazily from left to right leaving a comet's tail behind it. Flip the switch again and the point of light becomes a bar, bouncing backwards and forwards along the row. Press again and try one of the other six patterns... An LED display on the control box let's you see what the main lights are doing.

The Knight Raider can be fitted to any car (it makes an excellent fog light) or with low powered bulbs it can turn any child's pedal car or bicycle into a spectacular TV-age toy!

The parts set consists of box, PCB and components for control, PCB and components for sequence board, and full instructions.

Lamps not included.

PARTS SET £24.80 + VAT

THE MISTRAL AIR IONISER

The best ioniser design yet - this one has variable ion drive, built-in ion counter and enough power to drive five multi-point emitters. For the technically minded, it has nine main drive stages, five secondary drives, and a four section booster to give an output capability of almost fifteen billion (1.47×10^{10}) ions every minute, or 2.45×10^{11} ions per second. With extra emitters this can be increased still further!

PARTS SET £28.40 + VAT

The parts set includes case, printed circuit boards, 126 top grade components, all controls, lamps, hardware, a multi-point phosphor-bronze emitter and full instructions.

Some parts are available separately - please send SAE for lists, or SAE + £1 for lists, circuit and construction details and further information (free with parts set).

READY-BUILT MISTRAL

The Mistral Ioniser (and most of our other projects) can now be supplied built, tested and ready to go. For details, please contact Peter Leah at P.L. Electronics, 8 Woburn Road, Eastville, Bristol BS5 6TT. Tel: 0272 522703. Evenings Only

INTERNAL EMITTER £2.80 + VAT

Can be used in place of the P-B external emitter, or both can be used together for the highest ion output. Parts set includes PCB, ion emitters, components and instructions.

THE DREAM MACHINE

FEATURED IN ETI
DECEMBER 1987

Adjust the controls to suit your mood and let the gentle, relaxing sound drift over you. At first you might hear soft rain, sea surf, or the wind through distant trees. Almost hypnotic, the sound draws you irresistibly into a peaceful, refreshing sleep.

For many, the thought of waking refreshed and alert from perhaps the first truly restful sleep in years is exciting enough in itself. For more adventurous souls there are strange and mysterious dream experiences waiting. Take lucid dreams, for instance. Imagine being in control of your dreams and able to change them at will to act out your wishes and fantasies. With the Dream Machine it's easy!

The approved parts set consists of PCB, all components, controls, loudspeaker, knobs, lamp, fuseholders, fuse, mains power supply, prestige case and full instructions.

PARTS SET £19.80 + VAT

Ben Sweetland's best seller GROW RICH WHILE YOU SLEEP is now in stock.

£2.95 (NO VAT)

TV BOOSTER

Good TV pictures from poor aerials is what this project is all about. Keith Brindley's Aerial Booster gives a massive 23dB gain to ensure good viewing for campers and caravaners, from indoor aerials, or wherever a properly positioned high-gain antenna is not practical.


Based on the OM335 hybrid amplifier, the booster has specifications to rival the best: wideband operation from 10MHz to 1.4 GHz, mid-band gain of up to 26dB and a wide supply range of 9V to 26V (it will run from car batteries for caravaners, dry batteries for campers, or a mains 'battery eliminator' in the home). No special UHF construction skills are needed - the project could be made by a careful beginner.

There are two parts sets for the project. AA1 contains the printed circuit board, OM335 hybrid amplifier, components and instructions. AA2 is the optional case set, rugged screened box, front and rear panels, waterproofing gaskets, feet, sockets and hardware.

AA1 PARTS SET £12.80 + VAT

AA2 PARTS SET £4.80 + VAT

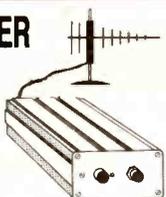AA3 OPTIONAL MAINS POWER SUPPLY PARTS SET £6.80 + VAT.



POWERFUL AIR IONISER

FEATURED IN ETI
JULY 1986

Ions have been described as vitamins of the air by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products. It was reliable, good to build... and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller tinned printed circuit board, 66 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs 'about a third of the price of the individual components. What more can we say?'

PARTS SET WITH BLACK CASE £12.60 + VAT

PARTS SET WITH WHITE CASE £12.80 + VAT



BURGLAR BUSTER

Be safe from intruders with our Burglar Buster alarm system! It has all the features you'd expect from a high-tech alarm: entry and exit delay, anti-tamper loop, delay warning and control-box protection.

The parts set includes all four PCBs and all components to go on them. Other parts (case, switches, etc.) are available separately, if you haven't got anything suitable in your spares box. Set contains 4 PCBs, ICs, transistors, relays, capacitors, resistors, diodes, regulator, piezo sounder and full instructions.

BB1 PARTS SET £12.80 + VAT

RAINY DAY PROJECTS



All can be built in an afternoon!

JUMPIN' JACK FLASH (ETI March 1988)

Spectacular rock, stage and disco lighting effect! £6.90 + VAT

CREDIT CARD CASINO (ETI March 1987)

The wicked pocket gambling machine £5.90 + VAT

MAINS CONTROLLER (ETI January 1987)

Isolated logic to mains interface £6.20 + VAT

MATCHBOX AMPLIFIERS (ETI April 1986)

Listen 50W of Hi-Fi power from an amp small enough to fit in a matchbox

Matchbox Amplifier (20W) £6.50 + VAT

Matchbox Bridge Amplifier (50W) £8.90 + VAT

L165V Power Amplifier IC, with data and circuits £3.90 + VAT

TACHO/DWELL METER (ETI January 1987)

Turn your Metro into a Porsche! £16.40 + VAT

HI-FI POWER METER (ETI May 1987)

Measures Hi-Fi output power up to 100W - includes PCB, components, meters

Mono power meter £3.90 + VAT

Stereo power meter £7.20 + VAT

ION DISPERSION METER

FEATURED IN ETI
FEBRUARY 1989

The Q-ion is a hand-held meter which emits out ions in the air. It can tell the good ones from the duds if you're thinking of buying a commercial ioniser, check the efficiency and output of one you've made yourself, help you set up and position the ioniser for best effect, do an ion-survey of your house or office - in short, it will tell you anything you want to know about ions in the air.

In direct mode the bar-graph readout will detect the presence of negative or positive ions and measure neg-ion strengths from 5×10^7 to 10^{10} ions per second, which covers the levels you can expect when an air ioniser is in use. For the smaller concentrations of natural air ions, integrator mode will increase the sensitivity as far as you like.

Our approved parts set comprises: case, ion collector, printed circuit board, all components (including six ICs, Schottky diode, varactor, VDR, zener, 37 resistors and capacitors, LEDs, plug, socket, earth lead, etc.) and full instructions.

PARTS SET £18.40 + VAT

Some parts are available separately - please send SAE for lists, or SAE + £1 for lists, circuit, construction details and further information (free with parts set).



BIO-FEEDBACK

FEATURED IN ETI
DECEMBER 1986

Bio-feedback comes of age with this highly responsive, self-balancing skin response monitor! The powerful circuit has found application in clinical situations as well as on the bio-feedback scene. It will open your eyes to what GSR techniques are really all about. The complete parts set includes case, PCB, all components, leads, electrodes, conductive gel, and full instructions.

PARTS SET £16.80 + VAT

BIO-FEEDBACK BOOK £4.50 (no VAT)

Please note: the book, by Stern and Ray, is an authorised guide to the potential of bio-feedback techniques. It is not a hobby book, and will only be of interest to intelligent adults.



LEDs

Green rectangular LEDs for bar-graph displays.


50 for £3.50 500 for £25

100 for £6 1000 for £45

DIGITAL AND AUDIO EQUIPMENT LEDs

Assorted 3mm LEDs: red, green, yellow and orange.

25 of each (100 LEDs) for £6.80

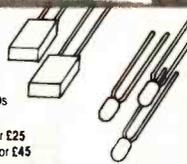

U.K. orders: please add 80p post and packing and 15% VAT to total.

Eire and overseas: no VAT. Carriage and insurance £4.50.

Please allow up to 14 days for delivery.

BRAINWAVE MONITOR

FEATURED IN ETI
AUGUST 1987

The most astonishing project ever to have appeared in an electronics magazine. Similar in principle to a medical EEG machine, this project allows you to hear the characteristic rhythms of your own mind! The alpha, beta and theta forms can be selected for study and the three articles give masses of information on their interpretation and powers.

In conjunction with Dr. Lewis's Alpha Plan, the monitor can be used to overcome shyness, to help you feel confident in stressful situations, and to train yourself to excel at things you're 'no good at'.

Our approved parts set contains case, two PCBs, screening can for bio-amplifier, all components (including three PIM precision amplifiers), leads, brass electrodes and full instructions.

PARTS SET £39.80 + VAT ALPHA PLAN BOOK £2.50

SILVER SOLUTION (for pairing electrodes) £3.80 + VAT

Parts set available separately. We also have a range of accessories: professional electrodes, books, etc. Please send SAE for lists, or SAE + £2 for lists, construction details and further information (free with parts set).



Specialist
SEMICONDUCTORS
LIMITED
Tel: (0600) 3715
SALES DEPT., ROOM 111, FOUNDERS HOUSE, REDBROOK, MONMOUTH, GWENT.

PCB SERVICE

Printed circuit boards for certain constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to **The PCB Service Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH.** Cheques should be crossed and made payable to **Everday Electronics (Payment in £ sterling only).**

Boards for some older projects - not listed here - can often be obtained from Magenta Electronics, 135 Hunter St., Burton-on-Trent, Staffs DE14 2ST. Tel: 0283 65435 or Lake Electronics, 7 Middleton Close, Nuthall, Nottingham NG16 1BX. Tel: 0602 382509.

NOTE: While 90% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail. Please check price and availability in the latest issue before ordering. We can only supply boards listed in the latest issue. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
200MHz Digital Frequency Meter NOV '86	548	£5.14
Automatic Car Alarm DEC '86	549	£3.00
BBC 16K Sideways RAM (Software Cassette)	551 551S	£3.00 £3.88
Mini Amp FEB '87	554 & 555	£5.68
Video Guard	556	£3.80
Spectrum I/O	557	£5.35
Spectrum Speech Synthesiser	558	£4.86
Computer Buffer/Interface MAR '87	560	£3.32
Infra-Red Alarm: Sensor Head	561	£4.19
PSU/Relay Driver	562	£4.50
Experimental Speech Recognition APR '87	563	£4.75
Bulb Life Extender	564	£3.00
Fridge Alarm MAY '87	565	£3.00
EE Equaliser-Ioniser	566	£4.10
Mini Disco Light JUNE '87	567	£3.00
Visual Guitar/Instrument Tuner	568	£3.97
Fermostat JULY '87	569	£3.34
EE Buccaneer Metal Detector	570	£4.10
Monomix	571	£4.75
Super Sound Adaptor Main Board AUG '87	572	£4.21
PSU Board	573	£3.32
Simple Shortwave Radio, Tuner & Amplifier	575/576	£4.90
Noise Gate SEPT '87	577	£4.41
Burst Fire Mains Controller	578	£3.31
Electronic Analogue/Digital Multimeter	579	£6.40
Transtest OCT '87	580	£3.32
Video Controller	581	£4.83
Accented Metronome NOV '87	582	£3.77
Acoustic Probe	584	£3.00
BBC Sideways RAM/ROM	585	£4.10
Pseudo Echo Unit DEC '87	586	£4.60
Dual Mains Light Flasher	587	£3.66
Twinkling Star	588	£3.00
Audio Sine Wave Generator	589	£3.03
Capacitance Meter JAN '88	590	£4.10
Bench Amplifier	591	£5.51
Transistor Curve Tracer	592	£3.00
Bench Power Supply Unit FEB '88	593	£4.01
Game Timer	583	£3.55
Semiconductor Tester MAR '88	594	£3.19
SOS Alert	595	£3.00
Guitar/Keyboard Envelope Shaper	596	£4.23
Stereo Noise Gate APR '88	597	£6.65
Pipe & Cable Locator	598	£3.00
Inductive Proximity Detector	574	£3.00
Multi-Chan Remote Light Dim MAY '88	599	£3.00
Transmitter	600	£3.07
Receiver	605	£3.00
Door Sentinel	606	£5.91
Function Generator - Main Board	607	£4.19
Function Generator - Power Supply	608	£4.78
Super Sound Effects Generator	608	£4.78

Multi-Chan Remote Light Dim JUNE '88	601	£4.86
Relay/Decoder	602	£3.07
Dimmer Board	603	£3.00
Power Supply	604	£7.76
Mother Board	611	£3.00
Headlight Reminder	612	£6.75
Video Wiper JULY '88	613	£4.21
Isolink		
Tea Tune AUG '88	609	£3.00
Time Switch	614	£4.84
Suntan Timer	610	£3.07
Car Alarm	615	£3.12
Breaking Glass Alarm SEPT '88	617	£4.27
Amstrad PIO	618	£6.77
Eprom Eraser OCT '88	620	£4.07
Doorbell Delay NOV '88	616	£3.56
Micro Alarm	621	£3.12
Infra-Red Object Counter Trans Receiver Display } £9.28 as a set	622 623 624	£4.61 £3.23 £3.05
Seashell Sea Synthesiser	625	£4.84
Reaction Timer Main Board DEC '88	626	£3.46
Display Board	627	£3.00
Downbeat Metronome	629	£4.84
EPROM Programmer (On Spec)	630	£8.29
Phasor	631	£5.64
Monkey/Hunter Game JAN '89	634	£3.36
Continuity Tester FEB '89	619	£2.67
4-Channel Light Dimmer	635	£7.67
Mini PSU	636	£3.23
Sound-to-Light Interface MAR '89	637	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel APR '89		
Main Control Board	632	£9.20
Remote Interface (4 boards)	633	£4.59
Electron User Port	638	£6.64
4-Channel Auto-Fader Interface	642	£6.80
Pet Scarer MAY '89	644	£3.00
Electron A/D Interface	645	£4.84
Spectrum EPROM Programmer JUNE '89	628	£7.87
Bat Detector	647	£4.95
Programmable Pocket Timer JULY '89	648	£3.82
Electronic Spirit Level AUG '89	649	£3.85
Distance Recorder	651	£5.23
Treasure Hunter	652	£3.73
Xenon Beacon SEPT '89	650	£4.13
Probe Pocket Treasure Finder	653	£4.12
Power Supplies { - Fixed Voltage	654	£4.08
{ - Variable Voltage	655	£4.48
Music on Hold OCT '89	646	£3.85
Power Supplies - 25V 700mA	656	£4.35
- 30V 1A	657	£4.55
EE Seismograph - Control	658	£4.08
- Detector	659	£4.22
Lego/Logo & Spectrum	660	£6.49

Please note that when ordering it is important to give project title as well as order code. Please print name and address in Block Caps. Do not send any other correspondence with your order.

EE PRINTED CIRCUIT BOARD SERVICE

Please send me the following p.c.b.s.
Make cheques/PO payable to: **Everyday Electronics**
(payment in £ sterling only)

Order Code Project Quantity Price

.....

.....

.....

.....

I enclose cheque/PO for £.....

Name.....

Address.....

Please allow 28 days for delivery (see note above)

BLOCK CAPITALS PLEASE

EVERYDAY ELECTRONICS

CLASSIFIED

Reach effectively and economically today's enthusiasts anxious to know of your products and services through our semi-display and classified pages. The prepaid rate for semi-display spaces is £8.00 (plus VAT) per single column centimetre (minimum 2.5 cm). The prepaid rate for classified advertisements is 30 pence (plus VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749.

A & G ELECTRONICS LTD.

If you are buying Electronic Components elsewhere you are almost certainly paying too much! Write to us for a free 1989 catalogue and start saving money. (Please send two 19p stamps towards postage.)

100 Park Avenue, London E6 2SR
Tel 01-552 2386

WALTONS OF WOLVERHAMPTON

Established since 1947 - offering a complete range - I.C.s, transformers, switches, pots, capacitors, resistors, kits, speakers, test equipment, books and lots, lots more!

COME AND SEE US AT: MON-SAT 9-6.00 pm
55A WORCESTER STREET,
WOLVERHAMPTON TEL: 0902 22039

ELECTRONIC COMPONENTS

EVERYTHING FOR YOUR NEXT PROJECT

THE BIGGEST DISPLAY IN THE SOUTH
IS AT

FRASER ELECTRONICS

42 ELM GROVE * SOUTHSEA *
HANTS

Telephone 0705-815584

SALE OF SURPLUS COMPONENTS Send for details. Also our popular G.C.S.E. electronics kits. Sir-Kit Electronics, 70 Oxford Road, Clacton, CO15 3TE.

BCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY

1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1/2 amp A.C. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection.

Fully variable. Operates from 240V AC. Compact Unit. size 9 x 5 1/2 x 3in.



£39 inc. VAT
+ Post £2

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 01-684 1665

List. Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

SERVICE MANUALS

Most available for Amateur Radio, Military Surplus, Test Equipment, Vintage Valve, Colour TV, Mono TV, Video Recorders etc. etc

Over 100,000 stocked. LSAE Enquiries with Make/Model wanted.

FREE catalogue unique repair and data guides for LSAE

MAURITRON (EE)

8 Cherry Tree Road, Chinnor,
Oxon OX9 4QY

Tel: (0844) 51694

RESISTOR PACKS

1/4W 5% CARBON FILM
E12 range 10R to 10M

10 of any 1 value 6p

10 OF EACH VALUE
Total 730 resistors **£3.95**

Add 35p p&p and 15% VAT

RMOS P.O. BOX 3
USK GWENT NP5 2YF

FROM DINKY TWEETERS TO MASSIVE
WOOFERS

THEY ARE ALL IN OUR LATEST
ILLUSTRATED CATALOGUE OF
QUALITY SPARES AND
ACCESSORIES. SEND TODAY
ONLY 75p

FAST BY-RETURN SERVICE


STRACHAN ELECTRONICS (EEW)
9 CROALL PLACE, LEITH WALK
EDINBURGH EH7 4LT

LEARN ELECTRONICS WITHOUT SOLDER

Build electronic circuits without solder on a S-Dec.

This has built-in contacts and holes into which you plug your components. Suitable for all ages. Can be used time after time. Ideal gift for students or experimenters. Full instructions and 2 circuit diagram with each S-Dec.

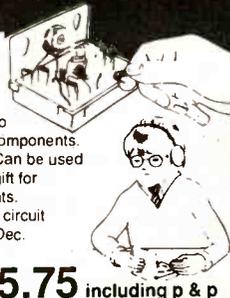Send Cheque or P.O. to:
Vistaplan, Dep EE
High Marsh, Daventry,
Northants NN11 4QE



£5.75 including p & p

NEW VHF MICROTRANSMITTER KIT

Tuneable 80-115 MHz, 500 metre range, sensitive electret microphone, high quality PCB, SPECIAL OFFER complete kit ONLY £5, assembled and ready to use £8.95 post free. Access/Visa orders telephone 021 411 1821 (24hrs).

Cheques/P.O.s payable to:

QUANTEK ELECTRONICS LTD
(Dept. EE), 45a Station Road
Northfield, Birmingham B31 3TE

MARAPET

COMPONENTS - TOOLS - ACCESSORIES

THIS MONTHS SPECIALS INCLUDE

The UNIROSS KB68PF BATTERY CHARGER - 'FAST' charge AA & AAA rechargeable batteries in just 5 hours. Features an integral mains plug - charging LED's. Reverse polarity protected.

ONLY £6.29 - POST FREE

RECHARGEABLE NI-CAD. BATTERIES - POST FREE

Size: RX6/AA (HP7) 96p each

Size: RX14/C (HP11) £2.08 each

Other sizes available

THIS IS JUST THE TIP OF THE MARAPET ICEBERG. Our full price list is sent FREE with above orders, or simply send 2 x 19p stamps for your copy.

NO VAT MAIL ORDER ONLY OFFERS END 31/10/89
Dept. EE, 1 HORNBEAM MEWS, GLOUCESTER GL2 0UE

TECHNICAL INFO SERVICES (EE)
76 Church St. Larkhall, Lanarkshire ML9 1HE
Phone 0636 884585 Mon-Fri. 9-5.
any other time 0636 883334. FOR FAST QUOTES

WORLD'S LARGEST COLLECTION SERVICE MANUALS - Most unobtainable elsewhere. Prices range from only £4.50 - large s.a.e. any quotation, no obligation to buy.

WORLD'S SOLE Suppliers of TV & Video Repair manuals, etc. from TV TECHNIC, also such publishers as Heinemann, Newnes, TV Technic, Thorn etc. Every published service sheet in stock, supplied full size, not bits & pieces. CTV's or any combination £3.50 plus Lsae; any other single item £2.50 plus Lsae. Complete Circuit Sets for most Videorecorders only £7 set (no sery this model).

LSAE for QUOTATIONS plus GIANT CATALOGUE - NEWSLETTERS - BARGAINS - FREE SSh as available

Comprehensive TV Repair Manual £9.50. Complete Radio Service and Repair Course £9.50. Complete Repair & Service Manuals - Mono TV £12.50. CTV £17.00. Video £19.50. Complete Repair Data with circuit - Mono TV £9.50. CTV £12.50. Video £19.50

£3.00 plus LSAE BRINGS THE ONLY COMPREHENSIVE SERVICE SHEETS & MANUALS, CATALOGUES plus FREE CHASSIS GUIDE and £4.00 OF VOUCHERS

FOR SALE

PART TIME MONEY SPINNER

This business would ideally suit someone with reasonable knowledge of micro-processor/digital electronics specifically 6800 series, who wants to turn electronic skills into cash, on a part time basis.

A mail order specialist computer repairs business with net annual profits of £10,000 per annum.

The sale includes full test equipment, all circuit diagrams, customer mailshot/database listing, miscellaneous spares and stock equipment.

Everything to start you off - at a price of £4,500 (no liabilities attached).

For details ring 0636 84220.

Kits

KITS, MICROTRANSMITTER, v.h.f./m., 25x15mm, £3.95. We also stock telephone transmitters/recording switches, beepers, radio transmitting alarms, circuit diagrams, etc. Kits and built available. Send s.a.e. to A.C.E., 99 Greenheath, Hednesford, Staffs.

Miscellaneous

SLIDER CONTROL AUDIOAMP £3.99 with mounted loudspeaker assembled KIA. 8 Cunliffe Road, Ilkley LS29 9EA. Design by Keith Lawrence.

TRANSMITTER CIRCUIT DIAGRAMS - F.M., Medium, Shortwave, C.B., some crystal controlled, minimum 17 circuits. Includes constructors' guide. Cheques/P.O.'s, £6.25 to D. Davies, 33 Gwaelodygarth, Merthyr Tydfil CF47 8YU.

Situations Vacant

ELECTRONICS TRAINER AT CAMDEN ITEC

Camden Itec is one of 175 training schemes in Information Technology for young people aged between 16 and 18. It has European links especially with Denmark. We are looking for someone who has practical experience of Digital, Analog, and mechanical systems to work in our hardware department. Applicants should preferably have an ONCHNC or City and Guilds full technical certificate in electronics. Hours 9.00am to 5.00pm five days a week. Holidays 6 weeks per year. Salary on scale 10,162-14,344. Further information from Ross on 01-485 3324. Send C.V. to Camden Itec, 7 Leighton Place, London NW5 2OL.

NATIONAL COMPONENT CLUB

SPECIAL OFFERS * SPECIAL OFFERS

SCANNER KIT(T)

A complete, six channel LED chaser kit for less than a fiver! The kit comes complete with all components, including PCB and instructions simple enough for even a complete novice. Works from 6-15vdc.

Only £4

MAINS POWER SUPPLY FOR ABOVE £1

* SPECIAL OFFER PACKS *

100 ASSORTED CAPACITORS £1

30 ASSORTED TRANSISTORS £1

25 ELECTROLYTIC CAPACITORS £1

12 LED's (5mm red or green) £1

5 555 TIMER IC's £1

5 741 OP-AMPS £1

FREE MYSTERY PACK WITH ALL ORDERS OVER £6

Please add £1 P&P, but do not add VAT.

P.O. or cheque to: NATIONAL COMPONENT CLUB, DEPT EE, BAILEY HILL, CASTLE CARY, SOMERSET BA7 7AD

We now accept Access - phone (0963) 51171

*** FREE CLUB MEMBERSHIP ***

Just phone above number or write for details

A Fair Deal For Our Advertisers


No guesses, no wishful thinking—the circulation of this magazine is audited to the strict professional standards administered by the Audit Bureau of Circulations



The Hallmark of Audited Circulation

OMNI ELECTRONICS

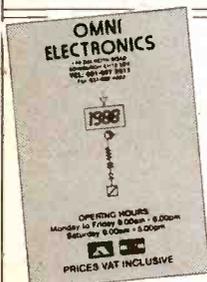174 Dalkeith Road, Edinburgh EH16 5DX • 031 667 2611



Have you sent for your copy of our catalogue yet?

If not, simply send 2x19p stamps for a copy by return.

A COMPREHENSIVE RANGE WITH SERVICE SECOND TO NONE

Open: Monday-Friday 9.00-6.00
Saturday 9.00-5.00



SHERWOOD ELECTRONIC COMPONENTS

45 Rutland St., Mansfield, Notts NG18 4AP

SPECIAL PACKS — Bigger selection, better value. All at £1 each

- SP1 12x5mm Red LEDs
 - SP2 12x5mm Green LEDs
 - SP3 12x5mm Yellow LEDs
 - SP4 10x5mm Amber LEDs
 - SP5 36x5mm 1 part LED clips
 - SP6 12x3mm Red LEDs
 - SP7 12x3mm Green LEDs
 - SP8 10x3mm Yellow LEDs
 - SP9 40x3mm 1 part LED clips
 - SP10 50x1N4148 signal diodes
 - SP11 25x1N4001 rectifier diodes
 - SP12 25x1N4002 rectifier diodes
 - SP13 25xRad.Elec.Caps. (1-1000µF)
 - SP15 20x2K2 Min. Hor. presets 0.1W
 - SP16 20x4K7 Min. Hor. presets 0.1W
 - SP17 20x100K Min. Hor. presets 0.1W
 - SP18 12xBC182 Transistors
 - SP19 12xBC183 Transistors
 - SP20 12xBC184 Transistors
 - SP21 10xBC212 Transistors
 - SP22 10xBC214 Transistors
 - SP23 10xBC549 Transistors
 - SP24 5xCmos 4001
 - SP25 5x555 Timer
 - SP26 5x741 Op-Amp
 - SP27 5xCmos 4002
 - SP28 5xCmos 4011
 - SP29 3xCmos 4013
 - SP30 5xCmos 4025
 - SP31 4xCmos 4071
 - SP32 4xCmos 4077
 - SP33 4xCmos 4081
 - SP34 2xCmos 4510
 - SP35 2xCmos 4511
 - SP36 20x10µF/25V Rad.Elect.Caps.
 - SP37 15x100µF/35V Rad.Elect.Caps.
 - SP38 20x47µF/25V Rad.Elect.Caps.
 - SP39 12x470µF/16V Rad.Elect.Caps.
 - SP40 10xBC237 Transistors
 - SP41 25xmixed
 - SP43 2xLM1458
 - SP44 12x5mm Leds-4 each, Red, Green
 - Yellow
 - SP47 5xminiature push button switches
 - SP102 15x8 pin DIL sockets
 - SP103 12x14 pin DIL sockets
 - SP104 12x16 pin DIL sockets
- 1 pack of your choice FREE when you buy any 10 of the above packs.

- ADDITIONAL PACKS**
- SP50 25x5mm Red LEDs £2.00
 - SP51 25x5mm Green LEDs £2.00
 - SP52 50xRad. Elec. Caps. £1.95
 - SP53 30x1.C. sockets—8 pin, 14 pin, 16 pin (10 off) £2.00
 - SP54 1xTIL38+1xTIL100 I.R. emitter+sensor £1.60

RESISTOR PACKS

- 0.25W Carbon Film resistors 10R-10M
- 5 each value — total 365 £2.75
 - 10 each value — total 730 £4.50
 - 1000 popular values £6.00
 - Individual resistors 2p ea.
 - 10+ one value 1p ea.
 - 100 one value 75p

I.C.s

- 555 22p
- 556 65p
- 741 22p
- 747 65p
- CA3140E 45p
- CA3240E £1.25
- LM339 50p
- LM380-14 £1.20
- LM723 55p
- LM1458 80p
- TL071 55p
- TL072 75p
- TL081 40p
- TL082 55p

V. REGS.

- 100mA 25p
- 78L05 25p
- 78L12 25p
- 78L15 26p
- 79L05 30p
- 79L12 30p
- 79L15 30p
- 1A 35p
- 7805 35p
- 7812 36p
- 7815 36p
- 7905 36p
- 7912 38p
- 7915 38p

CMOS

- 4000 25p
- 4001 25p
- 4002 25p
- 4011 25p
- 4012 27p
- 4013 38p
- 4017 55p
- 4023 30p
- 4025 25p
- 4027 50p
- 4040 70p
- 4047 65p
- 4049 40p
- 4066 45p
- 4070 27p
- 4071 27p
- 4072 27p
- 4073 27p
- 4075 27p
- 4077 32p
- 4081 27p
- 4083 27p
- 4510 65p
- 4511 65p
- 4514 £1.25
- 4515 £1.30
- 4516 65p
- 4528 70p

Cheques or P.O. to:

SHERWOOD ELECTRONIC COMPONENTS

Please add £1 P&P NO VAT

This only a small sample of components stocked, send 75p for new 1990 catalogue, contains vouchers redeemable against orders over £5.00.

FRASER ELECTRONICS

42 Elm Grove Southsea Hants PO5 1JG



BUDGET PACK SELECTION

The packs listed below are selected from our full list of 140 packs (sent free with all orders). Note that our prices include VAT and carriage charges—NO HIDDEN EXTRAS. All orders subject to a minimum value of £3.00. Access and Barclaycard accepted—and you can 'phone orders to

Portsmouth (0705) 815584

from 9.00am 'till 5.30pm any weekday

Qty.	Device	Description	Cost
50	1N4004	Rectifier diode 1A/400V	£2.00
12	BC327	PNP 0.8A transistor	£1.00
14	LED MIX	7 ea .3mm red & green LED	£1.00
2	ORP12	Light dependent resistor	£1.80
10	555	8-pin DIP timer	£1.80
10	741	8-pin DIP op.-amp	£1.80
5	SB1	9t x 24h. stripboard	£1.00
2	Z80CPU	2.5MHz 8-bit µ proc.	£2.00
12	DIL-14	14-pin DIL socket	£1.00
5	DX25PZ	D-min RS232 solder plug	£2.00

MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace. When and where you want, under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice.

GCSE / GCE / SCE ELECTRONICS BASIC ELECTRONIC ENGINEERING (City & Guilds) ELECTRICAL ENGINEERING ELECTRICAL CONTRACTING/ INSTALLATION	CAR MECHANICS COMPUTER PROGRAMMING TV, VIDEO & HI-FI SERVICING RADIO AMATEUR LICENCE EXAM (City & Guilds)	SEE QUOTE PAGE 671
Course of Interest Name: _____ P.Code _____ Address: _____ International Correspondence School, Dept ECSA9, 312/314 High Street, Sutton, Surrey SM1 1PR. Tel: 01-643 9568 or 041-221 2926 (24 hrs)		

- Varta Mempak nic. cad. rechargeable batteries 3.6V 100mA. 1.85p
- Miniature 3V DC Electric Motor with stabilising Capacitor. Approx. Dimensions, Length 42.5mm, Width 32mm, Shaft 10mm 70p each
- 4 Way 13amp Extension Block fitted with 2MTRS 13amp 3 core flex and a 13amp Plugtop £6.50
- 2 Way 13amp 10MTR Extension Reel with Safety Cut Out £12.95
- 2 Way Powerline Professional 25MTR 13amp Extension Reel with Cut Out £24.95
- QUALITY SCREWDRIVER SET** Manufactured in West Germany to Int. Standards. Rated at 1000V consisting of Four Parallel Blade Drivers, Blade sizes 75mmx2.5mm, 100mmx4mm, 125mmx5.5mm, 150mmx6.5mm, Two Cross Point, Blade Sizes 80mmx5.5mm, 100mmx6mm, One 70mm 240V Mains Screwdriver £9.36 per set
- LONG NOSE PLIERS 8"(200mm) Minors** £4.90 each
- WIRE CUTTERS 6 1/2"(160mm) 1000V** £5.50 each
- WIRE STRIPPER 6 1/2"(160mm) 1000V** £5.50 each
- ANTEX SK5 SOLDERING KIT** Consisting of a CS240 17 Watt 240V Soldering iron, an ST4 Solder Stand, Approx 1mtr of Solder and a booklet on How to Solder £9.12 each
- ARCOLITE ROCKER SWITCHES** On/Off snap-in type rated 200/250A.C. 6.3mm tab: **PACK ONE** Consisting of 10 assorted illuminated single-pole rocker switches. To fit panel hole approx. 28.2mmx11.5mm £4.00 per pack
- PACK TWO** Consisting of 10 assorted illuminated and non-illuminated double-pole rocker switches. To fit panel hole approx. 30mmx22.1mm £6.00 per pack

Substantial range of SILVA MICA/WAX POLYSTYRENE AND ELECTROLYTIC CAPACITORS in stock. Catalogue free with FIRST ORDER.

CHAFFORD VALLEY PRODUCTS

Chafford Lane, Fordcombe, Kent TN3 0SH.

Tel. 089 2740287 Fax. 089 2740216.

MAIL ORDER ONLY. ALL PRICES INCLUSIVE VAT. ADD 1.00p P&P UNLESS OTHERWISE STATED. TERMS CASH, CHEQUE OR POSTAL ORDER WITH ORDER. SCHOOL ACCOUNTS AVAILABLE

ADVERTISERS INDEX

AUDIO ELECTRONICS	661
BICC - VERO ELECTRONICS	635
B K ELECTRONICS	Cover (iii)
BLACKMORE ELECTRONICS	677
BULL J & N	Cover (ii)
CAMBRIDGE COMPUTER SCIENCE	667
CHAFFORD VALLEY PRODUCTS	688
CIRKIT DISTRIBUTION	672
CRICKLEWOOD ELECTRONICS	665
CROTECH INSTRUMENTS	637
CR SUPPLY CO.	659
EVERETT WORKSHOP ACCESS	659
FRASER ELECTRONICS	687
GREENWELD ELECTRONICS	621
HART ELECTRONIC KITS	637
HIGHGRADE COMPONENTS	620
HUMBERVALE ENGINEERING	688
ICS	688
JAYTEE ELEC. SERVICES	661
JIDENCO CD	685
KEMSOFT	677
KITMASTER	667
LIGHT SOLDERING DEVELOPMENTS	659
LONDON ELECTRONICS COLLEGE	688
MAGENTA ELECTRONICS	622/3
MAPLIN ELECTRONICS	Cover (iv)
MARCO TRADING	675
NATIONAL COMPONENT CLUB	687
OMNI ELECTRONICS	687
PHONOSONICS	675
RADIO & TV COMPONENTS	618
SERVICE TRADING CO.	659
SHERWOOD ELECTRONIC COMPONENTS	687
SPECIALIST SEMICONDUCTORS	683
STEWART OF READING	688
SUMA DESIGN	672
TANDY	643
TK ELECTRONICS	624

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

2 YEAR BTEC National Diploma (OND) ELECTRONIC & COMMUNICATIONS ENGINEERING
(Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

1 YEAR BTEC National Certificate (ONC) ELECTRONIC ENGINEERING
1—INFORMATION TECHNOLOGY
(Electronics, Satellite TV, Networks, Telecomms)

2—ELECTRONIC EQUIPMENT SERVICING
(Electronics, Television, Video Cassette Recorders, CCTV, Testing and Fault Diagnosis)

3—SOFTWARE ENGINEERING
(Electronics, Assembler, BASIC, Pascal, CAD/CAM)

4—COMPUTING TECHNOLOGY
(Electronics, Computing Software/Hardware, Microelectronics)

10 MONTHS BTEC Higher National Certificate (HNC) COMPUTING TECHNOLOGY & ROBOTICS
(Microprocessor Based Systems, Control, Robotics)

These courses include a high percentage of college based practical work to enhance future employment prospects. No additional fees for overseas students. Shortened courses of 3 to 6 months can be arranged for applicants with previous electronics knowledge. THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C. and H.N.C. Monday 18th September 1989

FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept. EE), 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
Tel: 01-373 8721

OSCILLOSCOPES

- TEKTRONIX 2213 Dual Trace 60MHz Delay Sweep £400
- TEKTRONIX 465 Dual Trace 100MHz Delay Sweep £500
- TEKTRONIX 454 Dual Trace 150MHz Delay Sweep £400
- GOULD/ADVANCE OS300A Dual Trace 40MHz Delay Sweep £300
- TRIO CS1568A Dual Trace 20MHz Delay Sweep £250
- PHILIPS PM3233 Dual Trace 10MHz £230
- TELEQUIPMENT D75 Dual Trace 50MHz Delay Sweep £275
- KIKUSUI 5530A Dual Trace 35MHz £250
- HP 1220A Dual Trace 15MHz £200
- GOULD/ADVANCE OS1100 Dual Trace 30MHz £210
- GOULD/ADVANCE OS255 Dual Trace 15MHz £210
- COSSOR CDU150 Dual Trace 35MHz Delay Sweep Solid State Portable 8 x 10cm Display £180
- Optional front cover containing 2 probes etc £10
- SE LABS SM111 Dual Trace 18MHz Solid State Portable AC or external DC operation 8 x 10cm Display £150
- SCOPEX 4D10B Dual Trace 10MHz £150

- MARCONI TF2015 AM/FM 10-520MHz Sig Gen with Synchroniser TF2171 £550
- MARCONI TF2015 without Synchroniser £425
- MARCONI TF2015 AM/FM 10MHz-120MHz with Synchroniser TF2173 £400
- MARCONI TF2016 without Synchroniser £300
- MARCONI/SANDERS SIG SOURCE 6055B. 850-2150MHz £500
- DYMAR 1525 AM/FM 0.1-18MHz Sig Gen £200
- HP 854 SWEEP OSCILLATOR 7-12GHz £600
- HP 820 Signal Generator 7-11GHz £400
- HP 814A Signal Generator 800-2100MHz £450
- FERROGRAPH RTS2 Recorder Test Set £275
- WOELKE Wow & Flutter Meter ME 108 £100
- LEADER LMV 186A Two channel Millivoltmeter 5Hz-500kHz, 100uV-300V £100
- LEVEILL TG200M 1Hz-1MHz Sine/Square £125
- MARCONI Automatic Distortion Meter TF2337A. 400Hz or 1KHz. Measures down to 0.01% £150
- MARCONI TF2700 UNIVERSAL LCR Bndge. Battery Operated From 150 £160

- PHILIPS PM6455 FM Stereo Generator £95
- ADVANCE S662B AM 150kHz-220MHz £45 (P & P £7)
- TEKTRONIX CURVER TRACER type CT71 £325
- TRIO SG402 AM Sig Gen 100kHz-30MHz Unused £75
- MARCONI ATTENUATOR TF2182 DC-1MHz 600 Ohm 0-11dB in 0.1dB Steps £35 (P & P £7)
- HATHFIELD ATTENUATOR DC 250MHz 50 Ohm 0-100dB. £90
- MARCONI RF POWER METER TF1152A1 DC 500MHz 0.25-25W 500 Ohm with manual ONLY £45 (P & P £7)

- TELEPHONES — YES! REAL DIAL TYPE TELEPHONES — that don't slide around the desk. Type No. 746 supplied with standard BT plug (used). ONLY £5 each P & P £3. Quantity discount.
- Batteries 15 volt £3 each, 10 off £25 (P & P extra)

USED EQUIPMENT — WITH 30 DAYS GUARANTEE. MANUALS SUPPLIED IF POSSIBLE. This is a VERY SMALL SAMPLE OF STOCK. VAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041 Fax. 0734 351696
Callers welcome 9 am-5.30 pm Mon.-Fri. (until 8 pm Thurs.)

SPECIAL OFFER HEWLETT PACKARD OSCILLATOR TYPE 1740A

Dual Trace 100MHz Delay Sweep. Trigger Vlew £575

HAMEG MODULAR SYSTEM

HM8001 Main Frame with HM8032 Sine Wave Generator 20Hz-20MHz; HM8030 2 Function Generator 0.1-1MHz Sine/Square/Triangle; and HM8011 2 Digital Multimeter 4 1/2 digit. **ONLY £400**

RACAL-NORSK Keyboard. CASED. ASCII & Function keys. Unused. Some info. **ONLY £5 each (P & P £3)**
FARNELL SWITCHED MODE PSU 5V 40A & ±12V 5A **£30 each (P & P £4)**
OTHER SWITCHED MODE PSUs available. Please enquire
DISK DRIVES 5 1/4in DS/DD 80 track from £50

MULTIMETERS (P & P all AVOs £10)


- AVO 8 Complete with Batteries & Leads From £50
- AVO 6 MkV Complete with Batteries & Leads £90
- AVO TEST SET No 1 (Military version of AVO 8) Complete with Batteries and Leads £65
- TEST LEADS suitable for AVOMETERS. Red & Black with 2 Croc-clips & 2 Prods £5 (P & P £3)
- Black 'Ever-Ready' case for AVOs. Unused £15 (P & P £4)
- AVO TRANSISTOR ANALYSIS Mk2 CT446 Suitcase style complete with batteries and operating instructions **ONLY £25 EACH (P & P £7)**

NEW EQUIPMENT

- HAMEG OSCILLOSCOPE 604 Dual Trace 60MHz. Delay Sweep. Component Tester + two probes £575
- HAMEG OSCILLOSCOPE 203.6. Dual Trace 20MHz. Component Tester with two probes £314
- All Other Models Available.
- BLACK STAR FREQUENCY COUNTERS (P & P £4)
Meter: 100-100MHz £99
Meter: 600-600MHz £129
Meter: 1000-1GHz £178
- BLACK STAR JUPITOR 500 FUNCTION GENERATOR. Sine/Square/Triangle. 0.1KHz. (P & P £4) £110
- BLACK STAR ORION PAL TV/VIDEO COLOUR PATTERN GENERATOR £209
- HUNG CHANG DMM 7030. 3 1/2 digit. Hand held 28 ranges including 10amp AC/DC 0.1%. Complete with batteries & leads. (P & P £4) £39.50
- As above DMM 6010 0.25% £33.50
- Carrying case for above £3 each
- OSCILLOSCOPES PROBES. Switched x1x10 £11

THE BENCHHAND CLAMP

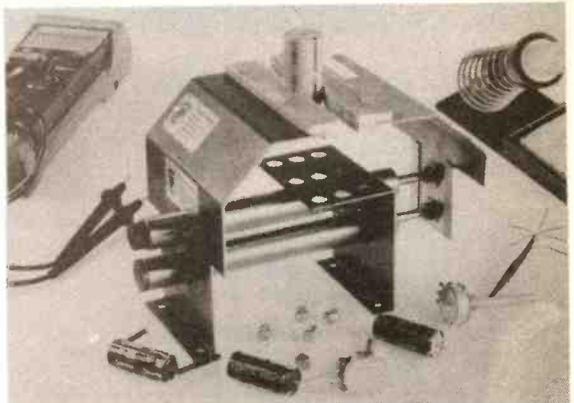COPYRIGHT DESIGN (1988) OF HUMBERVALE ENGINEERING



THE BENCHHAND CLAMP IS A SPRING OPERATED DEVICE, WHOSE SPRING IS SET AT OPTIMUM, BUT IS ADJUSTABLE. THE CLAMP GRIPS ARE MADE OF CAST ALLOY. SHAPED GRIPS ARE FITTED AS STANDARD AND CAPABLE OF HOLDING MOST SHAPES WITH A FIRM HOLD TO CARRY OUT A VARIETY OF FUNCTIONS SUCH AS SOLDERING, ETC. TWO 'D' CONNECTOR SIDE ENTRY SLOTS ARE ALSO INCORPORATED. UNSHAPED GRIPS ARE ALSO AVAILABLE FOR SHAPING AS AN OPTIONAL EXTRA. THE CLAMP CONSTITUTES A ROBUST, DIVERSE AND VERSATILE TOOL, A VALUABLE AID IN MANY FIELDS, SPARE PARTS ARE AVAILABLE. PERSONS WITH SOME DISABILITY MAY FIND IT USEFUL ALSO.

SEND S.A.E. FOR FULLER DETAILS
ALLOW UP TO 14 DAYS DELIVERY.

SPECIFICATION:		PRICE £68.36 plus P & P £3.00
Length closed	19.5 cm	HUMBERVALE ENGINEERING PO Box 15, Hessle, Humberside HU13 0HP
Jaw opening	7 cm	
Width	12 cm	
Height	12.5 cm	
Weight	1 kg	

Published on approximately the first Friday of each month by Wimborne Publishing Ltd., 6 Church Street, Wimborne, Dorset BH21 1JH. Printed in England by Benham & Co. Limited, Colchester, Essex. Distributed by Seymour, 334 Brixton Road, London SW9 7AG. Sole Agents for Australia and New Zealand — Gordon & Goich (Asia) Ltd., South Africa — Central News Agency Ltd. Subscriptions INLAND £15.70 and OVERSEAS £19 payable to "Everyday Electronics" Subscription Department, 6 Church Street, Wimborne, Dorset BH21 1JH. EVERYDAY ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 30p STAMPED FOR CURRENT LIST.

OMP POWER AMPLIFIER MODULES

Supplied ready built and tested.

OMP POWER AMPLIFIER MODULES Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. - 118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. PRICE £33.99 + £3.00 P&P.

NEW SERIES II MOS-FET MODULES



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. - 125dB, Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. - 130dB, Size 300 x 155 x 100mm. PRICE £62.99 + £3.50 P&P.



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. - 130dB, Size 330 x 175 x 100mm. PRICE £79.99 + £4.50 P&P.

NOTE:- MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS. STANDARD - INPUT SENS. 500mV BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS. 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.

McKENZIE:- INSTRUMENTS, P.A., DISCO, ETC.

- ALL MCKENZIE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID., DISCO. RES. FREQ. 80Hz. FREQ. RESP. TO 14KHz SENS. 99dB. PRICE £28.59 + £2.00 P&P.
 - 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 70Hz. FREQ. RESP. TO 6KHz SENS. 100dB. PRICE £34.70 + £2.50 P&P.
 - 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID. RES. FREQ. 45Hz. FREQ. RESP. TO 7KHz SENS. 103dB. PRICE £47.48 + £2.50 P&P.
 - 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES. FREQ. 45Hz. FREQ. RESP. TO 7KHz SENS. 98dB. PRICE £36.66 + £3.50 P&P.
 - 12" 100 WATT C12100TC TWIN CONE, HIGH POWER WIDE RESPONSE, P.A. VOICE, DISCO. RES. FREQ. 45Hz. FREQ. RESP. TO 14KHz SENS. 100dB. PRICE £37.63 + £3.50 P&P.
 - 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES. FREQ. 40Hz. FREQ. RESP. TO 7KHz SENS. 100dB. PRICE £64.17 + £3.50 P&P.
 - 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES. FREQ. 45Hz. FREQ. RESP. TO 5KHz SENS. 100dB. PRICE £85.79 + £3.50 P&P.
 - 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES. FREQ. 40Hz. FREQ. RESP. TO 5KHz SENS. 98dB. PRICE £53.70 + £4.00 P&P.
 - 15" 200 WATT C15200BS VERY HIGH POWER BASS. RES. FREQ. 40Hz. FREQ. RESP. TO 4KHz SENS. 99dB. PRICE £73.26 + £4.00 P&P.
 - 15" 250 WATT C15250BS VERY HIGH POWER BASS. RES. FREQ. 40Hz. FREQ. RESP. TO 4KHz SENS. 99dB. PRICE £80.53 + £4.50 P&P.
 - 15" 400 WATT C15400BS VERY HIGH POWER BASS. RES. FREQ. 40Hz. FREQ. RESP. TO 4KHz SENS. 102dB. PRICE £94.12 + £4.50 P&P.
 - 18" 400 WATT C18400BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES. FREQ. 27Hz. FREQ. RESP. TO 3KHz SENS. 99dB. PRICE £167.85 + £5.00 P&P.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC.

- ALL EARBENDER UNITS 8 OHMS EXCEPT EB8-50 AND EB10-50 DUAL 4 AND 8 OHM. BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED FOAM SURROUND**
- 8" 50 WATT EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz. FREQ. RESP. TO 7KHz SENS. 97dB. PRICE £8.90 + £2.00 P&P.
 - 10" 50 WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES. FREQ. 40Hz. FREQ. RESP. TO 5KHz SENS. 99dB. PRICE £12.00 + £2.50 P&P.
 - 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. RES. FREQ. 35Hz. FREQ. RESP. TO 3KHz SENS. 96dB. PRICE £27.50 + £3.50 P&P.
 - 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. RES. FREQ. 28Hz. FREQ. RESP. TO 3KHz SENS. 92dB. PRICE £21.00 + £3.00 P&P.
 - 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES. FREQ. 26Hz. FREQ. RESP. TO 3KHz SENS. 93dB. PRICE £32.00 + £3.50 P&P.
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 5 1/4" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz. FREQ. RESP. TO 20KHz SENS. 92dB. PRICE £9.99 + £1.50 P&P.
 - 6 1/4" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz. FREQ. RESP. TO 20KHz SENS. 94dB. PRICE £10.99 + £1.50 P&P.
 - 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz. FREQ. RESP. TO 18KHz SENS. 89dB. PRICE £12.99 + £1.50 P&P.
 - 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 35Hz. FREQ. RESP. TO 12KHz SENS. 86dB. PRICE £16.49 + £2.00 P&P.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP, PRICE £14.49 + £1.00 P&P

FM MICRO TRANSMITTER (BUG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT, PRICE £8.82 + £1.00 P&P



3 watt FM Transmitter



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



OMP VARISPEED TURNTABLE CHASSIS.



* MANUAL ARM * STEEL CHASSIS * ELECTRONIC SPEED CONTROL 33 & 45 * WARI PITCH CONTROL * HIGH TORQUE SERVO DRIVEN DC MOTOR * TRANSIT SCREWS * 12" DIE CAST PLATTER * NEON STROBE * CALIBRATED BAL WEIGHT * REMOVABLE HEAD SHELL * 1/2" CARTRIDGE FIXINGS * CUE LEVER * POWER 220 240V 50 60Hz * 390x305mm * SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE. PRICE £59.99 + £3.50 P&P.

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500
PRICE £16.99 + 50p P&P

GOLDRING G850
PRICE £6.99 + 50p P&P

OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



NEW MXF SERIES OF POWER AMPLIFIERS

THREE MODELS:- MXF200 (100w + 100w)
MXF400 (200w + 200w) MXF600 (300w + 30Qw)

All power ratings R.M.S. into 4 ohms.

FEATURES: * Independent power supplies with two Toroidal Transformers * Twin L.E.D. Vu meters * Rotary indexed level controls * Illuminated on/off switch * XLR connectors * Standard 775mV inputs * Open and short circuit proof * Latest Mos-Fets for stress free power delivery into virtually any load * High slew rate * Very low distortion * Aluminium cases * MXF600 Fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF 200 W19" x H3 1/2" (2U) x D11"
MXF 400 W19" x H5 1/4" (3U) x D12"
MXF 600 W19" x H5 1/4" (3U) x D13"

PRICES: MXF400 £228.85
MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH



OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS. FINISHED IN HARDWEARING BLACK VINYL WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE. INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE, 45Hz-20KHz BOTH MODELS 8 OHM. SIZE H18" x W15" x D12"

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR


OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL:- £12.00 PER PAIR

PIEZO ELECTRIC TWEETERS-MOTOROLA

PIEZO ELECTRIC TWEETERS - MOTOROLA

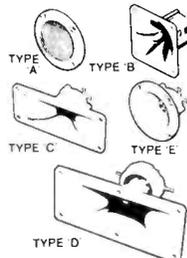Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 50p P&P.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.00 each + 50p P&P.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 50p P&P.


TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 50p P&P.

TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 50p P&P.

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £3.99 + 50p P&P.

STEREO DISCO MIXER

STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 Inputs with individual faders providing a useful combination of the following:-
3 Turntables (Mag), 3 Mics, 4 Line including CD plus Mic with talk over switch Headphone Monitor, Pan Pot L. & R. Master Output controls. Output 775mV. Size 360x280x90mm. Supply 220-240V.
Price £134.99 - £4.00 P&P

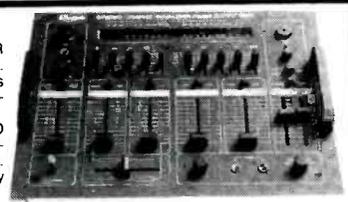

B. K. ELECTRONICS Dept EE

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR
TEL: 0702-527572 FAX: 0702-420243

AMAZING LOW PRICE

SOLDERING IRONS

FLAME MASTER HOT GAS SOLDERING TOOL

Superb Pocket Size Portable Gas
Soldering Iron

ONLY
£12.95
FSI20



★ Interchangeable Tips ★

- ★ Powered by Butane Gas
- ★ Simple to Refill
- ★ Temperature up to 400°C (750°F)
- ★ Up to 2 Hours Continuous Use

FLAME MASTER 5 IN 1 HOT GAS TOOL KIT

Complete with tough moulded to measure case and including:

MULTI-PURPOSE TOOL

- ★ 4 Interchangeable Soldering Iron Tips
- ★ Soldering Iron
- ★ Hot Cutting Knife
- ★ Wide Area Flame Torch
- ★ High Temperature Flame Torch
- ★ Hot Air Blower

GREAT FOR

- ★ Electrical and Electric Work
- ★ Cutting Plastics and Fibres
- ★ Sealing, Bonding and Shrinking
- ★ Removing Paint and Putty

ONLY
£19.95
FMK20



The Flame Master hot gas tool kit has many uses. It can be a soldering iron, a pencil flame torch, a hot air blower or a wide (flat) flame torch.

You can fit the soldering head with a selection of soldering tips and the hot knife, or you can fit the flame head, onto which you can attach the hot blower or the wide flame unit. The choice is yours!

Post Your Order Now ...

Order Coupon Send this coupon to P.O. Box 3, Rayleigh, Essex SS6 8LR

Quantity	Description	Code	Price

Name Add Carriage 50p
Address If order below £5 please add 50p
Post Code **Total**

I authorise you to debit my Credit Card account for the cost of goods despatched.

Credit Card No.

Access Amex Visa Delete as required.

If ordering by Credit Card please sign

Expiry date of Credit Card EE

Maplin ELECTRONICS

CREDIT CARD HOTLINE



0702 554161

PHONE BEFORE 5PM FOR SAME DAY DESPATCH

ALL PRICES INCLUDE VAT.

All items subject to availability, both items will be on sale in our shops in Birmingham, Bristol, Leeds, Hammersmith, Edware, Manchester, Nottingham, Southampton and Southend-on-Sea.