

EVERYDAY WITH PRACTICAL ELECTRONICS


NOVEMBER 1992

INCORPORATING ELECTRONICS MONTHLY

FULLY S.O.R. £1.80

21ST
Anniversary
Issue

TOMORROW'S TECHNOLOGY

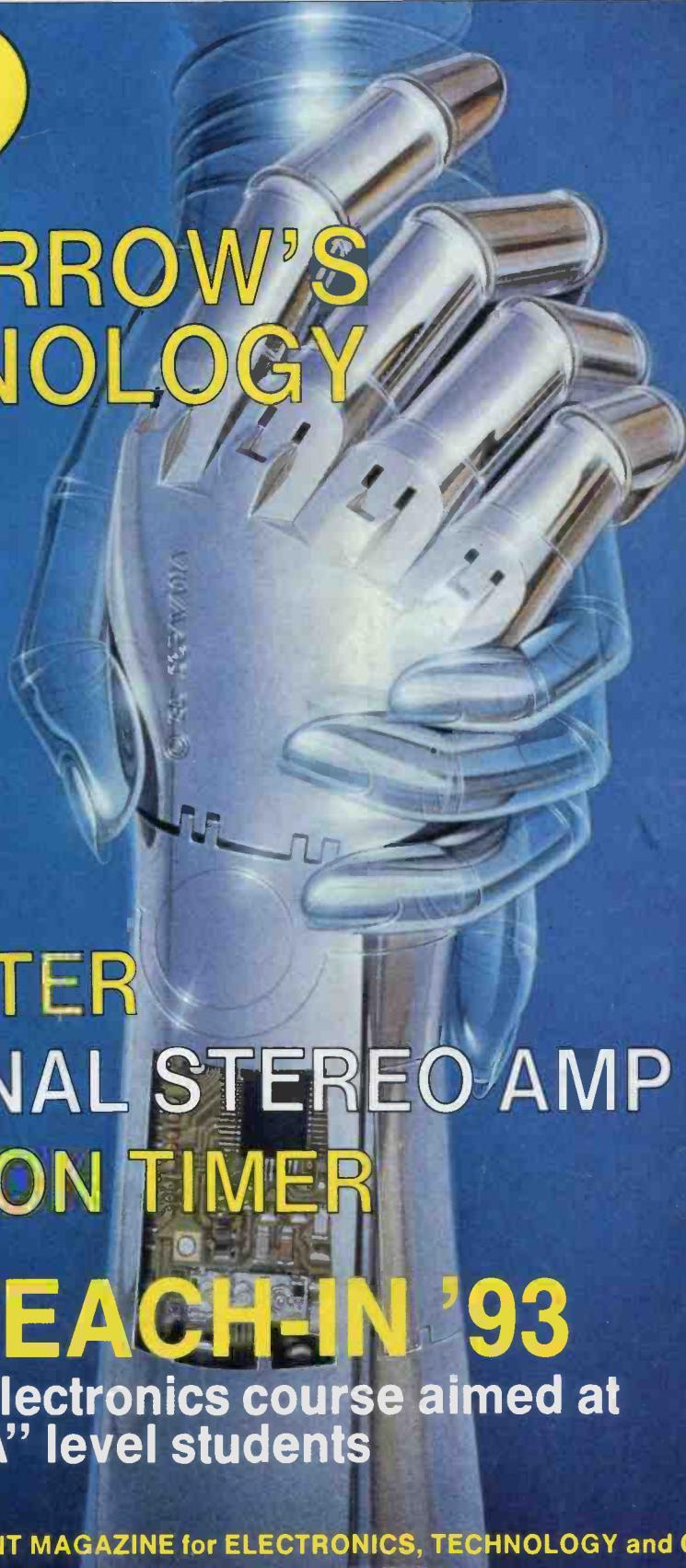

ALTIMETER

PERSONAL STEREO AMP

REACTION TIMER

New
Series

TEACH-IN '93

A complete electronics course aimed at
GCSE and "A" level students



AMSTRAD PORTABLE PC'S FROM £149 (PPC1512SD), £179 (PPC1512DD), £179 (PPC1640SD), £209 (PPC1640DD). MODEMS £30 EXTRA. NO MANUALS OR PSU.

HIGH POWER CAR SPEAKERS. Stereo pair output 100W each. 4ohm impedance and consisting of 6 1/2" woofer 2" mid range and 1" tweeter. Ideal to work with the amplifier described above. Price per pair £30.00 Order ref 30P7R.

MICROWAVE CONTROL PANEL. Mains operated, with touch switches. Complete with 4 digit display, digital clock, and 2 relay outputs one for power and one for pulsed power (programmable). Ideal for all sorts of precision timer applications etc. Now only £4.00 ref 4P151.

FIBRE OPTIC CABLE. Stranded optical fibres sheathed in black PVC. Five metre length £7.00 ref 7P29R.

12V SOLAR CELL. 200mA output ideal for trickle charging etc. 300 mm square. Our price £15.00 ref 15P42R.

PASSIVE INFRA-RED MOTION SENSOR.

Complete with daylight sensor, adjustable lights on timer (8 secs - 15 mins), 50' range with a 90 deg coverage. Manual override facility. Complete with wall brackets, bulb holders etc. Brand new and guaranteed. Now only £19.00 ref 19P29.

Pack of two PAR38 bulbs for above unit £12.00 ref 12P43R.

VIDEO SENDER UNIT. Transmit both audio and video signals from either a video camera, video recorder or computer to any standard TV set within a 100' range! (tune TV to a spare channel). 12v DC op. £15.00 ref 15P39R Suitable mains adaptor £5.00 ref 5P19R.

FM TRANSMITTER housed in a standard working 13A adapter (bug is mains driven). £26.00 ref 26P2R.

MINIATURE RADIO TRANSCEIVERS A pair of walkie talkies with a range of up to 2 kilometres. Units measure 22x52x155mm. Complete with cases. £30.00 ref 30P12R.

FM CORDLESS MICROPHONE. Small hand held unit with a 500' range! 2 transmit power levels reqs PP3 battery. Tunable to any FM receiver. Our price £15 ref 15P42R.

12 BAND COMMUNICATIONS RECEIVER. 9 short bands. FM, AM and LW DX/local switch, tuning eye, mains or battery. Complete with shoulder strap and mains lead NOW ONLY £19.00!! REF 19P14R.

CAR STEREO AND FM RADIO Low cost stereo system giving 5 watts per channel. Signal to noise ratio better than 45db, wow and flutter less than .35%. Neg earth. £19.00 ref 19P30.

LOW COST WALKIE TALKIES. Pair of battery operated units with a range of about 200'. Our price £8.00 a pair ref 8P50R.

7 CHANNEL GRAPHIC EQUALIZER. A 60 watt power amp! 20-21KHZ 4.8R 12-14v DC, negative earth. Cased. £25 ref 25P14R.

NICAD BATTERIES. Brand new top quality. 4 x AA's £4.00 ref 4P44R, 2 x C's £4.00 ref 4P73R, 4 x D's £9.00 ref 9P12R, 1 x PP3 £6.00 ref 6P35R.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR GUIDE. The ultimate equivalents book. Latest edition £20.00 ref 20P32R.

CABLE TIES. 142mm x 3.2mm white nylon pack of 100 £3.00 ref 3P104R. Bumper pack of 1,000 ties £14.00 ref 14P6R.

GOT A CARAVAN OR BOAT?

NEW 80 PAGE FULL COLOUR LEISURE CATALOGUE

2,500 NEW LINES FREE WITH ORDER ON REQUEST

OR SEND £1.00

GEIGER COUNTER KIT. Complete with tube, PCB and all components to build a battery operated geiger counter. £39.00 ref 39P1R.

FM BUG KIT. New design with PCB embedded coil. Transmits to any FM radio. 9v battery req'd. £5.00 ref 5P158R.

FM BUG Built and tested superior 9v operation £14.00 ref 14P3R.

COMPOSITE VIDEO KITS. These convert composite video into separate H sync, V sync and video. 12v DC. £8.00 ref 8P39R.

SINCLAIR CS MOTORS 12v 29A (full load) 3300 rpm 6" x 1/4" O/P shaft. New £20.00 ref 20P22R.

As above but with fitted 4 to 1 inline reduction box (800rpm) and toothed nylon belt drive cog £40.00 ref 40P8R.

ELECTRONIC SPEED CONTROL KIT for c5 motor. PCB and all components to build a speed controller (0-95% of speed). Uses pulse width modulation. £17.00 ref 17P3R.

SOLAR POWERED NICAD CHARGER. Charges 4 AA nicads in 8 hours. Brand new and cased £6.00 ref 6P3R.

ACORN DATA RECORDER ALF503 Made for BBC computer but suitable for others. Includes mains adapter, leads and book. £15.00 ref 15P43R.

VIDEO TAPES. Three hour superior quality tapes made under licence from the famous JVC company. Pack of 5 tapes. New low price £8.00 ref 8P161.

PHILIPS LASER. 2MW HELIUM NEON LASER TUBE. BRAND NEW FULL SPEC £40.00 REF 40P10R. MAINS POWER SUPPLY KIT £20.00 REF 20P33R READY BUILT AND TESTED LASER IN ONE CASE £75.00 REF 75P4R.

12 TO 220V INVERTER KIT As supplied it will handle up to about 15w at 220v but with a larger transformer will handle 80watts. Basic kit £12.00 ref 12P17R. Larger transformer £12.00 ref 12P41R.

VERO EASI WIRE PROTOTYPING SYSTEM Ideal for designing projects on etc. Complete with tools, wire and reusable board. Now low bargain price only £2.00 ref B2P1.

HIGH RESOLUTION 12" AMBER MONITOR 2v 1.5A Hercules compatible (TTL input) new and cased £22.00 ref 22P2R.

VGA PAPER WHITE MONO monitors new and cased 240v AC. £59.00 ref 59P4R.

25 WATT STEREO AMPLIFIER C. STK043. With the addition of a handful of components you can build a 25 watt amplifier. £4.00 ref 4P69R (Circuit dia included).

BARGAIN NICADS AAA SIZE 200MAH 1.2V PACK OF 10 £4.00 REF 4P92R, PACK OF 100 £30.00 REF 30P16R

FRESNEL MAGNIFYING LENS 83 x 52mm £1.00 ref BD827R.
12V 19A TRANSFORMER. Ex equipment but otherwise ok. Our price £20.00

ULTRASONIC ALARM SYSTEM. Once again in stock these units consist of a detector that plugs into a 13A socket in the area to protect. The receiver plugs into a 13A socket anywhere else on the same supply. Ideal for protecting garages, sheds etc. Complete system £25.00 ref B25P1 additional detectors £1.00 ref B11P1.

IBM AT KEYBOARDS Brand new 86 key keyboards £15.00 ref 15P612

AMSTRAD MP3.
UHF/VHF TV RECEIVER/CONVERTER
CONVERTS COLOUR MONITOR INTO A TV!

£9.00

286 MOTHER BOARDS. Brand new and tested complete with technical manual. £49.00 ref A49P1

UNIVERSAL BATTERY CHARGER. Takes AA's, C's, D's and PP3 nicads. Holds up to 5 batteries at once. New and cased, mains operated. £6.00 ref 6P36R.

IN CAR POWER SUPPLY. Plugs into cigar socket and gives 3.4, 5.6, 7.5, 9.0, and 12v outputs at 800mA. Complete with universal spider plug. £5.00 ref 5P167R.

RESISTOR PACK. 10 x 10 values (500 resistors) all 1/4 watt 2% metal film. £5.00 ref 5P170R.

CAPACITOR PACK 1. 100 assorted non electrolytic capacitors £2.00 ref 2P286R.

CAPACITOR PACK 2. 40 assorted electrolytic capacitors £2.00 ref 2P267R.

QUICK CUPPA? 12v immersion heater with lead and cigar lighter plug £3.00 ref 3P92R.

LED PACK. 50 red leds, 50 green leds and 50 yellow leds all 5mm £8.00 ref 8P52R

AMSTRAD 1640DD BASE UNITS

BRAND NEW AND CASED

TWO BUILT IN 5 1/4" DRIVES

MOTHER BOARD WITH 640K MEMORY

KEYBOARD AND MOUSE

MANUAL

OUR PRICE JUST

£79!!!!

BM PRINTER LEAD. (D25 to centronics plug) 2 metre parallel. £5.00 ref 5P186R.

COPPER CLAD STRIP BOARD 17" x 4" of. 1" pitch "vero" board. £4.00 a sheet ref 4P62R or 2 sheets for £7.00 ref 7P22R.

STRIP BOARD CUTTING TOOL. £2.00 ref 2P352R.

50 METRES OF MAINS CABLE £3.00 2 core black precut in convenient 2 m lengths. Ideal for repairs and projects. ref 3P91R.

4 CORE SCREENED AUDIO CABLE 24 METRES £2.00

Pre-cut in convenient 1.2 m lengths. Ref 2P365R

6 1/2" 20 WATT SPEAKER Built in tweeter 4 ohm £5.00 ref 5P205R

WINDUP SOLAR POWERED RADIO! FM/WM radio takes rechargeable batteries complete with hand charger and solar panel 14P200R



PC STYLE POWER SUPPLY Made by AZTEC 110v or 240v input. +5 @ 15A, +12 @ 5A, -12 @ 5A, -5 @ .3A. Fully cased with fan, on/off switch, IEC inlet and standard PC fyleads. £15.00 ref F15P4

ALARM PIR SENSORS Standard 12v alarm type sensor will interface to most alarm panels. £16.00 ref 16P200

MODEMS FOR THREE POUNDS!!

Fully cased UK modems designed for dial up system (PSTN) no data or info but only £3.00 ref 3P145R

TELEPHONE HANDSETS

Bargain pack of 10 brand new handsets with mic and speaker only £3.00 ref 3P146R

DATA RECORDERS

Customer returned mains battery units built in mic ideal for Computer or general purpose audio use. Price is £4.00 ref 4P100R

SPECTRUM JOYSTICK INTERFACE

Plugs into 48K Spectrum to provide a standard Atari type joystick port. Our price £4.00 ref 4P101R

ATARI JOYSTICKS

Ok for use with the above interface, our price £4.00 ref 4P102R

BENCH POWER SUPPLIES

Superbly made fully cased (metal) giving 12v at 2A plus a 6V supply. Fused and short circuit protected. For sale at less than the cost of the case! Our price is £4.00 ref 4P103R

BULL ELECTRICAL

250 PORTLAND ROAD HOVE SUSSEX

BN3 5QT TELEPHONE 0273 203500

MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

FAX 0273 23077

SPEAKER WIRE

Brown twin core insulated cable 100 feet for £2.00 REF 2P79R

DISC DRIVES

Customer returned units mixed capacities (up to 1.44M) We have not sorted these so you just get the next one on the shelf. Price is only £7.00 ref 7P1R (worth it even as a stripper)

MICROSCOPE 1200X MAGNIFICATION

Brand new complete with shrimp hatchery, shrimps, prepared slides, light etc. £29.00 ref 7P94R.

LIGHT ALARM SYSTEM

Small cased alarms that monitor a narrow beam area for sudden changes in light level. Complete with siren that sounds for a preset time when unit is triggered. £7.00 ref J7P1

JOYBALLS

Back in stock popular Commodore/Atari equiv (replace standard joystick) £5.00 ref JS8P

720K 3 1/2" DISC DRIVE

Brand new units made by JVC complete with tech info just £19.00!! ref J19P2

CAR BATTERY CHARGER

Brand new units complete with panel meter and leads. 6 or 12v output £7.00 ref J7P2

CUSTOMER RETURNED SPECTRUM +2

Complete but sold as seen so may need attention £25.00 ref J25P1 or 2 for £40.00 ref J40P4

CUSTOMER RETURNED SPECTRUM +3

Complete but sold as seen so may need attention £25.00 ref J25P2 or 2 for £40.00 ref J40P5

HEX KEYBOARDS

Brand new units approx 5" x 3" only £1.00 each ref CD42R

PROJECT BOX

51/2" x 31/2" x 1" black ABS with screw on lid. £1.00 ref CD43R

SCART TO SCART LEADS

Bargin price leads at 2 for £3.00 ref 3P147R

SCART TO D TYPE LEADS

Standard Scart on one end, Hi density D type on the other. Pack of ten leads only £7.00 ref 7P2R

OZONE FRIENDLY LATEX

250ml bottle of liquid rubber sets in 2 hours. Ideal for mounting PCB's fixing wires etc. £2.00 each ref 2P37R

QUICK SHOTS

Standard Atari compatible hand controller (same as joysticks) our price is 2 for £2.00 ref 2P380R

VIEWDATA SYSTEMS

Brand new units made by TANDATA complete with 1200/75 built in modem infra red remote controlled qwerty keyboard BT approved

Prestel compatible, Centronics printer port RGB colour and composite output (works with ordinary television) complete with power supply and fully cased. Our price is only £20.00 ref 20P1R

AC STEPDOWN CONVERTOR

Cased units that convert 240v to 110v 3" x 2" with mains input lead and 2 pin American output socket (suitable for resistive loads only) our price £2.00 ref 2P381R

CURLY CABLE

Extends from 8' to 6 feet! D connector on one end, spade connectors on the other ideal for joysticks etc (6 core) £1.00 each ref CD44R

COMPUTER JOYSTICK BARGAIN

Pack of 2 joysticks only £2.00 ref 2P382R

BUGGING TAPE RECORDER

Small hand held cassette recorders that only operate when there is sound then turn off 6 seconds after so you could leave it in a room all day and just record any thing that was said. Price is £20.00 ref 20P3R

NEW SOLAR ENERGY KIT

Contains 8 solar cells, motor, tools, fan etc plus educational booklet.

Ideal for the budding enthusiast! Price is £12.00 ref 12P2R

286 AT PC

286 MOTHER BOARD WITH 640K RAM FULL SIZE METAL CASE, TECHNICAL MANUAL, KEYBOARD AND POWER SUPPLY £139.00 REF 139P1 (no i/o cards or drives included) Some metal work req'd phone for details.

35MM CAMERAS Customer returned units with built in flash and 28mm lens for £8.00 ref 8P200

STEAM ENGINE Standard Mamod 1332 engine complete with boiler piston etc £30.00 ref 30P200

TALKING CLOCK

LCD display, alarm, battery operated.

Clock will announce the time at the push of a button and when the alarm is due. The alarm is switchable.

From voice to a cock crowing! £14.00 ref 14P200.R

HANDHELD TONE DIALLERS

Small units that are designed to hold over the mouth piece of a telephone to send MF dialling tones. Ideal for the remote control of answer machines. £5.00 ref 5P209R

AMAZING TALKING COINBOX!

Fully programmable talking, lockable coinbox BT approved, retail price £1.79 ours is just £2.99 ref J2P2.

ANSWER PHONES 1.5

Customer returned units with 2 faults one we tell you how to fix the other you do yourself! £18.00 ref J18P2 or 4 for £60.00 ref J60P3 BT approved (retail price £79.95 each)

COMMODORE 64 MICRODRIVE SYSTEM

Complete cased brand new drives with cartridge and software 10 times faster than tape machines works with any Commodore 64 setup.

The original price for these was £49.00 but we can offer them to you at only £25.00! Ref 25P1R

90 WATT MAINS MOTORS Ex equipment but ok. Good general purpose unit £9.00 ref 9P91

HIFI SPEAKER BARGAIN Originally made for TV sets they consist of a 4" 10 watt 4R speaker and a 2" 140R tweeter. If you want two of each plus 2 of our crossovers you can have the lot for £5.00 ref F5P2.

VIDEO TAPES E180 FIFTY TAPES FOR £70.00 REF F70P1

360K 5 1/4" Brand new drives white front. £20.00 ref F20P1

EMERGENCY LIGHTING SYSTEM

Fully cased complete with 2 adjustable flood lights. All you need is a standard 6v lead acid battery. Our price is just £10.00 ref J10P29

AMSTRAD 464 COMPUTERS

Customer returned units complete with a monitor for just £35.00 These units are sold as faulty and are not returnable.

IN SUSSEX? CALL IN AND SEE US!

EVERYDAY WITH PRACTICAL ELECTRONICS




INCORPORATING ELECTRONICS MONTHLY

ABC
CONSUMER PRESS

VOL. 21 No. 11 NOVEMBER 1992

The No. 1 Independent Magazine for Electronics,
Technology and Computer Projects

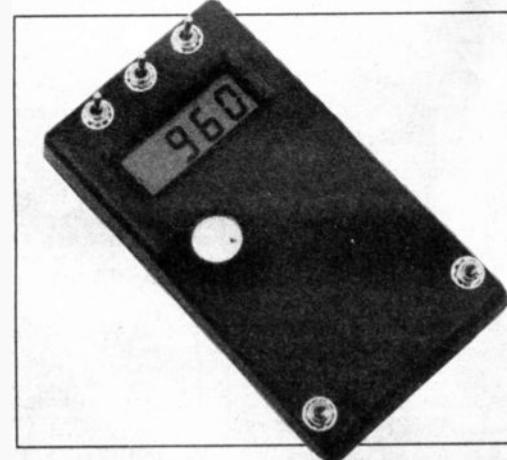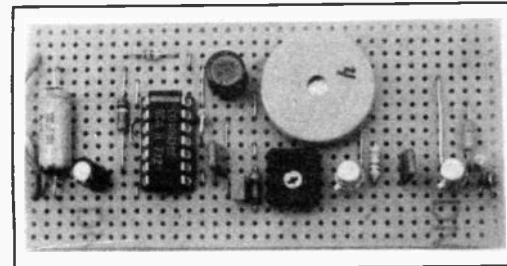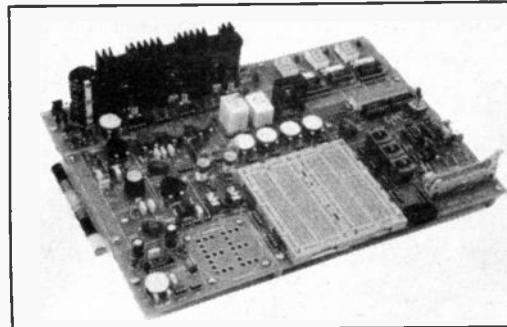ISSN 0262 3617
PROJECTS...THEORY...NEWS...
COMMENT...POPULAR FEATURES...



Projects

EPE ALTIMET by John Becker	694
A self-contained "pocket" altimeter for anyone who reaches a high.	
REACTION TIMER by T. R. de Vaux-Balbirnie	710
Test your reactions with this inexpensive unit	
BATTERY TO MAINS INVERTER	
DAUGHTER BOARD by Mark Daniels	718
A fix for the obsolete chip in the original design	
PERSONAL STEREO AMPLIFIER by I. A. Duncombe	720
An excellent easy to build design with various power supply options	
MINI LAB by Alan Winstanley and Keith Dye	736
A versatile test, development and prototyping board specially designed for Teach-In '93	
VIBRATION ALARM by M. G. Argent	742
Ingenious design that uses the piezo sounder as the vibration transducer	

Series

ALTERNATIVE ENERGY - 4	714
by T. R. de Vaux Balbirnie	
Power from water; tides, waves, hydro-electric and hydrogen	
TEACH-IN '93 - 1 by Alan Winstanley and Keith Dye	726
Our series for everyone learning about electronics and particularly GCSE and "A" level students	
TECHNIQUES - ACTUALLY DOING IT by Robert Penfold	740
Component substitution for project building	
CIRCUIT SURGERY by Mike Tooley	744
Clinic for constructors - your problems solved	
INTERFACE by Robert Penfold	747
Stepper motors; Pads-PCB program	
AMATEUR RADIO by Tony Smith G4FAI	756
What's in a name; Skilled involvement; Annual report; Numbers up	

Features

EDITORIAL	693
INNOVATIONS - EVERYDAY NEWS	702
News and new products from the world of electronics	
THE NEXT 21 YEARS by Barry Fox	704
A little crystal ball gazing - consumer product developments	
TOMORROW'S TECHNOLOGY by Ian Poole	705
Technological developments that could produce the products of the future	
SHOPTALK with David Barrington	724
Component buying for EPE projects	
ELECTRONICS VIDEOS	750
A range of educational videos	
DIRECT BOOK SERVICE	751
Selected technical books, our own books and all Babani books	
PRINTED CIRCUIT BOARD SERVICE	754
A special PCB SALE (while stocks last) - boards for EPE projects	
FREE WITH THIS ISSUE - GREENWELD 196 PAGE CATALOGUE	760
<i>Banded to the magazine</i>	
ADVERTISER'S INDEX	760

Readers Services • Editorial and Advertisement Departments 693

© Wimborne Publishing Ltd 1992. Copyright in all drawings, photographs and articles published in **EVERYDAY WITH PRACTICAL ELECTRONICS** is fully protected, and reproduction or imitation in whole or in part are expressly forbidden.



Our December '92 issue will be published on Friday, 6 November 1992. See page 683 for details.

THE ORIGINAL SURPLUS WONDERLAND!**COMPUTER SCOOPS****PC-AT 386 20-DX FULLY LOADED FOR £499!**

- 20 Mhz DX processor
- 2 megs RAM. Exp 10 meg
- 40 meg hard drive
- 1.2 meg 5-1/4" floppy
- 32K cache exp. 64K
- Installed VGA card
- Enhanced 102 key k/board
- Complete with MS-DOS 4.01
- 2 serial 1 parallel ports
- 8 free slots- 6 off 16 bit!

The MP386 quality made by Mitsubishi to last a lifetime! Brand new with all manuals and software plus Super PC-Quick Disk Accelerator for lightning disk access.

£499 (F)
Only.....

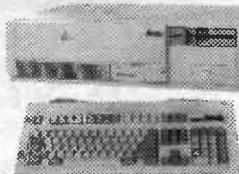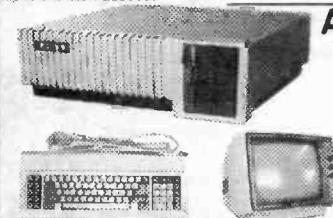**A COMPLETE IBM PC COMPAT SYSTEM FOR ONLY £99!!**

Just plug in and go - fully expandable - the Display PC-991 System supplied complete with 12" mono monitor, 84 key keyboard, 360K 5-1/4" floppy disk drive, 128K RAM, 2 serial and 1 parallel port plus DOS with manual. Many other features include 7 slot backplane, all metal case, 150 watt PSU and US made motherboard. In very good used condition with 90 day guarantee. At the unique price of:

Optional FITTED extras: 256K RAM £15; 640K RAM £39.
12" CGA colour monitor with card £89. 2nd 5-1/4" 720K floppy (or 360K if preferred) £29.95. 20 mbyte hard drive £99.

£99 (E)

FLOPPY DISK DRIVES

5 1/4 " from £22.95 - 3 1/2 " from £21.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported).

3.5" Panasonic JU364 720K*

3.5" Mitsubishi MF353C-L. 1.4 Meg. Laptops only*

3.5" Mitsubishi MF353C-D. 1.4 Meg. Non laptop*

5.25" Teac FD-55(36). 360K half height*

5.25" Teac FD-55(72). 720K half height.

* Data cable included in price.

Shugart 800/801 SS refurbished & tested

Shugart 851 double sided refurbished & tested

Mitsubishi M2894-63 double sided switchable

hard or soft sectors - BRAND NEW

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply! Ideal as exterior drives! £499.00(F)

End of line purchase scoop! Brand new NEC D2246 8" 85

megabyte of hard disk storage! Full CPU control and Industry standard SMD interface. Ultra hi speed transfer and access time leaves the good old ST506 interface standing. In mint condition and comes complete with manual. Only.....

£299(E)

THE AMAZING TELEBOX!

Converts your colour monitor into a
QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by manufacturers such as MICROVITTEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD and many more. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television or video channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Composite and RGB video outputs are located on the rear panel for direct connection to most makes of monitor. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

Telebox ST for composite video input monitors £32.95
Telebox STL as ST but with integral speaker £36.50
Telebox MB as ST with Multiband tuner VHF-UHF-Cable & hyperband For overseas PAL versions state 5.5 or 6mhz sound specification. £69.95

Telebox RGB for analogue RGB monitors (15kHz) £69.95
Shipping code on all Teleboxes is (B)

RGB Telebox also suitable for IBM multisync monitors with RGB analog and composite sync. Overseas versions VHF & UHF call. SECAM / NTSC not available.

No Break Uninterruptable PSU's

Brand new and boxed 230 volts uninterruptable power supplies from Densel. Model MUK 0565-AUAF is 0.5 kva and MUD 1085-AUBH is 1 kva. Both have sealed lead acid batteries. MUK are internal, MUD has them in a matching case. Times from interrupt are 5 and 15 minutes respectively. Complete with full operation manuals..... MUK.....£249 (F) MUD.....£525 (G)

POWER SUPPLIES

Power One SPL200-5200P 200 watt (250 w peak). Semi open frame giving +5v 35a, +5v 1.5a, +12v 4a (8a peak), -12v 1.5a, +24v 4a (6a peak). All outputs fully regulated with over voltage protection on the +5v output. AC input selectable for 110/240 vac. Dims 13" x 5" x 2.5". Fully guaranteed RFE. £85.00 (B)

Power One SPL130. 130 watts. Selectable for 12v (4A) or 24v (2A). 5v @ 20A, ±12v @ 1.5A. Switch mode. New. £59.95 (B)

Astec AC-8151 40 watts. Switch mode. +5v @ 2.5a, +12v @ 2a, -12v @ 0.1a, 6-1/4" x 4" x 1-3/4". New. £22.95 (B)

Greendale 19AB0E 60 watts. switch mode. +5v @ 6a, ±12v @ 1a, +15v @ 1a. RFE and fully tested. 11x 20 x 5.5cm. £49.95 (C)

Conver AC130. 130 watt hi-grade VDE spec. Switch mode. +5v @ 15a, -5v @ 1a, ±12v @ 6a, 27x 12.5 x 6.5cm. New. £49.95 (C)

Boshert 13090. Switch mode. Ideal for drives & system. +5v @ 6a, +12v @ 2.5a, -12v @ 0.5a, -5v @ 0.5a. £29.95 (B)

Farnell G6/40A. Switch mode. 5v @ 40a. Enclosed. £95.00 (C)

Farnell G24/5S. As above but 24v @ 5a. £65.00 (C)

BBC Model B APAM Board

£100 CASH FOR THE MOST NOVEL DEMONSTRATABLE APPLICATION!

WIN £100 CASH!

BBC Model B type computer on a board. A major purchase allows us to offer you the PROFESSIONAL version of the BBC computer at a parts only price. Used as a front end graphics system on large networked systems the architecture of the BBC board has so many similarities to the regular BBC model B that we are sure that with a bit of experimentation and ingenuity many useful applications will be found for this board!! It is supplied complete with a connector panel which brings all the I/O to 'D' and BNC type connectors - all you have to do is provide +5 and ±12 v DC. The APAM consists of a single PCB with most major IC's socketed. The IC's are too numerous to list but include a 6502, RAM and an SAA5050 teletext chip. Three 27128 EPROMS contain the custom operating system on which we have no data. On application of DC power the system boots and provides diagnostic information on the video output. On board DIP switches and jumpers select the ECONET address and enable the four extra EPROM sockets for user software. Appx. dims: main board 13" x 10", I/O board 14" x 3". Supplied tested with circuit diagram, data and competition entry form.

Only £29.95 or 2 for £53 (B)

SPECIAL INTEREST

Trio 0-18 vdc bench PSU. 30 amps. New

Fujitsu M3041 600 LPM band printer

DEC LS/02 CPU board

Rhode & Schwarz SBUF TV test transmitter

25-1000mhz. Complete with SBT2 Modulator

Calcomp 1036 large drum 3 pen plotter

Thurby LA 160B logic analyser

1.5kw 115v 60hz power source

Anton Pillar 400 Hz 3 phase frequency converter 75kW

Newton Derby 400 Hz 70 Kw converter

ADDS 2020 VDU terminals - brand new

Sekonic SD 150H 18 channel Hybrid recorder

HP 7580A 1A 8 pen high speed drum plotter

Kenwood DA-3501 CD tester, laser pickup simulator

BRAND NEW PRINTERS

Microline 183. NLQ 17x17 dot matrix. Full width.

Hyundai HDP-920. NLQ 24x18 dot matrix full width.

Quime LetterPro 20 daisy. Quime QS-3 interface.

Centronics 152-29 x 7 dot matrix. Full width.

Centronics 159-4 9 x 7 dot matrix. Serial. 9-1/2" width £99 (D)

Centronics 159-4 9 x 7 dot matrix. Serial. 9-1/2" width £99 (D)

HP Double Beam 100mhz Scopes

A Major purchase from a liquidated company enables us to offer you this superb Hewlett Packard quality HP1740A oscilloscope in HARDLY USED CONDITION at a fantastic price! Although exceptionally simple to use the full spec. of this scope would take up the whole page, so briefly here are a few of its features:

- 5 mV/dlv to 20v/dlv in 12 ranges
- Large 8 x 10cm CRT with scale illuminated
- 50ns/div to 2s/div 24 ranges (timebase)
- Third channel trigger view
- Dual Input impedance 50Ω/1 megΩ
- TV sync trigger
- Full delayed time base facilities
- Light weight fully portable, dual voltage

Fully guaranteed with full user manual.



Only £435.00 (F)

COLOUR MONITORS

SAVE £59 - ONLY £100 WHEN BOUGHT WITH THE 386 ABOVE!

14" Philips Model CM8873 VGA multisync all the way up to 34Khz with 640 x 480 resolution. This one has everything!

Two switches enable you to select CGA, EGA or VGA and digital/analog. Sound is also provided, with a volume control. There is also a special "Text" switch for word processing, spreadsheets and the like. Compatible with virtually all computers including IBM PC's, Amiga, Atari, BBC, Archimedes etc. Good used condition (possibly minor screen burns) 90 day guarantee. 15" x 14" x 12". Only..... £159 (E)

KME 12" high definition colour monitors. 0.28" dot pitch for superb clarity and modern two tone plastic styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13.5" x 12" x 11". Also works as quality TV with our RGB Telebox. Excellent used condition with 90 day guarantee. Beige and brown case. Only..... £149 (E)

Brand new Centronix 14" monitor for IBM PC and compatibles at a lower than ever price! Completely CGA equivalent. Hi-res Mitsubishi 0.42 dot pitch giving 669 x 507 pixels. Big 28 MHz bandwidth. A super monitor in attractive style moulded case. Full 90 day guarantee. Only..... £129 (E)

**20", 22" and 26" AV SPECIALS**

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & sound inputs. Attractive tract style case. Perfect for Schools, Shops, Disco, Clubs.

In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

CALL FOR PRICING ON NTSC VERSIONS!

Superb Quality 6 foot 40u

19" Rack Cabinets

Massive Reductions

Virtually New, Ultra Smart!

Less Than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvred back door and removable side panels. Fully adjustable internal fixing struts, ready punched

for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have

£ 470 ever sold. Racks may be stacked side by side and therefore require only two side panels or stand singly. Overall dimensions

£ 6500 are 77-1/2" H x 32-1/2" D x 22" W. Order as:

£ 650 Rack 1 Complete with removable side panels..... £275.00 (G)

£ 375 Rack 2 Less side panels..... £145.00 (G)

COOLING FANS

POA 3 Inch AC, 11/2" thick

£ 225 92 mm AC 230 v. 18mm thick

£ 2950 31/2" AC ETRI slimline. Only 1" thick.

£ 1850 31/2 Inch AC 230 v. 8 watts. Only 3/4" thick

£ 350 4 Inch AC 110/240v 11/2" thick.

10 Inch AC round, 31/2 thick. Rotron 110v

10 Inch As above but 230 vols

DC 1" thick. No. 812 for 6/12v. 814 24v.

60 mm DC 5 v. Papsit 105G 4w. 38mm. RFE.

£ 139 (D) £ 149 (D) £ 92 mm DC 12v. 12w 11/2" thick.

£ 149 (D) £ 149 (D) £ 99 mm DC 24v 8w. 1" thick.

£ 8.50 (B) £ 12.95 (B) £ 9.95 (B)

£ 12.95 (A) £ 19.95 (B) £ 19.95 (A)

£ 19.95 (A) £ 12.50 (B) £ 14.50 (B)

£ 14.50 (B)

1992 Summer Issue of **Display News** now available - send large SAE - PACKED with bargains!

DISPLAY ELECTRONICS

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. PO orders from Government, Universities, Schools & Local Authorities welcome - minimum order £30. Carriage charges (A)=£2.00, (B)=£3.75, (C)=£5.50, (D)=£11.50, (E)=£14.00 (F)=£18.00 (G)=Call. Scotland surcharge: call. All goods supplied subject to our standard Conditions of Sale and unless otherwise stated guaranteed for 90 days. All guarantees on a return to base basis. Rights reserved to change prices & specifications without prior notice. Orders subject to stock. Quotations willingly given for higher quantities than those stated. Bulk surplus always wanted for cash.



VERSATILE INFRA-RED REMOTE CONTROL

There are many applications for which constructors would like remote control. This versatile unit has been designed for application in a diverse range of equipment. Everything from one button operation of garage doors to 32 codes for three different receivers in one room, a total of 96 combinations.

The entire system, transmitter and receiver, uses just three i.c.s is compact and easy to build. Various output decoding and switching options are discussed and full detail of interfacing to our Mains Appliance Remote Control (MARC) system, published in 1990, are given. If you want remote control for almost anything this article should meet your needs.

BULL ELECTRICAL CATALOGUE

MIDI LEAD TESTER

This unit enables MIDI connecting leads to be quickly checked, and it will show up broken wires/connections or short circuits from one lead to another. In use it is much quicker and easier than using a multimeter or continuity checker. Checking leads with ordinary test equipment is easy enough provided you have four hands (two for the test leads and two for the plugs!) It should be possible to build the tester for less than the cost of ready made units, some of which seem to be rather crude in comparison to this device. It can help to greatly speed-up checks on a faulty MIDI system.

COMBINATION SWITCH

The Combination Switch or Combination Lock is a versatile project which may be used to unlock a door or switch off an alarm etc. The user's password is held in memory, which is protected by a back-up battery in case of power cuts. The password may be re-programmed by the user at any time, and up to 12 digits can be stored. If the wrong password is entered more than three times, a siren output is activated for a minute or so. There is also provision for a switch input so that the siren sounds if the switch is closed before the correct password has been entered. This may be used to detect a door or window being forced. The project may be fully integrated with an alarm system if required.

EVERYDAY WITH PRACTICAL ELECTRONICS

DECEMBER ISSUE PUBLISHED FRIDAY 6TH NOVEMBER.

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all of our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3-12V operation. 500m range.....£16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter Just 17mm x 17mm including mic. 3-12V operation. 1000m range.....£13.45

STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....£15.45

VTX500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range.....£16.45

VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range.....£19.45

HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range.....£19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range.....£22.95

SClx Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range.....£23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation.....£22.95

ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....£13.45

★★★ Specials ★★★

DLTX/BLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way dip switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits).....£50.95

Individual Transmitter DLTx.....£19.95

Individual Receiver BLRX.....£37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range.....£20.95

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 500m range.....£15.95

TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range.....£13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range.....£16.45

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation.....£22.95

CD400 Pocket Bug Detector/Locator

LED and piezo beeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation.....£30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate beeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation.....£50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range.....£40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range.....£40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m.....£35.95

QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Outpt to headphones. 60mm x 75mm. 9V operation.....£60.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCs.

DEPT. EE

THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY, NEAR AHERSTONE,
WARWICKSHIRE CV9 2LE

VISITORS STRICTLY BY APPOINTMENT ONLY

0827 714476



SUMA
DESIGNS

SPARKOMATIC 4 x 150 watt CAR AMPLIFIER



The SA3200 is our top of the line 4 Channel Amplifier which is extremely well specified. It is very powerful and versatile and features separate bass and treble controls which gives the user the possibility of reducing bass response to the front speakers and adding treble for better stereo imaging. The bass response can then be increased to the rear speakers which are usually larger and capable of offering better reproduction. The SA3200 features a bridge operation switch which offers the possibility of using the amplifier in 4, 3 or 2 channel mode. The 3 channel mode is ideal for installations where rear deck speakers are used in combination with a separate subwoofer.

- 4 x 150 Watts max ● 4 x 80 Watts into 4 Ohms at less than 0.5% THD
- 2 x 80 Watts plus 1 x 160 Watts at less than 0.5% THD
- 2 x 160 Watts into 4 Ohms at less than 0.5% THD
- Separate bass and treble controls for front and rear channels
- Separate sensitivity controls for front and rear channels
- 2, 3 or 4 channel operation
- Heavy duty power wires
- Glass blasted aluminium heatsink
- High current capacity

£251.65 plus £7 p&p

SPARKOMATIC 2 x 150 watt CAR AMPLIFIER

The SA1500 is a very highly specified 2 Channel Amplifier with built-in sub bass crossover. The SA 1500, which is ideal for powering medium sized subwoofers, will also operate in bridge mode as a 150 Watt mono amplifier.

- 2 x 150 Watts max, into 4 Ohms
- 2 x 70 Watts per channel at 0.5% THD
- Bridge mode operation
- Sensitivity adjustment ranging from 100mV to 1V
- Heavy duty power wires
- Built-in sub bass crossover
- Glass blasted aluminium heatsink
- High current capacity

£117.65 plus £6.50 p&p

SPARKOMATIC 80 watt CAR POWER AMPLIFIER

The AMP 7000 produces high power at low distortion. The amplifier accommodates low level, high level and high power radio speaker inputs. The response is linear and extends beyond the capability of all music sources. This compact unit mounts easily and its quick connect terminals accept RCA or straight wire input terminals. Power rating 2 x 40 watt per channel. MMP 2 x 20 watt at 10% THD response 20Hz-20kHz. Size 160mm x 130mm x 45mm.

£32.95 plus £3.50 p&p

11 BAND COMPONENT GRAPHIC EQUALIZER FOR CARS

This neat unit connects between the line output of your car stereo and your power amplifiers so that you are able to adjust the sound as in a studio compensating for soft furnishing and sound reflections from glass, also it has a sub-woofer output to drive a separate amplifier for that extra deep bass sound. FEATURES: 2 channel inputs 4 channel outputs via phono sockets, CD input via 3.5mm jack 11 band graphic. SPECIFICATION RANGE 20Hz-60kHz THD 0.05%, S/N RATIO 85dB. EQ FREQUENCIES 60Hz, 120Hz, 250Hz, 380Hz, 500Hz, 750Hz, 1kHz, 2kHz, 4kHz, 8kHz, 16kHz (boost cut of ±12dB) SIZE 178mm x 25mm x 140mm. **£32.70 postage £1.80**

EMINENCE 4Ω PROFESSIONAL USA MADE IN CAR CHASSIS SPEAKERS

All units are fitted with big magnets "Nomex" Voice coil NOT ALUMINIUM, "Nomex" is very light and can stand extremely high temperatures, this mixture makes for high efficiency and long lasting quality of sound. V6 6½" 200W Max Range 50Hz-3kHz £34.40 V6 8" 300W Max Range 45Hz-3kHz £39.45 V10 10" 400W Max Range 33Hz-4kHz £44.45 V12 12" 400W Max Range 35Hz-3kHz £45.95 BOSS 15" 800W Max Range 35Hz-4kHz £79.90 KING 18" 1200W Max Range 20Hz-1kHz P.O.A. Postage £3.85 per speaker.

Build your own Bazooka sub woofer tube to suit Eminence car speakers. 10mm thick fibre supplied with grille and clamp terminals finished in black vinyl.

Eminence U10, Size 270mm x 700mm

£25.95 £3.50 p&p

Eminence U12 Size 320mm x 710mm

£29.95 £3.50 p&p



MAIL ORDER BARGAIN PACKS

No.	Qty. per pack	
MO20	1	30W dome tweeter by Eagle/Japan Made size 90mm x 66mm
MO21	1	60W Hifi tweeter made for Jamo UK size 90mm sq.
MO22	2	30 watt 8 ohm Hifi chassis speakers. Made for Hitachi UK midi systems, size 125mm sq. with large 70mm magnet
MO23	2	Pod Car Speakers. Moulded in black plastic with 15 watt 10cm Goodmans unit fitted
MO23A	1pr	40 watt Car Speakers made for Roadstar of Switzerland. Fitted with dual polypropylene cone and foam rubber surround. Big 70mm magnet for good base response. Supplied with grills fixing screws and cable. Size 13cm, weight 1.5Kg
MO24	2	Audax JBL 40-100watt dome tweeters. High performance 10mm Ferrofluid cooled horn loaded unit for load distortion and high output. Supplied with 1st order crossover, spec. 40 watts at 3kHz, 100 watt at 8kHz; size 51mm x 51mm x 16.5mm. Ideal for car use
MO25	2	33000µF 10V d.c. can type computer grade quality electrolytic. UK made
MO25A	1	47µF 385V d.c. can type electrolytic. Size 350mm x 250mm. UK made by Phillips
MO26	2	6800µF 100V d.c. can type electrolytic size 45mm x 25mm
MO27	3	2200µF 25V d.c. can type electrolytic size 45mm x 25mm
MO28	1	15000µF 40V d.c. can type 23A electrolytic size 113mm x 50mm
MO29	1	33000µF 16V 27A can type electrolytic size 113mm x 50mm
MO30	20	Assorted Variable trimmers
MO31	4	Tuning capacitors 2-gang dielectric type
MO32	2	10k + 10k wirewound precision potentiometer
MO33	8	Rotary potentiometers
MO34	5	100k multiturn Varicap type tuning potentiometer with knob size 45mm x 5mm
MO35	200	Carbon resistors
MO36	2	LARGE VU meters. Japan Made
MO37	1	Large Tuning meter 125µA-0.125µA size 55mm x 47mm
MO38	1	Dual VU meter 280µA f.s.d., size 80mm x 42mm x 15mm
MO39	5	Coaxial Aerial Plugs, all metal type
MO40	6	Fuseholders, chassis mounting for 20mm size fuses
MO41	4	Fuseholders, in-line type for 20mm size fuses
MO42	20	5 Pin Din 180°chassis mount sockets
MO43	6	Double phone sockets
MO44	5	6.35mm (¼") Stereo Jack sockets
MO45	4	6.35mm (¼") Mono Jack Plugs
MO46	12	Coax Sockets chassis mount
MO47	2	Case handles plated U-shape, size 97mm x 50mm
MO48	30	Mixed control knobs
MO49	1	Cassette tape transport mechanism, belt-drive, top loading, six piano key operation with knobs, stereo record/replay, erase heads, heavy fly-wheel
MO50	1	Hifi stereo pre-amp. module. Input for CD Tuner record player with diagram. Made by Mullard
MO51	2	AM/FM tuner head modules'. Made by Mullard
MO52	3	AM I.F. modules'. Made by Mullard
MO53	1	FM stereo decoder module with diagram. Made by Mullard
MO54	3	UHF Varicap tuned tuner heads unboxed, untested but complete. Made by Mullard
MO55	1	25V d.c. 150mA Mains adaptor in neat plastic box, size 80mm x 55mm x 47mm ETRI Brand new 80mm Cooling Fan. Five bladed A.C. impedance corrected motor on a cast aluminium chassis. Size 80mm x 40mm. Voltage 115v a.c. working 130mA. Japanese made.
MO55A	1	£5.95 + £1.40 p&p, TWO for £11.20 UK post paid
MO56	2	6V-0V-6V 4VA p.c.b. mount mains transformer 240V input, size 42mm x 33mm x 35mm. UK Made
MO57	25	4 Volt miniature wire-ended bulbs
MO57A	1	SRBP Copper Clad Printed Circuit Board. Size 410mm x 360mm x 2mm £3.65 + 75 p&p
MO58	2	Mono cassette tape heads. Japan Made
MO59	2	Sonotone stereo cartridge with 78 and LP Styl. Japan Made
MO60	8	Bridge rectifiers 1amp 24Volt
MO61	10	OC44 transistors. Remove paint from top and it becomes a photo electric cell (ORP12)
MO63	6	14 watt output transistors. Three complementary pairs in T066 case (replacement for AD161 + 162)
MO64	5	5 watt Audio i.c. No. TBA800
MO65	5	Motor Speed Control i.c.
MO66	1	Digital DVM Meter i.c. Made by Plessey, with diagram
MO67	4	7-Segment 0.3in i.e.d. display (red)
MO68	1	Tape Deck i.c., with record/replay switching. No. LM1818, with diagram
MO69	2	Ferrite Rod. High grade with LW, SW & MW coils, size 140mm x 10mm
MO70	1	Moving coil dynamic, handheld, ball microphone. Ross Electronics customers returns (no warrantee)

No.	Qty. per pack	
MO71A	1	Analogue Multimeter. Ross Electronics customers returns (no warrantee)
		£3.90 + 90p p&p
MO72	1	WW II EX WD headphone, A BIT OF NOSTALGIA, low impedance
		£3.50 + £1.20 p&p
MO73	1	Koss Stereo Headphones on ear. Lightweight design, vari-fitting ear-cups with contour cushions, 36in. cord. 3.5mm + 6.35mm Jack plug adaptor
		£3.50 + £1 p&p
MO74	2	Tone dialling keypad, uses services that require DTMF tone signals for a rotary dial pulse phone, size 90mm x 55mm x 12mm
		£11.00 + 70p p&p
MO75	1	100 yard roll of single screened quick splice cable, good quality British Made
		£4.50 + £2 p&p
MO76	1	100 yard 3-core 3 amp cable, coded brown, blue and green/yellow
		£4.20 + £2 p&p
MO80	2	Solar Powered Wooden Kits. Easy to build aeroplane, with revolving propeller, and an old time gramophone with music chip. Supplied with glue, solar cells, electronics and pre-cut panels.
		One of each for £12.00 + £1.50 p&p
MO81	1	Bump and Go Space Ship Kit with motor, wheels, p.c.b. wire and diagram. An ideal introduction for youngsters into the world of electronics and mechanics; goes all the way to the moon on two AA batteries
		£8.95 + £1 p&p
MO82	1	Filofax Personal Organiser Radio/Calculator. This neat little unit simply fits inside your filofax so you can listen to AM Radio with earphone or use it as a solar powered 8-digit calculator. Punched with six holes to fit all personal organisers. UK Made under ½ price
		£8.95 + £1 p&p
MO83	1	Video Sender. With this handy unit you can transmit output of your home video, video camcorder or satellite equipment over the air to a receiving television within a range of 100ft. Simply connect the video and audio output of your equipment into this unit, and a 10-13.8V d.c. power supply - extra £3.75
		£11.75 + £2 p&p
MO84	1	Multi-band radio. Listen to air traffic control, aircraft, radar, public utilities VHF 54-176MHz + CB 1-80 with built in squelch control
		£17.95 + £2 p&p
MO85	2	AM, FM, LW Ross Pushbutton Radio. With this neat unit you can easily tune in to five pre-set stations of your choice without fiddling or fuss, runs off six C-cell batteries or 240V mains. Output 400mW, volume and tone control. Size 230mm x 150mm x 65mm
		£23.00 + £3.65 p&p
MO86	1	(As above)
MO87	1	Pushbutton Kit 30 + 30 Watt. An easy to build amplifier with a good specification. All components mount on single p.c.b. punched and back-printed for ease, case ready drilled finished in black vinyl with matching scale and knobs. Inputs for: CD/AUX tape 1; tape II; tuner and MC phono. Controls: bass; treble; volume; balance; mode and power switch. Featured project in <i>Everyday Electronics</i> , April 1989 issue; reprint with kit
		£40.00 + £3.65 p&p

All items prefixed with MO number MAIL ORDER only or can only be collected by prior appointment from address below. Where p&p not stated please add £3.65 per order for postage and carton charge.

★ VHF RADIO TRANSMITTERS

2 Watt transmitter kit, supplied with fibre glass PCB, all components, diagrams, ready for you to build. 12-24V d.c.

£8.50 + £0.70 pp

* We are only able to supply these devices if customers provide a written and signed disclaimer that they will not be used in the UK. Please include this with your order as they are not licensable in the UK.

RTVC	
376 EDGWARE ROAD LONDON NW2 1EB	MAIL ORDER TERMS, POSTAL ORDERS and/or CHEQUES with orders. Access & Visa accepted.
	Nett monthly accounts to Schools, Colleges and P.L.C. only.
	Overseas readers write for quote on delivery.
	Please cross all cheques and postal orders "Account Payee Only" and make payable to RTVC Ltd.
	Phone 071 723 3462 Fax 071 723 3467

electronize electronic kits

NEW! MOTOR SPEED CONTROL (FOR RADIO CONTROLLED MODELS)

- ★ Standard radio control input - no servo required.
 - ★ Smooth forward and reverse P.W.M. speed control.
 - ★ Runs any motor up to 10 amp. continuous current.
 - ★ 35 amp. short term stall rating.
 - ★ Low loss Power MOSFET switching.
 - ★ Neutral and span adjustment.
 - ★ Optional voltage regulator for single battery operation. (Type 43VR)
- Type 43X (2 to 24 v motors) parts kit £17.75 Assembled £25.95
 Type 43VR (7 to 24 v motors) parts kit £19.45 Assembled £27.95

MICRO-PRESSURE CAR ALARM

This new type of alarm is triggered by a unique pressure sensing system. As any vehicle door is opened air is drawn out, causing a minute drop in air pressure. A sensor detects this sudden pressure change and sets off the alarm. A sophisticated arrangement of electronic filters and timers provide features to match more expensive ultra-sonic systems.

- ★ Operates on all doors and tailgate - no switches needed.
- ★ Automatically armed 40 seconds after leaving vehicle.
- ★ 10 second entry delay with audible warning. (0.5 second available)
- ★ Sounds horn or siren intermittently for 30 seconds - then re-arms.
- ★ Easy fitting - only 3 wires to connect - no holes to drill.
- ★ Controlled by Ignition switch, hidden switch or coded remote control below.

MICRO-PRESSURE ALARM parts kit £15.95 Assembled £22.35

Also available :-

VOLT DROP CAR ALARM	parts kit £14.90	Assembled £20.95
I.R. CODED TRANSMITTER	parts kit £13.95	Assembled £17.95
I.R. CODE RECEIVER	parts kit £21.35	Assembled £26.55
120dB PIEZO SIREN (optional for the above alarms)	parts kit £11.95	Assembled £11.95
MICRO-PRESSURE TRIGGER	parts kit £10.95	Assembled £14.95
EXTENDED CDI IGNITION	parts kit £22.75	Assembled £28.45

All the above include cable, connectors and clear easy to follow instructions.
 All kits include case, PCB, everything down to the last washer, even solder.
 All prices are mail order discount and include post, packing and VAT on U.K. orders. Same prices apply to all European countries. For delivery outside Europe please add £3.

Telephone orders accepted with VISA or ACCESS payment.

Order direct (please quote ref. EE6) or send for more details from:-

ELECTRONIZE DESIGN

Tel. 021 308 5877

2 Hillside Road, Four Oaks, Sutton Coldfield, B74 4DQ

LIVE IN THE FUTURE

YOU CAN MAKE IT HAPPEN WITH HOME AUTOMATION COMPONENTS FROM US

A range of components making use of the X-10 power line carrier protocol - Remote control lighting/appliance modules, timers, computer interfaces, telephone diallers, motorised curtain tracks, powered radiator valves.

E1400e	Enerlogic completely programmable home automation controller. PC download.	£349.95
CP290	X-10 Computer Interface. Control up to 128 timed remote module events. PC download.	£ 79.95
MT522	Timer control of up to 4 remote modules	£ 29.95
LM565	Lamp remote control module-to 250W.	£ 19.95
AM566	Appliance remote control module-to 13A	£ 19.95
WS567	Wall switch remote control module-to 300W	£ 19.95
H1145	Powertrack curtain control motor	£ 59.99
BOOK	Understanding & Installing Home Systems - How to Automate Your Home.	£ 22.95

Shipping £3.75 orders under £90 (book post free)
 ACCESS/VISA/MASTERCARD accepted

Full Details from -

SMART HOUSE SYSTEMS LTD
 3 Buchanan Street, Largs, Ayrshire KA30 8PP

Tel: 0475 672589

JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail Order Prices.

SK18 Soldering Kit. £17.28

Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid.



ADAMIN Miniature Iron £7.90


nylon handle with finger grip. Interchangeable bits available. Fitted with 2.4mm. 240v 12w

Possibly smallest mains iron in the world. Ideal for fine work. Slim

'L' Series Lightweight Irons. 12w £8.34

High efficiency irons for all electronic hobby work. Non-roll handles with finger guards.

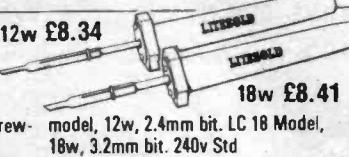Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12



Soldering Iron

Stands 3&4

£6.85



Designed specially for LITESOLD irons.

Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits.

No 4 stand for ADAMIN miniature Iron

No 3 stand for LA12 and LC18 Irons.

De-Solder Pumps £8.03

High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy

thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

Prices include p&p and VAT. Send order with Cheque/PO. Ring for Access/Visa sales

LIGHT SOLDERING DEVELOPMENTS LTD.
 97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 081 689 0574

HENRY'S

NEW STOCKS AND SPECIAL OFFERS

ASTEC SW mode power supply

Three pin mains socket input, on/off switch. Output +5 volt 3.75 amp, +12 volt 1.5 amp, -12 volt 0.4 amp. 115-230 V AC/DC input. Size 7.0 x 5.3 x 2.5 ins with circuit. £12.95 incl VAT



'POCKET' TEST INSTRUMENTS

(with case) Prices Incl VAT

• 135 Satellite Signal Finder. FS + Compass	£29.95
• 1065 Digital Lux Meter - 3 Ranges	£61.00
• 120N Sound Level Meter - 2 Ranges	£45.00
• 200A 20Hz to 200 MHz 2 Range Freq. Counter	£104.56
• 500A 20 Hz to 150 KHZ. Audio Gen. Switch Freq.	£47.95
• 510 Digital Capacitance Meter upto 2000 mfd	£51.00
KDM16 TR Grid Dip. 1.5 to 250 MHZ	£62.00
*Y225. VHS Video Head Tester	£38.95
H265. Component Tester - Add to any Scope	£41.00
*ST300. AC Clamp Meter. 0/300A. 0/600V. 0/1Kohm SPECIAL PURCHASE	£25.95
265. 0/2000 amp AC Clamp - Add to Dmm	£15.95
202. 0/20000 Amp AC/DC Version	£53.95
*320P. Wallet Type Digital Multimeter	£21.95



IN STOCK AUDIO-ELECTRONICS

(Details in colour catalogue and supplements)

FULL RANGE OF TEST INSTRUMENTS

- Scopes ■ Counters ■ Power Supplies

- Generators ■ Meters ■ Hameg ■ Metex

- Blockstar ■ Testlab ■ Thurlby ■ Thordar

SECURITY AND COMMUNICATIONS

- Alarms ■ Lighting ■ Detectors ■ Intercomms

- Doorphones ■ CCTV and CB Radios

AUDIO EQUIPMENT

- For Public Address

- Hi-Power Car Systems ■ Disco and Hi-Fi

- Speakers ■ Amplifiers ■ Mics ■ Effects etc

COMPONENTS AND TOOLS

- Large Range Inc.

- Fans ■ Large Value Caps ■ Relays

- Transistors

ACCESSORIES

- For TV ■ Video ■ Hi-Fi

- Telephones CB etc etc.



Open 6 days a week for callers and telephone orders
 UK Carr/Packins £2.05 - Post Free any two items

COLOUR CATALOGUE
 with supplements
 Send £4 (UK). £6 (export). £2 for callers
 FREE updates for your 91/92 catalogue send large SAE
 (34p stamp)
 FREE catalogues with trade prices for trade and education - write or fax.


HENRY'S 404 Edgware Rd, London W2 1ED
 Instruments, Audio, Equipment 071-724 3564
 Security, CCTV, Communications 071-724 0323
 Components, Service Aids 071-723 1008
 QUANTITY, EXPORT AND EDUCATION DISCOUNTS.
 OFFICIAL ORDER SALES Tel: 071-258 1831. Fax: 071-724 0322

INTRODUCTORY
PRICE JUST £179

SCHEMATIC DRAWING FOR WINDOWS

NEW

ISIS ILLUSTRATOR combines the high functionality of our DOS based ISIS products with the graphics capabilities of Windows 3. The result is the ability to create presentation quality schematics like you see in the magazines. ILLUSTRATOR gives you full control of line widths, fill styles, fonts, colours and much more. When the drawing is complete, transferring it to your WP or DTP program is simply a matter of cutting and pasting through the Windows Clipboard.

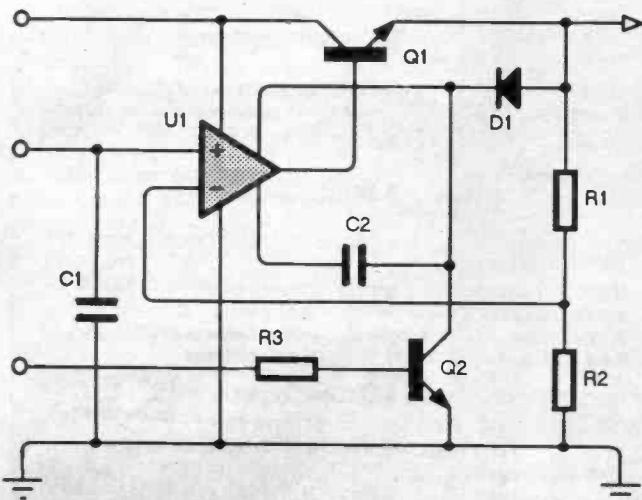

Features

- Runs under Windows 3.0 or 3.1.
- Full control of drawing appearance including line widths, fill styles, fonts, colours and more.
- Curved or angular wire corners.
- Automatic wire routing and dot placement.
- Fully automatic annotator
- Comes complete with component libraries; edit your own parts directly on the drawing.
- Full set of 2D drawing primitives + symbol library for logos etc.
- Output to Windows printer devices including POSTSCRIPT and colour printers.
- Loads ISIS SUPERSKETCH and DESIGNER files directly.

CADPAK - Two Programs for the Price of One.

ISIS SUPERSKETCH

A superb schematic drawing program for DOS offering Wire Autorouting, Auto Dot Placement, full component libraries, export to DTP and much more.

Only
£79

Exceptionally easy and quick to use. For example, you can place a wire with just two mouse clicks - the wire autorouter does the rest.

PCB II

High performance manual PCB layout package for DOS. Many advanced features including curved tracks, auto track necking, DXF export, Gerber and NC file generation, Gerber viewing and more.

Graphical User Interface with intuitive "point and do" operation gives unparalleled ease of use.

ISIS and ARES - The Professional's Choice

ISIS DESIGNER

from £275

ISIS DESIGNER forms the ideal front end of your CAD system, providing schematic capture, netlisting, bill of materials and electrical rules checks.


DESIGNER+ adds advanced design management features and is one of the most advanced DOS based schematics programs on the market.

ARES

from £275

The ARES range of advanced PCB design products links with ISIS DESIGNER and other schematics programs. Working from a netlist, ARES helps you get it right first time with each connection automatically verified against the schematic.

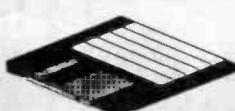ARES AUTOROUTE adds multi-strategy autorouting, whilst for the ultimate in performance, ARES 386 goes up to 400% faster with unlimited design capacity.



Call us today on 0274 542868 or
fax 0274 481078 for a demo pack.
Combination, multi-copy and educational
discounts available. Prices exc P&P and VAT.

14 Marriner's Drive, Bradford, BD9 4JT.

WHETHER ELECTRONICS IS YOUR HOBBY OR YOUR LIVELYHOOD . . . YOU NEED THE MODERN ELECTRONICS MANUAL



EVERYTHING YOU NEED TO KNOW ABOUT ELECTRONICS!

If the fascinating and fast-changing world of electronics is your livelihood, your study subject or simply your passion, the new revised edition of **THE MODERN ELECTRONICS MANUAL** is the reference work for you to have at your side.

The base manual contains information on the following subjects:

BASIC PRINCIPLES: symbols, components and their characteristics, passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, operational amplifiers, timers, physics for electronics.

CIRCUITS TO BUILD: construction techniques, radio, telephony, microcomputing, measuring instruments, vehicle electronics, security, audio, power supplies, electronic music (over 25 different projects).

REPAIRS AND MAINTENANCE: radio, television, audio/hi-fi, telephones.

DATA: diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors. The manual also covers **Safety, Specialist Vocabulary with Abbreviations and Suppliers.**

OVER 1,000 pages, A4 format weighing over 3.5kg.

Now – at last – the most comprehensive reference work ever produced at a price you can afford, the new revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.

Over 1,000 pages of well-organised and clearly explained information is brought to you by an expert editorial team whose combined experience ensures the widest coverage.

Regular supplements to this unique publication, each around 160 pages, mean that you will always be kept abreast of the latest developments from the UK, USA and Europe as they occur

ALL-IN-ONE AND EASY-TO-USE

A sturdy ring-binder allows you to use the manual on your workbench. The looseleaf format also means you can slot in the regular updates as they arrive – so all your information is there at a glance.

EXTENSIVE GLOSSARY

Should you come across a technical word, phrase or abbreviation you're not familiar with – simply turn to the glossary included in the manual and you'll find a comprehensive definition in plain English.

REGULAR UPDATES

Unlike a book or encyclopedia, the manual is a living work – continuously updated by new material. Recent or upcoming supplements include radio, superconductors, electric motors, basic electronic building blocks for beginners which can be joined together to construct elaborate circuits, filters, IBM PC and compatibles (including use of PC cards). Supplements are sent to you approximately every two months.

Each supplement contains approximately 160 pages – all for only £23.50 + £2.50 p&p. You can of course return any supplement which you feel is superfluous to your needs.

RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular articles in our updating supplements. Our unique updating system is based on answers from readers request questionnaires. Through this service you are able to let us know exactly what information you require in your manual. You can also contact the editor directly in writing if you have a specific technical request or query relating to the manual.

ASSEMBLING ...

There's nothing to beat the satisfaction of creating your own project. From basic principles to circuit-building, the manual describes clearly, with appropriate diagrams, how to assemble radios, loudspeakers, amplifiers, micro-computers and measuring instruments.

The new revised edition of The Modern Electronics Manual contains practical, easy-to-follow instructions for building and programming your own computer. It shows you how to make fun gadgets such as a remote control door opener and a digital rev. counter for your car. It also tells you how to construct useful devices like test gear, security and baby alarms – plus – many more popular devices.

**Wimborne Publishing Ltd., 6 Church St,
Wimborne, Dorset BH21 1JH
Tel: 0202 881749 Fax: 0202 841692**



THE MODERN ELECTRONICS MANUAL

New Revised Edition of Basic Work: Now contains over 1,000 pages of information.

Regular Updates: Approximately 160-page supplements of additional information which are forwarded to you immediately on publication. These are billed separately and can be discontinued at any time.

Presentation: Durable looseleaf system in large A4 format (197mm x 210mm)

Price of the Basic Work: £39.95 + £5.50 p&p (to include a recent supplement).

YES please send me on 10 days free approval THE MODERN ELECTRONICS MANUAL. If I decide to keep the manual, I shall then pay only £39.95 plus £5.50 postage and packing at the end of the 10 days approval period. I shall also receive the appropriate Updating Supplements several times a year. These are billed separately and can be discontinued at any time.

FULL NAME
(PLEASE PRINT)

ADDRESS

POSTCODE

I AM OVER 18

SIGNATURE

(Parent or guardian must sign if under 18)

ORDER FORM

Simply complete and return the order form to the following address

**The Modern
Electronics Manual
Wimborne Publishing Ltd
6 Church Street
Wimborne Dorset BH21 1JH**

OVERSEAS ORDERS: All overseas orders must be prepaid but are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the manual return it within a month for a refund of the purchase price (you do have to pay the postage). Add the following amounts to the price of the manual to cover postage:

EIRE £10.50 (air mail only)
EUROPE (including C.I.S.) £21.00 (air mail only)
MIDDLE EAST/FAR EAST/INDIA
AFRICA/SOUTH AFRICA
SOUTH AMERICA } £20 surface
REST OF THE WORLD £25 surface, £31 air } £37 air

Note surface mail can take around 8 weeks to some parts of the world. Each manual weighs about 4.5kg when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

BARGAINS - Many New Ones This Month

THIS MONTH'S SNIP is a Japanese-made 12V d.c. battery operated, brushless axial fan, 93mm square, its optimum is 12 but it performs equally well at only 6V and its current then is only 100mA so it could be made into a hand-held dry battery-operated cooler. Or, on your desk operated by a P.S.U. or in the car using the lighter socket. Snip price only £4, Order Ref. 4P65. Mains power unit to operate this at variable speeds £2, Order Ref. 2P3.

ANOTHER SNIP. Extra lightweight stereo headphones. Superior sound quality as these were made for a world famous airline. Adjustable headband makes these extra comfortable and they come complete with washable foam earpieces. Suitable for use with all types of cassette players and radios, good long lead terminating with 3.5mm jack plug. Yours for only £1 per pair, Order Ref. 898.

F.M. CORDLESS RADIO MIKE hand-held battery-operated professional model, has usual shaped body and head and is tuneable to transmit and be picked up on the F.M. band of any radio. Yours for only £8.50, Order Ref. 8.5P1.

4 MORE SPEAKERS: Order Ref. 1.5P11 is Japanese-made 6½", 8 ohm, rated at 12W max. This is a very fine reproducer. The makers are SANYO. Yours for £1.50.

Order Ref. 900 is another Far East made 6½", 4 ohm, 12W max speaker. Very nicely made, using Japanese Hitachi tools and technique, only £1.

Order Ref. 896 is 6½", 6 ohm, 10W, exceptionally good sounder and yours for only £1.

Order Ref. 897 is another 8 ohm speaker rated at 5W but its unusual feature is that it has a built-in tweeter. Price still only £1.

MOVEMENT ALARM goes off with slightest touch, ideal to protect car, cycle, doorway, window, stairway, etc. etc. Complete with Piezo shrieker, ready to use. Only £2 (PP3 battery not supplied). Order Ref. 2P282.

DRY BATTERIES CAN BE RECHARGED but not with a normal charger. It must be a periodic current reversal type. We can supply the kit, with data, for £9, Order Ref. 9P10.

SOLAR ENERGY EDUCATIONAL KIT an ideal present for electronics students. It shows how to make solar circuits and electrical circuits, how to increase the voltage current, how to use solar power to work a radio, calculator, cassette player and to charge nicad batteries. The kit comprises 8 solar cells, one solar motor, fan blades to fit motor and metal frame to hold it to complete a free-standing electric fan. A really well written instruction manual makes this a lovely little present. Price £8, Order Ref. 8P12B.

PROJECT BOX a first-class, Japanese two-part moulding size 95mm x 66mm x 23mm. Held together by 2 screws, this will hold a PP3 battery and a PCB and is ideal for many projects. To name just a few, the washer bottle monitor, the Quiktest and the model railway auto signal, described in September's issue of E.E. This is nicely finished and very substantial. You get 2 for £1, Order Ref. 876.

HOLD IT MAGNETIC BASE embedded in a circular metal shallow disc, diameter approximately 65mm (2½"), is the most powerful magnet. We have yet to find anyone who can remove this with their fingers. Ideal for adding extra shelves inside a metal case or to glass without drilling. Its uses, in fact, are innumerable. Price £2 each, Order Ref. 2P296.

WANT A SPARE 3" DISC DRIVE FOR YOUR AMSTRAD? We have, unused and believed O.K., Amstrad 3" disc drives that are all complete but need the front bezel. It shouldn't be too difficult a job to take the bezel off your old one and fit it to this and you should then have a new and perfect 3" disc drive which, as you probably know, are virtually unobtainable now. Price £15 each, Order Ref. 15P45. Or, if you haven't got a drive from which you can remove the bezel, we can supply one, with good bezel but with some other fault for only £5, Order Ref. 5P193. This may seem a lot to pay for the bezel but, remember, you will have a complete set of spare parts for your 3" drive so it really is a bargain.

OPD DUAL MICRO DRIVE UNIT. This is a twin unit, each unit having its own motor, record/playback head and PCB with all electronics. In addition to being a direct replacement in the OPD, this can also be used with the Spectrum or the QL. We have a copy of the procedure necessary and will gladly supply a photostat of this if you require it when you purchase the unit. The price is £5, Order Ref. 5P194.

12V 2A MAINS TRANSFORMER upright mounting with mounting clamp. Price £1.50, Order Ref. 1.5P8.

AM/FM RADIO CHASSIS with separate LCD module to display date and time. This is complete with loudspeaker and is mains powered. The price of the AM/FM radio chassis with LCD module is £3.50, Order Ref. 3.5P5. All purchasers will receive connection.

2, 3 AND 4 WAY TERMINAL BLOCKS the usual grub screw types. Parcel containing a mixture of the 3 types, giving you 100 ways for £1, Order Ref. 875.

12/24V DC SOLENOID. The construction of this is such that it will push or pull as the plunger is a combined rod and piston. With 24V this is terrifically powerful but is still quite good at 12V and, of course, it can be operated by any intermediate voltage. Price £1, Order Ref. 877.

2M 3-CORE LEAD terminating with flat pin instrument socket, £1, Order Ref. 879. Ditto but with plug on the other end so that you could use this to extend an instrument lead. £1.50, Order Ref. 1.5P10.

MULTI-CORE CABLES all with 8A 230V cores so suitable for disco and other special lighting effects. With earthable woven screen and thick PVC outer. 3 core, 30p per metre, 16 core, 50p per metre, 18 core, 80p per metre, 25 core, £1 metre and 36 core, £1.50 per metre.

ULTRA THIN DRILLS Actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack, Order Ref. 797B.

YOU CAN STAND ON IT! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10½" x 4½" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2, Order Ref. 2P283B.

BUILD YOUR OWN NIGHT LIGHT, battery charger or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket. We have two cases, one 3½" x 2¼" x 1¼" deep, £1 each, Order Ref. 845. The other one is 2½" x 2¼" x 1¼" deep, 2 for £1, Order Ref. 565.

SAFETY LEADS curly coil so they contract but don't hang down. Could easily save a child from being scalded. 2 core, 5A, extends to 3m, £1, Order Ref. 846. 3 core, 13A, extends to 1m, £1 each, Order Ref. 847. 3 core, 13A, extends to 3m, £2 each, Order Ref. 2P290.

ULTRA SONIC TRANSDUCERS 2 metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref. 1.5P4.

100W MAINS TRANSFORMERS normal primaries 20-0-20 at 2.5A. or 30V at 3.5A, £4, Order Ref. 4P24. 40V at 2.5A, £4, Order Ref. 4P59. 50V at 2A, £4, Order Ref. 4P60.

PHILIPS 9" HIGH RESOLUTION MONITOR black & white in metal frame for easy mounting, brand new still in maker's packing, offered at less than price of tube alone, only £15, Order Ref. 15P1.

16 CHARACTER 2-LINE DISPLAY screen size 85mm x 36mm, Alpha-numeric LCD dot matrix module with integral micro processor made by Epson, their Ref. 16027AR, £8, Order Ref. 8P48.

INSULATION TESTER WITH MULTIMETER internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges. AC/DC volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50, with leads, carrying case £2 extra, Order Ref. 7.5P4.

MAINS 230V FAN best make "PAPST" 4½" square, metal blades, £8, Order Ref. 8P8.

2MW LASER Helium neon by Philips, full spec. £30, Order Ref. 30P1. Power supply for this in kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref. 69P1.

1/3 HP 12V MOTOR - THE FAMOUS SINCLAIR C5 brand new, £15, Order Ref. 15P8.

SOLAR CHARGER holds 4 AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3.

FERRITE AERIAL ROD 8" Long x ¾" diameter, made by Mullard. Complete with 2 coil formers. 2 for £1, Order Ref. 832B.

AIR SPACED TRIMMER CAPS 2-20 pf ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B.

FIELD TELEPHONES just right for building sites, rallies, horse shows, etc., just join two by twin wire and you have two way calling and talking and you can join into regular phone lines if you want to. Ex British Telecom in very good condition, powered by batteries (not included) complete with shoulder slung carrying case, £9.50, Order Ref. 9.5P2.

MAINS ISOLATION TRANSFORMER stops you getting "to earth" shocks. 230V in and 230V out. 150watt upright mounting, £7.50, Order Ref. 7.5P5 and a 250W version is £10, Order Ref. 10P79.

MINI MONO AMP on PCB. Size 4" x 2" with front panel holding volume control and with spare hole for switch or tone control. Output is 4 watt into 4 ohm speaker using 12V or 1 watt into 8 ohm using 9V. Brand new and perfect, only £1 each, Order Ref. 495.

AMSTRAD POWER UNIT 13.5V at 1.9A encased and with leads and output plug, normal mains input £6, Order Ref. 6P23.

ATARI 65XE at 65K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £19.50, Order Ref. 19.5P5/B.

80W MAINS TRANSFORMERS two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each.

PROJECT BOX size approx 8" x 4" x 4½" metal, sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74.

12V SOLENOID has good ½" pull or could push if modified, size approximately 1½" long x 1" square, £1, Order Ref. 232.

BUILDING YOUR OWN PSU, battery charger, night light, or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket? We have two cases, one 3½" x 2¼" x 1¼" deep, £1 each, Order Ref. 845. The other one is 2½" x 2¼" x 1¼" deep, 2 for £1, Order Ref. 565.

EXPERIMENTING WITH VALVES don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A, £5, Order Ref. 5P167.

15W 8 OHM 8" SPEAKER & 3" TWEETER made for a discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57.

3V SOLAR PANEL price £3, Order Ref. 3P99B.

3 GANG .0005 MFD TUNING CONDENSER beautifully made by Jackson Brothers and current list price is probably around £20. Yours for £5, Order Ref. 5P189.

BT TELEPHONE LEAD 3m long and with B.T. flat plug ideal to make extension for phone, fax, etc. 2 for £1, Order Ref. 552.

WATER PUMP very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74. Ditto but with a single outlet. Same price & order ref. Please specify which one you require.

0-1MA FULL VISION PANEL METER 2½" square, scaled 0-100 but scale easily removed for re-writing, £1 each, Order Ref. 756.

PCB DRILLS 12 assorted sizes between .75 and 1.5mm, £1 the lot, Order Ref. 128.

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing.

Orders over £25 post free.

M & B ELECTRICAL SUPPLIES LTD

12 Boundary Road, Hove,

Sussex BN3 4EH

Telephone (0273) 430380

Fax or phone (0273) 410142



SHOP OPEN 9-5 Mon-Fri 9-2 Sat --- OFFICIAL ORDERS WELCOME --- KIT LIST - S.A.E

VERSATILE BBC INTERFACE

A comprehensive interface which allows the BBC computer to be connected safely to a wide range of input and output devices. Two leads connect the interface to the User Port and the Printer port. The interface connects to the real world via standard screw terminal blocks. Up to 16 outputs (all via plug-in single pole change over relays - 8 supplied) and 8 fully protected inputs. L.e.d. status monitoring is provided on all input and output lines. The interface requires an independent 12 Volt supply.

KIT 844.....£51.95

STEPPING MOTOR DRIVER & INTERFACE

A single board stand-alone stepping motor driver with built in oscillator and speed control circuits. A computer is not required with this board which will drive most unipolar 4 phase motors. Variable Acceleration, Speed, and Direction, may be controlled in HALF STEP, FULL STEP, and ONE PHASE modes. Up to 35V and 1.5A per phase. L.e.d. mimic display. Connector is provided for a computer port. The Kit includes our MD35 motor.

KIT 843 £29.95 - BUILT £44.95

DIGITAL LCD THERMOSTAT

A versatile thermostat using a thermistor probe and having an I.c.d. display. MIN/MAX memories, -10 to 110 degrees celsius, or can be set to read in Fahrenheit. Individually settable upper and lower switching temperatures allow close control, or alternatively allow a wide 'dead band' to be set which can result in substantial energy savings when used with domestic hot water systems. Ideal for greenhouse ventilation or heating control, aquaria, home brewing, etc. Mains powered, 10A SPCO relay output. Punched and printed case.

KIT 841.....£29.95

4 CHANNEL LIGHT CHASER

A 1000W per channel chaser with Zero Volt Switching, Hard Drive, and full inductive load capability. Built-in mic. and sophisticated 'Beat Seeker' circuit - chase steps to music, or auto when silent. Variable speed and mic. sensitivity control, L.e.d. mimic on front panel. Switchable for 3 or 4 channels. P552 output socket. Suits Rope Lights, Pin Spots, Disco, and Display lighting.

KIT 833.....£32.13

SUPERHET LW MW RADIO

At last an easy to build SUPERHET AM radio kit. Covers Long and Medium waves. Built in loudspeaker with 1 Watt output. Excellent sensitivity and selectivity provided by ceramic IF filter. Simple alignment and tuning without special equipment. Supplied with pre-drilled transparent front panel and dial, for interesting see-through appearance.

KIT 835.....£17.16

ACOUSTIC PROBE

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches, and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers, and noise parkers!

KIT 740.....£19.98

PESST SCARER

Produces high power ultrasound pulses. L.e.d. flashes to indicate power output. Battery powered 9-12V, or mains adaptor £2.00 EXTRA.

KIT 812.....£14.81

KIT HIGHLIGHT

DIGITAL CAPACITANCE METER KIT 493


This has been one of Magenta's best ever kits. It provides clear readings of capacitance values from a few pF up to thousands of μ F. It is ideal for beginners as there is no confusion over the placing of the decimal point, and it allows obscurely marked components to be identified quickly and easily. Quartz controlled accuracy of 1%, large clear 5 digit display and high speed operation make it a very useful instrument for production and testing departments. The kit is now supplied with a punched and printed front panel as well as the case, all components and top quality printed circuit board. When assembled it looks a really professional job. For a limited time this kit is offered at a new low price.



SPECIAL KIT PRICE £34.95
(reduced from £49.95)

MOSFET VARIABLE BENCH POWER SUPPLY 25V 2.5A

Our own high performance design. Variable output Voltage from 0 to 25V and Current limit from 0 to 2.5A. Capable of powering almost anything. Two panel meters indicate Voltage and Current. Fully protected against short-circuits. The variable Current limit control makes this supply ideal for constant current charging of NICAD cells and batteries. A Power MOSFET handles the output for exceptional ruggedness and reliability. Uses a toroidal mains transformer.

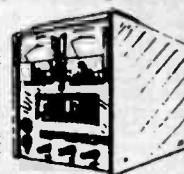

£56.82

8 CHANNEL LIGHT SHOW PROGRAMMABLE SEQUENCER

A superbly finished kit with pre-drilled case and screen printed front panel, this kit uses a microcontroller IC to generate over 100 light sequences. Programs include 3 and 4 channel versions so that existing light units can be used as well as 8 channel arrangements. NEW output design provides foolproof operation with pinspots and other difficult loads. Space in memory for 10 user programs up to 16 steps long. Keypad

KIT 838.....£57.17

BAT DETECTOR

An excellent circuit which reduces ultrasound frequencies between 20 and 100 kHz to the normal (human) audible range. Operating rather like a radio receiver the circuit allows the listener to tune-in to the ultrasonic frequencies of interest. Listening to Bats is fascinating, and it is possible to identify various different types using this project. Other uses have been found in industry for vibration monitoring etc.

KIT 814.....£21.44

QUICK CAPACITANCE TESTER

A low cost hand-held audio/visual unit which can identify short, open and working capacitors quickly and with a minimum of fuss. Also gives indication of leakage current. An ideal kit for beginners, built on a single printed circuit board which has large copper areas used as test pads. Only a minimum of wiring is needed. 21.e.d.s and a piezo transducer provide the output indication.

KIT 834.....£10.34

IONISER

A highly efficient mains powered Negative Ion Generator that clears the air by neutralising excess positive ions. Many claimed health benefits due to the ioniser removing dust and pollen from the air and clearing smoke particles. Costs virtually nothing to run and is completely safe in operation. Uses five point emitters.

KIT 707.....£17.75

ACTIVE I.R. BURGLAR ALARM

This alarm is useful where ordinary 'passive' (pir) detectors are not suitable. It works by detecting disturbances to its own short wave infra-red beam. Output is via mains rated relay contacts. Built in timer, and mains transformer.

KIT 700.....£40.74

SEE OUR FULL RANGE OF KITS, BOOKS, TOOLS, AND COMPONENTS IN OUR CATALOGUE

HAMEG HM203-7 20 MHz DUAL TRACE OSCILLOSCOPE & COMPONENT TESTER

Western Europe's best selling oscilloscope - It is RELIABLE, HIGH PERFORMANCE, & EASY TO USE. Sharp bright display on 8 x 10cm screen with internal graticule. A special extra feature is the built-in component tester which allows capacitors, resistors, transistors, diodes and many other components to be checked. The quality of this instrument is outstanding, and is supported by a two year parts and labour warranty.

If you are buying an oscilloscope - this is the one. - It costs a fraction more than some other 20 MHz 'scopes but it is far superior. Supplied with test probes, mains lead, and manual.

**£338.00 + £59.15 VAT Includes FREE Next-day delivery
(Cheques must be cleared)**

EDUCATIONAL BOOKS & PACKS

ADVENTURES WITH ELECTRONICS

The classic book by Tom Duncan used throughout schools. Very well illustrated, ideal first book for age 10 on. No soldering. Uses an S.DEC breadboard.

Book & Components £28.95. Book only £6.25

FUN WITH ELECTRONICS

An Usborne book, wonderfully illustrated in colour. Component pack allows 6 projects to be built and kept. Soldering is necessary. Age 12 on, or younger with adult help. **Book & Components £20.88. Book only £2.95**

30 SOLDERLESS BREADBOARD PROJECTS

A more advanced book to follow the others. No soldering. Circuits cover a wide range of interests.


Book & Components £20.69. Book only £2.95

DC MOTOR/GEARBOXES

Ideal for robots, buggies, and many other mechanical projects. Min. plastic gearbox with 1.5-4.5V DC motor. 6 ratios can be set up.

Small type MGS...£4.77

Large type MGL...£5.58

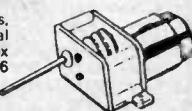

STEPPING MOTORS

For computer control via MD35 $\frac{1}{4}$ - standard 48 standard 4 pole unipolar steps per rev.....£12.99 drivers.

MD38 - miniature 48 MD200 - miniature 200 steps per rev.....£9.15 steps per rev.....£17.10

74LS Series
4000 Series
TRANSISTORS
LINEAR ICs
SOLDERING IRONS
RF CONNECTORS

74LS00	£0.44	4000	£0.17	2N1613	£0.31	BC184L	£0.08	BD441	£0.41	CA311E	£0.28	Antex Soldering irons	BNC Solder Plug
74LS01	£0.14	4001	£0.17	2N1711	£0.26	BC186	£0.33	BD442	£0.41	CA324	£0.23	M 12 Watt	BNC Crimp Plug
74LS02	£0.14	4002	£0.17	2N1893	£0.29	BC204C	£0.72	BD534	£0.47	CA555	£0.22	C 15Watt	BNC Solder Skt
74LS03	£0.14	4006	£0.32	2N2218A	£0.28	BC206B	£0.72	BD535	£0.48	CA741CE	£0.18	G 18Watt	BNC Chassis Skt
74LS04	£0.14	4007	£0.17	2N2219A	£0.25	BC207C	£0.72	BD536	£0.65	CA747CE	£0.39	C 17Watt	BNC Chassis Skt
74LS05	£0.14	4008	£0.31	2N2222A	£0.16	BC208	£0.72	BD646	£0.52	ST4 STAND	£2.96	XS 25Watt	BNC UHF socket
74LS08	£0.14	4009	£0.19	2N2646	£0.80	BC209A	£0.72	BD648	£0.52	CA3046	£0.37	35Watt Gas Iron	RND UHF socket
74LS09	£0.14	4010	£0.23	2N2904A	£0.25	BC212	£0.08	BD650	£0.53	CA3080	£0.72	Desolder Pump	F Plug RG58
74LS10	£0.14	4011	£0.16	2N2905A	£0.23	BC212L	£0.08	BD707	£0.42	CA3130	£0.98	Antistatic Pump	F Plug RG6
74LS107	£0.23	4012	£0.16	2N2907	£0.20	BC212LB	£0.08	BD807	£0.80	CA3130E	£0.98	25SWG 0.5kg Solder	N Plug RGB
74LS109	£0.21	4013	£0.17	2N2926	£0.16	BC213	£0.08	BDX32	£1.78	CA3140	£0.56	18SWG 0.5kg Solder	N Socket RGB
74LS11	£0.17	4014	£0.30	2N3053	£0.27	BC213LC	£0.08	BDX33C	£0.46	CA3240	£1.22	1mm 3yds Solder	BNC Crimp Pliers
74LS112	£0.21	4015	£0.31	2N3054	£0.90	BC214	£0.08	BDX34C	£0.50	Desolder Braid	£0.87	PCB EQUIPMENT	£15.50
74LS113	£0.21	4016	£0.18	2N3055	£0.62	BC214L	£0.08	BDX53C	£0.47	ICL7621	£1.70	UV EXPOSURE UNIT	£67.38
74LS114	£0.21	4017	£0.25	2N344F	£0.50	BC237B	£0.09	BDX64C	£0.50	ICM7555	£0.43	PL259 11mm	£0.85
74LS12	£0.14	4018	£0.27	2N3702	£0.09	BC238C	£0.09	BF180	£0.31	ICM7556	£0.96	RND UHF socket	£0.68
74LS122	£0.31	4019	£0.19	2N3703	£0.10	BC239C	£0.10	BF182	£0.31	LM301A	£0.25	SOR UHF socket	£0.40
74LS123	£0.31	4020	£0.31	2N3704	£0.10	BC251	£0.13	BF185	£0.31	LM348N	£0.31	FERRIC CHLORIDE CRYSTALS (0.5kg)	£2.45
74LS125	£0.21	4021	£0.31	2N3705	£0.10	BC252	£0.13	BF194	£0.19	LM351N	£0.36	TIN PLATING POWDER (90g)	£8.33
74LS126	£0.21	4022	£0.32	2N3706	£0.10	BC253B	£0.21	BF195	£0.19	LM353	£0.41	ETCH RESIST PEN	£0.72
74LS13	£0.14	4023	£0.16	2N3771	£1.51	BC267B	£0.34	BF244	£0.35	PCB POLISHING BLOCK	£1.84		
74LS132	£0.21	4024	£0.21	2N3772	£1.79	BC207	£0.10	BF257	£0.33	PCB EQUIPMENT			
74LS133	£0.18	4025	£0.15	2N3819	£0.40	BC308	£0.10	BF337	£0.36	BREADBOARD			
74LS136	£0.16	4026	£0.40	2N3820	£0.58	BC327	£0.10	BF355	£0.38	64mm x 25mm	£0.27		
74LS138	£0.24	4027	£0.18	2N3904	£0.10	BC328	£0.10	BF423	£0.13	64mm x 95mm	£0.90		
74LS139	£0.25	4028	£0.27	2N3905	£0.10	BC337	£0.10	BF451	£0.19	64mm x 127mm	£1.20		
74LS14	£0.18	4030	£0.17	2N3906	£0.10	BC338	£0.10	BF459	£0.29	64mm x 431mm	£3.22		
74LS145	£0.25	4031	£0.70	2N4036	£0.31	BC414C	£0.13	BF469	£0.36	95mm x 127mm	£1.50		
74LS147	£1.26	4033	£0.56	2N5296	£0.57	BC441	£0.40	BF29X	£0.29	mounting plate & posts	£6.88		
74LS148	£0.70	4034	£1.24	2N5321	£0.57	BC461	£0.40	BF8X4	£0.31	PCB POLISHING BLOCK			
74LS149	£0.14	4035	£29	2N6107	£0.60	BC463	£0.29	BF8X5	£0.31	COPPER BOARD (G. Fibre)			
74LS151	£0.25	4040	£0.29	AC126	£0.30	BC478	£0.32	BFY50	£0.29	PHOTO RESIST BOARD (G. Fibre)			
74LS153	£0.25	4041	£0.31	AC127	£0.30	BC479	£0.32	BFY51	£0.26	PHOTO RESIST BOARD (Paper)			
74LS154	£0.70	4042	£0.22	AC128	£0.28	BC490	£0.24	BFY52	£0.28	MINIATURE TOGGLE SWITCHES			
74LS155	£0.25	4043	£0.28	AC187	£0.37	BC516	£0.22	BSW66	£1.35	3PDT 250v 6.4mm φ mounting			
74LS156	£0.25	4044	£0.31	AC188	£0.37	BC517	£0.20	BU126	£1.32	SPST Toggle	£0.58		
74LS157	£0.25	4046	£0.31	AC197	£0.38	BC517	£0.20	BU205	£1.41	SPDT Toggle	£0.60		
74LS158	£0.25	4047	£0.25	AC199	£1.67	BC527	£0.20	BU208A	£1.34	SPDT CO Toggle	£0.64		
74LS160	£0.32	4048	£0.31	AC214	£0.32	BC528	£0.20	BU624	£1.40	DPDT Toggle	£0.68		
74LS161	£0.32	4049	£0.20	BC107	£0.14	BC546C	£0.20	BU625	£1.40	DPDT CO Toggle	£0.76		
74LS162	£0.32	4050	£0.20	BC107B	£0.15	BC548C	£0.20	BU626	£1.37	(biased)	£1.20		
74LS163	£0.32	4051	£0.25	BC108	£0.12	BC549C	£0.10	BU606	£1.06	DPDT CO Toggle (biased 1 way)	£1.20		
74LS164	£0.26	4052	£0.25	BC108A	£0.14	BC550C	£0.08	BU8X4	£0.77	DPDT mini slide	£0.15		
74LS165	£0.48	4053	£0.25	BC108C	£0.14	BC556A	£0.08	IRF540	£1.60	Rotary Wafer 1P...12W, 2P...6W,			
74LS167	£0.30	4054	£0.56	BC109	£0.14	BC557C	£0.08	IRF740	£1.63	SPST Toggle	£0.58		
74LS174	£0.24	4055	£0.30	BC109C	£0.15	BC558C	£0.08	IRF740	£1.63	SPDT Toggle	£0.60		
74LS175	£0.24	4056	£0.29	BC114	£0.41	BC559C	£0.08	IRF740	£1.63	DPDT CO Toggle	£0.64		
74LS190	£0.32	4056	£0.18	BC115	£0.41	BC560B	£0.09	IRF740	£1.63	DPDT CO Toggle (biased)	£0.68		
74LS191	£0.32	4057	£0.25	BC116	£0.41	BC567	£0.14	NE567N	£0.36	DPDT CO Toggle (biased 1 way)	£0.68		
74LS192	£0.14	4067	£0.17	BC118	£0.41	BC568	£0.10	NE552	£0.80	DPDT mini slide (biased)	£0.15		
74LS193	£0.24	4069	£0.20	BC132	£0.36	BC638	£0.21	NE553	£0.66	DPDT CO Toggle (biased 1 way)	£0.15		
74LS194	£0.24	4072	£0.25	BC135	£0.36	BC639	£0.21	NE554	£0.66	DPDT CO Toggle (biased 1 way)	£0.15		
74LS195	£0.24	4073	£0.25	BC141	£0.27	BC7Y2	£0.20	NE555	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS21	£0.14	4075	£0.17	BC142	£0.31	BC135	£0.20	NE556	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS22	£0.14	4076	£0.30	BC143	£0.34	BC136	£0.20	NE557	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS23	£0.14	4077	£0.17	BC154	£0.36	BD137	£0.20	NE558	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS240	£0.32	4081	£0.14	BC157	£0.12	BD139	£0.23	NE559	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS241	£0.32	4082	£0.17	BC158	£0.12	BD140	£0.24	NE560	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS242	£0.32	4085	£0.28	BC160	£0.28	BD150C	£0.42	NE561	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS243	£0.32	4086	£0.26	BC170	£0.16	BD165	£0.42	NE562	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS244	£0.32	4089	£0.55	BC170B	£0.16	BD187	£0.39	NE563	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS245	£0.33	4093	£0.15	BC171	£0.11	BD201	£0.40	NE564	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS247	£0.32	4094	£0.31	BC171B	£0.16	BD201	£0.40	NE565	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS251	£0.24	4095	£0.56	BC172	£0.13	BD202	£0.40	NE566	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS257	£0.24	4097	£0.17	BC172B	£0.13	BD203	£0.40	NE567	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS258	£0.24	4098	£0.31	BC177	£0.17	BD204	£0.40	NE568	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS262	£0.14	4099	£0.38	BC178	£0.17	BD222	£0.40	NE569	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS264	£0.14	4102	£0.38	BC179	£0.17	BD223	£0.38	NE570	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS27	£0.14	4103	£0.27	BC182L	£0.08	BD237	£0.32	NE571	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS273	£0.32	4104	£0.26	BC182LB	£0.08	BD238	£0.32	NE572	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS279	£0.25	4105	£0.34	BC183	£0.08	BD240B	£0.37	NE573	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS30	£0.14	4106	£0.25	BC183L	£0.08	BD243B	£0.50	NE574	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS32	£0.21	4107	£0.40	BC183LB	£0.08	BD244A	£0.53	NE575	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS37	£0.24	4108	£0.40	DIAC	£0.20	BD246	£0.16	NE576	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS393	£0.25	4109	£0.24	VOLTAGE REGULATORS	£0.37	ELECTROLYTIC RADIAL CAPACITORS	£0.10	NE577	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS395	£0.26	4109	£0.24	5mm Red LED	£0.09	NE578	£1.11	NE578	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS396	£0.62	4109	£0.31	5mm Green LED	£0.10	NE579	£1.11	NE579	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS397	£0.26	4109	£0.31	5mm Yellow LED	£0.10	NE580	£1.11	NE580	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS398	£0.26	4109	£0.31	5mm Orange LED	£0.10	NE581	£1.11	NE581	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS399	£0.62	4109	£0.31	5mm Red LED	£0.08	NE582	£1.11	NE582	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS400	£0.26	4109	£0.31	5mm Green LED	£0.12	NE583	£1.11	NE583	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS401	£0.26	4109	£0.31	5mm Orange LED	£0.13	NE584	£1.11	NE584	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS402	£0.26	4109	£0.31	5mm Yellow LED	£0.13	NE585	£1.11	NE585	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS403	£0.72	4109	£0.31	5mm Green LED	£0.13	NE586	£1.11	NE586	£1.11	DPDT CO Toggle (biased 1 way)	£0.15		
74LS404	£0.76	4109	£0.31	5mm Orange LED</td									

EVERYDAY WITH PRACTICAL ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

VOL. 21 No. 11 NOVEMBER '92

HISTORIC

As regular readers will know this is a historic issue which not only represents 21 years of *Everyday Electronics* but also sees the merger of *Practical Electronics* with *Everyday Electronics*. We have tried to expand the magazine to meet the needs of both sets of readers and we hope and believe that this issue represents the best possible electronics magazine for hobbyists, students and technicians alike.

Never before have we encompassed such a wide spread of articles with plenty to read on new technology and general developments, plus a good range of constructional projects. However we do not intend to rest there, please let us know what you think of the magazine; especially if we are failing to cover something which interests you. We cannot promise to meet every requirement but we can try.

DEMAND

We are anticipating a very heavy demand for this issue and have printed 43,000 copies in an effort to make sure everybody who wants one gets one. However we do want to make sure you can also get your copy next month. So why not take out a subscription (see page 738), or fill in the blue "Shop Save" card stitched into this issue. This card will also get you into our free draw for one of two Maplin multimeters, each worth £30 (UK readers only). Just fill in the card and hand it to your newsagent, there is no obligation to buy but he will keep an issue for you to look at - what have you got to lose?

There has been so much pressure on space this month that we have had to leave out one or two items. These include our *Readout* (EE) or *Wavelengths* (PE) readers letters page. We hope to fit this in next month so keep those letters coming, we should have room for a lively selection.



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £20. Overseas: £26 (£43.50 airmail). Cheques or bank drafts (**in £ sterling only**) payable to Everyday with Practical Electronics and sent to EPE Subscriptions Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: 0202 881749. Subscriptions start with the next available

issue. We accept Access (MasterCard) or Visa payments, minimum credit card order £5.

BACK ISSUES

Certain back issues of *EVERYDAY ELECTRONICS* and *PRACTICAL ELECTRONICS* are available price £2.00 (£2.50 overseas surface mail) inclusive of postage and packing per copy - **£ sterling only please**. Visa and Access (MasterCard) accepted, minimum credit card order £5. Enquiries with remittance, made payable to Everyday with Practical Electronics, should be sent to Post Sales Department, Everyday with Practical Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH Tel: 0202 881749. In the event of non-availability one article can be photostated for the same price. *Normally sent within seven days but please allow 28 days for delivery. We have sold out of Jan, Feb, Mar, Apr, June, Oct, & Dec. 88, Mar & May 89 & Mar 90 Everyday Electronics and can only supply back issues from Jan 92 to Oct 92 of Practical Electronics.*

BINDERS

Binders to hold one volume (12 issues) are available from the above address for £5.95 (£6.95 to European countries and £8.00 to other countries, surface mail) inclusive of post and packing. *Normally sent within seven days but please allow 28 days for delivery.*

Payment in £ sterling only please.

Visa and Access (MasterCard) accepted, minimum credit card order £5. Send card number and card expiry date with your name and address etc.

Editorial Offices:

EVERYDAY with PRACTICAL ELECTRONICS EDITORIAL,
6 CHURCH STREET, WIMBORNE,
DORSET BH21 1JH
Phone: Wimborne (0202) 881749
Fax: (0202) 841692. DX: Wimborne 45314.
See notes on Readers' Enquiries below - we regret that lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:

EVERYDAY with PRACTICAL ELECTRONICS
ADVERTISEMENTS,
HOLLAND WOOD HOUSE, CHURCH LANE,
GREAT HOLLAND, ESSEX CO13 0JS.
Phone/Fax: (0255) 850596

Editor: MIKE KENWARD

Secretary: PAM BROWN

Deputy Editor: DAVID BARRINGTON

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Editorial: WIMBORNE (0202) 881749

**Advertisement Manager:
PETER J. MEW, Frinton (0255) 850596**

**Classified Advertisements:
Wimborne (0202) 881749**

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self addressed envelope and international reply coupons.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data or answer queries on projects that are more than five years old.


ADVERTISEMENTS

Although the proprietors and staff of *EVERYDAY with PRACTICAL ELECTRONICS* take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.

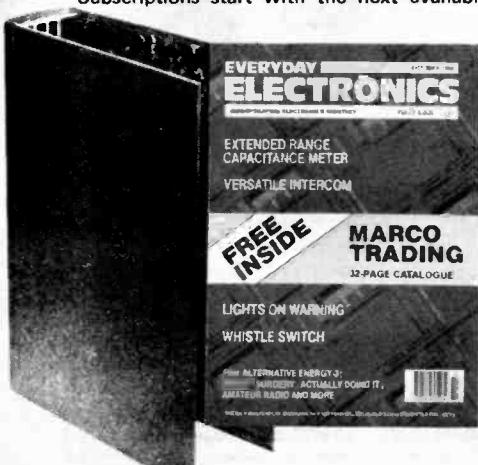

EPE ALTIMET

JOHN BECKER

Measure up to the outdoor high-life with this handy pocket altimeter

ANYONE with an interest in the ups and downs of outdoor activities, walkers, climbers, cyclists, balloonists, hang-gliders, pot-holers and so on, will find their curiosity further satisfied through using the EPE Altimet. It is a handheld unit which uses two sensors, a DPM (digital panel meter) chip and an I.C.D. (liquid crystal display) to monitor and display data about altitude in metres and feet, barometric pressure in millibars, and temperature in Fahrenheit or Celsius.


The maximum readout range is ± 1999 metres relative to sea level. To facilitate setting-up, access to a digital multimeter, a good thermometer and a nearby hill is recommended!

PRESSING FACTS

The earth is surrounded by an envelope of air extending to around 500 miles above its surface and having an estimated total weight of 5,000 billion tons. At sea level, the pressure exerted by this mass of air is on average 14.72 pounds per square inch (PSI), or 1kg per square centimetre. This average is also defined as a pressure of one atmosphere, or one bar, although meteorologists more commonly regard it as 1013.25 millibars (mb).

As one rises higher into the atmosphere, so the air pressure decreases, reducing to about one half (500mb) at 5,000 metres – see Fig. 1. At 16,000 metres the pressure has dropped to 100mb, while at 100,000 metres it is barely 0.001mb.

Fig. 1. Basic altitude to millibar graph.

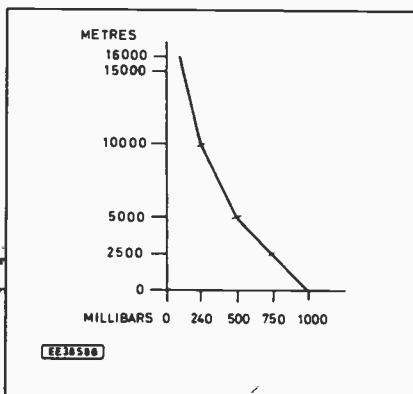

Although the pressure versus height relationship is not linear, for some purposes it may be regarded as such within the range of 0 to 5000 metres. It can thus be stated that up to a height of 5000 metres a

change of 1mb represents a change of 10 metres.

However, the atmosphere is in a constant state of turmoil and the total weight of air above a given location can vary considerably. Under extreme conditions the pressure can range from about 940mb to 1060mb, as indicated by the scale on a standard aneroid barometer. Obviously, therefore, an altimeter using the barometric principle must have a separate control to adjust for natural changes in atmospheric pressure.

Variations in height plotted against millibars across the range of 940mb to 1060mb is shown in the conversion graph Fig. 2. If the pressure at sea level is 1000mb (horizontal axis) and a barometer shows a reading of 900mb (right hand column) the barometer is at a height of 1000 metres (left hand column). If the pressure at sea level is 1060mb and the barometer's altitude is 1000 metres it should show a reading of 960mb.


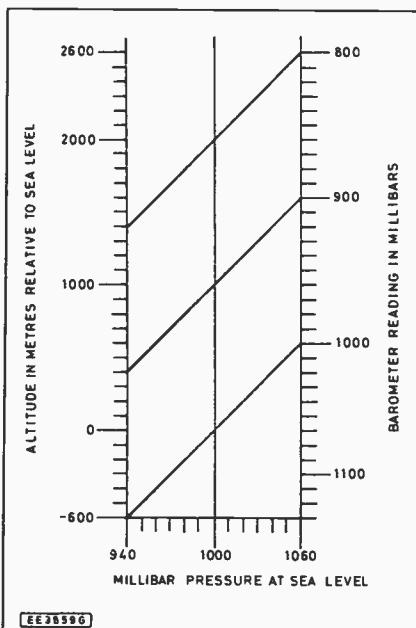


Fig. 2. Altitude to variable atmospheric pressure conversion graph.

Fig. 3. The MPX100A pressure transducer internal structure and function details.

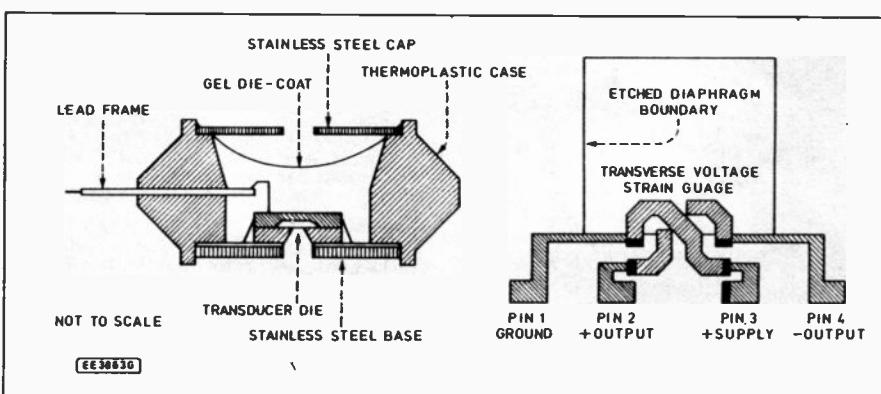

the guaranteed minimum to maximum manufacturing tolerance range, for a pressure change of 100 kiloPascals (kPa). 100kPa equals 14.5 PSI, which is approximately equal to one bar.

Taking the typical output as 60mV per 100kPa, a 1mb pressure change will produce a voltage change of approximately 0.06mV. Likewise, a change in altitude of one metre (below an altitude of 5,000 metres) produces a change of 0.006mV.

Consequently, the interface between the sensor and the l.c.d. readout must convert the voltage changes by a factor which will cause each 0.006mV step to result in a barometric display change of one unit per millibar. This factor then has to be multiplied by 10 for the metres display, and by a further 3.28 for the feet display (1 metre = 3.280839 feet).

In the practical circuit, whose block diagram is shown in Fig. 4, the sensor output is in fact multiplied by a factor related to unitary changes on the feet scale, and then separately divided for the metres and millibar scales.

SENSOR CIRCUIT

In order to ease the understanding of the EPE Altimet circuit, it has been divided in to three sections: pressure sensor and psu; temperature and battery level; an l.c.d. display and controller.

The details of the sensor amplification and division scaling circuit diagram is shown in Fig. 5. It also shows the power supply details.

TX1 is the pressure sensing transducer. Its internal resistance is predetermined in manufacture within the range of 400 to 550 ohms. The value of the resistor R5 in series with TX1 is selected to suit the resistance of the transducer at 25°C.

Several of the transducer parameters are temperature dependent and the value of resistor R5 is instrumental in minimising part of the effect of their changes. This will be discussed later.

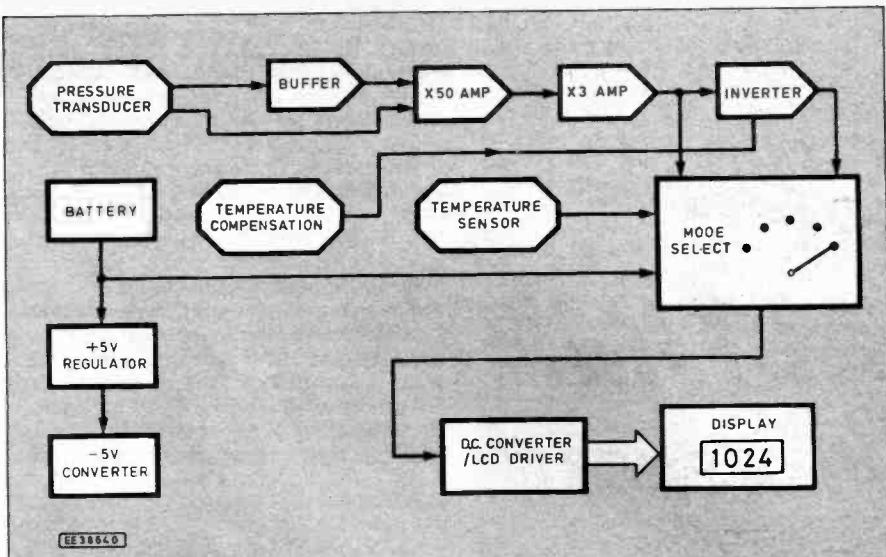


Fig. 4. Full block diagram for the EPE Altimet.

The transducer TX1 has two differential outputs, pins 2 and 4. The voltage span across them decreases as atmospheric pressure falls. Both are fed to the non-inverting inputs of op.amps IC2a and IC2b, which are configured respectively as a unity gain buffer and differential amplifier with a gain of about 50 set by the values of resistors R10 and R11.

From IC2b, the signal is inverted and is given an additional gain of around 3.3 by IC2c. Preset control VR2 in series with resistors R13 and R14 varies the bias at IC2c pin 12 so enabling the basic output voltage at IC2c pin 14 to be preset.

Before being further processed by IC2d, the voltage at IC2c pin 14 is tapped to provide barometric pressure data. Preset VR5 in series with resistor R20 divides the voltage by 32.8 presetting the span range required by the l.c.d. readout circuit. The inclusion of preset VR4 in series with resistor R21 is used to impose a bias voltage on


one side of VR5 to increase the barometer readout by approximately 1000mb.

Whereas a barometer shows a decrease in reading with a decrease in pressure, an altimeter has to show an increase. Consequently, IC2d is used to invert the voltage change direction but, within the tolerances of resistors R16 and R19, does not change the amplification.

A panel-mounted control VR3 provides IC2d with a variable bias voltage, allowing the altitude readout to be set to compensate for normal meteorological changes in atmospheric pressure. The range controlled by VR3 is about 300 metres. This may be increased by increasing the value of VR3 or by reducing the value of R17.

The output of IC2d directly provides the voltage data for an altitude readout in feet. For the metres scale, the output of IC2d is tapped by preset VR6 in series with resistors R22 and R23, dividing the voltage by 3.28. Switch S2 selects between

Fig. 5. Circuit diagram for the EPE Altimet sensor amplifier, division scaling and regulated power supply.

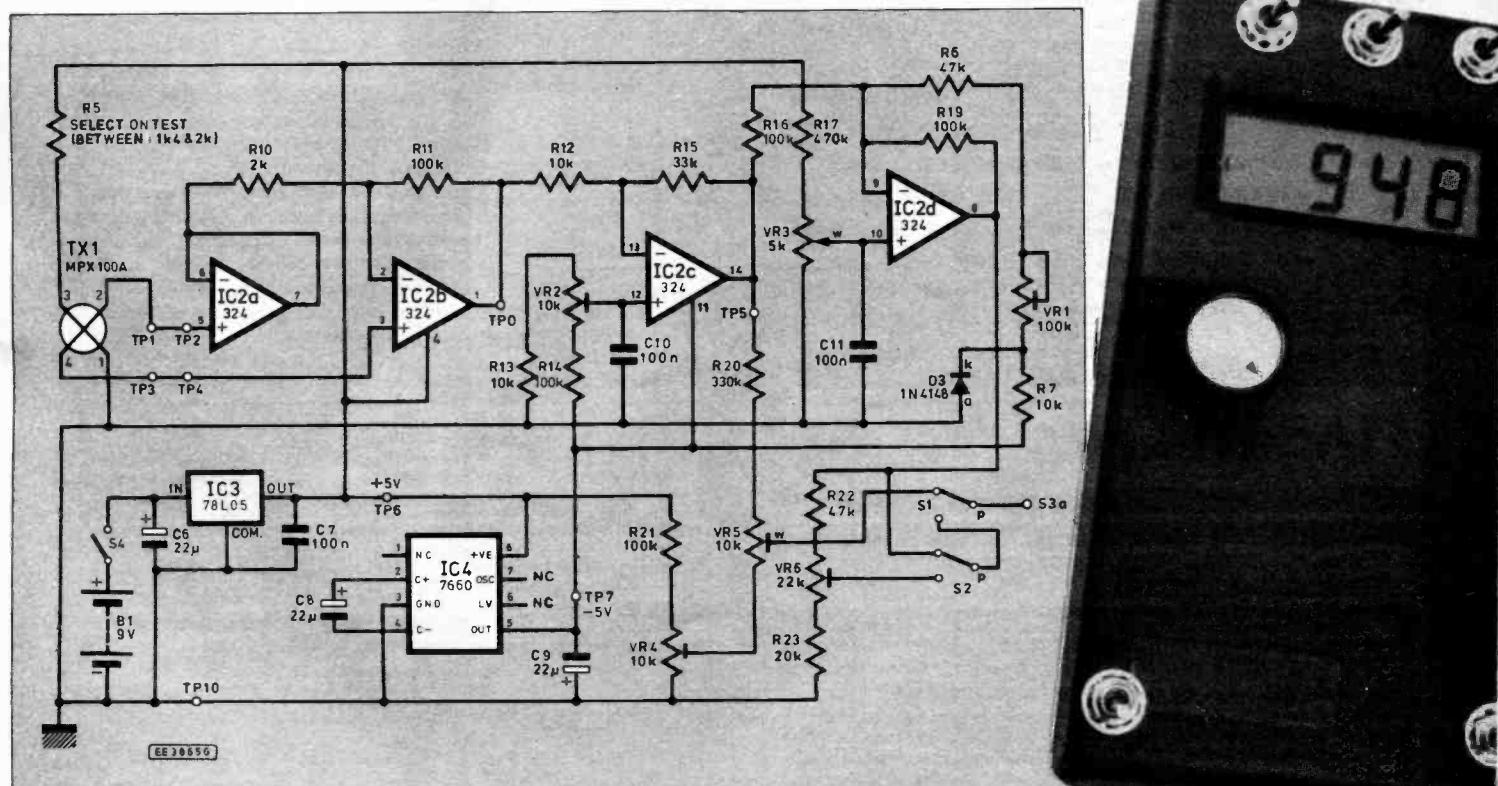

the Feet and Metres modes and feeds to switch S1 which selects between Height and Barometric modes.

TEMPERATURE COMPENSATION

In any d.c. amplification circuit there is a tendency for voltage levels to change as temperature changes. The component which causes most drift in the EPE Altimet is the transducer TX1.

Even with resistor R5 chosen correctly, the transducer's offset voltage typically changes with temperature by about $+/-15$ microvolts per degree Celsius. In the test model, the offset drift after amplification was 63mV per 40°F (22.2°C).

Compensation for this and other minor drifts is effected by the temperature-related change in voltage across the forward biased diode D3. The voltage at the junction of D3 and resistor R7 increases by about 1mV with each 1°F increase (1.8mV°C).

A proportion of the change, as controlled by the values of resistor R6 and preset VR1, is fed into IC2d to counterbalance the majority of the circuit drift from the altitude readouts. The barometer output is left uncompensated since the attenuation by VR5 reduces the effect to only about 2mV per 40°F (22.2°C).

TEMPERATURE AND BATTERY MONITORING

Another diode is used as the temperature sensing element, shown in Fig.6 as D4. Resistor R24 and preset VR9 form a potential divider across the +5V and 0V power lines providing a bias voltage to D4. The voltage across D4 changes at a similar rate to that across D3 (Fig. 5).

Preset VR9 adjusts the displayed temperature value and VR7 presets the voltage/temperature output span. The choice of whether temperatures are shown

in Fahrenheit or Celsius is made when setting up the unit, and simply entails adjusting VR7 for the desired ratio. S3a selects between temperature display and the modes routed via switch S1 as shown in Fig. 5.

Whereas height and barometric readings are shown as integer values, temperature is displayed to within one tenth of a degree. The decimal point control being switched in by S3b.

In height and barometric modes, the decimal point is pulsed in phase with the l.c.d. backplane clock, so rendering the point inactive. In temperature mode, the point is activated by connecting it via the OR gate around diodes D1, D2 and resistor R18 to two segments of the l.c.d. hundreds digit, one or other of which will

always be active irrespective of the number displayed.

Also shown in Fig.6 is a battery check facility. Resistors R8 and R9 form a potential divider across the battery input lines. The tapped voltage is switched to the l.c.d. circuit (Fig. 7) via switch S5, an action which switches the previous mode selectors out of circuit.

The R8/R9 ratio causes an l.c.d. readout of approximately 900 for a battery voltage of 9.0V. There was insufficient room in the case to fit a d.p.c.o. switch to activate a decimal point in a similar way to S3.

L.C.D. READOUT

The circuit diagram which converts the monitored voltages levels into an equivalent l.c.d. display is shown in Fig. 7. The DPM chip IC1 is the heart of the circuit. It assesses the input voltage level and relates it to the reference voltage set by VR8 in series with resistor R2, timing the rate at which capacitor C4 charges and discharges.

The timing is clock controlled at a rate set by resistor R1 and capacitor C1 and an internal counter counts the number of pulses required to discharge capacitor C4. The counter outputs are internally decoded to control the four l.c.d. digits and a negative polarity symbol.

The backplane pulsing and phasing necessary for controlling l.c.d.s is automatically generated by IC1 and is internally set at a sub-multiple of the main clock frequency. (Note that l.c.d. segments should *NOT* be controlled by a d.c. voltage since this steady state could damage them.)

Irrespective of the reference voltage set, the full scale range for that voltage is represented by 1999 steps. Input voltages outside the reference range cause the l.c.d. to blank the three right-hand digits and turn on the left-hand digit.

Preset VR8 is used to vary the reference voltage to suit the output voltage span produced by the transducer's amplifier stages. In effect, VR8 serves as an additional gain controller. This means that


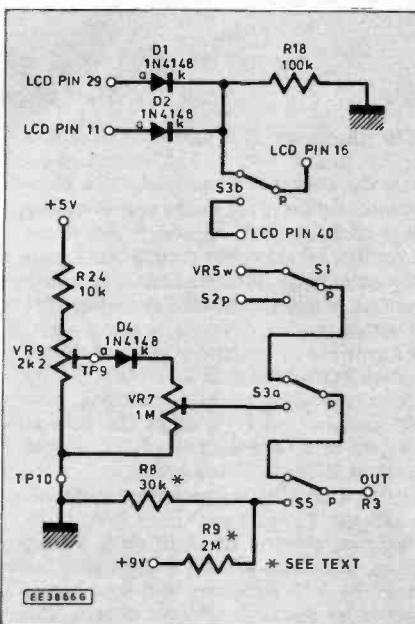


Fig. 6. Circuit diagram of the temperature and battery level section.

Fig. 7. Circuit diagram of the display section and interconnection details between the display driver IC1 and the l.c.d.

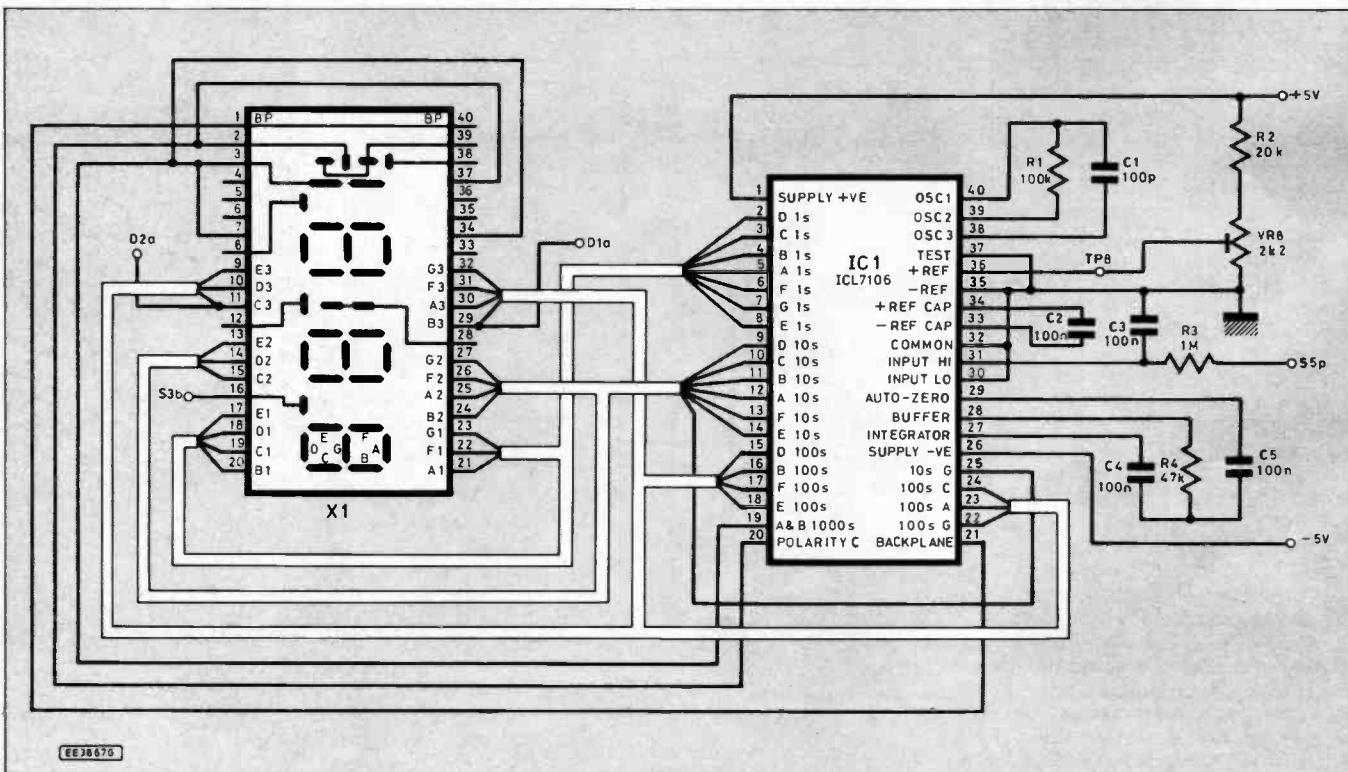

when VR5 and VR6 have been set to the relative span ranges for their mode scales, a common increase or decrease to the altitude and barometer mode gains can be effected by adjusting VR8.

It will be seen that the lines controlling the polarity symbol and the thousand's digit are apparently connected to unused pins of the I.C.D. These connections correspond with the equivalent 1000 and polarity segments of a 4-digit I.C.D. module which may be used in place of the 3·5 digit version.

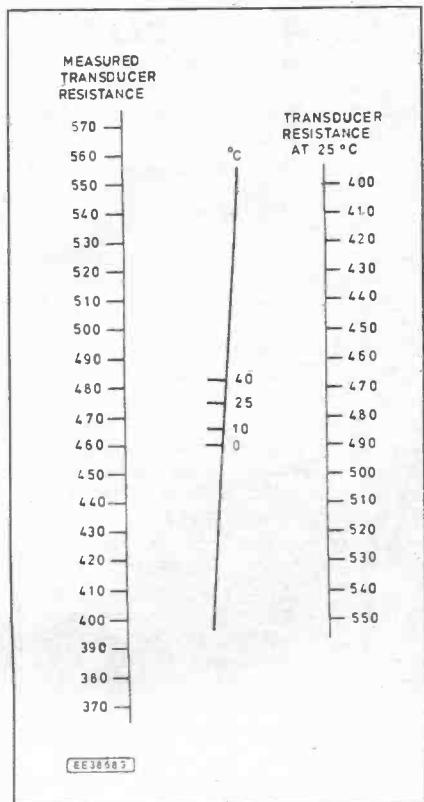


Fig. 8. Pressure transducer MPX100A resistance/temperature nomogram.

POWER SUPPLY

A regulated $+/-5V$ supply is generated from a single 9V battery. Referring back to Fig. 5, the battery voltage is switched on by S4 and is regulated down to $+5V$ by IC3.

Using an internal pulsed inverter, IC4 generates an almost equivalent negative voltage from the $+5V$ supply. The load driven by IC4, though, will slightly reduce the voltage from the nominal $-5V$ to around $-4.7V$.

Capacitor C8 is associated with the chip's internal switching and C9 is the output reservoir capacitor. There is inherently a very slight residual ripple of IC4's clock frequency left on the negative line, though the final effect of this upon the signal input to IC1 is nulled by the inclusion of resistor R3 and capacitor C3 in Fig. 7.

The current drawn by the circuit is around 13·5mA. If, as intended, the unit is used intermittently throughout a journey, a PP3-sized battery could last for weeks or even months.

Under continuous switched-on use, a PP3 battery life of around eight hours seems a reasonable expectation. The battery may be run down to about 7·3V before IC1 fails to regulate satisfactorily. A NiCad battery may be used.

COMPONENT TOLERANCES

Standard carbon-track miniature skeleton preset potentiometers and 5 per cent 0·25W carbon film resistors were used in the prototype, providing accuracy and stability well within the author's own requirements. A more tightly controlled performance can be obtained by using cermet presets and one per cent 0·25W metal film resistors. The main advantage of cermet over carbon presets in this application is the smooth linearity of their tracking, allowing more precise adjustment of their settings.


Metal film resistors have a better temperature stability than the standard carbon film variety. Typical temperature coefficients for the latter are -150 to -800 parts per million (ppm) per $^{\circ}C$, whereas for metal film they are typically $+/-50$ ppm per $^{\circ}C$. Even though temperature compensation is provided, the use of metal film resistors could still be beneficial.

RESISTANCE MATCHING

Since the correct value for resistor R5 is related to TX1 transducer's resistance at $25^{\circ}C$ ($77^{\circ}F$), it is preferable to take into account the transducer's temperature at the time that the measurement is made. The Nomogram in Fig. 8 shows how the resistance at a known temperature can be converted to its equivalent at $25^{\circ}C$ ($77^{\circ}F$).

Clip the leads of a digital multimeter to the transducer pins 1 and 3, and switch the meter to a range suitable for measuring up to about 550 ohms. Place a thermometer alongside the transducer and allow the temperature to stabilise.

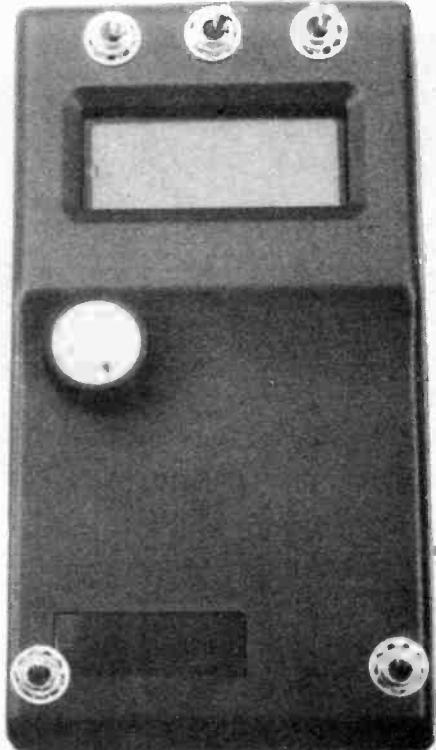Measure the resistance and note the temperature. Place a ruler so that its edge passes through the resistance value in the chart's left hand column and the temperature in the centre column. Read off the value in the right hand column and multiply it by 3·577 (a factor specified by the transducer manufacturer). This is the optimum value for R5.




The transducer used in the prototype has a resistance of 433 ohms at $25^{\circ}C$ and the value for R5 was calculated as 1548 ohms (1k548). The resistor with the measured value closest to this which was conveniently available was 1567 ohms. Although not the precise calculated value, the tolerance margin has proved to be acceptable.

Two or more resistors in series or parallel may be used to optimise the value. (There was not enough space on the p.c.b. to substitute a preset potentiometer for R5.)

CONSTRUCTION

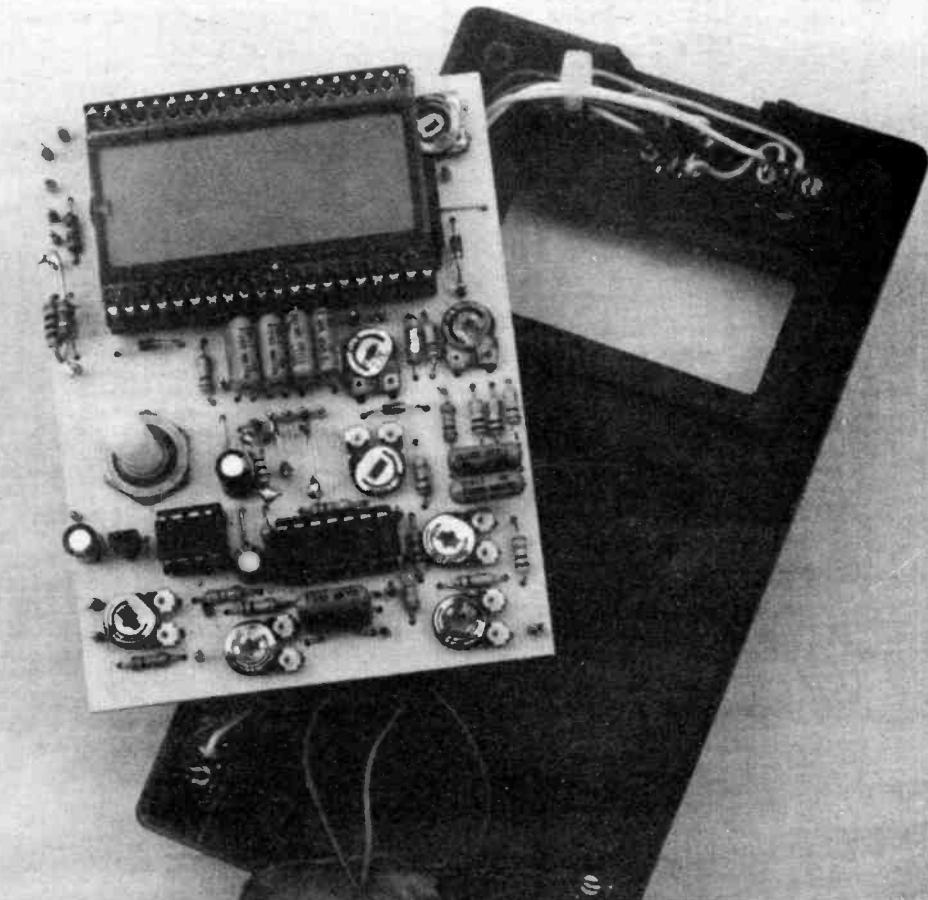The topside printed circuit board component layout and full size underside copper foil master pattern is shown in Fig. 9. This board is available from the EPE PCB Service, code EE807.



COMPONENTS

Resistors

R1, R11, R14,	
R16, R18, R19,	
R21	100k (7 off)
R2, R23	20k (2 off)
R3	1M
R4, R6, R22	47k (3 off)
R5	Between 1k4 and 2k - See Text
R8	30k - See Text
R9	2M - see text
R7, R12, R13, R24	10k (4 off)
R10	2k
R15	33k
R17	470k
R20	330k
R25	10
All 0.25W 5% carbon film or better.	

Potentiometers

VR1	100k min. skeleton preset, horiz.
VR2, VR4, VR5	10k min. skeleton preset, horiz. (3 off)
VR3	5k rotary carbon, linear
VR6	22k min. skeleton preset, horiz.
VR7	1M min skeleton preset, horiz.
VR8, VR9	2k2 min. skeleton preset, horiz. (2 off)
All presets carbon or cermet.	

Capacitors

C1	100p polystyrene
C2 to C5, C7, C10, C11	100n polyester (7 off)
C6, C8, C9	22μ radial elect., 16V (3 off)

Semiconductors

D1 to D4	1N4148 signal diode
IC1	ICL7106 ADC/display driver
IC2	LM324 quad op.amp
IC3	78L05 +5V 100mA voltage regulator
IC4	ICL7660 voltage converter

Switches

S1, S2,	
S4, S5	miniature s.p.c.o. toggle (4 off)
S3	miniature d.p.c.o. toggle

**See
SHOP
TALK**
Page

Miscellaneous

TX1	MPX100A pressure transducer
X1	3½ digit l.c.d. display

Handheld, calculator style plastic case, size 148mm x 60mm x 36mm (with 50mm x 20mm display window cutout); 8-pin d.i.l. socket, 14-pin d.i.l. socket; 40-pin d.i.l. socket (3-off - see text); PP3 battery and snap connector; knob; p.c.b. stand-off spacer; rubber grommet for VR3 shaft; connecting wire; fixings; solder etc.

Printed circuit board available from EE PCB Service, code EE807 (see PCB page 754).

Approx cost
guidance only

£50

Before mounting the components, check that the board fits the case satisfactorily, trimming off any excess fibre-glass if necessary. It may also, with some models of the case, be necessary to trim down the internal partitions to allow the board to fit lengthwise while still allowing for the battery and switches to be inserted.

The front panel drilling measurements and layout used in the prototype model is shown in Fig. 10. Check that they apply to your case before drilling any holes!

CIRCUIT BOARD

There are several link wires required on the p.c.b., some of which go below i.c. positions (see Fig. 9), and these should be inserted and soldered first, but omit links TP1/TP2 and TP3/TP4 until later. The preset "pots" and d.i.l. sockets for the i.c.s and the l.c.d. should be inserted next.

The board has been designed so that the display is mounted above IC1. This is achieved by first soldering two 20-pin s.i.l. (single-in-line) sockets into the l.c.d. position. If s.i.l. sockets are not available, cut a 40-pin d.i.l. socket in half. Once assembly is complete, a second level of s.i.l. sockets to hold the l.c.d. is plugged into the first.

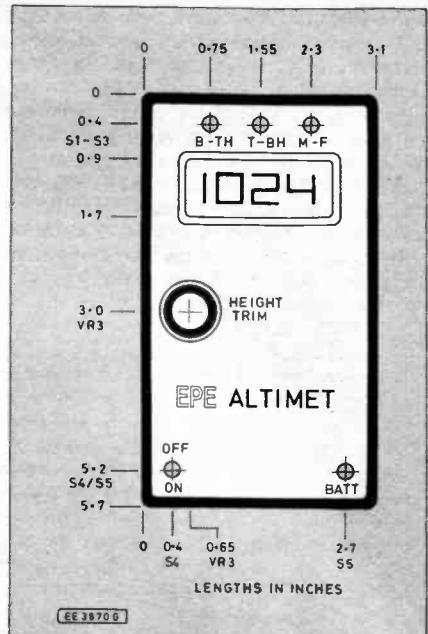


Fig. 10. Case drilling details.


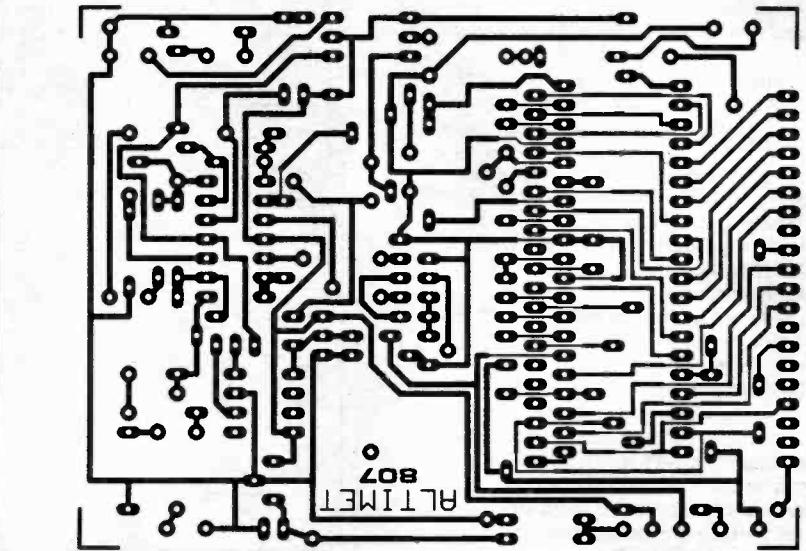
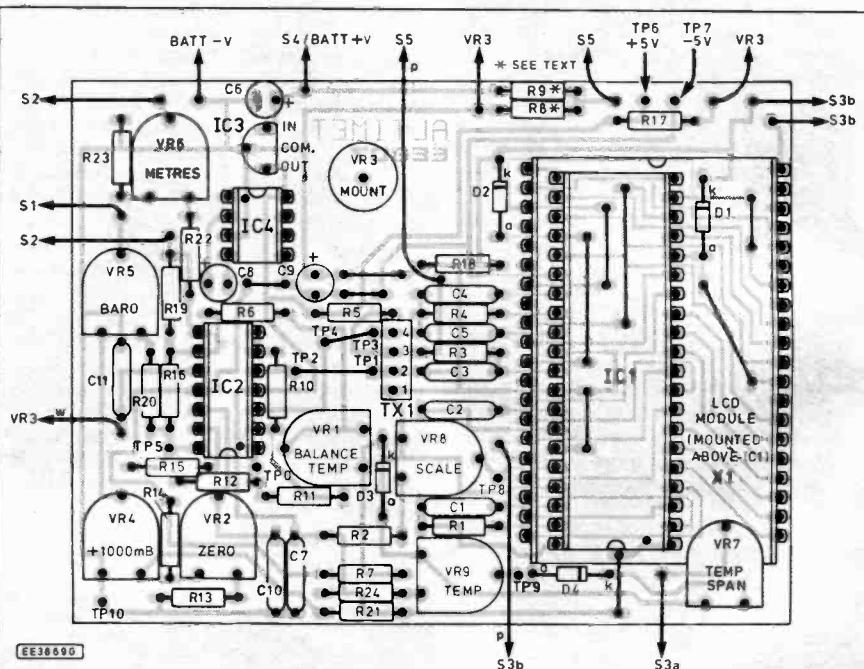


Fig. 9. Printed circuit board component layout and full size foil pattern.

Solder in the components in order of resistors, diodes, capacitors and voltage regulator IC3. Next mount the rotary potentiometer VR3 in its p.c.b. hole, shaft protruding from the component side, using an insulating washer between its body and the back of the board to prevent shorting across soldered joints. The transducer TX1 is also mounted on the trackside of the board, carefully bending its leads through ninety degrees so that its body lies parallel to the p.c.b. in the direction of IC2.

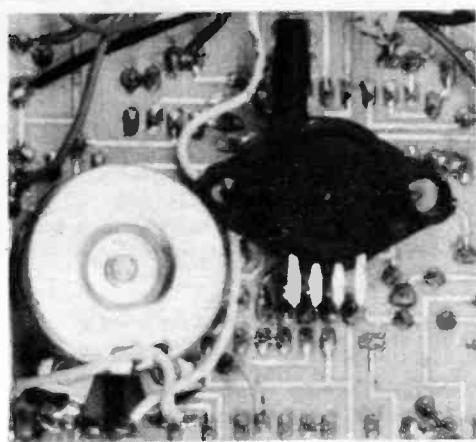Two versions of the MPX100A may be available (Fig. 12), one enclosed in a plastic case, the other not. Either may be used, but the unenclosed version must have insulating tape placed between its body and the p.c.b. tracks. Do NOT cover the hole in the transducer's centre, and under no circumstances poke anything into the hole below which is the very delicate pressure diaphragm.



(above) Transducer TX1 and VR3 mounted on the board track side and (below) the completed circuit board.

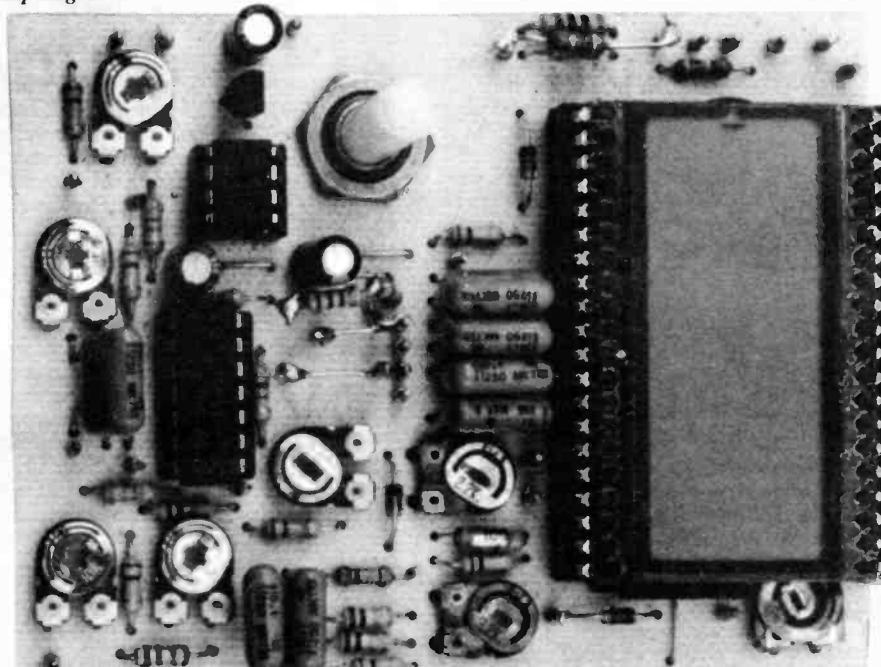


Fig. 11 (right). Interwiring from off-board components to the p.c.b. Note, VR3, TX1 and all wires are connected to trackside.

Details of the interwiring from the circuit board to all off-board components is shown in Fig. 11. Wire up all control connections from the trackside of the board and then thoroughly check with a close-up magnifying glass that there are no shorts between joints and adjacent tracks.

INITIAL TESTING

It is suggested that for the setting-up procedures the unit should be powered from a bench power supply delivering 9V, or that a 9V battery of greater size than PP3 be used. A 12V supply, such as a car battery, may be used though to avoid overtaxing IC3, a 390 ohm 0.5W resistor should be connected in series with the positive battery lead, so reducing the supply to about 9V when full load is applied.

Several test points (TP) are provided on the p.c.b. For ease of use it is recommended that terminal pins are soldered into these positions. All test measurements are made with respect to the negative terminal of the 9V battery which should be regarded as the 0V or "ground" line. The common lead of the voltmeter should be clipped to test point TP10.

For the first test, with IC3 and IC4


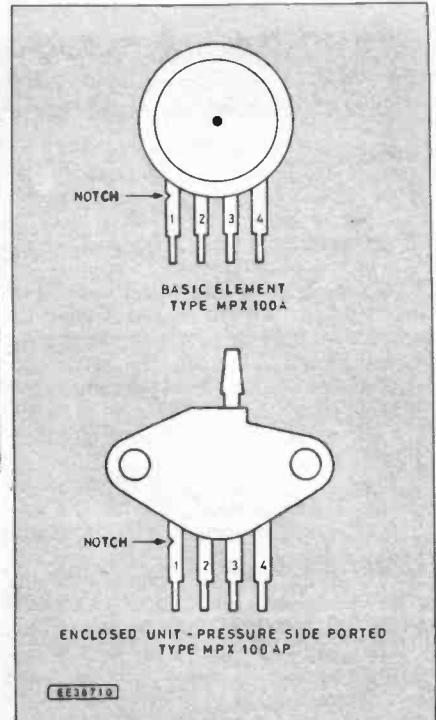


Fig. 12. Pressure transducer pintout details.

in circuit, but the I.C.D. and other I.C.s omitted, switch on and check that close to +5V is present at TP6 and that about -5V is present at TP7. Check the voltages at TP6 and TP7 again when IC1, IC2 and the display X1 have been inserted, but note that TP7 may now have fallen to about -4.7V. Any large deviation of the supply voltages will indicate a fault condition, such as a wrong component polarity or a track short or break.

BENCH SETTING

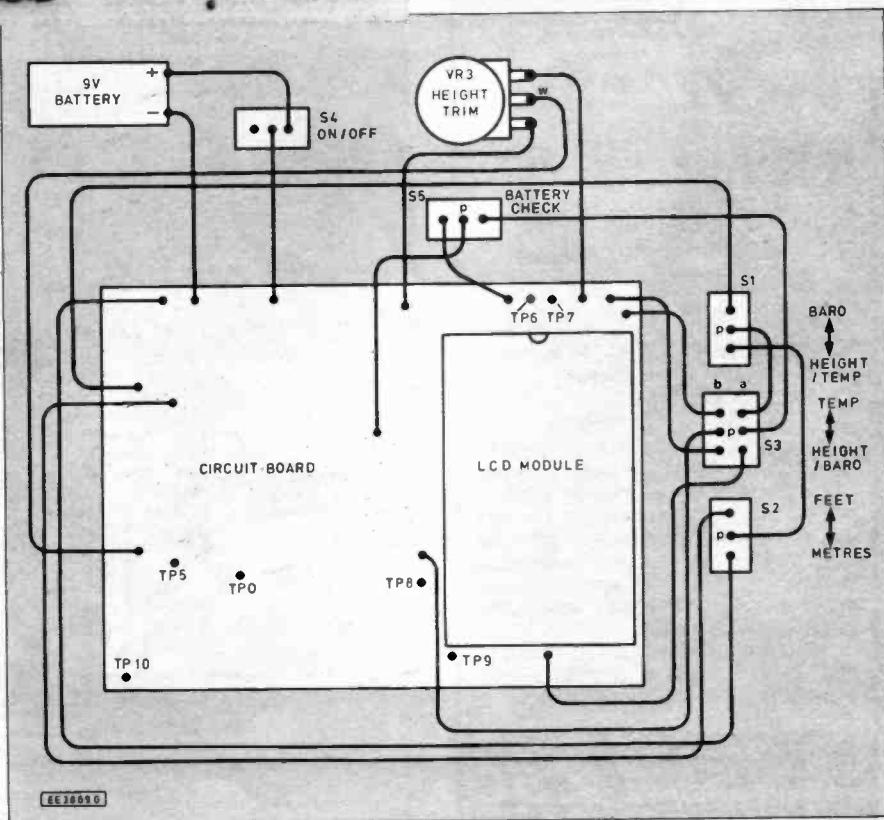Throughout this section of the setting-up, the figures obtained from the model are quoted in square brackets as an example. They will vary slightly for other units.



Setting-up falls into two parts, "workshop alignment" and fine tuning under "field conditions". Since the response of the transducer can vary in manufacture between 45mV and 90mV per 100kPa, the final alignment can only take place after subjecting the unit to known changes in barometric pressure, such as those experienced when using it at the top and bottom of a hill of known height.

However, the millibars and metres pre-sets VR4 to VR6 are aligned without the transducer fully in circuit, using the test circuit shown in Fig. 13. The circuit consists of R24 and VR9 from the temperature readout circuit, with the addition of a resistor R25 across VR9 to temporarily reduce its span range.

Temporarily link the outer terminals of the rotary control VR3 to TP6 and TP7 instead of to their normal designated points in Fig. 9. Set presets VR1, VR2 and VR3 midway, VR4 to ground, VR5 and VR6 to maximum output, and set VR8 for a reference voltage of about 200mV at TP8.

Clip a digital voltmeter across TP9 and TP10 and on its lowest suitable range measure the voltage when the wiper of VR9 is at its maximum resistance [4.9mV]. Link TP2 to TP9 and TP4 to TP10 (as links TP1/TP2 and TP3/TP4 have been left out, the transducer is not presently connected to IC2).

Assume for the moment that the transducer will have a span of 60mV per 100kPa and that 1000 metres = 10kPa. Therefore, 1000 metres represents a 6mV swing from the transducer which equals 3,280 feet (1000×3.28). Calculate the number of feet that the measured millivolt span range of VR9 represents: [3,280ft/6mV = 4.9mV = 2,678 feet].

FEET

Set the switches for Feet mode. Set VR9 midway and adjust VR2 and VR3 until the display X1 shows a reading of about zero (within a hundred units or so). Note the

Layout of function switches on the front panel and position of the p.c.b. inside the case, showing wiring to track side and switches S4, S5 either side of the battery compartment.

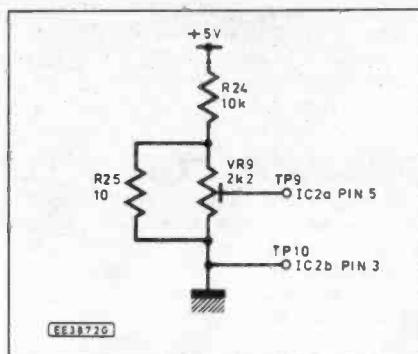


Fig. 13. Alignment and setting-up test circuit diagram.

total l.c.d. readout range with VR9 at its minimum and maximum settings.


Adjust VR8 until the full range controlled by VR9 is close to that calculated [-1305 to $+1373 = 2678$, TP8 = 178.4mV]. Set VR9 to maximum output [l.c.d. = 1373]. (If the feet range span obtained is not exactly that calculated, for the next calculations use the maximum output figure actually obtained.)

METRES

Switch S2 to the Metres range. Divide the maximum feet reading by 3.28 to produce the metres integer equivalent [$1373/3.28 = 418.597561 = 419$]. Without touching VR8, adjust VR6 until the l.c.d. reads as close as possible to the calculated metres value [419].

Set VR9 to minimum and check that the l.c.d. readout is the metres close equivalent to the minimum feet readout [$-1305/3.28 = 397.865854 = 398$]. There is likely to be a slight non-linearity between the feet and metres conversion figures within about 10 metres either side of a zero height readout.

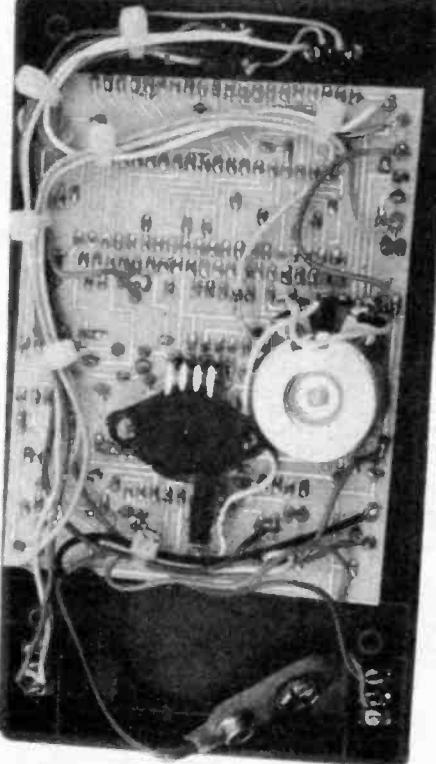Switch S1 to the Millibars range, set VR9 midway and adjust VR4 until an l.c.d. readout of about 1000 is produced. Do not adjust VR8. From the measured swing



range of VR9 [4.9mV] calculate the millibar range that this represents:

$$[60mV = 1000mb \text{ therefore } 4.9mV = 1000/60 \times 4.9 = 81.66mb = 82mb]$$

Swing VR9 back and forth across its range and adjust VR5 until the total l.c.d. range difference is the calculated millibar value [975 to 1057 = 82].

TRANSDUCER BALANCING

The next step is to put the transducer fully into circuit and adjust preset VR1 to compensate for l.c.d. readout drift with temperature. Remove "test" resistor R25 from across VR9, disconnect the temporary TP10/TP4 and TP9/TP2 links, link TP1 to TP2 and TP3 to TP4, and correctly reconnect VR3. Switch to the Feet or Metres range, then raise and lower the unit between floor and ceiling and observe that the display registers the height changes, even though accurate altitude setting has not yet been made.

After leaving the unit switched on for a few minutes to allow temperatures to stabilise, note the room temperature (as shown on a good mercury-filled thermometer). Switch to the metres range, set VR1 midway, adjust preset VR3 and/or VR2 for an l.c.d. readout of about zero. Note the l.c.d. readouts with VR1 at *minimum*, *midway* and *maximum* resistance settings.

Allow the room temperature to rise by as many degrees as is feasible, 20°F or 10°C for example. Note the l.c.d. readings at the three VR1 settings and judge approximately which value of VR1 produces the minimum readout change.

(A hair dryer blowing low heat across both sides of the p.c.b. was used in the original tests, allowing the temperature to rise slowly over about 15 minutes. Cooling to low temperatures was assisted by a fridge!

Beware, though, that rapid temperature changes and uneven p.c.b. heating can produce misleading results. If condensation forms on the unit when removed from the fridge dry it off using the hair dryer.)

Let the room and the unit cool naturally back to the original temperature, set VR1 to two or three positions close to the estimated value noting the l.c.d. readings. Allow the temperature to rise again and note the l.c.d. figures at each chosen VR1 position. Set VR1 to the resistance setting at which the minimum output change occurs.

The transducer TX1 and temperature compensation diode D3 may respond at different rates affecting the apparent stability of the readout during the early minutes of a significant temperature change. Once the transducer and diode reach the same temperature the readout should have returned to its original figures.

HYSERESIS

It should be recognised that there are component hysteresis factors which affect the maximum practical balance obtainable. Hysteresis applies particularly to the transducer and dictates that at any given pressure or temperature there will be a difference in the output voltages produced depending on whether this pressure or temperature is approached upwards or downwards.

The MPX100A has typical pressure and temperature hysteresis factors of $\pm -0.05\%$ and $\pm -0.5\%$ of full scale (100kPa) respectively. Without temperature drift correction the l.c.d. output

change on the test model was about 15 metres per °F (27 metres °C) the equivalent of around 1.5mV per °F (2.7mV °C). Although impaired by hysteresis, the compensation circuit allowed the drift to be kept down to only 20 metres over a massive 40°F (22.2°C) temperature change.

Hysteresis and drift factors, however, should be seen in context with the scale of potential atmospheric changes. A barometric change of only one millibar will cause an apparent change of 10 metres on the altimeter. At the time of writing, the weather forecast predicts a 15mb change from 1020mb to 1035mb over the next 24 hours. The effects of normal ambient temperature changes become minor by comparison.

TEMPERATURE AND BATTERY READOUTS

The unit may be set for either Celsius or Fahrenheit temperature readout scales, depending on the range set by preset VR7. Set VR9 and VR7 midway, switch to Temperature mode and note the display reading and that of a thermometer alongside the p.c.b.

Allow the room temperature to change across a reasonable range and note the difference in the l.c.d. reading and the difference in temperature. Adjust VR7 up or down as appropriate and again change the room temperature. Repeat until the temperature and l.c.d. spans are the same, and then adjust VR9 so that the l.c.d. reading matches the thermometer reading.

The values for resistors R8 and R9 should be selected after IC1's final

reference voltage has been set by VR8. The ratio of R8 to R9 should cause the l.c.d. to show a reading of approximately 900 with a battery voltage of 9.0V. If the reading is low, increase the value of R8 or decrease R9.

FIELD SETTING

Final altitude alignment can only be done by checking the unit's height readout against a known height change. Consult a local Ordnance Survey (OS) map, preferably the large scale Pathfinder (green) series, and find two locations where the heights are known and of several tens of metres apart.

Go to one location and using the rotary control VR3 set the height on the l.c.d., also noting the temperature. If the temperature is changing and the unit's temperature balance is not exact, while still at the same location note the l.c.d. height reading at different temperatures. Go to the other location and repeat.

Take two readings made at the same temperature and calculate the difference between the l.c.d. change and the actual height change. Slightly reduce or increase the setting of preset VR8 as appropriate and repeat the procedure until the actual and displayed height spans correspond. An l.c.d. reading change of 55 metres compared to an actual height change of 60 metres, for example, would require adjustment of VR8 to decrease IC1's reference voltage.

It is preferable for the time between high and low readings to be kept short to minimise the likelihood of atmospheric pressure changes occurring between readings. It is advisable, for the same reason, to choose

a day when the *BBC TV* weather forecast maps show the isobars well spaced out.

Once VR8 has been finally set, the current millibar setting for your area (watch *BBC TV* again!) can be set by adjusting VR4. It should be remembered that weather forecast charts give millibar figures referenced to sea level. If you live significantly higher than sea level, the true atmospheric pressure for your location can be calculated from the simple equation + 10 metres = - 1mb.

USING IT

Since atmospheric pressure is constantly changing throughout the day, the height trimming control VR3 should be adjusted prior to each outing, setting the display to show the correct height in metres for the starting location as established from an OS map. If significant isobar changes are forecast it is advisable to re-trim VR3 in association with an OS map occasionally throughout a prolonged land-bound journey.

It is assumed that balloonists and other leisure-aeronauts will not be aloft long enough for meteorological changes during their flight to have any significance. Try to avoid subjecting the EPE Altimet to rapid or excessive temperature changes. □



LOW COST RANGER1 PCB DESIGN FROM SEETRAX

- Circuit Schematic
- Circuit Capture
- PCB Design

Host Of Outputs

All-In-One Design System

REDUCED PRICE!

£100

Fully Integrated Auto Router

£50

Ask Us About Trade-In Deals

Call Now For Demo Disk on 0705 591037

Seetrax CAE • Hinton Daubney House
Broadway Lane • Lovedean • Hants • PO8 0SG

Tel: 0705 591037 • Fax: 0705 599036

What The Press Said About RANGER1

For most small users, Seetrax Ranger1 provides a sophisticated system at an affordable price. It is better than EasyPC or Tsien's Boardmaker since it provides a lot more automation and takes the design all the way from schematic to PCB - other packages separate designs for both, that is, no schematic capture. It is more expensive but the ability to draw in the circuit diagram and quickly turn it into a board design easily makes up for this.

Source JUNE 1991
Practical Electronics

Pay by Visa or Access



Innovations

A roundup of the latest Everyday News from the world of electronics

Amateur Radio Morse Test

THE Radiocommunications Agency has announced proposed changes to the format of the 12 words per minute *Amateur Radio Morse Test*.

It is claimed that the new format will prepare candidates better for the sort of operating conditions they can expect to encounter "On Air". It follows the same lines as the five words per minute test which was successfully introduced last year.



The new style test will come into operation from January 1, 1993. Candidates who have studied under the old format will still be able to take the old test until March 31, 1993 when the new test will become compulsory.

Simultaneously with the introduction of the new style test, 1 January, 1993 will also see a new procedure for the identification of candidates. Instead of written proof of identity, candidates will have to bring to the test centre two recent passport sized photographs of themselves. - *Shades of code breaking?*

In the new test, the candidate will be required to receive a minimum of 120 letters and 7 figures in the form of a typical exchange between radio amateurs. A manual Morse key will be used to send the message. This portion of the test will last approximately 2½ minutes and a maxi-

mum of six uncorrected errors will be permitted.


In the sending test, the candidate will be given a text to send by hand on a straight Morse key consisting of not less than 75 letters and five figures, also in the form of a typical exchange. This portion of the test will last approximately 1½ minutes. There must be no uncorrected errors in the sending and not more than four corrected errors.

The Radio Society of Great Britain conducts both the five and 12 w.p.m. Morse tests on behalf of the Agency. Further information on taking the test may be obtained from: **Radio Society of Great Britain, Lambda House, Cranborne Road, Potters Bar, Herts EN6 3JE.**

Patent News

The first ever report published by the Patent Office since becoming a Trading Fund on 1 October, 1991, and its accounts, prepared for the first time on a full commercial basis, show a surplus of £603,000 for the six month period to 31 March, 1992.

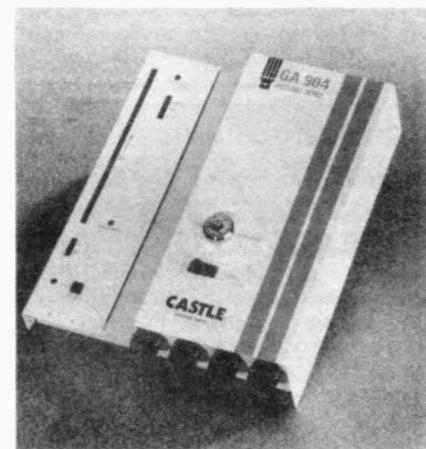However, in volume terms, patent applications in 1991 were two per cent down on 1990, while trade mark (including service mark) and design applications were down by 12 per cent respectively. A similar trend was evident in the European Patent Office where a down-turn in activity was recorded for the first time.



Orange Aid

No it's not a new fizzy drink but a new approach which may help anyone who has been a victim or does not want to be the perpetrator of excessive noise. Thanks to the Castle "Electronic Orange", the annoying sounds which may be escaping from the local disco may be a thing of the past.

The sound pressure (noise) within the room is picked up by a microphone and when the noise reaches the threshold, which is adjustable, a spherical yellow coloured lamp, "the orange", lights up. If the noise rises further, the device removes the power to the amplifiers. After resetting the electronics, either manually or automatically, the volume must be reduced to prevent another trip condition from occurring.

Further information and prices from **Castle Associates Ltd, Salter Road, Cayton Low Road Industrial Estate, Scarborough, North Yorks YO11 3UZ.**

THE PHILIPS LECTURE

Established in 1980 under the sponsorship of Philips Electrical, the Philips Lecture is given annually on the theme of science in industry. This year's lecture is entitled "Thermal Imaging - A New Eye On The World" and is being given by Dr. C. T. Elliott of the Defence Research Agency, Malvern.

A thermal imager produces a visible, television-like image using the infrared radiation that warm objects emit. It sees in complete darkness and through smoke and mist. This enhanced vision capability has given rise to numerous military and civil applications such as a pilot aid for military aircraft flying at low level in the dark, helping firemen to find people in smoke-filled buildings, and possibly, in future, helping to drive cars at night.

The development both of high performance imagers, based on cooled semiconductor detectors, and moderate performance imagers, using uncooled pyroelectric detectors, will be outlined together with illustrations of some of the applications.

The lecture will take place at the following venues and further details can be obtained from **The Royal Society, 6 Carlton House Terrace, London SW1Y 5AG. Tel: 071 839 5561.**

Venues: 7 October, 17.30 at The Royal Society, 6 Carlton House Terrace; 12 October, University of Surrey and the University of Durham on 16 October.


BOOKSHOP

To help make their renowned range of technical publications more readily available to industry and educational establishments alike, Texas have formed a "Technical Bookshop" and issued a catalogue.

The 1992 Technical Bookshop Catalogue contains a brief description of titles available and lists data books, user guides and applications manuals for engineers and students.


Texas Instruments Ltd, Dept EPE, Manton Lane, Bedford MK41 7AP. Tel 0234 270111.

Typical Applications for the TSL250

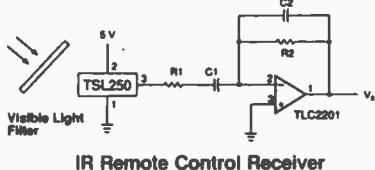

IR Remote Control Receiver

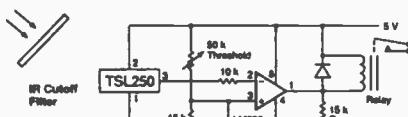The TSL250 and a simple active filter can be used as an IR remote control receiver. A visible light filter is used to reject visible light and pass infrared, thus reducing interference. R1, C1, R2, C2 and the TLC2201 form an active band pass filter. The actual values are chosen based on the data rate of the IR transmitter.



Adjustable Light-Activated Switch

The IR cutoff filter prevents the switch from being activated by infrared. Resistor R_f provides hysteresis to prevent false activation due to noise.

BRIGHT LIGHTS

Changes in light intensity can be used or monitored with high accuracy using one of the new family of light-to-voltage optical sensors (types TSL250/51/52) from Texas Instruments. The devices combine, in a single three-pin package, a large area photodiode, an operational amplifier and feedback components.

The devices operate from a single variable supply voltage (3V to 9V), and each device provides a voltage output proportional to the incident light intensity. Because the output is a voltage level, the devices can be easily interfaced to comparators or A/D converters.

Integrating an amplifier and a photodiode together on the same chip not only simplifies designs, but also enhances the noise immunity of the device. Thus they are particularly useful at low light levels or in noisy environments.


Potential applications for the TSL250/1/2 include light control, IR remote control, security systems and medical chemical testing.

Further details from: Texas Instruments Ltd, Dept EPE, Manton Lane, Bedford MK41 7AP.

Cable Gains

The number of homes connected to broadband cable systems rose in July to 330,630, according to the Independent Television Commission's (ITC) latest cable statistics. This was a net increase of 39,000 (13.5%) over the last three months and of 139,000 (72.5%) over the last year.

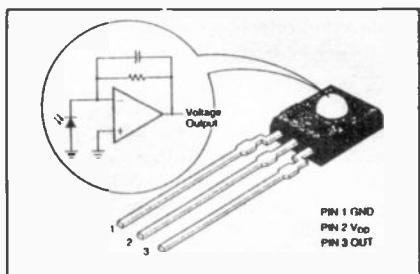Because research has shown cable households to be larger than average (3.1 people aged four years and over), it is claimed this means that over one million viewers now receive multichannel television via one of Britain's cable franchises. The take-up rate has increased by 2.25 percentage points over the last year.



The Car CD Multiplay (code GK74R) from Maplin.

**1992
CATALOGUE
NOW FREE**

**CRICKLEWOOD
ELECTRONICS**

CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET
Tel: 081 452 0161 Fax: 081 208 1441

BOOKS	BOXES & CASES	CABLE & WIRE	CAPACITORS	CONNECTORS	KITS	SEND NOW FOR THE / CRICKLEWOOD ELECTRONICS COMPONENT CATALOGUE ONE OF THE BEST RANGES AVAILABLE
						Name..... Address.....

In-Car Stereo CD

The closest thing yet to a sound studio on wheels is one of the claims from Maplin for their new add-on In-Car Stereo 6X CD Autochanger System. Mind you at £329.95 it's only what you'd expect.

The unit takes standard 5 in. discs and also 3 in. types with adaptors (not supplied). A stereo pair of phono sockets are supplied for the audio output, but if the radio cassette does not have spare CD inputs, there is no problem. The CD autochanger includes an ingenious v.h.f. f.m. modulator which can be simply inserted between the plug of the aerial lead and input socket of the radio unit – in principle just like a video recorder between antenna and TV at home.

The f.m. modulator provides an interface between the CD autochanger and the f.m. stereo radio. But please note: The radio unit *must* be f.m. stereo – the unit cannot work with MW and LW receivers.

The main CD autochanger player can be fitted distant from the existing stereo system, and is remotely controlled via a small keypad which can be fitted on the dashboard by means of the self-adhesive Velcro pad supplied.

THE NEXT 21 YEARS

BARRY FOX



FOR at least ten years the Japanese electronics companies have been trying to engineer the marriage of audio and video. They have many times promised consumers a single AV centre in the living-room, with TV screen, hi-fi sound system, video tape and disc and surround-sound speakers, perhaps with a computer keyboard and telephone tagged on. But most consumers – if only for convenience in room layout – still prefer to have a separate TV set and hi-fi system in different parts of the room, a telephone on the wall or table, and a computer in another room.

The situation is likely to change over the next ten years, because it becomes increasingly hard to draw any dividing line between audio, video and telecommunications. Also consumers are becoming increasingly unhappy with the proliferation of different boxes which serve related functions and all require their own cobweb of wiring. The time will soon, finally be right for a more unified approach to electronics in the home.

DIGITAL RECORDING

No-one can yet predict which of the two competing new digital home recording systems (DCC or Mini Disc) will win the standards battle due this winter, or whether both will fail and let recordable CD fill the gap. Whatever happens, digital sound recording will become a way of life, and with it legislation and technology to restrict cloning but at the same time legitimize some degree of copying – probably with the implementation of a tax on blank media.

Until now, making an audio recording has been a relatively troublesome business, with the need to set gain controls to avoid overload, or rely on automatic gain control circuitry which compresses the sound. With digital recorders, making a copy is as easy as copying computer data from disc to disc.

Once the public gets a feel for this there will be no turning back – just as people who have bought CD players seldom go back to playing vinyl LPs. It is not so much the sound quality which sells CDs, but the glorious convenience of the system.

ARMCHAIR RECORD STORE

From the success of any home digital audio recording format, it will be a logical step to combination units, which hard wire a CD player to a digital recorder. Digital audio broadcasting, whether by terrestrial transmitter or satellite, will open the door to what has been dubbed "the armchair record store". This is a digital recorder

which copies broadcast material, for a fee, and with copyright payment, as an alternative to record retailing.

Digital TV, whether conventional or high definition, will provide more channels from available terrestrial and satellite bandwidths. Viewers will need a digital decoder, which will probably double as a de-scrambling device for subscription entertainment and very probably control a VCR to tape and decode only what the viewer has paid to watch.

The advent of digital TV transmission will create the need for a new kind of home video recorder, which works digitally. This will tape the raw broadcast data stream for later decoding. Where several programmes are interleaved into the same stream, the video recorder will tape them all. When the tape is replayed the viewer will be able to decide which one to decode and watch. If some or all of the programmes are scrambled, the viewer will have to pay a fee to decode and watch them.

The broadcasters are already using digital video recorders to originate and edit programmes. The advantage of digital recording is that it allows repeated copying, through many generations, without loss of quality. For special effects work, TV producers may well have to copy through a dozen generations. There are several different digital formats on offer to professionals and as the technology matures it will become cheap enough to spin off into the domestic market.

HOME VIDEOS

Many people already use camcorders to make point and shoot video movies. An increasing number of hobbyists edit their home videos. These people will welcome the chance to use digital technology, and so avoid generation loss.

Recordable discs systems will let editors work much faster than they can from tape. Sony's Mini Disc may well find applications in video, with first generation units recording video as an f.m. analogue signal and later as digital code.

All the new digital audio and video formats will rely heavily on compression, with data rate drastically reduced by real time analysis of the signal by a coder which discards any redundant information.

INTERACTION

The new audio and video transmission technologies will be used with cable systems, and with the added benefit of interaction. Viewers will be able to control the choice of programmes and services sent to them by feeding signals back up the same cable. They will be able to vote too,

whether in quiz shows or political ballots.

Although a lot of effort has been made to provide interaction control without a keyboard, this will change. To anyone who uses a keyboard, it is infuriatingly clumsy to have to type text by using a mouse or similar control to select letters from a displayed alphabet. And more and more people are growing up with keyboards. Within a few years it will be commonplace to provide TV viewers with a portable keyboard which connects to the TV set by infra red link.

The growth of cable will be stimulated by growing realisation by the public that the Mercury service already offered or promised by twenty cable franchises gives a hassle-free alternative to British Telecom's practical monopoly to date.

Much of the talk about video phones is ill-informed, because few people need or want to watch who they are talking with by phone. Picture information can most easily be sent by fax. But cable links and/or the new ISDN phone lines should make it easier for video phones to provide security surveillance. This will marry the phone to a domestic TV screen.

CD-I

Although no-one knows how long it will take, interactive CD (almost certainly Philips CD-I format) will become a way of life, with games probably seeding a new revolution in home entertainment and education. Kodak's Photo CD looks likely to be a short lived product, simply because the compatibility bridge between CD-I and Photo CD has already made the Photo CD player little more than a CD-I player with a few microchips or wires removed to justify the lower price.

With full motion video, and Photo CD imaging technology, and the ability to play CD audio discs, the CD-I player could become the CD player of the future. There is likely to be a second standard, which quadruples the amount of information stored on disc, thereby doubling picture quality and playing time. This makes the five inch disc a carrier for movies as well as games, education, audio etc. So although digital FMV picture quality cannot yet match the twelve inch analogue Laser Disc, this will change. Pioneer, currently relaunching Laser Disc in Europe, is researching digital video technology.

STANDARD

The big advantage of digital video disc is not that the programme can be easily copied many times. Indeed this is seen by the movie studios as a very real disad-

vantage, and they will press for electronic copy controls similar to the Serial Management Copy System already adopted as a standard feature for digital audio recorders. The real advantage is that digital video can be made standards-independent. One disc or tape will play in any country, regardless of local TV standard.

This will apply both to conventional TV formats, and the new widescreen and high definition formats that will move into the home over the next decade. It is too early yet to predict which formats will prevail, except to be sure that the long term future must be digital.

The transition from conventional 4:3 TV screens to widescreen 16:9 displays will be governed more by artistic, than technical, considerations. Producers and broadcasters have to decide how to make programmes shot in 16:9 format acceptable to viewers with 4:3 sets, and how best to display 4:3 programmes in widescreen ratio.

All these strands lead to some simplification and rationalization of the mess of equipment now cluttering homes. Quite simply homes of the future will run out of space for separate boxes, and will stop buying unless they are presented with an acceptable alternative.

At the same time there should be a trend towards portable information centres, a Data Discman/CD-I player which sits on the desk or by the telephone, providing information such as telephone numbers from Yellow Pages or the standard telephone directory. But this will only happen when colour I.C.D. screens of reasonable size become affordable – and when British Telecom abandons its policy of charging over £2000 a year for use of directory data on a disc that cost only around £1 to press.

Public concern for the environment may help here. Why spend around 30 million a year on cutting down trees to print paper directories when all the information can be stored on a single piece of plastics, five inches in diameter?

CHOICES

Over the next decades it is clear that the consumer will be asked to make many choices between competing new technologies. It is also clear that legislators will be asked to make choices, for instance on the type of technology to be used for digital audio and TV broadcasting, and on the vexed question of taxing blank media.

The already tangled relationship between consumers' freedom of choice, natural rivalry between manufacturers and the need for governments to keep some kind of control on broadcasting, will become increasingly difficult to unravel.

Only one factor will remain constant. While the hardware industry struggles to keep prices down, the software industry will struggle to keep prices up. This, of course, is why the cash-rich Japanese electronics companies are already buying Western music, film and TV archives – and why they will continue to do so until the West has nothing left to sell.

HISTORY FORETELLS THE FUTURE

Here history foretells the future. Just look in your local electronics store and see how much of last year's hardware is still on sale. Then look in your local record and video shop and see how much old software is still being repackaged at a healthy price.

Special Feature

TOMORROWS TECHNOLOGY

IAN POOLE

TECHNOLOGY is advancing at an ever increasing rate. The necessity to stay ahead of the competition feeds companies with the incentive to spend many millions of pounds each year on research and development. This brings many advantages to the electronics enthusiast.

New components which are much better than anything previously available are constantly being launched onto the market. It does not normally take long after they are launched for them to fall in price quite dramatically and become normal everyday devices.

BRIEF HISTORY

To illustrate this fact it is worth looking back over technological advances of the past 21 years. Some of the components we take for granted today were very much at the forefront of technology, if they were even available, at that time. The one which stands out above all the others must be the introduction of the microprocessor.

The first processor was in fact launched 21 years ago in 1971. Designed by the Intel Corporation, microprocessors arose out of the first calculators which were beginning to hit the market.

The first microprocessor was the 4004. It contained about 2500 transistors – a very large number for a single I.C. at the time, and it used a 4-bit word.

Along with the processor itself Intel launched a number of other companion I.C.s. These included a RAM I.C., memory control, and an I/O expansion chip.

A year later Intel announced their first 8-bit processor, the 8008. Then in 1974 this was followed by the 8080. This processor was a great improvement on the previous chips. It used NMOS technology for increased speed and it soon became an industry standard.

Intel was not the only company in the microprocessor race, many other manufacturers started to produce them. These included many famous names. One was Motorola who launched their 6800, also in 1974.

MICRO-PROCESSOR DEVELOPMENT

The introduction of the microprocessor was a revolution in itself. It reflected many of the advances which were taking place particularly in I.C. manufacture. However, developments within the whole field of electronics were involved. If these had not been made then the idea of a microprocessor would not have been possible.

One of the major advances which enabled the very large scale integration used in microprocessors to become possible was the development of MOS technology. Bipolar I.C.s were limited in the number of transistors which could be placed on a single chip. This was because of the current they consumed and the resulting heat which had to be dissipated.

The foundations for MOS technology were laid in 1959 when the first F.E.T.s were produced. They caught on only slowly because they were expensive and unreliable. However development continued and improvements came. By 1970 MOS technology was well established and it was widely used. Suitably refined silicon was available. In addition to this complementary MOS (CMOS) was becoming a standard because it enabled less power to be used than ordinary bipolar technologies.

The development which led to all of this was the integrated circuit itself. Two people are credited with its discovery. One was Jack Kilby who worked for a small company called Texas Instruments. The other was Bob Noyce of Fairchild (who later co-founded Intel). They were both investigating ways of making electronics equipment smaller. By the end of 1961 their work had led to both their companies producing small quantities of I.C.s.

During the 1960s and 1970s a tremendous amount of effort was placed into research of I.C. technology. The American defence and space industries gave impetus to these developments and gradually their cost fell and they became far more widely used.

In fact, today much of the research and development in the electronics industry is devoted towards I.C. technology. Some of it may not bear any fruit, but some of it may be just as revolutionary as the I.C. or the microprocessor.

CURRENT EXAMPLES

Today a very large amount of research is allied to improvements in computer related technologies. This is not to say that other areas of electronics are not seeing major developments. However computer sales represent one of the major electronics sales areas.

Within the computer related developments there are a number of main areas of research. Size is obviously one major concern. Although today's personal computers represent a considerable achievement in terms of miniaturisation there is still a need to make the basic elements within I.C.s smaller. If this can be done then operating speeds can be increased

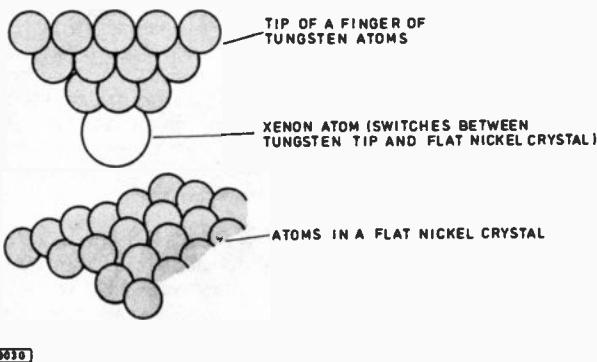


Fig. 1. Structure of the atom sized switch.

and production costs for the final units can be reduced.

One interesting development is being undertaken at IBM's Research Centre in California. It is aimed at enabling much more to be packed into integrated circuits. Currently the dimensions of the smallest transistors are around $0.5\mu m$. It is expected that this will be reduced to about half by the end of the century. This naturally limits the ultimate size of any i.c. which is made.

To make any major reductions in the size of basic i.c. components a complete review in thinking is needed. This is exactly what the IBM researchers have been doing. They have performed some experiments which have shown how the movement of a single atom can act as a switch.

In these experiments a single atom was successfully moved between two electrodes spaced apart by a few atom diameters (Fig. 1). The effect was monitored by looking at the change in tunnelling current as the atom changed its position. The two different values of current can then be equated to the different logic levels.

Unfortunately it is not easy to demonstrate the effect. A temperature of -269 degrees C is required together with some very specialised equipment. It is hardly surprising that the effect is not in a state where it can be used commercially. However it is likely to have an impact on future generations of miniaturised devices. Also if a method is found whereby it can be incorporated into an i.c. then it could help solve many of the problems facing i.c. designers today.

SUPER-CONDUCTING I.C.s

Another interesting idea which is more likely to bring some direct results in the near future uses superconducting technology in i.c.s. The advantage of it is that it enables i.c.s to operate at very fast speeds whilst dissipating only minute amounts of power. This is a great advantage because today's fast i.c.s are power hungry. This is a problem because the heat generated by the i.c. has to be removed otherwise the chip will overheat.

Using this superconducting technology, a company in the USA, called Hypress Inc. has made a shift register. It can operate at frequencies up to $4GHz$ whilst only dissipating $40\mu W$. In fact it is estimated that i.c.s using these techniques could be able to operate at $25GHz$ and more.

Another advantage of these devices is that the fabrication process uses temperatures of only 150 degrees C. This means that it is ideal for making i.c.s with both

silicon and gallium arsenide on the same chip.

The first superconducting i.c.s are likely to find uses in military equipment, particularly in radar systems where very high speed signal processing is required. Another use is in radio communications equipment where very high speed analogue to digital converters

type of structure in gallium arsenide. By generating a new type of structure called a complementary HFET (C-HFET) Honeywell have been able to create complementary structures.

The first departure from the normal is that these chips do not consist of straight gallium arsenide. Instead they use a structure containing aluminium gallium arsenide and indium gallium arsenide to achieve much better results. Like CMOS this new structure only draws current when it changes state. This means that power consumption is considerably reduced and integration levels can rise.

To produce the new structures required for this process it has been necessary to use a process called molecular beam epitaxial deposition. This enables the very precise structures required for the C-HFETs to be made (Fig. 2).

Although the development of these devices is still in its very early stages, a 4K bit static RAM has been produced. In tests this had an access time of only $4nS$ and it dissipated only $100mW$. This is about one fifth of that used by a standard gallium arsenide memory of the same size. These new devices are not available yet because there is still plenty of work to do. However they are likely to be very much in demand when they hit the market place.

3-D STORAGE

Memory development is one area of electronics which is also receiving plenty of attention. Whatever the capacity of disc drives people always want more. This has fuelled development of various storage media for many years. It is only about 15 years since disk drives for anything apart from a personal computer were housed in 19 inch rack mounting units. Now with much smaller disk drives available, development is still progressing quickly.

One of the major problems with disk storage is that it is relatively inefficient in terms of space because it can only use the surfaces of the discs. When the two sides of the disc are insufficient then several disks can be stacked to increase the capacity. Unfortunately this does not really overcome the root of the problem.

To overcome this a new idea of using 3-D storage blocks is being developed. Data can be stored in all positions in the cube and this means that the storage capacity can be dramatically increased.

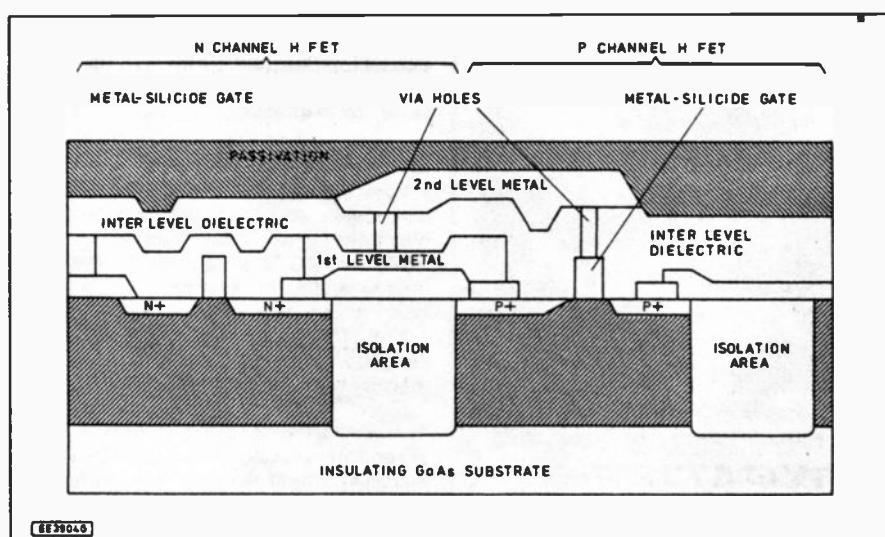


Fig. 2. C-HFET structure. In view of the complicated nature of the C-HFET it can be seen that it was not easy to develop.

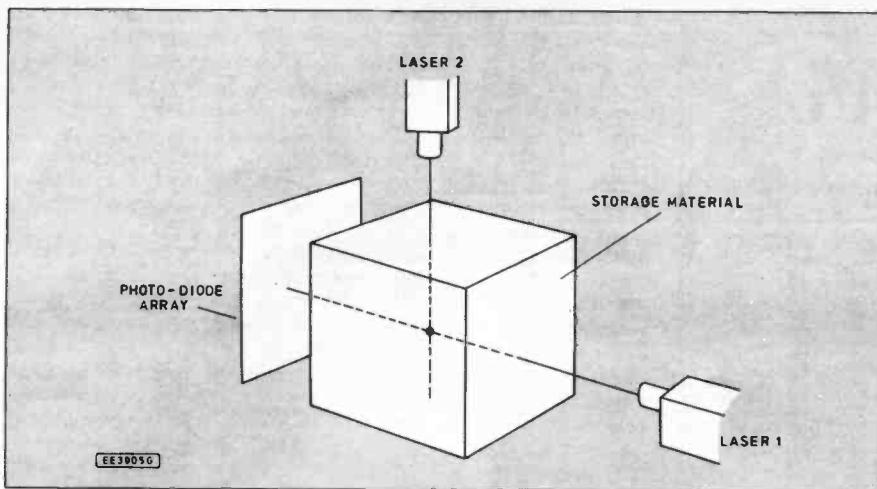


Fig. 3. 3-D storage medium.

NEW MATERIALS

To achieve this, radically new techniques and materials are needed. The basic idea involves the use of a specialised organic material which changes state when it is energised by two intersecting light beams. It is very fast and its storage density is very high. In fact the density is limited by the definition and registration of the light beams and not the material, which works at the atomic level.

The system is based around the fact that the material is normally absorbent to UV light and clear to wavelengths in the visible section of the spectrum. However when it is excited by two intersecting beams of light, its absorbency changes (Fig. 3). It then starts to absorb light in the red/green part of the spectrum. These two states of absorbency can be used to represent the two digital states.

To read data from the material an equivalent process is used. Two intersecting UV beams detect the absorbency of the material. The resulting light can then be detected by an array of photodiodes which convert the information into electrical signals.

Although the write process is fast, it can be speeded up even further by projecting an array or pattern of data onto the material. The second light beam is then used to fix the data in the correct plane in the cube. Using the process in this way large amounts of data can be stored exceedingly quickly.

Work on this idea is still very much in its experimental stages and there are many problems to be overcome. One is that the storage material which is used at the moment is only stable at low temperatures. If the process is to be widely used then it must be able to operate at room temperature. To achieve this other substances are being investigated.

The possibilities of this new technology are very exciting. Its size and speed mean that it could very quickly out-perform any other type of storage for many years to come. There are even further possibilities. Being an optical form of storage it could be ideal in linking into optical computers which are being discussed as the next revolution for the future. Not surprisingly many companies are taking a keen interest in this work.

NEW BATTERIES

Not all the developments which are taking place in electronics are associated with computers. Some are equally important and likely to have a large impact on the electronics world. One interesting area for research is in batteries.

Existing technologies have many drawbacks. Non-rechargeable or primary cells are expensive. They have to be discarded once they are used despite the fact that they remain basically intact after use. Their disposal also poses problems in this age when people are rightly conscious about the environment.

Rechargeable cells offer a very attractive alternative. Of the technologies which are available NiCads hold a virtual monopoly despite a number of difficulties. Firstly they only produce 1.2 volts instead of the 1.5 produced by a primary cell. They also have a finite number of charge/discharge cycles. Under ideal conditions this can be as many as several thousand, but under normal use it is somewhat less. One major mode of failure occurs as a result of the mechanical stresses which are set up in the cathode as a result of even normal use.

A new battery technology which is emerging could overcome these problems. The batteries use a form of ceramic called a ternary oxide. There is a wide variety of these ceramics and by choosing the correct types voltages over a relatively wide range can be generated. This means that it is possible to make batteries using this technology which will give a voltage of 1.5 volts.

The other advantage of these ceramic batteries is that they can endure an almost unlimited number of charge/discharge cycles. This results from the fact that there are almost no internal stresses set up during normal use: a fact which has been verified using X-rays.

Work is progressing quite rapidly on developing these cells. Although the results look very promising it will still be a few years before they are available.

SILICON LIGHT

Light emitting diodes are now a standard component, used in a wide variety of applications. However they have always been made from gallium arsenide. Whilst gallium arsenide performs very well it is difficult to handle and more expensive than silicon. If a process could be devised to use silicon then enormous savings could be made in view of the extensive use of I.e.d.s.

Some progress is now being made towards this goal. The key to it is based around a process being developed by Siemens. It involves an electrochemical process which creates minute pores in the silicon about 1nm in diameter.

These holes have the effect of restricting the movement of the charge carriers i.e. holes or electrons. In turn this causes the silicon to exhibit properties more like that

of gallium arsenide where light emission and absorption are concerned.

Work is still in its early stages. Experiments using the treated silicon have shown that it can be stimulated into generating red or yellow light when exposed to a blue laser. The actual colour of the light which is generated is dependent upon the size of the pores. Now it remains to generate light using an electric current.

FOR THE FUTURE

It is very difficult to gaze into the future and predict how the electronics world is likely to be in 21 years time. A few people have managed to produce predictions which have come true. For example Isaac Asimov talked about a man using a small hand-held calculating machine with its red numerals. This was many years before the calculator with either I.e.d. or I.c.d. displays was available.

To have an idea of what technology may be like in a few years time it is possible to look at today's research and see where it could lead. Alternatively one can look at today's needs and see how this could stimulate research and development.

SMALLER AND FASTER

Much of today's research seems to be associated with faster, more powerful and smaller computers with more memory. The need for this seems to have been amply demonstrated by the fact that whenever a more powerful computer comes on the market then it can be used immediately. The same can also be demonstrated with even the comparatively humble PC. Ever larger programs are being written which require more memory and higher speeds.

The original 8080 or 8086 machines cannot cope with most programs on the market today. Even the 286 machines are becoming obsolete and the 386 is being overtaken by the 486.

Storage is another area where there will be major advances. PCs today now have the disc storage capacity which only a large machine would have had ten or fifteen years ago. With this in mind it is quite possible that ideas like the 3-D storage system could become a reality relatively soon.

However one area which desperately needs to be addressed is that of the user friendliness of computers and computer related products. Even video recorders and similar items can be far too complicated for the non-technical man in the street. Far more research needs to be put into the man-machine interface. Currently this is the most difficult area of any computer product.

Apart from computer products there will be major advances in personal communications. Cellular phone technology has proved to be a great success and has shown that there is a need for flexible mobile communications. In the years to come this form of communications will become cheaper and more reliable. However whether there is a real need for a global system remains to be seen. After all most people really only want to speak regularly to someone less than 30 miles away.

Like all technology, the developments we see in the next 21 years will vary. Some will be good and others may seem like a retrograde step. What is certain is that the developments will be exciting. With what currently appears to be on the horizon the next 21 years will be just as exciting as the last 21 if not more so!

VIEWCOM

TEL 081-471 9338 TLX 929709 VICOM G FAX 081-552 0946

DIGITAL INTEGRATED CIRCUIT SPECIALIST

4000 SERIES	4513B	2.60	7406A	0.33	74L574A	0.18	74LS375	0.44	74HC4125	0.31	74HC4518	1.08	74C902	0.86	74F1243	2.41	4514BT	1.76	
	4514B	0.84	7407	0.30	74L575	0.21	74LS377	0.58	74HC4126	0.32	74HC4520	0.59	74HC4520	1.08	74F1244	2.12	4516BT	0.81	
4000B	0.10	4515B	0.68	7407A	0.32	74L576	0.22	74LS378	0.62	74HC4127	0.27	74HC4543	0.55	74HC4538	1.02	74C903	1.52	4518BT	0.94
4000UB	0.11	4516B	0.33	7412	0.40	74L576A	0.24	74LS379	0.86	74HC4130	0.31	74HC7001	0.68	74HC7046A	2.80	74C907	0.86	4520BT	0.94
4001A	0.11	4517B	0.96	7408	0.33	74L577	0.24	74LS381A	3.05	74HC4137	0.44	74HC7002	0.68	74HC740102	1.64	74C911	14.42	4521BT	0.86
4001B	0.10	4518B	0.29	7410	0.15	74L578	0.00	74LS385	2.22	74HC4138	0.43	74HC700	0.22	74AC11	0.49	74F00	0.28	4522BT	0.25
4001UB	0.12	4519B	0.28	7413	0.27	74L578A	0.22	74LS386	0.46	74HC4151	0.43	74HC703	0.22	74AC20	0.49	74F04	0.28	4523BT	0.25
4002B	0.11	4520B	0.32	7414	0.28	74L583	0.34	74LS390	0.39	74HC4152	0.43	74HC704	0.22	74AC21	0.49	74F06	0.28	4524BT	0.25
4006B	0.29	4521B	0.82	7416	0.33	74L583A	0.37	74LS393	0.34	74HC4153	0.55	74HC704	0.22	74AC22	0.49	74F07	0.28	4525BT	0.25
4007B	0.11	4522B	0.72	7417	0.30	74L585	0.34	74LS395	0.66	74HC4154	0.55	74HC704	0.22	74AC23	0.49	74F08	0.28	4526BT	0.25
4008B	0.31	4526B	0.46	7420	0.20	74L586	0.22	74LS395A	0.68	74HC4155	0.51	74HC704	0.22	74AC24	0.49	74F09	0.28	4527BT	0.25
4009AE	0.16	4527B	0.48	7425	0.15	74L590	0.24	74LS398	1.64	74HC4156	0.51	74HC704	0.22	74AC25	0.49	74F10	0.28	4528BT	0.25
4009UB	0.16	4528B	0.46	7426	0.20	74L591	0.50	74LS399	1.22	74HC4157	0.53	74HC704	0.22	74AC26	0.49	74F11	0.28	4529BT	0.25
4010B	0.18	4529B	0.62	7427	0.18	74L592	0.29	74LS399	0.65	74HC4158	1.30	74HC704	0.22	74AC27	0.49	74F12	0.28	4530BT	0.25
4011B	0.11	4530B	1.48	7430	0.22	74L593	0.24	74LS445	1.50	74HC4159	0.43	74HC704	0.22	74AC28	0.49	74F13	0.28	4531BT	0.25
4011UB	0.12	4531B	0.88	7432	0.27	74L595	0.36	74LS450	5.00	74HC4160	0.45	74HC704	0.22	74AC29	0.49	74F14	0.28	4532BT	0.25
4012AE	0.11	4532B	0.32	7437	0.24	74L596	0.46	74LS461A	4.97	74HC4161	0.49	74HC704	0.22	74AC30	0.49	74F15	0.28	4533BT	0.25
4012B	0.11	4534B	3.98	7438	0.38	74L597	0.25	74LS465	2.75	74HC4162	0.52	74HC704	0.22	74AC31	0.49	74F16	0.28	4534BT	0.25
4013B	0.17	4536B	1.98	7440	0.48	74L598	0.28	74LS467	2.75	74HC4163	0.40	74HC704	0.22	74AC32	0.49	74F17	0.28	4535BT	0.25
4014B	0.26	4538B	0.57	7442	0.38	74L599	0.25	74LS468	2.75	74HC4164	0.45	74HC704	0.22	74AC33	0.49	74F18	0.28	4536BT	0.25
4015B	0.31	4539B	0.62	7445	0.70	74L599A	0.28	74LS469	4.88	74HC4165	0.32	74HC704	0.22	74AC34	0.49	74F19	0.28	4537BT	0.25
4016B	0.18	4541B	0.32	7446	0.84	74L599B	0.25	74LS470	0.90	74HC4166	0.41	74HC704	0.22	74AC35	0.49	74F20	0.28	4538BT	0.25
4017B	0.25	4543B	0.62	7447	0.84	74L599C	0.27	74LS471	5.90	74HC4167	0.49	74HC704	0.22	74AC36	0.49	74F21	0.28	4539BT	0.25
4018B	0.26	4544B	1.48	7447A	0.90	74L599D	0.25	74LS472	2.60	74HC4168	0.49	74HC704	0.22	74AC37	0.49	74F22	0.28	4540BT	0.25
4019B	0.22	4547B	1.78	7451	0.25	74L599E	0.27	74LS473	0.93	74HC4169	0.44	74HC704	0.22	74AC38	0.49	74F23	0.28	4541BT	0.25
4020AE	0.29	4549B	4.24	7454	0.40	74L599F	0.25	74LS474	0.76	74HC4170	0.44	74HC704	0.22	74AC39	0.49	74F24	0.28	4542BT	0.25
4020B	0.28	4551B	1.06	7470	0.27	74L599G	0.27	74LS474	4.43	74HC4171	0.54	74HC704	0.22	74AC40	0.49	74F25	0.28	4543BT	0.25
4021B	0.31	4553B	1.82	7472	0.18	74L599H	0.33	74LS475	0.25	74HC4172	0.54	74HC704	0.22	74AC41	0.49	74F26	0.28	4544BT	0.25
4022B	0.32	4554B	4.62	7473	0.23	74L599I	0.33	74LS475	4.18	74HC4173	0.54	74HC704	0.22	74AC42	0.49	74F27	0.28	4545BT	0.25
4023B	0.11	4555B	0.32	7474	0.35	74L599J	0.28	74LS475	1.62	74HC4174	0.54	74HC704	0.22	74AC43	0.49	74F28	0.28	4546BT	0.25
4030B	0.15	4556B	2.34	7491	0.25	74L599K	0.30	74LS476	1.14	74HC4175	0.54	74HC704	0.22	74AC44	0.49	74F29	0.28	4547BT	0.25
4031B	0.085	4557B	0.30	7492	0.42	74L599L	0.35	74LS476	1.34	74HC4176	0.54	74HC704	0.22	74AC45	0.49	74F30	0.28	4548BT	0.25
4032B	0.08	4558B	1.98	7476	0.23	74L599M	0.28	74LS477	2.60	74HC4177	0.54	74HC704	0.22	74AC46	0.49	74F31	0.28	4549BT	0.25
4033B	0.22	4559B	1.78	7451	0.25	74L599N	0.27	74LS478	0.93	74HC4178	0.54	74HC704	0.22	74AC47	0.49	74F32	0.28	4550BT	0.25
4034B	0.72	4561B	1.68	7480	0.79	74L599O	0.25	74LS479	0.93	74HC4179	0.54	74HC704	0.22	74AC48	0.49	74F33	0.28	4551BT	0.25
4035B	0.36	4561B	1.80	7485	0.28	74L599P	0.28	74LS479	0.58	74HC4180	0.54	74HC704	0.22	74AC49	0.49	74F34	0.28	4552BT	0.25
4036B	0.25	4566B	2.52	7490	0.39	74L599Q	0.62	74LS479	6.25	74HC4181	0.54	74HC704	0.22	74AC50	0.49	74F35	0.28	4553BT	0.25
4037B	0.71	4567B	0.44	74107	0.72	74L599R	0.28	74LS479	3.74	74HC4182	0.54	74HC704	0.22	74AC51	0.49	74F36	0.28	4554BT	0.25
4038B	0.42	4568B	0.68	74110	0.41	74L599S	0.34	74LS479	1.76	74HC4183	0.54	74HC704	0.22	74AC52	0.49	74F37	0.28	4555BT	0.25
4039B	1.75	4569B	4.40	74116	3.10	74L599T	0.20	74LS479	1.66	74HC4184	0.54	74HC704	0.22	74AC53	0.49	74F38	0.28	4556BT	0.25
4040B	0.26	4569B	4.40	74119	1.98	74L599U	0.25	74LS479	1.34	74HC4185	0.54	74HC704	0.22	74AC54	0.49	74F39	0.28	4557BT	0.25
4041B	0.32	4569B	3.42	74121	0.48	74L599V	0.36	74LS479	1.34	74HC4186	0.54	74HC704	0.22	74AC55	0.49	74F40	0.28	4558BT	0.25
4042B	0.24	4720B	2.90	7420B	0.32	74L599W	0.25	74LS479	2.18	74HC4187	0.54	74HC704	0.22	74AC56	0.49	74F41	0.28	4559BT	0.25
4043B	0.29	4723B	2.87	7421	0.37	74L599X	0.30	74LS479	0.19	74HC4188	0.54	74HC704	0.22	74AC57	0.49	74F42	0.28	4560BT	0.25
4044B	0.68	4724B	1.30	74212	0.80	74L599Y	0.28	74LS479	1.88	74HC4189	0.54	74HC704	0.22	74AC58	0.49	74F43	0.28	4561BT	0.25
4045B	0.27	4725B	1.72	74215	0.30	74L599Z	0.25	74LS479	0.93	74HC4190	0.54	74HC704	0.22	74AC59	0.49	74F44	0.28	4562BT	0.25
4046B	0.11	4726B	1.36	74216	0.30	74L599A	0.25	74LS479	0.84	74HC4191	0.54	74HC704	0.22	74AC60	0.49	74F45	0.28	4563BT	0.25
4047B	0.11	4727B	1.72	74217	0.30	74L599B	0.25	74LS479	0.84	74HC4192	0.54	74HC704	0.22	74AC61	0.49	74F46	0.28	4564BT	0.25
4048B	0.31	47245	1.36	74205	0.10	74L599C	0.34	74LS479	0.84	74HC4193	0.54	74HC704	0.22	74AC62	0.49	74F47	0.28	4565BT	0.25
4049B	0.38	47257	1.31	74206	0.10	74L599D	0.50	74LS479	1.15	74HC4194	0.54	74HC704	0.22	74AC63	0.49	74F48	0.28	4566BT	0.25
4050B	0.34	47307	1.11	74207	0.10	74L599E	0.34	74LS479	0.84	74HC4195	0.54	74HC704	0.22	74AC64	0.49	74F49	0.28	4567BT	0.25
4051B	0.71	47307	1.10	74208	0.20	74L599F	0.36	74LS479	0.84	74HC4196	0.54	74HC704	0.22	74AC65	0.49	74F50	0.28	4568BT	0.25
4052B	0.34	47307	1.20	74209	0.10	74L599G	0.34	74LS479	0.84	74HC4197	0.54	74HC704	0.22	74AC66	0.49	74F51	0.28	4569BT	0.25
4053B	0.32	47307	1.11	74210	0.10	74L599H	0.34	74LS479	0.84	74HC4198	0.54	74HC704	0.22	74AC67	0.49	74F52	0.28	4570BT	0.25
4054B	0.74	47307	1.12	74211	0.10	74L599I	0.34	74LS479	0.84	74HC4199	0.54	74HC704	0.22	74AC68	0.49	74F53	0.28	4571BT	0.25
4055B	0.20	47307	1.13	74212	0.10	74L599J	0.34	74LS479	0.84	74HC4200	0.54	74HC704	0.22	74AC69	0.49	74F54	0.28	4572	

MICROPROCESSOR & SUPPORT ICs	P82C54-2	4.80	HW2256L-P10	7.93	ADC0817CCN	23.96	ICL7652BCPD	5.82	LM239N	1.26	LM741CN	0.26	SL360GCM	13.91	2N2369	0.24	2SC1845	0.20	
	PCF6584P	7.30	HW2646ALP-12	3.95	ADC094CCN	6.81	ICL7686CPA	1.40	LM248J	7.72	LM741H	0.40	SL486DP	2.98	2N2369A	0.24	2SC2009	0.38	
	PCF6586P	6.75	HW2646ASP-20	3.95	ADC094CCN	12.69	ICL7688CPA	3.24	LM2575T-12	6.26	LM741U	3.06	SL490B	2.51	2N2484	0.32	2SC2180N	8.95	
6321P	4.20	PCF6566T	6.75	HW2657SP-5	5.07	ADC84KGK-10	12.60	ICL7683CPA	3.12	LM2575T-15	6.26	LM748CH	0.56	SL6700CDP	5.47	2N2894	0.76	2SC2235	0.58
6348SPC32/SMD	32.50	PCF6570P	4.93	HW26812BLB-80	18.55	ADC3501CCN	23.67	ICL7684CPA	3.95	LM2575T-5.0	6.26	LM748CH	2.20	SL952DP	7.26	2N2905	0.32	2SC2238	0.76
63803XP	11.95	PCF6573P	5.81	HW66204L-12	15.80	ADG201AKN	3.60	ICL7685CPA	4.42	LM2575T-12	7.16	LM740CN	0.78	SN57107AN	1.57	2N2905A	0.32	2SC2238	0.68
65002	3.40	PCF6574P	5.90	KM62256ALP-10	4.95	ADP070CN	1.60	ICL7687CPA	2.66	LM2577T-12	7.07	LM77000CP	2.98	SN57107BN	1.57	2N2907	0.30	2SC2240	0.24
65020A	3.90	PCF6574T	5.90	LH1564D-10L	2.40	AM0015CD	17.20	ICL7680CPA	2.74	LM2577T-15	7.07	LM77000CP	1.52	SN57108BN	2.08	2N2907A	0.30	2SC2275	0.56
6520P	3.89	PCF6577T	7.70	P2114AL-2	3.40	AY-3-1276	3.60	ICL7673CPA	1.60	LM2577T-12	7.76	LM77000ACZ	0.30	SN57109AN	2.46	2N2923	0.32	2SC2230	0.56
6522	3.60	PCF6591P	9.35	P2114AL-4	3.40	AY-5-1013A	3.20	ICL8038CPD	4.70	LM2578H	8.26	LM77000CP	1.57	SN57109AN	1.57	2N2924	0.78	2SC2278	1.18
6522A	7.95	P6502AP	9.95	PCD5101P	3.30	AY-5-1013A	5.24	ICL8052CA2CPD	12.85	LM2578H	3.67	LM7912CT	0.36	SN57110AN	4.50	2N3053	0.34	2SC2362	0.20
6551	3.10	P6502P	3.89	UPD43256AGU10L	8.33	AY-5-1013B	6.45	ICL8088ACJD	13.40	LM2578T	1.51	LM7915CT	0.40	SN57113AN	4.57	2N3055	0.68	2SC2368	0.44
6551A	3.80	P6522	3.20	UDP43256C-12	5.60	BA6109	1.68	ICL8088CCSQ	2.59	LM2601N	1.16	LM833N	1.48	SN57114AN	4.57	2N3441	1.20	2SC2407	1.94
65C02P2	6.90	P6522AP	7.95	UPD434C-15	4.70	BA6208	1.40	ICL8088CSQ	2.88	LM2601N	0.98	LM837N	2.01	SN57115AN	3.60	2N3584	1.68	2SC2579	1.30
65C02P3	6.90	P65C02P2	5.84	UVPROMS															
65C102P2	8.40	P65C02P3	6.90	UVPROMS															
65C22P2	5.67	P65C22P2	5.67	UVPROMS															
65C51E1	3.85	P65C102P2	7.34	TC2128C-2	2.95	CA3028AE	0.52	ICL821CPA	2.28	LM2604N	1.79	LM75124N	2.42	SN3702	0.10	2SC2591	1.38		
65C51E2	4.45	SAB803C2P	6.75	TC2764A-15	2.74	CA3046	0.76	ICM7070P	7.68	LM817N	1.34	SN57136N	3.10	2N3704	0.10	2SC2603	0.38		
66000CP10	6.02	TMP8085AP-2	3.60	TC2765-15	3.95	CA3046	0.80	ICM7070P	5.78	LM817N	3.55	SN57138N	4.41	2N3705	0.10	2SC2705	0.68		
66000CP12	7.72	TMS3477LN	12.10	TC2765-25	3.95	CA3053	1.57	ICM7111AMP	4.98	LM8295T	3.36	SN57140P	1.20	2N3789	2.16	2SC2708	2.38		
66000CP16	12.87	TMS7701C01N	2.85	TD2725E	5.40	CA3064	0.94	ICM7111AUJ	2.72	LM8294CT	2.79	SN57152N	6.36	2N3886	1.24	2SC3181N	3.24		
66000CP18	4.95	TMS9900NL	24.40	HW27101G-10	9.80	CA3065	1.20	ICM7117API	9.85	LM8294CT	2.79	SN57154N	1.98	2N3894	0.11	2SC3203	1.60		
66000CP19	7.70	TMS9901NL	7.22	HW27101G-10	16.83	CA3066	1.50	ICM7121API	10.42	LM8301AN	2.36	LM706CN	1.36	SN57155P	5.68	2N3895	0.10	2SC3281	2.84
66000CP8	5.95	TMS9920ANL	7.98	HW27C48F-20T	3.40	CA3079	0.68	ICM7121BDI	6.41	LM8304N	2.69	LM707CP	4.07	SN57157P	5.68	2N3905	0.10	2SC3294	5.00
6602P	2.47	TMS9920NL	7.34	HW27C48G-10	4.20	CA3080	0.70	ICM7121EUL	16.88	LM8305H	3.39	LM709CP	2.79	SN57158P	4.94	2N3958	2.12	2SC3277	0.20
6603P	4.98	TMS9914ANL	18.94	HW27C48G-20	4.20	CA3081	0.96	ICM7124API	9.24	LM8305H	2.39	LM7104CJ	9.80	SN57159N	5.77	2N3957	0.48	2SC3651	0.58
6605P2P	9.18	TMS9928ANL	4.20	HW44625P-10	4.50	CA3082	1.32	ICM7126BPI	25.04	LM8307N	0.80	LM7108C	7.02	SN57160BN	7.35	2N3960	2.20	2SC3669	0.68
6610P	2.98	TMS9959JOL	6.65	HW44628-12/25	4.55	CA3083	1.32	ICM7127API	12.90	LM8308N	2.03	LM7103CN	3.28	SN57161AN	9.31	2N4062	0.32	2SC373	0.68
6621P	1.52	UM8459S	4.65	HW44628-12/25	4.55	CA3084	0.80	ICM7128CP	7.72	LM8308N	1.59	LM7102CN	2.98	SN57162BN	11.76	2N4091	0.78	2SC3907	4.20
6640P	3.10	UPD6822C	3.60	ICM7128CP-10	2.40	CA3088	1.10	ICM7155P	0.84	LM8308N	0.48	LM7103CP	4.07	SN57172N	4.56	2N4123	0.10	2SC458	0.15
6644P	17.20	UPD6822AD	3.60	ICM7128CP-12	2.40	CA3089	2.01	ICM7156P	1.30	LM8308N	2.36	LM7104CP	2.79	SN57174N	4.56	2N4124	0.20	2SC459	1.68
6645P	8.88	UPD6828C	3.60	ICM7128CP-15	2.40	CA3090	2.16	ICL7104-16CPL	26.08	LM8308H	2.36	LM7107CT	4.07	SN57175P	5.68	2N4125	0.18	2SC459	1.68
6645P2	5.40	UPD70108C-8	6.95	ICL7126J-4	3.30	CA3097	0.45	ICL7106CP	6.75	LM8310H	4.81	LM7107CJ	10.54	SN57175N	5.28	2N4126	0.32	2SC459	1.68
6645P3	8.92	UPD70108C-10	9.10	ICL7126J-6	4.00	CA3100	1.58	ICL7107CPL	6.95	LM8310H	3.39	LM7108CT	10.54	SN57176P	6.00	2N4127A	2.96	2SC538A	1.68
6646P	7.02	UPD70118C-8	9.20	ICL7126J-8	4.00	CA3103	0.78	ICL7118CP	5.25	LM8310H	3.22	LM7108C	10.54	SN57176N	6.00	2N4127	2.24	2SC538	0.68
6646P9P	7.83	UPD70118C-10	12.90	ICL7126J-10	5.00	CA3103	0.47	ICL7118CP	5.35	LM8310H	2.27	LM7108C	10.54	SN57177P	6.00	2N4127	2.24	2SC538	0.68
6647P	3.03	UPD7201AC	6.80	ICM72C56D-25	4.95	CA3140E	0.47	ICL7126CP	5.35	LM8310H	2.27	LM7108C	10.54	SN57177N	6.00	2N4128	0.20	2SC459	1.68
6648P	4.83	UPD7201C	6.80	ICM72C56D-40	4.95	CA3141E	1.42	ICL7111CPA	1.32	LM8311H	2.26	LM7108C	10.54	SN57178P	6.00	2N4129	0.20	2SC459	1.68
6648AS0P	2.82	UPD7654C	5.42	TMS216J-4	4.58	CA3146E	1.16	ICL7212CPA	1.98	LM8317C	5.05	LM7109CP	9.45	SN57179P	6.00	2N4130	0.20	2SC459	1.68
6648B0P3	15.25	UPD8085AC-2	4.95	TMS2172BL-25	4.60	CA3180	1.25	ICL7680CPA	1.40	LM8317H	0.50	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6649P	9.25	UPD8085AC-4	4.95	TMS2172BL-40	5.60	CA3181	1.25	ICL7682CPA	3.24	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6650P	9.25	UPD8085AC-6	4.95	TMS2172BL-60	5.60	CA3181	1.25	ICL7683CPA	4.00	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6651P	3.60	UPD8085AC-8	4.95	TMS2172BL-80	5.60	CA3181	1.25	ICL7684CPA	4.78	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6652P	3.60	UPD8085AC-10	4.95	TMS2172BL-100	5.60	CA3181	1.25	ICL7685CPA	5.56	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6653P	3.60	UPD8085AC-12	4.95	TMS2172BL-120	5.60	CA3181	1.25	ICL7686CPA	6.34	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6654P	3.60	UPD8085AC-15	4.95	TMS2172BL-150	5.60	CA3181	1.25	ICL7687CPA	7.12	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6655P	3.60	UPD8085AC-20	4.95	TMS2172BL-200	5.60	CA3181	1.25	ICL7688CPA	7.89	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6656P	3.60	UPD8085AC-30	4.95	TMS2172BL-300	5.60	CA3181	1.25	ICL7689CPA	8.67	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6657P	3.60	UPD8085AC-50	4.95	TMS2172BL-500	5.60	CA3181	1.25	ICL7690CPA	9.45	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6658P	3.60	UPD8085AC-70	4.95	TMS2172BL-700	5.60	CA3181	1.25	ICL7691CPA	10.23	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6659P	3.60	UPD8085AC-100	4.95	TMS2172BL-1000	5.60	CA3181	1.25	ICL7692CPA	11.00	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6660P	3.60	UPD8085AC-150	4.95	TMS2172BL-1500	5.60	CA3181	1.25	ICL7693CPA	11.78	LM8318H	3.64	LM7232EW/SMD	4.95	SN57180N	6.00	2N4131	0.20	2SC459	1.68
6661P	3.60	UPD8085AC-200	4.95	TMS2172BL-2000	5.60	CA3181	1.25	ICL7694CPA	12.56	LM8318H	3.64	LM7232EW/SMD							

REACTION TIMER

T. R. de VAUX-BALBIRNIE

Just how fast do you think you are?

THIS Reaction Timer project was originally designed for fun at a party. However, it could have other more serious applications – in school science lessons, for example.

Reaction time is the time taken for a person to detect something (a stimulus) and for the brain to process it and make something happen. For example, when a child runs out in front of a car, the motorist applies the brakes as quickly as possible. The time elapsing between seeing the child (stimulus) and producing an action (pressing the brake pedal) is the reaction time.


The Highway Code uses the term *thinking distance* since here the reaction time is translated into the distance travelled at various speeds. This is more easily understood by motorists. For example, if a car is travelling at 30mph, the Highway Code tells us that the thinking distance is 30ft. A simple calculation can turn this into a reaction time:

$$30\text{mph} = 44\text{ft}/\text{second}$$

So 30ft. is covered in

$$30/44 \text{ second} = 0.7\text{s approx.}$$

Fig. 1. Complete circuit diagram for the Reaction Timer.

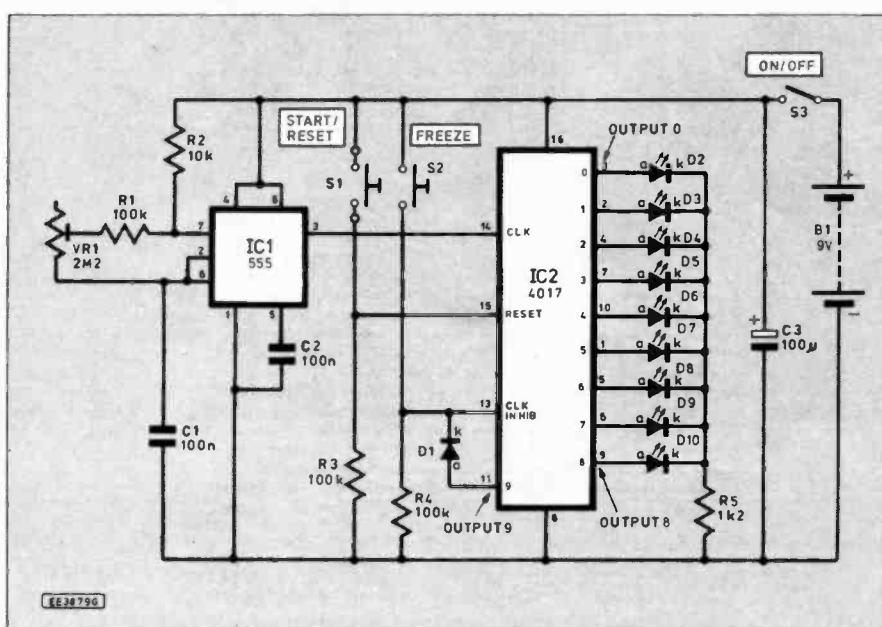

circuit panel and battery. The remote section has a Start/Reset pushbutton switch mounted on top.

TESTING TIMES

Two people are needed to perform the test. The person performing it (the tester) sits with the remote section in such a way that the person being tested (the subject) cannot see the Start/Reset switch and possibly anticipate the start. The subject sits in front of the main unit with his or her finger ready on the Freeze button.

The unit is switched on and the tester presses the Start/Reset button whereupon the first LED in the display lights up. After some random time the button is released.

At this point, the LEDs in the display operate one by one in rapid succession. As soon as the subject sees the first LED go off, he or she presses the Freeze button and keeps it pressed. This stops the display and the LED which remains lit indicates the reaction time against a scale of values marked alongside.

The button is now released ready for another try. Normally, several trials will be performed on the subject and an average time taken.

The prototype unit measures the reaction time in 0.1 second (100ms) increments up to 0.8s (800ms). If there is a delay of more than 0.8s between observing the display and pressing the button, the unit "locks out" automatically and all LEDs go off. The circuit could be adjusted at the setting-up stage to go up in larger steps, say, 150ms giving a maximum display readout of 120ms (1.2s).

In the prototype model, the first three LEDs are green, the next three yellow and the last three red. These could be used to indicate Good, Fair and Poor reaction times.

CIRCUIT DESCRIPTION

The full circuit diagram for the Reaction Timer is shown in Fig. 1. IC1 is a 555 timer IC which is connected as an *astable multivibrator*. Thus, while a supply exists – that is, with On-Off switch S3, on, pulses are produced continuously from the output, pin 3, at a nominal rate of 10 per second (10Hz).

The exact frequency depends on the values of fixed resistors, R1 and R2, preset potentiometer VR1 and capacitor, C1. To allow for component tolerances, and to enable different rates of operation, VR1 forms the adjustment for the pulse repetition frequency. The setting-up procedure for getting this right is described at the end.

The pulses supplied by IC1 are applied direct to the clock input pin 14 of IC2, a CMOS decade counter. This device has ten outputs, 0-9, each one (apart from number nine) being responsible for lighting one l.e.d. in the display, D2 to D10.

As each pulse is received, successive outputs 0-9 (pins 3, 2, 4, 7, 10, 1, 5, 6, 9 and 11 respectively go high (supply positive voltage) and each l.e.d. lights in sequence. Since only one l.e.d. is on at a given time, they can all share the same common current-limiting resistor, R5.

Normally, on the tenth pulse, IC2 would self-reset and begin a further cycle. To prevent this happening, so that timings above 0.8s are invalid, output 9 (pin 11), which has no l.e.d. connected to it, disables the i.c. by applying a high state to *clock inhibit* pin 13 through diode, D1.

Thus, output nine remains high continuously, further clock pulses then have no effect and all l.e.d.s are off. In use, the subject will try to press the Freeze button, S2, before the display reaches the last l.e.d. - this action also inhibits the clock by making pin 13 high.

The Start/Reset switch, S1, on the remote section resets the display by applying a high state to IC2 reset input (pin 15). In the reset state, output 0 goes high and the first l.e.d., D2, lights.

When S1 is released, pin 15 goes low via resistor R3 which enables the clock. The test then proceeds in the manner already described.

Since IC2 cannot supply a large output current, low current l.e.d.s were used in the prototype unit coupled with a relatively high value of current-limiting resistor, R5. Standard l.e.d.s could probably be used but they would not be very bright.

COMPONENTS

See SHOP TALK Page

Resistors

R1, R3,
R4 100k (3 off)
R2 10k
R5 1k2
All 0.25W 5%
carbon film

Potentiometer

VR1 2M2 skeleton preset, horiz.

Capacitors

C1, C2 100n ceramic (2 off)
C3 100μ p.c.b. mounting
elect., 10V

Semiconductors

D1 1N4148 signal diode
D2 to D10 Low current l.e.d.s: red
(3 off); yellow (3 off);
green (3 off)
IC1 555 bipolar timer
IC2 4017 decade counter

Miscellaneous

S1, S2 Miniature push-to-make
switch (2 off)
S3 Miniature toggle switch
B1 PP3 battery and connector
Stripboard, 0.1in. matrix, size 15 strips
by 27 holes; plastic boxes, size 114mm x
76mm x 38mm and 50mm x 37mm x
24mm; 8-pin d.i.l. socket; 16-pin d.i.l.
socket; 10-way "rainbow" ribbon cable;
stranded connecting wire; twin multi-
strand connecting cable; stand-off insulator;
fixings; solder etc.

Approx cost
guidance only

£12
excl. Batt

CIRCUIT BOARD

Construction of the Reaction Timer is based on a circuit panel made from a piece of 0.1in. matrix stripboard, size 15 strips x 27 holes. Fig. 2 shows full topside component layout and the track breaks required on the copper strip side.

Begin by cutting the material to size, drilling the single fixing hole and making all track breaks and inter-strip links as indicated. Follow with the soldered on-board components but do not insert the i.c.s into their sockets until the end of construction. Note that diode D1 and capacitor C3 are polarity-sensitive components and must be connected the correct way round.

Leave the anode (a) end of diode D1 unconnected for the moment. Solder a short stalk (clipped-off resistor end) to board matrix position H19. At the end of construction D1 anode end lead will be soldered to this stalk so completing the connection. The reason for doing this is to help in the setting-up procedure at the end.

It will help construction if 10-way "rainbow" ribbon cable is used for the edge connections to strips D, E, G, H, I, J, K, L, M and O on the right-hand side of the circuit panel. This will keep the wiring

100 ON

200

300

400 milli-seconds

500

600

700

800

900

1000

1100

1200

1300

1400

1500

1600

1700

1800

1900

2000

2100

2200

2300

2400

2500

2600

2700

2800

2900

3000

3100

3200

3300

3400

3500

3600

3700

3800

3900

4000

4100

4200

4300

4400

4500

4600

4700

4800

4900

5000

5100

5200

5300

5400

5500

5600

5700

5800

5900

6000

6100

6200

6300

6400

6500

6600

6700

6800

6900

7000

7100

7200

7300

7400

7500

7600

7700

7800

7900

8000

8100

8200

8300

8400

8500

8600

8700

8800

8900

9000

9100

9200

9300

9400

9500

9600

9700

9800

9900

10000

10100

10200

10300

10400

10500

10600

10700

10800

10900

11000

11100

11200

11300

11400

11500

11600

11700

11800

11900

12000

12100

12200

12300

12400

12500

12600

12700

12800

12900

13000

13100

13200

13300

13400

13500

13600

13700

13800

13900

14000

14100

14200

14300

14400

14500

14600

14700

14800

14900

15000

15100

15200

15300

15400

15500

15600

15700

15800

15900

16000

16100

16200

16300

16400

16500

16600

16700

16800

16900

17000

17100

17200

17300

17400

17500

17600

17700

17800

17900

18000

18100

18200

18300

18400

18500

18600

18700

18800

18900

19000

19100

19200

19300

19400

19500

19600

19700

19800

19900

20000

20100

20200

20300

20400

20500

20600

20700

20800

20900

21000

21100

21200

21300

21400

21500

21600

21700

21800

21900

22000

22100

22200

22300

22400

22500

22600

22700

22800

22900

23000

23100

23200

23300

23400

23500

23600

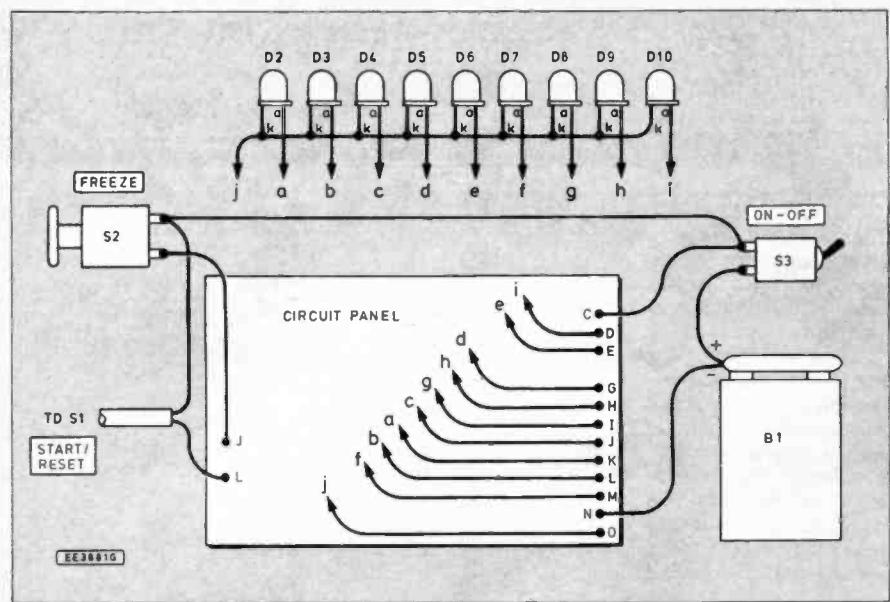


Fig. 3. Interwiring from the circuit board to the display I.e.d.s and other off-board components. Switch S1 is mounted inside the remote "tester" box.

MAIN UNIT


Referring to Fig. 3 and photographs, prepare the main unit box by drilling holes for S2 (Freeze) and S3 (On-Off) also a small hole in the side for the interconnecting wire to pass through. Drill holes for the nine I.e.d.s – it is worth measuring the positions of these carefully since the appearance of the finished project depends largely on the display being neat.

The holes should be of such a diameter that the I.e.d.s are a tight push-fit. They may then be secured with a little glue. Alternatively, I.e.d. mounting clips could be used.

Mount all remaining components. Note that everything is secured in the *main section* of the box with nothing on the lid – this avoids strain on the interconnecting wires.

Complete the internal wiring – note particularly the common connection for all I.e.d. cathode (k) ends. Follow the colours of the ribbon cable carefully so that the I.e.d.s end up lighting in the correct sequence.

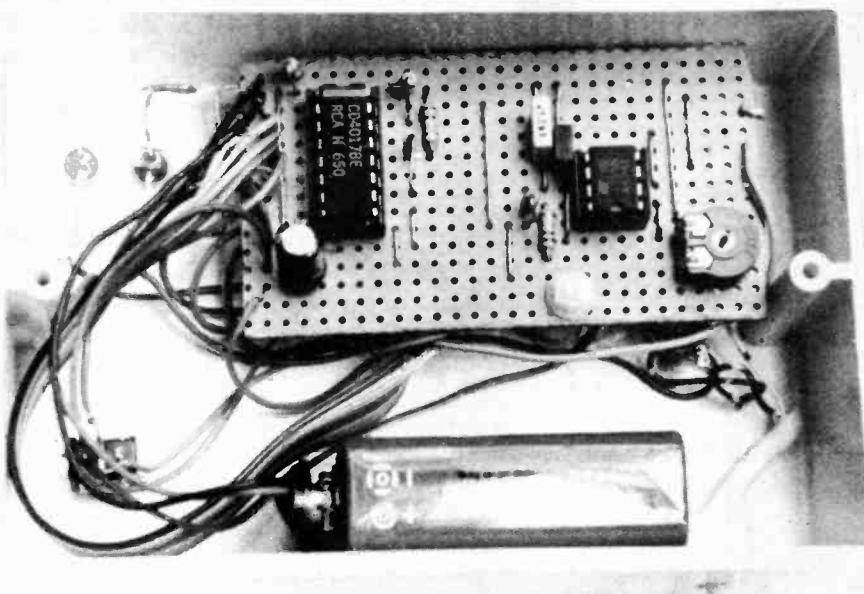Layout of components inside the completed main unit. The remote case is similar but only houses the Start/Reset switch S1.



side to be held clear of the I.e.d. connections. A long 6BA nylon bolt with three nuts was used for the purpose in the prototype – one nut to secure the bolt and two to sandwich the circuit panel.

Use a piece of thin plastic p.v.c. tape to provide some insulation for the copper strips if necessary. Secure the battery to the base of the case using an adhesive fixing pad.

REMOTE UNIT

Drill holes in the remote box for Start/Reset switch S1, and for the interconnecting lead to pass through. A keyboard-type switch was used in the prototype but any small push-to-make switch will do.

Mount switch S1, pass the twin wire interconnecting cable through the hole and tie a knot in it to provide strain relief. Solder the two end wires to S1 terminals leaving some slack in the wire so that it cannot pull free in service.

Back to the main unit. After a check for errors, insert the I.C.s with the correct orientation – note that IC2 is "upside down" compared with IC1. In theory at least, as IC2 is a CMOS device it can be damaged by any static charge which may exist. To be safe, touch a water tap or other earthed object before removing it from its packaging. Alternatively, avoid touching the pins when inserting it into its socket. Switch S3 *off* before proceeding.

TESTING AND ADJUSTMENT

Commence the testing and setting-up by connecting the battery and switching S3 *on*. The I.e.d.s should light rapidly one by one in sequence then start again (the cycle keeps repeating because one end of diode D1 has been left disconnected).

If any I.e.d. fails to light, suspect that it has been connected the wrong way round in the circuit. If any I.e.d.s operate out of sequence, they have been connected to the wrong IC2 outputs.

By timing ten complete cycles and adjusting preset VR1 to make this exactly 10 seconds (since it cycles through ten outputs), you will know that the time taken for the display to advance by one I.e.d. is 0.1s (100ms). This rate was found to be satisfactory in practice but it could be speeded up or slowed down as required by suitable adjustment to VR1.

Once this operation has been carried out, the wire stalling board matrix position H19 may be soldered to diode D1 anode. When tested, the unit should behave as before except that all I.e.d.s will go off after the first cycle.

It only remains to label the switches and I.e.d. display – this may be done in milliseconds i.e. 0.100, 200 so on – see photograph. Use dry print lettering to give a professional appearance.

REACTION

It is interesting to note that most people have a reaction time shorter than the *Highway Code* seems to suggest. This is probably because the situation in driving is not the same as here.

In these tests, the level of concentration is greater since it only needs to be kept up for a relatively short time. In driving, it would be impossible to maintain this degree of concentration.

This could be investigated by allowing a long time before releasing the Start/Reset switch. This will usually be found to increase the reaction time of the subject. □

IMPORTS EASY PC FILES
UPGRADE DISCOUNT AVAILABLE

Finally...an exceptional PCB and Schematic CAD system for every electronics engineer!

BoardMaker 1 is a powerful software tool which provides a convenient and professional method of drawing your schematics and designing your printed circuit boards, in one remarkably easy to use package. Engineers worldwide have discovered that it provides an unparalleled price performance advantage over other PC-based systems.

BoardMaker 1 is exceptionally easy to use - its sensible user interface allows you to use the cursor keys, mouse or direct keyboard commands to start designing a PCB or schematic within about half an hour of opening the box.

HIGHLIGHTS

Hardware:

- IBM PC, XT, AT or 100% compatible.
- MSDOS 3.x.
- 640K bytes system memory.
- HGA, CGA, MCGA, EGA or VGA display.
- Microsoft or compatible mouse recommended.


Capabilities :

- Integrated PCB and schematic editor.
- 8 tracking layers, 2 silk screen layers.
- Maximum board or schematic size - 17 x 17 inches.
- 2000 components per layout. Symbols can be moved, rotated, repeated and mirrored.
- User definable symbol and macro library facilities including a symbol library editor.
- Graphical library browse facility.
- Design rule checking (DRC) - checks the clearances between items on the board.
- Real-time DRC display - when placing tracks you can see a continuous graphical display of the design rules set.
- Placement grid - Separate visible and snap grid - 7 placement grids in the range 2 thou to 0.1 inch.
- Auto via - vias are automatically placed when you switch layers - layer pairs can be assigned by the user.
- Blocks - groups of tracks, pads, symbols and text can be block manipulated using repeat, move, rotate and mirroring commands. Connectivity can be maintained if required.
- SMD - full surface mount components and facilities are catered for, including the use of the same SMD library symbols on both sides of the board.
- Circles - arcs and circles up to the maximum board size can be drawn. These can be used to generate rounded track corners.
- Ground plane support - areas of copper can be filled to provide a ground plane or large copper area. This will automatically flow around any existing tracks and pads respecting design rules.


Output drivers :

- Dot matrix printer
- Compensated HP laser printer
- PostScript output.
- Penplotter driver (HPGL or DMPL).
- Photoplot (Gerber) output.
- NC (ASCII Excellon) drill output.

All trade marks acknowledged

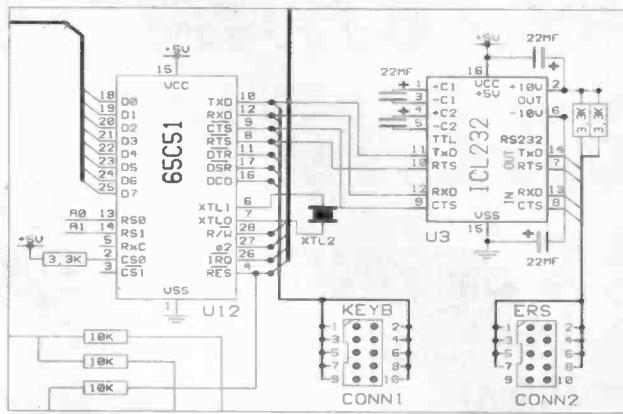

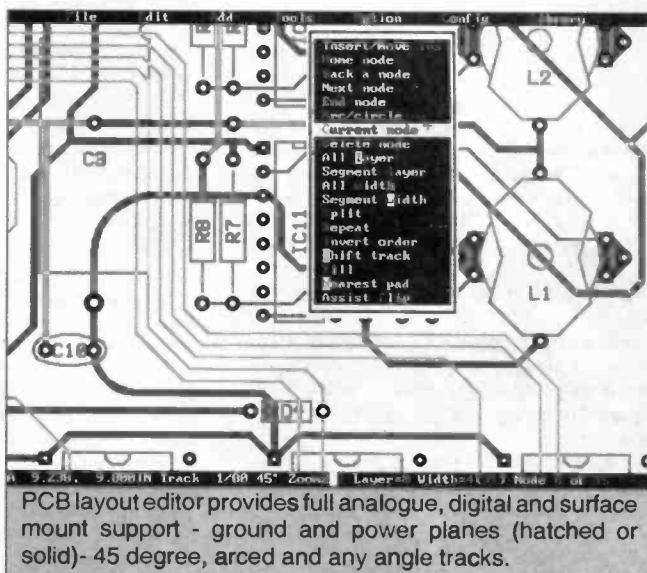Produce clear, professional schematics for inclusion in your technical documentation.




PCB layout editor provides full analogue, digital and surface mount support - ground and power planes (hatched or solid)- 45 degree, arced and any angle tracks.

£95

Despite its quality and performance, BoardMaker 1 only costs £95.00. Combine this with the 100% buy back discount if you upgrade to BoardMaker 2 or BoardRouter and your investment in Tsien products is assured. Price excludes carriage and VAT.

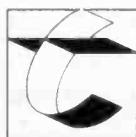Don't take our word for it. Call us today for a FREE demonstration disk and judge for yourself.



tsien

Tsien (UK) Limited

Cambridge Research Laboratories

181A Huntingdon Road

Cambridge CB3 0DJ


Tel 0223 277777

Fax 0223 277747

ALTERNATIVE ENERGY

T. R. de VAUX BALBIRNIE

Developments using renewable energy sources. Energy from water.

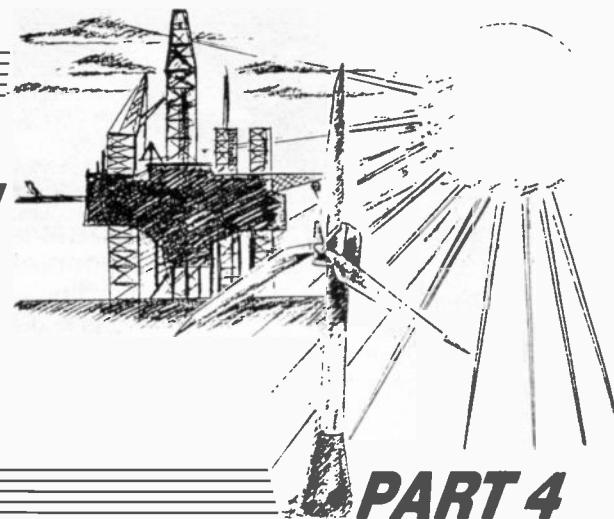

PART 4

THIS is the fourth article in a short series about renewable energy – that is, sources of power which will last for ever unlike those derived from the fossil fuels – coal, oil and natural gas – which will eventually run out. This month we shall examine various ways of using *water power*.

The Department of Energy has funded a programme of research and development into alternative energy methods since 1974. Some ideas turn out to be economically and technically attractive, some could be promising in the medium term and others are long shots and unlikely to be used in the foreseeable future.

The Government is working towards an electrical generating capacity of 1000MW from renewable energy sources by the end of the century – equivalent to the output of one large coal-fired power station. Technically, renewable energy sources could furnish *all* our needs but they are *diffuse* – that is, the power is spread out over a large area and this often makes exploitation difficult and therefore expensive.

WATER, WATER EVERYWHERE

Water power in its various forms, together with on-shore wind energy, geothermal energy and schemes producing energy from waste material (of which more will be said next month), are likely to make a significant contribution to Britain's total

energy needs in the 21st century. This, together with nuclear power and a smaller contribution from the dwindling supplies of fossil fuels, should maintain our increasing energy needs.

Water power in some form is an ancient technology – water wheels have been used for milling corn and other purposes for centuries. There is a reference to water power having been used in Greece during the First Century A.D. and in the Middle Ages the water wheel was in widespread use in several countries.

The traditional *overshot* and *undershot* types of water wheel are shown in Fig. 1. Today, the water wheel would be described as a *turbine* where the water turns blades on a shaft which can then provide useful work.

There are several ways of obtaining energy from water and hence to generate electricity – from the tides, from waves and from the power of falling water – that is, *hydroelectric power* schemes. It is also possible to use naturally-occurring hot water – springs and geysers – and this method will be discussed in more detail next month. Unlike tides, springs and geysers, both wave energy and hydroelectric schemes actually use indirect solar power.

Waves are caused by the wind blowing across the surface of the sea and it is the sun which causes the differences in temperature which cause the wind to blow. As well as causing horizontal currents, the water is

made to move up and down. It is this movement which carries vast amounts of energy and which may be exploited to generate electricity.

Hydroelectric power is also derived indirectly from the sun since it is the heat of the sun (solar radiation) which evaporates the water in the first place and carries it up as vapour to the high ground where it falls as rain. The energy held by the water on the high ground is called *potential energy* (energy due to position). As it falls, the power may be transferred to a turbine which rotates the shaft of a generator and produces electricity.

We saw in a previous article that approximately 20 per cent of solar energy falling on the earth causes evaporation of water but much of it happens very diffusely with small amounts of flowing water spread out over a very large area. It would be uneconomic to extract the energy from such small amounts of slow-moving water.


EBB AND FLOW

Tidal energy is an "odd man out" because here the power has not come from the sun. Tides are caused chiefly by the gravitational pull of the moon and, to some extent, the sun on the mass of water which makes up the oceans of the world. Although the sun is massive in comparison to the moon, it is also much further away so it is the moon which has the greater influence. The gravitational force causes the water to pile up and it moves as the earth turns on its axis.


Most parts of the world experience two tides each *tidal day* – that is, every 25 hours and 5 minutes. When the sun aligns with the moon there is a larger than normal gravitational force and a particularly high tide results. This occurs twice a month and is called a *spring tide*.

When the sun and the moon are in opposition, a smaller gravitational force results and this gives rise to a lower tide than usual called a *neap tide*. Even so, tides are very complex and far removed from the pattern suggested by simple theory. The size of a tide is influenced by the shape of the coastline with funnelling effects tending to increase the tidal range.

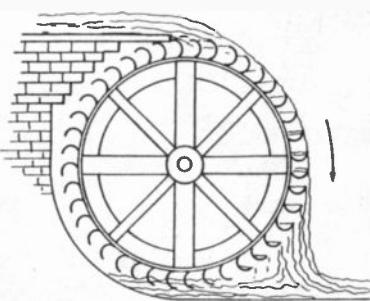Advisors to The Department of Energy believe that tidal energy and wind power (which has been discussed in previous parts of this series), have a promising future and together have the potential to generate a



OVERSHOT WATER WHEEL

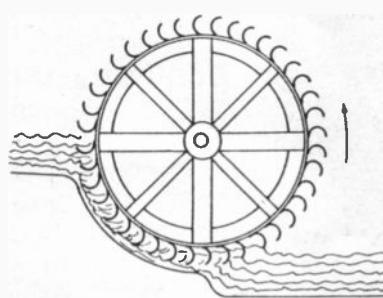

UNDERSHOT WATER WHEEL

Fig. 1. Types of traditional waterwheel.

EE36926



Potential sites for tidal barrage schemes.

significant fraction of the total electricity needs of the U.K. We may draw on the experience of the French, Americans and Canadians who have had large-scale tidal power schemes in operation for several years.

In Britain, we are fortunate in having some of the highest tides in Europe and these are ideal for economic exploitation. It is thought that the tidal range needs to exceed about five metres to make this method commercially worthwhile and many such sites are to be found around the west coast and elsewhere – see the map of potential barrage scheme sites.

In the Severn Estuary, funnelling and other effects combine to provide one of the largest tidal ranges in the world – over 11 metres in the region between Barry and Weston-Super-Mare (see Fig. 2). The flow of water carries a vast amount of energy and using this to generate electricity is a very attractive and economically viable proposition.

By maximum commercial exploitation, we could generate at least 20 per cent of Britain's total electricity needs by tidal power alone – rather more if we did not look too coldly at the commercial aspects but weighed them up against the indirect benefits. Even if we abstracted energy only from the largest tides – those of the Severn,

the Mersey and a few more, 10 per cent of our total energy needs could be realized. The eight largest schemes used together could save Britain about 25 million tonnes of coal per year.

We presume that by drawing energy out of the tidal system, we are slowing down the rate at which the earth spins on its axis. However, this effect is so small as to be imperceptible and is happening all the time anyway.

TIDAL BARRIERS

To exploit tidal energy, a *barrage* or dam needs to be built to control the flow. A river basin is thus formed. The barrage has a number of turbines set into it and as water flows in and out of the basin with each change of the tide, the turbines rotate, turn generators and make electricity (see Fig. 3).

The proposed Severn Tidal Barrage scheme is, at the moment, undergoing extensive study. The Severn Tidal Power Group has completed a programme of investigations and has confirmed that a suitable barrage could be constructed using existing technology. It is further believed that, once built, the scheme would be capable of delivering electricity to the public supply network for more than a century.

The Severn Barrage project, if put into operation, would be the largest tidal power scheme in the world. The barrage itself would be enormous – some 16km (10 miles) in length stretching between Lavernock Point (between Barry and Cardiff) to a point near Weston-Super-Mare (see Fig. 2). The basin would enclose an area of 480 square kilometres.

Into the barrage would be set 216 turbines each with a diameter of 9m and each having a generating capacity of 40MW giving a total power output of 8640MW – that is, it would exceed the output of eight large coal-fired power stations. This would provide seven per cent of the total electrical energy requirement of England and Wales.

Despite the great capital cost – some £8 billion (at 1988 prices) – the potential for saving fossil fuels would be vast – some 8 million tonnes per year. The reduction in carbon dioxide emission would be almost 18 million tonnes per year with consequent relief from the greenhouse effect.

Construction of the Severn Barrage would probably involve floating large hollow concrete sections to the site. Each section – called a *caisson* – would carry one of the turbines. It would be necessary to provide locks to allow the largest ships to pass to the ports along the river and some means of allowing fish through without harm. The

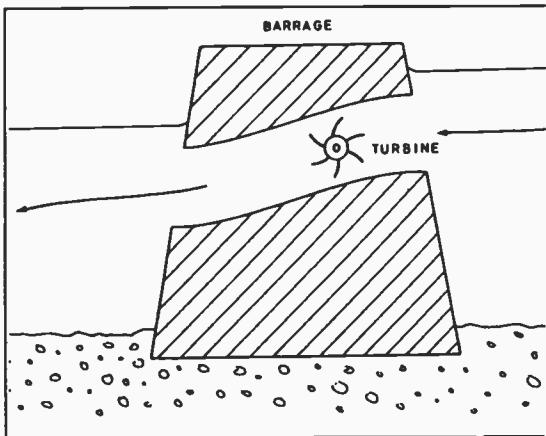


Fig. 3. Principle of the tidal barrage.

construction time scale would be approximately 14 years – about five years for preparation, a further seven for construction and first power production and a further two years for full-stream operation.

ACROSS THE MERSEY

A similar but much smaller *Mersey Barrage project* would use a dam 2km in length with a basin enclosing 61 square kilometres. There would be 28 turbines set into it, each having a diameter of 8m and each with a generating capacity of 25MW. This would provide a total peak output of 700MW. The Mersey is well suited to such a scheme with spring tides reaching a range of 8m.

The preferred siting for the barrage is between the Liverpool Garden Festival site near the city centre and a point close to New Ferry on the Wirral – see Fig. 4. As in the Severn project, a system of locks would be required to allow the passage of ships to the Manchester Ship Canal.

The Mersey Barrage scheme would save some 700,000 tonnes of coal per year. Constructional cost is estimated at £880M (at 1989 prices). If the scheme were approved by Parliament, the project could be complete and generating power within two years.

In addition to the two largest projects outlined above, Britain has the potential for several less ambitious schemes each making a small but significant contribution. A study made in 1986 identified 34 such sites each with the potential to generate between 30 and 150MW.

A feasibility study on a possible Conway (North Wales) Barrage shows the potential to generate 33MW while a Wyre Barrage (near Fleetwood in Lancashire) could

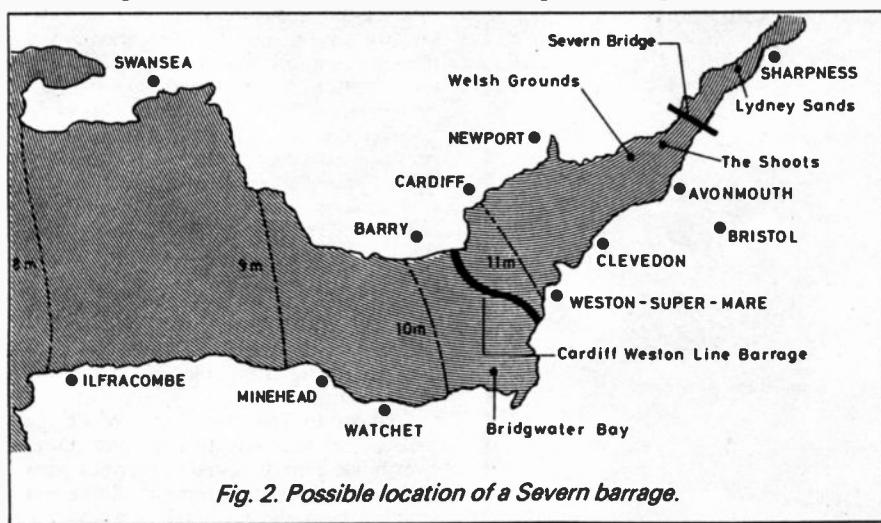


Fig. 2. Possible location of a Severn barrage.

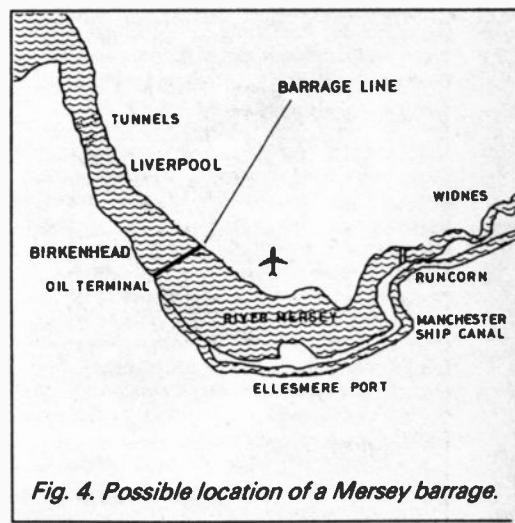


Fig. 4. Possible location of a Mersey barrage.

produce 47MW of electricity. Scotland tends to have lower tides so there are fewer commercially attractive sites there. However, Scotland has a greater potential for hydroelectric schemes than England and Wales.

EFFECTS ON THE ENVIRONMENT

Tidal energy has the advantage of being less diffuse than many other forms of renewable energy. Also, the energy in moving water is easily turned into electricity by well-known and relatively inexpensive technology. However, the use of tidal energy is not without some cost to the environment.

Abstraction of tidal power alters the pattern of water movement and lessens the speed of the currents. This can cause sediment build-up and lower turbidity with possible effects on wildlife. Within the river basin, the tidal range would be reduced and the low-water level raised.

It is thought that lower turbidity could increase the availability of food for fish and birds but, on the negative side, there would be a reduced mudflat area for feeding wading birds. However, taking everything into account, tidal power is thought to rank with the wind in being among the most environmentally-friendly sources of power.

Because a tidal energy scheme controls the flow of water, it prevents flooding along large stretches of the river during extreme high tides. Other methods of flood prevention would therefore not be required and the savings made here offset some of the constructional costs of the barrage itself.

WAVE ENERGY

It is well known that waves carry an enormous amount of energy. Our coast has a history of broken seawalls and seaside piers having been destroyed during violent storms. Research into abstraction of wave energy has been carried out since the mid-1970's and extensive studies have been made to find the best types of device for the job – some 300 ideas in all.


The best places for large-scale wave energy exploitation lie between latitude 40 and 60 degrees and many parts of Britain have a near-ideal situation. Off the West Coast, in the NW approaches, there is said to be available some 70MW of power per km of coastline – that is to say, over a stretch of approximately 15km (about 10 miles) there is available the equivalent energy of a large coal-fired power station.

In fact, the waves around our coast carry all the energy we need but its abstraction would prove very expensive and difficult. Also, the power of the waves is notoriously unpredictable depending as it does on wind speed and the exact way and time for which the wind blows across the water surface.

OFFSHORE

There are basically two wave energy extraction technologies – *offshore* and *shoreline*. Large off-shore wave energy projects are exciting and once seemed attractive on account of the vast amounts of energy available. The up and down wave energy could be extracted by transferring the motion to floating *nodding ducks* in the manner developed by Professor Salter of Edinburgh University (see illustration). The motion would then be transferred to an electrical generator. However, off-shore wave technology is difficult.

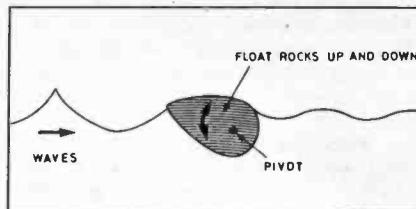The mighty 2000MW off-shore proposals originally investigated by the Department of Energy now seem far too expensive to imple-



Salter's Ducks, method of operation.

ment. The technique of bringing the energy ashore and difficulties in maintenance of the equipment would also raise problems. It appears that the economic viability of using off-shore waves as a source of energy would depend on other methods rising in price.

SHORELINE

On the other hand, due to the relatively low cost involved, small-scale *shoreline* projects seem to hold much promise. These would be of value as local power sources in remote regions where it is expensive to lay on a supply of electricity – perhaps by using diesel generators.

One such scheme under investigation is the Shoreline Rock Gully System developed by Queen's University, Belfast and funded by the Department of Energy. This is presently undergoing trials on Islay in the Inner Hebrides (see below). In this scheme, the energy is extracted from waves in a natural gully so greatly reducing construction costs.

The waves force water into a large chamber (a *capture chamber*). This rises like a piston and forces the air through a turbine which then operates an electrical generator. As the water retreats, the air re-enters the chamber and the turbine is operated once again.

A special air turbine developed by Professor Alan Wells – the *Wells Turbine* – can operate without reversing whichever way the air is moving through it and this is a great advantage. The output from the generator varies from a peak of some 100kW during a storm to some 75kW during normal working conditions. Work began on the project in 1985 with construction commencing in 1987. The output was connected to the National Grid in 1991.

One advantage of wave energy which is not always true of other alternative energy sources is that production tends to track

demand – in winter, when more electricity is needed, the waves are generally larger and so more electricity is produced.

HYDROELECTRIC POWER

The technique of producing energy from falling water has been well established in Britain – as in many other parts of the world – for many years. Unfortunately, there is little room for expansion since all the major resources are already in use.

Currently, about two per cent of U.K. electricity needs are supplied in this way – mainly in Scotland which holds 90 per cent of the total resource. Really large amounts of energy are only available where the head (height of fall) exceeds 50m and these provide 85 per cent of the total energy produced by H.E.P. technology.

Britain is not as fortunate as certain other countries (Canada and Sweden, for example) in having large masses of falling water. Perhaps the future lies in developing many small-scale projects which would nevertheless, provide a useful contribution to our total energy needs.


Work by the University of Salford has shown that some 300MW of power is available where the head is little more than three metres. It could be argued that 300MW is too small to be worthwhile – it is, after all, only one-third of the output of a large conventional power station, but the energy is available using well-established technology and at a reasonable price.

Many such schemes could provide up to one per cent of our total requirements in the future. This would be helpful to island communities too remote from the nearest conventional electricity supply.

PUMPED STORAGE

Although not a source of alternative energy as such, this month's work would not be complete without a brief mention of *pumped storage* power stations because these schemes provide an indirect saving in the use of fossil fuels and a consequent reduction in carbon dioxide emission.

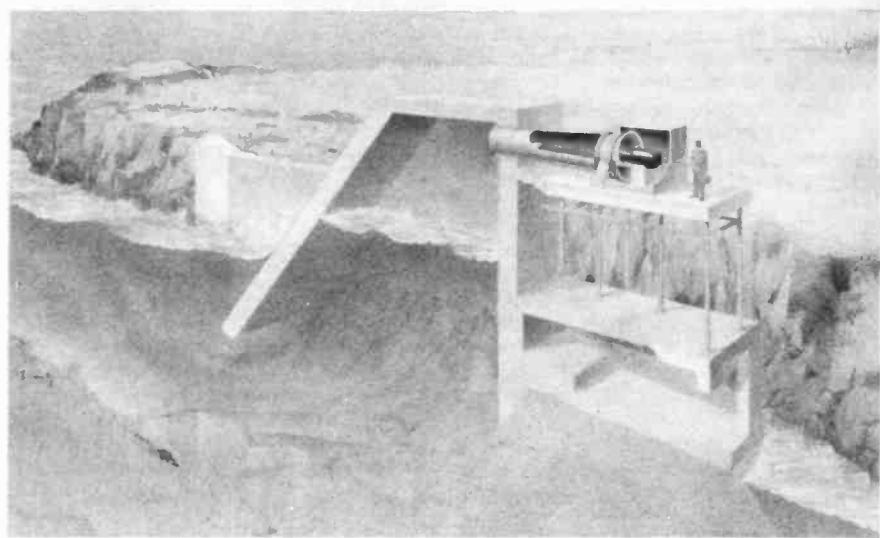To understand the principle of pumped storage power generation, we need to know that the public demand for electricity varies throughout the 24 hour cycle. During the night, the requirement both by private



The shoreline generation system, this cutaway artist's diagram shows the principle of operation.

homes and industry falls off considerably. The generating companies wish to boost demand in the off-peak period to provide a better balance between off-peak and on-peak usage since this makes for more efficient operation of the network.

Schemes such as *Economy-7* help to do this by offering electricity to the consumer at a discounted price between certain hours of the night and early morning. In this way, storage heaters and other pieces of equipment may be used to take advantage of the lower price.

On a much larger scale, off-peak power may be used to pump water from a lake at the bottom of a mountain to a reservoir at the top. At times of peak demand or perhaps when there is a sudden unexpected need for power such as during a spell of cold weather, the water is allowed to flow downhill again, turn the turbines, and generate electricity just as in a conventional hydroelectric scheme.

At Dinorwig in North Wales, this method is used to provide full generating capacity within ten seconds. The turbines which generate the electricity when the water flows downhill may be operated in reversing as pumps to drive the water up again. It is true that some energy is lost in the process – that is, some is turned into heat in the water and therefore unavailable for use. In modern systems this amounts to 10 per cent approximately.

A pumped storage system does not make much use of a renewable energy resource since mainly fossil fuel energy is used to raise the water to the higher level in the first place. However, by providing a more even demand, the overall efficiency of the distribution system is increased. Even taking into account the "lost" 10 per cent, this means an ultimate saving in the use of fossil fuels.

HYDROGEN AS A FUEL

A further way of obtaining energy from water – this time a *chemical* one – is to use *hydrogen gas* as a fuel. Water consists of only two basic materials (elements) – the gases *hydrogen* and *oxygen*. If hydrogen is removed from water, it may then be used to power a car. A conventional petrol-burn-

ing engine may be adapted to use hydrogen. However, as every schoolboy chemist knows, hydrogen must be treated with respect since it forms a highly explosive mixture with air.

To remove the hydrogen (and the oxygen) from water involves passing an electric current through it – that is, to perform *electrolysis*. Obviously, in order to do this, the electricity has to come from somewhere and this may be derived from fossil fuels, nuclear energy or some renewable energy source.

When the hydrogen burns and delivers power to the engine, we are simply regaining the energy which generated the electricity in the first place. However, there are some advantages in doing this. Firstly, the relatively inexpensive and well-known technology of the internal combustion engine may continue to be used. Also, hydrogen is a perfectly clean fuel.

The only product of combustion is water – that is, regaining the water which was electrolysed. This means that the exhaust is totally harmless and non-polluting. There is no carbon dioxide produced and therefore no contribution to the greenhouse effect.

GAS CAR

Since the early 80's, the German car manufacturer, BMW, has been carrying out a research programme to examine the use of hydrogen as a fuel for motor vehicles. The idea is to use solar cells to generate electricity which is then used to electrolyse water and produce hydrogen gas.

In the BMW system, the hydrogen is *liquefied* and so stores much more energy in a given space than the gas. This method brings certain problems, however. The greatest of these is that liquid hydrogen only exists at a temperature of -253°C .

In practice this means that the storage tank must be very well insulated to prevent the fuel from boiling off rapidly into the atmosphere. The fuel tank specially developed for the purpose is double-walled with very sophisticated insulation. This is capable of holding 93 litres (20.5 gallons) of liquid hydrogen which provides a range of 300km (190 miles approximately).

The tank is fitted in the 6-cylinder 3.5 litre long-wheelbase 735iL model across the lug-

gage compartment. This avoids problems with the rear seating which is unaffected.

Developing engines to produce maximum power using hydrogen fuel demands difficult and expensive technology. BMW see one possible way forward in not trying to develop maximum power but to reduce it by some 30 per cent compared with using petrol. A lean mixture is then used and this simplifies the procedure and reduces costs.

HAZARD

Even with the high degree of insulation used on the fuel tank, liquid hydrogen does boil off and is released through safety valves – a maximum of two per cent of the fuel is lost to the atmosphere this way each day. There are concerns about the safety aspects associated with this free hydrogen and also the possibility of damage to the fuel tank in an accident leading to large-scale release of gas into the atmosphere.

It is impossible to remove all risk but this must be compared with the hazard due to the storage of petrol. At least, unlike petrol, hydrogen is non-toxic and when released into the air is quickly diluted, and rapidly becomes harmless.

An interesting feature prevents accidental build-up of hydrogen in the passenger compartment. If a predetermined concentration of gas is exceeded, a sensor detects it and an electronic circuit causes the sliding roof, windows and boot lid to open so preventing an ignitable mixture accumulating.

In the event of an accident, the doors unlock, the windows and boot lid open and the sun roof slides back. Taking everything into account, it is doubtful if a car burning hydrogen as a fuel involves any more risk than a conventionally-powered car.


BMW are taking their Hydrogen Drive research project very seriously. To improve the development of hydrogen-burning engines they started to use the world's first purpose built test bed in March, 1989. This uses a complete data processing system with results being recorded electronically in a measuring and control room. Data is then analysed and optimum working conditions determined.

VIABLE

Research into hydrogen-powered cars suggests that this fuel could make a viable alternative to petrol. At the moment costs are still too high, however, and problems still remain. Experimental cars have been built using hydrogen compressed into cylinders but the quantity of gas is not sufficient to provide a satisfactory range. A further idea is to absorb the gas into various materials but this method has not been altogether successful either.

A variation of the method is to use *fuel cells*. Here, instead of burning the hydrogen in an engine, the hydrogen and oxygen obtained by electrolysis are passed over special porous plates. The two gases re-combine to provide water and in the process a voltage is formed between the plates. Thus, electrical energy is produced *direct* from the fuel. This may then be used to operate an electric motor to power the car. At the moment fuel cells are rather bulky but further research could possibly bring them down to a manageable size.

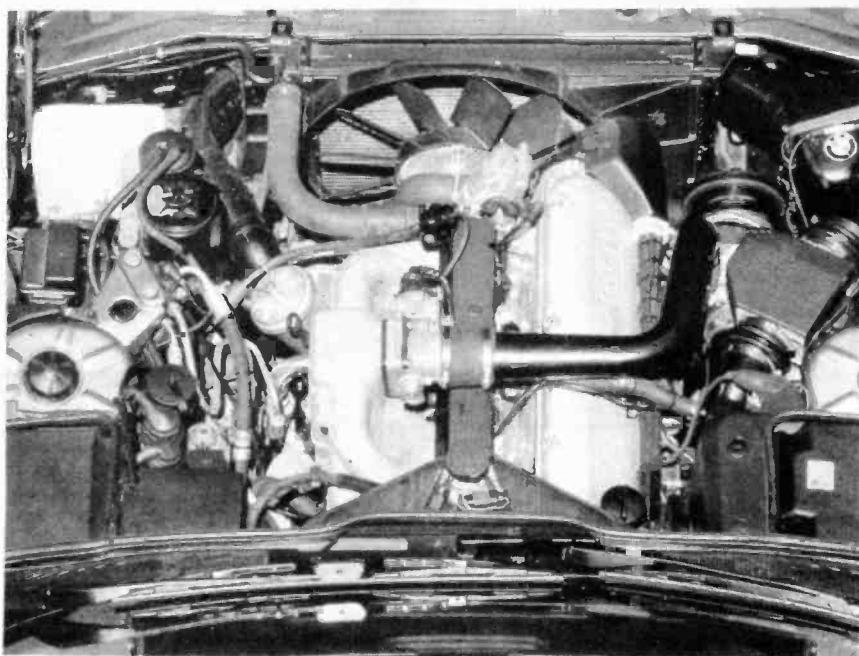Next month we shall look at some further examples of renewable energy sources – those using household waste, biomass and geothermal energy. We shall also look at some aspects of nuclear power to see how this fits into the complete *Alternative Energy* picture.



The BMW hydrogen drive engine in a 735iL.

BATTERY TO MAINS INVERTER DAUGHTER BOARD

MARK DANIELS

An add-on board for a past project.

THE Battery to Mains Inverter project which appeared in the March 1991 issue of *Everyday Electronics* used an M706B1 timebase i.c. to generate the accurate 50Hz timing signals required for its correct operation. Unfortunately, it would appear that this device is no longer readily available and no direct replacement or substitute for it is known to be in existence. To help readers already constructing this project or contemplating its construction an add-on daughter board has been designed to take the place of the now elusive M706B1. (The March '91 issue is available as a back number from the Editorial office - see the Editorial page for details - Ed.)

CIRCUIT REQUIREMENTS

The M706B1 i.c. which was specified for IC1 in the original design was supplied in a standard 8-pin d.i.l. package and provided complementary 50Hz square wave outputs from a 3.2768MHz crystal reference.

Ideally the circuit which replaces this device should make use of the existing components and i.c. socket for its connections. To enable us to mount extra components in place of the original device a small daughter board carrying the substitute parts is mounted above the main p.c.b. and connections between the two boards are made using tinned copper wire.

CIRCUIT DESCRIPTION


The circuit shown in Fig. 1, comprises two standard low power CMOS i.c.s., IC1(1) and IC1(2). IC1(1) is a 14 stage binary counter with an on board crystal oscillator section designed for connection to an external crystal. A number of the stages are made available on the device pins, but in this application the largest division ratio is chosen, giving an output of 200Hz at pin 3, using the original crystal, X1 (see original article).

The counter/oscillator IC1(1) has only a single output and a division ratio which is insufficient for our requirements, so extra stages in the form of a dual bistable, IC1(2) are added at its output.

The two bistables in IC1(2) are cascaded to provide a further division by four thus reducing the 200Hz at its input to the required 50Hz complementary outputs. Reference to Fig. 1 will show how the replacement components connect to the pins of the original IC1 position, using all other existing components on the parent board in their original positions and with no changes in their values.

CONSTRUCTION

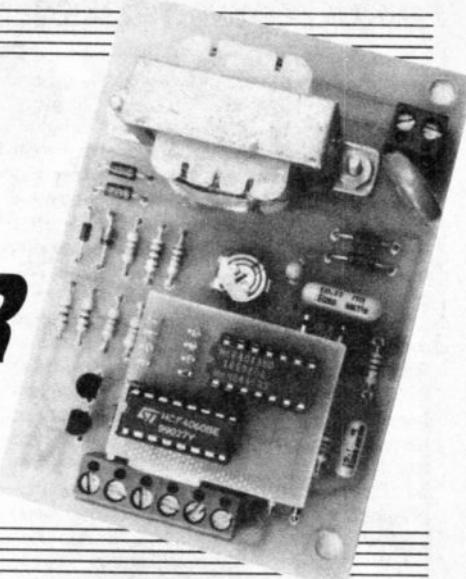The full size foil pattern and component overlay for the small daughter board are given in Fig. 2. For ease of construction it



is recommended that sockets are used for the two i.c.s.

Eight lengths of 20 s.w.g. tinned copper wire (30 amp fuse wire) approximately 30mm long are soldered to the remaining pads on the reverse of the p.c.b. to make the connections to the parent board.

If the parent board is already assembled IC1 and its socket (if fitted) will need removing before the daughter board can be offered up.

Feed the tinned wires into IC1 holes in the parent board allowing sufficient clearance above the parent board components to preclude the possibility of short circuits in the future. Check that the board is correctly aligned; the figures on the daughter board corresponding to the original IC1 connections, before soldering the connections. Reference to the photograph should clarify any obscurities.

Before fitting the two new i.c.s. it may be sensible to check that the power rails are all present and correct. 0V on IC1(1) pins 8 and 12 and IC1(2) pins 4, 6, 7, 8 and 10. Twelve volts should be present on IC1(1) pin 16 and IC1(2) pin 14.

TESTING

Fit the two i.c.s., observing CMOS handling precautions and polarity requirements and switch on.

The inverter should start immediately if the parent board was working prior to modification. If not, fault finding is pretty much the same as in the original design, with the possibility of a check for 200Hz at pin 3 of IC1(1). Use Fig. 1 of this article in conjunction with the main schematic of the original article if fault finding should become necessary.

CONNECTION CLARIFICATION

The small transformer T2 in the original article appears to have caused confusion among some readers, as its secondary is incorrectly labelled in the main circuit diagram, Fig. 2. It should be labelled 12V-0V-12V, not 0V-12V as shown. The p.c.b. layout of Fig. 3 is also incorrectly labelled, and should be marked 12V-0V-12V, the centre-tap lead being cut off as it is not required in this application.

Editorial Note: The author is presently working on a 250W inverter design together with an uninterruptible power supply add-on, which we hope to publish in a few months time. □


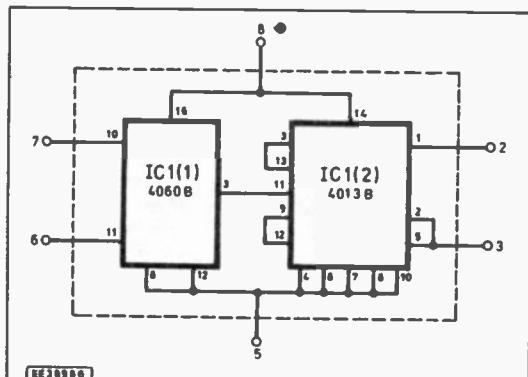


Fig. 1. Circuit diagram of the Daughter Board. Numbers outside the dotted line correspond to the original pin numbers.

Fig 2. (right) P.C.B. construction.

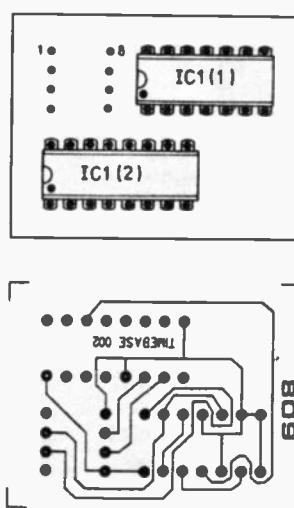

MARCO TRADING



INCORPORATING EAST CORNWALL COMPONENTS
WHOLESALE • MAIL ORDERS • RETAIL

SEND ORDERS TO - DEPT 11

MARCO TRADING

THE MALTINGS, HIGH STREET, WEM
SHROPSHIRE SY4 5EN

Tel: (0939) 232763 Telex: 35565

Fax: (0939) 233800

ELECTRICAL & ELECTRONIC
COMPONENT SUPPLIERS

24HR ANSAPHONE

LATEST 1992 CATALOGUE



POST & PACKING

NOW £3.00

All prices include VAT.
Delivery Guaranteed
within three days

VISIT

OUR OTHER BRANCHES

SUPERTRONICS
Tel: 021 666 6504
65 HURST STREET
BIRMINGHAM B5 4TE

WALTONS
Tel: 0902 22039
55A WORCESTER ST
WOLVERHAMPTON WV2 4LL

Visit our shop in
WEM
Tel 0939 232763

NOVEMBER SPECIAL OFFER

SOUND LAB CAR EQUALIZER/BOOSTER

B005G

KB211

High power stereo equalizer booster,
Twin 5-band graphic equalizer, fader
control for front/rear speakers and twin
10-LED power indicators. Inputs for high
or low level from car stereo. Mounting
hardware included.

Output power 30W per channel



Only £29.99

Normally £37.95

While Stocks Last

BROAD BAND RADIO RECEIVER £17.50

CB - FM - AIR BAND - POWER 4 x AA'S

RSGB CALL BOOK 1991-92
Now £2.50
While stocks last

NI-CAD CHARGER



Charges AA, AAA, C, D & PP3
Ni-Cads 240V AC

£4.99

NI-CAD RECHARGEABLE BATTERIES

PRICE	EACH
AAA	1.50
AA	95p
C	£1.95
D	£2.00
PP3	£3.90
	£1.80
	£1.85
	£3.75

QUARTZ-HALOGEN SPOTLIGHT

THIS UNIT SUBJECT TO DESIGN CHANGE

Hand held or hanging. Heat resistant polycarbonate housing, highly polished reflector. Protective lens cover doubles as base stand. With On/Off switch and 12m cable terminating in cigar lighter plug. Produces 250,000 candle power - 5 times the intensity of average car headlights.

Price £5.75

Power..... 12V dc, 4.5A 55W

Dims..... 160 x 88 x 110mm



TWIN FLUORESCENT LAMP - 12V



A very attractive twin tube lampholder with two 12V BW fluorescent tubes. White plastic case with clear plastic ribbed diffuser and ON/OFF switch. Supplied with 90cm of twin flex for connection to 12V battery (Red stripe to positive). Ideal for caravans, boats, vans, etc.

Overall dimensions: 370 x 65 x 41mm

ORDER CODE Opto TFL12

1+ 10+ 50+

Price £6.50 £6.00 £5.25

PORTABLE FLUORESCENT LAMP - 12V



Free-standing or hanging with 15ft cable terminating in cigar lighter plug. For use in car, boat, van or home emergency. 12V dc.

EVEN FLOATS IN WATER!

Overall dimensions: 430 x 30mm

ORDER CODE 1+ 10+ 50+

Price £6.50 £6.00 £5.25

SPARE TUBES

Replacement tube for above Twin and Single fluorescent lamps. Fits most 12V fluorescent lamps. Philips, etc. Tube length, approx 300mm (Incl. pins).

ORDER CODE Opto SL

£1.50 ea, 10 for £12

PIR FLOODLIGHT ONLY £29.99

HURRY WHILE STOCKS LAST



A high power security floodlight with built-in PIR detector which reacts to body heat, switching on the floodlight whenever somebody is within the detection zone. The PIR detector is adjustable for horizontal and vertical angle and contains a photo detection detector to prevent daylight operation.

Power: 220-240V a.c. 50Hz

DESOIDER TOOL

High quality, fitted with Teflon micro nozzle.
Length: 190mm
Dia: 20mm

PRICE: £2.99

SPARE NOZZLE
95P each

BLACK PLASTIC ABS BOXES

★★★
Quantity
prices
available
★★★



INTERNAL DIMENSIONS
mm A B C
76 58 35

ORDER CODE BOX/MB1 £1.25

95 71 35

BOX/MB2 £1.35

115 95 37

BOX/MB3 £1.58

145 95 55

BOX/MB5 £2.20

165 119 75

BOX/MB7 £3.20

207 122 77

BOX/MB4 £4.96

213 142 57

BOX/MB6 £3.78

174 117 80

BOX/MB7 £3.20

147 77 47

BOX/MB8 £2.15

PRICE: £2.50

0.5W RESISTOR PACK

Same as left
PRICE: £10.00

0.5W RESISTOR PACK

Same as left
PRICE: £2.50

PACK 020 £2.00

PERSONAL STEREO AMPLIFIER

I. A. DUNCOMBE

A versatile, low cost, add-on stereo amplifier (approx. one watt) for your personal stereo.

Let your friends hear your "top ten" to.

PERSONAL stereos (Walkmans) are excellent for the purpose they were designed, i.e. personal listening. If a wider listening audience is envisaged, then the output power is hardly adequate for the purpose.

This unit may be used directly from the mains supply or, as will probably be the case, from the personal stereo's own a.c./d.c. adapter. The output power has been chosen to be deliberately small for two reasons:

Cost – It is hardly worthwhile designing a larger more powerful amplifier as they already exist in the form of the home music centre etc.

Flexibility – The amplifier will work into a variety of loudspeaker impedances, and accept a wide range of inputs. Finally the amplifier may be varied to suit the users' individual requirements and pocket!


CIRCUIT DESCRIPTION

The complete circuit diagram for the audio stages of the Personal Stereo Amplifier is shown in Fig. 1. It is based upon the very popular audio amplifier i.c., the TBA820. This is capable of delivering a maximum of 1.6W, although in this design it is slightly lower than this.

The incoming stereo signal is applied, via plug PL1, to the individual volume controls VR1/VR101 and hence to the input, pin 3 of IC1 (left) and IC101 (right channel). Resistor R1, (the remainder of the description applies equally to the right hand channel – prefixed with one hundred), sets the input impedance and R2 the gain. The open loop gain is 70dB but is reduced substantially in this design.

Capacitor C4 provides for ripple rejection of the power supply. Capacitor C6 provides for a degree of "bootstrap" feedback and C5 adjusts the frequency response. Components R4 and C7 form a Zobel network.

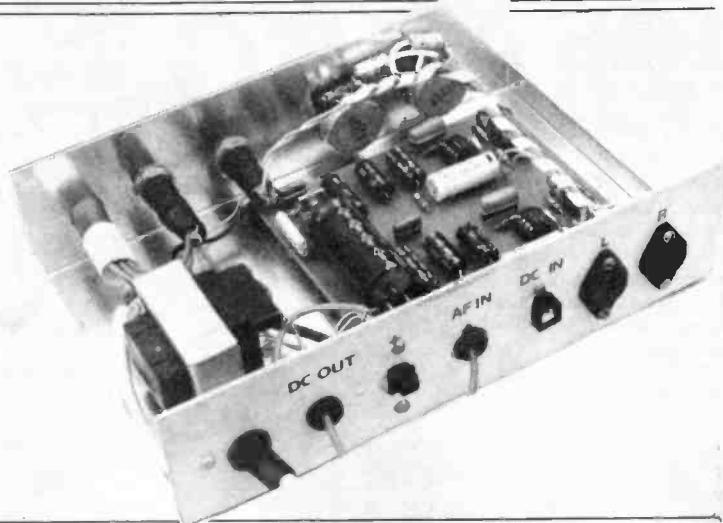The output signal is passed to the speaker via the electrolytic capacitor




POWER SUPPLY

The power supply (Fig. 1a) is a conventional full-wave one and consists of a 6VA transformer T1, "bridge" diodes D1 to D4 and smoothing capacitor C10 and provides a basic 14V to the main amplifier. The voltage regulator IC2, enables a variable stabilised voltage to be produced, which can be used to power most personal stereos.

The output voltage from IC2 may be varied, using preset-potentiometer VR2, from 5V (the regulator voltage) up to around 12V, thus making it fairly universal for most applications. A changeover switch S3 is provided to change the polarity of the d.c. applied to the personal stereo's d.c. input.

Fig. 1. Full circuit diagram of the audio section of the Personal Stereo Amplifier. The "preset" power supply circuit is shown opposite, output voltage is set by VR2.

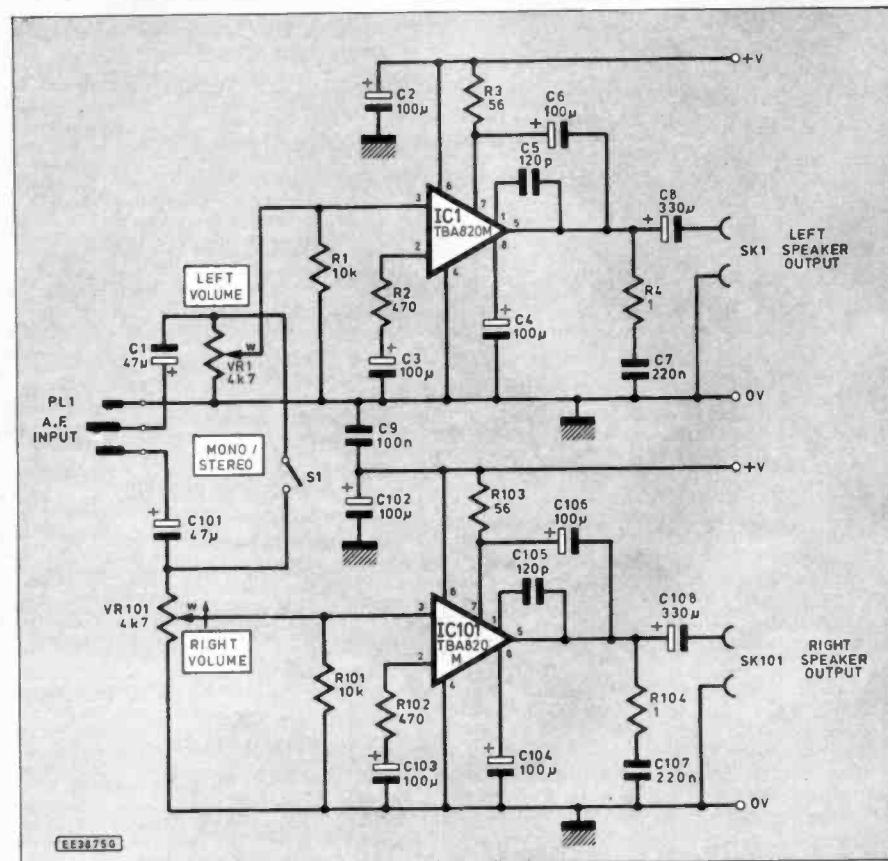

Socket SK2 allows for the user to use an already existing a.c.-d.c. adapter instead of the internal mains supply. A changeover switch is not necessary here as the bridge rectifier formed by D1 to D4 protects the circuit from any reverse voltages.

DESIGN OPTIONS

One or two features of the present design could be omitted or changed if desired. For example, the internal mains supply could be omitted – saving the cost of the transformer and associated components – and utilising the existing a.c./d.c. adapter. Note that the main amplifier will work off a variety of voltages and does not need the voltage to be especially stable.

The design used two separate volume controls as this is the writers' preference although it is probably more convenient to use a "ganged" stereo variable potentiometer. Note that whichever method is used, the control(s) must be of *LOG* law type.

A bridge rectifier in a single encapsulation could be substituted for the four separate diodes if this is more convenient. The author also preferred push switches for S1 and S2, (mainly because these were already to hand!) as they look more attractive than toggle switches. The constructor may wish to change these, in which case the mains neon could be omitted as the toggle



switch will show if the unit is switched on or off.

The Mono/Stereo switch could also be omitted as most cassette tapes and radio programmes are in stereo, but was considered to be useful for a.m. medium wave broadcasts.

CONSTRUCTION

The amplifier is built on a single-sided printed circuit board (p.c.b.), the topside component layout and full size underside copper foil master pattern being shown in Fig. 2. This board is available from the *EE PCB Service*, code EE808.

Some readers may note that the p.c.b. is reasonably spacious, not using in its construction any vertical mounting components (except the regulator). This allows a degree of flexibility in the size of components, particularly that of the capacitors. If desired (not part of the PCB Service) the p.c.b. could be scaled down to fit whatever case you may have.

If desired the circuit could also be constructed on plain perforated board following a similar layout as in the p.c.b. design. Stripboard is NOT recommended due to the capacitive effects of the unwanted tracks.

Before continuing with construction decide carefully on the options described earlier and vary the construction as you go.


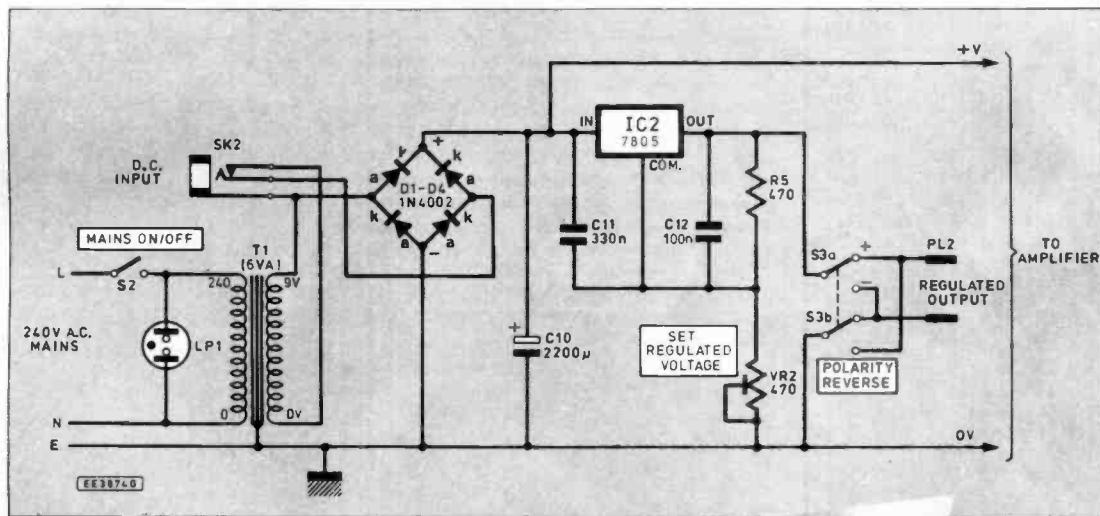


Fig. 1a. Power Supply

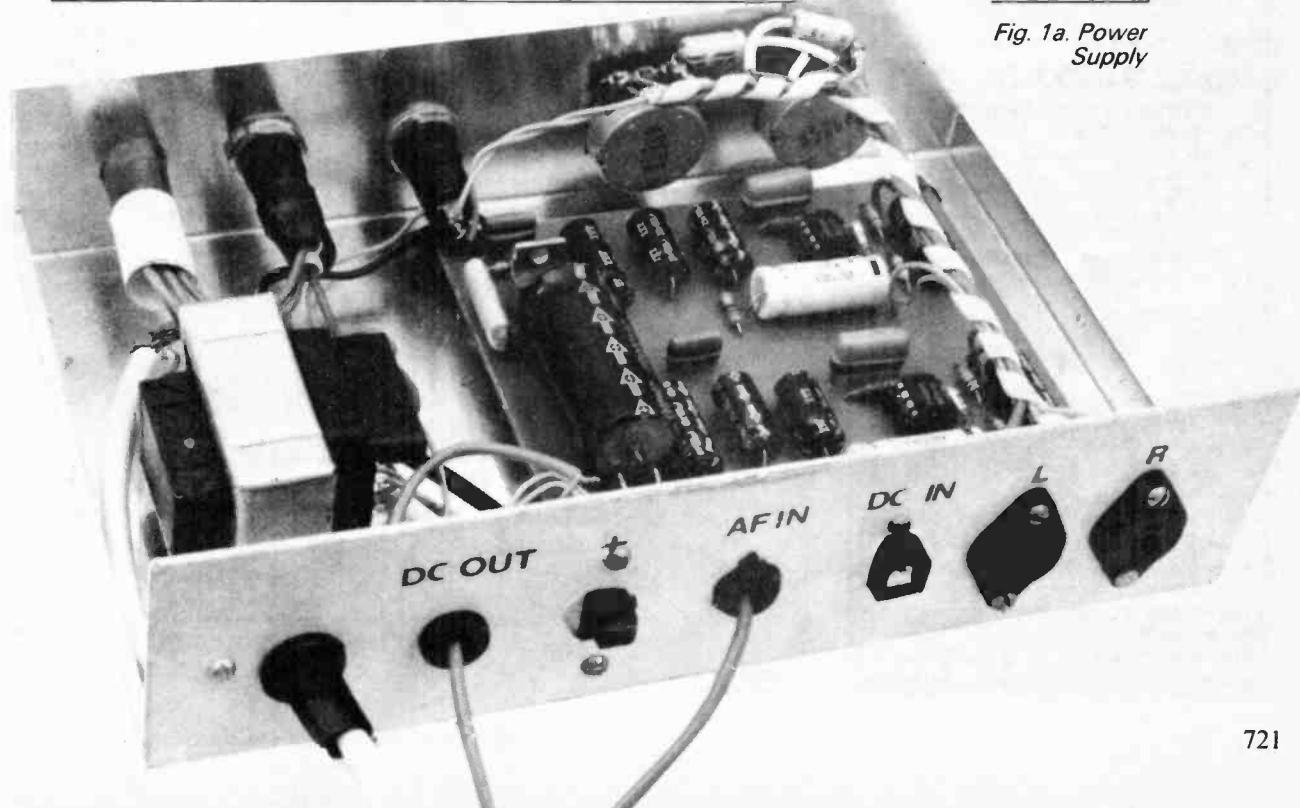

COMPONENTS

Resistors

R1, R101 10k (2 off)
 R2, R5, 470 (3 off)
 R102 56 (2 off)
 R4, R104 1 (2 off)
 All 0.25W 5% carbon film

**See
SHOP
TALK
Page**

Potentiometers

VR1, VR101 *4k7 min. rotary carbon,
 log (2 off)
 VR2 1k horizontal p.c.b.
 mounting preset, lin.

Capacitors

C1, C101 47 μ axial elect., 25V
 (2 off)
 C2, C3, C4,
 C6, C102,
 C103, C104,
 C106 100 μ axial elect. 25V
 (8 off)
 C5, C105 120p polystyrene (2 off)
 C7, C107 220n polyester (2 off)
 C8, C108 *330 μ axial elect. 25V
 (2 off)
 C9, C12 100n polyester (2 off)
 C10 2200 μ axial elect. 25V
 C11 330n polyester

Semiconductors





D1, D2, D3,
 D4 *1N4002 1A 100V
 rectifier (4 off)
 IC1, IC101 TBA820M audio
 amplifier (2 off)
 IC2 7805 5V 1A positive
 regulator

Miscellaneous

PL1 *Stereo jack plug 2.1mm
 or 2.5mm
 PL2 *Mono line jack socket
 2.1mm or 2.5mm
 SK1, SK101 Loudspeaker chassis
 socket (2 off)
 SK2 *Chassis mounting jack
 socket 2.1mm or
 2.5mm
 S1, S2 Single pole push or
 toggle switch
 S3 Standard d.p.d.t. slide
 switch
 LP1 Mains neon 240V
 T1 Mains 6VA transformer,
 mains primary; two
 secondaries 0-9V at
 300mA or one
 secondary 0-9V at
 600mA

Printed circuit board available from **EE PCB Service**, code EE808; metal case,
 leather-grain finish, size 200mm x
 125mm x 50mm; two control knobs;
 8-pin d.i.l. socket (2 off); stereo
 screened cable; mono screened cable;
 3-core mains cable; connecting wire;
 solder; hardware etc.

Items marked * - See text

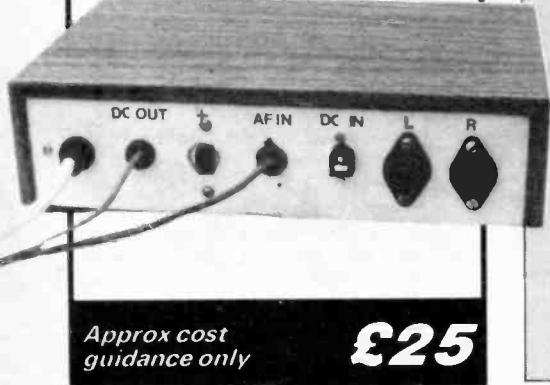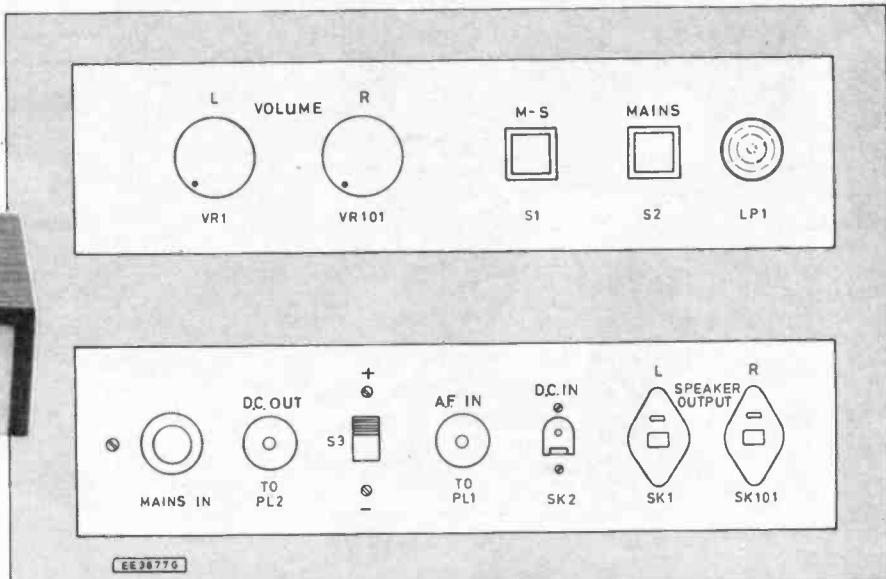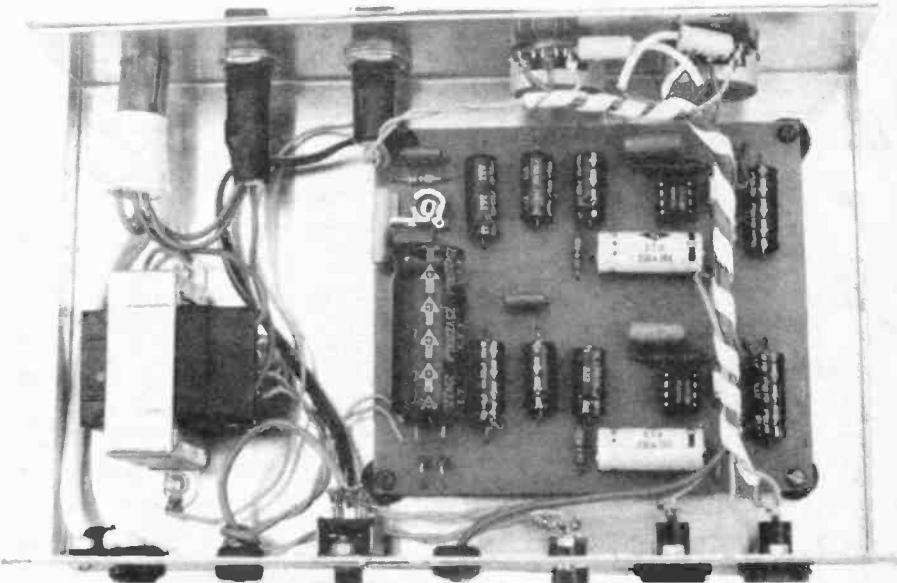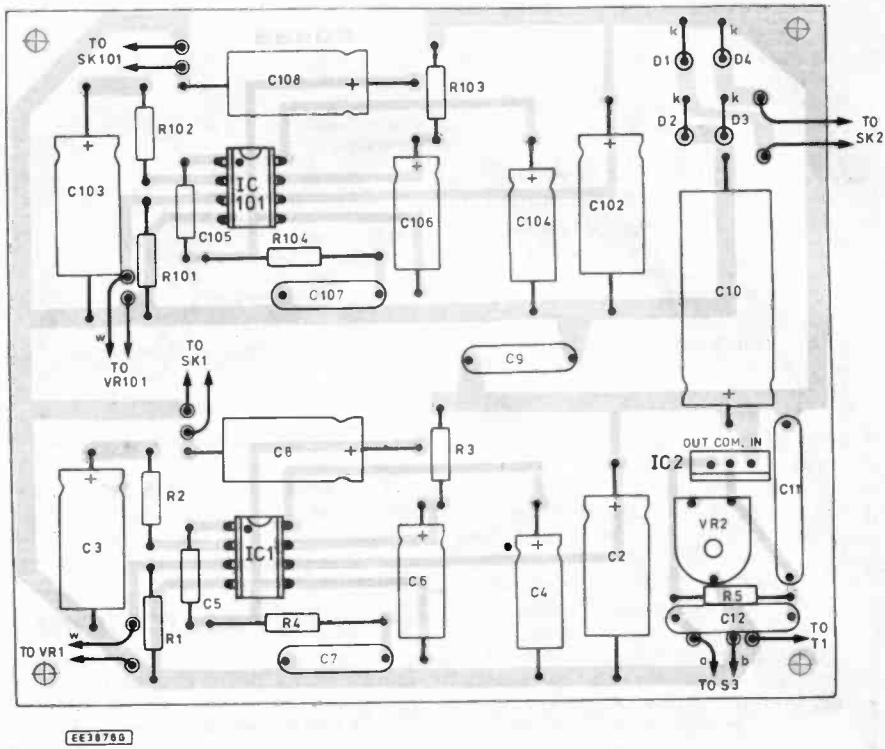


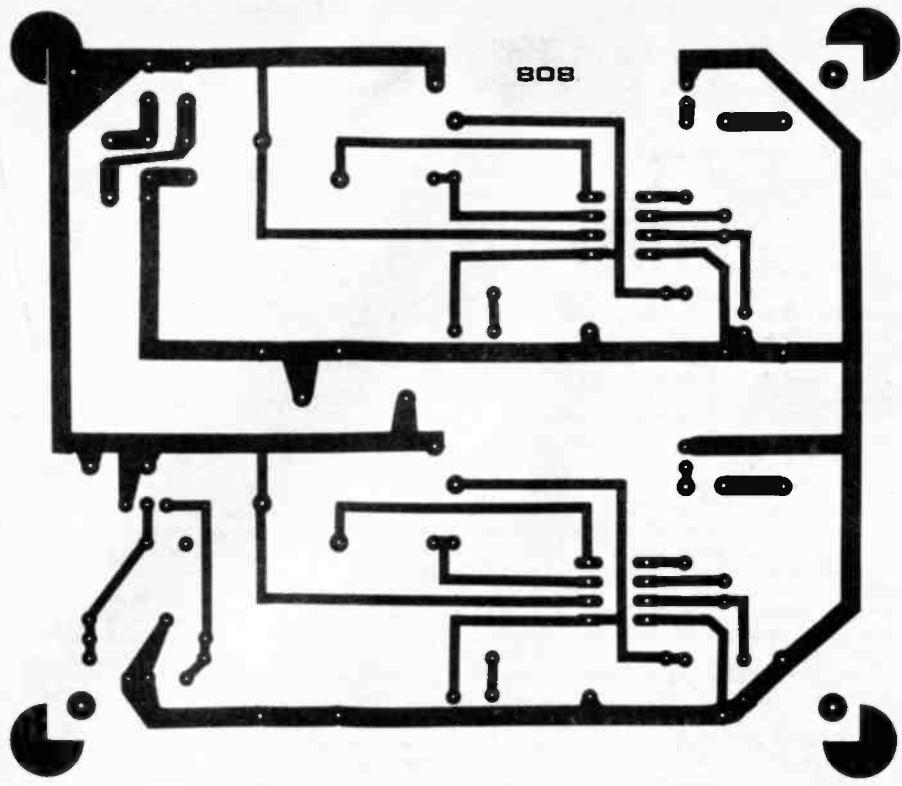


Fig. 2. The printed circuit board component layout (above left) and the full size underside copper foil master pattern (above).

Fig. 3. (bottom left). Suggested front and rear panel component layout.

Fig. 4. Interwiring details from the circuit board and front and rear panel mounted components. Layout of components inside the completed unit is shown in the photograph left centre.

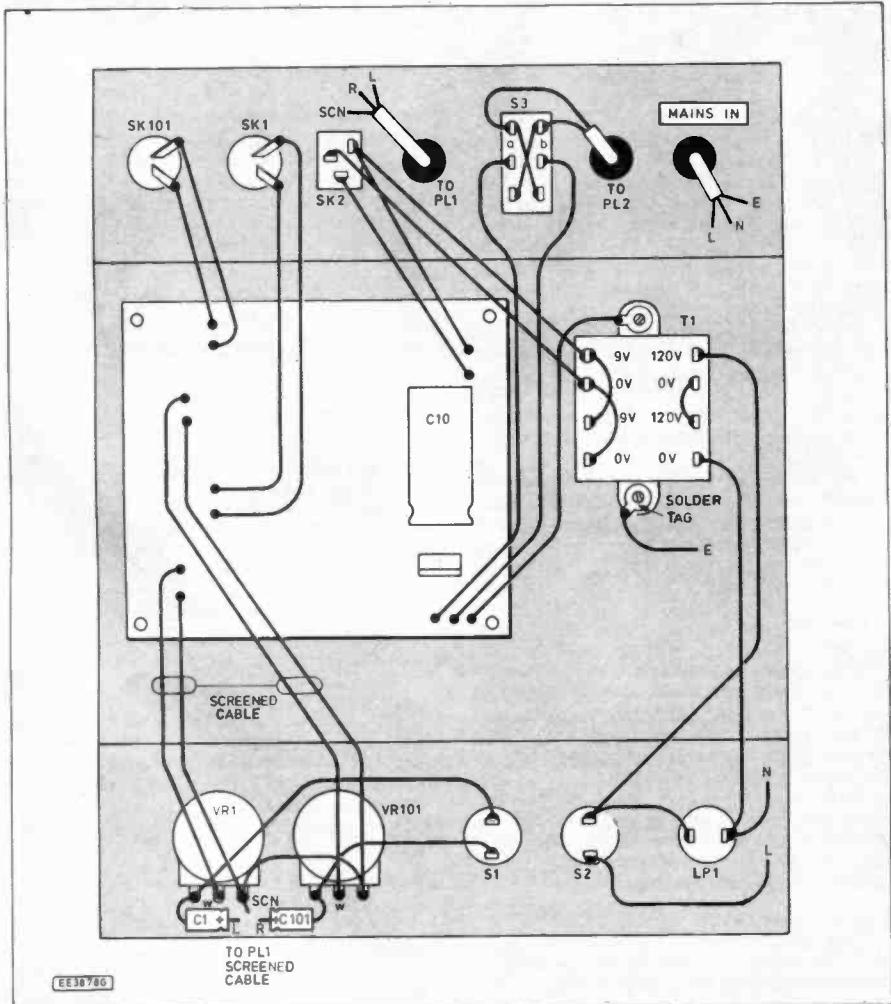

First though, examine your personal stereo and ascertain the diameter of the d.c. input socket and the headphone output socket. They will either be 2.1mm or 2.5mm, choose the correct type and fit them where shown.

The recommended layouts of the front and rear panels are shown in Fig. 3 and could, of course, be varied as desired. It is important though to use a metal case to provide a certain amount of screening.

INTERWIRING

The final wiring details are shown in Fig. 4. Check carefully the connections to the transformer as those shown may not correspond exactly to the type you are using. *It is most important to insulate ALL mains wiring using either sleeving or insulating tape.*

It is very important that the p.c.b. "earth" be connected to the metal case chassis, by means of a solder tag under the transformer mounting. Also, if you are using the mains supply connect the Earth lead of the mains input to a similar tag.

Remember to use screened cable when wiring from the potentiometer(s) to the p.c.b. and input plug to the potentiometers. The left-hand channel is normally the "tip" connection on the jack plug, but do check first.

If you are going to use the amplifier with just one type of stereo, then switch S3 may be omitted and the d.c. output cable can be connected permanently in whatever polarity is required. Use screened cable for this.

Some readers may note the lack of heatsinking on the amplifier i.c.s. and regulator. In the prototype version this was not a problem, although the regulator did operate slightly warm.

If needed then small squares of aluminium may be Superglued to the amplifier i.c.s and bolted to the regulator. No more than one square centimetre will be needed for the i.c.s, and perhaps slightly larger for the regulator.

Finally, remember to fit a 3A fuse in the mains plug, as the unit is not itself fused.

IN USE

Using the Personal Stereo Amplifier is quite straightforward. Simply plug the "A.F. In." lead into the Headphone output socket of the personal stereo, and the "D.C. Out." lead into the D.C. In socket of the stereo. If you are not using the internal mains supply then you will need to plug the stereo's a.c./d.c. adapter into the "DC In" socket on the amplifier.

Remember to adjust preset VR2 for the voltage required for the type of personal stereo you are using. Set the volume control of the stereo to three-quarters of maximum output – absolutely no more – if you do so distortion will be introduced and will overload the amplifier. It will be wise to experiment with the setting of the stereo's volume control to achieve a correct balance.

ON NO ACCOUNT connect the output from the amplifier to headphones of any type. Even with just over one watt output damage to the ears could result.

Remember that resistor R2 sets the gain, the smaller the value the larger the gain and hence larger the output. Conversely, increasing the value reduces the output and this may be a consideration if the output of the personal stereo overloads the amplifier even if the volume is well turned down. □

SHOP TALK

with David Barrington


Mini Lab

It is important when buying components for the Teach-In '93 series Mini Lab project that the items will fit on the p.c.b. and are suitable for use with the series. These restraints mean that a number of components must be of the correct type and manufacture and therefore we have provided the following detailed information.

The variable resistors are PIHER fully enclosed types with the optional clip-on thumbwheel, available in various colours, these come from Cricklewood Electronics. Toggle switches are from the C&K Z101 range available from Farnell, 148-705, or Maplin, FH00A. Although designed for panel mounting, they fit the p.c.b. without adaption.

The current rating is important because this switch later turns the 5V rail on/off, and 1A+ rating is required. Other types either will not fit the p.c.b. or have low ratings. ElectroValue also sell C&K toggle switches but they haven't been tried. We think they will also fit.

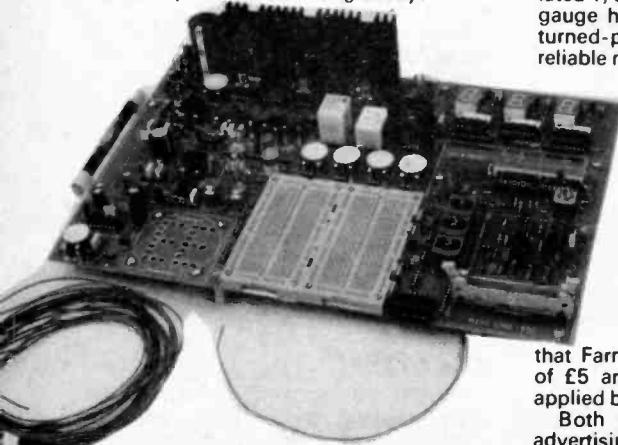The push switches are from the MEC range available from Farnell as follows (a limited range is listed by Maplin - part no's. in brackets): switch body 148-464 (FP51F); red bezel 148-474 (FP53H - black); buttons engraved 1, 2 or 3 149-245/6/7 (UH58N red unengraved).



It is important that the correct turned-pin s.i.l. sockets are used. We recommend beginning with two 32-way strips: Farnell 170-715 or Cricklewood Electronics also supply. The RS 402-642 (available from Electromail - see note below) is the more expensive wire-wrap version. These are repeatedly used in future parts, so buy in a small stock. No other types are suitable.

The buzzer or audible warning device is the RS 245-017 only. Very cheap, others won't fit the board. Otherwise, stick a wire-ended type onto the board and solder the leads to the p.c.b.

Relay, recommended RS 346-637 or Farnell 103-080. Again very cheap. 6V 0.1A M.E.S. bulb and holders, the p.c.b. was designed to fit the Maplin JX87U. The 6V 0.6W M.E.S. bulbs are commonplace.

P.C.B. mounting "Jacks", Farnell 149-318/9 or RS 434-712 will fit directly. Farnell 149-319 is recommended because it's gold plated. P.C.B. 0.5in. insulated shorting link plug, Farnell 149-315/6/7 (black/red/blue) is the only source we know for this part. The RS version won't fit. These components are used in future projects as on-board selector switches for frequency, i.e.d. voltmeter f.s.d. selection, etc.; in total the Mini Lab needs 17 "jacks" and four shorting plugs.

P.C.B. mounted "pluggable" screw terminals. The Pluggable types permit the terminal blocks to be unhooked without having to screw/unscrew terminals, thus reducing strain on the p.c.b. track. The screw terminal mates with a board-mounted pin header. Extremely convenient to use. RS 426-142 (2-way) and 426-143 (4-way) plus 24-way pin header 426-165.

Trouble is, RS only sell in packs of five. Therefore, choose the identical Farnell 105-499 (2-way), 152-007 (4-way) and one pack of 25 loose pins 105-503, all available singly. Alternatively, use normal screw terminal blocks but you need a screwdriver to unhook wires all the time.

Breadboard (solderless prototyping board) - Veroblock; check the prices carefully before buying! Maplin YL11M; Greenweld Hobbiblock looks suspiciously similar; ElectroValue or Cirkit Hobby Bloc.

P.C.B. mounting pillars and screws: 20mm length or more. Fully insulated nylon types are O.K. - they are needed to keep the p.c.b. clear of any working surfaces where the tracks might be shorted out.

In later parts, a loudspeaker is mounted under the board so it has to be stood off anyway. The central stand-offs also impart mechanical strength to the board and stop it from flexing when you press down on it.

Interconnecting wire - single core insulated 1/0.6mm (0.28mm²) as required. This gauge has been proven to work with the turned-pin sockets to provide a quick and reliable means of connection.

All RS items are available to anyone with an RS account directly from RS Components or via mail order from Electromail, PO Box 33, Corby, Northants NN17 9WZ (0536 204555) (many schools and colleges keep either an RS or an Electromail catalogue) Farnell Electronic Components are at Canal Road, Leeds, West Yorkshire LS12 2TU. Please note that Farnell have a minimum order charge of £5 and post and packing charges are applied by all the companies.

Both Cricklewood and Maplin are advertising in this issue. Electrovalue are at 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. (0784 433603). The Greenweld catalogue supplied free with this issue should also prove very helpful.

The Mini Lab p.c.b. is only available through the EPE PCB Service see page 754. Please remember that in consideration of the effort by both Authors which went into the Mini Lab design, the copper track layout remains Copyright Dytronics 1992.

We think the design of the Mini Lab is the most ambitious and versatile educational system undertaken in recent years by any magazine, and will be a credit to *Everyday with Practical Electronics*: we're justifiably proud of the system and hope it will capture the imagination of young readers and more mature students alike.

Since it contains everything needed for even quite advanced circuit development, the convenience of the Mini Lab might even appeal to experienced electronics technicians and enthusiasts.

EPE Altimet

The special pressure transducer type MPX100 called for in the EPE Altimet project comes in two versions, plastic cased and uncased.

Either type can be used, but it is preferable to use the cased version and this one carries the type prefix MPX100AP. The MPX100AP version is stocked by Maplin, code UH37S.

The uncased one is marked MPX100A and if this is to be used it must be insulated from the p.c.b. copper tracks. If any readers have difficulty in locating the voltage converter, ICL7660, or the display driver, ICL7106, they are listed by Viewcom and Electromail. The handheld case is also listed by Electromail (507-983) but it can now be obtained from most of our advertisers.

The altimeter printed circuit board is available from the EPE PCB Service, code 807.

Personal Stereo Amplifier

We do not expect too many problems when shopping around for parts for the Personal Stereo Amplifier. The plugs and sockets used in the model were purchased from Cricklewood but they also appear in many of our advertisers listings. When ordering the volume control potentiometer, be sure to ask for a "Log" type.

The TBA820M 2W power amp i.c. seems to be fairly widely stocked and most suppliers should also be able to offer a suitable 6VA mains transformer. The ones used in the prototype came from Maplin.

The woodgrain finish aluminum case used in the model no longer seems to be in existence. However, one of the "leather-grain", p.v.c. covered aluminium boxes from Marco Trading (0939 232763) seem ideally suited for this unit: Marco code Box/J9. You could opt for the "black" vinyl-cover type, available generally.

Vibration Alarm

Some readers may experience local difficulties sourcing the p.c.b. mounting choke for the Vibration Alarm. Looking through the Cirkit (0992 4444111) catalogue, their range of inductors, including chokes, is probably one of the largest in our market today and one of their RB series should fit the bill.

Although the photograph of the prototype model shows the use of a toggle switch, the slider version seemed to be more readily available and was used in the final version, hence its inclusion on the working diagram. It may seem strange to include the switch in the battery negative lead, but it ensures that capacitor C2 is fully discharged each time the unit is switched off.

Reaction Timer

We cannot see that there will be any component buying problems for those wishing to build the Reaction Timer project.

Be sure to make it clear that you require "low current" types when ordering the l.e.d.s. The multi-colour ribbon cable is now stocked by nearly all component advertisers.

Battery/Mains Inverter - Daughter Board

This time around, the i.c. used in the Battery/Mains Inverter - Daughter Board are from the ever popular 4000 series of i.c.s. and should be widely stocked. They are certainly listed in the current Viewcom (081 471 9338) advertisement and in the latest Greenweld, Cricklewood and Maplin catalogues.

The small printed circuit board is available from the EPE PCB Service, code EE809.

As a footnote and at the time of going to press, we understand that although the original M706B1 50Hz timebase i.c. is still being listed in the very latest Maplin catalogue they are only carrying stocks in the region of "tens" not hundreds; their quote!

PLEASE TAKE NOTE


Quicktest (Sept '92)

The op.amp (IC2) used in the Quicktest project is, of course, the ubiquitous 741.

Quite how the error escaped three checks we do not know, but please be assured we do try very hard.


EASY-PC PCB and Circuit Diagram CAD

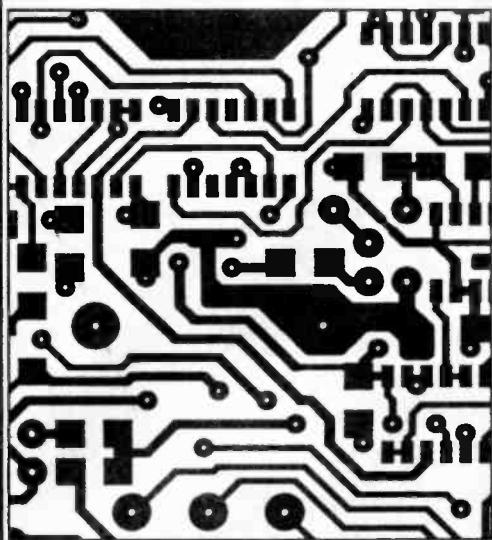Forget using tapes and lightbox! Create your Circuit Boards using CAD - like the professionals.



Over 13,000 Installations in 70 Countries Worldwide!

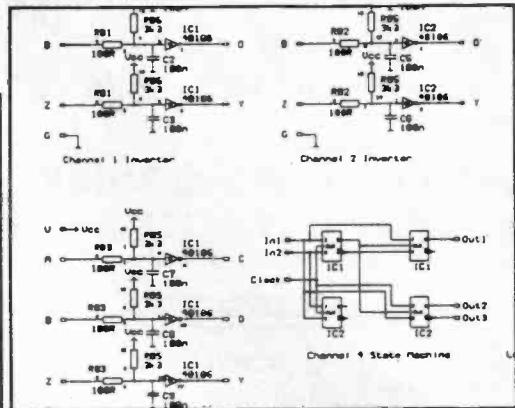- Runs on PC/XT/AT etc. with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design Schematics Single and Double sided and Multilayer boards including Surface Mount.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Extremely powerful.
- Very easy to use.






EASY-PC

**Only
£98.00!**

Plus P&P+VAT

Technical support
is free, for life!

Options:- 500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

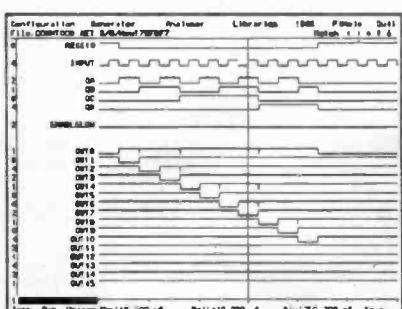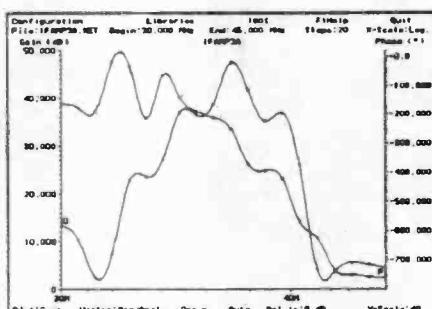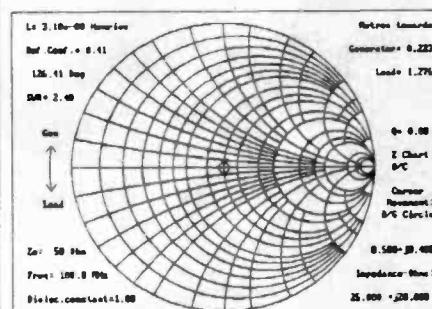DIGITAL SIMULATION £195	ANALOGUE SIMULATION £195	SMITH CHART CAD £195
 <ul style="list-style-type: none"> ● At last! A full featured Digital Circuit Simulator for less than £1000! ● PULSAR allows you to test your designs without the need for expensive test equipment. ● Catch glitches down to a pico second per week! ● Includes 4000 Series CMOS and 74LS Libraries. 74HC/HCT libraries only £48.00 each. ● Runs on PC/XT/AT/286/386/486 with EGA or VGA. 	 <ul style="list-style-type: none"> ● NEW powerful ANALYSER III has full graphical output. ● Handles R's, L's, C's, Bipolar Transistors, FET's, OP-amp's, Tapped and Untapped Transformers, and Microstrip and Co-axial Transmission Lines. ● Plots Input / Output Impedance, Gain, Phase & Group Delay. ● Covers 0.001 Hz to > 10GHz ● For PC/XT/AT/286/386/486 with EGA or VGA. ● Very fast computation. 	 <ul style="list-style-type: none"> ● Z-MATCH II simplifies RF matching and includes many more features than the standard Smith Chart. ● Handles transmission line transformers, stubs, discrete components, S Parameters etc. ● Supplied with many worked examples. ● Superbly easy to learn and use. ● Runs on IBM PC/XT/AT/386/486, CGA, EGA, VGA. ● Ideal for Education and Industry.

For full information, Write, Phone or Fax:-

Number One Systems Ltd. 

REF: EVD, HARDING WAY, ST.IVES, HUNTINGDON, CAMBS, ENGLAND, PE17 4WR.

Telephone: 0480 61778 (7 lines) Fax: 0480 494042

International: + 44 -480-61778, Fax: +44-480-494042 ACCESS, AMEX, MASTERCARD, VISA Welcome.

- TECHNICAL SUPPORT FREE FOR LIFE!
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

Teach-In '93

with Alan Winstanley
and Keith Dye B.Eng(Tech)AMIEE

Part 1

Teach In '93 continues a tradition of offering an interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles to give the student a solid foundation before proceeding onto further topics.

In accordance with the recommendations contained in the various GCSE Electronics Syllabuses, which themselves comply with the National Criteria for Science, no attempt is made to explain the "physics" behind any electronic components. Instead, we are much more interested in what they look like and how to use them, rather than what makes them work in the way they do. Many text books on electronics start with the very dry theory of atoms, electrons and semiconductor physics, much of which in our opinion may deter the less able candidate:

INTRODUCING THE MINI LAB

As a means of helping to demonstrate various topics, the authors have designed a unique electronics "Mini Lab" which should be of great assistance to the novice or student following the series. Once the series has been completed, the Mini Lab will be of on-going use to help readers develop ideas of their own, no doubt utilising many principles gleaned from Teach In.

The Mini Lab consists of a single printed circuit board (p.c.b.) which is divided into various areas. As we proceed through the Teach In course, the areas will gradually fill with a variety of interesting and economical circuits which demonstrates a topic and forms a useful piece of equipment to aid the student.

Although it is necessary to solder components to the board, the use of a p.c.b. helps to ensure a high success rate for candidates, with less chance of any disappointing failures. The component count is spread over many months, and the use of plastic boxes and enclosures is avoided, helping to keep construction costs down. A solderless plug-in prototyping board is incorporated which is regularly used to connect up reusable electronic components to form a circuit.

The Mini Lab develops from basic principles, working all the way through from switches, batteries and bulbs to a microprocessor development system - the "Micro Lab" - which is connected to the Mini Lab through an expansion unit. Constructional details relating to the Mini and Micro Labs are given separately, as and when required.

apart from being of academic interest only, it can also be a bit boring!


We invited a highly-qualified and experienced Moderator and GCE A Level Examiner to join us and the text incorporates his very valuable suggestions to enable Teach In to have maximum appeal to those candidates undertaking GCSE or GCE examinations and coursework. Teach In we hope will also appeal to the experienced *Everyday with Practical Electronics* reader who might like to brush up on his or her theory.

we have chosen is the popular "Veroblock" type, and several blocks can be joined together to form larger units for more ambitious designs.

Take care of your new breadboard: the wires of components should slide in and out easily. Don't force unduly large wires into the socket strips, and avoid bent or deformed wire ends which might damage individual

BREADBOARD

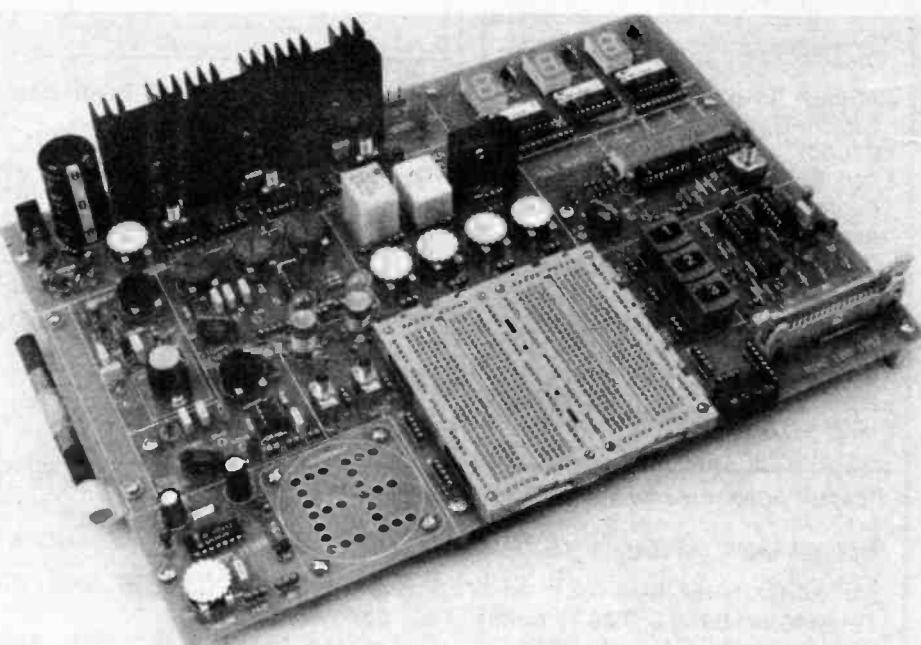We'll shortly be using the plug-in "breadboard" area of the Mini Lab. This is essentially a set of spring contacts interconnected to form a pattern of conducting rows. You can simply push components into them and connect parts together, without the need for soldering. Obviously you can remove and re-use the parts too. The breadboard



The complete Mini Lab which is used for the tests and experiments in Teach-In.

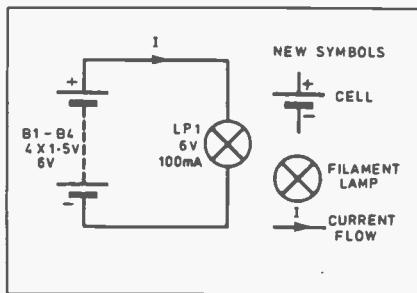


Fig. 1.1(a). Basic electrical circuit.

sockets. A pair of fine-nose pliers might help when inserting or removing wires. Used with care, your breadboard will last many years. In the meantime, welcome aboard to Teach In!

Our analysis of electricity starts with some simple battery and bulb experiments, and the Mini Lab is immediately pressed into service to help demonstrate a few basic principles. We won't let you proceed until the foundations are firmly laid!

ELECTRICITY – WHAT IS IT?

For the first two parts of Teach In the Mini Lab is operated by a battery at a safe low voltage. Later, as the Mini Lab grows, a mains power supply is described which you will be able to build with complete confidence. Take a look at Fig. 1.1(a), which shows a very simple electrical circuit consisting of nothing more than four 1.5 VOLT (V) "dry cells", labelled B1 to B4, and a bulb (LP1).

Don't worry too much about any symbols which may be unfamiliar, because soon you will be able to read a circuit diagram as easily as reading this text (we hope!). We will always introduce new symbols by highlighting them separately next to the circuit diagram. The symbols which you see represent the cells and bulb: B1 to B4 are four 1.5V cells, and the circle with a cross is a simple indicator bulb, like a torch bulb.

All four cells are connected together one after the other to make a six volt battery – just like you might need in a radio or cassette recorder for example. It's important that they are all connected the right way round with respect to each other or the circuit simply won't work.

As you will doubtless know, cells have two terminals marked "+" and "-" and the negative terminal of one is connected to the positive of the next. The diagram shows you which terminal is which. Often designers don't bother showing all four cells in the circuit diagram, just the "first" and "last".

The bulb is labelled "LP1" for "Lamp 1" and the supplier's catalogue says that it's rated at "6V 100mA". What do these ratings mean? To find out, let's build the circuit shown in Fig. 1.1(a).

BATTERY PACK

As we have said in the initial stages of this series, your Mini Lab is powered by an external battery pack. In Part Three it becomes mains-operated via a versatile power supply unit. For now, you must select the "EXT BATT" option as your source of power by inserting a selector shorting plug between the appropriate sockets of the "Power Supply" section: this is clearly marked on the board. You *must* do this, otherwise your battery pack will remain disconnected.

An on-off switch is also fitted to the Mini Lab, so that you can easily turn the 6V battery supply on or off when required. It's best to switch off before making any modifications to your experiment.

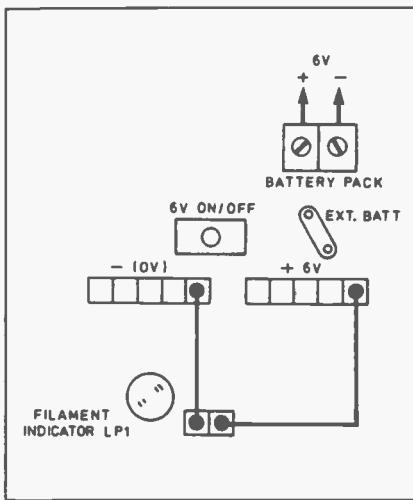


Fig. 1.1(b). The electrical circuit built on the Mini Lab. The 6V Battery Pack is connected externally by screw terminals. Use the ON/OFF switch as needed, and ensure the "EXT BATT" option is selected with a shorting plug. See the Mini Lab constructional details. The "6V ON/OFF" switch is not shown in any demonstration circuit diagrams.

Refer to the constructional details of the Mini Lab which describes the assembly and connection of the 6V battery pack. The positive and negative terminals of the 6V supply are available on distribution socket strips mounted on the Mini Lab board, and you can now build the circuit as shown in Fig. 1.1(b). Insert solid-core jumper wires as shown, to connect the battery to either one of the filament indicators clearly marked on your board.

The bulb should illuminate. (If not, check the bulb is screwed fully home, and the cells are the right way round.) So far so good! What is happening is that electric current is flowing out of the positive terminal of the 6 volt battery pack, through the bulb which lights up, and back into the negative terminal. (Take care not to "short out" the battery or a very high current will flow, which could ultimately damage it.) So what's the difference between voltage and current?

VOLTAGE

Batteries are a source of electrical energy. We call this the "electromotive force" or e.m.f. for short. The energy is still there in the battery even if you disconnect it from the circuit (unless the battery is flat).

Across the terminals of each individual 1.5V cell exists a potential difference of 1.5 volts. Fitting B1 to B4 together in the holder connects the cells in series to make an overall potential difference of 6 volts. So a potential difference (p.d.) can exist between two points in a circuit, compared with an electric current which flows through the circuit. This is the most fundamental of all rules in electronics.


Strictly speaking it's wrong to talk of "+6 volts and -6 volts" because this implies that the p.d. is actually 12 volts. More accurately we should say "+6 volts with reference to 0V", the p.d. is then 6 volts. This becomes important when we talk later about split power rails, which have both positive and negative voltage supplies with reference to 0V.

If no p.d. exists between two points, then no electromotive force is present and so no current can flow if you try to make a circuit. A voltage needs to exist before current can flow, and the current always flows from the higher voltage (the most positive one) to the lower voltage (the least positive/ most negative one) in the circuit.

Because the current only flows one way in this instance, it's called direct current or "d.c." for short. In other areas of electronics, we will be looking at currents which flow forwards then backwards – alternating current or "a.c." for short. You might see "240V a.c." marked on an electrical appliance designed to be plugged into the mains. When you're dealing with batteries, the voltages are always understood to be d.c.

CURRENT

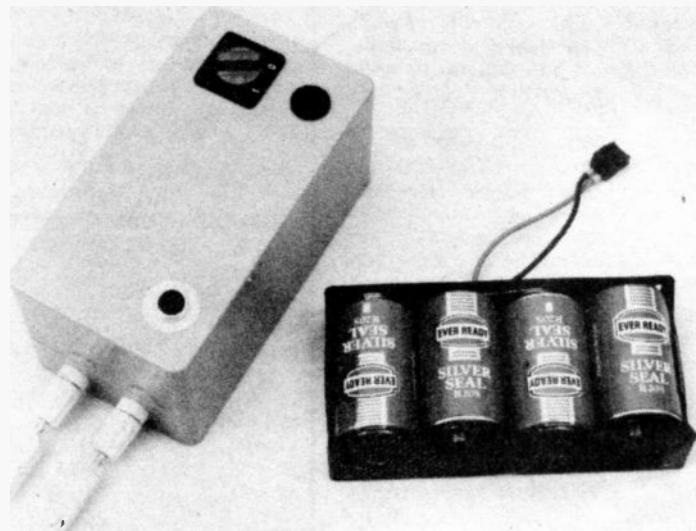The electric current which flows through the circuit is actually a measure of the rate of flow of electric charge past any given point. Electric charge is the fundamental "raw material" of electric current, which in simple terms consists of nothing more than a flow of electrons. More electric charge on



The mains supply unit (detailed in a later issue) and battery pack used with the Mini Lab.

the move implies a greater rate of flowing electrons – this means that a "faster" or higher current is flowing.

By convention it's easiest to think of current flowing from the most positive to the most negative potential: this theory dates back to the days of the earliest discoveries of the principles of electricity. The trouble is, we now know that the theory isn't true!

Scientists have since discovered that electrons have a negative charge and are attracted to a more positive charge (just like dissimilar poles of a magnet are attracted to each other), so in real life electrons actually flow from the most negative to the most positive potential and not the other way round.

There's no need to worry: mercifully everyone still talks in conventional current terms, where current is deemed to flow from positive to negative potentials. This doesn't affect circuit design or our understanding of electronics whatsoever. Those studying atomic physics, for instance, might talk in terms of what's happening in real life at sub-atomic level – but in electronics, we don't need to.

Some substances are very good at letting current flow through them. Copper is commonly used as the conductor in electric wire because it lets current flow through it extremely easily – it has plenty of loose electrons available which can carry lots of electric current. Other conductors include aluminium, steel, lead, gold, silver and tin. Gold is a particularly useful element which is often used to plate electrical contacts, so that they don't corrode with age and become unreliable.

INSULATORS

An insulator contains hardly any free electrons and so is very poor at letting current flow. For example, an electrical cable supplying your TV will have copper cores carrying "live" electric current, each core being insulated with a plastic such as P.V.C. The insulator will not allow current to flow through, so it protects you from electric shock. Other examples of insulators are glass, wood, ceramic and rubber.

Current is given the symbol I and is measured in Amperes, or often "Amps" (A) for short. Voltage is given the symbol V and, not surprisingly, is measured in Volts.

Sometimes the units of volts and amperes can be too large to be of use in electronics. Designers often have to use prefixes when talking about volts and amps to make them more manageable units. Common prefixes which we will use a lot when describing current and voltage are:

SYMBOL	PREFIX	FRACTION
m	milli	1/1000
μ	micro	1/1,000,000

Example:

1mV = 1 millivolt = 0.001 volts.
so 100mV = 100 millivolts = 0.1 volts.
1 μ A = 1 microamp = 0.000001 amps.

To answer our question posed earlier, LP1 is rated at 6V (the bulb's maximum reliable operating voltage), at which voltage a current of 100mA (0.1 amperes) will flow through the bulb. We'll talk about millamps, microamps, and also millivolts, as necessary from now on – it saves having to write lots of zeros. There are other prefixes which we use in other areas of electronics, which we'll introduce when appropriate.

SWITCHES

On its own, our circuit of Fig. 1.1(a) isn't much practical use (except as a torch!) but

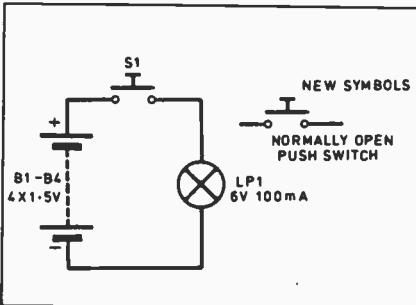


Fig. 1.2(a). Circuit with push switch.

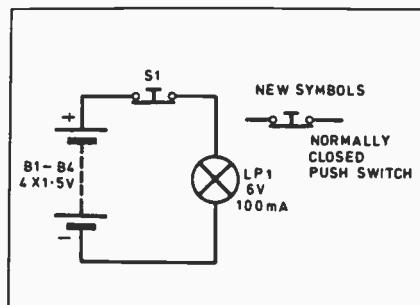


Fig. 1.3(a). Circuit with normally-closed switch

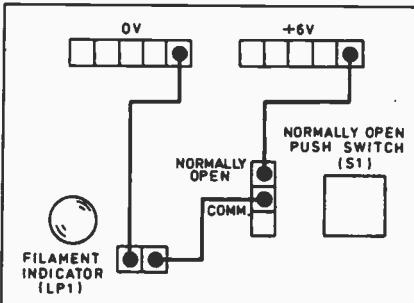


Fig. 1.2(b). Interwiring diagram – be sure to use the correct pins of the switch.

We can add some useful functions if we introduce some switches. The simplest of all switches is a basic push switch, see Fig. 1.2(a), which also shows the circuit symbol for this component (S1). This can be demonstrated with the Mini Lab as shown in Fig. 1.2(b), which places a normally-open (n.o.) push switch in series with LP1. Pressing S1 completes the circuit and the bulb lights – releasing it extinguishes the bulb.

A reverse effect can be achieved with a normally-closed (n.c.) switch, as shown in the circuit diagram of Fig. 1.3(a), which is wired up on the Mini Lab as shown in Fig. 1.3(b). Make sure you connect to the correct socket strips adjacent to the switch.

Here, pressing the switch actually breaks the circuit, interrupting the supply to the bulb. Releasing it restores power once more. Normally-closed circuits like this are used a lot in burglar alarms, for instance, where deliberately cutting a security wire or releasing a n.c. switch causes an alarm to sound.

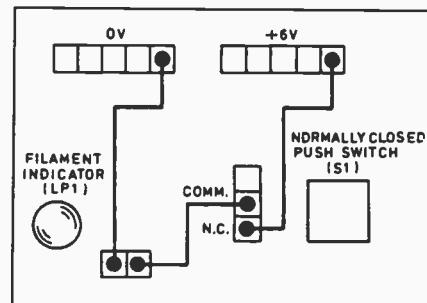


Fig. 1.3(b). Using the normally-closed contacts of a push switch.

Toggle switches are very widely used on equipment as on-off or control switches, and their circuit schematic symbol is shown in Fig. 1.4(a). S1 is a "changeover" toggle switch which can be switched between two circuits. Here, the two circuits are LP1 and a buzzer (audible warning device) labelled WD1. The moving contact (or "wiper") of S1 can be moved by operating the toggle (or "tang") between two positions.

Build this circuit on your Mini Lab by referring to Fig. 1.4(b), and compare your wiring with the circuit diagram so that you can see how we wired the circuit up. Now by operating S1, you can apply power alternately between the Mini Lab buzzer and the bulb. This type of switch is known as a single pole double throw switch or s.p.d.t. for short.

An interesting variation of this circuit is shown in Fig. 1.5(a) which utilises two s.p.d.t. toggle switches and a bulb. Connect up this circuit on your Mini Lab as shown in Fig. 1.5(b). What happens every time you

RESISTOR COLOUR CODE

Most resistors you see have four coloured stripes to indicate their resistance and tolerance. How do you know which way round to read the resistor? The gold or silver stripe features last in the code.


COLOUR NUMERAL MULTIPLIER TOLERANCE

1st & 2nd	%
Black	0
Brown	1
Red	2
Orange	3
Yellow	4
Green	5
Blue	6
Violet	7
Grey	8
White	9
Gold	5%
Silver	10%

EXAMPLES

Red/Red/Red/Gold =
 $2.2 \times 100R = 2,200 \text{ ohms or } 2k2\ 5\%$
Yellow/Violet/Orange/Gold =
 $47 \times 1k = 47k\ 5\%$
Grey/Red/Green/Silver =
 $82 \times 100k = 8,200,000 \text{ ohms or } 8M2\ 10\%$

We nervously offer the following mnemonic which might help you to remember the order of the colours: "Bad Boys Rape Our Young Girls But Violet Gives Willingly"! (Don't blame the authors.)

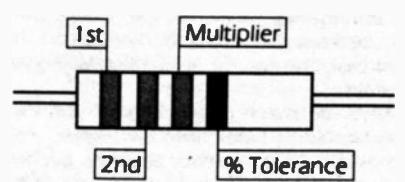

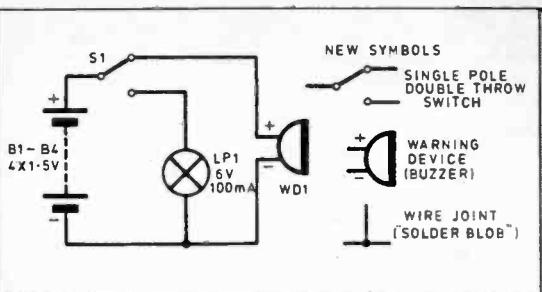


Fig. 1.4(a). Introducing a changeover switch to control a buzzer and bulb.

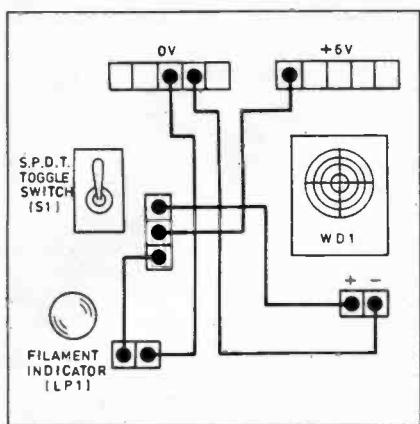


Fig. 1.4(b). Connecting diagram for a changeover circuit. The buzzer must be correctly polarised or it won't work. Use S1 to switch between the buzzer and bulb.

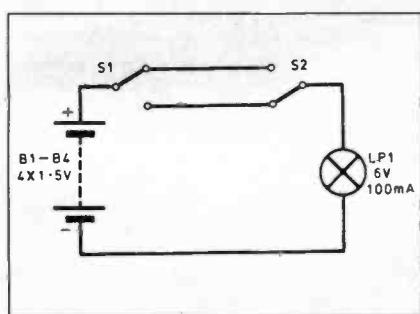


Fig. 1.5(a). Electrician's staircase lighting circuit.


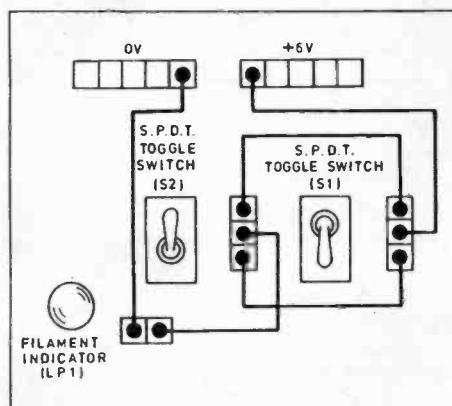
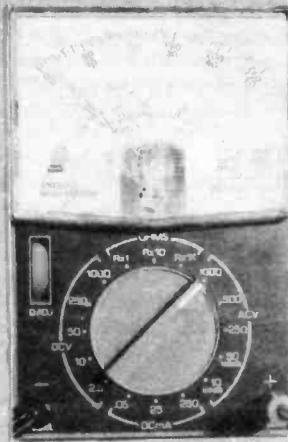


Fig. 1.5(b). Using both s.p.d.t. toggle switches to control a lamp.

operate a switch? You might find this sort of circuit in everyday use as a lighting circuit in a house – switches at the top and bottom of a staircase can control the light at the top of the stairs.

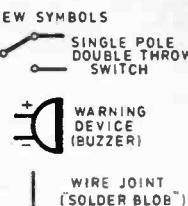There are many other types of switches available. Some types have two wipers, and can switch two completely separate circuits at the same time. These double pole (d.p.) switches, and some more switches besides,



An analogue multimeter.



A digital multimeter.

USING YOUR MULTIMETER

Multimeters are available in two types: *analogue* which uses a standard moving-coil meter movement, and *digital* which is much easier to read and generally more precise. They can measure current, voltage and resistance. Some can also measure other additional parameters like frequency or capacitance or even test transistors.

Multimeters, especially moving-coil types, are not perfect. When used to measure voltages, meters "look like" resistors in a circuit and can affect the circuit under test (see "Potential Dividers" for an explanation of loading effects). Typically, an analogue meter will be described as "20,000 o.p.v." (ohms per volt), which means that on, say, a 2V d.c. range, the meter acts like a 40k resistor. The higher the o.p.v. specification, the more accurate your voltage readings will be. In GCSE Electronics, "perfect" meters are always assumed so you need not worry about accuracy.

VOLTAGE MEASUREMENTS

When reading voltages, you need to make sure that your multimeter doesn't load your test circuit too much or you will obtain misleading results. Try to use a voltmeter on the highest range setting possible, so that the resistance of the meter is as large as practical. However, it's pointless trying to read a voltage of 500mV on a 50V f.s.d. (full scale deflection) scale, so you will have to compromise somewhere.

Voltmeters are of course used to measure potential differences across components such as resistors. It's wise to ensure that the resistance of your voltmeter (calculated from its o.p.v. rating) is at least ten times greater than any resistor across which you are measuring a voltage – see the "Ten Per Cent Rule". This way, you will not load the circuit excessively and will obtain acceptable accuracy.

CURRENT MEASUREMENT

Current flows from the most positive potential to the most negative, so connect the positive and negative test leads from your meter the right way round – see

the section on "Resistance and Ohm's Law" where we measure current through a resistor.

Always de-energise the circuit first, then insert the ammeter before powering up again. Start with a high current range, so that you avoid damaging the meter by overloading it. You can always switch to a lower range afterwards, but you should disconnect the power from the circuit in between switching ranges – unless you have an autoranging digital multimeter, which will take care of itself.

An ammeter "looks like" a short-circuit (almost) between its terminals. Never treat an ammeter as a load in itself – don't put it across a battery or power supply to see what happens, because any high short-circuit current which flows (several amps, in the case of an alkaline battery) may damage your meter and the battery.

RESISTANCE

If you have an analogue meter, you will notice that zero ohms is on the extreme right of the scale. Higher resistances are on the left, but the scale is non-linear and the calibrations tend to become cramped on the left. You should always "zero" your meter before testing resistance: do this by shorting the leads together and adjust the meter's zeroing control accordingly. You have to repeat this every time you change the resistance range.

Testing resistors etc. *in situ* in a circuit can often give strange results: this is generally because there might be other components actually in parallel with the component, which affects the resistor value – see "Resistors in Parallel" and "Potential Dividers" in the text.

Ohmmeters use an internal battery to enable them to measure resistance. You must always ensure that the circuit under test is fully de-energised when the meter is set to any resistance range, or damage may result.

RESISTOR COLOUR CODE

Most resistors you see have four coloured stripes to indicate their resistance and tolerance. How do you know which way round to read the resistor? The gold or silver stripe features last in the code.

are summarised in Fig. 1.6. We also show a one pole 3-way rotary switch.

Some switches are biased which means that they are spring-loaded in one direction. Press them to operate them, and release them to return to the previous state. An electric lawnmower uses this sort of switch – why?

Alternatively, some push switches are latching, which means that you press them once to operate them, and they stay like that when you release the actuator. Press them again to return to the previous state. A table lamp might use such a switch. Have a look through some catalogues to see if you can recognize different sorts of switches yourself.

In fact, we cheated a little when we designed the Mini Lab; you will have noted that both the n.o. and n.c. push switches (Figs. 1.2(b) and 1.3(b)) are both one and the same switch. It's actually a s.p.d.t. push switch which can form either a n.o. or n.c. function by selecting the relevant socket strip on your Mini Lab. Check it out by using the battery pack and bulb to confirm how it works.

Switches have electrical ratings which are indications of how large a voltage they can be allowed to switch without being damaged, and how much current their

is like squeezing the hosepipe to slow the water down.

We can examine the operation of the resistor by taking some measurements with a multimeter. We show you separately how to use your test meter – if necessary, read that section in conjunction with this part.

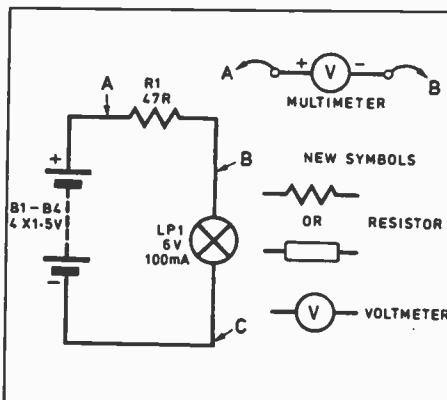


Fig. 1.7(a). A resistor in a circuit with the bulb. Also shown is the basic connection for using your multimeter when set to its voltage range. Connect the right way round!

voltmeter is represented by a circle containing the letter "V" and because voltmeters are polarised, you must connect them the right way round.

MULTIMETER

Connect the + terminal of your multimeter to location "A", and the - terminal to location "B" and read the voltage from the scale, noting it down as "Result 1" in the table below. Then repeat, with the + terminal to "B" and the - terminal to "C" (Result 2), and finally read the voltage at "A" (+) and C (-) to obtain Result 3.

OUR READING	TEST RESULTS:
Result 1 3.15V	(Voltage across the resistor)
Result 2 3.08V	(Voltage across the bulb)
Result 3 6.3V	(Voltage across the battery)

What has happened is that the potential difference (p.d.) across the battery pack has been split up between the resistor R1 and the bulb. The 6.3 volts of the battery is no longer placed solely across the bulb – some

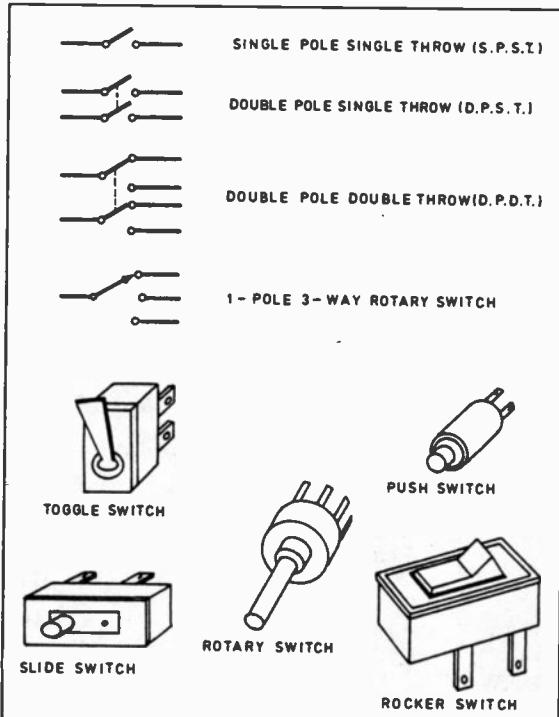


Fig. 1.6. A selection of switch types and styles.

contacts can carry. Exceeding these ratings could be dangerous. This is of particular importance when we examine how to safely switch mains electricity supplies, which is discussed in Part Three of *'Teach In'*.

RESISTANCE AND OHM'S LAW

Take a look at the circuit diagram of Fig. 1.7(a) – it's just like the battery and bulb of earlier experiments but included in series with the bulb is a zig-zag symbol, R1. (Many Examining Boards use an equally acceptable rectangle symbol instead of the traditional zig-zag.) This new component is a Resistor and not surprisingly, its job is to introduce resistance to electric current. If you imagine electric current as water flowing through a hosepipe, introducing a resistor

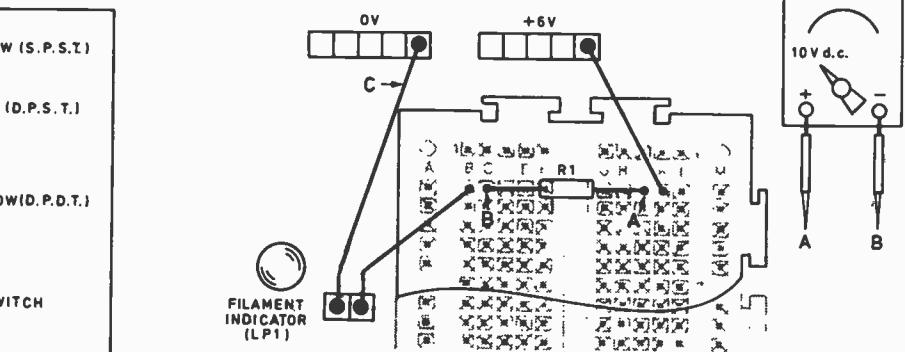


Fig. 1.7(b). Interwiring diagram. The locations "A" and "B" are connected to the positive and negative terminals respectively of your multimeter, set to a suitable voltage range. Repeat for BC and AC

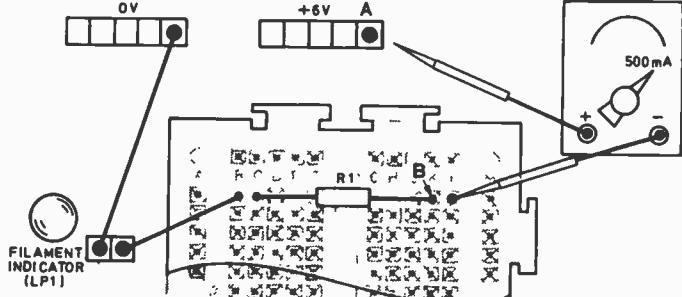


Fig. 1.7(d). Measuring current through the resistor and bulb.

Resistors all look the same, though they have different sizes and can be made of different materials. We measure resistance in ohms. The value of their resistance is shown in a series of coloured stripes printed on the body of the resistor. For now, you need to acquire a 47 ohm resistor. The coloured stripes to look for are yellow/ violet/ black/ gold. Buy a "quarter watt carbon film" type. (We'll explain the jargon later.)

Using the breadboard area of the Mini Lab, construct the circuit as shown in Fig. 1.7(b), connecting the battery pack and indicator bulb using jumper wires. (The bulb will glow when the circuit is completed.) Select the voltmeter function of your multimeter by choosing the "d.c. voltage" range, say 10V full-scale deflection (f.s.d.), which is safe for our circuit where the maximum voltage anywhere will be 6 volts. A

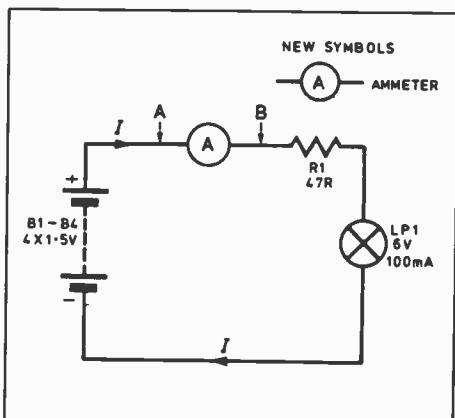


Fig. 1.7(c). Measuring current with an ammeter (Amps range of your multimeter).

of it appears across the resistor. In our own results, a small voltage (0.07V) actually appeared across the meter, which proves that meters aren't perfect, or all the battery voltage would be split between the bulb and resistor.

CURRENT MEASUREMENT

Now we are going to use the multimeter for another function, to measure the current flowing through the circuit. The symbol for an Ammeter is depicted in Fig. 1.7(c). To measure current, we have to break the circuit and insert the meter so that the current in the circuit flows through the meter to produce a reading. This is different to reading a voltage, where we simply take a measurement *between two points in a circuit*. Don't attempt to measure the current "across" the battery, because you will short out the battery pack and probably damage your meter.

Construct the circuit on the Mini Lab as in Fig. 1.7(d). Set your multimeter to "d.c. current" and select a high full scale deflection (f.s.d.) to be on the safe side, say 500mA (0.5 amps), and simply touch the + meter probe to point "A" (battery + terminal), and the - probe to "B" (resistor R1). This will complete the circuit, current will flow through the meter and the bulb will glow. Note the reading on the current range of your multimeter. We took a reading of 62mA. Call this Result 4, and note it here:

OUR READING	TEST RESULTS:
Result 4 62mA (Current flowing through the circuit)	

In this simple circuit, the current flows through the ammeter, resistor and the bulb, and the current will be the same wherever you measure it. Putting the ammeter in the circuit say between the bulb and the battery negative terminal instead, will produce the same result. Try it.

Now short out the resistor with a jumper wire and repeat the experiment. What happens to the bulb? This is in effect exactly the same as the very first circuit we saw in Fig. 1.1(a), because the resistor is now bypassed and no longer has any effect. What is the current reading on your multimeter now? We measured 97mA. Call this Result 5, and note it here:

OUR READING	TEST RESULTS:
Result 5 97mA (Current flowing through the bulb, resistor shorted out)	

OHM'S LAW

The Ohm's Law Equation states that:

$$R = V/I$$

where V is the voltage appearing across the resistor,

I is the current flowing through the resistor and R is the value of the resistance measured in Ohms.

From Fig. 1.7(a) V = Result 1 = 3.15V

From Fig. 1.7(c) I = Result 4 = 62mA (0.062 Amps)

Using our actual measurements and Ohm's Law, the resistance of R1 works out as 50 ohms ($3.15 / 0.062$). Looking at our various test results, we can also state that by adding a resistor into a circuit, two things happen:-

- It reduces the current flowing through the circuit. Compare Result 4 (resistor in circuit) with Result 5 (resistor shorted out with a wire). More resistance causes less current to flow. Current always takes the path of least resistance.
- A voltage appears across the resistor. Not all the voltage of the battery now appears across the bulb. Some of it is wasted by the resistor. We say that the resistor has produced a "voltage drop".

But wait! We reckoned we had put a 47 ohm resistor into our circuit (identified by its colour code), but our calculation using Ohm's Law showed it to be actually 50 ohms! (You might get slightly different results from ours.) Don't worry, here's why:

Manufacturers of resistors have a tolerance to work to. This means that the resistor values might not be exact, but will be within a certain range. The gold band of the colour code tells us that the tolerance is ± 5 per cent, so in fact our 47 ohm resistor could be anywhere between roughly 44 to 50 ohms. Rarely do you need a "tighter" tolerance, though sometimes you might see precision one per cent or two per cent types for critical circuits.

COLOUR CODE

We show separately the RESISTOR COLOUR CODE which enables us to identify the ohmic value of any common resistor. Rather than have an infinite number of different resistances, manufacturers also produce resistors in a range of *preferred values*. The so-called E12 values you will commonly use are:-

10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their multiples of ten. Larger resistor values are abbreviated and simplified by using prefixes to describe their value. We say *kilohm* (or letter "k") to mean thousands of ohms, and *megohms* (letter "M") for millions. The letter is a multiplier abbreviation which is often used in place of the decimal point to indicate the resistance value. You might see the letter "R" used instead of the Omega symbol (or nothing at all) just for ohms. Here are some examples:

$$47R = 47 \text{ ohms.}$$

$$820 = 820 \text{ ohms.}$$

$$1k = 1 \text{ kilohm} = 1,000 \text{ ohms.}$$

$$2k2 = 2.2 \text{ kilohms} = 2,200 \text{ ohms.}$$

$$10k = 10 \text{ kilohms} = 10,000 \text{ ohms.}$$

$$390k = 390 \text{ kilohms} = 390,000 \text{ ohms.}$$

$$1M = 1 \text{ megohm} = 1,000,000 \text{ ohms.}$$

$$4M7 = 4.7 \text{ megohms} = 4,700,000 \text{ ohms.}$$

When current flows through a resistor, the electrical energy is turned into heat. The temperature of the resistor will increase though you might not notice. We say that the resistor is *dissipating power*.

An electric fire element is an example of a large resistor which is deliberately allowed

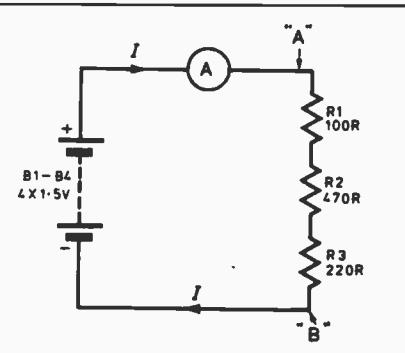


Fig. 1.8(a). Three resistors in series.

to dissipate so much power that it becomes red hot and warms the room. The filament of a light bulb is actually a resistor which dissipates so much power that it becomes white hot. (They are actually much more efficient sources of heat than light!)

The power dissipation, or rate at which the resistor converts electrical energy into heat, is determined by the simple formula:

$$P = I \times V$$

where P = Power dissipation (Watts, symbol "W")

I is the current flowing through the resistor (Amps)

and V is the voltage across the resistor (volts.)

In our earlier experiment of Fig. 1.7(b) the power dissipated by the 47 ohm resistor will be $0.062 \times 3.15 = 0.19$ Watts. The 47R resistor is rated at 0.25 Watts which is satisfactory. Exceeding the power dissipation rating of a resistor may damage it.

Substituting Ohm's Law into the above formula, we obtain two further formulae which can be very useful:

$$P = I \times I \times R = I^2 R$$

Alternatively,

$$P = V / R \times V = V^2 / R$$

Different materials are utilised by manufacturers when making resistors but the most common type you will use will be cheap and cheerful carbon film. Larger resistors can dissipate more power; for instance the electric fire element is actually a large wirewound resistor. Have a look through some supplier's catalogues to see if you can now recognise other types. What values are available? What tolerance (%) do they have? How much power can they dissipate? Lastly, how do they compare for cost?

RESISTORS IN SERIES

Three resistors in series are shown in Fig. 1.8(a), values 100R, 470R and 220R, connected across the 6V battery pack. Obtain suitable 0.25 watt carbon film five per cent resistors and build this circuit on the breadboard of the Mini Lab as per Fig. 1.8(b).

Firstly measure the voltage across the resistor chain at points "A" and "B", using your multimeter set to a d.c. voltage range of 10V f.s.d. Also record the voltages across each resistor. Then break into the circuit and measure the current I with your multimeter set to its "d.c. current" range, say 10mA f.s.d., recording all your readings below. Again, we show you what we obtained when we ran the experiment.

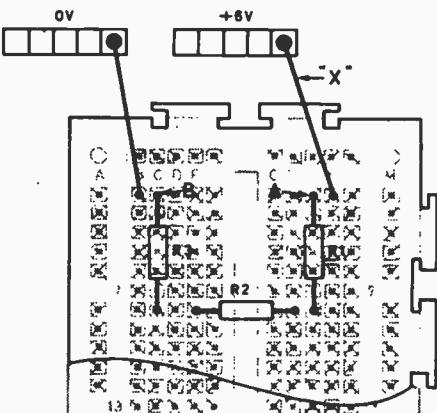


Fig. 1.8(b). Resistors R1 to R3 in series on the breadboard. Measure the current by placing your multimeter (set to 10mA) at the location "X". Then substitute with a jumper wire and measure the voltages as per the text.

OUR READING

Voltage "AB" 6.2V
V across R1 0.8V
V across R2 3.7V
V across R3 1.7V
Current I 7.9mA

TEST RESULTS:

The voltage A-B represents the voltage across the ends of the resistor chain. Of course, it's the same as the voltage across the battery in this example. Using Ohm's Law, we can calculate the actual value in real life of the overall resistance chain:

$$\text{R}_{\text{total}} = \frac{V}{I} \quad \text{YOUR CALCULATION:}$$

$$= 6.2 / 0.0079$$

$$= 784 \text{ ohms.}$$

Don't worry if your results are a little different to ours. Remember that resistors have a tolerance, so results are likely to vary somewhat in practice.

The formula for any number of resistors in series is simply:

$$\text{R}_{\text{total}} = \text{R}_1 + \text{R}_2 + \text{R}_3 \dots \text{etc.}$$

Thus in our circuit of Fig. 1.8(a) we could simply replace all three resistors with a single component of $100 + 470 + 220$ ohms = 790 ohms, if one existed.

Having calculated the overall value of the resistance chain, a practical alternative approach is to measure the resistance with a multimeter set to its Ohms range. Try this:

Disconnect the breadboard from the battery pack. Choose a low resistance range (say 1k f.s.d.), adjust your meter for zero ohms if required, and measure the resistance between points "A" and "B" in Fig. 1.8(b). We noted an overall resistance of 780 ohms using our digital multimeter, which compares favourably with the value of 784 ohms we calculated using Ohm's Law. Your own multimeter reading should be almost exactly the same as the value you calculated yourself with Ohm's Law.

In actual fact, if each resistor in the chain has a tolerance of five per cent, then the tolerance on the *overall* value of the resistors in series will also be five per cent. So our own actual reading of 784 ohms falls within the expected resistance range for the resistors in series, namely 750 to 829 ohms (790 ohms $\pm 5\%$).

The other aspect to note is that by connecting several resistors in series, the potential difference applied across the chain (voltage AB) is split up across the resistors. Total up the voltages across R1, R2 and R3 and compare against the p.d. across the chain: they should be the same. We promise we didn't fix our results!

RESISTORS IN PARALLEL

Two resistors, both connected to our 6V battery pack are shown in Fig. 1.9(a). We also show a current I which is flowing into the resistor network. At the junction where R1 and R2 are joined, I divides into two currents Ia and Ib, which themselves are determined by the values of the associated resistors.

Assemble the two resistors onto the Mini Lab breadboard using 0.25W types, and measure the three currents with your multimeter. Set it to a "d.c. current" range of about 100mA, and break into the circuit at locations A, B and C in succession, as shown in Fig. 1.9(b). Simply unhook one end of the resistor and link it back into circuit via the test leads of your ammeter, to measure the current flowing through the component.

Then fill in the results in the table below, and compare against our results.

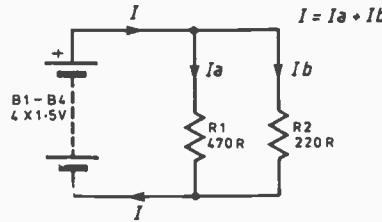


Fig. 1.9(a). Two resistors R1 and R2 in parallel across the 6V battery pack.

OUR READING

A: Current I 42mA
B: Current Ia 13mA
C: Current Ib 29mA

TEST RESULTS:

Clearly what happens is that current I splits into two components Ia and Ib. This leads us to Kirchhoff's First Law (or Current Law) which states that the amount of current flowing into the junction of the resistors is the same as the sum of the currents flowing out of it – because 42mA flows into the junction which divides into two currents coming out of 13mA and 29mA. The same is true if you have three or more currents coming out of a junction: they all add up to the value of the single current going in.

In Fig. 1.9 the two resistors are said to be connected in parallel. The formula for calculating the overall resistance of two resistors in parallel connection is:

$$\text{R}_{\text{total}} = \frac{\text{R}_1 \times \text{R}_2}{\text{R}_1 + \text{R}_2}$$

An alternative formula yielding the same result is:

$$\frac{1}{\text{R}_{\text{total}}} = \frac{1}{\text{R}_1} + \frac{1}{\text{R}_2} + \dots + \frac{1}{\text{R}_n} \text{ etc.}$$

(Take the reciprocal of R_{total} to reveal the answer.)

Our 470R and 100R resistors could thus be replaced by a single resistor of 150R. It's useful to remember that by placing two resistors in parallel, the overall resistance will always be smaller than either of the two individual resistors. It's impossible to make a resistance larger by placing another resistor in parallel with it.

Additionally, when you have two or more resistors in parallel with each other, the potential difference or "voltage drop" across each of the resistors is bound to be the same. In our example, the p.d. across both resistors happens to be that of the battery voltage.

POTENTIAL DIVIDERS

Earlier we saw how a potential difference placed across a chain of resistors in series, is divided up amongst those resistors. A p.d. appears across each resistor and when added together, they equal the p.d. across the extreme ends of the resistor chain.

A simple network consisting of two resistors is shown in Fig. 1.10. V_{in} is the voltage from the 6V battery pack and V_{out} is the output voltage from the potential divider.

Three different sets of values are shown in the table for R_a and R_b : construct this simple network on your breadboard using 1k, 2k2 and 4k7 0.25W five per cent carbon film resistors, then measure the voltage V_{out} – the p.d. across R_b – with your multimeter and record this in the table. Our results are shown too. If you are uncertain of the resistors' colour codes, double-check their values using your multimeter set to an ohms range.

This type of circuit is called a potential divider and is very useful in electronics for reducing the level of an input or output voltage. The output voltage from the divider depends on the ratio of the values of the two

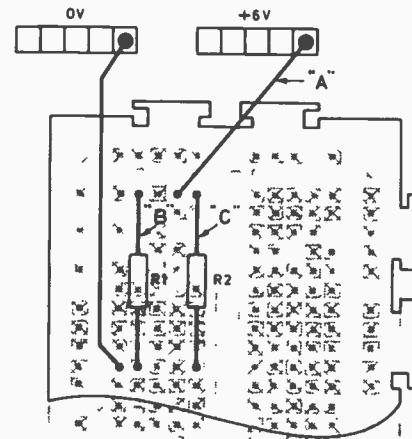


Fig. 1.9(b). Measure the currents using your multimeter at locations "A", "B" and "C".

resistors. In fact it's possible to calculate the output from a simple formula:

$$\text{V}_{\text{out}} = \text{V}_{\text{in}} \times \frac{\text{R}_b}{\text{R}_a + \text{R}_b}$$

Now try calculating the values of V_{out} and compare it against your actual test readings just recorded.

Our formula assumes that there is no current (I_o) drawn by anything connected to the output. By adding a "load" as shown in Fig. 1.11, in effect you reduce the resistance of the bottom half of the potential divider, by adding R_l in parallel with R_b . This has the effect of lowering the output voltage of the divider as it is "pulled down" towards 0V.

There comes a point when the potential divider formula may give misleading results, because it does not take into account the "shunting effect" – if any – which a load connected to the divider may have on R_b . How much effect the load has depends on its resistance – a lower resistance will pull down the output even more. We'll see in future parts of Teach In, how the load could be something more complex than a resistor.

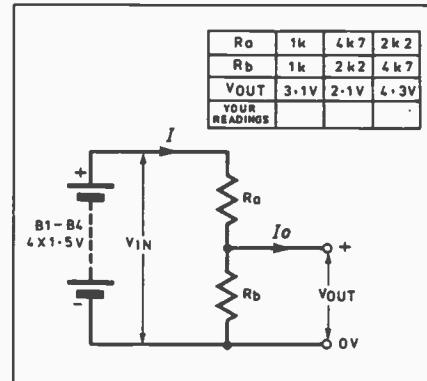


Fig. 1.10. The Potential Divider. Build this on the Veroblock yourself, and measure V_{out} (the voltage across R_b) – fill in your results in the table.

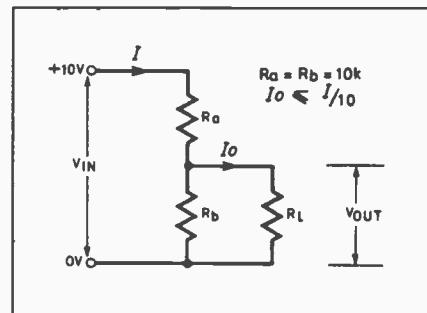


Fig. 1.11. The Ten Per Cent Rule. The output current should be no more than 1/10th the current I flowing into the divider.

GCSE QUESTION

MIDLAND EXAMINING GROUP
General Certificate of Secondary Education
ELECTRONICS

1751/1

PAPER 1

(reproduced with their permission)

2

Fig. 1 shows a buzzer in series with a pair of resistors.

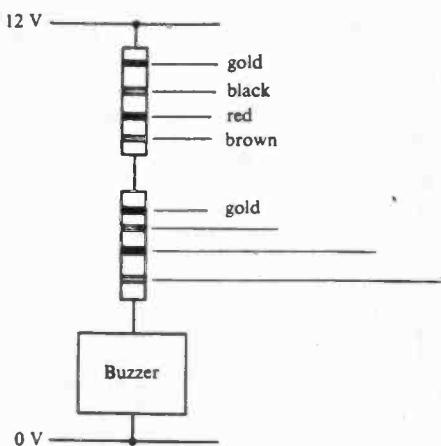


Fig. 1

- (a) The coloured bands on one of the resistors are labelled. Use the colour code to find the resistance of that resistor. [2]

Ω

- (b) The buzzer is rated at 6 V. When connected to a 12 V supply, it must have a resistance of $60\ \Omega$ in series. What is the value of the unlabelled resistor of Fig. 1? [1]

Ω

- (c) Select a suitable value for the unlabelled resistor from this table of preferred values. Draw a circle round your choice. [1]

10	11	12	13	15
16	18	20	22	24
27	30	33	36	39
43	47	51	56	62
68	75	82	91	100

- (d) Write in the colours of the bands on the unlabelled resistor. [3]

- (e) Draw on Fig. 1 a voltmeter which measures the potential difference across the buzzer. [2]

MEG 704

like the input of an amplifier section, where a.c. signals may be involved.

THE TEN PER CENT RULE

It's best to ensure that the output current from the divider is no more than 10 per cent of the current flowing through the divider itself, so that you don't unduly load the divider. Firstly work out the current I flowing through both R_a and R_b with no load attached. This is calculated very simply with Ohm's Law: $I = V_{in} / (R_a + R_b)$.

We know that the current I into the div-

ider will equal the current through the two resistors plus the output current, refer to Fig. 1.11. Ignoring the load current I_o , and with the values for R_a and R_b set at 10k for example, utilising a 10V supply the current through the divider is 0.0005 amps or 0.5mA.

The output current should be no more than 10 per cent of this, i.e. 50 microamps. This means that the load resistor should preferably be the equivalent of 100k or more, i.e. 5 volts ($= V_o$) / 50 microamps.

The circuit of Fig. 1.12 shows a 4k7 resistor and a normally-open push switch connected between the 6V and 0V rails of the

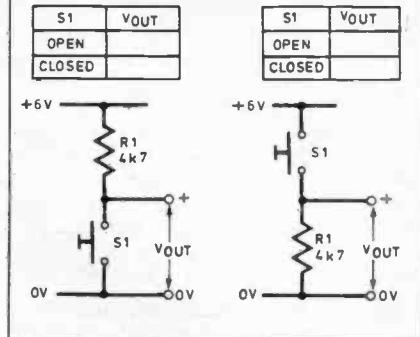


Fig. 1.12 (left). Switching System with Pull Up Resistor. Build this on the Mini Lab and record your voltage measurements in the table.

Fig. 1.13 (right). Switching System with Pull Down Resistor.

battery pack. Build this circuit on the Mini Lab yourself, and measure the d.c. voltage output using the multimeter, recording the result both when the switch is open and closed.

Resistor R1 serves as a *pull up* resistor because it "biases" the output towards the +6V rail when the switch is open. Pressing the switch shunts the output to 0V. This is one way of obtaining a signal which is normally at 6V (or whatever the supply rail happens to be) and which is sent to 0V as a result of an operation.

A similar circuit is shown in Fig. 1.13 but this time a *pull-down* resistor R1 biases the output to 0V. Thus the output will be at zero potential when the switch is open, but a "high" signal of +6V is generated when the switch is closed. Prove it by building it on your Mini Lab.

These simple "input systems" enable us to obtain a suitable electrical signal – normally high or normally low, whichever we need – as a result of performing a mechanical operation. Both these functions are of great importance when we come to look at the world of *digital systems*. These only have two states – on and off, or high and low. It's even more relevant when we introduce the Micro Lab, an optional microprocessor expansion unit for the Mini Lab, later on.

VARIABLE RESISTORS

The simple switching systems just introduced enable one of two states – "high" or "low" – to be obtained from simply pushing a button. There will be many times when you will want to *vary* a voltage. A very common method of doing this is based on a variable potential divider. Fig. 1.14(a) introduces the potentiometer (pronounced "po-ten-she-oh-meter") which is a three terminal variable resistor. It has a moving contact B which forms a *wiper* on a resistance material.

By connecting the potentiometer as a voltage divider to an input voltage V_{in} , it's easy to change the output voltage V_o by rotating the shaft of the potentiometer. The varying voltage output is available at the wiper of the pot. Thus by performing a mechanical operation (rotating the spindle), an electrical function is carried out.

A very common application of this arrangement is a *volume control* of a radio or a hi-fi. Sometimes you need to adjust a voltage just once, in order to set up a signal, perhaps on a television circuit board. Small "trimmer resistors" or "preset potentiometers" are available, and these are generally fitted to a circuit board so that they

GCSE QUESTION (see previous page)

The Teach In Reader would have no problems with this straightforward question which concerned resistors in series. The following answer would have earned you full marks.

- Simply use the resistor colour code. The brown and red bands mean that the numerals of the code are 12. The black band means that the multiplier is 1R ($x 1$). **Answer 12 ohms (12R).**
- Use the formula for resistors in series. We are told that the total resistance in series with the buzzer must be 60 ohms. We have shown one of the resistors to be 12 ohms – the unlabelled component must therefore be 48 ohms
- The nearest preferred values to 48 ohms in the table are 47 or 51 ohms. Either was marked as correct.
- Resistor Colour Code again. 47R is yellow/violet/black. 51R is green/brown/black.
- The voltmeter is drawn in parallel with the buzzer. Voltmeters measure the voltages (p.d.) across components, i.e. between two points in a circuit.

N.B. No extra marks would have been awarded by mentioning the resistor tolerance. Also, the Resistor Colour Code was shown on the Exam Paper for reference.

to enable the switch contacts to join together. The contacts themselves may be capable of switching very heavy currents, in the order of several amps or more. Fig. 1.15(a) is a demonstration circuit of a relay RLA, the coil of which is activated by pressing S1. The relay actually has changeover contacts (RLA1) so that a load can either be switched on or off when the coil operates. Here, a bulb LP1 is connected as the load. The whole circuit is powered by the 6V battery pack.

Build this on your Mini Lab as shown in Fig. 1.15(b). When you press S1, you will hear the relay click and the bulb will illuminate. Now add the audible warning device (correctly polarised) between the n.c. terminal (buzzer +) of RLA and OV (buzzer -). What happens now when you press the switch?

The relay used on the Mini Lab has the

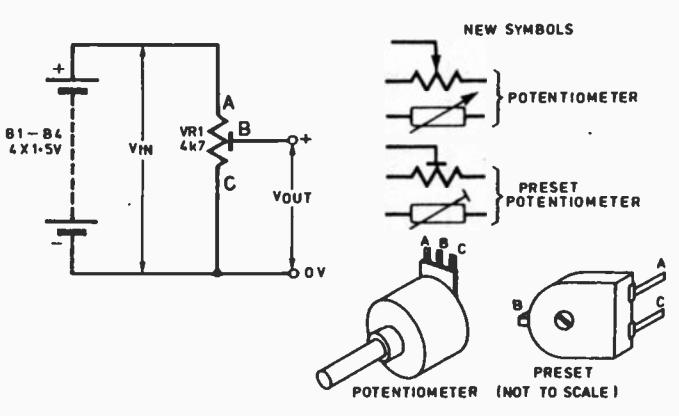


Fig. 1.14(a). A preset variable resistor. Physical forms are also shown.

Fig. 1.14(b) (below). Connecting one of the preset potentiometers mounted on your Mini Lab. Measure the voltage between "B" and 0V, when you rotate the control.

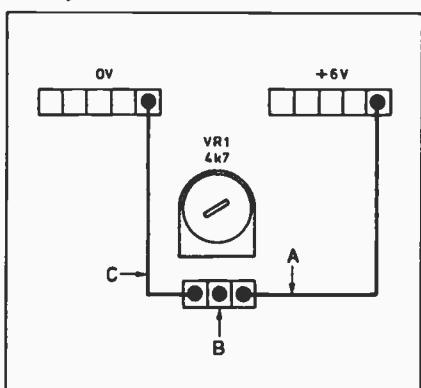


Fig. 1.15(a) (above right). The Relay, used here to switch between a bulb and the buzzer. Add the buzzer (WD1) after building and testing the rest of the circuit.

Fig. 1.15(b) (right). Operating the buzzer and bulb with the changeover contacts of the relay. Connect WD1 the right way round.

can be adjusted with a screwdriver. The symbol for a preset (or trimmer) is also shown in Fig. 1.14.

Potentiometers and trimmers are specified by the ohmic value of their tracks. Anything between 100R to 1M is common. Additionally, the power dissipation of the track, in watts, is also generally given. Small presets might only be 0.15 watts, but large "wirewound" potentiometers could dissipate up to 25 watts of power. Look through a catalogue to check out some other variable resistors, comparing specifications and prices.

The Mini Lab incorporates a selection of preset resistors which can be used as volume or level controls in future experiments. Fig. 1.14(b) shows how to try out a 4k7 preset mounted on the Mini Lab, by connecting it to the 6V battery pack. Measure the voltage between "B" (positive)



and "C" (0V) with your multimeter set to a d.c. voltage range. See what effect rotating the control has on the meter reading.

RELAYS

The simple switching systems we have looked at so far are limited by the current they can carry and the voltage they can switch. The smallest switches available can only carry a few tens of millamps and switch up to 20V d.c. or so. In some applications, this could be far too restricting when we want to switch a heavy load such as a motor.

A relay is an output device in which a small current can be used to control a much larger current. They take advantage of the electromagnetic effect where a potential applied to a small coil turns it into an electromagnet. This magnetically operates some contacts to form a switch.

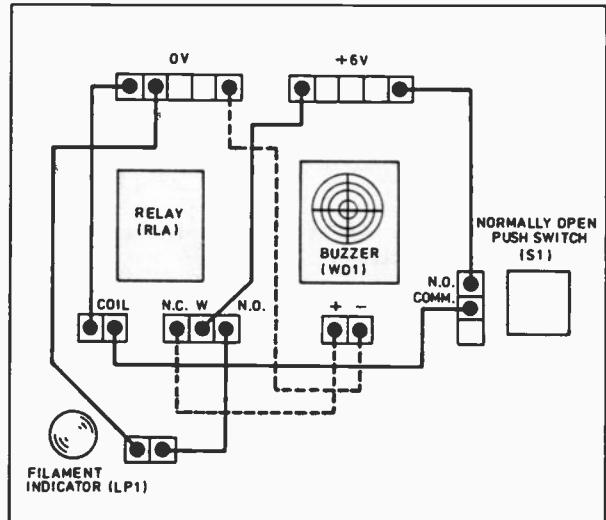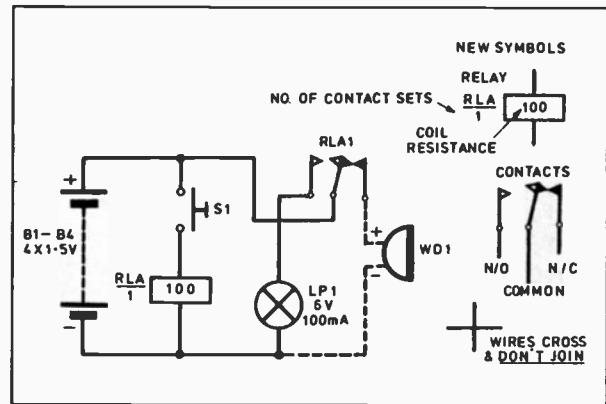Only a small current is needed in the coil



following specification:

Coil Resistance: 100 ohms

Coil Voltage: 6 volts

Contact Current: 3 amps maximum

Contact Voltage: 24V d.c./120V a.c. maximum

Contact Configuration: single pole changeover

What will be the current flowing through the coil when 6 volts is applied? (Use Ohm's Law ($I = V / R$) and compare your answer (60mA) against the much higher contact current which the relay can safely switch.

We need to take certain precautions when using relays in transistorised circuits. Next month we see how relay coils can generate some unbelievably high voltages when they are switched off. This can ruin certain electronic components unless precautionary measures are taken. We also introduce more electronic devices.

Scanning Receivers

MVT 7000

- 100kHz to 1300MHz, continuous coverage
- 200 programmable channels
- Search and scan facilities
- AM, FM and WBFM modes
- 10 programmable bands
- Excellent sensitivity
- LC display with signal strength meter
- Supplied with ni-cad batteries, mains charger/adaptor, telescopic aerial, carry strap, belt clip, 12Vdc lead and manual.

£289.00
40-17000



HP2000

- Continuous tuning from 500kHz to 1300MHz
- 1000 programmable channels
- Search and scan facilities
- AM, FM and WBFM modes
- 10 programmable bands
- Supplied with telescopic, UHF and VHF antennae, ni-cad batteries, carrying case, dc cable, mains charger/adaptor and manual.

£269.00
40-31001



VT225

- Civil and military airband receiver
- Covers 108 to 391MHz in 3 bands
- AM and FM modes
- 100 programmable channels
- Scan and search facilities
- LC display with signal meter
- Supplied with ni-cad batteries, mains charger/power supply, rubber duck antenna, carry strap, belt clip, 12Vdc lead and manual.

£229.00
40-00225



VT125UK

- VHF, AM Airband receiver
- Covers 108 to 142MHz
- 30 programmable channels
- LC display with signal meter
- Supplied with ni-cad batteries, mains charger/power supply, rubber duck antenna, carry strap, 12Vdc lead and manual

£149.00
40-00125



Full details of all the above are included in our comprehensive catalogue, £1.70 (plus 30p p&p)

All the above are currently in stock and available for immediate delivery. Standard p&p £1.40, next day delivery £4.60.

Cirkit

All prices include VAT (at 17.5%)



CIRKIT DISTRIBUTION LTD

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ
Telephone (0992) 444111 · Fax (0992) 464457




AUTONA LTD
UK's leading module manufacturer since 1972

★AUDIO MODULES★

AL 12580-125W AMPLIFIER

A rugged high powered module that is ideal for use in discos & P.A. Systems where powers of up to 125W, 4 ohms are required. The heavy duty output transistors ensure stable and reliable performance. It is currently supplied to a large number of equipment manufacturers where reliability and performance are the main considerations, whilst for others its low price is the major factor. Operating from a supply voltage of 40-80V into loads from 4-16 ohms.

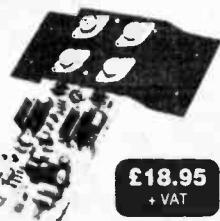

£18.95
+ VAT

AL 2550-COMPACT LOW-COST 25W AMPLIFIER

One of our most popular audio modules with tens of thousands installed. Ideal for domestic applications where low distortion and compact size are the prime requirements. Used with supply raids of 20V-50V into loads of 8-16 ohms.



£6.55
+ VAT

MM 100-BUDGET 3-INPUT MIXER

With a host of features including 3 individual level controls, a master volume and separate bass and treble control, it provides for inputs for microphone, magnetic pick-up and tape, or second pick-up (selectable), and yet costs considerably less than competitive units. This module is ideal for discos and public address units and operates from 45V-70V.

£17.49
+ VAT



£17.49
+ VAT

MM 100G GUITAR MIXER

As MM100 with two guitar + 1 microphone input intended for guitar amplifier applications.

COMPLETE AUDIO RANGE FROM 10W-125W
SEND FOR DETAILS TODAY

SECURITY EQUIPMENT

MINIATURE PASSIVE INFRA-RED SENSOR-RP33

Switchable Dual range, detects intruders up to 6 or 12 metres. This advanced sensor operates by detecting the body heat of an intruder moving within the detection field. Slow ambient changes such as radiators, etc. are ignored. Easily installed in a room or hallway. Providing reliable operation from a 12V supply, it is ideal for use with the CA 1382 or equivalent high quality control unit. Supplied with full instructions. Size 80x60x40mm



£17.95
VAT



£14.93
+ VAT

EASILY INSTALLED



£44.95
+ VAT

ADVANCED CONTROL UNIT-CA 1382

Automatic Loop Test On Switch On ★ Automatic Siren Re-Set ★ Audible Entry/Exit Warning Buzzer ★ Two Separate Loop Inputs + 24-hr Circuits ★ Easily Installed. Full Instructions Supplied.

This advanced control panel provides effective and reliable control for all security installations, yet its operation is sheer simplicity for all members of the family, and is supplied with two keys. Housed in a steel case with an attractive moulded front panel, it compares with units costing twice the price.



This tried and tested control unit provides the finest value for money in control systems, with many thousands protecting houses all over the country. A suitable steel enclosure is available separately.

LOW COST CONTROL UNIT-CA 1250

The IR1470 consists of a separate transmitter and receiver providing a beam of up to 50ft which, when interrupted, operates a relay in the receiver which in turn may be used to control external equipment. The system requires only 65mA from a 12V supply. Size: (each unit) 82 x 52 x 57mm

£25.61
+ VAT

PLUS FULL RANGE OF SECURITY ACCESSORIES FOR
COMPLETE HOME PROTECTION
TELEPHONE FOR FREE LITERATURE TODAY


**DEPT EE 11
51 POPPY ROAD
PRINCES RISBOROUGH
BUCKS HP17 9DB
TEL: (084 44) 6326
FAX: (084 44) 7102**

Order by Credit Card for
immediate despatch



Add VAT. Carriage only £1.50
Export 10% minimum £1.50

MINI LAB

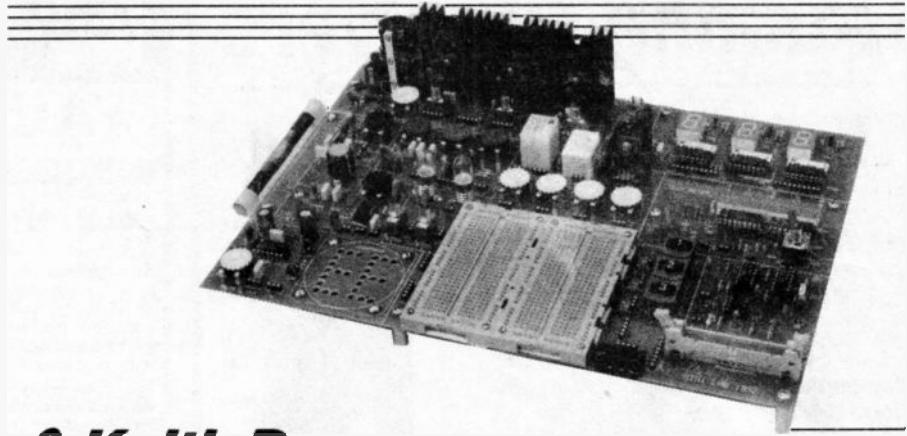

Alan Winstanley & Keith Dye B.Eng(Tech)AMIEE

The Everyday with Practical Electronics Mini Lab has been created to accompany Teach In '93, and enables the reader to assemble demonstration circuits by following the clear instructions and diagrams contained in the main text, with every chance of it working first time. The Mini Lab is an exciting learning aid which brings electronics to life in an enjoyable and interesting way: you will both see, and hear, the electron in action.

A SPECIALLY-DESIGNED printed circuit board (p.c.b.) forms the heart of the Mini Lab which includes a "breadboard" area or plug-in contact block with which basic circuits can be tested. One Veroblock breadboard is required initially and the Mini Lab has room for another.

Ancillary components such as presets, switches and buzzers etc. which cannot be plugged directly into the breadboard are also permanently fitted to the Mini Lab board, and are easily connected to the Veroblock through breadboard-type sockets which are conveniently located nearby.

All the areas are interconnected to a common power supply and the Mini Lab becomes mains-operated in due course. However, only low voltages are ever present on the Mini Lab, so the unit is completely safe to use at all times. A microprocessor expansion port facilitates connection to our Micro Lab microprocessor add-on system which is introduced later in the series for GCE A Level.

When the Mini Lab is finished, you will possess an excellent self-contained development unit complete with a range of test and demonstration items which will help you to widen your knowledge and produce your own designs. We hope that you will enjoy building and using your Mini Lab, and find it of continued use when *Teach In '93* draws to a close. Thereafter, we hope to follow up with occasional articles which will utilise the Mini and Micro Labs in some interesting applications.

Should you have any particular queries or problems, please write to us c/o The Editor - we'll be only too glad to help. We also welcome any comments and constructive criticism from both teachers and students alike, so do get in touch with a progress report: we'll be delighted to hear from you!

Alan Winstanley and Keith Dye.

The printed circuit board designs of the Mini and Micro Labs are © Copyright Dytronics 1992.

FIRST STEPS IN CONSTRUCTION

The *Teach In* Mini Lab is constructed on a p.c.b. measuring approximately 295mm x 210mm (the size of a page of EPE) and is divided into distinct sections. Every month *Teach In* discusses a particular topic and accompanying the text will be a brief constructional article describing a relevant circuit which fills one of the sections on the Mini Lab board. There is, however, the requirement to solder a number of components to the board each month, so a little practice with a soldering iron will be useful. Space precludes us from exploring the circuits in any depth: the main thing is to build them!

For Part One of *Teach In*, it is necessary to assemble the "general-purpose" central area of the Mini Lab which contains the plug-in breadboard and other components. The breadboard readily copes with most of the electronic components used in *Teach In*, but cannot directly handle certain parts like switches, bulbs or preset potentiometers. These components are instead soldered directly to the Mini Lab p.c.b., then

the components' terminals connect via the p.c.b. to adjacent groups of contact strips which form breadboard-style connection points for these parts.


It therefore becomes very easy to connect switches, pots etc. to the breadboard with standard solid core 0.28mm² insulated wire, see Fig. 1. Simply cut some wire to length, strip about 5mm of insulation from each end and push the jumper wire into the relevant sockets on the Mini Lab and connect over to the Veroblock. You might often find it easier to use a pair of fine-nose pliers to grip and locate the wires into the sockets. The system works perfectly but it's im-

tant that you use both the correct socket strips and also the right gauge of wire so that a reliable connection can be made each time.

COMPONENTS

The Components List gives all those parts which you can solder to the Mini Lab board for Part One. It does not list the extra parts required to fill the other sections of the board: these will be gradually introduced as required in each month's article which makes the Mini Lab extremely cost-effective. Also, rest assured that we have chosen the most economical components wherever

Fig. 1. Using a jumper wire to connect a s.i.l. socket on the Mini Lab printed circuit board.

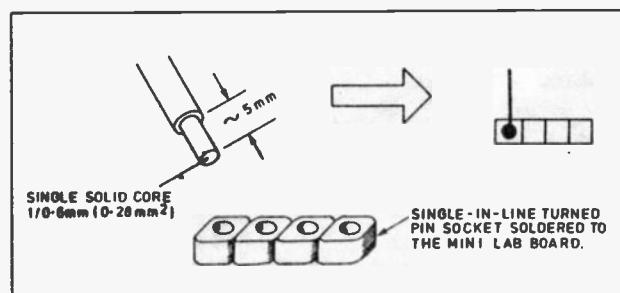

Mini Lab Components

Variable Resistors

VR1 4k7
VR2 47k
VR3 100k
VR4 2M2

See
**SHOP
TALK**
Page

Switches

S1 to S3 S.P.D.T. sub-miniature toggle switch (3 off)
S4 to S6 2-pole n/o + 2 pole n/c mom. action push switch, p.c.b. mounted with bezel and button (3 off)

Miscellaneous

WD1 6V p.c.b. mounted audio warning device
RLA 6V 100ohm s.p.c.o. p.c.b. mounting relay
LP1, LP2 6V 100mA M.E.S. bulbs with skeleton holders (2 off)


Mini Lab Printed Circuit Board 295mm x 210mm approx. (available from the EPE PCB Service - order code MINI LAB); p.c.b. mounting "jacks" (3 off); 0.5 inch shorting selector plug; single-in-line turned-pin sockets, 2 x 32-way, "pluggable" p.c.b. mounting screw terminals, 1 each 2-way, 4-way, Veroblock breadboard; M2.5 x 12.5mm screws and nuts to mount breadboard (4 off); 20mm p.c.b. stand-offs with screws (8 off); wire - single core insulated 1/0.6mm (0.28mm²) as required.

A detailed Buyers Guide is given in Shop Talk which shows all part numbers, alternative sources and additional information.

Price


£38

Approx

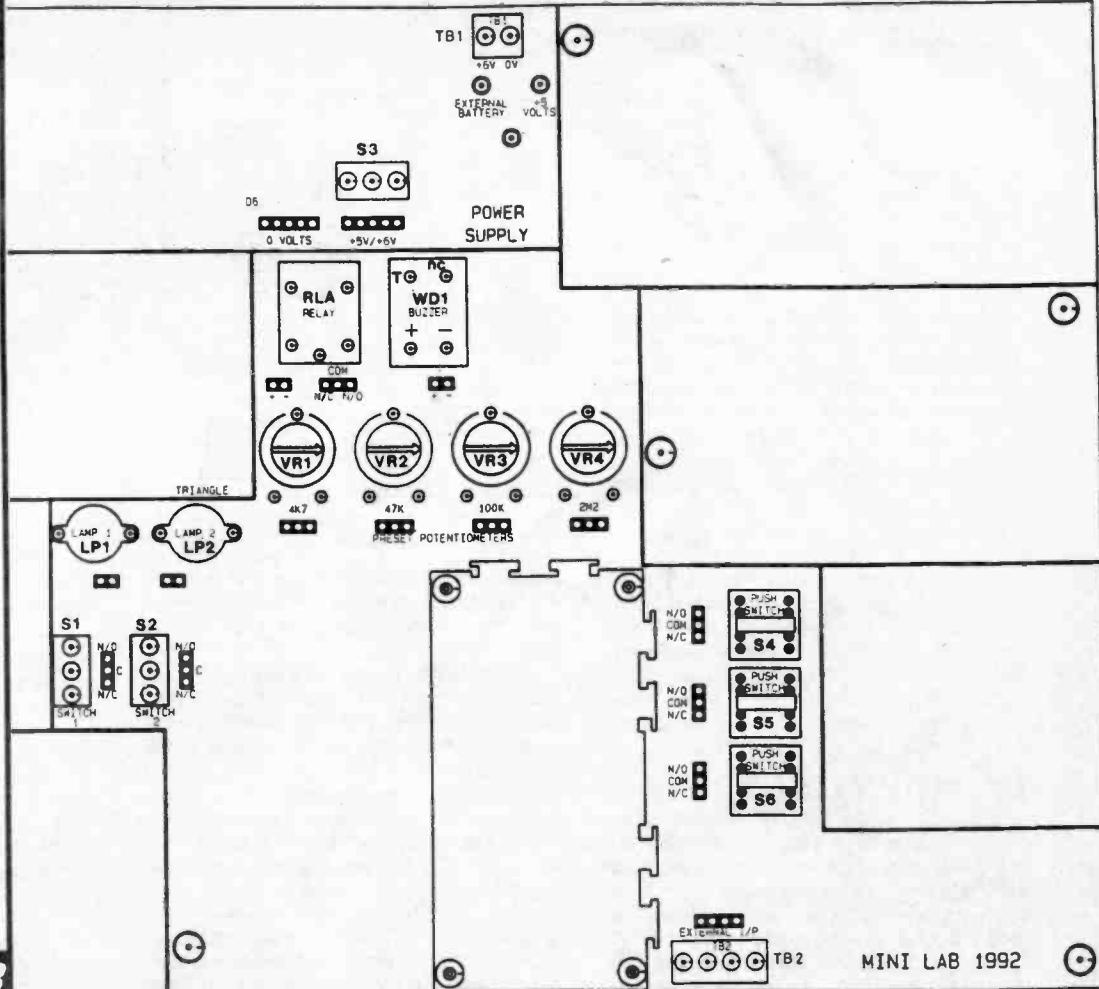

MINI LAB 1992

Fig. 2. Construction of the central part of the Mini Lab as required for Part 1 of Teach-In. The photograph below shows the complete Mini Lab.

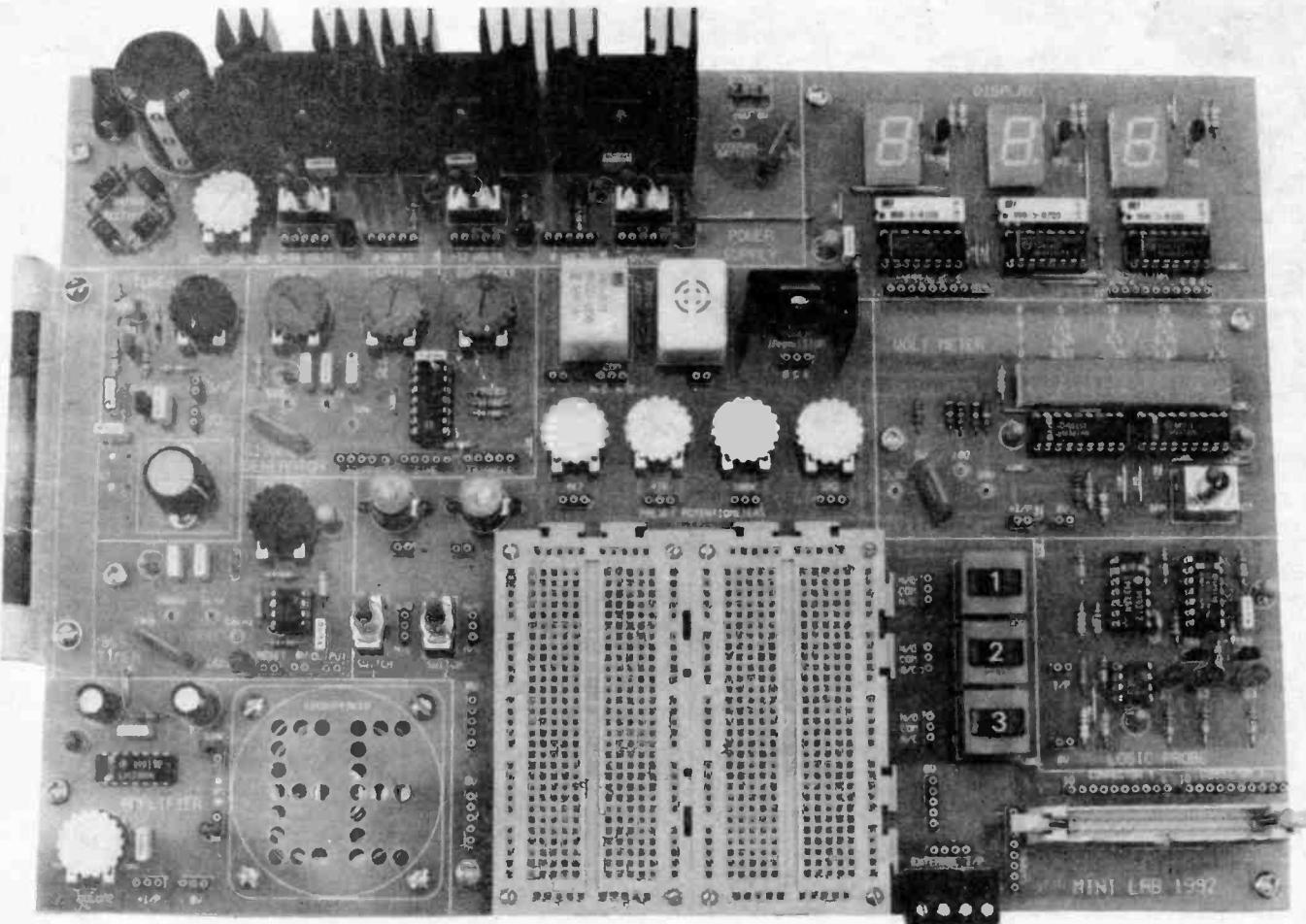

possible. We also give a list of other requirements for tools, etc. which the newcomer might find useful.

The top side of the Mini Lab p.c.b. is fully silk screen printed with the descriptions and locations of the various components, and you should find the initial assembly very straightforward. Fig. 2 shows the arrangement of the central part of the Mini Lab which can now be constructed.

BATTERY PACK

Also assemble the battery pack (B1 to B4); use four 1.5V cells such as R20S types and connect them the right way round into a suitable holder to make 6 volts. It is connected to the Mini Lab through screw terminals on the printed circuit board, see Fig. 3. We recommend "pluggable" terminals, so that the relatively bulky battery can be conveniently unhitched when desired, without straining the printed circuit board.

The battery must be selected for use by inserting a shorting plug (see Parts List) between two small sockets marked "EXT BATT", and also a d.c. on-off switch is fitted, so that you can readily disconnect the battery. Later, this switch serves a different purpose: it turns a 5V supply on and off for digital circuits, once the battery has been replaced with a very comprehensive Mains Power Supply.

I.C. MOUNTING

The s.i.l. ("single in line") socket strips are designed to carry integrated circuits and mainly come in lengths of 32 terminals, and these are snapped off as required to form small groups which can then be soldered to the p.c.b., perhaps using sticky tape to hold them down while you solder the pins. Because they are central to the whole design, we again emphasise that only "turned pin" s.i.l. sockets should be used: other types will not work in this application. Invariably, some terminals will break, so allow for a little wastage.

Many parts have to be pin-compatible with the hole layout in the p.c.b. or they will not fit, so consider the Components List and Shop Talk carefully. The recommended parts should solder directly to the board without any problems. A 4-way screw ter-

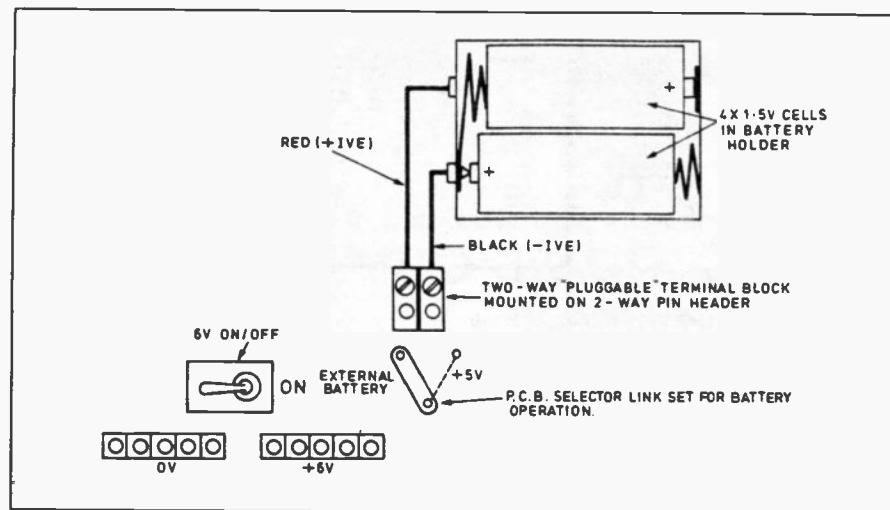


Fig. 3. Connection arrangement for external battery pack. The connection link for selecting "External Battery" is shown.

minal is fitted at the bottom of the board so that later on, components with long wire leads can be made to connect to the Mini Lab.

The bulbholders can be mounted by soldering their tags to a couple of solder pins fitted to the board. The push switches must be the approved type or they will not fit the board: those used on the prototypes used a bezel with engraved buttons marked 1 to 3 as a nice touch. They are, incidentally, the only p.c.b. switches we know of which have an acceptable current rating for our purposes.

Finally, to finish off, the board requires quite a number of 20mm stand-off pillars as shown so that the board can stand on a desk or table top. They stop the whole p.c.b. from flexing unduly when engaged in frenzied experiments!

To avoid confusion, it's important to note that the component designations (VR1, VR2, S1 etc.) shown both in the Components List and Fig. 2 are only used here for the purpose of helping you to assemble this part of the Mini Lab. In the main tutorial of Teach In, you will find that the components are given different designations in various circuit and interwiring diagrams.

TOOLS

The following is a list of basic requirements for tools and equipment, and is given as guidance to those approaching the subject for the first time:

Fine-pointed long nose pliers with serrated jaws.

Wire stripper, variable gauge, with built-in wire cutter.

Round-jaw pliers (luxury, useful for bending leads neatly).

Screwdrivers, small flat-bladed and cross-head No. 0 and No. 1 types.

Soldering iron, 15 Watt mains operated pencil type with fine tip, preferably with bench stand.

Soldering Iron Tip Cleaner and Tinner (Multicore TCC1).

Solder 60/40 22 s.w.g.

Suction Desoldering Tool (luxury but useful to have).

Small Freezer aerosol (handy)

Multimeter, 20,000 ohms per volt or higher: reading 250V d.c./500mA d.c. minimum plus resistance range. Or Digital Pocket Multimeter, same readings or better. A modest multimeter will be quite adequate for following Teach-In

Next month: L.E.D. Voltmeter Module.

EVERYDAY WITH PRACTICAL ELECTRONICS

SUBSCRIPTION ORDER FORM

Annual subscription rates (1992/3): UK £20.00.
Overseas £26 (surface mail) £43.50 (airmail)

To: Everyday with Practical Electronics,
6 Church Street, Wimborne, Dorset BH21 1JH

Name.....

Address.....

Post code.....



I enclose payment of £ (cheque/PO
in £ sterling only, payable to Everyday with
Practical Electronics)

Access or Visa No.

Signature.....

Card Ex. Date

Please supply name and address of card-holder if different
from the subscription address shown below. Subscriptions
can only start with the next available issue. For back
numbers see the Editorial page.

MAILTECH

ELECTRONIC COMPONENTS

MAINS TRANSFORMER Pri. 120V-0V, 120V-0V.

Sec. 0V-12V, 0V-12V, at 3VA £2.62 each

PROJECT BOXES A range of high quality boxes moulded in black high impact ABS, easily drilled or punched to produce a professional looking end product

TYPE	W	L	H	PRICE
T2	75	56	25	£0.77
T4	111	57	22	£0.92
MB1	79	61	40	£1.35
MB2	100	76	41	£1.47
MB3	118	98	45	£1.71
MB4	216	130	85	£5.19
MB5	150	100	60	£2.35
MB6	220	150	64	£3.95
MB7	177	120	83	£3.42
MB8	150	80	50	£2.22

All sizes are in millimetres

SPECIAL OFFER - PROJECT BOX

As above boxes 50 x 70 x 25mm
60p each 10 for £5.00

KEY SWITCH

3 Position keyswitch
£2.35

MICRO SWITCH roller arm operation spdt 40p each
MINIATURE TOGGLE SWITCHES

spdt	60p each	spdt 3 position c/off	70p each
dpdt	70p each	dpdt 3 position c/off	80p each
spdt biased	60p each	spdt 3 position c/off biased both ways	70p each
		dpdt 3 position c/off biased one way	80p each

MINIATURE TOGGLE SWITCH pcb mounting 3pdt 50p each 10 for £4.00
MINIATURE PUSH TO MAKE SWITCH 50p each

DIL RELAYS 5 volt dp/changeover 60p 10 for £5.00
12 volt dp/changeover 80p 10 for £6.00

RELAY 10 amp contacts sp/changeover 12 volt coil £1.20 each

CAR HORN RELAY in metal can with fixing lug, s/pole on

10 amp contacts £1.00 each 6 for £5.00

20 AMP RELAY dp on 12 volt coil £1.50 each 4 for £5.00

REED RELAY 12 volt 50p each 10 for £4.00

240 VOLT AC RELAY 3-pole c/o 10 amp contacts £1.50 each 4 for £5.00

12 VOLT DC RELAY BOARD A useful PCB (196mm x 71mm) with 3 x s/pole c/o relays and 1 x d/pole c/o relay. Connections to relay contacts and coils are brought out to pcb mounting terminal blocks £1.00 each 6 for £5.00

DIL SKTS

8 pin	10 for	£0.60	plug	socket	cover
14 pin	10 for	£0.90	9 pin	30p	35p
16 pin	10 for	£1.00	15 pin	40p	35p
18 pin	10 for	£1.00	25 pin	50p	40p
20 pin	8 for	£1.00			
24 pin	8 for	£1.00			
28 pin	6 for	£1.00			
40 pin	5 for	£1.00			

ALL COMPONENTS FULL SPECIFICATION DEVICES

SEMICONDUCTORS - TRANSISTORS - ICS - DIODES - REGULATORS - ETC					
2N3702 10p ea 12 for £1.00 VOLTAGE REGS					
BC337 10p ea 12 for £1.00 7812/7805/7912/7905					
2N3904 10p ea 12 for £1.00 all 35p each, any 4 for £1.20					
TIP31B 30p ea	AD592An Temperature Sensor i.c.				
TIP 3055 90p ea	mounted on 1.5m screened lead				
2N3055H 60p ea	complete with data and				
2N3771 £1.20 ea	application notes £1.50 ea				
741 op-amp 25p ea	5 for £1.00 LM3914/LM3915 Bargraph lcs £2.95 ea				
555 timer ic 30p ea	4 for £1.00 LM317T Variable voltage regulator				
LM324 quad op-amp 30p ea	4 for £1.00 mounted on a small heat sink				
1N4007 diode 20 for £1.00			4 for £1.00		

Dept EE, Mailtech
PO Box 16 Ludlow
Shropshire
SY8 4NA
Tel: 058 474475

OPTO DEVICES - LEDS - ETC

PHOTO SENSITIVE SCR

Mounted on a PCB. No data,
60p each, 2 for £1.00

7 SEG DISPLAY

MAN6610 2 digit 0.6" high com anode, amber

60 p each, 4 for £2.00

OPTO-ISOLATOR OP1225

50p each 10 for £4.00

SLOTTED OPTO

£1.00 each

LEDS - LEDS - LEDs

5mm rnd red/yellow/green/amber 10p each 12 for £1.00 any mix

5mm rnd high brightness red/green 20p each 6 for £1.00 any mix

5mm rnd flashing red 60p each, yellow/green 70p each

5mm rnd bl-colour 20p each, tri-colour 30p each

Rectangular 6 x 6 x 2mm red stackable 10p each 12 for £1.00

LED mounted in chrome bezel red, yellow or green 30p each, 4 for £1

LED mounted in a black bezel red only 25p each, 5 for £1.00

PLASTIC BEZEL for 5mm rnd leds 10 for 40p

20 ASSORTED FULL SPEC LEDS. Various shapes and colours £1.00

CONSTANT CURRENT LED 5mm round, red, 2V-18V a.c. or d.c.

Nom. 14mA 30p each, 4 for £1

ALARM CONTROL UNIT

Single zone alarm control unit built into a domestic light switch box. Ideal for home, caravan, boat, garage, shed etc.

Facilities: - Normally closed loop for pir sensors, door/window contacts etc.

Normally open loop for pressure mats.

24-hour loop for personal attack button

Visual indication that the system is operational.

Automatic entry/exit delay.

Automatic system reset.

Alarm output cmos logic level.

SIREN

12 volt dc for external use

115db £8.95

BELL BOX

A plastic bell box cover supplied with backplate.

Red/yellow/white £6.95 each

PRICE COMPLETE WITH FULL INSTRUCTIONS


BELL/SIREN INTERFACE BOARD COMPLETE £8.95

BELL/SIREN INTERFACE PCB ONLY £3.95

BELL/SIREN INTERFACE PCB ONLY £1.50

PASSIVE INFRA-RED ALARM SENSORS

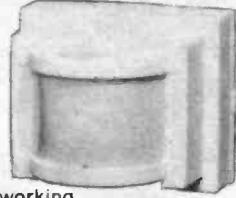SUB-MINIATURE PASSIVE INFRA-RED SENSOR ONLY £5.95



Brand new passive infra-red sensor, measures only 33mmW x 24mmH x 29mmD. Logic level output. Full data and application notes supplied.

EX INSTALLATION SENSORS tested working.

Type 1. Measures 180 x 112 x 70mm with walk test led, relay output and tamper protection. 12 volt dc supply required £8.50 ea

Type 2. As above but a smaller unit 123 x 62 x 50mm £11.75 ea

DOOR/WINDOW CONTACTS

Surface or flush mounting, white £1.10 ea

JUNCTION BOX

white 6 way 60p

Please note: There may be variations in the size of the above passive Infra red sensors depending on stock at the time of ordering. But the unit will certainly be within the stated sizes.

DUAL TECH SENSOR Microwave and passive infra-red combined. Separate led indication for each function. Measures 120 x 75 x 50mm. Relay output 12 volt dc tamper protection £29.95 ea

BREADBOARDS - CAPACITORS - SOLAR CELLS - HEATSHRINK - ETC

SOLAR CELL 2 volt 150mA max, size 60 x 100mm £1.35 ea 5 for £6

HEATSHRINK SLEEVING 8mm dia x 40mm long 5 lengths for £1.00

BNC SOCKETS 50 ohm single hole fixng 50p ea 10 for £4.00

MIN BNC PLUG AND SOCKET 2 pairs for £1.50

PIEZOTRANSUDER 5 assorted types £1.00

MERCURY TILT SWITCH

Standard on/off £1.00 each

4 Contact (Directional) £1.50 each

PIEZOVIBRATION SENSOR

with data sheet £1.00 each

BREADBOARD 173 X 65mm 840TP £5.25 each

TEXT TOOL ZIF SOCKET

28 pin zero insertion socket £5.95 each

SOLID STATE RELAY

Switch mains up to 7 amp 12 or 5 volt control voltage both types £2.95 ea

6 VOLT NI-CAD PACK 5AA NI-CADS, fast charge type £3.95

CAPACITOR 10,000 mfd 25 volt with fixing clip 60p each

CAPACITOR 470 mfd 400 volt £1.50 each 4 for £5.00

CAPACITOR 0.1mfd 63volt 6p each 10 for 50p

EPROMS 27C256 - 30 27C512 - 25. Once programmed but never usedeprom. Mounted on a plastic carrier, can easily be removed from the carrier or used with a low insertion force socket.

27C256 £1.00 each 6 for £5.00 27C512 £1.20 each 5 for £5.00

Suitable low insertion force socket 28 pin 40p ea 3 for £1.00

MULTITURN PRESETS 20mm RECT, 500R, 1K, 5K, 10K, 20K, 50K, 100K 1MO. 40p ea, 3 for £1.00

All prices include VAT.

Please add 75p carriage to all orders

Techniques

ACTUALLY DOING IT!

by Robert Penfold

LAST MONTH the topic of customising projects was discussed. This is something that the majority of constructors indulge in, and it adds to the interest and enjoyment obtained from the hobby. You do need to be slightly careful when doing your own thing though, and in particular, you need to be careful when using substitute or equivalent components.

SUBSTITUTION

There are several possible reasons for using substitutes. One is simply that you cannot find exactly the right component listed in any of the component catalogues.

Another is that you have almost the right component in your spares box, and that you would prefer to use this rather than buy the right component. A third possibility is that the project under construction is an old design, and that some of the components used in the original unit are no longer available.

It is clear from readers' letters that many constructors are simply not sure if certain components are the right ones or not. A fair percentage of queries from readers who are having difficulty getting projects to work include inquiries about the suitability of one or more components. In most cases the components in question seem to be perfectly suitable, but in a few cases a misunderstanding has resulted in a totally unsuitable component being used.

For complete beginners at electronic construction the best advice is to only build projects using what you are certain are the correct components. When building a project from "Everyday with Practical Electronics" remember to consult the *Shoptalk* feature.

If for one reason or another you cannot obtain all the right parts, then it is best not to go ahead with the project. Once you have gained a small amount of experience it is probably safe to start making some simple substitutions.

SWITCHES

In theory, provided a switch has the right number of ways (contacts) and a sufficient number of poles ("moving contact"), it will do the job. It does not matter whether you use a pushbutton, slider, rotary, or rocker type.

In reality you need to be very careful that the switch contacts have suitable current and voltage ratings. The most important point to watch is that you do not use an unsuitable switch on the mains supply. This could be lethal for the switch and anyone who uses it!

Generally speaking, miniature switches are *not* intended for operation on the 240V a.c. mains supply. Most of those that are intended for use on mains supplies are only suitable for continental and US supplies of around 110V to 120V. For mains operation use the larger switches that are intended for on/off switching of the 240V UK mains supply.

Sometimes a components list specifies that a switch should be a *make-before-break* or a *break-before-make* type. These terms only apply to changeover and multi-way switches, not simple on/off types.

With a "make-before-break" switch, as the moving contact is shifted from one terminal to the next it momentarily short circuits the two terminals together.

With "break-before-make" switches the moving contact (pole) becomes briefly isolated from both terminals as it is switched from one to the other.

In most cases it does not matter which of these switch types is used. However, where one type or the other is *specifically* called for in a components list it is essential to use the right kind. Otherwise you might, for example, find that the power supply is short circuited each time you operate the switch. At best the switch would be short lived, and at worst expensive damage would be caused to other components in the circuit.

CAPACITORS

If you look in one of the larger electronic component catalogues there will almost certainly be more than a dozen different types of capacitor on offer. Capacitors that operate well in some respects tend to be less impressive in others.

Circuit designers therefore have to look at the important requirements for each capacitor, and choose a type which measures-up to these requirements. Using a capacitor having the right value, voltage rating, etc., but having the wrong type of construction, may not be a safe substitute.

Ceramic capacitors provide good performance at high frequencies. They are often used for supply decoupling and signal coupling in radio frequency circuits. In other respects the performance of ceramic capacitors tends to be poor.

The tolerance figures are mostly quite high, and the values drift significantly with changes in temperature and the passage of time. They can also give problems with microphony in audio circuits (i.e. they act like crude microphones). It is unwise to substitute another type of capacitor for a ceramic

type, or to use a ceramic capacitor where some other kind has been specified.

The various plastic foil capacitors, such as Mylar, polyester, polystyrene, and polycarbonate types have broadly similar characteristics. In fact components list sometimes just specify "plastic foil" capacitors rather than a particular type within this category.

Provided the electrical ratings are suitable it is unlikely that there will be any problem if one kind of plastic foil capacitor is substituted for a different type. Bear in mind though that there are substantial variations in the sizes and shapes of plastic foil capacitors. A substitute capacitor might have suitable electrical characteristics, but can it be fitted onto the circuit board?

POLARISED

Higher value capacitors are mostly of the electrolytic and tantalum types. The latter are physically very small, and have superior electrical characteristics. Accordingly, a tantalum type can be used instead of an electrolytic type. A substitution in the opposite direction is unlikely to give good results though. In a timing circuit for instance, the higher leakage of an electrolytic capacitor could result in greatly extended times, with the times possibly carrying on indefinitely.

Tantalum and electrolytic capacitors are polarised components which must be connected the right way round if they are to function properly. It is not a good idea to use a polarised capacitor in place of a non-polarised type. The signal across a polarised capacitor must include a d.c. component if the component is to function reliably.

If a large non-polarised capacitor is called for, it is likely that this d.c. component is not present, or that the application is a critical one where the quality of a polarised component would simply not be good enough anyway.

Silvered mica capacitors are sometimes specified for radio frequency circuits. These are very high quality components with price-tags to match.

Mica capacitors are still available, but are becoming increasingly difficult to track down. A good quality polystyrene capacitor is about the only reasonable substitute for a mica type.

LOUDSPEAKERS

The main ratings of loudspeakers are the physical size, the power rating, and the impedance. Using a slightly smaller or larger loudspeaker than that specified is fine, but only if the substitute component has a high enough power rating. Be especially careful about using a loudspeaker that is smaller than the specified size.

In general, the larger the physical size of a loudspeaker, the higher its power rating. Some miniature loudspeakers have very low power ratings. Bear in mind that seriously overloading a loudspeaker can burn out the coil, or (more probably) result in it literally ripping itself apart.

If an eight ohm impedance loudspeaker is required there should be no difficulty in obtaining a suitable component, since virtually all loudspeakers have this impedance. The main exceptions are the high impedance types, where there is a definite lack of standardisation.

A variety of impedances from about 50 to 80 ohms are used. Using a loudspeaker of not quite the right impedance should not cause any difficulties. A 64 ohm component should work perfectly well in place of (say) a 50 ohm or 80 ohm loudspeaker.

Never use an eight ohm loudspeaker instead of a high impedance type. This could damage the semiconductors in the circuit driving the loudspeaker, and (or) result in severe overloading of the loudspeaker. Substituting a high impedance loudspeaker for a low impedance type should be quite safe, but the maximum output power and volume will both be substantially reduced.

DIODES

Occasionally a special diode of some kind will be required, but in most cases projects just use "bog standard" silicon types such as the 1N4148 and 1N914, or very occasionally germanium diodes such as the OA90 and OA91. Substituting one silicon diode for another, or one germanium device for another should not give any problems.

However, do not use a germanium device in place of a silicon type, or vice versa. They have very different characteristics, and are not usually interchangeable.

On the face of it there is no problem in using a silicon rectifier such as a 1N4002 instead of a silicon diode such as a 1N4148. In practice this is not usually a good idea. There are subtle differences between the two types of component which could cause difficulties.

Rectifiers generally have lower forward voltage drops which could cause problems in biasing applications. They also have slow response times which could produce poor results in a.c. applications.

Substituting a rectifier having a higher than specified voltage or current rating is perfectly safe. For example, a 1N4002 (1A 100V) rectifier can be used in place of a 1N4001 (1A 50V) type. Going up to a higher current rating is safe from the electrical point of view, but bear in mind that a higher current rating usually means a much larger physical size as well.

Never use rectifiers having lower voltage or current ratings than the specified components. Apart from the almost certain and spectacular destruction of the substitute rectifiers, other components in the circuit could be damaged.

RESISTORS

Most components list specify something like "0.25 watt 5 per cent carbon film" for all the resistors. This is a minimum requirement, and it is quite in order to use higher quality components such as one per cent metal film resistors.

It is also in order to use a higher wattage than that specified in the "Comps list." However, note that in many cases this would mean trying to use resistors that were far to large to fit into the available spaces on the circuit board.

In the vast majority of cases you can get away with using one value up or down from the correct one (e.g. a 12k or 8k2 resistor instead of a 10k type). This may cause some loss of performance though, and it is advisable to fit the correct value as soon as a suitable component can be obtained.

If you try using a "logarithmic" (log.) potentiometer instead of a "linear" (lin.)

type, or vice versa, the project will work properly. The substitute potentiometer will have rather an odd control characteristic though.

For example, suppose you used a logarithmic potentiometer instead of a linear type for the balance control in a stereo amplifier. This would provide the correct channel balance with the control set almost at one end of its adjustment range, rather than at a roughly middle setting. This is again fine for a temporary fix until you can obtain the right type, but does not provide a satisfactory long term solution.

TRANSISTORS

With projects that operate from a small 9V battery and use transistors as simple amplifiers and switches, BC549s and BC559s can respectively be used in place of virtually any *npn* and *pnp* transistors. There are plenty of other transistors which are suitable as general purpose *npn/pnp* substitutes (BC109/179, BC547/557, etc.).

When using substitutes make sure that you connected the transistors correctly. The fact that two transistors have the same case style does not necessarily mean that they have the same pin leadout configuration.

Using substitutes where higher powers and higher frequencies are involved is rather more tricky. Even very experienced constructors can run into difficulties when attempting this type of thing. For the beginner the best advice is to not bother trying substitutes for any transistor that is at all out of the ordinary.

INTEGRATED CIRCUITS

In general it is not possible to use substitutes for integrated circuits (i.c.s.) due to their specialist nature. However, one exception is operational amplifiers.

There are plenty of operational amplifiers which are designed to be superior versions of the industry standard μ A741C. This includes popular devices such as the TIL071CP, TIL081CP, CA3140E, and LF351N. Using one of these instead of a μ A741C, or in place of another "super" 741C device is almost invariably all right.

Using a μ A741C instead of a "super" 741C is more dubious. The project is almost certain to work, but with some reduction in performance.


Some circuits make use of the CA3140E's ability to operate with a single supply rail in situations where other types require dual supplies. Using a substitute in such a circuit is more or less guaranteed to prevent it from working at all.

There are various families of TTL logic integrated circuits, with each family having "pin-for-pin" equivalents to the devices in the other families. Compatibility between these logic families is actually quite an involved topic, but there is a fairly high degree of compatibility between most of them.

Compatibility is to some extent dependent on the exact way in which a device is used. A substitution might be successful in one circuit, but unreliable in another.

Compatibility is very good between the original 74 series, the popular 74LS series, and the increasingly popular 74HCT devices. It is highly unlikely that an unsuccessful substitution will cause any damage, so the "suck it and see" approach is quite acceptable.

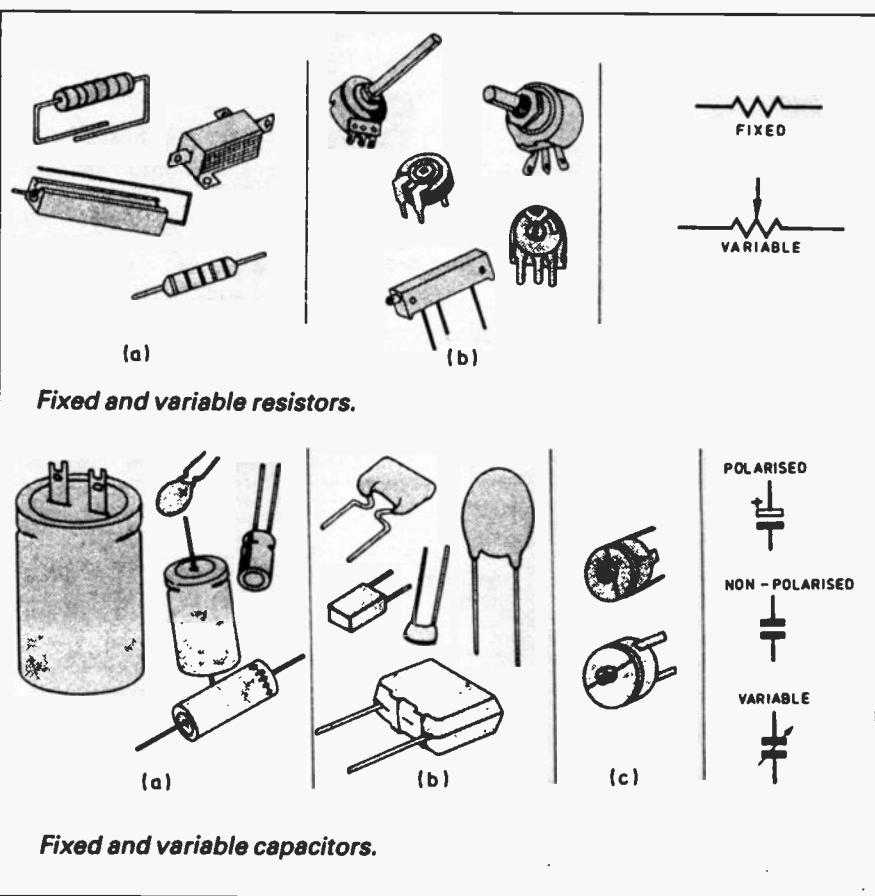In practice with 74 series substitution you seem to be able to get away with rather more than the theory would dictate. Unfortunately, this is not the case with most component substitution.



VIBRATION SENSITIVE ALARM

M. G. ARGENT

Safeguard your valuables with this novel alarm.
Endless possible applications in and around the home.

THE VIBRATION alarm circuit to be described here consists of a piezoelectric sounder (which is used both as a vibration sensor and also a mini speaker), a latch and two oscillators formed by a CMOS quad 2-input NAND Schmitt trigger i.c., and two transistor amplifiers.

HOW IT WORKS

The circuit block diagram is shown in Fig. 1. Vibration of the piezoelectric transducer WD1 generates small voltages which are amplified by the transistor amplifier TR2 and provides a negative "feedback" pulse to flip the latch IC1a and IC1b.

When the unit is switched on, the latch automatically resets itself. When triggered by TR2, the latch changes over, and remains in this "alarm" state until the unit is switched off.

The output of the latch enables two oscillators, creating the required pulsed tone for the alarm sound. The output from the last oscillator is connected to the same transducer WD1 as is used for the alarm sensor. This eliminates the need for two piezoelectric devices and also provides a

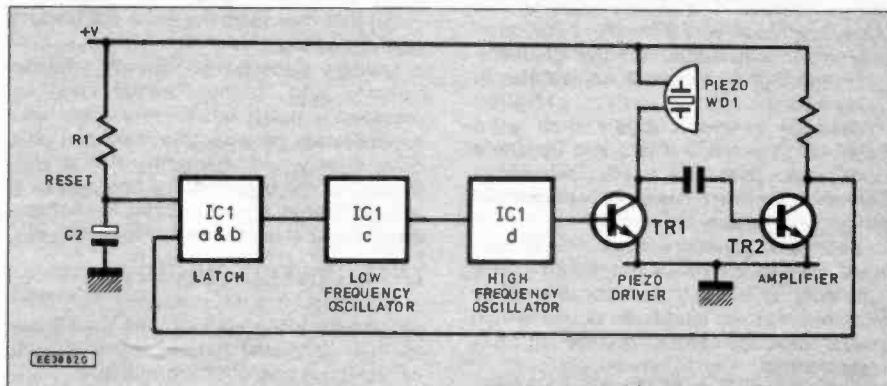


Fig. 1. Block diagram for the Vibration Sensitive Alarm.

regenerative action, guaranteeing positive triggering.

CIRCUIT DESCRIPTION

The full circuit diagram for the Vibration Sensitive Alarm is shown in Fig. 2. The latch, IC1a/IC1b, mentioned earlier is reset by the resistor capacitor combination R1/C2. Capacitor C2 always starts up from


the uncharged state due to it being shorted out by the On/Off switch S1 each time the unit is switched off.

The latch output at IC1 pin 3 will be "low" (0V) when the unit is on but not triggered. When the latch changes state, due to a negative pulse from TR2, its output goes "high" (+9V) enabling the low frequency oscillator formed by IC1c.

This oscillator pulses on and off at a high pitched audio oscillator IC1d, providing the alarm sound. The frequency of the second oscillator is adjustable by VR1 to set the loudest (and most nauseating) frequency. This is then buffered by transistor TR1 to drive the piezo sounder WD1.

Piezoelectric devices are excellent for low power consumption but are not generally loud enough to be heard far away. This problem is easily overcome by connecting an inductor L1 across it. When transistor TR1 is switched on or off at the high pitched audio frequency, L1 "rings" and provides a large voltage swing across the transducer WD1, giving a greatly increased volume than otherwise available.

Fig. 2. Complete circuit diagram for the Vibration Sensitive Alarm.

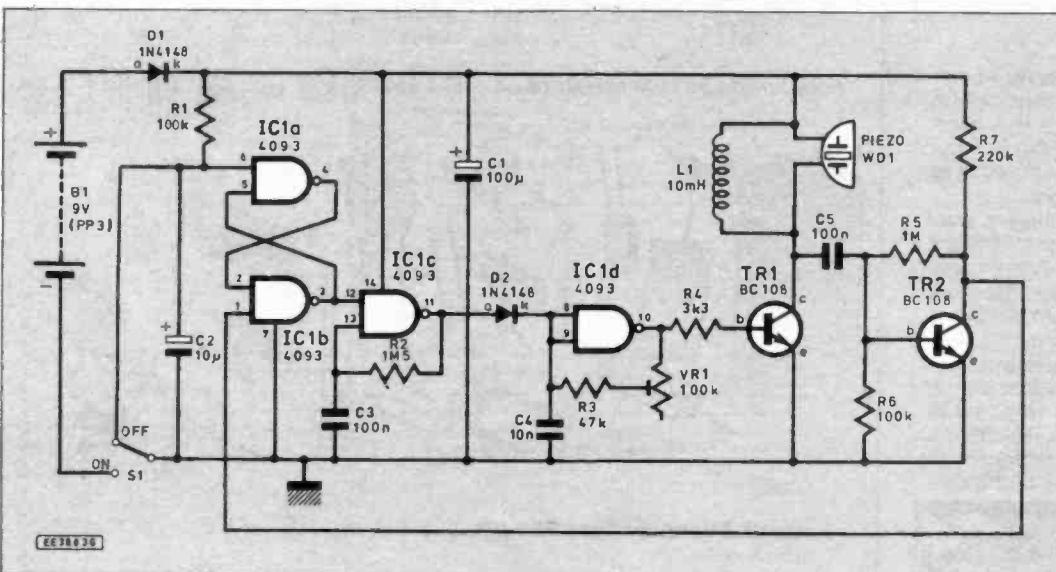

If an inductor is not readily available, it can be substituted with a resistor, typically 10 kilohms, and the unit will function as normal except for the reduced volume, which might still be sufficient in many cases.

Diode D1 is provided to protect the unit against accidental battery reversal.

CONSTRUCTION

The complete unit can be built up on a piece of 0·1in matrix stripboard, size 36 holes by 17 strips, and the topside component layout is shown in Fig. 3. There are 14 copper track breaks required and these are shown in the underside plan view.


Commence construction by inserting the 1J link wires and i.c. socket. This provides a good reference point when mounting components later. The i.c. should not be mounted in its socket until all wiring has been completed and checked.

The small links can be made with bare off-cuts from component leads, but the longer ones should be made with insulated wire. Before adding the components, double check the position and wiring of the links; this will save a lot of headaches at the testing stage.

The rest of the components should now be mounted and soldered on the circuit board. The order should be in ascending size, i.e. diodes, resistors, capacitors . . . transducer.

It might be wise to leave the transistors until last as they are not too happy about being exposed to heat and they must be put in the right way round. Also, be careful to check the polarity of the diodes and the electrolytic capacitors.

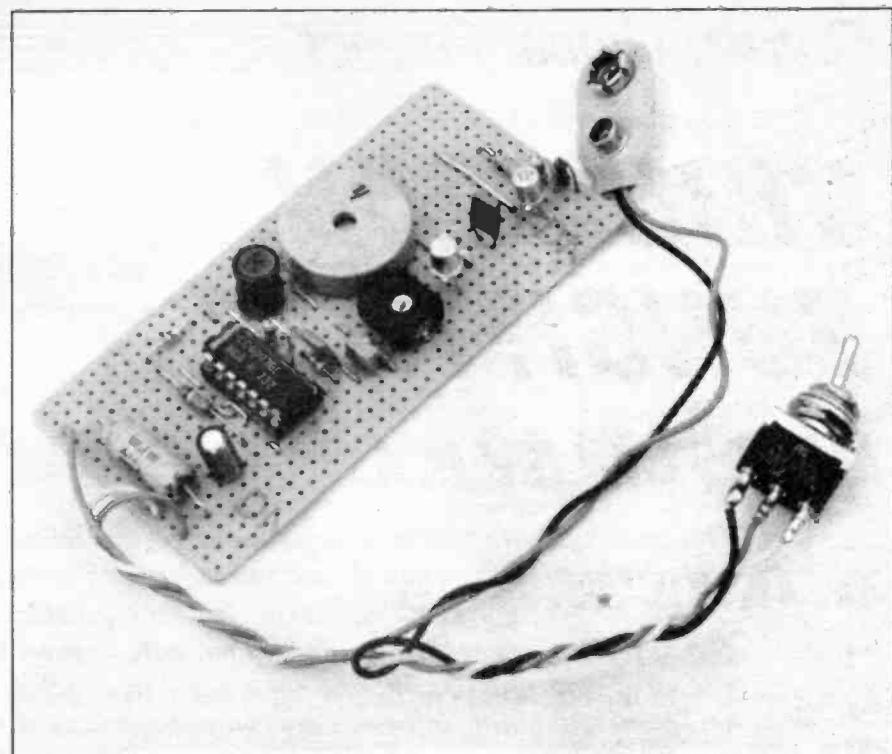It only remains to wire the slide switch to the board and the battery clip leads to the board and switch. In this design, the On/Off slide switch is wired in the negative,



black, battery lead. This is to ensure that in the off position the electrolytic capacitor C2 is discharged.

No details have been provided for a case and this has been left to individual choice. However, a small hole or series of holes should be drilled in the case above the sound transducer.

TESTING

Once assembled, check the board for any errors or solder shorts across copper

tracks, plug the i.c. into its socket and connect up the battery. The diode D1 protects against reverse battery polarity.

Switch on and wait a few seconds while the unit resets itself, via R1/C2. Tap the piezoelectric transducer WD1, this should give out a pulsed high pitched sound.

Leave the alarm running and adjust preset VR1 for the loudest and most annoying output. This type of sound carries a long way and would, hopefully, deter most unwanted intrusions.

COMPONENTS

Resistors

	See SHOP TALK Page
R1, R6	100k (2 off)
R2	1M5
R3	47k
R4	3k3
R5	1M
R7	220k
	All 0·25W 5% carbon film

Potentiometer

VR1 100k skeleton carbon preset, lin.

Capacitors

C1	100μ axial elect., 35V
C2	10μ radial elect., 16V
C3, C5	100n ceramic or poly (2 off)
C4	10n ceramic or poly

Semiconductors

D1, D2	1N4148 signal diode
TR1, TR2	BC108 npn silicon transistor (or similar)
IC1	4093 quad 2-input CMOS Schmitt trigger

Miscellaneous

L1	10mH p.c.b. mounting choke
S1	Single-pole slide or toggle changeover switch
WD1	Piezoelectric transducer
	Stripboard, 0·1in. matrix, size 36 holes x 17 strips; 9V PP3 battery and connector leads; plastic case to choice; board spacers; fixing nuts and bolts; solder etc.

Approx cost
guidance only

£4
plus case


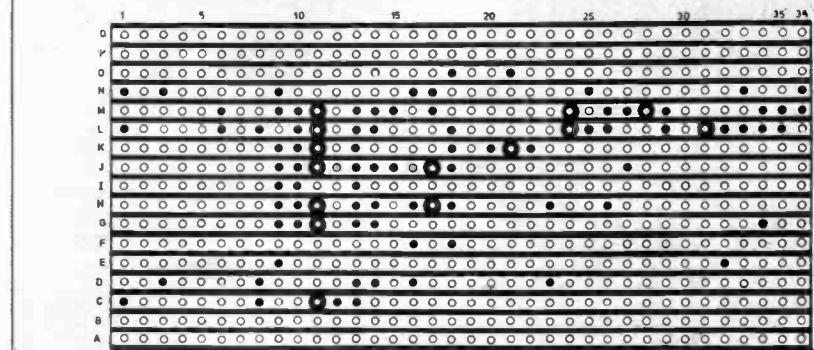
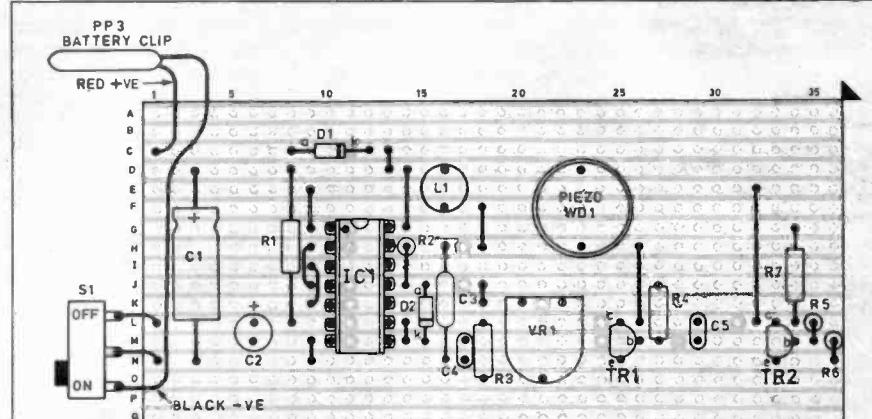


Fig. 3. Stripboard component layout and underside details of breaks required in the copper tracks.

CIRCUIT SURGERY

MIKE TOOLEY B.A.

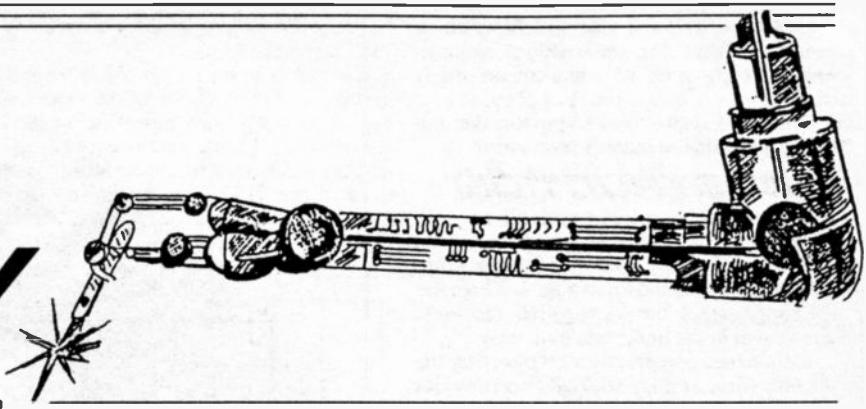

Welcome again to Circuit Surgery, our regular clinic for readers' problems and a particularly warm welcome to readers of Practical Electronics. For the benefit of our new readers, Circuit Surgery provides a regular "self-help" forum for readers' problems. We aim not only to provide a regular cocktail of practical hints and tips but also some rapid feedback (including modifications and trouble-shooting information) concerning many of the projects which have appeared in the pages of both Everyday and Practical Electronics. Naturally, this column relies almost entirely on input from readers, so please drop me a line and let me know what topics you would like me to cover.

This month's *Surgery* should have a particular appeal to the audio enthusiast. We shall be describing some simple circuitry for compressing audio signals, a power supply for a low-noise pre-amplifier stage, and also suggesting some useful background reading on "digital audio".

Finally, for those who may not be so interested in audio, we include some information on the popular RS-232 serial communications interface.

Constant level

Audio enthusiast *Chris North* writes from Bristol with a request for a simple circuit which will help him keep the level of a microphone signal reasonably constant. Chris writes:

"I am regularly involved with public address work and often have difficulty with varying microphone levels. I need a circuit which will accept a signal from a medium impedance dynamic microphone and deliver a constant output signal to the power amplifier."

The output signal from a microphone can vary from less than a hundred microvolts to several tens of millivolts depending upon the distance of the source and the intensity of the sound and such varying signal levels can be a real problem with public address equipment.

Unfortunately, inexperienced public address users are often blissfully ignorant of this fact and frequent adjustment of the volume control may be required in order to provide an acceptable output level (neither deafening an audience nor straining their ears).

The solution to this particular problem is a circuit which will provide a rapidly falling voltage gain as the amplitude of an input signal is increased above a threshold level. Such a circuit is known as a "compressor" and a practical example (based on two commonly available operational amplifiers) is shown in Fig. 1.

The compressor circuit can be used to replace an existing microphone pre-amplifier but offers the advantage that its output remains reasonably constant (at about 2V peak-peak) for any input greater than 20mV peak-peak. The circuit has a frequency response which extends from 100Hz to over 10kHz and thus should be more than adequate for most public address work.

Preset VR1 sets the amount of compression provided by the circuit and the correct setting for this component will usually require a little experimentation. If no compression is required, VR1 should be set to minimum (slider at 0V). In this case, the

circuit will operate as a "straight" pre-amplifier with a voltage gain of about 750 (the signal shunt, TR1, will never be driven into conduction).

If high-quality low-output microphones are to be used, greater sensitivity may be required. In this case both R2 and R7 can be increased to 470k. The onset of compression will then be reduced to approximately 5mV with VR1 at maximum setting.


30V power supply

Regular reader *Simon Jones* writes from Liverpool with a request for information on the design of a 30V power supply. Simon writes:

"I am constructing an ultra low-noise pre-amplifier based on a TDA3410. This requires a 30V power supply. Can you provide me with a circuit which can power two identical pre-amplifiers using this chip?"

The TDA3410 requires a fairly modest supply current (approximately 10mA) and thus a simple

Fig. 1. Circuit of the audio compressor.

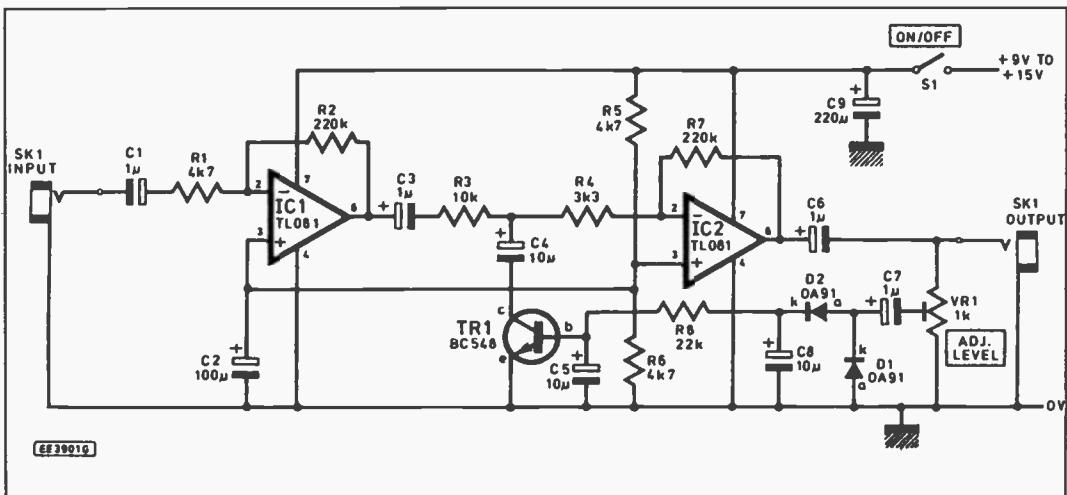

transformer/rectifier/regulator combination should suffice, see Fig. 2.

The 14-pin d.i.l. regulator (IC1) is capable of operation over a very wide voltage range (2V to 37V at a maximum load current of 150mA) and thus should be more than adequate for this application. The output voltage of the power supply is set by means of VR1 whilst the current limiting resistor (R2) has been chosen so as

connected in series. Maplin's WB10L is ideal for use in this circuit. The bridge rectifier, D1-D4, is a W01 device (100V PIV) rated at 1A.

It is worth pointing out that care should be taken when positioning the power supply within the pre-amplifier enclosure. The transformer, T1, and mains wiring should be kept well away from the input connections to the TDA3410 devices in order to

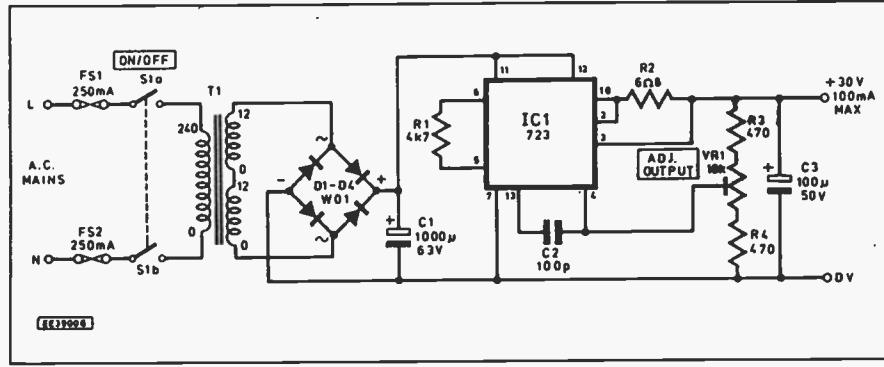


Fig. 2. Circuit of the 30V power supply.

to provide a maximum output current of 100mA (sufficient for several TDA3410 devices).

The mains transformer, T1, should be rated at 6VA (or more) and should have two 12V secondaries (each rated at 250mA)

prevent hum and induced noise. Furthermore, an earthed metal enclosure should be employed (with ground connections taken to a single common earth point in order to prevent earth loops) and all internal signal wiring should use screened audio cable.

Modem connections

George Smith writes from Edinburgh with a query relating to the serial port connections on a BBC Micro:

"On reading your Circuit Surgery article in which you supplied Mr Ron White with connection details of the SCART connector, I wonder if you could help me with a similar problem.

I purchased a British Telecom Mainstream modem model FM 1200 from a sale. Unfortunately it did not contain any technical data. The problem is that there is a 25-way D-socket on the rear panel of the modem which I wish to connect to the 5-pin domino DIN socket fitted to the RS-423 port of a BBC Micro.

The pins on the RS-423 port are: A - data in; B - data out; C - 0V; D - CTS; and E - RTS. Do you have any idea of the pinout of the 25-way D-socket?"

The RS-232/CCITT V.24 interface undoubtedly reigns supreme as the most widely used standard for serial communication between microcomputers, peripheral devices, and remote host computers, which were not defined under RS-232C. The standard was first defined by the Electronic Industries Association (EIA) in 1962 as a recommended standard (RS) for modem interfacing.

RS-232 relates essentially to two types of equipment; Data Terminal Equipment (DTE) and Data Circuit Terminating Equipment (DCE). Data Terminal Equipment (e.g. a microcomputer) is capable of sending and/or receiving data via an RS-232 serial interface. It is thus said to "terminate" a serial link.

Data Circuit Terminating Equipment (formerly known as Data Communications Equipment), on the other hand, is generally thought of as a device which can facilitate serial data communications and a typical example is that of a modem (modulator-demodulator) which forms an essential link in the serial path between a microcomputer and a conventional analogue telephone line.

Digital audio

Judging from a number of readers' letters "Digital Audio" is quite a "hot" topic these days! Unfortunately, the subject often does not feature in many of the older textbooks and several readers have asked me to suggest sources of information. Two books which are well worth reading are:

The Art of Digital Audio (Focal Press, ISBN 0-240-51270-7) by John Watkinson provides an excellent introduction to the subject. It contains all of the essential theory of digital audio and should appeal to those with little previous experience of the subject. John Watkinson provides a very detailed description of digital audio coding, processing and conversion without getting too bogged-down in complex mathematics. The book then continues with a description of a number of current digital standards and error correcting techniques before describing a variety of equipment.

Digital Audio and Compact Disk Technology (Heinemann Newnes, ISBN 0-434-91868-7) is edited by staff from the Sony Service Centre (Europe) and contains a wealth of information relating to a wide variety of digital audio equipment. The book provides a useful introduction to the principles of digital signal processing, sampling, quantization, conversion and coding and also contains chapters on Compact Disk players, Video 8, Digital Audio Tape (DAT) and Digital Audio Stationery Head (DASH) formats.

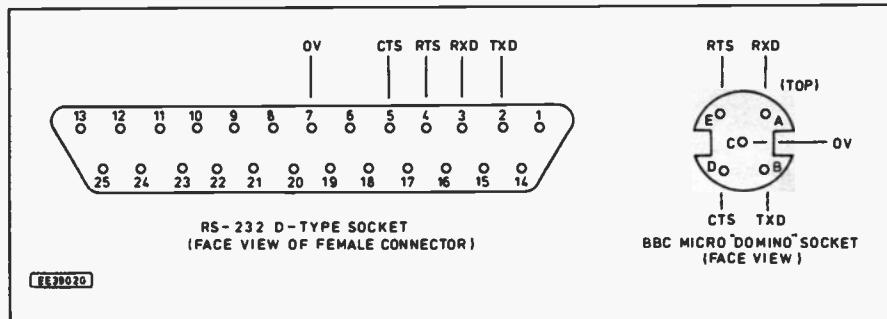


Fig. 3. Pin connections for the 25-way D-Connector.

Data terminal equipment (DTE) is normally fitted with a male connector whilst data circuit terminating equipment (DCE) conventionally uses a female connector (note that there are a few exceptions to this rule!).

Fortunately the solution to Mr Smith's problem should be fairly straightforward since the BBC Micro uses only a subset of the full set of RS-232 port connections. Furthermore, the wiring of the 25-way

modem connector should be reasonably standard and should obey the following convention in respect of the most important signals present:

Pin no:	Signal	Function
1	FG	Earth connection to the equipment frame or chassis.
2	TXD	Serial data transmitted from DTE to DCE.
3	RXD	Serial data received by the DTE from the DCE.
4	RTS	When active, the DTE is signalling that it wishes to send data to the DCE.
5	CTS	When active, the DCE is signalling that it is ready to accept data from the DTE.
6	DSR	When active, the DCE is signalling that a communications path has been properly established.
7	SG	Common signal return path (0V).
8	DTR	When active, the DTE is signalling that it is operational and that the DCE may be connected to the communications channel.

Next month:

In next month's *Surgery* we shall be attempting to explain the mysteries of "safe area protection". We shall also be taking a look at several probes which can be used to extend the functions provided on basic test equipment. We also have a "round-up" of hints and tips sent in by readers over the past six months.

In the meantime, if you have any comments or suggestions for inclusion in *Circuit Surgery*, please drop me a line at: Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey, KT13 8TT. Please note that I cannot undertake to reply to individual queries from readers however I will do my best to answer all questions from readers through the medium of this column.

HART

HART AUDIO KITS – YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART KITS give you the opportunity to build the very best engineered hi-fi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

Our list will give you fuller details of all our Audio Kits, components and special offers.

AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get £K performance for a few tenths of the cost!. Featured on the front cover of 'Electronics Today International' this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic:- "The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This impression is greatly reinforced by the internal appearance, which is redundant of quality, both in components and in layout." Options include stereo LED power meter and a versatile passive front end giving switched inputs using ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility so that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monobloc' versions without the passive input stage and power meter are also available. All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heatsink fitted with IEC mains input and output sockets. All the circuitry is on professional grade printed circuit boards with roller tinned finish and green solder resist on the component ident side, the power amplifiers feature an advanced double sided layout for maximum performance. All wiring in this kit is pre-terminated, ready for instant use!

RLH1 Reprints of latest articles.....£1.80

K1100CM HART Construction Manual.....£5.50

LINSLEY HOOD 1400 SERIES ULTRA HIGH-QUALITY PREAMP

Joining our magnificent 80 Watt power amplifier now is the most advanced preamplifier ever offered on the kit, or indeed made-up marketplace. Facilities include separate tape signal selection to enable you to listen to one programme while recording another, up to 7 inputs, cross recording facilities, class A headphone amplifier, cancellable 3-level tone controls and many other useful functions, all selected by high quality relays. For full details see our list.

Send or 'phone for your copy of our List (50p) of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows:- INLAND Orders up to £20 - £1.50

Orders over £20 - £3.50 Express Courier, next working day. £10 (For safety all computer parts are only sent by courier) OVERSEAS - Please see the ordering information with our lists.

Send or 'phone for your copy of our List (50p) of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows:- INLAND Orders up to £20 - £1.50

Orders over £20 - £3.50 Express Courier, next working day. £10 (For safety all computer parts are only sent by courier) OVERSEAS - Please see the ordering information with our lists.

LINSLEY HOOD 'SHUNT FEEDBACK' R.I.A.A. MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIERS



Modern, ultimate sound systems are evolving towards built-in preamplifiers within or near the turntable unit. This keeps noise pickup and treble loss to a minimum. We now offer two units, both having the sonically preferred shunt feedback configuration to give an accurate and musical sound, and both having the ability to use both moving magnet and moving coil cartridges.

Kit K1500 uses modern integrated circuits to achieve outstanding sound quality at minimal cost. The very low power requirements enable this unit to be operated from dry batteries and the kit comes with very detailed instructions making it ideal for the beginner. K1500 Complete kit with all components, printed circuit board, full instructions and fully finished case.....£67.99


Instructions only.....£2.80

Kit K1450 is a fully discrete component implementation of the shunt feedback concept and used with the right cartridge offers the discerning user the ultimate in sound quality from vinyl disks. Can be fitted inside our 1400 Preamp, used externally or as a standalone unit. It has a higher power requirement and needs to be powered from our 1400 Series preamplifier or its own dedicated power supply. K1450 Complete kit of board mounting parts for discrete component RIAA preamplifier.....£61.06

1500/2-8 Case to suit, Including Hardware...£39.52

K1565 Power Supply in matching case. Features shielded toroidal transformer and upgrade path to full preamp power supply.....£79.42

ALPS PRECISION LOW-NOISE STEREO POTS.

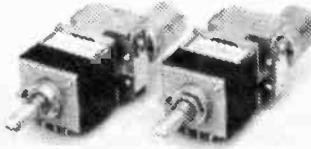

To fulfil the need for higher quality controls we are now importing an exciting new range of precision audio pots in values to cover most quality amplifier applications. All in 2-gang stereo format, with 20mm long 6mm dia. steel shafts. Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motorised versions have 5v DC Drive motor.

2-Gang 100K Lin.....£8.67

2-Gang 10K & 50K Log.....£9.40

2-Gang 10K Special Balance, zero

crosstalk and zero centre loss.....£10.48

2-Gang 20K Log (Volume Control)

MOTORISED.....£19.20

2-Gang 10K Special Balance,

MOTORIZED, zero crosstalk and

< 10% centre loss with near

Log/Antilog Tracks.....£19.98

STUART REEL-TO-REEL TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias circuit system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allows a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. Ideal for bringing that old valve tape recorder back to life. Suitable stereo heads are in our head list. This basic kit is suitable for advanced constructors only. K900W Stereo Kit with Wound Coils and Twin Meter Drive.....£123.93

RJS1 Reprints of Original Descriptive Articles.....£3.60

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are suitable for use with any high quality cassette deck. Switched bias and equalisation to cater for chrome and ferric tapes. Very versatile, with separate record and play circuits and easy to assemble on plug-in PCBs. Complete with full instructions. Complete Stereo Record/Play Kit.....£62.58

VU Meters to suit.....(Each) £3.99

RLH1 & 2 Reprints of original Articles.....£2.70

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. For top performance cassette recorder heads should be replaced every 1,500 hours. Fitting one of our high quality replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines (Sony are special dimensions, we do not stock) and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users. HC80 NEW RANGE High Beta Permalloy Stereo head. Modern space saver design for easy fitting and lower cost. Suitable for chrome metal and ferric tapes, truly a universal replacement head for everything from hi-fi decks to car players and at an incredible price too!.....£8.30

HS16 Sendust Alloy Stereo Head.....£21.49

HRP373 Downstream Monitor Stereo Combination Head.....£53.90

HC15 Special Offer of Standard Quality Stereo R/P Head with slight face scratches.....3 for Only £4.80

HQ551A 4-Track RECORD & Play Permalloy Head for auto-reverse car players or quadraphonic recording.....£8.75

HM120 Standard Mono R/P Head.....£3.44

H524 Standard Erase Head.....£1.90

H561 Hi Field Erase Head for METAL Tapes.....£3.49

SM150 2/2 (Double Mono) DC Erase Head.....£5.20

HQ751E 4/4 True 4-Track Erase Head.....£57.06

REEL TO REEL HEADS

999R 2/4 Record/Play 110mH. Suits Stuart Tape Circuits.....£13.34

998E 2/4 Erase Head 1mh. Universal Mount. Suits Stuart.....£11.96

TAPE RECORDER CARE PRODUCTS

DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation.....£4.08

DEM115 Electronic, Cassette Type, demagnetizer.....£8.61



QUALITY
AUDIO KITS

24 hr. SALES LINE
(0691) 652894

ALL PRICES
INCLUDE VAT
AT 17.5%

HART
HART ELECTRONIC KITS LTD
6 PENYLAN MILL
OSWESTRY, SHROPSHIRE
SY10 8AF

INTERFACE

Robert Penfold



JUDGING from readers' letters, playing around with stepper motors is currently a popular pastime for the electronic hobbyist. Driving stepper motors is actually much more simple than many people seem to imagine. It looks complex because most stepper motors have about six leads, as opposed to the two of an ordinary d.c. motor.

Also, stepper motors are normally driven via special driver circuits which are almost invariably based on dedicated integrated circuits. The circuit diagram therefore gives few clues as to what is going on.

Next Step

The stepper motors that are available to the hobbyist are virtually all of the four-phase variety. You need to be slightly wary of cheap surplus stepper motors as these are often something other than four-phase types, and could be very difficult to drive properly. Fig. 1 shows the basic way in which a normal four-phase stepper motor functions.

The basis of the motor is two electro-magnets in an "X" formation. Each electro-magnet has two coils wound in anti-phase, so that the polarity of the magnetic field can be changed by switching over from one coil to the other.

Obviously the same thing could be achieved by having a single coil and changing the polarity of the drive voltage. However, the driver circuit can be more simple if twin anti-phase windings are used.

A bar magnet is fitted to the drive shaft, and the orientation of this magnet will depend on the polarities of the electro-magnets. Bear in mind here that like poles repel, and unlike poles attract.

As you will see from Fig. 1, by altering the polarities of the electro-magnets in

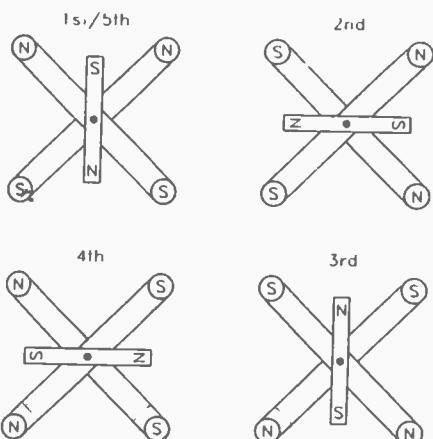


Fig. 1 Method of operation used in a four-phase stepper motor.

the correct manner the bar magnet can be dragged round in 90 degree increments. By repeating the sequence over and over again the magnet can be made to rotate continuously. By reversing the sequence it can move in the opposite direction.

In a practical stepper motor there are usually several sets of electro-magnets, giving much smaller steps. The Maplin stepper motor for instance, has 7.5 degree steps, or some 48 steps per complete turn.

Clearly a much finer degree of control will be needed in most applications, but this can be provided by some step-down gearing. For example, with an eight-to-one step-down ratio there would be 384 steps per turn, and slightly better than one degree resolution.

Stepping Power

An important point to bear in mind is that stepper motors are not very powerful, and even with the aid of step-down gearing they can only drive light loads. It should also be borne in mind that they are not really a good choice where continuous rotation is required. An ordinary d.c. electric motor can usually handle that type of thing perfectly well, and at a fraction of the price.

Four-phase stepper motors have six leadout wires. Two of these are "common" leads which simply connect to the positive supply rail. The other four are driven from open collector outputs, which should include protection diodes because the solenoids in the motor obviously provide highly inductive loads.

One way of handling things is to simply control the solenoids directly from some digital outputs of the computer. Outputting the appropriate values in the correct order then steps the motor in the required direction. Most people prefer to use a proper driver circuit, which usually means one based on the SAA1027 integrated circuit. Control of the motor is then very straightforward, and is achieved using two outputs. Pulses on one output provide stepping of the motor, while the logic state of the other output determines the direction of the motor.

Next month we will consider some practical stepper motor interface circuits.

P.C.B. Shareware


In the past there has been plenty of high cost software for producing printed circuit board designs on a computer, but there has been little low cost commercial or shareware software of this type. In recent times some good low cost p.c.b. software has appeared, some existing programs have been subjected to spec-

tacular price cuts, and some good shareware p.c.b. programs for the PCs have appeared. I reviewed the British produced "Quickroute" a couple of months ago, and this was probably the first shareware program to offer a real alternative to the low cost commercial p.c.b. programs.

Pads-PCB

Now there are two new shareware p.c.b. programs for the PCs in the form of "Pads-PCB" from the USA, and "Layo1" from France. These are both sophisticated programs, and "Pads-PCB" would seem to be the most advanced shareware p.c.b. program currently available. It has facilities which rival the cheaper and mid-priced commercial offerings.

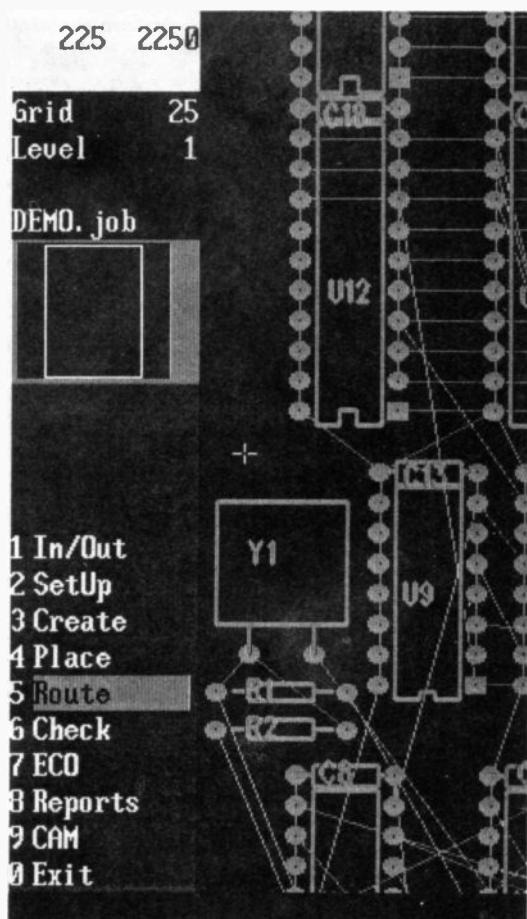Unfortunately, it is sufficiently advanced to be *unusable* on many PCs. To run this program you require at least an 80286 based PC fitted with 640K of RAM and a hard disk with at least seven megabytes of free space. A V.G.A. display is also needed, and some super V.G.A. modes are also supported.



Control of the program is via a combination of the keyboard and a Microsoft compatible mouse. The program is supplied on three high density 3.5 inch or 5.25 inch disks.

There are really two programs, one of which is a front-end which is used to produce circuit diagrams (or "schematics" in American terminology), and to produce netlists which are fed to the second program. A netlist is basically just a components list together with details of all the interconnections.

The second program takes the netlist and converts it into physical representations of the components, complete with a "ratsnest" of interconnections. The components can be placed onto the board manually, or there is an auto-placement facility which can be used. This is quite an advanced feature which is normally only found on very expensive p.c.b. design programs.

In the "ratsnest" each connection runs straight from one pin to the next, probably crossing several other tracks and a few pads on the way. Each track therefore has to be carefully routed to avoid any short circuits. The routing can be performed manually, and there are plenty of editing tools which permit corners and angles to be placed in the tracks, the track width to be varied, etc.

Auto-Routing

There is also an automatic routing facility with various options that can alter its approach to routing a "ratsnest". In common with other auto-routers which use "maze-search" and other relatively simple methods, it will work quite well with certain types of board, but is virtually useless with many other types.


The problem with virtually all auto-routers is that they tend to produce complex two-sided layouts, whether or not the design really justifies it. Also, they generally complete about 90 per cent or so of the tracking, leaving the user to finish the rest.

This would be fine, but most auto-routers tend to "paint you into corners", possibly leaving a board that is impossible to finish without some substantial redesigning. Simple auto-routers are great fun to try out, but are not usually of much practical help.

The "Pads-PCB" actually has two auto-routers, and these seem to be better than most. Although the success rate is not exceptionally high, the routers do seem to route the tracks more sensibly than much of the competition.

Both routers are also much faster than many other auto-routers I have tried. Great claims are made for the 100 per cent rip-up-and-retry and "power" routers, but unfortunately these are not included in the shareware version of the program.

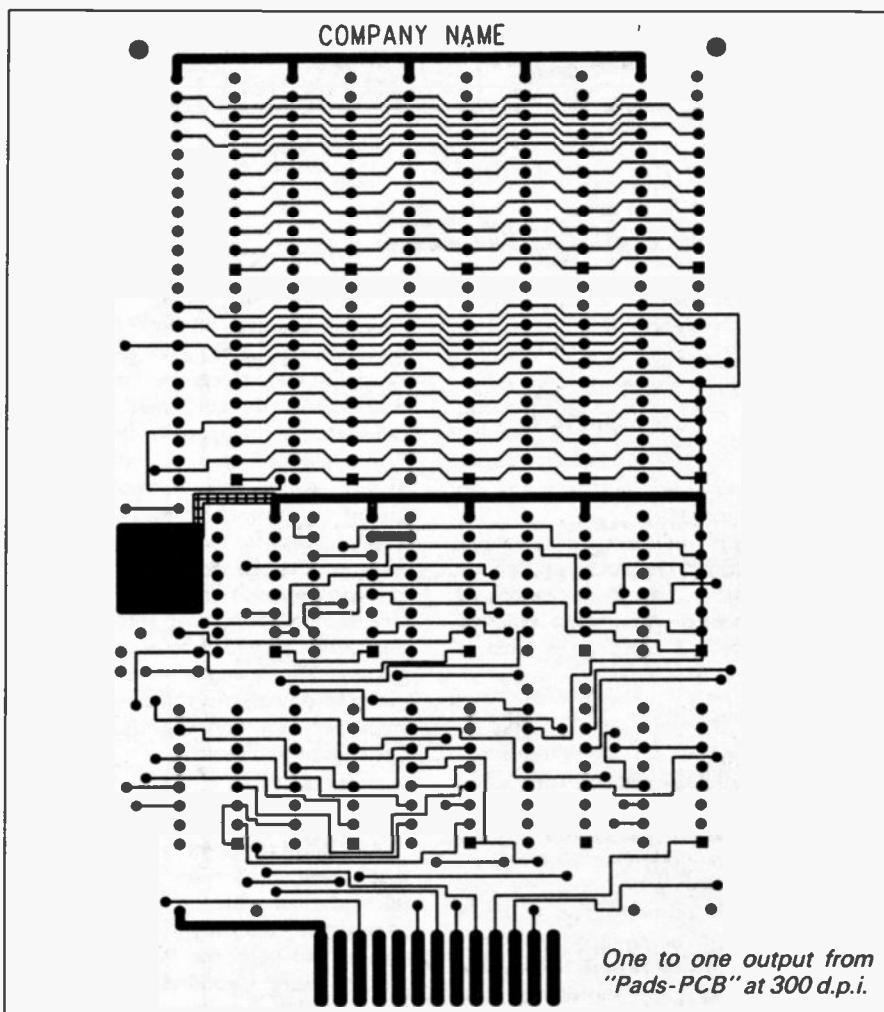The netlist approach is the one favoured by most professional p.c.b. designers, but it is a bit over the top if you only need to draw up relatively simple printed circuit designs. Like most p.c.b. design programs, "Pads-PCB"



One to one output from
"Pads-PCB" at 300 d.p.i.

allows you to use the p.c.b. design part of the program as an electronic drawing board if that is all you need.

The program can output to a wide range of devices, including dot-matrix printers, laser printers, plotters, and photo-plotters. I tried printing out one of the demonstration designs on a 24-pin dot-matrix printer and a 300 d.p.i. laser printer, and the quality seemed to be about as good as the printers would allow.

In a short review of this type it is impossible to cover such a complex piece of software in detail. It is a very sophisticated and well thought out program, and it seems to be reasonably bug-free. There is plenty of documentation in the form of ASCII files on the disk, and the documentation is very concise and complete by shareware standards.

If you have a suitable computer and you are interested in electronics, then this is a program that you should definitely give a try. The running demonstration for the p.c.b. section of the program will give you a good idea of what "Pads-PCB" can do.

The shareware version is limited to logic boards having about 30 integrated circuits, or analogue boards having an equivalent number of interconnections. However, this should be sufficient for the majority of do-it-yourself projects.

If the shareware version is sufficient for your needs, then "PADS Software Inc." are apparently quite happy for you to go

on using their program, with no registration fee being required. All you pay is the £18.00 (including V.A.T. and postage) for the three high density distribution disks. This must be one of the best software buys of all time!

LAYO1

It is difficult to comment on the "LAYO1" program. It is produced in France, but the on-disk documentation is in English. At least, it is almost in English. Unfortunately, the documentation is rather cryptic and contains more than a few errors. The program seems to be fairly sophisticated - it includes an auto-router for example. I found it difficult to get this program to do anything worthwhile though.

The hardware requirements seem to be similar to those of "Pads-PCB", and the program is supplied on a single high density disk. Be warned that the installation program generates a large sub-directory structure which it fills with dozens of files. If you have suitable computer equipment it is probably worth giving this program a try, but you will need plenty of time to work out how to use it!

"LAYO1" and "Pads-PCB" are available from *The PDSL, Dept EE, Winscombe House, Beacon Road, Crowborough, Sussex, TN6 1UL* (0892 663298), and are on disks H027 and H031A/B/C respectively. They might be available from other shareware libraries, but will have different catalogue numbers.

CONTROL PORT for PCs

This I/O Port follows the general approach of the 'INTERFACING to PCs' series in this mag, BUT allows user's prototype control circuitry to be set up and run OUTSIDE the PC.

The double sided PCB fits into an I/O slot, and a ribbon cable terminating in a D-25 plug allows the control of projects with little risk to the PC. On board facilities include: 8-bit A-D, 8-bit D-A, 8 inputs, 8 latched outputs, 3 strobes and 1 IRQ.

Available as:

- (a) Etched double sided board with full instructions for drilling/assembly/testing using BASIC..... £12.50
- (b) Complete I/O card with ribbon cable and BASIC test programs. (Built and tested)..... £29.00

Also available: Test pod with D-25 socket providing analogue and digital test signals/outputs for the I/O card, with BASIC test programs on disc..... £17.00

All above prices include P&P. Mail Order only from:

R. BARTLETT,
17, LIME TREE AVENUE, TILE HILL,
COVENTRY CV4 9EY

LOW COST 418MHz UHF RADIO SWITCHING

AS USED BY THE PROFESSIONAL SECURITY MARKET

Incorporating the latest Surface Acoustic Wave technology, the system consists of a small "zero-power", UHF transmitter with digital encoder and a UHF receiver unit with digital decoder and momentary output. Transmitter available either as fully assembled unit in its own key-fob case which is fully MPT approved (codes set by cutting tracks) or in kit form with 8-way DIL switch. Receiver also available in two kit forms, one which uses cut tracks to set code (over 13,000 codes available), the other uses an 8-way DIL switch (256 codes).

Kit Sizes:	Tx 45 x 30mm
Kit Supplies:	Tx 3-15V Rx (both) 9-15V
Approved Key-fob Transmitter:	TXKF..... £25.99
Individual Kit Transmitter:	TXKT..... £15.99
Individual Kit Receiver (8-way DIL switch):	RXDS..... £19.99
Individual Kit Receiver (Cut Tracks):	RXCT..... £18.99
1 x TXKF + 1 x RXCT: SYS1.....	£39.99
1 x TXKT + 1 x RXDS: SYS2.....	£29.99

Quantity Discounts Available. Please allow 28 days for delivery
Cheques/P.O.s to:

BLB Electronics


341 Darwen Road, Bromley Cross, Bolton BL7 9BY

PICO ADC-10

8-bit Analog to Digital Convertor for IBM PCs & compatibles

- 10-25 kHz typical sampling speed
- 0-5 v input range

£49
+ VAT
(including p+p)

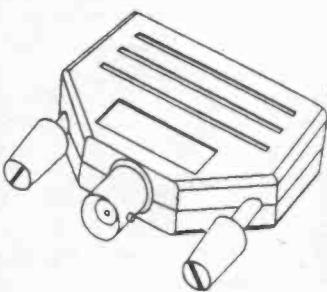


- Plugs directly into parallel printer port
- Requires no external power or expansion slots
 - BNC input connector
- Supplied with software to use as a voltmeter & oscilloscope, plus Turbo C and Pascal drivers

Pico Technology Limited
Broadway House, 149-151 St. Neots Road.
Hardwick, Cambridge CB3 7QJ
Tel. 0954 211716 Fax. 0954 211880


OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX ★ 031 667 2611

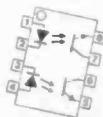The supplier to use if you're looking for:-



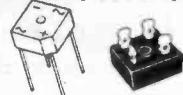A WIDE RANGE OF
★ COMPONENTS AIMED AT THE ★



HOBBYIST



★ COMPETITIVE VAT INCLUSIVE ★
PRICES



★ MAIL ORDER – generally by ★
RETURN OF POST



★ FRIENDLY SERVICE ★

OPEN:

Monday-Thursday 9.15 - 6.00



Friday 9.15-5.00



Saturday 9.30-5.00



Micro AMPS

£99 8051 'C' COMPILER £99

- Preprocessor, compiler, optimiser
- Integer implementation
- Inline assembler
- Assembler level simulator and monitor
- Single chip to fully expanded memory

£99 8051 BASIC COMPILER £99

- Integer BASIC compiler
- Supporting single chip mode
- 8051 cross assembler included
- High Level debugger runs on PC
- Standard Basic commands supported

8051 ICE (ICE51™)

- Low cost 8051 In-Circuit Emulator
- Low power, 5 volt operation
- Plugs directly into the 8051 processor socket on target hardware
- 32K Bytes of battery-backed RAM for program/data
- Single stepping and break points

TMICE51 is a trademark of Intel Corp.

87C751 ICE (ICE751)

- Low cost 87C751 In-Circuit Emulator
- Emulation cable plugs into the 87C751 processor socket on target hardware
- On-board programmer for DIL devices
- PLCC adaptor available for 87C751
- Programs 87C752 DIL and PLCC devices through optional adaptors

TMICE751 is a trademark of Intel Corp.

87C751 ICE (ICE751)

- Monitor uses only 48 bytes of program memory
- Upload/download INTEL hex files
- PC host software communicates via serial port
- Monitor file supplied in assembly form
- On-screen disassembly of code
- I²C drivers available
- Real time clock version available

8051 BOOK

Architecture, Programming and Applications (£49.95). This book includes a free assembler and simulator for personal or educational use

PEB552

The Philips evaluation board for the 80C552 processor variant, a monitor and programming adaptor are available for this product

I²C

Quick Basic development tools available which includes I²C monitor program, I²C connector/cable assembly and parallel I/O demo board

MACH 1

An RTX 2000/1 PC based evaluation board featuring the RTX 2001 RISC Forth processor capable of sustaining up to 12 MIPS

ICC2000

An 8 channel intelligent communications card using the RTX2001 RISC Forth processor capable of sustaining up to 12 MIPS

FORTH + +

A low cost RTX200/1 compiler optimised for use on the IBM PC based MACH1 development board but can be interfaced to other boards

The 8051: An Introductory Course

This is a one day course aimed at customers who need to become familiar with the MCS51 (8051) microcontroller family, and designed to give a detailed look at the generic 8051 processor facilities.

66 Smithbrook Kilns, Cranleigh, Surrey, GU6 8JJ, UK

Tel: +44(0)483 268999, Fax: +44(0)483 268397



VIDEOS ON ELECTRONICS

Everyday Electronics is pleased to announce the availability of a range of videos designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They should prove particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.

The first four videos available are:

- 1** *Electronics And You – Part 1: D.C. Series and parallel circuits and the use of a digital multimeter.* Running time approx. 51 mins.
Order code VT1 **£29.95 inc. VAT**

2 *Part 2: A.C. Coils, capacitors, transformers and other a.c. devices.*
Running time approx 62 mins.
Order code VT2 **£29.95 inc. VAT**

3 *Part 3: Semiconductors.* Basic semiconductor theory plus fifteen different semiconductor devices explained. Running time approx. 56 mins.
Order code VT3 **£29.95 inc. VAT**




4 *Part 4: Power Supplies.* A step by step look at how they work plus trouble shooting tips. Running time approx. 56 mins.
Order code VT4 **£29.95 inc. VAT**

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier.

To order see our Direct Book Service "Ordering Details" – the postage for tapes is the same as for our range of books and you can order tapes and books at the same time and pay only one lot of postage.

(All videos are to the UK PAL standard on VHS tapes)

£29.95
each

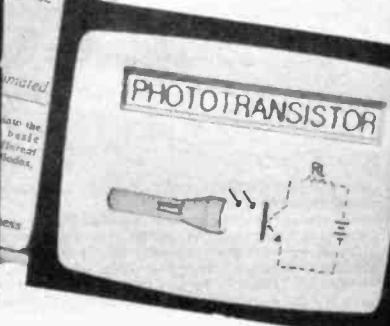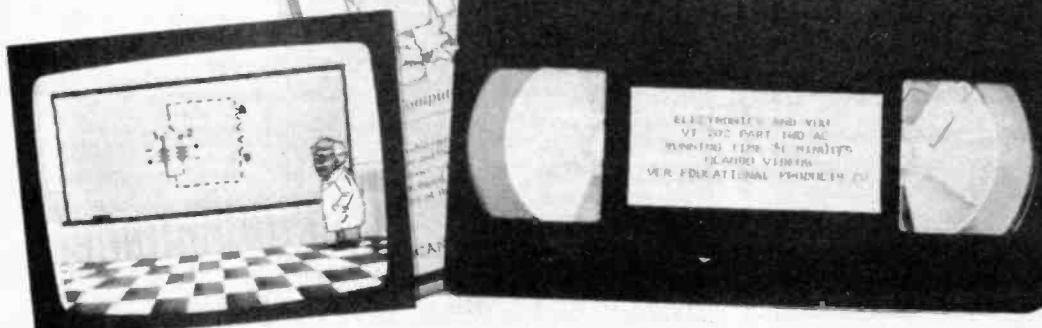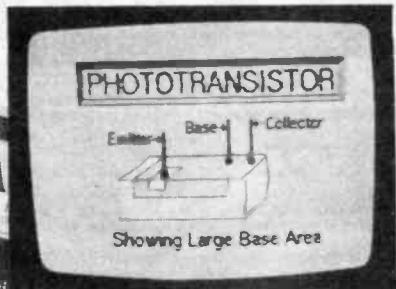

SPECIAL EVERYDAY ELECTRONICS BOOKS



ELECTRONICS TEACH-IN 88/89—INTRODUCING MICROPROCESSORS

Mike Tooley BA (published by *Everyday Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Micro-processors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering the most popular microprocessor chips.

An excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment.

80 pages (A4 size) Order code 11-88-89 £2.45

ELECTRONIC PROJECTS BOOK 1

Published by *Everyday Electronics* in association with Magenta Electronics.

Contains twenty of the best projects from previous issues of EE each backed with a kit of components. The projects are: Seashell Sea Synthesiser, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16K sideways Ram, Simple Short Wave Radio, Insulation Tester, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser

Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider — (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.

128 pages (A4 size) Order code EP1 £2.45

ELECTRONICS TEACH-IN No. 3 – EXPLORING ELECTRONICS (published by *Everyday Electronics*)

Owen Bishop

Another EE value for money publication aimed at students of electronics. The course is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

Exploring Electronics contains more than 25 useful projects, assumes no previous knowledge of electronics and is split into 28 easily digestible sections.

88 pages (A4 size) Order code 113 £2.45

ELECTRONICS TEACH-IN No. 4 INTRODUCING DIGITAL ELECTRONICS (published by *Everyday Electronics*)

Michael J. Cockcroft

Although this book is primarily a City & Guilds Introductory level course (726/301), approximately 80% of the information

forms a very basic introduction to electronics in general, it therefore provides an excellent introductory text for beginners and a course and reference book for GCSE students.

Full details on registering for C&G assessment, details of assessment centres, components required and information on the course in general are given.

The City & Guilds Introduction to module 726/301 reads: "A candidate who satisfactorily completes this module will have a competence to identify basic components and digital integrated circuits and connect them together to form simple working circuits and logic units." This provides an excellent introduction to the book.

112 pages (A4 size) Order code T14 £2.95

ELECTRONICS TEACH-IN No. 5 GUIDE TO BUILDING ELECTRONIC PROJECTS

Published by *Everyday Electronics*

Due to the demand from students, teachers and hobbyists we have put together a range of articles from past issues of *Everyday Electronics* that will assist those involved with the construction of electronic projects.

The book contains the complete *Project Development for GCSE* series.

Contents: Features – First Steps In Project Building; Building with Vero; Project Development for GCSE; Getting your Projects Working; Guide to Printed Circuit Boards; Choosing and Using Test Equipment – The Multimeter, The Oscilloscope, P.S.U.s, Logic Probes, Digital Frequency Meters, Signal Generators, etc; Data – Circuit Symbols; Component Codes; Resistors; Identifying Components; Capacitors; Actually Doing It – Understanding the Circuit Diagram, Component Codes, Mounting circuit boards and controls, Understanding Capacitors; Projects – Lie Detector; Personal Stereo Amplifier; Digital Experiments's Unit; Quizmaster, Siren Effects Unit; UV Exposure Unit; Low-cost Capacitance Meter; Personal Radar.

88 pages (A4 size) Order code T15 £2.95

EVERYDAY ELECTRONICS DATA BOOK

Mike Tooley BA (published by EE in association with PC Publishing)

This book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but it also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available "industry standard" components and devices.

A must for everyone involved in electronics!

266 pages Order code DATA £8.95

DIRECT BOOK SERVICE

The books listed have been selected by *Everyday with Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page. For another selection of books see next month's issue

ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

The principles of operation of the various types of test instruments are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of the instruments are also examined.

Everything from Audio oscillators, through R, C & L measurements (and a whole lot more) to Waveform Generators and testing Zeners. A truly comprehensive book for the hobbyist, student, technician and engineer.

206 pages Order code T109 £8.95

HOW TO TEST ALMOST EVERYTHING ELECTRONIC – 2nd EDITION

Jack Darr and Delton T. Horn

Describes electronic tests and measurements – how to make them with all kinds of test equipment, and how to interpret the results. New sections in this edition include logic probes, frequency counters, capacitance meters, and more. (An American book.)

190 pages Order code T2925 £9.05

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages Order code BP239 £2.95

MORE ADVANCED USES OF THE MULTIMETER

R. A. Penfold

This book is primarily intended as a follow-up to BP239, (see above), and should also be of value to anyone who already understands the basics of voltage testing and simple component testing. By using the techniques described in chapter 1 you can test and analyse the performance of a range of components with just a multimeter

(plus a very few inexpensive components in some cases). Some useful quick check methods are also covered.

While a multimeter is supremely versatile, it does have its limitations. The simple add-ons described in chapter 2 extended the capabilities of a multimeter to make it even more useful. The add-ons described include an active r.f. probe, a high resistance probe, an a.c. sensitivity booster, and a current tracer unit.

84 pages Order code BP265 £2.95

THE ILLUSTRATED DICTIONARY OF ELECTRONICS – 4th EDITION

Rufus P. Turner and Stan Gibilisco

With more than 27,000 terms used in electronics today, this collection is THE most comprehensive dictionary available. Including all practical electronics and computer terms, it is as up-to-date as the latest advances in the field itself! Tables and data on subjects most often consulted for projects and experiments are included. Other conversion tables include English/metric and metric/English conversions for units of energy, power and volume, and Fahrenheit/Celsius temperature conversion charts.

Setting this edition apart from other electronic dictionaries is its emphasis on illustration. Featuring more than complete definitions, this fourth edition includes over 450 detailed drawings and diagrams.

All entries are listed in alphabetical order. Abbreviations and initials are listed in sequence with whole words. All terms of more than one word are treated as one word. (An American book.)

648 pages Order code T2900 £23.95

ELECTRONICS – A "MADE SIMPLE" BOOK

G. H. Olsen

This book provides excellent background reading for our *Introducing Digital Electronics* series and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity.

330 pages Order code NE10 £4.95

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F.A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M. Bridges the gap between complicated technical theory, and "cut-and-tried" methods which may bring success in design but leave the experimenter unfulfilled. A strong

practical bias – tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-current Circuits, Passive Components, Alternating-current Circuits, Networks and Theorems, Measurements.

256 pages Order code BP53 £3.95

PRACTICAL DIGITAL ELECTRONICS HANDBOOK

Mike Tooley BA (published in association with *Everyday Electronics*)

The vast majority of modern electronic systems rely heavily on the application of digital electronics, and the *Practical Digital Electronics Handbook* aims to provide readers with a practically based introduction to this subject. The book will prove invaluable to anyone involved with the design, manufacture or servicing of digital circuitry, as well as to those wishing to update their knowledge of modern digital devices and techniques. Contents: Introduction to integrated circuits; basic logic gates; monostable and bistable devices; timers; microprocessors; memories; input and output devices; interfaces; microprocessor buses. Appendix 1: Data. Appendix 2: Digital test gear projects; tools and test equipment; regulated bench power supply; logic probe; logic pulser; versatile pulse generator; digital IC tester; current tracer; audio logic tracer; RS-232C breakout box; versatile digital counter/frequency meter. Appendix 3: The oscilloscope. Appendix 4: Suggested reading. Appendix 5: Further study.

208 pages Order code PC100 £6.95

ELECTRONICS-BUILD AND LEARN

R. A. Penfold

The first chapter gives full constructional details of a circuit demonstrator unit that is used in subsequent chapters to introduce common electronic components – resistors, capacitors, transformers, diodes, transistors, thyristors, fets and op amps. Later chapters go on to describe how these components are built up into useful circuits, oscillators, multivibrators, bistables and logic circuits.

At every stage in the book there are practical tests and experiments that you can carry out on the demonstrator unit to investigate the points described and to help you understand the principles involved. You will soon be able to go on to more complex circuits and tackle fault finding logically in other circuits you build.

120 pages Order code PC103 £6.95

AUDIO AND MUSIC

LOUDSPEAKERS FOR MUSICIANS

Vivian Capel

This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages

Order code BP297

£3.95

MAKE MONEY FROM HOME RECORDING

Clive Brooks

Now that you've spent a fortune on all that recording gear, MIDI and all, wouldn't it be nice to get some of it back? Well here's the book to show you how.

It's packed with money making ideas, any one of which will recoup the price of the book many times over. Whether you have a fully fledged recording studio at home, or just a couple of stereo cassette recorders and a microphone, you'll be able to put the ideas in this book into practice and make money.

105 pages

Order code PC104

£5.95

INTRODUCTION TO DIGITAL AUDIO

(Second Edition)

Ian Sinclair

Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring digital audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages

Order code PC102

£6.95

SYNTHESIZERS FOR MUSICIANS

R. A. Penfold

Modern synthesizers are extremely complex, but they mostly work on principles that are not too difficult to

understand. If you want to go beyond using the factory presets or the random poking of buttons, this is the book for you.

It covers the principles of modern synthesis - linear arithmetic as used by Roland, phase distortion (Casio), Yamaha's frequency modulation, and sampling - and then describes how the instruments are adjusted to produce various types of sound - strings, brass, percussion, etc. The theoretical side of synthesis is treated in an easy to understand way - the technical information being restricted to what you need to know to use your instrument effectively.

168 pages

Order code PC105

£6.95

AUDIO

F. A. Wilson, C. G. I. A., C. Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Analysis of the sound wave and an explanation of acoustical quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapter on audio systems - amplifiers, oscillators, disc and magnetic recording and electronic music.

320 pages

Order code BP111

£3.95

CIRCUITS AND DESIGN

REMOTE CONTROL HANDBOOK

Owen Bishop

Remote control systems lend themselves to a modular approach. This makes it possible for a wide range of systems, from the simplest to the most complex, to be built up from a number of relatively simple modules. The author has tried to ensure that, as far as possible, the circuit modules in this book are compatible with one another. They can be linked together in many different configurations to produce remote control systems tailored to switch a table lamp on and off, or to operate an industrial robot, this book should provide the circuit you require.

226 pages

Order code BP241

£3.95

COIL DESIGN AND CONSTRUCTION MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now rather old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages

Order code 160

£2.50

30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1

R. A. Penfold

Each project, which is designed to be built on a "Verobloc" breadboard, is presented in a similar fashion with a brief circuit description, circuit diagram, component layout diagram, components list and notes on construction and use where necessary. Whenever possible, the components used are common to several projects, hence with only a modest number of reasonably inexpensive components, it is possible to build in turn, every project shown. Recommended by BICC-Vero.

160 pages

Order code BP107

£2.95

BOOK 2 -

All projects use CMOS I.C.s. but the items on component identification etc., are not repeated from Book 1.

160 pages

Order code BP113

£2.25

ELECTRONIC CIRCUITS HANDBOOK

Michael Toohey BA

This book aims to explode two popular misconceptions concerning the design of electronic circuits: that only those with many years of experience should undertake circuit design and that the process relies on an understanding of advanced mathematics. Provided one is not too ambitious, neither of these popularly held beliefs is true.

Specifically, this book aims to provide the reader with a unique collection of practical working circuits together with supporting information so that circuits can be produced in the shortest possible time and without recourse to theoretical texts.

Furthermore, information has been included so that the circuits can readily be modified and extended by readers to meet their own individual needs. Related circuits have been grouped together and cross-referenced within the text (and also in the index) so that readers are aware of which circuits can be readily connected together to form more complex systems. As far as possible, a common range of supply voltages, signal levels and impedances has been adopted.

As a bonus, ten test gear projects have been included. These not only serve to illustrate the techniques described but also provide a range of test equipment which is useful in its own right.


277 pages

Temporarily out of print

AUDIO IC CIRCUITS MANUAL

R. M. Marston

A vast range of audio and audio-associated I.C.s. are readily available for use by amateur and professional design engineers and technicians. This manual is a guide to the most popular and useful of these devices, with over 240 diagrams. It deals with I.C.s. such as low frequency linear amplifiers, dual pre-amplifiers, audio power amplifiers, charge coupled device delay lines, bar-graph display drivers, and power supply regulators, and shows how to use these devices in circuits ranging

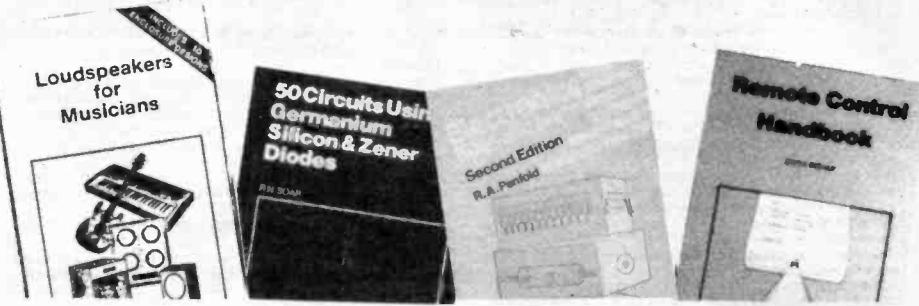

from simple signal conditioners and filters to complex graphic equalizers, stereo amplifier systems, and echo/reverb delay line systems etc.

168 pages

Order code NE13

£12.95

HOW TO DESIGN ELECTRONIC PROJECTS

R. A. Penfold

The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics. Hints on designing circuit blocks to meet your special requirements are also provided.

128 pages

Temporarily out of print

50 CIRCUITS USING GERMANIUM SILICON AND ZENER DIODES

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most simple and inexpensive of components - the diode. Includes the use of germanium and silicon signal diodes, silicon rectifier diodes and Zener diodes, etc.

64 pages

Order code EP36

£1.95

DESIGNING WITH LINEAR ICs

G. C. Loveday

A book that deals with the design of the vital area of analog circuitry covering design with modern linear integrated circuit devices. The first chapter introduces the reader to important design techniques, test strategies, layout, and protection and also includes a section on the use of a typical CAD tool. There are separate chapters that cover in depth the use of op-amps, comparators and timers each with detailed design examples and reader exercises. A final chapter brings all the previous work together in a number of complete design problems with fully worked solutions. The text is essentially non-mathematical and is supported by many diagrams.

64 pages

Order code BM3

Special Price £5.00

SALE PRICE

TIMER/GENERATOR CIRCUITS MANUAL

R. M. Marston

This manual is concerned mainly with waveform generator techniques and circuits. Waveform generators are used somewhere or other in most types of electronic equipment, and thus form one of the most widely used classes of circuit. They may be designed to produce outputs with sine, square, triangle, ramp, pulse, staircase, or a variety of other forms. The generators may produce modulated or unmodulated outputs, and the outputs may be of single or multiple form.

Waveform generator circuits may be built using transistors, op-amps, standard digital I.C.s, or dedicated waveform or "function" generator I.C.s.

The manual is divided into eleven chapters, and presents over 300 practical circuits, diagrams and tables. The subjects covered include: Basic principles; Sine wave generators; Square wave generators; Pulse generator circuits; "Timer IC" generator circuits; Triangle and sawtooth generators; Multi-waveform generation; Waveform synthesizer I.C.s; Special waveform generators; Phaselocked loop circuits; Miscellaneous "555" circuits.

267 pages

Order code NE18

£12.95

OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston

A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the I.C.s. and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages

Order code NE14

£12.95

POPULAR ELECTRONIC CIRCUITS - BOOK 1

POPULAR ELECTRONIC CIRCUITS - BOOK 2

R. A. Penfold

Each book provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed construction information. Any special setting-up procedures are described.

BOOK 1 160 pages

Order code BP40

£2.95

BOOK 2 160 pages

Order code BP98

£2.95

CMOS CIRCUITS MANUAL

R. M. Marston

Written for the professional engineer, student or enthusiast. It describes the basic principles and characteristics of these devices and includes over 200 circuits.

All the circuits have been designed, built and fully evaluated by the author; all use inexpensive and internationally available devices.

187 pages

Order code NE12

£12.95

Note - our postage charge
is the same for one book or
one hundred books!

OPTOELECTRONICS CIRCUITS MANUAL

P. M. Marston



PROJECT CONSTRUCTION

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.S.

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.

80 pages

Order code BP21

£2.50

ELECTRONIC SCIENCE PROJECTS

O. Bishop

These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained.

144 pages

Temporarily out of print

magazines and books. Also includes examples in the form of simple projects.

112 pages

Order code 227

£1.95

HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

96 pages

Temporarily out of print

£2.50

BEGINNER'S GUIDE TO BUILDING ELECTRONICS PROJECTS

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in

TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included: AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Millivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.

104 pages

Order code BP248

£2.95

DATA AND COMPONENT IDENTIFICATION

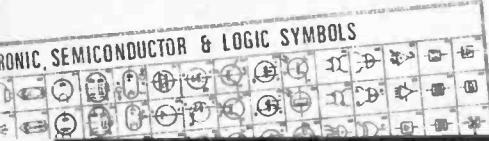


CHART OF RADIO, ELECTRONIC, SEMICONDUCTOR AND LOGIC SYMBOLS

M. H. Banani B.Sc. (Eng.)

Illustrates the common, and many of the not-so-common, radio, electronic, semiconductor and logic symbols that are used in books, magazines and instruction manuals, etc., in most countries throughout the world.

Chart

Order code BP27

£0.95

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

A. Michaels

Helps the reader to find possible substitutes for a popular selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.

320 pages

Order code BP85

£3.95

RADIO, TV, SATELLITE

AN INTRODUCTION TO RADIO DXING

R. A. Penfold

Anyone can switch on a short wave receiver and play with the controls until they pick up something, but to find a particular station, country or type of broadcast and to receive it as clearly as possible requires a little more skill and knowledge. The object of this book is to help the reader to do just that, which in essence is the fascinating hobby of radio DXing.

112 pages

Order code BP91

£1.95

worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.

72 pages

Order code BP278

£3.50

EXPERIMENTAL ANTENNA TOPICS

H. C. Wright

Although nearly a century has passed since Marconi's first demonstration of radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily

NEWNES SHORTWAVE LISTENING HANDBOOK

Joe Pritchard G1UQW

Part One covers the "science" side of the subject, going from a few simple electrical "first principles", through a brief treatment of radio transmission methods to simple receivers. The emphasis is on practical receiver designs and how to build and modify them, with several circuits in the book.

Part Two covers the use of sets, what can be heard, the various bands, propagation, identification of stations, sources of information, QSLing of stations and listening to amateurs. Some computer techniques, such as computer Morse decoding and radio teletype decoding are also covered.

224 pages

Order code NE16

£14.95

COMPUTING

The subjects covered include: PC overview; Memory upgrades; Adding a hard disk drive; Adding a floppy disk drive; Display adaptors and monitors; Fitting a maths co-processor; Keyboards; Ports; Mice and digitisers; Maintenance (including preventative maintenance) and Repairs, and the increasingly popular subject of d.i.y. PCs.

156 pages

Order code BP271

£4.95

AN INTRODUCTION TO PROGRAMMING THE BBC MODEL B MICRO

R. A. & J. W. Penfold

Written for readers wanting to learn more about programming and how to make best use of the incredibly powerful model B's versatile features. Most aspects of the BBC Micro are covered, the omissions being where little could usefully be added to the information provided by the manufacturer's own manual.

144 pages

Order code BP139

£1.95

AN INTRODUCTION TO 6502 MACHINE CODE

R. A. & J. W. Penfold

No previous knowledge of microprocessors or

machine code is assumed. Topics covered are: assembly language and assemblers, the register set and memory, binary and hexadecimal numbering systems, addressing modes and the instruction set, and also mixing machine code with BASIC. Some simple programming examples are given for 6502-based home computers like the VIC-20, ORIC-1/Atmos, Electron, BBC and also the Commodore 64.

112 pages

Order code BP147

£2.95

The PRE-BASIC BOOK

F. A. Wilson, C.G.I.A., C.ENG., F.I.E.E., F.I.E.R.E., F.B.I.M.

Another book on BASIC but with a difference. This one does not skip through the whole of the subject and thereby leave many would-be programmers floundering but instead concentrates on introducing the technique by looking in depth at the most frequently used and more easily understood computer instructions. For all new and potential micro users.

192 pages

Order code BP146

£2.95

DIRECT BOOK SERVICE ORDERING DETAILS

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.50 for all countries outside Europe, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to Direct Book Service or credit card details (including card expiry date), Visa or Mastercard (Access) – minimum credit card order is £5 – quoting your name and address, the order code and quantities required to DIRECT BOOK SERVICE, 33 GRAVEL

HILL, WIMBORNE, DORSET BH21 1RW (mail order only).

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of Everyday with Practical Electronics) before ordering from old lists.

Note – our postage charge is the same for one book or one hundred books!

MORE BOOKS NEXT MONTH

DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD.

BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or in next months issue of *Everyday with Practical Electronics* (the books with a BP prefix to the order code are Babani books).

Many readers have asked us to also supply various other Babani books, which have a reputation for value for money. Our customers tell us they appreciate our speedy service and low postage charge and they

would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (75p for UK p&p no matter how many books you buy). We are pleased to be able to respond; with the aid of Michael Babani (M.D.) we are now able to meet all your requirements for their books. If it's Babani and in print we can supply it. Babani presently list over 180 different technical titles those not described in detail on the previous Direct Book Service pages or in next months issue are listed below:

Code	Title	Price	Code	Title	Price	Code	Title	Price
208	Practical Stereo & Quadrophony Handbook	£0.75	BP145	25 Simple Tropical and MW Band Aerials	£1.75	BP250	Programming in FORTRAN 77	£4.95
214	Audio Enthusiast's Handbook	£0.85	BP148	Computer Terminology Explained	£1.95	BP251	Computer Hobbyists Handbook	£5.95
219	Solid State Novelty Projects	£0.85	BP149	A Concise Introduction to the Language of BBC Basic	BP258	Learning to Program in C	£4.95	
225	A Practical Introduction to Digital ICs	O.O.P.	BP152	An introduction to Z80 Machine Code	£1.95	BP259	A Concise Introduction to UNIX	£2.95
BP28	Resistor Selection Handbook	£0.80	BP153	An Introduction to Programming the Amstrad CPC 464 & 664	BP260	A Concise Introduction to OS/2	£2.95	
BP37	50 Projects using Relays, SCRs and TRIACs	£2.95	BP154	An Introduction to MSX BASIC	BP261	A Concise Introduction to Lotus 1-2-3 (Revised Edition)	£3.95	
BP39	50 (FET) Field Effect Transistor Projects	£2.95	BP156	An Introduction to QL Machine Code	BP262	A Concise Introduction to Wordperfect (Revised Edition)	£3.95	
BP44	555 Projects	£2.95	BP157	How to Write ZX Spectrum & Spectrum + Games Programs	BP263	A Concise Introduction to dBASE	£3.95	
BP48	Electronic Projects for Beginners	£1.95	BP158	An Introduction to Programming the Commodore 64 & Plus 4	BP264	A Concise Advanced User's Guide to MS-DOS	£3.95	
BP49	Popular Electronic Projects	£2.50	BP159	How to Write Amstrad CPC464 Games Programs	BP265	An Introduction to Desktop Publishing	O.O.P.	
BP56	Electronic Security Devices	O.O.P.	BP161	Into the QL Archive	BP270	A Concise Introduction to Symphony	£5.95	
BP58	50 Circuits Using 7400 Series IC's	£2.50	BP162	Counting on QL Abacus	BP272	Interfacing PC's & Compatibles	£3.95	
BP63	Alternating Current Theory (Elements of Electronics - Book 2)	£3.50	BP171	Easy Add-on Projects for Amstrad CPC 464, 664, 6128 and MSX Computers	BP273	Practical Electronic Sensors	£4.95	
BP68	Choosing and Using Your Hi-Fi	£1.65	BP174	More Advanced Electronic Music Projects	BP274	A Concise Introduction to SuperCalc	£3.95	
BP74	Electronic Music Projects	O.O.P.	BP175	How to Write Word Games Programs for the Amstrad CPC 464, 664 and 6128	BP276	Short Wave Superhet Receiver Construction	£2.95	
BP76	Power Supply Projects	£2.50	BP182	MIDI Projects	BP277	High Power Audio Amplifier Construction	£3.95	
BP78	Practical Computer Experiments	£1.75	BP187	A Practical Reference Guide to Word Processing on the Amstrad PCW8256 and PCW8512	BP279	A Concise Introduction to Excel	£3.95	
BP84	Digital IC Projects	£1.95	BP190	More Advanced Electronic Security Projects	BP280	Getting the Most From Your PC's Hard Disc	£3.95	
BP86	An Introduction to BASIC Programming Techniques	£1.95	BP191	Simple Application of the Amstrad CPCs for Writers	BP283	A Concise Introduction to SmartWare II	£4.95	
BP90	Audio Projects	£2.50	BP192	More Advanced Power Supply Projects	BP284	Programming in QuickBASIC	£4.95	
BP94	Electronic Projects for Cars and Boats	£1.95	BP193	LOGO for Beginners	BP286	A Reference Guide to Basic Electronics Terms	£5.95	
BP95	Model Railway Projects	£2.95	BP196	BASIC & LOGO in Parallel	BP287	A Reference Guide to Practical Electronics Terms	£5.95	
BP97	IC Projects for Beginners	£1.95	BP197	An Introduction to the Amstrad PC's	BP288	A Concise Introduction to Windows 3.0	£3.95	
BP99	Mini-matrix Board Projects	£2.50	BP198	An Introduction to Antenna Theory	BP291	A Concise Introduction to Ventura	£3.95	
BP106	Modern Op-amp Projects	£1.95	BP199	A Concise Introduction to GEM	BP292	Public Address Loudspeaker Systems	£3.95	
BP109	The Art of Programming the 1K ZX81	£1.95	BP200	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 1: Language	BP293	An Introduction to Radio Wave Propagation	£3.95	
BP114	The Art of Programming the 16K ZX81	£2.50	BP201	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 2: Graphics and Disk Files	BP294	A Concise Introduction to Microsoft Works	£4.95	
BP122	Audio Amplifier Construction	£2.95	BP205	Digital Audio Projects	BP298	A Concise Introduction to the Mac System & Finder	£3.95	
BP125	25 Simple Amateur Band Aerials	£1.95	BP206	Musical Applications of the Atari ST's	BP299	Practical Electronic Filters	£3.95	
BP126	BASIC & PASCAL in Parallel	£1.50	BP207	More Advanced MIDI Projects	BP302	A Concise User's Guide to Lotus 1-2-3 Release 3.1	£3.95	
BP128	20 Programs for the ZX Spectrum & 16K ZX81	£1.95	BP208	More Advanced Test Equipment Construction	BP303	Understanding PC Software	£4.95	
BP129	An Introduction to Programming the ORIC-1	£1.95	BP209	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 1: Language	BP307	A Concise Introduction to QuarkXPress	£4.95	
BP132	25 Simple SW Broadcast Band Aerials	£1.95	BP210	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 2: Graphics and Disk Files	BP311	An Introduction to Scanners and Scanning	£4.95	
BP133	An Introduction to Programming the Dragon 32	£1.95	BP211	4-Channel Auto-Fader Interface	BP312	An Introduction to Microwaves	£3.95	
BP136	25 Simple Indoor and Window Aerials	£1.75	BP212	Electron A/D Interface	BP313	A Concise Introduction to Sage	£3.95	
BP137	BASIC & FORTRAN in Parallel	£1.95	BP213	Spectrum EPROM Programmer	BP314	A Concise Introduction to Quattro Pro	£4.95	
BP138	BASIC & FORTH in Parallel	£1.95	BP214	Programmable Pocket Timer	BP318	A Concise User's Guide to MS-DOS 5	£4.95	
BP143	An Introduction to Programming the Atari 600/800XL	£1.95	BP215	Electronic Spirit Level	BP325	A Concise User's Guide to Windows 3.1	£4.95	
BP144	Further Practical Electronics Calculations & Formulae	O.O.P.	BP216	Distance Recorder				
			BP217	Xenon Beacon				
			BP218	Probe Pocket Treasure Finder				
			BP219	Power Supplies: Fixed Voltage				
			BP220	Variable Voltage				
			BP221	Music on Hold				
			BP222	Power Supplies - 25V 700mA				
			BP223	30V 1A				
			BP224	EE Seismograph - Control				
			BP225	Detector				
			BP226	Lego/Logo & Spectrum				
			BP227	Wash Pro				
			BP228	Logo/lego & Sepctrum Interface				
			BP229	Biofeedback Monitor - Front End Processor				
			BP230	EEG Electrode Impedance Meter				
			BP231	Biofeedback Signal Generator				

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **The PCB Service, Everyday with Practical Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH**. Cheques should be crossed and made payable to *Everyday with Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail.

Please check price and availability in the latest issue.

Boards can only be supplied on a payment with order basis.

SALE! ½ PRICE

(Just send half the price shown, while stocks last.)
PCBS ON OPPOSITE PAGE PRICES AS SHOWN

PROJECT TITLE	Order Code	Cost
Video Guard Alarm	FEB 87	£3.80
Computer Buffer/Interface	MAR 87	£3.32
Fridge Alarm	MAY 87	£3.00
Monomixer	JULY 87	£4.75
Noise Gate	SEP 87	£4.41
Game Timer	FEB 88	£3.55
Multi-Chan Remote Light Dim Relay/Decoder	JUNE 88	£4.86
Power Supply	603	£3.00
Video Wiper	JULY 88	£6.75

PROJECT TITLE	Order Code	Cost
Tea Tune Thermostat	AUG 88	£3.00
Time Switch	614	£4.84
Suntan Timer	610	£3.07
Car Alarm	615	£3.12
Eeprom Eraser	OCT 88	£4.07
Doorbell Delay	NOV 88	£3.56
Infra-Red Object Counter (Set)	622/3/4	£9.28
Downbeat Metronome	DEC 88	£4.84
Phasor	631	£5.64
Continuity Tester	FEB 89	£2.67
Mini PSU	636	£3.23
Sound-to-Light Interface	MAR 89	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel: Main Board	APR 89	£9.20
Remote Interface (4 bds)	633	£4.59
4-Channel Auto-Fader Interface	642	£6.80
Electron A/D Interface	MAY 89	£4.84
Spectrum EPROM Programmer	JUNE 89	£7.87
Programmable Pocket Timer	JULY 89	£3.82
Electronic Spirit Level	AUG 89	£3.85
Distance Recorder	651	£5.23
Xenon Beacon	SEP 89	£4.13
Probe Pocket Treasure Finder	653	£4.12
Power Supplies: Fixed Voltage	654	£4.08
Variable Voltage	655	£4.48
Music on Hold	OCT 89	£3.85
Power Supplies - 25V 700mA	656	£4.35
30V 1A	657	£4.55
EE Seismograph - Control	658	£4.08
Detector	659	£4.22
Lego/Logo & Spectrum	660	£6.49
Wash Pro	NOV 89	£3.83
Logo/lego & Sepctrum Interface	664	£5.60
Biofeedback Monitor - Front End Processor	661	£4.52
EEG Electrode Impedance Meter	DEC 89	£4.56
Biofeedback Signal Generator	JAN 90	£4.08

PCB SERVICE

See opposite page for ordering details.

PROJECT TITLE	Order Code	Cost
Quick Cap Tester	668	£3.92
Weather Stn: Anemom. - Freq./Volt Board Optional Display	670	£3.94
Wind Direction	669	£3.73
System Power Supply	673/674	£4.22
Prophet In-Car Ioniser	675	£3.59
	676	£3.18
Weather Stn: Display Driver Display and Sensor	672 & 678	£4.22
Fermostat Mk2	671	£4.47
Superhet Broadcast Receiver/Tuner/Amp	677	£4.28
Stereo Noise Generator	679/680	£4.22
Digital Experimenter's Unit - Pulse Generator Power Supply	681	£4.24
Enlarger Timer	682	£4.46
Weather Stn: Rainfall/Sunlight Display Rainfall Sen and Sunlight Sen	683	£3.66
	684	£4.28
	685	£4.27
	686/687	£4.16
Amstrad Speech Synthesiser	689	£4.68
80 Metre Direct Conversion Radio	691	£4.95
Mains Appliance Remote Control	694	£6.61
Encoder Board A	695	£4.78
Encoder Board B	696	£4.15
The Tester		
Mains Appliance Remote Control	697	£4.55
Mains ON/OFF Decoder (5 or more 697's ordered together £3.25 each)	698	£3.94
Simple Metronome	699, 700	£10.95
Hand Tally: Main Bd and Display Bd	701	£4.10
Alarm Bell Time-Out		
Mains Appliance Remote Control	702	£5.20
Temperature Controller (p.c.b. only)		
Ghost Waker	703	£4.32
Frequency Meter	704	£5.25
Freq. Meter/Tachometer	705	£3.98
EE Musketeer (TV/Video/Audio)	706	£5.78
Colour Changing Christmas Lights	707	£4.39
Microcontroller Light Sequencer	708/709	£10.90
Versatile Bench Power Supply Unit	710	£4.24
Teach-In '91, Part 1 - L200 Module	711	£3.93
Dual Output Module	712	£4.13
LM723 Module	713	£4.21
Spatial Power Display	714	£5.33
Amstrad PCW Sound Generator	715	£5.03
Teach-In '91, Part 2 - G.P. Transistor Amp	717	£3.77
Dual Op.Amp Module	718	£3.83
Intercom (Teach-In '91 Project 2)	719	£4.41
Analogic Test Probe	720	£3.24
MARC Phone-In	721	£6.87
Teach-In '91 Part 3 - TBA820M Amplifier	723	£4.05
High Quality Power Amp	724	£4.93
Bench Amplifier (Teach-In '91 Project 3)	725	£4.45
Gingernut 80m Receiver	726/7/8	£3.06 per board
R.F. section (726), Voltage Regulator (727)		all 3 together £8.16
Audio Amplifier (728)		
Pocket Tone Dialler	729	£4.36
Battery To Mains Inverter	730	£4.97
Simple Basic Alarm	731	£4.50
Car Code Lock (pair)	732a/b	£4.69
Teach-In '91 Part 4 -	733	£4.39
Sinusoidal Oscillator	734	£4.15
8038 Oscillator	735	£4.72
Waveform Generator (Teach-In '91 Project 4)		
Humidity Tester	716	£4.97
Model Train Controller (double-sided)	736	£9.75
Electronic Die (Teach-In '91 Project 5)	737	£4.93
Teach-In '91 Part 5 - Digital Counter Module	738	£4.35
Modular Disco Lighting System	739	£5.91
Switched Power Output Module	740	£4.05
Digital LCD Thermostat-Control Board	£5 for pair	
-Power/Relay Board	741	£3.76
Pulse Generator (Teach-In '91 Project 6)	742	£4.97
Teach-In '91 Part 6 - Timer Module	743	£4.62
Digilogue Car Tachometer	744	£5.63
Modular Disco Lights - Simple Chaser	745	£5.00
Sweeper Module	746	£5.17
Automatic Light Control - PSU Board	747	£4.88
Logic Board	748	£5.17
Radio Receiver (Teach-In '91 Project 7)	749	£4.57
Teach-In '91 Part 7 - R.F. Amplifier Module	750	£4.23

PROJECT TITLE	Order Code	Cost
Modular Disco Lights - Masterlink	JULY '91	752
Ultrasonic Proximity Meter	753/754	£7.06
Display Unit (753) & Sensor Unit (754)		
Disco Lights (Teach-In '91 Project 8)	755	£4.54
PSU and Pre-amplifier	756	£11.00
Low, Mid, High Filter/Triac (set of 3 boards)	757	£4.24
Teach-In '91 Part 8 - Solid State Switch Module		
Mod. Disco Lights - Pattern Gen	AUG '91	760
Teach-In '91 Part 8-Light Sensitive Switch	761	£4.74
Opto-Link (Teach-In '91 Project 9) - Transmitter	762	£4.85
Receiver	763	£4.88
Portable PESt Scarer	764	£3.77
Capacitance Meter	SEP '91	751
Modular Disco Lights - Dimmer Interface	765	£8.17
Mod. Disco Lights	OCT '91	767
VU Sound Module (Double-sided)	768	£8.68
UV Exposure Unit	769	£6.95
PC-Scope Interface - Main Board	770	£5.96
Expansion Plug (Double-sided)		
Mod. Disco Lights	NOV '91	771
Superchaser (Double-sided)	772	£6.91
Supersweep (Double-sided)	773	£8.26
Bicycle Alarm	774	£5.01
Darts Scorer		£7.90
Knockerbox	DEC '91	775
Signal Generator - Main Board	776	£5.35
PSU	777	£7.46
Mind Machine - Main Board	778	£4.73
Auto Nightlight	779	£7.00
Mind Machine - Programmer Board	JAN '92	780
Transistor Checker	781	£5.03
Stepping Motor Driver/Interface	782	£10.39
Micro-Sense Alarm	783	£4.42
Telesound	FEB '92	784
Programmable Timer	785	£4.66
Auto Garage Light	MAR '92	786
Versatile BBC Computer Interface	787	£6.10
Economy Seven Timer	788	£11.59
Sonic Continuity Tester	APR '92	789
Telephone Ringer	790	£5.20
Experimental Weighing Scale	MAY '92	792
12V Drill Charger/PSU (both boards)	793	£5.17
Digital Servo Interface	JUNE '92	791
Tie Pulser	794	£5.31
CCD Reverb Unit	795	£5.19
Switch-Mode Power Supply	796	£6.39
UV Exposure Timer	JULY '92	797
Cricket Game	798	£7.01
Quick Prom	799	£6.77
Gas Alarm	AUG '92	800
Dual Metronome	801	£5.61
Ultrasonic Tape Measure	SEP '92	802
Quicktest	803	£4.82
Extended Range Capacitance Meter	OCT '92	804
Whistle Switch	805	£5.63
Traffic Lights System	806	£4.89
Mini Lab	NOV '92	MINI LAB
EPE Altimet (Altimeter)	807	£14.95
Personal Stereo Amplifier	808	£6.30
Inverter Daughter Board	809	£6.47
		£3.00

REPORTING

AMATEUR RADIO

Tony Smith G4FAI

WHAT'S IN A NAME?

From the earliest days, radio amateurs in the United States have been known as "radio hams", or simply "hams", although amateurs in some countries have resisted the term for various reasons, preferring to be known as "radio amateurs". Some are simply resisting the spread of "Americanisms", and others see it as a derogatory term, wrongly implying a less than satisfactory level of competence.

There are any number of different explanations of the origin of the term. One version credits three amateurs whose combined initials spelt out the word HAM to provide their station's call-sign. This particular station is said to have been discussed by Congress when considering a Wireless Regulations Bill in 1911, and nationwide publicity of the proceedings resulted in the term being used from that time on to describe all amateur radio stations.

Another version describes how *Home Amateur Mechanic* magazine, in the early 1900's, published details of how to build the "Home Amateur Mechanic" (HAM for short) radio. Thus, those who built and used these sets became known as HAM radio operators.

A less complimentary explanation is that landline Morse operators used the word to describe inexperienced or poor operators. I have a copy of *The Telegraph Instructor* by G. M. Dodge, proprietor of Dodge's Institute of Telegraphy in Valparaiso, Indiana, 4th edn. 1908, for instance, which defines a "ham" (or alternatively a "plug") as a telegraph operator who is not proficient. It has been suggested that the professionals extended this term to apply to the new amateur radio operators who were trying to emulate their skills.

SKILLED INVOLVEMENT

There are any number of other sug-

amateur radio operator. This policy was revoked early this year after taking into account "the increased use, public understanding and acceptance of the expression to denote a radio amateur without any derogatory intent; the meanings of 'ham' and 'amateur' in the Australian Macquarie dictionary; and the need to explain amateur radio in terms easily understood by the public and so raise their awareness of our hobby."

Having said that, the WIA added a conciliatory note for the benefit of the "anti-hams" to the effect that it was not actively advocating the use of the word "ham", but was simply no longer objecting to people using it when describing an amateur radio operator.

ANNUAL REPORT

The 1991/92 Annual Report of the Radiocommunications Agency, as ever, covers the whole range of the Agency's activities, national and international, involving many different types of radio service from amateur to popular radio and TV broadcasting, including technical issues, law enforcement, and much more. Space permits reference here only to hobby radio but a free copy of the full report can be obtained from the RA Information and Library Service, Tel: 071-215 2352.

In the year under review, a contract for amateur licence distribution was awarded to Subscription Services Ltd (SSL), a subsidiary of the Post Office, the aim of which was to achieve cost savings and an improved licence issue service.

The Agency and the Radio Society of Great Britain have been working to improve the management of the amateur repeater network and a new licensing procedure has been introduced. A scheme for reporting interference on the amateur bands to the Agency has also been established to some

saw the launch of (Novice) Licence, rage young people and the first licences onally by John Red- or Corporate Af- now aims to improve tributions have been tated parties about the ing course and the

telecommunications cy has sought views radio community on third party traffic by cy continues to spon- teur of the Year Award, e given in this column, h 1992, there were

33,280 Amateur Radio "A" Licences, 27,738 "B" Licences, 46 Novice "A" licences, and 378 Novice "B" Licences, representing an increase of 558 in the total number compared with the previous year.

The Radio Investigation Service continued to investigate interference and other problems over the whole range of licensed transmissions covered by the Agency. Four amateurs were prosecuted and convicted for activities contravening the licence regulations, and warning letters were sent to three others.

Virtually all amateur radio information sheets published by the Agency were revised during 1991/92 and of particular interest to those considering taking up the hobby is RA 190 *How to become a Radio Amateur* - March 1992, available free of charge by telephoning 071-215 2072 (24-hour answerphone service).

In the CB field, a consultative exercise confirmed the view of users that CB should continue to be a licensed service and licensing was centralised through SSL. The new arrangements are expected to save some £200,000 which would otherwise have had to be recovered by increasing the licence fee.

As at 31 March 1992, there were 64,944 CB licences on issue compared with 69,803 the previous year. 112 persons were prosecuted and convicted for licence offences and 655 warning letters were sent out. A revised set of CB information sheets has been published and these are available from the Library Service, as above.

An intriguing implication of the licence statistics suggests that if the present trend continues the number of amateur licences next year may well exceed the number of CB licences on issue. This compares dramatically with the situation following the introduction of CB in the UK when the number of licences surged initially to around a quarter of a million.

AMATEUR SSB ENHANCER

A recently unveiled amateur radio version of its Link-Plus digital signal processing technology, called the MULE (Multi-Use Link Enhancer), is claimed by Link Plus Corp. of Columbia, Maryland, USA, to eliminate most noise and interference from single sideband voice communications, thus producing a significant boost in effective signal strength.

In 18 separate tests, carried out on three days, over an 1800 mile path under a variety of transmission conditions, Link-Plus processing produced an average 22dB improvement in HF-SSB signal-to-noise ratio. In layman's terms, the unprocessed signal had, on average, 160 times more noise content than the Link-Plus signal.

The MULE connects to any HF radio by external cables, but at \$2,995 it is probably beyond the reach of most amateurs at the present time. (*W5YI Report*).

NATIONAL
COLLEGE OF
TECHNOLOGY

DISTANCE LEARNING COURSES

The National College of Technology offer a range of packaged learning short courses for study at home or in an industrial training environment which carry national BTEC awards. Study can commence at any time and at any level enabling you to create a study routine to fit around existing commitments. Courses on offer include:

- Analogue Electronics
- Digital Electronics
- Fibre/Optoelectronics
- Programmable Logic Controllers

Tutor support and BTEC certification are available as options with no travelling or college attendance required. These very popular courses which are ideal for vocational training contain workbooks, audio cassette lecturettes, PCB's, instruments, tools, components and leads as necessary to support the theoretical and practical training. Whether you are a newcomer to electronics or have some experience and simply need an update or certification, there is probably a distance learning course ready for you. Write or telephone for details to:

National College of Technology
NCT Ltd., PO Box 11
Wendover, Bucks
Tel: (0296) 624270

LEDs 3mm or 5mm red or green 6p each, yellow 1p each. High intensity red, green or yellow, 5p, 20p each.

Cable ties 1p each, £5.95 per 1000, £49.50 per 10,000.

Stepper motor 4 phase 12V 7.5° step 50 ohms

SAA1027 stepping motor driver chip... £3.95

FM Transmitter kit, good quality sound... £8.60

High quality photo resist copper clad epoxy glass boards

Dimensions single sided double sided £0.95 £1.07

3x4 inches £2.40 £2.68

6x8 inches £5.37

12x12 inches £10.66

Rechargeable Batteries

AA (HP7) 500mA... £0.99

AA 700mA... £1.35

C 2Ah with solder tags... £3.60

D 4Ah with solder tags... £4.95

1/2AA with solder tags... £1.55

AAA (HP16) 180mAh... £1.75

AA 500mAh with solder tags... £1.55

C (HP11) 1.8AH... £2.20

D (HP2) 1.2AH... £2.60

PP3 8.4V 110mA... £4.95

Sub C with solder tags... £2.50

1/3 AA with tags (Philips CT)... £1.95

Standard charger, charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours + 1xPP3 (1.2, 3 or 4 cells may be charged at a time)... £5.95

High power charger, as above but charges the Cs and Ds in 5 minutes. AAs, Cs and Ds must be charged in 2s or 4s... £10.95

Special offers - please check for availability

F cells 32da x 87mm... £3.95

F cell with solder tags, 1.2V... £4.30

42mm x 16mm dia. 1.2V... £1.45

Stick of 4171mm x 16mm dia., with red & black leads 4.8V... £6.95

4 cell battery 94mm x 25mm dia. (1/2C cells)... £3.50

Computer grade capacitors with screw terminals, 38000uF 20V £2.50, 87000uF 10V £1.95; 68000uF 15V £2.95; 10000uF 16V £1.50

7 segment common anode led display, 12mm... £0.45

LM2931AT 5.0 low drop out 5V regulator TO220 package... £0.85

7812 and 7912 1.2V 1A regulators... £0.20 per 100

LM337L TO233 case variable regulator... £1.60

BS250 P channel mosfet 45p, BC559 transistor, 100+ £1.10

74LS05 hex inverter... £0.10 per 100 £3.95

Used 8748 Microcontroller... £3.50

SL952 UHF Limiting amplifier LC 18 surface mounting package with data sheet... £1.95

AM27S02... £1.25 each, 900 100+ £1.95

CD4007UB... 10p 100+, 6p 1000+

TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 10 £3.95

DC-DC converter, Reliability model V12P5, 12V in 5V 200mA A 300V input to output, Isolation with data, £4.95 each or pair of 10 £39.50

Hour counter, uses 7 day 240p, 50Hz... £1.45

Resistor pack 2500 resistors 1/8-2W 50 different values... £8.95

Resistor jumbo pack 25000, 1/4 and 1/2W resistors our choice of values and size, will be supplied in boxes or rolls of 1000, 2000 and 5000 of one type.

£25.00 Qwerty keyboard, 58 key good quality switches new.

£6.00 Qwerty keyboard with serial output, no data (used).

Polyester capacitors, box type, 22.5mm lead pitch 1μF 250V dc 20p each, 15p 100+, 10p 1000+

2.2μF 250V dc 30p each, 20p 100+, 15p 1000+

3.3μF 100V dc 30p each, 20p 100+, 15p 1000+

1μF 50V bipolar electrolytic axial leads, 15p each, 0.75p 1000+

0.22μF 250V polyester axial leads, 15p each, 100+ 7.5p each.

Philips 123 series solid aluminium axial leads, 33μF 10V & 2.2μF 40V 40p each, 25p 100+

Multilayer AVX ceramic capacitors, all 5mm pitch, 100V 100pF, 150pF, 220pF, 1000pF (10n)

10p each, 5p 100+, 3.5p 1000+

Welwyn W23 9W 120 ohm 35p each, 20p 100+

680 ohm 2W metal film resistor, 4p 100+

2p 1000+

Solid carbon resistors, very low inductance, ideal for RF circuits, 270hm 2W, 68ohm 2W 25p each.

15p each 100+, we have a range of 0.25W, 0.5W, 1W and 2W solid carbon resistors - please send SAE for list.

Intelligent 4 digit alphanumeric (5x7 dot 0.145") red LED display, 12 pin 0.6 inch wide package.

Siemens type DLR1414 £2.50 each, £2.00 30+, data sheets £1.00

AMD 27256-3 Eproms £2.00 each, £1.25 100+ DIP switch 3PCD 12 pin (ERG SDC-3-023) 60p each, 40p 100+

MDDEMS

V22/V22bis IBM PC internal full length card modem, BT approved, can be set to com 1 or 2, 1200/2400 baud with software and manual, not Hayes compatible, made by Plessey... £58.00

V32 9600 baud and 4800 baud GEC Plessey telecom external modem, model 9632, Hayes compatible and BT approved, with auto call, auto answer and V25, V25bis and Hayes AT protocols, 6500 baud local diagnostics, it does not work on slower speeds, V22/1200 baud etc and needs 1 internal dip switch to be switched on to select Hayes commands. It comes with a 100+ page comprehensive A4 size manual. An all together brilliant machine for only... £199+ VAT = £233.83

All products advertised are new and unused unless otherwise stated.

Wide range of CMOS TTL 74HC 74F Linear Transistors kits, rechargeable batteries, capacitors, tools etc, always in stock

Please add 95p towards P&P
VAT included in all prices

JPG ELECTRONICS
276-278 Chatsworth Road
Chesterfield S40 2BH
Access / Visa Orders:
(0246) 211202
Callers welcome

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

7603 with 7A26 & 7B53A Dual Trace 100MHz, Delay Sweep with Cursors...	£450	PHILIPS PM2525 Multi-Function DMU 4.5-5.5 digit, with GPIB/IEEE-488...	Only £300
7403H with TA18 & 7B50 Dual Trace 50MHz...	£300	RACAL-DANA Syn Sig Gen 9048 0.01-10MHz...	£300
7504 with TA12 & 7B52 Dual Trace 30MHz Delay Sweep...	£250	RACAL-DANA RF Power Meter 9104...	£250
7503 with TA12 & 7B50 Dual Trace 50MHz...	£200	RACAL-DANA 0.54G Auto ranging measurements of L, C, R & Q...	£250
TA13 Differential Comparator Amplifier DC 10-50MHz...	£125	WAYNE KERR 8424 RCL Meter, LCD Display...	£125
Other Plug-in options are available 1/4 Trace etc		WAYNE KERR 4210 LCR Meter, Accuracy 0.1%	£600
TEKTRONIX 2445B Four Chan 150MHz Delay Sweep with Cursors...	£1750	AVO ACTC Breakdown Leakage & Ionisation Tester RM215L/2...	£600
WATTS 55511 Four Channel 100MHz Delay Sweep...	£700	RACAL-DANA 9915 Freq Counter 10Hz-52MHz Crystal Oscill...	£150
TRB CS2101 Four Channel 100MHz Delay Sweep...	£500		
TEKTRONIX 2355 Dual Trace 100MHz Delay Sweep Ruggedised...	£1000		
HITACHI T0505 Dual Trace 100MHz Dual TB with 4 CH, Modem...	£550		
SCHLUMBERGER S21B Dual Trace 200MHz Delay Sweep with Trig View...	£500		
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep...	£550		
TEKTRONIX 476 Dual Trace 100MHz Delay Sweep...	£500		
TEKTRONIX 215 Dual Trace 50MHz Delay Sweep...	£500		
TEKTRONIX 225 Dual Trace 50MHz Alternate TB Magnification...	£500		
PHILIPS PM2110 Dual Trace 50MHz Delay Sweep...	£400		
COULD OS1110 Dual Trace 20MHz...	£180		
COULD OS3000A Dual Trace 40MHz Delay Sweep...	£250		
THORN T2015 100MHz 0.5-100MHz...	£800		
WATTS 55702 Dual Trace 20MHz...	£225		
TELEQUANTUM TF200 Dual Trace 25MHz...	£150		
TRB CS1720 Programmable 20MHz Dual Trace...	£300		
HITACHI V209 Dual Trace 20MHz Portable AC-DC Operation...	£450		

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

JUST IN

HAMEG 2404 20MHz Microwave Counter with 2 probes and copy of manual ONLY £69.00

MARCONI 2440 20MHz Microwave Counter

MARCONI 2610 20MHz Multimeter

FARNSIEL SSG1000 Sig Gen 10MHz-1GHz Synthesised

FARNSIEL SSG1000 Sig Gen 10MHz-1GHz Synthesised

MARCONI T2015 1

Everyday with Practical Electronics reaches twice as many UK readers as any other independent monthly hobby electronics magazine, our audited ABC sales figures prove it. We have been the leading independent monthly magazine in this market for the last seven years

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+ VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+ VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday with Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday with Practical Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749.

For rates and information on display advertisements (1/8th page and larger spaces) please contact our Advertisement Manager, Peter Mew on 0255 850596.

SERVICE MANUALS

Available for Most Equipment
TV, Video, Audio, Test etc
Any Age, Make or Model

Write or Phone for Quotation

MAURITRON (EE)

8 Cherry Tree Road
Chinnor, Oxfordshire

VSA OX9 4QY

Tel: (0844) 351694
Fax: (0844) 352554



We do. The Advertising Standards Authority ensures advertisements meet with the strict Code of Advertising Practice.

So if you question an advertiser, they have to answer to us.

To find out more about the ASA, please write to:
Advertising Standards Authority, Dept X, Brook House,
Torrington Place, London WC1B 7HN



THE BRITISH AMATEUR ELECTRONICS CLUB
exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.
For details, write to the Secretary

Mr J. S. Hind, 7 Carlyle Road
West Bridgford, Nottingham NG2 7NS
Space donated by Everyday with Practical Electronics

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
1 to 24 volts up to 1/2 amp, 1 to 20 volts up to 1 amp, 1 to 16 volts up to 1/2 amp d.c. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection.
Fully variable.
Operates from 240V a.c.
Compact Unit.
Size 9 x 5 1/2 x 3in.
£45 inc VAT
+ Post and Insurance £4
NEW MODEL Up to 38volts d.c. at 6amps. 10amps peak. Fully variable.
Twin panel meters. Size 14 1/2 x 11 x 5 1/2in. £98 inc VAT. Carr £8

RADIO COMPONENT SPECIALISTS
337 WHITEHORSE ROAD, CROYDON
SURREY, U.K. Tel: 081-684 1665

List. Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT
AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C., O.N.D. and H.N.C.

Next course commences
Monday 11th January 1993
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EE) 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: 071-373 8721

N. R. BARDWELL LTD (EE)

200	Signal diodes 1N4148.....	£1.00
75	Rectifier Diodes 1N4001.....	£1.00
50	Rectifier Diodes 1N4007.....	£1.00
56	Rectifier Diodes 1N5401.....	£1.00
100	Asstd Zener.....	£1.00
10	NE555 Timer ICs.....	£0.00
8	C1068 400V 6 amp thyristors.....	£1.00
8	BFY51 Transistors.....	£1.00
30	BC478 Transistors.....	£1.00
30	MPSA42 Darlington Transistors.....	£1.00
50	Rectangular red I.e.d.s.....	£1.00
25	Asstd. high brightness I.e.d.s.....	£1.00
24	Miniature red I.e.d.s 3mm dia.....	£1.00
50	Axial I.e.d.s (Diode package) wide angle I.e.d.s.....	£1.00
12	Asstd. seven segment displays.....	£1.00
30	Asstd. I.F. Transformers.....	£1.00
48	Asstd. coil formers.....	£1.00
100	Asstd. RF chokes (Inductors).....	£1.00
30	Asstd. connectors edge-dil-sil etc.....	£1.00
10	4P 3W MBB min. rotary switches.....	£1.00
20	1Inch Glass Reed switches.....	£1.00
20	Magnetic ear pipe plus lead & plug.....	£1.00
20	MIN SP/CO slide switches.....	£1.00
30	Asstd. dim. sockets up to 40 pin.....	£1.00
24	24-way edge I.e.d. wire wrap pin sockets.....	£1.00
2	OPR12 light dependent resistors.....	£1.00
200	Printed circuit board 20mm pitch clips.....	£1.00
200	Asstd. disc ceramic capacitors.....	£1.00
80	Asstd. capacitors 1nf to 1uf.....	£1.00
80	Asstd. electrolytic capacitors.....	£1.00
47UF	16V Radial electrolytics.....	£1.00
75	4.7UF 16V Radial electrolytics.....	£1.00
80	10UF 16V Radial electrolytics.....	£1.00
50	10UF 25V Radial electrolytics.....	£1.00
80	22UF 25V Radial electrolytics.....	£1.00
60	33UF 16V Radial electrolytics.....	£1.00
50	47UF 50V Radial electrolytics.....	£1.00
80	100UF 10V Radial electrolytics.....	£1.00
50	220UF 16V Radial electrolytics.....	£1.00
60	470UF 10V Radial electrolytics.....	£1.00
40	1000UF 10V Radial electrolytics.....	£1.00
12	10000UF 25V Axial electrolytics.....	£1.00
1	1 Farad 5.5V memory back up capacitor.....	£1.00
1	Peltier effect heat pump.....	£1.95
1	10 watt Stereo power, 4 controls plus data.....	£2.95

Prices include VAT, postage £1.25. Stamp for Lists

288 Abbeydale Road, Sheffield S7 1FL
Phone (0742) 552886. Fax (0742) 500689

Typefit

The Typesetting programme for all your Typesetting needs.

If you need typesetting for your Adverts, Brochures, etc.
Typefit can help you.

Tel: 0202 882299

NEW VHF MICROTRANSMITTER KIT

Tunable 80-135MHz, 500 metre range, sensitive electret microphone, high quality PCB.

SPECIAL OFFER complete kit ONLY £5.95

Assembled and ready to use £9.95 post free.

Credit card orders telephone 021 411 1821. Fax 021 411 2355

Send 2x1st class stamps for Catalogue. Cheques/P.O.s payable to:

QUANTUM ELECTRONICS

Kits Dept. (EE), 3 Houlden Road, West Heath,

Birmingham B31 3HL

SHOP NOW OPEN - CALLERS WELCOME

Contact

HST for all your component needs.
Send for your free catalogue and details of special offers.

HST Ltd

Technology House
Prospect Road, Carlton
Nottingham NG4 6LA

Tel: 0602 587225. Fax: 0602 484530.

The Electronics & Radio Book Listing

To be published regularly. Containing 100s of out of print, hard to get secondhand and new Electronics and Radio books, Magazines and Journals. Send FIVE FIRST CLASS STAMPS for next copy or £3.50 for next four issues.

WANTED TO BUY
Secondhand Electronics and Radio Books and Magazines
Dept EPE. CHEVEY BOOKS
157 Dickson Rd, Blackpool FY1 2EU. Tel 0253 751858

Miscellaneous

G.C.S.E. ELECTRONICS KITS at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT ELECTRONICS, 70 Oxford Road, Clacton CO15 3TE.

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Sussex BN3 8GR, or phone Brighton 720203.

STUDY ELECTRONICS on the BBC Micro. An interactive approach to learning. Four program titles available 'Introduction to Electronics Principles', 'Electronics Mathematics', 'Digital Techniques' and now 'Programming for Electronics'. Programs include theory, examples, self test questions, formulae, charts and circuit diagrams. User inputs and calculated outputs, £29.95 each plus £2 p&p. Cheque or Postal Order to E.P.T. Educational Software, Pump House, Lock Lane, Witham, Essex CM8 2BJ. Please state BBC 'B' or Master series and disc size.

AVO 8 Multimeter with leads and batteries for sale. Good condition, £35. Tel 0543 450437.

OUTDOORS electronic photo-electric control unit for switching mains lights on at dusk, off at dawn. 5A rating, £15.40. Taytronics, 8 Park Avenue, Markfield, Leicestershire LE67 9WA.

SATELLITE DISHES 35cm, new and boxed. Complete with LNB £20.00. DMAC Satellite receiver - Ferguson SRB1 (less transformer and case). Can be adapted to D2MAC and Astra PAL. Including remote control, only £14.50 inc. postage. Service manuals £3.00 each. EPROMS (used, cleaned and erased) 2764 75p, 27128 90p, 27256 £1.25, 27512 £3.00, 27010 £3.25. Most others available. Gadget Computer Services, Freepost Dunstable, Bedfordshire LU5 5SX. Tel 0582 868687. Fax 0582 868688.

THE HOMEBUILT DYNAMO (Plans). Reviewed 1989 in PE January and Model Engineer December 15th. Price £42 post paid airmail from Alfred Forbes, PO Box 3919, Auckland, New Zealand. Tel (09) 818-8967.

MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 10 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 100 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert personal tutors. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/> TV, Video & Hi-Fi Servicing
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/> Refrigeration & Air Conditioning
Electrical Engineering	<input type="checkbox"/> Car Mechanics
Electrical Contracting / Installation	<input type="checkbox"/> Computer Programming
GCSE/GCE/SCE over 40 examination subjects to choose from	

Name _____ Address _____



International Correspondence Schools Dept ECS B2
312/314 High Street, Sutton, Surrey SM1 1PR or 041-221 7373 (24 hours).

COMPONENTS
For TV ★ Video
Audio ★ Computer

WE CAN SUPPLY A VAST RANGE OF SPARES for many makes of TV, Video, Computer & Audio Equipment. WRITE (Encl. s.a.e. please) or PHONE
FOR A 'PRICE & AVAILABILITY' on your requirements.

0452 526883

VIDEO BELT KITS

AMSTRAD VCR4600/4700/5200.....	£3.19
FISHER FVHP905/906/908.....	£3.03
HR3300/3330/3660.....	£3.30
Large range of Pinch Rollers, Idlers, Heads, etc., from stock.	
SERVICE MANUALS	

ZX3000 Chassis.....	£7.50
PHILIPS KT4/K40 Chassis.....	£12.50
TOSHIBA STU2/L Tuner.....	£6.99

SEMICONDUCTORS

BU508A.....	£1.18
LM733CN.....	£2.49
B2.27 UC3884.....	£8.95
P8255A.....	£2.85
UPC1378L.....	£2.45
STK024.....	£14.34
STK4141W.....	£8.79
USP-8039C.....	£9.99
TA7280P.....	£6.88
V20-8MHz.....	£9.99
TA8210H.....	£6.52
27C256-200.....	£2.95

SERVICE ITEMS	
SHARP RGF2614 Main belt.....	£1.40
FIDELITY 14"16"20" General LOPTX (+PCB).....	£17.65
QL Membrane.....	£8.99
PHILIPS (CM8633) Service Manual - MK 1.....	£4.71
Line O/P TX - Mk 1.....	£29.37

This is just a very small sample of our stock.

Order by Post or Phone. We accept payment by VISA, ACCESS, DELTA, SWITCH, Cheque or P.O. Post & Packing is £1.20. No VAT to add on.

All items subject to availability.

Prices can change without notice.



MARAPET (EEL)
1 HORNBEAM MEWS
GLOUCESTER GL2 0UE



Technical Information Services

76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE

Tel. (0698) 884585 Mon-Fri 8.30am - 5.00pm

Tel. (0698) 883334 Outwith business hours

FAX facility available all day on both lines

Write now with an SAE for your

FREE QUOTE FREE VOUCHERS & FREE CATALOGUE

Remember, not only do we have EVERY service sheet ever produced, but we also have

THE WORLDS LARGEST COLLECTION OF SERVICE MANUALS

& WE ARE SOLE SUPPLIERS OF VARIOUS FAULT-FINDING GUIDES REPAIR MANUALS & TECHNICAL MANUALS

CTV, Video, CD, Hi-Fi, Camcorder, Satellites, Computers, Domestic Equip', etc.

DATA REFERENCE MANUAL ".....essential for the serious electrician"
FREE updating and a 10% discount voucher only £5.95
Incorporates Unique Model Identification and Chassis Data

POWER SUPPLY BARGAINS!

ALL POWER SUPPLIES ARE NEW BUT UNCASED

FOUR OUTPUT SWITCH-MODE 120V/240V input.

+5V @ 15A; +12V @ 4A; +12V @ 4A; +12V @ 6A.
(Can be bridged to give +12V @ 14 amps!).....Bargain at £25

THREE OUTPUT SWITCH-MODE 120V/240V input.

+12V @ 600mA; +55V @ 420mA; -12V @ 210mA
outputs. Originally intended for plasma display.....£20

5 VOLT-8 AMP SWITCH-MODE 120V/240V input.....Bargain at £12

+/-12V @ 1AMP REGULATED 120V/240V input.

Can be modified to give +/-15V @ 800mA.....£10

THYRISTOR MOTOR CONTROLLER made by RMB, for

controlling D.C. shunt motors.....£25

CHASSIS MOUNTING IEC MALE SOCKET with integral mains filter.....Snip at £3 each

PRICES INCLUDE VAT, PLEASE ADD 10% FOR P&P

WORLD LEISURE CORPORATION BROADCAST

22 SOHO SQUARE, LONDON W1V 5FJ

Tel: 071-437 2004 Fax: 071-437 2021

19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack cases features satin black finished 16SWG (1.5mm) steel front panels (no fixing holes visible), with the rear box assembly constructed from 20SWG (.9mm) steel. The standard units are 10" (254mm) deep. 19" project cases only 4" (101mm) deep and are available in the following popular sizes:

PROJECT CASES

Type	Height	Price
PU1	1 1/2" (44mm)	£18.02
PU2	3 1/2" (88mm)	£20.07
PU3	5 1/2" (133mm)	£22.11
PU4	7" (178mm)	£24.16
PU6	10 1/2" (266mm)	£28.25

PU1

PU2

U3

EQUIPMENT CASES

Type	Height	Price
U1	1 1/2" (44mm)	£22.33
U2	3 1/2" (88mm)	£25.85
U3	5 1/2" (133mm)	£29.38
U4	7" (178mm)	£31.72

Delivery included (UK only).

All prices include VAT.

BLANKING PANELS, RACKING CONSOLES

and RACK CABINETS are also available.

Please send SAE for details.

Tel: 0272 373983 for Access/Visa Sales or cheque

with order to:

RACKZ PRODUCTS

PO Box 1402 Mangotsfield, Bristol, England, BS17 3RY

CAMBRIDGE COMPUTER SCIENCE LIMITED

LCD modules.....

16 char by 1 £4.00, 20 char by 2 £6.00, 40 char by 1 £8.00

£25.00 each

£9.00 each

5.25" Disk Drives, 80 Tk, DSDD

£3.00/box

5.25" Disk Drives, 80 Tk, DSDD Used, No Wty.

£16.00 each

The £15.00 drives are sold on a strictly "as is" basis!

£10.00 each

5.25" Disks, 80 Tk, DSDD, boxes of 10 (free disk cleaner with 5 boxes).

£18.00 each

Digital multimeter, 14 ranges, inc. leads & manual.

£10.00 each

Apricot Data Drive PSU 5V a 2.5A, 12V u 2A

£4.00 each

5V to 10A PSU

£4.00 each

Disk Drive Data lead BBC Micro to Disk Drives).

Single £2.00 Dual £4.00

Disk Drive Power lead BBC Micro to Disk Drives).

Single £2.00 Dual £4.00

8086 CPU chips

£2.00 each

2804 CPU CTC, PIO

£1.20 each

27128 EPROMS (Ex equipment)

£0.50 each

256K DRAM (Ex Equipment)

£0.40 each

1MBIT-10 DRAM (Ex Equipment)

£1.40 each

256K Byte DRAM Modules, removed from equipment

£6.00 each

16, 18 & 20 pin dill low profile IC sockets 0.3" wide

£0.40/10: £3.00/100

22 & 24 pin dill low profile IC sockets 0.4" wide

£0.40/10: £3.00/100

24, 28, 32, 40 & 48 pin dill low profile IC sockets 0.6" wide

£0.40/10: £3.00/100

Circuit tester, finds faults in TTL & CMOS logic circuits, Inc. leads

£8.00 each

Metal project boxes drilled & painted but unused 28 x 32.5 x 5cm

£5.00 each

Used computer cards many useful components (large ones socketed)

Floppy disk card INEC FDC chip £1.00, Winil controller (WD HDC chip)

£1.00 each

CPU card (8088, 280, 80 & EPROMs)

£3.00 each

Keyboards, full Qwerty, number pad and LCD

£8.00 each

Desktop computer case with 200W mains PSU used.

£30.00 each

Prices include postage. Add 50p (plus VAT) to orders below £5.00. All items new unless stated.

Add 17.5% VAT to all prices. Send an SAE for our latest list or for more info.

Dept EE, 374 Milton Road, Cambridge CB4 1SU


Tel: 0223 424602, 0831 430496 or 0831 430552 (Mail order only)

ULP
TRANSFORMERS FROM
JAYTEE

The UK Distributor for
Standard Toroidal Transformers

* 106 types available from stock

* Sizes from 15VA to 625VA

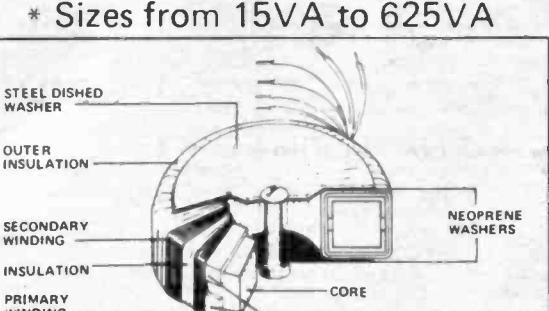

Write or phone for free Data Pack

Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL

Telephone: (0227) 375254

SHERWOOD ELECTRONICS

9 Lower Birchwood, Somercotes, Derbyshire DE55 4NG

To celebrate *Everyday Electronics* 21st and the merger with *Practical Electronics*, we are extending our Special Offer of 2 FREE packs with every 10 purchased until the end of November.

SP1	15 x 5mm Red LEDs	SP26	5 x 741 Op-amps
SP2	15 x 5mm Green LEDs	SP28	6 x Cmos 4011
SP3	12 x 5mm Yellow LEDs	SP29	4 x Cmos 4013
SP6	15 x 3mm Red LEDs	SP36	25 x 10uf/25V radial caps.
SP7	12 x 3mm Green LEDs	SP37	20 x 100uf/40V radial caps.
SP8	10 x 3mm Yellow LEDs	SP38	25 x 47uf/25V radial caps.
SP10	100 x 1N4148 diodes	SP42	200 x Mixed 0.25W C.Film resistors
SP11	30 x 1N4001 diodes	SP44	12 x 5mm LEDs-4 ea Red, Grn., Yel.
SP12	30 x 1N4002 diodes	SP47	5 x Min.push button switches
SP18	20 x BC182 transistors	SP102	20 x 8pin DIL sockets
SP19	20 x BC183 transistors	SP103	15 x 14pin DIL sockets
SP20	20 x BC184 transistors	SP104	15 x 16pin DIL sockets
SP22	20 x BC214 transistors	SP109	15 x BC557 transistors
SP23	20 x BC549 transistors	SP112	6 x Cmos 4093
SP24	6 x Cmos 4001	SP119	6 x Cmos 4072
SP25	5 x 555 timers	SP125	10 x 1000uf/16V radial caps.

RESISTOR PACKS - 0.25W C.Film

RP3 5 each value - total 365 £2.30

RP7 10 each value - total 730 £3.95

RP10 1000 popular values £5.35

Cheques or P.O. to

NO VAT

Please add £1 P&P to all orders

SHERWOOD ELECTRONICS

Millions of quality components at lowest ever prices!

Plus Tools, Watches, Fancy Goods, Toys.
Mail order UK only.

All inclusive prices –

NO post, or VAT etc to add on.

Send 34p stamped self addressed label or envelope for catalogue/clearance list.

At least 2,100 offers to amaze you.

Brian J Reed

**6 Queensmead Avenue, East Ewell
Epsom, Surrey KT17 3EQ**
Tel: 081-393 9055

Metal detector boards with Data has tuner, mode, discriminate, headphone jack, on/off volume & push button facilities.....	£7.95 ea*
35mm Camera returns with auto flash, wind on etc.....	£6 ea or 2 for £10
100k Lin. Joystick, mech.....	£1
Dictaphone cassette, mech/record erase playback heads, 6V solenoid, motor, hall effect switch.....	£2.00 ea*
T.V. Printer stands.....	£3.95 ea
Bicc-Vero Easivire construction kit.....	£4.95 ea*
Dot matrix LCD 10x2 lines.....	£3.75 ea*
40 characters x 1 line dot matrix LCD with data.....	£15.00*
2 digit 16 segment VF display with data.....	£2.95 ea*
4 digit intelligent dot matrix display.....	£6.00*
17 segment V.F. display with driver board and data.....	£2.99 ea*
8 digit liquid crystal display.....	£1.75 ea*
4 digit LCD with 7211 driver chip.....	£3.50 ea*
Digital clock display.....	£2.50*
11 key membrane keypad.....	£1.50 ea*
Keyboard 392mm x 180mm/100 keys on board + LCD + 74HC05/80C49 easily removable.....	£4.95
19" 3U sub rack enclosures.....	£8.95
12V stepper motor, 48 steps per rev, 7.3° step angle.....	£3.95 ea*
Stepper motor board with 2 slotted opto + 2 mercury tilt switches.....	£3.95 ea*
1000 mixed 1% watt 1% resistors.....	£4.95 ea*
250 electrolytic axial + radial caps.....	£4.95 ea*
200 off mixed polyester caps.....	£7.95*
100 Mixed trimmer caps popular values.....	£4.95*
100 off Phono plugs (red/black/grey).....	£3.50*
50 Mixed terminal blocks.....	£2.95*
25 off astl. buzzers & sounders.....	£4.95*
Cable box UHF modulator/video preamp/transformer R's + C's/leads.....	£6.95
1000 off mixed Multilayer Ceramic Caps.....	£7.95
Solar cell modules 0.45V 700mA.....	£2.95 ea*
8.B.C. Micro to disc drive lead.....	£1.50*
Car burglar alarm vibration auto entry/exit delay.....	£5.95 ea*
Single zone alarm panel auto entry/exit delay housed in domestic light socket.....	£9.95 ea*
P.C. P.S.U. 50 watt 115-230V input + 5V +12V 2.5A output with built in fan, IEC inlet + on off.....	£9.95 ea*

**QUANTITY DISCOUNTS AVAILABLE
PLEASE RING**

We also buy all forms of electronic components, p.s.u.'s, disk drives etc.

Lists to below address.

**ALL PRICES INCLUDE V.A.T.
PLEASE ADD £2.00 p&p EXCEPT
ITEMS MARKED * WHICH ARE 50P.
SAE FOR BULK BUYING LIST
PAYMENT WITH ORDER TO:**

**Dept EE, COMPELEC,
14 Constable Road
St. Ives, Huntingdon,
Cambs PE17 6EQ.
Tel/Fax: 0480 300819**

ADVERTISERS INDEX

AUTONA.....	735	MAGENTA ELECTRONICS.....	691
N. R. BARDWELL.....	758	MAILTECH.....	739
R. BARTLETT.....	749	MARLIN ELECTRONICS...Cover (iv)	749
BK ELECTRONICS.....	749	MARAPET.....	759
BLB ELECTRONICS.....	749	MARCO TRADING.....	719
BRIAN J. REED.....	760	MAURITRON.....	758
BULL ELECTRICAL.....	760	M&B ELECT. SUPPLIES.....	690
CAMBRIDGE COMP. SCIENCE	759	MICRO AMPS.....	749
CIRKIT DISTRIBUTION.....	735	MODERN ELECTRONICS.....	688
COMPELEC.....	760	MANUAL.....	688/689
CRICKLEWOOD ELECTRONICS.....	703	NATIONAL COLLEGE OF TECH.	757
CR SUPPLY COMPANY.....	760	NUMBER ONE SYSTEMS.....	725
DISPLAY ELECTRONICS.....	682	OMNI ELECTRONICS.....	749
ELECTRONIZE DESIGN.....	686	PICO TECHNOLOGY.....	749
ESR ELECTRONIC COMP.....	692	RACKZ PRODUCTS.....	759
HART ELECTRONIC KITS.....	746	RADIO & TV COMPONENTS.....	685
HENRY'S AUDIO ELECTRONICS.....	686	SEETRAZ CAE.....	701
HESING TECHNOLOGY.....	760	SHERWOOD ELECTRONICS.....	760
ICS.....	759	SMART HOUSE SYSTEMS.....	686
JAYTEE ELECTRONIC SERVICES.....	757,759	STEWART OF READING.....	757
JPG ELECTRONICS.....	757	SUMA DESIGNS.....	684
LABCENTER ELECTRONICS.....	687	TECHNICAL INFO. SERVICES.....	759
LITESOLD.....	686	TISEN.....	713
		TYPESETTING BUREAU.....	758
		VIEWCOM ELECTRONICS	708/709
		WORLD LEISURE CORP.....	759

Hesing Technology



Cromwell Chambers, 8 St. Johns Street,
Huntingdon, Cambs. PE18 6DD

Tel: (0480) 433156
Fax: (0480) 214488

TEST EQUIPMENT

Supply

Maintenance

Commissioning

SYSTEM CONSULTANCY

Replacement Parts

Supply of Service &

Operators Manuals

Components

Distributors for:
WAUGH INSTRUMENTS, RAMTEST LTD., KRENZ ELECTRONICS, PANTHER

Carbon Film resistors 1/2W 5% E24 series 0.51 R to 10MO.....	1p
100 off per value - 75p, even hundreds per value totalling 1000.....	£6.00p
Metal Film resistors 1/2W 10R to 1 MO 5% E24 series - 2p, 1% E24 series.....	3p
Mixed metal/carbon film resistors 1/2W E24 series 1R0 to 10MO.....	1/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms.....	5p
Linear Carbon pre-sets 100mW and 1/2W 100R to 4M7 E6 series.....	7p
Miniature polyester capacitors 250V working for vertical mounting	
015, 022, 033, 047, 068-4p, 0.1 - 0.5, 0.12, 0.15, 0.22 - 6p, 0.47 - 8p, 0.68 - 10p, 1.0 - 12p	
Mylar (polyester) capacitors 100V working E12 series vertical mounting	
1000pF to 8200pF - 3p, 0.01 to 0.068 - 4p, 0.1 - 5p, 0.12, 0.15, 0.22 - 6p, 0.47/50V - 8p	
Submin ceramic plate capacitors 100V wkg vertical mountings. E12 series	
2% 1.8pF to 47pF - 3p, 2% 56pF to 330pF - 4p, 10% 390pF-4700pF - 4p	
Disc/plate ceramics 50V E12 series 1PO to 1000P, E6 Series 1500P to 47000P - 2p	
Polystyrene capacitors 63V working E12 series long axial wires	
10pf to 820pF - 2p, 1000pf to 10,000pf - 6p, 12,000pf - 7p	
741 Op Amp - 20p, 555 Timer - 20p	
cmos 4001 - 20p, 4011 - 22p, 4017 - 40p	
ALUMINIUM ELECTROLYTICS (Mfd's/Volts)	
1/50, 2/50, 4/75, 10/50, 10/25, 10/15, 10/10, 6/10, 5/10, 4/10, 3/10, 2/10, 1/10, 1/5, 1/2, 1/1, 1/10, 1/20, 1/30, 1/6020, 1	



POWER AMPLIFIER MODULES-TURNTABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE (A4) S.A.E. 50P STAMPED FOR CATALOGUE *

OMP MOS-FET POWER AMPLIFIERS HIGH POWER/TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED
BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)

MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV Inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" xH3½" (2U)xD11"

MXF400 W19" xH5¼" (3U)xD12"

MXF600 W19" xH5¼" (3U)xD13"

MXF900 W19" xH5¼" (3U)xD14½"

PRICES:- MXF200 £175.00 MXF400 £233.85

MXF600 £329.00 MXF900 £449.15

SPECIALIST CARRIER DEL. £12.50 EACH

OMP VARISPEED TURNTABLE CHASSIS



★ Manual arm ★ Steel chassis ★ Electronic speed control 33 & 45 R.P.M. ★ Vari pitch control ★ High torque servo driven DC motor ★ Transit screws ★ 12" die cast platter ★ Neon strobe ★ Calibrated balance weight ★ Removable head shell ★ ½" cartridge fixings ★ Cue lever ★ 220/240V 50/60Hz ★ 390x305mm ★ Supplied with mounting cut-out template.

PRICE £61.30 + £3.70 P&P

OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500mkII GOLDRING G950

PRICE £16.95 + 50P P&P PRICE £7.15 + 50P P&P

STEREO DISCO MIXER DJ6500


★ WITH ECHO ★



SIZE: 482 x 240 x 120mm

PIEZOELECTRIC TWEETERS - MOTOROLA

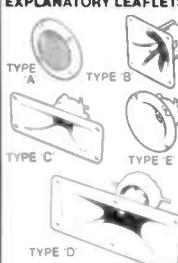Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.

TYPE 'B' (KSN1005A) 3½" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.

TYPE 'C' (KSN1016A) 2" x5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.

TYPE 'D' (KSN1025A) 2" x6" wide dispersion horn. Upper frequency response related extending down to mid-range (2kHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.

TYPE 'E' (KSN1038A) 3¼" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.

LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE

Made especially to suit today's need for compactness with high output sound levels, finished in hard wearing black vinyl with protective corners, grille and carrying handle. Each unit incorporates a 12" driver plus high frequency horn for a full frequency range of 45Hz-20kHz. Both models are 8 Ohm Impedance. Size: H20" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100WATTS (100dB) PRICE £163.50 PER PAIR

OMP 12-200WATTS (200dB) PRICE £214.55 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR



IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

150 WATTS (75 + 75) Stereo, 150W Bridged Mono

250 WATTS (125 + 125) Stereo, 250W Bridged Mono

400 WATTS (200 + 200) Stereo, 400W Bridged Mono

ALL POWERS INTO 4 OHMS

Features: ★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

POSTAL CHARGES PER ORDER £1.00 MINIMUM, OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC.
PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.




OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.


These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

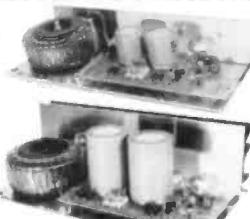THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor > 300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 300 x 123 x 60mm.

PRICE £40.85 + £3.50 P&P

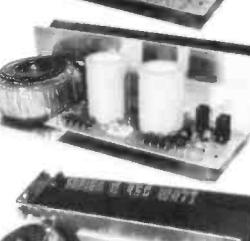

OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor > 300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 300 x 155 x 100mm.

PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor > 300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 330 x 175 x 100mm.

PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100kHz -3dB, Damping Factor > 300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 385 x 210 x 105mm.

PRICE £132.85 + £5.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100kHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50kHz. ORDER STANDARD OR PEC.



VU METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D.s (7 green, 4 red) plus an additional on/off indicator. Enclosed logic control for very fast rise and decay times. Tough moulded plastic case, with acrylic tinted front. Size 84 x 27 x 45mm.

PRICE £8.70 + 50p P&P

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (50P STAMPED) FOR COMPLETE LIST.

From McKenzie Professional Series

From McKenzie Studio Series

MCKENZIE: INSTRUMENTS, P.A., DISCO, ETC

ALL MCKENZIE UNITS 8 OHMS IMPEDANCE

8" 100 WATT PCB-100GP GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £31.45 + £2.00 P&P

RES. FREQ. 80Hz, FREQ. RESP. TO 7KHz, SENS 9db. PRICE £31.45 + £2.00 P&P

10" 100WATT PCB-100GP GUITAR, VOICE, KEYBOARD, DISCO, EXCELLENT MID. PRICE £38.89 + £2.50 P&P

RES. FREQ. 72Hz, FREQ. RESP. TO 6KHz, SENS 97db. PRICE £38.89 + £2.50 P&P

10" 200WATT PCB-100GP GUITAR, KEYBD, DISCO, EXCELLENT HIGH POWER MID. PRICE £53.21 + £2.50 P&P

RES. FREQ. 69Hz, FREQ. RESP. TO 5KHz, SENS 97db. PRICE £53.21 + £2.50 P&P

12" 100WATT PCB-120GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. PRICE £40.35 + £3.50 P&P

RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 98db. PRICE £40.35 + £3.50 P&P

12" 100WATT PCB-120GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, KEYBOARDS, DISCO. PRICE £41.39 + £3.50 P&P

12" 200WATT PCB-120GP HIGH POWER BASS, KEYBOARDS, DISCO. PRICE £71.91 + £3.50 P&P

RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS 99db. PRICE £71.91 + £3.50 P&P

12" 300WATT PCB-120GP HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO. PRICE £95.66 + £3.50 P&P

RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 100dB. PRICE £95.66 + £3.50 P&P

15" 100WATT PC15-100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. PRICE £59.05 + £4.00 P&P

RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 98db. PRICE £59.05 + £4.00 P&P

15" 200WATT PC15-200BS VERY HIGH POWER BASS. PRICE £80.57 + £4.00 P&P

RES. FREQ. 40Hz, FREQ. RESP. TO 3KHz, SENS 98db. PRICE £80.57 + £4.00 P&P

15" 250WATT PC15-250BS VERY HIGH POWER BASS. PRICE £90.23 + £4.50 P&P

RES. FREQ. 39Hz, FREQ. RESP. TO 4KHz, SENS 99db. PRICE £90.23 + £4.50 P&P

15" 400WATT PC15-400BS VERY HIGH POWER, LOW FREQUENCY BASS. PRICE £105.46 + £4.50 P&P

RES. FREQ. 40Hz, FREQ. RESP. TO 4KHz, SENS 100db. PRICE £105.46 + £4.50 P&P

18" 500WATT PC18-500BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. PRICE £174.97 + £5.00 P&P

RES. FREQ. 27Hz, FREQ. RESP. TO 2KHz, SENS 98db. PRICE £174.97 + £5.00 P&P

EARBENDERS: HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm) BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND

8" 50WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P

RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97db. PRICE £8.90 + £2.00 P&P

10" 50WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P

RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 99db. PRICE £13.65 + £2.50 P&P

10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P

RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 98db. PRICE £30.39 + £3.50 P&P

FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND. PRICE £42.12 + £3.50 P&P

5½" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P

RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92db. PRICE £9.99 + £1.50 P&P

6½" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + £1.50 P&P

RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94db. PRICE £10.99 + £1.50 P&P

8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P

RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 98db. PRICE £12.99 + £1.50 P&P

10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P

RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98db. PRICE £16.49 + £2.00 P&P

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT DIAGRAM AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £9.99 + £1.00 P&P

PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA,

ESSEX, SS2 6TR.

Tel.: 0702-527572 Fax.: 0702-420243

BUYER'S GUIDE TO ELECTRONIC COMPONENTS 1993

Maplin



BS 5750
Part 2 1987

Level B:
Quality Assurance
RS12750



Order your copy of the New MAPLIN Catalogue on sale **NOW!**
Pick up a copy from any branch of WHSMITH or from our chain of shops for just £2.95 or
post this coupon now to receive your copy for just £3.45 inc. P&P. If you live outside the
U.K. send £5.50 or £10.65 or £14 IRC's for Airmail in Europe/surface mail or outside Europe,
enclose £3.45/£5.50/£10.65 (delete as applicable).

Name _____
Address _____

Post Code _____
Send to Maplin Electronics,
P.O. Box 3, Rayleigh,
Essex, England,
SS6 8LR.
EEG3

Over 700 product packed pages with
hundreds of brand new products.
On sale now, only £2.95

Available from all branches of WHSMITH and
Maplin shops nationwide. Hundreds of new
products at super low prices!