

**EVERYDAY**

FEBRUARY 1998

**PRACTICAL**



# ELECTRONICS

<http://www.epemag.wimborne.co.uk>

£2.65

**KISSOMETER**  
**Fun Passion**  
**Presenter**

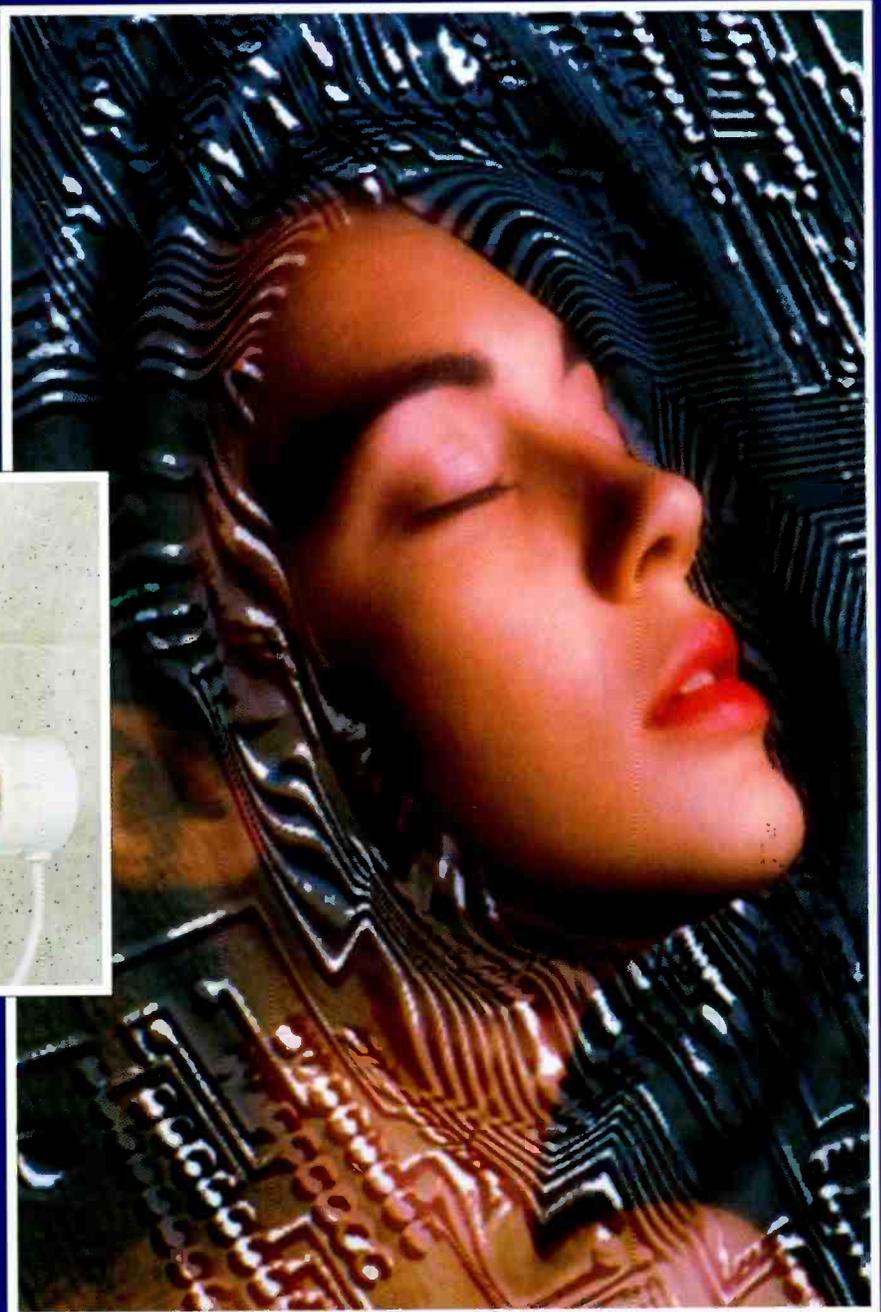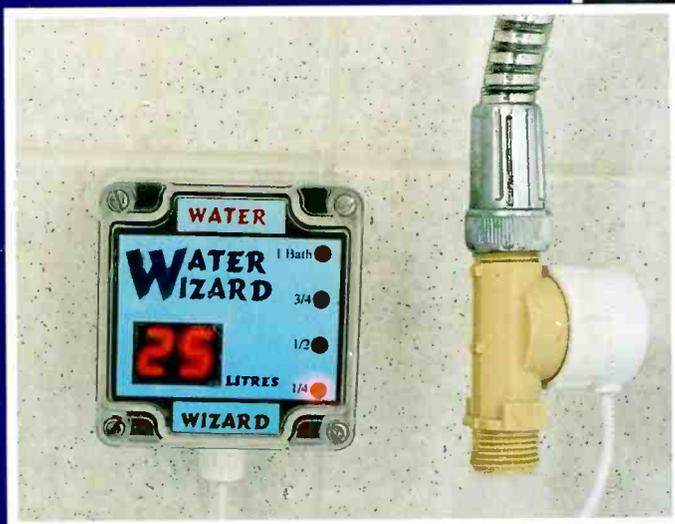**WATER WIZARD**  
Automatically  
measures  
water flow



**WAA WAA**  
Semi-automatic  
guitar gizmo


**EPE VIRTUAL**  
**SCOPE**

Dual trace PC based  
oscilloscope  
Part 2 - Construction Details

**THE No.1** MAGAZINE FOR  
ELECTRONICS TECHNOLOGY  
& COMPUTER PROJECTS



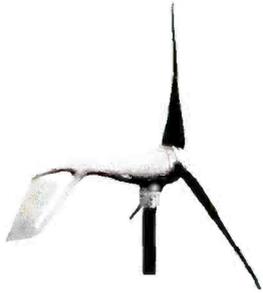**PLUS** Ingenuity Unlimited - New Technology Update  
Circuit Surgery - Net Work - Techniques



## WIND GENERATORS 380 WATT

1.14 metre dia blades, carbon matrix blades, 3 year warranty, 12vdc output, 24v version available, control electronics included, brushless neodymium cubic curve alternator, only two moving parts, maintenance free, simple roof top installation, start up speed 7mph, max output (30mph) 380w. £499 ref AIR1

## PLANS

**PORTABLE X RAY MACHINE PLANS** Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref F/XP1.

**TELEKINETIC ENHANCER PLANS** Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £4/set Ref F/TKE1.

**ELECTRONIC HYPNOSIS PLANS & DATA** This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set Ref F/EH2.

**GRAVITY GENERATOR PLANS** This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means- cause it to levitate. £10/set Ref F/GRA1.

**WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS** Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, 'Plasma in a jar', St Elmo's fire, Corona, excellent science project or conversation piece. £5/set Ref F/BTC1/LG5.

**COPPER VAPOUR LASER PLANS** Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set Ref F/CV1.

**VOICE SCRAMBLER PLANS** Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/set Ref F/VNS9.

**PULSED TV JOKER PLANS** Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM too! DISCRETION ADVISED. £8/set Ref F/TJ5.

**BODYHEAT TELESCOPE PLANS** Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £8/set Ref F/BHT1.

**BURNING, CUTTING CO2 LASER PLANS** Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £12/set Ref F/LC7.

**DYNAMO FLASHLIGHT** Interesting concept, no batteries needed just squeeze the trigger for instant light apparently even works under water in an emergency although we haven't tried it yet! £6.99 ref SC152

**ULTRASONIC BLASTER PLANS** Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewelry, coins, small parts etc. £6/set Ref F/ULB1.

**ANTI DOG FORCE FIELD PLANS** Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £6/set Ref F/DOG2.

**LASER BOUNCE LISTENER SYSTEM PLANS** Allows you to hear sounds from a premises without gaining access. £12/set Ref F/LLIST1.

**PHASOR BLAST WAVE PISTOL SERIES PLANS** Handheld, has large transducer and battery capacity with external controls. £6/set Ref F/PSP4.

**INFINITY TRANSMITTER PLANS** Telephone line arabler/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.


**BUG DETECTOR PLANS** Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5/set Ref F/BD1.

**ELECTROMAGNETIC GUN PLANS** Projects a metal object a considerable distance- requires adult supervision £5 ref F/EML2.

**ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND!** £5/set Ref F/EMA1.

**PARABOLIC DISH MICROPHONE PLANS** Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8/set ref F/PM5.

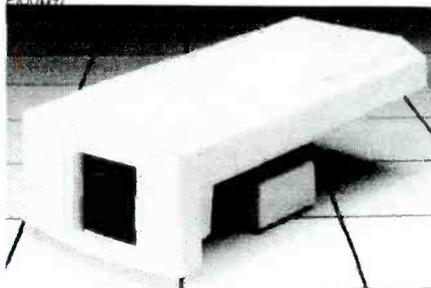
**2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS** Operates on 9-12vdc, many possible experiments. £10 Ref F/EMM2.


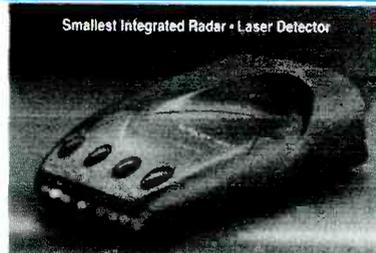
## COLOUR CCTV VIDEO CAMERAS,

BRAND NEW AND, CASED, FROM £99.  
Works with most modern video's, TV's, Composite monitors, video grabber cards etc

Pal, 1v P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8, 500x582, 12vdc, mounting bracket, auto shutter, 100x50x180mm, 3 months warranty, 1 off price £119 ref XEF150, 10 or more £99 ea 100+ £89



## SUPERWIDEBAND RADAR DETECTOR 360 deg COVERAGE

Detects both radar and laser, X, K, superwide KA bands. LED signal strength display Audio and visual alerts, Alert priority, Rear and front facing optical waveguides, Triplecheck verification, city mode, tutorial mode, dark mode, aux jack, volume control. These may be illegal to use in certain countries. 1.1"x2.7"x4.6"

Superband £149 ref RD2

PLACE YOUR ORDER VIA OUR WEBSITE AT [BULL-ELECTRICAL.COM](http://BULL-ELECTRICAL.COM)

## BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE WITH ORDER PLUS £3.50 P&P PLUS VAT.


24 HOUR SERVICE £5.00 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50 (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

'phone orders: 01273 203500

FAX 01273 323077

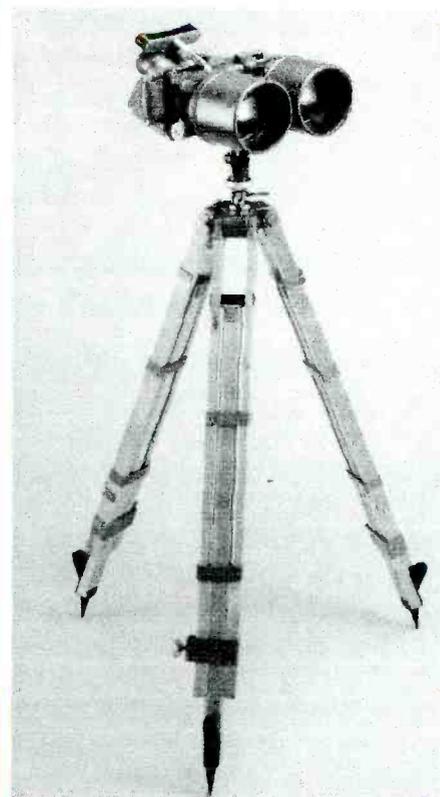E-mail [bull@pavilion.co.uk](mailto:bull@pavilion.co.uk)



## HELIOS PNB-2 RUSSIAN BORDER GUARD OBSERVATION BINOCULARS £1799

Intended for the medium to long range observation of air and ground targets and the determination of their angular co-ordinates. These giant binoculars are a tribute to Russian optical ingenuity, with a performance that simply has to be seen to be believed. A large exit pupil diameter of 7.33mm provides exceptional light passing power, which when combined with its high

magnification of x15 allows the user to view over vast distances with delightfully bright, crisp, high resolution images. Robust and able in construction incorporating an uncomplicated yet thoughtfully designed mechanical layout ensuring ease of operation and quick precise targeting. These binoculars have a wide variety of applications and are suitable for use by coastguards, law enforcement organizations, customs, farmers etc.

Specifications  
x15 magnification, 110mm objective, 6 deg angle of view, Field at 100m=105m, focusing 10m-inf, fully coated precision ground optics, orange and neutral filters, rubber lens caps, rapid targeting hand grips, padded headrest, screw in silica gel cartridges, wooden tripod, operating temperatures -40 c to +50 c, weight 25kg, (15kg without tripod), supplied in wooden carrying case.  
Border guard binoculars £1799 ref PNB2



## TZS4 INFRARED NIGHT SIGHT

One of our top most selling night sights is this Russian TZS4. This sight enable you to see in very low light levels, or with the aid of the built in infra red illuminator- in total darkness. In 1/4 moonlight you would spot a man at 150m, in total darkness at 75m. Magnification 2.3x, 240x66x190mm, 0.9kg, focusing range 1.5m-infinity, M42 camera mount included, runs on 2xAA batteries, 100mm focal length, 8 deg illuminator divergence, 50hrs continuous (no illuminator) 10hrs with carrying case and strap.

TZS4 Nightsight £199 ref BAR61

ISSN 0262 3617  
PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .

VOL. 27 No. 2 FEBRUARY 1998





EVERYDAY

PRACTICAL
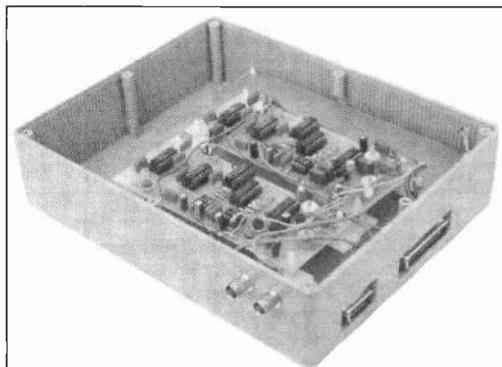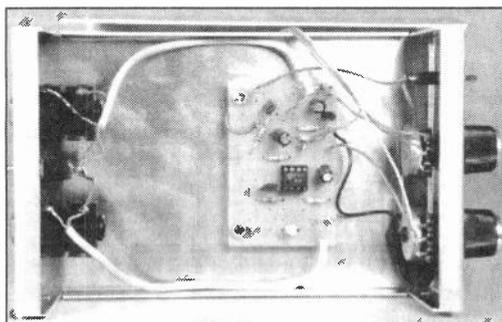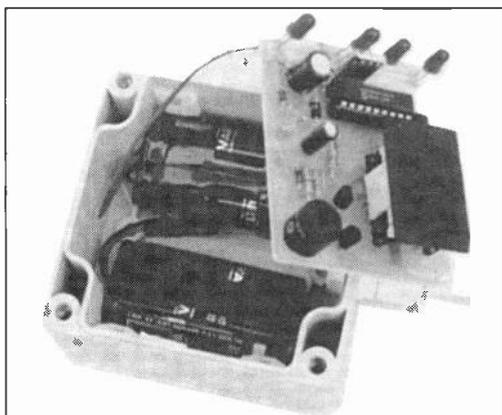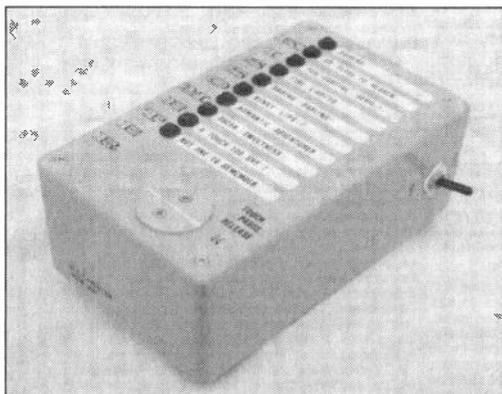
# ELECTRONICS

<http://www.epemag.wimborne.co.uk>

The No. 1 Magazine for Electronics Technology  
and Computer Projects



© Wimborne Publishing Ltd 1998. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our March '98 issue will be published on Friday, 6 February 1998. See page 83 for details.

Everyday Practical Electronics, February 1998

## Projects and Circuits

- WATER WIZARD** by Andrew Buckmaster and Max Horsey 92  
Don't waste money down the drain – use our shower-watch/hose meter to monitor the flow
- INGENUITY UNLIMITED** hosted by Alan Winstanley 104  
Cheap L.E.D. Blinker; Simple Thermostat; Simple Liquid Crystal Display Tester; Isolated Multi-output Power Supply; Daisy-chaining Decoder Chips; Neon Torch
- WAA-WAA EFFECTS PEDAL** by Robert Penfold 110  
How to easily and inexpensively add expression to your playing
- KISSOMETER** by William Chester 126  
Take the wraps off your blind-date's hidden talents – and not just on Valentine's Day!
- CHIP SPECIAL – HT7630 D.C. PIR CONTROLLER** by Andy Flind 132  
Holtek's new passive infra-red controller chip has a lot of functions in its favour – try it!
- EPE VIRTUAL SCOPE – 2** by John Becker 135  
Describing construction and software operation of this flexible computer-controlled dual-trace oscilloscope simulator

## Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole 102  
50 years on from its invention, the transistor still dominates electronics and its development continues apace
- TEACH-IN '98 – An Introduction to Digital Electronics – 4** 114  
by Ian Bell, Rob Miles, Dr Tony Wilkinson, Alan Winstanley  
Supporting students and hobbyists in their quest for basic knowledge and practical experience – this month: binary numbers; digital logic systems; gates and processing circuits; logic in the real world
- TECHNIQUES – ACTUALLY DOING IT** by Robert Penfold 124  
How to turn a completed circuit board into a finished project
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell 148  
High Current Regulator; Why no PLCs?; Diode and Resistor Queries
- NET WORK – THE INTERNET PAGE** surfed by Alan Winstanley 150  
PC Technology Race; Hand Over Your Cache; Suggested Links

## Regulars and Services

- EDITORIAL** 91
- INNOVATIONS** – Barry Fox highlights technology's leading edge 99  
Plus everyday news from the world of electronics
- READOUT** John Becker addresses general points arising 107
- PARTS GALLERY + ELECTRONIC CIRCUITS AND COMPONENTS CD-ROM** 134
- BACK ISSUES** Did you miss these? 145
- SHOPTALK** with David Barrington 147  
The *essential* guide to component buying for *EPE* projects
- ELECTRONICS VIDEOS** Our range of educational videos 152
- DIRECT BOOK SERVICE** 153  
A wide range of technical books available by mail order
- PRINTED CIRCUIT BOARD SERVICE** 156  
PCBs for *EPE* projects – some at "knockdown" prices! Plus *EPE* software
- ADVERTISERS INDEX** 160

Readers Services • Editorial and Advertisement Departments 91

Surplus always wanted for cash!

# THE ORIGINAL SURPLUS WONDERLAND!


THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

## LOW COST PC's -

### SPECIAL BUY 'AT 286'

40Mb HD + 3Mb Ram

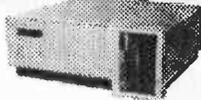

LIMITED QUANTITY only of these 12Mhz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!

|  |                         |
|--|-------------------------|
| Order as HIGRADE 286                                     | <b>ONLY £129.00 (E)</b> |
| Optional Fitted extras: VGA graphics card                | £29.00                  |
| 1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)       | £19.95                  |
| Wordperfect 6.0 for Dos - when 3 1/2" FDD option ordered | £22.50                  |
| NE2000 Ethernet (thick, thin or twisted) network card    | £29.00                  |

## LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard SIMM connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3 1/2" floppy disk drive. Fully tested and guaranteed. Fully expandable

Only **£399.00 (E)**  
Many other options available - call for details.

## FLOPPY DISK DRIVES 3 1/2" - 8"

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

|  |            |
|--|------------|
| 3 1/2" Panasonic JU363/4 720K or equivalent RFE            | £24.95(B)  |
| 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only           | £25.95(B)  |
| 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only           | £18.95(B)  |
| 5 1/4" Teac FD-55FR 1.2 Meg (for IBM pcs) RFE              | £18.95(B)  |
| 5 1/4" Teac FD-55F-03-U 720K 4080 (for BBC's etc) RFE      | £22.95(B)  |
| 5 1/4" BRAND NEW Mitsubishi MF501 360K                     | £22.95(B)  |
| Table top case with integral PSU for HH 5 1/4" Flopp or HD | £29.95(B)  |
| 8" Shugart 8010/81 SS refurbished & tested                 | £195.00(E) |
| 8" Shugart 810 B" SS HH Brand New                          | £275.00(E) |
| 8" Shugart 851 B" double sided refurbished & tested        | £250.00(E) |
| Mitsubishi M2894-63 8" double sided NEW                    | £275.00(E) |
| Mitsubishi M2896-63-02U 8" DS slimline NEW                 | £285.00(E) |
| Dual 8" cased drives with integral power supply 2 Mb       | £499.00(E) |

## HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard SMD interface, replaces Fujitsu equivalent model. Full manual. Only £299.00 or 2 for £525.00 (E)

|  |            |
|--|------------|
| 3 1/2" FUJII FK-309-26 20mb MFM I/F RFE              | £59.95(C)  |
| 3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE    | £59.95(C)  |
| 3 1/2" CONNER CP3044 40mb IDE I/F (Mac & Acorn)      | £69.00(C)  |
| 3 1/2" RODIME R0367S 40mb SCSI I/F (Mac & Acorn)     | £169.00(C) |
| 3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New       | £185.00(C) |
| 5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv) RFE   | £49.95(C)  |
| 5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb          | £69.95(C)  |
| 5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested       | £69.95(C)  |
| 5 1/4" HP 9754B 850 Mb SCSI RFE tested               | £89.00(C)  |
| 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested | £195.00(C) |
| 8" FUJITSU M2322K 160Mb SMD I/F RFE tested           | £195.00(E) |

Hard disc controllers for MFM, IDE, SCSI, RLL etc. from £16.95

## THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

|  |        |
|--|--------|
| TELEBOX ST for composite video input type monitors | £36.95 |
| TELEBOX STL as ST but fitted with integral speaker | £39.50 |
| TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner | £69.95 |

For overseas PAL versions state 5.5 or 6 MHz sound specification. \*For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

## DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 1,000 Power Supplies Ex Stock Call for info / List.

## IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK  
6,000,000 items EX STOCK  
For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

## VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-LENT little used condition.

Tilt & Swivel Base £4.75  
VGA cable for IBM PC included.  
Only **£119 (E)** Order as MITS-SVGA

External cables for other types of computers CALL.

As New - Used on film set for 1 week only!  
15" 0.28 SVGA 1024 x 768 res. colour monitors.  
Swivel & tilt etc. Full 90 day guarantee. £145.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SVH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed  
Dimensions: W14" x H12 1/4" x 15 1/2" D.  
Only **£95 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen bums). In attractive square black plastic case measuring W10" x H10" x 1 1/2" D. 240 V AC mains powered.  
Only **£79.00 (D)**

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.  
Only **£125 (E)**

## 20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive leak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.


20"....£135 22"....£155 26"....£185 (F)

## SPECIAL INTEREST ITEMS

|   |           |
|---|-----------|
| MITS. FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400 KHz - 400 Hz 3 phase power sources - ex stock | £245 EPOA |
| IBM 8250 Type 1, Token ring base unit driver  | £950      |
| IBM 8250 Type 1, Token Ring iCS 20 port lobe modules  | £750      |
| IBM MAU Token ring distribution panel 8228-23-5050N   | £95       |
| AIM 501 Low distortion Oscillator 9KHz to 330KHz, IEEE  | £550      |
| Trend DSA 274 Data Analyser with G703(2M) 64 Jo   | £6500     |
| Marconi 6310 Programmable 2 to 22 GHz sweep generator   | £3750     |
| HP1650B Logic Analyser  | £3750     |
| HP3781A Pattern generator & HP3782A Error Detector  | £1800     |
| HP APOLLO RX700 system units  | £950      |
| HP621A Dual Programmable GPIB PSU 0-7 V 160 watts   | £175      |
| HP3081A Industrial workstation c/w Barcode swaped reader  | £675      |
| HP624 Rack mount variable 0-20V @ 20A metered PSU   | £1850     |
| HP54121A DC to 22 GHz four channel test set   | £650      |
| HP7580A A1 8 pen HPGL high speed drum plotter   | £650      |
| EG-G Brookdale 95035C Precision lock in amp   | £1425     |
| Video Eng. Mod 1200 computerised inspection system  | £1425     |
| Ling Dynamics 2Kw programmable vibration test system  | £1425     |
| Computer controlled 1056 x 560 mm X Y table & controller  | £1425     |
| Keithley 590 CV capacitor / voltage analyser  | £3750     |
| Racal ICR40 dual 40 channel voice recorder system   | £9500     |
| Fiskers 45KVA 3 ph On Line UPS - New basis Dec. 1995  | £2200     |
| ICI R5030U3V4 Cleanline ultrasonic cleaning system  | £1200     |
| Mann Tally MT645 High speed line printer  | £1150     |
| Intel SBC 486/133SE Multibus 486 system, 8Mb Ram  | £1450     |
| Zeta 3220-05 A0 4 pen HPGL plus fast drum plotters  | £1450     |
| Nikon HFX-11 (Ephiphot) exposure control unit   | £1450     |
| Motorola VME Bus Boards & Components List. SAE / CALL   | £550      |
| Trlo 0-18 vdc linear, metered 30 amp bench PSU. New   | £1950     |
| Fujitsu M3041D 600 LPM band printer   | £1250     |
| Perkin Elmer 2998 Infrared spectrophotometer  | £3750     |
| VG Electronics 1035 TELETEXT Decoding Margin Meter  | £950      |
| Andrews LARGE 3.1 m Satellite Dish & mount (For Voyager)  | £1995     |
| Sankonic SD 1501 40 channel digital Hybrid chart recorder   | £750      |
| TAYLOR HOBSON Tallylux amplifier / recorder   | £485      |
| System Video 1152 PAL waveform monitor  | £300      |
| Test Lab - 2 mir square quietised acoustic test cabinets  | £650      |
| Kenwood 9601 PAL Vectroscope - NEW  | £650      |

Please call for further details on the above items

## 19" RACK CABINETS

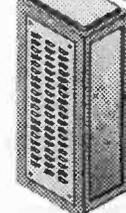

Superb quality 6 foot 40U  
Virtually New, Ultra Smart  
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

|   |             |
|---|-------------|
| OPT Rack 1 Complete with removable side panels. | £335.00 (G) |
| OPT Rack 2 Rack, Less side panels               | £225.00 (G) |

## 32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a designer style smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extra available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and a 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)  
Sold at LESS than a third of makers price!!

A superb buy at only **£195.00 (G)**

Over 1000 racks - 19" 22" & 24" wide  
3 to 44 U high. Available from stock!!  
Call with your requirements.

## TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost!! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size!! A host of available translation software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc etc. Imagine using your finger with 'Windows', instead of a mouse!! (a driver is indeed available!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00 (B)**  
Full MICROTUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

## LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95(A1)  
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data.  
Order as: XT RAM UG. 256k. £34.95 or 512k £39.95 (A1)

## FANS & BLOWERS

|  |                |
|--|----------------|
| EPSON D0412 40x40x20 mm 12v DC   | £7.95 10 / £65 |
| PAPST Type 612 60x50x25 mm 12v DC  | £8.95 10 / £75 |
| MITSUBISHI MMF-06D12DL 60x60x25 mm 12v DC  | £4.95 10 / £42 |
| MITSUBISHI MMF-08C12DM 80x80x25 mm 12v DC  | £5.25 10 / £49 |
| MITSUBISHI MMF-09B12DH 92x92x25 mm 12v DC  | £5.95 10 / £53 |
| EX-EKAKE 12-3.5 92x92x18 mm 12v DC   | £7.95 10 / £69 |
| PANCAKE AC fans. ALL TESTED 120 x 120 x 38 mm specify 110 or 240 v. £6.95. 80 x 80 x 38 mm - specify 110 or 240 v. £5.95 |                |
| IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240V NEW   | £79.95         |

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

Display Electronics

ALL MAIL & OFFICES  
Open Mon-Fri 9.00-5.30  
Dept PE. 32 Biggin Way  
Upper Norwood  
LONDON SE19 3XF

LONDON SHOP  
Open Mon - Sat 9.00 - 5.30  
215 Whitehorse Lane  
South Norwood  
On 684 bus route  
Ne. Thornton Heath & Seahurst Park SR Rail Stations

NEW DISTEL ©  
The Original  
FREE On line Database  
Info on 20,000 + stock items!  
RETURNING SOON!

ALL ENQUIRIES  
0181 679 4414  
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.00, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996 E & O.E. 06/6

**FREE  
SUPPLEMENT**

# NEXT MONTH

## EPE PIC TUTORIAL

*The best introduction to using PIC microcontrollers ever written! Based around the PIC16C84, this tutorial series takes you by the hand and leads you down the adventurous path of getting to know about PICs.*

*First we ask you to assemble a versatile demonstration p.c.b., with this board connected to the printer port of any IBM-compatible PC computer, we discuss in considerable detail the techniques and methods by which you can get the PIC to perform a variety of useful functions. From describing the very minimum of commands that a PIC requires, we examine the codes and the ways in which they need to be grammatically used, progressing from simply lighting an l.e.d., through sound generation and typical data display techniques, to a security alarm system – all with the same demo board.*

*At each stage of the thirty-odd tutorials, we encourage you to change various bits of the simple programs we supply you with on disk, loading them into the PIC and getting it to do other tasks related to each discussion. In this way you build up your experience and knowledge about PICs. At the end of the series, you should be perfectly capable of writing your own programs for PICs – and getting them to fulfil that task you've always wished you could put under microcontroller control!*

*So, get yourself on the PIC-it line – it's easy when you know how!*

**The EPE PIC Tutorial will be presented as three FREE Supplements in the March, April and May issues – don't miss it, order your copies NOW!**


## HANDY THING

*This project is an electronic analogue of the Swiss Army Knife. It probably can't be used for predicting earthquakes or eclipses, but it will do just about everything else.*

*It will detect static electricity, track interference and live wires, test continuity and assess very high resistances. It will also test whether or not a capacitor is functioning, check diodes and batteries and even test for dampness in walls. The creative user will no doubt come up with several other useful functions.*
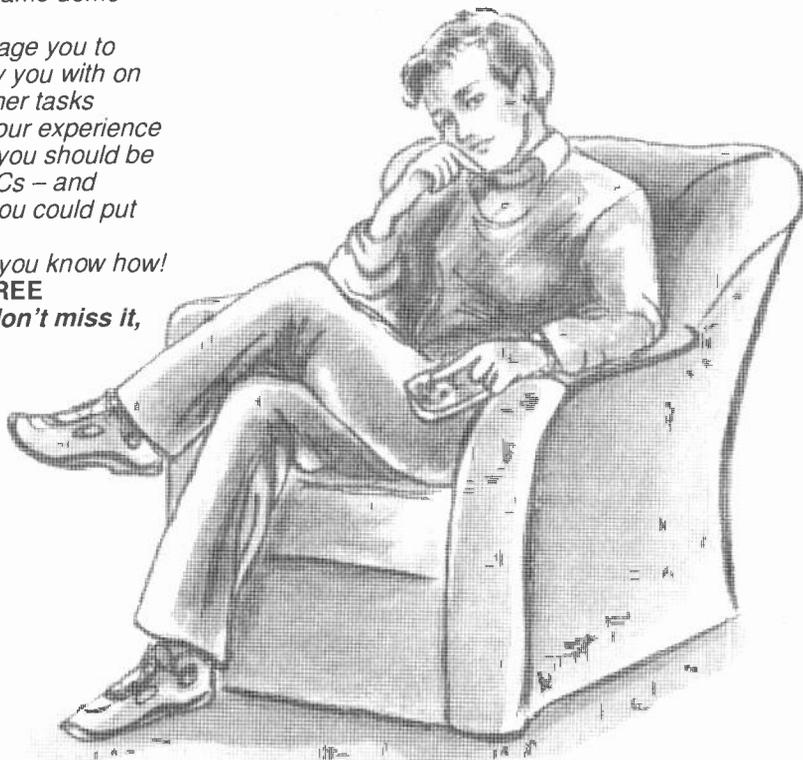
## AUDIO SYSTEM REMOTE CONTROLLER

*Adding Infra-Red remote control to your audio system is easier than you think. PIC based, this relatively simple unit can be used with an existing universal remote controller to switch between audio sources and to vary volume, treble, bass, etc. In this way you can add IR remote control to your existing hi-fi system without modifying the equipment.*



## SWITCH ACTUATED BURGLAR ALARM

*Although there are now some very high-tech alarms available, for most purposes something more basic is perfectly adequate. The burglar alarm project featured here is very simple indeed, and it relies on simple sensor switches to detect intruders. Nevertheless, it can provide very effective protection for a house or flat or even a caravan or boat, and it can also be used with sophisticated sensors if preferred.*

# NO ONE DOES IT BETTER

## PLUS ALL THE REGULAR FEATURES

**EVERYDAY**

**PRACTICAL**

# ELECTRONICS

**DON'T MISS AN ISSUE –  
PLACE YOUR ORDER NOW!**

**MARCH ISSUE ON SALE  
FRIDAY, FEBRUARY 6**

# SURVEILLANCE PROFESSIONAL QUALITY KITS

## No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

**Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!**

### UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible size of 10mm x 20mm including mic. 3V-12V operation. 500m range..... **£16.45**

### MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter. Just 17mm x 17mm including mic. 3V-12V operation. 1000m range..... **£13.45**

### STX High-performance Room Transmitter

High performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm, including mic. 6V-12V operation, 1500m range. **£15.45**

### VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9V-12V operation. 3000m range..... **£16.45**

### VXT Voice-Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range. **£19.45**

### HVX400 Mains Powered Room Transmitter

Connects directly to 240V A.C. supply for long-term monitoring. Size 30mm x 35mm. 500m range..... **£19.45**

### SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range..... **£22.95**

### SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range..... **£23.95**

### SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9V-12V operation..... **£22.95**

### ATR2 Micro-Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line..... **£13.45**

### UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range..... **£15.95**

### TLX 700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range..... **£13.45**

### STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range..... **£16.45**

### TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation..... **£22.95**

### CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation..... **£30.95**

### CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation..... **£50.95**

### QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range..... **£40.95**

### QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range..... **£40.95**

### QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m..... **£35.95**

### QRX 180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as pre-built and aligned module ready to connect on board so no difficulty setting up. Output to headphones. 60mm x 75mm. 9V operation..... **£60.95**

**A build-up service is available on all our kits if required.**

UK customers please send cheques, POs or registered cash. Please add £2.00 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send Sterling Bank Draft and add £5.00 per order for shipment. Credit card orders welcomed on 01827 714476.

**OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.**

## ★★★ Specials ★★★

### DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way d.i.l. switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits)..... **£50.95**

Individual Transmitter DLTX..... **£19.95**

Individual Receiver DLRX..... **£37.95**

### MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your HI-FI, tape or CD and transmits HI-FI quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle.

Size 27mm x 60mm. 9V operation. 250m range..... **£20.95**


**SUMA  
DESIGNS**

DEPT. EE  
THE WORKSHOPS, 95 MAIN ROAD,  
BAXTERLEY, NEAR ATHERSTONE,  
WARWICKSHIRE CV9 2LE  
VISITORS STRICTLY BY APPOINTMENT ONLY




**Tel/Fax:  
01827 714476**
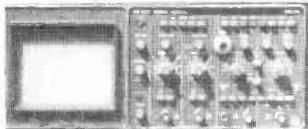
# HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS 'SCOPE' FOR IMPROVEMENT!




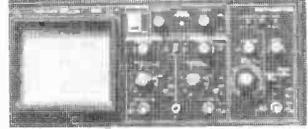PHILIPS PM3217 (This is a Proper Scope)  
Dual Trace 50MHz delay sweep, incl. 2 probes ..... £400



HC3502 Dual trace 20MHz 5mV-20V/Div. 0.2µs secs-0.5 sec/div  
X-Y, X5 magnifier, TV sync etc. .... Hardly used £150. Unused £200

### THE CLASSIC TEKTRONIX 400 SERIES

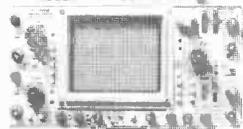

- 468 Digital storage dual trace 100MHz delay ..... £650
- 466 Analogue storage dual trace 100MHz delay ..... £395
- 475 Dual trace 200MHz delay sweep ..... £500
- 465 Dual trace 100MHz delay sweep ..... £400
- FLUKE PM3082 2+2 100MHz delay TB cursors ..... £1200
- PHILIPS PM3296A dual trace 40MHz dual TB delay cursors IEEE ..... £1750
- TEKTRONIX 2465A 4-trace 350MHz delay cursors etc. £2500
- TEKTRONIX TAS465 dual trace 100MHz delay cursors ..... £900
- TEKTRONIX TDS340 dual trace 100MHz 500Msa/samples dig storage ..... £1300
- TEKTRONIX 2215 dual trace 60MHz delay sweep ..... £400
- PHILIPS 3035 2+1 Ch 50MHz dual TB delay ..... £475
- PHILIPS PM97 dual trace 50MHz Scopemeter dig storage ..... £600
- GOULD OS1100 dual trace 30MHz ..... £200, with delay £240
- GOULD OS300 dual trace 20MHz ..... £200

AND REMEMBER ALL OUR EQUIPMENT IS TESTED PROPERLY



- MARCONI 2019A syn AM/FM signal gen 80kHz-1040MHz ..... £1800
- MARCONI 2019 syn AM/FM signal gen 80kHz-1040MHz ..... £1500
- MARCONI 2018 syn AM/FM signal gen 80kHz-520MHz ..... £800
- MARCONI 2017 AM/FM signal gen 10kHz-1024MHz ..... £1750



- FARNELL SSG520 syn Am/Fm signal gen 10-520MHz ..... £325
- FARNELL PSG520 syn AM/FM sig gen 10-520MHz portable. £450

- MARCONI 6311 programmable sweep gen 10MHz-20GHz ..... £4500
- MARCONI 2022G AM/FM signal gen 10kHz-1GHz ..... £2000
- HP 8656A syn signal gen 0.1-990MHz ..... £1500
- HP 8640B PhaseLock/syn sig gen 500kHz-512MHz ..... £750
- HP 8640A AM/FM signal gen 500kHz-1024 MHz ..... £650
- PHILIPS PM5193 programmable syn func gen 0-1MHz-50MHz ..... £1500
- PHILIPS PM5192 programmable syn func gen 0-1MHz-20MHz ..... £1000
- HP 3325A syn function gen 21MHz ..... £1250
- PHILIPS PM5134 sweep func gen 0-001Hz-20MHz sine/sq/tri etc. .... £400
- PHILIPS PM5132 sweep func gen 0-1Hz-2MHz sine/sq/tri etc. .... £250



- CLASSIC AVON VAS in case with batteries and leads ..... £50
- FLUKE 77 DMM 3 1/2 digit with carrying case and leads ..... £60




- RACAL COUNTERS**
- 9918 10Hz-560MHz ..... £125
- 9916 10Hz-520MHz ..... £150
- 9904 DC-50MHz ..... £50




- RACAL 1998 counter 1-3GHz GPIB ..... £650
- RACAL 1991 counter/timer 160MHz ..... £450
- RACAL 1990 counter 120MHz ..... £300
- SOLARTRON 7151 DMM 6 1/2 digit IEEE ..... £450
- SOLARTRON 7150 DMM 6 1/2 digit IEEE ..... £300

True RMS
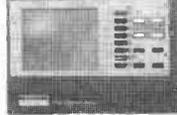
### LOOK!!! BRAND NEW OSCILLOSCOPES - NEVER USED. LIMITED STOCK



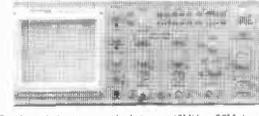- DMS 3850A digital storage/DMM, handheld LCD display, 2 channel 50Ms/s, auto range, 4-digit DVM/capacitance/frequency counter, battery operation or external 7.5-9V d.c. i.e. AC adaptor (not supplied), RS232, comes in black carrying pouch complete with 2 scope probes, DMM leads, manual ..... FOR ONLY £400



- DTS 40 digital storage, dual trace 40MHz, 20Ms/s storage, cursors and on-screen readout, sweep delay, interface etc. etc., supplied unused in original box complete with 2 probes and manual ..... AMAZING VALUE AT £400



- DTA 20/40/60 dual trace with air magnification, TV trig etc. etc. lots of specification ..... £100



- DTA20 dual trace 20MHz ..... £225
- DTA40 dual trace 40MHz-12kV EHT ..... £300
- DTA60 dual trace 60MHz-12kV EHT ..... £375



- All unused and boxed, supplied with 2 probes and manual
- DTV 100 3-channel 100MHz sweep delay etc. .... £425
- DTV 60 3-channel 60MHz sweep delay etc ..... £375
- DTV 20 dual trace 20MHz ..... £200

All unused, boxed with 2 probes and Manual

### NEW AND HARDLY USED




- PANASONIC VP8177A FM/AM signal generator, 100KHz-100MHz, FM 0-100KHz, output 19dB-99dB, AM 60%, 32 preset memory, digital display frequency and output ..... Used £450 Unused £750
- PANASONIC VP7637A stereo signal generator, generates broadcast FM-RDS/ARI, preset memory, GPIB ..... Used £400 Unused £700




- KENWOOD FL180A wow/flutter meter, 0-0.03%-10% Freq 3kHz-15kHz 1m.s. average/peak, weighted filters, digital display of rpm, 4-digit freq counter (0-0.1kHz-9.999kHz/0-0.1kHz-55kHz) ..... Used £400 Unused £500



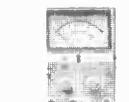
- POWER SUPPLY Model HSP3010, 0-30V, 0-10A, current limiting, 2 meters ..... Used £160 Unused £200



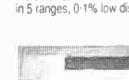- GOODWILL GVT427 dual channel AC millivoltmeter, 10µV-300V in 12 ranges, frequency 10Hz-1MHz ..... Used £100 Unused £125



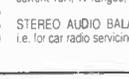- GOODWILL GAG-808G audio generator, sine/square 10Hz-1MHz in 5 ranges, 0-1% low distortion, 5 steps output attenuator ..... Used £80



- GOODWILL GFC 8010G frequency counter, range 1Hz-120MHz, 8-digit display, 15mV r.m.s. sensitivity ..... Unused £75



- ANALOGUE MULTIMETER Model HC260TF AC/DC volts, DC current 10A, 17 ranges, continuity buzzer, transistor tester ..... Unused £15



- STEREO AUDIO BALANCE to UNBALANCED CONVERTOR, i.e. for car radio servicing ..... Unused £20

## STEWART of READING

110 WYKEHAM ROAD, READING, BERKS. RG6 1PL  
Telephone: (0118) 9268041. Fax: (0118) 9351696

Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)



Used Equipment - GUARANTEED. Manuals supplied  
This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering.  
CARRIAGE all units £16. VAT to be added to Total of Goods and Carriage

# NOW AVAILABLE

## RANGER 2 for Windows 95™

### The Complete, Integrated Schematic & PCB Layout Package

#### Windows Ranger 2

For Windows 95 & NT

- New Hierarchical Circuit
- Split Devices • Gate & Pin Swap
- New Edit Devices in Circuit
- Copper Fill • Power Planes
- Autorouter • Back Annotation

£250

**Ranger 2 Outputs:**  
Full Windows Outputs  
Plus - HP-GL  
Gerber  
NC Drill  
AutoCad DXF

#### Windows Ranger 2 with Spectra SP2

Ranger & Spectra Autorouter provide the most cost effective PCB Design system available. A powerful, intuitive system at an outstanding price!

£500

#### Windows Ranger 2 Upgrade

Upgrade your existing PCB Package to Windows Ranger 2.

£150

Demo disc available £5.00 (Prices exc VAT/P&P)

Call 01730 260062

Fax 01705 599036

Old Buriton Limeworks, Kiln Lane,  
Buriton, Petersfield, Hants. GU31 5JZ




**SEETRAX**  
Advanced Systems & Technology for PCB Manufacture

## £1 BARGAIN PACKS - List 4

One item only per pack unless otherwise stated.  
See last month for Nos 1, 2 and 3 and next month for No 5.

**IN-HANDLE MAINS ON/OFF SWITCHES**, sometimes known as pistol grip switches, pack of 2, Order Ref: 839.  
**5A DOUBLE-POLE CHANGEOVER TOGGLE SWITCHES**, ideal reversing DC motors, etc., pack of 2, Order Ref: 841.  
**3M 2-CORE CURLY LEAD**, 5A, Order Ref: 846.  
**1M 3-CORE CURLY LEAD**, 13A, Order Ref: 847.  
**AC SHADED-POLE MAINS MOTOR** with base fixing plate, Order Ref: 848.  
**4" PLASTIC DIAL**, fits flatted 1/4" spindle, transparent so dial can be underneath, pack of 2, Order Ref: 851.  
**2,500 µF 12V CAPACITORS**, pack of 5, Order Ref: 853.  
**DELAY SWITCH** on BTG base, Order Ref: 854.  
**3 CHANGEOVER RELAY**, 6V AC or 3V DC, 3 changeover contacts, Order Ref: 859.  
**NORMALLY ON, V3 MICROSWITCH**, pack of 4, Order Ref: 862.  
**HIVAC NUMICATOR TUBE**, Hivac ref XN3, Order Ref: 865.  
**DITTO** but reference XN11, Order Ref: 866.  
**SUB MIN NORMALLY OFF MICROSWITCH**, pack of 4, Order Ref: 867.  
**SUB MIN CHANGEOVER MICROSWITCH**, pack of 3, Order Ref: 868.  
**EX-GPO TELEPHONE DIAL**, rotary type, Order Ref: 904.  
**QUARTZ LINEAR HEATING TUBES**, 360W but 110V so would have to be joined in series, pack of 2, Order Ref: 907.  
**2" ROUND LOUDSPEAKERS**, 50 ohm coil, pack of 2, Order Ref: 908.  
**EDGE TYPE PUSH SWITCHES**, BCD system, pack of 2, Order Ref: 915.  
**10M 4-CORE FLEX**, suitable for telephone extension, Order Ref: 918.  
**OLD TYPE KETTLE ELEMENT**, 2-pin plug, Order Ref: 925.  
**6V 24W HEADLAMP BULB**, normal BC plug in cap, Order Ref: 928.  
**40 LAMP UNIT** to make a figure or letter display, Order Ref: 930.  
**10K HORIZONTAL PRESET RESISTORS**, pack of 10, Order Ref: 931.  
**1M 64-WAY RIBBON CABLE**, Order Ref: 932.  
**MAINS PSU**, 15V 320mA AC, Order Ref: 934.  
**15V + 15V 1.5VA POTTED PCB MAINS TRANSFORMER**, Order Ref: 937.  
**16 OHM 3" SPEAKERS**, pack of 2, Order Ref: 962.  
**MAINS RELAY** with 15A changeover contacts, Order Ref: 965.  
**IN-LINE FUSEHOLDERS**, take 20mm fuse, just cut the flex and insert, pack of 4, Order Ref: 969.  
**OBLONG PANEL MOUNTING NEONS**, pack of 4, Order Ref: 970.  
**COPPER CLAD PANELS**, size 7" x 4", pack of 2, Order Ref: 973.  
**STANDARD SIZED AUDIO PLUG** adapted to take two 3mm plugs, Order Ref: 974.  
**3.5MM JACK PLUGS**, pack of 10, Order Ref: 975.  
**DRILL CONTROL CASE**, ready punched and with control logos, Order Ref: 979.  
**8µF 350V ELECTROLYTICS**, pack of 2, Order Ref: 987.  
**SCREW-IN NEON BULBS**, pack of 4, Order Ref: 990.  
**VERY SMALL SLIDE SWITCH**, pack of 4, Order Ref: 992.  
**50µF + 50µF 350V WORKING ELECTROLYTICS**, pack of 2, Order Ref: 994.  
**8700µF 7V WORKING ELECTROLYTIC**, Order Ref: 996.  
**1 MEG PRESET POTS**, pack of 4, Order Ref: 998.  
**WHITE PROJECT BOX**, 78mm x 115mm x 35mm, Order Ref: 1006.  
**SLIDELOCK 15A FUSES**, panel mounting, pack of 3, Order Ref: 1011.  
**6V SOLENOIDS**, good length pull, pack of 2, Order Ref: 1012.  
**RELAY WITH 3 SETS OF CHANGEOVER 8A CONTACTS**, 24V AC or 12V DC, 3 sets 8A changeover contacts, Order Ref: 1016.  
**WHITE TOGGLE SWITCH**, push-in spring retain type, pack of 4, Order Ref: 1019.  
**2M MAINS LEADS**, 2-core, black outer, pack of 4, Order Ref: 1020.  
**2M MAINS LEADS**, 3-core, black outer, pack of 3, Order Ref: 1021.  
**FERRITE SLAB AERIAL** with coils, pack of 2, Order Ref: 1027.  
**12V DC POLARISED RELAY**, 2 changeover contacts, Order Ref: 1032.  
**12in. x 12in. PAXOLIN PANEL**, medium thickness, Order Ref: 1033.  
**TUNING CAPS**, solid DIA, for LW and MW, pack of 2, Order Ref: 37.  
**TRIMMER CAPS**, screw down type, 10 assorted, Order Ref: 38.  
**IF TRANSFORMERS**, 465kHz, pack of 4, Order Ref: 40.  
**SOCKETS** for stripboard, make your own IC holders, pack of 10, Order Ref: 54.  
**6 1/2" 4 OHM SPEAKER**, Order Ref: 137.  
**100K STEREO POTS**, pack of 4, Order Ref: 143.  
**FUSE HOLDERS**, chassis mounting for 20mm fuses, pack of 5, Order Ref: 144.  
**SOCKET COVERS**, child protectors for twin 13A sockets, pack of 4, Order Ref: 149.  
**DITTO** but for single 13A sockets, pack of 4, Order Ref: 150.  
**POT CORES**, circular, ferrite, 54mm x 18mm, pack of 2 pairs, Order Ref: 156.  
**AIR SPACED TUNER**, 20pF with 1/4" spindle, Order Ref: 182.  
**METAL BOX**, slightly sloping, 8x3x4, 1 only, Order Ref: 209.  
**TELEPHONE LEADS**, 5-core curly reinforced telephone leads, pack of 2, Order Ref: 213.  
**STEREO PRE-AMP**, Mullard 9001, 1 only, Order Ref: 216.  
**PUSH-ON TAGS** for 1/4" spades, pack of 100, Order Ref: 217.  
**DITTO** but right-angled, pack of 100, Order Ref: 218.
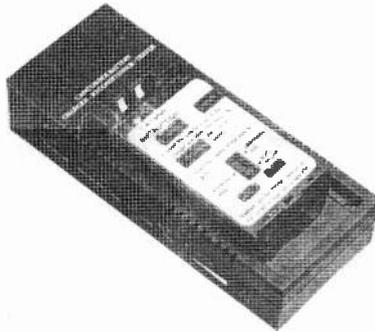
## CAMCHARGER CAMCORDER BATTERY QUICK CHARGER (WITH RECONDITIONER & TESTER)



Brand new and boxed. Normal price £35, yours for £15, Order Ref: 15P73.

## TOROIDAL MAINS TRANSFORMERS

All with 220/240V primary winding.  
**0-30V + 0-30V** at 120VA, would give you 30V at 4A or 60V at 2A, price £8. Order 8PE2. Order Ref: 8PG2. **0-110V + 0-110V** at 120VA would give you 110V at just over 8A or 220V at 1/2A, price £8, Order Ref: 8PG3. **0-35V + 0-35V** at 150VA would give you 35V at 4A or 70V at 2A. Price £8. Order Ref: 8PG9. **0-35V + 0-35V** at 220VA would give you 35V at 6 1/2A or 70V at 3 1/4A, price £9, Order Ref: 9PG4. **0-110V + 0-110V** at 220VA would give you 110V at 2A or 220V at 1A, price £10, Order Ref: 10PG5. **0-45V + 0-45V** at 500VA would give you 45V at 11A or 90V at 5 1/2A, price £20, Order Ref: 20PG7. **0-110 + 0-110V** at 500VA would give you 110V at 5A or 220V at nearly 3A, price £25, Order Ref: 25PG7.



**SUPER WOOFERS**. A 10" 4ohm with a power rating of 250W music and normal 150W. Normal selling price for this is £55 + VAT, you can buy at £29 including VAT and carriage, Order Ref: 29P7. The second one is a 8" 4ohm, 200W music, 100W normal. Again by Challenger, price £18, Order Ref: 18P9. Deduct 10% from these prices if you order in pairs or can collect. These are all brand new in maker's packing.



**SOLDERING IRON**. Super mains powered with long life ceramic element, heavy duty 40W for that extra special job. Complete with plated wire stand and 245mm leads, £3, Order Ref: 3P221.

## YOU SAVE £40

**THE JAP MADE 12V 12A-SEALED BATTERY** from regular suppliers costs £50, you can have one from us for only £10 including VAT if you collect or £12 if we have to send. Being sealed it can be used in any



position and is maintenance free. All in tip top condition and fully guaranteed, Order Ref: 12P32. Or if you want a smaller one we have 12V 2.3AH, regular price £14, yours for only £3.50, Order Ref 3.5P11.

**FLASHING BEACON**. Uses an XENON tube and has amber-coloured dome with separate bracket, 12V operated. Price only £5, Order Ref: 5P.267.

**HIGH RESOLUTION MONITOR**. 9" by Philips, in metal frame for easy mounting. Brand new, offered at less than the price of the tube alone, £15, Order Ref: 15P1.

**15W 8" SPEAKER AND 3" TWEETER**. Amstrad, made for their high quality music centre, £4 per pair, Order Ref: 4P57.

**INSULATION TESTER WITH MULTIMETER**. Internally generates voltages which enables you to read insulation directly in megohms. The multimeter has four ranges, AC/DC Volts, 3 ranges milliamps, 3 ranges resistance and 5 amp range. These instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50, yours for only £7.50 with leads, carrying case £2 extra, Order Ref: 7.5P4. We have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply, diagram, £3, Order Ref: 3P176.

**250W LIGHT DIMMER**. Will fit in place of normal wall switch, only £2 each, Order Ref: 2P380. Note these are red, blue, green or yellow but will take emulsion to suit the colour of your room. Please state colour required.

**LCD 3 1/2" DIGIT PANEL METER**. This is a multi-range voltmeter/ammeter using the A-D converter chip 7106 to provide five ranges each of volts and amps. Supplied with full data sheet. Special snip price of £12, Order Ref: 12P19.

**MINI BLOW HEATER**. 1kW, ideal for under desk or airing cupboard, etc. Needs only a simple mounting frame, £5, Order Ref: 5P23.

**MEDICINE CUPBOARD ALARM**. Will warn when cupboard door is opened. Light makes the bell ring. Neatly cased, requires only a battery, £3, Order Ref: 3P155.

**DON'T LET IT OVERFLOW**. Be it bath, sink, cellar, sump, etc., this device will tell you when the water has risen to the pre-set level. Adjustable, neatly cased for wall mounting, £3, Order Ref: 3P156.

**DIGITAL THERMOMETER**. Suitable for outdoors or indoors, has an extra wide temperature range -50° to +70°C, complete with heavy duty battery which should last several years. Its sensor can be outside, but with the read-out inside, £4, Order Ref: 4P104.

## SMART HIGH QUALITY ELECTRONIC KITS

All kits are complete with PCB and other components in a blister pack. If you want more information about them, we have copies of the illustrated Smart catalogue available price £1.

| Cat. No. | Description                               | Price £ | Cat. No. | Description                        | Price £ |
|----------|---|---------|----------|------------------------------------|---------|
| 1003     | 5 watt electronic siren                   | 2.53    | 1090     | Stress meter                       | 3.22    |
| 1005     | Touch switch                              | 2.87    | 1093     | Windscreen wiper controller        | 3.68    |
| 1008     | SF function generator                     | 6.90    | 1094     | Home alarm system                  | 12.42   |
| 1010     | 5-input stereo mixer, with monitor output | 19.31   | 1095     | Lead acid battery charger          | 3.45    |
| 1016     | Loudspeaker protection unit               | 3.22    | 1100     | 2 x 18 watt integrated amplifier   | 18.39   |
| 1017     | Linear CB 30W amp                         | 4.70    | 1101     | Dollar tester                      | 4.70    |
| 1020     | 0-5 min. time switch                      | 4.70    | 1103     | L.E.D. power meter                 | 1.84    |
| 1023     | Dynamic headphone preamp                  | 2.50    | 1106     | Thermometer with l.e.d.s           | 6.90    |
| 1025     | 7 watt hi-fi power amplifier              | 2.53    | 1107     | Electronics to help win the pools  | 3.68    |
| 1026     | Running lights                            | 4.60    | 1112     | Loudspeaker protection with delay  | 4.60    |
| 1027     | NiCad battery charger                     | 3.91    | 1113     | 2 x 18 watt power amplifier        | 5.98    |
| 1030     | Light dimmer                              | 2.53    | 1115     | Courtesy light delay               | 2.07    |
| 1032     | Stereo tone control                       | 3.55    | 1118     | Time switch, with triac, 0-10 mins | 4.14    |
| 1035     | Space sound effects                       | 2.30    | 1119     | Telephone line recording device    | 5.25    |
| 1039     | Stereo VU meter                           | 4.60    | 1123     | Morse code generator               | 1.84    |
| 1042     | AF generator 250Hz-16kHz                  | 1.70    | 1124     | Electronic bell                    | 2.76    |
| 1043     | Loudness stereo unit                      | 3.22    | 1125     | Telephone lock                     | 2.68    |
| 1047     | Sound switch                              | 5.29    | 1126     | Microphone preamplifier            | 4.60    |
| 1048     | Electronic thermostat                     | 3.68    | 1127     | Microphone tone control            | 4.60    |
| 1050     | 3-input hi-fi stereo preamplifier         | 12.42   | 1128a    | Power flasher 12V d.c.             | 2.53    |
| 1052     | 3-input mono mixer                        | 6.21    | 1133     | Stereo sound-to-light              | 5.26    |
| 1053     | Electronic metronome                      | 3.22    |          |                                    |         |
| 1054     | 4-input instrument mixer                  | 2.76    |          |                                    |         |
| 1056     | 8V-20V 8A stabilised power supply         | 12.42   |          |                                    |         |
| 1057     | Cassette head preamplifier                | 3.22    |          |                                    |         |
| 1059     | Telephone amplifier                       | 4.60    |          |                                    |         |
| 1060     | +40V 8A power supply                      | 8.28    |          |                                    |         |
| 1061     | 12V 1/2A stabilised power supply          | 3.36    |          |                                    |         |
| 1062     | 5V 0.5A stabilised supply for TTL         | 2.30    |          |                                    |         |
| 1063     | 12V 2A power supply                       | 2.30    |          |                                    |         |
| 1064     | +12V 0.5A stabilised supply               | 3.22    |          |                                    |         |
| 1067     | Stereo VU meter with leads                | 9.20    |          |                                    |         |
| 1068     | 18V 0.5A stabilised power supply          | 2.53    |          |                                    |         |
| 1070     | Hi-Fi preamplifier                        | 7.47    |          |                                    |         |
| 1085     | D.C. converter: 12V to 6V or 7.5V or 9V   | 2.53    |          |                                    |         |
| 1086     | Music-to-light for your car               | 4.60    |          |                                    |         |
| 1089     | L.E.D. flasher/555 tester                 | 1.61    |          |                                    |         |

### TERMS


Send cash, PO, cheque or quote credit card number - orders under £25 add £3.50 service charge.

**J & N FACTORS**  
**Pilgrim Works (Dept. E.E.)**  
**Stairbridge Lane, Bolney,**  
**Sussex RH17 5PA**  
**Telephone: 01444 881965**

# B<sup>2</sup> Spice & B<sup>2</sup> Logic

**New Features  
Outstanding Performance**

**New Version**

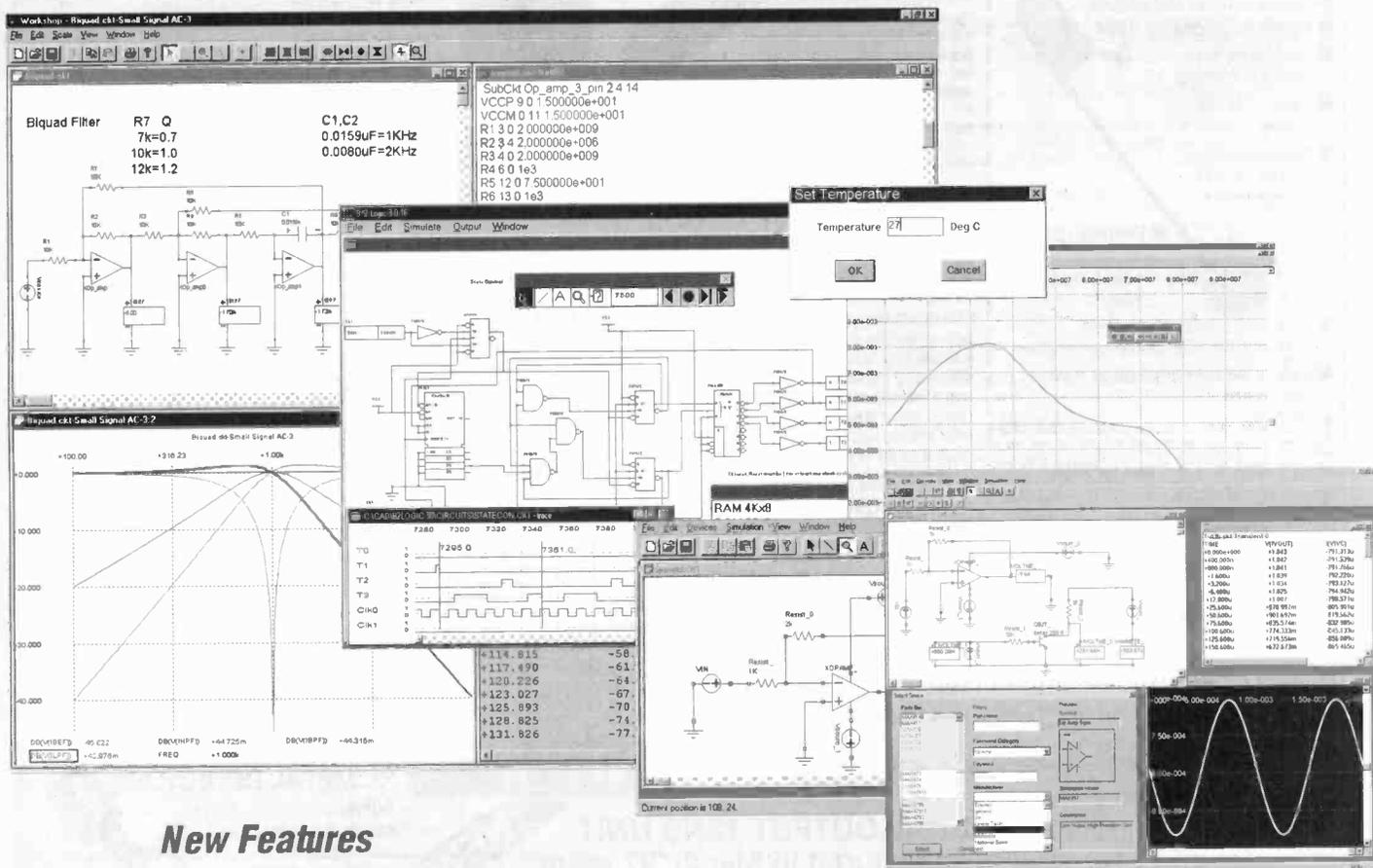

## New Features

- Even more simulation options.
- Perform full temperature and parameter sweeps.
- New graphical functions.
- New libraries of parts including the entire Texas Instruments library.
- Nothing extra to pay for the libraries...they are all included in the price.

## As always..

- Everything you would expect from a professional quality SPICE simulator.
- Fully integrated and interactive.
- No limit no maximum circuit size.
- Free technical support.
- 30 day money back guarantee.

## Software for design engineers

B<sup>2</sup> Spice & B<sup>2</sup> Logic will give you the accurate results you need quickly and easily.

This software is used by thousands of designers, research institutions and universities around the world. But the best way to be certain that it's right for you is to try it, which is we're are giving you the opportunity to do, risk free for 30 days.

For more information call:

**01603 872331**

<http://www.paston.co.uk/spice>  
email: [rd.research@paston.co.uk](mailto:rd.research@paston.co.uk)

B<sup>2</sup> Spice for analogue simulation £199  
B<sup>2</sup> Logic for digital simulation £199  
Special bundle price £295  
B<sup>2</sup> Spice Lite (ideal for first time users) £42.75

Prices quoted exclude VAT  
Existing users. If you have purchased a copy within the last 12 months you are entitled to a free upgrade.

**RD Research**

Research House, Norwich Road, Eastgate, Norwich. NR10 4HA  
Postage & packing £4.50. All trademarks are acknowledged.

Now available direct from Maplin Electronics & Cirkuit Distribution Ltd.



## MAIL ORDER ONLY ● CALLERS BY APPOINTMENT

### EPE MICROCONTROLLER PI. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with MC control of all timing functions and advanced pulse separation techniques.

- New circuit design 1994
- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847.....£63.95

### PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is used to give maximum output without any special setting up.

KIT 842.....£22.56

### SUPER ACOUSTIC PROBE

Our very popular project - now with ready built probe assembly and diecast box. Picks up vibrations amplifies, and drives headphones. Sounds from engines, watches, and speech through walls can be heard clearly. Useful for mechanics, instrument engineers and nosey parkers! A very useful piece of kit.

KIT 865.....£29.95

### KITS UNDER £10.00

Older style kits - some using P.C.B., others stripboard. All popular 'oldies'. Instructions included with each kit.

- K386 Drill Speed Controller.....£9.95
- K561 Light Rider Lapel Badge.....£9.98
- K101 Electronic Dice.....£7.50
- K242 Two Intercom.....£6.50
- K455 Electronic Doorbell.....£9.25
- K816 Stepper Motor Interface.....£8.52
- K481 Soldering Iron Controller.....£6.90
- K512 Mains Tester/Fuse Finder.....£10.00
- K776 Lie Detector.....£9.90
- K240 Egg Timer.....£7.85
- K181 Soil Moisture.....SOLD
- K263 Buzz Off.....£6.49
- K569 Automatic Car Alarm.....£9.95

Reprints of these special kits - send 50p stamps per kit + stamped addressed envelope

### MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2-5A.

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.




Kit No. 845.....£64.95

### \*NEW

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEEP FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B, coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor

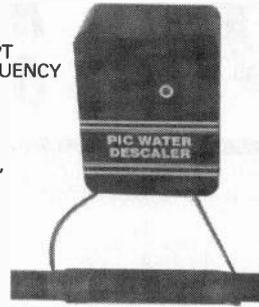

KIT 868 .....£22.95 POWER UNIT.....£3.99

### MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pests/pests away from newly sown areas, play areas, etc. Uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION

Plug-in power supply £4.99

KIT 867.....£19.99

KIT + SLAVE UNIT.....£32.50



### WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856.....£28.00

## ★ TENS UNIT ★

### DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

KIT 866.... Full kit including four electrodes £32.90



### 1000V & 500V INSULATION TESTER

Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms. Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95

### SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with 'MERRY XMAS'. Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849.....£16.99

### 12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£28.51

### SUPER BAT DETECTOR

1 WATT O/P, BUILT IN  
SPEAKER, COMPACT CASE  
20kHz-140kHz

NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full bridge' audio amplifier i.c., internal speaker, and head-phone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

KIT 861.....£24.99

ALSO AVAILABLE Built & Tested ....£39.99

### E.E. TREASURE HUNTER PI. METAL DETECTOR MK1

Magenta's highly developed & acclaimed design. Quartz crystal controlled circuit MOSFET coil drive. D.C. coupled amplification. Full kit includes PCB, handle, case & search coil.

- KIT INC. HEADPHONES
- EFFICIENT CMOS DESIGN
- POWERFUL COIL DRIVE

- DETECTS FERROUS AND NON-FERROUS METAL - GOLD, SILVER, COPPER ETC.

- 190mm SEARCH COIL
- NO 'GROUND EFFECT'

KIT 815.....£45.95



## SIMPLE PIC PROGRAMMER

INCREDIBLE LOW  
PRICE!

Kit 857 **£12.99**

INCLUDES 1-PIC16C84 CHIP  
SOFTWARE DISK, LEAD  
CONNECTOR, PROFESSIONAL  
PC BOARD & INSTRUCTIONS

Power Supply **£3.99**

EXTRA CHIPS:  
PIC 16C84 **£7.36**

Based on the design in February '96 *EPE* article, Magenta have made a proper PCB and kit for this project. PCB has 'reset' switch, Program switch, 5V regulator and test L.E.D.s. There are also extra connection points for access to all A and B port pins.

## PIC16C84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16C84  
WITH DEMO PROGRAM  
SOFTWARE DISK, PCB,  
INSTRUCTIONS AND  
16-CHARACTER 2-LINE  
LCD DISPLAY

Kit 860 **£17.99**

Power Supply **£3.99**

FULL PROGRAM SOURCE  
CODE SUPPLIED - DEVELOP  
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers - Just waiting for your application!

★ Chip is pre-programmed with demo display ★

## SUPER PIC PROGRAMMER

**NEW!**

- READS, PROGRAMS, AND VERIFIES
- WINDOWS™ SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP ● HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED PIN SOCKETS FOR 18, 28, AND 40 PIN ICs.

● SEND FOR DETAILED  
INFORMATION - A  
SUPERB PRODUCT AT AN  
UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply **£3.99**

## PIC STEPPING MOTOR DRIVER

**NEW!**

INCLUDES: PCB,  
PIC16C84 WITH  
DEMO PROGRAM,  
SOFTWARE DISK,  
INSTRUCTIONS  
AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED.  
ALSO USE FOR DRIVING OTHER  
POWER DEVICES e.g. SOLENOIDS.

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor - up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

## PIC16C84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16C84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING - 10 CHASE PATTERNS
- OPTO ISOLATED
- 4 X 3 KEYPAD CONTROL
- SPEED CONTROL POT.
- HARD FIRED TRIACS
- 4 CHANNELS @5 AMPS

Now features full  
4-channel chaser software  
on DISK and  
pre-programmed  
PIC16C84 chip. Easily  
re-programmed for your  
own applications.  
Software source code is  
fully 'commented' so that  
it can be followed easily.

Kit 855 **£39.95** LOTS OF OTHER APPLICATIONS

## DOLBY PRO-LOGIC DECODER



Brings full Genuine PRO-LOGIC Surround Sound to you at a fantastic price. The circuit meets all 'DOLBY' specifications, with "Stereo", "3-Stereo" and "Surround" selections. Featured in *EPE* APRIL '96

Full kit with case and transformer,  
Kit Ref: 869 **£124.99**  
Short Form KIT, Kit Ref: 858  
**£99.00**

\*DOLBY and the double-D symbol are trademarks.

## DC Motor/Gearboxes

Our Popular and Versatile DC motor/Gearbox sets. Ideal for Models, Robots, Buggies etc. 1-5 to 4-5V Multi ratio gearbox gives wide range of speeds.



LARGE TYPE - MGL **£6.95**  
SMALL - MGS - **£4.77**


## Stepping Motors

MD38...Mini 48 step...**£8.65**  
MD35...Std 48 step...**£12.98**  
MD200...200 step...**£16.80**  
MD24...Large 200 step...**£22.95**


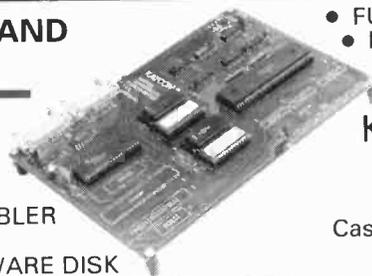
## 68000 DEVELOPMENT AND TRAINING KIT

- USED WORLDWIDE IN SCHOOLS COLLEGES & UNIVERSITIES
- DOUBLE EUROCARD, 2 SERIAL PORTS
- NOW WITH EXPANDED RAM & ROM
- FULL FEATURED MONITOR & LINE ASSEMBLER IN ROM
- CROSS-ASSEMBLER AND COMMS SOFTWARE DISK



- FULL 8MHz 68000 16-BIT DATA BUS
- EXPANDABLE - PIT OPTION 68230
- FULL MANUAL PLUS DATA
- SUPER LOW PRICE:

KIT 601.....**£69.95**

EXTRAS: 9-way P.C. lead **£6.99**

25-way P.C. lead **£6.99**

Case - black bottom, clear lid - **£5.99**

PSU +5V, +12V, -12V **£12.99**


## Mini-Lab & Micro Lab Electronics Teach-In 7

As featured in *EPE* and now published as Teach-In 7. All parts are supplied by Magenta. *Teach-In 7* is £3.95 from us or *EPE*  
Full Mini Lab Kit - £119.95 - Power supply extra - £22.55  
Full Micro Lab Kit - £155.95 Built Micro Lab - £189.95
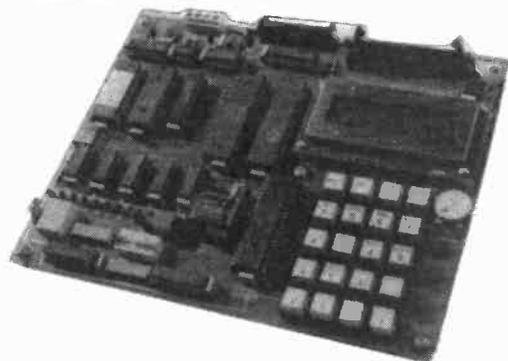
# MAGENTA

All prices  
include VAT.  
Add **£3.00** p&p.

Tel: 01283 565435 Fax: 01283 546932 E-mail: [Magenta\\_Electronics@compuserve.com](mailto:Magenta_Electronics@compuserve.com)





Station Road, Cullercoats, Tyne & Wear, NE30 4PQ



All Major Credit cards Accepted

Prices Exclude Vat @17.5%. Add £1.25 carriage & Vat to all orders. Cheques / Postal orders payable to ESR Electronic Components.

See Next / Last Months Ad. for COMPONENT ACCESSORIES

Table of electronic components including 4000 Series, 74HC Series, and 74LS Series. Columns include part numbers and prices.

Table of electronic components including EPROM's, RAM, A/D Converters, Data Acquisition, Thyristors, Triacs, Diac, Si. Switch, Transistors, Voltage Regulators, Diodes, and Linear ICs. Columns include part numbers and prices.

Table of electronic components including Bridge Rectifiers, Thyristors, Triacs, Diac, Si. Switch, Transistors, Voltage Regulators, Diodes, and Linear ICs. Columns include part numbers and prices.

Table of electronic components including Electrolytic Radial, Electrolytic Axial, Ceramic Mini Disc, Dipped Ceramic Multilayer, Resistors - Please State Value Required, Preset Resistors - Please State Value Required, and Potentiometers - Please State Value Required. Columns include part numbers and prices.

Tel: 0191 2514363 Fax: 0191 2522296 Email: sales@esr.co.uk http://www.esr.co.uk

**EVERYDAY****PRACTICAL****ELECTRONICS****VOL. 27 No. 2 FEBRUARY '98****Editorial Offices:**EVERYDAY PRACTICAL ELECTRONICS EDITORIAL  
ALLEN HOUSE, EAST BOROUGH, WIMBORNE  
DORSET BH21 1PF

Phone: Wimborne (01202) 881749

Fax: (01202) 841692. **Due to the cost we cannot reply to overseas orders or queries by Fax.**

E-mail: editorial@epemag.wimborne.co.uk

Web Site: http://www.epemag.wimborne.co.uk

See notes on **Readers' Enquiries** below – we regret lengthy technical enquiries cannot be answered over the telephone.**Advertisement Offices:**EVERYDAY PRACTICAL ELECTRONICS  
ADVERTISEMENTS

MILL LODGE, MILL LANE

THORPE-LE-SOKEN, ESSEX CO16 0ED

Phone/Fax: (01255) 861161

**ANOTHER ERA**

Some interesting correspondence has come in recently from a couple of readers who would like us to support computers other than PCs – in both cases the readers are still using BBC Micros. We actually dropped our dedicated support of the BBC Micro through *Interface* back in December 1990 (over seven years ago now). Frankly it is simply no longer possible for us to offer any special support for machines from another era, the time and cost involved in doing this is simply not commercially sensible. While we do try to offer a service to readers we do also need to make a living and therefore make a profit.

This led me to take a look at how many readers own or have access to PCs and I was pleased to see that ninety-five per cent of *EPE* readers can get their hands on a PC, while seventy-nine per cent of readers own their own PCs. In fact these figures came from our Readership Survey back in November 1996 and, at that time, nearly half of those readers who did not own a PC stated their intention to buy one, so the ownership figure could be even higher now.

It's interesting to see that a national survey of the public, carried out around the same time, indicated that only about eighteen per cent of the adult UK population regularly used a computer at home, and that over sixty per cent of those only used the computer for games.

**IMMEASURABLE**

Obviously electronics as a hobby can readily be enjoyed by those without a PC but we find that the use of computers extends the interest and possibilities of our hobby immeasurably. It is, therefore, not a surprise to find so many of our dedicated readers using PCs in conjunction with project development and building. Just take a look through the advertisements in this issue for an insight into the number and variety of software available to the hobbyist, student, technician, designer and engineer – all, of course, for PCs.

We can understand those who don't want to get involved with computers (computers do after all generate their own set of new problems – see last month's Editorial) and, as I have said before, I believe there will always be plenty in *EPE* to interest you, but we must also be aware of the needs of the vast majority of our readers and provide them with interesting, stimulating and innovative material, like *EPE PIC Tutor* coming next month (see page 83).

Progress, particularly in technology, forges ahead at an ever increasing rate; we cannot stop it, nor would we wish to try.


**Editor:** MIKE KENWARD**Secretary:** PAM BROWN**Deputy Editor:** DAVID BARRINGTON**Technical Editor:** JOHN BECKER**Business Manager:** DAVID J. LEAVER**Subscriptions:** MARILYN GOLDBERG**Editorial:** Wimborne (01202) 881749**Advertisement Manager:**

PETER J. MEW, Frinton (01255) 861161

**Advertisement Copy Controller:**

PETER SHERIDAN, Wimborne (01202) 882299

**READERS' ENQUIRIES**

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**. **Due to the cost we cannot reply to overseas queries by Fax.**

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

**COMPONENT SUPPLIES**

**We do not supply electronic components or kits** for building the projects featured, these can be supplied by advertisers (see *Shoptalk*).

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that **we cannot provide data, or answer queries, on projects that are more than five years old.**

**ADVERTISEMENTS**

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

**TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT**

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; overseas readers should check local laws.

**AVAILABILITY**

Copies of *EPE* are available on subscription anywhere in the world (see below), from all UK newsagents (distributed by Seymour) and from the following UK electronic component retailers: Maplin – all stores throughout the UK (and in S. Africa); Greenweld Electronics; Circuit Distribution; Omni Electronics. The magazine can also be

purchased from many retail magazine outlets around the world.

**SUBSCRIPTIONS**

Annual subscriptions for delivery direct to any address in the UK: £26. Overseas: £32 standard air service, £49.50 express airmail. Cheques or bank drafts (**in £ sterling only**) payable to *Everyday Practical Electronics* and sent to EPE Subscriptions Dept., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Subscriptions start with the next available issue. We accept MasterCard or Visa. (For past issues see the *Back Issues* page.)

**BINDERS**

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 post and packing (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). *Normally sent within seven days but please allow 28 days for delivery – more for overseas orders.*

*Payment in £ sterling only please. Visa and MasterCard accepted, minimum credit card order £5. Send, fax or phone your card number and card expiry date with your name, address etc.*



# WATER WIZARD



ANDREW BUCKMASTER (Design) and MAX HORSEY (Text)

*Learn to save water - shower with a friendly monitor!*

**T**HE Water Wizard is a water monitoring device designed for showers and hosepipes, which records the number of litres used on a digital display. It also includes a set of four l.e.d.s which progressively light at each 25 litres.

Since a typical bath requires about 100 litres of water, the l.e.d.s provide a reading in terms of each quarter of a bath used. An audible warning sounds at each 25 litre step.

A typical shower will consume about 25 litres of water. However, modern power showers can supply a surprising amount of water in a short time, in fact a typical power shower at full setting can deliver 14 litres per minute. The average shower time is seven minutes. This would use the same quantity of water as a bath - hence the justification for this project!

When using a hosepipe, water is consumed at an even greater rate, and the design should encourage the user to reduce consumption. The current water shortage in various parts of the UK, and the possibility of more extensive water metering, have made the use of this type of product more pressing.

## HOW IT WORKS

The design does not require an on/off switch, in fact there are no controls at all, making the casing easier to waterproof and the device simple to use. It switches on automatically when water begins to flow through the sensor and, when the water flow stops, the circuit waits for 30 seconds before switching off.

Just before it switches off, it stores the value displayed in memory so that this reading can be recalled the next time it starts up. This makes it possible to check the amount of water consumed by the previous user before displaying the new total.

The system allows counting to 499 litres. The digital readout counts to 99, and l.e.d.s indicate the equivalent fraction of a bath, i.e. quarter, half, three-quarters.

If the count exceeds 99, then the first l.e.d. flashes, indicating that the digital reading must be added to 100 litres. At 200 litres the next l.e.d. flashes, and so on, allowing a count to 499 litres.

The system is based around the PIC16C54 microcontroller, an electrically

programmable read only memory (Eprom) device. The suggested system employs an external water flow sensor, and no plumbing skills are required. However, it would be possible to employ a larger case if preferred, and include an internal water flow sensor.

## CIRCUIT DESCRIPTION

The circuit diagram for the Water Wizard is shown in Fig.1. The PIC16C54 microcontroller is designated as IC1. A 2.4576MHz crystal (X1) drives the microcontroller's oscillator, aided by capacitors C1 and C2.

Capacitor C3, along with resistors R1 and R2 force IC1 to reset when power is first applied. This ensures reliable start-up. Diode D1 allows C3 to discharge quickly when power is removed.

The water flow sensor module (X2) is a ready-built device with compatible hosepipe/shower-hose connections. It comprises an infrared l.e.d. (D2) and sensor unit in a single housing complete with a set of blades which revolve as water passes through the unit. As the blades revolve, they interrupt the infrared beam between the l.e.d. and sensor causing a square wave output to be generated. The frequency of the output is determined by the rate of water flow.


A schematic representation of the sensor's internal circuit is shown in Fig.2.

Be aware that the current flowing through the sensor's l.e.d., i.e. D2, affects the mark/space ratio of the output. Changing the value of R3 (Fig.1) will have a significant affect on this ratio.

The value of 680 ohms as shown is suitable for a 6V supply, but it may need reducing if a lower voltage power source is used. A value of about 470 ohms to 560 ohms may be more suited to a 5V supply. (The circuit *must not* be used with a supply greater than about 6.25V - the maximum that the PIC16C54 can accept.)
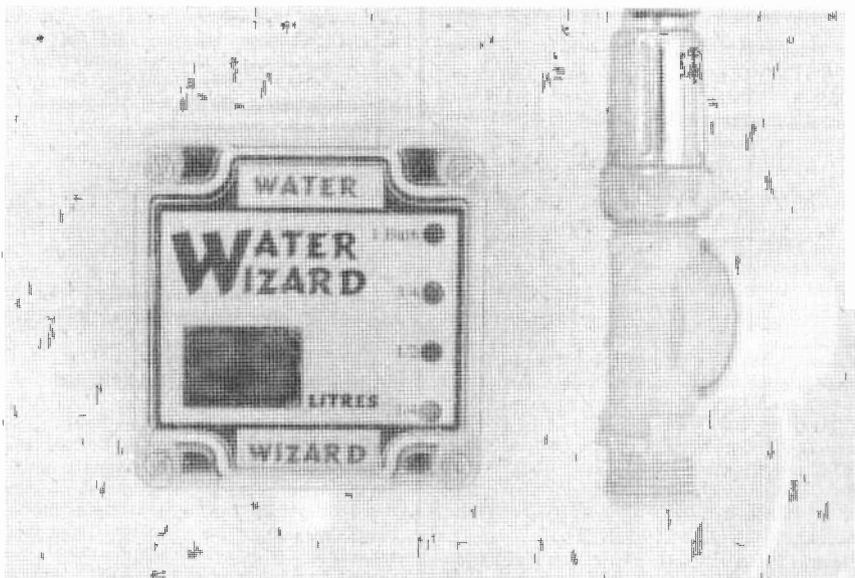
## POWER SAVING

The Water Wizard has been designed to minimise electrical current consumption. For example, if the cathode (k) side of l.e.d. D2, and the 0V connection of the sensor had been connected directly to 0V in the circuit, power would undesirably flow through the sensor and l.e.d. when the circuit is inactive. This is avoided by controlling the sensor via the PIC.



Completed Water Wizard showing front panel display layout.

The PIC is programmed to "wake up" at regular intervals in order to switch on the sensor and check for an output waveform. If no waveform is present, the PIC returns to its Sleep mode.

Ideally, the sensor and l.e.d. should be switched on and off via one of the pins of the PIC dedicated to this task. However, no spare pins were available but, when the PIC is active, at least one of the outputs RA0, RA1 and RA2 is always at 0V. Hence the negative (0V) power supply for the sensor and l.e.d. is via these outputs and diodes D3, D4 and D5.

The inclusion of the diodes allows the pins RA0, RA1 and RA2 to fulfil their normal task, namely to drive l.e.d.s D6 to D9. These are the l.e.d.s which indicate the fraction of a bath of water used.

Since each output RA0, RA1 and RA2 can be at logic 1, logic 0 or open circuit, the combinations shown in Table 1 allow full control of the four l.e.d.s.

Notice that when the PIC is in Sleep mode (circuit inactive), the outputs are all open circuit (X), so preventing current wastefully flowing through the sensor and D2. When the PIC is active, the three outputs are switched to logic 0, allowing the sensor to operate, but still keep-

ing l.e.d.s D6 to D9 switched off until required.

The output from the sensor is delivered to pin 3 of the PIC, which is configured as an input. This is the only input required and the status of the signal on it is used to sense when water is flowing, to set the PIC to its active state, and to determine the flow rate.

Output RA3 is used to control the buzzer (WD1) via transistor TR1.

## DISPLAYS

The two 7-segment l.e.d. displays, X3 and X4, are strobed. In other words, the individual segment connections from the two displays are connected to a single set of outputs, namely RB1 to RB7. There is only one output pin remaining, RB0, and so this is made to control which display is on at any one time, by toggling between logic 0 and logic 1.

Output RB0 is connected to the bases of two transistors, TR2 and TR3. Transistor TR2 is a *pn*p type, and TR3 is an *np*n. Hence, when RB0 is low (logic 0), TR2 turns on, allowing current from display X3 to sink to 0V.

In this condition, the outputs RB1 to RB7 are taken high (logic 1) to turn on the selected segment of the display. For example, if RB1 to RB7 are all low, then X3 is blank. If RB1 to RB7 are all high, then an "8" is displayed. Note that X3 is a *common cathode* type, i.e. all the l.e.d. segment cathodes are joined to a single pin.

Table 1: L.E.D. Control Combinations

| RA0 | RA1 | RA2 | D6  | D7  | D8  | D9  |
|-----|-----|-----|-----|-----|-----|-----|
| X   | X   | X   | off | off | off | off |
| 0   | 0   | 0   | off | off | off | off |
| X   | 0   | 1   | off | off | off | on  |
| X   | 1   | 0   | off | on  | off | off |
| 1   | 0   | X   | on  | off | off | off |
| 0   | 1   | X   | off | off | on  | off |

(X = open circuit)



Andrew demonstrating his water monitor at the 1997 Young Electronics Designer Awards co-sponsored by Texas and Mercury.

When RB0 is low, transistor TR3 will be switched off since it is an *np*n type and requires its base to be at least 0.7V before turning on. Hence X4 will be blank.

If RB0 is switched high by the PIC, then TR2 will turn off, making X3 blank regardless of the logic levels at RB1 to RB7. However, TR3 will now turn on, causing X4 to display a number determined by the outputs RB1 to RB7.

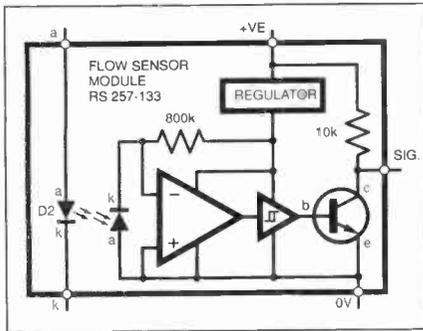


Fig.2. Internal circuit schematic of the water flow sensor module.

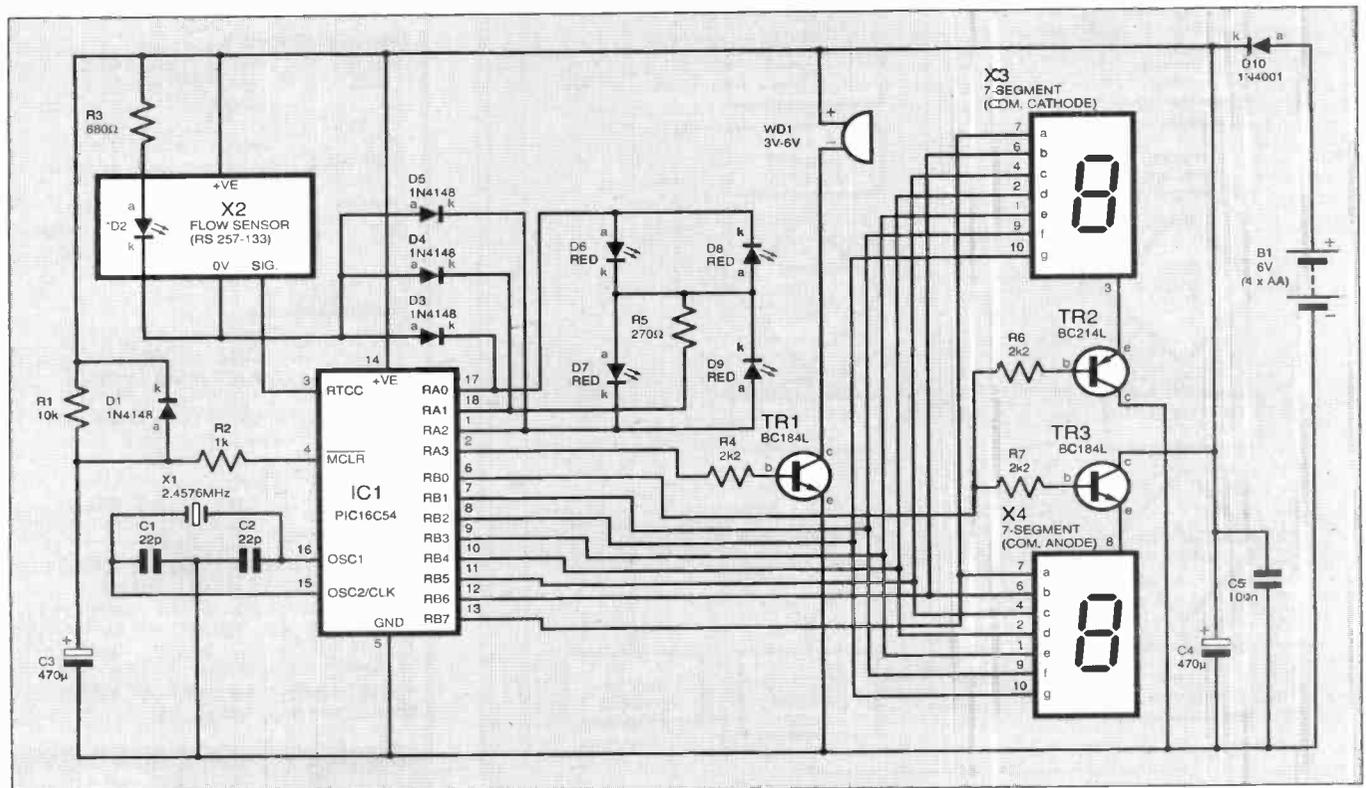


Fig.1. Complete circuit diagram of the Water Wizard water flow monitor.

Note that since X4 is a *common anode* type, each segment will be turned on by a logic 0 rather than a logic 1. Hence if RB1 to RB7 are low, then X4 will display a number "8". If RB1 to RB7 are high, then X4 will be blank.

The PIC program causes RB0 to change state very quickly so that both displays appear to be lit continuously. This is known as strobing or multiplexing. Output levels on RB1 to RB7 must be synchronised with RB0, noting that when RB0 is low, then "highs" determine the number on X3, and when RB0 is high, then "lows" determine the number on X4. This complicates the programming, but allows two displays to be controlled by only eight pins.

Capacitors C4 and C5 decouple the circuit power lines, and diode D10 protects the circuit if the battery is connected the wrong way round.

## PROGRAM

The Water Wizard program flow chart is shown in Table 2. The left hand chain of boxes deals with the count from one to 100 litres, the right hand side deals with counts from 100 to 500 litres. The chart is slightly simplified, for example the buzzer produces three beeps when 25 litres have passed, five beeps at 50 litres, etc.

When the system goes into Sleep mode, the reading on the display is stored in a file register. At wake-up, this reading is displayed until the first litre has been used.

For example, if you used 27 litres of water in the shower, the reading of 27 will remain on the display for 30 seconds after switching off the water. After 30 seconds the display will blank, and the circuit will shut down.

When the water is turned on again, the reading of 27 will be displayed until the first litre has been used, at which time the display will revert to 1. This enables members of a family to check on each other's water consumption! The count value is lost if power is removed from the circuit.

The program was written and assembled using the system supplied by Microchip, namely MPASM and MPLAB. Details about obtaining the software and preprogrammed PIC16C54 chips are given in the *Shop Talk* column and on the *EPE PCB Service* page.

Note that as the PIC16C54 microcontroller is an Eprom device, once programmed it can only be reprogrammed after being erased by an ultraviolet erasure unit.

## CONSTRUCTION

A fairly compact printed circuit board




Printed card facia panel

(p.c.b.) layout, as shown in Fig.3, is required in order to fit the board into the suggested case. This board is available from the *EPE PCB Service*, code 180.

Ensure that the p.c.b. fits the case before starting work.

Begin by soldering in an 18-pin dual-in-line (d.i.l.) socket for the PIC and two

Table 2: Water Wizard Program Flow Chart

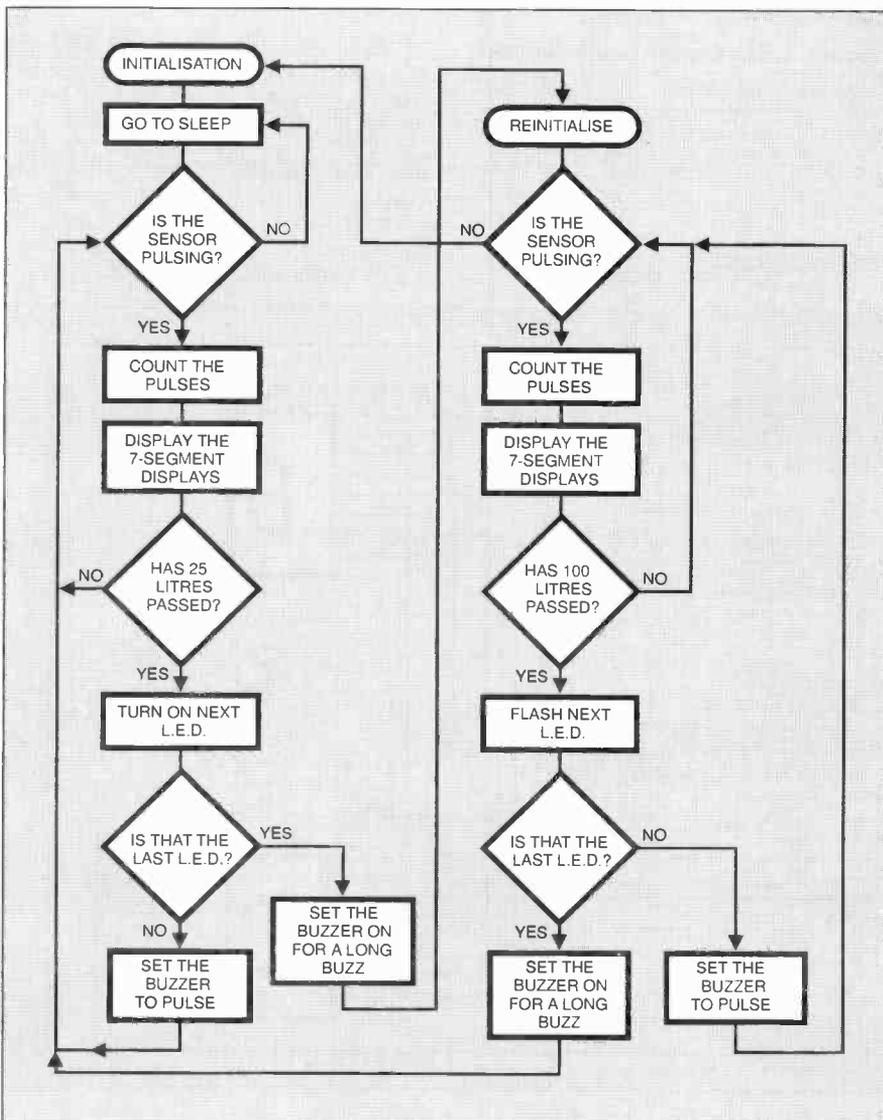

## COMPONENTS

### Resistor

|            |             |
|------------|-------------|
| R1         | 10k         |
| R2         | 1k          |
| R3         | 680Ω        |
| R4, R6, R7 | 2k2 (3 off) |
| R5         | 270Ω        |

See  
**SHOP  
TALK**  
Page

### Capacitors

|        |                                |
|--------|--------------------------------|
| C1, C2 | 22p ceramic disc (2 off)       |
| C3, C4 | 470μ radial elect. 10V (2 off) |
| C5     | 100n ceramic disc              |

### Semiconductors

|              |  |
|--------------|--|
| D1, D3 to D5 | 1N4148 signal diode (4 off)                        |
| D2           | (integral with sensor X2)                          |
| D6 to D9     | 5mm red l.e.d. (4 off)                             |
| D10          | 1N4001 rectifier diode                             |
| TR1, TR3     | BC184L <i>npn</i> transistor (2 off)               |
| TR2          | BC214L <i>pnp</i> transistor                       |
| IC1          | PIC16C54 microcontroller, preprogrammed (see text) |

### Miscellaneous

|     |  |
|-----|--|
| B1  | 6V battery (4 x AA) and clips (see text) |
| WD1 | buzzer, 3V to 6V, p.c.b. mounting        |
| X1  | 2-4576MHz crystal                        |
| X2  | flow sensor type RS257-133               |
| X3  | 7-segment common cathode l.e.d. display  |
| X4  | 7-segment common anode l.e.d. display    |

Printed circuit board, available from the *EPE PCB Service*, code 180; splashproof plastic case with transparent lid, 82mm x 80mm x 55mm; 18-pin d.i.l. socket; 10-pin s.i.l. socket (2 off); red filter; 4-core cable (1 metre approx.); shower hose extension to suit (see text); solder, etc.

Approx Cost  
Guidance Only

**£50**

single-in-line (s.i.l.) sockets for the 7-segment displays. Then solder in the resistors, crystal and small capacitors. Take care to fit the diodes, transistors and electrolytic capacitors the correct way round as shown. Also take care not to create any solder bridges, particularly where tracks run between the pins of IC1.

The four l.e.d.s should be fitted the correct way round, noting that the longer of the two leads is the anode (a). Note that the l.e.d.s are not in line, and D6 and D8 are displaced in order to allow the p.c.b. to be clipped into place inside the case.

It is necessary to bend the l.e.d. wires a little so that all the l.e.d.s are aligned, and their tops are at the same height as the 7-segment displays. If necessary, push the displays into their sockets to check this, but be sure to note which is the common cathode display, and which is the common anode. No great harm will occur if they have become mixed up, but

if in doubt, test the circuit with one display chosen at random to see if it works.

### FLOW SENSOR

The flow sensor should be connected to the p.c.b. via a length of 4-core cable. Use the thinnest cable available, and do not forget to push the cable through the hole in the sensor cover.

The sensor cover is a push-fit and should be removed to expose the five connections. These include two for the internal l.e.d. and three for the sensor itself, as seen in Fig.4.

Note that the cathode of the l.e.d. should be connected to the sensor's 0V pin with an insulated wire link. Although this point is intended to be connected to diodes D3, D4 and D5 when the unit is in normal use, a direct 0V connection is provided on the p.c.b. and is shown in Fig.3 as "0V Test Point". This is useful for initial testing as the output signal

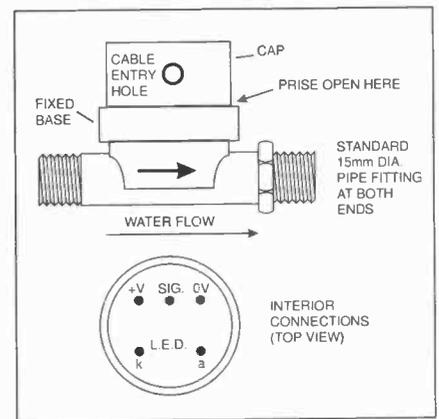


Fig.4. Connecting details for the Water Flow sensor.

from the sensor may be tested without the PIC being active.

Connect the 4-core cable to the p.c.b. on the *trackside*, so that the cable does not show above the p.c.b. Note that the connection is temporary at this stage, since the cable will have to be fitted through a hole in the case.



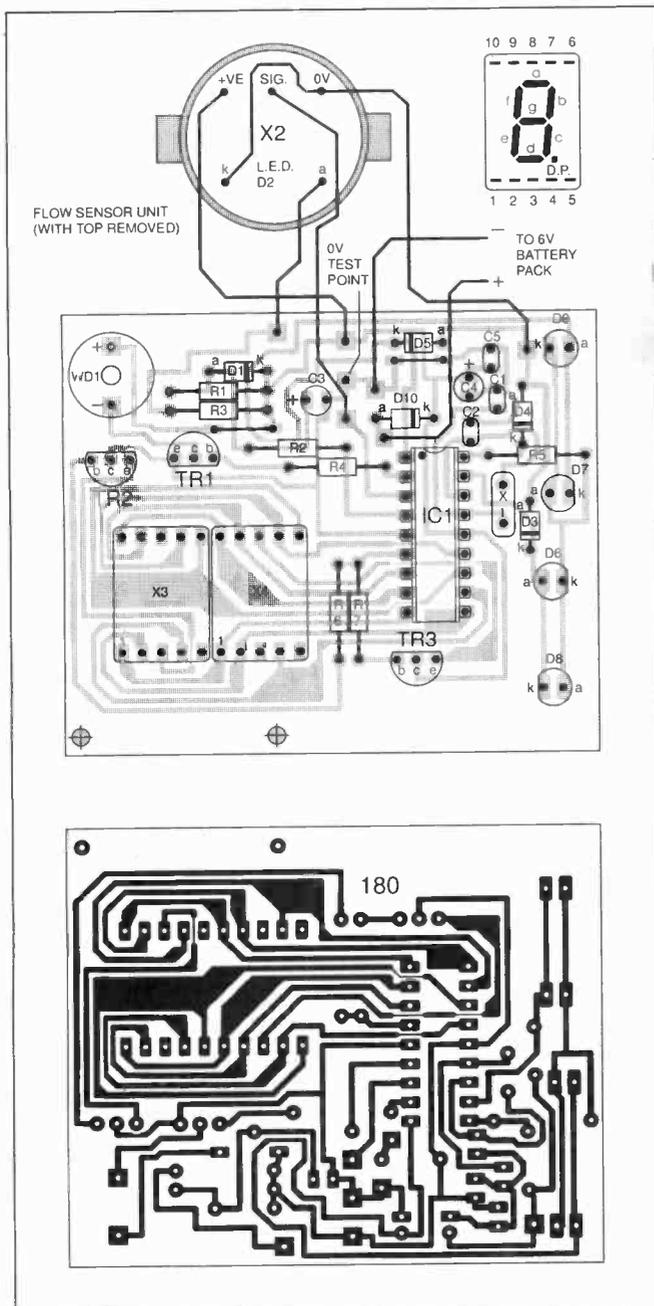



Fig.3. Water Wizard printed circuit board component layout, wiring to flow sensor, and full-size copper foil master. Note the lead-off wires should be soldered to the *trackside*.

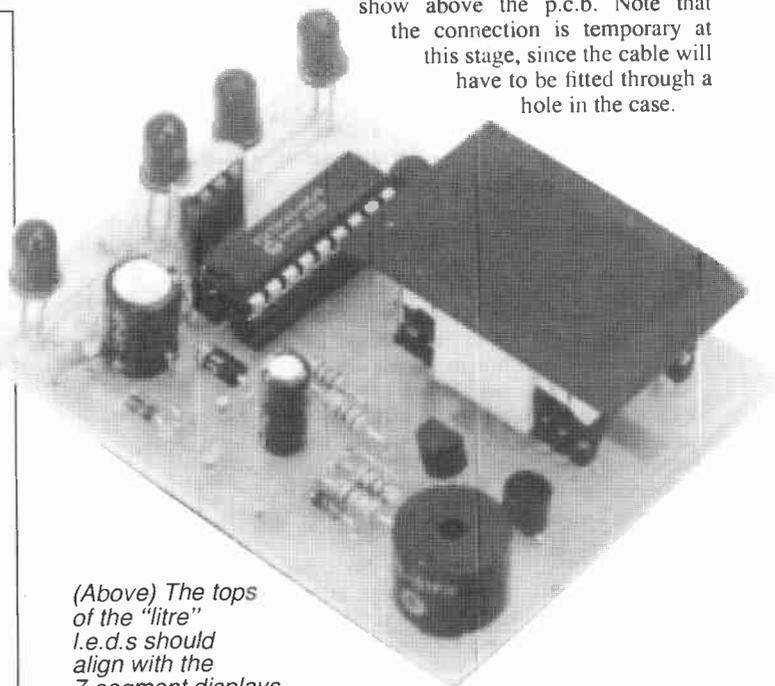


(Above) The tops of the "litre" l.e.d.s should align with the 7-segment displays.

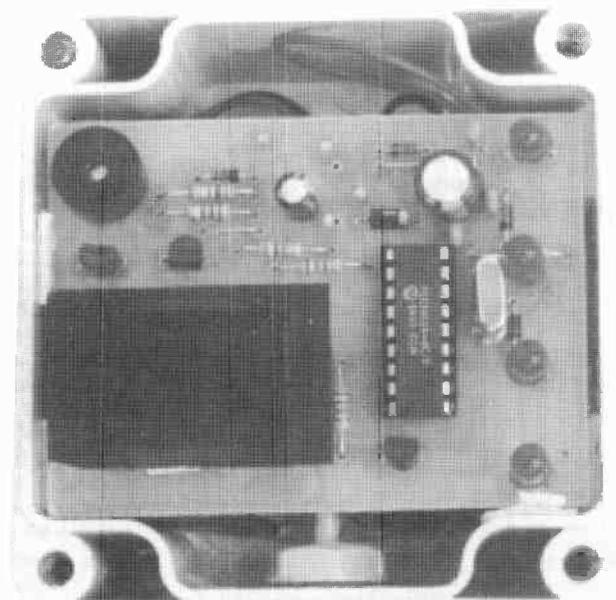(Below) The p.c.b. is wedged into its case using adhesive pads. The battery holders are sited in the bottom.



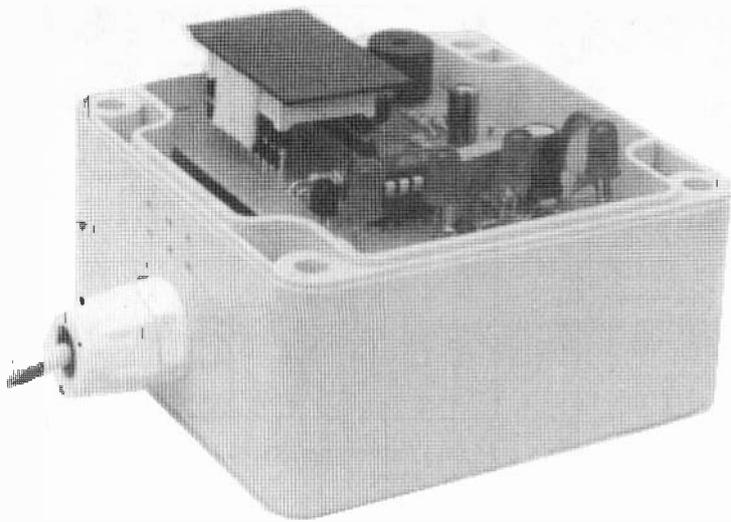

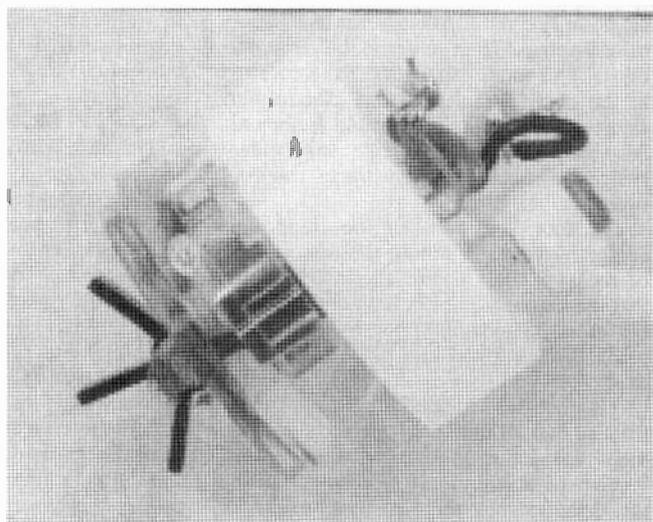Control unit with lid removed. The 7-segment displays and l.e.d.s should protrude into the lid area.



Dismantled sensor showing "water paddle" rotor and wiring.

The battery clip should also be connected to the power supply pads on the trackside of the p.c.b.

Finally, fit the programmed PIC, checking that its notch faces towards the top of the circuit board, as shown in Fig.3.

### TESTING

The circuit can now be tested by connecting a 5V power supply or 6V battery pack. Blowing air through the sensor should make its rotor spin and produce a square wave output signal, which can be checked by an oscilloscope, if available.

If all is well, the display should light when air is blown through the sensor. Continuous blowing should cause the display reading to increase, and at 25 litres the first l.e.d. should light and the buzzer should pulse for a short time.

Remember that the PIC will not "wake up" until a square wave is present on pin 3 of the PIC.

Since continual blowing into the water flow sensor unit is inconvenient, if not stressful, it may be helpful to apply a square wave (not above 6V) from a signal generator to IC1 pin 3 (with the sensor's signal lead disconnected).

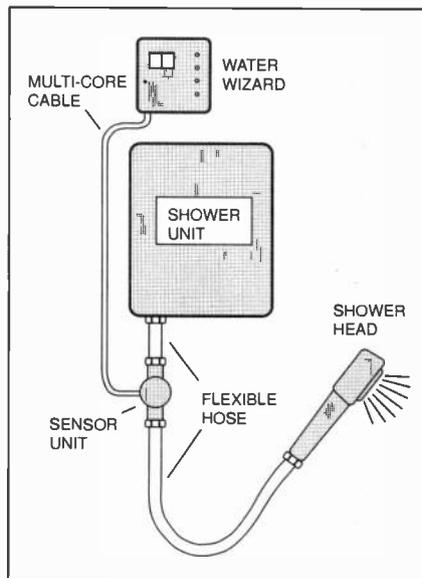


Fig.5. One suggested method of attaching the Water Wizard to a shower unit.

The whole sequence may then be observed at higher speed to 500 litres, without wasting any water or breath!

### CASE DETAILS

The Water Wizard prototype was housed in a plastic case measuring 82mm x 80mm x 55mm, with a clear lid. The case *must be sealed and water resistant* as it may well be splashed with water.

Several holes are required in the case, one for the 4-core cable, and a few *very small* holes for the sound to penetrate from the internal buzzer.

The cable entry should be protected with a tight fitting grommet, and the sound holes possibly protected with a thin membrane, although if located at the base or rear of the unit (as with the prototype - six small holes), water penetration should not be a problem.

It may be necessary to drill small securing holes in the rear section if the unit is to be fitted to a wall.

A 6V battery supply is required, and this is achieved with four AA-size cells. Two 3V battery packs will fit the case more easily than a single 6V pack. The two 3V packs may be glued inside to the

rear of the case, although the type used in the prototype were wedged into place without the need for glue.

Ensure that the packs are connected in series, i.e. the red wire from one should be connected to the black wire from the other. The remaining red and black wires then provide the positive and negative supply to the circuit.

The p.c.b. may be mounted at the top of the lower section of the case, or in the transparent lid using adhesive wedges. A red filter may be placed over the 7-segment displays to improve their appearance; it should be fitted directly on the displays, as any space between the displays and the filter will cause blurring.

The prototype's cover panel seen in the photographs was drawn on coloured card, the l.e.d. circles and 7-segment display box being cut out with a craft knife. The panel was fitted inside the clear case top to provide a neat finish.

### INSTALLATION


A diagrammatic representation of how the Water Wizard is attached to the shower unit via an additional flexible hose is shown in Fig.5. With the prototype, the additional hose was reduced in length so that the sensor was immediately below the shower unit. However, this type of alteration requires a degree of plumbing skill to produce a water tight joint, and it may be wiser to leave the additional hose at its standard length.

The 4-core cable links the sensor to the Water Wizard, and the cable may be routed neatly behind the hose and shower unit. □
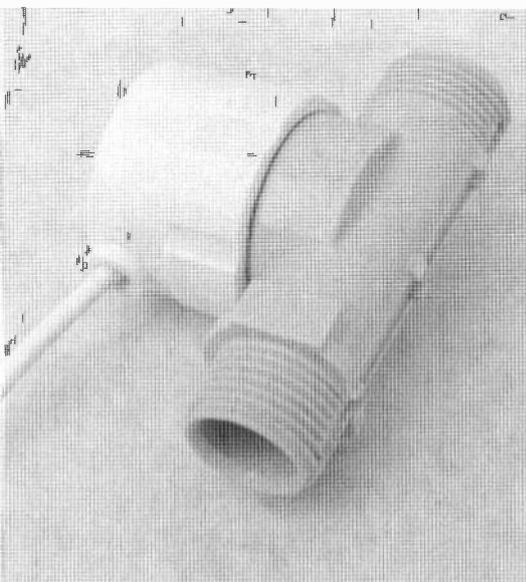
### EDITORIAL NOTE

Andrew Buckmaster received "Highly Commended" recognition for his Water Wizard in the Intermediate (15 to 17 years) category of the *Young Electronic Designer Awards (YEDA)* for 1997, as reported in our June '97 issue. For his achievement, he was awarded a certificate and the prize of a Texas Instruments T180 graphics calculator.

Andrew is a pupil at Radley College, Abingdon, near Oxford, where Max Horsey is Head of Electronics.




Water Flow Sensor module. Check the water flow direction indicated on the body of the module.



# Looks like Quickroute 4.0 has Got the Lot!
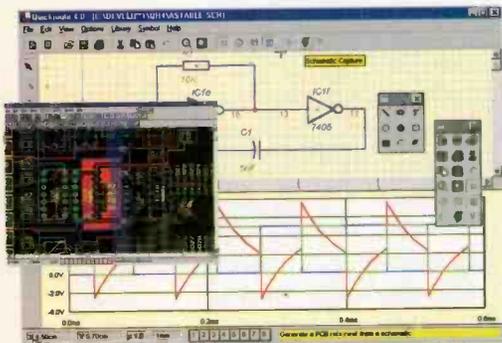
## Simulation, Schematic Capture, PCB AutoRouting & CAD/CAM Support for just £79\*\*

Announcing Quickroute 4.0! Now all versions of Quickroute 4.0 have the full range of great features you've come to expect from Quickroute including a FREE integrated mixed mode simulator, plus a new modern user interface with active buttons, a fast new symbol browser, and dockable tool bars. The only difference now between the various versions of Quickroute is the size of design you can create.



Best of all, you can now try Quickroute 4.0 with complete confidence because all orders are covered with our 30 day money back guarantee\*. Simply fill in the coupon and fax, mail (FREEPOST address below) or FREEphone 0800 731 28 24 to place your order.

### Yes, I would like to order (please tick box)

- Quickroute 4.0 (max 300 pins) at £99.88 inclusive
  - Quickroute 4.0 (max 800 pins) at £182.13 inclusive
  - Quickroute 4.0 (full access) at £299.63 inclusive
  - Quickroute 4.0 Information Pack (free)
- Inclusive price includes U.K. post & packing & V.A.T.

### My payment choice (please tick box)

- I enclose a cheque payable in U.K sterling for £
- Please debit my Visa/Mastercard/American Express/Switch\* card (\*please delete)

Card No.  Expiry

Signature

### Delivery Address

- New user interface with dockable tool bars
- Multi-sheet schematic capture
- Power rail & Data bus support
- Analogue+Digital Simulation
- PCB Design with Autorouter
- Copper flood fill
- Netlist import and export
- CAD/CAM import and export
- WMF, DXF & SPICE file export
- 1000+ Library Symbols
- Engineering Change

● 30 Day Money Back Guarantee\*

**FREEphone 0800 731 28 24** Ref 403

Quickroute Systems Ltd FREEPOST NWW13136 Stockport SK4 1YR.  
FAX 0161 476 0505 FREE Demo on WEB <http://www.quickroute.co.uk>



# Electronics Principles 5.0

'A COMPLETE PC BASED ELECTRONICS COURSE'

If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics then this is the software for you.

Now includes the PIC16C84 & PIC16C71 hardware and instruction set.

Electronics Principles 5.0

DC AC Power Semi-Cond Op-Amps Maths Logic Measure Micro PIC Help

MEASURING VOLTAGE ANALOGUE TO DIGITAL A/D Conversions and Input Selection

Binary 'ADCON0' = '01010011' CHS1: CH50

THANISOR THEORY: Equivalent NPN Transistor Circuit.

Circuit parameters set up in previous screen.

$h_{ie} = 749.9999R$   
 $h_{fe} = 2.5$   
 $h_{oe} = 416.6666\mu S$   
 $h_{ie} = 0.125$   
 $R1 = 56k$   
 $R2 = 12k$   
 $RL = 2.2k$   
 $R_{out} = 2.4k$

$R_{in} = \frac{1}{\frac{1}{R1} + \frac{1}{R2} + \frac{1}{h_{ie}}} = 697.0953R$   
 $Load\ R_L = \frac{R_{out} \times RL}{R_{out} + RL} = 1.1478k$   
 $Current\ gain = \frac{h_{fe} \times RL}{RL} = 1.3043$

Resistance 'R1' 56k  
Resistance 'R2' 12k  
Resistance 'RL' 2.2k

Calculations, Topic Notes, Printing, Equivalent NPN Transistor Circuit

Calculations, Topic Notes, Printing, Basic 555 Timer



Electronics Principles 5.0 is a significant upgrade of our popular electronics educational software. Now containing ever more analogue, digital and microcomputer theory. PLUS over a hundred new mathematics topics to further your understanding of formulae and calculations. Telephone for a comprehensive list or upgrade details.

This software has been developed to teach electronics and is suited to both the complete novice and the more advanced student or hobbyist wanting a quick revision and access to hundreds of electronics formulae. It is extremely easy to use. Just select a topic, which is always presented as a default diagram (no blank screens!) and input your own values. Alternatively, use those from any standard electronics text book to see the results as frequency response curves, calculations, logic states, voltages and currents etc.

Graphics presentation has been enhanced and speeded-up with new menus and indexing which enables a quicker access and more informative description of the extended range of five hundred and sixty electronics and mathematics topics.

The PIC16C84 microcontroller hardware and instruction set has been introduced and brought to life through colourful interactive graphics where you can study the architecture of this device by changing the data values to simulate all of the registers, direct/indirect addressing, program/data memory and input/output port configuration. Along with those analogue to digital functions of the PIC16C71. If you would like to learn more about the principles of these popular microcontrollers then it could not be made easier.

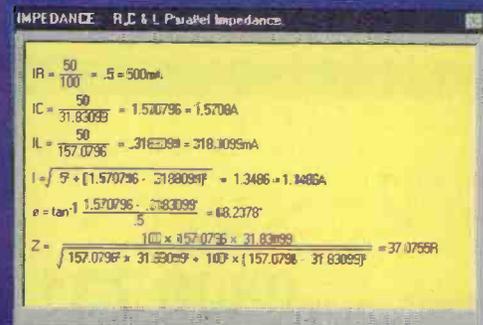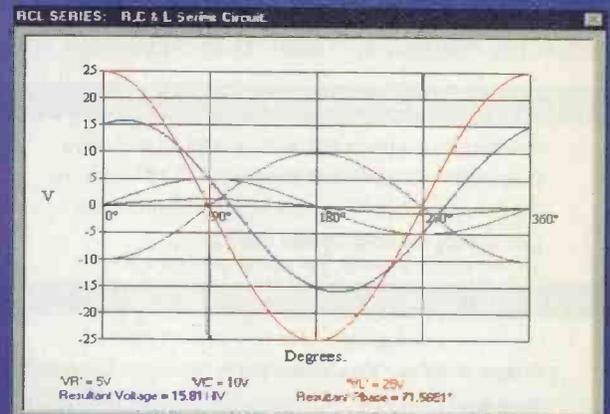Electronics Principles software is currently used in hundreds of UK and overseas schools and colleges to support City & Guilds, GCSE, A-level, BTEC and university foundation courses. Also NVQ's and ENVQ's where students are required to have an understanding of electronics principles.



Still only £99.95\*

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.

Tel/Fax: 01376 514008. sales@eptsoft.demon.co.uk <http://www.eptsoft.demon.co.uk>

\*UK and EC countries add £2 per order for post & packing. VAT should be added to the total.

Outside Europe £3.50 for air mail postage by return.

Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date. Cheques & Postal Orders should be made payable to EPT Educational Software.

## PC SPEECH TRANSLATION

Real-time translation between spoken languages is a mere two years away, reveals Barry Fox.

**M**ICROSOFT has paid \$45 million for an eight per cent share in Belgian electronics company, Lernout and Hauspie. In return for the investment, Microsoft is free to use L&H's speech recognition and text-to-speech software in its Windows operating system. L&H will use the money to develop the translation software on which the licensed programs rely.

President and CEO Gaston Bastiaens (ex-Philips and ex-Apple) recently demonstrated where the technology is today, and predicted where it will go next.

Within two years, says Bastiaens, L&H will be selling a hand-held translator, which responds to an English voice and speaks a Chinese translation, and vice-versa. There will also be a Japanese-English version. Bastiaens predicts that video and computer games will very soon respond to speech "zap" commands.

"Expansion of the EC is good news for us", says Bastiaens. "As more European states with more unfamiliar languages join the EC, there will not be enough human translators to handle their conferences and meetings. They will have to use machine translation."

L&H now has a staff of seven hundred, five hundred of them engineers and linguists, working on the problem. Instantaneous translation is two years away, but only if the conversation uses a limited vocabulary. Complicated conversations, with innuendo and slang, could take up to ten years to translate in real-time.

"It is easier to handle this kind of translation in non-realtime batches", says Bastiaens. "The machine listens to the speech, then translates it and speaks".

At a recent demonstration, L&H showed how mail order catalogue firms and pizza chains in the US are already taking telephone orders without human involvement. A computer recognises the speech and repeats the order with virtually no delay. The core software is now on sale in Germany for 600Dm.

Although several companies are already selling speech recognition software which claims to let anyone talk to their computer instead of type at the keyboard, performance is erratic. This is often because the system has been tuned to recognise an American voice, and finds difficulty with the English accent. VoicePad Pro from US company Kurzweil suffered this problem. Significantly L&H has now bought Kurzweil.

Philips is also very active in speech recognition, and like L&H is aiming initially for vertical markets, where users in a specialised field call on a relatively limited vocabulary. Philips is supplying the Swiss Railways with a system which lets people phone and ask a computer for train times. L&H's first system will be aimed at American doctors, who are paranoid over law suits and thus need to dictate what they are doing during an operation.

Text translation is easier than speech translation, because there is no need for the computer to recognise words before translating them. But L&H is still selling text translation only to professional translators, who use a computer to make a first draft, and then polish the it to avoid contextual nonsenses which can arise when a word has several meanings.

The long-term aim is Internet ferret software, which takes a query in one language, translates it into several languages, searches the Internet, retrieves information in several languages, then translates the text back into the original language and condenses it into a summary. Again this is seen only as a professional tool.

### My Word - What Next!

But one L&H product will soon be available as a low cost consumer tool. For around £50, speech recognition software works with Windows 95 and Microsoft Word to edit and manipulate text. Instead of trying to remember which command in Word does what, the user simply speaks a plain English order, such as, "underline first word, italicize second line, use one inch margin, break into columns, highlight in red".

At a demonstration in London recently, L&H's chief technical officer Bob Kutnick, spoke to the PC in his American accent, then handed the microphone to several Brits with different English accents. All were able to control the edit functions.

"There are things I can do with Word by talking, that I don't know how to do with key strokes", admitted Kutnick, summing up the dilemma many users face with the increasingly bloated Word software. Small wonder Microsoft has bought a share in Lernout and Hauspie, and the right to use its speech recognition engine in all Microsoft software.



CROTECH have introduced their new Zebra series of bench power supplies. The company have over 30 years experience in design and manufacture of power supplies for both the educational and professional user.

They say that the Zebra range represents outstanding value for money, offering high quality, safe, rugged and easy to use bench power supplies. There are 20 different models in the range, in single, dual and triple output types. Many features are offered, such as independent series or parallel mode, constant current, tracking and large clear digital display meters for reading both voltage and current.

All models have low ripple and noise, combined with good voltage line and load regulation of <0.01% at full load, as well as full automatic overload and short circuit protection. They comply with BS EN 61010 Electrical Safety Standard, suitable for use in educational establishments.

For more information, contact Crotech Instruments Ltd., Dept. EPE, Unit A1, Farday Road, Newbury, Berks RG14 2AD. Tel: 01635 550789. Fax: 01635 49305.



## YEDA CALLING

THE CALL for entries to the *Young Electronics Designer of the Year Award* (YEDA) 1998 has been made.

There are three categories, Junior (under 15 years), Intermediate (15-17 incl.), and Senior (18-25 incl.). To enter YEDA, all you need to do is obtain an entry form, fill it in with a brief description of the device or system which you have invented, and return the form to YEDA before 2 March 1998. Your design will then have to be ready for regional judging between 20 April and 1 May 1998.

If you are successful at this stage, you will then have the opportunity to develop your project further before the national final in Manchester on 28-29 June 1998.

The judges will be looking for five principle qualities in your design: originality, technical competence and reliability, construction and presentation, everyday usefulness, commercial feasibility.

Last year the Junior Category prize went to Edward Brocklebank of Radley College, Abingdon, for his bicycle enhanced visibility and indication system. Radley, of course, is where Max Horsey is Head of Electronics, Max being the author of our *Teach-In '96* series.

Interestingly, the Manchester presentation takes place as part of the celebrations marking the 50th anniversary of the world's first stored program computer. This machine – the antecedent of the programmable computers in use today – was unveiled in June 1948 by a team of engineers at the University of Manchester.

To find out more about the awards, contact The YEDA Trust, Dept EPE, 60 Lower Street, Pulborough, W. Sussex RH10 2BW. Tel: 01798 874767. Fax: 01798 873550. E-mail: postmaster@yeda.compulink.co.uk. Web: <http://www.yeda.org.uk>.

## Global Weather

A GLOBAL network of weather satellites could mean significant new orders for the British space industry, according to John Battle, Minister for Science, Energy and Industry.

John Battle has confirmed the UK's £27 million commitment to the European Space Agency's METOP-1 programme, which could bring an estimated £55 million in orders to Britain.

The meteorological polar orbiting satellite (METOP) is the first of three European satellites which will form part of the World Meteorological Organisation's Global Observing System. From 2003 onwards, the three will cross the poles to provide a constant stream of weather data.

## PIC16C84 Rumours False!

THERE are rumours circulating that the PIC16C84 microcontroller is to be deleted by Microchip. We have spoken with the UK office of Microchip who assure us that they have no intention of deleting it, or any of their PIC range.

There are further comments, about the PIC16C84 and sister PIC16F84 on the *Readout* pages.

For more information contact Arizona Microchip Technology Ltd, Dept EPE, Unit 6, The Courtyard, Meadowbank, Furlong Road, Bourne End, Bucks SL8 5AJ.

Tel: 01628 851077.  
Fax: 01628 850259.

# EMF Safety Update

THE NRPB (National Radiological Protection Board) has sent its annual report. In it is stated that "Whereas biological studies provide no persuasive evidence that power frequency EMFs can influence cancer processes, the epidemiological evidence remains equivocal".

The question as to whether EMFs (electromagnetic fields) can cause cancer was first posed some years ago. We periodically publicise the latest statements made by NRPB on the issue.

Two further statements in the report are interesting: "Restrictions on human exposure to low frequency magnetic fields recommended by the Board are based in part on the need to avoid the adverse effects of induced electric current on the brain and nervous system. Experiments at the Board have indicated that magnetic fields may temporarily affect certain types of memory"; and that a European Commission has recommended "a programme of international research on the effects related to the use of mobile phones".

For more information contact: NRPB, Dept EPE, Chilton, Didcot, Oxon OX11 0RQ.

Tel: 01235 831600.

Fax: 01235 833891.

E-mail: [nrpb@nrpb.org.uk](mailto:nrpb@nrpb.org.uk).

Web: <http://www.nrpb.org.uk>.

## GREENS SHOCK STORE

FRIENDS of the Earth groups recently demonstrated outside Dixons stores calling for the UK electrical industry to pay for the collection of electrical goods for reuse and recycling, for products to be labelled with their expected lifespan, and for retailers to offer free extended guarantees.

Dixons are the UK's leading electrical retailer and the demonstrations were aimed at influencing discussions on a new European law which could ensure that electrical goods are designed for durability, repair, reuse and recycling.

Apparently six million electrical items are dumped every year in the UK. The proposed European Directive is the first "producer responsibility" Directive for household consumer goods that will ensure manufacturers take responsibility for their product from cradle to grave.

Friends of the Earth are at Dept EPE, 26-28 Underwood Street, London N1 7JQ.

Tel: 0171 490 1555.

Fax: 0171 490 0881.

Web: <http://www.foe.co.uk>.

# POWER FROM TEXAS

NEWLY-FORMED company Power Innovations have acquired from Texas Instruments all that part of their business which designs, manufactures and markets the well established and highly successful range of TI discrete bipolar devices, including high voltage transistors.

This management buy-out included all the relevant patents and intellectual property rights, wafer fabrication facilities, processes and procedure. All these functions, and the people responsible for them, will continue to operate at the Manton Lane plant, which for many years has been TI's sole manufacturing centre for power devices.

Now the handover has taken place, PI has assumed responsibility for any inventory and for all products in the course of manufacture.

For more information contact Power Innovations, Dept EPE, Manton Lane, Bedford MK41 7BJ.

Tel: 01234 223001.

Fax: 01234 223000.

E-mail: [info@powinv.com](mailto:info@powinv.com).

Web: <http://www.powinv.com>.

## Engaged US Telecoms

BT's rival, Mercury, has identified a puzzling problem for subscribers who use a BT line and Mercury 131 access code to make low cost transatlantic telephone calls. Sometimes the calls fail, giving the characteristic North American engaged or busy tone. But other times calls fail with the quite different British engaged tone. This suggests that the Mercury system is overloaded and unable to get calls out of Britain.

According to Mercury this is not so. Engineers have traced failed calls and found that when they are routed to the US by satellite, the UK caller hears a US engaged tone if the number is busy. But if the call goes to the US by optic fibre undersea cable, and the called number is busy, a signal is returned to the UK which triggers a locally generated engaged tone. So the two quite different tones mean the same, the US number is busy. Barry Fox

### ADVERTISERS

Have you got an interesting new product you would like publicised in *Innovations*? If so drop us a line with details (and a photo if possible).

# Overloud Movies

Barry Fox has some good news

**D**OLBY Laboratories, the US company which made it possible for cinemas to surround audiences with super loud-sound, admits that audiences do not always like what they hear. Many movie-goers now regularly complain that movies are too loud. Trailers, promoting future attractions, are the worst offenders. When cinema managers reduce the volume setting to curb audience complaints, the dialogue in the feature film becomes unintelligible. The engineers in the studios who record and mix the sound listen so loud that they risk damage to their hearing.

Following critical articles in *The Los Angeles Times*, *Miami Herald* and *Economist*, as well as the movie industry's trade press, Dolby's Vice President, Ian Allen, says he wants to take the "first step towards sanity" by proposing a standard for measuring cinema sound loudness. The new standard is based on techniques developed to safeguard factory workers from industrial noise.

In the 1970s, Dolby Labs developed high quality analogue stereo and surround systems for the cinema. These let cinemas play movies louder. Because the human ear's ability to hear speech through a mix of music and sound effects varies with the overall volume level, Dolby developed a calibration system.

## FADE TO PINK

Before a movie studio mixes a soundtrack, it plays a random pink noise reference signal into the control room at 85 decibels. All cinemas play the same reference signal while adjusting their volume controls or "faders" so that the sound in the auditorium is also at 85dB. The mix of sound heard by the cinema audience then always matches that heard by the studio engineers.

Dolby now realises that the recent transition from analogue to digital sound has given soundtracks more headroom. Like rock groups, movies start loud and then get louder. "Things have gone wrong", says Allen. "The phrase *cut to the chase* no longer has any meaning - the chase frequently starts at the beginning of reel one."

Trailers are even louder than the movies they advertise. The loudspeakers in the cinema may overload and cause distortion which roughens the sound and offends the audience's ears.

When customers complain, the cinema manager reduces the overall volume level to around one half the calibrated setting. Speech is then swamped by music and effects, and audiences complain that they cannot hear what the actors are saying.

## AUDIENCE ANNOYANCE

Dolby has tested audience reaction to a selection of film excerpts and trailers and found that conventional meters give no useful indication of nuisance value. Loudness meters as now used to monitor TV commercials are no help because they give an instantaneous reading which does not measure audience annoyance over a two or three hour screening.

Dolby is now modifying a system used to safeguard factory workers from hearing loss caused by intermittent exposure to loud but varying noise. An LEQ (equivalent continuous sound level) meter measures the sound energy dose over an exposure period and averages it over an 8-hour day. Because movie soundtracks do not usually resemble factory noise, and audiences find overloud music and speech frequencies in the 2kHz to 4kHz band most upsetting, Dolby "weights" the LEQ measurement to be more sensitive in this range.

Weighted LEQ provides a measurement tool which quantifies loudness in the cinema, and Dolby is proposing that the Society of Motion Picture and Television Engineers now agree an LEQ value which defines the threshold between too loud and acceptable. Cinema managers can then go back to using standard settings for their faders. Movies will still contain loud passages but the overall effect will not be so wearing on the audience.

Allen warns SMPTE members that it is in their interests to take urgent action on the special case of trailers. Analysis of trailers produced in Hollywood shows them to have much higher LEQ levels than the movies they advertise. Worst offenders include *The Empire Strikes Back*, *Twister* and *Star Wars*. If sound engineers work for four hours a day mixing the sound for these trailers, they exceed the safe dose for industrial noise and "have a real chance of hearing damage".

Environmental Health Officers now look to the Health and Safety Executives for guidelines on noise risk, both to audiences and cinema staff, who are subjected to prolonged exposure. The HSE says "a number of Councils have now drawn our attention to the problem". The HSE is now working on guidelines for Environmental Health Officers through the Broadcasting and Performing Arts Joint Advisory Committee, which is a forum for unions and employers.

# New Technology Update

50 years on from its invention, the transistor still dominates electronics and its development continues apace.  
Ian Poole reports.

**T**HE TRANSISTOR is now 50 years old! Its invention was announced in 1948 after the first demonstrations took place late in 1947. The team of Shockley, Bardeen and Brattain made their first transistor on 16th December 1947, and demonstrated it to senior managers at Bell Laboratories the day before Christmas Eve.

No one at that demonstration could have realised the enormous effect the invention would have on daily life. Research started after Bell Labs realised the importance of the work which had taken place into semiconductors during the Second World War. In this work, new semiconductor diodes were used to give improved performance for radar systems. These developments lead to Bell seeing the possibilities in new technologies and they set up specialised research teams.

## First Investigations

Initially, Shockley, Bardeen and Brattain had been investigating a field effect device, but had been unable to make the device work. After several setbacks they finally looked at the effect of two  $p-n$  junctions placed close together. First experiments showed promising indications but they realised they had to place the two junctions very close together – about 0.05mm apart – if they were to achieve sufficient gain.

This they did in a rather crude fashion by today's standards. They took a small wedge of perspex and plated it with gold. A razor blade was taken down the edge to cut the gold on either side of the wedge. This was placed onto the substrate of germanium, and held in place by the force from a small spring. The device worked first time and the transistor age had dawned.

It took several years before production devices were available. Materials technology still needed developing so that the devices could be made reliably. This slowly improved over the years with Shockley making the first transistor manufactured using doping techniques.

A major step forwards occurred in 1954 at a conference organised by the Institute of Radio Engineers. Up until this time transistors had all been made from germanium. Several speakers mentioned that it would be several years before a silicon transistor could be manufactured. To their surprise an ex-Bell employee named Teal demonstrated one at the conference, on behalf of a little known company called Texas Instruments.

Since then the development of the transistor has progressed unabated. Higher frequencies, lower noise levels, higher levels of gain and improvements in all other specifications have been seen. Now the transistor and its developments are all part of today's electronics scene.

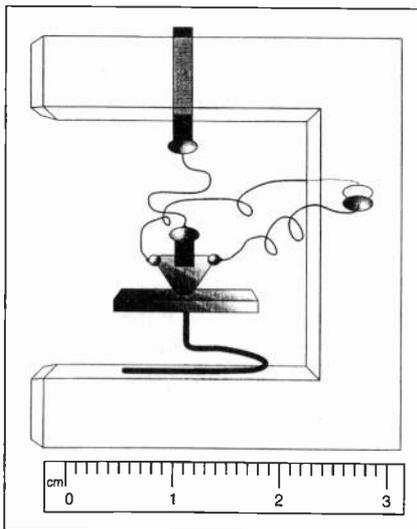


Fig.1. The first commercial transistor, from Western Electric (1951).

## High Frequencies

One of the main areas for development these days is in increasing the speed of transistors. Bipolar devices are often used in radio frequency applications. With the radio spectrum becoming increasingly congested at lower frequencies more activity is taking place at higher frequencies. Many mobile phones operate at frequencies around 1800MHz. This can result in more expensive components having to be used than for 900MHz bands.

A process taken over by Maxim from Tektronix is being employed to make bipolar devices. It is being used to manufacture items for frequencies up to 2GHz. With costs being kept to a minimum, it is ideal for devices aimed at the mobile phone market in both bands, i.e. at both 900MHz and 1800MHz.

Called the GST-2 (Giga-speed Sampling Technology) process, it has an  $f_t$  of 27GHz. It uses trench isolation between different areas and a self-aligned double poly-silicon process. It operates down to voltages in the region of 2V, making it ideal for use in handheld phones.

The original process developed by Tektronix was used for giga sample-per-second ADCs. The new process gives a three-fold improvement over its predecessor, and now that Maxim have taken the process over they have been able to use its speed for radio frequency applications.

The process is relatively complicated, although it can still be made at a sufficiently low cost to make it attractive for mobile phones. Despite its complexity, yields are high and this means that low costs can be maintained.

To produce the i.c.s, a variety of processes are required. The more usual processes of epitaxial growth, photolithography and etching are central to the process, together with very fine geometries and ion implantation. However, the major differences with other technologies are found in the use of gold, and barrier metals. Another innovation is the use of active ions to achieve geometry tightness. These all combine to give the exceedingly high performance of the technology.

This new process gives the possibility of manufacturing radio frequency i.c.s, low noise amplifiers, power amplifiers, Schottky diodes and a variety of other devices, all of which could find widespread use in vast quantities in mobile phones.

## High Voltage Transistor

A new transistor which has been launched recently by SGS Thomson Microelectronics combines both bipolar and f.e.t. technology in a single device to allow voltages of up to 1.5kV to be switched. Essentially it consists of a bipolar-f.e.t. cascode pair which can be controlled by logic signals.

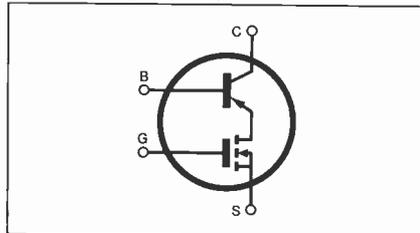


Fig.2. Cascade bipolar-f.e.t. high voltage switch.

From the circuit symbol of the device it can be seen that the emitter of the bipolar transistor is connected to the load through the f.e.t. By maintaining the emitter at a constant voltage, it can be switched on and off by switching the f.e.t. Both the bipolar transistor and the f.e.t. take the full load current, but the way in which the circuit operates means that the bipolar transistor takes the high voltage.

Often high voltage semiconductor devices have a slow turn-off speed in view of the large amounts of stored charge. This device has a much faster turn-off than many others because of its unusual configuration. The f.e.t. device turns off and collector current can no longer flow through the emitter for the transistor. Instead, it flows back through the gate, removing the stored charge and turning the device off much faster than would normally happen. Typically, turn-off times of under 100ns are quoted, which is very fast for a device of this nature.

# SQUIRES

MODEL AND CRAFT TOOLS

A comprehensive range of miniature hand and power tools featured in a fully illustrated

144 page Mail Order Catalogue

## New 1998 Issue

*SAME DAY DESPATCH  
FREE POST & PACKING*

For your free copy of our catalogue write, telephone or fax to:

Squires, The Old Corn Store,  
Chessels Farm, Hoe Lane,  
Bognor Regis, West Sussex  
PO22 8NW



Tel/Fax: 01243 587009



## JANUARY SALE!

GREAT DISCOUNT OFFERS ON USED EQUIPMENT  
SO DON'T DELAY - ORDER TODAY!

### OSCILLOSCOPES

|  |        |
|--|--------|
| TEKTRONIX 475 Real-Time Scope 200 MHz..... | £250   |
| TEKTRONIX 475A Real-Time Scope 250MHz..... | £275   |
| H.P. 1725A 275MHz Real-Time Scope.....     | £280   |
| H.P. 54501A 100MHz Digitising Scope.....   | £995   |
| YOKOGAWA DL1200 4-Channel 100MHz           |        |
| Digitising Scope with plotter.....         | £750   |
| TEKTRONIX 2430 DSO 100MHz.....             | £1,295 |

### SIGNAL PULSE OTHER GENERATORS

|   |      |
|---|------|
| TEKTRONIX SG503 Levelled Sine Wave Generator          |      |
| Including Tm501Power Frame. Excellent value for.....  | £295 |
| TEKTRONIX PG506 Calibration Generator                 |      |
| Including TM501 Power Frame. Excellent value for..... | £295 |
| FARNELL LFM4 Sine/Square Wave.....                    | £50  |
| TEKTRONIX FG501 Function Generator                    |      |
| Including TM501 Power Frame. Excellent value for..... | £295 |
| WAYTEK Signal Generator Model 130.....                | £75  |
| WAYTEK Signal Generator Model 103.....                | £50  |
| ADVANCE Pulse Generator Model PGS8A.....              | £75  |
| EXACT Voltage Controlled Function Generator           |      |
| 10Hz to 10MHz Model S13.....                          | £170 |
| DATAPULSE 117 Pulse Generator.....                    | £195 |
| TEKTRONIX 106 Square Wave Signal Generator.....       | £50  |
| KIKUSUI Signal Generator Model 417A.....              | £50  |

### GENERAL EQUIPMENT

|  |      |
|--|------|
| DECCA Sound and Vision off air Receiver..... | £60  |
| RACAL True RMS Millivoltmeter 9301.....      | £195 |
| EASI-DISK 5.25 Programmable Disk Drive.....  | £85  |
| JTT Eprom Programmer Model PEP1.....         | £150 |
| DATRON Temp/Humidity Pen Recorder.....       | £35  |
| DATRON 3000 Gang Prom Copier.....            | £195 |

### POWER SUPPLIES

|  |     |
|--|-----|
| FARNELL L30BT 0-30V 1A twin p.s.u.....       | £85 |
| FARNELL L12-10C 0V-12V 10A single p.s.u..... | £95 |
| FARNELL 0V-30V 2A twin p.s.u.....            | £85 |

### OSCILLOSCOPE CALIBRATORS

|  |      |
|--|------|
| BRADLEY 192 Volts/Time/Pulse Edge..... | £125 |
|--|------|

### VOLTAGE CALIBRATORS BREAKDOWN LEAKAGE IONISATION TESTERS

|  |      |
|--|------|
| FLUKE High Accuracy Volts and Current Calibrator                               |      |
| Model 332A.....  | £395 |
| AVO RM215 L2 A.C.-D.C. Breakdown/Leakage and Ionisation Tester.....            | £350 |
| ROTEK High Current Adaptor.....  | £60  |
| VALLHALLA SCIENTIFIC INSTRUMENTS A.C.-D.C. Current Calibrator Model 2500E..... | £195 |
| FLUKE 341A D.C. Voltage Calibrator.....  | £475 |
| TIME ELECTRONICS D.C. Voltage Calibrator Model 2003S.....                      | £395 |

### EX DEMO STOCK

(12 MONTHS GUARANTEED)  
EXCELLENT CONDITION ACTIVE PROBES

|   |      |
|---|------|
| ARMEX FSP 500 500MHz Switchable (1x1x10)..... | £245 |
|---|------|

### TEKTRONIX MODULAR POWER FRAMES FOR PG506 SG503 TG501 FG501 ETC

|  |     |
|--|-----|
| TEKTRONIX TM501 Single Module Frame..... | £40 |
| TEKTRONIX TM502 Twin Module Frame.....   | £80 |
| TEKTRONIX TM503 Triple Module Frame..... | £80 |

### GENERAL EQUIPMENT

|                                      |     |
|--------------------------------------|-----|
| CAMBRIDGE High Accuracy AVO. vo..... | £75 |
| SELECT TEST AVO.....                 | £25 |

Please call for stock availability and details. Carriage for units over £200 is £12. Carriage for units under £200 is £8. VAT to be added to the total value of the order. User manuals are supplied if possible. Used equipment guaranteed.

TELEPHONE: 01492 580080. FAX: 01492 580081  
E-MAIL: ARMEX123@MCMAIL.COM. WEB SITE ADDRESS: WWW.ARMEX123.MCMAIL.COM  
19 FFORDD SAM PARI, CONWY MORFA INDUSTRIAL ESTATE,  
CONWY, N. WALES LL32 8HH

**FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!  
FREE!**


**FREE! FREE! FREE! FREE! FREE! FREE!**  
**OUR 1998**  
**CATALOGUE**  
**AND LATEST**  
**BARGAIN LIST**  
**ABSOLUTELY**  
**FREE!**

**PHONE, FAX OR WRITE TODAY!**

## GREENWELD


27D Park Road · Southampton · SO15 3UQ  
TELEPHONE: 01703 236363 FAX: 01703 236307  
INTERNET: <http://www.herald.co.uk/clients/G/Greenweld/greenweld.html>

# INGENUITY UNLIMITED

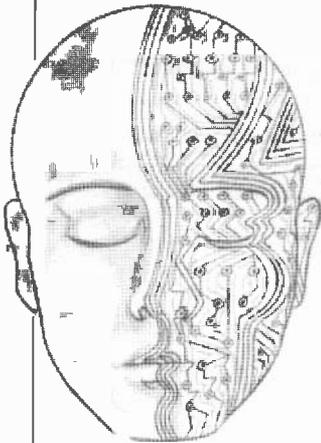

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit tips, not simply mechanical or electrical ideas. Ideas *must be the reader's own work* and **not have been submitted for publication elsewhere**. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should preferably be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. **Please draw all circuit schematics as clearly as possible.**

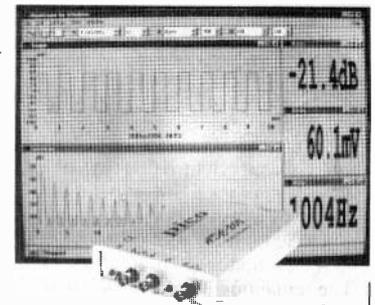Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. They could earn you some real cash and a prize!



## WIN A PICO PC BASED OSCILLOSCOPE

- 50MSPS Dual Channel Storage Oscilloscope
- 25MHz Spectrum Analyser
- Multimeter
- Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours.

Every six months, Pico Technology will be awarding an ADC200-50 digital storage oscilloscope for the best IU submission. In addition, two single channel ADC-40s will be presented to the runners up.

## Cheap L.E.D. Blinker – Flash Back.

**T**HE OBJECTIVE of the circuit of Fig.1 was to flash an l.e.d. once per second, using a 1.5V battery, at such a low current that it would last up to the shelf life of the battery. The solution uses two transistors and is cheaper than using a custom l.e.d. flasher chip.

When current flows through resistor R1, transistor TR1 turns on along with TR2. Inductor L1 initially presents a high impedance so TR2 collector (c) is pulled low. This is passed by capacitor C2 to provide some regenerative feedback to TR1 base (b).

Soon, L1 starts to pass current and eventually TR1 collector starts to swing high due

to feedback passed via C2. Thus TR1 is switched out, which consequently switches off TR2 very quickly.

The inductor's collapsing field will try to induce a current towards TR2 collector but instead serves to illuminate l.e.d. D1, the induced voltage being more than enough to do this. This occurs many times in approximately 20ms. The cycle starts again about a second later.

The circuit could be used as a bicycle l.e.d. flasher or imitation burglar alarm blinker.

*John Hyland,  
Strood, Kent.*

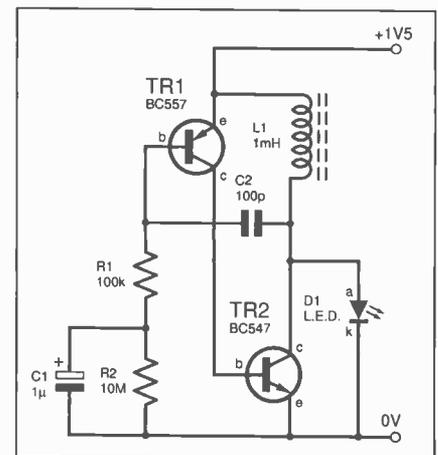


Fig.1. Cheap L.E.D. Blinker circuit.

## Simple Thermostat – Keeping it Cool

**W**HEN challenged to design a cheap system to switch on a cooling fan for an electronics enclosure when a certain cabinet temperature was reached, the circuit of Fig. 2 was eventually arrived at. The fan relay RLA had to switch when the detected temperature rose to a certain value above ambient, so a differential thermostat was required.

Probably the cheapest transducer available is the ordinary silicon diode: 1N4148s cost 50 pence per hundred! A normal diode has a forward voltage drop which varies by 2-3mV per degree Celsius.

When fed with a constant current, it forms a simple and reliable temperature sensor which is reasonably linear over a wide range. If a differential temperature control is required, it is a fairly simple matter to use a pair of diodes in a bridge circuit, and use a potentiometer to set up any offset required.

In Fig. 2, both the sensor and reference diodes are "doubled up" to give an increased sensitivity of about 4.5mV per degree Celsius. The op.amp IC1 has no feedback and operates in open-loop mode as a comparator, fed by the bridge network which itself is supplied by the 12V regulated supply (Zener D5); one pair of diodes D3, D4 acting as

an ambient temperature reference whilst the other set (Sense) is used as a probe, with capacitor C1 removing noise.

The trimmer potentiometer VR1 provides any offset required and allows temperature control of around 12°C. The fan is switched

by relay RLA which is driven by the transistor switch TR1. An ordinary 741 op.amp will be quite adequate in this application although a CA3140 was used for IC1 in the prototype.

*Ted Whittaker, Stone, Staffs.*

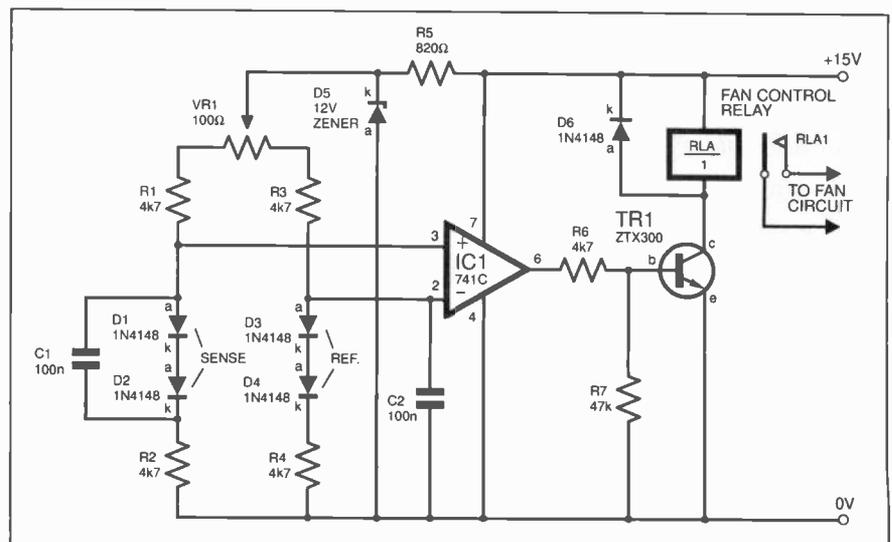


Fig.2. Circuit diagram for a Cooling Fan Thermostat.

## Simple Liquid Crystal Display Tester – Enlightened Performance

A SIMPLE circuit which will help test the performance of an l.c.d., and is ideal for experimenters, is shown in Fig.3. The circuit produces a bi-phase square wave with negligible d.c. content and uses a hex Schmitt inverter, 40106.

An oscillator is based around IC1a whilst IC1b is a phase splitter. The remaining inverters form a pair of buffers and drivers.

The outputs of the circuit are terminated with 47k (kilohms) resistors in series with a pair of test probes. With the values shown, IC1 generates a square wave of approximately 45Hz, and the circuit will operate on a d.c. voltage from 3V to 15V d.c.

To test a particular l.c.d., touch the backplane using either of the test probes – usually the backplane is the left-hand or right-hand connection – and apply the other probe to any segment connection. The segment should change accordingly. If the display is a multiplexed type, then all segments should change.

*Rupen Chanda,  
Madras, India.*

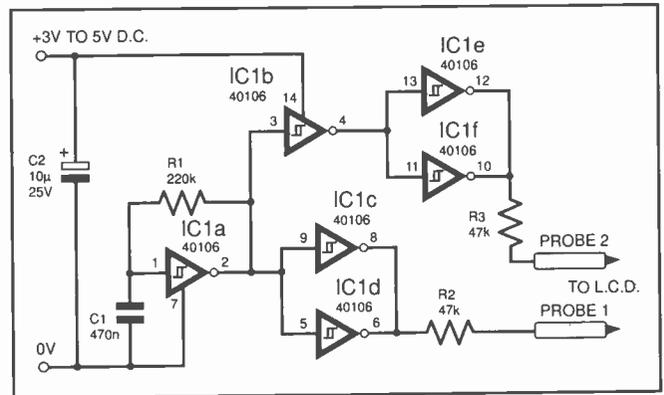


Fig.3. Circuit diagram for a simple Liquid Crystal Display (LCD) Tester.

## Isolated Multi-output Power Supply – Four for One

A CIRCUIT was required which would provide several *isolated* power supplies, for use in driving a power FET bridge network. Multiple mains transformers could have been used but this would have been bulky and expensive, and because the current demanded by the power supplies was low, the circuit shown in Fig.4 was devised.

The secondary of a mains transformer (not shown) is rectified by diodes D1 to D4 and filtered to provide a regulated +15V supply via voltage regulator IC1. This is used as the

input to a small inverter circuit. Resistor R1, capacitor C5 and IC3a form a 200kHz oscillator which is passed to a flip-flop formed by IC2b, one half of a 4027, the output of which is 100kHz with 50 per cent duty cycle applied alternately to the two MOSFETs TR1 and TR2.

A delay is included by the diode and RC networks present on the inputs to the inverters IC3e and IC3d. This eliminates the possibility that both transistors could switch on together for a short period. Both transis-

tors then drive the primary winding (18 turns each) of transformer T1 which is a small custom-wound high frequency transformer.

Transformer T1 is wound on a standard "RM8" bobbin with an inductance factor ( $A_L$ ) of 250. The circuit has four secondary windings (20 turns each) which are rectified and filtered to provide the isolated supplies. Each output is easily capable of providing 15V at 20mA.

*Duncan Boyd,  
Blackburn, West Lothian.*

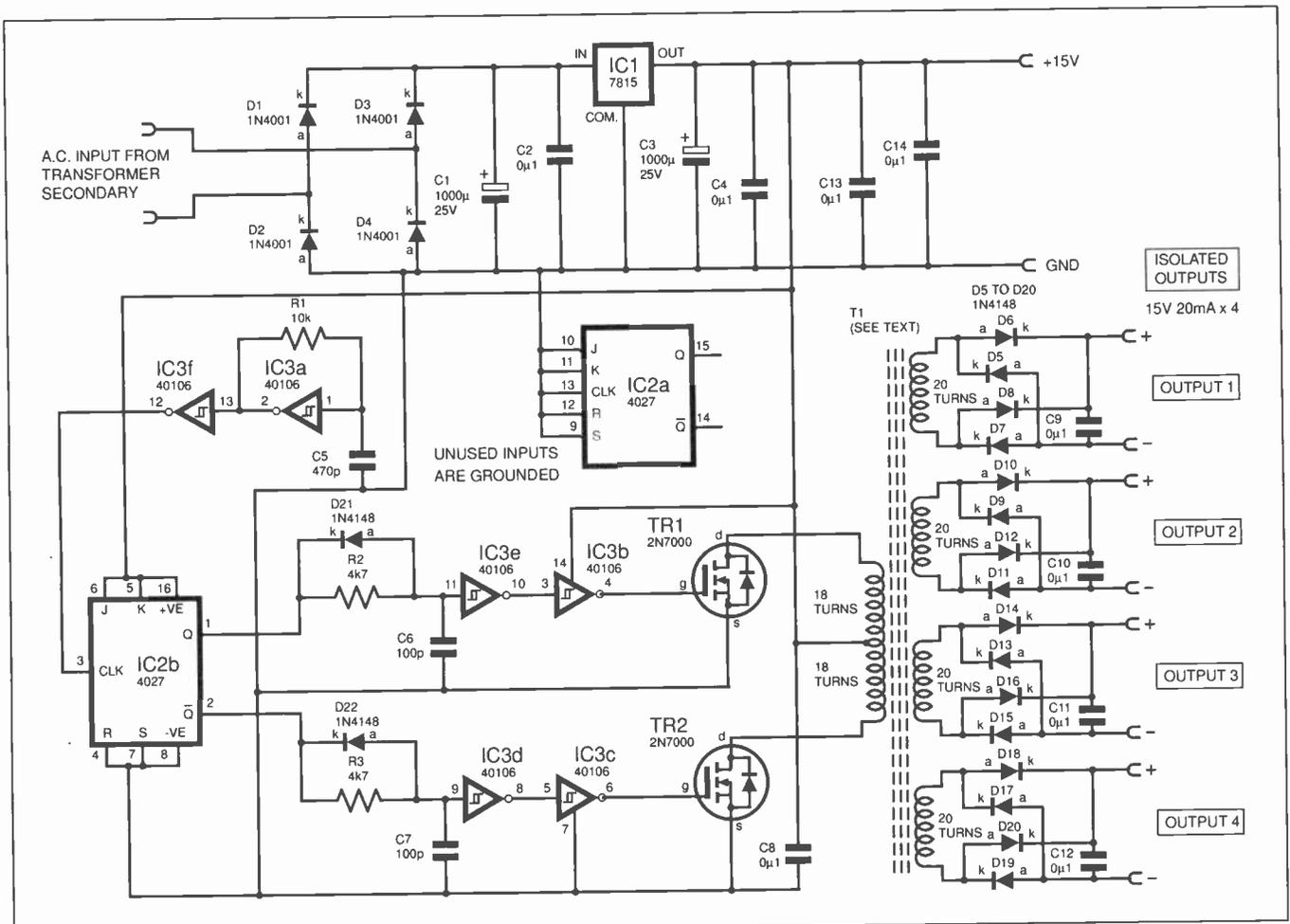


Fig.1. Circuit diagram for the Isolated Multi-output Power Supply

## Daisy-chaining Decoder Chips – A Thorny Problem

THE JOHNSON counter with fully decoded outputs can be a very useful device indeed. However, as far as I can discover, the only readily available CMOS chips are the CD4022, with eight fully decoded outputs, and the CD4017, with ten.

A recent project involved the generation of three-phase signals using digital techniques, based upon the synthesis of sinewaves as a series of voltage levels. This was accomplished using a Johnson counter with a set of “weighted” resistors to create an artificial sine wave. To improve the resolution of the sinewave, I wanted to “daisy chain” several counters and after much consideration arrived at the circuit of Fig. 5.

If we consider the state after reset, both counters will have a logic high on their 0 output. Since the 9 output of counter “A” will be low and this is wired to its Count Inhibit pin, counter “A” is enabled, and the inverter “A” causes counter “B” to be disabled.

As the clock cycles, a logic High ripples along the outputs of counter “A” until it reaches 9. At this point, several things happen very rapidly! Counter “A” is disabled, and conversely counter “B” is enabled via

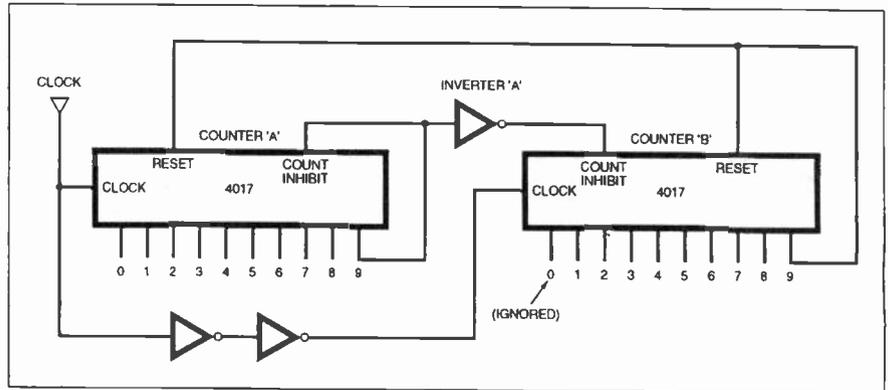


Fig.5. Circuit diagram for cascading decoders to improve the resolution of an artificial sine wave signal.

the inverter “A”. The clock pulse, which is very slightly delayed by the two inverters in series, clocks the high from the 0 output to the 1 output in counter “B”.

Subsequent clock pulses ripple the logic-high along counter “B” until it reaches the 9 output, when the system will reset and we are back to 0. Consequently a fully-decoded ring counter with up to 17 outputs (nine in counter “A”, eight in counter “B”) is

produced. The system could be extended further if necessary.

Ted Whittaker,  
Stone,  
Staffordshire.

● See also *Circuit Surgery*, November 1997 in which Ian Bell of the University of Hull discusses further techniques for cascading digital counters. A.R.W.

## Neon Torch – Electronic Gas Light

AN electronic version of a torch which uses a neon gas-filled bulb instead of a filament bulb, is shown in Fig. 6. It is based on a 555 running in astable mode. T1 is a 3V-0V-3V transformer wired in reverse “step up” mode which is used to step up pulses delivered by the timer.

A small neon indicator (LP1), of a type called a “green fluorescent glow lamp” (an ordinary neon indicator will give poor results) is used for the bulb.

The neon bulb also has a much longer life expectancy than a traditional filament bulb.

The frequency of operation is determined by the resistor-capacitor network R1-R4/C1, and this is adjusted using a d.p.d.t. switch (S1) to offer “bright” and “economy” settings. Although not as bright as a conventional torch, the Neon Torch can easily light the way three or four metres in front.

Whereas an ordinary krypton torch consumes some 3W of electricity, this novel design uses 0.7W in “bright” modes and 0.3W in “economy” setting – one tenth that of an ordinary torch. Powered by six AA size alkaline cells in bright mode, the torch will shine for two days and two nights continuously. For best results, the neon bulb should be set into a reflector salvaged from a torch.

Rev. Thomas A. Scarborough,  
Fresnaye, Cape Town,  
South Africa.

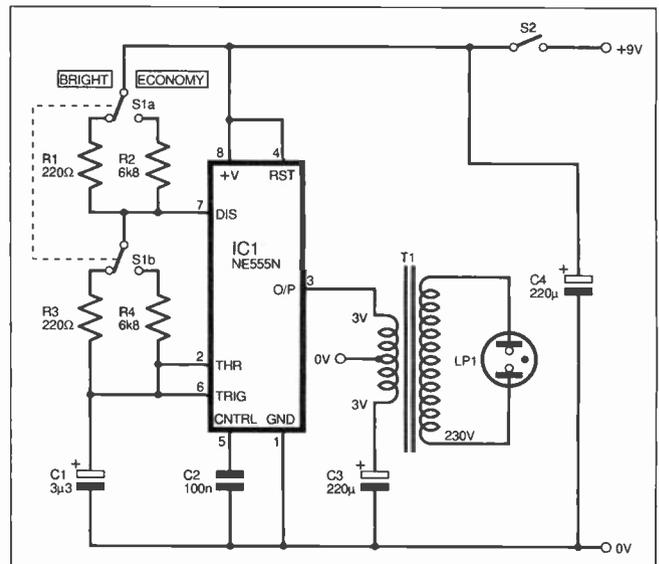



Fig.6. Circuit diagram for a Neon Torch.

# INGENUITY UNLIMITED
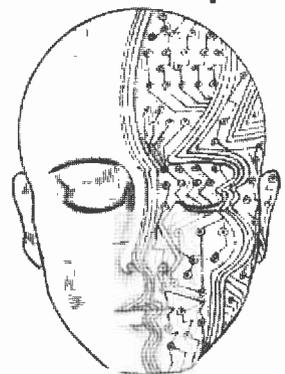
## BE INTERACTIVE

IU is *your* forum where you can offer other readers the benefit of your Ingenuity.

Share those ideas and earn some cash and a prize!



# READOUT

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

## Win a Peak DTA30 Transistor Analyser

The DTA30 will test and identify the type (*nnp/npn*) and the leads of any bipolar transistor connected to it.

Every month Peak Electronic Design Ltd will be giving a DTA30 to the author of the best *Readout* letter published.



### ALCHEMY?

Dear EPE,

To answer JB's question about conflicting evidence concerning water descalers (*Readout* Dec. '97), the reason my father had his descaler removed was because it was sold as an "electric water softener" and if it did anything it certainly didn't soften the water!

Some manufacturers make vague claims which seem to imply a softening effect which overlooks the fact that the terms *hard* and *soft* water have a specific meaning chemically, and unless calcium and magnesium ions are removed from hard water, or exchanged for sodium ions, then the water will remain hard.

I'm not prepared to believe that a descaler does this unless the alchemists were on the right track after all but looking for the wrong product! However, I have found that scale around my kitchen sink is reduced and cleans off more easily, so while I accept that the scale seems to be less "sticky" I cannot accept that the water is softened in any way.

As regards research, yes I do spend quite a bit of time researching my various interests. In the case of electronics, I have a 2-drawer filing cabinet full of notes, cuttings, data sheets etc., as well as a decent collection of technical books including even my old A Level text books.

I thoroughly recommend keeping notes on everything one tries even if it was unsuccessful. I also study every circuit in

*EPE* and make note of any sub-circuit that strikes me as ingenious, even if the whole project is of no interest to me.

JB's request for info on a Kirlian camera rang a bell and a hunt through my cuttings turned up a design published in *Elektror* (Oct '77). The article gives reference to an item by Pehek, Kyler and Faust entitled *Image Modulation in Corona Discharge Photography* published in *Science*, Oct. '76, page 263. Photography is another interest of mine, by the way; strange how it often seems to go with an interest in electronics.

Best of luck JB, I'll be interested to see what design you come up with, but don't ask me to believe it will produce a photograph of something's "psychoic aura"!

**Barry J. Taylor,  
Rickmansworth,  
Herts**

*What a useful contributor you are! Thanks for all the info - sorry we have to cut your letters down, but do keep communicating.*

*I would also refer readers to Don Phillips' Kirlian Camera of PE (not EPE) May '89 (if their local reference library has a copy on file). I liaised with Don in the publishing of that article while I was on PE, before PE and EE combined to become EPE.*

*My hope is to try to achieve the same effect using modern technology and "daylight" processing photographic*

*materials (photography has featured greatly in my life too - but that's another story!).*

*Any more info on Kirlian Cameras and Water Descalers will be appreciated.*

### PIC-ING PIPES

Dear EPE,

I would wish to attempt the *PIC Water Descaler* (Oct. '97), but the article appears to assume that all water pipes are of copper. My inlet (the house was built in 1938) is lead. There is, of course, a "normal" internal stop-cock and I suppose the windings could be wound around this, but not in one run. I assume that lead is an insulative material and the diameter is a lot more than 15mm.

**G. Wilsher,  
Hanwell,  
London W7 2AP**

*We do not believe that the descaler will work correctly if wound around a stop-cock. If the pipe after the stop-cock is copper or plastic, then wind it onto that.*

*If you have no copper or plastic pipes, but only steel or lead (which we understood had all been replaced because of the health hazard - contact your local Water Board with urgency about yours!) then you will not be able to use the descaler.*

*We are not clear why you think lead insulative - certainly it is resistant to penetration by radioactivity, but to electricity it is highly conductive.*

### METEORS

Dear EPE,

In his *Satellite Celebration* article in the November '97 issue, Barry Fox refers to meteors as "the scraps of dust and rock which travel through space at high speed and eventually fall to earth as shooting stars".

I would like to highlight a popular misconception regarding the nature of a meteor.

Barry Fox should, in fact, be referring to *meteoroids* which only become *meteors* when they enter our atmosphere at a height of approximately 60 miles and are seen as flashes of light. A meteoroid which survives its path through the Earth's atmosphere and actually reaches the ground is then referred to as a *meteorite*.

A satellite at risk from meteor damage would therefore need to be in a rather low orbit!

**Martin R. Sturgess,  
via the Net**

*Which, of course, we all ought to have known from the days when we had Patrick Moore's Space Watch column in PE!*

## ★ LETTER OF THE MONTH ★

### PSEUDO SCIENCE

Dear EPE,

I was somewhat disappointed with your reply to Mr Taylor (*Readout* Dec. '97) and would take issue with you as to how you should present such pseudo science, if that it is.

When people buy a magazine such as yours, they learn to rely upon the information that you give. For example, if you recommend a transistor to carry a certain current then it is accepted because you have the relevant technical knowledge and you know that the recommended transistor has certain operating characteristics within limits. You also know that those operating characteristics will be near enough the same if they are measured in a blue agate pyramid or whist chanting an esoteric mantra. This reproducibility is surely the basis of Scientific Method.

Because your readers expect such objectivity from your magazine, by virtue of the act of publishing anything, you

appear to give your imprimatur to the scientific basis of that subject; I must admit that I assumed that "water descalers" were more scientifically based after seeing the project in the Oct. '97 issue.

I think, therefore, that if there are such doubts about such projects these should be clearly stated. Just because something is for sale does not give it any more credibility; I trust that you do not drive around with a strap hanging from the rear bumper of your car to prevent car sickness!

**Martin Chandler M.Sc,  
Ashford,  
Kent**

*In principle we agree with what you say, although it is a subject that is worthy of a good debate. Suffice to say for the moment that we tried to find out more about electronic water descaling, including through one university, but we have been unable to find out more.*

## CHEERS TO THE BEEB

Dear EPE,

I actually cheered when I saw the letter from I. Scott-Young in the December '97 issue. No, he is not the only one with a BBC "B"! I am also enduring the same frustration regarding programming PIC devices.

I do fully understand the impracticalities as explained by JB in his reply. However, I am sure that I speak for many when I say that, we "vintage" computer types are NOT asking for listings for our individual "ancient" machines. Most of us enjoy the challenge of writing our own programs which we can tailor to our particular need.

To do this, all we really need to know are the input requirements for the PIC device, i.e. the sequence, timing and clocking in of the data program. (Mr Scott-Young is ahead of me there!) Also, in the case of a published project, a listing of the PIC's actual program. This wouldn't be all that lengthy, would it?

Fear not, we'll get the program in there if you'll just tell us what the darn thing is supposed to contain!

Excellent mag none-the-less! I am looking forward to the *PIC Tutorial*, hoping and praying that it will provide some information which we enthusiasts with "steam driven" computers can use.

**Raymond Ridgwell,  
Torrington, Devon**

*Editor Mike Kenward offers his comments on the non-PC problem in his Editorial this month. In many ways, I've already offered my thoughts in my reply to I. Scott-Young.*

*I have to re-iterate, though, that we cannot publish PIC software on the magazine pages - it IS too long. My Time Machine source listing is 1216 lines long and up to 70 characters wide. Its object code (binary) is not printable without conversion to hex in an ASCII character format, then it would be 86 lines by 59 characters - still too long.*

*Don't you, and others who are in a similar predicament, know someone who has access to a PC who can do printouts or conversions for you? It's also not hard to interface a PC to a BEEB via the PC's parallel or serial ports and the BEEB's User Port. I did it between an Amstrad 1640 and a PET 32K (very similar in command architecture to the BEEB) some year's back. Although I wrote machine code for both machines in order to do it (8086 and 6502), that was only for speed; Basic will do it just as accurately, if at a slower rate.*

*Come on folks, you're obviously into computing - surely you and a friend or colleague can come up with a solution that uses our disks!*

## PSEUDO-CODE

Dear EPE,

As someone who at the moment is in the programming camp, but who wishes to learn more about electronics, I have started buying *EPE*. I note in your December issue a letter (*How QBasic?*) which makes the statement that Microsoft and QuickBASIC introduced the idea of pseudo-code as a stepping stone between the source code and machine code.

As far as I am aware, this was first used by Nick Wirth when he designed PASCAL in the early 1970s, using P-code. If it had been an MS invention, then we wouldn't have heard the last of it!

As a point of interest, this idea of an interim code has made a comeback in recent years in the shape of Java, the current flavour of the programming month, as it allows a 2-stage translation process. The first stage is from source to P-code. This is the same for all processors. The P-code is then used as the input for a translator unique to each processor.

In this way, one initial program can be run on any type of computer for which the second stage, called a Java Virtual Machine, has been written. Perhaps one day PICs will have a JVM of their own!

I hope this is of interest - have fun, it's not worth it otherwise!

**Bob Wightman,  
via the Net**

*It is of interest, and we do have fun! You might be interested to know that TASM, which we supply as our PIC16C84 compiler, is capable of compiling code to suit many processors other than the PIC. It is also possible to write your own translation table for use with processors of your own choice - as Derren Crome did for the PIC16C84.*

## TIMELY TICKINGS AND PIC-INGS

Dear EPE,

I have just recently completed the construction of the *EPE Time Machine* clock featured in the November issue. The pre-programmed PIC chip was purchased from Magenta.

However, I was surprised to discover that the time displayed after the Rugby time signal had been correctly decoded is one second fast. It appears that the seconds counter is being reset on second number 59, i.e. at the end of the frame code sync pulse.

I should add that I have built two different types of Rugby clock which work perfectly to the exact second.

**J.M. Baldwin, Bradford, Yorks,  
via the Net**

*Absolutely right and my error (of +800ms, not +1s)! In an early prototype of the software, I had another flag which was set on receipt of the Rugby sync pulse. On detection of this flag, one second later, the Rugby decoding process was then entered, and the time updated correctly.*

*In the complex process of compacting the code in order to make room for the Millennium countdown, I was desperately in need of more dedicated registers than I had available. Somehow I made a fundamental mistake when recoding to do without that flag register, entering the decoding routine on receipt of the sync code, rather than on the second following it.*

*I have corrected the error, using the sync register itself as the flag, and putting the decoding routine call prior to updating the shift register chain. As confirmed by the "time sponsored by Accurist" via BT's 123 code, the pips and the seconds now correspond within about -200ms!*

*It should be pointed out that the updating can never occur immediately on*

*the leading edge of "second zero" due to the sequential nature of the program commands that cause the updating. Pure electronic circuitry could achieve such synchronisation, but software (even if triggered by an external interrupt generated by the occurrence of the Rugby pulse) automatically introduces a delay before the update actually occurs.*

*In theory, the period could be shortened by decoding prior to the receipt of the trigger signal, but this would require additional temporary storage registers to hold the decoded data prior to putting it onto the l.c.d. screen. Such additional registers were not available, nor was there enough program data space available to use the technique anyway.*

*The decoding actually commences at the end of the first pulse of "second zero", i.e. 200ms after the pulse begins, the updating is then complete well within then next 1/50th of a second.*

**If any reader who has bought the Time Machine's pre-programmed PIC16C84 from Magenta would care to send it to me at the editorial address I will be pleased to re-program it with the new software. Similarly, I will update anyone's EPE PIC-Disk if they return it to me. The amended software is also on our website. Please send an adequately stamped and self-addressed package for me to return the PIC or disk to you. Also note that for security reasons the disk or PIC must be the same one you received from us or Magenta.**

*Interestingly, the programming for the Time Machine might have been simplified had the new PIC16F84 been available at the time. In many ways the PIC16F84 is totally interchangeable with the PIC16C84. It does, though, have 68 RAM data bytes (compared to the C84's 36), which is a significant advantage.*

*Microchip describe the F84 as having a "flash" program memory instead of conventional E<sup>2</sup>prom memory. They are coy, though, with information about what flash actually means in this context. It does not mean that the F84 can be programmed faster than the C84, nor does it run at a faster speed (still 10MHz max.); the program memory capacity remains at 1KB.*

*There are false rumours circulating that the C84 is to be dropped in favour of the F84. We are assured by Microchip that they have no intention of dropping it. They say that while they will encourage the use of the F84, the C84 will continue to be available. Microchip also commented that they never delete products from their range.*

*It is likely that I, as a designer/author, will probably move over to the F84 when the greater number of registers are needed. This may mean in future that programs written for the F84 may not be usable on the C84. But, anything written for the C84 will always run on the F84.*

*A further advantage of the F84, as said by Microchip, is that its price is likely to become lower than that of the C84. As to whether component suppliers will pass on any price advantage to customers remains to be seen. Do encourage your supplier to stock the F84 and to offer a good price on it.*

# Electronic CAD For Windows

£19.95 ea




Compatibility from the



*The complete,  
powerful schematic  
and PCB layout  
tools for Windows.*

*This is really easy!*

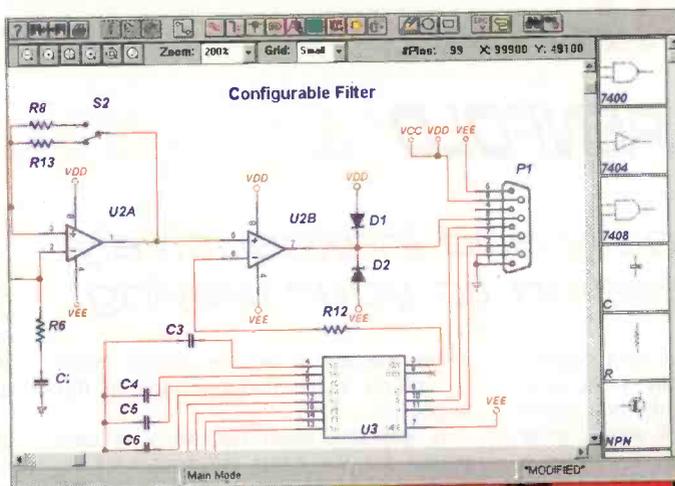

WinDraft v2  
Now Shipping

## ① Design your schematic with WinDraft...


- Choose from over 10,000 parts in WinDraft's complete library of components.
- All the utilities you need are included in the package from an Electrical Rules Checker to netlist output to printing and plotting outputs.
- Cut and Paste into other Windows applications such as Microsoft Word. Makes it easy to document your projects!

## ② Create the artwork for the PCB with WinBoard...

- Quickly route boards on up to 16 layers.
- Use SMD or through-hole components — or mix them for maximum flexibility.
- Unique pad-stack editor can create pads of virtually any size or shape.
- Rotate components in 0.01° increments.

## ③ Create a Gerber photoplot, NC Drill, pick and place, and other manufacturing outputs!
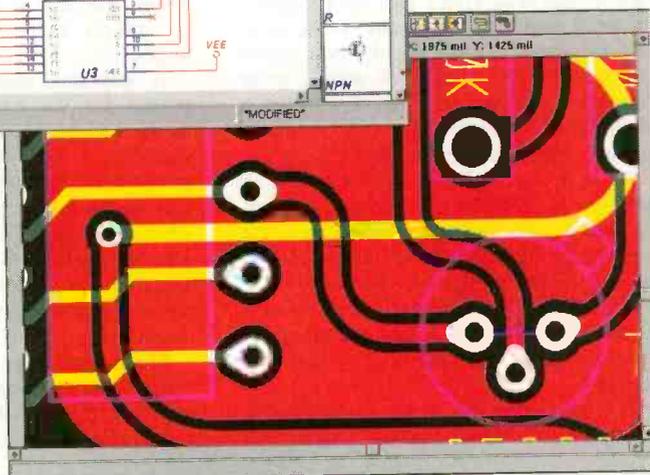
## ④ Expand the program capacity at any time!



### WINDRAFT®

Schematics

### WINBOARD®

PCB Layout

Easily create designs up to **200** pins. Compatible with industry standard formats. Expand the capacity at any time. IVEX Products are also available from all Good high street electronics shop's, <http://www.thepcsol.demon.co.uk> for your closest retailer.

The  
PC  
Solution

The PC Solution,  
2a High Road Leyton  
London, E15 2BP.  
Fax 0181 926 1160

<http://www.thepcsol.demon.co.uk>  
email [info@thepcsol.demon.co.uk](mailto:info@thepcsol.demon.co.uk)  
All trademarks acknowledged. E & OE

**Tel 0181 926 1161**

# WAA-WAA EFFECTS PEDAL

ROBERT PENFOLD



*How to easily and inexpensively add expression to your playing.*

**T**HE waa-waa effect has been popular with guitarists for many years now, and one reason for this popularity is that it provides an easy means of adding great expression to your playing. It is also a relatively simple effect that can be implemented using inexpensive circuitry.

A waa-waa unit is basically just a tunable filter that boosts a narrow band of frequencies. As the pedal is operated, the operating frequency of the filter is moved up and down, giving the familiar "waa-waa" sound. The filtering boosts certain harmonics in the signal, and operating the pedal changes the harmonics that are affected.

For good results, it is essential that the processed signal contains reasonably

strong harmonics, but an electric guitar is unlikely to be found lacking in this respect.

A waa-waa pedal represents an easy project for the home constructor as far as the electronics are concerned, but the mechanical side of construction can be problematic. The difficulty is that the effect is normally controlled by a pedal which operates a potentiometer. Producing a pedal mechanism that is genuinely reliable and will not let you down at the worst possible moment is more difficult than one might expect.

Most waa-waa units for the home constructor use some form of alternative approach that avoids the need for a pedal mechanism. The most simple of these

alternatives is to use a low frequency oscillator to automatically operate the effect at a preset rate, but this gives rather "mechanical" results with no real opportunity for the player to add expression to the music.

The other alternative, and the one used here, is to have the effect controlled via a pushbutton switch. The switch is foot operated, and acts as a sort of pseudo foot-pedal. Operating the switch results in the effect being swept upwards in frequency, and releasing the switch results in the effect being swept back down again.

This is not quite as versatile as using a conventional foot-pedal mechanism, since the pushbutton switch does not give any control over the rate at which the effect is swept up and down.

However, these rates are individually adjustable via front panel controls and can be set at appropriate rates prior to

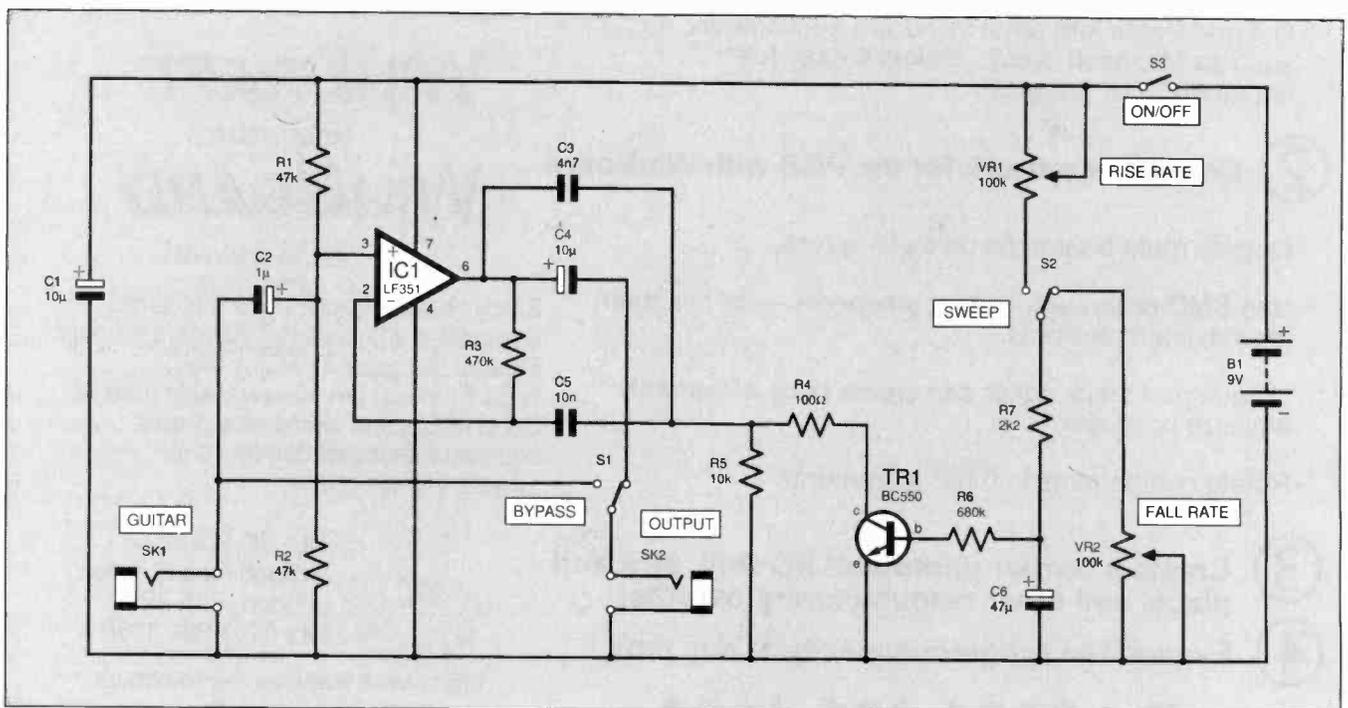


Fig. 1. Complete circuit diagram for the Wah-Wah Effects Pedal.

commencing a piece. This gives the player much better control of the effect than simple automatic control, and does enable the effect to be used in an expressive fashion.

## CIRCUIT OPERATION

The circuit diagram for the Waa-Waa Effects Pedal is shown in Fig.1. IC1 is an operational amplifier which is used in the non-inverting mode, with input biasing provided by resistors R1 and R2. These set the input impedance at 11 kilohms.


The negative feedback circuit includes a simple R-C (resistor-capacitor) network that provides frequency selective feedback, and produces a bandpass filter action. The configuration used is almost the standard op.amp bandpass filter circuit, with the frequency selective negative feedback provided by capacitors C3, C5 and resistor R3, together with the series resistance of R4 and R5.

These components set the centre frequency of the circuit at a middle audio range, but in this application we need the filter frequency to be variable over middle to high audio frequencies.

It is possible to tune the filter by adding a variable resistance in parallel with resistor R5. This is the purpose of transistor TR1, which acts as a sort of crude voltage controlled resistor. The resistance across TR1's collector (c) and emitter (e) terminals depends on its base (b) input current, with higher currents giving reduced collector to emitter resistance.

Resistor R6 effectively converts TR1 from current to voltage operation, and also provides a boost in input resistance. There is a slight drawback in using an ordinary bipolar transistor as a voltage controlled resistor, which is simply that it does not provide pure resistance.

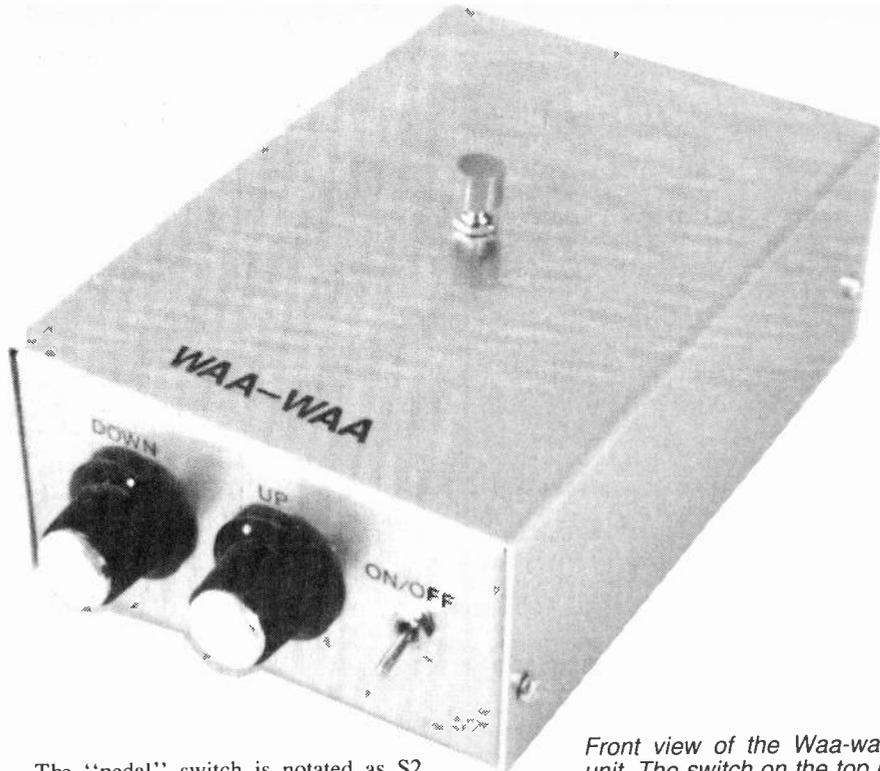Changes in the signal voltage result in variations in the effective resistance provided by TR1, which in turn produce distortion on the output signal. Hi-fi performance is not really essential in this application, but the distortion will be reasonably low provided the circuit is not fed with an excessive input level.



Front view of the Waa-waa unit. The switch on the top is the sweep control, S2.

The "pedal" switch is notated as S2, and it is biased to the position shown in Fig.1. Under standby conditions, no current flows into the base of TR1, and the resistance provided by TR1 is, therefore, so high that it has no significant effect on the circuit.

Operating S2 results in capacitor C6 starting to charge via potentiometer VR1 and resistor R7. As the charge potential on C6 rises TR1 receives an increasing base bias current. This results in its collector to emitter resistance steadily reducing, and the centre frequency of the filter being swept upwards.

This continues until the charge voltage on C6 reaches almost the full supply potential, but the filter frequency then remains constant until S2 is released. C6 then starts to discharge via R7 and VR2, causing the resistance provided by TR1 to increase and the centre frequency of the filter to decrease. This action continues until the charge on C6 drops below about 0.7 volts, at which point TR1 becomes cut off and once again has no significant effect on the circuit.

The required action is therefore obtained, with the filter frequency being swept upwards when S2 is operated, and swept back down again when it is released. VR1 controls the rate at which the filter frequency rises, and VR2 controls the rate at which the filter frequency falls. In both cases the rate of change is very rapid at minimum resistance, but takes several seconds for a full sweep at maximum resistance.

This type of voltage controlled bandpass filter is very simple, but it is slightly flawed in that the Q (quality) value of the filter rises as the operating frequency is increased. This results in a narrower response and higher maximum gain at high frequencies, and a broader response with lower maximum gain at low operating frequencies.


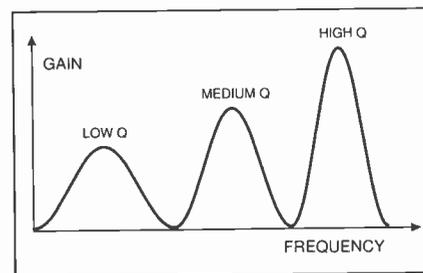


Fig.2. Filtered frequency response.

In Fig.2 is shown the general way in which the response changes as the filter frequency is altered. In practice, this does not seem to have a detrimental affect on results, and the effect obtained is perfectly acceptable. In fact, it is probably better to have things this way, as it avoids having a high level of boost on the fundamental signal, which could easily cause overloading.

Switch S1 enables the circuit to be bypassed when the waa-waa effect is not required.

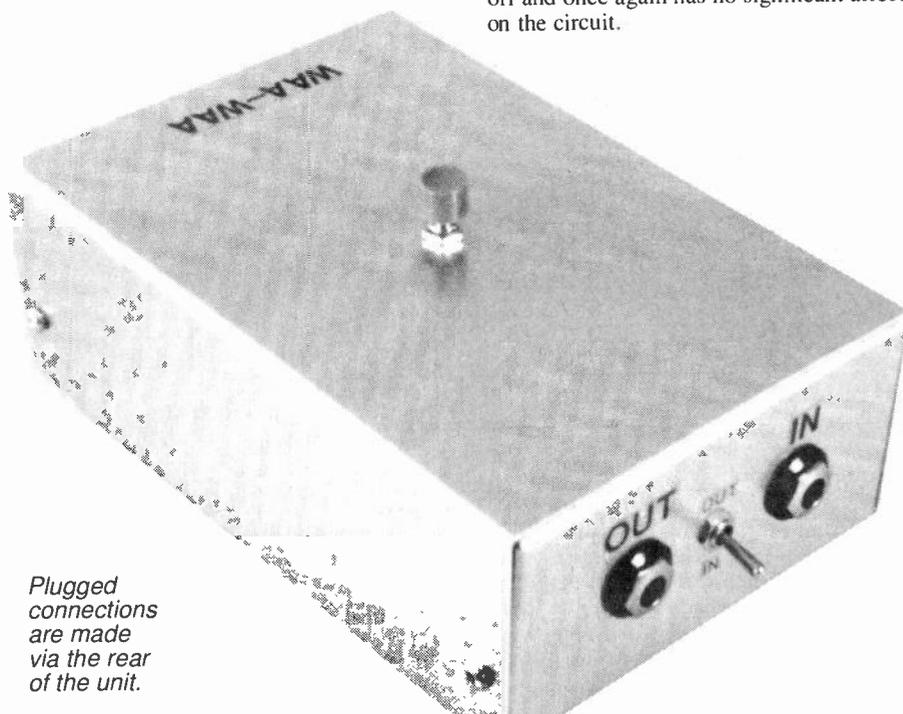The circuit is powered from a small 9V battery, and this should have a very long operating life as the current consumption of the circuit is typically just under two milliamps.



Plugged connections are made via the rear of the unit.

# COMPONENTS

## Resistors

|        |             |
|--------|-------------|
| R1, R2 | 47k (2 off) |
| R3     | 470k        |
| R4     | 100Ω        |
| R5     | 10k         |
| R6     | 680k        |
| R7     | 2k2         |

See  
**SHOP  
TALK**  
Page

All 0.25W 5% carbon film

## Potentiometers

|          |                                 |
|----------|---------------------------------|
| VR1, VR2 | 100k rotary carbon lin. (2 off) |
|----------|---------------------------------|

## Capacitors

|        |                               |
|--------|-------------------------------|
| C1, C4 | 10μ radial elect. 25V (2 off) |
| C2     | 1μ radial elect. 50V          |
| C3     | 4n7 mylar                     |
| C5     | 10n mylar                     |
| C6     | 47μ radial elect. 16V         |

## Semiconductors

|     |                      |
|-----|----------------------|
| TR1 | BC550 npn transistor |
| IC1 | LF351N bifet op.amp  |

## Miscellaneous

|          |  |
|----------|--|
| S1       | s.p.d.t. min. toggle switch (see text) |
| S2       | s.p.d.t. pushbutton switch (see text)  |
| S3       | s.p.s.t. min. toggle switch            |
| SK1, SK2 | standard mono jack socket (2 off)      |
| B1       | 9V battery (PP3 size)                  |

Printed circuit board, available from the *EPE PCB Service*, code 932; metal case (see text); control knob (2 off); battery connector; 8-pin d.i.l. socket; wire; solder; nuts and bolts, etc.

**Approx Cost**  
**Guidance Only** **£20**  
excluding batteries

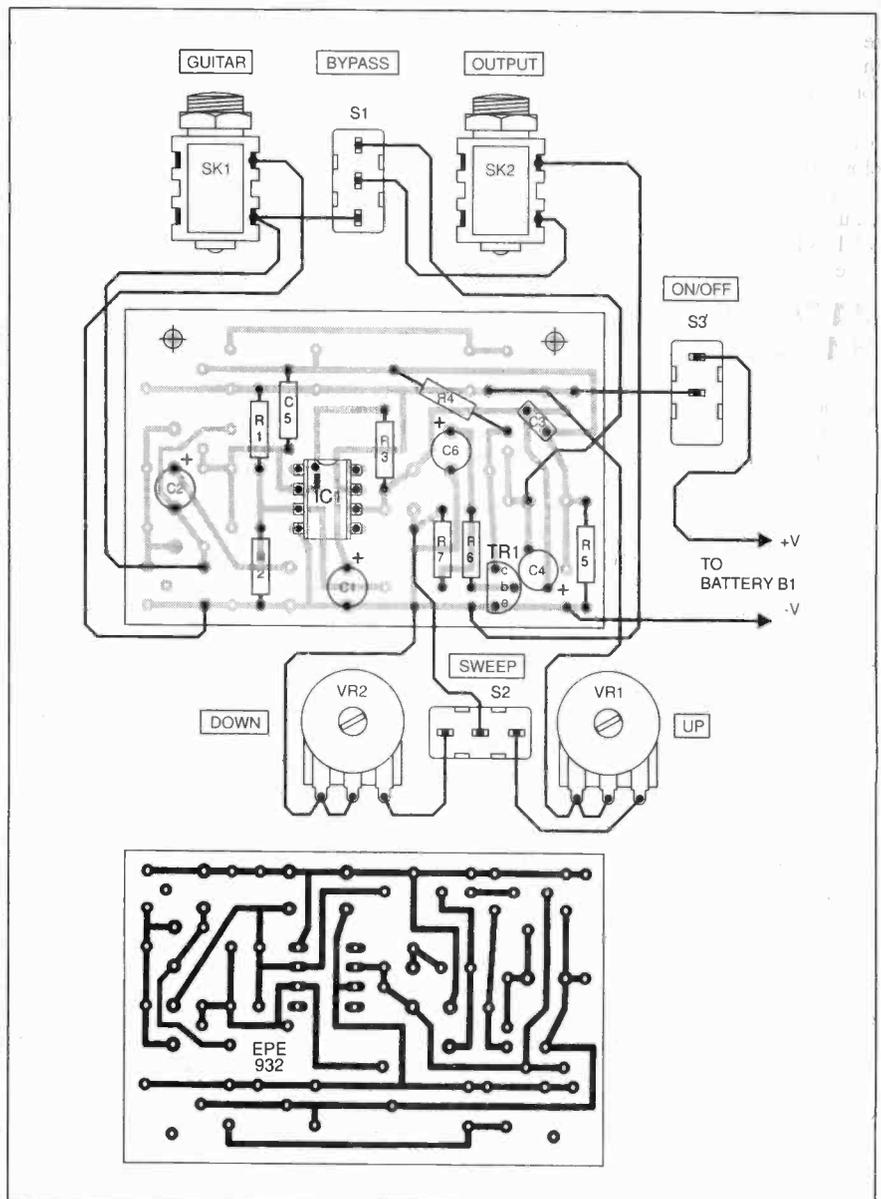


Fig.3. Printed circuit board component layout and full size underside copper foil track master pattern for the Waa-Waa Effects Pedal.

## CONSTRUCTION


The Waa-Waa Effects Pedal is built using the *EPE* multi-project printed circuit board. This board is available from the *EPE PCB Service*, code 932.

Construction of this board is mainly straightforward, but the usual warning has to be given. This is not a custom printed circuit board in the conventional sense, and many of the holes in the board are left unused. Consequently, it is relatively easy to get a component fitted in the wrong place and extra care, therefore, has to be exercised when fitting the components.

The board's component overlay, master track pattern and hard wiring details are shown in Fig.3.

IC1 is not a static sensitive device, but it is a good idea to use a holder for any d.i.l. integrated circuit. Be careful to fit IC1 and the electrolytic capacitors with the correct orientation. From the electrical point of view, C3 and C5 can be any form of plastic foil capacitor, but mylar capacitors are the easiest type to fit into this layout.

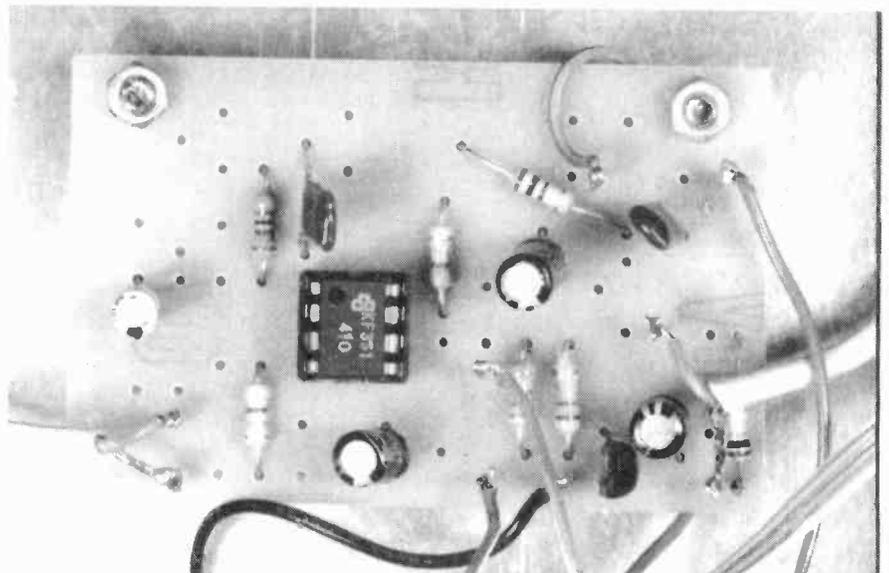Fit single-sided solder pins to the board at the points where connections will be made to the controls and sockets. "Tin" the tops of the pins with plenty of solder, but do not make any connections to them at this stage.



As this project will be controlled by foot, it is clearly essential for it to be housed in a tough case that will not crush or crack easily. It is also a good idea to use a metal case as this will provide the circuit with good screening from mains "hum" and other electrical noise.

A diecast aluminium box is ideal, but might prove to be rather expensive. A case of folded aluminium construction is just about strong enough, and represents a good low-cost alternative. It is possible to fit everything into quite a small case, but the use of a medium size box is

recommended as this will be more stable in use. It also provides more panel space for the controls and sockets.

The exact layout used is not critical, but it is advisable to have switch S1 mounted close to the input and output sockets. On the prototype, S1 and the sockets are mounted on one end panel, with controls VR1, VR2 and S3 fitted on the other end panel.

## JACKS AND SWITCHES


In Fig.3, the input and output sockets are shown as insulated jacks, which are the type favoured by many guitarists. These are often fitted with switch contacts, and then have two extra tags which are left unused in this application. Open style jack sockets can of course be used if preferred.

Switch S2 is a pushbutton type that must be mounted on the top panel of the case so that it can be operated by foot. It has single-pole changeover contacts, and it must be of the non-locking variety. Ideally, S2 would be a heavy duty switch, but a suitable component seems to be unobtainable. An ordinary type should be adequate provided it is of good quality.

Switch S1 could also be a pushbutton type mounted on the top panel of the case so that it can be operated by foot. This enables the effect to be totally eliminated while playing the guitar. Totally switching out the effect is not essential though, as the unit has little effect if the filter is left at its minimum frequency and is not swept.

The printed circuit board is mounted on the base panel of the case using either plastic stand-offs or metric M3 bolts. If you use mounting bolts it is essential to include spacers about 6mm or more in length to hold the connections on the underside of the circuit board well clear of the metal case.

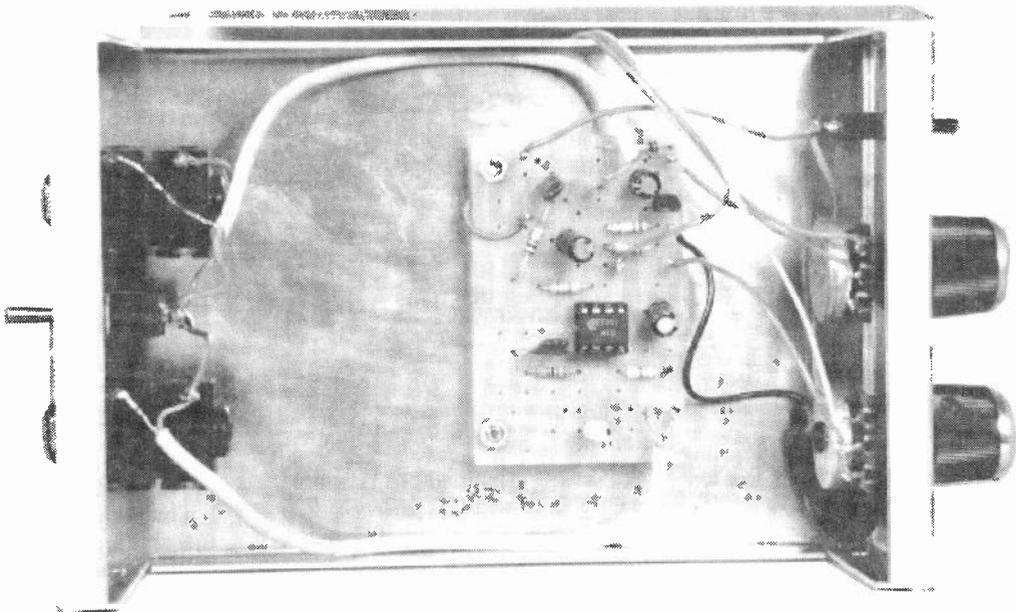It is not essential to use screened leads for any of the connections, but try to keep



the wiring reasonably short and direct. The wires to S2 must be quite long as this switch is mounted on the removable lid of the case, but long wires here should not compromise performance.

## TESTING AND USE

Standard screened jack leads are used to connect the guitar to SK1, and SK2 to the input of the guitar amplifier. With the unit switched on, the signal should be coupled straight through to the amplifier with S1 set to the bypass position.

With S1 switched to the other position, the waa-waa effect should be obtained when S2 is operated. If the filter is swept downwards when S2 is pressed, and upwards when it is released, reverse the connections to the outer two tags of S2.

It is worth experimenting with the settings of VR1 and VR2 to obtain the control characteristic that you like best. Remember that you do not have to use the

same settings all the time and that, if necessary, different settings can be used for each piece that you play.

If you intend to use many different settings it might be worthwhile using control knobs having "0" to "9" calibrated skirts. These make it easy to note down each pair of settings, and quickly dial them up when they are required again.

As pointed out previously, the circuit will only provide low distortion if it is used with a fairly low input level. When using the unit with a high output guitar pick-up it will almost certainly be necessary to back-off the volume control on the guitar, and advance the volume control on the guitar amplifier. Otherwise quite severe distortion may occur at some filter frequencies.

With low and medium output pick-ups there should be no problems with distortion, even if the guitar is set for maximum volume. □

**NEXT MONTH - Special Supplement ★ EPE PIC TUTORIAL ★**

**DON'T MISS OUT - ORDER YOUR COPY NOW!**

**EVERYDAY**  
**PRACTICAL**

**ELECTRONICS**

**SUBSCRIPTION ORDER FORM**

Annual subscription rates:

UK £26.00.

Overseas £32 standard air service,  
£49.50 express airmail

To:

Everyday Practical Electronics,  
Allen House, East Borough  
Wimborne  
Dorset BH21 1PF  
Tel: 01202 881749  
Fax: 01202 841692



**VISA**

(We cannot reply to overseas orders or queries by Fax)

E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk)  
Web site: <http://www.epemag.wimborne.co.uk>

Name .....

Address .....

.....

.....

.....

.....

..... Post code .....

I enclose payment of £ ..... (cheque/PO in £ sterling only,  
payable to Everyday Practical Electronics).

Alternatively send Mastercard or Visa number and card expiry date.

Please charge my Visa/Mastercard

Card  
Number

Signature .....

Card Ex. Date .....

Please supply name and address of cardholder if different from the  
subscription address shown above. Subscriptions can only start with the  
next available issue. For back numbers see the Back Issues page.

## An Introduction to DIGITAL ELECTRONICS



Ian Bell, Rob Miles, Dr. Tony Wilkinson, Alan Winstanley

**T**EACH-IN is a ten part series designed to support candidates following City and Guilds (C&G) 726 Information Technology, with reference to the following specific syllabuses: \*7261/301 Introductory Digital Electronics, \*726/321 Elementary Digital Electronics, \*726/341 Intermediate Digital Electronics.

Even if you are not undertaking the City and Guilds syllabus, there is much to be learned from following *Teach-In*, whether you are a GCSE or "A" level student, apprentice technician or you simply want to discover the exciting world of Digital Electronics.

### Lab Work

Throughout *Teach-In*, attempts are made to involve the student with practical "Lab Work" experiments and demonstrations, and complex mathematics and physics will be avoided unless really necessary – and even then, plenty of help is to hand! We make a point of identifying practical components in special sections of *Teach-In*, so that you will learn to recognise parts, even if you don't necessarily use them yourself just yet. We also take a light-hearted view from time to time, because electronics really is *fun* to learn.

### Part Four: BINARY NUMBERS AND DIGITAL LOGIC SYSTEMS. GATES AND PROCESSING CIRCUITS. LOGIC IN THE REAL WORLD.

**M**ANY people are aware that computers "work with 1s and 0s", but what does this mean, and why is it done this way?

The key points to understand here are the concepts of *binary* numbers, *Boolean logic* and the reasons for implementing computers and other circuits using these concepts. We introduce these ideas in this part of *Teach-In* and return to them at various points in the course.

#### Binary Numbers

Human beings, when working with numbers, usually use 0, 1, 2, 3, 4, 5, 6, 7, 8 and 9 – that is, ten possible values each with their own "symbol". If we want to count larger numbers we use a "tens" column (so 23 is 2 10s and 3 units), and so on.

Mathematically, the system we are all so familiar with is called *decimal*, or "base-10". We probably use this base because we have a total of ten fingers and thumbs! A clever octopus, if one could count, would probably count up to eight in *octal*, or base-8, starting with 0 and carrying over to the next column (8s) when it reached 7.

However, numbers can be manipulated in any base, from 2 upwards. Base-2 (or *binary*) is used by digital computers (and other digital circuits) – only two symbols are used: 0 and 1. If we want to count above 1 in binary we need a 2s column (so 11 in binary is 1 two plus 1, or 3 in decimal).

Just as the digits in a decimal number represent powers of 10 (10 multiplied by itself a certain number of times: 10s, 100s (10×10), 1000s (10×10×10), and so on, the digits in a

binary number represent powers of 2: 2s, 4s (2×2), 8s (2×2×2), and so on. Thus the binary number 1001011 is 75 in decimal. See Fig. 4.1.

|                 |    |    |   |   |   |   |
|-----------------|----|----|---|---|---|---|
| 64              | 32 | 16 | 8 | 4 | 2 | 1 |
| 1               | 0  | 0  | 1 | 0 | 1 | 1 |
| 64 + 8 + 2 + 1  |    |    |   |   |   |   |
| = 75 IN DECIMAL |    |    |   |   |   |   |

Fig.4.1. The binary 1001011 is 75 in decimal.

OK, so we can represent numbers using 1s and 0s, but what about other types of data? The answer is relatively straightforward, all we have to do is *code* the data using numbers.

If you are a computer user, the most obvious example is text, where for example, the well-known ASCII (*American Standard Code for Information Interchange*) code uses binary numbers from 0 to 127 (decimal) (0000000 to 1111111 binary) to represent upper and lower case letter, numerals, punctuation symbols and other information relating to typing text into a computer. In general, coding data into 1s and 0s in an efficient and useful way may be difficult, but the basic principle remains.

So far we have been concerned with *data* – numbers, text

etc., but digital circuits and computers also deal with decision making and *control* of actions or operations. We also do this in 1s and 0s which are implemented in exactly the same as the data 1s and 0s – only their use and interpretation is different.

#### Boolean Logic

The 1s and 0s being used to form binary numbers also naturally represent basic two-way decision-making concepts such as *yes/no*, *true/false*, *on/off*, and *high/low*. The mathematical study of the processes of inference and reasoning is referred to as *logic* and a significant branch of this field concerns the processing of true/false values.

To get a better feel for this, imagine that I am going to go for a walk. If it rains, then I will get wet unless I use an umbrella. We could represent this using symbols for the state of being wet, rain, and not using an umbrella, so that the statement "if it is raining and I am not using an umbrella, I will get wet" would be written as shown in Fig. 4.2.

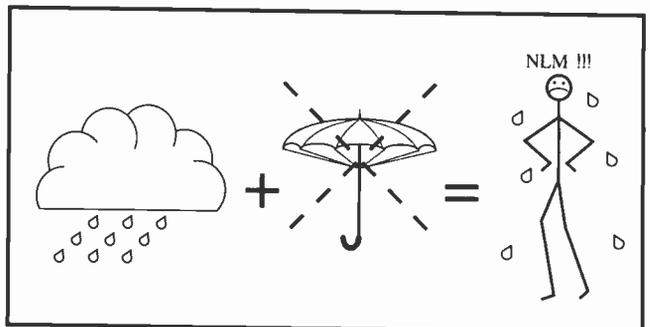


Fig.4.2. Symbolic representation of a simple logic statement – if it is raining, and I don't have an umbrella, I will get wet!

These symbols are fun and easy to understand, but they are not practical for serious use as not everyone is a good artist. Furthermore, some concepts we may wish to use are abstract and don't have an obvious picture.

So unfortunately we have to use letters instead of pictures. For example, I can use **W** (for "wet") which is *true* if I am wet and *false* if I am not wet, **U** (for "umbrella") which is *true* if I use my umbrella and *false* if I don't, and **R** (for "raining") which is *true* if it is raining and *false* if it is not raining.

Then I could write the statement "I will get wet if it is raining **and** I am **not** using an umbrella" using these symbols as:

$$W = R \text{ AND NOT } U$$

Note that *W*, *R* and *U* are referred to as *variables* because they can take on more than one possible value (in this case either *true* or *false*).

Now to extend the example, if I am wet (i.e. if  $W = \text{true}$ ) I will want to change my clothes. However, I will also want to change my clothes if they are dirty.

Thus, I can define two more variables: **C** for "changes clothes?", true or false (yes or no), and **D** to represent whether or not my clothes are dirty. Thus I can write the statement "I will change my clothes if they are dirty or wet" as:

$$C = D \text{ OR } W$$

Just as we represent addition (or PLUS) with the symbol  $+$ , we can use symbols to represent the logic operations of AND, OR and NOT.

In "Boolean Algebra", AND and OR are usually written as  $\bullet$  and  $+$  respectively (note the  $+$  symbol means OR, not AND, in logic), and NOT (inversion) is represented by a line above the variable: so "I am not wet" which is NOT *W*, can be written  $\bar{W}$ . Thus we can re-write our statements:

$$W = R \bullet \bar{U}$$

(wet = raining AND no umbrella)

$$C = D + W$$

(change clothes = dirty OR wet).

I can now combine these to give a single equation which tells me if I have to change my clothes:

$$C = R \bullet \bar{U} + D$$

(change clothes = raining AND no umbrella OR dirty).

Note that *R*, *U* and *D* can each be one of two possible values (true or false) so that there are actually a total of eight different possible combinations of all three. These can easily be listed as shown in Table 4.1.

#### --- THE AUTHORS ---

*Teach-In* has been co-written for *Everyday Practical Electronics* by Ian Bell, Rob Miles and Dr. Tony Wilkinson who are lecturers in the Department of Electronic Engineering at the University of Hull, England. Regular readers will know Alan Winstanley, of course, as the author of several columns in *EPE*. Alan has co-ordinated the series.

**Table 4.1: Possible True or False Combinations**

| It is raining<br><b>R</b> | I am using an umbrella<br><b>U</b> | My clothes are dirty<br><b>D</b> | I need to change my clothes<br><b>C</b> |
|---------------------------|------------------------------------|----------------------------------|---|
| false                     | false                              | false                            | false                                   |
| false                     | false                              | true                             | true                                    |
| false                     | true                               | false                            | false                                   |
| false                     | true                               | true                             | true                                    |
| true                      | false                              | false                            | true                                    |
| true                      | false                              | true                             | true                                    |
| true                      | true                               | false                            | false                                   |
| true                      | true                               | true                             | true                                    |

This is known as a *Truth Table*. Now if I represent *true* with a "1" and *false* with a "0" I can write the true table like this:

**Table 4.2. True Truth Table**

| R | U | D | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Notice that the *R*, *U* and *D* columns (4s, 2s and 1s respectively) of the truth table go through the binary numbers from 0 to decimal 7 in sequence. This illustrates the close link between binary numbers and logic. I may not want to build a circuit, or program a computer, to decide if I am to change my clothes but similar concepts can be used in more appropriate situations, for example: "switch valve 3 on if level detector is on or if temperature is high and valve 2 is off".

You may be thinking that the "change clothes" logic is not fool-proof as, for example, I may not need a change of clothes if the rain is very light or if I am wearing waterproofs. This is of course true, but we have to limit our example to something manageable.

There is also a more serious issue here which is fundamental to engineering design, that of understanding the problem, "modelling" (or describing) it, and specifying what we want to do to solve it. The logic will only do what we design it to do.

In our example we have "modelled" the rain as simply *on* or *off*, but we could be more detailed about the way we model it by adding a light/heavy variable (ignored if "rain" is false). Then we have an issue of specification: do we require a change of clothes for all rain, or just for heavy rain?

We could design either circuit. A design may go wrong (i.e. a product lets us down) if the problem was not properly understood and described, or if the specification had some flaw in it, or if the design did not meet the specification.

All these points must be kept in mind

when designing circuits and software. Companies carrying out designs often go to great lengths to ensure that all these steps are carried out correctly, but we can all probably think of examples where they didn't quite manage it!

The branch of mathematics concerning logic based on true/false values is called **Boolean Algebra** after its inventor, English Mathematician George Boole (1815-1864). It is of fundamental importance to digital logic circuits, computers and programming and we will return to it in more detail later.

### Why Binary Circuits?

As to why binary is used in computers, it is simply that this is the easiest and most cost effective system to implement using electronic technology. Furthermore, the special mathematical properties of Boolean algebra provide a powerful means of expressing and solving decision-making problems.

Both binary numbers and Boolean logic are based on 1s and 0s, i.e. there are two possibilities for each symbol, bit of information or digit within a number. This is easy to handle in circuitry because switches can be either *on* or *off* and a voltage can easily be switched between a fixed value (e.g. +5V) and ground (0V) - see Part 3 of *Teach-In*, in which we described MOS-FET transistors and inverters.

What would happen if we tried a different number base, say base-3? This has three values per digit i.e. 0, 1 and 2. We can no longer directly relate this to a switch being on or off because a switch does not have a natural third state.

We could, of course, use a set of fixed voltages to represent the numbers, for example 0V, +2.5V, and +5V for 0, 1 and 2, but it turns out that if we do this, then the circuits to handle logic and numbers are far harder to design and have poor performance in terms of power consumption, speed and susceptibility to electrical noise.

A possible advantage of base-3 is that we could represent "maybe" as well as "yes" and "no", and in fact such systems are used in specialist circumstances ("fuzzy logic" plus Artificial Intelligence), but in most cases the practical disadvantages of the circuits used outweigh the conceptual advantages. We can always use another digit in binary to indicate a "maybe" condition if we require this.

## Circuits which "Do Logic"

Using transistors, we can build small circuits which perform the basic logic operations of AND, OR, and NOT. These circuits are called **gates** and their logic gate symbols together with their Truth Tables are shown in Fig. 4.3.

The NOT gate (inverter) was actually introduced in the previous part of *Teach-In*. We can connect different gates together to form more complex functions, using *Combinational Logic*.

For example, if we have three inputs indicating if we have dirty clothes (D), if it is raining (R), and if we are using an umbrella (U) we can build a logic circuit which indicates if we need to change clothes (C), see Fig. 4.4.

Note that the "internal" wires of the circuit can also be labelled, in this case with  $\bar{U}$  (no umbrella) and W (wet). Here the internal wires have some easily definable meaning to us, but this may not be the case in all logic circuits.

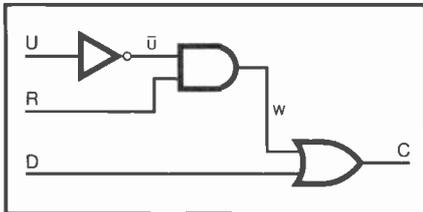


Fig.4.4. Circuit to decide if we should change our clothes using information on Dirt, Rainfall and Umbrella use.

## Circuits which Process Data

We've seen the beginnings of how we can build circuits to make decisions, but how do we actually process data? For example how do we add two numbers together? Here's a simple "addition table" in decimal. (Adding a number from the top row to one in the side row gives the corresponding result.)

Table 4.3: Decimal Addition

|   |   |   |
|---|---|---|
| + | 0 | 1 |
| 0 | 0 | 1 |
| 1 | 1 | 2 |

Now consider the same "addition table", this time written in binary.

Table 4.4: Binary Addition

|   |    |    |
|---|----|----|
| + | 0  | 1  |
| 0 | 00 | 01 |
| 1 | 01 | 10 |

Since we are adding together two one-digit binary numbers, we have a total of four possibilities. We can tabulate these as follows, one per line, rather than in the conventional "times table" format.

We have called the two numbers being added  $A_0$  and  $B_0$ , where the 0 subscript indicates that they represent units (two to the power zero, or  $2^0$ ). The result (the sum) requires two binary digits to represent it, because its maximum value is 2 (10 in binary), so we've labelled these  $S_1$  for the twos ( $2^1$ ) and  $S_0$  for the units.

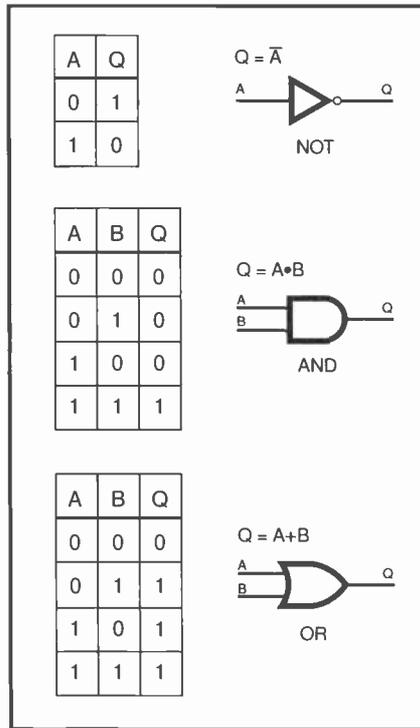


Fig.4.3. Truth Tables and Boolean symbols for basic logic gates.

| Numbers being added |       | Sum   |       |
|---------------------|-------|-------|-------|
| $A_0$               | $B_0$ | $S_1$ | $S_0$ |
| 0                   | 0     | 0     | 0     |
| 0                   | 1     | 0     | 1     |
| 1                   | 0     | 0     | 1     |
| 1                   | 1     | 1     | 0     |

This looks like a Truth Table: in fact it is two Truth Tables - one for  $S_0$  and one for  $S_1$ , which we can write separately as follows

| $A_0$ | $B_0$ | $S_1$ | $A_0$ | $B_0$ | $S_0$ |
|-------|-------|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     | 0     | 0     |
| 0     | 1     | 0     | 0     | 1     | 1     |
| 1     | 0     | 0     | 1     | 0     | 1     |
| 1     | 1     | 1     | 1     | 1     | 0     |

You should be able to recognise  $A_0$ ,  $B_0$  and  $S_1$  as being the AND truth table, so we can simply use a single AND gate to get  $S_1$ . The logic function for  $S_0$  is a little more difficult. We can see that  $S_0$  is 1 (true) if  $A_0$  is 0 AND  $B_0$  is 1, OR if  $A_0$  is 1 AND  $B_0$  is 0. In Boolean algebra we write this as:

$$S_0 = \bar{A}_0 \bullet B_0 + A_0 \bullet \bar{B}_0$$

It may help to recall that the overbar means "inversion". Hence, for example, if  $A_0$  is 0 then  $\bar{A}_0$  is 1. The table above can be used in comparison with the Truth Tables for AND and OR logic gates (earlier), to prove that the Boolean statement is correct.

Hopefully you can see from this that we need two AND gates, two NOT gates and one OR gate. You will see shortly that this can be simplified drastically by replacing them with another type of gate, the Exclusive-OR, or XOR gate.

Another word for a binary digit is bit. The full circuit of the "adder" is

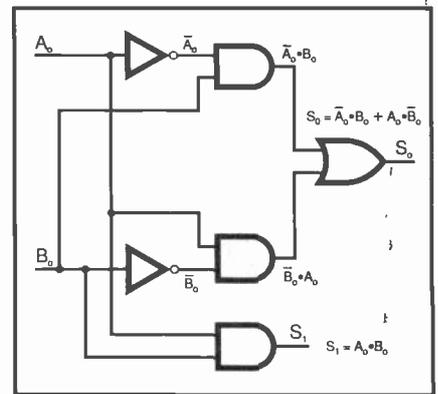


Fig.4.5. Circuit to add two 1-bit binary numbers together to give a 2-bit binary result.

given in Fig. 4.5, which is a circuit that adds two "one-bit" binary numbers together (0 or 1), to give a "2-bit" binary result (from 00 to 11). Thus we see that we can use basic logic gates to build circuits which do arithmetic as well as make "logical" decisions - as with the "change of clothes" circuit. We will return to both types of function later in the course.

## More Gates

In addition to the AND, OR and NOT functions, other basic logic gates

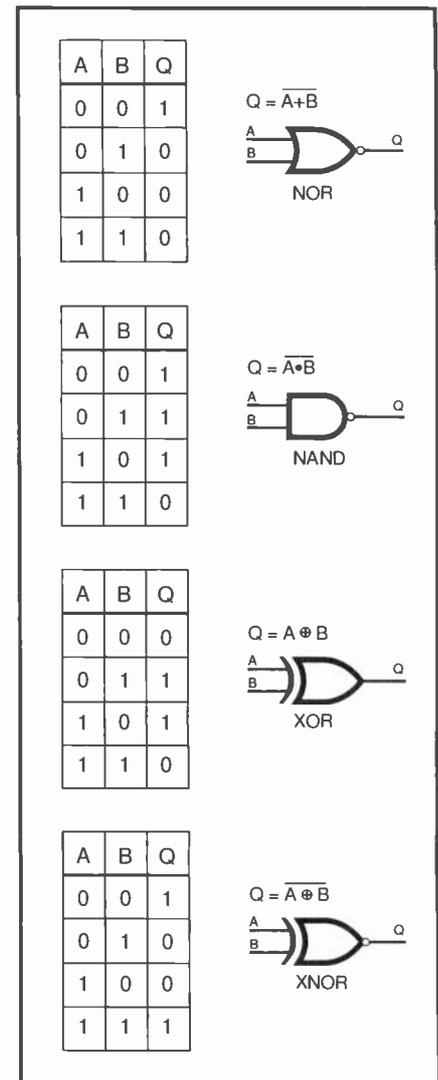


Fig.4.6. Truth Tables and logic gate symbols for NOR, NAND, XOR and XNOR.

# Check Out: Integrated Circuits

A "discrete" component is an individual part, e.g. a single MOSFET transistor. Technology being what it is (i.e., unstoppable), mankind has managed to miniaturise millions of MOSFETs on a sliver of silicon, to form an *integrated circuit* (i.c. for short). Whilst the first silicon chips contained one or two dozen miniaturised transistors, an Intel Pentium microprocessor (for example) contains millions, making the MOSFET the most common micro-electronic component in the world!

Using photographic and chemical methods, dozens of chips are simultaneously formed onto a wafer (a thin slice of single crystal silicon). After testing, individual chips or dies are separated from the wafer by sawing it up.

Each correctly functioning die is then glued into a package, and miniature wires (about 25 micrometers thick) are bonded between small metal "bond pads" (about 100 micrometers square) on the chip's surface and the pads on a "lead frame", thus connecting the die to the larger legs or pins on the outside world. The package is sealed to protect everything, and the chip is re-tested.


Many integrated circuits are comparatively large in size, but only because of the need for human beings to physically handle and connect to the package. The die embedded within the package is far smaller than the overall size suggests. Smaller packages suitable for automated handling systems are also available.

## Get the Number


The most common type we use is the *dual-in-line* (d.i.l.) package, which has anything from 8 pins to 48 pins, aligned in two rows of 4 to 24 pins. The 4000 CMOS range we test in **Lab Work 4** uses a variety of chips in 14-pin and 16-pin dual-in-line packs. Pins are spaced 0.1 inch with rows 0.3 inch apart.

In order to identify the pin numbers, a notch will usually be found at one end of a d.i.l. chip, and/or a dimple may be used to indicate pin 1. The numbers then continue in an anti-clockwise direction – the diagram depicts 8-pin and 16-pin types.

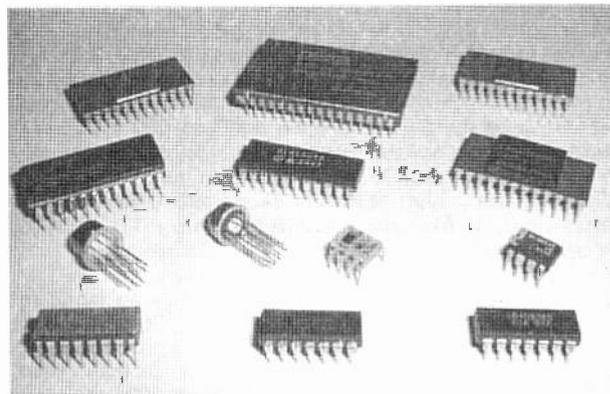Dual-in-line chips can be soldered directly to a printed circuit board (p.c.b.), but it can then be a little tricky to desolder for replacement. It is wise therefore – although adding to the cost – to use dual-in-line i.c. sockets, so that you can easily "swap out" a chip at a later date.



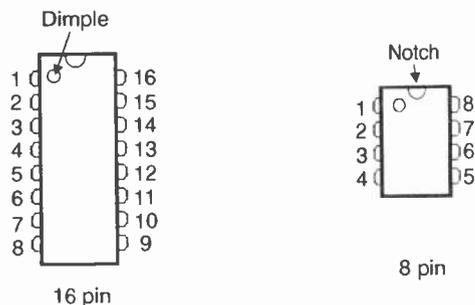Collection of multi-pin integrated circuit (i.c.) devices.



Care is needed to ensure that all pins align properly and that none are bent out of place. Special extractor tools are used by professionals.

Surface mount technology (SMT) is of enormous interest to manufacturing industry. These devices (SMDs) use much smaller package sizes (for i.c.s. as well as certain discrete parts) which requires highly specialist equipment to install them on top of circuit boards.

are available. Two commonly used gates are NAND and NOR, which are complements (opposites) of the AND and OR functions (i.e. NOT-AND and NOT-OR). These are achieved by *inverting* the gate outputs, hence the small circle on the output of the logic symbol in Fig. 4.6..

The function we met in the previous section for  $S_0$  is also very commonly used. As well as being one-bit addition (without "carry") it can be thought of as an "A and B but not both" function and is therefore called exclusive-OR (abbreviated XOR or EXOR). The complement of the XOR is called the Exclusive-NOR, or XNOR.

Truth Tables for these gates are given in Fig. 4.6. Note the Boolean logic XOR symbol.

## Logic in the Real World

Are 1 and 0 sufficient to describe what happens in real logic circuits? The answer of course depends on what you are trying to do and how accurately you need to model what is happening. There are some important issues to address when considering real logic circuits, including sensitivity to noise and speed of operation.

The first question is how we actually represent 1 and 0 in a real-life

electronic circuit. We have already hinted that we could use two voltages, say +5V for logic 1 and 0V for logic 0, but this is arbitrary. It could be -2V for 0 and +2V for 1, or 0V for 1 and +5V for 0.

In general, if the more positive voltage is used for 1 we refer to this a *positive logic* and if the more negative voltage is used for 1 we have *negative logic*. In this *Teach-In* course we always use positive logic, as do the most common off-the-shelf logic devices. We can also build logic circuits using *currents* to represent 1s and 0s, but again that is beyond the scope of this course.

If we select 5V for logic 1 and 0V for logic 0 then what does 4.9V mean? In real circuits we have to define a range of voltages which represent a valid logic level, say 0V to 2V for 0 and 3V to 5V for 1. We need to do this because we cannot build circuits which handle precisely fixed voltages under varying conditions of loading, temperature and factors affecting manufacture, particularly as they must be as small and as fast as possible.

In general, logic gates will accept a given range of inputs as 1 or 0 and are guaranteed to produce a smaller range of possible output voltages,

closer to the ideal voltage (say 4V to 5V for 1 and 0V to 1V for 0 in our example). This means that each gate tends to restore the voltage towards the ideal for that logic level.

The difference between the worst case output level and worst acceptable input level for a given logic value is called the *noise margin*. This figure indicates how well the gate can cope with disturbances (such as external electrical interference) without losing the correct value of the data.

If the voltage is *in between* the defined logic levels for any reason (except for the brief time when switching between levels) then we have an undefined logic value and the circuit may behave unpredictably. The undefined condition is sometimes represented by the symbol X (for example, by logic simulators), meaning "don't know" and indicates that there is something wrong with the circuit or the design.

The symbol X is also used in the design and specification of logic functions to mean "don't care", indicating that a value may legitimately be either 1 or 0 under certain conditions without affecting the outcome. Whether X means "don't know" or "don't care" should be obvious from the context in which it is used.

## Logic Families

There are a bewildering number of "logic families", i.e. types of circuitry and technology for implementing digital systems. The first commercially available logic family was resistor-transistor logic (RTL), introduced in 1962. This was followed by diode-transistor logic (DTL) and then the transistor-transistor logic (TTL) of the classic 7400 series. All these are based on the bipolar junction transistor (BJT), with TTL using a "multiple emitter" transistor at logic gate inputs.

New versions of TTL have continued to be introduced which provide higher operating speed and/or lower power dissipation, for example Advanced Schottky TTL (ASTTL). Another type of bipolar logic is Emitter-Coupled Logic (ECL) which provides a very high speed of operation.

MOS logic circuits on the other hand may be fabricated using *n*-type or *p*-type transistors alone (NMOS and PMOS), or both together (CMOS) as described in the previous part of *Teach-In*. NMOS provides higher performance than PMOS, but the advantages of CMOS mean that most MOS logic is of this complementary type.

### Classic 4000

The classic CMOS logic family is the 4000 series, but just to confuse you, CMOS versions of the 7400 series are also available (74HC00 and others)! CMOS 4000 series are static sensitive, can operate on 3V to 15V supplies but may behave unpredictably if inputs are left unconnected, as we demonstrate in **Lab Work 4**. The original 7400 and other TTL series must have a supply of 5V ( $\pm 0.5V$ ), are not static sensitive and their inputs behave as logic 1 when left floating.

The 4000 series provides some "multiplexers" which can be used for switching and selecting analogue signals, but there are no analogue functions in the standard 7400 series. Other series have different properties, for example 74LVCM00 is CMOS series operating on a 3-3V supply. Not all functions are available in all families though.

Although there are differences in the behaviour and types of function available in the CMOS 4000 and TTL 7400 series, MOS and bipolar transistors can be used together to exploit the advantages of both, in Bi-CMOS, the 74ABTC series for instance.

### These are just some of the 74 series variations . . .

|          |   |
|----------|---|
| 7400     | Standard bipolar TTL, the originals!                              |
| 74LS00   | Early TTL "low-power Schottky" improvement over basic 7400 series |
| 74ALS00  | Higher speed, lower power TTL than LS                             |
| 74F00    | High speed "Fast" TTL improvement on LS                           |
| 74HCT    | Direct CMOS equivalents to LSTTL. 4.5V to 5.5V supply             |
| 74AC00   | CMOS, with CMOS logic levels                                      |
| 74ACT00  | CMOS, with TTL logic levels                                       |
| 74FCT00  | CMOS. Lower power than 74F, by virtue of CMOS technology          |
| 74HC00   | Basic high speed CMOS, similar to TTL. 2V to 6V supply            |
| 74LV00   | CMOS 3-3V supply  |
| 74LVCM00 | CMOS 3-3V supply, faster, improved output over LV.                |

There are digital circuits which are able to disconnect and isolate their outputs (such circuits are used to control the flow of data around computers, for example between memory chips and the CPU). We will say more about this type of circuit later in the course.

The binary numbers 1 and 0 do not cover the situation where there is no value due to the output being physically disconnected, and X is not appropriate because the disconnection is a deliberate setting of a known condition.

We use the symbol Z to represent this state (Z for "high impedance", as Z is the symbol for impedance). Thus in real life, the specification of digital circuits (e.g. using Truth Tables) may use the symbols 0, 1, X and Z. Some-

times H and L (high and low) are used instead of 1 and 0.

### High Speed Switching

Another extremely important property of digital circuits is the *speed* with which they react to changes at their inputs. Boolean algebra and Truth Tables define what the output of a circuit will be with certain inputs, but do not convey the fact that it will take a finite time for this to happen.

If we look at the adder circuit we described earlier (Fig.4.5.), it should not be too surprising to learn that the  $S_0$  output will react faster than the  $S_1$  output because the signal has to go through three gates to reach  $S_0$ , but only one gate to reach  $S_1$ . Therefore, if the number at the input changes, the output may be "wrong" after  $S_1$  has reacted, but before  $S_0$  has done so. This time will be very short, probably nanoseconds or shorter, but time enough for another logic circuit to react.

In true-life digital design we have to be careful to make sure that intermediate states, which occur as circuits switch, do not cause incorrect behaviour. The term *glitch* is used to describe unwanted transient logic values which occur as circuits switch.

The switching delay is not only important as a complex factor in logic design, but also for economic reasons as faster circuits can be priced higher, or will attract more customers. A good example of this is the increase in speed of personal computers.

There are two ways of getting faster circuits: one is to improve the basic fabrication technology, usually by making the transistors and gates smaller. The second is to use clever design techniques (e.g. "pipelined burst cache"). Both approaches can

be seen in the development of microprocessors in PCs: Intel 8086, 286, 386, 486 and Pentium.

### Power Game


So far we have not mentioned anything about where the power comes from to make logic circuits work. Boolean algebra and truth tables have nothing to say on the matter and logic circuit schematics using gate symbols leave out power connections because they would overcrowd the diagram.

Logic chips do have power pins (usually 0V - GND or  $V_{SS}$ ) and positive supply ( $V_{DD}$  or  $V_{CC}$ ) which you connect to an appropriate source. Check the pin-out drawings in **Lab Work 4**.

Power consumption is an important issue in modern digital design, for two reasons. First, because all digital activity consumes power then the smaller the transistors become, the more power is consumed per unit area so the hotter the chips get. This is why you need a heatsink and a fan on a Pentium microprocessor, but didn't need one for a 386.

Second, there is a big market for portable, battery powered electronics such as mobile phones and laptop computers. Customers of these products want the batteries to last a reasonable period, so the circuits have to be designed to use a minimal amount of power. Every time a gate switches state, some power is consumed which will not be replaced until you can next plug in the charger!

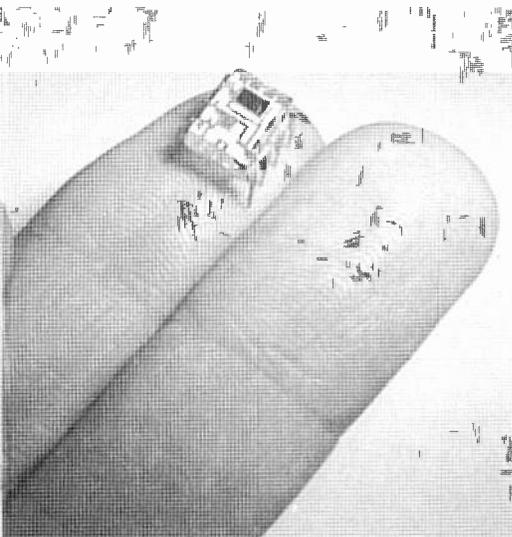
Now go to the **Lab Work** section, where you will actually construct the circuits introduced here, using CMOS logic on a solderless breadboard, in conjunction with your 5V Add-on Regulated Power Supply built previously.



This totally "transparent" light-to-frequency converter chip (TSL220) from Texas demonstrates just how small the "active" element (photodiode - black area) is in comparison to package size.
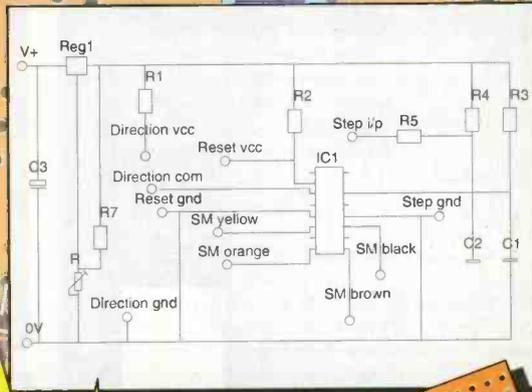
# StripboardMagic™

The innovative  
new computer-  
aided circuit  
layout program  
for  
stripboard



Don't  
solder on  
without it!

## Features:

- Fully-automatic physical circuit layout
- Stripboard or breadboard layout
- Assisted interactive layout options
- Simple drag-and-drop circuit editor
- Detailed construction diagram to guide the assembly stage
- Comprehensive, fully extensible component library
- Provision for off-board components
- Automatic generation of component order forms
- Printout function of all stages
- Full technical support

Windows  
95/NT  
PC

Only  
**£39.95**  
incl VAT\*

Tel/Fax:  
**+44 (0) 1635-521285**

**Ambyr**  
a spark of genius

Email:  
[info@ambyr.com](mailto:info@ambyr.com)  
<http://www.ambyr.com>


Ambyr Limited. Reg office 84-86 Park Lane, Thatcham, Berkshire, RG18 3PG.

\*Price does not include postage & packaging. Diagrams shown are for illustration purposes only.  
Ambyr & StripboardMagic are trademarks of Ambyr Ltd. Windows & Windows NT are registered trademarks of Microsoft Corporation.

# PROTEUS


## Schematic Capture

NEW Version IV

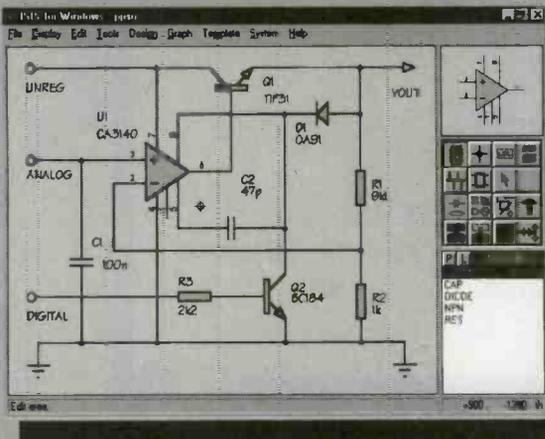

- Produces attractive schematics like you see in the magazines.
- Netlist, Parts List & ERC reports. ● Hierarchical Design. ● Full support for buses including bus pins. ● Extensive component/model libraries. ● Advanced Property Management. ● Seamless integration with simulation and PCB design.

## Simulation

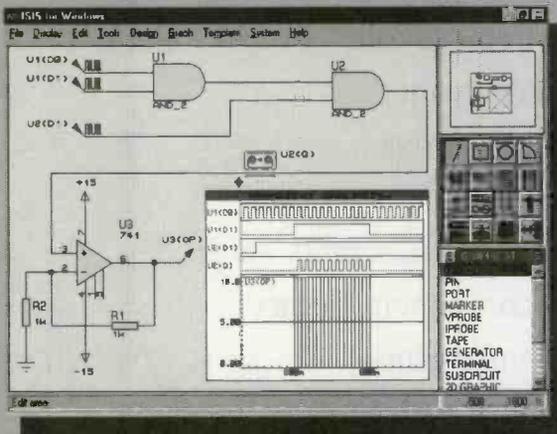

- Non-Linear & Linear Analogue Simulation. ● Event driven Digital Simulation with modelling language. ● Partitioned simulation of large designs with multiple analogue & digital sections. ● Graphs displayed directly on the schematic.

# The IV<sup>th</sup> Generation


## New Features

- Component Auto-Placer
- Pinswap/Gateswap Optimizer
- Background Regeneration of Power Planes
- Enhanced Autorouting with Tidy Pass
- Full Control of Schematic Appearance
- Extensive New Component Libraries

Available in 5 levels - prices from £295 to £1625 + VAT.  
Call now for further information & upgrade prices.

## PCB Design

NEW Version IV

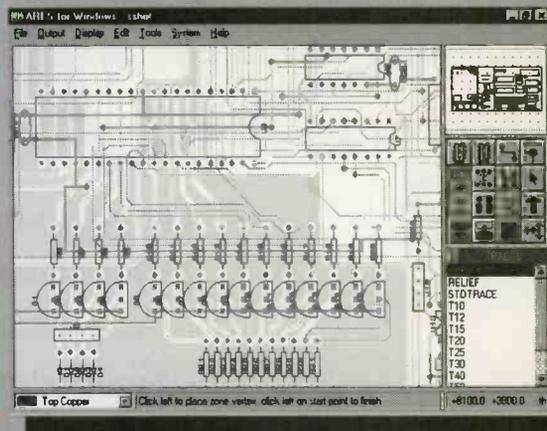

- Automatic Component Placement. ● Rip-Up & Retry Autorouter with tidy pass. ● Pinswap/Gateswap Optimizer & Backannotation. ● 32 bit high resolution database. ● Full DRC and Connectivity Checking. ● Shape based gridless power planes. ● Gerber and DXF Import capability.

**"PROTEUS**  
is particularly good

with its rip-up-and-retry **autorouter"**

EWV January 1997

labcenter  
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.  
Tel: 01753 753440. Fax: 01756 752857. EMAIL: [info@labcenter.co.uk](mailto:info@labcenter.co.uk)  
53-55 Main St, Grassington, BD23 5AA. WWW: <http://www.labcenter.co.uk>

Fully interactive demo versions available for download from our WWW site.  
Call for educational, multi-user and dealer pricing - new dealers always wanted.  
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

# LAB WORK

# 4

*Objectives: To investigate the operation of fundamental logic gates. Observing the behaviour of "floating" logic inputs. The use of pull-up and pull-down resistors. Assembling combinational logic circuits and deducing truth tables by observing logic states using light-emitting diodes.*

**T**HIS month's Lab Work practical undertaking sets out to investigate the operation and behaviour of fundamental logic gates.

### Lab 4.1

Our first experiment uses an inverter and an l.e.d. to monitor logic levels in our circuits. Fig. 4.7a shows an inverter with an l.e.d. connected directly to its output.

The l.e.d. used is a 5V "direct connection" type with an internal ballast resistor. "Standard" l.e.d.s require the use of an external resistor in series with it, typically 330Ω for a 5V supply.

The inverter is part of a CMOS CD4049 i.c. in a dual in-line package which contains six inverters (hence its name "hex inverter")

The l.e.d. D1 is connected between the positive supply rail and the inverter output (pin 2). When the inverter output is logic 0 (0V) the l.e.d. will *illuminate* because its anode (a) is connected to +5V and its cathode (k) to 0V via pin 2.

Therefore, for the l.e.d. to be on, (inverter output low), the inverter's input at pin 3 must be **high** (logic 1); so l.e.d. on indicates a logic 1 input, and l.e.d. off indicates logic 0 input. Check the Truth Table of inverters ("NOT" gates) in the main tutorial.

Using basic anti-static (ESD) precautions (refer back to Part Three), insert a

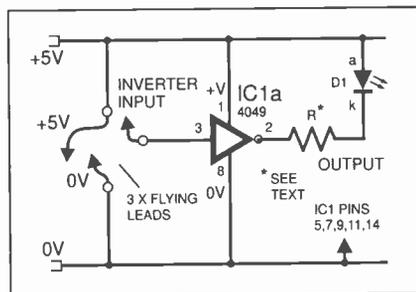


Fig.4.7a. A CMOS inverter is used as a "logic level" indicator. When l.e.d. D1 is lit it indicates Logic 1 (high) at its input.

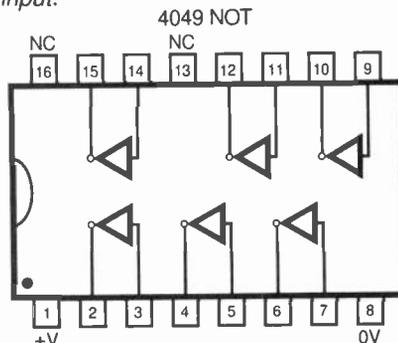


Fig.4.7b (above). Pinout details for a 4049 hex inverter i.c.

CD4049 into the solderless breadboard, noting that the dimple or notch indicates the orientation of the chip i.e. pin 1. Fig. 4.7b is the pin-out diagram for the 4049.

Only one inverter is used in this experiment, so all the other unused inputs should be connected to 0V (pins 5, 7, 9, 11, 14). Pin 1 of this 16-pin d.i.l. chip is connected to the +5V supply, and pin 8 to 0V, via two long "buses" set up on the breadboard to act as power rails. Both supply buses should then be hooked over to your 5V power supply adaptor.

To form the interconnections, use short pieces of solid-core hook-up wire and connect the chip as shown in Fig. 4.7c. Using fine-pointed pliers may help manipulate the wires, and the use of different coloured wires will aid identification.

Check back to Lab Work 1 if necessary, to recall how the breadboard sockets are interconnected. (We'll tell you now that, for future circuits, you may be expected to design the breadboard layout for yourself, cross-referring to the circuit diagram – the example of Fig. 4.7c shows how easy it is!)


The l.e.d. D1 is also placed on the breadboard, observing its polarity (flat notch = cathode). Also, a flying lead is to be connected to the invert input (pin 3), the other end stands out in "mid-air". Two more flying leads connect to the breadboard supply rails at +5V and 0V, offering a source of logic 1 and logic 0 signals.

### How Does It Work?

Grasp the insulation of the +5V flying lead and briefly touch it to the inverter input wire. Release it, then do the same with the 0V lead, touching this briefly to the inverter input lead. For best results, try to keep your own hand well away from the inverter input wire, and obviously *avoid connecting the +5V and 0V wires together!*

You should hopefully find that when you connect the 0V flying lead to the inverter input wire, the l.e.d. will extinguish (indicating logic 0 input), and when you touch the +5V lead to it instead, the l.e.d. will glow (indicating logic 1 input).

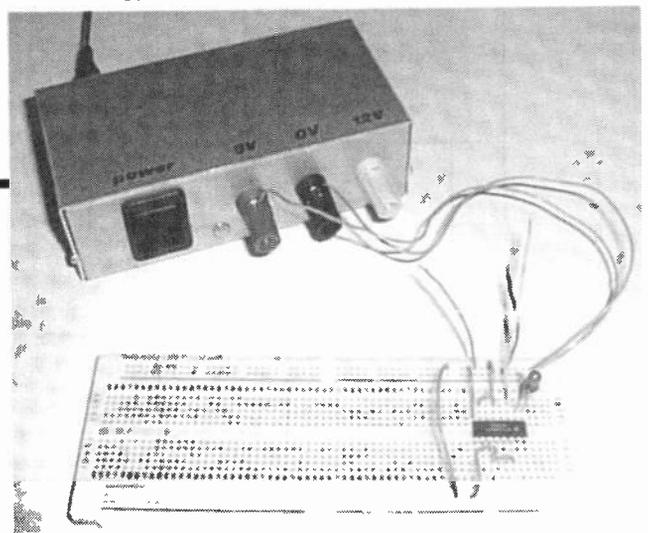However, when *neither* lead is connected, the l.e.d. will remain in the state it was prior to disconnecting the flying leads. It may not be as bright, or it may flicker "on its own".



Using the 5V Add-on Regulator, detailed in Lab Work 3, to power the breadboard demonstrations.

## You Will Need

### Resistors

R1 to R3 10k 0.25W 5% carbon film (3 off)

### Integrated Circuits

CD4001 quad 2-input NOR  
 CD4011 quad 2-input NAND  
 CD4049 hex inverter buffer  
 CD4081 quad 2-input AND  
 CD4071 quad 2-input OR  
 CD4070 quad 2-input EXOR

(Retain CMOS chips in anti-static packaging until needed for use.)

### Miscellaneous

Solderless breadboard; 5mm 5V direct connection light emitting diode (l.e.d.), red (4 off); 5V power supply unit (p.s.u.); hook-up wire.

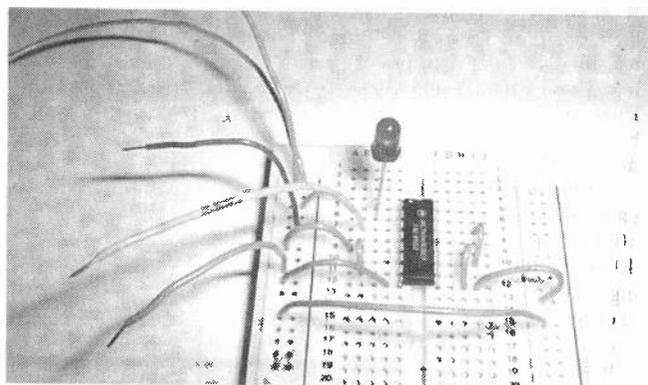
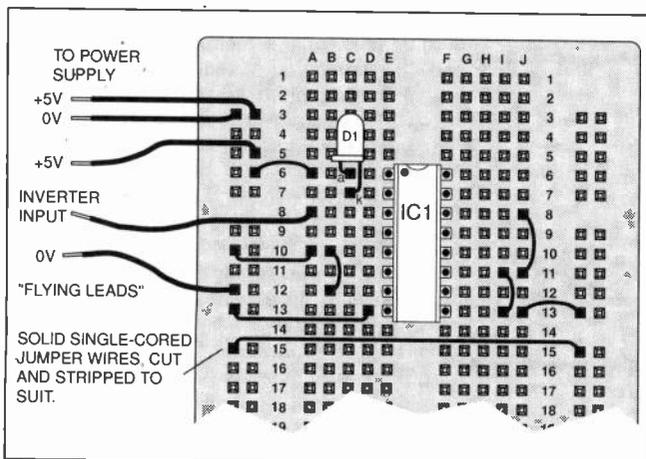


Fig.4.7c (left). Arrangement of IC1 and I.e.d. D1 of our simple logic level indicator circuit Fig.4.7a. (above) Practical layout of components on a breadboard.

• The 4049 is a special type of device classed as a **buffer** – it has a higher current rating than many ordinary CMOS devices, ideal for driving an I.e.d. directly, via an internal or external ballast resistor, of course.

• Because current flows from the +5V rail, through the I.e.d. (and its resistor) and then disappears ("sinks") into the inverter output pin (when at 0V), we call this *sink* current. The opposite state is called *source* current, which flows out from a high output, through a load, to 0V.

• Curiously, many logic devices are far better at *sinking* current than *sourcing* current. Just because an output has gone high to logic 1, doesn't necessarily mean that there is lots of current available to drive loads.

### Lab 4.2

Now set the I.e.d. to "off" (0V wire) and disconnect both 0V and +5V flying leads. Touch the inverter input lead with your hand, and the I.e.d. may illuminate. We're not being definite about what happens here because the behaviour of CMOS with "floating" (unconnected) inputs can be unpredictable!

Experiment a bit to see what effect touching the input lead has. Do you need

to touch the wire itself, or will just touching the insulated sleeving turn the I.e.d. on or off?

### Lab 4.3

Now connect a 10k (kilohms) resistor (R1) between the inverter input (pin 3) and 0V as shown in Fig. 4.8. You will find that the circuit will now behave completely predictably.

The I.e.d. will be lit if the inverter input lead is connected to +5V (simply touch it to the +5V rail on the breadboard), and the I.e.d. will extinguish when pin 3 is grounded to 0V.

• The job of the resistor is to "bias" the input pin safely to 0V which prevents it from floating. It is called a **pull-down resistor**.

The opposite case – where the resistor is hooked to the +5V rail to bias it high – would be called a **pull-up resistor**.

• The unused pins of CMOS gates should be grounded to ensure that they don't float and behave unpredictably, which could affect the reliability of the gate or even the entire chip.

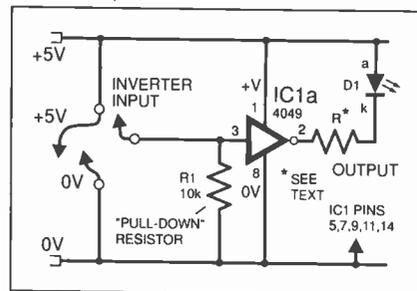


Fig.4.8. Using an additional "pull-down" resistor (R1) biases the inverter input to the 0V rail.

### Lab 4.4

Now things are becoming more challenging – take your time and enjoy it! Fig.4.9 shows how the Truth Tables of all the basic 4000 CMOS 2-input logic gates can be verified.

Three inverters are now used as logic level indicators with light-emitting diodes.

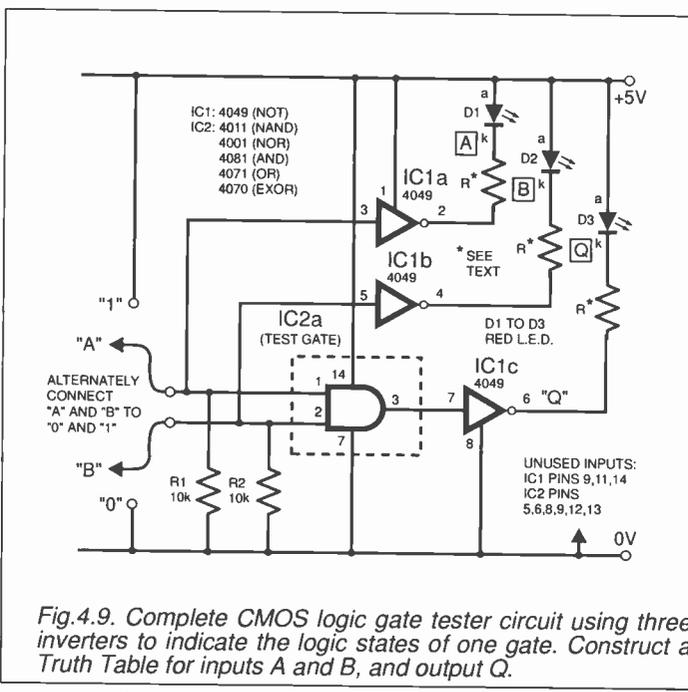


Fig.4.9. Complete CMOS logic gate tester circuit using three inverters to indicate the logic states of one gate. Construct a Truth Table for inputs A and B, and output Q.

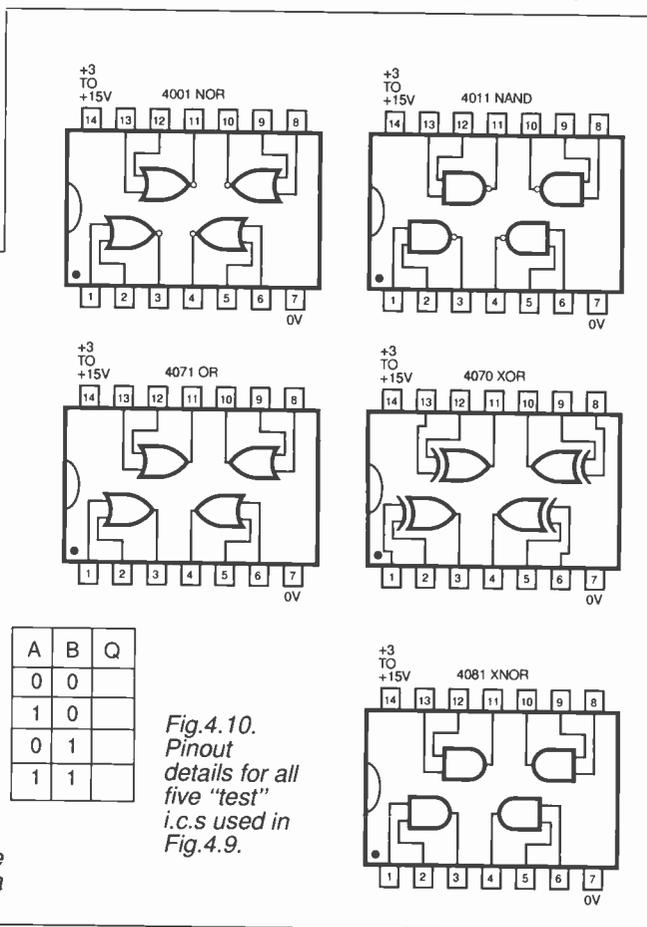


Fig.4.10. Pinout details for all five "test" i.c.s used in Fig.4.9.

IC1a and IC1b should be rewired on your breadboard using two 10k "pull-down" resistors R1 and R2 to prevent them floating. Two l.e.d.s D1 and D2 show the logic levels of the CMOS gate inputs (A and B) being tested, whilst D3 along with IC1c displays the output state of the gate (Q).

A selection from the 4000 series of logic gates will be tested: the 4011 (NAND), 4001 (NOR), 4081 (AND), 4071 (OR) and 4070 (XOR). Note that we are only testing one gate (IC2a) within a 14-pin d.i.l. package, and so steps are taken to ensure that all the other unused pins are grounded.

In this example, the supply pins are the same for each chip, and the pinouts of all the following gates are also the same – it's only the logic function which differs. So, all you have to do is swap IC2 for another type, leaving the wiring of your breadboard in place each time, provided that you align the chip properly on the breadboard. We show the pinouts for all five chips separately, see Fig.4.10.

### Breadboarding

There is plenty of space on the suggested breadboard to build the test circuit, so spread out. As an exercise, you should be able to translate the simple circuit diagram into the physical layout on the breadboard, remembering to follow the pin numbers given in the circuit diagram.

Ensure you polarise the chips correctly, looking for the dimple or notch identifier. All unused pins of both the 4049 inverter and the chip under test (IC2), should be connected to 0V. Also double check the +5V and 0V rails are wired the right way round!

Start by assembling the inverter (IC1) section with three l.e.d.s., using jumper wires as necessary to ensure that everything is connected together. Insert the first "test" chip (IC2), and complete all the

hard wiring around it. The two test inputs (A and B) are effected with two jumper wires which can be hooked to high or low as needed.

Work through the possible combinations of input logic levels (00, 01, 10 and 11), and verify the Truth Tables for the first test gate by noting the pattern of l.e.d.s (remember, '1' = "alight"). Prise out the chip gently, then insert the next test device, and repeat your tests.

### Lab 4.5

The circuit diagram of the "should I change my clothes?" demonstration, described in the main *Teach-In* tutorial, is shown in Fig.4.11. We have included all pin numbers, and identified those unused logic pins which should be connected to 0V, as well as which pins go where for the power supply connections.

Although it looks more complex, if you follow it methodically, you should have no difficulties in assembling this multi-chip demonstration circuit. By now, you should be able to identify the parts from the circuit diagram, and also assemble it on your solderless breadboard using solid-core insulated wires.

Three flying leads are used for the inputs which, you will recall, we labelled as "Umbrella", "Raining" and "Dirty clothing". Observe the pattern of l.e.d.s to confirm the Truth Table for the demo circuit.

• *Combinational Logic* uses a combination of basic logic functions to perform specific logic tasks. You have just constructed such a combinational logic circuit.

### Lab 4.6

For more adventurous readers, try to assemble the "adder" circuit of Fig.4.5 in the main *Teach-In* text. Identify the chips used, deduce the pin numbers, then go ahead and construct this on the solderless breadboard. Then work out how to use the XOR gate to display S<sub>0</sub> instead.

### End of Lab 4 Tasks

If you've followed us through Part 4 and completed the experiments in **Lab Work 4**, you're doing really well! You can now identify dual-in-line chips and their pinout numbering scheme, use CMOS logic gates in basic testing circuits, and assemble and deduce the Truth Tables for a combinational logic circuit containing a variety of different gates. Well done!

**In Lab Work 5:** We develop our knowledge of logic systems further, using more advanced combinational logic circuits, and "Karnaugh maps" – a multi-dimensional Truth Table which helps when developing logic functions.

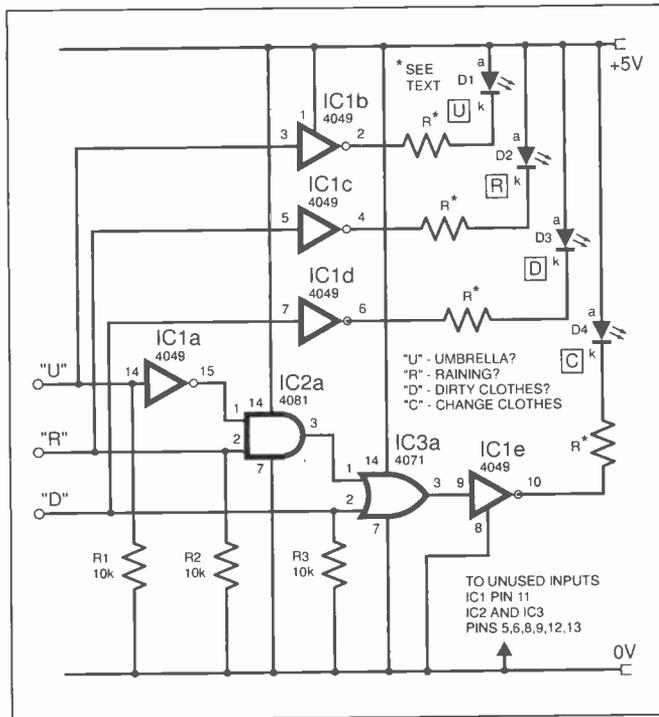
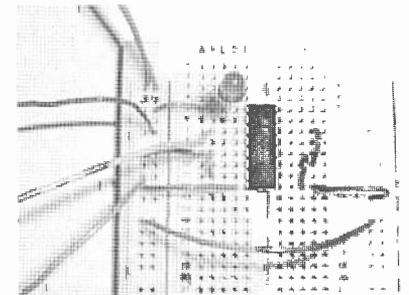


Fig.4.11. Circuit diagram of the complete "Change My Clothes" indicator. Use all three i.c.s on the breadboard, following the pin numbering carefully, construct the Truth Table for all combinations of U, R, D and observe the output C. (Refer to main tutorial text for circuit explanation.)

## SHERWOOD ELECTRONICS

### FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

|       |                                  |       |                                      |
|-------|----------------------------------|-------|--------------------------------------|
| SP1   | 15 x 5mm Red Leds                | SP130 | 100 x Mixed 0.5W C.F. resistors      |
| SP2   | 12 x 5mm Green Leds              | SP131 | 2 x TL071 Op.amps                    |
| SP3   | 12 x 5mm Yellow Leds             | SP132 | 2 x TL082 Op.amps                    |
| SP10  | 100 x 1N418 diodes               | SP133 | 20 x 1N4004 diodes                   |
| SP11  | 30 x 1N4001 diodes               | SP134 | 15 x 1N4007 diodes                   |
| SP12  | 30 x 1N4002 diodes               | SP136 | 3 x BFY50 transistors                |
| SP18  | 20 x BC182 transistors           | SP137 | 4 x W005 1-5A bridge rectifiers      |
| SP20  | 20 x BC184 transistors           | SP138 | 20 x 2-2/63V radial elect. caps.     |
| SP21  | 20 x BC212 transistors           | SP140 | 3 x W04 1-5A bridge rectifiers       |
| SP22  | 20 x BC214 transistors           | SP142 | 2 x Cmos 4017                        |
| SP23  | 20 x BC549 transistors           | SP144 | 3 x TIP31A transistors               |
| SP24  | 4 x Cmos 4001                    | SP145 | 6 x ZTX300 transistors               |
| SP25  | 4 x 555 timers                   | SP146 | 10 x 2N3704 transistors              |
| SP26  | 4 x 741 Op.amps                  | SP147 | 5 x Stripboard 9 strips x 25 holes   |
| SP28  | 4 x Cmos 4011                    | SP151 | 4 x 8mm Red Leds                     |
| SP29  | 4 x Cmos 4013                    | SP152 | 4 x 8mm Green Leds                   |
| SP33  | 4 x Cmos 4081                    | SP153 | 4 x Yellow Leds                      |
| SP36  | 25 x 10/25V radial elect. caps.  | SP154 | 15 x BC548 transistors               |
| SP37  | 15 x 100/35V radial elect. caps. | SP156 | 3 x Stripboard, 14 strips x 27 holes |
| SP39  | 10 x 470/16V radial elect. caps. | SP160 | 10 x 2N3904 transistors              |
| SP40  | 15 x BC237 transistors           | SP161 | 10 x 2N3906 transistors              |
| SP41  | 20 x Mixed transistors           | SP165 | 2 x LF351 Op.amps                    |
| SP42  | 200 x Mixed 0.25W C.F. resistors | SP167 | 6 x BC107 transistors                |
| SP46  | 20 x 400mW zener diodes          | SP168 | 6 x BC108 transistors                |
| SP47  | 5 x Min. PB switches             | SP175 | 20 x 1/63V radial elect. caps        |
| SP102 | 20 x 8-pin DIL sockets           | SP177 | 10 x 1A 20mm quick blow fuses        |
| SP103 | 15 x 14-pin DIL sockets          | SP182 | 20 x 4-7/50V radial elect. caps.     |
| SP104 | 15 x 16-pin DIL sockets          | SP183 | 20 x BC547 transistors               |
| SP105 | 5 x 74LS00                       | SP187 | 15 x BC239 transistors               |
| SP109 | 15 x BC557 transistors           | SP191 | 3 x Cmos 4023                        |
| SP112 | 4 x Cmos 4093                    | SP192 | 3 x Cmos 4066                        |
| SP115 | 3 x 10mm Red Leds                | SP193 | 20 x BC213 transistors               |
| SP116 | 3 x 10mm Green Leds              | SP194 | 10 x OA90 diodes                     |
| SP118 | 2 x Cmos 4047                    | SP195 | 3 x 10mm Yellow Leds                 |
| SP120 | 3 x 74LS93                       | SP197 | 6 x 20 pin DIL sockets               |
| SP121 | 6 x Rectangular Red Leds 5x2mm   | SP198 | 5 x 24 pin DIL sockets               |
| SP122 | 6 x Rectangular Green Leds 5x2mm |       |                                      |

#### RESISTOR PACKS – C.Film

|      |                                 |       |
|------|---------------------------------|-------|
| RP3  | 5 each value – total 365 0-25W  | £2.80 |
| RP7  | 10 each value – total 730 0-25W | £4.00 |
| RP10 | 1000 popular values 0-25W       | £5.80 |
| RP4  | 5 each value-total 365 0-5W     | £3.75 |
| RP8  | 10 each value-total 730 0-5W    | £6.35 |
| RP11 | 1000 popular values 0-5W        | £8.10 |

1998 Catalogue £1 inc. P&P or FREE with first order.

P&P £1.25 per order. **NO VAT.**

Orders to:  
**Sherwood Electronics,**  
7 Williamson St., Mansfield,  
Notts. NG19 6TD.

# Techniques

## ACTUALLY DOING IT!

by Robert Penfold

**T**HE FIRST stage of project construction is usually the building of the circuit board. Having successfully completed that task it is tempting to sit back and consider the project virtually finished. In reality, the mechanical aspects of construction and any hard wiring that is required may well take longer than building the circuit board.

Turning a completed circuit board into a finished project is definitely somewhat lower-tech than building the board itself, and to a large extent it involves familiar tools such as screwdrivers and pliers. There are still a few pitfalls to avoid though, and any lack of thought or care on this aspect of construction will at best result in a rather rough but working project. At worst, a circuit board which has been built correctly could be damaged and rendered useless by carelessness during the later parts of construction.

### Guided Tour

Having constructed the circuit board it is obviously necessary to mount it in the case. This is not quite as straightforward as it once was, as there are now several common methods of mounting circuit boards, plus seemingly endless variations on these.

A few projects have a circuit board which simply slides into guide rails moulded into the case. Guide rails are often to be found in plastic and diecast aluminium boxes, but are not a feature of most other cases.

The boxes that have these guide rails almost invariably have a slightly tapered shape, and it is often necessary to file the board slightly to give it a matching taper. Apart from this, the guide rail method is perfectly straightforward.

Its only real drawback is that it is often impractical except where a circuit has been specifically designed to suit a particular case. It is sometimes possible to produce an over-length version of the circuit board so that it will fit into the rails, but this is only possible with stripboard construction or if you are making your own custom p.c.b.s.

There is a slight variation on the guide rail system which has four plastic clips fitted onto the board first, and then the board is slotted into the guide rails via these clips. The idea of this system is that it enables the circuit board to be mounted at right angles to the rails, which often enables a larger circuit board to be accommodated. It has a slight drawback, which is simply that getting everything into place can be awkward. Experience has shown that the board is not held as securely as one would wish.

### Above Board

With most projects the circuit board must be held in place using either nuts, bolts, and spacers, or using some form of plastic stand-off.

If the case is a metal type this will result in the soldered connections on the underside of the board short-circuiting through the case, almost certainly short-circuiting the battery or power supply in the process! Even if the case is made from plastic, the board must still be held slightly clear of the case.

The underside of the circuit board is far from flat, with the soldered joints standing a few millimetres proud of the board's surface. When the mounting nuts are tightened, the areas of board immediately around them are pressed flat against the case, but the areas around soldered joints are kept a few millimetres clear of the case.

There are two possible outcomes to this. If the circuit board is made from s.r.b.p. (silicon resin bonded paper) or some similar material, it will become badly distorted, and may even break. The brittleness of stripboard makes it especially vulnerable to this problem. If the board is made from fibreglass it might be distorted, but with something like a folded aluminium case it is quite possible that the case will be deformed and ruined.


Omitting the spacers more or less guarantees disaster. In fact taking short cuts when building anything almost invariably proves to be a false economy.

### Wobble Board


Plastic stand-offs exist in a variety of forms, so you need to look carefully at the descriptions and illustrations in catalogues to make sure you are getting the exact type you require. The original types were designed to clip into holes drilled in the case, with the circuit board then clipping in place onto the tops of the stand-offs.

This may seem to be a very convenient way of doing things, but it does not seem to hold the board as securely as other methods. In fact there seems to be a certain amount of built-in wobble with this method.

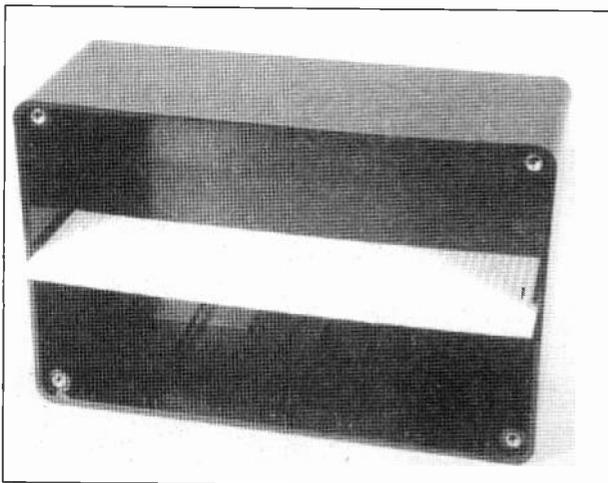The mounting holes in the board and the case must be just the right size or the board will not clip in place properly at all. Many of these stand-offs require rectangular cut-outs



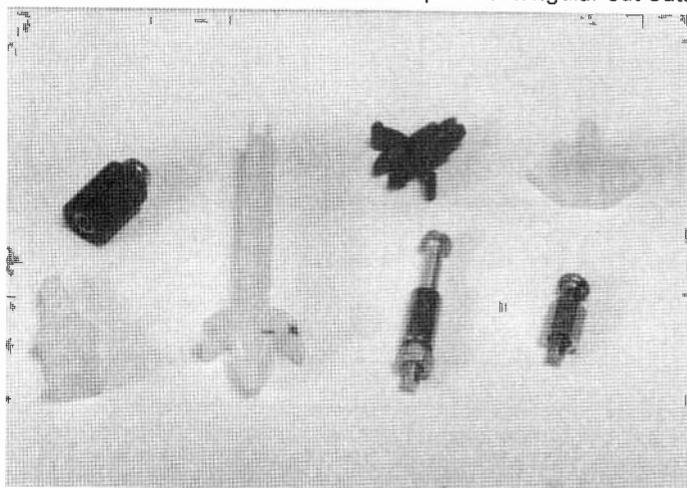Many plastic cases have built-in guide rails, but they are little used in practice.



A selection of circuit board plastic stand-offs, plus threaded and non-threaded spacers.

in the case. Probably the easiest way of making these is to first drill a small circular hole, and then file it out to the right size and shape using a miniature square or triangular file.

There is an alternative type of stand-off which clips into holes in the case, but at the other end it has a long guide into which the circuit board is slotted. Unlike other forms of stand-off, the board is mounted at 180 degrees to the stand-offs rather than perpendicular to them.

This might mean having to mount the board on (say) the rear panel of the case rather than the base panel, and in some cases it might not be practical to use this kind of mounting at all. Also, a few millimetres at each end of the circuit board must be free from components so that board will fit into the guides properly.

Another form of stand-off is secured to the case by way of a self-tapping screw, and then the board clips in place on top of it. This seems to give better reliability, but it would not be a good idea to use it with circuit boards that carry the mains supply or any high current/voltage wiring.

Yet another type of mounting pillar has threaded bushes at both ends. The idea is that the pillars are bolted to the board using short screws (usually M3 size), and then the circuit board is fixed in place using the same method. This is a very secure way of mounting circuit boards, but the threaded mounting pillars are relatively expensive.

There is one final variation in the form of stand-offs which are glued to the case and clip into the circuit board. The bases of these are usually ready-fitted with self-adhesive pads.

This type of stand-off offers the ultimate in simplicity, since you can fit them onto the board, peel off the paper covers from the pads, and then simply press the board into place on the case. Self-adhesive stand-offs are ideal for small boards.

### Spaced Out

In a similar vein, threaded metal spacers can be obtained. These are used with bolts that are several

millimetres longer than the spacers, so that each bolt protrudes above the top of its spacer. The circuit board is then fitted onto the ends of the bolts, and nuts are used to fix it in place. This method works well, and holds the board securely in place.

There is a variation on this approach which utilizes non-threaded spacers, and this also works well. It can be a bit fiddly getting everything in place, especially if the board has three or four mounting bolts, but some Bostik Blu-Tack or Plasticine can be used to hold the bolts in place while everything is loosely assembled. With the Blu-Tack or Plasticine removed, the mounting nuts can be fully tightened. Spacers and mounting bolts are almost certainly the most popular method of fixing circuit boards in place.


### Call for M

The standard choice for mounting bolts used to be the 6BA variety, but the imperial sizes are gradually being phased out and replaced with the metric M\* series. The number after the letter "M" is the bolt diameter in millimetres, and the most popular size for mounting circuit boards is M3. This is fractionally larger than 6BA, but the difference is small. In both cases most mounting holes of about 3.2mm to 3.5mm are required.

When using stripboard there is something to be said for using slightly smaller mounting bolts, as it permits the use of smaller mounting holes in the board. Stripboard is drilled with one millimetre diameter holes on a 2.54mm matrix. Enlarging one of the holes to much more than about three millimetres can result in that hole starting to merge with the four holes that surround it.

This effectively gives a mounting hole which is much larger than is really needed. Experience suggests that M2.5 bolts together with mounting holes of 2.8mm to 3mm diameter are a better option for stripboard.

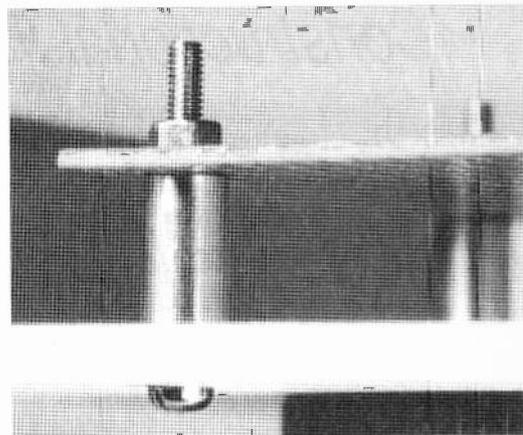Stripboard and plastic stand-offs that clip onto the circuit board do not usually work well together. Plastic stand-offs of this type seem to




*Although a board clamped to a case by a nut, bolt and spacer is perfectly adequate, adding a second "lock" nut between the spacer and board enables easy removal of the board, without the bolt and spacer being dislodged.*

require quite large mounting holes in the board, which inevitably means that there are problems with the existing matrix of holes. You end up with an odd shaped and oversized mounting hole which will not clip onto the stand-off properly. It is probably best to only use mounting bolts plus some form of spacer with stripboard, or plastic stand-offs of a type that bolt to the circuit board.


When using bolts and spacers it is essential to position the mounting holes in the case with a high degree of accuracy. Even quite small errors can put the board under a fair amount of stress when the mounting nuts are tightened.

When using stripboard, which tends to be quite brittle, there is a definite risk of the board shattering. Use the circuit board as a template when marking the positions of the mounting holes, and this makes it easy to achieve good accuracy.

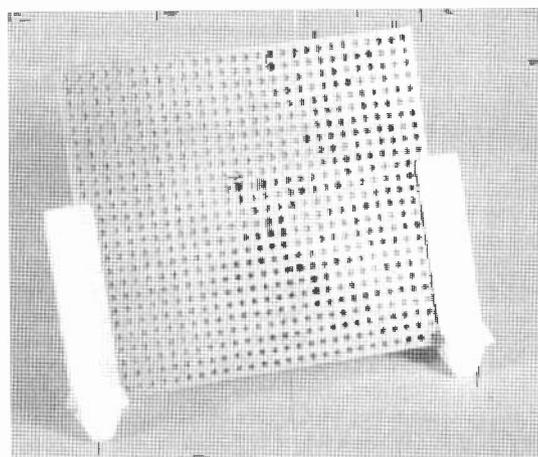Once the holes have been drilled, you should hold the board in place over them to check that there is a good match. If necessary, use a miniature round file to elongate one or two of the mounting holes in the case to obtain better correlation between the two sets of holes.



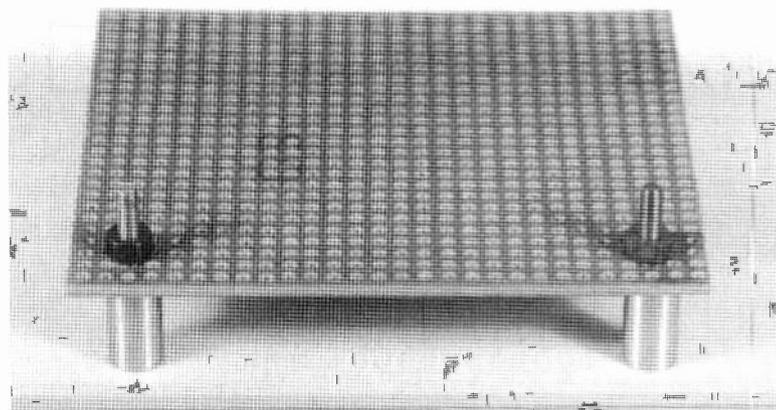
*Printed circuit guides are a simple and effective means of mounting small to medium size boards.*



*Old fashioned nuts, bolts and spacers seem to be the most popular method of mounting printed circuit boards and stripboard.*

# KISSOMETER

WILLIAM CHESTER

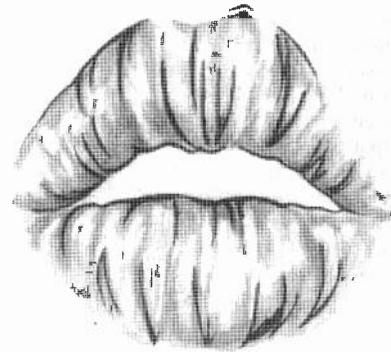

Find your true Valentine with this low-cost, fun project

THE TITLE of this project may well suggest a rather frivolous use for discrete electronics. You could be well advised, however, to drop that stiff upper lip for a while and avoid your medication in favour of some good old fashioned fun; the fairground variety to be precise!

If you have read this far, you must have at least identified with some originality in the title. However, you may be surprised to learn that some similar such "machines" have long since been an attraction in amusement arcades and similar environments. Even dating back to Victorian times, electromechanical novelties have exploited our human capacity for curiosity and... sometimes, loose change!

The Kissometer is very much an arbitrary title; as you will see, with simple label changes it could be called almost any other kind of...-ometer. Presented here as the Kissometer, this project may well prove to be a worthy curiosity, especially on St. Valentines day, for instance.

## SOFT TOUCH

In essence, if you have not already guessed, the principle of operation goes like this: Place one's finger, or perhaps other bodily appendage, upon some touch

pad contacts. Wait for the auditory senses to be sufficiently stimulated (or more likely at the moment onlookers ask you to kill the unearthly thing making the noise); lift your clammy finger - and take delight in the visual wonder that is... well, the means by which the Kissometer judges your "kissability".

The jumping light emitting diode (l.e.d.) dot display will gradually slow down until it settles and stops so as to light only one l.e.d. The label adjacent to the lit l.e.d. now indicates your rating.

The more observant individuals amongst you will realise that this "decision" is an almost perfectly random indication. But, before you reach for the nearest re-design engineer, remember one very appropriate saying; "most people can be fooled at least some of the time". Especially if love's mischievous cupids have let fly a stray arrow and temporarily blinded the Romeo or Juliet concerned.

Just remind them that their skin resistance falls as vigorous hormone activity causes small yet detectable changes in body perspiration. It's true, honestly!

## SYSTEM OPERATION

A block diagram for the Kissometer is shown in Fig.1. The presence of a

finger across the touch pads is detected and amplified to produce a voltage which is then stored on the plates of a capacitor. When this voltage exceeds a preset level, the threshold detector switches the audio amplifier on, and turns the display off.

The voltage stored in the charge reservoir capacitor continues to rise while the touch pads remain bridged. The voltage is also routed to the voltage controlled oscillator (v.c.o.), whose output frequency rises while the level at its control input rises. The varying frequency is taken to the audio amplifier and then output directly from the loudspeaker.

Although the display is turned off, the decade counter is clocked rapidly by the square wave output from the oscillator. When the finger is lifted, the reservoir capacitor is discharged in a controlled fashion. As the voltage falls back below the preset level, the threshold detector operates the display switch, turning the display back on.

By this time, the frequency has fallen sufficiently, allowing the individual on and off lighting action of each l.e.d. to be clearly seen. The moving l.e.d. dot display continues slowing down in speed and soon stops, as a consequence of full discharge of the reservoir capacitor.

Several factors introduce a random element to the operation. These include skin resistance, contact pressure, contact duration and frequency variation. At the time of design, it was not considered desirable to have the display showing the effects of the higher clock frequencies. The l.e.d.s would, in any case, be switched so fast that to the human eye they would all appear to be on simultaneously. This is why a display switch is used.

## CIRCUIT DESCRIPTION

The full circuit diagram for the Kissometer is shown in Fig.2. The junction of the lower touch contact with resistor R1, is taken to the non-inverting input of IC1a. This is half of an LM358 operational amplifier. Here it is configured as a d.c. amplifier with a gain of ten.

When a finger is placed on the contacts, the surface skin resistance forms a potential divider with R1. The d.c. voltage at pin 3 input will rise, causing an amplified level to appear at the output pin 1.

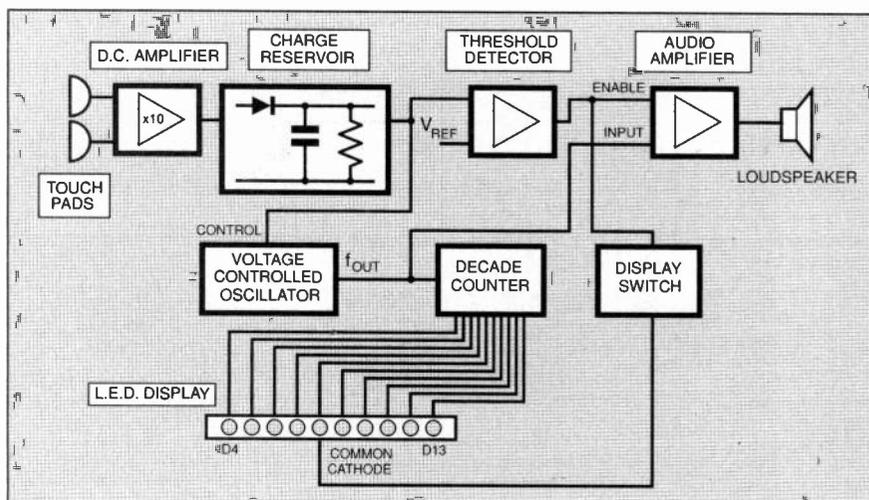


Fig.1. Block schematic diagram for the Kissometer.

Capacitor C1 is now charged, through resistor R4 and forward biased signal diode D1. Resistor R5 comes into effect later, providing a much longer discharge time-constant after the finger is lifted.

The rising voltage on capacitor C1 does two main things. First, when it exceeds the reference level, set at pin 5 of IC1b, the output of this comparator switches down to virtually the 0V supply. This level change enables the audio amplifier and buffer built around TR1 and also switches TR2 off – thereby blanking the l.e.d. display. Since resistor R7 is very small compared to the value of R6, the comparator threshold is reached quickly.

Second and simultaneously, the d.c. level on C1 is transferred through diode D3 to the control voltage input of IC2 at pin 9. Here the voltage is slightly delayed but further stored by electrolytic capacitor C4. Resistor R11 plays no part at this stage of events.

The popular 4046 CMOS phase-lock-loop is selected for IC2 and, in this application, it is only the internal v.c.o. which is used here. Components R12 and C5 set the maximum frequency, or upper limit of the v.c.o. output to approximately 1kHz.

### SKIN EFFECT

The actual skin resistance, peculiar to each individual will determine the absolute value of the control voltage at pin 9 of IC2. The v.c.o. output, at pin 4 of IC2 is coupled, via R13 and C3 to the input of the audio amplifier TR1.


Once the threshold of IC1b has been reached, the subsequent antics of the v.c.o. frequency output will be heard from the loudspeaker LS1. The resulting siren-like din is certainly loud enough to alert people and other animate objects within about fifty metres. Actually the sound is more pleasing than confusing. As one's finger plays upon the Touch Pads, the fluctuating frequency content is rather reminiscent of a "wolf-whistle". Quite appropriate really.

When the person lifts their finger, either out of surprise or utter consternation, capacitor C1 will start to discharge, via resistor R5. This is due to IC1a pin 1 switching to "low" (0V) in response to now having 0V present at pin 3 input.

After a little time, the threshold set at IC1b pin 5 is passed but in the opposite direction. Consequently the output at pin 7 goes "high" (to within 2V of the d.c. supply line) which reverse biases diode D2, disabling transistor TR1 by removing the d.c. base bias needed for its operation. At the same time, current fed through resistor R15 now turns TR2 back on and the l.e.d. display is lit.
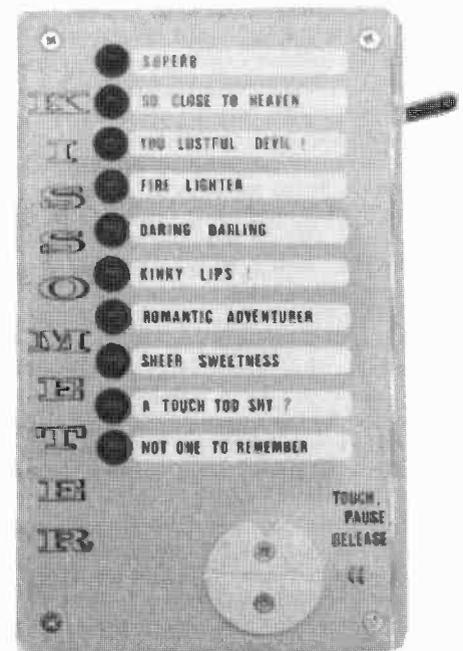
### YOUR POTENTIAL

As capacitor C1 continues to lose its stored potential, audio is now absent but in its place is the l.e.d. display. This behaves like a dot display, since only one l.e.d. is lit at any instant. However, the unique operation means that the l.e.d. movement gradually slows down and finally settles; an action that almost seems to suggest



the machine has some inbuilt capacity for decision making.

The l.e.d. movement slows because as the control voltage at IC2, pin 9 falls, so too does the output frequency. Capacitor C4 is included to ensure that a suitable delay exists between IC1b switching high and the v.c.o. halting. In other words, movement of the display continues for a time, determined by C4 and R11, after audio output has ceased.

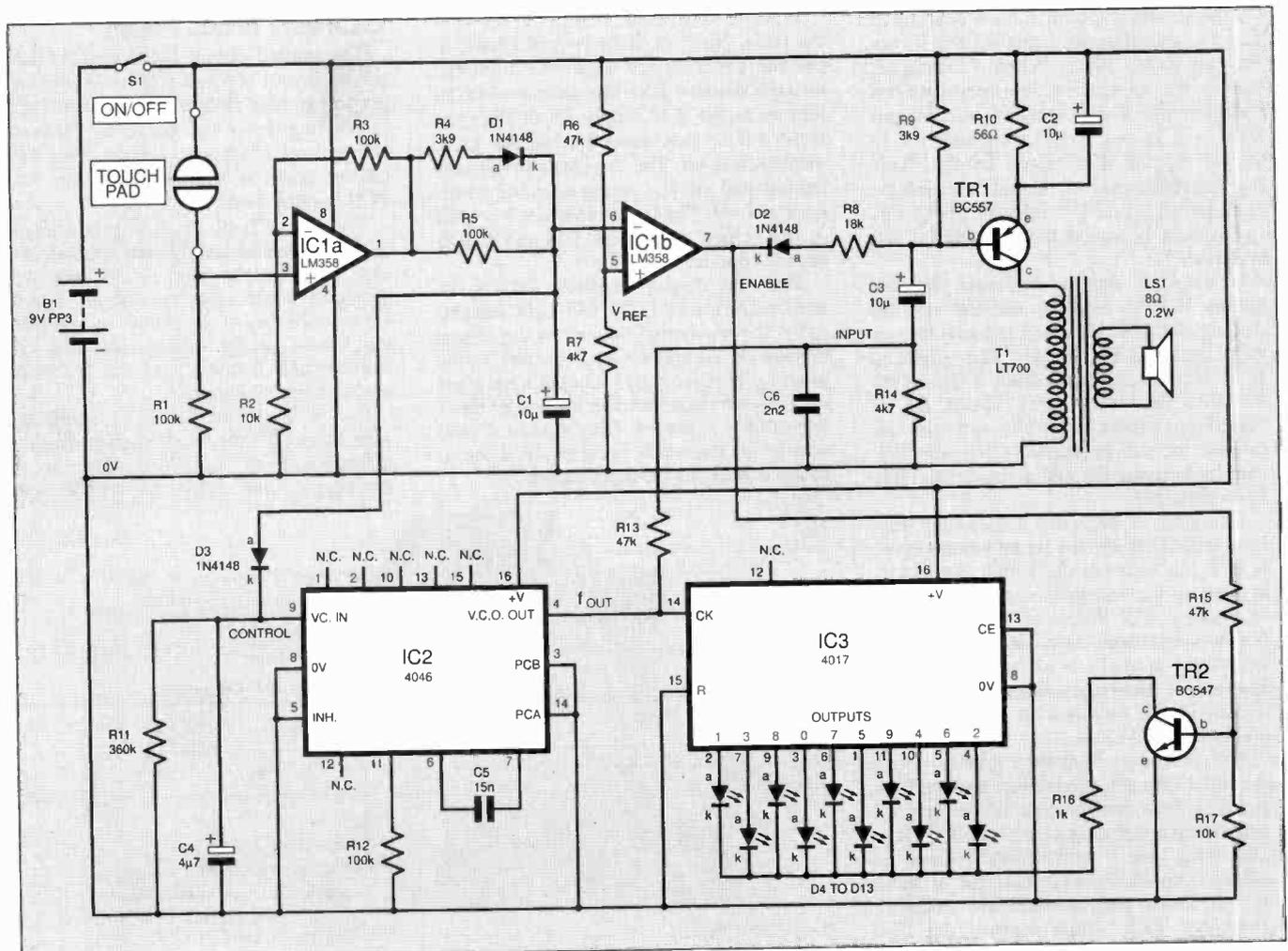


Fig.2. Complete circuit diagram for the Kissometer.



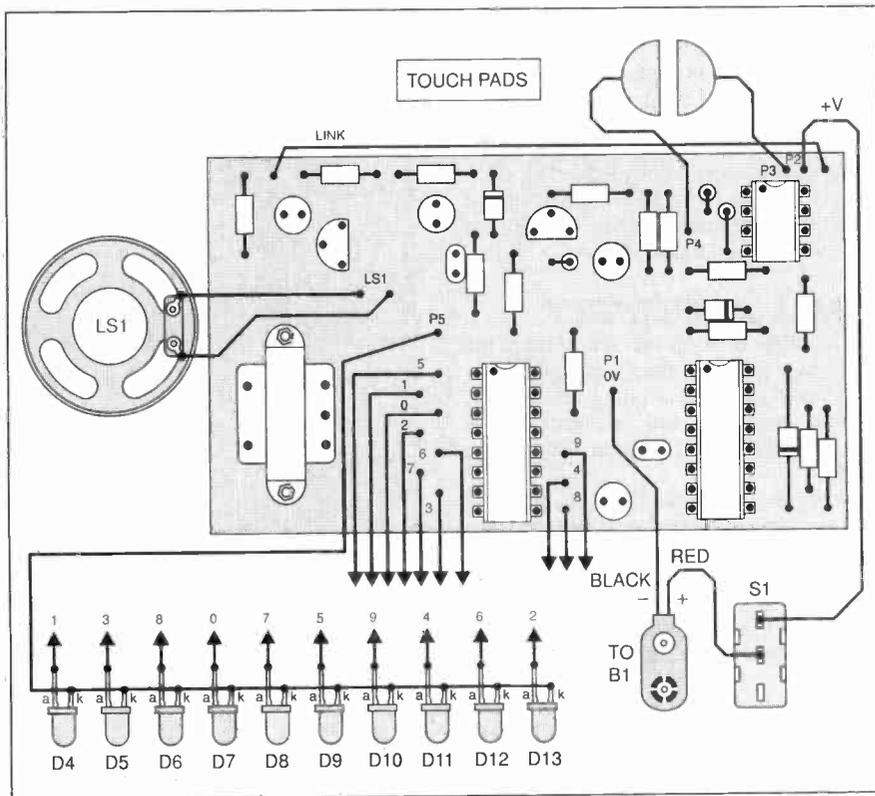


Fig.4. Interwiring from p.c.b. to off-board components. The wiring to the l.e.d.s is not in sequence to add to the random effect.


copper pads to the "positive" ends of TR1 amplifier components.

Follow this by mounting the low value capacitors, C5 and C6. Then the polarised, radial lead electrolytics; C1, C2 and C3, C4. Observe the correct polarity in each case.

The two transistors are next. Note that TR1 is a *pn*p type and TR2 a *np*n type. However, they both have the same lead-outs and the preformed lead variants will fit directly on the p.c.b., automatically giving correct orientation. If yours come

with the leads in-line, just make sure that the flat side of the transistor body coincides with the component layout diagram.

Now fit the output transformer T1. The core mounting tags can be inserted through the board and then soldered underneath onto the copper lands. This method provides a rigid mechanical fixing, preferable to sole reliance on the strength of the winding leads. Position T1 so that the primary winding (three leads) is on the same side as IC3. Bend the unused middle lead upward, against the insulated windings.

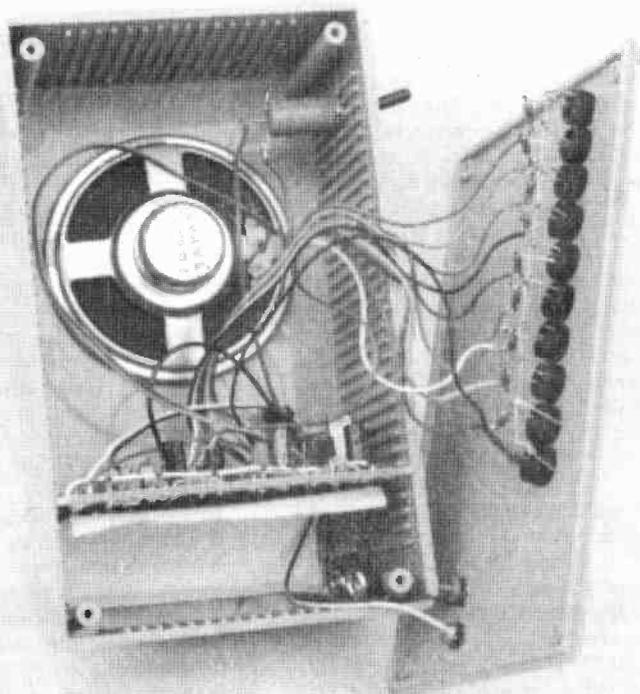

Circuit board slotted into case and interwiring to display l.e.d.s. Note the protective card in the battery compartment.

## PRELIMINARY WIRING

At this stage, before fitting the i.c.s. the flying leads from the p.c.b. can be attached (see Fig.4.). Take two of these, each about 200mm long, to the loudspeaker LS1 pads. Twist them together a few times to form a pair, in readiness for connection to the loudspeaker. Two separate wire lengths are also soldered to the Touch Pad points.

The black, negative (0V) wire from the battery clip is soldered to pad P1, beside R13. The battery positive lead (red) should be taken to the pole contact of the single-pole power switch S1. Depending upon what kind of switch is employed, S1 may need to be fitted into the case before solder connections to it can be completed. The other side of S1 is soldered to the +V solder terminal P2 on the p.c.b.

## ON DISPLAY

The final connecting wires are those for the random l.e.d. display. Random is the

## COMPONENTS

### Resistor

|                         |              |
|-------------------------|--------------|
| R1, R3, R5,             |              |
| R12                     | 100k (4 off) |
| R2, R17                 | 10k (2 off)  |
| R4, R9                  | 3k9 (2 off)  |
| R6, R13,                |              |
| R15                     | 47k (3 off)  |
| R7, R14                 | 4k7 (2 off)  |
| R8                      | 18k          |
| R10                     | 56Ω          |
| R11                     | 360k         |
| R16                     | 1k           |
| All 0-25W 2% metal film |              |

See  
**SHOP  
TALK**  
Page

### Capacitors

|            |                                  |
|------------|----------------------------------|
| C1, C2, C3 | 10μ radial elect. 25V<br>(3 off) |
| C4         | 4μ7 radial, elect. 25V           |
| C5         | 15n polyester                    |

### Semiconductors

|            |   |
|------------|---|
| D1, D2, D3 | 1N4148 signal diode<br>(3 off)  |
| D4 to D13  | 5mm standard or high<br>brightness l.e.d., with<br>panel mounting clips<br>(10 off) |
| TR1        | BC557 <i>pn</i> p silicon<br>transistor   |
| TR2        | BC547 <i>np</i> n silicon<br>transistor   |
| IC1        | LM358 dual op.amp   |
| IC2        | 4046B CMOS phase-<br>locked loop  |
| IC3        | 4017B CMOS decade<br>counter  |

### Miscellaneous

|     |  |
|-----|--|
| T1  | LT700 transistor output<br>transformer     |
| LS1 | 8 ohm miniature<br>loudspeaker (0-2W)      |
| B1  | 9V battery (PP3),<br>with clip             |
| S1  | on/off s.p.s.t. slider or<br>toggle switch |

Printed circuit board available from EPE PCB Service, code 181; plastic box, size 90mm x 149.5mm x 52.5mm; 8-pin d.i.l. socket; 16-pin d.i.l. socket (2 off); 10-way multi-coloured ribbon cable or multistrand connecting wire, approx. 200mm lengths; solder pins, if required; metal pieces (aluminium) for touch pads; rub-down decals (transfers); self-adhesive paper labels; solder etc.

Approx Cost  
Guidance Only

**£17**

term used here since the sequential outputs of IC3 are not matched physically by the l.e.d. positions on the Kissometer front panel. In practice this adds to the element of surprise, especially when the counter is about to stop.

A suggested front panel display layout for the l.e.d.s is shown in the photographs of the completed unit. From the top to the bottom this follows the IC3 output sequence of: 1, 3, 8, 0, 7, 5, 9, 4, 6, 2.

A length of 10-way multi-coloured ribbon cable or individual connecting wires can be used to hook-up the l.e.d.s to the circuit board. Either way, an initial length of 200mm should prove adequate. Each wire can then be trimmed to length as they are soldered between the p.c.b. and top (lid) display panel during final assembly.

All the l.e.d. cathodes (adjacent to the flat side of the l.e.d. body) are commoned together. Take a flying lead from p.c.b. solder terminal P5 to the common cathode (k) link so formed. Mount the l.e.d.s into holders on the top panel, *before* wiring the cathode (k) leads together.

Finally, fit IC1, IC2 and IC3. A socket is not essential for IC1 but sockets are advisable for IC2 and IC3 since these are CMOS types and therefore sensitive to static.

## CASE DETAILS

The case employed is a plastic type that is easy to obtain. Being plastic, holes and apertures are so much easier and faster to accomplish, compared with aluminium or steel panel work. Photographs of the completed "machine" show a suggested top panel layout. As can be seen, the mounting hole requirements are quite straight forward. Mark-out and drill the ten in-line holes for the l.e.d. display. Since these are on the front panel, take care to protect the surface from scuff and scratch marks. Self-adhesive clear tape may prove useful.

It is important that the p.c.b. occupies a slot in the case where it cannot foul with the leads of the bottom l.e.d. (D13) or the fixings for the Touch Pads. With this in mind, choose a suitable site for the touch pad mounting holes before carefully drilling them.

The design of these is really open to personal preference, allowing you to exercise your own brand of creativity. Relatively plain looking aluminium pads were fabricated for the prototype but the sheet material could so easily be shaped to resemble an upper and lower lip, for example.

Bear in mind the following factors, concerning the pads. Ideally they should be of a material that does not quickly oxidise in the presence of moisture. In an indoor environment, aluminium is fine. It might benefit from an occasional polish however. Zinc plated screws, bolts or sheet would provide ultimate reliability in more adverse conditions and stainless steel would give a real glitzy appearance.

The area of bodily skin making contact on each pad should be relatively high, compared with the gap between the pads themselves. Position the pads close together so that there is always adequate contact resistance to operate the circuit, no matter who is trying.

The lower half of the case needs an aperture cutout in one side panel to take the On/Off slider or toggle switch S1, and a matrix of sound output holes drilled in the "floor" for LS1. The loudspeaker itself can be fixed most simply by using double-sided sticky tape. The thick variety is best. The tape is applied so that it forms a continuous sealing ring around the cone to panel fixing surface.

## FINAL ASSEMBLY

Complete construction by sliding the p.c.b. into the case, then wire all the appropriate flying leads to the l.e.d. display, switch, touch pads and loudspeaker. Use the interconnection diagram, Fig.4 as a guide.

Using the specified case, the p.c.b. is best positioned in the fourth slot from the bottom end. The battery can then be conveniently accommodated in the void created between the track side of the board and the case. Also, it avoids fouling the bottom l.e.d. and the touch pad fixings.

It is advisable to insert a pre-shaped piece of card or foam padding into the "battery compartment" to cushion the battery. This will stop it rattling around and possibly shorting out any solder joints on the underside of the p.c.b.

The final touch is effected by applying four self-adhesive feet on the underside of the case. These will lift the case clear of whatever surface the unit is placed upon, allowing the audio frequencies to escape.


## TESTING

Before applying battery power, recheck the battery clip connections. With a multimeter, set to an ohms range, check between solder pins P1 and P2 for any obvious short-circuits. Place the positive probe on terminal P2. A brief examination of your soldering workmanship at this stage will allow the quick location of unwanted anomalies like solder bridges and dry joints.

Connect the battery and switch S1 on, initially there should be no sound from the loudspeaker and only one l.e.d. should be lit. If some noise is present, check that the output of IC1b, at pin 7 is not more than 2V below the d.c. positive supply. The input at pin 6 of IC1 should be at the 0V level.

Place a finger or some conductive material across the touch pads. Almost immediately, sound will emanate from loudspeaker and the stationary, single l.e.d. will extinguish. If you are using a finger across the touch pads, the sound will vary in frequency in a fashion that is dependant on the applied pressure and skin resistance, as discussed earlier in the text.

In this state, the output of IC1b, at pin 7 should be within 2V of the 0V supply potential at terminal pin P1. For confirmation that the audio amplifier is biased on correctly, measure the voltage dropped across resistor R10. This level should be between 0.8V and 1V, indicating a collector current of, typically 16mA d.c. The l.e.d. display will be off since the voltage at the base (b) of transistor TR2 will be no higher than 0.3V.

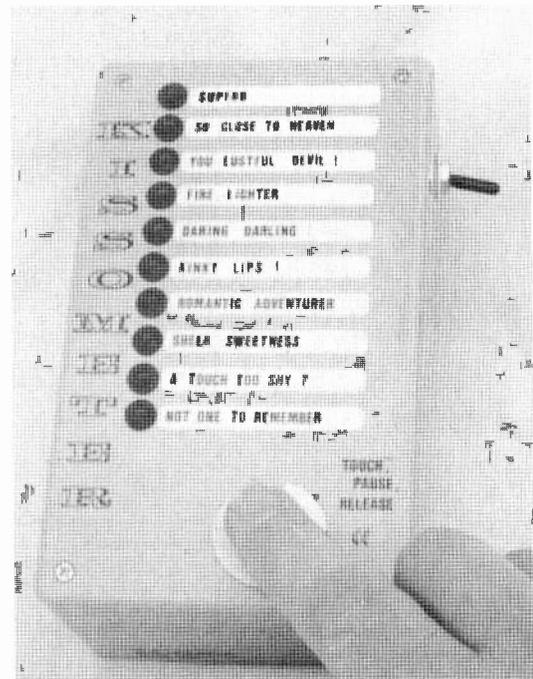

If no activity occurs at all, first suspect the possible incorrect positioning of diode D3 before thinking that the amplifier may be at fault. If D3 is fitted the wrong way round, then no control voltage will reach the voltage controlled oscillator; therefore no output frequency will be available to the amplifier, or indeed to clock the counter of IC3.

Assuming all is well, finally lift the object off the touch pads and note what happens next. After a short delay the sound should cease and the l.e.d. display will light up. The movement of the l.e.d. light may be quite fast to begin with, or slower, depending on what upper frequency the oscillator was taken to. Whichever is the case, the l.e.d. should soon slow and then come to a stop.

If the l.e.d. settles at the same time as the sound stops, then check that capacitor C4 is correctly positioned and in circuit, also that the value of resistor R11 is 360 kilohms.

## IN USE

Operation of the Kissometer is quite straightforward; it is the specific application or interpretation of its output that is open to one's own imagination. With this in mind, it is a good idea to use a method of labelling each l.e.d. position that allows changes to be made with relative ease.

For the prototype model, the front panel l.e.d. annotations were made using self-adhesive white labels, upon which rub-down dry transfer lettering was applied. This was carried out *before* the labels were stuck on the front panel, adjacent to each l.e.d.

To ensure a good degree of reliability it is advisable to clean the Touch Pads from time to time. Over extended periods of use, the deposits of dust – even grease and grime of biological origin – will reduce the unit's response slightly.

Be aware that too much moisture could engage the sound output continuously. Certainly do not leave it out in the rain or take it into the bath!

Happy Valentine's Day!

More than

0 0 2 5 8 1

Electronic

**DESIGNERS**

know how to get their

**PROTOTYPE PCBs**

from their **usual manufacturer** for a

**FRACTION** of the **COST!**

DO YOU ?

STOP WASTING YOUR MONEY!

CALL NOW: 00353 65 66500

**Beta**  
L A Y O U T  
**PCB-POOL®**

**get**  
**connected**

pcbpool@betalayout.ie  
<http://www.pcb-pool.com>



**FAX**  
on-Demand  
66515

**EURO**  
File-Transfer  
66520

**analog**  
BBS  
66516

**isdn**  
BBS  
66518

☎ 00353 65 66500  
FAX 66514

# HT7630 D.C. PIR CONTROLLER

ANDY FLIND

*Taking a constructor's look at Holtek's extremely useful new PIR controller chip.*

THE Holtek HT7630 is a complete PIR (Passive Infra-Red) amplifier and alarm control system contained in a single 16-pin d.i.l. i.c. With a "micro-power" standby current of around 30µA and a supply voltage range of 5V to 12V it is ideally suited to stand-alone battery-powered applications, although its various programmable control options could easily find other uses.

The pin functions for the HT7630 are shown in Fig.1. In broad terms it contains an analogue section consisting of two op.amps and a window comparator, and a digital section to process received signals and provide various control functions. Conveniently, all analogue inputs are on the left-hand side of the device, whilst all but one of the digital ones are on the right.

Intending users of this i.c. should be aware that much of the internal circuitry tends to treat the positive supply rail as "ground" instead of the more usual negative ground rail. This doesn't cause problems in stand-alone battery applications, and there should not be too much

difficulty in adapting it to fit into other systems. However, it should be borne in mind when following the operation of the circuit.

## ANALOGUE SECTION

Starting with the analogue section, this has an internal voltage reference output "V<sub>EE</sub>" which is available from pin 1. A

typical PIR amplifier circuit has high gain at very low frequency and is therefore easily affected by small changes in supply voltage, such as might occur when a battery power supply is called upon to operate a siren or similar warning device.

The effect of these changes can be minimised by careful use of a stable voltage supply for the sensor and amplifier biasing. The "V<sub>EE</sub>" output is nominally 4V, but note that this is a negative voltage with respect to the positive supply rail.

Two op.amps are provided, both having inputs and outputs fully accessible by the user. Those of the first, OP1, are uncommitted but the second, OP2, has a bias voltage applied internally to its non-inverting input and its output is connected to a window comparator stage as shown in Fig.2.

The two amplifiers can be used together with the reference voltage to construct circuits to suit most types of PIR sensor, and the internal comparator senses voltage excursions greater than about 0.25V in either direction as "trigger" signals.

The external circuit shown in Fig.2 was

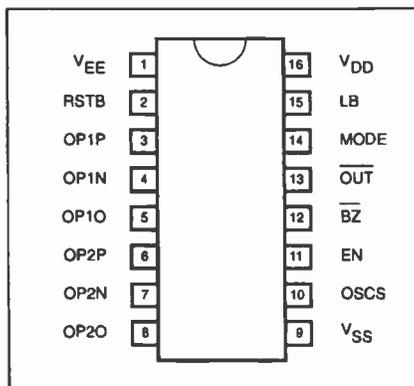


Fig.1. Pin connections for the HT7630.

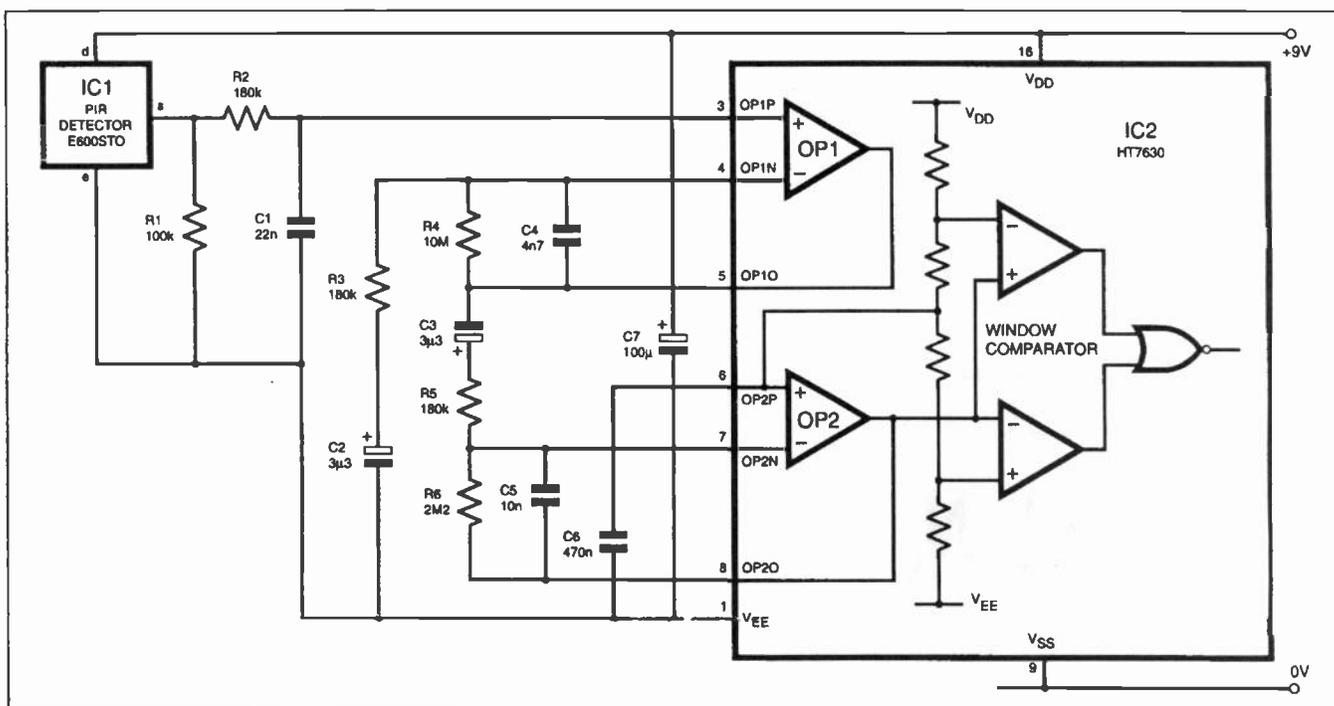


Fig.2. Internal analogue circuit and external input circuit for a PIR Detector.

developed from the author's *Micropower PIR* circuit in *EPE* July-Sept '97, and worked very well in bench tests. Sadly, the output of the internal comparator is not available to the user but goes directly to the control logic provided within the i.c.

The sensitivity of the circuit shown may be altered by adjustment of the value of resistor R6 and tests suggest that this could be doubled before general noise and drift would start generating false alarms. If the value of R6 is changed it is advisable to alter the value of C5 in roughly inverse proportion, e.g. with 4M7 for R6, C5 should be 4n7 or 5n6.

## VALIDITY CHECKING

Before moving on to the control logic section of the device it is worth looking at the way input signals are interpreted for validity. Three types of signal will trigger the output. The first is simply three pulses from the comparator within two seconds. The second is two pulses where one continues for longer than 160ms and the third is a single pulse exceeding 340ms.

These timings assume a system clock of 8kHz, which will be described shortly. This combination is intended to eliminate most false triggering signals but its effectiveness will depend upon factors such as the type and position of the sensor.

The control logic offers some interesting functions and is easily programmed through simple pin connections. Readers wishing to experiment with the device might like to construct a "breadboard" version of the circuit shown in Fig.3, which will allow a "feel" for the various functions to be obtained without the complication of actually triggering it through a PIR circuit.

To provide trigger signals, OP2 is connected so that when the input to R2 is touched against either supply rail the comparator will give an output.

## DIGITAL LOGIC

Moving to the logic side of the device, the first requirement is the system clock, which is set by resistor R4 and capacitor C2. The value of R4 given by the data sheet is 910k for a clock frequency of 8kHz but in practice the circuit works happily with the 1M shown. Note that other frequencies and timings described here all depend upon a correct clock frequency.

The next essential for circuit operation is a connection to the low supply voltage detection input LB, pin 15. If this function is not required it may be disabled by connecting pin 15 to V<sub>SS</sub>, but with the two resistors R5 and R6 as shown it will detect supply voltages below about 6.8V. Other voltages can be programmed by selection of suitable resistor values using the formula  $V_{inip} = 1.45 \times (R5 + R6)/R5$ .

A 100nF capacitor, C1, is connected between the reset input, RSTB, pin 2, and the reference output V<sub>EE</sub>. Input RSTB is active when pulled low, so this capacitor helps to ensure reliable start-up. During operation, RSTB settles to the supply voltage V<sub>DD</sub>. If it is required to reset the device without switching off, this may be achieved by connecting it momentarily to V<sub>EE</sub>, or through R1 to either V<sub>EE</sub> or V<sub>SS</sub>. It should *not* be connected directly to V<sub>SS</sub> as this results in heavy current flow, which may cause damage.

Status indication is provided from the BZ output at pin 12. Signals from this pin consist of a burst of negative-going pulses with a frequency of 4kHz, which can drive an l.e.d. or a piezo buzzer or both, as shown. The buzzer should be of the simple type containing just the piezo element, not the variety with a built-in oscillator intended for d.c. operations.

## WARMING UP

When first powered up, the i.c. provides a warm-up period of about 40 seconds. This is intended to allow the PIR circuit to settle, but will obviously also allow time for the user to leave the detection area after arming the device. For most of this period, the status output will give single output pulses at intervals of 1.5 seconds, but for the last eight seconds the output pulses will be in groups of four, indicating that active operation is imminent.

During the warm-up period, the i.c. checks for a low supply voltage condition. If this is detected a series of eight rapid pulses is given from output BZ and operation halts. Otherwise, following the warm-up period the system should become operational. Each valid trigger input will now result in four rapid pulses from output BZ, and with Mode and Enable (pins 14 and 11) wired to positive supply as shown, there should be a four-second output from the OUT connection, pin 13.

The latter is an open-drain output which can sink but not source current. If it is interfaced to a logic input it may require a pull-up resistor. Maximum load is about 12mA, so most sirens or similar output devices will require a current-boosting stage of some kind.

The Enable input, pin 11, enables operation of the main output when high (positive). If it is taken low (negative) it will disable this output, although the rest of the system will continue to operate as before.

## OPERATING MODES

Two modes of operation are possible, selectable with the Mode input pin 14. If this is made positive as shown in Fig.3

(connection of V<sub>DD</sub>), the i.c. will be in Doorbell mode. A valid trigger input will result in a four-second output, following which the system returns to the Ready state.

If Mode is made negative (connected to V<sub>SS</sub>), the mode will change to Alarm. Triggered outputs will now last for 32 seconds, and in addition the status output, BZ, will pulse every three seconds until the system is manually reset to indicate that an alarm has taken place.

For initial experimenting and testing it is suggested that Mode is set to Doorbell.

## PRACTICAL USES

There should be a host of applications for this i.c. From automatic doorbells to personal property protection systems, to alarms for garages and garden sheds where mains power is not available, possible uses seem endless. The logic section could be used by itself as part of a larger system, as it would be simpler (and cheaper) than a processor or a board full of timing logic.

For more sophisticated processing of trigger signals an output could be taken from BZ with the device in Doorbell mode. Sensors other than PIR detectors might be used, employing the two op.amps in the i.c. for any analogue functions.

The micropower supply requirements make long-term battery operation possible with circuits using HT7630 running for months or even years from an alkaline PP3 or a pack of AA cells.

## ENJOY IT!

Finally, this i.c. is fun to play with! Using just a handful of external parts the experimenter can have it beeping away and flashing l.e.d.s in no time as it goes through its warm-up and detection routines, and with very little extra effort it can be operating as a very sensitive PIR detector unit.

For those of us who enjoy this side of the hobby it's well worth investing in one for the entertainment value alone.

The HT7630 is available from Maplin, whose code is JA43W.

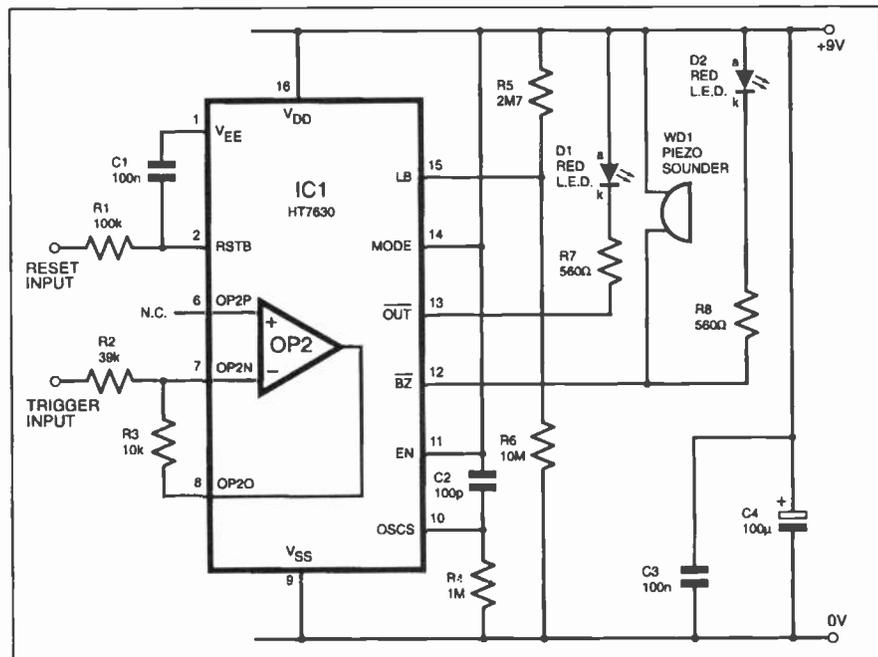


Fig.3. Experimenter's circuit for the HT7630 chip.

# THE PARTS GALLERY + ELECTRONIC CIRCUITS AND COMPONENTS

by **MIKE TOOLEY** Brooklands  
College of Further and Higher Education

**TWO  
APPLICATIONS  
ON ONE  
CD-ROM**

**HOBBYIST/STUDENT  
CD-ROM**  
£34 including VAT  
(UK post free)

**INSTITUTIONAL LICENCE  
CD-ROM**  
(Schools/HE/FE/Industry)  
£89 plus VAT  
(UK post free)

**INSTITUTIONAL  
10 USER CD-ROM**  
(10 user network licence)  
£169 plus VAT  
(UK post free)



**FREE DEMO** from Web site – <http://www.MatrixMultimedia.co.uk>

Many students have a good understanding of electronic theory, but still have difficulty in recognising the vast number of different types and makes of electronic components. The **Parts Gallery** has been designed to help overcome this problem; it will enable students to recognise common electronic components and their corresponding symbols in circuit diagrams.

This CD-ROM also incorporates component and symbol quizzes so that students can test their knowledge.

- ★ Over 150 component and circuit photographs
- ★ 100's of electronic symbols
- ★ Self-test component and symbol quizzes

All text shown on each page is also spoken. Suitable for hobbyists, trainees and students. Covers Design and Technology: Key Stage 4 Electronics GCSE, Key Stage 3 Science. GNVQ Electronics Key Stage 4. Intermediate BTEC Electronics.

Minimum system requirements: PC with 486/25MHz, VGA + 256 colours, CD-ROM drive, 8MB RAM, 8MB hard disk space. Windows 3.1, DOS 3.1, mouse, sound card.

**Electronic Circuits and Components** provides a sound introduction to the principles and application of the most common types of electronic components and how they are used to form complete circuits. Sections on the disc include: fundamental electronic theory, active components, passive components, analogue circuits and digital circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding of each section on the CD-ROM.

- ★ Virtual laboratories
- ★ Full audio commentary
- ★ Over 20 links to pre-designed Electronics Workbench circuits

## CD-ROM ORDER FORM

Please send me **The Parts Gallery + Electronic Circuits and Components** on CD-ROM

Full name: .....

Address: .....

.....

..... Post code: ..... Tel. No: .....

.....

Signature: .....

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £.....

Please charge my Visa/Mastercard: £ ..... Card expiry date: .....

Card No: .....

**ORDERING: Student Version – price includes postage to most countries in the world**  
**EU residents outside the UK add £5 for airmail postage per order**

**OVERSEAS ORDERS: Institutional Licence Versions** – overseas readers add £5 to the basic price of each CD-ROM for airmail postage (do not add VAT unless you live in an EU country, then add 17½% VAT or provide your official VAT registration number).

**Send your order to: Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)**


Direct Book Service is a division of Wimborne Publishing Ltd. To order by phone ring 01202 881749. Fax: 01202 841692

We cannot reply to overseas orders by Fax. CD-ROMs are normally sent within seven days

## EPE VIRTUAL SCOPE

### Part 2

### JOHN BECKER

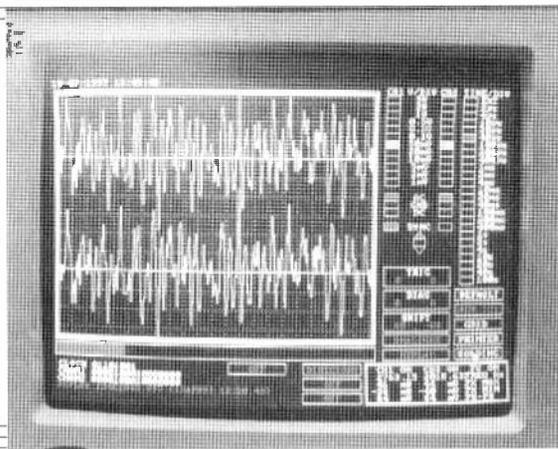

*Dramatically improve your workshop facilities with this flexible computer-controlled dual-trace oscilloscope simulator.*

**L**AST month we made the statement "any computer with a screen display can be used as an oscilloscope, provided the right interfaces are used with it". We then proceeded to give all the circuits and components lists to make this possible, at least with most PCs.

We conclude this month with the constructional details for the Digital and Analogue circuit boards, setting-up and use.

### CONSTRUCTION

Details of the Digital Control printed circuit board (p.c.b.) component layout, together with the full size copper foil master, are shown in Fig.8 and those for the Analogue p.c.b. are given in Fig.9. Both boards are available from the *EPE PCB Service*, codes 176 (Digital) and 177 (Analogue), respectively.

Two copies of the analogue p.c.b. are needed for the full dual channel system. Only one digital board is needed irrespective of whether you are building the single or dual channel version.

### SCREENING PLATE

Before assembling the p.c.b.s, cut a sheet of copper-clad fibreglass to the same size as the digital p.c.b. This will serve as a screen between this board and the analogue boards, and also provide a mounting platform for the latter. A sheet of aluminium may be used instead.

With all the p.c.b.s, drill out to size (typically 4mm) the holes into which the p.c.b. supports will be pushed, and those for the bolt holes of sockets SK1 and SK2. Four 4mm holes should also be drilled into the screening plate in line with the four corner holes of the digital p.c.b. – use the latter as a template.

The holes for voltage regulator IC27 should be drilled out to 1.3mm, and those for all the terminal pins to 1.0mm. It may also be necessary to drill out to 1.0mm the pin holes for SK1 and SK2.

When enlarging any of the p.c.b. holes, use a drill bit of the correct size – trying to use "bodge" techniques will damage the copper track and pad adhesion on the p.c.b.

Numerous wire links are required by the p.c.b.s. These should be made the *first* assembly task. Use 24s.w.g. tinned annealed copper wire for the links – it is available on small bobbins from a variety of sources. You won't need the whole bobbin, but a roll of this wire is invaluable to have in the workshop.

Don't waste your time by trying to use ordinary stranded connecting wire; individual strands are too thin for convenience and stripping off the plastic sheathing is tedious.


Note that many link wires will end up under the dual-in-line (d.i.l.) socket positions. The links should be neatly bent to shape using thin-nosed pliers.

Next insert all the d.i.l. sockets – do not solder the d.i.l. chips into the board. Then assemble the remaining components in ascending order of size, observing their polarities as appropriate.


The analogue board has been designed to accept multi-turn or single turn presets. The latter are cheaper but less precise in their adjustment – let your wallet dictate your choice!

Insert sockets SK1 and SK2, bolt them to the board and tighten down the nuts *before* soldering their pins. Solder 1mm terminal pins into all the remaining holes.

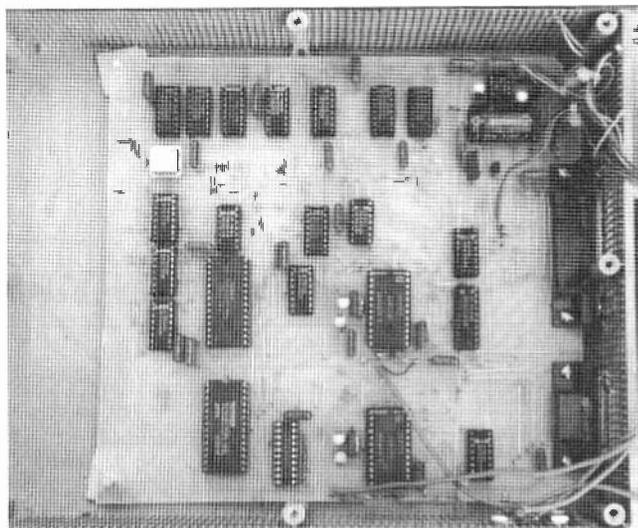Thoroughly check all soldered joints with a close-up magnifying glass, and recheck that all components are correctly inserted.



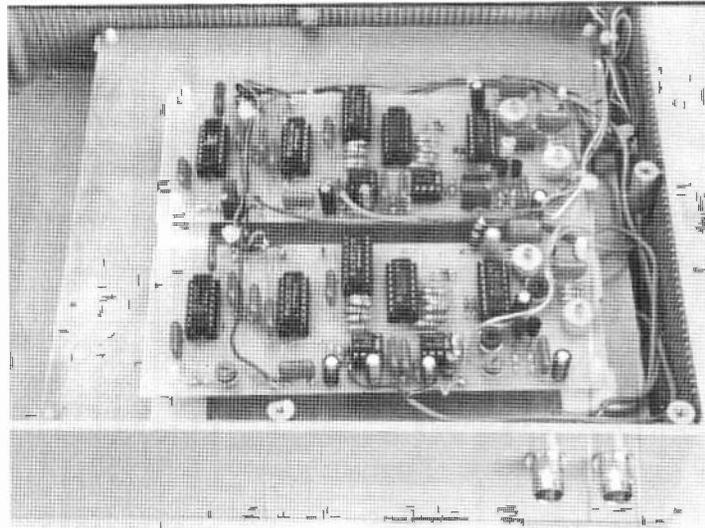The digital circuit board is mounted on the case base via self-adhesive plastic supports.



Stacking pillars are used to attach the "screening plate" between the digital and analogue boards.


## CASE PREPARATION

Temporarily remove the bolts from SK1 and SK2. Push the self-adhesive feet (supports) into all the p.c.b.s but leave their protective film in position for the moment. Push the four stacking pillars into the lower side of the screening plate (copper face upwards), and loosely onto the tops of the supports for the digital board.


Cut (or file) horizontal slots in the two central pillars (long side) of the case so that the digital board and the screening plate can fit inside. Having done so, the case now needs to be drilled for the sockets.

With the digital board and screening plate in position, mark and cut out slots so that SK1 and SK2 protrude to the exterior. Check that the connectors fit into the sockets from outside. You may need to slightly file off the corners of the p.c.b. and screening plate.

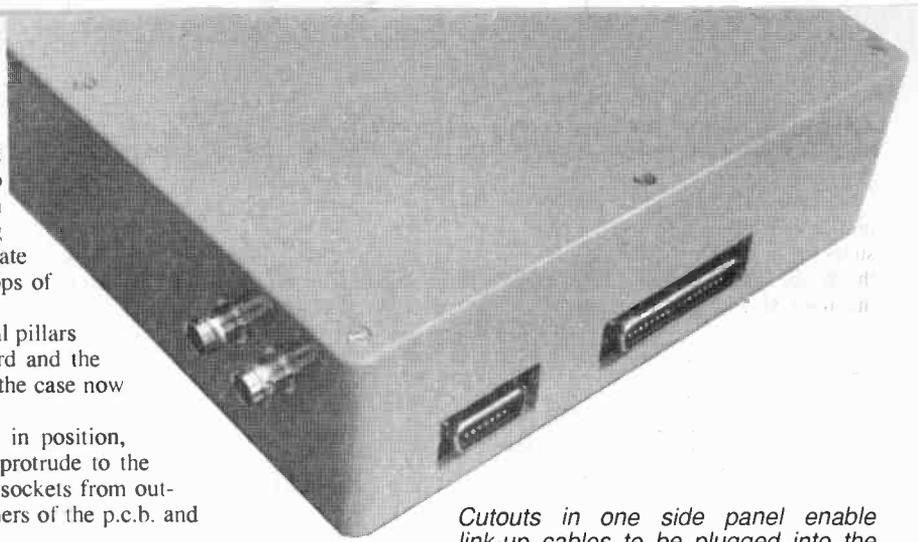Remove the screening plate and reposition the p.c.b. with SK1 and SK2 protruding correctly. Mark and drill holes through the base



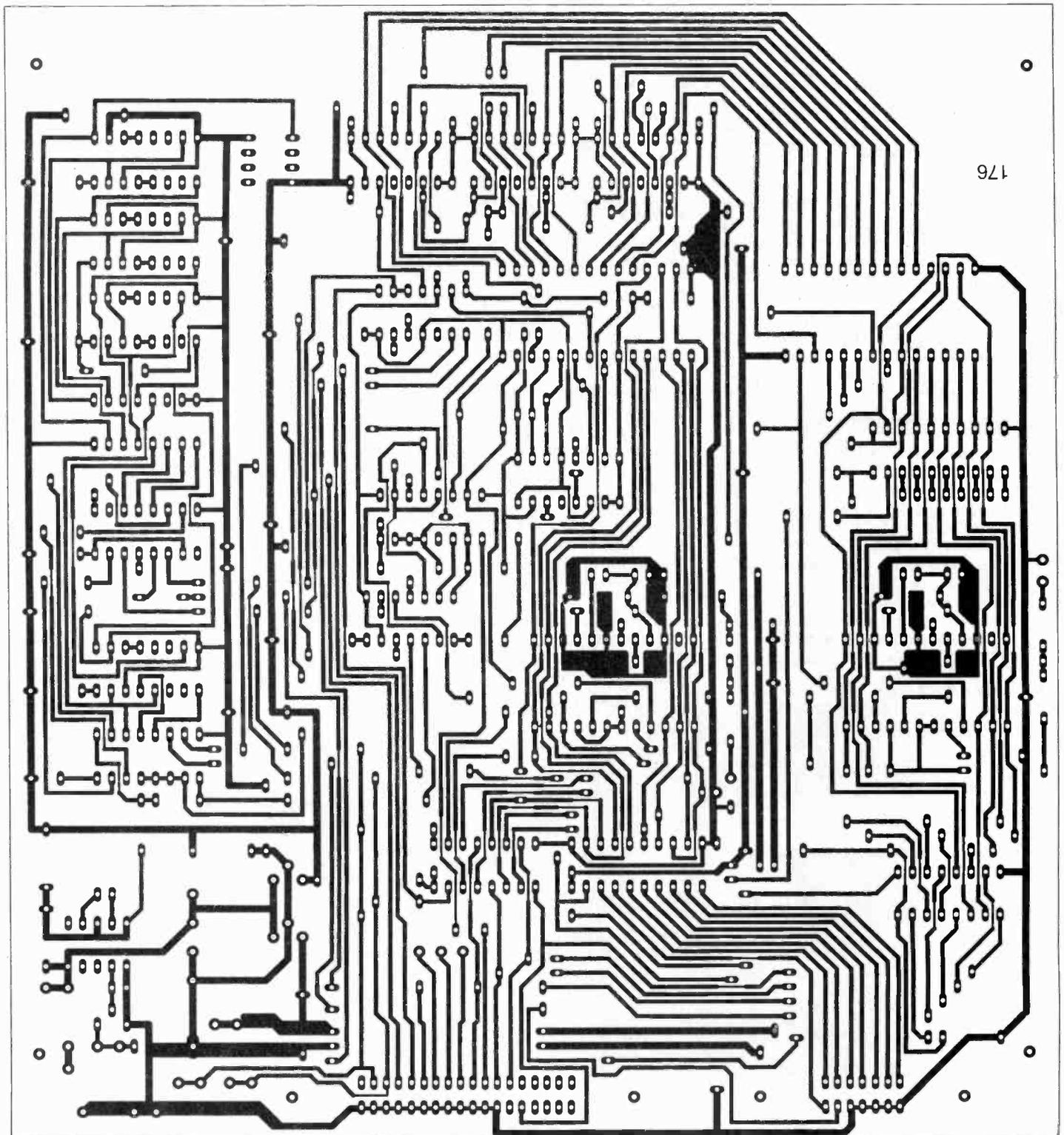*Cutouts in one side panel enable link-up cables to be plugged into the connectors.*



of the case in line with the downwards bolt holes of SK1 and SK2. Now cut these holes into slots lengthwise along the case floor.

Re-bolt SK1 and SK2, add additional nuts to each bolt so that they and the p.c.b. supports sit evenly on the case floor. Refit the p.c.b. with the bolts passing through the floor slots. Slide it into position and

secure nuts to the bolts (with grip-washers) to hold the p.c.b. securely in place.

When bolting down, ensure that the spacer nuts prevent the p.c.b. from buckling when the external nuts are fully tightened.

Sockets SK3, SK4, SK102 and SK103 can be mounted where you prefer, but take care that their position will allow the

digital board and screening plate to be removed if necessary. Sockets SK3 and SK103 are seen in the photographs; the author did not use SK4 and SK102.

Peel off the protective film from the feet of the self-adhesive supports for the analogue p.c.b.s. and carefully position both these boards on top of the screening plate (see photograph).

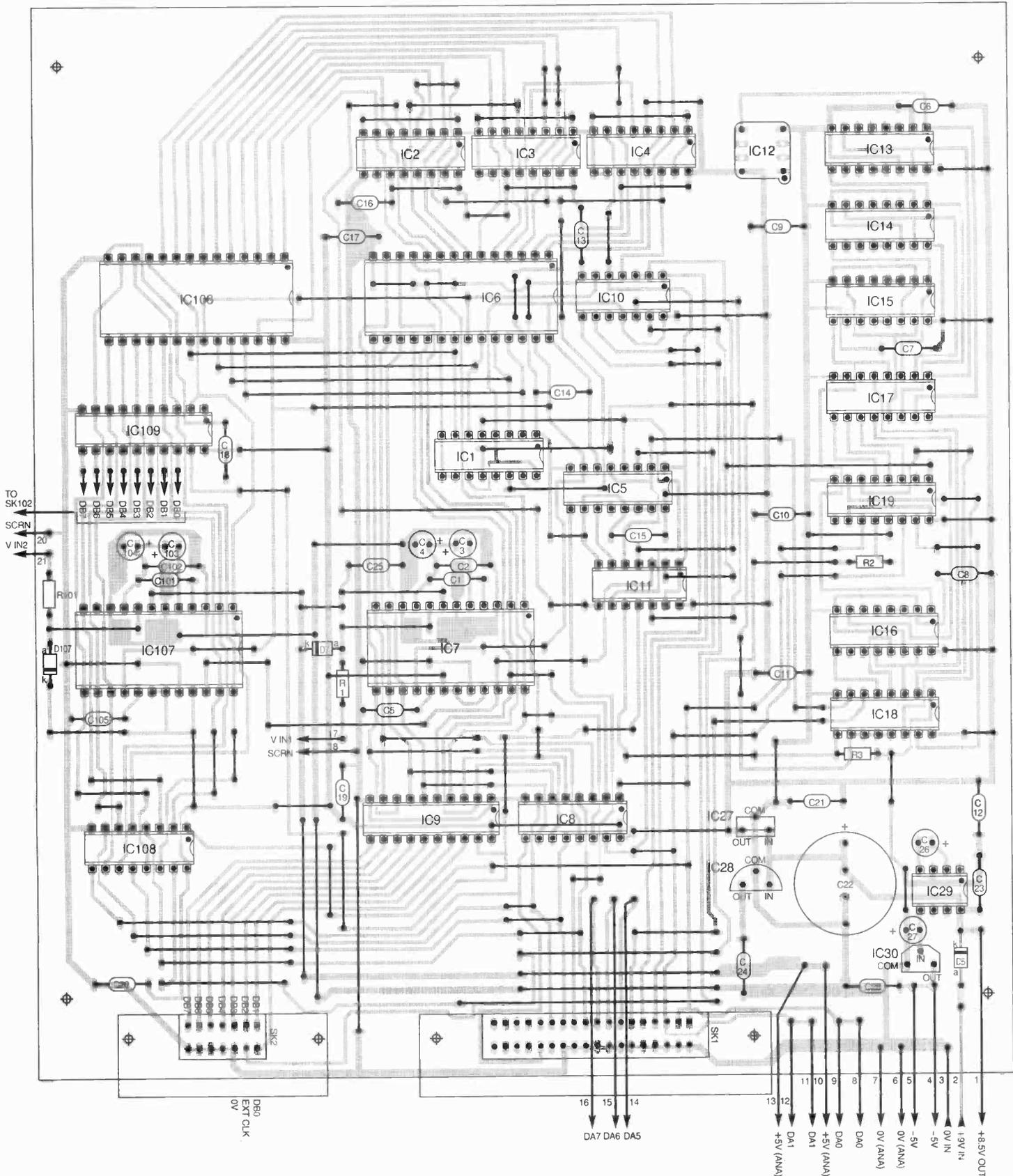


Fig.8. Digital printed circuit board component layout and (left) underside copper foil master pattern.

## INTERWIRING

Remove the entire p.c.b. and screening plate assembly from the case and wire-up between the boards as detailed in Fig.10. Screened wire is required for the four analogue signal connections but normal stranded wire (plastic sheathed 7/0.2mm) can be used for all other connections.

It is preferable to keep the shift register connecting wires in a separate harness, held neatly by cable ties. These connections are numbered 9, 10, 11, 15 and 29 to 32.


Power supply lines should also be neatly harnessed (connections 1, 4, 6, 22, 23, 26). Solder the required 0V connection to the screening plate (via a bolted solder tag if the plate is aluminium).

Keep all connections reasonably short but allow for the boards to be turned over for access to the track side if necessary.

Return the p.c.b. assembly to the case and complete the wiring to sockets SK3, SK102, SK103 and SK4. Neatly harness the SK102 connections.

DO NOT combine the separate wiring harnesses into one larger harness.

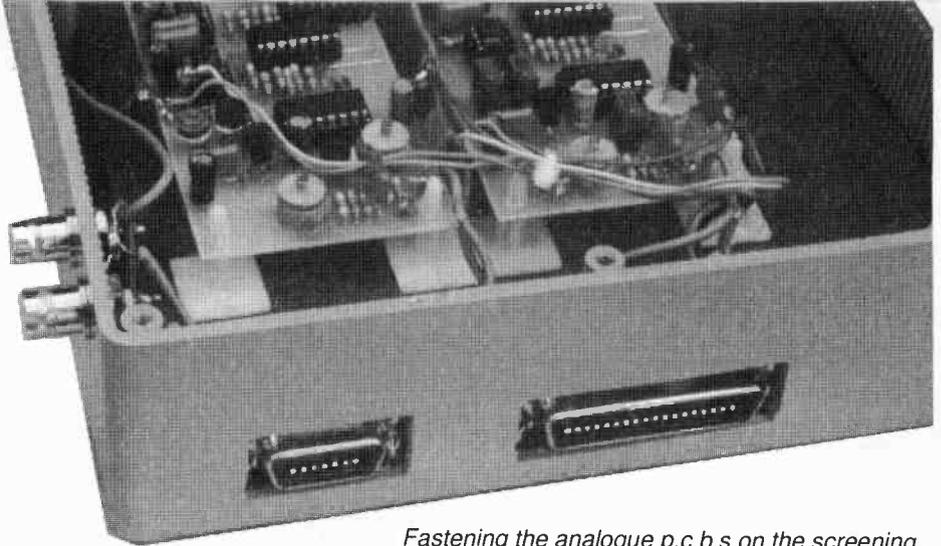Now make up the external connectors for the digital input sockets. Use coloured ribbon cable of about one metre in length. Carefully solder the cable to the required



Fastening the analogue p.c.b.s on the screening plate is achieved by using self-adhesive stand-off pillars. The BNC analogue signal sockets can be seen on the left.

connector pins, in colour coded order, i.e. black to DB0, brown to DB1, red to DB2 etc.

Connector SK102 does need the external clock input pin to be connected.

## CHECKING OUT

It is imperative that the power supply is checked out first of all. Insert IC29 but do not insert any of the other d.i.l. chips.

During overall checking, always switch off the power *before* making any corrections or inserting chips. All chips should be regarded as static-sensitive and treated accordingly – touch an earthed item before handling them.

Connect the unit to a 9V d.c. supply. Check the voltages stated alongside the p.c.b. wiring connection pins as shown in Fig.8 and Fig.9. Also check that +5V

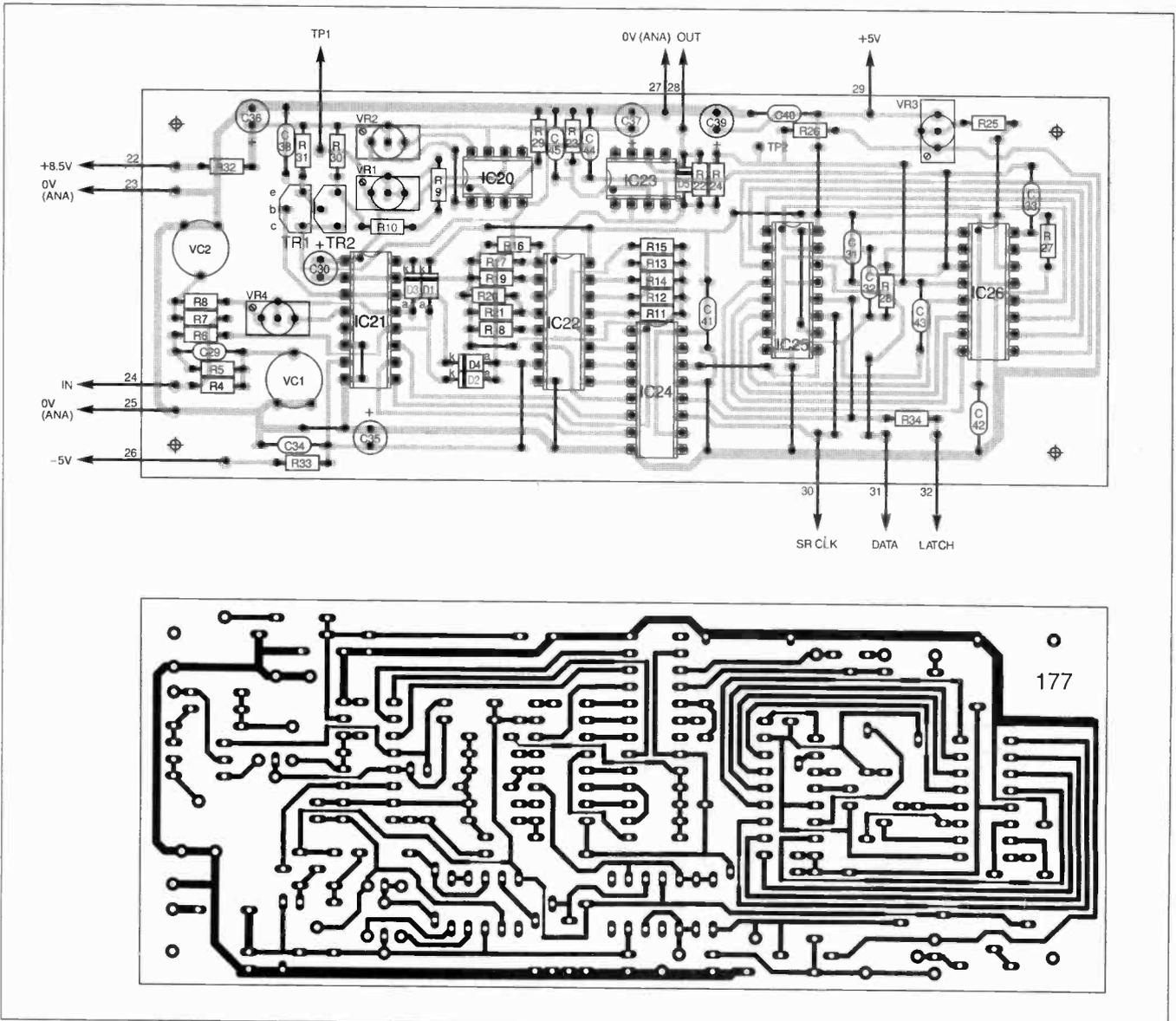


Fig.9. Printed circuit board and full size copper master pattern for one channel of the analogue section.


exists at the OUT pin of IC27. The value of 8.5V at pin 1 might be a bit lower, but the others should be almost identical to the voltages stated.

Insert the remaining chips and again check the voltages.
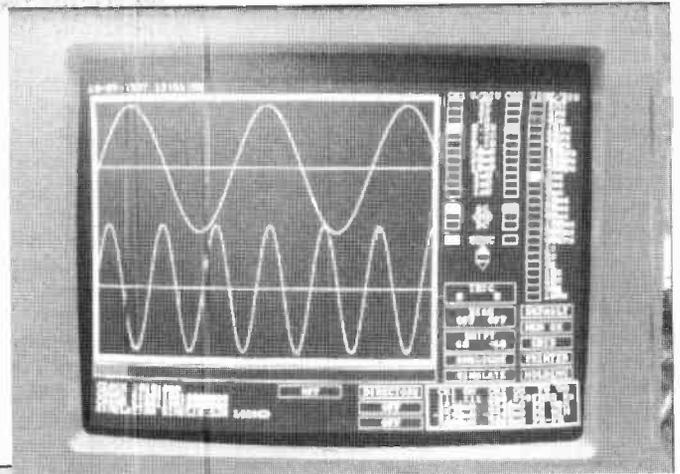
## DISPLAY FUNCTIONS

Connect the unit to the computer, switch on and then load and run the program. The software will start running with all parameters set to default values. *Until setting-up has been done, DO NOT click the mouse on any box unless you are told to.* (See also the DEFAULT paragraphs later.)

The horizontal box below the display area should show a short light-blue bargraph fractionally changing length as various samples are read from the unit. The rate of change will be entirely dependent on the speed at which the computer is running. The maximum bargraph length reflects the amount of interface unit memory space in use.



*Twin sine waves at different frequencies. Note the functional details in the boxes.*

Two other screen boxes should show that AC mode is selected for both analogue channels (the boxes being coloured yellow). Channel 1 is the left hand column of that section (CH1), Channel 2 its right hand column (CH2). Click the mouse on the two GND boxes; the boxes should turn yellow, and the AC boxes become clear (background-blue).

The far right hand column of boxes (TIME/DIV) is for selecting the sampling rate. The rate should be seen as 400µs per division.

## ANALOGUE ALIGNMENT

Allow a few minutes for the unit to stabilise its running temperature. Then, with each analogue channel and using a multimeter on a range suitable to read +5V d.c., adjust preset VR2 until IC20 pin 6 has an output voltage as near to 0V as you can set it. Switch to a lower range for the final stages.

If you are using multiturn presets, you may find that it takes several turns before any response is noted. When clicks are heard from the preset, you have reached the end of its wiper travel.


Plug in the scope probes to sockets SK3 and SK103. They should be set to  $\times 1$  attenuation, using their  $\times 1/\times 10$  switch. Note that probes without attenuation switches are likely to have  $\times 10$  attenuation built in, consequently the screen display will appear to be ten times less than that expected.

Clip each probe's screening connection clip to the tip of the probe, thereby grounding the tip and its input to the unit. Click the mouse on DC for both channels and check that IC20 pin 6 is at the same 0V level. The accuracy of the 0V setting determines the unit's relative response to d.c. inputs (although some compensation is available via the software).

## TRUE LINE-UP

Click both GNDs back on and observe the screen. Taking one channel at a time, establish which white horizontal lines in the display area are associated with which control box.

Now left-click on the TRIG box (its appropriate left or right numerical portion – zero at present) and, while still holding down the mouse button, press any

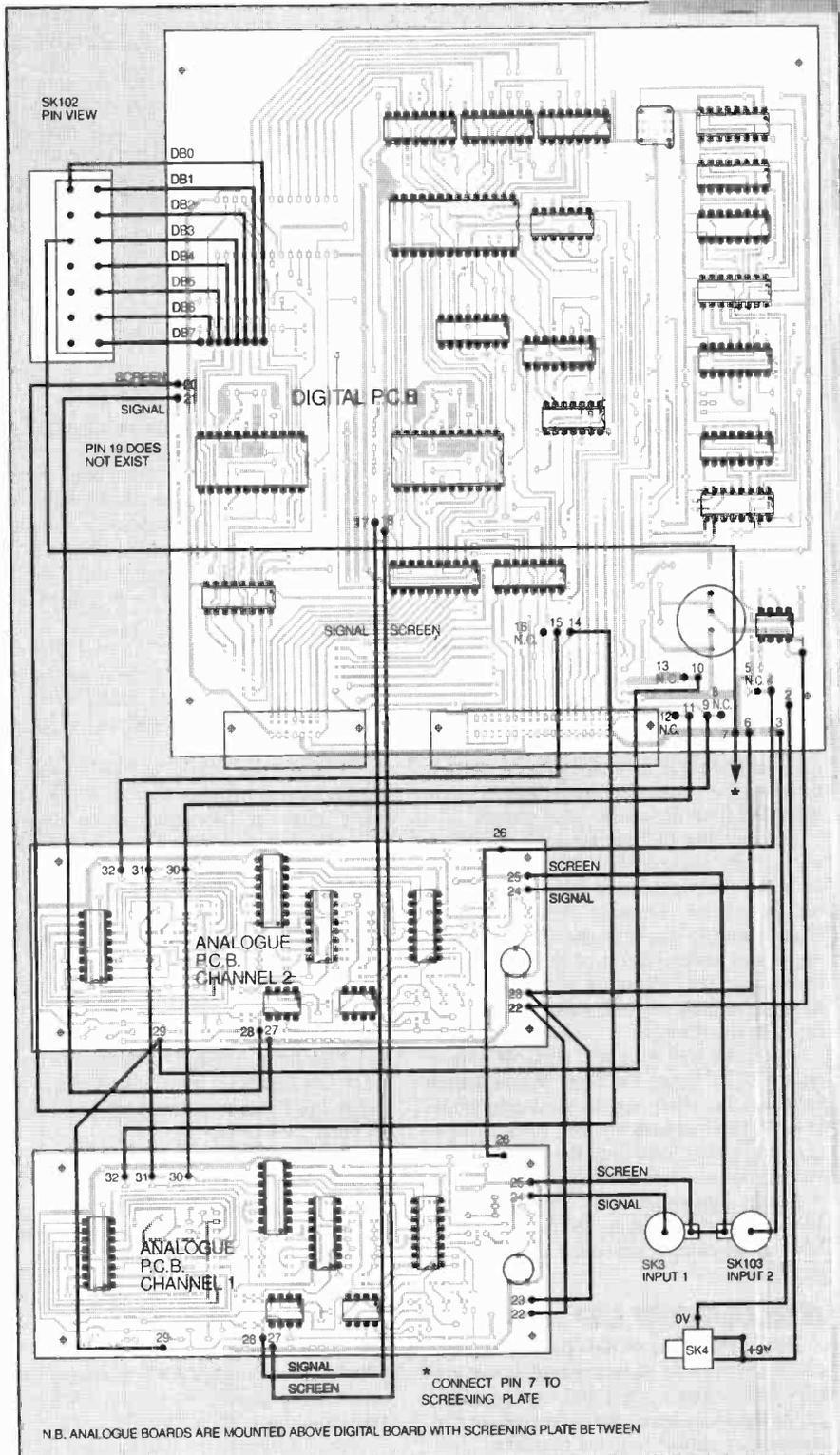

*Fig.10. Interwiring details between the digital and analogue boards and off-board connectors.*

keyboard key. One of the lines in the upper half of the screen should shift upwards and become apparent as a dotted line, revealing a continuous white line when doing so.

The dotted line is the one that shows the voltage level at which sync is triggered when Sync mode is on (it's off at the moment). It is only a software control and does not affect the unit itself.

The continuous line that has been revealed shows the 0V reference position for that channel. This is the position on the screen to which the signal display line for that channel has to be shifted by using the bias-setting preset VR3 (V-REF).

The value in the TRIG box will be seen to be incrementing from zero upwards while the mouse is clicked and a key pressed.

Changing to the mouse righthand button and with the key still pressed, allow the line to return to its start position at zero. It will descend below zero if the button and key remain pressed.

Adjust VR3 and watch for another (continuous) white line to start moving on the screen. Again, it may take some time before any movement becomes apparent. Move this line until it coincides with the dotted TRIG line (and the other continuous line); this is the required position for 0V.

While pressing a key, alternate between pressing each mouse button with the cursor on the BIAS box numeral area, to check that the newly set line can be shifted up and down the screen. The value associated with the BIAS box should change from zero and increment or decrement accordingly. Return the box value to zero.

## SHIFT CONTROL

The SHIFT control can now be checked. This is purely a software control and does not affect the electronics of the unit. Periodically alternating between left and right mouse buttons, click the mouse on the number in the appropriate box while pressing a key. All three lines (0V REF, BIAS and TRIG) for this channel should be seen to shift together, appearing to be just one line moving.

You can also check that the lines move together in harmony by first changing the TRIG line position.

The default value for the SHIFT control is 60 for Channel 1 and -60 for Channel 2. This is purely for visual convenience so that the two signal traces can normally be observed at different parts of the screen. When direct comparison between two signals is required, the two waveforms can be shifted to coincide.

If you haven't already spotted it, each click on a mouse button increases or decreases a box's numerical value by one - useful for fine correction of settings.

You might also have noticed that three text lines at the bottom left of the screen may change their binary values when some functions are changed. These are the control codes that are output to the three shift registers. They may be helpful if you have to trouble-shoot the assembly. The same bit values should occur in order on the output pins of the relevant registers.

## GAIN SETTING

Channel gain factors can be optimised using presets VR1 and VR4. First of all set

the unity gain ( $\times 1$ ) accuracy using an a.c. signal as the input.

Note that the gain setting values shown on the screen are in volts per screen grid division. Clicking on the value column changes the units to gain factors as set on the amplifier. The next click reinstates the voltage factors. Set the display for the gain factors. You should see that a gain of  $\times 1$  is indicated (the default value when the program is started).

Ensure that the SHIFT settings are at 60 and -60 respectively.

Connect both probes to the same output of a sine wave signal generator set for about 1kHz at an amplitude of exactly 1.0V peak-to-peak. A digital multimeter set to a suitable a.c. range can be used to precisely monitor the amplitude. A peak-to-peak voltage of a perfect sine wave has an r.m.s. value of 0.353V. Adjust the level control of the sine wave generator until this output value is read on the meter, then disconnect the meter.

Click the mouse on AC for both channels. Two similar sine waves should be seen traversing the screen. The box at the righthand bottom of the screen should be showing the calculated voltage and frequency values for both inputs. Set SYNC on for Channel 1 (see later).

Using preset VR1, adjust the gain of each channel until the peak-to-peak value is shown as 1000mV. The MIN and MAX values should show -500mV and +500mV respectively. (The frequency value should also be shown in the same box.)

Voltage and frequency calculations are performed only when the screen trace reaches the right hand side of the display. Therefore, if your computer is somewhat slow, the values shown may not immediately change with each fractional adjustment of VR1. Be patient!

Also note that since the ADC only has 8-bit resolution, decimal places of a value may not remain static even when the signal level is, and there may be slight disparities between the values for both channels even when fed from the same signal source.

The equality of both waveforms can be checked by using SHIFT for each channel to bring the waveforms into coincidence on the screen. Observe how using the BIAS controls results in the values for the upper and lower aspects of the waveforms (relative to 0V) changing accordingly, although the peak-to-peak value remains essentially the same.

To set the 1/10 accuracy, click the mouse on the 1/10 boxes for both channels and increase the input signal level amplitude to 10V peak-to-peak (3.53V r.m.s.). Now carefully adjust VR4 until the values in the voltage box correspond with this amplitude.


If your signal generator cannot produce a 10V p-p output, estimate the correctness of VR4 in relation to any other known input amplitude.

## SQUARING UP

Due to the nature of the op.amps, the circuit's response to square waves is not totally linear. The leading and trailing edges of the square waves when observed on the screen may appear rounded or peaked. Full correction for this fact cannot be achieved, although it can be minimised using the variable capacitors VC1 and VC2.

Set the signal generator for a square wave output at about 1kHz and 1V peak to peak (neither value is critical). With the channels set for unity gain, adjust VC1 until the best shaped square wave is seen on the screen. Do the same with VC2 when the 1/10 setting is selected for a greater value input square wave.

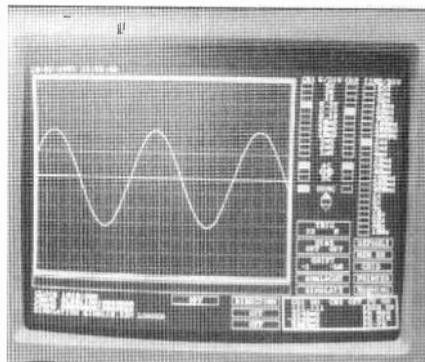It is worth while comparing the appearance of the waveform at different frequencies and choosing the VC1 and VC2 settings which produce the most uniform shape. (You may change the sampling rate via the TIME/DIV column if you wish.)



Single sine wave and grid background. Note the sync trigger line.

## SAMPLING RATE

The sampling rate can be changed via the Rate boxes at the righthand side of the screen, clicking on the chosen one.

Be cautious when interpreting the screen display and calculated frequency factors. It is possible for the sampling and source frequencies to be at the wrong ratio and for harmonic waveforms to be displayed as a result.

This can cause a very fast input frequency to be seen as a slow frequency, because the samples are being taken on closely similar points of the waveform, but at several cycles apart.

Click on the values shown beside the rate selection column: instead of the sampling rates in time per screen division being shown, the values become the sampling frequency in Hertz. Clicking again returns to the time/division values.

## CHANNEL SELECTION

At the bottom right hand side of the screen is the box which displays amplitude and frequency factors. Channel selection is performed via this box. Clicking the Channel 1 column cyclically switches between CH1 ON and CH1 OFF. Similarly, clicking in the Channel 2 column controls CH2 ON and CH2 OFF.

The software does not allow both channels to be switched off together. If you attempt to do so, the other channel will come back on. Channel selection is available in Analogue and Digital modes, but not in Lissajous.

Note that voltage and frequency calculation routines can be inhibited from within the same box by clicking on the FV ON column, revealing FV OFF. Clicking again restores the mode. Waveform plotting is somewhat faster with FV OFF.

Note that frequency is calculated in relation to at least four crossings of the sync trigger value "window" by the waveform. Although the trigger value is shown as a

single line and value on the screen, the "window frame" is set ten sample bits above and below the value (a 20-bit window – just over one vertical grid division's worth). The respective frame value has to be crossed before the trigger value crossing is registered.

This hysteresis (Schmitt trigger principle) makes frequency analysis cleaner in the presence of slightly noisy source signals. If sufficient window crossings are not detected, the frequency value is displayed as zero.

## WAVEFORM SYNC

You will have seen the waveforms shift their relative positions across the screen. As with a normal scope, the waveforms can be synchronised to begin at a set trigger value, stabilising their display. Synchronising can be set for a rising voltage or a falling one; it is a software control and does not affect the interface electronics.

Immediately below the word SYNC is a 3-section box with upwards and downwards triangles. At present, a yellow oblong will be seen between them. This is the OFF position for sync. Change the signal generator back to sine wave mode at a reasonable amplitude and a frequency at which just a few cycles of the waveform are seen.

Click on the upwards pointing triangle. It will change to yellow and both waveforms will appear far more stationary. Using the TRIG control, vary the value in the box for Channel 1. It will be seen that the position at which the waveform starts varies in amplitude.

Next click on the downwards pointing sync triangle and observe how the starting position has changed to the opposite side of the waveform. Now click on the box immediately to the right of the word SYNC. It will become yellow and the equivalent left hand box will clear. Synchronisation is now in relation to CH2, whereas before it was for CH1.

If you have a signal generator which can output two waveforms at different frequencies, couple one frequency into CH1 and the other into CH2. Experiment with different sync source selections, modes and triggering values, observing the results.

As with frequency calculation, a window technique is used for sync detection. It too is 10 bits above and below the sync trigger line. The waveform value has to cross through the window in both directions for a sync point, of either phase, to be recognised.

If a sync point is not found when SYNC is on, the display freezes while the software continues to sample in expectation of finding one. The situation can be remedied by increasing the signal amplitude, either at the input, or via the gain controls. It can also be terminated by clicking SYNC off.

It is not possible to synchronise both channels simultaneously.

Sync can be used in Digital mode but, unlike Analogue mode, a trigger level line is not shown. Consequently, the trigger level must be judged from the value in the TRIG box, or set via Analogue mode before entering Digital mode.

Whilst the sync function is available in

Lissajous mode, its use appears to have little benefit.

## GRID OPTION

The GRID box on the right hand side allows grid lines to be turned on or off. Click on it to see it in operation.

In Analogue mode, the grid boxes are spaced at 20×20 pixel intervals. Horizontally, each box covers 20 sample bytes; vertically it covers 20 sample value bits. The sub-division dots are at 4-pixel intervals.

In Digital mode, only the horizontal grid lines are shown, again at 20-pixel (sample) intervals. The grid is not available in Lissajous mode.

The grid is redrawn in machine code while the signal traces are being drawn. Trace drawing is marginally faster with the grid switched off, especially in Digital mode.

This is because only the screen sections where the digital waveforms need to be plotted have to be changed. These waveforms are of a fixed amplitude and so the screen area immediately above and below them does not need to be cleared.

In Analogue mode, however, the full screen area is available for waveform plotting, therefore the entire area has to be updated for each new screen display.

An additional fixed reference grid is provided in Digital mode. This takes the form of small red rectangles at the sides of the display area and indicates the range of each logic waveform. The top of the box is, of course, logic 1.

## RUN AND HOLD

To the right of the screen is a box in which the yellow word RUNNING is shown. With Sync off and a waveform moving on the screen, click on this box to reveal the words HOLD ON. The waveform will freeze as soon as it reaches the right of the display and the word HOLDING will appear.

No further sampling takes place until you press a key or click the mouse again. Each time you press a key, another trace will traverse the screen and hold. This can continue for as many sweeps as you wish, allowing each display to be examined. The display always advances with time, you cannot step backwards to re-examine a previous display. To exit the Hold mode, click the mouse on the box, whereupon normal running will recommence.

## LISSAJOUS MODE

To examine the Lissajous function, input two sine waves at different frequencies while in normal running mode. Right-click on the box which says ANALOGUE. The word LISSAJOUS will appear and gyrating patterns will be seen. Adjusting the input frequencies so that they are nearly identical, more detail of these patterns will become apparent. (Inputting waveforms of equal frequency and phase will result in a single diagonal line.)


The vertical and horizontal aspects of the waveform can be increased or decreased by changing the channel gain settings. Their relative screen positions cannot be changed. Use the HOLD function to examine the waveform in detail.

As you will probably be aware, Lissajous patterns can be used for phase

relationship analysis (it's beyond the scope of this article to discuss it, though).

To return from LISSAJOUS to ANALOGUE, left-click on LISSAJOUS. Should you inadvertently press the wrong mouse key on this box, DIGITAL mode will be selected. Unless a digital data source is connected to the unit via sockets SK2 and SK103, only garbage waveforms will be shown.

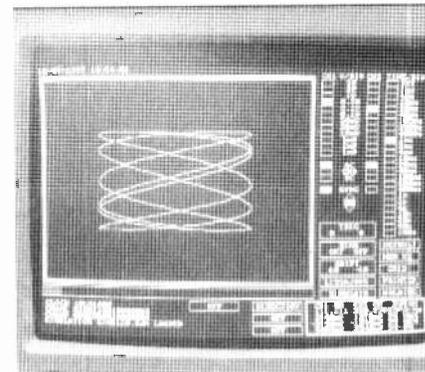To get out of Digital mode, click the mouse button again. The mode selection operates on a repeating cycle of three. The left button clicks "forwards", the right button "backwards".



Displaying a Lissajous figure on screen.

## DIGITAL MODE


To use Digital mode, the "floating" ends of the ribbon cable are connected to the external circuit under examination. This must have the standard digital logic of 0V and 5V.

Do not use digital inputs with any other voltage range; at best the circuit will not respond correctly; at worst the interface chips IC9 and IC109 could die, with possible damage to other parts of the circuit. (There are "level-changing" chips available through which you could externally feed any non-standard logic signals if you need to examine them – the CMOS 4504, for example.)

It is not necessary to use the external clock input facility when in Digital mode. However, an external clock that is synchronous with the digital input will, in the case of rapidly changing input logic, result in cleaner sampling of the data.

Entering Digital mode (as you will have probably already found) is done by left-clicking on the ANALOGUE box so that DIGITAL is shown. Right-click on the same box to return to Analogue mode.

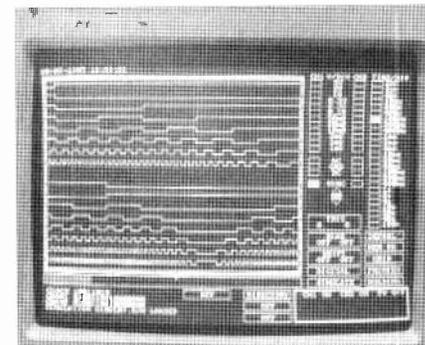As with Analogue mode, either channel can be switched off by clicking on the



Up to 16 digital waveforms can be displayed on the screen.

channel selection box at the bottom right hand side.

## MEMORY SIZE

There are three interface memory size options: MEM 2K, MEM 32K and MEM OFF. Normally, the mouse can be clicked to change to any setting – on another repeating cycle of three, left for “forwards”, right for “backwards”. There are, though, some situations where the memory size is fixed and when the mouse clicks are ignored. In Auto Save mode, for example, the size is fixed at 32K. (In Simulation mode, it's actually set at 8K, for file creation convenience.)

With a 2K memory, less interface memory has to be filled before being input for displaying on screen. The 32K capacity allows a longer continuous block of data to be sampled before being input for screen display.

When MEM OFF is selected, the computer causes the sampling to occur in direct response to individual commands from the computer itself, and in relation to the clock rate selected. Each separate sample taken is immediately plotted on screen. Input signal frequency factors are not calculated in this mode since the sampling rate is essentially unknown.

The advantage of being able to sample without interruption is that the samples are continuous, rather than in blocks.

How fast you can sample in this mode depends on your computer speed; there is a maximum rate limit which you can only find by trying.

Be aware that the display rate affects how fast the waveform crosses the screen. Since there are 440 pixels horizontally, 440 samples are needed to complete the display. A sampling rate of 0.2Hz thus takes a minimum of 2200 seconds for each full display crossing! It will take longer if SYNC is on.

## SAVING DATA

Any Live waveform on the screen can be saved to disk (the Simulation test and Replay waveforms cannot, the program inhibits this). There are two Saving modes, automatic and manually triggered.

At the bottom centre of the screen are four boxes, AUTO SAVE, DIRECTORY, SAVE OFF and WAIT SAVE. Ignore DIRECTORY for the moment.

For manually saving waveforms, click on SAVE OFF. This display changes to SAVE ON. Simultaneously, the memory size defaults to 32K to ensure that the maximum amount of data is saved in each block.

When the next full screen display has been completed, the WAIT SAVE box changes to SAVE NOW. If you wish to save, left-click on SAVE NOW.

This action causes a uniquely-named disk file to be opened with a date and time related name. When Save mode is on, the data is also automatically stored in the computer's memory while being sampled. This 32K block of data is output to the disk immediately after the file has been opened.

Note that it is not a screen dump which is saved, but the actual source data. This allows the data to be subsequently re-input and manipulated on screen.

Having saved the data, the file is closed

automatically and the next sample batch is taken and displayed, followed by the option to save this new 32K block. Even though the samples may be only a few seconds apart, their saved file name remains unique.

(The last statement assumes that your computer will not sample and save at a rate faster than one 32K block per second. The saved file name is only accurate to whole seconds and the computer will overwrite a previous file of the same date/time name.)

If you don't wish to save a particular block, right-click on SAVE NOW, or on any part of the screen except SAVE ON. This causes the next screenful of data to be plotted, followed again by the option to save. To turn off the Save mode, click on SAVE ON, restoring the SAVE OFF message.

Automatic Saving mode is entered by clicking on AUTO SAVE. The latter (normally-white) message changes colour to yellow. Simultaneously, SAVE OFF changes to SAVE ON, WAIT SAVE goes blank and the memory size defaults to 32K.

Now, each time the screen display completes its 32K data block, the data is automatically saved to unique file names again.

To exit AUTO SAVE, click on AUTO SAVE or SAVE ON to revert to SAVE OFF.

Be aware that Auto Save mode can consume a lot of disk space (32K per block). Its use is probably best reserved for short runs of high speed sampling or long runs of slow sampling. Remember to delete disk files (from DOS mode) when they are no longer wanted. The Virtual Scope's directory screen should not be allowed to become full.

## DATA RECALL

To recall disk file data to the screen, left-click on DIRECTORY. The entire screen display now blanks out and displays all the file names having the extension .Y?? (where ?? is any two letters or numbers) in the order in which they are stored on disk. Note that the order is not sorted and depends on where DOS (Disk Operating System) finds the first space available when saving.

Moving the mouse will cause a highlight bar to appear on individual file names. To select one, left-click on it. At the bottom of the screen a text line asks if this is the file you want to load, quoting its name and concluding with y/n.

In answer for yes, you can either press keyboard letter Y, or just left-click the mouse. For no press N or right-click the mouse. (Key letters may be in caps or lower case.)

If yes is the answer, the file is loaded and the full normal screen display is resumed with the loaded file being played back as screen waveforms. If no is the answer, again the full normal screen resumes, but still showing the previous waveform before the directory was entered.

When a directory file is loaded, on return to the normal screen, various boxes will now be seen to be coloured red, and LIVE to now read REPLAY. The red settings are the ones that existed when the file was recorded. You may change some

of the settings, such as gain and sync, but not memory size or rate.

When settings are changed, the new setting is coloured yellow. There is no facility for returning to the recorded settings once they have been changed, other than by reloading the same file via the directory.

Both screen modes show the name of the file currently loaded, both as its coded name and as the expanded translation. The directory listing itself, though, is only shown as the coded name.

## FILE NAME CODING

Recorded disk file names are coded as indicated by the following example:

File name = 20910241.Y97

Imagine it is split as 20 9 1 02 41 .Y97

Digits 1 and 2 = day of the month (20)

Digit 3 = month number in hex from 1 to C (9 = September)

Digit 4 = hour in hex-fashion – 0 to 9 followed by A to N (0 to 23), in this case 1 = 1 a.m.

Digits 5 and 6 = minutes in decimal (02)

Digits 7 and 8 = seconds in decimal (41)

.Y97 = Year (19)97 (will become .Y00 for the year 2000 – thoroughly Non-Millennium Compliant, sorry!)

The above file name thus translates as 20th September 1997 at 1:02.41 a.m., and would be shown as 20SEP97 1:02.41 if selected.

To exit Directory mode, right-click on DIRECTORY. Immediately all red colours will change to yellow but the currently loaded file will continue to be displayed, and REPLAY will change to SIMULATE.

To return to Live sampling mode, click on SIMULATE to restore the word LIVE.

Note that all Save options are inhibited during Directory mode.

## PRINTING DISPLAYS

When the screen display is HOLDING, it can be output to a dot matrix printer (Epson ESC/P2 compatible, 24-pin). This, though, requires the connector cable to be removed from the unit and plugged into the printer.


Having done so, click on PRINTER, whereupon the full screen display is printed, showing not only the waveforms, but also all the function parameters associated with it. The date and time at the top left of the screen is also printed for reference purposes.

Once the print has been completed, reconnect the cable to the unit, and click on DEFAULT as described in the next section.

Do not click on PRINTER if the printer cable is not connected to the printer, or if the printer is not ready to receive data. Doing so will result in a Device Fault error from the computer and a program crash.

You may be able to recover from the crash by ensuring that the cable is plugged into the printer and that the printer is ready to receive data. Then press the Enter key on the screen display word OK. This will reveal the program listing at the point at which the error occurred. Now press function key F5.

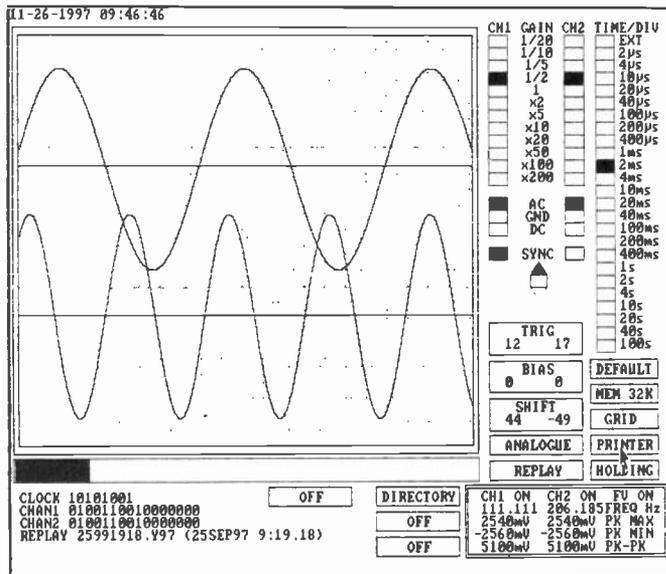If the computer finds that all is well, it will resume the program at the point where it crashed and send screen data to the printer.



Example screen display printout with function selection legends on the right.

Failing that, you will need to fully restart the program using shift-F5.

The data to be printed is collated and formatted by a dedicated routine within the main machine code program. It is then output to the printer from QBasic.

The code is specifically written for outputting bit-image graphics to an Epson-compatible ESC/P2 24-pin printer, using the codes and format detailed in the *Epson ESC/P Reference Manual, August 1991* (obtained from Epson). It is not suitable for other printers.

If your printer is different and you wish to inhibit the PRINTER option, search the QBasic listing for the routine labelled PRINTER: and insert the word RETURN: immediately after the label. Resave the program having done so.

## DEFAULT CONTROL

On the screen righthand side is a DEFAULT box. Clicking on this causes the program to re-output all the current control register settings to the interface, and restart the sampling block from the beginning.

There are two principal situations where this action needs to be taken: after power to the interface has been switched off and on again, and following a screen printout to the printer.

Where the power supply for the unit is used to also power a circuit upon which you are working, you will sometimes need to switch off the power to make a change to the development circuit.

When power is switched back on, the interface configuration settings will need to be re-established. Clicking down on DEFAULT for a couple of seconds will usually achieve this.

For reasons unknown, however, the author has found on rare occasions that this fails to happen. Should it do so, the program should be halted (brought back into QBasic edit mode) by using the CTRL and BREAK keys together, and then re-run using shift-F5 (instead of just pressing F5).

Also, when first powering up and running, the use of DEFAULT has occasionally been found necessary.

The word DEFAULT changes colour to purple when the mouse is clicked on it, letting you know that it is responding. The

white returns when the mouse button is released.

You may press DEFAULT any time you wish the interface sampling to restart.

## EXTERNAL CLOCK

At the top of the rate selection column is a box marked EXT CLK. An external clock having an amplitude swing of 0V/+5V can be connected via socket SK2/PL2. This amplitude requirement must be respected – do not use any other level. To select EXT CLK, click on it. Clicking on any other rate box will restore the system to internal clock use at the rate selected.

The external clock may be used in Analogue or Digital modes (also see the Digital mode paragraphs). Note that when using an external clock in Analogue mode, frequency calculations are not performed because the software does not know the clock rate.


## MOUSE SOFTWARE

Many readers may have previously wondered how the mouse can be used when running QBasic programs. The Virtual Scope software illustrates one way in which it can be done.

You cannot control it *directly* from QBasic (so far as the author can establish), but you can do so via a simple machine code program. This writes control data to the mouse registers and reads back position and button press data, storing it in locations which are readable from QBasic. It also causes the cursor to be shown as an arrow.

On return to QBasic from the machine code, the parameter data can then be acted on accordingly. A similar technique is used to transfer data from QBasic to the machine code.

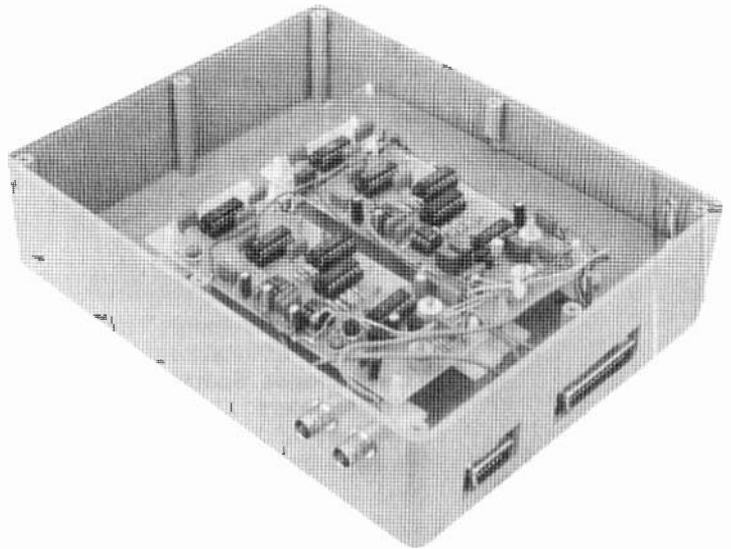The information for mouse control was found in the *The Programmer's PC Cookbook*, Second Edition (1991), Thom Hogan, Microsoft Press, ISBN 1-55615-321-X. Starting at page 5-40, the relevant section is 5.066 INT 33H, Mouse Functions Summary.



You will find the book full of essential information on PC register use – ask your PC dealer or local library about it.

To see how the information was used for the Virtual Scope, refer to the EPE software disk and examine text file VSCOPEMS.J via a text editor, e.g. the EDIT program accessible from DOS. Also study the QBasic listing, searching for any reference to *mouse*. (The text for the main control program is VSCOPE.DG.J.) Program MOUSE01.BAS also shows mouse control.

## USING A SCOPE

It is not possible to discuss the general use of oscilloscopes here. You are, though, recommended to obtain books on the subject, from the *Direct Book Service* for example (as advertised in EPE as part of our service). We also published Roy Bebbington's articles on scope use, *More Scope for Good Measurements*, EPE June and July '96 – see the *Back Issues* page.

An oscilloscope really opens up a large window on the world of electronics. If you feel competent to take on the construction of this (admittedly) complex design, we are sure you will find its use to be an eye-opener! Even if you have a scope already, the *EPE Virtual Scope* will be a useful addition to the workshop. □


## PLEASE NOTE

Fig.2, page 57 last month. The pin numbering of the lead-off leads above SK1 should read as follows, top to bottom: IC108 pin 1, 4, 12, 7 and 9.


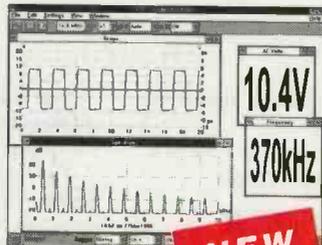
# 'Pico's Virtual Instrument is the most powerful, flexible test equipment in my lab.'

Pico's virtual instruments emulate the functions of traditional instruments such as **Oscilloscopes, Spectrum Analysers and Multimeters**. Controlled using the standard Windows interface, the software is easy to use with full on line help.



**NEW**  
100 MS/s

## ADC-200

### Dual Channel High Speed

- ▼ 100, 50 or 20 MS/s sampling.
- ▼ 50, 25 or 10 MHz spectrum analysis.
- ▼ Advanced trigger modes - capture intermittent one-off events.
- ▼ Less than half the cost of a comparable benchtop scope.

ADC 200-100 £499.00  
ADC 200-50 £399.00  
ADC 200-20 £299.00

Supplied with cables and power supply.



## ADC-100

### Dual Channel 12 bit resolution

The ADC-100 offers both a high sampling rate 100kS/s and a high resolution. Flexible input ranges ( $\pm 50\text{mV}$  to  $\pm 20\text{V}$ ) make the unit ideal for audio, automotive and education use.

ADC-100 with PicoScope software £199.00  
with PicoScope & PicoLog software £219.00

## ADC-40/42

### Single Channel - low cost

- ▼ 20 kS/s sampling.
- ▼ 10 kHz spectrum analysis.
- ▼  $\pm 5\text{V}$  input range.

ADC-40 8 bit resolution £59.00  
ADC-42 12 bit resolution £85.00



Call for free demo disk or download our web site:  
<http://www.picotech.com>

All prices exclusive of VAT.

Broadway House, 149-151 St Neots Rd,  
Hardwick, Cambridge. CB3 7QJ UK  
Tel: (0)1954 211716 Fax: (0)1954 211880  
E-mail: [post@picotech.co.uk](mailto:post@picotech.co.uk)



## DISTANCE LEARNING COURSES in:

Analogue and Digital Electronic Circuits, Fibres & Opto-Electronics Programmable Logic Controllers Mechanics and Mechanisms Mathematics

- Courses to suit *beginners* and those wishing to *update* their knowledge and practical skills
- Courses are delivered as self-contained kits
- No travelling or college attendance
- Learning is at your own pace
- Courses may have BTEC Certification and Tutoring

For information contact:  
NCT Enterprises  
Barnfield Technology Centre  
Enterprise Way, Luton LU3 4BU  
Telephone 01582 569757 • Fax 01582 492928

## RADIOMETRIX TRANSMITTERS, RECEIVERS & TRANSCEIVERS AT LOW PRICES!

### 3V, 5V & 9V TXM Data Transmitter Modules!



TXM-418-A or F Transmitter



SILRX-418-A or F Receiver

### Special Offer Only £29.99 per pair

### World Leading BIM Transceiver @ 84.95 per pair!



BIM-418-F  
Approved to MPT1340

World leading in price, performance and size the BIM high speed transceiver has already found a home around the World in many wire free products from computer networks, hand held terminals to EPOS. Available on 418 and 433.92MHz

- \* 5V Operation, PIC Compatible \*
- \* Exclusive RS232 Version 79.95 \*
- \* Packet Controller Board 79.95 \*
- \* Evaluation Kit + 2 BIM's 149.95 \*
- \* Sold Separately From 1 - 1000 pcs \*



BIM-433-RPC

#### Transmitters

|                        |       |
|------------------------|-------|
| TXM-418-A 0.25mW.....  | 10.99 |
| TXM-433-A 0.25mW.....  | 12.75 |
| TXM-418-F 0.25mW.....  | 12.75 |
| TXM-433-F 0.25mW.....  | 12.75 |
| TXM-403-A 0.25mW.....  | 12.75 |
| TXM-173-4689 1mW.....  | 22.48 |
| TXM-173-4689 10mW..... | 24.48 |
| TXM-184-4689 10mW..... | 29.95 |

#### Antennas

|                       |       |
|-----------------------|-------|
| Helical-173MHz.....   | 4.90  |
| 1/4 Wave 418MHz.....  | 4.90  |
| Dipole 418MHz.....    | 23.50 |
| VHF Whip Antenna..... | 35.00 |

#### Receivers

|                  |       |
|------------------|-------|
| SILRX-418-A..... | 22.48 |
| RXM-418-A.....   | 28.05 |
| SILRX-433-A..... | 22.95 |
| SILRX-403-A..... | 22.48 |
| RXM-403-A.....   | 22.48 |
| SILRX-418-F..... | 22.48 |
| SILRX-433-F..... | 22.45 |
| RXM-173-60.....  | 31.62 |
| RXM-184-60.....  | 31.62 |

Prices unless otherwise stated exclude VAT. Carriage free on all non-account mainland UK orders. Insurance available at additional cost.

Credit Card Payments Welcome. Exports 2/4 day delivery by DHL, UPS or Air Express Available. All prices in Pounds Sterling

Radio - Tech Limited, Overbridge House, Weald Hall Lane,  
Thornwood Common, Epping, Essex CM16 6NB.  
Sales +44 (0) 1992 57 6107 Fax +44 (0) 1992 56 1994  
<http://www.radio-tech.co.uk> e-mail: [sales@radtec.demon.co.uk](mailto:sales@radtec.demon.co.uk)

We can supply back issues of *EPE* by post, many issues from the past five years are available. An index for the last five years is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price.

## DID YOU MISS THESE?

### AUG '96 Photostats Only (see below)

**PROJECTS** ● Component Analyser ● Garden Mole-Ester ● Mono "Cordless" Headphones ● Bike-Speedo ● Mobile Miser.  
**FEATURES** ● Teach-In '96 Part 10 ● Circuit Surgery ● Ingenuity Unlimited ● Spies, Lies and Electronics ● EPT 3.0 Review.

### SEPT '96

**PROJECTS** ● Analogue Delay and Flanger ● Simple Exposure Timer ● PIC-Tock Pendulum Clock ● Draught Detector ● Power Check.  
**FEATURES** ● Circuit Surgery ● Ingenuity Unlimited ● Net Work – The Internet ● MAX038 Waveform Generator.

### OCT '96

**PROJECTS** ● Video Fade-To-White ● Direct Conversion Topband and 80m Receiver ● Vehicle Alert ● 10MHz Function Generator.  
**FEATURES** ● Introduction to Satellite Television ● Ingenuity Unlimited ● Circuit Surgery ● Net Work – The Internet.

### NOV '96

**PROJECTS** ● D.C.-to-D.C. Converters ● Central Heating Controller ● EPE Elysian Theremin, Part 1 ● Tuneable Scratch Filter.  
**FEATURES** ● Build Your Own Projects, Part 1 ● Ingenuity Unlimited ● Circuit Surgery ● Net Work ● Interface.



### DEC '96

**PROJECTS** ● Vari-Colour Christmas Tree Lights ● PIC Digital/Analogue Tachometer ● Stereo Cassette Recorder ● EPE Elysian Theremin, Part 2.  
**FEATURES** ● Build Your Own Projects, Part 2 ● Interface ● Circuit Surgery ● Ingenuity Unlimited ● Net Work – Internet News.

### JAN '97

**PROJECTS** ● Earth Resistivity Meter, Part 1 ● Psycho Rat ● Theremin MIDI/CV Interface, Part 1 ● Mains-Failure Warning.  
**FEATURES** ● Ingenuity Unlimited ● Build Your Own Projects, Part 3 ● Circuit Surgery ● Interface ● Net Work – Internet News ● PCS32 Storage 'Scope Interface Review.

### FEB '97

**PROJECTS** ● Pacific Waves ● How To Use Intelligent L.C.D.s, Part 1 ● PsiCom Experimental Controller ● Earth Resistivity Meter, Part 2 ● Theremin MIDI/CV Interface, Part 2.  
**FEATURES** ● Ingenuity Unlimited ● Build Your Own Projects, Part 4 ● Circuit Surgery ● Interface ● Net Work – Internet News.

### MARCH '97

**PROJECTS** ● Simple Dual-Output TENS Unit ● Video Negative Viewer ● Tri-Colour NiCad Checker ● How To Use Intelligent L.C.D.s – 2 ● Oil Check Reminder.  
**FEATURES** ● Interface ● Ingenuity Unlimited ● Build Your Own Projects, Part 5 ● Digital TV – The Reality ● Circuit Surgery ● Net Work.

### APRIL '97

**PROJECTS** ● 418MHz Remote Control System ● Midi Matrix ● Puppy Puddle Probe ● PIC-Agoras Wheelie Meter – 1.  
**FEATURES** ● Interface ● Ingenuity Unlimited ● Digital TV and MPEG2 ● EDWin NC Software Review ● Circuit Surgery ● Net Work.

### MAY '97

**PROJECTS** ● 2 Metre F.M. Receiver ● EPE PIC-A-Tuner ● Alarm Operated Car Window Winder ● Quasi-Bell Door Alert ● PIC-Agoras – 2.  
**FEATURES** ● Ingenuity Unlimited ● Circuit Surgery ● Techniques – Actually Doing It ● Great Experimenters – 1 ● Type 7660 Voltage Converters ● Net Work.



### JUNE '97

**PROJECTS** ● PIC Digilogue Clock ● Child Minder Protection Zone ● Pyrotechnic Controller ● Narrow Range Thermometer.  
**FEATURES** ● Great Experimenters – 2 ● Circuit Surgery ● Interface ● Reactobot and Virtual Reality ● Ingenuity Unlimited ● Net Work.

### JULY '97

**PROJECTS** ● Micro PESt Scarer ● Karaoke Echo Unit ● Infra-Red Remote Repeater ● Computer Dual User Interface ● Micropower PIR Detector – 1.  
**FEATURES** ● Ingenuity Unlimited ● Techniques – Actually Doing It ● Circuit Surgery ● Great Experimenters – 3 ● Electronics Workbench V5.0 Review ● Net Work.

### AUG. '97

**PROJECTS** ● Variable Bench Power Supply ● PIC-olo Music Maker ● Universal Input Amplifier ● Micropower PIR Detector – 2.  
**FEATURES** ● Interface ● Ingenuity Unlimited ● Colossus Recreated ● Circuit Surgery ● Great Experimenters – 4 ● Net Work.

### SEPT '97


**PROJECTS** ● PIC-Noughts & Crosses Game ● Ironing Safety Device ● Active Receiving Antenna ● Soldering Iron Controller ● Micropower PIR Detector – 3.  
**FEATURES** ● Ingenuity Unlimited ● Raising the Pressure – RC4190 Switch-Mode I.C. ● Circuit Surgery ● Techniques – Actually Doing It ● Great Experimenters – 5 ● Net Work.

### OCT '97

**PROJECTS** ● PIC Water Descaler ● Remote Control Finder ● Multi-Station Quiz Monitor ● Rechargeable Handlamp.  
**FEATURES** ● Ingenuity Unlimited ● It's Probably Murphy's Law ● Interface ● Circuit Surgery ● Kanda PIC Explorer Review ● Network ● Special Offer – Pico Virtual 'Scopes.
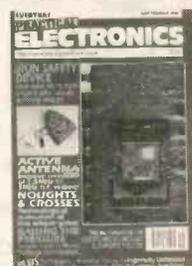
### NOV '97

**PROJECTS** ● Portable 12V PSU/Charger ● Case Alarm ● Auto-Dim Bedlight ● EPE Time Machine.  
**FEATURES** ● Satellite Celebration ● Ingenuity Unlimited ● TEACH-IN '98 – An Introduction to Digital Electronics-1 ● New Technology Update ● Techniques – Actually Doing It ● Circuit Surgery ● Net Work ● Special Offer – Pico Virtual Scopes ● Free Greenweld Catalogue.



### DEC '97

**PROJECTS** ● Safe and Sound – Security Bleepers ● Active Microphone ● Car Immobiliser ● Mini Organ.  
**FEATURES** ● TEACH-IN '98 – An Introduction to Digital Electronics-2 ● Circuit Surgery ● Interface ● B<sup>2</sup> Spice Review ● Ingenuity Unlimited ● Alternative and Future Technologies-1 ● Net Work – The Internet ● Free Giant Data Chart – Formulae.

### JAN '98

**PROJECTS** ● Disco Lights Flasher ● Simple M.W. Radio ● EPE Virtual Scope-1 ● Surface Thermometer.  
**FEATURES** ● TEACH-IN '98 – An Introduction to Digital Electronics-3 ● Circuit Surgery ● Ingenuity Unlimited ● Alternative and Future Technologies-2 ● Net Work – The Internet ● Free – Giant PIC Data Chart.

## BACK ISSUES ONLY £2.75 each inc. UK p&p.

Overseas prices £3.35 each surface mail, £4.35 each airmail.

We can also supply issues from earlier years: 1990 (except Jan., March, Oct. and Dec.), 1991 (except May, June, Aug., Sept. and Nov.), 1992 (except April and Dec.), 1993 (except Jan., Feb., March, April, May and Dec.), 1994 (except April, May, June and Nov.), 1995 (except Jan., March, May, June, Aug., Sept., Nov. and Dec.), 1996 (except Feb., July, Aug.). Please note we are not able to supply copies (or 'stats of articles) of *Practical Electronics* prior to the merger of the two magazines in November 1992.

Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

### ORDER FORM – BACK ISSUES – PHOTOSTATS – INDEXES

Send back issues dated .....

Send photostats of (article title and issue date) .....

Send copies of last five years indexes (£2.75 for five inc. p&p – Overseas £3.35 surface, £4.35 airmail)

Name .....

Address .....

I enclose cheque/PO./bank draft to the value of £.....

Please charge my Visa/Mastercard £.....

Card No. .... Card Expiry Date .....

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.  
SEND TO: **Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.**  
Tel: 01202 881749. Fax: 01202 841692. (Due to the cost we cannot reply to overseas queries or orders by Fax.)  
E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk)

Payments must be in £ sterling – cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.  
Send a copy of this form, or order by letter if you do not wish to cut your issue.

# 'Pico's PC Converters monitor and record temperature and humidity'.

## EnviroMon Temperature / Humidity Logger & Alarm System

EnviroMon has many applications in:  
**food processing** - storage and distribution, **energy management** - waste energy, heating and processing, **agriculture** - monitoring humidity in greenhouses, and in **hospitals** - accurate monitoring of temperature sensitive items.



- ▼ Monitors up to 30 channels of temperature over a 400 m. distance.
- ▼ -55 to 100°C temperature range (typical accuracy  $\pm 0.2^\circ\text{C}$ ).
- ▼ Data can be downloaded to PC.

### EnviroMon

**Starter Kit from £393.00**  
3 temperature Sensors on 5m lead, 3 channel Converter, Enviromon Logger, cables & fittings. Expandable at any time for around £50 / channel

## TC-08 8 channel Thermocouple to PC Converter

Simple to use thermocouple to PC interface.

- ▼ Connects to serial port - no power supply required.
- ▼ Supplied with PicoLog data logging software.
- ▼ Resolution  $0.1^\circ\text{C}$ .

**TC-08 £199.00**

Supplied with serial cable and adaptor. Calibration certificate £25.00. Thermocouple probes available.

## TH-03 3 channel Thermistor to PC Converter

- ▼ Connects to serial port - no power supply required.
- ▼ PicoLog data logging software.
- ▼ -55 to  $105^\circ\text{C}$  temperature range
- ▼ Resolution  $0.01^\circ\text{C}$ .

**TH-03 £79.00**

Supplied with serial cable and adaptor. Thermistor sensors available.



Call for free demo disk or download our web site:  
<http://www.picotech.com>

All prices exclusive of VAT.

Broadway House, 149-151 St Neots Rd,  
Hardwick, Cambridge. CB3 7QJ UK  
Tel: (0)1954 211716 Fax: (0)1954 211880  
E-mail: [post@picotech.co.uk](mailto:post@picotech.co.uk)



# Winter 97/98 Catalogue

## Includes 32 page full colour Computer Equipment Catalogue

### The Winter 97/98 Edition brings you:

- Our most comprehensive selection of Computer equipment ever, including all the latest CPU's, the fastest CD-ROM's, new ranges of Scanners, Printers, Motherboards, Graphic & Sound cards etc. etc., extending our range of PC components and accessories at unbeatable prices.
- £25 worth discount vouchers.
- 208 Page main Catalogue, plus 32 Page full Colour Computer Catalogue, incorporating 26 Sections with over 4000 Products from some of the Worlds Finest Manufacturers.
- Available at WH Smith, John Menzies and most large newsagents, or directly from Cirkit.
- **Get your copy today!**

**£2.20**  
+ 30p p&p



## Cirkit Distribution Ltd

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ  
Tel: 01992 448899 · Fax: 01992 471314  
Email: [mailorder@cirkit.co.uk](mailto:mailorder@cirkit.co.uk)  
Website: <http://www.cirkit.co.uk/cirkit>

# Pico

Technology Limited

# SHOP TALK

with David Barrington

## Water Wizard

When selecting the 7-segment displays for the *Water Wizard*, it is important to choose ones that have the pin line-up across the top and bottom of the device, looking at the display underside, if they are to plug into the p.c.b. The ones in the model came from **Maplin**, codes FR1U (com. cath.) and FR39N (com. anode).

The splashproof case and water flow sensor are both RS components and can be ordered through their mail order outlet **Electromail** (☎01356 204555), codes 581-199 (case) and 257-133 (flow sensor).

The Wizard program for the PIC16C54 was written and assembled using the system supplied by Microchip, namely MPASM. For those readers who do not have facilities to program PIC chips, a ready-programmed 16C54 microcontroller is available (*Mail Order Only*) from the Electronics Dept at Radley College for the sum of £8; add £1 for overseas orders. Payments should be made out to **Radley College** and addressed to: **Mr Max Horsey, Radley College, Electronics Dept, Abingdon, Oxon, OX14 2HR**.

If you wish to do your own programming, the software is available on a 3.5 inch PC-compatible disk from the Editorial Offices - see *PCB Service* page for details. If you are an Internet user, it is available *Free* from our FTP site: <ftp://ftp.epemag.wimborne.co.uk/pub/PICS/Waterwizard>.

The small printed circuit board is obtainable from the *EPE PCB Service*, code 180 (see page 157).

## Waa-Waa Effects Pedal

The single-pole, foot-operated "sweep" switch S1 required for the *Waa-Waa Effects Pedal* is a biased or non-locking type. Ideally, it should be a robust heavy duty type, but only a locking on/off switch seems to be available. An ordinary non-locking pushbutton switch should be adequate provided it is of good quality. Alternatively, for around £5 to £6 a custom "momentary" action footswitch pedal, with a 6-35mm mono jack plug attached, can be purchased from **Maplin**, code DU99H.

The unit is built on the multi-project printed circuit board available from the *EPE PCB Service*, code 932.

## Kissometer

The miniature transistor output matching transformer type LT700 called for in the *Kissometer* project were once fairly common, but in case of local supply difficulties it can be sourced from **Maplin**, code LB14Q.

The plastic case is a Union Brothers PX-3 type sold by the above company (code YU54) and the miniature Lo-Z 8 ohm 0.2W loudspeaker also came from the same source, code WB08J.

The single-sided printed circuit board is available from the *EPE PCB Service*, code 181.

## EPE Virtual Scope

Nearly all the "special" parts called up for the *EPE Virtual Scope* project are RS components and will need to be purchased through your local *bona-fide* RS distributor or through their mail order outlet, namely **Electromail** (☎01356 204555).

Starting with the semiconductor devices first: the SRAMS type TC55257DPL-85L (12MHz) and CXK58257AP-70LL (14MHz) are carried as 298-190 and 193-6310; and the 10MHz crystal module, code 267-922. The rest of the semiconductors should be readily available, once again RS types have been used in the prototype model.

Moving on to the connectors, these should now be stocked by most of our components advertisers, such as **ESR Electronic Components** (☎0191 251 4363). Last month we gave the RS type numbers for the Centronics connectors used in the prototype. We have now learnt that these have been discontinued, but alternative types are: right-angle 36-way 239-1178, and 14-way 239-1156.

The large plastic case is ordered as 503-650. The 24s.w.g. tinned annealed copper wire should be ordered as 355-085. Finally, the large printed circuit boards are available from the *EPE PCB Service*, codes 176 (Digital) and 177 (Analogue) - See page 157.

The software for this design is available on a 3.5 inch PC-compatible disk from the *EPE PCB Service*, see page 157. Alternatively, the files can be downloaded *free* from our Internet FTP site:

<ftp://ftp.epemag.wimborne.co.uk/pub/vscope>.

It is recommended that readers run the software to check to see if their computer will run the *EPE Virtual Scope* before they buy parts. Also, an additional file is on the disk. It is MOUSE01.BAS and is not discussed in the text. It allows you to check your mouse response from Basic without loading the full VSCOPE.BAS. program.

## Teach-In '98

Only one observation regarding parts for this month's *Lab Work 4* chapter of *Teach-In '98* Part 4 needs to be highlighted and that concerns the I.e.d.s. All the 4000 series of CMOS i.c.s specified should be readily available.

The I.e.d. used in the breadboard demo model is a 5V "direct connection" type, with an integral ballast resistor. Most of our components advertisers should carry the 5mm version of this device. However, you can use a standard 5mm I.e.d. provided you use an external resistor in series with it, typically 330 ohm for a 5V supply.

## PLEASE TAKE NOTE

### EPE Time Machine (Nov '97)

There has a minor software update, see *Readout* page 107. All software sources have been updated.

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 220V/240V AC 50/60 OUTPUT 0V-260V

PANEL MOUNTING Price P&P

0-5KVA 2.5 amp max £33.00 (£45.83 inc VAT)

1KVA 5 amp max £45.25 (£61.39 inc VAT)

SHROUDED Price P&P

0-5KVA 2.5 amp max £34.00 (£47.00 inc VAT)

1KVA 5 amp max £46.25 (£62.57 inc VAT)

2KVA 10 amp max £65.00 (£86.36 inc VAT)

3KVA 15 amp max £86.50 (£111.63 inc VAT)

5KVA 25 amp max £150.00 (+ Carriage & VAT)

10KVA 45 amp max £300.00 (+ Carriage & VAT)

6KVA 3 PHASE Star £205.00 (+ Carriage & VAT)

Buy direct from the importers. Keenest prices in the country

## 500VA ISOLATION TRANSFORMER

New manual surplus 'C Core' tropicalised with top plate and solder connections 0-240V AC 5-0-100-110-120V & Screen Wt 10.5k

Size: H 195 x 155 x 135mm

Price £35.00. Carr £7.50 (£49.94 incl.)

## COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO

110V-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery

## ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft 40 watt £14.00 (callers only) (£16.45 inc VAT)

2ft 20 watt £9.00 (callers only) (£10.58 inc VAT)

12in 8 watt £4.80 + 75p p&p (£5.52 inc VAT)

9in 6 watt £3.96 + 50p p&p (£4.24 inc VAT)

6in 4 watt £3.96 + 50p p&p (£4.24 inc VAT)

## 230V AC BALLAST KIT

For either 6in, 9in or 12in tubes £6.05 + £1.40 p&p (£8.75 inc VAT)

The above tubes are 3500/4000 angst (350-4000nm) ideal for detecting security markings, effects lighting & Chemical applications

Other Wavelengths of UV Tube available for Germicidal & Photo Sensitive applications. Please telephone your enquiries

## 400 WATT BLACK LIGHT BLUE UV LAMP

GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast

Only £39.95 incl. p&p & VAT

## RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

## SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical use etc.

Approx 16 joules Adjustable speed £50.00 + £3.00 p&p (£52.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)

SAE for further details including Hy-Light and Industrial Strobe Kits

EUROCARD  
MasterCard  
Open Monday/Friday

## SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

TEL: 0181-995 1600 FAX: 0181-995 0549

ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

## 5 KVA ISOLATION TRANSFORMER

As New Ex-Equipment, fully shrouded, Line Noise Suppression, Ultra Isolation Transformer with terminal covers and knock-out cable entries.

Primary 120V/240V Secondary 120V/240V, 50/60Hz, 0-0050F Capacitance. Size: L 37cm x W 19cm x H 16cm. Weight 42 kilos Price £120 + VAT. Ex-warehouse. Carriage on request.

## 24V DC SIEMENS CONTACTOR

Type 3TH8022-0B 2 x NO and 2 x NC 230V AC 10A. Contacts. Screw or Din Rail fixing. Size H 120 x W 45 x D 75mm. Brand New Price £7.63 incl. P&P and VAT.

## 240V AC WESTOOL SOLENOIDS

TT2 Mod. 1 Rat. 1 Max. stroke 3/16in. Base mounting 1/2in stroke 5lbs pull approx. TT6 Mod. 1 Rat. 1 Max. stroke 1 in. Base mounting 1/2in. stroke 15lbs pull approx. SERIES 400 Mod. 1 Rat. 2 Max. stroke 1/2in. Front mounting 1/2in. stroke 15lbs pull approx. Price incl. p&p & VAT. TT5 £5.88, TT6 £8.81, SERIES 400 £7.64.

## AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan. Price £7.29 incl. P&P and VAT.

Other voltages and sizes available from stock. Please telephone your enquiries.

## INSTRUMENT CASE

Brand new. Manufactured by Imhof. L 31 x H 18 x 19cm Deep. Removable front and rear panel for easy assembly of your components. Grey textured finish. complete with case feet. Price £16.45 incl. P&P and VAT. 2 off £28.20 inclusive.

## DIE CAST ALUMINIUM BOX

with internal PCB guides internal size 265 x 165 x 50mm deep. Price £9.93 incl. p&p & VAT. 2 off £17.80 incl.

## 230V AC SYNCHRONOUS GEARED MOTORS

with internal PCB guides internal size 265 x 165 x 50mm deep. Price £9.93 incl. p&p & VAT. 2 off £17.80 incl.

Brand new Ovoid Gearbox Couzlet type motors. H 65mm x W 55mm x D 35mm. 4mm dia shaft x 10mm long. 6 RPM anti cw. £9.99 incl. p&p & VAT.

20 RPM anti cw. Depth 40mm. £11.16 incl. p&p & VAT.

## SOLID STATE HT UNIT

Input 230V/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, e.g. supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS.

## EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Kit of parts less case includes 12in 8 watt 2537 Angsi Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.99 inc VAT)

## WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled can be used for a variety of purposes. Inlet 1 1/2in, outlet 1in. dia. Price includes p&p. & VAT £11.20 each or 2 for £20.50 inclusive.

## NEW SPECIAL OFFERS

Mini waterproof TV camera 40x40x15mm requires 9 to 13 volts at 120mA with composite video output (to feed into a video or a TV with a SCART plug) it has a high resolution of 450 TV lines Vertical and 380 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a small lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3 wire lead (12v in gnd and video out). Now also available with wall mount tilt and swivel case (at the same price). £93.57 + vat = 109.95 or 10 + 89.32 + vat. = 104.95

Board cameras all with 512x582 pixels 4.4x3.3mm sensor 9-13 volts power supply and composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts. 47MR size 60x36x27mm with 8 infra red leds (gives the same illumination as a small torch would). £50.00 + vat = £58.75

40MP size 39x38x23mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. £57 + vat = £66.98 40MC size 39x38x26mm camera for 'C' mount lenses 358.79 + vat = £80.63, standard 'C' mount lens F1.6 16mm for 40MC. £26.43 + vat = £31.06

High quality stepping motor kits (all including stepping motors) 'Comstep' independent control of 2 stepping motors by PC (Through the parallel port) with 2 motors and software. Kit £67.00 ready built £98.00

power interface 4A kit £36.00 power interface 8A kit £46.00

Stepper kit 4 (manual control) includes 200 step stepping motor and control circuit. £23.00

DTA30 Hand held transistor analyser it tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty (NEW VERSION does not say FETs & SCRs are transistors) DTA30. £38.34

HMA20 hand held MOSFET analyser identifies gate drain and source and if P or N channel HMA20. £38.34

Speaker cabinets 2 way speaker systems with Motorola tweeters

15" 12" 8"

360W dia 250WRMS 175WRMS 100WRMS

power rating 80hm 80hm 80hm

frequency range 40hz-20khz 45hz-20khz 60hz-20khz

sensitivity(1W/1M) 97dB 94dB 92dB

size in mm 500x720x340 450x640x345 315x460x230

weight 21.1kg 16.8kg 7.4kg

price each for back vinyl coating £139.95 £99.99 £54.94

grey felt coating £169.97\*\* £119.97\*\* £64.99

(\* = not normally in stock allow 1 week for delivery)

Power amplifiers 19" rack mount with gain controls & VU meters

STAG90 2x190Wrms (40hm load) 11kg £339.00

STAG90 2x490Wrms (40hm load) 15kg £585.00

LED's 3mm or 5mm red or green 7p each, yellow 11p each, cable ties 1p each £5.95 per 1000 £49.50 per 10,000

Rechargeable Batteries

AA 950mAh £0.99

AA 950mAh £1.75

C 2AH with solder tags £3.60

D 4AH with solder tags £4.95

1/2AA with solder tags £1.55

AAA (HP18) 180mAh £1.75

AA 500mAh with solder tags £1.65

CHP11) 1.2AH £2.60

D(HP2) 1.2AH £2.60

PP3 8 4V 110mAh £2.50

Sub C with solder tags £2.50

1/3 AA with tags (philips CTV) £1.95

Nickel Metal Hydride AA cells high capacity with no

memory. It charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates). £3.75

Special offers please check for availability

5 button cell 6V 280mAh battery with wires (Varta 5x2500K). £2.45

Orbitt B66 battery pack 12v 1.6AH contains 10 sub C cells with solder tags (the size still commonly used in cordless screwdrivers and drills 22 dia x 42mm tall). It is easy to crack open and was manufactured in 1994. £8.77

each or £110.50 per box of 14

BCI box 190x106x50mm with slots to house a pcb the lid contains an edge connector (12 way 8mm pitch) and screw terminals to connect to wires and 5 slide in cable blanks. £2.95

7 segment common anode led display 12mm. £0.45

GAAs FET low leakage current S8873 £1.25 each £9.65 10+ 7.95

BC547A transistor. £20 for £1.00

LS92 UHF Limiting amplifier L.C. 16 surface mounting package with data sheet. £1.55

DC-DC converter Reliability model V12P5 12v in £1.50

200v out 300v input to output isolation with data £4.95 each or pack of 10 £39.50

Airpax A82903-C large stepping motor 14v 7.5 step 270hm 68mm dia body 6.3mm shaft. £8.95 or £200.00 for a box of 50

Solid carbon resistors very low inductance ideal for RF circuits 270hm 2W, 680hm 2W 25p each 15p each 100

We have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list

P.C. 400W PSU (intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and minitel/ultra connectors on back and switch on the side (top for lower case) dims 212x149x149mm excluding

price: £25.00 each £138.00 for 6

MX180 Digital multimeter 17 ranges 1000v dc 75Vv ac 20mAhm 200mA transistor Hfe 5v and 1.5v battery test. £3.65

Hand held ultrasonic remote control. £3.65

CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £8.50 per 100

Verbatim R300NH Streamer tape commonly used on r.c. machines and printing presses etc. It looks like a normal cassette with a slot cut out of the top £4.95 each (£3.75 100+)

Heatsink compound tube. £0.65

DV5-2405-ES 5-24v 50mA regulator ic 18-264vdc input 3 pin DIL package. £3.49 each (100+ £2.25)

LM 555 timer c 16p, 8 pin DIL socket 6p. £0.65

All products advertised are new and untested otherwise stated wide range of CMOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitor tools etc. always in stock

Please add £1.95 towards P&P (orders from the Scottish Highlands, North Ireland, Isle of Man, Isle of Wight and overseas may be subject to higher P&P for heavy items)

VAT included in all prices

## JPG ELECTRONICS

276-278 Chatsworth Road

Chesterfield S40 2BH

Access/Visa Orders:


Tel: (01246) 211202 Fax: (01246) 550953

Callers welcome 9.30am to 5.30pm

Monday to Saturday

# CIRCUIT SURGERY

ALAN WINSTANLEY

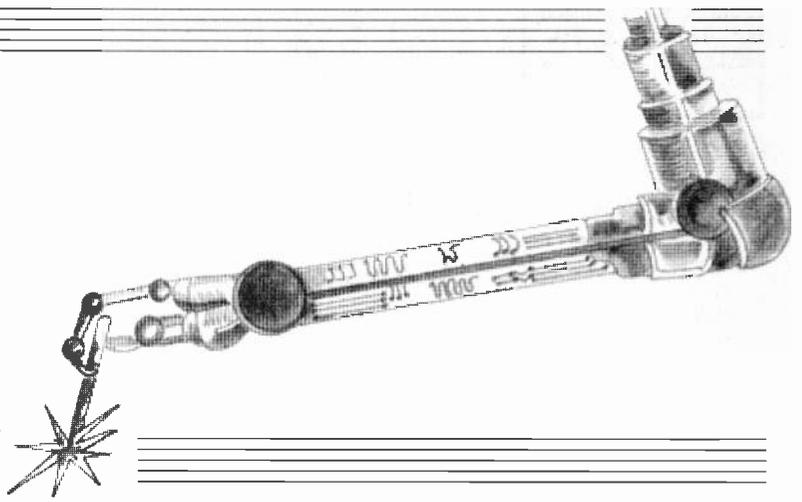

*This month we help with a high-powered question on regulators, follow up on PLCs, put diode markings under the microscope and ponder resistor ratings.*

## High-Current Regulator

Power supply queries continue to crop up from time to time, and *Mr. Philip Tate* asks by E-mail:

*I need to build a not-necessarily-highly-regulated power supply providing about 8V at 10A maximum. The switched-mode power supplies I have tried do not work down to zero load, so I hope to build a conventional power supply instead.*

*All the textbook designs stop short at the LM338 regulator, and hence at 5A output! My question is, can regulator i.c.s be wired up in parallel to provide higher currents? What happens if I don't match the output voltages perfectly? Alternatively, do you think I could build a good old-fashioned power supply around a hefty power transistor like the 2N3055, and expect it to survive at 80 watts?*

In January's issue I showed some regulated power supply circuits using Zener diodes and external "pass" transistors. These are simple but effective, and might be adapted to your own application. The main problems are that the external pass element will dissipate (read: waste!) most power under maximum output (when the voltage across them and current through them is highest); also the circuits are not blow-out proof, with no protection built in.

Whether your power transistor can safely survive at 80W dissipation depends on the combination of collector-emitter voltage (Vce), collector current Ic, and temperature. Whilst the power dissipated by the transistor is the product of VceIc, the device should be operated within its *safe operating area* (SOA) for reliability.

Otherwise, you run the risk of "secondary breakdown", when areas of the transistor may overheat, thereby drawing more current, which generates more heat and eventually creating catastrophic thermal runaway.

Manufacturers' data will give the maximum permissible case temperatures for a range of power values, shown in a power derating curve. (In the example of a 2N3055, the maximum case temperature is 75°C at a power of 80W; it will dissipate

up to 115W, but only if its case temperature does not exceed 25°C.) Furthermore, the safe operating area curves should be considered, as this restricts the maximum VceIc allowed before secondary breakdown occurs. (At 10A d.c., the maximum Vce is about 12V to remain within the recommended SOA.) So you are probably safe to use the 2N3055, but the thermal resistance of the heatsinking should ensure that the maximum case temperature stated is not exceeded.

The answer to your regulator query is, yes you can place regulator i.c.s in parallel, connecting them together for a higher output current. One problem is that the devices will not have identical "drop-out" voltages, so there will be a contest of wills, with the one that has the lowest drop-out voltage attempting to do more work by shunting the others, and it will be the first to current limit before the others start to "join in".

The work-around is to include a low-value series ballast resistor in series with each regulator output. The voltages across all parallel devices will balance out, with the resistors dropping any differences.

There are various circuits suggested in data sheets and application notes; Fig. 1 shows a typical circuit for an adjustable 10A regulator which uses two LM338 5A adjustable regulators (*National Semiconductor*). It requires a minimum 100mA load.

Allowing a drop-out voltage of at least 2.5V, then the input voltage must not fall below 8V + 2.5V, or 10.5V. The circuit's performance is also affected by the heatsinking used on each device, as they will shut down if their power dissipation becomes excessive.

Incidentally, even though the chips are thermally protected, long-term reliability might also be affected by totally inadequate heatsinking, causing an aggressive heating/cooling cycle (eventually creating a sort of thermal fatigue, apparently).

As an alternative, consider the National LM396, which is a fully-fledged 10A adjustable regulator with a guaranteed 10A output current, presettable from 1.25V to 15V, see Fig. 2. Its maximum power limit

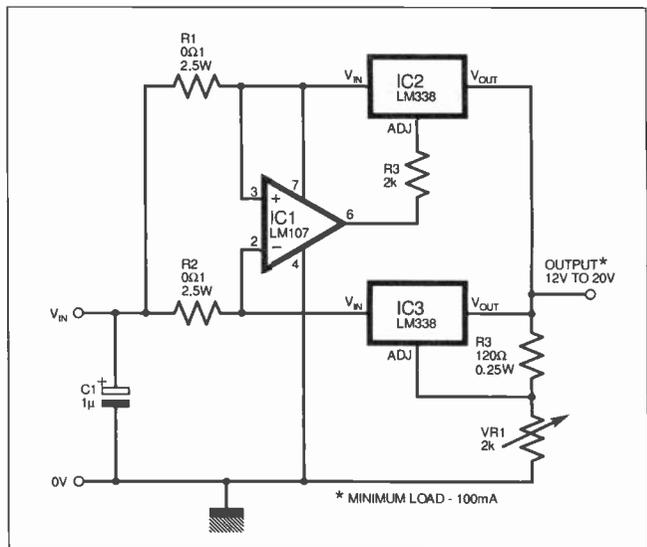


Fig.1. 10A regulator using a pair of 5A variable regulator i.c.s. (courtesy National Semiconductor).

is 70W. Many other factors have to be taken into the design, though, including the gauge of the wiring and any unwanted resistance on the output, which may give rise to noise.

The circuit diagram in Fig.2 also shows how the 0V rail is grounded at a common point, and the load is taken from as close to the device output pin as possible, to avoid introducing any unwanted resistance on the output side. Once again, a major constriction is heatsinking (and consider fan cooling: maybe buy some surplus or ex-equipment fans), and again, National Semiconductor's data sheet is commendably informative. You will have to shop around and order the device specially, as I

couldn't find it listed in the mainstream catalogues, but it is probably the ultimate answer to building a simple 10A regulator, 3-terminal style.

## Why no PLCs?

In December's issue I alluded to a product called the "PLC". R. Grodzik of Bradford comments on their use:

*Following on from your item in the December issue, I was somewhat surprised and bemused to read that PLCs were outside the remit of EPE since they are "designed for industrial process control applications".*

*That is so, but the whole point of the PLC is the ease of programming, viz. ladder logic versus assembler if naked embedded controllers are used. Since the program is held in EEPROM and the PLC usually has a simple hand-held keypad, an electrician can easily debug the program - e.g. alter delay routines. The alternative for programming a processor or embedded controller is to edit the source code, reassemble or compile (if a run time library is used) and then program the memory (Flash, EPROM, EEPROM etc.).*

*Now that small PLCs are available with six inputs and eight outputs for under £200 there is no reason to use PLCs only in an industrial environment. I'm sure a PLC would be an ideal model train system controller, or could be the "brains" of a simple robot. So think again, EPE, if it works on electricity we want to know about it!*

For the benefit of readers not acquainted with them, Programmable Logic Controllers (PLCs) - not to be confused with PIC microcontrollers - are sophisticated self-contained control units which are mainly intended for industrial process control. An engineering colleague agrees that they probably are under used, as they are mainly seen in industrial "mission critical" applications, from supervising the processes in a fizzy drinks production line, through to controlling the operation of a steel smelting works or a huge swing bridge. (A large bridge in the city of Hull apparently has "dual redundancy" PLCs - if one should fail, the other PLC takes over seamlessly.)

Curiously, the teaching of PLC programming and operation seems to be somewhat sporadic. This is probably because their use tends to be concentrated in certain regions where there is a considerable amount of PLC-equipped processing machinery in local industry. There has never been any mention of them in this magazine in the past, which should not be taken as our disapproving of them, simply that they are not relevant to what we know to be the expectations of our own core readership!

We are much more interested in what happens at component level (e.g. microcontrollers, integrated and discrete

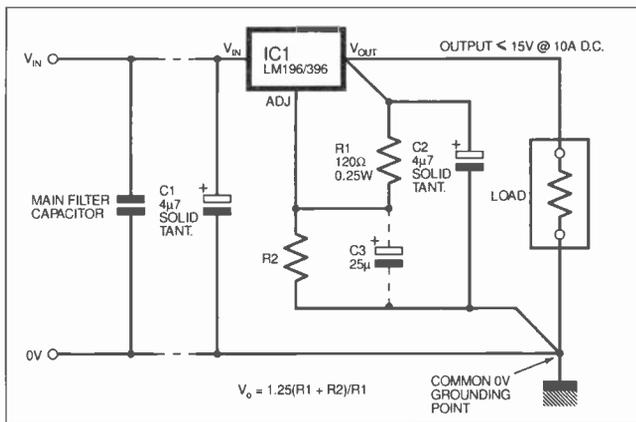


Fig.2. Variable voltage 10A regulator using a single 10A device (courtesy National Semiconductor).

devices), whereas PLCs are electrically rugged, industrially-hardened boxes with memory, battery back-up, real time clocks, networkability and big screw terminals, all designed to be used by electrical fitters and engineers who don't (need to) know about component-level systems. For the same reasons, we don't talk about DIN rail (specially-profiled steel rail, onto which all sorts of electrical terminals, relays and gear can be clipped) or contactors, either!

As an academic exercise, it is true that a PLC would make a very fine model train controller or robotics control system, but in the context of EPE, simply buying a sturdy programmable control box plus programmer software, then programming it with relay ladder logic would really be inappropriate and is beyond the remit of the magazine.

We're, of course, primarily a hobbyist, project and educational journal, with a little bit of spin-off into other areas. Hence we can do nothing more than mention PLCs in passing, as a general interest item. Just like I have done, in fact.

## Diodes and Resistor Queries

Mr. J.W. Pritchard of Holywell, Flintshire queries the symbology of diodes.

*I work in p.c.b. assembly, and have a couple of queries: on some of our boards we orientate diodes with the cathode to '+', which is confusing when the diode must have its anode more positive than the cathode if it is to work! The other query is, why we choose 0.25W resistors when 0.5W types are freely available, both being metal film and of the same tolerance. In other words, do lower wattage resistors have any advantages over higher wattage resistors of the same type?*

Your diode query first. A quick rummage through my groaning bookcases, and I turned up *Everyday Electronics*, May 1979 edition - an Intruder Alarm by the late F. G. Rayer, see the excerpt in Fig. 3. Yes, I thought as much - the cathodes of diodes were indeed marked on circuit diagrams with a plus sign! So we used to do the same.

I guess there was much confusion about the markings of diodes, and I seem to remember that a decision was taken years ago to drop the "+" sign as well as the circle (envelope) surrounding the symbol. This reduces the clutter of circuit diagrams.

We do however mark anode and cathode as "a" and "k", to help beginners. Traditionally, *Everyday Electronics* marked the terminals of bipolar transistors as e, b and c, (and MOSFETs, d, g, and s) also to assist newcomers. This habit has stuck as part of our house style. I guess the best way of dealing with it is to think that the plus sign on your boards indicates the striped or banded end of the diode body.

As to why use 0.25 watt resistors, well, when I first started out in electronics, I treated myself to a complete range of resistor values, ten of each, all in 0.5W ratings, purchased from Doram Ltd. (the adventurous "Doorway to Amateur Electronics" - as opened and slammed shut again by the major group which owned it). Most of them are still here, unopened in their packets.

Why? The trend is towards miniaturisation coupled with better power efficiency. 0.25W types are used universally in our projects as well as on traditionally-made commercial p.c.b.s (even 0.125W at times) and I guess economies of scale, which affect manufacturing industry enormously, created the demand for 0.25W types at the keenest prices.

From the practical point of view, it proves extremely difficult to use 0.5W resistors in many project boards. A quarter-watt resistor spans four or five holes on a 0.1-inch pitch, whereas a typical half-watt takes seven or eight. Power ratings permitting, they're generally just too big for most p.c.b.s, or for breadboarding, especially when resistors are placed adjacent to each other on a tight-fitting board.


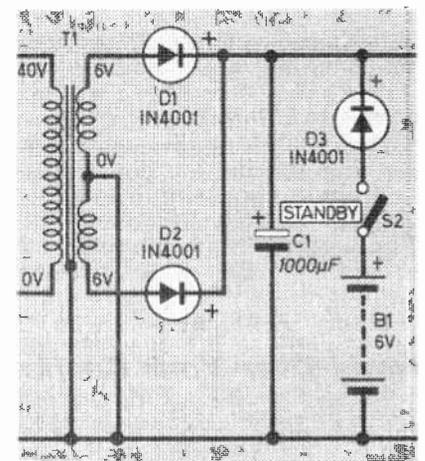


Fig.3. Traditional circuit diagrams showed diode cathodes marked with a "+" sign.

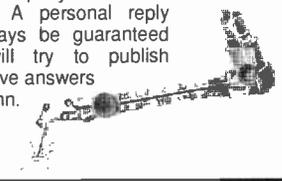
## CIRCUIT THERAPY

*Circuit Surgery* is your column. If you have any queries or comments, please write to: Alan Winstanley, *Circuit Surgery*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset, BH21 1PF, United Kingdom. E-mail [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk). Please indicate if your query is not for publication. A personal reply cannot always be guaranteed but we will try to publish representative answers in this column.



# SURFING THE INTERNET NET WORK

ALAN WINSTANLEY

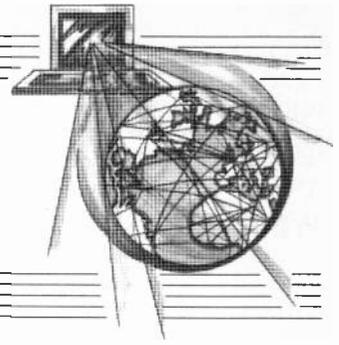

REGULAR readers will know that *EPE* maintains a presence on the Internet in the form of our web site <http://www.epemag.wimborne.co.uk> where you can subscribe or renew a subscription via our secure server, also you can remind yourself about the main contents of recent issues, with snapshots of major projects. Don't forget to check the "What's Ahead" pages for details of our plans in the pipeline, and there are alphabetical indexes for 1996 and 1997 constructional projects, with the very few "Please Take Note" corrections preserved on line as well.

Our FTP site <ftp://ftp.epemag.wimborne.co.uk> contains a variety of text files and the source codes for most of our PIC projects (and other project files too), for you to download freely.

Software for the *EPE Virtual Scope* is at subdirectory `/pub/Vscope` and that for the *Water Wizard* is at `pub/PICS/WaterWizard`.

## PC Technology Race

An acquaintance of mine works for a PC manufacturer in the States, and he's responsible for sending out samples of the latest machines to American computer magazines, for review purposes. A problem, he tells me, is that the lead time on publishing some magazines is up to four months, and such is the bewildering pace of technology at the moment that by the time the reviews are published, the PCs themselves are all but obsolete!

This has always been the way with personal computers. There is never a good time to buy one, unless you are prepared to wait until a particular processor falls out of favour and manufacturers have a clear-down sale, when the price will bottom out. You can thus save yourself something like £50-£75 per month in the interim, by sitting back and waiting.

There's plenty of hardware muscle around, and if you have say £1,000 or so to blow on a new PC and printer, you will not help but finish up with a fairly awesome machine; it's hard to come away with much less. However, just because a processor is no longer listed in mainstream adverts (which fuel the demand for the latest and fastest in the first place), doesn't necessarily mean that it is no longer available, and local suppliers may be able to sort out a slower, but still highly respectable, machine for a price you'll find unbeatable. By the time you read this, the Pentium II 233MHz will be the entry model being pushed by the PC giants.

## Hand Over Your Cache

*Netscape Navigator* and *Microsoft Internet Explorer* each have their own "cache" sub-directories which are portions of your hard disk in which downloaded pages (.htm files, images, etc.) are retained for reference by the browser during on-line sessions.

The good thing about the cache is that it saves having to wait every time for every graphic or text to be downloaded onto your PC, because the browser refers first to any files already held in cache, and it will fetch it from there rather than from the network, provided that the files haven't changed on the web site subsequently.

You can control what the browser should do when it stumbles upon web pages which may have been previously cached:

*Netscape*: Options/Network Preferences/Cache and you can set the amount of space to be donated to cache, and how frequently *Netscape* should verify any cached pages. The settings can have a fundamental effect on your "surfing speed" – choose "Once per session" if in doubt.

*Explorer*: View/Options/Advanced/Temporary Internet Files/Settings (or, View Files to have a peek in the cache contents – 2,500 items in my case). Again, frequency and cache size controls are available for you to tune up.

You can clear out the cache to make space, using the same controls. The bad thing about all this is that although the cached files can be trivial in size, say 1KB, the bigger your hard disk, then

the bigger the "cluster size" will be. The cluster represents the minimum "chunk" of data which can be stored on your hard disk.

For example, a 100MB hard disk on my old 486 is reported as having a cluster size of 2,048 bytes. In contrast, my 1.6 Gigabyte hard disk has a cluster size of 32,768 bytes. So even a 1KB file held in cache will hog 32K – one cluster – of space. The net result is that 31K goes to waste. Hence of the 90MB allocated, my Temporary Internet Files cache wastes no less than 71MB of it! 330MB of my total hard disk is just wasted space! So, when spring-cleaning your hard disk, the first place to start is with the cache.

Users of the very latest release of Windows 95 (OE version only) and Windows 98 won't have such a problem: they use 4K cluster sizes for drives up to 8GB. Disk partitioning programs (e.g. *Quarterdeck Partition-It*) will let you re-size and move disk partitions on the fly, shrinking the cluster size as needed. A freeware utility which emphasises this waste graphically is the *TreeSize* program, available from [www.jam-software.com/software.html](http://www.jam-software.com/software.html). This will analyse and display hard disk usage in a variety of ways.

Also try the impressive-looking program *More Space* by *Contact Plus* which will help free up disk space, manage your cache and it includes an excellent disk analyser which tells you all about the "overhang" or wasted disk space. It costs US\$20, with W95 and W3.1 versions. Demo. from [www.contactplus.com](http://www.contactplus.com).

## Suggested Links

*Explorer 4* includes an option to "browse offline". It can now crawl all over any sites of interest and deliver them to your desktop, and you can browse them off-line at your leisure. By "subscribing" to them, *Explorer 4.0* will also notify you if any favourite sites have changed, all of which sound like cool features for the busy surfing executive.

This month, in place of the usual electronics URLs, I'm listing some interesting sites related to cache control software and viewing. Here are a few ways in which you can check your favourite sites and view them off-line, at leisure. *Unmozify* and *Near Site* from Info Evolution in the UK are two well-established programs which let you control your "cache", and view them off-line. Trial versions for each browser are available at [www.evolve.co.uk](http://www.evolve.co.uk). (Why *Unmozify*? It's named after Mozilla, the friendly dinosaur *Netscape* mascot, and cache files originally had their own ".moz" filename extension.)


*WebSnake* by Anawave uses an *Explorer*-like window, with suitably serpent-like icons, and is an extremely cool way of grabbing an entire web site onto your hard disk for viewing later on, or for "snaking" E-mail addresses from a web site. It costs US\$29.95. More at [www.anawave.com](http://www.anawave.com).

*Got It!* by Go Ahead ([www.goahead.com](http://www.goahead.com)) is a caching control which works in the background. Based on what it learns from your pattern of access to the Web, *Got It!* prioritizes the retrieved data and caches it intelligently on your hard drive (it says here). It also claims to accelerate your web surfing. It costs US\$19.95.

Forefront's *Webwhacker* ([www.ffg.com/whacker/](http://www.ffg.com/whacker/)) for Windows, Macintosh and PowerPC costs US\$49.95 and is another web accelerator and off-line browser worth investigating.

*LinkSync* ([www.bluesquirrel.com/linksync/](http://www.bluesquirrel.com/linksync/)) is an accessory for both *Netscape Navigator* and *Internet Explorer* web browsers. It claims to let you merge your *Netscape* bookmarks and *MSIE* "favorites" folder without producing duplicates or unwanted bookmarks. *LinkSync* also applies any changes (add, delete, rename, move) made to your *Netscape* bookmarks, to your "favorites" folder and vice versa. US\$19.95.

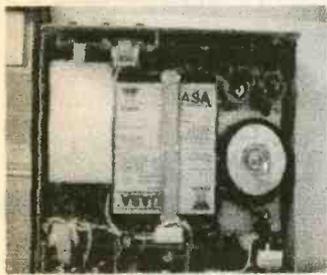Don't forget to keep me posted with your favourite electronics sites. More next month. You can E-mail me at [alan@epemag.demon.co.uk](mailto:alan@epemag.demon.co.uk). My Home Page is at [homepages.tcp.co.uk/~alanwin](http://homepages.tcp.co.uk/~alanwin).



**SALE PRICE £9.95**

**VIDEO PROCESSOR UNITS 7/6v 10AH BATT/24V 8A TX** Not too sure what the function of these units is but they certainly make good strippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2 x 6V 10AH sealed lead acid batts, pcb's and a 8A? 24v toroidal transformer (mains in), sold as seen, may have one or two broken knobs etc due to poor storage. £9.95 ref VP2X




**Dell switched mode psu  
12v 15amp £9.95**

140x 150 x 90mm, fully cased with built in fan, +12 @ 13A, +5 @ 15A IEC power inlet, flylead output. £9.95 ref DEL2



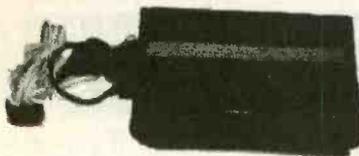UK made energy saving device that can give you a 15% saving on the running costs of fridges etc. Suitable for mains appliances fitted with a motor of up to 2A rating. We have tried the device on other things like soldering irons, conventional bulbs and still achieved a saving. One off price is £9 ref LOT71 Pack of 10 is £89 ref LOT72 Pack of 20 is £119 ref LOT73




**SALE PRICE £10**

These units must be cleared at the absurd price of just £10! you get loads of leads, an Infra red remote keyboard and receiver, a standard uhf modulator, a standard bt approved modem 1200/75 and loads of chips, resistors, capacitors etc etc all for just £10 ref bar33

**Switched mode  
psu special offer  
£2.99**

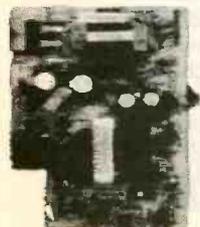Brand new psu's giving 5v at 4.4Amps. Originally made for the Archimedes but obviously have many other uses. Fitted on/off switch and fly lead. 150 x 100 x 42mm, £2.99 ref ARCH1X



**SALE PRICE £2.50**

Customer returns, domestic telephone coin boxes, used to convert ordinary phones in to pay phones. ref CBT1X



**The ultimate enclosure for  
your projects must be one of  
these!**

Well made ABS screw together beige case measuring 120 x 150 x 50mm. Already fitted with rubber feet and front mounted LED. Inside is a pcb fitted with other bits and pieces you may find useful. Sold either as a pack of five for £10 ref MD1 Or as a pack of 20 for £19.95 ref MD2

**Order via our web site at  
www.bull-electrical.com**

**SOLAR PANELS**

3' x 1' Amorphous silicon, 7 watt 12-14v  
output. Unframed. Ref SOLX  
**SALE PRICE 4 for £59**

**PC KEYBOARDS**

**sale price just £2.99**

Standard ps2 type connector, 104 keys. ref  
PCX



**Compaq**

**244 watt pc power supplies  
buy 2 for £16**

Ex equipment but in full working order direct from one of the top manufacturers. 145 x 175 x 85mm, fitted fan and IEC inlet, switch on flylead. Outputs are 3.3vdc, +5vdc, -5vdc, +12vdc, -12vdc. You may need to change the mother board connector so we have included another one with the power supply to help. £16 for 2 ref COM2

**BULL ELECTRICAL**

250 PORTLAND ROAD, HOVE, SUSSEX

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3.50 P&P PLUS VAT.

24 HOUR SERVICE £5.00 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50

(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)


**'phone orders: 01273 203500**

FAX 01273 323077

E-mail [bull@pavilion.co.uk](mailto:bull@pavilion.co.uk)



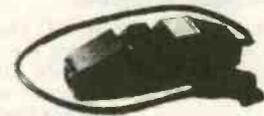**12V FANS, EX EQUIPMENT  
COMPLETE WITH METAL CASES  
PACK OF 10 FOR £9.95**




**RCB UNITS £2.99**

This in line miniature earth leakage unit instantly shut off the mains supply in the event of any current flowing between live and earth thus preventing a potentially lethal shock. IEC plug one end, socket the other, fitted in seconds, reset button. The ultimate safety aid when working on electronic equipment, computers etc.

As these units are fitted with an in-line IEC plug on one end and socket on the other than could even be used to extend standard IEC computer leads.

**Complete accounts system  
for your PC for just £9.95**

Unlimited companies, general ledger, multiple cash books, debtors and creditors, stock, invoicing, purchasing, budgets, report writer, calculator, wordprocessor, automated backups, on line help, windowing, networkable up to 10 workstations. Free telephone support for 30 days from MAP computer products 01616788413 all for the bargain price of just £9.95! worth it for the 200 page Pastel manual alone! ref SA12 3.5" disk version only. £9.95 ref PAS2

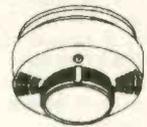

**MAINS SMOKE ALARMS (GENT)  
NEW AND BOXED £4.99 ref SMKX**

**BBC selector videocrypt 's'  
tv tuner with smart card  
sale price £9.95**

Interesting new item in this week is this Selector. Originally made for the BBC to send encrypted video films to your VCR at night time. The project seems to have failed.

Very complex units consisting of a smart card slot in the front plus several switches and an IR receiver. Fully cased and measuring 230 x 430 x 90mm, new and boxed.

On the back of the unit is a smart socket plus a UHF input and output. A channel tuning control numbered 28 to 40 and an IR socket. Inside is a comprehensive tuner section, smart card reader mechanism and control electronics plus a power supply section.

These units are sold as strippers but we imagine you could use one to convert a monitor into a TV or maybe use the videocrypt side of things for something else. Supplied complete with manual and mains lead. Clearance price just £9.95 ref BBC1X.



**Introducing our mega magnet  
that lifts 33 kilo's!**

Just in this week are these incredible Neodymium magnets that will lift an incredible 33 kilo's! Each magnet has a threaded bolt protruding from the rear for easy fixing. 32mm diameter. £15 ref MAG33

# VIDEOS ON ELECTRONICS

A range of videos (selected by EPE editorial staff) designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes originate from VCR Educational Products Co, an American supplier. (All videos are to the UK PAL standard on VHS tapes,)

## BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.


**Order Code VT201**

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

**Order Code VT202**

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

**Order Code VT203**

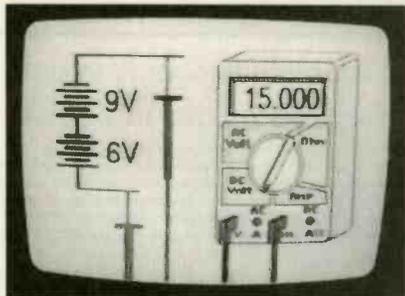

VT204 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply.

**Order Code VT204**

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

**Order Code VT205**

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

**Order Code VT206**

**£34.95** each  
inc. VAT & postage

Order 8 or more get one extra FREE  
Order 16 get two extra FREE

## VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

**Order Code VT102**

VT103 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

**Order Code VT103**

## DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

**Order Code VT301**

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

**Order Code VT302**

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc.

**Order Code VT303**

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits.

**Order Code VT304**

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

**Order Code VT305**

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

**Order Code VT306**



## RADIO

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

**Order Code VT401**  
VT402 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver.

**Order Code VT402**

VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

**Order Code VT403**


## MISCELLANEOUS

VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

**Order Code VT501**

VT502 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO<sub>2</sub> gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning.

**Order Code VT502**

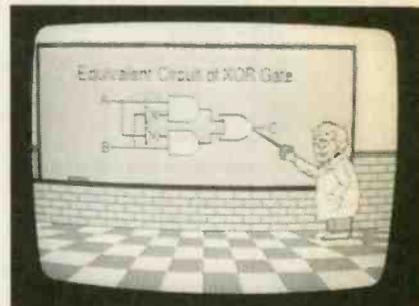

## VIDEO ORDER FORM

Full name: .....

Address: .....

Post code: ..... Telephone No. ....

Signature: .....

I enclose cheque/PO payable to WIMBORNE PUBLISHING LTD

Please charge my Visa/Mastercard: Card expiry date .....

Card No: .....

Please send video order codes: .....

Please continue on a separate sheet of paper if necessary.

**ORDERING: Price includes postage to anywhere in the world.**

**OVERSEAS ORDERS:** We use the VAT portion of the price to pay for airmail postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank).

Send your order to:

Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)

Direct Book Service is a division of Wimborne Publishing Ltd.

Tel: 01202 881749 Fax: 01202 841692

Videos are normally sent within seven days of receipt of order.

E22

# DIRECT BOOK SERVICE

## EPE BOOKS

### ELECTRONICS TEACH-IN 88/89

#### INTRODUCING MICROPROCESSORS

Mike Tooley B.A. (published by *Everyday Practical Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Microprocessors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering popular microprocessors.

And excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment.  
80 pages **Order code TI-88/89** £2.45

### TEACH-IN No. 7. plus FREE SOFTWARE ANALOGUE AND DIGITAL ELECTRONICS COURSE


(published by *Everyday Practical Electronics*)

Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE

This highly acclaimed *EPE Teach-In* series, which included the construction and use of the Mini Lab and Micro Lab test and development units, has been put together in book form. Additionally, EPT Educational Software have developed a GCSE Electronics software program to complement the course and a FREE DISK covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The Mini Lab and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way: you will both see and hear the electron in action! The Micro Lab microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.  
160 pages **Order code T17** £3.95

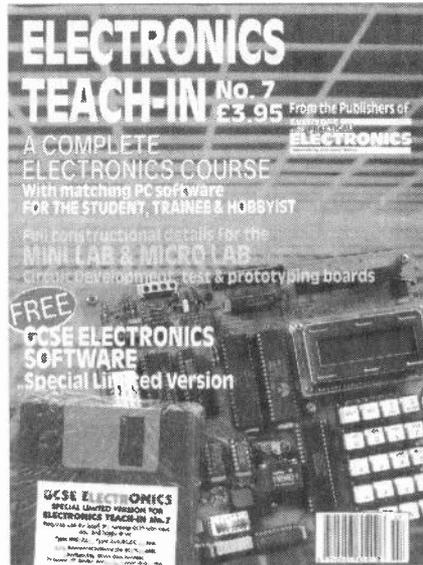

### ELECTRONIC PROJECTS BOOK 1 (published by *Everyday Practical Electronics* in association with *Magenta Electronics*)

Contains twenty projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesizer, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three-Channel Sound to Light, BBC 16K sideways RAM, Simple Short Wave Radio, Insulation Tester, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser, Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider - (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.  
128 pages **Order code EP1** £2.45

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF EPE.

Note our UK postage costs just £1.50 no matter how many books you order!

## RADIO / TV VIDEO

### ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS

R. A. Penfold

This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.  
109 pages **Order code BP356** £4.95

### SETTING UP AN AMATEUR RADIO STATION

I. D. Poole

The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aerials to use; Methods of construction; Preparing for the licence.

An essential addition to the library of all those taking their first steps in amateur radio.  
86 pages **Order code BP300** £3.95

### EXPERIMENTAL ANTENNA TOPICS

H. C. Wright

Although nearly a century has passed since Marconi's first demonstration of radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.  
72 pages **Order code BP278** £3.50

### 25 SIMPLE INDOOR AND WINDOW AERIALS

E. M. Noll

Many people live in flats and apartments or other types of accommodation where outdoor aerials are prohibited, or a lack of garden space etc. prevents aerials from being erected. This does not mean you have to forgo shortwave listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aerials that the author has proven to be sure performers.

Much information is also given on shortwave bands, aerial directivity, time zones, dimensions etc.  
50 pages **Order code BP136** £1.75

## PROJECT COSTRUCTION

### PRACTICAL REMOTE CONTROL PROJECTS

NEW

Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infrared, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.  
160 pages **Order code BP413** £5.99

### PRACTICAL ELECTRONIC MODEL RAILWAY PROJECTS

NEW

R. A. Penfold

The aim of this book is to provide the model railway enthusiast with a number of useful but reasonably simple projects that are easily constructed from readily available components. Stripboard layouts and wiring diagrams are provided for each project. The projects covered include: constant voltage controller; pulsed controller; pushbutton pulsed controller; pulsed controller with simulated inertia, momentum and braking; automatic signals; steam whistle sound effect; two-tone horn sound effect; automatic two-tone horn effect; automatic chuffer.

The final chapter covers the increasingly popular subject of using a computer to control a model railway layout, including circuits for computer-based controllers and signalling systems.  
151 pages **Order code BP384** £4.99

### A PRACTICAL INTRODUCTION TO SURFACE MOUNT DEVICES

NEW

Bill Mooney

This book takes you from the simplest possible starting point to a high level of competence in handworking with surface mount devices (SMD's). The wider subject of SM technology is also introduced, so giving a feeling for its depth and fascination.

Subjects such as p.c.b. design, chip control, soldering techniques and specialist tools for SM are fully explained and developed as the book progresses. Some useful constructional projects are also included.

Whilst the book is mainly intended as an introduction, it is also an invaluable reference book, and the browser should find it engrossing.  
120 pages **Order code BP411** £4.99

### FAULT-FINDING ELECTRONIC PROJECTS

NEW

R. A. Penfold

Starting with mechanical faults such as dry joints, short-circuits etc, coverage includes linear circuits, using a meter to make voltage checks, signal tracing techniques and fault finding on logic circuits. The final chapter covers ways of testing a wide range of electronic components, such as resistors, capacitors, operational amplifiers, diodes, transistors, SCRs and triacs, with the aid of only a limited amount of test equipment.

The construction and use of a Tristate Continuity Tester, a Signal Tracer, a Logic Probe and a CMOS Tester are also included.  
136 pages **Order code NP391** £4.99

### TEST EQUIPMENT CONSTRUCTION

R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:-

AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe.

The designs are suitable for both newcomers and more experienced hobbyists.  
104 pages **Order code BP248** £3.99

### HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books, and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.  
80 pages **Temporarily out of print**

### AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

The purpose of this book is to provide the reader with a wide range of preamplifier and power amplifier designs that will, it is hoped, cover most normal requirements.

The preamplifier circuits include low noise microphone and RIAA types, a tape head preamplifier, a guitar preamplifier and various tone controls. The power amplifier designs range from low power battery operation to 100W MOSFET types and also include a 12 volt bridge amplifier capable of giving up to 18W output.

All the circuits are relatively easy to construct using the p.c.b. or stripboard designs given. Where necessary any setting-up procedures are described, but in most cases no setting-up or test gear is required in order to successfully complete the project.  
100 pages **Temporarily out of print**

# TWO EXCITING NEW BOOKS

Specially imported by *EPE*

## Bebop To The Boolean Boogie

By Clive (call me Max) Maxfield  
ORDER CODE BEB1 £24.95

An Unconventional Guide to Electronics Fundamentals, Components and Processes

The Foreword by Pete Waddell, Editor, *Printed Circuit Design*, reads:

My first exposure to the unique writing style of Clive (call me Max) Maxfield was a magazine article that he co-wrote with an associate. The article was technically brilliant (he paid me to say that) and very informative, but it was the short biography at the end of the piece that I enjoyed the most. I say enjoyed the most because, as you will soon learn, Max does not necessarily follow the herd or dance to the same drummer as the masses. Trade journals have a reputation for being informative and educational but also as dry as West Texas real estate.

Anyway, Max's personally submitted biography not only included a message from his mom, but also made mention of the fact that he (Max) is taller than his co-author, who just happened to be his boss at the time. Now to some people this may seem irrelevant, but to our readers (and Max's boss), these kind of things – trivial as they may seem to the uninitiated – are what helps us to maintain our off-grid sense of the world. Max has become, for better or worse, a part of that alternate life experience.

So now it's a couple of years later, and Max has asked me to write a few words by way of introduction. Personally, I think that the title of this tome

alone (hmmm, a movie?) should provide some input as to what you can expect. But, for those who require a bit more: be forewarned, dear reader, you will probably learn far more than you could hope to expect from *Bebop to the Boolean Boogie*, just because of the unique approach Max has to technical material. The author will guide you from the basics through a minefield of potentially boring theoretical mish-mash, to a Nirvana of understanding. You will not suffer that fate familiar to every reader: re-reading paragraphs over and over wondering what in the world the author was trying to say. For a limey, Max shoots amazingly well and from the hip, but in a way that will keep you interested and amused. If you are not vigilant, you may not only learn something, but you may even enjoy the process. The only further advice I can give is to "expect the unexpected."

*By importing these books ourselves we have managed to make them available in the UK at an exceptional price.*

## Bebop Bytes Back

By Clive "Max" Maxfield and Alvin Brown  
ORDER CODE BEB2 £29.95

An Unconventional Guide To Computers

Plus FREE CD-ROM which includes: Fully Functional Internet-Ready Virtual Computer with Interactive Labs

The Foreword by Lee Felsenstein reads:

This book is not for everyone.

It's for people who want to make a dinosaur dance . . . to exactly the tune that suits them at the moment. Who want to take the most complex, precision-built machines available and make them do something bizarre, inexplicable, or totally unexpected.

It's for people who keep looking for what's underneath the surface, who never stop wondering "how does this work?" And when they find what's underneath, they want to know how that works.

It's for young people, or more exactly, people who haven't grown old. People who don't believe that they've already done everything remarkable they're ever going to do. It's for people with a future.

If you're the right person for this book, you need to know a few facts:

1. The more time you spend with this book and its accompanying CD-ROM, the more you'll get out of it. Skimming through it won't take you where you want to go. Paying serious attention, on the other hand, will teach you more about computers than you can imagine. (You might also see a few beautiful sunrises.)

2. The labs work on two levels: on and under the surface. When you're performing the labs you'll need to look for patterns that build up from individual events.


3. When you're done, you won't look any different. You won't get a trophy or a certificate to hang on your wall. You'll have some knowledge, and some skill, and you'll be ready to find more knowledge and develop more skill. Much of this will be recognisable only to someone who has the same knowledge and skill.

This book will admit you to the company of people who have deep knowledge of computer technology. It is only a beginning (there is no end), and there are many possible directions for you to go.

And this book makes it fun. Written by a couple of wise-cracking English computer engineers with overactive imaginations, it is rich in jokes, trivial information, and overblown vocabulary (with a lexicon). Maxfield and Brown have masterfully made the task of learning computer technology engaging.

Good luck, enjoy your voyage of discovery, and I expect to see some of you in the near future.

bebop

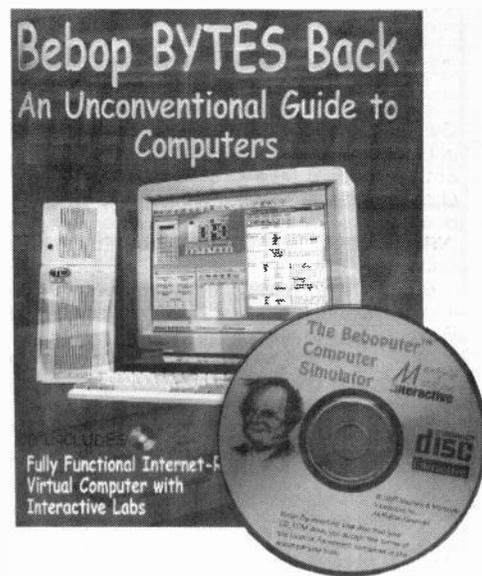

# CIRCUITS AND DESIGN

## AN INTRODUCTION TO PIC MICROCONTROLLERS

Robert Penfold

Designing your own PIC based projects may seem a daunting task, but it is really not too difficult providing you have some previous experience of electronics. The PIC processors have plenty of useful features, but they are still reasonably simple and straightforward to use. This book should contain everything you need to know.

Topics covered include: the PIC register set; numbering systems; bitwise operations and rotation; the PIC instruction set; using interrupts; using the analogue to digital converter; clock circuits; using the real time clock counter (RTCC); using subroutines; driving seven segment displays.

166 pages **Order code BP394** £5.99

## PRACTICAL OSCILLATOR CIRCUITS

A. Flind

Extensive coverage is given to circuits using capacitors and resistors to control frequency. Designs using CMOS, timer i.c.s and op.amps are all described in detail, with a special chapter on "waveform generator" i.c.s. Reliable "white" and "pink" noise generator circuits are also included.

Various circuits using inductors and capacitors are covered, with emphasis on stable low frequency generation. Some of these are amazingly simple, but are still very useful signal sources.

Crystal oscillators have their own chapter. Many of the circuits shown are readily available special i.c.s for simplicity and reliability, and offer several output frequencies. Finally, complete constructional details are given for an audio sinewave generator.

133 pages **Order code BP393** £4.99

## PRACTICAL ELECTRONIC CONTROL PROJECTS

Owen Bishop

Explains electronic control theory in simple, non-mathematical terms and is illustrated by 30 practical designs suitable for the student or hobbyist to build. Shows how to use sensors as input to the control system, and how to provide output to lamps, heaters, solenoids, relays and motors.

Computer based control is explained by practical examples that can be run on a PC. For stand-alone systems, the projects use microcontrollers, such as the inexpensive and easy-to-use Stamp BASIC microcontroller. These projects are chosen to introduce and demonstrate as many aspects as possible of the programming language and techniques.

198 pages **Order code BP377** £5.99

## PRACTICAL ELECTRONICS HANDBOOK -

Fourth Edition. Ian Sinclair

Contains all of the everyday information that anyone working in electronics will need.

It provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Discrete component circuits, Sensing components, Linear I.C.s, Digital I.C.s, Microprocessors and microprocessor systems, Transferring digital data, Digital-analogue conversions, Computer aids in

**NEW**

electronics, Hardware components and practical work, Standard metric wire table, Bibliography, The HEX scale, Index.

440 pages **Order code NE21** £12.99

## COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages **Order code NE10** £3.95

## AUDIO IC CIRCUITS MANUAL

R. M. Marston

A vast range of audio and audio-associated i.c.s are readily available for use by amateur and professional design engineers and technicians. This manual is a guide to the most popular and useful of these devices, with over 240 diagrams. It deals with i.c.s such as low frequency linear amplifiers, dual pre-amplifiers, audio power amplifiers, charge coupled device delay lines, bar-graph display drivers, and power supply regulators, and shows how to use these devices in circuits ranging from simple signal conditioners and filters to complex graphic equalizers, stereo amplifier systems, and echo/reverb delay lines etc.

168 pages **Order code NE13** £13.95

## OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston

A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications

and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages **Order code NE14** £14.99

## OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold

The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA preamplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages **Order code BP335** £4.95

## A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.c. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

The emphasis is on a practical treatment of the subject, and all the circuits are based on "real" CMOS devices. A number of the circuits demonstrate the use of CMOS logic i.c.s in practical applications.

119 pages **Order code BP333** £4.95

# AUDIO AND MUSIC

## INTRODUCTION TO DIGITAL AUDIO

(Second Edition)

Ian Sinclair

Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and

methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages **Order code PC102** £7.95

## PROJECTS FOR THE ELECTRIC GUITAR

J. Chatwin

This book is for anyone interested in the electric guitar. It explains how the electronic functions of the instrument work together, and includes information on the various pickups and transducers that can be fitted. There are complete circuit diagrams for the major types of instrument, as well as a selection of wiring modifications and pickup switching circuits. These can be used to help you create your own custom wiring.

Along with the electric guitar, sections are also included relating to acoustic instruments. The function of specialised piezoelectric pickups is explained and there are detailed instructions on how to make your own contact and bridge transducers. The projects range from simple preamps and tone boosters, to complete active controls and equaliser units.

92 pages **Order code BP358** £4.95

## MIDI SURVIVAL GUIDE

Vic Lennard

Whether you're a beginner or a seasoned pro, the MIDI Survival Guide shows you the way. No maths, no MIDI theory, just practical advice on starting up, setting up and ending up with a working MIDI system.

Over 40 cabling diagrams. Connect synths, sound modules, sequencers, drum machines and multitracks. How to budget and buy secondhand. Using switch, thru and merger boxes. Transfer songs between different sequencers. Get the best out of General MIDI. Understand MIDI implementation charts. No MIDI theory.

104 pages **Order code PC111** £6.95

## PRACTICAL ELECTRONIC MUSICAL

EFFECTS UNITS

R. A. Penfold

This book provides practical circuits for a number of electronic musical effects units. All can be built at relatively low cost, and use standard, readily available components. The projects covered include: Waa-Waa Units; Distortion Units; Phaser; Guitar Envelope Shaper; Compressor; Tremolo Unit; Metal Effects Unit; Bass and Treble Boosters; Graphic Equaliser; Parametric Equaliser. The projects cover a range of complexities, but most are well within the capabilities of the average electronics hobbyist. None of them require the use of test equipment and several are suitable for near beginners.

102 pages **Order code BP368** £4.95

## LOUDSPEAKERS FOR MUSICIANS

Vivan Capel

This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages **Order code BP297** £4.99

## BOOK ORDERING DETAILS

Our postage price is the same no matter how many books you order, just add £1.50 to your total order for postage and packing (overseas readers add £3 for countries in the EEC, or add £6 for all countries outside the EEC, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to **Direct Book Service** or credit card details, Visa or Mastercard - minimum credit card order is £5 - to: **DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET BH21 1RW (mail order only).**

Books are normally sent within seven days of receipt of your order. Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see the next two issues of *EPE*.

**DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD. Tel 01202 881749**

**Fax 01202 841692. Due to the cost we cannot reply to overseas orders or queries by Fax.**

**E-mail:editorial@epemag.wimborne.co.uk**

## BOOK ORDER FORM

Full name: .....

Address: .....

Post code: ..... Telephone No: .....

Signature: .....

I enclose cheque/PO payable to WIMBORNE PUBLISHING LTD for £ .....

Please charge my Visa/Mastercard £ ..... Card expiry date .....

Card Number .....

Please send book order codes:.....

Please continue on separate sheet of paper if necessary

1a

# BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or the next two issues of *Everyday Practical Electronics* (all books with a BP prefix to the order code are Babani books). Many readers have asked us to also supply various other Babani books, which have a reputation for value for money.

Our customers tell us they appreciate our speedy service and low postage charge and they would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (**1.50p for UK p&p no matter how many books you buy**). We are pleased to be able to respond; we are now able to meet *all* your requirements for Babani books – if it's in print we can supply it.

| Code  | Title   | Price  | Code  | Title   | Price  | Code  | Title  | Price |
|-------|---|--------|-------|---|--------|-------|--|-------|
| BP36  | 50 Circuits Using Germanium, Silicon and Zener Diodes   | £1.95  | BP324 | The Art of Soldering  | £3.99  | BP383 | Understanding the Mathematics of Electronics               | £5.99 |
| BP37  | 50 Projects using Relays, SCRs and TRIACs               | £2.95  | BP325 | A Concise Users Guide to Windows 3.1                                    | £4.95  | BP387 | Windows One Step at a Time                                 | £4.95 |
| BP44  | IC 555 Projects   | £3.99  | BP326 | An Introduction to Satellite Communications                             | £5.95  | BP388 | Why Not Personalise Your PC                                | £4.99 |
| BP76  | Power Supply Projects                                   | £3.99  | BP327 | DOS One Step at a Time (covers Version 6.2)                             | £4.99  | BP389 | Power Point for Windows Explained                          | £5.95 |
| BP125 | 25 Simple Amateur Band Aerials                          | £1.95  | BP328 | Sage Explained  | £5.95  | BP390 | An Introduction to the World Wide Web for PC and Mac Users | £6.99 |
| BP132 | 25 Simple SW Broadcast Band Aerials                     | £1.95  | BP329 | Electronic Music Learning Projects                                      | £4.95  | BP395 | PC Software Explained                                      | £5.99 |
| BP144 | Further Practical Electronics Calculations & Formulae   | £4.95  | BP331 | A Beginners Guide to MIDI   | £4.95  | BP398 | Sage Instant Accounting Explained                          | £5.95 |
| BP145 | 25 Simple Tropical and MW Band Aerials                  | £1.75  | BP334 | Magic Electronics Projects  | £4.95  | BP399 | Windows '95 One Step at a Time                             | £4.95 |
| BP182 | MIDI Projects   | £2.95  | BP337 | A Concise Users Guide to Lotus 1-2-3 for Windows                        | £5.95  | BP403 | The Internet and World Wide Web Explained                  | £5.95 |
| BP184 | An Introduction to 68000 Assembly Language              | £2.95  | BP341 | MS-DOS Explained (covers V6.2)  | £6.99  | BP404 | How to Create Pages for the Web Using HTML                 | £5.99 |
| BP192 | More Advanced Power Supply Projects                     | £2.95  | BP343 | A Concise Introduction to Microsoft Works for Windows (Revised Edition) | £5.95  | BP405 | MS Works for Windows 95 explained                          | £5.95 |
| BP198 | An Introduction to Antenna Theory                       | £3.99  | BP345 | Getting Started in Practical Electronics                                | O.O.P. | BP406 | MS-Word 95 Explained                                       | £6.99 |
| BP249 | More Advanced Test Equipment Construction               | £4.99  | BP346 | Programming in Visual BASIC for Windows                                 | £5.95  | BP407 | Excel 95 Explained   | £6.99 |
| BP258 | Learning to Program in C                                | £4.95  | BP349 | Practical Opto-Electronic Projects                                      | £4.95  | BP408 | Access 95 – One Step at a Time                             | £5.99 |
| BP259 | A Concise Introduction to UNIX                          | £4.95  | BP350 | Electronic Board Games  | £4.95  | BP409 | MS Office 95 One Step at a Time                            | £6.99 |
| BP261 | A Concise Introduction to Lotus 1-2-3 (Revised Edition) | £3.95  | BP351 | WordPerfect 6 Explained   | £5.95  | BP410 | 35 Opto-Display Terminal Block Projects                    | £4.99 |
| BP262 | A Concise Introduction to Wordperfect (Revised Edition) | £3.95  | BP352 | Excel 5 Explained   | £5.95  | BP412 | A Practical Approach to Excel for Windows 95               | £4.99 |
| BP273 | Practical Electronic Sensors                            | O.O.P. | BP353 | WordPerfect 6.0 for Windows Explained                                   | £5.95  | BP415 | Using Netscape on the Internet                             | £6.99 |
| BP274 | A Concise Introduction to SuperCalc5 (revised edition)  | £4.95  | BP354 | Word 6 for Windows Explained  | £5.95  | BP416 | Practical Alarm Projects                                   | £4.99 |
| BP275 | Simple Short Wave Receiver Construction                 | £3.95  | BP355 | A Guide to the World's Radio Stations (1995/6 Edition)                  | £5.95  | BP417 | Explaining Microsoft Publisher for Windows 95              | £5.99 |
| BP281 | An Introduction to UHF/VHF for Radio Amateurs           | O.O.P. | BP357 | A Concise Introduction to Pressworks                                    | £5.95  | BP418 | Word 95 Assistant  | £6.99 |
| BP284 | Programming in QuickBASIC (revised edition)             | £5.99  | BP360 | A Practical Introduction to Sage Sterling + 2 for Windows               | £4.95  | BP419 | Using Microsoft Explorer on the Internet                   | £6.99 |
| BP292 | Public Address Loudspeaker Systems                      | O.O.P. | BP361 | Sage Sterling + 2 for Windows Explained                                 | £5.95  | BP420 | E-Mail on the Internet                                     | £6.99 |
| BP293 | An Introduction to Radio Wave Propagation               | £3.95  | BP362 | Access One Step at a Time   | £4.95  | BP421 | Windows 95 Assistant                                       | £6.99 |
| BP298 | A Concise Introduction to the Mac System & Finder       | £3.95  | BP363 | Practical Electronic Music Projects                                     | £4.95  | BP422 | Essentials of Computer Security                            | £5.99 |
| BP301 | Antennas for VHF and UHF                                | £4.95  | BP364 | A Concise Introduction to Designworks 2                                 | £5.95  | BP424 | Microsoft Exchange for Business and Home Use               | £6.99 |
| BP305 | Learning CAD with AutoSketch for Windows                | £5.95  | BP367 | Electronic Projects for the Garden                                      | £4.95  | BP425 | Microsoft Internet Explorer Assistant                      | £5.99 |
| BP306 | A Concise introduction to Am Pro 3 (covers V3.1)        | £5.95  | BP370 | The Superhet Radio Handbook   | £4.95  | BP426 | MS Office 97 Explained                                     | £6.99 |
| BP309 | Preamplifier and Filter Circuits                        | £4.99  | BP372 | CA-SuperCalc for Windows Explained                                      | £5.95  | BP427 | Netscape Internet Navigator Assistant                      | £5.99 |
| BP311 | An introduction to Scanners and Scanning                | £4.99  | BP373 | An Introduction to Networks for PC and Mac Users                        | £5.95  | BP428 | MS Word 97 Explained                                       | £6.99 |
| BP312 | An Introduction to Microwaves                           | £3.95  | BP375 | The Novice Radio Amateurs Examination Handbook                          | £4.95  | BP429 | MS Excel 97 Explained                                      | £6.99 |
| BP313 | A Concise Introduction to Sage                          | £3.95  | BP380 | Advanced Projects For The Electric Guitar                               | £4.99  | BP430 | MS Access 97 – One Step at a Time                          | £5.99 |
| BP315 | An introduction to the Electromagnetic Wave             | £4.95  |       |   |        | BP432 | Simple Sensor Terminal Block Projects                      | £4.99 |
| BP317 | Practical Electronic Timing                             | £4.95  |       |   |        | BP434 | PC Hardware Assistant                                      | £6.99 |
| BP320 | Electronic Projects for Your PC                         | £3.99  |       |   |        | BP435 | Programming in C++   | £6.99 |

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)  
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

## PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749; Fax 01202 841692 (NOTE, we cannot reply to orders or queries by Fax); E-mail: [editorial@epemag.wimborne.co.uk](mailto:editorial@epemag.wimborne.co.uk). Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required – see the *Back Issues* page for details.

Please check price and availability in the latest issue.  
Boards can only be supplied on a payment with order basis.

### Special KNOCK DOWN SALE of PCBs.

We have a few p.c.b.s left from past projects these are being offered at the knock down price of £2.00 each – no matter what size they are (some of these boards are worth over £15.00 each) while stocks last. This price includes VAT and UK post – overseas orders please add 50p postage (or £1 per board for airmail postage).

Bike Odometer (pair of boards), 836/7; Amstrad PCW A to D Converter (double-sided), 838; 1W Stereo Amplifier, 851; Visual Doorbell, 863; CCD TV Camera - Combined Video, Test & Ext Plug Boards, 866a/e; EPE SoundDAC PC Sound Board, 868; Microprocessor Smartswitch, 881; Print Timer, 874; Simple NiCad Charger, 884; Stereo HiFi Controller – Power Supply, 886 – Main Board, 887 – Expansion/Display Boards, (pair) 888; Dancing Fountains – Filter, 891 – PC-Compatible Interface (double-sided), 892; Seismograph – Sensor/Filter, 896 – PC-Compatible Interface (double-sided), 898 – Clock/Mixer, 897; Visual/Audio Guitar Tuner, 900; Audio Auxplexer – Control Board, 903 – Receiver, 904; Power Controller, 905; 1000V/500V Insulation Tester, 906; Active Guitar Tone Control, 907; TV Off-er (pair), 908/909; Video Modules – 1 Simple Fader, 910 – Improved Fader, 911 – Video Enhancer, 912; Rodent Repeller, 913; Video Modules – 4-Channel Audio Mixer, 918; Spacewriter Wand, 921; Universal Digital Code Lock, 922; Video Modules – 3 Dynamic Noise Limiter, 919 – System Mains Power Supply, 920; Magnetic Field Detector, 923.

Any of the above for just £2 each inc. VAT and p&p.

Back numbers or photostats of articles are available see the *Back Issues* page for details.

**£2.00**  
EACH  
inc. VAT  
and p&p

| PROJECT TITLE   | Order Code | Cost   |
|---|------------|--------|
| The Ultimate Screen Saver                                 | 927        | £5.66  |
| Foot-Operated Drill Controller                            | 928        | £5.73  |
| Model Railway Signals                                     | 929        | £5.96  |
| 12V 35W PA Amplifier                                      | 930        | £12.25 |
| Multi-Purpose Thermostat                                  | 931        | £6.30  |
| Multi-Project PCB   | 932        | £3.00  |
| Sound-Activated Switch                                    |            |        |
| Audio Amplifier   |            |        |
| Light Beam Communicator (2 boards required)               |            |        |
| Multi-Project PCB   | 932        | £3.00  |
| Light-Activated Switch                                    |            |        |
| Switch On/Off Timer                                       |            |        |
| Continuity Tester   |            |        |
| Auto Battery Charger                                      | 934        | £5.36  |
| *National Lottery Predictor                               | 935        | £5.34  |
| MIDI Pedal  | 938        | £7.78  |
| Club Vote Totaliser                                       | 939        | £6.05  |
| PIC-DATS Development System (double-sided p.t.h.)         | 940        | £9.90  |
| EPE HiFi Valve Amplifier –                                |            |        |
| Phase splitter  | 941        | £6.71  |
| PIC-DATS 4-channel Light Chaser                           | 942        | £7.90  |
| HV Capacitor Reformer                                     | 943        | £5.60  |
| Ramp Generator  |            |        |
| Logic Board (double-sided p.t.h.) & Analogue board (pair) | 944/5      | £32.00 |
| Automatic Curtain Winder                                  | 946        | £6.75  |
| Windicator  | 947        | £4.10  |
| Microcontrolled 3-Digit Timer                             | 933        | £6.61  |
| IR Remote Control – Transmitter                           | 948        | £5.76  |
| Receiver  | 949        | £6.14  |
| Personal Practice Amplifier                               | 950        | £6.09  |
| Low-Range Ohmmeter Adaptor                                | 926        | £5.55  |
| Simple Theremin   | 952        | £6.68  |
| Vandata   |            |        |
| Boot Control Unit   | 953        | £10.52 |
| Display Unit  | 954        | £6.61  |
| Sound Switch  | 915        | £6.55  |
| Multiple Project PCB                                      | 932        | £3.00  |
| Audio Sinewave Generator                                  |            |        |
| Treble Booster  |            |        |
| Infra-Red Controller/Alarm (2 boards required)            |            |        |
| Capacitor Check   | 955        | £5.76  |
| Ginormous VU Meter  | 956        | £9.31  |
| Multiple Project PCB                                      | 932        | £3.00  |
| Video Enhancer – Current Tracer – Distortion Effects Unit |            |        |
| Digital Delay Line  | 958        | £8.04  |
| 50Hz Field Meter  | 959        | £8.32  |
| Temperature Warning Alarm (Teach-In '96)                  | 960        | £6.15  |

| PROJECT TITLE   | Order Code   | Cost   |
|---|--|--|
| Stereo "Cordless" Headphones<br>Transmitter<br>Receiver<br>*EPE Met Office - Sensor/Rainfall/Vane<br>Spiral transparency free with above p.c.b.   | DEC'95<br>961<br>962<br>963/965                              | £8.04<br>£7.66<br>£11.33                           |
| Light-Operated Switch<br>Modular Alarm System (Teach-In '96)<br>*EPE Met Office -<br>Computer Interface (double-sided)  | JAN'96<br>966<br>967a/b<br>964                               | £6.37<br>£7.12<br>£7.69                            |
| Audio Signal Generator<br>Mains Signalling Unit, Transmitter and Receiver<br>Automatic Camera Panning (Teach-In '96)<br>Printer Sharer  | JAN'96<br>969<br>970/971 (pr)<br>972<br>973                  | £6.58<br>£9.09<br>£6.63<br>£9.93                   |
| Analogue Frequency Meter<br>Vari-Speed Dice (Teach-In '96)<br>Mains Signalling Unit - 2 12V Capacitive PSU<br>*PIC-Electric Meter - Sensor/PSU - Control/Display  | FEB'96<br>957<br>974<br>975<br>977/978 (pr)                  | £6.70<br>£5.69<br>£6.07<br>£9.90                   |
| Multi-Purpose Mini Amplifier<br>*PIC-Electric - Sensor/PSU - Control/Display<br>High Current Stabilised Power Supply<br>Mind Machine Mk III - Sound and Lights<br>Infra-Zapper Transmitter/Receiver<br>(Teach-In '96) | MAR'96<br>976<br>977/978 (pr)<br>979<br>980<br>981/982 (pr)  | £6.12<br>£9.90<br>£6.62<br>£7.39<br>£8.01          |
| Mind Machine Mk III - Programmer<br>Bat Band Converter/B.F.O.<br>Hearing Tester<br>Event Counter (Teach-In '96)   | APR'96<br>983<br>984a/b<br>985<br>986                        | £7.36<br>£5.80<br>£6.87<br>£8.39                   |
| B.F.O. and Bat Band Converter<br>Versatile PIR Detector Alarm<br>Mind machine Mk III - Tape Controller<br>Midi Analyser<br>Countdown Timer (Teach-In '96)   | MAY'96<br>984a/b<br>988<br>989<br>992<br>993                 | £5.80<br>£6.76<br>£6.70<br>£6.74<br>£9.44          |
| Sarah's Light<br>Home Telephone Link<br>*PulStar<br>VU Display and Alarm  | JUNE'96<br>996<br>997 (pr)<br>998<br>999                     | £7.17<br>£10.72<br>£6.60<br>£7.02                  |
| Ultra-Fast Frequency Generator<br>and Counter - Oscillator/L.C.D. Driver<br>Timed NiCad Charger<br>Single-Station Radio 4 Tuner<br>Twin-Beam Infra-Red Alarm - Transmitter/Receiver<br>*Games Compendium              | JULY'96<br>994/995 (pr)<br>100<br>101<br>102/103 (pr)<br>104 | £12.72<br>£6.99<br>£7.02<br>£10.50<br>£6.09        |
| Mono "Cordless" Headphones<br>- Transmitter/Receiver<br>Component Analyser (double-sided p.t.h.)<br>Garden Mole-Ester<br>Mobile Miser<br>Bike Speedo  | AUG'96<br>990/991 (pr)<br>105<br>106<br>107<br>108           | £10.16<br>£12.18<br>£6.07<br>£6.36<br>£6.61        |
| *PIC-Tock Pendulum Clock<br>Power Check<br>Analogue Delay/Flanger<br>Draught Detector<br>Simple Exposure Timer  | FEB'96<br>109<br>110<br>111<br>112<br>113                    | £6.31<br>£6.42<br>£7.95<br>£6.22<br>£6.63          |
| Video Fade-to-White<br>Direct Conversion 80m Receiver<br>Vehicle Alert<br>10MHz Function Generator - Main Board<br>- PSU  | OCT'96<br>114<br>116<br>117<br>118<br>119                    | £6.98<br>£7.52<br>£6.55<br>£7.33<br>£5.39          |
| Tuneable Scratch Filter<br>*Central Heating Controller<br>D.C. to D.C. Converters - Negative Supply Generator<br>- Step-Down Regulator<br>- Step-Up Regulator   | NOV'96<br>115<br>120<br>122<br>123<br>124                    | £7.83<br>£7.85<br>£5.96<br>£6.01<br>£6.12          |
| EPE Elysian Theremin<br>(double-sided p.t.h.)<br>*PIC Digital/Analogue Tachometer<br>Stereo Cassette Recorder<br>Playback/PSU<br>Record/Erase   | DEC'96<br>121<br>127<br>128<br>129                           | £22.00<br>£7.23<br>£7.94<br>£9.04                  |
| *Earth Resistivity Meter<br>Current Gen. - Amp/Rect.<br>Theremin MIDI/CV Interface (double-sided p.t.h.)<br>Mains Failure Warning   | JAN'97<br>131/132 (pr)<br>130 (set)<br>126                   | £12.70<br>£40.00<br>£6.77                          |
| Pacific Waves<br>PsiCom Experimental Controller   | FEB'97<br>136<br>137   | £9.00<br>£6.78                                     |
| Oil Check Reminder<br>Video Negative Viewer<br>Tri-Colour NiCad Checker<br>Dual-Output TENS Unit (plus Free TENS info.)   | MAR'97<br>125<br>135<br>138<br>139                           | £7.16<br>£6.75<br>£6.45<br>£7.20                   |
| *PIC-Agoras - Wheelie Meter<br>418MHz Remote Control - Transmitter<br>- Receiver<br>Puppy Puddle Probe<br>MIDI Matrix - PSU<br>- Interface  | APRIL'97<br>141<br>142<br>143<br>145<br>147<br>148           | £6.90<br>£5.36<br>£6.04<br>£6.10<br>£5.42<br>£5.91 |
| Quasi-Bell Door Alert<br>2M F.M. Receiver<br>*PIC-A-Tuner<br>Window Closer - Trigger<br>- Closer  | MAY'97<br>133<br>144<br>149<br>150<br>151                    | £6.59<br>£7.69<br>£7.83<br>£4.91<br>£4.47          |

| PROJECT TITLE   | Order Code                                 | Cost   |
|---|--|--|
| Child Minder Protection Zone<br>- Transmitter<br>- Receiver<br>Pyrotechnic Controller<br>*PIC Digilogic Clock<br>Narrow Range Thermometer   | JUN'97<br>153<br>154<br>155<br>156<br>158  | £6.58<br>£6.42<br>£6.93<br>£7.39<br>£6.37          |
| Micropower PIR Detector - 1<br>Infra-Red Remote Control Repeater<br>(Multi-project P.C.B.)<br>Karaoke Echo Unit - Echo Board<br>- Mixer Board<br>Computer Dual User Interface<br>*PEST Scarer | JULY'97<br>932<br>159<br>160<br>161<br>162 | £6.69<br>£3.00<br>£6.40<br>£6.75<br>£6.70<br>£6.60 |
| Variable Bench Power Supply<br>Universal Input Amplifier<br>Micropower PIR Detector - 2 Controller<br>*PIC-OLO  | AUG'97<br>932<br>146<br>163<br>164         | £3.00<br>£6.55<br>£6.72<br>£7.02                   |
| Active Receiving Antenna<br>Soldering Iron Controller<br>*PIC Noughts & Crosses Game<br>Micropower PIR Detector - 3<br>Alarm Disarm/Reset Switch<br>Ironing Safety Device                     | SEPT'97<br>140<br>157<br>165<br>166<br>167 | £6.59<br>£6.63<br>£7.82<br>£5.72<br>£5.12          |
| Remote Control Finder<br>Rechargeable Handlamp<br>*PIC Water Descaler   | OCT'97<br>168<br>169<br>170                | £6.32<br>£6.23<br>£6.90                            |
| *EPE Time Machine<br>Auto-Dim Bedlight<br>Portable 12V PSU/Charger  | NOV'97<br>171<br>172<br>173                | £8.34<br>£6.63<br>£6.61                            |
| Car Immobiliser<br>Safe and Sound (Security Bleeper)  | DEC'97<br>175<br>179                       | £7.00<br>£7.32                                     |
| Surface Thermometer<br>Disco Lights Flasher   | JAN'98<br>174<br>178                       | £7.64<br>£8.30                                     |
| Waa-Waa Pedal (Multi-project PCB)<br>*Virtual Scope - 1<br>Digital Board<br>Analogue Board (per board)<br>*Water Wizard<br>Kissometer   | FEB'98<br>932<br>176<br>177<br>180<br>181  | £3.00<br>£14.49<br>£7.34<br>£7.69<br>£7.67         |

## EPE SOFTWARE

Software programs for the EPE projects marked above with an asterisk (\*) are available altogether on a single 3.5 inch PC-compatible disk, or as needed via our Internet site. The same disk also contains the following additional software: Simple PIC16C84 Programmer (Feb '96). The disk (order as "PIC-disk") is available from the EPE PCB Service at £2.75 (UK) to cover our admin costs (the software itself is free). Overseas £3.35 surface mail, £4.35 airmail. Alternatively, the files can be downloaded Free from our Internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.

## EPE PRINTED CIRCUIT BOARD SERVICE

Order Code      Project      Quantity      Price

Name.....

Address.....

I enclose payment of £..... (cheque/PO in £ sterling only) to:

Everyday  
Practical Electronics  
Access (MasterCard) or Visa No.  
Minimum order for credit cards £5

Signature..... Card Exp. Date.....

Please supply name and address of cardholder if different from the address shown

NOTE: You can order p.c.b.s via our Internet site on a secure server:  
<http://www.epemag.wimborne.co.uk>

# ELECTRONICS

Everyday Practical Electronics reaches nearly twice as many UK readers as any other independent monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading independent monthly magazine in this market for the last thirteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

## RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY

Up to 38 volts d.c. at 6 amps continuous, 10 amps peak, fully variable from 1 to 38 volts. Twin Voltage and Current meters for easy read-out. 240 volt a.c. input. Fully smoothed, size 14½ x 11 x 4½ inches. 20 volt 1 amp model £44, post £4.



£76 inc. VAT carriage £6

## RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON SURREY, CR0 2HS. Tel: 0181-684 1665

Lots of transformers, high volt caps, valves, speakers, in stock. Phone or send your wants list for quote.

## LIGHT ENGINEERING SERVICES (PRECISION)

Machining, sheet metalwork, instrument/toolmaking etc – most engineering processes in most materials. One offs, parts, prototypes, panels, mods, jigs, repairs, anything – no job too small – trade or private – for quick friendly service contact Richard:

Tel/Fax: 01954 260804

## BTEC ELECTRONICS TECHNICIAN TRAINING

GNVQ ADVANCED ENGINEERING (ELECTRONIC) – PART-TIME  
HND ELECTRONICS – FULL-TIME  
B.Eng FOUNDATION – FULL-TIME

Next course commences  
Monday 2nd February 1998  
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE  
(Dept EPE) 20 PENYERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: 0171-373 8721

## BRAND NEW SINCLAIR SPECTRUM & QL PARTS

ZX MICRODRIVES £15, INTERFACE ONE £20, CARTRIDGES 10 FOR £15, 50 FOR £50.

QL BOARDS 5, 6 & 7, POPULATED WITH JS ROMS, £30; UNPOPULATED, £12; MICRODRIVES £10 EACH. TOP & BOTTOM CASES £15, MEMBRANES £15.

THE P.C., MAC and QL's "Little Friend" MAC LINK £10 – P.C. LINK £25 – QL LINK £12

CAMBRIDGE 288 A4 NOTEBOOK COMPUTER AVAILABLE AGAIN £99, RECONDITIONED £60

ONLY 1" THICK, 4xAA BATTs, 20 HOURS WORK. LCD SCREEN, 72 Cs, 6 LINES, 32K RAM, EXTRA RAMS & EPROMS, 9 pin D SERIAL PORT, ROM HAS BBC BASIC, W/PROCESSOR, SPREADSHEET, DATA BASE, IMP/EXPORT TO PC etc, V52 TERMINAL.

W.N. RICHARDSON & CO.

PHONE/FAX 01494 871319  
6 RAVENSMEAD, CHALFONT ST PETER, BUCKS, SL9 0NB.  
POST £5. ACCESS, VISA, ETC. SAE

## THE BRITISH AMATEUR ELECTRONICS CLUB

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.

For membership details, write to the Secretary:

Mr. J. F. Davies, 70 Ash Road, Cuddington, Northwich, Cheshire CW8 2PB.

Space donated by Everyday Practical Electronics

## Miscellaneous

**PRINTED CIRCUIT BOARDS – QUICK SERVICE.** Prototype and Production. Artwork raised from magazines or draft designs at low cost. PCBs also designed from schematics. Production assembly also undertaken. For details send to P. Agar, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX, or phone/fax 01232 738897.

**ANYONE REPAIRING TOYOTA/other engine management control units, car spares marketing/distribution company seeks supplier.** Malcolm Jackson, Phone/Fax 0181 467 6671.

**L.C.D. TEMPERATURE GAUGE,** 80mm x 40mm x 10mm, reads 0-199°C, high/low temp., display alarm, low battery, sleep, requires battery, thermistor, case. Full instructions supplied. £23.50 inc. VAT and P&P. Phone or Fax for details: 015395 34503.

**VALVE ENTHUSIASTS:** Capacitors and other parts in stock. For free advice/lists please ring. Geoff Davies (Radio), Tel. 01788 574774.

**75 WATT AMPLIFIER MODULES,** glass p.c.b. + heatsink + directions, ex-equipment £5. K.I.A., 1 Regent Road, Ilkley, LS29 9EA.

**PROTOTYPE PRINTED CIRCUIT BOARDS** one offs and quantities, for details send s.a.e. to B. M. Ansbroy, 38 Poyning Drive, Hove, Sussex BN3 8GR, or phone Brighton 883871, fax 01273 706670.

**G.C.S.E. ELECTRONIC KITS,** at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB.

**TREAT YOURSELF – £5 EACH!!** Pre-amplifier + sliders, TB + V!! 30 watt stereo amplifier + controls!! Regulated PSU 12-40V!! K.I.A., 1 Regent Road, Ilkley, LS29 9EA.

**LOW COST ELECTRONIC PROJECT KITS.** Alarms to sound effects to power supplies. Make ideal gifts. Skill level from novice to expert. S.A.E. for FREE catalogues. B. A. Newton, 303 Gleneagles Park, Hull, HU8 9JT.

**PRACTICAL ELECTRONICS VOL. 1, No. 1** (November '64) to August '69 complete, except January '68, reasonable condition. Offers to 01243 822986.

**PLASTIC MOULDING.** Low cost tooling, no minimum quantity. To discuss your requirements phone/fax Economic Mouldings on 01685 874763.

## EPE NET ADDRESSES

**EPE FTP site:** <ftp://ftp.epemag.wimborne.co.uk>

Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:

PIC-project source code files: **/pub/PICS**

PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. *Do not try to download the folder itself!*

**EPE text files: /pub/docs**

Basic Soldering Guide: **solder.txt**

**EPE TENS Unit** user advice: **tens.doc** and **tens.txt**

**Ingenuity Unlimited** submission guidance: **ing\_unlt.txt**

New readers and subscribers info: **epe\_info.txt**

Newsgroups or Usenet users advice: **usenet.txt**

Ni-Cad discussion: **nicadfaq.zip** and **nicad2.zip**

UK Sources FAQ: **uksource.zip**

Writing for **EPE** advice: **write4us.txt**

Ensure you set your FTP software to ASCII transfer when fetching text files, or they may be unreadable.

**EPE Website:** <http://www.epemag.wimborne.co.uk>

Check it for up-to-date information on FAQs, subscribing, buying PCBs and Back Issues via our new Secure Server.

**E-mail addresses:**

Circuit Surgery: **alan@epemag.demon.co.uk**

Reader services: **editorial@epemag.wimborne.co.uk**

Teach-In '98, queries and feedback:

**Teach\_In98@epemag.demon.co.uk**

Webmaster, for comments and feedback about the web and FTP sites:

**webmaster@epemag.demon.co.uk**

## TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your

Electrical Contracting & Installation  
Electrical Engineering  
C&G Basic Electronic Engineering  
C&G Basic Mechanical Engineering  
TV and Video Servicing  
Radio and Hi-Fi Servicing  
Refrigeration Heating & Air Conditioning  
Motorcycle Maintenance

**FREEPHONE 0500 581 557**

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Clydesway Skypark, Glasgow, G3 8BR. Tel. 0500 581 557 or Tel/Fax: Ireland 01 285 2533.

Please send me my Free Information on your Electronics Courses.

Mr/Mrs/Ms/Miss (BLOCK CAPITALS PLEASE) \_\_\_\_\_ Date of Birth: / / \_\_\_\_\_  
Address \_\_\_\_\_  
Postcode \_\_\_\_\_  
Occupation \_\_\_\_\_ Tel. No. \_\_\_\_\_

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box  Dept. ZEEE060198



## 88-108MHz FM TRANSMITTERS

Professional PLL transmitter, Stereo Coder, and Compressor/Limiter kits licensable in the UK.

Also very stable VFO transmitter kits.

Prices from under £10 and a 'Ready Built' service is available.

Contact us for a free brochure including prices and more detailed information.



18 Victoria St., Queensbury, BRADFORD, BD13 1AR



Tel 01274 816200 Email veronica@legend.co.uk  
Website: <http://www.legend.co.uk/~veronica/>

## TECHNICAL INFORMATION SERVICES

76 Church St, Larkhall, Lanarks, ML9 1HE  
Tel: 01698 883334/884585 Fax: 01698 884825

PHONE NOW FOR YOUR FREE QUOTE

**We have the World's Largest Collection of**

## SERVICE MANUALS

**Why not join Europe's fastest growing "Information Library Service"**

Buy ANY Service Manual for £10.00 and return any manual no longer needed for a £5.00 credit

CALL/WRITE NOW FOR FURTHER DETAILS

Initial joining fee of £65 : Thereafter £20 Yearly  
Join Now: Get your first Manual FREE!

## COMPONENTS FROM H.S.T.

HST SUPPLIER OF RESISTORS, CAPACITORS, L.E.D.s, CRYSTALS, SEMICONDUCTORS, SWITCHES, CABLE, SECURITY PRODUCTS ETC.

SEND OR FAX YOUR PARTS LIST REQUIREMENTS FOR PRICES.

1997 catalogue £1.50 FREE WITH FIRST ORDER

H.S.T. LTD, UNIT 4, FREETH COURT, FREETH STREET, NOTTINGHAM NG2 3GU

TEL. 01159 851810 FAX 01159 562142

## SERVICE MANUALS & Technical Books

Available for most equipment, any make, age or model.  
Technical Book and Manual Compilations now on CD-ROM  
Return the coupon for your FREE catalogue on Floppy Discs.

PRICE CRASH ON ALL OUR CD-ROM's

**MAURITRON TECHNICAL SERVICES (EPE)**  
8 Cherry Tree Road, Chinnor, Oxon, OX9 4PY.  
Tel:- 01844-351694. Fax:- 01844 352554.

Email:- sales@mauritron.co.uk Web site at:- <http://dialspace.dial.pipex.com/mauritron/>  
Please forward your latest Disc catalogue for which I enclose 4 x 1st Class Stamps.  
or £5.00 for the complete Service Manuals Index on PC Disc plus catalogue.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

POSTCODE \_\_\_\_\_

Photocopy this coupon if you do not wish to cut the magazine

## MEL BASIC Compiler for PICs

**Takes the hassle out of working with PICs!**

With MEL PicBasic just write your code in Basic, and then instantly compile it to produce the hex or binary files needed to program your standard 18, 28 or 40 pin PIC chip.

English-like instructions make programming a joy instead of a struggle - serial comms, if/then, pulse measurement, time delays, etc., etc., each takes just one command!

Comprehensive user manual.

More info on the web at <http://www.melabs.com/mel/pbc.htm>

Mail order only from  
**Pineapple Presentations**  
30 Breckhill Road  
Nottingham NG5 4GP  
Tel. 0115 903 1851  
Fax 0115 903 2172

**£79.95**

plus £3.00 p&p per order



## COVERT VIDEO CAMERAS

Black and White Pin Hole Board Cameras with Audio. Cameras in P.I.R., Radios, Clocks, Briefcases etc. Transmitting Cameras with Receivers (Wireless). Cameras as above with colour. Audio Surveillance Kits and Ready Built Units, Bug Detector etc.

## A.L. ELECTRONICS

Please phone 0181 203 0161 for free catalogue.

Fax 0181 201 5359

New DTI approved Video Transmitters and Receivers (Wireless)

## N. R. BARDWELL LTD (EPE)

|     |  |       |     |   |       |
|-----|--|-------|-----|---|-------|
| 100 | Signal diodes 1N4148.....                                  | £1.00 | 80  | Asstd. capacitors 1nF to 1µF.....                       | £1.00 |
| 75  | Rectifier Diodes 1N4001.....                               | £1.00 | 200 | Asstd. disc ceramic capacitors.....                     | £1.00 |
| 50  | Rectifier Diodes 1N4007.....                               | £1.00 | 50  | Asstd. Sikel Presets (sm, stand, cermet).....           | £1.00 |
| 10  | W01 Bridge Rectifiers.....                                 | £1.00 | 50  | Asstd. RF chokes (inductors).....                       | £1.00 |
| 5   | NE555 Timer I.C.s.....                                     | £1.00 | 50  | Asstd. grommets.....                                    | £1.00 |
| 4   | 741 Op Amps.....   | £1.00 | 80  | Asstd. solder tags, p/cons, terminals.....              | £1.00 |
| 50  | Assorted Zener Diodes 400mW.....                           | £1.00 | 10  | Asstd. crystals - plug in.....                          | £1.00 |
| 12  | Assorted 7-segment Displays.....                           | £1.00 | 24  | Asstd. coil formers.....                                | £1.00 |
| 25  | 5mm l.e.d.s, red, green or yellow.....                     | £1.00 | 8   | Asstd. di1 switches.....                                | £1.00 |
| 25  | 3mm l.e.d.s, red, green or yellow.....                     | £1.00 | 20  | Miniature slide switches sp/co.....                     | £1.00 |
| 50  | Axial l.e.d.s, 2mpd red Diode Package.....                 | £1.00 | 10  | Standard slide switches dp/dt.....                      | £1.00 |
| 25  | Asstd. High Brightness l.e.d.s, var coils.....             | £1.00 | 30  | Asstd. if transformers.....                             | £1.00 |
| 20  | BC182L Transistors.....                                    | £1.00 | 100 | Asstd. beads (ceramic, teflon, fish spine).....         | £1.00 |
| 25  | BC212L Transistors.....                                    | £1.00 | 80  | Asstd. small stand offs, Uthroughs etc.....             | £1.00 |
| 30  | BC237 Transistors.....                                     | £1.00 | 30  | Asstd. di1 sockets up to 40 way.....                    | £1.00 |
| 20  | BC327 Transistors.....                                     | £1.00 | 10  | TV coax plugs, plastic.....                             | £1.00 |
| 30  | BC328 Transistors.....                                     | £1.00 | 20  | Small spring loaded terminals.....                      | £1.00 |
| 30  | BC547 Transistors.....                                     | £1.00 | 40  | metres very thin connecting wire, red.....              | £1.00 |
| 30  | BC548 Transistors.....                                     | £1.00 | 20  | 1in. glass reed switches.....                           | £1.00 |
| 30  | BC549 Transistors.....                                     | £1.00 | 20  | Magnetic ear pins with lead and plug.....               | £1.00 |
| 25  | BC557 Transistors.....                                     | £1.00 | 100 | Any one value 1/4W 5% cf resistors range 1R to 10M..... | £0.45 |
| 30  | BC558 Transistors.....                                     | £1.00 |     |   |       |
| 30  | BC559 Transistors.....                                     | £1.00 |     |   |       |
| 20  | 2N3904 Transistors.....                                    | £1.00 |     |   |       |
| 100 | 50v wkg Axial Capacitors 1nF.....                          | £1.00 |     |   |       |
| 100 | 50v wkg Axial Capacitors 4n7.....                          | £1.00 |     |   |       |
| 100 | 50v wkg sub-miniature Capacitors 33nf.....                 | £1.00 |     |   |       |
| 100 | Radial Film Capacitor 22nf.....                            | £1.00 |     |   |       |
| 12  | luf 250v encapsulated radial plastic cased capacitors..... | £1.00 |     |   |       |
| 80  | Asstd capacitors electrolytic.....                         | £1.00 |     |   |       |

Prices include VAT, postage £1.25. 3p stamp for Lists

288 Abbeydale Road, Sheffield S7 1FL

Phone (0114) 2552886 Fax (0114) 2500689

E-mail [Bardwell@compuserve.com](mailto:Bardwell@compuserve.com)

Web site: <http://ourworld.compuserve.com/homepages/BARDWELLS>

**DREMEL** ONE OF THE UK'S LARGEST  
**X-ACTO MINICRAFT** INDEPENDENT DREMEL DEALERS! (E&OE)  
2yr Guarantee!

DREMEL D-3950 Multi-Tool Set w/40 Accs. £89.00  
Free £10 Voucher with every D-3950  
Please ask for further details

D-1371 Precision Scroll Saw £139.95  
D-1731 Moto Sander £139.95  
NEW!! D-7701 Cordless Multi w/25 Accs £54.95  
D-225 Flexible Shaft £36.50

MINICRAFT MB Variable Speed Fretsaw £104.99

X-ACTO FULL range of Knives & Blades from £1.25

**VENTURA**  
H O B B Y  
It's our business to know your hobby

134 CROSSLET VALE, LONDON, SE10 8DL. TEL: 0181-694 9913 FAX: 0181-691 4399

Quad speed Toshiba 1/3rd height SCSI cd-rom drives.....£20 each, 6 for £100  
1 meg. 30-pin parity simms.....£3.75 each, 4 for £12  
4 meg. 30-pin parity simms.....£13 each, 4 for £50  
Trident 512k video cards.....£12 each  
Trident 1mb VLB video cards.....£20 each  
Future Domain SCSI I controller cards.....£15 each  
Internal VGA leads.....£2.50 each, 10 for £20  
Sim Isle on cd-rom.....£5  
10 memory BT approved phones.....£7.50 each  
BT approved phone and answer machine.....£20  
3lb mixed component pack.....£4.95  
Jumbo component pack.....£10  
250 off mixed capacitors.....£4.95  
250 off i.c. sockets.....£3.95  
1000 off mixed ceramic caps.....£7.50  
20 off mixed crystals/filters.....£4.95  
25 off mixed relays.....£3.50  
Brand new 360k 5 1/4" floppy drive.....£4.50  
5 1/4" to 3 1/2" floppy drive converter leads.....£1.50\*  
1-2MB 5 1/4" floppy drive.....£10  
12V d.c. 200 r.p.m. geared motor.....£1.50 each, 10 for £12  
220V 1500 r.p.m. geared motor.....£6 each, 10 for £50  
7V-12V d.c. motor, 4/6000 r.p.m. 700mA-1450mA.....£4 each, 10 for £30

12V d.c. motor, 13,000 r.p.m. 180mA.....£1 each, 10 for £8  
6V d.c. motor, 1,200 r.p.m. 600mA.....£1 each, 10 for £8  
9V d.c. motor, 13,000 r.p.m. 460mA.....£1 each, 10 for £8  
10-5V d.c. motor, 9,000 r.p.m., 220mA.....£1 each, 10 for £8  
S.M. P.S.U., mains input, +5-2V 6A, +24V 0-5A, +24V 5-5A outputs.....£6 each

**QUANTITY DISCOUNTS AVAILABLE PLEASE RING.**  
We also buy all forms of electronic components, p.s.u.'s, disk drives etc.  
Lists to below address.

**ALL PRICES INCLUDE V.A.T.**  
**PLEASE ADD £2.00 p&p EXCEPT ITEMS MARKED \* WHICH ARE 50P.**  
**SAE FOR BULK BUYING LIST PAYMENT WITH ORDER TO:**  
**Dept EE, COMPELEC,**  
**14 Constable Road,**  
**St. Ives, Huntingdon,**  
**Cambs PE17 6EQ**  
**Tel/Fax: 01480 300819**

**Millions of quality components at lowest ever prices!**

Plus anything from bankruptcy – theft recovery – frustrated orders – over production etc.  
**NO VAT to add on.**  
Send 45p stamped self addressed label or envelope for clearance lists.

**Brian J Reed**  
**6 Queensmead Avenue, East Ewell**  
**Epsom, Surrey KT17 3EQ**  
**Tel: 0181-393 9055 Mail order UK only.**

Lists are updated and only 40 are sent out every 2 weeks. This normally ensures that orders can be fulfilled where only a few thousand of an item is available. (Payment is returned if sold out. I do not deal in credit notes). This will sometimes entail a delay of up to eight weeks – but the prices will be worth the wait!

**Program your PIC12C508/9s**


Visible Sound's Pentium Friendly PIC programmer will program the PIC12C508/9, PIC16C71/84. The programmer includes a ZIF socket to easily mount the device to be programmed. (H137A).

**All this for only £25 inc. P&P (UK Only) and VAT.**  
**25 way M/M cable £6 (A057A). Power Supply £5 (A061A).**

| Qty→           | 1     | 10    | 50    | 1            | 10     | 50     |        |
|----------------|-------|-------|-------|--------------|--------|--------|--------|
| PIC12C508-04/P | £2.30 | £2.00 | £1.88 | PIC12C508/JW | £13.50 | £12.00 | £11.00 |
| PIC12C509-04/P | £2.70 | £2.40 | £2.20 | PIC12C509/JW | £15.00 | £13.50 | £12.50 |
| PIC16C71-04/P  | £6.99 | £6.00 | £4.50 | PIC16C71/JW  | £25.00 | £20.00 | £15.00 |
| PIC16C84       | £6.00 | £5.50 | £4.50 |              |        |        |        |
| 24C16          | £2.49 | £2.00 | £1.05 | 24C65        | £6.00  | £4.50  | £2.50  |

Visible Sound Ltd., 151, The Exchange Building, Mount Stuart Square, Cardiff, CF1 6EB. Tel (01222) 458417. Fax (01222) 480326. email [Info@vsltec.demon.co.uk](mailto:Info@vsltec.demon.co.uk). WWW <http://www.vsltec.demon.co.uk>.

**A scope at your fingertips**

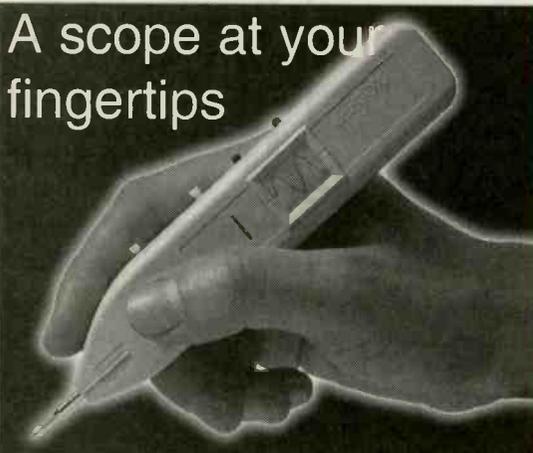

Oscilloscopes are becoming smaller and lighter, now Pico Technology brings you the latest development, the **osziFOX** hand held scope.

- ▶ Sample rates from 50ns to 1 ms
- ▶ Can connect to a PC via serial port
- ▶ Voltmeter (AC and DC)
- ▶ Backlit LCD display

**£80** Unit is supplied with appropriate cables and software disk.  
Complete price £98.11 including VAT and £3.50 P&P (UK).

**Pico Technology Limited, Broadway House, 149-151 St. Neots Rd, Hardwick, Cambridge, CB3 7QJ UK**  
Tel: 01954 -211716 Fax: 01954 -211880  
E-mail: [post@picotech.co.uk](mailto:post@picotech.co.uk) <http://www.picotech.com>

**Pico**  
Technology Limited

**ADVERTISERS INDEX**

|                                     |                |
|-------------------------------------|----------------|
| A. L. ELECTRONICS.....              | 159            |
| ARMEX ELECTRONICS.....              | 103            |
| N. R. BARDWELL.....                 | 159            |
| BETA LAYOUT.....                    | 131            |
| B.K. ELECTRONICS.....               | Cover (iii)    |
| BRIAN J. REED.....                  | 160            |
| BULL ELECTRICAL.....                | Cover (ii)/151 |
| CIRKIT DISTRIBUTION.....            | 146            |
| COMPELEC.....                       | 160            |
| DISPLAY ELECTRONICS.....            | 82             |
| EPT EDUCATIONAL SOFTWARE.....       | 98             |
| ESR ELECTRONIC COMPONENTS.....      | 90             |
| GREENWELD.....                      | 103            |
| H.S.T.....                          | 159            |
| ICS.....                            | 159            |
| J&N FACTORS.....                    | 86             |
| JPG ELECTRONICS.....                | 147            |
| LABCENTER ELECTRONICS.....          | 120            |
| MAGENTA ELECTRONICS.....            | 88/89          |
| MAPLIN ELECTRONICS.....             | Cover (iv)     |
| MAURITRON.....                      | 159            |
| NATIONAL COLLEGE OF TECHNOLOGY..... | 144            |
| THE PC SOLUTION.....                | 109            |
| PEAK ELECTRONIC DESIGN.....         | 119            |
| PICO TECHNOLOGY.....                | 144/146/160    |
| PINEAPPLE PRESENTATIONS.....        | 159            |
| QUICKROUTE SYSTEMS.....             | 97             |
| RADIO-TECH.....                     | 144            |
| RD RESEARCH.....                    | 87             |
| SEETRAX CAE.....                    | 85             |
| SERVICE TRADING CO.....             | 147            |
| SHERWOOD ELECTRONICS.....           | 123            |
| SQUIRES.....                        | 103            |
| STEWART OF READING.....             | 85             |
| SUMA DESIGNS.....                   | 84             |
| TECHNICAL INFORMATION SERVICES..... | 159            |
| VENTURA HOBBY.....                  | 160            |
| VERONICA KITS.....                  | 159            |
| VISIBLE SOUND.....                  | 160            |

**ADVERTISER MANAGER:** PETER J. MEW  
**ADVERTISER OFFICES:**  
EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS,  
MILL LODGE, MILL LANE, THORPE-LE-SOKEN,  
ESSEX CO16 0ED.  
Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 91.

Published on approximately the first Friday of each month by Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Printed in England by Wiltshire (Bristol) Printers Ltd., Bristol, BS20 9XP. Distributed by Seymour, Windsor House, 1270 London Road, Norbury, London SW16 4DH. Subscriptions INLAND £26 and OVERSEAS £32 standard air service (£49.50 express airmail) payable to "Everyday Practical Electronics", Subs Dept, Allen House, East Borough, Wimborne, Dorset BH21 1PF. EVERYDAY PRACTICAL ELECTRONICS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade or more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

**POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS**

★ PRICES INCLUDE V.A.T. ★ PROMPT DELIVERIES ★ FRIENDLY SERVICE ★ LARGE (A4) S.A.E. 60p STAMPED FOR CATALOGUE ★

**OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK**

**THOUSANDS PURCHASED BY PROFESSIONAL USERS**



**THE RENOWNED MXF SERIES OF POWER AMPLIFIERS**

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W) ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

**FEATURES:** ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

**SIZES:-** MXF200 W19"xH3 1/2" (2U)xD11"  
MXF400 W19"xH5 1/4" (3U)xD12"  
MXF600 W19"xH5 1/4" (3U)xD13"  
MXF900 W19"xH5 1/4" (3U)xD14 3/4"

**PRICES:-** MXF200 £175.00 MXF400 £233.85  
MXF600 £329.00 MXF900 £449.15  
SPECIALIST CARRIER DEL. £12.50 EACH



**OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER**



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

**Price £117.44 + £5.00 P&P**

**STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS ★**

**STEREO DISCO MIXER** with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.

**Price £144.99 + £5.00 P&P**



**SIZE: 482 x 240 x 120mm**

**PIEZO ELECTRIC TWEETERS - MOTOROLA**

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

**TYPE 'A'** (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.  
**TYPE 'B'** (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.  
**TYPE 'C'** (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.  
**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.  
**TYPE 'E'** (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.  
**LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

TYPE A, TYPE B, TYPE C, TYPE D, TYPE E

**ibl FLIGHT CASED LOUDSPEAKERS**

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

**POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz**

**ibl FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR**  
**ibl FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR**

SPECIALIST CARRIER DEL. £12.50 PER PAIR

**OPTIONAL STANDS PRICE PER PAIR £49.00**  
Delivery £6.00 per pair



**IN-CAR STEREO BOOSTER AMPS**



**PRICES: 150W £49.99 250W £99.99**  
**400W £109.95 P&P £2.00 EACH**

**THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS**

150 WATTS (75 + 75) Stereo, 150W Bridged Mono  
250 WATTS (125 + 125) Stereo, 250W Bridged Mono  
400 WATTS (200 + 200) Stereo, 400W Bridged Mono  
**ALL POWERS INTO 4 OHMS**  
**Features:**  
★ Stereo, bridged mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

**OMP MOS-FET POWER AMPLIFIER MODULES**


**SUPPLIED READY BUILT AND TESTED.**

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

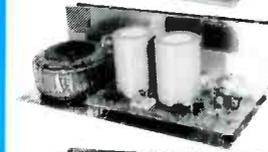**THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS**



**OMP/MF 100 Mos-Fet** Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.  
**PRICE £40.85 + £3.50 P&P**



**OMP/MF 200 Mos-Fet** Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.  
**PRICE £64.35 + £4.00 P&P**



**OMP/MF 300 Mos-Fet** Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.  
**PRICE £81.75 + £5.00 P&P**



**OMP/MF 450 Mos-Fet** Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.  
**PRICE £132.85 + £5.00 P&P**



**OMP/MF 1000 Mos-Fet** Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.  
**PRICE £259.00 + £12.00 P&P**

**NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.**

**LOUDSPEAKERS**



**LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.**

McKenzie and Fane Loudspeakers are also available.

**MINENCE:- INSTRUMENTS, P.A., DISCO, ETC**

**ALL EMINENCE UNITS 8 OHMS IMPEDANCE**

8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB. **PRICE £32.71 + £2.00 P&P**  
10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB. **PRICE £33.74 + £2.50 P&P**  
10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB. **PRICE £43.47 + £2.50 P&P**  
12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB. **PRICE £35.64 + £3.50 P&P**  
12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. **PRICE £36.67 + £3.50 P&P**  
12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB. **PRICE £46.71 + £3.50 P&P**  
12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB. **PRICE £70.19 + £3.50 P&P**  
15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB. **PRICE £50.72 + £4.00 P&P**  
15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB. **PRICE £73.34 + £4.00 P&P**

**EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC**

**ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohms)**

**BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**  
8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. **PRICE £8.90 + £2.00 P&P**  
10" 50watt EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. **PRICE £13.65 + £2.50 P&P**  
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.  
10" 100watt EB10-100 BASS, HI-FI, STUDIO. **PRICE £30.39 + £3.50 P&P**  
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.  
12" 100watt EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. **PRICE £42.12 + £3.50 P&P**  
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.  
**FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**  
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB. **PRICE £9.99 + £1.50 P&P**  
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB. **PRICE £10.99 + 1.50 P&P**  
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 89dB. **PRICE £12.99 + £1.50 P&P**  
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB. **PRICE £16.49 + £2.00 P&P**

**TRANSMITTER HOBBY KITS**

**PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS**  
3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. **PRICE £14.85 - £1.00 P&P**  
FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. **PRICE £8.80 - £1.00 P&P**



PHOTO: 3W FM TRANSMITTER

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



**B.K. ELECTRONICS**

UNITS 1 & 5 COMET WAY, SOUTHERN-ON-SEA, ESSEX, SS2 6TR.

Tel.: 01702-527572 Fax.: 01702-420243

# New Project Kits from Maplin

## AUDIO LEAD CHECKER KIT

- No home or professional studio should be without one!


### FEATURES:

- Rapidly and clearly identifies connections on most audio cables
- Will test very long cables
- Clear led readout
- Robust design
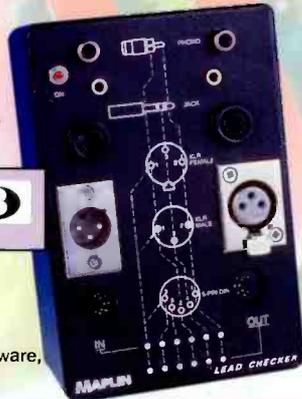
### IDEAL FOR:

- PA/Sound engineers
- Gigging bands
- Fault diagnosis

Kit includes all components, PCB, fixing hardware, case, front panel label and full instructions.




**PROJECT RATING 3**  
Average

**AUDIO LEAD CHECKER KIT LU26D £19.99**

Construction details: Audio Lead Checker Leaflet XZ20W 80p  
Issue 114 / June 1997 Electronics & Beyond XD14Q £2.25

## MELODY GENERATOR KIT

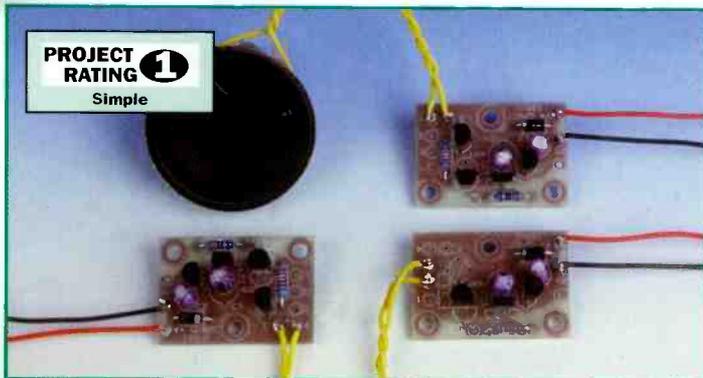

**PROJECT RATING 1**  
Simple

### FEATURES

- Ideal beginners project
- Safe, low voltage operation
- Low current giving long battery life
- Directly drives speakers (included) or piezo sounders
- Large range of melodies supported (15 available)

### APPLICATIONS

- Children's toys
- Teaching nursery rhymes
- Turn ordinary cards and gifts into novel presents

Kit includes all components, PCB, speaker, connecting wire and full instructions. One or two 1.5V batteries are required (not supplied).

### MELODY GENERATOR KIT:

|                      |                           |                          |
|----------------------|---------------------------|--------------------------|
| LU64U Happy Birthday | LU66W London Bridge       | LU67 Old McDonald        |
| LU68 Greensleeves    | LU69 Love Me Tender       | LU70 Jingle Bells        |
| LU75 Merry Christmas | LU76 12 Days of Christmas | LU77 You Are My Sunshine |
| LU80 I Just Called   | LU81 Twinkle Twinkle      | LU84 I'd Like To Teach   |
| LU90 White Christmas | LU91 Warning Tone         | LU92 Wedding March       |

All at £4.99

Construction details: Melody Generator Leaflet XZ47B 50p  
Issue 120 / December 1997 Electronics & beyond XD20W £2.65

### These kits are:

- Supplied with high-quality fibre-glass PCBs - pre-tinned, with printed legend and solder resist
  - Supplied with comprehensive instructions and a constructors' guide
  - Covered by the Maplin Get-You-Working Service and 12-month warranty
- Kits do not include tools or test equipment. Kits may require additional components or products, depending on application, please refer to construction details or contact the Maplin Technical Support Helpline (Tel: 01702 556001) if in doubt.

**PROJECT RATING 1**  
Simple

## NATIONAL LOTTERY PREDICTOR KIT

### FEATURES

- Ideal beginners project
- Simple to use - one switch operation
- Automatic switch off saves batteries
- Full source code available

### APPLICATIONS

- Use to choose your lottery numbers!
- Excellent introduction to microcontrollers
- Use in other games

Kit includes all components, PCB, fixing hardware and full instructions. Two AAA batteries are required (not supplied).



**NATIONAL LOTTERY PREDICTOR KIT LU61R £9.99**

Construction details: National Lottery Predictor Leaflet XZ46A 50p  
Issue 120 / December 1997 Electronics & beyond XD20W £2.65

## PAL COLOUR ENCODER KIT

### FEATURES

- PAL and NTSC compatible
- TTL compatible inputs
- 64 colour palette
- Composite video and UHF outputs
- Analogue or digital RGB inputs
- Optional S-video output

### APPLICATIONS

- Colour bar generation
- RGB to composite and UHF conversion
- Computer displays

Kit includes all components, PCB, Modulator, hardware to connect the Maplin Colour Bar Generator LT50E and full instructions. A +12V DC @ 300mA, regulated supply is required (not supplied).



**PROJECT RATING 3**  
Average

**PAL COLOUR ENCODER KIT LU74R £24.99**

Construction details: PAL Colour Encoder Leaflet XZ41U 80p  
Issue 115 / July 1997 Electronics & beyond XD15R

## .....ORDER NOW!.....

Tel: 01702 554000, Fax: 01702 554001, E-mail: Sales@maplin.co.uk  
Or write to Maplin Electronics, P.O. Box 777, Rayleigh, Essex, SS6 8LU  
Or Tel: 01702 554002 for details of your nearest Maplin or Mondo store.

Please quote **Priority Reference Code MA043** When ordering.



For orders over £30.00 inc VAT goods are dispatched free of handling charges. A small order charge of £2.95 inc VAT is applied to orders less than £30.00 inc VAT. All items subject to availability. All prices are inclusive of VAT and are subject to change. E&OE.



Internet Web Site:  
<http://www.maplin.co.uk>