

EVERYDAY

MAY 1999

PRACTICAL

ELECTRONICS

With **ETI**
ELECTRONICS
TODAY INTERNATIONAL


**FREE
INSIDE!
GIANT 74 SERIES
IC DATA
CHART**

£2.65

PIC TOOLKIT Mk2

Upgraded programmer for PIC 16x84 and new 'F87x series with FREE software

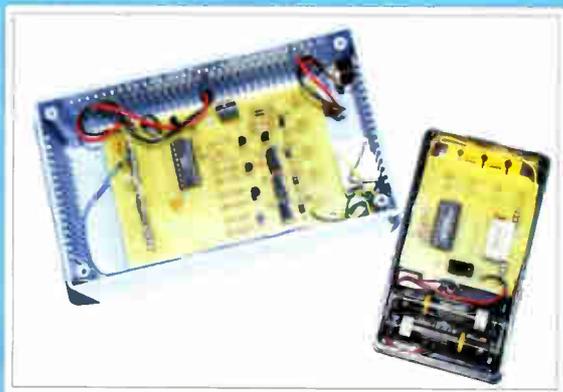**VERSATILE AM/FM
REMOTE CONTROL
SYSTEM** Uses DTI approved modules




PC ENGINES

From 4004 to Pentium III

MIDI "HANDBELLS"
Modern equivalent to handbells

PLUS Ingenuity Unlimited • **Circuit Surgery** • **News**

<http://www.epemag.wimborne.co.uk>

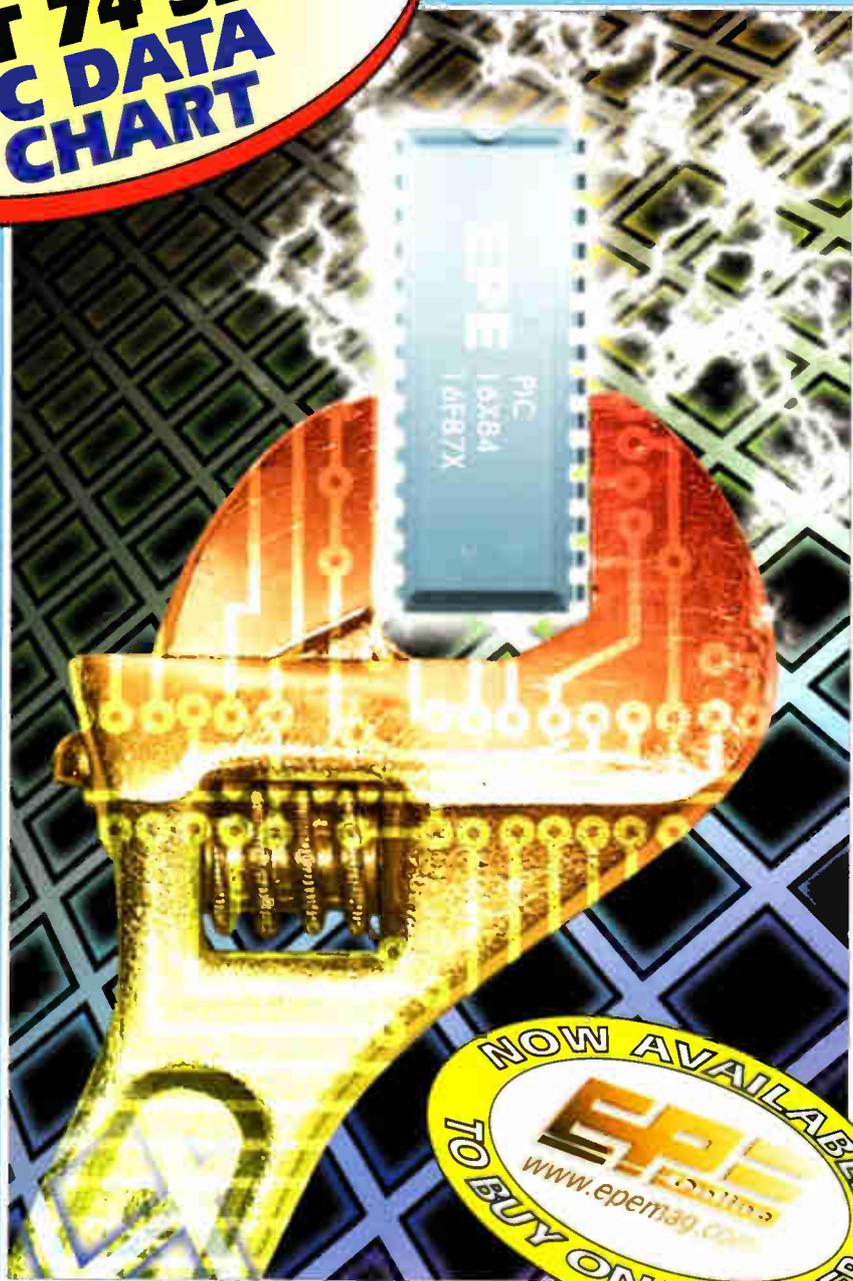

NOW AVAILABLE
TO BUY ON THE WEB
EP
www.epemag.com

THE No.1 MAGAZINE FOR
ELECTRONICS TECHNOLOGY
& COMPUTER PROJECTS



HYDROPONICS DO YOU GROW YOUR OWN?

We have a full colour hydroponics catalogue available containing nutrients, pumps, fittings, environmental control, light fittings, **WINDOWS 95 CD** As supplied with Hewlett Packard PC's these CD's have all the window files on them and were intended to be used to restore windows on a PC after a crash etc £15 REF SX06

SATELLITE MODULATOR MODULES prices from just 99p Surface mount modulators full of components. Fitted with an F type connector and a uhf type connector. Pack of 100 £9.95 ref SS20

PROJECT BOXES

Another bargain for you are these smart ABS project boxes smart two piece screw together case measuring approx 6"x5"x2" complete with panel mounted LED. Inside you will find loads of free bits, tape heads, motors, chips resistors, transistors etc. Pack of 20 £19.95 ref MD2.

REMOTE HEATING CONTROLLERS WITH 30A MAINS RELAY from just 99p These units were designed to be plugged into a telephone socket. You then called the phone and some how it turned the heating on. Each box contains lots of bits including a mains 30A relay. pack of 20 £20 ref SS34

.TALKING COINBOXES Prices from just 95p These units were made to convert standard telephones into pay phones, complete with console assemblies and switches etc. OFFERED TO YOU AT A BARGAIN PRICE BECAUSE WE NEED THE SPACE! Pack of 10 £19.95 ref SS29

AC MOTOR BONANZA! prices from just 59p Again we have piles and piles of these brand new mixed motors which we need to clear in bulk at ridiculous prices! Pack of 50 for £30 ref SS13

PIR CAMERA Built in CCTV camera (composite output) IR strobe light, PIR detector and battery backup. Designed to 'squirt' pictures down the 'phone line but works well as a standalone unit. Bargain price £49.95 ref SS81, 3 or more £44.95 ref SS80. These units are brand new modules designed to take 'pictures' of intruders and then transmit the pictures down the telephone line. The PIR detects the intruder, fires the strobe light this ensures a perfect picture even in total darkness. The picture is stored in memory inside the module and then sent by modem (not included) down the telephone line. The units also have a nicad battery pack included presumably to maintain operation in the event of mains power failure. Output from the camera is standard b/w composite 320x240 pixels with a 90x65 degree field of view, the picture quality is excellent. Each PIR also contains a video capture and compression unit. The infra red strobe has a range of 15m. The pir has a range of 12m. Power requirements are 12v dc 400mA. Power supplies available at £5 ref SS80. The units are supplied with connection details etc but we do not have any information on using the compression and capture unit or interfacing to modems etc. The units do have operational PIR's, strobes and camera's (camera is 12vdc and gives out standard composite 1v p-p video) how you adapt these to work together is entirely up to you! Retail price for the units was in excess of £200 each sale price £39.95 ref SS81. Power supplies £5 ref SS80

TELEPHONES Just in this week is a huge delivery of telephones, all brand new and boxed. Two piece construction with the following features:- illuminated keypad, tone or pulse (switchable), recall, redial and pause, high/low and off ringer switch and quality construction finished in a smart off white colour and is supplied with a standard international lead (same as US or modems) if you wish to have a BT lead supplied to convert the phones these are also available at £1.55 each ref BTLX. Phones £4.99 each ref PH2 10 off £30 ref SS2

3HP MAINS MOTORS Single phase 240v brand new, 2 pole, 340x180mm, 2850 rpm, built in automatic reset overload protector, keyed shaft (40x16mm) Made by Leeson. £99 each ref LEE1

BUILD YOUR OWN WINDFARM FROM SCRAP

New publication gives step by step guide to building wind generators and propellers. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! £12 ref LOT81

CHEFTAN TANK DOUBLE LASERS 9WATT+3

WATT+LASER OPTICS Could be adapted for laser listener long range communications etc. Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, no circuit diagrams due to MOD, new price £50,000? Made £199. Each unit has two gallium arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. £199 ref LOT4

MAGNETIC CREDIT CARD READERS AND

ENCODING MANUAL £9.95 Cased with flyleads designed to read standard credit cards! complete with control electronics PCB and manual covering everything you could want to know about whats hidden in that magnetic strip on your card! just £9.95 ref BAR31

HIPOWER ZENON VARIABLE STROBES Useful 12v PCB fitted with hi power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects etc. 70x55mm 12vdc operation. £6 ea ref FLS1, pack of 10 £49 ref FLS2

CENTRAL POINT PC TOOLS

Award winning software 1,300 virus checker, memory optimiser, disk optimiser, file compression, low level formatting, backup scheduler, disk defragmenter, undelete, 4 calculators, D base, disc editor, over 40 viewers, remote computing, password protection, encryption, comprehensive manual supplied etc. £8 ref lot 97 3 5" disks £10 ref LOT97

VIDEO PROCESSOR UNITS 76V 10AH BATT/

24V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390x320x120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear. Inside 2 x 6v 10AH sealed lead acid batts pcb's and a BA724v toroidal transformer (mains in) sold as seen, may have one or two broken knobs etc due to poor storage. £15.99 ref VP2


DIFFERENTIAL THERMOSTAT KIT

Perfect for heat recovery, solar systems, boiler efficiency etc. Two sensors will operate a relay when a temp difference (adjustable) is detected. All components and pcb. £29 ref LOT93

SOLAR WATER HEATING PLANS £6 REF S0P

PC POWER SUPPLIES PACK OF 8 £9.95

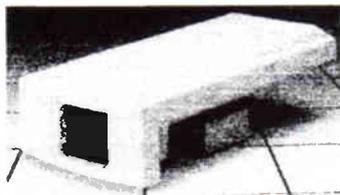That's right! 8 power supplies for £9.95! These are all fan cooled (usually 12v) our choice of specs etc, and are sold as seen. But worth it for the fans alone! ref XX17



COLOUR CCTV VIDEO CAMERAS From £99

Works with most modern video's, TV's, Composite monitors, video grabber cards, Pal, 1v P-P, composite, 75ohm, 1/3" CCD, 4mm F2.8, 500x582, 12vdc, mounting bracket, auto shutter, 100x60x180mm, 3 months warranty, 1 off price £119 ref XEF150, 10 or more £99 ea 100+ £89

We get over 5,000 hits a day.... check us out!

<http://www.bullnet.co.uk>

SMOKE ALARMS Mains powered made by the famous Gent company easy fit next to light fittings power point. Pack of 5 £15 ref SS23, pack of 12 £24 ref SS24

4AH D SIZE NICADS pack of 4 £10 ref 4AHPK

ELECTRIC FENCE KIT Everything you need to build a 12vdc electric fence, complete with 200m of fence wire. £49 ref AR2

SENDER KIT Contains all components to build a AV transmitter complete with case £35 ref VSXX2

33 KILO LIFT MAGNET

Neodymium 32mm £15 ref MAG33

10 WATT SOLAR PANEL

Amorphous silicon panel fitted in a anodized aluminum frame. Panel measures 3' by 1' with screw terminals for easy connection. 3' x 1' solar panel £55 ref MAG45

Unframed 4 pack (3'x1') £58.99 ref SOLX

12V SOLAR POWERED WATER PUMP

Perfect for many 12v DC uses ranging from solar fountains to hydroponics! Small and compact yet powerful works direct from our 10 watt solar panel in bright sun. Max hd 17 ft. Max flow = 8 Lpm 1. 5A Ref AC8 £18.99

SOLAR ENERGY BANK KIT 50x6"x12" 6v solar panels(amorphous)+50 diodes £99 ref EF112

PINHOLE CAMERA MODULE WITH AUDIO!

Superb board camera with on board sound! extra small just 28mm square (including microphone) ideal for covert surveillance. Can be hidden inside anything even a matchbox! Complete with 15 metre cable, psu and tv/vcr connectors. £49.95 ref CCGJ

SOLAR MOTORS

Tiny motors which run quite happily on voltages from 3-12vdc. Works on our 6v amorphous 6" panels and you can run them from the sun! 32mm dia 20mm thick. £1.50 each

WALKIE TALKIES 1 MILE RANGE £37/PAIR REF MAG30

LIQUID CRYSTAL DISPLAYS Bargain prices,

20 character 2 line, 83x19mm £3.99 ref SMC2024A
16 character 4 line, 62x25mm £5.99 ref SMC1640A
40 character 1 line 154x16mm £6.00 ref SMC4011A
LM255X HITACHI LAPTOP SCREENS 240x100mm, 640x200 dots. New with data £15 ref LM2

SEALED LEAD ACID BATTERIES

12V 7AH, S/HAND

PACK OF 4 £10 REF XX1

YOUR HOME COULD BE SELF SUFFICIENT

IN ELECTRICITY

Comprehensive plans with loads of info on designing systems, panels, control electronics etc £7 ref PV1

REGISTER FOR OUR ELECTRONIC NEWSLETTERS BULL-ELECTRICAL.COM

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX. BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE WITH ORDER PLUS £4.00 P&P PLUS VAT.

24 HOUR SERVICE £6.50 PLUS VAT.

OVERSEAS ORDERS AT COST PLUS £3.50

(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

'phone orders : 01273 203500

FAX 01273 323077

Sales@bull-electrical.com

200 WATT INVERTERS

plugs straight into your car cigarette lighter socket and is fitted with a 13A socket so you can run your mains operated devices from your car battery. £49.95 ref SS66

THE TRUTH MACHINE

Tells if someone is lying by micro tremors in their voice. Battery operated works in general conversation and on the 'phone and TV as well! £42.49 ref TD3

INFRA RED FILM

6" square piece of flexible infra red film that will only allow IR light through. Perfect for converting ordinary torches lights. headlamps etc to infra red output. Only using standard light bulbs. Easily cut to shape. 6" square £15 ref IRF2

HYDROGEN FUEL CELL PLANS

Loads of information on hydrogen storage and production. Practical plans to build a Hydrogen fuel cell (good workshop facilities required) £8 set ref FCP1

STIRLING ENGINE PLANS

interesting information pack covering all aspects of Stirling engines. pictures of home made engines made from an aerosol can running on a candle! £12 ref STIR2

ENERGY SAVER PLUGS

Saves up to 15% electricity when used with fridges. motors up to 2A. light bulbs. soldering irons etc. £9 ea ref LOT71. 10 pack £69 ref LOT72

12V OPERATED SMOKE BOMBS

Type 3 is a 12v trigger and 3 smoke canisters. each canister will fill a room in a very short space of time! £14.99 ref SB3. Type 2 is 20 smaller canisters (suitable for simulated equipment fires etc) and 1 trigger module for £29 ref SB2. Type 1 is a 12v trigger and 20 large canisters. £49 ref SB1

HIPOWER ZENON VARIABLE STROBES

Useful 12v PCB fitted with hi power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects etc. 70x55mm 12vdc operation. £6 ea ref FLS1. pack of 10 £49 ref FLS2

NEW LASER POINTERS

4.5mw 75 metre range. hand held unit runs on two AA batteries (supplied) 670nm. £29 ref DEC49J

HOW TO PRODUCE 35 BOTTLES OF WHISKY

FROM A SACK OF POTATOES. Comprehensive 270 page book covers all aspects of spirit production from everyday materials. includes construction details of simple stills. £12 ref MS3

NEW HIGH POWER MINI BUG

With a range of up to 800 metres and a 3 days use from a PP3. this is our top selling bug! less than 1" square and a 10m voice pickup range. £28 ref LOT102

IR LAMP KIT

Suitable for cctv cameras. enables the camera to be used in total darkness! £6 ref EF138

INFRA RED POWERBEAM

Handheld battery powered lamp. 4 inch reflector. gives out powerful pure infrared light! perfect for CCTV use. night sights etc. £29 ref PB1

SUPER WIDEBAND RADAR DETECTOR

Detects both radar and laser. XK and KA bands, speed cameras, and all known speed detection systems. 360 degree coverage front & rear. 1" x 2" x 4" 6" fits on visor or dash. £149

LOPTX

Made by Samsung for colour TV. £3 each ref SS52

LAPTOP LCD SCREENS

240x175mm. £12 ref SS51

WANT TO MAKE SOME MONEY? STUCK

FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

HIGH POWER DC MOTORS, PERMANENT

MAGNET. 12 - 24v operation, probably about 1/4 horse power. body measures 100m x 75mm with a 60mm x 5mm output shaft with a machined flat on it. Fixing is simple using the two threaded bolts protruding from the front. £22 ref MOT4

INFRA RED REMOTE CONTROLS

made for TVs but may have other uses. pack of 100 £39 ref IREM

ELECTRONIC SPEED CONTROLLER KIT

For the above motor is £19 ref MAG17. Save £5 if you buy them both together. 1 motor plus speed controller rrp is £41, offer price £36 ref MOT5A

SONY STEREO TV CHASSIS

assemblies comprising complete TV PCB excluding tube and scan coils. Nicam stereo. mains input. Appear to be unused but sold as seen. Would probably be good for spares or as a nicam stereo TV sound receiver and amplifier. For KV29F1U and KV25F1U (BE3D) PCB no's 1-659-827-12 1-659-826-14 1-711-800-11 £20 ref STV1

RCB UNITS

Inline IEC lead with fitted RC breaker. Installed in seconds.

Pack of 3 £9.98 ref LOT5A

RADIO CONTROLLED CARS etc

No remotes but good strippers for servo's motors and receivers. Sold as is. no returns. mixed types. £3 each ref RCC2

VOICE CHANGERS

Hold one of these units over your phone mouth piece and you can adjust your voice using the controls on the unit. Battery operated £15 ref CC1

LOW COST CORDLESS MIC

500 range. 90 - 105mhz. 115g. 193 x 26 x 39mm, 9v PP3 battery required. £17 ref MAG15P1

AUTOSUNCHARGER

155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £12.99 REF AUG10P3

SOLAR POWER LAB SPECIAL

2x 6"x6" 6v 130mA cells, 4LED's, wire, buzzer, switch + 1 relay or motor. £7.99 REF SA27

SOLAR NICAD CHARGERS

4 x AA size. £9.99 ref 6P476. 2 x C size. £9.99 ref 6P477

5.25" FLOPPY DISKS

pack of 500 disks. £25 ref FDJ

Online web catalogue

bull-electrical.com

ISSN 0262 3617
PROJECTS ... THEORY ... NEWS ...
COMMENT ... POPULAR FEATURES ...

VOL. 28 No. 5 **MAY 1999**
Cover illustration by Jonathan Robertson

EVERYDAY





PRACTICAL

ELECTRONICS



<http://www.epemag.wimborne.co.uk>

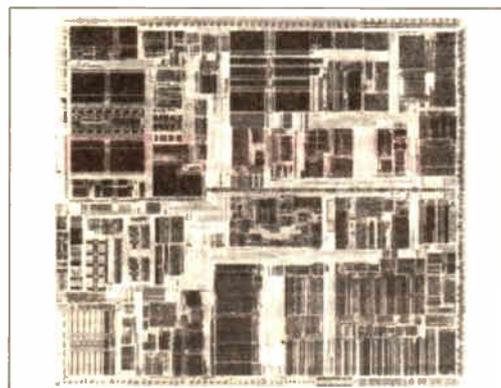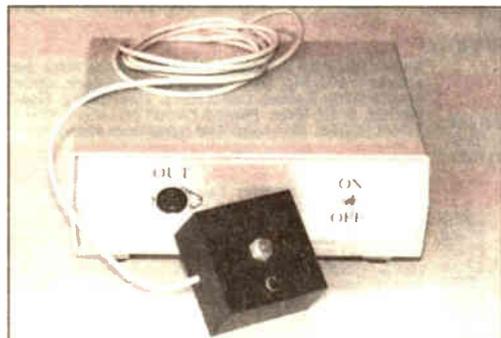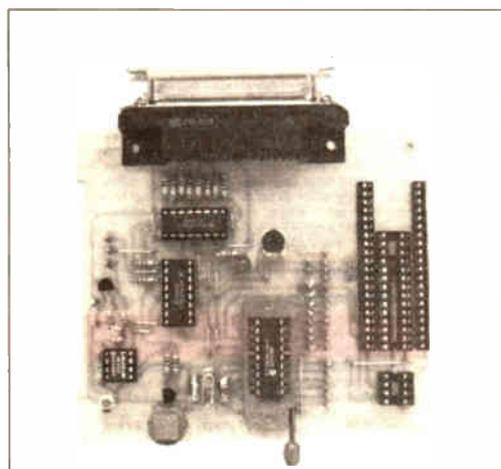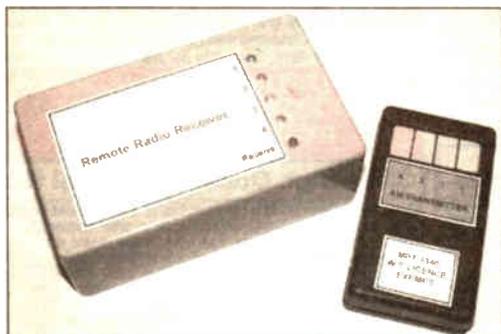**The No. 1 Magazine for Electronics
Technology and Computer Projects**



© Wimborne Publishing Ltd 1999. Copyright in all drawings, photographs and articles published in **EVERYDAY PRACTICAL ELECTRONICS/ETI** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our June '99 issue will be published on Friday, 7 May 1999. See page 315 for details.

Everyday Practical Electronics/ETI, May 1999

Projects and Circuits

- MIDI HANDBELLS** by Robert Penfold **324**
Ring out thy bells with merry tolling – plus a MIDI PIC-up, of course!
- A.M./F.M. RADIO REMOTE CONTROL** by Max Horsey **344**
Coded radio remote control has become straightforward and requires no UK licence
- PhizzyB COMPUTERS – 7** by Clive "Max" Maxfield, Alvin Brown and Alan Winstanley **360**
Ma, it's making eyes at me! The PhizzyBot now has vision – here's how ...
- PIC TOOLKIT MK2** by John Becker **369**
Expanding Toolkit Mk1 to include the new PIC 16F87x devices as well as the familiar 'x84s, plus many more features!
- INGENUITY UNLIMITED** hosted by Alan Winstanley **379**
Photo Slave Flash Unit; Siren Sounder; Space Case Alarm; Electronic Rotary Switch; Pico Prize Winners

Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole **334**
New bonding techniques enhance power handling for IGBT devices
- CIRCUIT SURGERY** by Alan Winstanley **336**
Current Sources – a close-up explanation
- PC ENGINES – FROM 4004 TO PENTIUM III** by Ernest Flint **338**
A brief history of time as Intel's microprocessors see it
- PRACTICALLY SPEAKING** by Robert Penfold **353**
The nuts and bolts of casing your projects more easily
- PhizzyB COMPUTERS – 7** by Clive "Max" Maxfield and Alvin Brown **356**
Giving PhizzyBility to PhizzyBot needs a bit of software, but not much
- NET WORK - THE INTERNET PAGE** surfed by Alan Winstanley **387**
The worms have turned; Under attack; Don't panic; Update

Regulars and Services

- EDITORIAL** **323**
- NEWS** – Barry Fox highlights technology's leading edge
Plus everyday news from the world of electronics **331**
- SHOPTALK** with David Barrington **335**
The *essential* guide to component buying for *EPE* projects
- PLEASE TAKE NOTE** PC Capacitance Meter (Oct '98) **335**
- CD-ROMS FOR ELECTRONICS** **364**
Parts Gallery + Electronic Circuits and Components; Digital Electronics; Analogue Electronics; *plus* PICtutor, *plus* Modular Circuit Design
- READOUT** John Becker addresses general points arising **367**
- DIRECT BOOK SERVICE** **382**
A wide range of technical books available by mail order
- BACK ISSUES** Did you miss these? **385**
- ELECTRONICS VIDEOS** Our range of educational videos **386**
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** **388**
PCBs for *EPE* projects – some at "knockdown" prices! Plus *EPE* software
- ADVERTISERS INDEX** **392**

FREE

**GIANT PULL OUT DATA CHART –
7400-SERIES LOGIC GATE PINOUTS** **between pages 352/353**

Readers Services • Editorial and Advertisement Departments **323**

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!



TV SOUND & VIDEO TUNER CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner £89.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite 1V pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52mm enable full software control via a simple 2 wire link to any IBM type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**

IC's - TRANSISTORS - DIODES

OBsolete - Short Supply - Bulk

6,000,000 Items EX STOCK

For MAJOR SAVINGS - CALL OR SEE OUR WEBSITE

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with the 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PCs in CGA, EGA, VGA & SVGA modes. BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched facelate, test switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. Tilt & Swivel Base £4.75. **Only £119 (C)** Order as MITS-SVGA. VGA cable for IBM PC included. External cables for other types of computers CALL.

As New - Ex Demo
17" 0.28 SVGA Mitsubishi Diamond Pro monitors Full multisync etc. Full 90 day guarantee. £325.00 (E)

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed. Dimensions: W14" x H12 1/4" x 15 1/4" D. **Only £99 (E)**

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered. **Only £79.00 (D)**

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition. **Only £125 (E)**

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive teak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

DC POWER SUPPLIES


Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock. Call or see our web site.

LOW COST PC'S

Always over 1000 PC's from stock. 1000's of spares and accessories. Call or see our web site for info.

19" RACK CABINETS

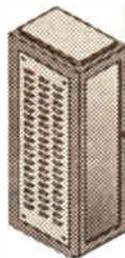Superb quality 6 foot 40U Virtually New, Ultra Smart Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we

have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/4" H x 32 1/2" D x 22" W. Order as: OPT Rack 1 Complete with removable side panels. £345.00 (G) OPT Rack 2 Rack, Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories 19" 22" & 24" wide 3 to 46 U high. Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extra available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W) Sold at LESS than a third of makers price !!



A superb buy at only £245.00 (G) 42U version of the above only £345 - CALL

BATTERY SCOOP - 50% off !!

A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type S8S15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each! **Our Price £35 each (C) or 4 for £99 (D)**

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive stocks covering types such as - Military, Octal, Cradle, Hermetically Sealed, Contactors, Time Delay, Reed, Mercury Wetted, Solid State, Printed Circuit Mounting, CALL US WITH YOUR NEEDS. Many obsolete types from stock. Save ££££'s

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (288 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. £59.95 Half length & 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data. Order as: XT RAM UG. 256k. £34.95 or 512k £39.95

SIMM SPECIALS

1 MB x 9 SIMM 9 chip 120ns Only £9.50
1 MB x 9 SIMM 3 chip 80 ns £10.50 or 70ns £11.95
1 MB x 9 SIMM 9 chip 80 ns £10.50 or 70ns £11.75
4 MB 70 ns 72 pin SIMM - with parity- Only £35.00
INTEL 486-DX33 CPU £19.95 INTEL 486-DX66 CPU £59.00
FULL RANGE OF CO-PROCESSORS EX STOCK - CALL FOR £££
MOTOROLA 25 Mhz 68040 (XC88040RC25M) CPU'S £59.00 shipping charges for RAM / CPU upgrades is code B

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. **Special Price ONLY £99.00**
Microsoft - Windows for Workgroups 3.11 & DOS 6.22. Supplied on 3 1/2" disks with licence & concise documentation. £39.95
DOS 5.0 on 3 1/2" disks with concise books & QBasic. £14.95
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95 shipping charges for software is code B

FLOPPY DISK DRIVES 2 1/2" - 14"

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call for over 2000 unlisted drives for spares or repair.

- 3 1/2" Panasonic JU363/4 720K or equivalent RFE £24.95(B)
- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptop only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 3 1/2" Teac FD-55GF 1.2 Meg (for IBM pcs) RFE £18.95(B)
- 3 1/2" Teac FD-55F 03-U 720K 4080 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 360K £22.95(B)
- Table top case with integral PSU for HH 5 1/4" Flopp or HD £29.95(B)
- 8" Stuttgart 800/801 8" SS refurbished & tested £210.00(E)
- 8" Stuttgart 810 8" SS HH Brand New £195.00(E)
- 8" Stuttgart 851 8" double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £285.00(E)
- 8" Mitsubishi M2898-63 02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES

- 2 1/2" TOSHIBA (19 mm H) MK2101MAN 2.16 Gb. New £199.00
 - 2 1/2" TOSH (12.5 mm H) MK1002MAV 1.1 Gb laptop. New £115.00
 - 2 1/2" to 3 1/2" conversion kit for PC's, complete with connectors £12.95
 - 3 1/2" FUJI FK-309-26 20mb MF4M V/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE V/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40mb IDE V/F (or equiv.) RFE £89.00
 - 3 1/2" RODIME RQ3057S 45mb SCSI V/F (Mac & Acorn) £89.00
 - 3 1/2" QUANTUM 40S Prodrive 42mb SCSI V/F, New RFE £49.00
 - 3 1/2" WESTERN DIGITAL 850mb IDE V/F New £185.00
 - 5 1/4" MINISCRIBE 3425 20mb MF4M V/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RLL V/F Refurb £89.95
 - 5 1/4" CDC 94205-51 40mb HH MF4M V/F RFE tested £89.95
 - 5 1/4" HP 97548 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 8" NEC D2246 85 Mb SMD interface. New £199.00
 - 8" FUJITSU M2322K 180Mb SMD V/F RFE tested £195.00
 - 8" FUJITSU M2392K 2 Gb SMD V/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (D)

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3445ETKL 14" Industrial spec SVGA monitors 1Kw to 400 kW - 400 Hz 3 phase power source - ex stock £245
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2800
- IBM SP3501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel 8228-23-5050N £95
- AIM 801 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360.11805-1880 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 Vo EPOA
- Marconi 6310 Programmable 2 to 22 GHz sweep generator £8500
- Marconi 2022C 10KHz-1GHz RF signal generator £1550
- Marconi 2030 opt 03 10KHz-1.3 GHz signal generator, New £5150
- HP1850B Logic Analyser £2750
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP8621A Dual Programmable GPIB PSU 0-7 V 180 watts £1800
- HP8284 Rack mount variable 0-20V @ 20A metered PSU £675
- HP84121A DC to 22 GHz four channel test set EPOA
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £8500
- HP A1, A0 8 pen HPGL high speed drum plotters - from EG+G Brookdeal 86036C Precision lock in amp £850
- View Eng. Mod 1200 computerised inspection system EPOA
- Sony DXC-9000A High quality CCD colour TV camera £1100
- Kennley 590 CV capacitor / voltage analyser EPOA
- Rackl IPC400 dual 40 channel video recorder system £3750
- Fluores 45KVA 3 Ph On Line UPS - New batteries £9500
- ICI R5030UV34 Cleanline ultrasonic cleaning system EPOA
- Mann Tally MT645 High speed line printer £2200
- Intel SBC 486/133SE Multibus 486 system. 8Mb Ram £845
- Siemens K4400 64Kb to 140Mb demux analyser £2950

- Intel SBC 486/125C08 Enhanced Multibus (MSA) NEW £1450
- Zeta 3220-05 A0 4 pen HPGL fast drum plotters £1150
- Nikon HFX-11 (Ephiphop) exposure control unit £1450
- Motorola VME Bus Boards & Components List. SAE / CALL EPOA
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM band printer £1950
- Fujitsu M3041D 800 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer A £500
- Perkin Elmer 597 Infrared spectrophotometer £3500
- Vg Electronics 1035 TELETEXT Decoding Margin Meter £3750
- LightBead 80 output high spec 2u rack mount Video VDA's £495
- Sekonic SD 150H 18 channel digital Hybrid chart recorder £1995
- Taylor Hobson Talysurf amplifier / recorder £750
- ADC B2200 Carbon dioxide gas detector / monitor £1450
- System Video 1152 PAL waveform monitor £485
- ANRITSU 9854A Optical DC-2.5Gb/waveform monitor £5,850
- ANRITSU MS9001B1 0.8-1.7 uM optical spectrum analyser EPOA
- ANRITSU ML93A optical power meter £990
- ANRITSU Fibre optic characteristic test set EPOA
- VISION ENGINEERING T53 Dynascopic microscope £1850
- R&S FTD2 Dual sound unit £850
- R&S SBUF-E1 Vision modulator £775
- WILTRON 6630B 12.4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1850
- TEK 1502 Portable TDR (time domain reflectometer) £500
- PHILIPS PW179010 XYRAY generator with accessories EPOA
- CLAUDE LYONS 12A 240V single phase auto. volt. regs £325
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs £2900

DISTEL on the web !! - Over 16,000,000 Items from stock - www.distel.co.uk

distel
-ELECTRONICS-

ALL MAIL & OFFICES
Open Mon - Fri 9.00 - 5.30
Dept PE , 32 Biggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehouse Lane
South Norwood
On B&A Bus Route
N. Thornton Heath & Selsouth Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email admin@distel.co.uk

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - tester CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks, tradenames etc acknowledged. © Display Electronics 1998. E & O E. 05/98

NEXT MONTH

MUSICAL SUNDIAL

TRAVESTY – that's the word, it's an absolute and utter travesty – this Sundial thingy, it's a gross and total misuse of sophisticated electronics. Well, think about it – In the Beginning was the Big Shout that echoed throughout the Multiverse: "Let there be Light", and so it was, and so came about shadow where light could not reach. And man saw the shadow and how it moved when the light moved, and thus he saw the motion of time and that it can be measured in its motion beneath the plants and trees around him, and thus the sundial was there for his enlightenment from the beginning.

And what happens? Aeons later along comes a bright spark who says to himself "Electronics can tell the time from the motion of sunlight", and set about to prove it. But why he should bother was never questioned – and it should have been; the sundial already IS and needs no improvement, and it certainly doesn't need to be made with technology.

Nonetheless, it's been done and we feel you should know about it, perhaps even build it and marvel at how petty we humans can be at trying to replicate what nature has already achieved without even thinking about it.

So what does this Musical Sundial contraption actually do? It monitors the motion of the sun of course – a pointer casts a shadow which rotates with the sun. Sensors in an arc detect the position of the shadow and when a sensor is completely covered by the shadow, electronically generated musical chimes and pips mark the hour of the event, one pip for each hour past. Then . . . and then, you get a tune played! And what tune might it be – what else but something that might perhaps remind you of the old classic "You are my Sunshine" (although a real musician wouldn't think so)!

But that's not all – on any day when the weather's changeable, with the sun coming and going, appropriate phrases of the "tune" mark the disappearance or re-appearance of the sun.

So that's what you do next month, build our Sundial (never mind what the neighbours might say about your sanity!). We provide the info, where you find the sun is up to you!



STARTER PROJECT

Next month we commence publishing a series of "Starter Projects" designed with the novice in mind. They are all easy to build and inexpensive, the first one is a

CLIPPING VIDEO FADER.

Many camcorders include a video fader facility, but this is often in the form of a pushbutton control with a fixed rate of fade. A fader of this type is certainly usable, but offers no creative control to the user. This extremely simple video fader project has a conventional control knob that offers precise control over the fade characteristic. It provides what is virtually a conventional fade to black action, but the fading is provided by asymmetric clipping of the picture modulation rather than by attenuating it.

This method of fading operates in a different manner to a conventional fader, and it produces a different effect on-screen when the picture is faded. With the clipping method the brightest parts of the picture are faded first, then the mid-tones, and finally the darker areas. The picture collapses rather than fades from the screen. This project offers an interesting alternative to a conventional video fade effect, and it costs very little to build.

ALAN DOWER BLUMLEIN – A TOUCH OF MAGIC

Many readers will have never heard of Alan Dower Blumlein, we hope we can put that right next month. He either originated or made profound contributions to Telephony, Monaural and Stereo Recording, Television, Radar, Amplifier Technology, and Signal Processing circuits.

Few will ever match A. D. Blumlein in his insight, breadth of knowledge or ability to solve problems in electronics and electrical engineering. If one defines genius as "original thought" then Blumlein had genius in abundance. In a life that was cut short during the second world war, he created more in a career lasting only 17 years than the vast majority do collectively in a lifetime. In all, Blumlein held 128 patents – on average one for every six weeks of his working life.

PLUS • ALL THE REGULARS

NO ONE DOES IT BETTER

EVERYDAY

PRACTICAL

ELECTRONICS




DON'T MISS AN ISSUE – PLACE YOUR ORDER NOW!

Demand is bound to be high

JUNE ISSUE ON SALE FRIDAY, MAY 7

Computer Controlled Robotics


Bring Electronics to Life

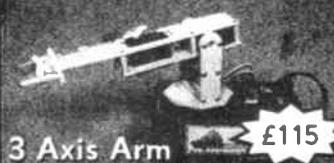

3 Axis Arm £115



Carpet Rover £89

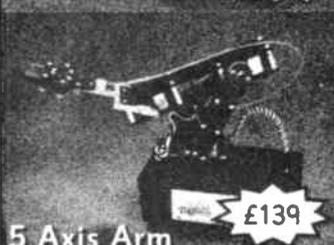

5 Axis Arm £139



Mobile Arm £179



Hexapod Walker £110



Micro Mouse £79

Technology Education Index

Telephone for our catalogue or visit our web site for further details

40 Wellington Road, Orpington, Kent BR5 4AQ

Telephone - (01689) 876880

Web Site - <http://www.technologyindex.com>

Prices exclude VAT and £5.00 next day carriage



VARIABLE VOLTAGE TRANSFORMERS

INPUT 220V/240V AC 50/60 OUTPUT 0V-260V

PANEL MOUNTING	Price	P&P
0.5KVA 2.5 amp max	£33.00	£6.00 (£45.83 inc VAT)
1KVA 5 amp max	£45.25	£7.00 (£61.39 inc VAT)
SHROUDED		
0.5KVA 2.5 amp max	£34.00	£6.00 (£47.00 inc VAT)
1KVA 5 amp max	£46.25	£7.00 (£62.57 inc VAT)
2KVA 10 amp max	£65.00	£8.50 (£86.36 inc VAT)
3KVA 15 amp max	£86.50	£8.50 (£111.63 inc VAT)
5KVA 25 amp max	£150.00	(+ Carriage & VAT)

Buy direct from the Importers. Keenest prices in the country

500VA ISOLATION TRANSFORMER

Input lead 240V AC Output via 3 pin 13A socket 240V AC continuously rated Mounted in fibre glass case with handle Internally fused Price £35.00 carriage paid - VAT (£41.13)

TOROIDAL L.T. TRANSFORMER

Primary 0-240V AC Secondary 0.30V - 0.30V 500VA F ring bolt supplied Price £30.00 carriage paid - VAT (£35.25)

COMPREHENSIVE RANGE OF TRANSFORMERS-IT-ISOLATION & AUTO 110V-240V Auto transfer either cased with American socket and mains lead or open frame type Available for immediate delivery

ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft 40 watt	£14.00 (callers only)	(£16.45 inc VAT)
2ft 20 watt	£9.00 (callers only)	(£10.58 inc VAT)
12in 8 watt	£4.80 - 75p p&p	(£6.52 inc VAT)
9in 6 watt	£3.96 - 50p p&p	(£5.24 inc VAT)
6in 4 watt	£3.96 - 50p p&p	(£5.24 inc VAT)

230V AC BALLAST KIT

For either 6in 9in or 12in tubes £6.05 - £1.40 p&p (£8.75 inc VAT)

The above Tubes are 3500-4000 angstrom 350-400um ideal for detecting security markings effects lighting & Chemical applications Other Wavelengths of UV TUBE available for Germicidal & Photo Sensitive applications. Please telephone your enquiries

400 WATT BLACK LIGHT BLUE UV LAMP

GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast Only £39.95 incl p&p & VAT



SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB
TEL: 0181-995 1560 FAX: 0181-995 0549
ACCOUNT CUSTOMERS MIN. ORDER £10

5 KVA ISOLATION TRANSFORMER

As New Ex-Equipment fully shrouded Line Noise Suppression Ultra Isolation Transformer with terminal covers and knock out cable entries Primary 120V 240V Secondary 120V 240V 50/60Hz 0.0050F Capacitance Size L 37cm x W 19cm x H 16cm Weight 42 kilos Price £120 + VAT Ex-warehouse Carriage on request

24V DC SIEMENS CONTACTOR

Type 3TH8022 0B 2 x NO and 2 x NC 230V AC 10A Contacts Screw on Din Rail fixing Size H 120 x W 45 x D 75mm Brand New Price £7.88 inc VAT

240V AC WESTCOOL SOLENOIDS

TT2 Mod 1 Rat 1 Max stroke 1/2in Base mounting 1/2in stroke 5lbs pull approx TT6 Mod 1 Rat 1 Max stroke 1 in Base mounting 1/2in stroke 15lbs pull approx SERIES 400 Mod 1 Rat 2 Max stroke 1/2in Front mounting 1/2in stroke 15lbs pull approx Price incl p&p & VAT TT5 £5.88, TT6 £8.81, SERIES 400 £7.64

AXIAL COOLING FAN

230V AC 120mm square x 38mm 3 blade 10 watt Low Noise fan Price £7.29 incl P&P and VAT Other voltages and sizes available from stock Please telephone your enquiries

INSTRUMENT CASE

Brand new Manufactured by Imhoff L 31 x H 18 x 19cm Deep Removable front and rear panel for easy assembly of your components Grey textured finish complete with case feet Price £16.45 incl P&P and VAT 2 off £28.20 inclusive

DIE CAST ALUMINIUM BOX

with internal PCB guides internal size 265 x 165 x 50mm deep Price £9.93 incl p&p & VAT 2 off £17.80 incl

230V AC SYNCHRONOUS GEARED MOTORS

Brand new Ovoid Gearbox Couzlet type motors H 65mm x W 55mm x D 35mm 4mm dia shaft x 10mm long 6 RPM anti cw £9.99 incl p&p & VAT 20 RPM anti cw Depth 40mm £11.16 incl p&p & VAT

SOLID STATE EHT UNIT

Input 230V 240V AC Output approx 15KV Producing 10mm spark Built-in 10 sec timer Easily modified for 20 sec 30 sec to continuous Designed for boiler ignition Dozens of uses in the field of physics and electronics e.g. supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made up unit Kit of parts less case includes 12m 8 watt 2537 Argon Tube Ballast unit, pair of b.p.n leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 - £2.00 p&p (£19.98 inc VAT)

WASHING MACHINE WATER PUMP

Brand new 240V AC fan cooled Can be used for a variety of purposes Inlet 1 1/2in outlet 1/2 in dia Price includes p&p & VAT £11.20 each or 2 for £20.50 inclusive



FREE!

OUR LATEST BARGAIN LIST - 32 PAGES FULL OF QUALITY SURPLUS STOCK AND ALL AT THE LOWEST PRICES!



GREENWELD ELECTRONIC COMPONENTS

27D Park Road · Southampton · SO15 3UQ
TELEPHONE: 01703 236363 FAX: 01703 236307
E-Mail: greenweld@aol.com INTERNET: <http://www.greenweld.co.uk>

PHONE, FAX OR WRITE TODAY FOR YOUR FREE COPY!



**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Beckman 8020 - 20MHz - Dual Channel	£150
Coscor 3102 - 60MHz Dual Channel	£250
Gould OS 245A/250/255/300/3000/351/4000	from £125
Hewlett Packard 180A/180C/181A/182C	from £200
Hewlett Packard 1740A, 1741A, 1744A, 100MHz dual ch.	from £350
Hewlett Packard 54100D - 1GHz Digitizing	£1500
Hewlett Packard 54200A - 50MHz Digitizing	£1250
Hewlett Packard 54201A - 300MHz Digitizing	£1500
Hitachi V152F/V302B/V302F/V353F/V550B/V650F	from £125
Hitachi V650F - 60MHz Dual Channel	£295
Hitachi V1100A - 100MHz 4 Channel	£950
Intron 2020 - 20MHz Digital Storage (NEW)	£450
Watsu SS 5710/SS 5702 - 20MHz	from £125
Meguro - MSO 1270A - 20MHz Digital Storage (NEW)	£450
Nicolet 310 - L.F. D.S.O. with twin Disc Drive	£400
Nicolet 3091 - L.F. D.S.O.	£750
Lacroy 9450A - 300MHz/400 Ms/s D.S.O. 2 ch.	£2250
Panasonic VP5741A - 100MHz - Dual Channel D.S.O.	£1750
Phillips PM 3055 - 50 MHz DUAL Timebase	£450
Phillips PM 3211/PM 3212/PM 3214/PM 3217/PM 3234/PM 3243/PM 3244/PM 3261/PM 3262/PM 3263/PM 3540	from £125
Phillips PM 3295A - 400MHz Dual Channel	£1750
Phillips PM 3335 - 50 MHz/20Ms/s D.S.O. 2 ch.	£1500
Tektronix 434 - 25MHz - 2 Channel Analogue Storage	£250
Tektronix 454 - 150MHz - 2 Channel	£400
Tektronix 455 - 50MHz Dual Channel	£0000
Tektronix 464/466 - 100MHz An storage	from £0000
Tektronix 465/465B - 100MHz dual ch.	from £0000
Tektronix 468 - 100MHz D.S.O.	£850
Tektronix TAS 475 - 100 MHz - 4 Channel	£995
Tektronix 475/475A - 200MHz/250MHz Dual Channel	from £0000
Tektronix 485 - 350MHz - 2 channel	£750
Tektronix 2213 - 60MHz Dual Channel	£375
Tektronix 2215 - 60MHz Dual trace	£400
Tektronix 2220 - 60MHz Dual Channel D.S.O.	£1250
Tektronix 2221 - 60MHz Digital Storage 2 Channel	£1250
Tektronix 2225 - 50MHz dual ch.	£395
Tektronix 2235 - 100MHz Dual trace	£800
Tektronix 2335 - Dual trace 100MHz (portable)	£800
Tektronix 2440 - 300 MHz/500 Ms/s D.S.O. 2 Ch.	£2950
Tektronix 2445 - 150 MHz - 4 Channel + DMN	£1200
Tektronix 2445A - 100 MHz - 4 Channel	£900
Tektronix 2445A - 150 MHz - 4 Channel	£1250
Tektronix 5403 - 60MHz - 2 or 4 Channel	from £200
Tektronix 7313, 7803, 7813, 7823, 7833, 100MHz 4 ch.	from £225
Tektronix 7704 - 250MHz 4 ch.	from £450
Tektronix 7904 - 500MHz	from £800
Trio CS-1022 - 20MHz - Dual Channel	£125

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20MHz DUAL TRACE	£160
HITACHI V222 - 20 MHz DUAL TRACE + ALTERNATE MAGNIFY	£180

SPECTRUM ANALYSERS

Ando AC8211 - Spectrum Analyser 1.7GHz	£2250
Anritsu MS82B - 10KHz - 1700MHz	£2250
Anritsu MS341A + MS3401B - (10Hz - 30MHz)	£3995 + £4500
Anritsu MS610B - 10KHz - 2GHz (Mini)	£4750
Anritsu MS710F - 100KHz - 20GHz Spectrum Analyser	£9950
Avcom PSA65 S - 1000MHz - portable	£850
Hameg 8028/8038 - Spectrum Analyser/Tracking Gen +100MHz Oscilloscope	£1250
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
Hewlett Packard 182T + 8558B - 0.1 to 1500MHz	£1750
Hewlett Packard 853A + 8558B - 0.1 to 1500MHz	£2500
Hewlett Packard 8591A - 9KHz - 1.8GHz with Option 10 Tracking Generator	£6500
Hewlett Packard 8594E - 9KHz - 2.9GHz	£7000
Hewlett Packard 35601A - Spectrum Analyser Interface	£1000
Hewlett Packard 3561A - Dynamic Signal Analyser	£4750
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£6500
Hewlett Packard 3580A - 5Hz-50KHz	£995
Hewlett Packard 3582A - 0.02Hz - 25.6KHz (dual ch.)	£2900
Hewlett Packard 3585A - 20Hz - 40MHz	£4500
Hewlett Packard 8753A - Network Analyser	£4995
Hewlett Packard 8753B - Network Analyser	£6500
IFR 7750 10KHz - 1GHz	£2500
Marconi 2370 - 110MHz	£500
Marconi 2371 - 30KHz - 2000MHz	£750
Meguro MSA 4901 - 1-300GHz (AS NEW)	£850
Meguro MSA 4912 - 1-1GHz (AS NEW)	£1250
Rohde & Schwarz - SWOB 5 Polyskop 0.1 - 1300MHz	£1500
Takeda Ritken 4132 - 1.0GHz Spectrum Analyser	£2500
Tektronix 7L18 with mainframe (1.5-60GHz with external mixers)	£2000
Tektronix 485F - 100Hz - 1.8GHz programmable	£4950
Tektronix 496P - 1KHz - 1.8GHz Spectrum Analyser	£4500

MISCELLANEOUS

Adret 740A - 100KHz - 1120MHz Synthesised Signal Generator	£800
Anritsu MG 360A Signal Generator 0.1-1040MHz	£1500
Anritsu ME 482B Dr/3 Transmission Analyser	£2500
Anritsu MG 645B Signal Generator 0.05-1040MHz	£2850
Boonton 92C R/F Millivoltmeter	£350
Boonton 93A True RMS Voltmeter	£250
Dranetz 626 - AC/DC - Multifunction Analyser	£800
EIP 331 - Frequency counter 18GHz	£800
EIP 545 - Frequency counter 18GHz	£1250
EIP 575 - Frequency counter 18GHz	£1450
Etek SMP5 - Power Supply 60-30V	£400
ENI 550L - Power Amplifier (1.5-4000MHz) 50W	£1500
Farnell TSV-70 MKII Power Supply (70V - 5A or 35V - 10A)	£250
Farnell DSG-1 Synthesised Signal Generator	£125
Farnell ESG-1000 Synthesised Signal Generator 1GHz (as new)	£995
Farnell AP 30250A Power Supply 3v - 250A	£1750
Feedback PFG 605 Power Function Generator	£1750
Fluke 5100A - Calibrator	£2500
GN ELM1 EPR31 PCM Signalling Recorder	£3000
Guideline 9152 - T12 Battery Standard Cell	£550
Hewlett Packard 1830D - Logic Analyser (43 Channels)	£650
Hewlett Packard 16500A - Fitted with 16510A/16515A/16530A/16531A - Logic Analyser	£4000
Hewlett Packard 331A - Distortion Analyser	£300
Hewlett Packard 333A - Distortion Analyser	£300
Hewlett Packard 334A - Distortion Analyser	£300
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen.	£1500
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz - 21MHz)	£1000
Hewlett Packard 3437A System voltmeter	£250
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 3455A 6 1/2 Digit Multimeter (Autocal)	£300
Hewlett Packard 3456A Digital voltmeter	£800
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-ins available)	£550

Hewlett Packard 3478A - Multimeter (5 1/2 Digit) - HP - 1B	£550
Hewlett Packard 35600A Dual Ch Dynamic Signal Analyser	£3750
Hewlett Packard 3586A - Selective Level Meter	£1000
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£2250
Hewlett Packard 3746A - Selective Measuring Set	£750
Hewlett Packard 3776A - PCM Terminal Test Set	£1500
Hewlett Packard 3779C - Primary Max Analyser	from £500
Hewlett Packard 3784A - Digital Transmission Analyser	£5000
Hewlett Packard 3785A - Jitter Generator + Receiver	£1250
Hewlett Packard 37900D - Signalling Test Set (No 7 and ISDN)	£4250
Hewlett Packard P382A Variable Attenuator	£250
Hewlett Packard 4192A - LF Impedance Analyser	£7000
Hewlett Packard 4292A - Digital LCR Meter	£1250
Hewlett Packard 4278A - 1MHz C/V Meter	£450
Hewlett Packard 4342A Q Meter	£800
Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 4948A - (TIMS) Transmission Impairment M/Set	£1500
Hewlett Packard 4972A - Lan Protocol Analyser	£1750
Hewlett Packard 5183 - Waveform Recorder	£250
Hewlett Packard 5238A Frequency Counter 100MHz	£250
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5316A - Universal Counter (IEEE)	£500
Hewlett Packard 5335A - 200MHz High Performance Systems Counter	£600
Hewlett Packard 5370B - Universal Timer/Counter	£2000
Hewlett Packard 5384A - 225 MHz Frequency Counter	£650
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005	£995
Hewlett Packard 6033A Power Supply Auroranging (20V - 30A)	£350
Hewlett Packard 6033A Power Supply Auroranging (20V - 30A)	£750
Hewlett Packard 6253A Power Supply 20V - 3A Twin	£200
Hewlett Packard 6255A Power supply 40V - 1.5A Twin	£200

**HEWLETT PACKARD 6261B
Power Supply 20V-50A Discount for Quantities**

Hewlett Packard 6264B - Power Supply (0 - 20V, 0 - 25A)	£400
Hewlett Packard 6266B Power Supply 40V - 5A	£220
Hewlett Packard 6271B Power supply 60V - 3A	£225
Hewlett Packard 6632A - Power Supply (20V - 5A)	£300
Hewlett Packard 7475A - 6 Pen Plotter	£250
Hewlett Packard 7550A - 8 Pen Plotter A3/A4	£450
Hewlett Packard 8015A - 50MHz Pulse Generator	£750
Hewlett Packard 8152A - Optical Average Power Meter	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 - 011)	£1100
Hewlett Packard 8165A - 50MHz Programmable Signal Source	£1650
Hewlett Packard 8180A - Data Generator	£1500
Hewlett Packard 8182A - Data Analyser	£1500
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various plug-in options available)	£2500
Hewlett Packard 8355A - Wave Source Module 26.5 to 40GHz	£3500
Hewlett Packard 8355A - Millimeter - Wave source Module 33-50GHz	£4250
Hewlett Packard 8405A - Vector Voltmeter	£350
Hewlett Packard 8620C Sweep oscillator mainframe	from £225
Hewlett Packard 8640B - Signal Generator (512MHz - 1024MHz)	from £850
Hewlett Packard 8656A - Synthesised Signal Generator (90MHz)	£1250
Hewlett Packard 8656B - Synthesised Signal Generator	£1750
Hewlett Packard 8657A - Signal Generator (100KHz-1040MHz)	£2500
Hewlett Packard 8660D - Synthesised Signal Generator (10KHz-2600MHz)	£3250
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8756A - Scalar Network Analyser	£1500
Hewlett Packard 8757A - Scalar Network Analyser	£2250
Hewlett Packard 8901A - Modulation Analyser	£2750
Hewlett Packard 8901B - Modulation Analyser	£3750
Hewlett Packard 8903A - Audio Analyser (20Hz - 100KHz)	£1600
Hewlett Packard 8903B - Distortion Analyser	£2500
Hewlett Packard 8903E - Distortion Analyser (Mini)	£2000
Hewlett Packard 8920A - R/F Comms Test Set	£4995
Hewlett Packard 8920B - GSM Radio Comms Test Set	£8500
Hewlett Packard 8958A - Cellular Radio Interface	£2000
Keytek MZ-15/EC Minizap 15Kv Hand Held ESD Simulator	£1750
Krohn-Hite 2200 Lin/Log Sweep Generator	£995
Krohn-Hite 4024A Oscillator	£250
Krohn-Hite 5200 sweep, Function Generator	£350
Krohn-Hite 6500 Phase Meter	£250
Leader LDM-170 - Distortion Meter	£350
Leader 3216 - Signal Generator (100KHz - 140KHz z) AM/FM/CW with built-in FM stereo modulator (mnt)	£995
Marconi 2019 - 80KHz - 1040MHz Synthesised Sig. Gen.	£950
Marconi 2019A - 80KHz - 1040MHz - Synthesised Signal Generator	£1250
Marconi 2305 - Modulation Meter	£1995
Marconi 2337A - Automatic Distortion Meter	£1150
Marconi 2810 - True RMS Voltmeter	£850
Marconi 2871 Data Comms Analyser	£1000
Marconi 2955 - Radio Comms Test Set	£2250
Marconi 6960 - Power Meter & Sensor	from £950
Phillips PM 5167MHz function gen	£400
Phillips 5190 L.F. Synthesiser (S.P.I.B)	£800
Phillips 5193 Synthesised Function Generator	£1500
Phillips 5518 Synthesised Signal Generator	£1500
Phillips PM5519 - TV Pattern Generator	£350
Phillips PM5716 - 50MHz Pulse Generator	£525
Prima 4000 - 6 1/2 Digit Multimeter (NEW)	£450
Quartzlock 2A - Off Air Frequency Standard	£200
Racal 1992 - 1 GHz Frequency Counter	£800
Racal 6111/6151 - GSM Radio Comms Test Set	£POA
Racal Dana 9081/9082 Synth. sig. gen. 520MHz	from £500
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal 9301A - True RMS R/F Multivoltmeter	£300
Racal Dana 9302A R/F multivoltmeter (new version)	£375
Racal Dana 9303 R/F Level Meter & Head	£550
Racal Dana 9917 UHF Frequency meter 500MHz	£175
Rohde & Schwarz LFM2 - 60MHz Group Delay Sweep Gen.	£1600
Rohde & Schwarz Scud Radio Code Test Set	£300
Rohde & Schwarz CMTA 94 GSM Radio Comms Analyser	£7500
Schaffner NSG 203A Line Voltage Variation Simulator	£950
Schaffner NSG 222A Interference Simulator	£850
Schaffner NSG 223 Interference Generator	£850
Schlumberger 2720 1250MHz Frequency Counter	£1500
Schlumberger 4031 - 1GHz Radio Comms Test Set	£4995
Schlumberger Stabilock 4040 Radio Comms Test Set	£2995
Schlumberger 7060/7065/7075 Multimeters	from £350
Solartron 1250 - Freq. Response Analyser	£2500
Stanford Research DS 340 - 15MHz Synthesised Function (NEW) and arbitrary waveform generator	£1200
Syston Donner 6030 - Microwave Frequency Counter (26.5GHz)	£2500
Tequipment CT71 Curve Tracer	£250
Tektronix AM503 + TM501 + P6302 - Current Probe Amplifier	£995
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope Calibrator	£1995
Tektronix 577 - Curve Tracer	£1150
Tektronix 1240 Logic Analyser	£500
Tektronix 141A PAL Test Signal Generator	£250
Tektronix AA5001 + TM5006 M/F - Programmable Distortion Analyser	£1995
Tektronix TM5003 + AFG 5101 Arbitrary Function Gen	£1500
Tektronix DAS9100 - Senses Logic Analyser	£500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PG502, TG501, TR503 + many more	£250
Time 9811 Programmable Resistance	£400
Time 9814 Voltage Calibrator	£550
Valhalla Scientific - 2724 Programmable Resistance Standard	£P.O.A.
Wandel & Gottmann PF-J-8 - Error/Jitter Test Sat.	£12500
Wandel & Gottmann PCM44 (+ options)	£9950
Wandel & Gottmann MU30 Test Point Scanner	£2000
Wayne Kerr 4225 - LCR Bridge	£300
Wavetek 171 - Synthesised Function Generator	£250
Wavetek 172B Programmable Sig Source (0.0001Hz - 13MHz)	£P.O.A.
Wavetek 184 - Sweep Generator - 5MHz	£250
Wavetek 3010 - 1-1GHz Signal Generator	£1250
Whitron 8409 - RF Analysers (1MHz - 2GHz)	£POA
Whitron 8620S - Programmable Sweep Generator (3.6 - 6.5GMHz)	£850
Whitron 8747-20 - Sweep Frequency Synthesiser (10MHz-20GHz)	£4950
Yokogawa 3655 - Analysing Recorder	£POA

**MANY MORE ITEMS AVAILABLE -
SEND LARGE S.A.E. FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED -
WITH 30 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE
ORDERING - CARRIAGE & VAT TO BE ADDED
TO ALL GOODS**

£1.50 BARGAIN PACKS


NICAD BATTERY 3-6V p.c.b. mounting prongs. Order Ref: 1.5P2.
6 DIGIT COUNTER 12V. Order Ref: 1.5P3.
PAIR OF ULTRASONIC MODULES, one sender, one receiver. Order Ref: 1.5P4.
100 CORE CABLE, any length. Order Ref: 1.5P6 per metre.
KEY SWITCH, 2 position, complete with 2 Yale type keys. Order Ref: 1.5P12.
CASSETTE MOTOR, 9V brushless. Order Ref: 1.5P14.
80 OHM COAX TV CABLE, extra thin, 10m. Order Ref: 1.5P17.
WATERPROOF SPEAKER, 3/4in. round, 8 ohm 11W. Order Ref: 1.5P27.
6V 1A ENCASED POWER SUPPLY with leads. Order Ref: 1.5P22.
FLUORESCENT CHOKE for 60 or 80W tube. Order Ref: 1.5P23.
3in. TWEETER 15W 8 ohms. Order Ref: 1.5P28.
RELAY, flash proof, 12V coil, SPCO. Order Ref: 1.5P31.
ENCASED PSU, twin outputs, 15V 850mA and 9V 550mA, both AC. Order Ref: 1.5P32.
12V MOTOR, mini but quite powerful, 32mm diameter, 25mm long. Order Ref: 1.5P33.
3V PRECISION CASSETTE MOTOR. Order Ref: 1.5P34.
12V 1/2A TRANSFORMER, frame mounted. Order Ref: 1.5P41.
12V 800mA DC PSU. Order Ref: 1.5P44.
BT PLUG WITH SOCKET for 2 flat plug phones. Order Ref: 1.5P56.
TWIN 13A MAINS SOCKET, white for flush mounting. Order Ref: 1.5P61.

£2 BARGAIN PACKS

20W TWEETER, 4in. x 4in. 8 ohm by Goodmans. Order Ref: 2P403.
BATTERY CHARGER METER 0-3A. Order Ref: 2P366.
W-SHAPED 30W FLUORESCENT. Philips, ideal name plate illuminator. Order Ref: 2P372.
DIMMER SWITCH, standard size flush plate, state colour - red, yellow, green or blue. Order Ref: 2P380.
TELEPHONE EXTENSION LEAD, 12m with plug end, socket ends. Order Ref: 2P388.
FIGURE 8 FLEX, mains voltage, 50m. Order Ref: 2P345.
INFRA-RED RECEIVER, as fitted TV receiver. Order Ref: 2P304.
L.C.D. CLOCK MODULE with details of other uses. Order Ref: 2P307.
AM/FM RADIO RECEIVER with speaker but not cased. Order Ref: 2P308.
12V 200mA PSU on 13A base. Order Ref: 2P313.
2A MAINS FILTER AND PEAK SUPPRESSOR. Order Ref: 2P315.
45A DP 250V SWITCH on 6in. x 3in. gold plate. Order Ref: 2P316.
SOLAR CELL 3V, 200mA, 5 of these in series would make you a 12V battery charger. £2 each. Order Ref: 2P374.
PERMANENT MAGNET SOLENOID, opposite action, core is released when voltage is applied. Order Ref: 2P327.
HEATER PAD, not waterproof. Order Ref: 2P329.
15V 320mA AC POWER SUPPLY, in case with 13A base, ideal for bell or chime controller. Order Ref: 2P281.
POWERFUL MAINS MOTOR with 4in. spindle. Order Ref: 2P262.
20M 80 OHM TV COAX. Order Ref: 2P215.
6 DIGIT COUNTER, mains operated. Order Ref: 2P235.
13A ADAPTORS, take 2 13A plugs, pack of 5 - £2. Order Ref: 2P187.
3-CORE 5A PVC FLEX, 15m. Order Ref: 2P189.
MAIN TRANSFORMER, 15V 1A. Order Ref: 2P198.
7-SEGMENT NEON DISPLAYS, pack of 8. Order Ref: 2P126.
MODERN TELEPHONE HANDSET, ideal office extension. Order Ref: 2P94.
500 STAPLES, hardened pin, suit burglar alarm or telephone wire. 2P99.
PAD SWITCH for under carpets. Order Ref: 2P119.
24V STEREO POWER SUPPLY, Mullard. Order Ref: 2P80.
UP TO 90 MIN 25A SWITCH, clockwork. Order Ref: 2P90.
POWER SUPPLY FOR MODELS, 6-12V variable and reversible. Order Ref: 2P3.
MAIN TIME AND SET SWITCH 25A, up to 9 hours delay. Order Ref: 2P9.
MOTORISED 6 MICRO SWITCHES but motor 50V AC. Order Ref: 2P19.
TWIN EXTENSION LEAD, ideal lead lamp, Black & Decker tools, etc., 20m. Order Ref: 2P20.
MAIN COUNTER, resettable, 3 digit. Order Ref: 2P26.
20M 30 GAUGE COPPER WIRE, silver plated and PTFE insulated. Order Ref: 2P415.
WIDE AIR SPACED 2 GANG TUNING CAP for transmitter, etc. Order Ref: 2P425.
6 RPH MAINS DRIVEN 2W MOTOR. 2P430.
6-HOUR CLOCKWORK TIMESWITCH with scale. Order Ref: 2P432.
GALVANISED BOX, 6in. x 6in. x 1in. deep. Order Ref: 2P433.
FLUORESCENT CHOKE for 5ft. tube. Order Ref: 2P440.
BALANCE KIT for chemical experiments, with weights. Order Ref: 2P444.
9V 1A PSU, encased, plugs into 13A socket. Order Ref: 2P450.
END OF TRAVEL MICROSWITCH. Order Ref: 2P455.

LIGHT ALARM. A circuit for this appears in the February issue. However, we have a rather less complicated model already made up and in a nice case, price only £3. Order Ref: 3P155.

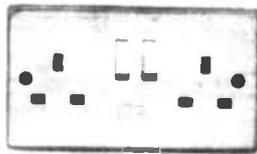TWIN 13A SWITCHED SOCKET. Standard in all respects and complete with fixing screws. White, standard size and suitable for flush mounting or in a surface box. Price £1.50. Order Ref: 1.5P61.



VERY POWERFUL BATTERY MOTORS. Were intended to operate portable screwdrivers. Approximately 2 1/2in. long, 1 1/2in. diameter, with a good length of spindle. Will operate with considerable power off any voltage between 6 and 12 D.C. Price £2. Order Ref: 2P456. Quantity discount 25% for 100.

RECHARGEABLE BATTERIES. AAA size, pack of 4. £2.50. Order Ref: 2.5P32.

BIG 12V TRANSFORMER. Over 4A normal working. Beautifully made and well insulated, terminals are in a plastic frame so can't be accidentally touched. Price £3.50. Order Ref: 3.5P20.

SPECIAL YUASA BATTERY OFFER. You can have 5 x 12V Yuasa batteries, the one we normally sell for £3.50, for £15. These batteries have a capacity of 2-3AH. This may be a bit low for some jobs, but remember you can join them in parallel to give you a higher amperage. Order Ref: 15P77.

BUY ONE GET ONE FREE

CASED POWER SUPPLIES which, with a few small extra components and a bit of modifying, would give 12V at 10A. Originally £9.50 each, now 2 for £9.50. Order Ref: 9.5P4.

3 OCTAVE KEYBOARD with piano size keys, brand new, previous price £9.50, now 2 for the price of one. Use the same Order Ref: 9.5P5.

SOUND SWITCH. Can be operated by clapping hands, shouting or almost any other noise. Comes complete with instructions, assembled and ready to work but needs casing. Price only £3. Order Ref: 3P246.

1MA PANEL METER. Approximately 80mm x 55mm, front engraved 0-100. Price £1.50 each. Order Ref: 1/16R2.

VERY THIN DRILLS. 12 assorted sizes vary between 0.6mm and 1.6mm. Price £1. Order Ref: 128.

EVEN THINNER DRILLS. 12 that vary between 0.1mm and 0.5mm. Price £1. Order Ref: 129.

BT PLUG WITH TWIN SOCKET. Enables you to plug 2 telephones into the one socket for all normal BT plugs. Price £1.50. Order Ref: 1.5P50.

D.C. MOTOR WITH GEARBOX. Size 60mm long, 30mm diameter. Very powerful, operates off any voltage between 6 and 24 D.C. Speed at 6V is 200 rpm, speed controller available. Special price £3 each. Order Ref: 3P108.

FLASHING BEACON. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses an Xenon tube and has an amber coloured dome. Separate fixing base is included so unit can be put away if desirable. Price £5. Order Ref: 5P267.

MOST USEFUL POWER SUPPLY. Rated at 9V 1A, this plugs into a 13A socket. Is really nicely boxed. £2. Order Ref: 2P733.

MOTOR SPEED CONTROLLER. These are suitable for D.C. motors for voltage up to 12 and any power up to 1/6 h.p. They reduce the speed by intermittent full voltage pulses so there should be no loss of power. In kit form these are £12. Order Ref: 12P34. Or made up and tested, £20. Order Ref: 20P39.

VARTA BATTERIES. A big purchase enables us to offer you 8 Varta AA batteries for only £1. These are really good batteries, give you long life. Order Ref: D511.

BT TELEPHONE EXTENSION WIRE. This is proper heavy duty cable for running around the skirting board when you want to make a permanent extension. 4 cores properly colour coded, 25m length. Only £1. Order Ref: 1067.

A MUCH LARGER PROJECT BOX. Size 216mm x 130mm x 85mm with lid and 4 screws. This is an ABS box with normally retails at around £6. All brand new, price £2.50. Order Ref: 2.5P28.

LARGE TYPE MICROSWITCH with 2in. lever, changeover contacts rated at 15A at 250V, 2 for £1. Order Ref: 1/21R7.

BALANCE ASSEMBLY KITS. Japanese made, when assembled ideal for chemical experiments, complete with tweezers and 6 weights 0.5 to 5 grams. Price £2. Order Ref: 2P444.

CYCLE LAMP BARGAIN. You can have 100 6V 0-5A MES bulbs for just £2.50 or 1,000 for £20. They are beautifully made, slightly larger than the standard 6-3V pilot bulb so they would be ideal for making displays for night lights and similar applications.

DOORBELL PSU. This has AC voltage output so is ideal for operating most doorbells. The unit is totally enclosed so perfectly safe and it plugs into a 13A socket. Price only £1. Order Ref: 1/30R1.

£3 BARGAIN PACKS

MAINS SUPPRESSOR/FILTER, 15a. Order Ref: 3P13.

MAINS TRANSFORMER, 36V 3A. Order Ref: 3P14.
SIGNAL BOX, 3 pilot lamps in white metal case. Order Ref: 3P16.

120W CHOKE, 8ft. tube. Order Ref: 3P17.

0-5A PANEL METER, ex-W.D. equipment. Order Ref: 3P20.

KEYBOARD intended for OPD computer. Order Ref: 3P27.

SOLAR CELL, 750mA. Order Ref: 3P42.

PROJECT BOX with lid, 165mm x 119mm x 75mm. Order Ref: 3P49.

INSTRUMENT TYPE MAINS INPUT SOCKET with built-in filter. Order Ref: 3P50.

6-CORE 3A FLEX, 15m. Order Ref: 3P54.

20V 3A MAINS TRANSFORMER. Order Ref: 3P59.

1/2 RPM 2W MOTOR. Order Ref: 3P64.

METAL PROJECT BOX, size 8in. x 4 1/2in. x 4in., made for GPO. Order Ref: 3P74.

THIN CONNECTING WIRE, 2 cores twisted together, full length 500m. Order Ref: 3P78.

12V 1A PSU, filtered and regulated on p.c.b. with relays and Piezo sander. Order Ref: 3P80.

HORN SPEAKER, 8 ohm, size 4 1/4in. Order Ref: 3P82.

20A TIME SWITCH, ex-electricity board. Order Ref: 3P84.

ABS PROJECT BOX, 145mmx95mmx58mm. Order Ref: 3P85.

HEAT AND LIGHT LAMP IBC 250W. Order Ref: 3P86.

BT INSULATION TESTER, faulty but should be repairable. Supplied with circuit diagram. Order Ref: 3P103.

MODERN TELEPHONE HANDSET without dial, cream. Order Ref: 3P104.

20V 3A MAINS TRANSFORMER. Order Ref: 3P106.

40V 2A MAINS TRANSFORMER. Order Ref: 3P107.

3-CORE 20A FLEX, 10m. Order Ref: 3P109.

CUPBOARD DOOR ALARM. Order Ref: 3P155.

WATER LEVEL ALARM, fully adjustable. Order Ref: 3P156.

HEAVY DUTY MAINS MOTOR with 2 1/2in. spindle each side. Order Ref: 3P157.

RESETTABLE 6-DIGIT 12V COUNTER. Order Ref: 3P158.

6FT MINERAL FILLED METAL CLAD 1000W ELEMENT. Order Ref: 3P161.

TIME AND SET SWITCH for mains at 30A. Order Ref: 3P164.

AMSTRAD 8in. 15W WOOFER. Order Ref: 3P167.

12V BRUSHLESS FAN mounted in frame with its own drive circuit. Order Ref: 3P168.

SOLENOID AIR VALVE, 110V. Order Ref: 3P178.

TRANSFORMER AND RECTIFIER for 12V charger. Order Ref: 3P188.

12-0-12V 25VA MAINS TRANSFORMER. Order Ref: 3P181A.

5in. 8 OHM SPEAKER IN WOODEN CABINET. Order Ref: 3P183.

15UF 440V AC CAPACITOR. Order Ref: 3P190.

25UF 370V AC CAPACITOR. Order Ref: 3P202.

MAINS OPERATED WATER VALVE, suit high or low pressure. Order Ref: 3P192. Order Ref: 3P194.

AMSTRAD AMPLIFIER, ref. no. not known, is stereo and has 10 LEDs on front panel. Order Ref: 3P195.

HALOGEN LAMP, 12V 20W. Order Ref: 3P200.

18in. ROD THERMOSTAT, calibrated for water temperature. Order Ref: 3P211.

120W FLUORESCENT CHOKE, badly stored so cases need repainting, pack of 2. Order Ref: 3P213.

MICROPHONE, hand held, dynamic, 500 ohm. Order Ref: 3P220.

HEAVY DUTY SOLDERING IRON, mains 40W. Order Ref: 3P221.

12V BATTERY MOTOR WITH GEARBOX. Order Ref: 3P108.

TWIN 13A SOCKET, panel sockets are switched. Order Ref: 3P241.

SOUND OPERATED SWITCH, made up but not boxed. Order Ref: 3P346.

5in. UV BLACK LIGHT TUBE. Order Ref: 3P247.

FM FRONT END. Order Ref: 3P248.

TERMS

Send cash, P.O. cheque or quote credit card number - orders under £25 add £3.50 service charge.

J & N FACTORS
Pilgrim Works (Dept. E.E.)
Stairbridge Lane, Bolney,
Sussex RH17 5PA
Telephone: 01444 881965

#1 For Broadcasting Kits Since 1980

88 - 108 MHz

VERONICA



FM Radio Transmitter Kits


- FM transmitter Kits From just **£13.95**.
- Professionally built FM transmitters from only **£19.95**.
- **Powerful** kits: up to **35-Watts** power!
- Professional systems up to **220-Watts** power!
- Range of **Aerials** and Accessories available
- Professional **Link systems** available.



Special Offer!



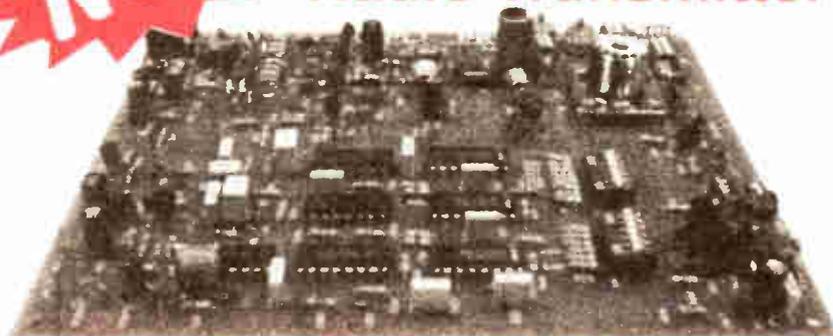1-Watt PLL Pro II
88-108MHz FM
Radio Transmitter



Now even better performance!

PRICE FREEZE!
STILL ONLY £67.95

Get in touch
now for more
information
and claim your
FREE
Brochure



24 hour
phone / fax

01274 816200



Or contact us
by post @:


18 Victoria Street,
Queensbury,
Bradford,
W YORKS.
BD13 1AR.

MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

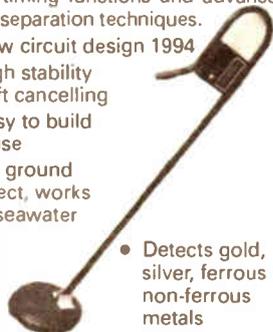- New circuit design 1994
- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847.....£63.95

PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

SUPER ACOUSTIC PROBE

Our very popular project - with probe components and diecast box. Picks up vibrations amplifies, and drives headphones. Sounds from engines, watches, and speech through walls can be heard clearly. Useful for mechanics, instrument engineers and nosey parkers! A very useful piece of kit.

KIT 865.....£29.95

DC Motor/Gearboxes

Our Popular and Versatile DC Motor/Gearbox sets. Ideal for Models, Robots, Buggies etc. 1.5 to 4.5V Multi ratio gearbox gives wide range of speeds.

LARGE TYPE - MGL £6.95
SMALL - MGS - £4.77



Stepping Motors

MD38...Mini 48 step...£8.65
MD35...Std 48 step...£9.99
MD200...200 step...£12.99
MD24...Large 200 step...£22.95



MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A.

Based on our MkI design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845.....£64.95

PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, P.C.B, coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor

KIT 868£22.95 POWER UNIT.....£3.99



MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets pests away from newly sown areas. play areas, etc. Uses power source from 9 to 24 volts.

- RANDOM PULSES
- HIGH POWER
- DUAL OPTION

Plug-in power supply £4.99

KIT 867.....£19.99

KIT + SLAVE UNIT.....£32.50



WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856.....£28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.


KIT 866.... Full kit including four electrodes £32.90

Set of 4 spare electrodes £6.50

1000V & 500V INSULATION TESTER

Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms. Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95

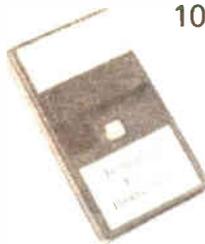

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849.....£16.99!

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV

KIT 790.....£28.51

SUPER BAT DETECTOR

1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE

20kHz-140kHz

NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full bridge' audio amplifier i.c., internal speaker, and head-phone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.

KIT 861.....£24.99

ALSO AVAILABLE Built & Tested£39.99

E.E. TREASURE HUNTER P.I. METAL DETECTOR MKI

Magenta's highly developed & acclaimed design. Quartz crystal controlled circuit MOSFET coil drive. D.C. coupled amplification. Full kit includes PCB, handle, case & search coil.

- KIT INC. HEADPHONES
- EFFICIENT CMOS DESIGN
- POWERFUL COIL DRIVE

- DETECTS FERROUS AND NON-FERROUS METAL - GOLD, SILVER, COPPER ETC.
- 190mm SEARCH COIL
- NO 'GROUND EFFECT'

KIT 815.....£45.95



EPE PROJECT PICs

NOW £5.90

Programmed PICs for all* EPE Projects
Now one price
£5.90 each

(*some projects are copyright)

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS
- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812.....£14.81



SIMPLE PIC PROGRAMMER

INCREDIBLE LOW
PRICE!

Kit 857 **£12.99**

INCLUDES 1-PIC16F84 CHIP
SOFTWARE DISK, LEAD
CONNECTOR, PROFESSIONAL
PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:
PIC 16F84 £4.84

Based on the design in February '96 *EPE* article, Magenta have made a proper PCB and kit for this project. PCB has 'reset' switch, Program switch, 5V regulator and test L.E.D.s. There are also extra connection points for access to all A and B port pins.

PIC16C84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16F84
WITH DEMO PROGRAM
SOFTWARE DISK, PCB,
INSTRUCTIONS AND
24-CHARACTER 2-LINE
LCD DISPLAY

Kit 860 **£19.99**

Power Supply £3.99

FULL PROGRAM SOURCE
CODE SUPPLIED – DEVELOP
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers – Just waiting for your application!

★ Chip is pre-programmed with demo display ★

PIC16C84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16F84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING – 10 CHASE PATTERNS
- OPTO ISOLATED
- 4 X 3 KEYPAD CONTROL
- SPEED CONTROL POT.
- HARD FIRED TRIACS
- 4 CHANNELS @5 AMPS

Now features full 4-channel chaser software on DISK and pre-programmed PIC16F84 chip. Easily re-programmed for your own applications. Software source code is fully 'commented' so that it can be followed easily.

Kit 855 **£39.95**

LOTS OF OTHER APPLICATIONS

PhizzyB

ALL PARTS FOR SERIES INCLUDING PCBs, PROGRAMMED CHIP, CD-ROM AND DISPLAYS

MAIN BOARD – FULL KIT ... **£131.95** BUILT ... **£149.95**
I/O PORTKIT **£16.99** BUILT **£24.99**
L.C.D. **£12.49** POWER SUPPLY **£3.99**
8-BIT SWITCH/LATCH **£7.95** INT. MODULE **£10.45**

68000

DEVELOPMENT AND
TRAINING KIT

KIT 621

£99.95


8 MHz 68000 16-BIT BUS
MANUAL AND SOFTWARE
2 SERIAL PORTS, PIT,
AND I/O PORTS



PSU £6.99
SERIAL LEAD £3.99

Mini-Lab & Micro Lab Electronics Teach-In 7

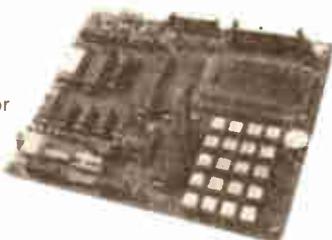As featured in *EPE* and now published as Teach-In 7. All parts are supplied by Magenta. *Teach-In 7* is £3.95 from us or *EPE*
Full Mini Lab Kit – £119.95 –
Power supply extra – £22.55
Full Micro Lab Kit – £155.95
Built Micro Lab – £189.95



EPE PIC Tutorial

NEW!

At Last! A Real, Practical, Hands-On Series
3-Part Series – Starting March '98

- Learn Programming from scratch
- Uses Re-Programmable PIC16F84 Chip
- Start by lighting an l.e.d. and work up through over 30 tutorials to Sound Generation, Data Display, and a Security System
- PIC TUTOR Board has Input Switches, Output l.e.d.s, and on board programmer

PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components* (*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

KIT 870 **£27.95**, Built & Tested **£42.95**
Optional: Power Supply – £3.99, ZIF Socket – £9.99

LCD Display – With Software and Connection details **£7.99**

LED Display – Including Software..... **£6.99**

PIC TOOLKIT

- PROGRAMS PIC16C84 and 16F84
- ACCEPTS TASM AND MPASM CODE

Full kit includes PIC16F84 chip, top quality p.c.b. printed with component layout, turned pin PIC socket, all components and software* *Needs QBASIC or QUICKBASIC

KIT 871 . . . **£13.99**. Built and tested **£21.99**

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS™ SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED PIN SOCKETS FOR 18, 28, AND 40 PIN ICs.

- SEND FOR DETAILED INFORMATION – A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

DISASSEMBLER
SOFTWARE **£11.75**

PIC STEPPING MOTOR DRIVER

INCLUDES: PCB,
PIC16F84 WITH
DEMO PROGRAM,
SOFTWARE DISK,
INSTRUCTIONS
AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED.
ALSO USE FOR DRIVING OTHER
POWER DEVICES e.g. SOLENOIDS.

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor – up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

MAGENTA

All prices include VAT. Add £3.00 p&p. Next Day £6.99

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ



All Major Credit cards Accepted

Prices Exclude Vat @17.5%. Add £1.25 carriage & Vat to all orders. Cheques / Postal orders payable to ESR Electronic Components.

See Next / Last Months Ad for COMPONENT ACCESSORIES

DIL Sockets

6 Pin DIL 0.3"	£0.06
8 Pin DIL 0.3"	£0.06
14 Pin DIL 0.3"	£0.11
16 Pin DIL 0.3"	£0.11
18 Pin DIL 0.3"	£0.12
20 Pin DIL 0.3"	£0.11
24 Pin DIL 0.6"	£0.13
28 Pin DIL 0.6"	£0.13
40 Pin DIL 0.6"	£0.19
Turned Pin	
8 Pin DIL 0.3"	£0.11
14 Pin DIL 0.3"	£0.20
16 Pin DIL 0.3"	£0.23
18 Pin DIL 0.3"	£0.25
20 Pin DIL 0.3"	£0.28
24 Pin DIL 0.6"	£0.35
28 Pin DIL 0.6"	£0.41
40 Pin DIL 0.6"	£0.64

SIL Pin Header Strip

1 x 36 Way Straight	£0.58
2 x 36 Way Straight	£0.36
1 x 36 Way 90°	£0.54
2 x 36 Way 90°	£0.80

Available in 2,3,4,5 & 10 way. Also female PCB sockets & jumper links.

20 Way Socket Strip

20 Way Socket Strip £0.48

Transistor Sockets

T018-4 Base Socket	£0.24
T05 Base Socket	£0.24

IDC Cable Sockets

10 Way Socket	£0.23
14 Way Socket	£0.34
16 Way Socket	£0.28
20 Way Socket	£0.35
26 Way Socket	£0.35
34 Way Socket	£0.52
40 Way Socket	£0.66
50 Way Socket	£0.75

PCB Box Headers

10 Way Straight	£0.27
14 Way Straight	£0.36
16 Way Straight	£0.36
20 Way Straight	£0.32
26 Way Straight	£0.57
34 Way Straight	£0.57
40 Way Straight	£0.63
50 Way Straight	£0.96
10 Way 90°	£0.33
16 Way 90°	£0.42
20 Way 90°	£0.53
26 Way 90°	£0.70
34 Way 90°	£0.81
40 Way 90°	£0.83
50 Way 90°	£0.95

PCB Latch Headers

10 Way Straight	£0.50
16 Way Straight	£0.70
20 Way Straight	£0.78
26 Way Straight	£0.81
34 Way Straight	£0.86
40 Way Straight	£1.56
50 Way Straight	£1.29
10 Way 90°	£0.58
16 Way 90°	£0.78
20 Way 90°	£0.82
26 Way 90°	£1.06
34 Way 90°	£1.14
40 Way 90°	£1.14
50 Way 90°	£1.74

DIL Headers

14 Way DIL	£0.54
16 Way DIL	£0.59
24 Way DIL	£0.90
40 Way DIL	£1.02

Transition Headers

10 Way Transition	£0.49
14 Way Transition	£0.47
16 Way Transition	£0.47
20 Way Transition	£0.54
26 Way Transition	£0.62
34 Way Transition	£0.66
40 Way Transition	£0.90
50 Way Transition	£1.02

D Type Connectors

9 Way Male Plug	£0.29
9 Way Female Socket	£0.28
15 Way Male Plug	£0.36
15 Way Female Socket	£0.39
15 Way H.D. Plug	£0.47
15 Way H.D. Socket	£0.78
23 Way Male Plug	£0.49
23 Way Female Socket	£0.49
25 Way Male Plug	£0.36
25 Way Female Plug	£0.39

IDC Ribbon Mounting

9 Way Female Socket	£1.08
25 Way Male Plug	£1.08
25 Way Female Socket	£1.13

Right Angled PCB

9 Way Male Plug	£0.37
9 Way Female Socket	£0.35
15 Way H.D. Socket	£0.77
25 Way Male Plug	£0.53
25 Way Female Socket	£0.51

Audio Connectors

2.5mm Jock Plug	£0.21
2.5mm Line Socket	£0.16
2.5mm Chassis Socket	£0.09
3.5mm Mono Plug	£0.24
3.5mm Mono Chassis	£0.14
3.5mm Stereo Plug	£0.33
3.5mm Stereo Line Skt	£0.37
3.5mm Stereo Chassis	£0.34
1/4" Mono Plug	£0.34
1/4" Mono Line Socket	£0.32
1/4" Mono Chassis Skt	£0.35
1/4" Stereo Plug	£0.40
1/4" Stereo Line Socket	£0.38
1/4" Stereo Chassis Skt	£0.40

Neutrik Speakon Plug

Neutrik Speakon Plug £2.65

DIN Series

2 Pin Line Plug	£0.19
2 Pin Chassis Socket	£0.15
2 Pin Line Plug	£0.27
3 Pin Chassis Socket	£0.28
4 Pin Line Plug	£0.24
4 Pin Chassis Socket	£0.26
5 Pin Line Plug 180°	£0.30
5 Pin Chassis Skt 180°	£0.33
5 Pin Line Plug 240°	£0.24
5 Pin Chassis Skt 240°	£0.32
5 Pin Line Plug 360°	£0.24
5 Pin Chassis Skt 360°	£0.32
6 Pin Line Plug	£0.35
7 Pin Line Plug	£0.35
7 Pin Chassis Socket	£0.37
8 Pin Line Plug	£0.44
8 Pin Chassis Socket	£0.36

Phone Series

Red Line Plug	£0.20
Black Line Plug	£0.20
Yellow Line Plug	£0.20
White Line Plug	£0.20
Red Line Socket	£0.20
Black Line Socket	£0.20
Yellow Line Socket	£0.20
White Line Socket	£0.20
Red Chassis Socket	£0.20
Black Chassis Socket	£0.20
Gold Plated Plug Red	£0.66
Gold Plated Plug Black	£0.66

XL8 Series - metal

3 Pin Line Plug	£1.46
3 Pin Line Socket	£1.71
3 Pin Chassis Plug	£1.50
3 Pin Chassis Socket	£1.41
Neutrik Line Plug	£1.68
Neutrik Line Socket	£1.99
Neutrik Chassis Plug	£2.13
Neutrik Chassis Socket	£2.32

RF Connectors

BNC Plug 50Ω Solder	£0.99
BNC Plug 50Ω Crimp	£0.62
BNC Plug 75Ω Solder	£0.70
BNC Plug 75Ω Crimp	£0.70
BNC Chassis Socket	£0.83
F Plug - Twist	£0.24
F Plug - Crimp	£0.26
TNC Plug 50Ω Solder	£1.24
TNC Plug 50Ω Crimp	£0.85
TNC Plug 75Ω Solder	£1.40
TNC Plug 75Ω Crimp	£1.16
UHF Plug 5mm Cable	£0.63
UHF Plug 11mm Cable	£0.50
UHF Chassis Skt - Sqr	£0.50
UHF Chassis Skt - Rnd	£0.73

Extensive range of RF connectors in stock, inc.FME, SMA, Mini UHF & N Type.

Terminals

Colours Red, Black, Green, Blue, White or Yellow	
2mm Solder Plugs	£0.18
2mm Chassis Sockets	£0.20
4mm Solder Plugs	£0.36
4mm Chassis Sockets	£0.40
4mm Binding Posts	£0.54
33mm Crocodile Clips	£0.13

Power Connectors

DC Plug 0.7ID 2.35OD	£0.47
DC Plug 1.3ID 3.4OD	£0.32
DC Plug 1.7ID 4.0OD	£0.47
DC Plug 1.7ID 4.75OD	£0.46
DC Plug 2.1ID 5.0OD	£0.24
DC Plug 2.1ID 6.3OD	£0.46
DC Line Socket 2.1mm	£0.56
DC Chassis Skt 2.1mm	£0.40
DC Chassis Skt 2.5mm	£0.41

IEC Mains 6A 250Vac

3 Pin IEC Line Socket	£1.08
3 Pin IEC Line Plug	£1.83
3 Pin Chassis Socket	£0.55
3 Pin Chassis Plug	£0.72

8 Way Bulgin

8 Pin Line Plug P551	£4.08
8 Pin Chassis Skt P552	£1.39

Toggle Switches

9M Gender Changer	£2.18
9F Gender Changer	£2.29
25F Gender Changer	£2.80
9 Male - 25 Female	£1.90
9 Female - 25 Male	£1.90
9M - 6 Mini Din Male	£2.40
9F - 6 Mini Din Female	£2.40
5M Din - 6M Mini Din	£2.08
5F Din - 6M Mini Din	£2.08

Sub-Miniature

3A 125V 1A 250V	
5mm Ø Mounting Hole	
SPST 5 x 10mm	£0.58
SPDT 5 x 10mm	£0.60
SPDT c/Off 5 x 10mm	£0.81
DPDT 9.2 x 10mm	£0.66

Miniature

6A 125V 3A 250V	
6.2mm Ø Mounting Hole	
SPST 8 x 13mm	£0.65
SPDT 8 x 13mm	£0.60
SPDT c/o Biased 2 way	£1.10
SPDT c/o Biased 1 way	£1.04
DPDT 12 x 13mm	£0.72
DPDT c/Off 12 x 13mm	£0.80
DPDT c/o Biased 2 way	£1.28
DPDT c/o Biased 1 way	£1.28

Standard

10A 250V Push on terminals	
12mm Ø Mounting Hole	
SPST 18 x 30mm	£1.28
SPDT 18 x 30mm	£1.31
SPDT c/Off 18 x 30mm	£1.43
DPDT 21 x 30mm	£1.65
DPDT c/Off 21 x 30mm	£1.68

Slide Switches

Miniature 300mA 125V	
7 x 15mm Mounting Hole	
DPDT 7 x 23mm	£0.20

Standard

1A 125V	
5.5 x 12mm Mounting Hole	
DPDT 12 x 35mm	£0.25
DPDT c/o 12 x 35mm	£0.27

Rotary Switches

150mA 250V	
Make before Break 22mm Ø	
9.8mm Ø Mounting Hole	
1 Pole 12 Way	£0.84
2 Pole 6 Way	£0.84
3 Pole 4 Way	£0.84
4 Pole 3 Way	£0.84

Push Switches

Miniature Round 250mA 125V 28 x 10mm	
7mm Ø Mounting Hole	
Non Latching Push to Make	
Black PTM	£0.24
Red PTM	£0.24
Yellow PTM	£0.24
Green PTM	£0.24
Blue PTM	£0.24
White PTM	£0.24
Non Latching Push to Break	
Black PTB	£0.24

Standard Square

1A 250V	
39 x 15MM	
12mm Ø Mounting Hole	
Non Latching Push to Make	
Black PTM	£0.60
Red PTM	£0.60
Blue PTM	£0.60
White PTM	£0.60
Latching - push On push Off	
Black	£0.65
Red	£0.65
Blue	£0.65
White	£0.65

Rocker Switches

Miniature 6A 250V Solder Togs	
SPST 21 x 14 x 16mm	£0.69
SPST - Red Neon	£1.02
SPST - Green Neon	£1.02
SPST - Amber Neon	£1.02

Standard

15A 250V Push on Togs	
SPST 30 x 11 x 22mm	£0.58
DPDT 30 x 25 x 22mm	£1.12

Illuminated

15A 250V Push on Togs	
SPST 30x14mm Red	£0.84
DPST 30x25mm Red	£1.40
DPST 30x25mm Amber	£1.40
DPST 30x25mm Green	£1.40

Relays

PCB Mounting	
1A 24Vdc DPDT 5V	£1.44
1A 24Vdc DPDT 12V	£1.60
3A 110V SPDT 6V	£0.58
3A 110V SPDT 12V	£0.58
5A 110V SPDT 6V	£0.72
5A 110V SPDT 12V	£0.72
5A 110V DPDT 6V	£0.93
5A 110V DPDT 12V	£0.93
5A 240V DPDT 6V	£1.76
5A 240V DPDT 12V	£1.76
10A 240V SPDT 6V	£1.25
10A 240V SPDT 12V	£1.44
10A 240V SPDT 24V	£1.44

Computer Accessories

Adaptors

9M Gender Changer	£2.18
9F Gender Changer	£2.29
25F Gender Changer	£2.80
9 Male - 25 Female	£1.90
9 Female - 25 Male	£1.90
9M - 6 Mini Din Male	£2.40
9F - 6 Mini Din Female	£2.40
5M Din - 6M Mini Din	£2.08
5F Din - 6M Mini Din	£2.08

Yosters / Patch Boxes

Mini Tester 7 LEDs	£6.68
Check Tester 18 LEDs	£6.32
Enhanced + Switches	£15.25
25D Jumper Box M-F	£2.90
25D Patch Box M-F	£7.32
Anti-Static Wrist Strap	£4.76
R5232 Surge Protector	£5.43
Mains Surge Protector	£11.99
4 Gang Surge Block	£15.50

Leads & Cables

1.5m Printer Lead	£3.40
5m Printer Lead	£9.38
10m Printer Lead	£8.75
Serial Printer 25M-9F	£4.50
Serial Printer 25M-25F	£4.45

Null Modem Leads

9 Female - 9 Female	£3.45
25 Female - 25 Female	£4.63
9 Female - 25 Female	£2.90
9&25F to 9&25F	£5.54

Modem Leads

25 Male to 9 Female	£4.08
25 Male to 25 Female	£4.75

PC Link Leads

Interlink 25M to 25M	£4.38
----------------------	-------

Patch Lead

25 Male to 25 Male	£4.50
36 Male to 36 Male	£4.30

Internal Leads

EVERYDAY
PRACTICAL
ELECTRONICS

With



Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS/ETI EDITORIAL
ALLEN HOUSE, EAST BOROUGH, WIMBORNE
DORSET BH21 1PF
Phone: Wimborne (01202) 881749
Fax: (01202) 841692. **Due to the cost we cannot reply to overseas orders or queries by Fax.**

E-mail: editorial@epemag.wimborne.co.uk
Web Site: <http://www.epemag.wimborne.co.uk>
See notes on **Readers' Enquiries below** - we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:
EVERYDAY PRACTICAL ELECTRONICS/ETI
ADVERTISEMENTS
MILL LODGE, MILL LANE
THORPE-LE-SOKEN, ESSEX CO16 0ED
Phone/Fax: (01255) 861161

VOL. 28 No. 5

MAY '99

COVER CHANGES

Whilst we have had a number of important changes to our front cover over the last 23 years (from *Everyday Electronics* to *Everyday Electronics and Computer Projects* to *Everyday Electronics and Electronics Monthly* back to *Everyday Electronics*, then to *Everyday Practical Electronics/ETI*) our back cover has only carried one name - Maplin (they first took the *EE* back cover in the Jan 1976 issue). So another era comes to a close, as you will notice, this month.

A number of readers have speculated over the last year or so that Maplin are moving away from the hobby market and, with the cancellation of their regular advertising after so many years on our back cover, we wondered if there was in fact something behind this speculation. With this in mind we wrote to David O'Reilly, Marketing Manager at Maplin Electronics, to ask if Maplin had decided to reduce its support to the hobbyist in the UK. David's reply is reassuring, the relevant part of his letter reads:

"Maplin Electronics is categorically supporting the electronics hobbyist in the UK. We are doing this in a number of ways, most importantly we are developing our e-commerce site to assist retail consumers.

"Both myself and Maplin totally understand the benefits of your magazine, and your company, like ours, is one of the few organisations to continue to support this very important market.

"As with all things, budgets and time constraints mean that all communications to customers have to be constantly reviewed. We have to find the most cost effective method to provide our customers with information on special offers. Sometimes it is more appropriate to invest the time and money in providing good products at good prices, than provide promotional material specifically relating to a catalogue launch.

"I hope you find the points that I have raised in this letter cover your concerns. I cannot stress how important the hobbyist market is to Maplin, it is our heritage, our customer and it is what pays our wages."

HARD TIME

Maplin Electronics have not had an easy time over the last couple of years, the Saltire company of which they are part lost £5.34 million (pre-tax loss) in 1997 and the interim report for the half-year to July '98 shows a further pre-tax loss of £2.01 million. Their shares were trading at just 4p each at the time of writing, up from a low of 3.5p.

Maplin now have a new MD and hopefully their fortunes will soon change. They are by far the largest supplier of electronic components to hobbyists, but in recent years have been stepping up their services to industry in competition to the likes of Famell (the largest distributor of electronic components) and RS. It is, however, clear from David's letter that the hobbyist still "pays our wages".

We expect that Maplin will continue to advertise in our pages from time to time, but their regular back page advert has come to an end.

AVAILABILITY

Copies of *EPE/ETI* are available on subscription anywhere in the world (see right), from all UK newsagents (distributed by Seymour) and from the following UK electronic component retailers: Maplin - all stores throughout the UK (and in S. Africa); Greenweld Electronics; Omni Electronics. *EPE* can also be purchased from retail magazine outlets around the world. An on-line version can be purchased from www.epemag.com



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £26.50. Overseas: £32.50 standard air service, £50 express airmail. Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subscriptions Dept., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Fax: 01202 841692. E-mail: subs@epemag.wimborne.co.uk. Subscriptions start with the next available issue. We accept MasterCard or Visa. (For past issues see the *Back Issues* page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 post and packing (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). *Normally sent within seven days but please allow 28 days for delivery - more for overseas orders.*

Payment in £ sterling only please. Visa and MasterCard accepted, minimum credit card order £5. Send, fax or phone your card number and card expiry date with your name, address etc. Or order on our secure server via our web site. Overseas customers - your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MIKE KENWARD

Secretary: PAM BROWN

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

On-Line Editor: ALAN WINSTANLEY

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Editorial: Wimborne (01202) 881749

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, Wimborne (01202) 882299

READERS' ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a **stamped self-addressed envelope or a self-addressed envelope and international reply coupons. Due to the cost we cannot reply to overseas queries by Fax.**

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*).

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

E-mail: adverts@epemag.wimborne.co.uk

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS/ETI take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; overseas readers should check local laws.

MIDI HANDBELLS

ROBERT PENFOLD

*Ring out thy bells with merry tolling
— plus a MIDI PIC-up, of course!*

THIS project was primarily designed with children in mind, and was actually produced in response to a request from a reader who required the gadget for a group of handicapped children. However, it is capable of providing hours of fun for "children" of all ages! It could be regarded as a modern equivalent to a set of handbells.

It is really a form of MIDI interface, and is incapable of making any sound without the aid of a MIDI equipped synthesiser, sound sampler, or other MIDI instrument. The output of the interface connects to the MIDI input of the instrument, which is set to produce a bell sound or any other sound you like. Up to 11 pushbutton switches can be connected to the inputs of the interface.

The general idea is for each player to control one or two pushbutton switches. By operating the switches in the correct sequence and with the correct timing the desired tune can be produced. In other words, the melody is played in much the same way that it would be produced by traditional handbell players.

This simple MIDI method has the advantage of not restricting the players to a single instrument sound, but it also has the drawback of not permitting any control over the dynamics of the instrument. Most MIDI instruments are capable of responding to velocity information, but it is not possible to derive this information from a simple on/off pushbutton switch. All notes, therefore, have the same mid-range velocity value of 64.

A unit of this type is potentially very complex, but the use of a PIC processor in this design minimises the amount of hardware required. In fact, only a handful of components plus the pushbutton switches are required. The circuit is powered from a 4.5V battery which has an extremely long operating life due to the low current consumption of the interface.

The unit should be usable with any MIDI equipped musical instrument, and it connects to the instrument via a standard MIDI cable. Any modern MIDI equipped instrument should be polyphonic, and so is this interface. It should

therefore be possible to play several notes at once if desired.

MIDI BASIC

MIDI is a form of serial interface which operates in conjunction with a standard set of message codes that control the actions of the slave devices. The basic action of this interface is to monitor the 11 pushbutton switches, and to generate the appropriate pulse train each time a switch is pressed or released.

In this case only two types of MIDI message are involved, and these are the note-on and note-off varieties. These both involve the transmission of three bytes of data, and both types of message follow the same general format.

The first byte is the status byte, and this breaks down into two four-bit nibbles. The four most significant bits indicate the type of message involved, and in this case binary values of 1000 (note-off) or 1001 (note-on) are used. Where appropriate, the four least significant bits carry the MIDI channel number. In this case both types of message are of the channel variety, and must include a channel number.

It will not normally matter which channel is used, and the slave device could actually be set to Omni mode so


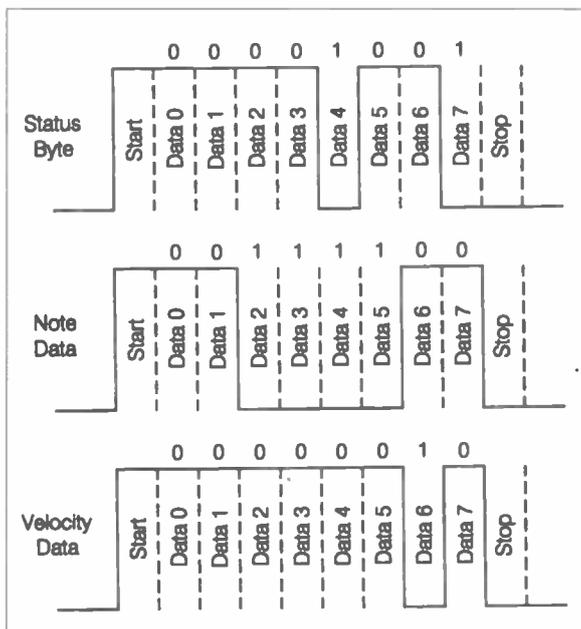


Fig. 1. Example waveforms for a "note-on" message.

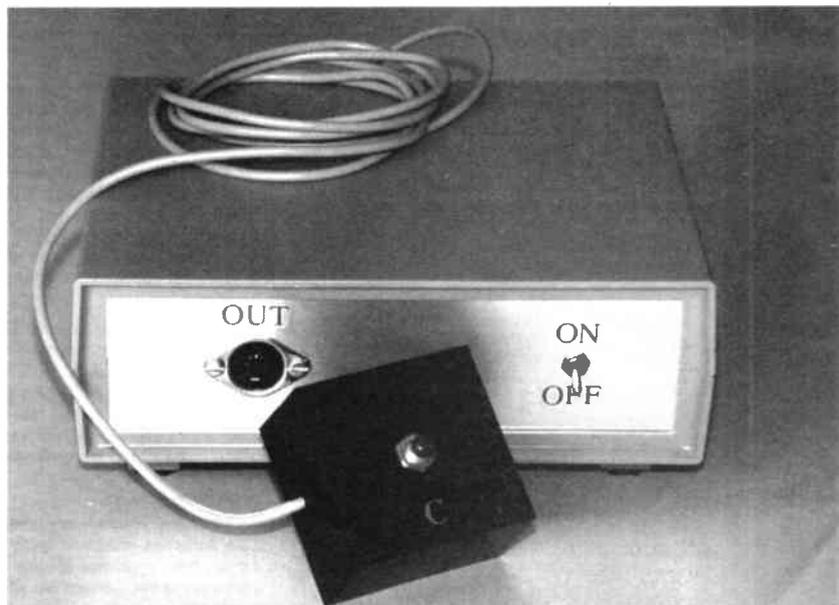

Completed unit with one "handbell" in the foreground. Eleven such "bells" are required.

that it responds to messages on any channel. The convention is for devices to default to channel one, which actually requires a binary value of 0000 in the status byte. This anomaly is due to the fact that MIDI channels are, as one would expect, in the range one to 16, whereas the values used in the status bytes are from 0 to 15.

NOTE VALUE

The status byte is followed by the note value, and like all MIDI data values this is in the range 0 to 127. Middle C is at a value of 60, and the system has a resolution of one semitone. The third byte carries the velocity value, which in a note-on message is a measure of how hard the key of a keyboard instrument has been played, how hard a drum pad has been struck, or whatever. In the current context there is no way of detecting how hard the pushbutton switch has been operated, and the convention is for a dummy value of 64 to be used in these circumstances.


Note-off messages also have a third byte containing velocity information, but this feature is not implemented in many MIDI devices. The third byte must always be included though, and the convention is to use a dummy value of zero where this feature is not implemented.

NOTE-ON

The illustration in Fig.1 shows the output waveforms needed to produce each byte in a message that will switch on middle C. MIDI is actually a current loop system that operates by switching a 5mA current on and off. This current is used to control the l.e.d. in an opto-isolator at the input of the receiving device. The opto-isolation helps to avoid problems with "hum" loops, and with digital noise leaking into the audio circuits.

Logic 0 and 1 are respectively represented by the current being switched on and off, which respectively require the output of the PIC processor to go high and low. For this reason the waveforms of Fig.1 do not have the expected polarity, and logic 1 is represented by a low voltage.

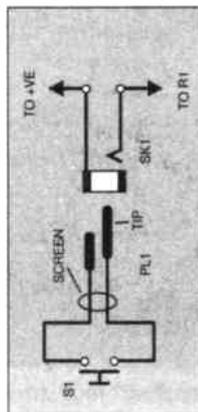Under standby conditions the output current is switched off, and the output of the PIC processor is low. At the beginning of a new byte of data the current is switched on for one bit in duration, and



Circuit alteration for including a jack socket to separate the handbell switches from the main circuit

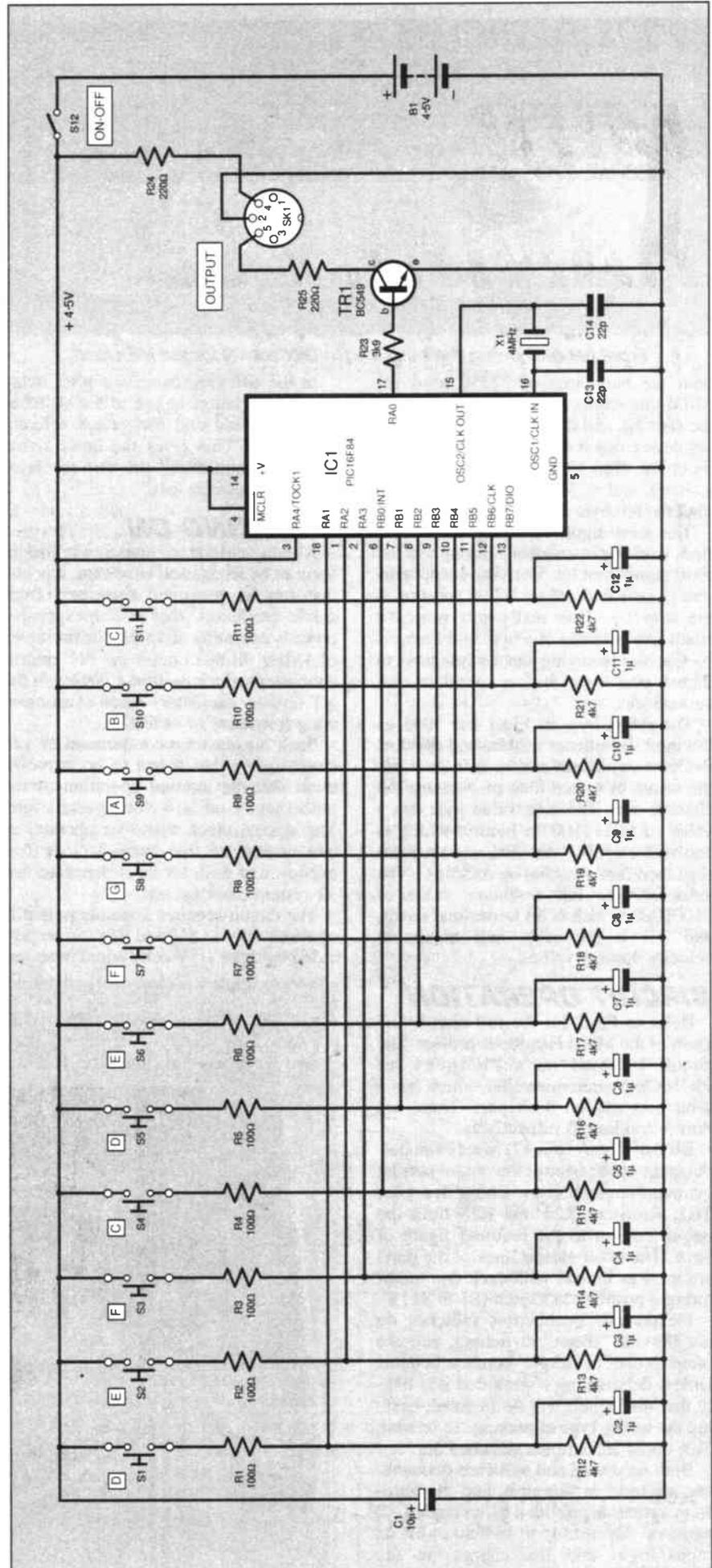


Fig.2. Complete circuit diagram for the Midi Handbells.



Front panel showing the output 5-pin DIN socket for the MIDI lead.

with the baud rate of 32150 used for MIDI this works out at 32 μ s. This bit is the start bit, and it indicates to the receiving device that it must test the state of the input line 48 μ s after the beginning of the start bit, and at 32 μ s intervals thereafter until the full byte of data has been read in.

The least significant data bit is sent first, working in sequence through to the most significant bit. Then the output current is switched off for 32 μ s, and this is the stop bit. This really just places a small gap between one byte and the next so that the receiving device has time to digest one byte before another one commences.

The status byte in Fig.1 has 1001 as the most significant nibble, and 0000 as the least significant nibble. It is therefore the status byte in a note-on message on channel one. The note value byte has a value of 00111100 in binary, which is equivalent to 60 in decimal, and the message therefore switches on middle C. The velocity byte has a binary value of 01000000, which is 64 in decimal terms, and this is the usual half maximum velocity dummy value.

CIRCUIT OPERATION

Refer to Fig.2 for the full circuit diagram of the MIDI Handbells project. The circuit is based on a PIC16F84 (or PIC16C84) microcontroller which has a 4-bit port and an 8-bit port. These are Port A and Port B respectively.

Bit 0 of Port A (pin 17) is set as an output and used to control the output current via common emitter switching transistor TR1. Resistors R24 and R25 limit the output current to the required figure of 5mA. The other eleven lines of the ports are used as inputs, with each one monitoring a pushbutton switch (S1 to S11).

Inexpensive pushbutton switches do not provide "clean" switching, and are often prone to severe contact bounce. Unless debouncing is provided it is likely that the switch will be misread, causing the wrong type of message to be sent. This could leave notes switched on.

Both hardware and software debouncing are used in this unit, and the hardware variety is provided by a simple C-R network. Operating a switch pulls its input high, and the charge on the debouncing capacitor prevents any rapid return to the low state.

In the software there is a brief delay between a change in one of the switches being detected and the switch actually being read. This gives the input signal time to stabilise at the correct level before the input is read.

CLOCKING ON

Although MIDI operates at what might seem to be an unusual baud rate, it is one that can be generated accurately from clock oscillators that use inexpensive crystals operating at 1MHz, or multiples of 1MHz. In this circuit the PIC microcontroller's clock oscillator is used in the XT (crystal oscillator) mode at an operating frequency of 4MHz.

Each bit must have a duration of 128 clock cycles, but it has to be borne in mind that the internal operation of the processor is on a 4-clock pulse cycle. The system clock therefore operates at one quarter of the external clock frequency, and each bit must therefore last 32 system clock cycles.

The circuit requires a supply potential of about 4.5V to 5V, and this can be provided by three 1.5V cells wired in series.

COMPONENTS

Resistors

R1 to R11	100 Ω (11 off)
R12 to R22	4k7 (11 off)
R23	3k9
R24, R25	220 Ω (2 off)

All 0.25W 5% carbon film.

See
**SHOP
TALK**
page

Capacitors

C1	10 μ radial elect., 25V
C2 to C12	1 μ radial elect., 63V (11 off)
C13, C14	22p ceramic plate (2 off)

Semiconductors

TR1	BC549 npn transistor
IC1	PIC16F84 or PIC16C84 microcontroller, preprogrammed (see text)

Miscellaneous


S1 to S11	Push-to-make switch (11 off)
S12	s.p.s.t. min. toggle switch
SK1	5-way (180 degree) DIN socket, chassis mounting
B1	AA size 1.5V cell (3 off), plus holder
X1	4MHz wire-ended crystal

Plastic case, medium size (see text); plastic case, small (see text) (11 off); 0.1in matrix stripboard, size 40 holes \times 27 strips; battery connector, PP3 type; screened connecting cables; connector block or 3.5mm jack plugs and sockets (see text); 18-pin d.i.l. socket; connecting wire; solder pins; solder, etc.

Approx. Cost
Guidance Only

£24

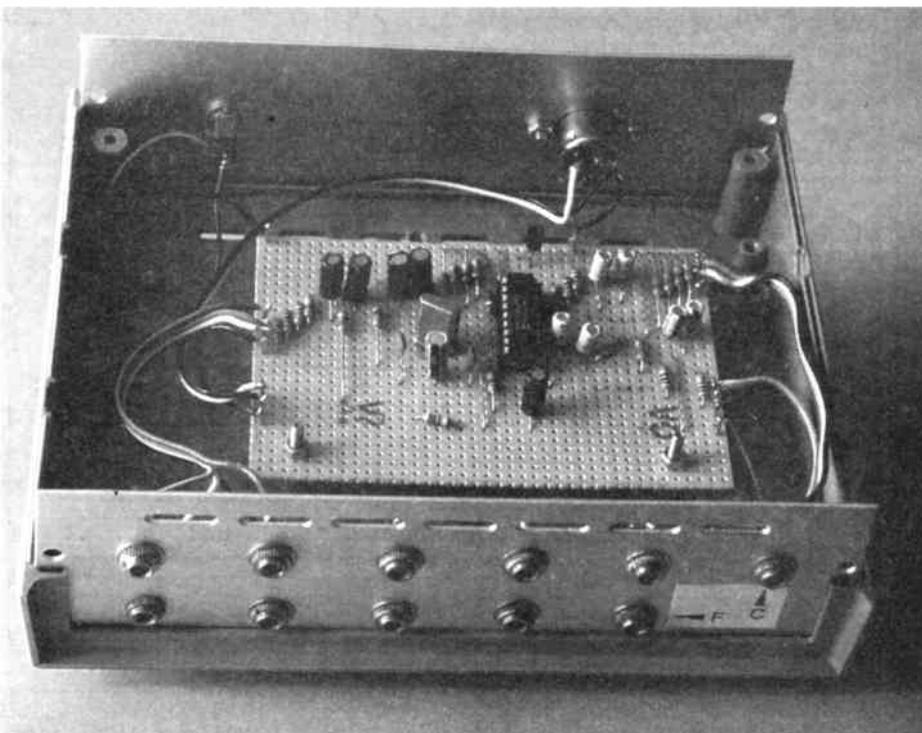The current consumption is only two or three milliamps under standby conditions, but it increases slightly when the unit is active. Each set of AA size cells should provide several hundred hours of



Interior layout of components and the "handbell" jack sockets mounted on the metal rear panel of the case.

use, and "bog-standard" batteries are perfectly adequate.

CONSTRUCTION

The circuit is assembled on a strip-board panel that measures 40 holes by 27 strips. The component layout, inter-

wiring and details of breaks required in the underside copper strips are provided in Fig.3. Construction of the board follows along the normal lines, with the board being trimmed to size, the two mounting holes being drilled, and the breaks being made in the copper strips.

Next the components are added, starting with the small components and link-wires, working through to the larger components such as crystal X1 and the PIC processor (IC1). There are only a few link-wires, but some of them are quite long and it might be worthwhile

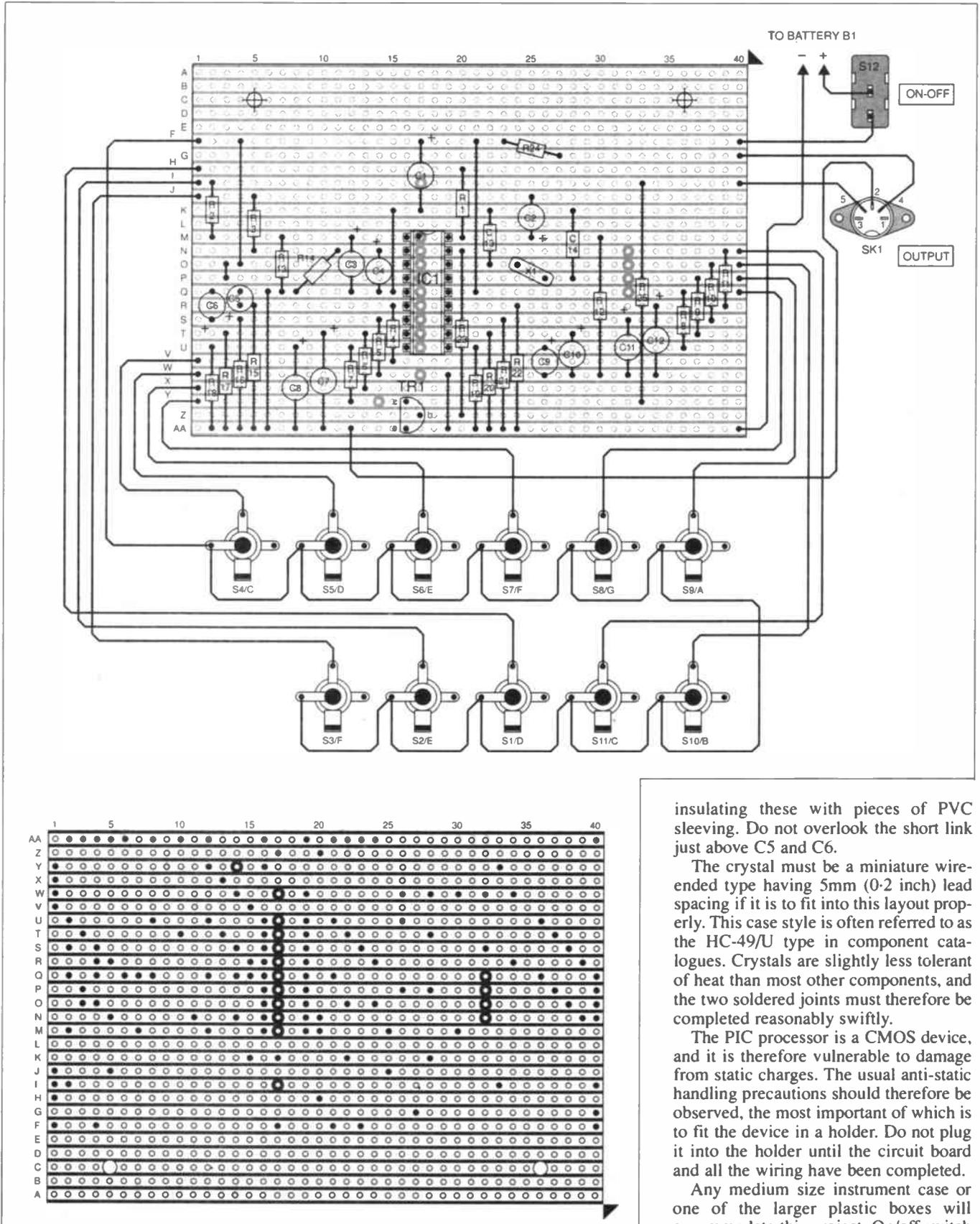


Fig.3. Stripboard component layout, wiring and details of breaks required in the underside copper strips.

(180 degree) DIN socket connected in the manner shown in wiring diagram Fig.3. The unit can then be connected to the MIDI input socket of the synthesiser via a standard MIDI lead.

SWITCHES

The main problem with a project of this type is getting the pushbutton switches connected to the circuit board. One solution is to drill eleven small holes in the rear panel for the leads to the switches, and to then connect the leads direct to the circuit board.

This is not a good way of handling things, since anyone tripping over the leads is likely to damage both the interface and themselves. There could also be major problems with the leads getting tangled.

It is much better to connect each switch to the main unit by way of a 3.5mm jack plug at the end of its lead, and matching socket on the rear panel. The only problem with this approach is that the cost of eleven 3.5mm jack plugs and sockets will significantly boost the cost of the system.

However, it is likely to be money well spent as it makes it much easier to sort out tangled leads, and to store the equipment neatly. Also, if anyone should trip over one of the leads the plug will simply pull free from its socket and no harm should be done.

INTERWIRING

The interwiring shown in Fig.3 assumes that the connections to the pushbutton switches are via 3.5mm open style jack sockets. These have a built-in switch that connects to a third tag, but this extra tag is left unused in this application. The lead connecting all the earth tags (which connect to the positive supply rail in this case) is not needed if the switches are mounted on a metal panel. This connection will then be provided via the panel.

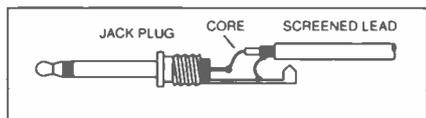


Fig.4. Connecting a screened lead to a 3.5mm jack plug.

If you require a cheap alternative to jack sockets, make the connections to the leads by way of a 22-way connector block. It is definitely not advisable to connect the leads direct to the stripboard.

For the system to be usable, the leads will need to be at least two metres long, and something closer to three metres is better. Around 30 metres of cable will therefore be required. Any thin twin cable should be suitable, but an inexpensive audio screened lead is probably the best choice. The screen connects to the positive supply rail, and the inner conductors connect to the inputs of the circuit board (see Fig.4).

In order to make things neater and easier to use, the pushbutton switches

should be mounted in small plastic boxes. The cheapest of plastic boxes are adequate, and "potting" boxes (which only have five sides) are a good choice. A type measuring about 48mm x 48mm x 29mm is about right.

TESTING

Output socket SK1 connects to the MIDI IN socket of the instrument using a standard MIDI lead. At least one lead of this type is normally supplied with a MIDI equipped instrument, and ready-made MIDI leads are readily available.

The interface transmits on MIDI channel one, and the instrument must therefore be set to receive on this channel, or set to Omni mode so that it responds to messages on all MIDI channels.

With everything connected up and switched on, pressing any of the push-buttons should result in the appropriate notes being played on the instrument. If there are any signs of a problem, switch off at once and recheck the circuit board and all the wiring, etc.

As pointed out previously, the interface is polyphonic, and the maximum number of notes that can be played simultaneously is eleven, or the number supported by the instrument if this is less than eleven. There should be no problem in playing an accompaniment on the keyboard while the instrument is being played via the MIDI interface, provided the instrument can handle all the notes.

SOFTWARE

For details on obtaining the software and pre-programmed PICs, see *Shop Talk* page.

The PIC's program requires the fuses to be set for crystal clock (XT) operation with the watchdog timer switched off and the power-up timer switched on. The initial part of the program sets RA0 as an output and leaves the other lines of both ports as inputs. Next, the values used in the transmitted bytes of data are stored in file registers. At this stage the file register used to store the note values is left empty, because this cannot be filled until a switch has been operated and the correct note value can be determined.

The program then goes into a loop that checks Port B and then Port A to see if a switch has been operated or released. The same method is used for both ports, which is to compare the previous value read from the port with the new value.

This is done by exclusive ORing (XORing) the two values, which will return a value of zero and set the zero flag if there has been no change. The returned value will be other than zero if a switch has been operated or released. Of equal importance, the bit of the returned value that is set to one indicates which switch has produced the change.

Once a change in the switch settings has been detected a short debouncing delay is provided by an "empty" loop. Then the program branches to a routine that checks each bit of the returned value.

one by one, until it finds the bit that has been set to logic 1. The program then branches to the appropriate subprogram where the correct note value is written to file register TRDATA2, which is the one used to store note values.

The relevant bit of the appropriate port is then checked to determine whether it is low or high and, depending on the result, the program branches to a subroutine that produces either a note-on message or a note-off message.

ROUTINE CALL

The two subroutines operate in the same basic manner, so we will only consider the note-on routine (NTON) here.

First RA0 is set high and a timing loop plus an NOP operation are used to keep it in that state for 32µs. This produces the start bit. The program then moves into a loop where it is looped eight times, as controlled by the value placed in variable CNTR2.

On each loop one of the data bits is generated. First the value for the status byte is complemented (inverted) and loaded into the W register. Remember that the serial data bits use high/on to represent logic 0, and low/off to represent logic 1, making this inversion of the data necessary. The value in the W register is written to Port A, but as only RA0 is set to the output mode, it is only bit 0 that has any affect.

After a simple delaying routine, the data byte is rotated one place to the right, making what was previously bit one the least significant bit. The program then loops back to the beginning of the routine, with the data being complemented and then written to Port A again. This process continues until all eight bits have been output on RA0 for 32µs, and all the data bits have been transmitted. Next RA0 is set low, and a delay of 32µs is provided. This generates the stop bit.

Basically, the same 8-loop routine is then performed again, but this time the note value in TRDATA2 is output on RA0 in serial form. Another loop routine then transmits the velocity data byte stored in TRDATA3. Finally, any stored values that have been altered are restored to their normal values, and the program returns to the main loop where it resumes checking for a change in the switch data.

The note values in the KEY subprograms can be altered to provide any desired notes. The sample values give a C major scale from middle C to the F an octave and a bit higher. A full set of semitones would be a useful alternative.


The PIC16x84 has EEPROM program memory that is easily reprogrammed, making it easy to alter the note data if you have access to a suitable programmer system.

Bear in mind that although MIDI can handle note values from 0 to 127, most instruments have a more restricted compass. The MIDI implementation chart supplied with MIDI instruments should give details of the note range covered. □

PROTEUS

including **NEW SIMULATOR**

PRO SPICE 3F5

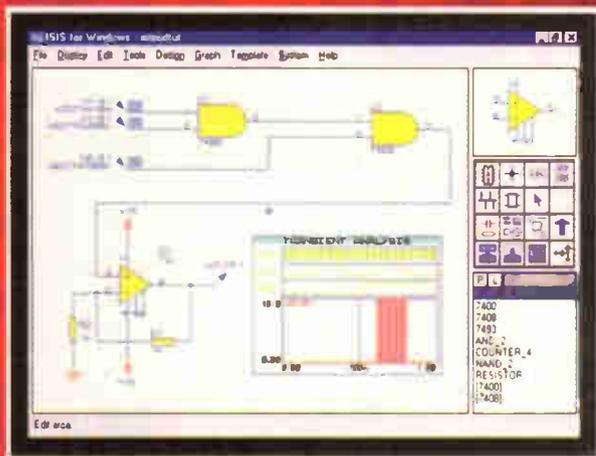


Simulation

- Berkeley SPICE3F5 analogue simulation kernel.
- True mixed mode simulation.
- New analysis types include multi-plot sweeps, transfer curves, distortion and impedance plots.
- Active Components: Switches, Pots etc.
- Over 1000 new library parts with SPICE models.
- Greater ease of use.

“a constant high level of capability throughout”

EWW CAD Review Round Up September 1998

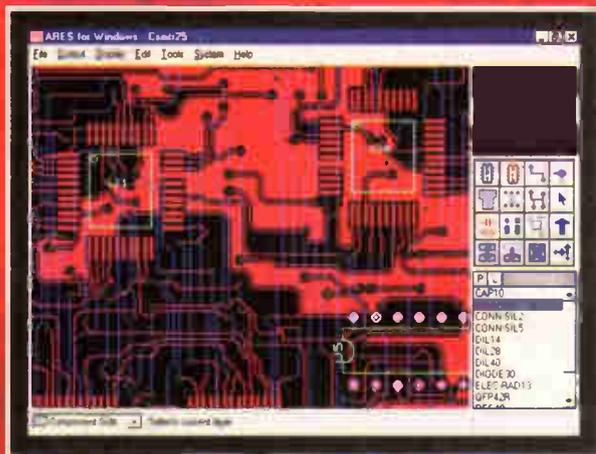

Schematic Capture

- Produces attractive schematics like in the magazines.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Full support for buses including bus pins.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.

PCB Design

- Automatic Component Placement.
- Rip-Up & Retry Autorouter with tidy pass.
- Pinswap/Gateswap Optimizer & Back-Annotation.
- 32 bit high resolution database.
- Full DRC and Connectivity Checking.
- Shape based gridless power planes.
- Gerber and DXF Import capability.

“the BEST all-round PROGRAM”

EWW CAD Review Round Up September 1998

Available in 5 levels - prices from £295 to £1625 + VAT.
Call now for further information & upgrade prices.


labcenter
Electronics

Write, phone or fax for your free demo disk, or ask about our full evaluation kit.
Tel: 01756 753440. Fax: 01756 752857. EMAIL: info@labcenter.co.uk
53-55 Main St, Grassington. BD23 5AA. WWW: http://www.labcenter.co.uk

Fully interactive demo versions available for download from our WWW site.
Call for educational, multi-user and dealer pricing - new dealers always wanted.
Prices exclude VAT and delivery. All manufacturer's trademarks acknowledged.

Electronics, Electrical & Mathematics Principles V6

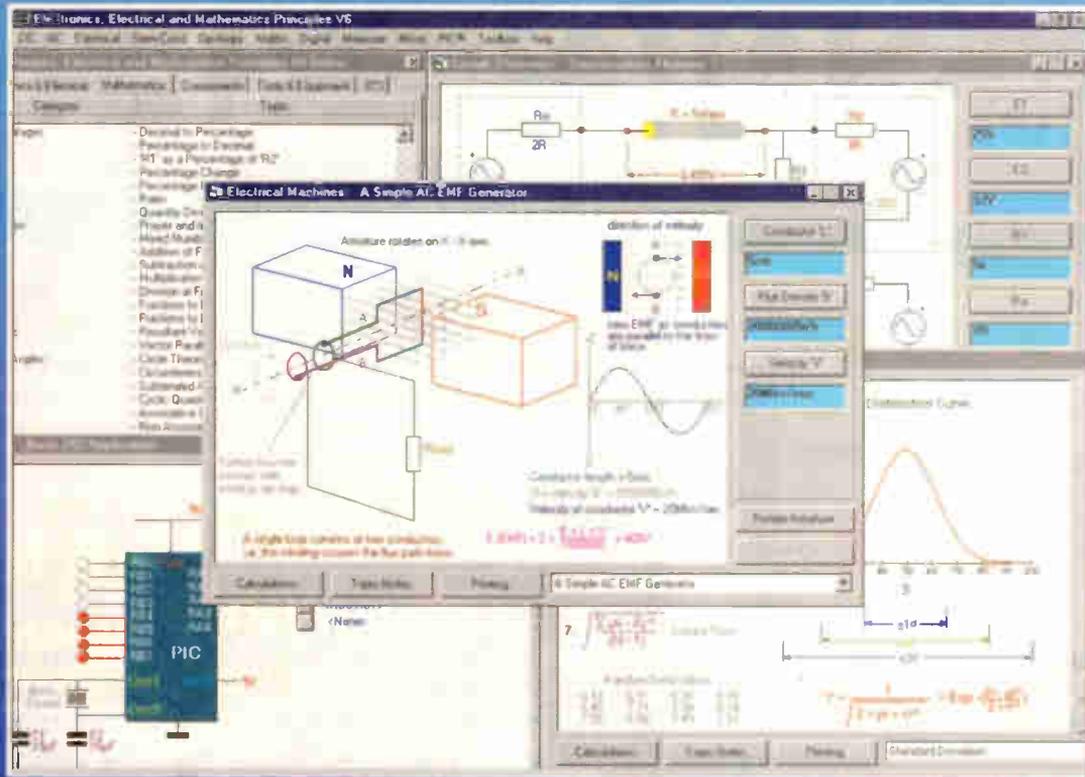If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics and maths then this is the software for you.



"Electronics Principles is a well thought out and comprehensive program that is also easy to install and stable in operation. It can be wholeheartedly recommended."

Robert Penfold. Everyday Practical Electronics magazine. October 1998.

And now upgraded to V6 a 32-bit package for Windows '95, '98 & NT. It's bigger, faster and better.

Additions include:- Circuit theorems, Norton, Thevenin's & Superposition...Magnetism & Electromagnetism...Motors, Generators & Transformers..Three phase systems....More on complex numbers.....A beginners introduction to PIC's..... Statistics...

PLUS: all the Electronics Toolbox routines, along with an Illustrated Components, Tools & Equipment Dictionary. A total of over 900 main menu selections.

Windows 3.1, 3.11 users please enquire.

By Clive W. Humphris.

Currently used in hundreds of UK and overseas schools and colleges to support GCSE, A Level, City and Guilds, BTEC, GNVQ's and University courses.

A COMPLETE PC BASED ELECTRONICS AND MATHEMATICS COURSE, where the colourful interactive graphics make it ideally suited for both personal study and a more enjoyable way of revising.

Multi-user site licence additional £500*

Complete Package still only £99.95*

EPT Educational Software. Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ.

Tel/Fax: 01376 514008. sales@eptsoft.demon.co.uk <http://www.eptsoft.demon.co.uk>

*UK and EC countries add £2 per order for post & packing. VAT should be added to the total.

Outside Europe £3.50 for air mail postage by return.

Switch, Delta, Visa and Mastercard orders accepted - please give card number and expiry date.

Cheques & Postal Orders should be made payable to EPT Educational software.

YOUR NUMBER'S UP - YET AGAIN!

Equal misery is the policy adopted for the forthcoming new telephone number system. Barry Fox reports.

As a result of piecemeal planning, Londoners must change their telephone numbers and stationery for the third time in ten years. Other areas will suffer too. A cross-party Trade and Industry Select Committee of MPs blames the UK's telecoms watchdog, Ofstel, for the inconvenience and cost to users. Ofstel admits it "did not do a cost/benefit analysis".

Ofstel has adopted the principle of equal misery. Dial codes will be radically changed in cities as they run out of numbers, with capacity for new subscribers created by forcing existing subscribers to use completely different 4-digit prefixes.

The proliferation of direct-dial extensions, mobiles, faxes and modems has created a world shortage of numbers, especially in the UK where codes are tied to geographical location and rural areas have spare capacity.

In May 1990 BT, which was then still in charge of numbering, split London's 01 code into 071 for the centre and 081 the outer zone. In April 1994 Ofstel took over and increased the number pool tenfold by adding an extra digit to every number in the country. So London changed to 0171 and 0181.

On 22 April 2000, Ofstel creates a completely new 02 range. This re-unites London as 020, with 0207 for the inner city and 0208 for outer zones. Cardiff gets 029, Southampton and Portsmouth share 023, Coventry becomes 024 and Northern Ireland changes to 028.

Ofstel decided against the US system of giving new subscribers new range numbers and leaving existing subscribers alone, because some local calls would then need full code dialling.

Says David Rogerson, Principal Consultant at Ovum, the telecoms analyst which in 1989 advised Ofstel to introduce 10-digit numbers, "Ofstel said that people did not like number changes, or dialling extra digits for local calls. This seemed a perverse conclusion because there are now to be widespread changes with more to come. People don't mind dialling a few extra digits as long as the call costs the same and the digits are familiar".

To smooth the change, the networks will start accepting new 02 numbers as well as old 01s, from 1 June 1999. But the National Code and Number Change steering group warns that this will create problems if payphones, call loggers and routers throughout the UK are not modified before June so that they recognise both old and new codes. So far only one in ten firms has taken any action.


Ofstel's Director General David Edmunds argues "There has been full consultation with consumers, business users and telecom companies. If the code changes do not take place London will run out of capacity by summer 2000. Customers need more information."

Ofstel is leaving this job to the telecoms operators and their Big Number campaign. A spokeswoman for Big Number admits that there has been no publicity for the June change since last October but the campaign will "soon" run reminder adverts.

Other countries have adopted different approaches. As cities in the US, like New York and Los Angeles, run out of numbers, new subscribers get numbers with whatever new 3-digit prefix is spare. But existing subscribers keep their old numbers.

When French cities started to run out, France Telecom split the country into four zones and added an extra 2, 3, 4 or 5 to the numbers in those zones. It was all done at one fell swoop at 2300 hours on 18 October 1996. Calls dialled to the old numbers simply failed to get through.

BRUSH-UP YOUR TESTING!

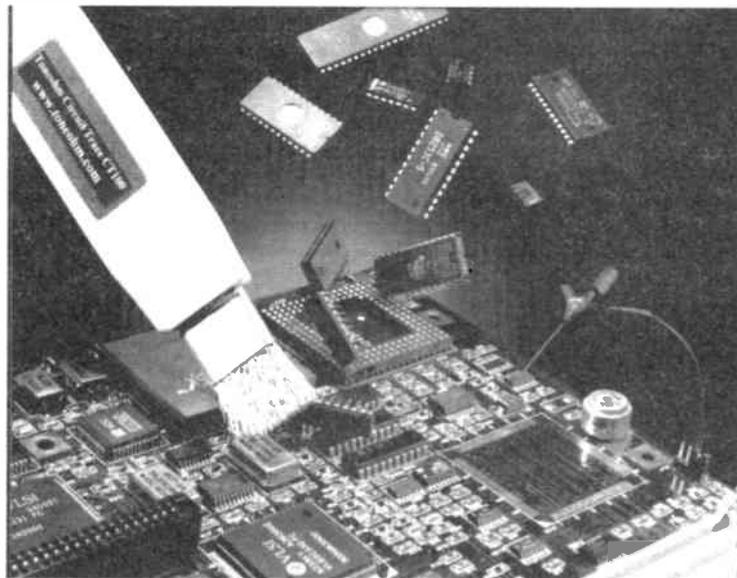

NOW here's a seemingly innovative idea – a p.c.b. test tool that uses a brush-technique to trace connections.

Circuit Trace are the manufacturers, who tell us that they are a start-up company that intends to sell direct via the Web. Their new CT100 is a small handheld connectivity tester that enables users to accurately locate all interconnected points on a p.c.b. within seconds, simply by wiping a conductive brush over the surface of the board and listening for an audible tone.

It seems obvious that this extremely simple approach can be used to significantly reduce fault finding time on any type of p.c.b., regardless of component technology or board complexity. The CT100 has a maximum output of 150mV, making it suitable for testing p.c.b.s containing all types of components, including CMOS devices. A sliding collet enables the stiffness of the conductive brush to be adjusted to suit the type of board being tested. It can also be set to a very loose condition that is ideal for sweeping edge connectors.

The tool is supplied complete with test probes, circuit marker, carrying case and comprehensive user manual. It costs £93.50, including P&P, anywhere in the world. It is available via <http://www.toneohm.com>, or contact Circuit Trace, Dept EPE, PO Box 70, Retford DN22 0SY. Tel/fax: 01777 248993. E-mail: mrbass@globalnet.co.uk.

DIGITAL RADIO TUNER



ARCAM, the renowned British manufacturer of audio equipment, has announced the introduction of the world's first digital radio hi-fi tuner – the Alpha 10 DRT. It went on sale throughout the UK on 15 March.

Over 60 per cent of the UK is covered by BBC Digital Radio broadcasting and rapid expansion of the network is planned, with Commercial Radio going live in October '99. Digital Radio will eventually replace all current analogue broadcasting.

The Alpha 10 DRT is, say Arcam, the first home DRT to be developed and the first to go on retail sale. It is a standalone unit incorporating radical new technology, and is easily added to any hi-fi system, much as one would add a new CD player. It matches other units in Arcam's range.

The price is around £800 (but the music is free, say Arcam!), and the tuner is on sale nationally through around 100 Arcam hi-fi dealers within range of a BBC Digital transmitter.

For more information, contact your local Arcam dealer, or A&R Cambridge Ltd., Dept EPE, Pembroke Avenue, Denny Industrial Centre, Waterbeach, Cambs CB5 9PB. Tel: 01223 203200. Fax: 01223 863384. E-mail: custserv@arcam.co.uk. Web: www.arcam.co.uk. (For more info on Digital Radio, go to www.arcam.co.uk/news/digiguide.html.)

MARS EXPRESS

MATRA Marconi Space has been recommended as the Prime Contractor for the Mars Express spacecraft. Its development should now proceed swiftly to meet the deadline of an exceptionally favourable launch window in early June 2003, going into Mars orbit by Christmas of the same year.

Mars Express is the first flexible mission of the revised ESA long-term scientific programme, Horizons 2000. It is designed to be a pivotal element of an international multi-mission for the exploration of Mars. Seven scientific instruments on board will perform a variety of tasks, one of which is to search for sub-surface water. The craft will also provide relay communication services between Earth and the landers and rovers to be deployed on Mars between 2003 and 2007.

On board Mars Express will be the *Beagle 2* lander, a project led by the UK's Open University and the University of Leicester, which will perform exobiology and geochemistry research on the planet's surface, looking for evidence of life.

More information is on web site <http://www.matra-marconi-space.com>.

Another press release informs us that Emkay's microphone technology will be used to detect sound on Mars. Emkay's electret EK-3132 Mars Microphone is onboard NASA's Mars Surveyor mission, launched on 3 Jan '99, with its Mars Polar Lander reaching the Martian surface at the end of this year.

Any sounds which are captured will be sent back to Earth and made freely available on web site <http://sprg.ssl.berkeley.edu/marsmic>. Mark Johnson, Emkay's sales and marketing manager, explains: "Our microphone will pick up not only sounds from the Lander itself, e.g. motors, robotic arm and other mechanical parts, but also sand blown against the Lander and the surrounding terrain, other wind sounds, and possible sounds from electrical discharges in the dust clouds. We may even pick up some unexpected sounds as well!"

Emkay's web site is at <http://www.emkayproducts.com>.

A Really Smart Card!

By Barry Fox

TRAVELLERS can now carry a PC database in an electronic credit card. Rex Pro is a PCMCIA memory card that slots into a laptop, or connects to a desktop PC through a docking station. The card sucks address lists, diary entries and to-do notes direct from the PC and stores them in 512K of on-board RAM.

Readout is by a built-in l.c.d., with six buttons to control scrolling and searching. Two button-cells run it for six months; if one cell at a time is changed no data is lost. Size is reduced by forming the chips on the l.c.d. glass. Rex Pro was developed by Franklin Electronic Publishers, Starfish Software and Citizen Watch, made in China and costs £140.

Antex solders us on web!

WE take it as a compliment that Antex have included the *EPE Basic Soldering Guide* as an active hyperlink within their own Web site. Alan Winstanley's authoring of this guide is increasingly becoming a "standard source" on the subject, referred to and accessed by many in industry and education.

Antex' new web site has much to offer in its own right as well and really should be browsed by anyone who is involved in soldering (and hands up any of you who are not – just as we thought, nil!).

As a leading producer of soldering equipment and accessories for schools and colleges, hobby electronics and product servicing worldwide, they have justifiably included on their site many subjects other than catalogues of equipment.

In addition to our link, the site includes features on a wide range of soldering topics, from selecting products and accessories to techniques, problem solving and safety. There is also a comprehensive list, with Internet links, to the network of distributors worldwide handling Antex products.

The site has been designed for use by visitors of all ages and soldering experience. Enticingly, Antex is offering all visitors the chance to win free, top of the range soldering products. Visit the site! It's at <http://www.antex.co.uk>.

Once in, the route to the *EPE Soldering Guide* is via Technical – Papers – Introduction to Soldering, at the end of which is the hyperlink to us. (You can, of course, also access our *Guide* through the normal *EPE* site <http://www.epemag.wimborne.co.uk>.)

New Technology Update

A new bonding technique promises to break the barriers that have held up the progress of IGBTs reports Ian Poole

INSULATED Gate Bipolar Transistors (IGBTs) are widely used for switching applications in many areas of the electronics industry. One of the main areas where development is focussed for these devices is on improving their speed.

In the past few years a number of improvements have been made in their performance using a variety of new techniques. Now manufacturers are looking to address new market areas where these devices may be used.

In particular, they anticipate that they will achieve large degrees of acceptance in a broad range of power supply applications including uninterruptable power supplies where power MOSFETs and bipolar devices are chiefly used today.

What Are IGBTs?

The structure of an IGBT is shown in Fig.1. It can be viewed as an SCR (silicon controlled rectifier) with a MOSFET connecting the cathode to the base region. For traditional IGBTs there are two main styles of structure, one vertical and one lateral. In the lateral structure, the anode is situated at the surface, and the *p*-type material in between achieves isolation from the substrate.

The electrodes for these devices are often given different names. Cathode, anode and gate are used by some manufacturers because of the similarity to an

SCR, whilst emitter, collector and base are used by others because of the similarities with bipolar transistors. Even the terms drain, source and gate are sometimes seen.

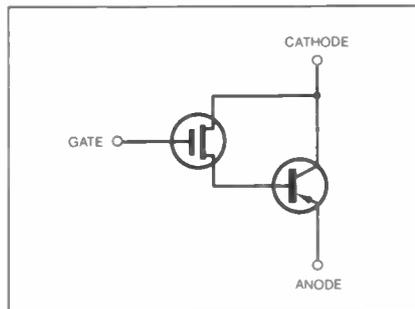


Fig.2. Equivalent circuit of an IGBT.

The operation of the IGBT is fairly complicated, although much of its operation can be understood from a view of its equivalent circuit shown in Fig.2. Here it can be seen to be a *pnp* bipolar transistor driven by a MOSFET, in a Darlington type configuration. In this way it is able to switch large voltages and currents by the action of a small input signal.

In operation excess holes are injected from the anode, they are not totally absorbed by the middle *p*-type region and they contribute to a *pnp* bipolar transistor current. In this way the MOSFET current becomes the base current for the bipolar transistor.

The devices are made from silicon because of the high breakdown voltage and good thermal conductivity of the material. Both of these attributes are required in view of the high current and high voltage applications for which these devices are used.

IGBTs have advantages over both bipolar transistors and power MOSFETs. The IGBT has a much better current density for a given voltage drop. Power MOSFETs come in second, and bipolar transistors are a poor third. The device also has a very high input impedance and low input

capacitance as might be expected from the fact that it has an insulated gate input.

However, the main disadvantage of the existing types of IGBT is that they have a relatively low switching speed. To illustrate this, they may typically have a fall time of around 200ns whereas a power MOSFET may be only 50ns.

Recent Improvements

In recent years, a number of improvements have been made to these devices. In one case a company is developing a device that can switch voltages at rates of 50kHz, but the maximum voltage is limited to 600V. The company hopes that their technology will be able to achieve switching rates of at least 100kHz with some further development.

Another company has released devices where it has been possible to achieve speeds of 150kHz, with currents between 5A and 50A, but again the voltage is limited to a maximum of 600V.

Direct Bonding

To break the barriers that have been hit by other manufacturers, researchers at Samsung have used a new process called silicon direct bonding (SDB). The process starts with *p*- and *n*- wafers. The *p* wafer is implanted with *p* ions to create a *p+* wafer, and the *n* wafer is implanted with *n* ions to create an *n+* layer in the wafer, see Fig.3.

Implantation at this stage is very precise, and this is one of the keys to the success of this method of fabrication. Next, the two wafers are bonded to form a single wafer and an *n* buffer layer is optimised for minority carrier injection into the IGBT's drift region.

This factor means that the switching speed is greatly improved and switching

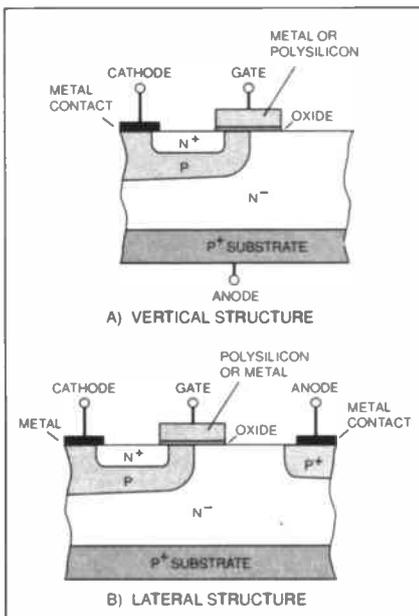


Fig.1. Structure for an Insulated Gate Bipolar Transistor (IGBT).

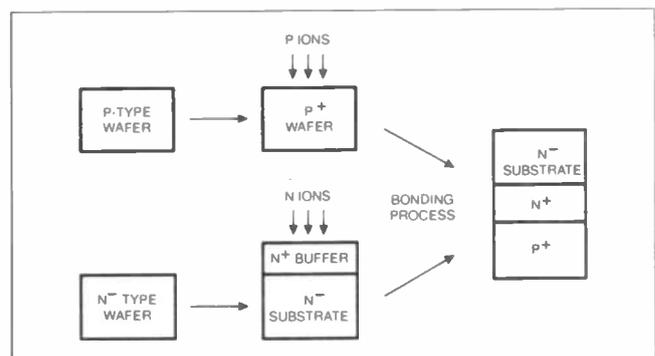


Fig.3. Block diagram of the silicon direct bonding process.

losses are reduced. In addition to this the wafer has a very low defect rate and a very uniform doping level, making it ideal for these devices.

Apart from improving the switching characteristics of the device, the short circuit capability has been improved. This has been achieved by including an emitter ballast resistor in the device.

Although these devices cannot withstand indefinite short circuits, their resilience to transient overloads of this nature has been greatly improved.

Performance

Samsung is offering five devices in the family with current ratings from 5A to 25A in steps of 5A. The devices are fast, offering switching speeds up to 150kHz, all with a saturation voltage of only

2-4V. The reduction in forward voltage drop has resulted in a number of advantages. First, the efficiency of the device is high, and this will enable the systems using these devices to improve their levels of efficiency as well.

A second advantage is that the heat generated in the device is reduced as a result not only of the lower forward voltage drop, but also the increase in switching speed. This has meant that heat-sinking requirements are much less.

In fact, the 1200V 10A version is mounted in a TO3P package and requires no special heat sinking. This fact alone will enable the cost of any units using these devices to be reduced as a result of the simpler, and less costly mounting arrangements.

The switching speed has shown a

significant improvement over previous devices. For the 10A version the typical turn on and turn off times for a resistive load are 15ns and 80ns, and even with an inductive load the turn off time is only 100ns.

Long Term

Plans for the future include a wider variety of devices using the new SDB process. These will include some to operate at lower voltages, although it is hoped to introduce some devices that are able to operate with even higher voltages of 1500V and more.

Other plans include offering the devices in high current modules configured as half and full bridge modules for motor drives and other power applications.

SHOP TALK

with David Barrington

MIDI Handbells

Thanks to the use of a microcontroller chip, the component count for the *MIDI Handbells* project is fairly small, when you take away the pushswitches and jack sockets/plugs, so we do not expect any real "clangers" when shopping for components. Made up MIDI leads are sold by many of our advertisers.

As usual you will, of course, have to purchase a larger piece of stripboard than you really need and cut it down to size. Also, the open style, chassis mounting, 3-5mm switched jack socket is now regarded as a "commonplace" component and most of our component advertisers, such as **ESR**, **Greenweld**, **Sherwood** and many others should carry stocks or be able to offer an alternative. With eleven required, try for a discount, especially if you include the miniature pushswitches in your order.

The 4MHz clock crystal for this project should be a miniature wire-ended metal can type having 5mm lead spacing. The package style of this crystal is usually referred to as having an HC-49U can case in catalogues and should be widely available.

The choice and size of metal-fronted case is left to the constructor's personal preference, but make sure there is plenty of room for the circuit board and battery holder within it. The small resin potting boxes for the "handbells" are listed in numerous advertisers' catalogues and should be available from local sources.

This just leaves us with the PIC chip. For those unable to program their own PIC16F84, a ready-programmed PIC microcontroller is available from **Magenta Electronics** (☎ 01283 565435 or <http://magenta2000.co.uk>) for the all inclusive price of £5.90 (overseas readers add £1 for postage) – a strong case here for building the *PIC Toolkit Mk2*!

For those who are able to "blow" their own PICs, the software is obtainable from the Editorial Offices on a 3-5in. PC-compatible disk, see *EPE PCB Service* page 389. There is a nominal admin charge of £2.75 each (UK), the actual software is Free. For overseas readers the charge is £3.35 surface mail and £4.35 airmail. If you are an Internet user, it can be downloaded Free from our FTP site: <ftp://ftp.epemag.wimborne.co.uk/pub/PICS/handbells>.

PIC Toolkit Mk2

The only component listed in the *PIC Toolkit Mk2* project that is most likely to cause sourcing problems is the regulated +12V charge-pump d.c. to d.c. converter i.c. Currently, the only listing we have found for the Maxim MAX662A is from **Electromail** (☎ 01536 204555), code 299-575. It is the CPA (MAX662CPA) version and to obtain a data sheet at the same time also quote code 138-802.

All good PIC micro suppliers should be stocking up on the PIC16F87x devices, including **Farnell**, **RS (Electromail)** and **Magenta**, so supplies should be plentiful. Web users may be interested in checking out Microchip's site for further data (including world-wide agents) on: <http://www.microchip.com>.

The Toolkit Mk2 software is available from the Editorial Offices on a 3-5in. PC-compatible disk, see *EPE PCB Service* page 389. There is a small admin charge of £2.75 (overseas readers £3.35 surface mail and £4.35 airmail). Internet users can download it Free from our FTP site: <ftp://ftp.epemag.wimborne.co.uk/pub/PICS/PICtoolkit2>.

The printed circuit board is available from the *EPE PCB Service*, code 227 (see page 389).

A.M./F.M. Radio Remote Control

A number of parts for the *A.M./F.M. Radio Remote Control* project may pose the question "where do I find that?" This applies particularly to the radio modules, the 12-bit HT6014 encoder and HT6034 decoder i.c.s.

Well, starting with the radio modules, we understand that **Maplin** (VY47B-pair) are presently out of stock of the "low cost" pair and cannot give a delivery date for new supplies. Also, we have been informed that the HHR1-418 a.m. receiver module is now discontinued and unobtainable.

The good news is that **RF Solutions** are able to supply readers with the HRR3 replacement a.m. receiver module. They will also supply all the modules, including the f.m. versions, outlined in the article. They can be contacted on ☎ 01273 488880 or web site: www.rfsolution.co.uk (there is a handling charge).

The only listing for the HT6014 encoder (JA35Q) and HT6034 decoder (JA37S) is Maplin. They also supplied the transmitter case, with pushbuttons (CW26D).

If you elect to use relay outputs, the ones in the model are 12V 10A s.p.c.o. types stocked by **Electromail** (☎ 01536 204555), code 350-529. The two printed circuit boards are obtainable from the *EPE PCB Service*, codes 228 (Trans) and 229 (Rec).

PLEASE TAKE NOTE

PC Capacitance Meter


(Oct '98)

Page 756. Robert Penfold, the designer, has pointed out that there seem to be slight differences to the Listing program published and one on his current machine. The correct version is as follows:

10 REM capacitance meter program	300 X=X * R
20 PORT1=&H278	310 LOCATE 5,30
30 PORT2=&H279	320 PRINT "
40 PORT3=&H27A	330 LOCATE 10,30
50 CLS	340 PRINT X B\$"
60 LOCATE 7,30	350 GOTO 100
70 PRINT "RANGE 3"	360 LOCATE 5,30
80 B\$="n"	370 PRINT "OVERLOAD"
90 R=1	380 RETURN
100 OUT PORT3,35	390 R=10
110 OUT PORT3,33	400 B\$="p"
120 OUT PORT3,35	410 LOCATE 7,30
130 OUT PORT3,34	420 PRINT "RANGE 1"
140 OUT PORT3,35	430 RETURN
150 A\$=INKEY\$	440 R=.1
160 IF A\$="1" THEN GOSUB 390	450 B\$="n"
170 IF A\$="2" THEN GOSUB 440	460 LOCATE 7,30
180 IF A\$="3" THEN GOSUB 490	470 PRINT "RANGE 2"
190 IF A\$="4" THEN GOSUB 540	480 RETURN
200 IF A\$="s" THEN END	490 R=1
210 FOR D=1 TO 4000	500 B\$="n"
220 OVER=INP(PORT2) AND 128	510 LOCATE 7,30
230 IF OVER=128 THEN GOSUB 360	520 PRINT "RANGE 3"
240 NEXT D	530 RETURN
250 X=INP(PORT1)	540 R=.01
260 Y=INP(PORT2) AND 16	550 B\$="u"
270 IF Y=16 THEN X=X+256	560 LOCATE 7,30
280 Z=INP(PORT2) AND 32	570 PRINT "RANGE 4"
290 IF Z=32 THEN X=X+512	580 RETURN

CIRCUIT SURGERY

ALAN WINSTANLEY
and IAN BELL

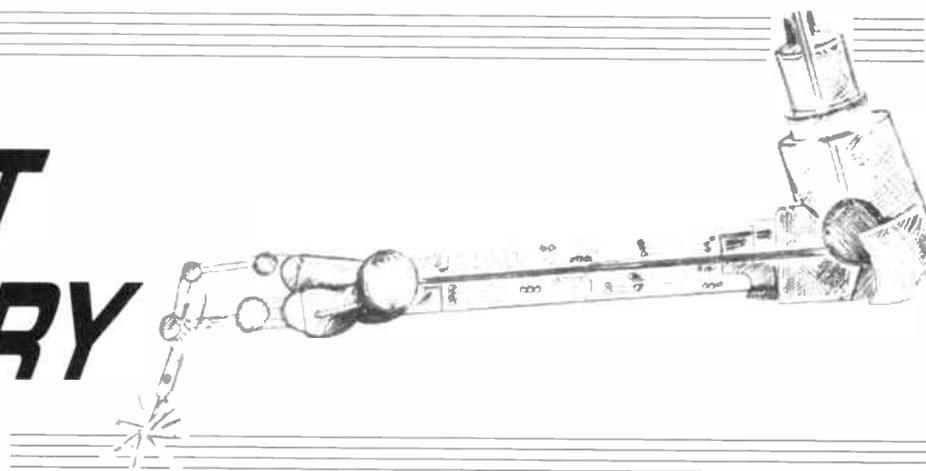

More readers' queries receive attention in our monthly round-up of solutions offered by our team of surgeons.

REGULAR readers of *Circuit Surgery* will remember previous contributions to this column (e.g. the thorny subject of detecting the number of bats entering a roost!) written by Ian Bell of the School of Engineering at the University of Hull. Ian was one of the co-authors of our tutorial series *Teach-In '98 - An Introduction to Digital Electronics*.

From this month, Ian joins me as co-writer of *Circuit Surgery*. We believe that our individual knowledge and experience of electronics complement one another well and this will allow us to provide a good coverage of topics in this extremely popular column.

Current Sources

Let's dip into the mailbag. From *Harsh Mehta* in India comes this query by E-mail: "What are current sources and why are they useful in circuits?"

Current sources are very important in electronic circuit design. Hobbyists probably do not meet them very often, but they are to be found lurking inside almost every analogue i.e., such as operational amplifiers or other linear circuits.

In order to understand the basic concept of a current source, it will help if we first describe *voltage sources*, so we can see

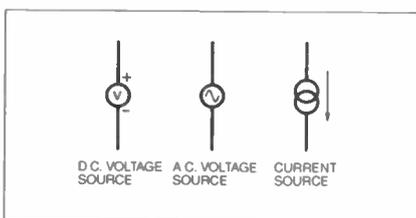


Fig. 1. Voltage and current source symbols.

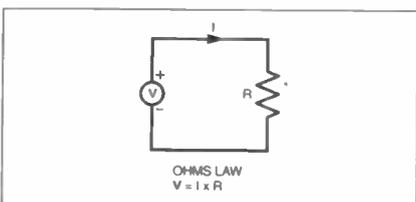


Fig. 2. Ohms Law applied to a fixed resistor R .

some fundamentals in a more familiar context. Fig. 1 shows the symbols for voltage and current sources. Most people are familiar with voltage sources (batteries, bench power supplies and the mains are good examples), but unfortunately there is no similar everyday current source.

A voltage source produces a constant voltage at its output irrespective of the current you draw from it. Well that's not quite true in practice of course - a battery's voltage will *drop* if you connect a heavy load (low resistance), a bench power supply may cut out or limit the current, and a mains supply should blow a fuse before too much damage is done.

An *ideal voltage source* can output any current without the voltage changing or cutting out. Such things do not exist in the real world; however, they can be useful in simplified calculations and simulations. In fact, when analysing circuits we often assume that the power supply is an "ideal" voltage source for simplicity.

Ohms Law

To pursue this further we need to use *Ohms Law* - the basic relationship between current, voltage and resistance. This is $V = I \times R$.

To find the voltage (V in Volts) across a resistor, multiply the current through it (I in Amps) by the resistance (R in Ohms). If we connect a voltage source across a resistor, as shown in Fig. 2, it must produce a current given by $I = V/R$. If we connect a very low value resistor across the voltage source, then it must produce a very high current in order to satisfy Ohms Law.

For example, a 9V battery with a 0.5 ohm resistor across it (*do NOT attempt this in practice*) would ideally produce 18A but a small battery such as a 9V PP3 type is just not up to the task! So what happens if the voltage source is not capable of producing the required current? Is Ohms Law broken?

The answer, of course, is no; what happens is that the voltage source pushes out as much current as it can and its output voltage reduces to the point given by Ohms Law for the resistance and current involved. The PP3 battery is no longer a 9V voltage source with a 0.5 ohm load.

Resistance to Change

We can understand what is going on by using the concept of *internal resistance*. Real voltage sources can be thought of comprising an ideal voltage source (with voltage V_S) and a resistor (R_{INT}), as shown in Fig. 3a.

So when we connect a resistor to a voltage source the current (I) flows through *both* resistors with a voltage dropped across each one. The voltage at the terminals of the real source (V_{OUT}) therefore becomes smaller when R is reduced and so a greater proportion of V_S is dropped across R_{INT} . Note that the internal resistance limits the maximum available output current to V_S/R_{INT} , at which point V_{OUT} is zero. In practice we cannot physically separate the voltage source and internal resistance.

A battery's internal resistance is noticeable as a drop in its voltage when we decrease load resistance, and because its internal resistance increases when it becomes exhausted, this becomes worse with older batteries. The effective internal resistance of bench power supplies (and regulator chips) can be made very small using control circuits. These monitor V_{OUT} and effectively change V_S so that V_{OUT} remains constant, compensating for the drop across R_{INT} .

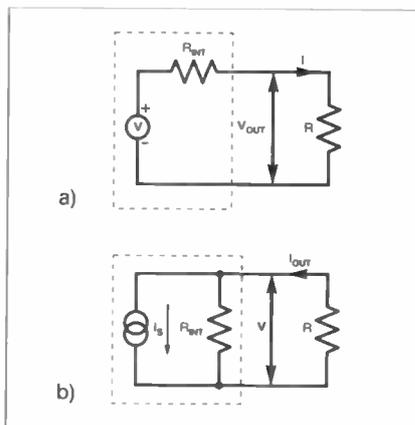


Fig. 3a. Internal resistance R_{INT} of a real voltage source and (b) a real current source.

This cannot go on forever of course, since at some point we reach the maximum current or voltage rating of one or more of the power supply's internal components. So bench power supplies can sometimes deliver the same voltage (with little "drooping") up to a maximum current at which point they cut out. Due to the active control circuitry, the maximum output current may be much less than that implied by the internal resistance (V_S/R_{INT}).

By now you may have guessed that an ideal current source outputs a particular current irrespective of the voltage, and that real current sources are limited in some way. Real current sources also have internal resistance (see Fig.3b), but it appears in parallel with the source and is usually large, unlike voltage sources which have the (usually small) internal resistance in series.

The internal resistance of a current source limits its output voltage to $I_S R_{INT}$, at which point I_{OUT} is zero. Real current sources may also have a limited range of voltages over which they can operate (sometimes called compliance), determined by factors other than the internal resistance (like the current range of a bench power supply).

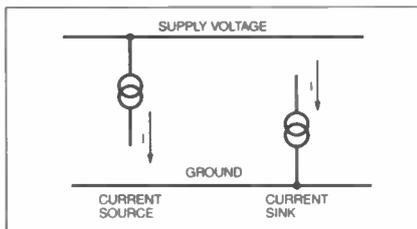


Fig.4. Current sources and current sinks.

If we short-circuit a current source then, unlike a voltage source, it has no problem – its output current simply flows through the wire. If we connect a large resistance across a current source, then by Ohms Law it must develop a large voltage across the resistor. For example, if we connect a 1M (megohm) resistor across a 1mA current

source it would have to produce 1000V across the resistor to maintain the required current. If a current source is open circuit then it cannot operate (unless it can produce arcing!). Note the opposites here: voltage sources have an easy life with open circuits and a hard time with short circuits, but for current sources it is the other way round.

Current sources connected to ground (0V), through which current flows to ground, are sometimes called *current sinks* (see Fig.4). However, the term *current source* is used in both cases.

On Stream

Water is sometimes used as an analogy for electricity, and can help us see the difference between a voltage source and a current source. In the water analogy a *voltage source* is a large tank of water suspended above the ground, in which the water is kept at a constant level by some means. The higher the tank then the greater the voltage.

A pipe at the base of the tank allows water (current) to flow – any level of current can flow, depending on the diameter of the pipe. A short circuit would be like the bottom falling off the tank causing a massive flow!

A *current source* is like a pump producing the same rate of flow (current), irrespective of its height above ground (voltage). If we block the pump's output then we get the equivalent of a current source with an electrical open circuit: the pressure builds until something gives up.

The concepts of voltage and current sources are very important in electronics. All real sources of power or signals can be thought of as either voltage sources or current sources with an internal resistance.

We can use this idea further to understand the requirements for circuit designs. For

CIRCUIT THERAPY

Circuit Surgery is your column. If you have any queries or comments, please write to: Alan Winstanley, *Circuit Surgery*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset, BH21 1PF, United Kingdom. E-mail alan@epemag.demon.co.uk. Please indicate if your query is not for publication. A personal reply cannot be guaranteed but we will try to publish representative answers in this column.

example, if we have a sensor producing an output voltage, but with a large internal resistance, we will need a very high input impedance amplifier to process these signals, to prevent all the source voltage from being dropped across the internal resistance. This can be achieved using a unity gain buffer amplifier or a more sophisticated instrumentation amplifier circuit.

Current sources are important in biasing and obtaining high gains in the analogue circuits used on integrated circuits. They provide very high impedances, which are useful for developing large voltage gains. However, they still allow relatively large bias currents to flow without incurring a large voltage drop.

Next month Ian continues his investigation into current sources with some practical suggestions.

SQUIRES

MODEL AND CRAFT TOOLS

A comprehensive range of Miniature Hand and Power Tools and now an extensive range of Electronic Components featured in a fully illustrated

336-page Mail Order Catalogue

1999 Issue

**SAME DAY DESPATCH
FREE POST & PACKING**

Catalogue free of charge to addresses in United Kingdom. For overseas send 6 International Reply Coupons to:

Squires, 100 London Road,
Bognor Regis, West Sussex
PO21 1DD

Tel: 01243 842424

Fax: 01243 842525

SHOP NOW OPEN



EPE Online
www.epemag.com

Buy your magazine online. **EPE**, the first magazine in the world to be available to buy from the web. \$3.95 per issue, \$23.95 for a year's subscription.

**TAKE A LOOK,
A FREE ISSUE IS AVAILABLE**

PC ENGINES - FROM 4004 TO PENTIUM III

ERNEST FLINT

Tracking the Intel microprocessor to its lair!

I'll see your PII and raise you two Celerons!

IN THE not-so-distant past, very few people had the faintest clue as to which type of microprocessor was ensconced in their personal computer (PC). Instead, in the early days, consumers purchased computers by type, such as an IBM PC-AT or PC-XT. Even for those who did know, the playing field was fairly easy to understand as things tended to progress in a fairly leisurely and obvious manner. Each new generation was faster and better than the one before and, more importantly, each new generation quickly replaced the previous one "on the store shelves".

By comparison, it's now hard to turn on the television without being accosted with yet another "Intel Inside" advert. In fact, those little rascallions at Intel are rolling out new types of microprocessors so fast it makes one's head spin. Even worse, there are now multiple concurrent architectures targeted at different markets.

It was bad enough when all we had to contend with was the choice between a Pentium and a Pentium with MMX. Suddenly, as if from nowhere, we were being barraged with the additional options of Celerons, Pentium IIs, and Pentium II Xeons. And now we are staring Pentium IIIs and Pentium III Xeons in the face, desperately trying not to be the first to blink.

In fact there are now so many flavors of microprocessor on the loose (each of which is available in a range of clock frequencies), that even those of us who are "in the trade" are beginning to lose whatever tenuous grip we once had on reality. So in this article we will rend the veils asunder and expose the horrors within.

THE EARLY DAYS

Before we plunge too deep into the quagmire of today's micro-

processor product offerings, it is advantageous to consider the path by which we arrived at where we are (Fig.1).

The world's first microprocessor - the 4004 - was presented to the market by Intel in 1971 (in fact the 4004 was originally called a microcomputer, and the term microprocessor was not coined until sometime later). The 4004 contained only 2,300 transistors and performed 60,000 operations per second.

The "4"s in the 4004's name were intended to reflect the fact that it had a 4-bit data bus. The 4004 was followed in 1972 by the 8008, which was pretty much the same sort of thing, but with an 8-bit data bus (and 3,300 transistors). The 4004 was also enhanced to form the 4040, which contained additional logical and compare instructions and a small internal stack.

The 4004, 4040, and 8008 were all interesting, but they were also all designed with specific applications in mind, and it wasn't until 1974 that the 4040 and 8008 evolved into the 8080, which contained 4,500 transistors and could perform 200,000 operations per second. The 8080 was the first truly general-purpose microprocessor, and was destined to become the central processor of many early home computers.

By 1978, the 8080 had evolved into the more sophisticated 8-bit 8088 and the 16-bit 8086. The 8088 was to become pivotal in the history of microprocessors as we know it, because IBM decided to use this as the CPU in what is now considered to be the first true PC, which was presented to the market in 1981.

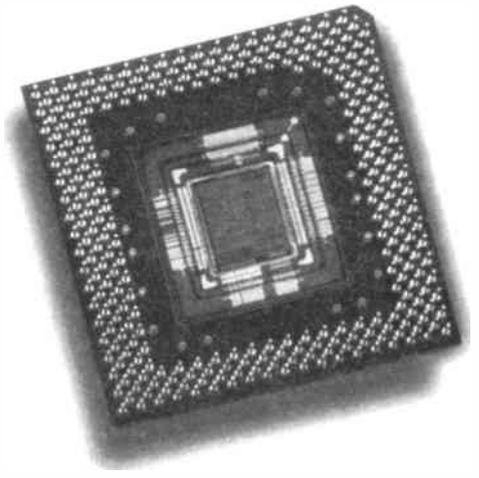


Fig.2. The Pentium processor in a Socket 7 configuration (Photo courtesy of Intel Corp.)

THE MIDDLE KINGDOM

In 1982, Intel released the 16-bit 286 microprocessor (also known as the 80286). With 134,000 transistors, the 286 sported approximately three times the performance of other 16-bit processors of the time. Amongst other things, the 286 provided "backwards compatibility", which meant it could run programs that had been written for its predecessors. This was considered to be a pretty revolutionary concept at the time.

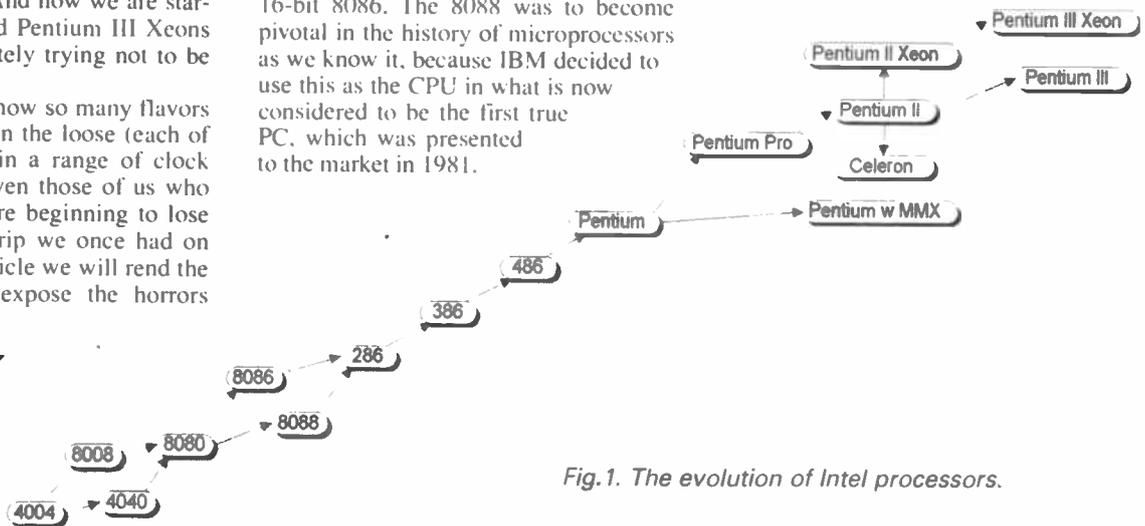


Fig.1. The evolution of Intel processors.

The 16-bit 286 was followed by the 32-bit 386 in 1985. This device, which contained 275,000 transistors, was designed to support "multitasking" (running multiple programs at the same time). In turn, the 386 was followed in 1989 by the 486, which contained an amazing (for the time) 1.2 million transistors.

In the early days, complex math functions (multiplication and division) were performed as a series of simple steps, such as "shift-and-add" algorithms. Later schemes employed external math coprocessor devices, which were special units dedicated to performing complex math functions as quickly as possible. The 486's 1.2 million transistors allowed it to include an on-chip math coprocessor as part of the main CPU (this was considered to be mega-cool by those of us who cared).

The first 486s had system clocks (see sidebar) running at 25MHz. These were soon followed by 33MHz and 66MHz versions (and various "clock doublers" appeared later in the market).

THE GOLDEN AGE

The start of the current golden age of microprocessors (insofar as this article is concerned) occurred in 1993, when Intel first introduced the Pentium processor (Fig.2). With 3.1 million transistors, the Pentium was approximately five times faster than its 486 ancestor. The Pentium sported a 16 kilobyte L1 cache (see sidebar) and up to 512KB L2 cache (this L2 cache was mounted on the main motherboard).

The first Pentiums started with clock speeds of 75MHz, and over time additional options were added to 233MHz (note that the host bus speed remained at 66MHz – see sidebar). Also, the Pentium was presented in a pin grid array (PGA) package, which plugged into an Intel-defined pinout format called "Socket 7."

The next major development occurred in 1995 with the Pentium Pro, which sported a number of innovations and improvements (and a whopping 5.5 million transistors).

Quite apart from anything else, the Pentium Pro was presented as a multichip

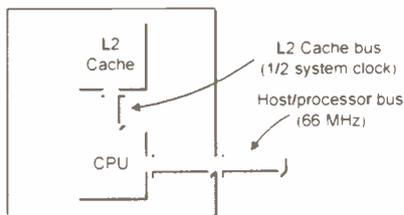


Fig.3. The Pentium Pro architecture (two chips in a multichip module).

module package containing two silicon chips: the Pentium Pro processor itself (with a 16-kilobyte on-chip L1 cache) and an L2 cache chip. The original Pentium Pros came equipped with 256KB L2 caches, and 512KB versions became available later. One really cunning innovation associated with the Pentium Pro was that it had two busses (an external processor-to-main-memory (host) bus and an internal processor-to-L2-cache bus) and the processor could access both busses simultaneously (Fig.3).

The original Pentium Pros supported a 150MHz system clock, and this was quickly followed by 200MHz versions. The multichip module of the Pentium Pro allowed the processor core and the L2 cache to be located very close to each other, which in turn facilitated the cache bus running at half the main system clock frequency. (This was much faster than the Pentium's L2 cache, which was located on the motherboard, and which was therefore obliged to run at the 66MHz host bus frequency.)

The end result of this dual-bus architecture (plus other cunning stuff that's too complex to go into here) made the Pentium Pro go "like a bat out of hell." The Pentium Pro module plugged into an Intel-defined pinout format called "Socket 8".

The pace really started to pick up in 1997, when Intel introduced two new developments. The first was the concept of MMX instructions (see sidebar), which first appeared in the "Pentium with MMX." The second was the Pentium II processor (with a mind-boggling 7.5 million transistors), which also included MMX instructions (Fig 4).

At a first glance, the Pentium II appeared

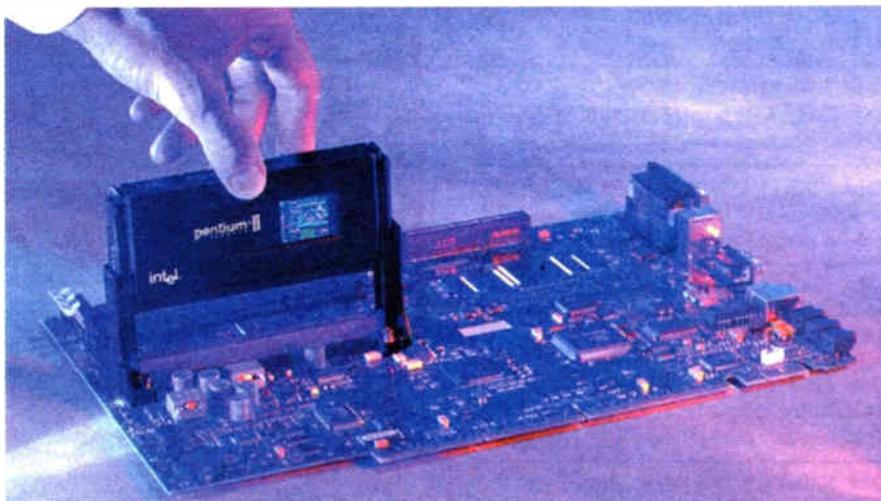


Fig.4. The Pentium II shown in slot 1 configuration (Photo courtesy of Intel Corp.).

TECHNICAL TERMS - A BRIEF OVERVIEW

During the course of this article, one or two terms are mentioned such as "cache", "host bus," MMX, and so forth. For those amongst us who aren't too familiar with these (and certain other) terms, a brief overview is presented here.

SRAM vs DRAM

Semiconductor memory comes in a variety of flavors. The two main categories are read-only memory (ROM) and random-access memory (RAM). (The purists amongst us would prefer to replace the term RAM with read-write memory (RWM), but realistically this is never going to happen).

ROM devices contain instructions and/or data that is "hard-wired" into them during their construction. By comparison, RAM devices only contain whatever data and instructions the computer last wrote into them (and they "forget" their contents when power is removed from the system).

Furthermore, RAM is itself split into two core technologies, which are known as Static RAM (SRAM) and Dynamic RAM (DRAM). Each memory cell in an SRAM device requires between four and six transistors, while each cell in a DRAM device requires only one transistor (so you can get more memory in a DRAM device).

SRAMs are faster than DRAMs, but they use more power, run a lot hotter, and are much more expensive. Thus, the bulk of a computer's main memory is formed from DRAM devices, and SRAMs are only used where extreme speed is required.

SIMMs vs DIMMS

Multiple memory devices are typically mounted on small p.c.b.s (known affectionately as "sticks" of memory). These are referred to as SIMMs (single inline memory modules) if they only have chips on one side, or DIMMS (dual inline memory modules) if they have chips on both sides.

FDO vs EDO vs SDRAM vs . . .

As was previously noted, the bulk of a computer's RAM is composed of DRAM devices, but these can be presented in different ways. When you purchased a computer in the not-so-distant past, it came with FDO (fast data out) memory. This was subsequently replaced in later systems by EDO (extended data out) memory, which was in turn superseded by SDRAM (synchronous DRAM) memory.

This is a bit confusing at first, but underneath it's really quite simple. These memory schemes are all basically formed around a core of standard DRAM chips, but each uses a different way of controlling and accessing the devices to squeeze more "throughput" out of them.

Also, note that the term ECC (error correcting and control) memory used in higher-end machines refers to the fact that these memory devices contain additional bits that can be used to detect (and correct) errors in the data.

continued . . .

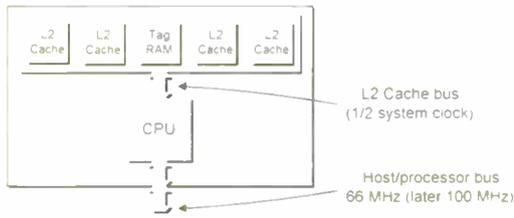


Fig.5. The Pentium II architecture.

to be radically different to the Pentium Pro, because it was presented in a relatively large package called a single-edge-connect (SEC) cartridge, which plugged into a new Intel-proprietary socket configuration called Slot 1 on the motherboard.

Internally, the Pentium II is constructed as a hybrid using a printed circuit board substrate. This circuit board contains the processor chip, which is essentially a Pentium Pro with a 32KB L1 cache and MMX instruction support. This board also contains four industry-standard burst-static cache RAM devices and a tag RAM chip, which together form the 512KB L2 cache (Fig.5).

(Note that Fig.5 is only an illustration. In reality the processor core and two of the cache RAM devices are mounted on one side of the board, while the remaining cache RAMs and the Tag RAM are mounted on the other side.)

The first Pentium IIs supported clock

frequencies of 233MHz and 266MHz. These were quickly followed by 300MHz, 333MHz, and 350MHz versions, which were in turn superseded by 400MHz and 450MHz versions. This obviously has a huge impact on processor operations, and also cache-intensive operations (because the Pentium II cache is running at half of the main clock frequency). Furthermore, the first Pentium IIs supported a host/processor bus frequency of 66MHz, but this was boosted up to 100MHz in later versions, which dramatically improved access to the main memory.

Last but not least, the Pentium II supported Intel's AGP (advanced graphics port). Actually, to be more precise, it's the Pentium II's supporting chipset that provides AGP capability, but supporting chipsets are part of a completely different discussion, so we'll ignore them in this article (for which you can be truly thankful). The AGP is also outside the scope of this discussion, except to say that it is designed to streamline the transfer of data from the CPU to AGP-compatible graphics accelerator cards.

AND THEN . . .


For a long time things had appeared (at least on the surface) to be relatively well ordered. The 268 was followed by the

386, which was in turn followed by the 468. The 486 begot the Pentium, which led to the Pentium Pro, which in turn paved the way for the Pentium II. And then things began to get more complicated . . .


In 1998, Intel introduced the Celeron processor, which was based on the Pentium II. The first Celerons didn't have any L2 cache at all, which caused

Table 1: Intel microprocessor development


1971	4004	2,300 transistors, 4-bit, 60,000 operations per second
1972	8008	3,300 transistors, 8-bit
1972	4040	4-bit (like a 4004 but with additional instructions)
1974	8080	4,500 transistors, 8-bit, 200,000 operations per second
1978	8088/8086	8-bit/16-bit (the 8088 was used in the first IBM PC)
1982	286	134,000 transistors, 16-bit
1985	386	275,000 transistors, 32-bit (multitasking)
1989	486	1.2 million transistors, 32-bit (first math coprocessor) 25MHz system clock (-> 66MHz over time)
1993	Pentium	3.1 million transistors, 32-bit, 16KB L1, 512KB L2 (external) 75MHz system clock (-> 233MHz), 66MHz host bus, Socket 7
1995	Pentium Pro	5.5 million transistors, 32-bit, 16KB L1, 256KB L2 (internal) 150MHz system clock (-> 200MHz), 66MHz host bus L2 Cache bus runs at 1/2 main system clock, Socket 8
1997	Pentium II	7.5 million transistors, 32-bit, 32KB L1, 512KB L2, MMX 233MHz system clock (-> 500MHz), 66MHz host bus (-> 100MHz) L2 Cache bus runs at 1/2 main system clock
1998	Celeron	7.5 million transistors, 32-bit, 32KB L1, 0KB L2 (later 128KB L2), MMX 266MHz system clock (-> 400MHz), 66MHz host bus L2 Cache (when provided) bus runs at 1/2 main system clock
1998	Pentium II Xeon	7.5 million transistors, 32-bit, 32KB L1, 512KB / 1MB / 2MB L2, MMX 400MHz system clock (-> 500MHz), 100MHz host bus L2 Cache bus runs at FULL main system clock
1999	Pentium III	7.5 million transistors, 32-bit, 32KB L1, 512KB L2, MMX II 500MHz system clock (-> 550MHz), 100MHz host bus L2 Cache bus runs at 1/2 main system clock
1999	Pentium III Xeon	7.5 million transistors, 32-bit, 32KB L1, 512KB / 1MB / 2MB L2 MMX II 500MHz system clock (-> 550MHz), 100MHz host bus L2 Cache bus runs at FULL main system clock

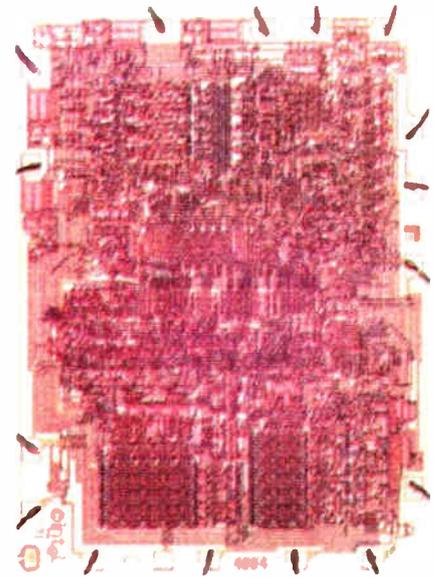

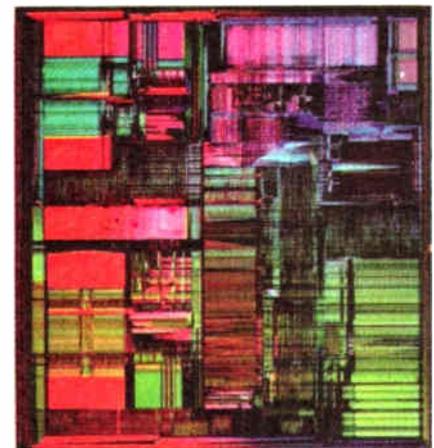Bare (unpackaged) silicon (die) for the 4004 processor.



The Pentium die.

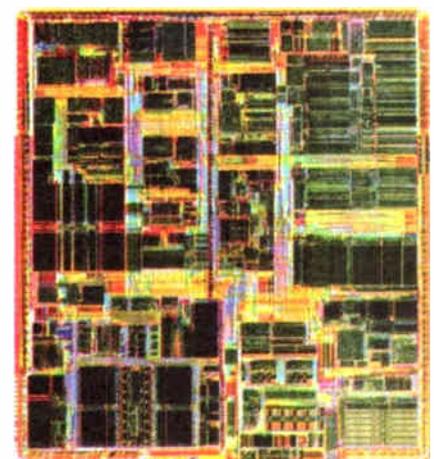

The Pentium II die.

(The photos above are courtesy of Intel Corporation).

some observers to refer to them as "brain dead Pentium IIs." Subsequent implementations had 128KB L2 caches, and versions with larger cache configurations wouldn't be too surprising.

Later on in 1998, just to make life interesting, Intel introduced the Pentium II Xeon. This little rascal arrived in a yet bigger package, which plugged into a new Intel-proprietary socket configuration called Slot 2 on the motherboard.

The Pentium II Xeon contains two devices: the main processor and a honking big new L2 cache device. One key point about the Xeon (apart from its high price) is that its L2 cache, which is available in 512KB, 1MB, and 2MB options, runs at the same frequency as the main processor clock. (Remember that the cache bus on the standard Pentium II runs at half the main clock frequency.) This high-speed cache can have a significant effect for certain high-end applications such as database hosting and other server-bested applications.

And last but not least (as we pen these words), Intel have just announced the Pentium III and the Pentium III Xeon processors. These are essentially the same as their Pentium II forebears, but with higher clock frequencies (commencing at 500MHz and 550MHz as they launched), including a special CPU ID, and supporting MMX II instructions (see sidebar).

Each Pentium III has a unique ID number hardwired into it, which is intended to allow querying software to positively identify the CPU (note that the CPU does not "broadcast" the ID, but instead programs have to actively read it). Intel's main (stated) goal was to provide increased security for electronic transactions (E-commerce) over the Internet. There are a number of other possible uses for such an ID, ranging from identifying stolen processors, to locking (licencing) applications to a specific machine.

An unexpected result (for Intel) is that a variety of civil liberties groups are currently "up in arms" campaigning about possible invasion of privacy issues. In response, Intel is providing a utility that will allow users to enable and disable the CPU ID at will, and the majority of machines will be shipped with the ID disabled by default (which sort of makes you wonder if it was worth it in the first place).

WHICH SIZE FITS YOU?

So which processor is right for you? This is a tricky one, because it can be difficult to separate the "hype" from the reality. Let's start with the Celeron, which is essentially a Pentium II with a smaller L2 cache (*whatever you do, don't buy one of the earlier Celerons without any L2 cache at all*).

Intel's marketing position is that the Celeron is intended for home use (games, entertainment, simple word processor-type applications) by the more cost-conscious buyer. In reality, Intel would probably have preferred not to have introduced the Celeron at all – they main-

L1 vs L2 CACHE

Modern semiconductor memories are extremely fast, but computer programs typically perform a humongous amount of memory accesses (reads and writes), so anything that can be done to speed things up is generally considered to be very desirable.

If we analyse programs, we tend to find that they are often composed of blocks of instructions, where each block may be performed multiple times before moving on to the next block. A key point is that these blocks of instructions tend to be relatively small compared to the size of the total program.

Computer designers can take advantage of this knowledge by creating a special "chunk" of high-speed memory called the cache. When the CPU starts running a program and it reads an instruction (or data) for the first time, in addition to processing that instruction it also stores it in the cache. The next time the CPU attempts to read that instruction, it first checks to see if it's already in the cache – if so it can read it from the cache much faster than it could from the main memory.

The cache is formed from the fastest SRAM devices available, so the designer (who would ideally prefer as large a cache as possible) has to keep it smaller than he or she would like to balance cost and performance.

In fact computer designers use a hierarchy of memory. The L1 ("Level 1") cache is very small, but very, very fast, because it is constructed as an integral part of the CPU itself (on the same silicon chip). The L2 ("Level 2") cache is significantly bigger than the L1 cache, but it's father away from the CPU and thus not as fast. In fact some computers have L1, L2, and L3 caches between the CPU and the main memory!

SYSTEM CLOCK vs HOST BUS

The main system clock is used to synchronize the internal actions of the CPU and also the rest of the system. The CPU communicates with the rest of the system by means of the main system bus, which may also be referred to as the "host bus", the "processor bus", or the "front bus."

Increasing the frequency of the system clock increases the rate by which the CPU performs its internal actions. However, the frequency of the host bus is not directly related to the frequency of the main system clock.

OVERCLOCKING

In order to understand the concept of overclocking, we first need to know that computer motherboards are designed to support a range of system clock frequencies. This allows a Pentium II motherboard, for example, to support say 350MHz, 400MHz, and 450MHz versions of the processor. Theoretically, this allows end-users to upgrade their main processor (although this rarely happens in practice).

Most Intel processors are reasonably robust. One by-product of this is that it is possible to take a processor rated for one clock frequency, say 350MHz, and "tweak the jumpers" or otherwise modify the motherboard to

clock the processor at a higher frequency.

There are a number of sites on the web with instructions on how to tweak different motherboards to overclock different processors. One downside of this is that the processor will run hotter than it's rated for (and than the computer's cooling system is expecting), which may cause problems. Another thing to bear in mind is that if you do this you've just waved goodbye to any warranty that came with your system (assuming they find out what you did).

MMX vs MMX II

In 1997, Intel introduced the Pentium II and a new version of the Pentium, both of which boasted something called MMX. After wading through the "razzmatazz", we find that MMX Stands for "MultiMedia eXtensions", which are actually a group of 57 special SIMD (single instruction multiple data) instructions.

To understand what this means, we first need to understand that many applications like to use data in small "chunks." For example, multimedia and image processing programs largely view the world as a series of picture elements (pixels), where each pixel consists of red, green, blue, and alpha (transparency) values (abbreviated to RGBA). Furthermore, many applications use 8-bits to represent each of these values, which makes it easy to pack all four values into a single 32-bit word (the size currently used by the Pentium, Pentium Pro, Pentium II, and so forth).

The interesting point is that these applications often want to perform operations on pairs of 32-bit RGBA values, such as adding two of them together. However, the application doesn't simply want to add these two values as 32-bit quantities. Instead, it wishes to add the two 8-bit R values together, and likewise for the two 8-bit G values (and the B values and the A values).

The old way of doing this required multiple operations to separate out each of the 8-bit values, perform the requisite function, and then "munge" the results back together. Hence the introduction of MMX instructions, which direct the CPU to treat the data as four 8-bit chunks (but to still perform all four additions in a single clock beat!).

Of course these instructions are only of value if you have applications that make use of them. But once they became available, application developers began to take advantage of them, and MMX versions of certain programs do go substantially faster than their non-MMX counterparts.

The original MMX instructions only worked on integer data representations. However, the new Pentium III and Pentium III Xeon processors have been enhanced to support MMX II. Also known as SSE (for "Streaming SIMD Extensions"), MMX II comprises around 70 additional instructions that allow operations to be performed on four floating point numbers simultaneously. Future applications that take advantage of these instructions (such as analytical programs, graphics applications, and 3D games) will see a major speed increase.

ly did so in response to other processors from manufacturers like AMD, which were starting to "eat Intel's lunch" at the home consumer end of the market.

Pentium IIs (and now Pentium IIIs) are primarily targeted towards the high-end consumer and professional desktop (although television adverts often position them for home entertainment machines also). By comparison, Pentium II Xeons (and now Pentium III Xeons) are typically presented as being the processors of choice for high-end technical and professional applications.

In reality, Xeons typically only deliver approximately five percent performance boost for many applications at a very significant cost premium over their non-Xeon counterparts. Where the Xeons really score (especially with the larger cache versions) is in server-type applications.

BOILING IT DOWN

Thus, for the majority of home users, the choice really boils down to one between a Celeron, a Pentium II, and a Pentium III. Let's see if we can reduce this choice a little further. In reality, the vast majority of home users won't be able to spot any difference in performance between a Celeron (with 128KB L2 cache) and a Pentium II (with 512KB L2 cache) running at the same frequency. However, the Celeron will be several hundred pounds cheaper, and you can invest some of this money on additional RAM, which can provide a *HUGE* speed increase for memory-intensive applications. In fact some savvy users purchase a Celeron-based machine and then overclock it (see sidebar), which provides the increased performance associated with higher clock frequencies.

Of course for those users who want (may NEED) to live on the cutting edge of technology, only a Pentium III processor will suffice (and there aren't any Pentium III-based versions of the Celeron to play with). Sad to relate, however, the Pentium III won't actually perform any faster than a Pentium II running at the same clock frequency (at least not today). This is because the only real difference between the two processors (apart from the fact that the Pentium III has a CPU ID) is the presence of MMX II streaming SIMD instructions in the Pentium III.

The problem is that it will take time for mainstream applications to be upgraded to take advantage of these instructions (and then you'll have to purchase these upgraded versions). Another consideration is that, in the same timeframe, you'll be able to get even faster processors for less money (see the next section). But it was always thus, and at the end of the day it's a case of "you pays your money and you takes your choice" as the old saying goes.

AS FOR TOMORROW

"And what about tomorrow?" – you ask – "What new wonders are heading our way?" Well there are a whole host of

exciting developments racing towards us.

First, processor clock frequencies are going to rise yet higher. Internet news-groups are confidently predicting 600MHz clocks by the end of 1999, 700MHz clocks by mid-2000, and 1GHz clocks soon thereafter.

Next, Intel are working furiously on a 64-bit processor (the current generation all work with 32-bit wide chunks of data), which should give another huge performance boost (when applications are rewritten and/or recompiled to take advantage of this feature).

Also, new integrated circuit production technologies are allowing increasing numbers of transistors to be squeezed onto each chip. In the foreseeable future it will be possible to cram 100 million transistors onto a single device. What will all of these transistors be used for? Well in addition to making the processors more powerful, it will be possible to dramatically increase the sizes of the local memory caches and locate the caches on the core CPU device, which will significantly improve the processor's performance.

Meanwhile, processors will be able to handle ever larger amounts of memory (which shall hopefully continue its trend to become even cheaper). Some high-end Intel-based professional workstations can already access 3GB of RAM or more (which makes the author's 64MB look positively measly by comparison). Also, Intel are working on bringing a next-generation memory system called Direct RAMBUS to the market, which will dramatically speed up processor-to-memory accesses.

It's also worth noting that, despite the Intel-centric focus of this article, Intel aren't the only game in town. There are a number of other players developing processors that look set to give Intel a run for their money.

Last but not least, there are a whole host of technologies that are outside the scope of this article, including optical fiber-based disk drives, and but that would be telling, wouldn't it? Suffice it to say that, for those of us who love computers, the future promises nothing less than faster, better, and cheaper, and who amongst us can find fault with that?

FURTHER READING

The hybrid and multichip module packaging technologies mentioned in this article are described in detail in an

amazingly useful book called *Bebop to the Boolean Boogie (An Unconventional Guide to Electronics)*. For those who want to understand more about how microprocessors work, *Bebop BYTES Back (An Unconventional Guide to Computers)* is jolly good. By some strange quirk of fate, both of these tomes are available from the *EPE Direct Book Service*.

For those who want the inside scoop on the latest breaking news in the processor wars, an excellent place to start is Tom Pabst's web site at www.tomshardware.com

INTEL WHO?

There are many fine microprocessors around, including those from Motorola (as found in Apple's Macintosh machines), AMD, Cirrus, and others. So why has this article concentrated on those from Intel (you may ask)?

Strange to relate, Intel never really intended to manufacture microprocessors – their original goal was to supply the world with semiconductor memory devices. So it rather took them by surprise when one of their design teams created the world's first microprocessor – the 4004. In fact the fate of the 4004 was precarious at best, and one of the main reasons that persuaded Intel's management to invest in continued development was the argument that the availability of microprocessors would help them to sell more memory devices.

In the mid-1970s, Intel considered adding a keyboard and a monitor to a board containing their 8080 microprocessor to sell it to the home user, but no one could think of a use for it (apart from something for housewives to keep recipes on) so they dropped the idea.

Some time later IBM decided that there was a market for computers for the small business user, so they set about creating the world's first PC. At that time, the two main contenders to supply the CPU for this PC were Intel's 8088 and Motorola's 6800. Had IBM opted for the Motorola device, we would all now doubtless have "Motorola Inside" logos tattooed on our foreheads.

Why did IBM choose Intel over Motorola? Who knows? Who cares? The decision was made, with the result that Intel Corporation are now arguably the best known manufacturer of microprocessors on the face of the planet.

The Pentium III is home to 7.5 million transistors! (Courtesy Intel Corp.)



RAYDON ELECTRONICS

Electrolitics can
 330µf/450v £2 each
 330µf/200v £1 each
 330µf/40v £0.50 each
 1000µf/40v £0.40 each
 6800µf/10v £0.40 each

Electrolitics radial
Packs of: 1µf/50v, 2.2µf/63V
 4.7µf/63v, 10µf/35v, 47µf/16v
 100µf/10v, 100µf/50v, 220µf/10v
 220µf/25v, 470µf/35v, 2200µf/16v
 5 off each value - total 55
 £3.00 pk
 10 off each value - total 110
 £5.00 pk

£1 packs
 25 assid ceramic disc/plate
 25 assid tantalum bead
 20 assid Leds R.Y.G 4.5 x 1.5mm
 20 assid Leds R.Y.G 2.5 x 5mm dia.

Loudspeakers Shielded
 8R/20W 4in. dia. £2.00 each
 16R/2.5W 3in. dia. £1.00 each
 16R/0.5W 2.4in. x 3.5in. £0.75 each
 8R/10W 5in. x 3in £3.00 pair

Loudspeakers Unshielded
 8R/5W 8in. dia. £1.50 each

Phono 1m leads
 1 way £0.50 each
 2 way £0.75 each
 3 way £1.00 each

Resistors carbon film
 10 each E12 value total 30 1/4W £4.50
 500 popular values 1/4W £2.00
 250 popular values 1/2W £1.75

Welwyn 21-FRG58ER wire wound 2.5W
 10p each
 R22, 1R, 10R, 220R, 270R, 560R, 680R

Voltage Regulators
 5 off 7815CT £1.00 pk
 5 off 7812CV £1.00 pk
 5 off 7912CT £1.00 pk

FERGUSON Boom Microphone

Unidirectional electret condenser fitted with 3.5mm jack. Includes telescopic boom, stand and video camera shoe. £8.75 each



Brushless Fan
 12v dc 0-1 amp



Metal box black with vented top and mounting studs



80 x 80 x 25mm
 £2.50 each

App. 110 x 80 x 56 h mm
 £2.00 each

Remotec 900 Preprogrammed 8 in 1



Universal Remote Control £10.00 each

Transistor			
TIP50		£0.25 each	
TIP142		£0.50 each	
TIP147		£0.50 each	
BC546	10 off	£0.50 pk	
BC157	20 off	£1.00 pk	
Diodes			
20 off IN5400		£1.00 pk	
20 off IN5401		£1.00 pk	
15 off IN5406		£1.00 pk	

Please send your order, while stocks last, including £1.25 p&tp to:

RAYDON ELECTRONICS

VALE HOUSE • RAYDON • IPSWICH • SUFFOLK IP7 5LW
 Cheques & Postal Orders should be made to Raydon Electronics



DISTANCE LEARNING COURSES in:

Analogue and Digital Electronics
 Circuits, Fibres & Opto-Electronics
 Electronic Testing & Fault Diagnosis
 Programmable Logic Controllers
 Mechanics and Mechanisms
GCSE and BTEC Mathematics

Courses to suit **beginners**
 and those wishing to **update**
 their knowledge and practical skills
 Courses are delivered
 as self-contained kits
 No travelling or college attendance
 Learning is at your own pace
 Courses may have
 BTEC Certification and Tutoring

For information contact:
 NCT Ltd., P.O. Box 11
 Wendover, Bucks HP22 6XA
 Telephone 01296 624270; Fax 01296 625299
 Web: http://www.nct.ltd.uk

Established 1990

QUASAR ELECTRONICS

Product data
FAX back
 01279 306504



PROJECT KITS

10W STEREO AMPLIFIER MODULE Uses TDA2009 class AB audio power amp IC designed for quality stereo applications. **3089-KT £9.95**

17W BRIDGE AMPLIFIER 40W of brute power 12VDC into 4W speakers. Ideal car booster amp. **3091-KT £6.25**

IR REMOTE TOGGLE SWITCH Use any remote control unit to switch onboard relay on/off. **3058-KT £9.95**

SPEED CONTROLLER for any common DC motor up to 100V/5A. Pulse width modulation gives maximum torque at all speeds. **5.15VDC 3067-KT £9.95**

PIC 16C71 FOUR SERVO MOTOR DRIVER Simultaneously control up to 4 servo motors (not supplied). Only 50mm x 70mm. **2102-KT £14.95**

UNIPOLAR STEPPER MOTOR DRIVER for any 5 or 6 lead motors. 3 run modes. **3109-KT £13.95**

PC BASED STEPPER MOTOR DRIVER Connects to parallel port. Drives two stepper motors up to 3A each. **3113-KT £15.95**

TRANSMITTER RECEIVER PAIR 2-button key lock style. 300-375MHz Tx with 30m range. Receiver encoder module with matched decoder IC. **30A15 £13.75**

STEREO VU METER Shows peak music power using 2 rows of 10 LED's. Green, yellow, red, moving bar display. **3018-KT £10.95**

NEGATIVE POSITIVE ION GENERATOR Standard 2000V Hi-Voltage multiplier circuit. Mains voltage experience required. **3057-KT £9.95**

AM RADIO KIT Tuned Radio Frequency front end single chip AM radio IC & 2 stages of audio amplification. All components & speaker provided. **PCB 32x102mm 3063-KT £9.95**

PELTER JUNCTION HEAT PUMP Boil & freeze water. Use fan regulated cooling of temperature sensitive components & much more. Heatsink required. **3066-KT £16.50**

LED DICE Classic intro to electronics & circuit analysis. 7 LED's simulate dice roll, slow down & land on a number at random. **555 IC circuit 3003-KT £7.95**

STAIRWAY TO HEAVEN Tests hand eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. **3005-KT £7.95**

ROULETTE LED Ball spins round the wheel, slows down & drops into a slot. 10 LED's. CMOS decade counter & Op Amp. Educational & fun! **3006-KT £9.95**

DUAL LED DICE PIC 16C54 circuit performs similar function to 3003-KT above but two dice. Good intro to micro-controllers. Software code supplied on disk. **3071-KT £9.95**

AUDIO TO LIGHT MODULATOR Controls intensity of one or more lights in response to an audio input. Safe, modern opto coupler design. Mains voltage experience required. **3012-KT £6.95**

9V XENON TUBE FLASHER Transformer circuit steps up 9V battery supply to flash the 25mm long Xenon tube. Adjustable flash rate (0.25-2 Sec). **3022-KT £10.95**

LED FLASHER 5 ultra bright red LED's flash in sequence or randomly. Ideal for model railways. **3052-KT £4.50**

16C84 PIC PROGRAMMER Reads programs & verifies. Uses any PC parallel port. All hardware, software & documentation needed to learn & test this IC provided. **3081-KT £21.95**

SERIAL PIC PROGRAMMER for all 8, 18, 28 and 40 pin DIP serial programmed PIC's. Third party software supplied. Expires after 21 days, and costs US\$25 to register. **3096-KT £9.95**

12-BIT PC DATA ACQUISITION SYSTEM Use your PC to monitor and control external events and devices through its parallel port. **3118-KT £34.95**

3V 1.5V TO 9V BATTERY CONVERTER Replace expensive 9V batteries with economical 1.5V batteries. IC based circuit steps up 1 x 2 AA batteries to give 9V. **18mA 3035-KT £4.75**

LIGHT ALARM Protect your valuables. Alarm sounds if circuit detects smallest amount of light. Place in cash box etc. **3008-KT £4.50**

PIEZO SCREAMER 110db of ear piercing noise. PCB fits in box with has 2 x 35mm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! **6-9VDC 3015-KT £8.75**

COMBINATION LOCK Versatile electronic lock comprising main circuit & separate keypad for remote opening of lock. Relay supplied. **3029-KT £8.95**

ULTRASONIC MOVEMENT DETECTOR Crystal locked detector frequency for maximum stability and reliability. PCB 75 x 40mm houses all components. 4-7m range. Adjustable sensitivity. Output will drive external relay circuits. **3VDC 3049-KT £12.95**

PIR DETECTOR MODULE 3-lead assembled unit just 25x35mm as used in commercial burglar alarm systems. **3076-KT £8.25**

TRAIN SOUNDS 4 selectable sounds - whistle, blowing, level crossing bell, chugging & chattering. All components in speaker supplied. **SG1 £4.50**

ANIMAL SOUNDS Cat, dog, chicken and cow. Ideal for kids farmyard toys and schools. All components inc. speaker supplied. **SG10 £3.95**

MUSIC BOX Activated by light. Plays eight Christmas songs and 5 other tunes. All components inc. speaker supplied. **3104-KT £5.95**

FUNCTION GENERATOR Quad Op Amp oscillator & wave shaper circuit generates audio range square wave, 16Hz-6KHz, triangle & pseudo sine wave outputs. **9VDC 3073-KT £4.25**

LOCK PROBE Tests 5V TTL circuits & detects fast pulses. Visual & audio indication of state. Full instructions supplied. **3024-KT £7.25**

SURVEILLANCE

High performance surveillance kits. Room transmitters supplied with sensitive electret microphones & battery holders. All transmitters can be received on an ordinary VHF FM radio.

MTX - MINIATURE 3V TRANSMITTER
 Easy to build & guaranteed to transmit 500 metres (over 1000m possible with higher voltage & better aerial). 3-9V operation. Only 45x18mm. **3007-KT £4.95**

MRTX - MINIATURE 9V ROOM TRANSMITTER
 As sensitive as the super sensitive high power 1000m range. Up to 2 miles with 18V supply & aerial. **9V operation 45x19mm 3018-KT £9.95**

HTPX - HIGH POWER ROOM TRANSMITTER
 High performance, 2 stage transmitter gives greater stability & high quality reception. 1000m range with 9V battery. 6-12V operation. **Off switch 70x15mm 3022-KT £6.95**

MMTX - MICRO-MINIATURE 9V TRANSMITTER
 The best selling micro-miniature room transmitter. 15mm x 25mm. It has a range of up to 500m. **9V operation 3051-KT £7.95**

VTX - VOICE ACTIVATED TRANSMITTER
 Only 2 stage voice activated transmitter. Only operates when sounds are detected. 14m range. Low standby current. Conserves battery power. Adjustable sensitivity & turn-off delay. Only 63x38mm. **3028-KT £7.95**

TRI - TELEPHONE RECORDING INTERFACE
 Connect between phone line & cassette recorder. Automatic ally switches when phone is used. Records all conversations. Powered from line. **48x32mm 3033-KT £5.95**

TRVS - TAPE RECORDER VOX SWITCH
 Very sensitive voice activated switch. Automatically turns on cassette recorder when sounds are detected. Adjustable sensitivity & turn-off delay. 19mm inc. mic. **3013-KT £6.95**

MTTX - MINIATURE TELEPHONE TRANSMITTER
 Attaches anywhere to phone line. Transmits only when phone is used. Uses phone line as aerial & power source. **500m range 45x15mm 3016-KT £4.95**

TWO STATION INTERCOM/HARD WIRED BUG
 Each unit has its own speaker, microphone & amplifier. Turn into a hard wired bug by using 4 standard cable supplied to connect to receiving station. **Remain bug unit 9V 3021-KT £11.75**

TELEPHONE AMPLIFIER KIT
 Pick up coil & sensitive amplifier let you hear conversations without even holding the phone! Can be used for surveillance purposes. **3055-KT £9.25**

X FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!
 Full details of all X.Factor Publications can be found in our catalogue. **N.B. Minimum order charge for reports and plans is £5.00 PLUS normal P&P.**

SUPER-EAR LISTENING DEVICE Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. **R002 £3.50**

TELEPHONE BUG PLANS Build your own micro-bee telephone bug. Suitable for any phone. Transmits over 250 metres. More with good receiver. Made from easy to obtain cheap components. **R006 £2.50**

LOCKS - How they work and how to pick them This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. **R008 £3.50**

RADIO & TV JOKER PLANS We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities! **DISCRETION REQUIRED R017 £3.50**

INFINITY TRANSMITTER PLANS Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone & activate the unit to hear all room sounds. Great for home office security! **R019 £3.50**

THE ETHER BOX CALL INTERCEPTOR PLANS Grab telephone calls out of thin air! No need to wire in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! **R025 £3.00**

20 MHz FUNCTION GENERATOR Coarse and fine tuning TTL output. 2V p.p. Uses MAX038 IC. Full assembly and operating instructions and box provided. **3101-KT £49.95**

POCKET SAMPLE DATA LOGGER Sample analogue inputs from 0.2V and 0.20V. Unit fits into DSHELL case supplied. PC powered. Software supplied. **3112-KT £18.95**

plus AUDIO • EDUCATIONAL • LASER • SECURITY • TEST GEAR • BOOKS & more

Out high quality project kits are supplied with all components, fibre glass PCB's & comprehensive instructions. **FREE CATALOGUE** will include our award 2 x 1st class stamps, international air freight details of other 1000 kits & publications that can be yours. Please **ADD £2.00 P. & P. to all orders** (Europe £3.50 Rest of World £5) & make cheques/PO's payable to **Quasar Electronics**. Goods normally despatch within 5 working days but please allow 28 days for delivery. **Prices include VAT at 17.5%.**

Quasar Electronics Unit 14 Sunningdale BISHOP'S STORTFORD Herts CM23 2PA
 Tel./Fax 01279 306504 E-mail: epesales@quasar-electronics.freemove.co.uk
 Web site: http://www.quasar-electronics.freemove.co.uk

A.M./F.M. RADIO REMOTE CONTROL



MAX HORSEY

Coded radio remote control has become straightforward and requires no licence.

REMOTE control systems are increasingly popular, and the introduction of pre-tuned radio modules, and their steadily falling prices has made radio a viable alternative to infra-red control. The advantage of radio is the ability of the signal to pass through objects and walls. Its range is also impressive, 100 metres or more (in free space) being typical.

No licence is required in the UK, providing the radio modules operate on the 418MHz waveband, and there are a number of conditions, one of which is that setting up and tuning is carried out by a DTI (Department of Trade and Industry) approved company. Hence if the module is purchased from such a company the home constructor can enjoy the benefits of radio remote control.

The DTI regulations also include limitations regarding the antenna (aerial) dimensions and mandatory labelling. This is to ensure that interference is not caused

to other radio users. The basic requirements under these regulations are given at the end of the article. Leaflets giving further information are available from the DTI.

This article describes how to use the radio modules in a similar way to those in the *Reliable Infra-red Remote Control* system which was published in *EPE* Oct/Nov '98. We will examine both a.m. and f.m. (amplitude modulated and frequency modulated) systems, and begin with a brief outline of the difference between these.

A.M./F.M. PRINCIPLES

In order to carry useful information, radio waves must be modulated, in other words the required signal must be superimposed on the radio wave (known as the *carrier wave*).

With Amplitude Modulation transmissions, it is the *amplitude* of the carrier wave that is made to change in accordance with the required signal. It is reasonably easy to generate, but can suffer from interference.

With Frequency Modulation transmissions, it is the *frequency* of the carrier wave that is made to change in accordance with the required signal. The f.m. modules described here tend to be more expensive than the a.m. modules, but they are almost immune to interference, can carry a higher data rate and have a longer range.

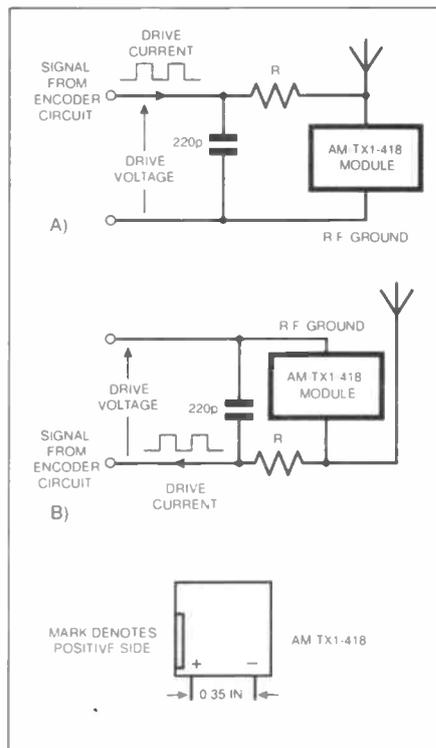


Fig.1. AM-TX1-418 transmitter driven from (a) +ve supply and (b) -ve supply.

Both types operate at 418MHz and have been tested for the purpose of this article, and the a.m. system proved very reliable with an impressive range. However, we will describe how to use both systems.

A number of a.m. 418MHz modules are available, but we have chosen two transmitters and one receiver. The cost of these modules has fallen in recent months and a transmitter/receiver pair can be obtained for less than £8.

TRANSMITTER AM-TX1-418

The RF Solutions a.m. transmitter module type AM-TX1-418 is a 2-pin device, and looks like a capacitor. It is very simple to use – the basic arrangement is shown in Fig.1.

There are two circuits shown: (a) allows the encoder signal (i.e. the message being sent) to drive the positive side of the radio module; (b) allows the encoder signal to drive the negative side



Table 1. Resistor selection for AM-TX-418 module

Supply voltage	Resistor value
12V	2k2
9V	1k8
6V	1k
4.5V or 5V	470Ω
3V	100Ω

Current consumption: 2.5mA (typical)
CMOS/TTL compatible input
Data throughput: 1200 baud

of the radio module. The only additional components required are a capacitor and resistor. The value of the resistor (R) is chosen according to the supply voltage employed in the circuit (between 3V and 12V), as shown in Table 1.

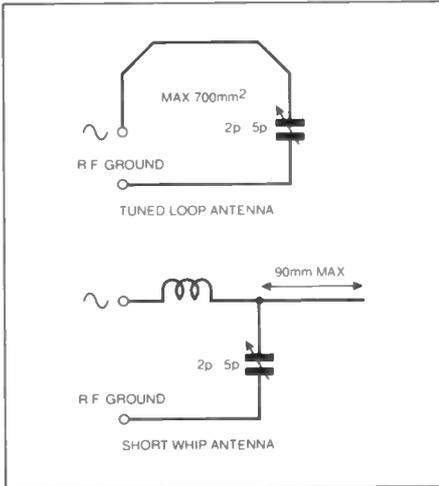


Fig. 2. Two possible alternative antenna arrangements.

The module requires an antenna which is a little more complicated to set up than the transmitter module described later. Two possible arrangements are shown in Fig. 2. A variable capacitor having a 2pF to 5pF range is also required, and must be adjusted to provide the strongest signal. In practice, this is not easy to check, and the practical project described now employs a transmitter module which requires no such adjustment.

AM-RT4-418 TRANSMITTER

An alternative 418MHz a.m. transmitter module is the RF Solutions type AM-RT4-418. It is a d.i.l. device and its mechanical dimensions and pin descriptions are given in Fig. 3.

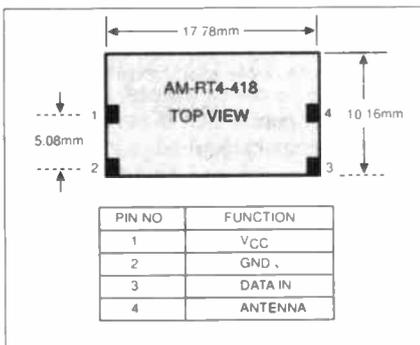


Fig. 3. Pinouts of the d.i.l. version of the AM-RT4-418 transmitter.

Note that an RF Solutions type AM-RT5-418 is also available. The only difference is that it is supplied in a s.i.l. (single-in-line) package, i.e. its pins are arranged in a straight line.

Apart from the fact that the RT4 operates at 418MHz, the other main operational factors are:

- Operating voltage: 2V to 14V
- Current consumption: 4mA
- Maximum data rate: 4kHz.

The antenna used with this module could be a "whip" type or a helical coil. The latter consists of a coil made of 34 turns of enamelled copper wire (diameter 0.5mm), close wound on a 2.5mm diameter former. The helical coil consumes much less space than a whip antenna, but its performance may be a little lower, and small adjustments may be needed to its length for best results.

A whip is the simplest antenna for use with the RT4 transmitter. It can simply be a straight piece of rigid wire (or p.c.b.

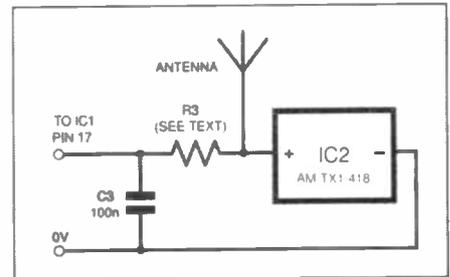


Fig. 5. Insertion circuit of alternative AM-TX1-418.

12V, and it does not produce a modulated output. In other words, the i.c. encodes the signal but modulation is performed inside the radio module.

The circuit diagram for the encoded Radio Remote Control A.M. Transmitter module is shown in Fig. 4. It uses the AM-RT4-418 a.m. radio module (IC2) and the HT6014 encoder (IC1). The module can send up to four encoded signals, or

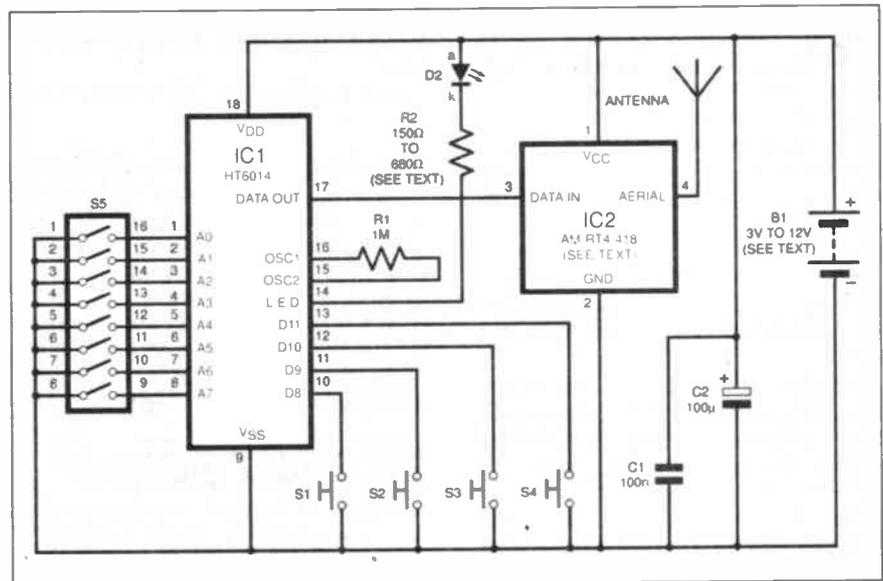


Fig. 4. Circuit diagram for the encoded Radio Remote Control A.M. Transmitter module.

track) 17cm long. It works very well in practice, though it should not be close to metal objects. The wire should be as straight as possible.

The simplicity and reliability of this arrangement is the reason for the choice of this particular radio module in the constructional project about to be described.

In tests, this transmitter was able to cover a range of 100m in open space. Note that unlike the previous radio module (AM-TX1-418), the AM-RT4-418 is permanently connected to the power supply, but if no switch is pressed the current consumption is virtually zero.

CODED TRANSMITTER

All remote control systems are more reliable if a coded message is sent, and the use of an encoder integrated circuit (i.c.) is suggested, such as the Holtek HT6014. This is similar to the type HT12B used in the *Reliable Infra-red Remote Control* system, except that it can operate at up to

combinations of signals. Whenever one of the switches, S1 to S4, is pressed the circuit becomes active. If no switch is pressed, the circuit virtually shuts down — hence saving battery power.

The optional light emitting diode (l.e.d.) D1 lights when any switch is pressed. The value of its ballast resistor (R2) depends on the power supply used, typical values being 680Ω for a 9V or 12V supply, 150Ω for 3V. If the l.e.d. is not required, R2 can be omitted.

An AM-TX1-418 transmitter module can be substituted for the AM-RT4-418 as shown in Fig. 5.

CODING SWITCH

The transmitter is encoded by means of the multiple switch S5, which comprises eight independent on-off switches in a d.i.l. (dual-in-line) package. The purpose is to allow any or all of IC2's pins labelled A0 to A7 to be connected to 0V, the pattern of connection setting the code

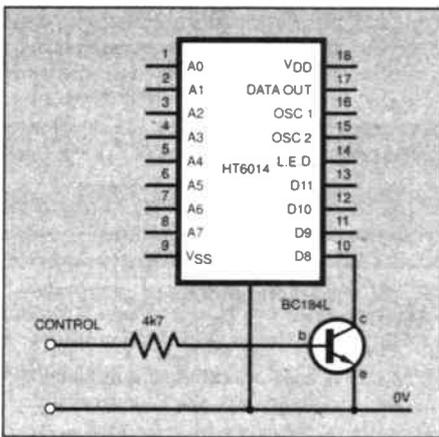


Fig.6. Transistor coupling a control input.

to be transmitted. The transmitted signal will only be decoded by a receiver's decoder which has a similar combination of pins connected to 0V.

This technique is useful if you wish to control a door lock (for example) — it would be difficult for an intruder to match the particular combination you may have chosen.

The d.i.l. switches allow you to change the combination whenever you wish. However, in practice you may never need to change the combination, and it is easier and cheaper to permanently connect one or more of A0-A7 pins to 0V, using link wires. *It is essential to have the same combination of pins connected to 0V on both the transmitter and receiver.*

Capacitors C1 and C2 are included for decoupling purposes; C1 removes any voltage spikes on the supply rails, and C2 removes slower voltage fluctuations.

If you wish to interface the circuit to an input module, Fig.6 shows how a transistor may be employed (no provision for this has been made on the p.c.b., however). When the control input is at about 0V, the *nnp* transistor is turned off and the effect is similar to the equivalent hardware switch in Fig.4 (S1 in this case) not being pressed.

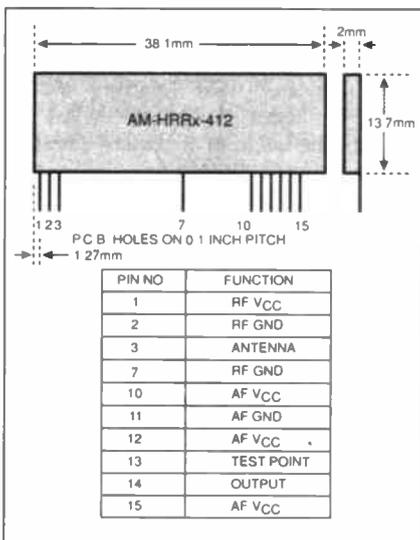


Fig.7. Pinouts for the AM-HRR1-418 receivers.

When the control input is made positive (i.e. more than about 0.7V) the transistor turns on and data input D8 is connected to 0V — like pressing S1 in Fig.4. Each of the four data inputs may be treated in the same way if required.

A.M. RECEIVER

Only one type of receiver is described, although three versions are available.

They have the same pin layouts and can be interchanged with each other in your circuit. The three versions are:

- AM-HRR1-418: This is inexpensive (e.g. less than £3) and although superseded by the next type, it works very well.
- AM-HRR3-418: As above, but laser trimmed for accuracy
- AM-HRR5-418: As above, but very low current consumption (0.5mA)

The receiver modules have the following specifications:

Supply voltage: 4.5V to 5.5V
 Supply current: 2.5mA (HRR5 version: 0.8mA)
 Output is compatible with CMOS/TTL
 Maximum data rate: 2kHz.

The pin layout is shown in Fig.7. Note the slightly odd numbering used, and the way in which the r.f. (radio frequency) ground is separate from the a.f. (audio frequency) ground. Although both grounds should be connected to 0V in the circuit, it is best to use separate tracks on the p.c.b., with separate decoupling capacitors. A look at the receiver p.c.b. will illustrate this (Fig.12 later).

DECODING A.M. RECEIVER CIRCUIT

Details of how the receiver module may be used with an HT6034 decoder to make up the A.M. Receiver circuit are shown in Fig.8.

Signals detected by the receiver module IC1 are output to the decoding device, IC2. The signal is only decoded if the settings on the d.i.l. switch S1 match those of the transmitter.

When a correctly coded signal is received, the pin labelled VT on IC2 switches to positive. The VT pin only remains positive for the duration of the decoded signal (i.e. for as long as the appropriate switch is pressed on the transmitter).

During this period, the data outputs (D8 to D11) copy the logic level at the data inputs of the transmitter. They will normally be positive, but if (for example) the switch (S1) connected to data pin D8 on the transmitter is pressed, this pin will be pulled to 0V and will make data pin D8 on the receiver switch to 0V.

The same applies to the other data switches (S2 to S4) and associated pins (D9 to D11). Note that this is different to the encoder/decoder system used previously on the infra-red modules.

The data outputs can be used to drive logic gate inputs (TTL or CMOS), or can be connected to transistors as described later.

As with the transmitter module, the purpose of the d.i.l. switch (S1) is to allow any or all of IC2's pins labelled A0 to A7 to be connected to 0V, allowing you to change the combination whenever you wish. As before, you may use link wires instead of a switch if you prefer. Again note that it is essential to have the *same* combination of pins connected to 0V on both the transmitter and receiver.

INTERFACE CIRCUIT

Most of the rest of the circuit in Fig.8 (to the right of the dotted line) shows how IC2's VT and data outputs can be interfaced in order to allow the module to control l.e.d.s, buzzers, relays, motors, solenoids etc. If all the output options are not required many components can be omitted.

The VT pin is connected via resistor R10 to the base of TR1. This can be a TIP122 (or TIP121) *nnp* Darlington transistor, enabling higher-current devices (such as those above) to be controlled. A small-signal transistor (such as a BC184L) could be substituted for the TIP122 if only a small buzzer or l.e.d. is required.

A relay coil (RLA1) is shown as the driven load for TR1. A motor or solenoid could be connected here if preferred. Diode D1 removes any back e.m.f. spikes produced by the relay/motor etc (which could damage the transistor). An l.e.d. D2 serves as an indicator whenever a signal is received. Any or all of these components may be omitted if not required.

DATA OUTPUT INTERFACING

The fact that each data output switches to 0V when the appropriate transmitter button is pressed causes a slight complication at this stage. It is possible to switch on a *pnp* transistor with a 0V signal, but if the transistor is also being used as an interface between two voltage levels then this option is difficult. Hence additional transistors TR2 to TR5 are used to invert the logic level.

For example, if data output pin D11 is positive (no signal received), TR2 will be switched on, and its collector will be at 0V. This will switch off TR6. If output D11 switches to 0V, then TR2 will be switched off, and its collector will be pulled to 5V via resistor R6. Consequently, Darlington transistor TR6 will switch on, causing l.e.d. D4 to light.


As with TR1, a relay (RLA2) is the driven load for TR6. Other higher current devices may be driven instead. Diode D3 removes any back e.m.f. If only an l.e.d. or small buzzer is required, a low-power *nnp* transistor such as a BC184L can be substituted for the TIP122.

The other three data outputs are interfaced in the same way.

POWER SUPPLY

As shown in Fig.8, the power supply for the receiver is a 12V battery, since many applications will require the circuit to drive 12V relays/solenoids etc.

Fig. 8. Complete circuit diagram of the decoding receiver.

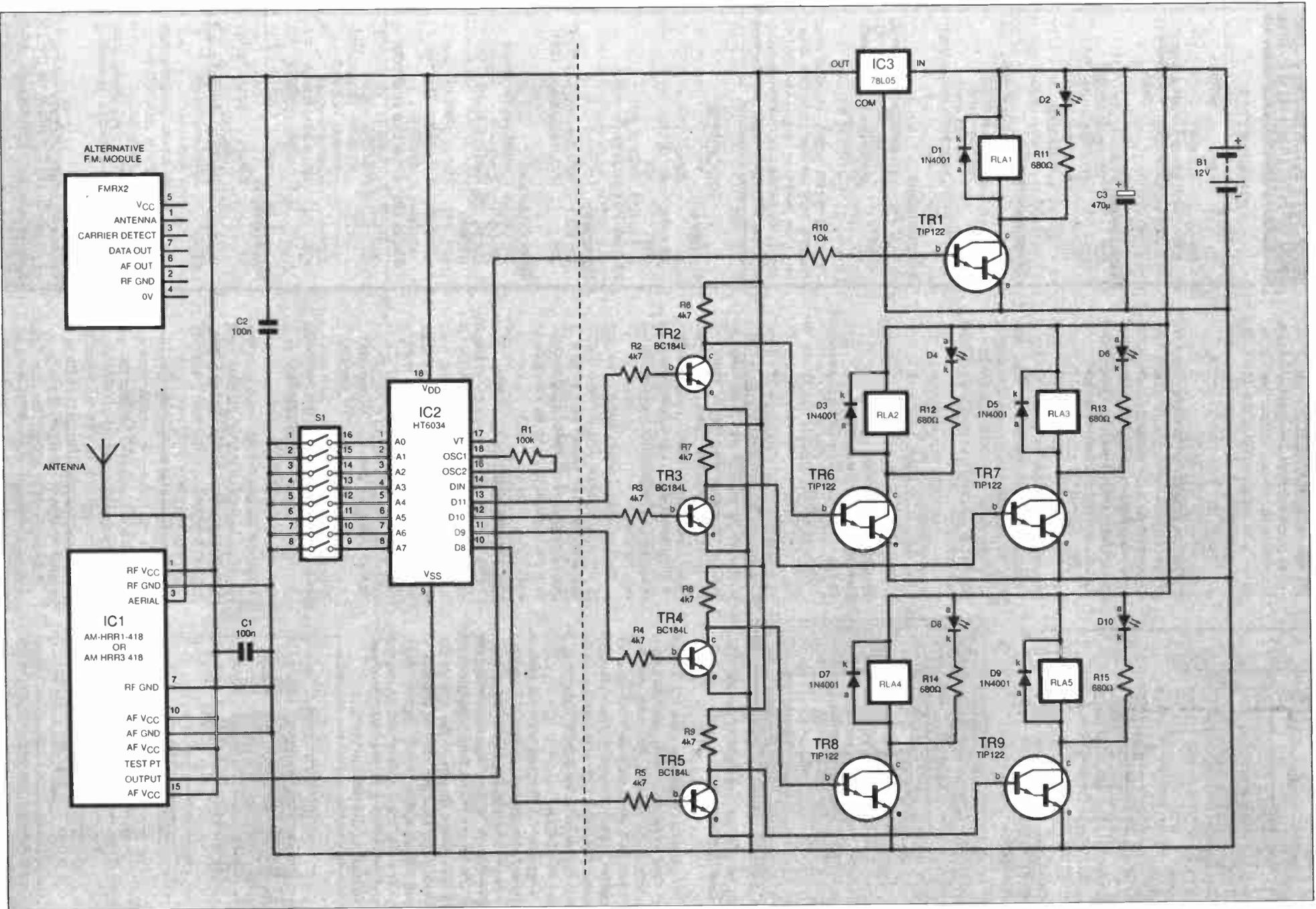

COMPONENTS

TRANSMITTER

Resistors
 R1 1M
 R2 see text
 R3 see text
 All 0.25W 5% carbon film or better.

See SHOP TALK page

Capacitors
 C1 100n ceramic disc
 C2 100µ radial elect., 25V
 C3 100n ceramic disc (see text)

Semiconductors
 D1 red l.e.d. (see text)
 IC1 HT6014 encoder
 IC2 AM-RT4-418 or AM-TX1-418 or FM-TX2-418 (see text)

Miscellaneous
 S1 to S4 min push-to-make switch, p.c.b. mounting (4 off)
 S5 8-way d.i.l. s.p.s.t. switch (see text)

Printed circuit board, available from the EPE PCB Service, code 228; antenna, 17cm wire (see text); AAA-size 1.5V cell (2 off); plastic case, 105mm x 60mm x 25mm with four integral push buttons; connecting wire; solder, etc.

RECEIVER

Resistors
 R1 100k
 R2 to R9 4k7 (8 off)
 R10 10k
 R11 to R15 680Ω (5 off)
 All 0.5W 5% carbon film or better.

Capacitors
 C1, C2 100n ceramic disc (2 off)
 C3 470µ radial elect., 16V

Semiconductors
 D1, D3, D5 1N4001 rectifier diode
 D7, D9 (5 off)
 D2, D4, D6, red l.e.d. (5 off)
 D8, D10
 TR1, TR6 TIP122 or TIP121 *n*p*n* Darlington (see text) (5 off)
 TR2 to TR5 BC184L *n*p*n* transistor (4 off)
 IC1 AM-HRR1-418 or FM-RX2-418 transmitter module (see text)
 IC2 HT6034 decoder
 IC3 78L05 +5V 100mA voltage regulator

Miscellaneous
 S1 8-way d.i.l. s.p.s.t. switch (see text)
 RLA1 to RLA5 12V relay, contacts to suit application (5 off) (see text)

Printed circuit board, available from the EPE PCB Service, code 229; antenna, 17cm wire (see text); 12V mains adaptor plus socket to suit; plastic case, 148mm x 90mm x 54mm; connecting wire; solder, etc.

Approx. Cost Guidance Only

£54
 excl. batt & p.s.u.

F.M. MODULES

For readers wishing to employ an f.m. transmitter/receiver combination (instead of an a.m. combination), the following will be helpful.

F.M. TRANSMITTER

The f.m. transmitter module suggested is type FM-TX2-418-3V, since it is able to operate on a 3V supply (as its reference code implies). This can be provided by two AAA cells, which fit neatly inside the recommended transmitter case.

A 5V module is also available, code FM-TX2-418-5V. Note that the f.m. transmitter module is designed for a particular voltage, unlike the a.m. version which can operate on a range of voltages. Apart from that, the module is similar to use, and its specification is as follows:

Supply Voltage 2.2V to 4V (3V version)
 4V to 6V (5V version)
 Supply Current 6mA
 Data Rate up to 40k bits/s
 Range 300m in open ground

Pinouts for the module are shown in Fig.9 and circuit connection details are shown in Fig.10. It is similar to the 4-pin a.m. transmitter module described earlier, except that a fifth pin is included so that the r.f. ground and the 0V supply to the rest of the module can be separated. This reduces the problem of interference.

The transmitter p.c.b. layout has been designed to accept either the a.m. or the f.m. module.

The f.m. module costs about twice that of the a.m. module, but it has a higher specification and greater range. If it is chosen in preference to the a.m. module, then the receiver must be an f.m. type as well.

F.M. RECEIVER

The f.m. receiver module is much more expensive than the a.m. version. It is available in 3V and 5V versions, both of which are available as two Data Rate versions, standard and fast. The specifications are as follows:

Supply Voltage 3V to 4V (3V version)
 4V to 6V (5V version)
 Supply Current 13mA
 Data Rate 40k bits/s (fast version)
 14k bits/s (standard version)

The 5V version of the module is the most convenient in this application, and the standard version is denoted FM-RX2-418-A5V while the fast version is coded FM-RX2-418-F5V.

The pin layout of the module is shown in Fig.11. It features a similar arrangement to the a.m. module, but note that pin 6 provides an analogue output, while pin 7 provides a digital output. In this application we use the digital output which is a squared version of the signal at pin 6.

The application circuit for the f.m. receiver is virtually identical to the a.m. circuit shown in Fig.8. As with the trans-

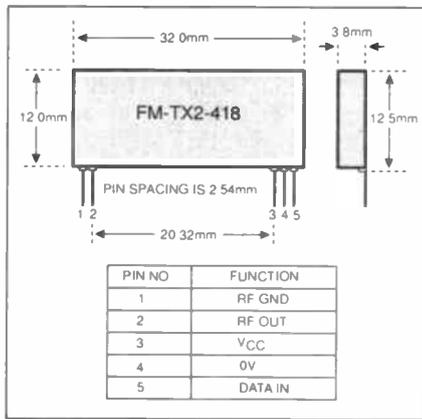


Fig.9. Pinouts for the FM-TX2-418 transmitter.

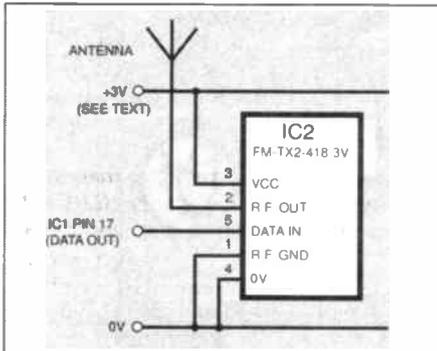


Fig.10. Circuit connection for the FM-TX2-418 transmitter.

However, whereas the HT6034 decoder chip IC2 will operate on a supply of 3V to 12V, the radio receiver module IC1 must only be used on a 5V supply. Hence the inclusion of the 5V voltage regulator IC3. If the entire circuit is to be powered by a 4.5V battery, IC3 may be omitted.

Capacitor C1 decouples the r.f. section of the radio module, while C2 and C3 decouple the main part of the circuit. Note that on the printed circuit board the r.f. 0V supply line is kept separate from the 0V power supply to the rest of the circuit. The two are only connected to each other at the power supply input point. This helps reduce the chance of interference being induced into the sensitive parts of the radio module.

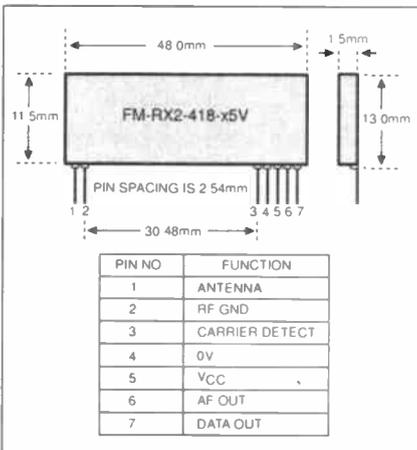


Fig.11. Pinouts for the FM-RX2-418-A5V/F5V receiver.

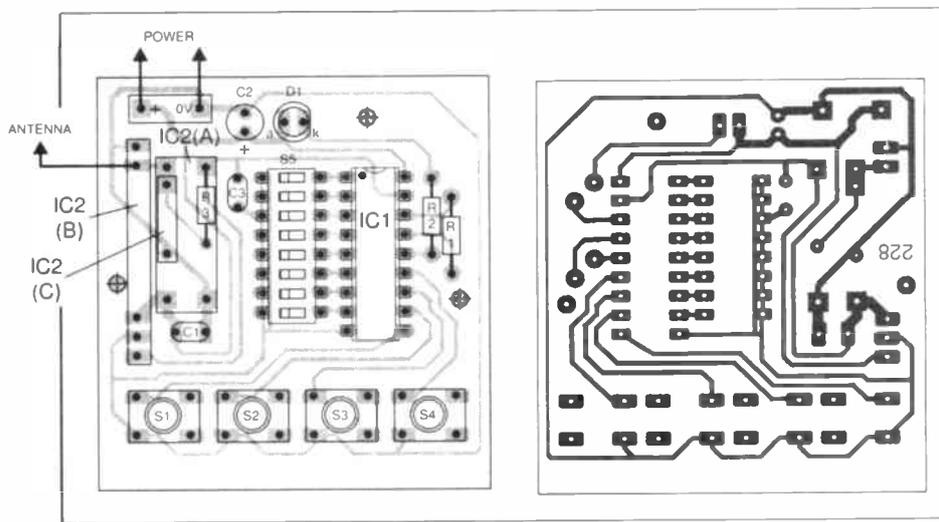


Fig.12. Component layout and master track foil pattern for the Transmitter p.c.b.

mitter, the receiver p.c.b. has provision for either the a.m. or f.m. modules.



PRACTICAL SYSTEM

Emphasis has been placed on a transmitter circuit designed around the AM-RT4-418 a.m. module, and in tests it performed extremely well, and the antenna arrangement is straightforward, with no adjustable components.

It is this circuit for which the transmitter p.c.b. has been designed. However, provision has been made on the p.c.b. for the AM-TX1-418 module plus its extra resistor (R3) and capacitor (C3). The same board will also accept the f.m. transmitter module as an alternative.

The radio modules can be used in all sorts of ways, and so as much flexibility as possible has been allowed for. The remote control system can be a single momentary signal, i.e. when any switch is pressed on the transmitter, a single action occurs at the receiver; when the switch is released the action stops.

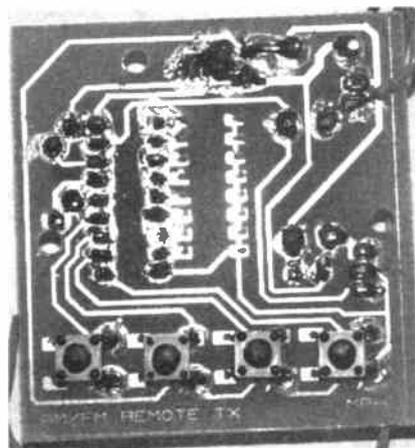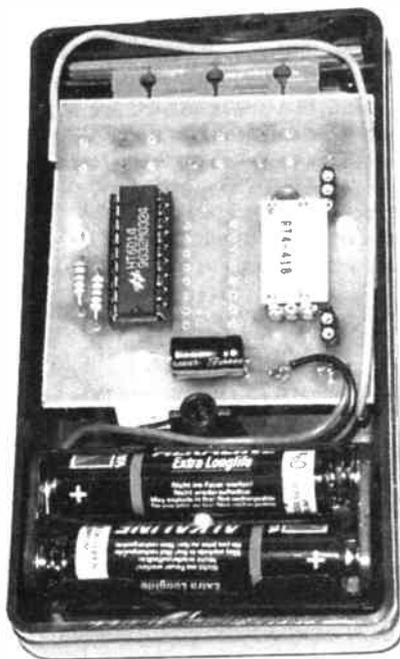In this context the word *action* means that (a) an l.e.d. can light, (b) a buzzer can sound, (c) a relay can be activated etc.



There is provision for any or all of these options on the p.c.b.. If a single way momentary system is required, it is necessary to fit only one switch – ideally one near the centre of the p.c.b., say S2 or S3.

There is provision for up to four latching ways. Pressing another switch unlatches the previous one. For example, if two switches are fitted on the transmitter p.c.b., say S1 and S4, then S1 can be used to latch the appropriate output. When S4 is pressed, the output unlatches. Note that it is possible to latch two or more outputs at the same time if the appropriate buttons are pressed at the same moment.

It is possible to include all options, i.e. one momentary and four latching ways if required. The momentary way can be used to indicate "message received".

Power Darlington transistors have been chosen at the receiver in case motors or solenoids are required. If you only wish to drive small buzzers or l.e.d.s, then the Darlington may be replaced by BC184L transistors.

The l.e.d. D1 on the transmitter is optional; it indicates that a switch is being pressed, and that the circuit is active (e.g. battery is OK). If the l.e.d. is omitted, then you can also omit R2 on the transmitter.

CONSTRUCTION

We will begin construction with the coded transmitter. Ensure that you are

clear about the options available (see above), particularly whether you are using the a.m. or f.m. modules.

The p.c.b. component and track layout details are shown in Fig.12. This board is available from the *EPE PCB Service*, code 228.

Begin assembly by fitting sockets for IC1 and IC2. (Do not fit the i.c.s (especially the delicate/expensive radio module) at this stage.) Whereas IC1 requires a normal d.i.l. socket, IC2 (as an a.m. module, position marked as IC2(A)) requires four single pin sockets. The best way to accommodate this is to buy a strip of s.i.l. sockets and cut two strips of 3-ways each. Next cut off the pin of the middle socket of each strip. The strips can now be soldered into the p.c.b. – one strip at each end of IC2.

This is much easier and stronger than soldering in single sockets. The f.m. version of IC2 (position marked as IC2(B)) requires one 2-way and one 3-way s.i.l. strip.

The alternative 2-pin a.m. transmitter has its position marked as IC2(C). It requires the addition of capacitor C3 and resistor R3 (which are only required for this transmitter version). The value for R3 should be chosen from Table 1 (earlier) to suit the power supply.

Solder in the resistors and capacitors taking care to fit C2 the correct way round and with its leads long enough to allow it to be bent over flat against the p.c.b.. This enables the p.c.b. to be housed in the rather thin case specified.

The optional l.e.d. occupies a central position on the p.c.b. so that it can be aligned with a hole drilled in the case. Note that the l.e.d. should be fitted on the copper side of the p.c.b., with its leads long enough to allow the l.e.d. to rest against the hole. Similarly, switches S1 to S4 must be mounted on the copper side of the p.c.b., assuming that the recommended case is employed.

CODING SWITCHES

As discussed earlier, the set of eight switches within the d.i.l. switch modules allow the system to be encoded to prevent a signal from another transmitter from activating the receiver. The switches enable the code to be changed easily if necessary. It is essential to set the same code at both the transmitter and receiver.

Many people will have little cause to change the code, and so one or two wire links can be fitted in place of the d.i.l. switches to set a permanent code. It is essential to insert the same wire links in both the transmitter and receiver. If security is not an issue, it is not necessary to fit any wire links (or d.i.l. switches) – the associated pins on the coder/decoder chips can remain unconnected.

Solder in the d.i.l. switch if required, or any wire links to set the code as necessary.

Connect power leads as shown. Note that the f.m. version requires a 3V supply; the a.m. version can cope with a

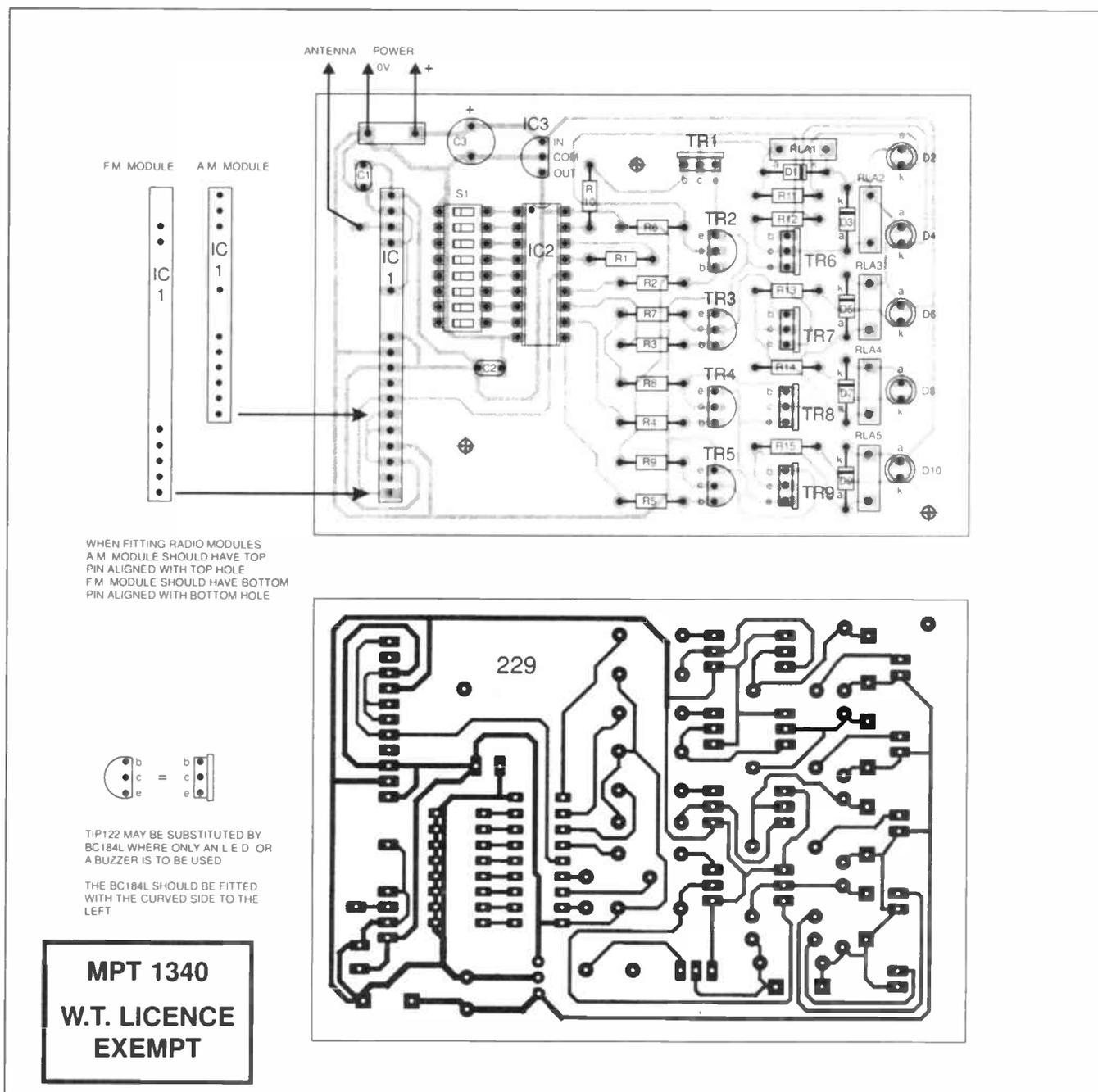


Fig.13. Component layout and full size master foil track pattern for the Receiver p.c.b.

wider voltage range, but 3V is also convenient. A battery holder housing two AAA cells fits neatly into the recommended case.

The antenna in the a.m. version must be connected to the pad as shown in Fig.12. If using the f.m. module, the antenna must be connected to the pad intended for pin 4 of IC2 (the top left hand corner of IC2 as in Fig.12). This arrangement allows either module to be employed without compromising the requirements of the antenna, i.e. a single conductor. The antenna can be an ordinary wire of total length 17cm.

Finally, insert IC1 and the radio module. The a.m. version fits parallel with the p.c.b.: note that the "overhang side" is towards the edge of the p.c.b. Treat both IC1 and IC2 as static sensitive devices, i.e. briefly earth yourself before handling them.

The alternative f.m. radio module fits upright, but it may be necessary to bend

it parallel with the p.c.b. in order to fit the case. If so, use pointed-nose pliers to carefully bend the pins of the device.

TRANSMITTER CASE

The transmitter is housed in a case which has one, two or four pushswitch buttons built in. These align with the switches mounted on the copper side of the transmitter p.c.b. Drill a hole on the front of the case (buttons side) as shown to allow the l.e.d. to show through.

The p.c.b. may be fixed with self-adhesive p.c.b. supports. It may be necessary to cut the base of two of the supports to allow them to fit inside the case. Three points have been marked on the p.c.b. to indicate positions for the supports.

It is important that the buttons make contact with the switches on the p.c.b. and spacers cut from small pieces of plastic or rubber feet may be needed to lift the p.c.b. slightly. Double-sided self-


adhesive pads are also very helpful at this stage.

Ensure that the switches are aligned properly when fitting the p.c.b., so that they click when each button is pressed. If the p.c.b. flexes too much, a pad of non-conductive material can be fixed to the back of the case to push against the p.c.b. above the positions of the switches.

RECEIVER CONSTRUCTION

Details of the p.c.b. for the Receiver module are shown in Fig.13. This board is available from the *EPE PCB Service*, code 229.

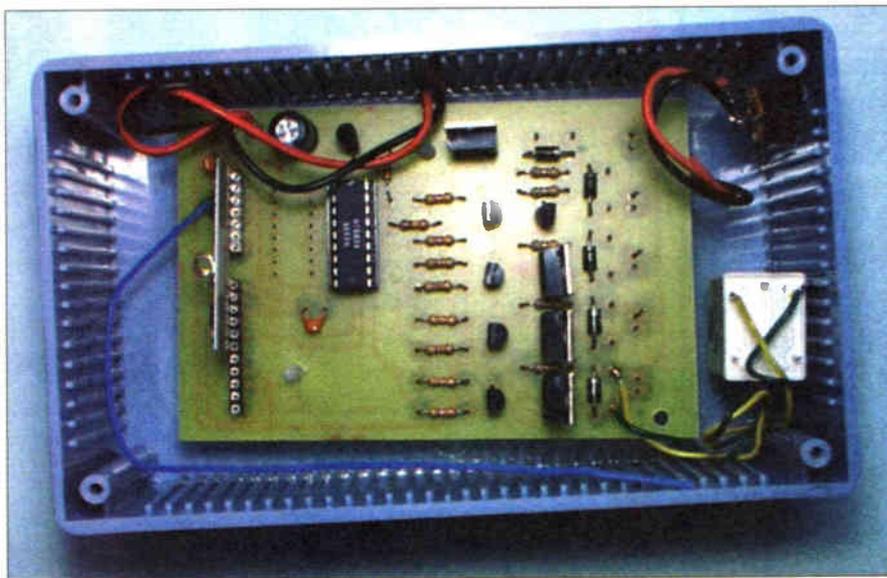The receiver p.c.b. is constructed in a similar way to the transmitter, again noting carefully which options are required. The a.m. and f.m. receiver modules are both "in-line" types, and care must be taken to fit the chosen one in the correct place.



The a.m. module requires three s.i.l. sockets, one each of 3-way, 1-way and 6-way. The f.m. module requires a 2-way and a 5-way s.i.l. socket. Alternatively, fit s.i.l. strips to occupy all the pads for both modules. Do not fit any i.c. or radio module at this stage.

Fit the d.i.l. socket for IC2, the optional d.i.l. switch or wire links, followed by resistors and capacitors, noting that C3 must be connected the correct way round. Leave out the l.e.d.s for the moment.

The power Darlington transistors can be replaced with BC184L transistors if you only wish to control small buzzers or l.e.d.s. The insert in Fig.13 shows how the flat side of the BC184L is equivalent to the metal tab of the TIP122.

The l.e.d.s may be joined to the p.c.b. via wires or, more conveniently, soldered on the copper side of the p.c.b. so that they align with a set of holes drilled in the case.

Fit leads for the power supply and solder on a rigid wire of length 17cm for the antenna.

It is wise at this stage to test the circuit without IC1 or IC2 fitted. With a 9V or 12V power supply applied, use a voltmeter to check that the positive (Vcc) and ground (0V) pads of both devices correctly receive 5V (see the circuit

diagram in Fig.7 for the pin numbers). If this is not the case, check that the regulator IC3 has been fitted correctly.

Note that l.e.d.s D4, D6, D8 and D10 should light up when power is applied, assuming that IC2 is not fitted. If they do not, then check resistors R6 to R9 and transistors TR6 to TR9 to locate the fault before proceeding.

Finally, insert IC2 and the appropriate radio module. The a.m. module is fitted with its top end (pin 1) at the top of the row of pads, with the component side of the module facing the edge of the p.c.b.

The f.m. module is fitted with its bottom end (pin 7) at the bottom end of the row of pads. Note that the antenna pin of either module is correctly aligned by the pad labelled "ANTENNA". It should not be necessary to bend the module parallel with the p.c.b. since the case suggested is reasonably large. If bending is necessary take great care and use pointed-nose pliers to avoid straining the delicate material housing the module.

TESTING

As with infra-red remote control, testing is a classic chicken and egg situation. Failure of the system to work could be due to the transmitter or receiver.

Connect suitable power supplies and check that the l.e.d. (if fitted) on the transmitter lights when any switch is pressed. See if the receiver responds – l.e.d. D2 is very useful for detecting a signal.

If the system fails, an oscilloscope will show whether data is present at the data pin of the transmitter and, if so, a similar test will show if the same data is present at the receiver. Use a voltmeter to check the power pins on the radio modules and encoder/decoder i.c.s. Check the value of resistor R1 on both the transmitter (1M Ω) and the receiver (100k Ω).

More detailed tests can be made by attaching the negative lead of a voltmeter or oscilloscope to the 0V rail on either circuit, and measuring voltages or signals around the circuit as detailed earlier.

RECEIVER CASE

The receiver may be mains powered via a suitable mains adaptor, in which case begin by drilling the necessary hole for its connection socket.

The l.e.d.s require holes drilled in the front of the case. If the l.e.d.s have been fitted to the copper side of the p.c.b. it is only necessary to drill appropriate holes which allow the l.e.d.s to show through when the p.c.b. is located into the case.

If the receiver is to be used to control mains devices via relays, the relays should be in an area away from the p.c.b. (see photo), or in another case. *(Only constructors who are competent at mains wiring should connect up this circuit for mains control switching.)*

USING THE SYSTEM

The range offered by the system (even with the a.m. version) is likely to be much greater than required, and a poor antenna (e.g. where the wire is bent to fit the case) is of little consequence.

However, if range is important then the antenna should be as straight as possible, and away from metal objects. Note that the use of a super high gain antenna is prohibited under MPT1340 regulations.

LICENCE EXEMPTION

The transmitter modules referred to in this article have been approved by the Department of Trade and Industry for use in the UK under specification MPT1340 and require no radio operating licence. However, to comply with MPT1340, the following requirements must be observed:

1. All transmitters shall use integral antennas only. Receivers may use an external or integral antenna. An integral antenna is defined as one which is designed to be connected permanently to the transmitter or receiver without the use of an external feeder.

2. The equipment in which the module is used must carry an inspection mark located on the outside of the equipment which is clearly visible. It shall state "MPT1340 W.T. Exempt". The minimum dimensions of the mark shall be 10mm \times 15mm and the figure height shall be not less than 2mm. \square

**Free Additional Transmitter
with every order !**

Transmitters & Transceivers

418, 433, 863 & 868MHz

UK Manufactured

Low Prices!

Order the FM TXM-418-A/F and SILRX-418-A/F pair (as shown above) for only £25.00 + VAT and get an additional transmitter free! P & P £ 1.50

Please call for a free catalogue, wall chart or a competitive volume quotation on any Radiometrix Ltd module. Simply just e-mail sales@radtec.demon.co.uk. alternatively Fax or Telephone quoting ref: EPE-RM1



Telephone +44(0)1992 576107
Fax +44(0)1992 561994
<http://www.radio-tech.co.uk>

Radio-Tech Limited

Your official Radiometrix Distributor



PLASTIC BOXES & ENCLOSURES

Contact us for your free catalogue

S.L.M. (Model) Engineers Ltd
Chiltern Road
Prestbury
Cheltenham
GL52 5JQ

Telephone 01242 525488
Fax 01242 226288

OUR LATEST IRONS WILL SAVE YOU SOME BRASS

Our quality range of thermally balanced irons is now even better than ever. Easier to handle, cooler to use, each iron is manufactured in the UK and meets CE conformity. There's an 'In Handle' adjustable temperature model and burn proof lead option and a wide selection of soldering bits. That's the good news. The even better news is that all our irons are still very competitively priced.

Tel: 01822 613565 Fax: 01822 617598

www.antex.co.uk



NOT JUST ANY OLD IRON

PRACTICALLY SPEAKING

Robert Penfold looks at the Techniques of Actually Doing It!

ELECTRONIC project construction is not just soldering irons, electronic components, and test meters, there is also a "nuts and bolts" side to things. Having successfully completed a circuit board you usually have a fair amount of work left to do before you are ready to show off your new masterpiece.

If you have a good selection of tools and are familiar with DIY jobs around the house you should not find things too difficult, but project construction and general DIY tasks are certainly different. It is certainly worth making the point to anyone experienced in putting up shelves or dealing with car servicing that electronic project construction requires a tender-handed approach.

You will often be dealing with plastic or aluminium cases that will not take kindly to the "bull in a china shop" approach. Some of the plastic cases are actually quite tough, but others are prone to cracking, and it is easy to buckle aluminium cases. Also, most cases have finishes that are easily damaged. When dealing with the "nuts and bolts" side of construction it is normally necessary to proceed carefully and use the minimum amount of force.

Planning

Project articles normally give precise instructions for building the circuit boards and undertaking the wiring but tend to be a bit "sketchy" when it comes to the mechanical side of construction. This is simply because most constructors prefer to "do their own thing" with this aspect of construction, rather than producing a clone of the original project. You normally have great freedom to do things the way you want to, but this also creates a golden opportunity to make a complete mess of things!

When building anything it is important to carefully plan things rather than just pressing on hoping that you can muddle through successfully. With the muddling through approach you are likely to produce the perfect project, apart from the fact there is nowhere to put the battery, you cannot adjust the volume control when the headphones are plugged in, or something of this nature.

Box Clever

There are numerous types of case available at present, but they break down into two general categories. These are simple boxes and instrument cases.

The cases of all-plastic construction are mostly simple plastic boxes consisting of a five-sided main moulding plus a removable lid or front panel. You can also obtain diecast aluminium and folded aluminium construction boxes, both of which take the same general form as the plastic variety.

Boxes are fine for projects that require a small to medium size enclosure, but they are often a bit awkward

when applied to larger projects. For the bigger projects, and some smaller types, an instrument case is usually the more practical option. These vary considerably in design, but consist of something like a base section combined with front and rear panels, plus the lid and sides in another section.

Some cases of this type have removable front and rear panels which makes working on the panels very much easier. Instrument cases are mostly of all-metal construction, but there are a few plastic types, and plenty that have plastic outer casings plus metal front and rear panels.

Take Note

It pays to read the notes on construction very carefully before selecting a case. While it is normally possible to use any type of case you like provided it is big enough, there are sometimes other considerations. This is mainly where it is necessary to use a metal case for some particular reason.

Metal cases are sometimes required because the project uses power devices and a metal case helps to conduct heat away from them. More usually a metal case is needed to provide screening. This can be needed to prevent a sensitive project from picking up electrical interference such as mains "hum", or to prevent a circuit from radiating interference.

If the article specifies a certain type of case, such as a diecast aluminium type for its good screening properties, you should definitely follow the advice. Otherwise it is a matter of choosing one that is within your budget and is large enough to accommodate the project.

Simple boxes are much cheaper than instrument cases, and are perfectly adequate for most small projects. They tend to be awkward to use with larger projects that have numerous controls, sockets, etc., and for these it is probably worthwhile paying the extra for an instrument case.

Size Is Important

In theory it should be quite easy to work out whether or not a likely looking case will fit your latest project. Some measurements taken from the bits and pieces that will go into the case will give you a good idea of the minimum requirements, but even at this early stage you will have to give some thought to the general layout of the unit.

If you are lucky,

the catalogue entry for the case will give internal dimensions and not just the external size. If not, deducting about eight millimetres from the external dimensions usually provides figures that are quite close to the internal ones.

The real problem is that modern cases often have various internal obstructions, which effectively reduce the internal dimensions. These include mounting pillars and guide-rails for printed circuit boards (p.c.b.s), threaded pillars for the lid's mounting screws, and various mouldings that have no obvious purpose at all.

Plastic cases are the worst offenders, and I have encountered one or two that have so many internal lumps that it is difficult to fit anything into them. Even with simple two-part metal cases you have to allow for the fact that the fixing screws for the cover will each penetrate several millimetres into the case. It is easy to come up with a plausible locking layout that results in one of the fixing screws going straight into the battery or a circuit board.

Unless a project really does need to be as small as possible it is best to err on the side of caution and choose a case that seems to be slightly too large. Making projects small just for the sake of it makes construction difficult and may make the finished project awkward to use. Anyway, a case that initially seems to be slightly too large will probably turn out to be just about right when you start installing the components.

Before starting any drilling it is certainly a good idea to place the circuit board, battery, and any other large components inside the case to make sure that everything fits, and that nothing prevents the lid from fitting into place properly. Make careful measurements to ensure that you do not have controls and the circuit board vying for the same space.



A hand-drill is adequate for electronic project work, but a cordless power drill is probably the best option. Remember to keep it well charged!

Measured Approach

Before starting work on a case you have to finalise the overall layout for the unit and make any adjustments if necessary. With most projects there are few restrictions on the placement of the controls, etc. and it is just a matter of coming up with something that looks reasonably good and is ergonomic.

However, read the article carefully to see if there are any pitfalls to avoid. For example, with some projects it is important to keep input and output sockets well separated. Ignore this sort of advice and you can reasonably expect the finished unit to be erratic in operation, if it works at all.

Otherwise, it is just a matter of trying to keep things reasonably neat and avoiding the classic mistake of crowding the controls so close together that they are difficult to adjust. If necessary, relegate sockets to the rear of the unit to give more space for the controls or use smaller control knobs.

Things will be neater if the spacing between control knobs of the same size is kept constant, but it does not usually pay to be too mathematical when designing front panel layouts. The neatest layout is the one that looks the neatest in real life, and not the one that looks the best "on paper".

My favoured method is to place the control knobs onto the front panel, together with fixing nuts to represent things like toggle switches or panel l.e.d.s, so that you can see almost exactly what the finished project will look like. When everything looks right it is a matter of making some careful measurements so that a plan of the layout can be sketched out.

Making Your Mark

Having finalised and checked the layout it is then a matter of transferring it to the case. You will mainly be dealing with plastic and aluminium cases, both of which are relatively soft materials. There are actually some steel cases available, but these are best avoided unless you have proper facilities and the know-how to deal with them.

The softness of plastic and aluminium means that you have to be careful

not to scar the case for life when marking the centres of holes and cutouts. Indelible marks inside the case will not matter too much, but you have to be careful with the exposed sides of front and rear panels.

The softest of pencils (about 5B or 6B) will do the job quite well, as will some fibre-tipped pens. It is best not to use fibre-tipped pens having spirit-based inks on plastic cases as they can etch into them slightly.

The safest method is to cover the panel with paper held in place using double-sided tape or a water-based adhesive such as Pritt-Stick. It is then easy to make the marks with great precision, and they should be very clear. You can even use a computer drawing program to produce the design, and then fix the printout onto the panel.

Either way, the paper will give a degree of protection to the panel while you are working on it. The paper can be peeled away once the work has been completed, and any adhesive or bits of paper that remain are simply washed off. This method clearly involves a lot more work than marking straight onto the panels, but it is the one recommended for soft plastic cases which can otherwise be difficult to deal with.

With aluminium cases use a centre punch to mark the centres of all holes prior to drilling them. The indentation acts as a guide for the drill and makes accurate drilling much easier. An automatic punch is the best type to use, but a conventional punch and small hammer will do, provided you do not get carried away. Remember that aluminium panels buckle and distort quite easily.

Neither type of centre punch is a safe option when dealing with plastic cases, which could be shattered by the punch. It is still necessary to make an indentation to stop the drill bit from wandering, and this is best done using a hand bradawl or similar tool, using a minimum amount of pressure.

You are now ready to start the drilling and cutting. Several ways of dealing with large cutouts were covered in the previous "Techniques" (March '99 issue) article and this subject is something we will not consider here.

Most panel mounting components require round mounting holes of up to about 10mm in diameter, and do not require the use of any unusual tools. Plastics and aluminium are quite soft, which means that you do not need a powerful electric drill. In fact, a powerful electric drill is a bit "over the top" for project construction and can be rather unmanageable at times.

Plastic cases can actually start to melt if the drill bit rotates too fast, producing some very rough results. A hand-drill is perfectly adequate and much more controllable. Recently I have changed over to a cordless power drill, and these seem to be ideal for project construction.

Due to the softness of the materials you will be working on it is not essential to use top quality drill bits. As an emergency fill-in measure I bought a set of inexpensive drills from the local "Woollies" store a while back, and several dozen projects later they are still perfectly usable.

A Firm Hand

It is important to have the case or panel firmly fixed in place before you start drilling, and to have a piece of scrap timber, MDF, etc. under the work piece. You may be able to clamp everything into some form of vice, but it is usually a matter of using G-clamps to fix everything to the worktop.

Some clamps are kinder to panels and cases than are others, but if necessary use pads of kitchen towel to prevent the clamps from scratching the work piece. The backing piece will stop the drill from crashing through the completed holes and will also help to give "clean" holes.


However, drilling hardly ever gives perfect results and a certain amount of de-burring will usually be required. There are tools specifically for this purpose, but a miniature round file ("needle" file) will do the job quite well.

With soft materials such as plastic and aluminium the small blade of a penknife is also very effective, but always proceed carefully when using a sharp tool. With the holes and cutouts completed it is time to fit everything into the case and complete the wiring.



An automatic centre punch (top) is ideal for use with aluminium but should not be used with plastic. Instead use a sharp bradawl or stiletto (bottom) with no more than moderate pressure.

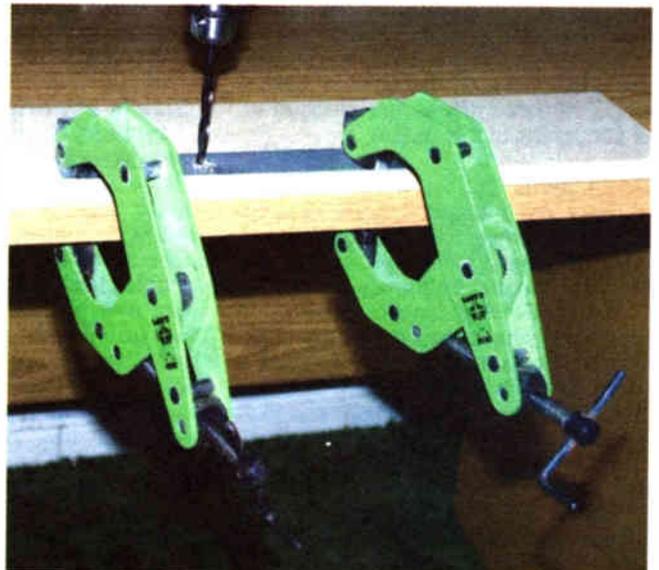(Right) It is dangerous to work on a case or panel that is not firmly fixed in place. Clamp the workpiece and a backing board to the workbench.



CONTROL & ROBOTICS from Milford Instruments

BASIC Stamps-

- Re-Programmable
- BASIC language
- RS232 Serial ports
- 8 or 16 I/O lines
- SPI/DTMF
- Fast development



Scenix

- Fastest 8-bit micro
- 50MIPS
- Flash Eprom
- 18/28 pins
- PIC16C5x pin replacement




Serial LCDs

- RS232 Serial interface
- 2x16 to 4x40
- Simple 3-pin connection
- Integral Keypad option
- Large Numerics option
- Driver chips available for OEM use



Robotics

- Humanoid
- 5-Axis Arm
- Walking Insect

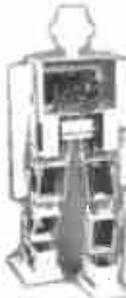

3-Axis Machine

- Stamp 2 based
- Drills PCBs
- 3-Axis movement
- Stepper drive
- 4 thou resolution
- Win 3.1 software



Servo Controller

- Control up to 8 servos
- RS232 Commands



IR Decoder

- Uses any remote
- 7 digital outputs
- Toggle/momentary
- Re-Programmable

Milford Instruments 01977 683665 www.milinst.demon.co.uk

Bell College of Technology
Almada Street
Hamilton ML3 0JB
Tel: 01698 283100
Fax: 01698 459790



Make your expertise pay!

In today's world you need qualifications to obtain and keep employment. Our open learning courses make obtaining those qualifications as convenient as possible.

Choose from our dozens of SQA accredited units, either singly to update your skills or as a group to obtain a Higher National Certificate.

- Learn at your own pace in your own home
- Support from professional engineers via phone, FAX and the Internet
- Courses from introductory Bridging Modules to HNC Electronics
- Units from Programmable Logic Controllers to Engineering Computing

DON'T DELAY - we are waiting to hear from you.

Contact: Laura Murdoch, Open Learning Co-ordinator

Tel: 01698 283100 Extension 214.

E-mail: l.murdoch@bell.ac.uk

Web: <http://floti.bell.ac.uk/openlearning>

Member of the British Association for Open Learning
Preview Centre for Financial Times Management



Bell College of Technology
is a registered charity No. SC 021170
providing quality Higher Education and
training opportunities for all.



Transformers

100 VA to 100 kVA and beyond
Single Phase & 3 Phase
Mains Transformers
Auto-transformers
Inverter Transformers
Single to 3 Phase Converters
Standard or Custom Wound
Next day delivery normally
available - even on custom wound!

Call us with your custom transformer requirements or fill out the Custom Transformer Design Form on our Web Site for a quotation.

Single Phase Transformers

Standard Primaries	Standard Secondaries
0-115 V, 0-115 V	0-6 V, 0-6 V
0-380-400-415 V	0-9 V, 0-9 V
	0-12 V, 0-12 V
Standard Ratings	0-15 V, 0-15 V
100 VA, 200 VA,	0-18 V, 0-18 V
250 VA, 500 VA,	0-24 V, 0-24 V
750 VA, 1 kVA,	0-55 V, 0-55 V
1.5 kVA, 2.2 kVA,	0-115 V, 0-115 V
3 kVA, 4 kVA,	
5 kVA, 6 kVA,	
7.5 kVA, 10 kVA,	
15 kVA, 20 kVA	

5 - 15 V Regulated 30 A D.C. Power Supply

230 V mains input
Digital Volt and Ammeters
Full Overload Protection
Variable Output
Current limiting

Only £299.99

inc. VAT and delivery
(UK mainland only)

The CCD Camera Cookbook

Build this amazing cooled CCD camera for deep-space imaging. A complete design with full constructional details is provided in this American book. Full support is offered by a group of British companies for UK constructors, including a completely re-vamped PSU design for European mains supplies. Visit our Web Site for circuit ideas, data, components, high energy xenon flash tubes and lots more.

www.third-millennium.demon.co.uk

JEM Electronics

0870 787 1708

E&OE

NEW SPECIAL OFFERS

Amiga genlock pcb (uncased) for tiling videos if it has a 23pin D lead to plug into the computer and pot pins for composite video in and out. When no video input is connected the normal computer display is shown on the composite video out when the video input is added the white areas on the screen are replaced by the video image. The pcb is powered from the computer. £19.98

WATCH SLIDES ON TV "Liesegang dial" automatic slide viewer with built in high quality colour tv camera, composite video output with a BNC plug. In very good condition with few signs of use. £198.00

Board cameras all with 512x582 pixels 4.4x3.3mm sensor with composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts and require 10 to 12vdc power supply.

47MMR size 60x36x27mm with 6 infra red leds (gives the same illumination as a small torch would). £50.00+vat = £58.7540

MP size 39x38x23mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. £57+vat = £66.98

40MC size 39x38x28mm camera for 'C' mount lens this gives a much clearer picture than with the small lenses. £68.79

Standard 'C' mount lens F1.6 16mm for 40MC £26.43+vat = £31.06

Waterproof camera stylus £109.00 or 10+£89.32+vat = £104.95

DTA30 Hand held transistor analyser It tells you which lead is the base, the collector and emitter and if it is NPN or PNP or faulty. HMA20 hand held MOSFET analyser identifies gate drain and source and if P or N channel. DTA30 & HMA20 £38.34 each

DCA50 component analyser with led readout identifies transistors mosfets diodes & LEDs lead connections. £69.95

Speaker cabinets 2 way speaker systems with speaker dia 15" 12" 8" power rating 250WRMS 175WRMS 100WRMS impedance 8ohm 8ohm 8ohm freq. range 40hz-20khz 45hz-20khz 80hz-20khz sensitivity(1W/1M) 97db 94db 92db size in mm 500x720x340450x400x345 315x460x230 weight 21.1kg 16.8kg 7.4kg price each for black vinyl coating £139.95 £99.99 £54.94 grey full coating £159.97 £119.97 £64.99 (**=not normally in stock allow 1 week for delivery)

Power amplifiers 19" rack mount with gain controls STA150 2x160WRms (4ohm load) 14kg £202.11 STA300 2x190WRms (4ohm load) 11kg £339.00 STA900 2x490WRms (4ohm load) 15kg £585.00 LEDs 3mm or 5mm red or green 7p each yellow 11p each cable ties 1p each £5.95 per 1000 £49.50 per 10,000

Rechargeable Batteries AA(HP7) 500MAH £0.99 AA 500MAH with solder tags £1.55 AA 950MAH £1.75 (HP11) 1.2AH £2.80 C-2AH with solder tags £3.80 (HP2) 1.2AH £2.80 D 4AH with solder tags £4.95 PPS 8.4V 110MAH £4.95 1/2AA with solder tags £1.55 Sub C with solder tags £2.50 AAA (HP16) 180MAH £1.75 1/3 AA with tags (phosphate) £1.95 Nickel Metal Hydride AA cells high capacity with no memory. If charged at 100ma and discharged at 250ma or less 1300MAH capacity (lower capacity for high discharge rates) £2.95 or £200.00 for a box of 30

Special offers please check for availability stock of 4 42x16mm nicad batteries 171mmx16mm dia with red & black leads 4.8v £5.95 5 button cell 6V 280MAH battery with wires (Varta CR2500K) £2.45 Orbital 966 battery pack 12v 1.60AH contains 10 sub C cells with solder tags (the size most commonly used in cordless screwdrivers and drills 22 diax42mm tall) it is easy to crack open and was manufactured in 1994. £0.45 GAA FET low leakage current 58873 £12.95 each £9.95 10+ 7.95 100+ BC547A transistor 20 for £1.00 PL952 UHF limiting amplifier LC 16 surface mounting package with data sheet £1.95 DC-DC converter Reliability model V12P5 12v in 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50 Airpax AB2903-C large stepping motor 14v 7.5 step 270hm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 30


Polyester capacitors box type 22.5mm lead pitch 0.9uf 250vdc 18p each 14p 100+ 9p 1000+ 1uf 250vdc 20p each 15p 100+ 10p 1000+ £1.95 100+ Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch 32x29x17mm case 75p each 60p 100+ Philips 123 series solid aluminum axial leads 33uf 10v & 2.2uf 40v 40p each, 25p 100+ Solid carbon resistors very low inductance ideal for RF circuits 270hm 2W, 680hm 2W 25p each 15p each 100+, we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors, please send SAE for list: MX180 Digital multimeter 17 ranges 1000vdc 750vac 2kMohm 200mA transistor Hfe 9v and 1.5v battery test £3.95 Hand held ultrasonic remote control £3.95 CV2486 gas relay 30x10mm dia with 3 wire terminals will also work as a neon light £20 each or £8.50 per 100

Verbatim R300NH Streamer tape commonly used on nc machines and printing presses etc. It looks like a normal cassette with a slot cut out of the top. £4.95 each (£3.75 100+) Heatsink compound tube £0.95 HV3-2405-E5 5-24v 50mA regulator ic 18-264vac input 8 pin DIN package £3.49 each (100+ 2.25)

All products advertised are new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors kits, rechargeable batteries, capacitors, tools etc always in stock. Please add £1.95 towards P&P (orders from the Scottish Highlands, Northern Ireland Isle of Man, Isle of Wight and overseas may be subject to higher P&P for heavy items). VAT included in all prices.

JPG ELECTRONICS

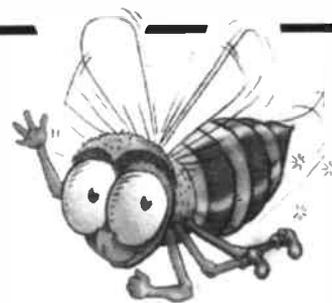276-278 Chatsworth Road
Chesterton S40 2BH
Access Visa Orders.
Tel: (01246) 211202 Fax: (01246) 550959
Callers welcome 9.30am to 5.30pm
Monday to Saturday



PhizzyB COMPUTERS

Part 7: Equipping the PhizzyBot with Optical Sensors

Clive "Max" Maxfield and Alvin Brown

HI THERE! Last month, as you no doubt recall, we created a rather cunning program to detect when the PhizzyBot collided with something and to respond in an appropriate manner. This program was designed to be user-friendly, such that it was relatively easy to

specify, read, and modify the sequences of actions performed by the PhizzyBot, thereby facilitating our ability to experiment with different sequences. This month we get PhizzyBot involved in measured space travel, and add to its senses by giving it eyes – six of them.

THE ACTIONS and movements discussed last month were specified using constant declarations like `STOP`, `FORWARD`, `TURN_L` (turn left), and `SPIN_CW` (spin clockwise). However, the "units" associated with these actions were always those of time (measured in tenths of seconds).

WAITS AND MEASURES

Associating actions with units of time made sense in the context of the way we developed our program. But when you come to think about it, a command like "Go forward for three seconds" isn't perhaps quite as useful as being able to present an instruction in the form: "Go forward for fifteen centimetres".

Similarly, the command "Spin clockwise for two seconds" doesn't convey the same intent as "Spin clockwise for ninety degrees". Well, perhaps it does convey the same intent (if you want to be pedantic), but it is certainly less people-friendly when it comes to working out exactly what's going to happen.

So what we need is a technique that will allow us to replace delay values with units like centimeters and degrees. In order to do this, we first need to ascertain the relationship between time and distance travelled. One way to do this would be to mark out a specific distance (say three metres) and time how long the PhizzyBot takes to travel this distance.

Alternatively, you could easily modify last month's program such that clicking Switch 1 will cause the PhizzyBot to travel forwards for some specified time (say ten seconds) and measure the distance travelled.

Whichever technique you choose to use, you should repeat the process a number of times and average the results to compensate for experimental errors. In the case of our PhizzyBot, it took approximately fifteen seconds to travel three metres. This equates to five seconds per metre, or 0.5 seconds to travel ten centimetres, or 0.1 seconds to travel two centimetres.

As 0.1 seconds is the smallest interval we can measure with our current program, this means that the smallest distance we can instruct the PhizzyBot to travel is two centimetres. (In order to achieve finer control, we could modify the program, or change the gearing on the motors to make them slower, or reduce the diameter of the PhizzyBot's wheels, or . . .)

But let's stick with what we've got. One

thing we could do would be to create a whole host of constant declarations as follows:

```
_2cm:      .EQU 1
_4cm:      .EQU 2
_6cm:      .EQU 3
_8cm:      .EQU 4
:
etc.
```

Remember that label names cannot commence with a number, so we can't use 2cm, 4cm, 6cm, and so forth, but labels can start with an underscore as shown above. So this would allow us to specify action sequences in the form:

```
FORWARD,  _4cm
BACKWARD, _8cm
:
etc.
```

(We've omitted the labels and `.BYTE` statements associated with these action sequences for clarity and space considerations.) One problem with this technique is that it requires us to create one heck of a lot of constant declarations to cover every time value from 1 to 255. One alternative would be to just create one constant declaration (say `_2cm .EQU 1`) and to then use expressions to modify this in the action sequences, for example:

```
FORWARD,  10 * _2cm
```

That's right, we can use expressions in these statements, as you doubtless recall from reading Appendix D from *The Official Bebopter Microprocessor Databook*.

In reality we might create a small number of constant declarations to cover any "standard" values like `_10cm`, `_20cm`, and so forth, and to then modify these with expressions as required.

IN A SPIN

Now set the PhizzyBot to spinning clockwise, and time how long it takes to make ten complete revolutions. As before, repeat the process a number of times and average the results to compensate for experimental errors.

In our case, it took our PhizzyBot approximately 25 seconds to complete ten revolutions, which equates to 2.5 seconds per revolution (360 degrees). Remembering that the smallest interval we can measure with our

current program is 1/10 of a second, this means that the smallest rotation we can instruct the PhizzyBot to perform is 14.4 degrees (which we can "round up" to 15 degrees for the sake of this discussion).

So once again we could create some constant declarations along the lines of:

```
_15deg:    .EQU 1
_30deg:    .EQU 2
_45deg:    .EQU 3
_60deg:    .EQU 4
:
etc.
```

In fact, in this case we really only have twelve labels to declare to cover 15, 30, 45, 60, 75, 90, 105, 120, 135, 150, 165, and 180 degree increments, because we can use these declarations as assignments to both clockwise and anticlockwise spin commands. (And we can always use expressions to modify these constants if we wish; for example, `4 * _180deg` will instruct the PhizzyBot to perform two full revolutions.)

NO HISTORY

There is an old saying that those who fail to learn the lessons of history are doomed to repeat them (this is particularly true in the case of history courses at high school)! One of the limitations of last month's program is that it had no sense of history, which means that the PhizzyBot has no knowledge of anything that's happened before the current time.

The end result is that the PhizzyBot could easily get itself stuck in a repetitive "loop", such as endlessly bouncing back and forth between two closely spaced objects. If the program were modified to maintain some record of what had gone before, then we might be able to circumvent this sort of thing.

As a simple example, if the program had some method of checking its last few moves, it could essentially say, "Hmmm, I seem to be cycling between the same two action sequences, perhaps I should try something else and see if that gets me out of this jolly awkward predicament".

Not that we're going to tell you how to do this, you understand – we've got too much new stuff to be getting on with. The only reason we're mentioning this here is that we thought that you might be desperately looking for something to do this coming weekend . . .

Listing 1

```

### Start of Constant Declarations
LSENSORS: .EQU $F011      # Light Sensors
MGRAPH:   .EQU $F030      # Motor bargraph display
TGRAPH:   .EQU $F031      # Timer bargraph display
MCONTROL: .EQU $F032      # Motor controller board
DELCONST: .EQU $0C        # Delay constant value
STOP:     .EQU %00000000  # Stop motors
FORWARD:  .EQU %00001010  # Go forward
SPIN_CW:  .EQU %00000110  # Spin clockwise
SPIN_ACW: .EQU %00001001  # Spin anticlockwise
_lsec:    .EQU 10         # Delay = 1 second
_10cm:    .EQU 5          # Delay = 10 centimeters
_30deg:   .EQU 2          # Delay = 30 degrees
_60deg:   .EQU 4          # Delay = 60 degrees
_90deg:   .EQU 6          # Delay = 90 degrees
_120deg:  .EQU 8          # Delay = 120 degrees
_150deg:  .EQU 10         # Delay = 150 degrees
_180deg:  .EQU 12         # Delay = 180 degrees
### End of Constant Declarations

### Start of main program initialization
.ORG $4000      # Start of program
BLDSP $4FFF     # Load stack pointer
### End of main program initialization

### Start of Main Program Body
### End of Main Program Body

### Start of Subroutines
### End of Subroutines

### Start of Temp Locations and Data Values
GOFLAG: .BYTE $01      # Flag (0=stop, 1=go)
TVALUE: .BYTE          # Main timer temp value
TEMPX:  .2BYTE $0000   # Temp index register
### End of Temp Locations and Data Values
.END

```

COMING INTO THE LIGHT

But we digress . . . In Alan Winstanley's construction article in this issue, he describes how to use a set of six light-dependent resistors (l.d.r.s) as the basis for a rudimentary optical sensor for the PhizzyBot.

For our part, we are going to create a simple program that utilizes this optical sensor to make the PhizzyBot act the role of a "Moth-Bot". That is, a Bot that's attracted to the light from a torch (or a flashlight as they would have it in the vernacular of the good old US-of-A, which is where we Phizzy authors happen to find ourselves at this moment in time).

SKELETON PROGRAM

As for last month, the first thing we're going to do is to create a skeleton (framework) program, which we'll develop as we go along. Invoke your PhizzyB Simulator, activate the assembler, and enter the program shown in Listing 1.

Note that the values you assign to the `_10cm`, `_30deg`, `_60deg`, and so forth labels to control your PhizzyBot may be different to the ones shown here, because the gearing of your motors and the size of your wheels may differ from ours (bounce back to the In a Spin section earlier for more details).

Before you do anything else, save this skeleton program as `ffxp1.asm`. Now consider the Constant Declarations section at the beginning of the program. The `LSENSORS` label will be used to associate our new light sensor device with the input port at address `$F011` (so make sure you connect the little rascal to this port).

Next we're going to use the PhizzyB's on-

board 8-bit l.e.d. bargraph display to indicate the value we're driving to the motors. Thus, we equate the `MGRAPH` label to the address of this output port, which is `$F030`.

As for last month, we're also going to connect the 8-bit l.e.d. bargraph display we created in Part 2 (Dec '98) to the output port at address `$F031`, and then use this to reflect the current value in the timer. Thus, we equate the `TGRAPH` label to the address of this output port.

Also, we're going to connect our motor controller board from Part 5 (Mar '99) to the output port at address `$F032`. Hence the `MCONTROL` declaration.

The `DELCONST` label, which is used to persuade our timing subroutine to loop around

for 1/10 of a second, is assigned a value of `$0C` (12 in decimal). (We determined the value of `DELCONST` by trial and error as discussed in Part 5).

The `STOP`, `FORWARD`, `SPIN_CW`, and `SPIN_ACW` labels are assigned values that can be used to control the PhizzyBot's motors so as to stop the Bot, drive it forward, spin it clockwise, or spin it anticlockwise, respectively. Ideally we would use the multi-label approach we introduced last month: assigning these values directly is a "quick and dirty" solution, but it serves our purposes here.

The remaining constant declarations (`_lsec`, `_10cm`, `_30deg`, `_60deg`, and so forth) have been discussed in excruciating detail above. The rest of the skeleton program consists of two initialization statements, the reserving of some temporary locations, and some comments, all of which have been discussed into the ground earlier in this series. So, without further ado, let's leap into the fray!

TIMER SUBROUTINES

In a moment we're going to leap into the really interesting stuff, but before we do we need to add the timer routines shown in Listing 2 (add these between the "Start and End of subroutines" comments in the skeleton program).

These routines are exactly the same as last month, so we won't spend any time discussing them here. The only point to note is the test of the `GOFLAG` label at the beginning of the `TIMER` routine. We really aren't going to have any use for the `GOFLAG` label this month, but we will leave it (and the test) where it is, because we don't want to do anything to affect the delays in the `TIMER` routine. Note that we pre-assigned a value of `$01` (the "go" value) to the `GOFLAG` location when we declared it at the bottom of Listing 1, so we won't have to concern ourselves with this flag anymore.

SIMPLE TEST PROGRAM

Before you do anything else, make sure that the new light sensor device is plugged into the PhizzyB's input port at address `$F011`. Also ensure that this device is oriented on top of the PhizzyBot such that the l.d.r. driving bit `IP0` of the input port is pointing towards the front of the Bot (Fig.1).

Now, add the following statements between the two comments saying Start and End of main program body in your skeleton program:

Listing 2

```

=== Start of "Main Timer" Routine
TIMER:   STA   [TVALUE]      # Store original count
TLOOPA:  JSR   [ONETENTH]    # Call 1/10 Sec loop
        LDA   [GOFLAG]      # Load flag
        JZ    [TRETURN]     # Jump if flag=0
        LDA   [TVALUE]     # Load count value
        DECA                # Decrement it
        STA   [TVALUE]     # Store it
        STA   [TGRAPH]     # Store it to LEDs
        JNZ   [TLOOPA]     # Loop again if !=0
TRETURN: RTS                 # Exit subroutine
=== End of "Main Timer" Routine

=== Start of "1/10 Second" Routine
ONETENTH: LDA   DELCONST    # Load count value
OTLOOPA:  DECA                # Decrement it
        JNZ   [OTLOOPA]    # Loop again if !=0
OTRETURN: RTS                 # Exit subroutine
=== End of "1/10 Second" Routine

```

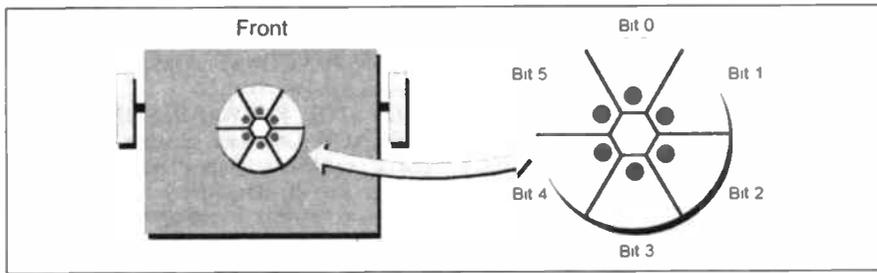


Fig. 1. Ensure that the l.d.r. driving port bit IPO is pointing towards the front.

```

LOOP:      LDA [LENSORS]
           AND %00111111
           STA [MGRAPH]
           JMP [LOOP]

```

All this program does is to loop around reading from the port connected to the light sensors and writing to the 8-bit l.e.d. bargraph display connected to output port \$F030 (label MGRAPH) on the PhizzyB. However, it is worth taking special note of the AND instruction, which is used to "mask out" the top two (unused) input port bits and force them to zero values.

The way the sensor circuits work is that if an l.d.r. is not illuminated it will have a high resistance, so the tap (connection) point between the 22kΩ resistor and 10kΩ potentiometer will be pulled up towards a logic 1 (+5V) value. This will be inverted by IC1 to present a logic 0 to the input port.

Similarly, if an l.d.r. is illuminated, its resistance will fall and the tap point will be pulled down towards a logic 0. This, in turn, will be inverted by IC1 to present a logic 1 to the input port. The end result is that any of the l.d.r.s that are illuminated will be "seen" as logic 1 values by the PhizzyB.

In order to test this, assemble your program, download the resulting fexp1.ram file to the PhizzyB, and set the program running. Assuming that you've calibrated the sensors as described in Alan's constructional article, then all of the l.e.d.s on the bargraph display should initially be off. Now shine a light at each of the l.d.r.s in turn, and ensure that the corresponding l.e.d. lights up.

(Note that even if you don't have a real PhizzyB and PhizzyBot, you can still perform all of the experiments described in this article on the PhizzyB Simulator by presenting the appropriate values to input port \$F011 and observing the results.)

When you've satisfied yourself that everything is working as it should, reset the PhizzyB (and/or the PhizzyB Simulator) and proceed to the next section.

BLINDED BY THE LIGHT

Although you may not have fully appreciated this, the way in which we implemented last month's "Collision Detection" program was based on the assumption that only one microswitch would be triggered at a time. However, in the case of our new light sensor device, it is more than possible for multiple l.d.r.s to be activated simultaneously (Fig.2).

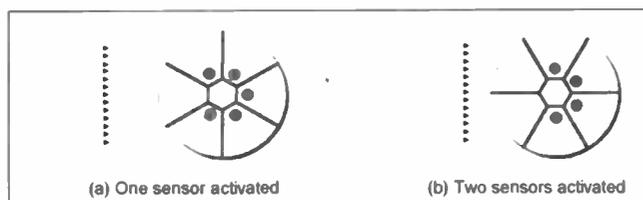


Fig. 2. Multiple l.d.r.s may be activated simultaneously.

This article is based on the assumption that either one sensor will be activated as shown in Fig.2a, or two adjacent sensors as shown in Fig.2b. However, depending on how you construct your sensor housing (including the positioning of the sensors and the lengths of the internal dividing "spokes"), it might be possible for your torch (flashlight) beam to activate one, two, or even three adjacent sensors.

In fact, we also have to consider the fact that stray light beams from external sources may activate one or more sensors (e.g. the sun shining through a window). And it's not beyond the bounds of possibility that a prankster may be sabotaging your experiments by surreptitiously shining their own light source at the PhizzyBot from behind the sofa...

So although we're only going to focus on

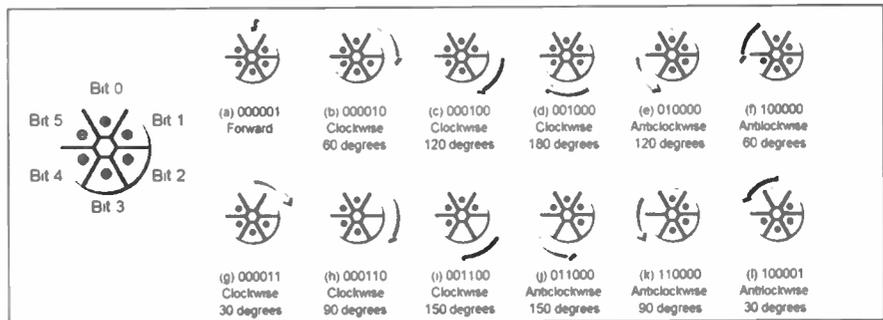


Fig. 3. All 12 of the one and two (adjacent) active sensor cases.

the cases involving one or two (adjacent) sensors, our program has to accommodate the fact that any combination of l.d.r.s may be illuminated. As we have six sensors, and each may be in one of two states (On or Off), we actually have $2^6 = 64$ different patterns of 0s and 1s to deal with. (This is one reason why we didn't use eight sensors, because we didn't want to have to contend with $2^8 = 256$ different patterns). But fear not, because this isn't going to be as tricky as you might suspect...

$2^6 = 64$ EEEKKK!

The first thing we need to do is to create 64 labels just before the "End of Temp Locations and Data Values" comment in Listing 1. Each of these labels will commence with the characters "LS" (standing for "light sensors") followed by a 6-bit binary code. Each label will also be followed by a

.BYTE statement and associated values as shown in Listing 3 (we'll discover the purpose of these values in the not-so-distant future).

As we see from this listing, the binary codes associated with these labels follow a standard binary count sequence. This should be easy enough, but just in case you're a little unsure, here's a simple trick you can use to create these entries.

Start off by entering the first line for label LS000000 (including the .BYTE STOP, _lsec portion), then copy this line 64 times. In order to edit these 64 lines such that they reflect a binary count, commence by making the least-significant (bit 0) column alternate between 0 and 1, for example:

```

LSxxxxx0: etc
LSxxxxx1: etc
LSxxxxx0: etc
LSxxxxx1: etc
LSxxxxx0: etc
LSxxxxx1: etc
etc

```

Now make the bit-1 column alternate between two 0s and two 1s, for example:

```

LSxxxx00: etc
LSxxxx01: etc
LSxxxx10: etc
LSxxxx11: etc
LSxxxx00: etc
LSxxxx01: etc
etc

```

Continue with the bit-2 column alternating between four 0s and four 1s; the bit-3 column alternating between eight 0s and eight 1s; the bit-4 column alternating between sixteen 0s and sixteen 1s; and finally the bit-5 column starting with thirty-two 0s and ending with thirty-two 1s (phew!).

In reality our program only needs the first of these labels as we'll see. The other labels are intended for us so that we can see what we're doing.

WHICH WAY TO TURN?

As we previously noted, we're only going to focus on the cases where one or two (adjacent) sensors are activated (Fig.3.)

As there are 360 degrees in a circle, each of our six sensors is responsible for a 60-degree

Listing 3

```

##543210 # Bit numbers
LS000000: .BYTE STOP, _lsec # Stop & wait
LS000001: .BYTE STOP, _lsec # Stop & wait
LS000010: .BYTE STOP, _lsec # Stop & wait
LS000011: .BYTE STOP, _lsec # Stop & wait
:
:
:
LS111101: .BYTE STOP, _lsec # Stop & wait
LS111110: .BYTE STOP, _lsec # Stop & wait
LS111111: .BYTE STOP, _lsec # Stop & wait
### End of Temp Locations and Data Values

```

Listing 4

```

LS000001: .BYTE FORWARD,    _10cm
LS000010: .BYTE SPIN_CW,    _60deg
LS000011: .BYTE SPIN_CW,    _30deg
LS000100: .BYTE SPIN_CW,    _120deg
LS000110: .BYTE SPIN_CW,    _90deg
LS001000: .BYTE SPIN_CW,    _180deg
LS001100: .BYTE SPIN_CW,    _150deg
LS010000: .BYTE SPIN_ACW,   _120deg
LS011000: .BYTE SPIN_ACW,   _150deg
LS100000: .BYTE SPIN_ACW,   _60deg
LS1J0001: .BYTE SPIN_ACW,   _30deg
LS110000: .BYTE SPIN_ACW,   _90deg
    
```

arc. If only the forward (bit 0) sensor is active, we want the PhizzyBot to trundle forwards (Fig.3a). If only the bit 1 sensor is active (Fig.3b), we want the PhizzyBot to spin clockwise for 60 degrees, which should suffice to align the bit 0 sensor with the light source again. And so forth for the remaining one-sensor cases.

Similarly, if both the bit 0 and bit 1 sensors are active (Fig.3g), and if we assume that the light source is located exactly between them, then we want the PhizzyBot to spin clockwise for 30 degrees, which should serve to bring the bit 0 sensor in line with the light source once more. And so forth for the remaining two-sensor cases.

Fortunately, we've already got everything in place to easily accommodate these requirements. All we have to do is modify the assignments to the twelve labels associated with these cases as shown in Listing 4.

MAIN PROGRAM BODY

Delete our earlier test program statements from between the two comments saying "Start and End of main program body", and replace them with the code shown in Listing 5. Unlike last month, this program is going to be "easy-peasy!"

As we see, the main loop for this program is really small. First of all we read the value on the sensors and store it in the accumulator. Next we use an AND instruction to mask out the two MS bits, which aren't connected to any sensors (this masking operation ensures that these two bits don't confuse us with unexpected values).

We know that each of our LSxxxxxx labels has two bytes associated with it, so we shift the value in the accumulator left one bit, which is the same as multiplying it by two (this technique was discussed in the bonus article accompanying Part 3).

Now this is the cunning part, because we save this "Sensor × 2" product in the LS byte of our 2-byte TEMPX value, then we use a BLDX instruction to load this value into our index register. Next we use an indexed addressing mode instruction LDA [LS000000,X]. This loads the accumulator with the data byte it finds at the address calculated by adding the address of label LS000000 with the contents of the index register.

As an example, let's assume that the pattern read from the sensors was 000110 (6 in decimal). Shifting this left results in 001100 (12 in decimal). Remember that each of our LSxxxxxx labels has two bytes associated with it, so adding a value of 001100 to the address of label LS000000 will give us the address of label LS000110, which is what we wanted in the first place. (We know that this

seems a bit convoluted at first, but once you've wrapped your brain around it, you will come to realize that this is actually rather elegant... or not as the case might be.)

We know that this first data byte is a "motor control action", so we store it to the i.e.d.s displaying the state of the motors and also to the output port driving the motor controller device.

We now increment the index register, load the next data byte (which is the "delay"), and jump to the TIMER subroutine to wait for this delay to time out. Finally we jump back to the beginning of the loop and do it all again.

If you return to the LSxxxxxx labels, you can now see that whenever no sensors are active (or if an unexpected combination is active), the program will simply stop the motors and wait for a second. After this short delay, it will recheck the sensors to see if anything has changed.

Thus, when left to "roam wild and free", the PhizzyBot should hunker down and wait for you to shine a light at it. As soon as it "sees" the light, it should spin around to orient itself towards the light and race towards it. If the light should be extinguished, the PhizzyBot will stop where it is and wait for the light to reappear.

Save this new program as ffexp2.asm, assemble it, download the resulting ffexp2.ram file to your PhizzyBot (or load it into your PhizzyB Simulator) and experiment away with gusto and abandon!

MORE PRECISION

One thing that may have struck you is that the "visual resolution" of the PhizzyBot leaves something to be desired. This is because we only have six sensors, each of which handles a 60-degree field of view (Fig.4).

This means that our program as described above can't guarantee that the PhizzyBot will trundle directly towards a light source. Instead, the PhizzyBot may initially head off at a slight tangent until the light hits a second sensor, at which point the PhizzyBot will detect its error and attempt to correct it (Fig.5).

Suppose we wanted to make the PhizzyBot more accurate using just these six sensors –

Listing 5

```

LOOP: LDA  [LSENSORS]    # Load ACC from sensors
      AND  %00111111    # AND to mask unused bits
      SHL                    # Shift ACC left 1 bit
      STA  [TEMPX+1]    # Store to LS byte of X
      BLDX [TEMPX]
      LDA  [LS000000,X]  # Get action
      STA  [MGRAPH]     # Store to LEDs
      STA  [MCONTROL]   # Store to motor control
      INCX                # Increment index reg
      LDA  [LS000000,X]  # Get delay
      JSR  [TIMER]      # Call timer subroutine
      JMP  [LOOP]       # Do it all again
    
```

how could we do this? Well first of all we'd have to modify our TIMER subroutine to measure smaller units of time. For example, we know that 1/10 of a second equates to the PhizzyBot spinning approximately 15 degrees. Thus, if we could time delays in 1/100 of a second increments, then the PhizzyBot could be instructed to spin in increments of 1.5 degrees.

Of course our current subroutine has a maximum delay of $255 \times 1/10$ of a second, which equals 25.5 seconds. If we started counting in 1/100 of a second, our maximum delay would only be 2.55 seconds, which would be somewhat limiting. One way around this would be to use two bytes to specify the delay. Two bytes can represent 0 through 65,535 in decimal, which gives us a maximum delay of $65,535 \times 0.01$ seconds = approximately 655 seconds (almost 11 minutes), which should be more than enough for our purposes.

Assuming that we had the ability to time in 1/100 second intervals, then we could use this to improve the "visual resolution" of the PhizzyBot. When a light was first detected, we could spin the PhizzyBot until its bit 0 sensor was activated. Next we could spin the PhizzyBot clockwise in 1.5 degree increments until the bit 0 sensor went inactive and/or the bit 5 sensor became active. This gives us one "end" of the bit 0 sensor's field of view.

Next we could spin the PhizzyBot anti-clockwise in 1.5 degree increments using the bit 0 and bit 1 sensors to detect the other end of the bit 0 sensor's field of view. Our program could count how many 1.5 degree

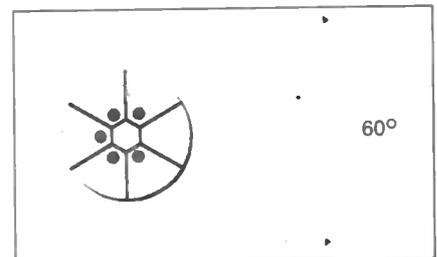


Fig.4. Each sensor covers a 60-degree arc.

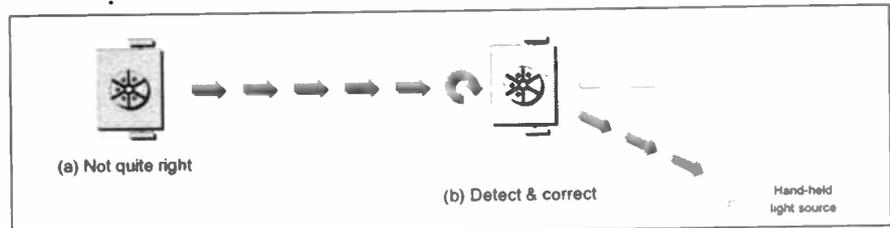


Fig.5. The program may "hunt and seek" a little.

increments it took to go from one end to the other. Now all we would have to do would be to spin the PhizzyBot clockwise for half of this number, which should leave it pointing almost directly at the light source.

MOTHBOT VERSUS ROACHBOT

Our program has so far focused on making the PhizzyBot act the role of a MothBot that's attracted to the light. Another simple experiment you could perform would be to modify this program such that it now acts like a RoachBot that scurries away from the light and

furtively tries to hide itself away in dark places.

Now what we'd like you to do is to combine the program we've just discussed here with the program from last month (Part 6). Your mission (should you decide to accept it) is to create a program that allows the PhizzyBot to meander around the room bumping into things and responding appropriately. But as soon as it "sees" a light source, it should stop whatever it was doing and hurl itself towards the light at full pelt.

NEXT MONTH

Sad to relate, next month is the final issue


in this PhizzyB series (little tears are rolling down our cheeks as we pen these words and our lower lips are all aquiver). But turn that frown upside down into a smile, because in the final issue we'll be discussing all sorts of exciting experiments you can perform with your PhizzyB Simulator, PhizzyB, and PhizzyBot, plus we'll be inviting you to contribute your own input/output device suggestions to the *Ingenuity Unlimited* column.

So "keep on trucking" with your PhizzyBot, and we'll be with you again next month.

Understanding Computers

PhizzyB COMPUTERS

Construction – PhizzyBot Eyes

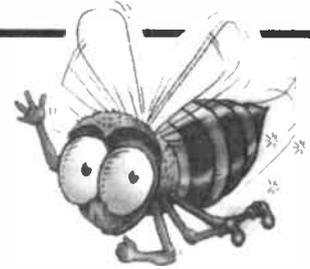

Alan Winstanley

Six eyes give PhizzyBot a whole new view of the world and open up a range of possibilities.

LAST month we described a simple method of adding "feelers" to the PhizzyBot computer-controlled motorised platform. By using a series of microswitches around the periphery of the PhizzyBot, it can detect the presence of an obstacle and, under the control of a computer program, the PhizzyBot can avoid it by spinning, turning or reversing.

As usual, the control program was fully detailed in the Tutorial, and it could be developed and refined on a Windows-compatible PC using the PhizzyB Simulator software on CD-ROM: the PhizzyB is programmable via the PC's serial port and programs can be uploaded to the PhizzyB in a trice. Many of the demonstrations could also be followed on-screen without the use of the hardware PhizzyB, although you'll be missing a heck of a lot of good fun in the process!

PRACTICALLY FINAL

This month sees the final practical project related to the unique PhizzyB Computers series. In the accompanying tutorial article, Max and Alvin describe further techniques related to controlling the direction and travel of the PhizzyBot buggy. We show how the computer program used by the PhizzyBot can be refined to offer a greater degree of control of the PhizzyBot's motorised movements.

One further tutorial will be presented next month to "wrap" the series and then it is hoped that readers will develop further applications, circuitry and programs for the powerful PhizzyB computer.

Apart from "doing your own thing", readers may rest assured that help will continue to be available to those picking up this series for the first time, even when the published series has drawn to a close. You

can write to the authors c/o the Editorial address or by E-mail – see the details at the end of this article.

MULTIPLE EYES

The constructional details which follow describe the addition of an array of light-dependent resistors (l.d.r.s) which are used to provide the PhizzyBot with "eyes". This addition can be used to demonstrate how the PhizzyBot, with the aid of a suitable computer program, can be made to react when it detects a source of light.


It also demonstrates the principles of how the PhizzyBot can in general be made to respond to externally-generated control signals – whether by being attracted to a

stimulus or, indeed, by recoiling away from it! This opens up new possibilities for applying a PhizzyBot in a number of computerised control systems – perhaps as a white line follower, or a buggy armed with magnetic detectors (or Hall Effect switches) which follows an "invisible" metal stripe buried in the carpet underneath.

All it requires is a simple input device, such as the light-sensitive type described next, and an appropriate computer program to help the PhizzyB make sense of it all.

ALL-ROUND VIEW

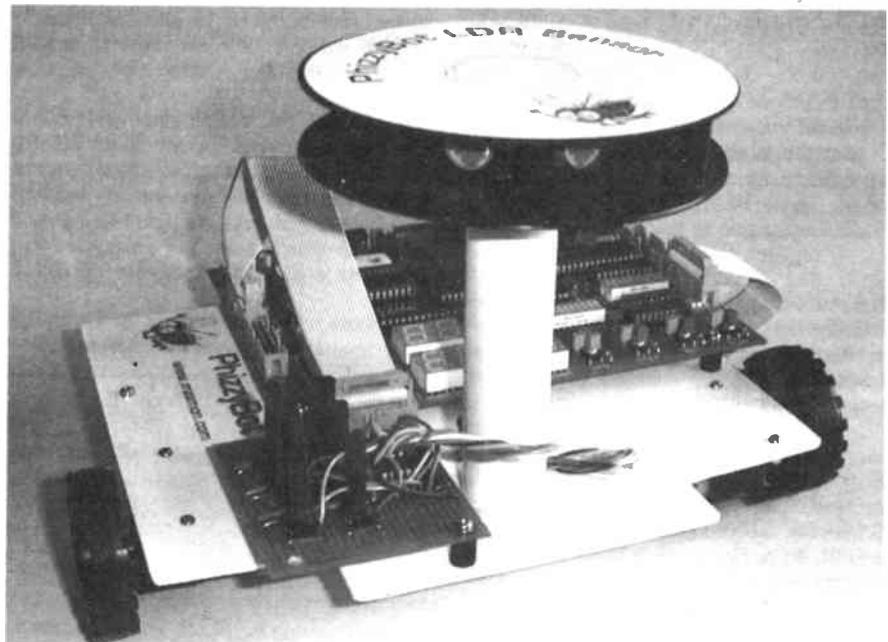The light-dependent resistor array described in the main feature consists of



six photo-conductive cells coupled to a series of electronic switches. A common NORP12-type l.d.r. is used which has a resistance of several megohms in darkness, this falls to a few hundred ohms under bright conditions.

The tutorial article describes the very cunning way in which the six devices are arranged around a hexagon, and by separating each l.d.r. from its neighbour using a divider, a 360 degree field of view can be created. The hexagon arrangement is sandwiched between two discs to make the unit "directional".

It is designed such that either one or two l.d.r.s can be illuminated at any one time by a source of light, and this can be decoded by the computer program to enable the PhizzyB to "know" the direction from which the light is being emitted.

The assembly of the l.d.r. sensor falls into two parts: an interface board which connects to a PhizzyB input port, plus the construction of the hexagonal array itself. Now here's an opportunity to have some fun and practise one's model engineering skills once again!

The building of the optical sensor and circuit is straightforward and somewhat easier than some of the more ambitious I/O circuits presented in earlier parts of the series.

SENSOR CIRCUIT

Circuit diagram details for of the l.d.r. sensor are shown in Fig.1. All six sensors use an identical circuit based on a Schmitt inverter. A Schmitt-triggered device is one which converts a slowly-moving signal to a rapid "snap action" on-off voltage, whilst an inverter merely outputs a logic state opposite to that of the input signal so a "low" voltage is inverted to a logic "high".

In the circuit diagram, an l.d.r. and a variable trimmer resistor (potentiometer) are used with a fixed "pull up" resistor to produce a potential divider. In the case of the first digital bit, based around LDR0 and IC1a, when light falls upon the l.d.r., its resistance will fall, which may take a short time because an l.d.r. has a relatively slow response.

In order to generate a clean on-off signal (i.e. a fast pulse edge) this is converted by the Schmitt inverter IC1a. The voltage at pin 1 of IC1 is sent by the l.d.r. towards 0V. A point will be reached where the inverter will suddenly detect a low input signal. Consequently, a logic 1 is sent from pin 2 to IP0 of the PhizzyB input port at pin 19.

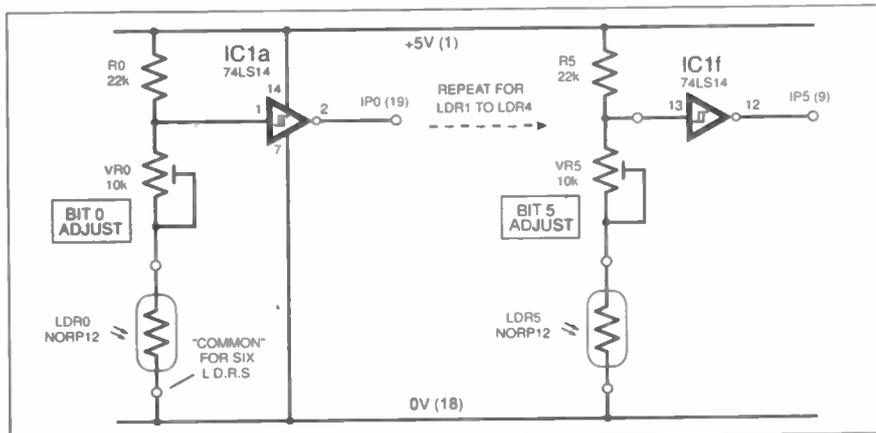


Fig.1. Circuit diagram for the optical sensors.

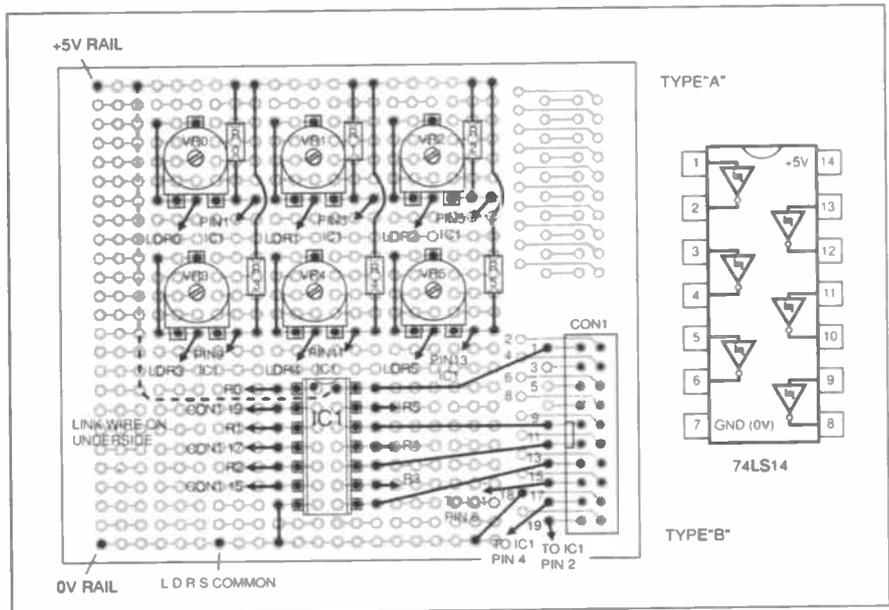


Fig.2. The presets and hex inverter are mounted on the board, but the sensors are wired off-board.


This arrangement is repeated for the five remaining l.d.r.s, each having its own trimmer resistor and outputting via a Schmitt inverter gate to the PhizzyB input port. The trimmer resistor (preset) is used to enable some adjustment of the triggering point for each l.d.r., also allowing the user to compensate for ambient light conditions.

EYES OFF THE BOARD!

In Fig.2 is shown the layout of all the "eyesight" components, mounted on one half of a PhizzyB I/O board, with the exception of the six l.d.r.s which are mounted externally. Commence construction by soldering the trimmer resistors and i.c. socket into place to act as a reference, then complete all interwiring as shown. On the prototype, extension spindles were used for the trimmer resistors to make adjustment and setting up more convenient.

The component layout should be followed closely, noting that three resistors (R3 to R5) should be insulated with PVC sleeving or similar to prevent shorting to nearby flying leads. A single link wire is soldered on the underside of the board as indicated, and both tinned copper wire and general-purpose hook-up wire can be used for the jumper wires.

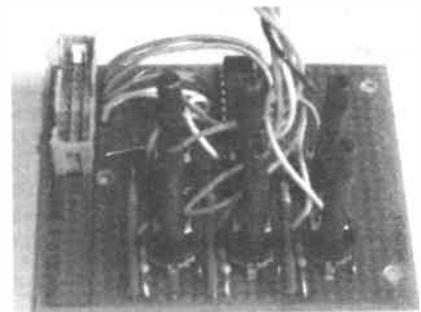The wiring doesn't need to be very neat but it should be effective. It will prove very useful to use six different colours for the



jumper leads which connect to IC1 and CON1, in order to identify the six connections IP0-IP5. The same colours should be used in relation to the l.d.r. assembly, described next. Hence, use six colours to identify the wiring of each "channel".

COMPONENTS

Resistors

R0 to R5 22k (6 off)
All 0.25W 5% carbon film

Potentiometers

VR0 to VR5 10k min. horiz. preset (6 off) with extension spindles (see text)

Semiconductors

LDR0 to LDR5 NORP12 (or ORP12) light-dependent resistor (6 off)
IC1 74LS14 hex Schmitt trigger inverter



Miscellaneous

CON1 20-way IDC box header

One half PhizzyB I/O board; 14-pin d.i.l. socket; hook-up wire (assorted colours); materials for l.d.r. assembly, including two CDs (see text); 20-way IDC connector cable.

Approx. cost guidance only

£15

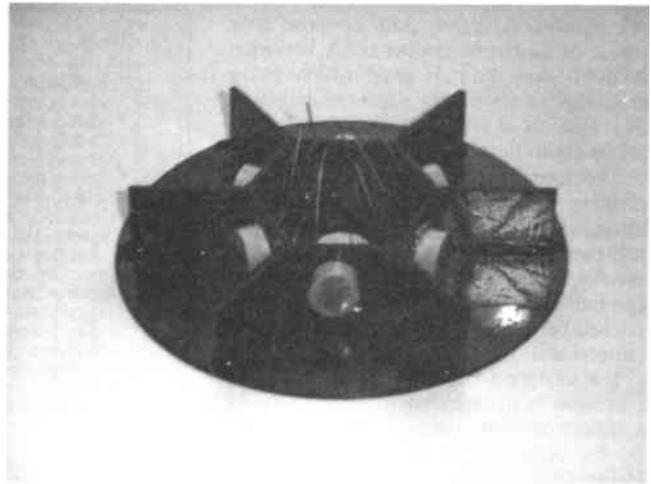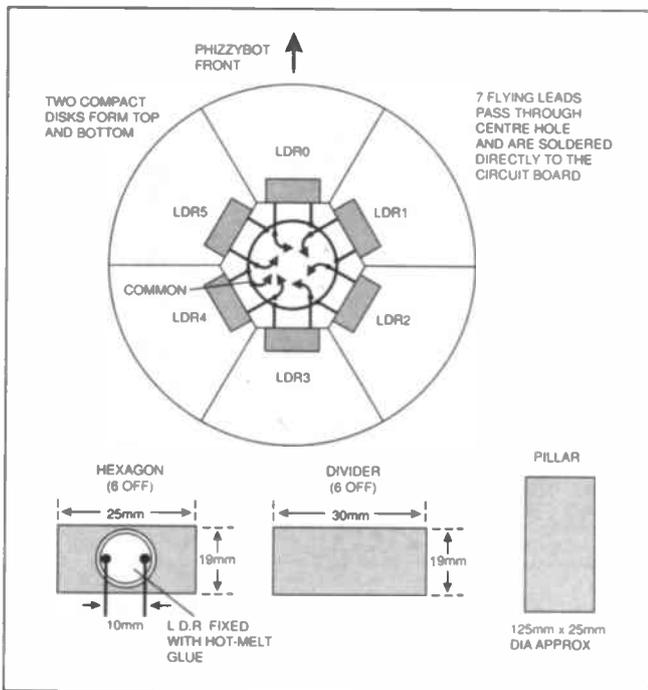

Above: The l.d.r.s on their hexagonal disc.

Left: Fig.3. Showing how the l.d.r.s are arranged, plus the extra bits that are needed

OPTICAL DISCS

Two discs are used to sandwich the hexagonal arrangement of six light-dependent resistors. Rather than attempting to produce the discs from, say, plastic card, it was found that a pair of unwanted compact discs (e.g. outdated catalogue CDs – at last, a practical use for them!) proved admirable for this purpose.

The hexagonal centre and the six dividing pieces can be cut from plastic available from model shops, and the approximate dimensions are shown in Fig.3. Note that two holes (10mm apart and approximately 1mm diameter) are required in each hexagon face to carry an l.d.r., so drill these next. File all edges so that they are reasonably square and level.

Use a felt tip pen to mark out the layout on the lower CD. The six centre pieces can then be glued to the shiny side (glue may not adhere to the printed side) of the CD to form the hexagon. Hot-melt glue is perfect for this, but any general-purpose plastic cement or super glue could be used (CDs being made of polycarbonate which glues readily).

When the glue has set, the surface of the resulting assembly should be spray-painted black (preferably matt) using cycle or car aerosol touch-up paint. The paint will help prevent unwanted reflections and stray light from "confusing" the PhizzyBot light sensor array, which might otherwise generate erroneous signals. The other CD which will fit on top should also be spray painted on both sides.

The six light-dependent resistors should then be glued to the faces of the hexagon by feeding their leads through the plastic, scraping off any paint prior to gluing.

FLYING LEADS

Manipulate one wire of each l.d.r. to join them all together within the hexagon, and solder these together as one large joint, to create a common rail for all the l.d.r.s. A single flying lead (approximately 230mm) should then be soldered to this common rail and fed out through the centre hole in the

disc. This will ultimately be wired to 0V on the circuit board. Solder six more flying leads, one to each remaining l.d.r. leadout. It is very important that you are able to identify the l.d.r. used for Bit 0 because this must face forwards when fitted to the PhizzyBot. Perhaps mark the underside of the disc with a felt-tip pen or label, to indicate which l.d.r. is Bit 0.

Six 230mm flying leads should then be soldered to the remaining leads of each l.d.r., using a coloured wire to correspond with the wiring scheme used on the circuit board: this is necessary to identify each digital bit once the l.d.r. assembly is complete (refer also to the diagrams in the main tutorial article at this point).

Feed each wire out through the centre hole in the disc. The second disc can then be glued on top, using hot melt glue which hides a multitude of sins as far as accuracy and alignment is concerned! Obviously, once the l.d.r.s are sealed into position like this, the only way of identifying which l.d.r. signal is which, will be to refer to the colour-coded wires.

HOT WIRED

The final aspect is to mount the completed l.d.r. array on a form of "pillar" which will raise it above the PhizzyBot platform. Some resourcefulness may be needed! The prototype used a plastic plunger from a

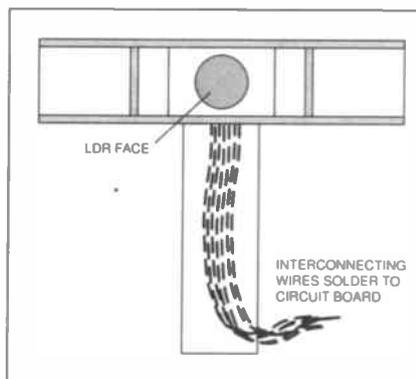


Fig.4. Sideways view of the l.d.r. sandwich assembly.

small empty silicone sealant "syringe" which proved ideal at about 130mm high and 25mm diameter. On the prototype, the seven wires were fed through the middle and the tube was then glued to the underside of the discs using more hot-melt glue.

The seven flying leads can then be soldered directly to the circuit board, and the sequence of coloured wires should then be seen to follow all the way through from the l.d.r. directly to the PhizzyB input port connector. At this point, the final positioning of the circuit board and l.d.r. array should be determined, noting that a 20-way IDC lead is needed to connect CON1 to \$F011, so locate the circuit board on the chassis so that the lead will reach: you can use one of the cables made in the earlier parts of the series.

Lastly, the round pillar can be glued down onto the PhizzyBot chassis with hot-melt adhesive: remember that Bit 0 must point towards the front of the PhizzyBot. As a finishing touch, a decorative CD-ROM label was created and applied to the top disc. (Enterprising readers can fetch the Flying Bee logo from the Maxmon web site!) With the l.d.r.s now installed, the circuit board can be connected to \$F011 and assembly is then complete.

SIGHT TEST

In order to test the photo-sensors, the on-board l.e.d. bargraph \$F030 can be used along with the following test program to adjust the six trimmer resistors (VR0 to VR5) for ambient light and sensitivity. This is best carried out away from windows or any sources of direct light. Load the PhizzyBot with the following program:

```

LSENSORS: .EQU $F011
LEDS: .EQU $F030
.ORG $4000
LOOP: LDA [LSENSORS]
AND %00111111
STA [LEDS]
JMP [LOOP]
.END

```

This just loops around reading from the sensors plugged into input port \$F011 and writes that value to the on-board bargraph. Shine a torch (flashlight) at the sensor array from across the room and "tweak" each

Everyday Practical Electronics are pleased to be able to offer all readers these

ELECTRONICS CD-ROMS

NEW

ANALOGUE ELECTRONICS by Mike Tooley

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.


FUNCTIONS

The component values on all circuits can be edited and the user can use the simulation engine to see how the value of each component affects circuit performance. You can, for instance, alter frequency and phase angle and plot outputs on a virtual oscilloscope or show load line graphs etc.


COVERAGE

Sections on the CD-ROM include: **Fundamentals** – Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections); **Op.Amps** – 17 sections covering everything from Symbols and Signal Connections to Differentiators; **Amplifiers** – Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections); **Filters** – Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections); **Oscillators** – 6 sections from Positive Feedback to Crystal Oscillators; **Systems** – 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

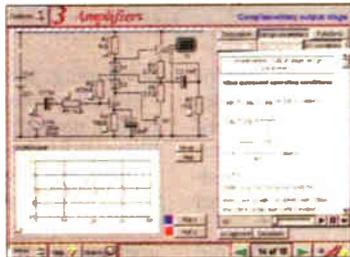
- Includes SPICE circuit simulator with over 50 circuits
- Unique virtual laboratories
- Editable assignments
- Design parameters for circuits included
- Complete hi-fi amplifier case study



Complimentary output stage.

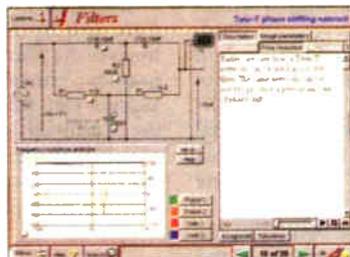


Twin-Phase shifting network

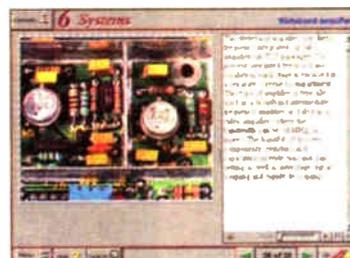


Gallery – Wideband Amplifier

DIGITAL ELECTRONICS by Mike Tooley

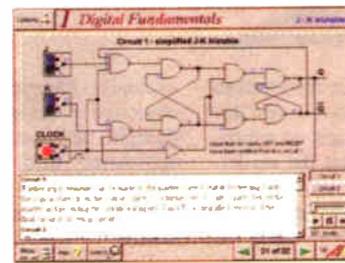
Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (below), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.



Virtual laboratory – Flip-Flops

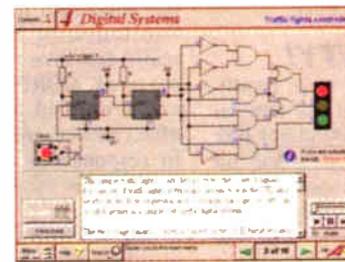

Virtual laboratory – Traffic Lights

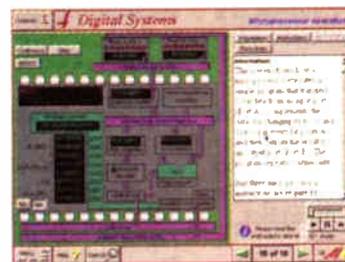

Microprocessor

FUNDAMENTALS

Fundamentals introduces the basics of digital electronics including binary and hexadecimal numbering systems, ASCII, basic logic gates and their operation, monostable action and circuits, and bistables – including JK and D-type flip-flops.

COMBINATIONAL LOGIC

Multiple gate circuits, equivalent logic functions and specialised logic functions such as majority vote, parity checker, scrambler, half and full adders. Includes fully interactive virtual laboratories for all circuits.

SEQUENTIAL LOGIC

Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers.

DIGITAL SYSTEMS

A/D and D/A converters and their parameters, traffic light controllers, memories and microprocessors – architecture, bus systems and their arithmetic logic units.

GALLERY

A catalogue of commonly used IC schematics taken from the 74xx and 40xx series. Also includes photographs of common digital integrated circuits and circuit technology.

Prices for each of the two CD-ROMs above are:

Hobbyist/Student£45 inc VAT
Institutional (Schools/HE/FE/Industry).....£99 plus VAT
Institutional 10 user (Network Licence).....£199 plus VAT

TWO APPLICATIONS ON ONE CD-ROM

ELECTRONIC CIRCUITS & COMPONENTS + THE PARTS GALLERY by Mike Tooley


Electronic Circuits & Components provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding as they proceed through the sections on the CD-ROM. Sections on the disk include: **Fundamentals**: units & multiples, electricity, electric circuits, alternating

circuits. **Passive Components**: resistors, capacitors, inductors, transformers. **Semiconductors**: diodes, transistors, op.amps, logic gates. **Passive Circuits**. **Active Circuits**

The Parts Gallery – many students have a good understanding of electronic theory but still have difficulty in recognising the vast number of different types of electronic components and symbols.

The Parts Gallery helps overcome this problem: it will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Selections on the disk include: **Components**, **Components Quiz**, **Symbols**, **Symbols Quiz**, **Circuit Technology**

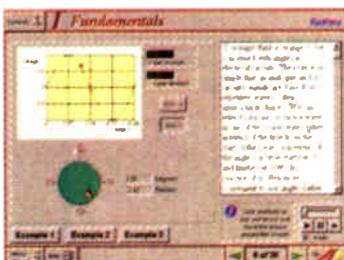Hobbyist/Student£34 inc VAT
Institutional (Schools/HE/FE/Industry)£89 plus VAT
Institutional 10 user (Network Licence)£169 plus VAT




Virtual laboratory – sinusoids



Circuit technology screen

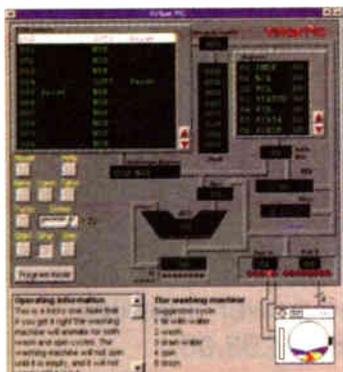Interested in programming PIC microcontrollers? Learn with **PICtutor** by John Becker



The Virtual PIC


Developed from John's *EPE* series, this highly acclaimed CD-ROM, together with the PICtutor experimental and development board, will teach you how to use PIC microcontrollers with special emphasis on the PIC16x84 devices. The board will also act as a development test bed and programmer for future projects as your programming skills develop. This interactive presentation uses the specially developed **Virtual PIC Simulator** to show exactly what is happening as you run, or step through, a program. In this way the CD provides the easiest and best ever introduction to the subject. Nearly 40 Tutorials cover virtually every aspect of PIC programming in an easy to follow logical sequence.

HARDWARE

Whilst the CD-ROM can be used on its own, the physical demonstration provided by the **PICtutor Development Kit**, plus the ability to program and test your own PIC16x84s, really reinforces the lessons learned. The hardware will also be an invaluable development and programming tool for future work once you have mastered PIC software writing.

Two levels of PICtutor hardware are available – Standard and Deluxe. The Standard unit comes with a battery holder, a reduced number of switches and no displays. This version will allow users to complete 25 of the 39 Tutorials.

The Deluxe Development Kit is supplied with a plug-top power supply (the Export Version has a battery holder), all switches for both PIC ports plus l.c.d. and 4-digit 7-segment l.e.d. displays. It allows users to program and control all functions and both ports of the PIC and to follow the 39 Tutorials on the CD-ROM. All hardware is supplied fully built and tested and includes a PIC16F84 electrically erasable programmable microcontroller.

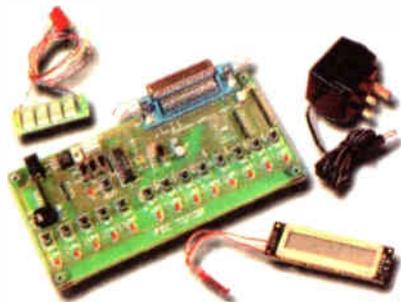

Deluxe PICtutor Hardware

PICtutor CD-ROM

Hobbyist/Student£45 inc. VAT
 Institutional (Schools/HE/FE Industry)£99 plus VAT
 Institutional 10 user (Network Licence).....£199 plus VAT

HARDWARE

Standard PICtutor Development Kit£47 inc. VAT
 Deluxe PICtutor Development Kit£99 plus VAT
 Deluxe Export Version£96 plus VAT
 (UK and EU customers add VAT at 17.5% to "plus VAT" prices)

MODULAR CIRCUIT DESIGN by Max Horsey and Philip Clayton

Developed from Max Horsey's *Teach-In* series *A Guide to Modular Circuit Design* (*EPE* Nov '95 to Aug '96). This highly acclaimed series presented a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects.

Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinouts, power supplies, decoupling etc.


Single User Version £19.95 inc. VAT
 Multiple User Version £34 plus VAT

A Web Browser is required for Modular Circuit Design – one is provided on the *EPE CD-ROM No. 1* (see below) but most modern computers are supplied with one.

Minimum system requirements for these CD-ROMs: PC with 486/33MHz, VGA+256 colours, CD-ROM drive, 8MB RAM, 8MB hard disk space. Windows 3.1/95/98/NT, mouse, sound card (not required for *PICtutor* or *Modular Circuit Design*).

designing your circuit

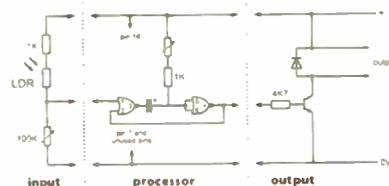Simply select your modules from the wide choice available, read how they work and join them up to make your circuit



"I found that I could design a circuit without my teacher's help. And it worked! Everything was to hand – which chips to use – and which pins did what" Andrew Preston (GCSE student)

CD-ROM ORDER FORM

Please send me:

- | | |
|--|--|
| <input type="checkbox"/> Electronic Circuits & Components +The Parts Gallery | <input type="checkbox"/> Hobbyist/Student |
| <input type="checkbox"/> Analogue Electronics | <input type="checkbox"/> Institutional |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Institutional 10 user |
| <input type="checkbox"/> PICtutor | |

- | | |
|--|--|
| <input type="checkbox"/> PICtutor Development Kit – Standard | <input type="checkbox"/> Deluxe Export |
| <input type="checkbox"/> PICtutor Development Kit – Deluxe | |

- | |
|---|
| <input type="checkbox"/> Modular Circuit Design – Single User |
| <input type="checkbox"/> Modular Circuit Design – Multiple User |

Full name:

Address:

Post code: Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard: £ Card expiry date:

Card No:

Please supply name and address of cardholder if different to the delivery address.

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world
 EU residents outside the UK add £5 for airmail postage per order

OVERSEAS ORDERS: Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

Direct Book Service
 33 Gravel Hill, Merley, Wimborne
 Dorset BH21 1RW
 (Mail Order Only)

Direct Book Service is a division of Wimborne Publishing Ltd. To order by phone ring

01202 881749. Fax: 01202 841692

We cannot reply to overseas orders by Fax
 Goods are normally sent within seven days

Demos (not Modular Circuit Design) available on the *EPE CD-ROM No. 1* (Free with the November '98 issue) – send £2 for this CD-ROM if you require the demos. For Modular Circuit Design demo send £6.95 for cut down version (£5 refunded if you buy full version). Minimum order for credit card payment is £5.

Prices include VAT
and free delivery (UK only)

Vann Draper Electronics Ltd

Unit 5, Premier Works, Canal St, South Wigston, Leicester LE18 2PL
Tel 0116 27711400 Fax 0116 2773945
E-mail sales@vanndraper.co.uk Home page www.vanndraper.co.uk

Limited
Stocks

SPECIAL OFFERS

New equipment

DT830B

Multimeter £12.56 £8.00



- AC & DC volts
- DC current to 10A
- Transistor test
- Diode test
- Basic accuracy 0.5%

AG2601

1MHz Audio gen £161.58 £99.00



- 10Hz-1MHz in 5 ranges
- Sine and square outputs
- 600ohm output impedance
- 240Vac mains operation
- Sync input

MX800

Multimeter £69.33 £39.00



- AC and DC voltage
- AC and DC current to 20A
- Resistance to 2000Mohm
- Capacitance to 20,000µF
- Complete with holster

Kenwood power supplies
from £95.00



PA18-1-2	0-18V 1-2A digital display	£346.63	£95.00
PR18-3	0-18V 3A analogue display	£299.63	£99.00
PAC20-3	0-20V 3A digital display	£217.38	£119.00
PD18-10A	0-18V 10A analogue display	£940.63	£325.00

- Twin analogue or digital displays
- Constant voltage & constant current modes

Ex-demonstration equipment

MO30 Grundig

30MHz scope £466.83 £329.00



- 30MHz bandwidth
- 2 channels
- 8 x 10cm screen
- X and Y modes
- 5mV to 20V /div
- 0.5µs to 200ms
- Tilt carrying handle

FG100 Grundig

20MHz Function gen £581.63 £399.00



- 0.5Hz to 20MHz range
- 2 x 16 digit alphanumeric display
- Microprocessor self test
- RS232 interface
- Frequency & output level display
- Back lit I.c.d.
- Sine, square, triangle & sawtooth

RLC100 Grundig

RLC meter £386.58 £275.00



- 0.5% accuracy
- 2 x 16 digit alpha display
- Microprocessor self test
- RS232 interface
- Resistance 1m ohm to 2M
- Inductance 0.1µH to 200H
- Capacitance 0.1pF to 2mF

RF1000 Grundig

RF millivoltmeter £476.88 £339.00



- 10kHz to 1GHz range
- 1mV to 10V ranges
- Analogue recorder output
- -47dBm to +33dBm
- Average accuracy 3%
- Includes RF probe & insertion head complete with N-plug socket

Others including: UZ2400 2-4GHz Freq counter £386.58 £275.00 DM100 4.5 digit 0.05% bench multimeter £440.08 £295.00

Data sheets available as hard copies or on our web site and all equipment (new or ex-demo) is supplied with manuals, all accessories in original manufacturers' packaging and include a 1 year guarantee. Ex-demo units are unmarked, in virtually new condition and have generally only been used once for exhibitions/demonstrations. Other new and ex-demo models for Grundig & Kenwood available.

Use this coupon for your order

or phone, fax or E-mail quoting EPE

Name Address Tel No

Model	Description	Quantity	Price each	Total
.....
.....

Cheques payable to Vann Draper Electronics Ltd, or debit my Visa, Mastercard or Switch:

Card No Exp date Switch Iss No Signature

READOUT

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

WIN A DIGITAL MULTIMETER

The DMT-1010 is a 3½ digit pocket-sized I.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a DMT-1010 Digital Multimeter to the author of the best *Readout* letter.



★ LETTER OF THE MONTH ★

RE-FUELING FOR THOUGHT

Dear EPE,

I write with regard to the *Fuel for Thought* letter in *Readout* April '99. Two years ago I retired from the Motor Industry Research Association (MIRA - <http://www.mira.co.uk>) where I was employed as a Technician Engineer. The letter(s) brought back some memories of technicians' "panic" solutions when a fuel gauge was found to be faulty at the last minute before testing:

- Use a dip stick - normally a long screwdriver
- Drop an old golf ball in the tank - it will rattle around when the fuel is low
- Tie a fishing line to a golf ball and hang 3/4 way down into tank - it will hit the tank when the level goes down by 3/4
- Fill the tank to the brim, zero trip meter and drive 10 to 12 miles. Fill tank to brim again and note the amount of fuel used. Zero trip meter again. Calculate mileage for 3/4 of a tank, from then on watch the mileage! (This is quite accurate as long as the driver is not changed!)
- "T" a polythene tube into the fuel line (before any fuel pump!) and use it as a sight glass. The tube needs a restriction, like a smaller diameter tube, near the "T" piece to dampen fuel movement (the end of the tube needs blanking when driving as carburation will take place with vehicle movement and can be very dangerous).

My proposed solution:

Principle: measure the "head pressure" of the fuel in the tank

Method: Use a low pressure piezo transducer (Maplin, RS, old engine management system). "T" it into the tank or fuel line. Low-pass-filter the transducer output and use three comparators/I.c.d.s (3/4, 1/2, 1/4 full). I assume

that when the tank is full and when it is empty will be known to the driver!

I believe that I am correct in saying that petrol is only 80 per cent the weight of water, so the pressures we are talking of are not high. At a depth of 300mm the pressure in water is approximately 0.3psi. This will not work if the fuel tank is pressurised, but is likely to be OK on a motor cycle.

On another subject - I hope you do not mind me criticising the "Next Month" paragraph on page 279 of the April '99 issue and written by the American authors, but do they realise that Europe, and most of the world, works in metric and a lot of youngsters have great problems in understanding the difference between old-fashioned *1 niche* and *25-umm*?? Maybe they could use a metric protractor too (ha, ha)?

I must say there is a lot of reading in *EPE*, normally I get through mags in less than 30 minutes... Thanks and best regards,

Ivor Mantell,
via the Net

Are there no limits to readers' levels of ingenuity? A remarkable set of suggestions Ivor! Thanks.

As to Metrics - in fact Max and Alvin are both English, but like a lot us who are a bit long in the tooth(!), they still work in inches. In fact it's me "wot tyakes 'a blyame (ayin'tit arl a blyading shyame?)" - we normally change Imperial measurements to metric, or quote both. On this occasion I didn't, and no-one else spotted my misdemeanour!

And yes, folks, Ivor does say "1 niche and 25-umm"! But rather than "protract" the issue, I'll just comment that metric angles would probably send us all off at a tangent (or would they make us "radiant"?)!

POWERING PhizzyB AND SENDING 98

Dear EPE,

With respect to the hardware *PhizzyB*, is there any reason for using a regulated 9V power supply? Will an unregulated 12V supply which I have to hand be OK given the use of the LM340-T5 voltage regulator?

Also, I thought you would like to know that I have upgraded a 1-year old Dell computer from Win 95 to 98 and now somewhat regret it. In particular, the &H378 TASM Send program I use for programming PICs now does not work from a DOS window. I have to re-boot the computer into DOS mode to get it to work.

Thomas Walton (age 11),
via the Net

No, 12V would be too high (says Alan Winstanley, who is our PhizzyB expert on the UK side of the planet). The on-board regulator is 5V and it would tend to dissipate too much heat because there is no room for a heatsink. This won't damage the device because it will thermally shut itself down, but it won't run very well when, for example, all the 7-segment

displays are in use, when current consumption is highest.

Of the seven computers I use from time-to-time, three are Dells and I speak highly of them and their manufacturer to anyone who cares to listen. As I understand the comments about Win 98 that we receive here, it's having upgraded to 98 that is causing problems for many people. It seems to be a problem caused by other software already being on the system and which may have changed an unknown variety of system parameters, rather than due to any specific computer.

Those who are purchasing new machines with 98 already installed are, we understand, not likely to experience the same difficulties. (I'm not an expert on computer systems per se, so I would welcome Readout input on this from those who are.)

Knowing from several sources (including Alan Winstanley) that Dell are very helpful, we suggest that you contact them for advice. We suspect that trying to contact Microsoft directly might result in lengthy waits before you can get into their telephone queuing system (though an E-mail might do the trick).

PEEEPEHEEMETI

Dear EPE,

I think that you should not be concerned (*Readout* April '99) that a change of name would lose you existing readers. It is the content which matters and, with notification in preceding issues, regular readers would readily recognise the change.

Lee Elvin was right in his concurrent letter that it is new readers whom you need to attract, especially potential readers who are coming of age. You acknowledged that electronics hobbyist activity has declined since the 1980s and presumably your takeover of *ETI* implies that it is continuing to do so. And of recreational activities it is not only hobby electronics which is suffering from the draw of the goggle box and the computer game, and the consequences of depreciating educational standards.

Electronic engineering at its academic and professional level is an esoteric discipline and one requiring competence in advanced mathematics, both well beyond the ken of all but a tiny proportion of the populace. The great virtue of "PEEEPEHEEMETI" is that it can inspire those who have an incipient interest in the applications of electronics to convert their interest to practical purpose.

Lee Elvin was also right in saying that a simple name for your magazine is needed. Whilst his *Electronics* might be too all-encompassing, a more specific name would be appropriate. *Practical Electronics* would be fine; but your integration of numerous past titles declares a need for a new and easily-recognisable name to accord with the magazine's role.

Wireless World was a respected journal of many decades' vintage long before the 1970s/80s splurge of amateur electronics magazines. It has had no trouble in changing to *Electronics World* - which title I suggested to its then publishers in a letter of 2 August '82.

Jack Easthaugh,
Chesham, Bucks

Your further comments on the subject are appreciated. Nonetheless, we feel very strongly that people become loyal to a "brand image" and could well respond negatively if that image changes. In this context, I heavily regard our Title as being a brand image, one which people expect to see and have learned to trust. If images have to be changed, my personal opinion is that the change should be made subtly over time - and this would rule out any significant name change.

You quote one example of such a change and I cannot comment on what it has actually done for the magazine, only its publishers can answer that, but I could not support any change that might put us at risk of losing an existing market. Certainly we need to attract new readers (and we do so), but we need to have full regard to the expectations of readers who have been with us for far longer - some have been with us since we first began (as EE) in 1971.

Having said that, I would also stress that we do listen and respond to what people say about us. We welcome letters such as yours which offer considered opinions. We like hearing from you all!

NO NEW THING

Dear EPE.

Bart Trepak's *Mechanical Radio* of April '99 prompts me to quote the Bible, "There is no new thing under the sun". During the 1939/45 War, aircraft whose duties carried them over the sea carried inflatable dinghies whose kit included a "Gibson Girl". This was a buoyant yellow container with a handle on the top and a waist so that it fitted neatly between the legs of a seated person; the shape inspired its name.

Turning the handle operated a generator through a gear chain giving 12 volts for the heaters and 400 volts for the anodes of a valved radio transmitter. As the handle was turned it moved a set of cams which switched the transmitter to provide a Morse distress signal. After the War the generators were available on the surplus market; I still have one.

In the 1950s, electronic flash was available for amateurs at low cost but using expensive 90V or 180V dry batteries to charge electrolytic capacitors which stored energy, about 25 joules, for the flash tube. I found that the high voltage output from the Gibson Girl generator charged the capacitor with a few turns of the handle. A diode was necessary to prevent discharge causing the generator to motor, and a neon to indicate operating voltage had been reached.

The high cost of the Bayliss radio is to a large extent due to the use of an excellent Tensator spring motor. These give constant power as they unwind and were widely used in 8mm cine cameras in the 1960s. However, the price of electric motors dropped and hand power was replaced with battery power in these cameras.

Hand-powered torches can be obtained from Bull Electrical. Regular squeezing of the handle keeps a flywheel and coupled generator spinning, so lighting a bulb; the output should power a small radio.

Guy Selby-Lowndes,
Plaistow, Billingshurst

Fascinating! And could it be that the Gibson whose Girl it was, was Guy Gibson who (if memory serves me right) was in charge on the Dam Busters raids?

You have also reminded me of the mechanical shaver my father used in the late '40s/early '50s. It had a handle that caused the generation of rotational power when squeezed, and used a flywheel for energy storage between squeezes.

MORE ON BASIC

Dear EPE,

I have noticed in the past few months that people have been going on about what format the software for some EPE programs should be written in. I think that a switch to Visual Basic would be quite easy for yourself and the readers!

Visual Basic allows Windows programs to be written easily and is very easy to pick up and would allow readers to modify the programs to suit their own needs. Books can be found online and there are plenty of source codes and tutorials available on the Web.

I am currently a sandwich student on Placement and have been teaching myself Visual Basic and Visual C++ in preparation for getting a job when I graduate. My degree might be in Electrical & Electronic Engineering but I find the computing side really enjoyable, including the learning curve that comes with learning new programming languages. I hope you think about switching to Visual Basic.

Robin Smith,
via the Net

Yes indeed, and once you know one language it becomes that much easier to learn others (this is one of the many great things about PhizzyB - teaches you programming techniques that can be used almost anywhere, even when the languages/dialects differ, the concepts remain the same.

POWERED START

Dear EPE,

Those who are well established in the field of electronics find your constructional projects quite interesting and worth building. This is not the kind of feedback received from newcomers to this wonderful world. Why not include projects that aid students in understanding the basics of electronics?

A mains operated power supply unit would be an excellent project for the student still trying to grasp the functions and implications of rectifier diodes, filter capacitors, etc.

Karl V. Grant, via the Net

Slightly tricky one this, Karl. Whilst many of us started off having an interest in electronics by learning that fuses can be blown, as a magazine we have to be very aware that we do not encourage readers to blow themselves through the misuse of mains electrical power.

You will have noticed that when publishing mains-powered projects we always give warnings about not attempting their construction unless the constructors are suitably qualified/experienced. We go on to recommend that readers should consult a qualified electrician if they are in any doubt about their capabilities. It would be difficult, therefore, to publish a mains power supply specifically for beginners.

We do publish power supplies from time to time but they are not intended for construction by beginners, even though we have no doubt that some readers do not heed our warning - that is entirely at their own risk.

On subjects where mains safety is not an issue, we frequently publish designs which are ideal for beginners. Notable in this respect are the Teach In series that we run every couple of years - each series taking a different viewpoint of elementary material. We are also about to publish a series of "Starter" projects aimed at beginners.

Forest Electronic Developments

Microchip PIC, ATMEL AVR & Scenix Development Support

PIC BASIC products - Modules and Compiler

Straightforward, capable, powerful, rapid development. Operating within a Windows Development Environment our modules need no assembler or UV eraser to program your PICs, and operate from a serial link to your PC.

16C74 module features - 8k EEPROM, up to 2000 lines of BASIC, 27 lines of programmable I/O, 8 A/D inputs, User defined interrupt support, Interrupt driven serial RS232 interface, Peripheral I2C bus interface, LCD display driver routines, up to 178 bytes for variables and stack, extendible with optional external RAM and all the standard 16C74 features. BASIC features block structure 1-16 bit variables packed in RAM, functions, local variables, arrays in RAM & EEPROM.

Download the development environment from our web site! 16C57 version still available - ask for details.

NEW!! - PIC BASIC MICRO MODULE

Run 16C74 FED PIC BASIC on a module which is only 65x27mm and is plug compatible with the 16C74 device

Uses Surface Mount techniques and includes power supply, serial interface and oscillator. Operate as a standalone module, or plug the module as a daughter card directly in place of a 16C74 into your application circuit.

BASIC COMPILER! - The FED PIC BASIC compiler for the 16C74. It produces hex code to program your 16C74 directly with no need for external EEPROM. Compatible with the EEPROM versions of PIC 16C74 BASIC modules - develop on an EEPROM based module then compile and program your PIC chips directly.

PIC BASIC Micro-Module 4MHz - £35.00, 20MHz - £40.00
16C74 Module Kit (8k EEPROM, 4MHz) £35.00, Pre-built £42.00
16C74 Module Kit (8k EEPROM, 20MHz) £40.00, Pre-built £46.00
Compiler - £30.00

Scenix, PIC, & AVR Programmers

PIC Serial - Handles serially programmed PIC devices in a 40 pin multi-width ZIF socket. 16C55X, 16C6X, 16C7X, 16C8X, 16F8X, 12C508, 12C509, PIC 14000 etc. Also In-Circuit programming. Price: £45/kit, £50/built & tested.

PIC Introductory - Programs 8 & 18 pin devices: 16C505, 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508/9, 12C671/2 etc. £25/kit.

AVR - 1200, 2313, 4144, 8515 in ZIF. Price: £40/kit £45 built & tested.

Scenix - SX18/SX28 in a 40 pin ZIF. Price: £40/kit £45 built & tested.

Programmers operate on PC serial interface. No hard to handle parallel cable swapping! Programmers supplied with instructions, + Windows 3.1/95/98/NT software. Upgrade Programmers free of charge from our web site!

AVR, PIC, Scenix - Windows Development

Assembler/Simulator allows development of your AVR, PIC or Scenix projects in **one Windows program**. Incorporate multiple files, view help file information directly from code, edit within project, build/track errors directly in source, then simulate. Simulator has many breakpoint types, follow code in source window, set breakpoints in source. Run, single step, or step over.

Logic Analyser Display! Track variable values and trace for display on the Trace Analyser. **Input stimuli includes clocks, direct values and serial data.** Profiler - examine and time frequently called routines use the information to optimise out bottle necks. PIC Version Simulates up to 50 times faster than MPSIM!

Cost £20.00. Specify PIC/Scenix or AVR version

AVR & PIC devices

PIC16C74/JW Erasable 20MHz £18.00 PIC16C558 £5.00
PIC16C74A-04P 4MHz £8.00 PIC16C74A-20P 20MHz £10.00
PIC16F84-04P 4MHz £6.00 PIC12C508-04P 4MHz £1.80
AVR - 8515 £8.00



Forest Electronic Developments

60 Walkford Road, Christchurch, Dorset, BH23 5QG.

Email - "robin.abbott@diat.pipex.com"

Web Site - "http://d-pacc.diat.pipex.com/robin.abbott/FED"

01425-274068 (Voice/Fax)

Prices are fully inclusive. Add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments, or phone with credit card details.



PIC TOOLKIT Mk2

JOHN BECKER

Part One



How to improve your PIC programming options in a Flash, and it's a real pleasure to use!

MICROCHIP'S new PIC16F87x series of Flash EEPROM micro-controllers offer greater program capacity and more facilities than the familiar PIC16x84 series. The latter, though, will still find a plethora of uses in less-demanding circuits where the greater sophistication of the '87s is not required. There are roles for both families.

Consequently, the *PIC16x84 Toolkit* of July '98 has been upgraded to make it compatible with both the '84 and the '87. The printed circuit board has been redesigned to accept the 18-pin '84s and the 28/40-pin '87s. The power supply control has been redesigned to remove the need for a regulated 12V/14V PSU – the Mk2 will run from any d.c. supply of between 5V and 20V (at around 10mA). The PC interface I/O lines have been buffered for greater stability.

Additionally, the controlling software has been considerably enhanced in a number of ways, offering more functions than the Mk1 version.

Whilst Toolkit can be used entirely as a stand-alone design, it can also be interfaced with the *PIC Tutorial* (Mar-May '98) and the *PICtutor* (CD-ROM) development boards, as discussed later.

The Mk2 Toolkit has the same basic options as the Mk1:

- Configure PIC
- Program PIC with TASM .OBJ
- Program PIC with MPASM .HEX
- Translate MPASM .HEX to TASM .OBJ
- Translate TASM .OBJ to MPASM .HEX
- Disassemble PIC to TASM .OBJ
- Disassemble PIC to MPASM .HEX
- Translate TASM .ASM to MPASM .ASM
- Translate MPASM .ASM to TASM .ASM

It also has the following additional options:

- Assemble TASM .ASM to .OBJ – totally replacing the need for a TASM shareware Assembler and its associated Send programs
- Directory paths display/change – eliminating any need to make changes to the Basic program (as required by Mk1)
- Directory display/select – displays file directories of choice, and allows automatic loading of selected file for use in any main program option
- Setup function allows PC ports to be tested and selected, and the PC's ability/inability to read (for PIC verify/disassemble) from its selected port established

- Load/read data to/from the PIC's internal EEPROM data memory
- Direct access to and return from DOS EDIT for editing any text files (.ASM source code files, for example).

This software is far more sophisticated than the Mk1 and is supplied as a suite of four chained programs which call each other as required without the user's intervention. It can be run in QBasic, QuickBASIC, or as a stand-alone (.EXE) program without any need for a Basic controller.

By design, the software can also control Toolkit Mk1 without modification.

The full suite of programs may be run under DOS mode or Windows 3.1 or Windows 95. It is likely to run under Windows 98 though this has not been tested. The author has run it on several desk-top computers with a range of processor types, including '386, '486 and Pentium. Additionally, the software has been accessed and run via the *PICtutor* CD-ROM package. All-in-all it is very comprehensive in its facilities.

About 350K bytes of hard disk space are required.


It seems likely that other PICS which use 14-bit instructions (as do the '84s and '87s) could also be programmed using Toolkit, although this has not been tested and readers should check the PIC data sheets for themselves. Such devices might include: 16C54, 16C56, 16C58, 16C62, 16C71, 16C72, 16C74. (Note that some PICs use 12-bit and 16-bit instructions and are not suitable for Toolkit's programming software.)

WHY A TOOLKIT?


In answer to the occasional question from readers, "Why do I need *PIC Toolkit* if I've already got *PIC Tutorial/Tutor*?" – because it makes life even easier!

The assembly and PIC loading programs (TASM and Send) used with *PICtutor* and *PIC Tutorial* (from hereon jointly referred to as *PIC Tutor* unless stated otherwise) were those which were originally published with Derren Crome's *Simple PIC16C84 Programmer* of Feb '96.

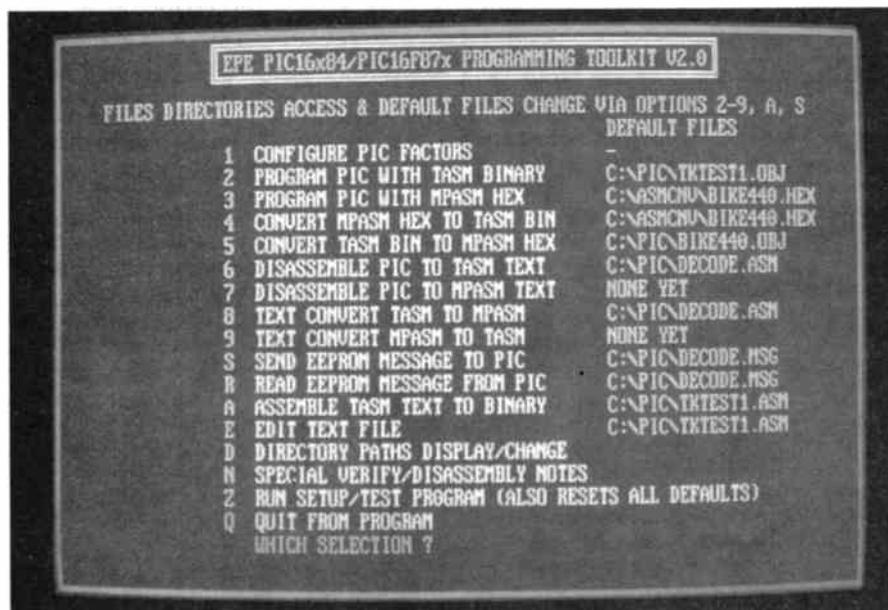As such, the hardware had to be switched to apply +12V to the PIC's MCLR pin in programming mode, and to apply 0V to the same pin in order to reset



The main menu for the Toolkit Mk2.

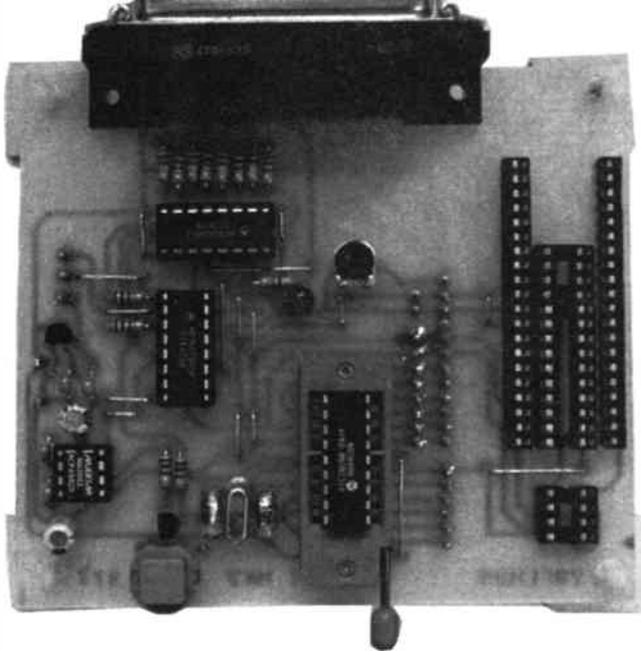

the PIC. In normal running mode +5V is applied to that pin. Additionally, it had been found disadvantageous to have the computer's DA0/DA1 lines connected to the PIC at the same time that the PIC's RB6/RB7 pins were also connected to any development circuit.

Consequently, in *PIC Tutor*, two additional changeover switches were included to prevent this joint interconnection. This meant that four switches had to be manually operated before and after programming a PIC. No great problem in itself, but becoming a bit tedious when frequent programming was called for.

One main purpose of Toolkit is to have the computer perform all the switching needed via control lines and a

multiplexing chip, completely removing the need for manual switching. The original Send program did not include facilities to do this, and the programming software for Toolkit was written to perform this operation and to replace Send.

Secondly, there are several PIC assembly programs available on the general market, two of which are TASM and MPASM. TASM is a shareware general-purpose assembler to

which PIC16x84 assembly facilities had been added on behalf of *EPE*, but which requires a registration fee to be paid to its designers if used beyond an evaluation period. MPASM is the assembly software available from Microchip (the PIC's manufacturer) and intended for use with their MPLAB hardware. Both TASM and MPASM are variously used by contributors to *EPE* and they are not mutually compatible.

For a start, although the two assemblers have much in common, the "grammar" used by each is not quite the same, different literal-value representations in particular being used, plus other subtle differences in command statements.

Secondly, TASM assembles the source

code into a simple sequential binary code format, whilst MPASM assembles it into a complex hexadecimal format complete with checksum validation codes interspersed between the required program codes. Although TASM can be told to generate a similar hex code output, the order of the individual MSBs and LSBs (Most and Least Significant Bytes) is reversed.

The upshot is that neither TASM (and Send) nor MPASM can make use of the other's files. This eventually became a problem to readers who already had one of the assemblers and wanted to make use of the other's program files. As a result, Toolkit's software was written to provide automatic translation between the two formats to suit readers' needs.

Additionally, Toolkit was given the facility to read back program data already in a PIC16x84, allowing verification that the PIC had correctly received the data, and allowing program code within a PIC16x84 to be disassembled to a source code text file.

In other words, Toolkit Mk1 was introduced to add more (and easier) facilities which would be of benefit to PIC-users who were using TASM or MPASM, with or without *PIC Tutor*.

As you will have seen from the functions listed in the introduction, Toolkit Mk2 offers even more facilities than Mk1 already offers. TASM and MPASM inter-translation is retained and source code can be written in either format. The emphasis of this article, though, is placed on TASM grammar, even though TASM itself is no longer used as the assembler program. The author finds the TASM

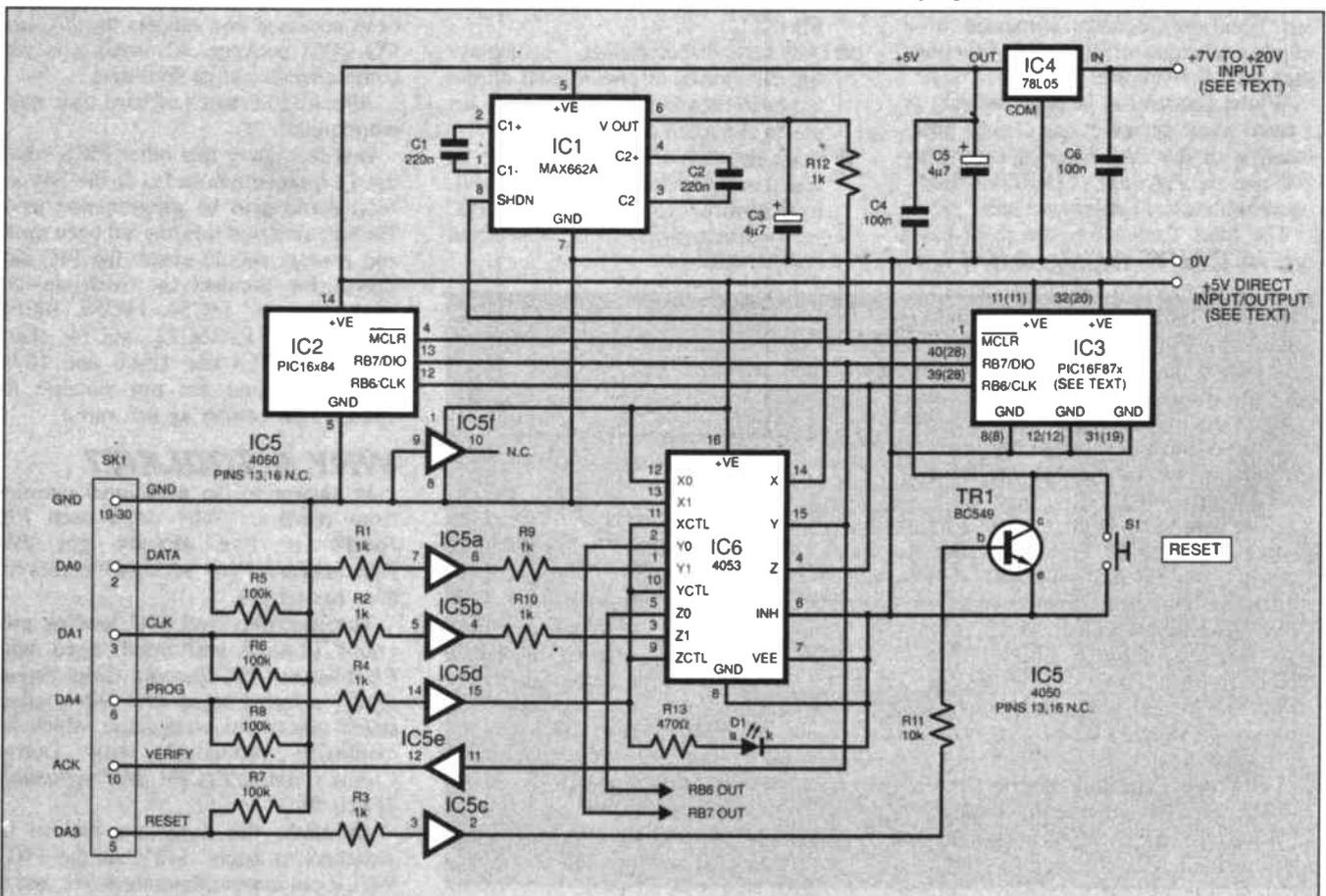


Fig.1. Main circuit diagram for the PIC Toolkit Mk2 programmer.

format somewhat easier to use and prefers to write his code in that format.

The use of the various functions offered by Toolkit Mk2 will be discussed as we progress, but first let's describe its basic hardware.

BASIC BOARD FUNCTIONS

In keeping with the original Mk1, and for use with the PIC16x84 when *in situ*, the printed circuit board includes a crystal oscillator and terminal pin connections so that it can be used as an elementary test bed. The pins are arranged so that an alphanumeric liquid crystal display (l.c.d.) can be plugged straight in. A contrast control preset is included on the p.c.b. (not shown in the circuit diagram).

The l.c.d. pins on the Toolkit Mk2 board are in the same order as those used on the *PIC Tutor* boards (original and CD-ROM versions). Consequently, the l.c.d. modules (and l.c.d. software) already used with those boards can be used with Toolkit Mk2.

It was felt, though, that the complexity of the '87s precluded the use of the Mk2 board as a test bed for them. Consequently, no terminal pin connections for the '87s are included on the board. There are, though, two programming techniques available.

One is that the '87s can be programmed on the Mk2 board and then transferred to the board that is being assembled for a specific project and for which the software is already provided.

Alternatively, to facilitate prototype development, the three principal lines required for programming the PICs (RB6, RB7 and MCLR) have output pins from which connecting wires can be taken to any prototype board, so that any of the '84 or '87 PICs can be programmed *in situ* where they are being used. The devices don't actually have to be plugged into the Mk2 board.

CIRCUIT DESCRIPTION

The main circuit diagram details for the PIC Toolkit Mk2 programmer are shown in Fig.1. IC2 and IC3 represent the power and programming connections for the PIC16x84 and PIC16F87x families respectively. Apart from the power supply connections, only three wires are needed between a PIC and the computer used to program it.

The data to be loaded into the PIC is supplied to its RB7 pin. A clocking signal goes to pin RB6 and the programming/running/reset voltage is applied to pin MCLR (master clear). Note that there are two sets of pin numbers shown for IC3. Those within brackets are for the PIC16F873 and '876 (28-pin devices); those outside brackets are for the PIC16F874 and '877 (40-pin devices). Their pinouts are shown in Fig.2.

There are two devices that separate the PICs from the computer connections, IC5 and IC6. The computer is coupled to the circuit via socket SK1, using an

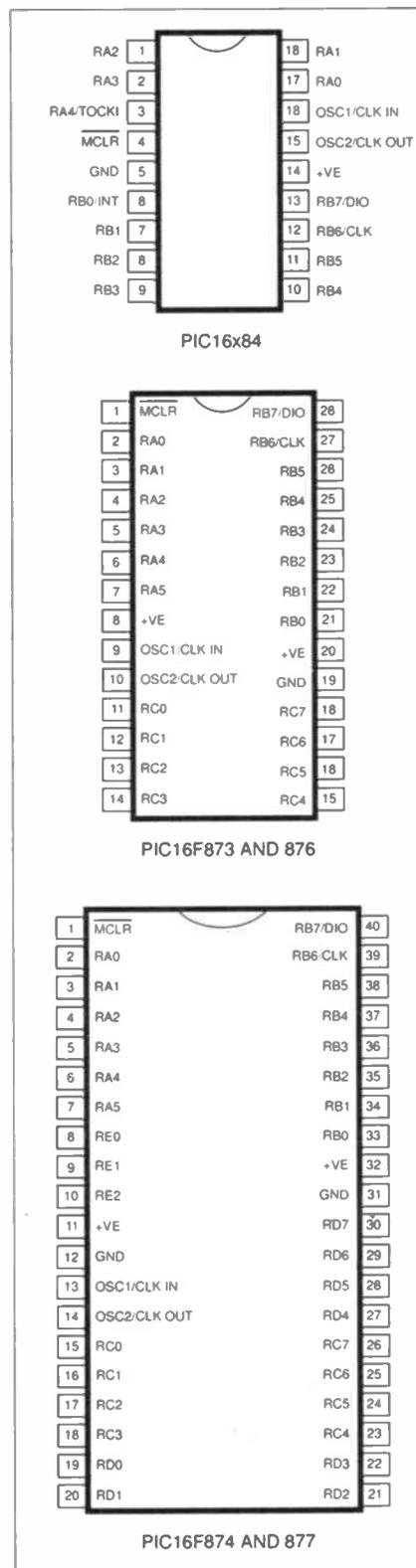


Fig.2. Pinouts for the PIC16x84 and PIC16F87x families. The widths are not to scale.

ordinary (Centronics) printer cable connected to the computer's parallel printer port. The computer lines being input to Toolkit are buffered by resistors R1 to R4 and non-inverting buffer gates IC5a to IC5d, whilst IC5e buffers Toolkit's single output back to the computer (IC5f is not used).

The resistors provide protection to the computer's output lines when Toolkit is unpowered. It was not felt desirable to resistively protect Toolkit's output

connection to the computer since the latter might have pull-up/down biasing which could be affected by any intermediate resistor.

Resistors R5 to R8 bias IC5's inputs to 0V when Toolkit is not connected to a computer.

Tri-state bidirectional multiplexer IC6 routes the PIC's RB6/RB7 and MCLR control according to whether the PIC is being written to/from or is actively controlling a prototype development circuit (replacing switches S1, S3 and S4 in *PIC Tutor*).

Programming/read mode is set by taking computer line DA4 high (logic 1). This sets IC6 to its secondary routing configuration in which inputs X1, Y1 and Z1 are routed to outputs X, Y and Z respectively. This allows data lines DA0 and DA1 (data and clock signals) to reach PIC pins RB7 and RB6.

With DA4 high, IC6 disconnects RB7 and RB6 from any development circuit that is connected to its Y0/Z0 pins via paths RB7 OUT and RB6 OUT. When DA4 is low, these paths are re-instated and the DA0 and DA1 lines are isolated from the PIC.

VOLTAGE CONVERTER

We now come to a significant difference between Toolkit Mk2 and its predecessors (*Toolkit Mk1*, *PIC Tutor*, *Simple PIC16C84 Programmer*). The latter all require an external +12V (to +14V) d.c. supply to be used during programming mode. In itself this is no great problem, but there is a more versatile option.

The PIC only requires +12V on its MCLR pin while it is being programmed or data read back from it. During normal running, +5V is applied to this pin. This dual requirement necessitates switching between the two voltages. In Toolkit Mk1 this was achieved by using line DA4 to switch a configuration of two transistors on or off (the other mentioned circuits used switches).

For Mk2, a more elegant solution is used — a device specifically designed to provide either +5V or +12V depending on the status of a controlling pin. The device is shown in Fig.1 as IC1 and is a readily-available Maxim product, MAX662A. It is described as a +12V 30mA Flash Memory Programming Supply device.

Its SHDN pin is internally biased to be normally held high, in which situation output pin VOUT is held at +5V. When SHDN is taken low, IC1 uses an internal oscillator to generate +12V from the +5V supply line. Charge-pump capacitors C1 and C2 set the oscillator's frequency and output current availability.

Although the maximum rated output current is stated as 30mA, in practice the author has noted that a saw-tooth ripple occurs on the output, rising in peak-to-peak value with increasing current being drawn.

With this mind, in some instances it might be preferable to omit the l.c.d. from the *PIC Tutor* board if Toolkit is

connected to it (to reduce the current required from the MAX662A in its 12V mode), although the author has not experienced any problems through leaving that l.e.d. in place.

The great advantage of using a step-up voltage converter is that Toolkit can be supplied from a d.c. power source other than a regulated +12V d.c. supply, as discussed later.

CONTROLLING MCLR

With computer line DA4 normally low, IC1 outputs +5V to the PIC's MCLR pin. The route to IC1's SHDN pin is via IC6 path X0/X, which couples the pin to the +5V power line (even though the pin has internal positive biasing, it was no problem to provide the +5V connection).

When line DA4 is taken high, the SHDN pin is taken low via IC6 path X1/X and IC1 outputs the required +12V. The status of DA4 is shown on l.e.d. D1, which is controlled by IC5d. When DA4 is high, D1 is turned on via ballast resistor R13.

A third control voltage level is needed for the MCLR pin. It needs to be taken low (0V) when the PIC has to be reset. Regrettably, the MAX662A is not capable of having its output set to 0V via a control pin. Consequently, the reset level is taken low by the same technique used in Toolkit Mk1.

Resistor R12 is placed in series with IC1's output and MCLR. To MCLR is connected transistor TR1, which is controlled by line DA3 via buffer IC5c, plus resistors R3 and R11. With DA3 low, TR1 is turned off and MCLR will be at either +12V or +5V, depending on DA4's status.

When DA3 is taken high, TR1 is turned on and MCLR is taken low, R12 preventing conflict with the output from IC1.

You will see that switch S1 has also been included across TR1. This has nothing at all to do with programming PICs. It is merely there to allow the PIC to be reset when it is in running mode as part of an attached prototype development board – a convenience the author finds useful from time to time.

POWER SUPPLY

A wide range of power supply voltages can be used with Toolkit Mk2. With regulator IC4 in circuit, the supply can be between about 7V and the maximum limits that this device can handle – typically up to about 20V.

The maximum voltage, though, also depends on the current being drawn through IC4. The maximum current IC4 (a 78L05) can supply is 100mA, but the wattage dissipated must also be taken into account – if it gets too hot it will shut down.

With Toolkit used independently (not attached to PIC Tutor or other circuits) and with a PIC16F84 inserted, the prototype currents drawn were:

- 4.5mA in run mode
- 8mA in program mode with Reset off
- 47mA in program mode with Reset on

The high current demand is believed to be due to IC1 trying to keep up its obligation to supply 12V. Normally, having Reset on in program mode is under computer control and only lasts for a fraction of a second.

An ideal conveniently available supply would be 9V with, for example, just an l.c.d. connected to the board.

The other power source option is to use a directly-input regulated supply of 5V, omitting IC4 entirely. This is particularly viable if Toolkit is used with a PIC Tutor board, since the 5V supply can be tapped directly from it, and take advantage of the 1A capability of its 5V regulator.

Do not feed any other voltage into the direct +5V input – the use of a 6V battery supply, for example, is *strictly not allowed* (unless fed in via a 1N4001 rectifier to reduce it by 0.7V). Regard all i.c.s as having an absolute minimum/maximum positive voltage range of 4.5V to 5.5V.

CRYSTAL OPTION

As said earlier, Toolkit Mk2 can be used as a simple "test bed" when used with a PIC16x84. The circuit diagram for these options is given in Fig.3.

Here a crystal oscillator is shown, comprised of crystal X1 and two capacitors, C7 and C8. The crystal frequency is stated as 3.2768MHz, as this is a convenient frequency from which to derive real-time clock timings in seconds, minutes and hours. Other crystal frequencies may be used, though, up to 10MHz (provided the 10MHz version of the '84 is used and correctly configured).

The connections in the outline box to the right of the PIC are terminal pins on the p.c.b. for use as connections to other circuits, including the l.c.d. module previously referred to. (In fact, on the p.c.b., two terminal pins for each of RB0 to RB7 are provided, allowing the direct plug-in of the l.c.d. while still leaving access to terminal pins for other use. Details of typical l.c.d. pin connections are shown in various earlier EPE projects, including PIC Tutorial Part 3 (May '98).

PIC PINOUTS

It is not the intention of this article to discuss the detailed operation of the '84 and '87 PICs. PIC Tutor covers the former in extensive detail. Microchip's data sheet should be obtained for the intimate details of the '87 family.

Nonetheless, it is appropriate to show the pinouts of both families, as we do in Fig.2.

Be aware that only the simple pin

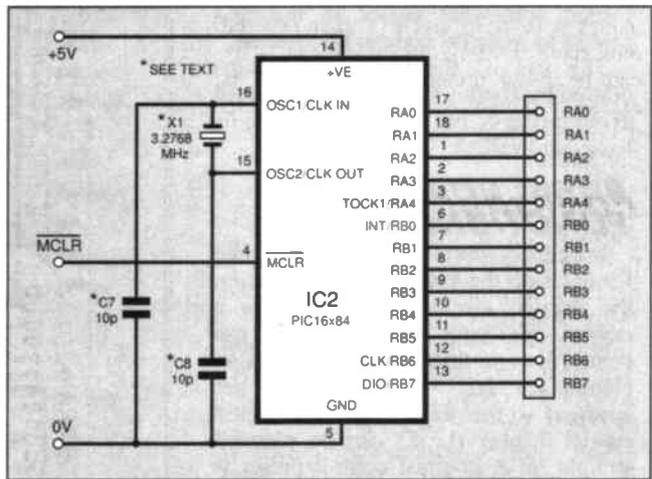


Fig.3. Oscillator option for the PIC16x84.

COMPONENTS

Resistors

- R1 to R4, R9, R10, 1k (7 off)
- R5 to R8, 100k (4 off)
- R11, 10k
- R13, 470Ω

All 0.25W 5% carbon film or better.

Potentiometer

- VR1, 10k preset, min. round (see text)

Capacitors

- C1, C2, 220n min. ceramic disc (2 off)
- C3, C5, 4μ7 axial elect. 16V (2 off)
- C4, C6, 100n min. ceramic disc (2 off)
- C7, C8, 10p polystyrene or ceramic (2 off) (see text)

Semiconductors

- D1, red l.e.d.
- TR1, BC549 npn transistor
- IC1, MAX662A +12V 30mA Flash memory programming supply
- IC2, PIC16x84 microcontroller (see text)
- IC3, PIC16F87x microcontroller (see text)
- IC4, 78L05 +5V 100mA regulator (see text)
- IC5, 4050 non-inverting hex buffer
- IC6, 4053 triple 2-channel analogue multiplexer

Miscellaneous

- S1, s.p. pushswitch, p.c.b. mounting
- SK1, 36-way Centronics female parallel printer connector, p.c.b. mounting
- X1, 3.2768MHz crystal (see text)

Printed circuit board, available from the EPE PCB Service, code 227; 8-pin d.i.l. socket (2 off); 16-pin d.i.l. socket (2 off); d.i.l. or s.i.l. sockets for IC2 and IC3 (see text); p.c.b. supports (4 off); connecting wire; solder, etc.

Approx. Cost
Guidance Only

£19

(excl. microcontrollers)

names have been given – many of the pins have multiple functions that they can be programmed to perform. It is essential to read the appropriate sheet to understand them (see the Resources section later).

CONSTRUCTION

Right then, so that's the basic outline finished with. We can now get into building the little rascal – as PhizzyB friend "Max" Maxfield might say!

Full details of the printed circuit board component and track layouts are shown in Fig.4. This board is available from the *EPE PCB Service*, code 227.

Note that IC4 *must* be omitted if Toolkit is to be powered from a regulated 5V source, such as from *PIC Tutor*. (In which case capacitor C6 can be omitted too.)

Additionally, resistors R9 and R10 must be replaced by link wires if Toolkit is to be connected to *PIC Tutor*. Failure to do so will result in incorrect voltage levels being applied to the DA6 and DA7 pins of the PIC on the *PIC Tutor* board.

Assemble the Toolkit Mk2 board in order of link wires first (note that one is under the IC6 socket position), and then the rest of the components in ascending order of size. Especially note the correct orientation of the semiconductors, electrolytic capacitors and switch S1. Do not insert any of the dual-in-line i.c.s into their sockets until after preliminary testing has been carried out (you'll be told when).

A special note on the use of sockets for IC2 and IC3 (the PIC sockets): ideally a ZIF (zero insertion force) socket should be used for IC2, although it can be an ordinary socket if funds don't run to ZIFs.

Now, on ZIFs, an 18-pin version is available and can be used for IC2. However, it is more expensive (for some odd reason) than a universal 24-pin ZIF. Consequently, provision has been made on the board for either version to be used (hence the two outlines shown for IC2).

It's up to you whether you solder the ZIF in place, or use an ordinary socket and then plug the ZIF into it when needed (the 18-pin ZIF is a bit difficult in this respect since its pins have been found to be thicker than those on the 24-pin).

It's worth noting, however, that if Toolkit is to be connected permanently to a *PIC Tutor* board, the socket for Toolkit's IC2 is likely to be seldom used and an ordinary d.i.l. socket will probably prove satisfactory (or even unnecessary), have a think about it.

ZIF sockets for IC3 are much more expensive still and it seemed inappropriate to even think about using them. Thus the board has been designed for ordinary d.i.l. 28-pin and 40-pin sockets to be nested in the same location.

The 28-pin socket is made up from a 20-pin and an 8-pin (narrow, 0.3-inch) d.i.l. socket. The 40-pin (broad, 0.6-inch) is made from two 20-pin s.i.l. (single-in-line) strips. A 40-pin d.i.l.

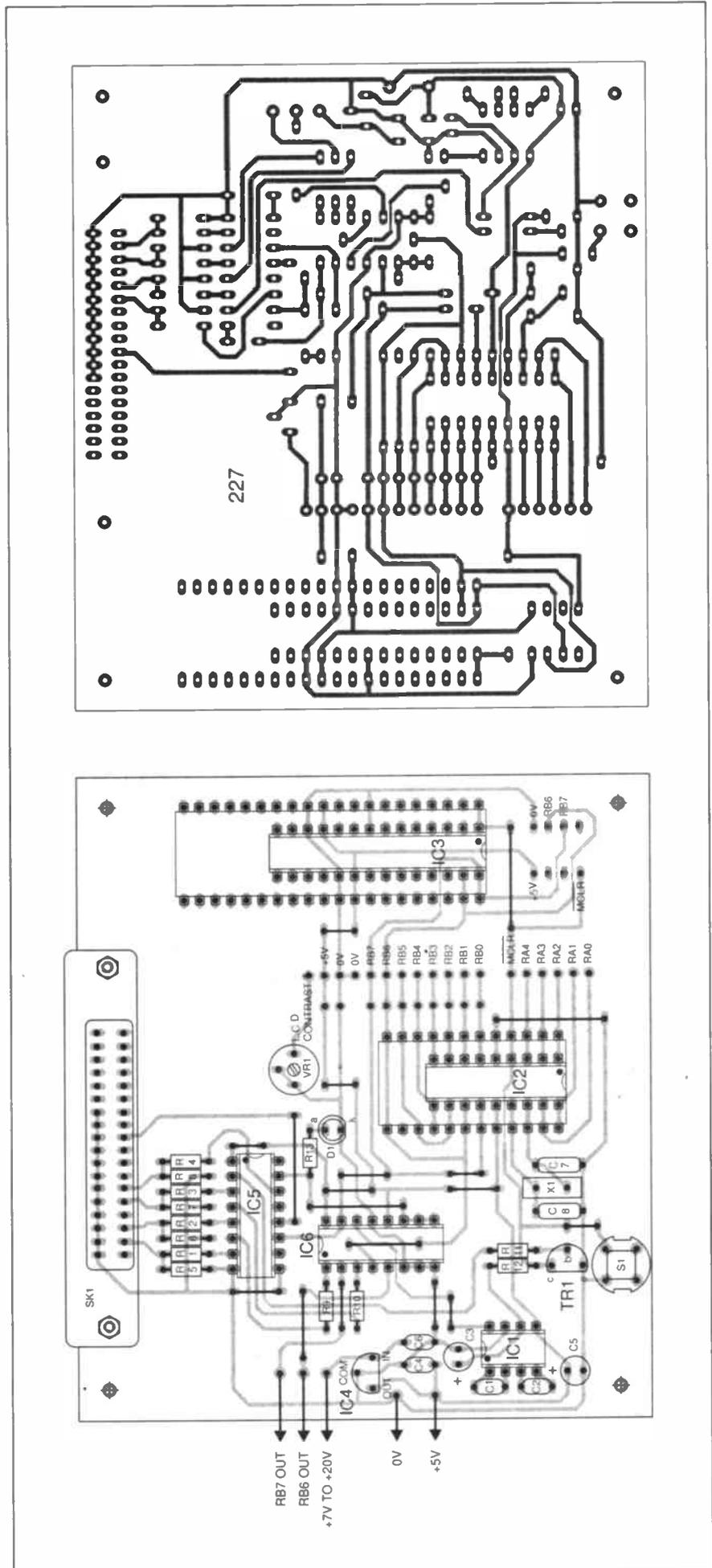


Fig.4. Component and full size track master pattern layouts for PIC Toolkit Mk2.

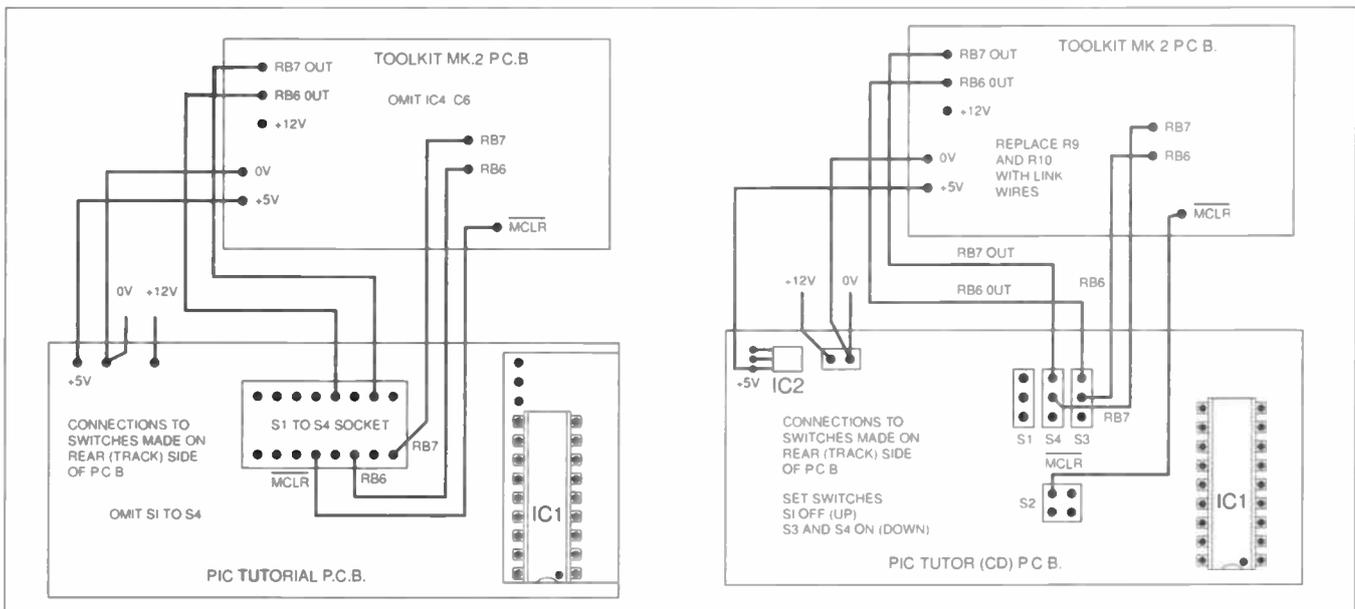


Fig.5. Optional connections between Toolkit Mk2 and the PIC Tutorial and PICtutor boards.

socket could be used if its cross struts are removed.

Since only a few of the IC3 position pads are actually used, you might consider using s.i.l. strip sections soldered only into those p.c.b. holes. It seems that this would actually make insertion and removal of an IC3 PIC a bit easier (this was only thought of after the prototype had been built. It has not been put to the test!).

At the bottom right of the p.c.b. is shown an additional 8-pin socket. It is from this socket that power and programming connections could be made to a prototype development board. Solder its connecting wires into another 8-pin d.i.l. socket and plug it into Toolkit's 8-pinner. Alternatively, you could just solder the connecting wires to the correct terminal pins on the board.

PIC TUTOR CONNECTIONS


This brings us to using Toolkit with either of the two versions of the *PICtutor* board.

Details of the connections to the *PIC Tutorial* board published in March '98 are shown in Fig.5. This board uses a 4-switch module for S1 to S4 and this should be removed. Then solder the Toolkit connections to the *trackside* of the *PIC Tutorial* board (noting that Fig.5 shows them from the component side).

Connections to the board for the CD-ROM based *PICtutor* are also shown in Fig.5. With this board, different switch types and positioning were used. The switches for this board should be left in position. Note that switch S1 must remain permanently Off (up), while S3 and S4 must be set permanently On (down). The connections are again made to the trackside of the board.

Beware that you make these connections to the commercially manufactured and assembled Tutorial boards entirely at your own risk – their guarantees are invalidated by such action.

The 0V connection to this board (CD-

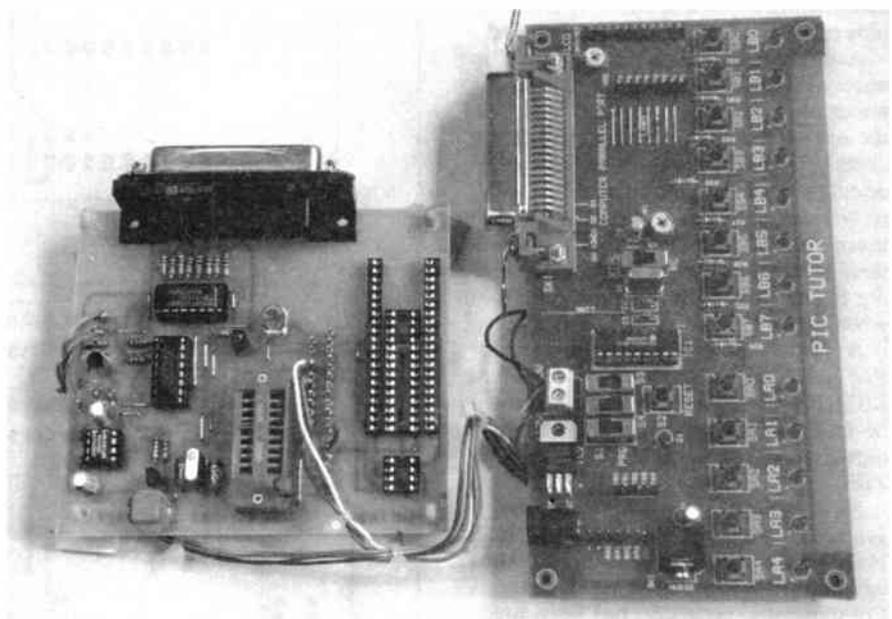


Toolkit Mk2 connected to the PICtutor board.

ROM *PICtutor*) may be connected to the 0V terminal of the on-board power input connector. The +5V connection should be soldered to the +5V (Out) pin of *PICtutor's* regulator IC2, preferably on the track side.

As an alternative, you could retain Toolkit's IC4 and C6 and take the +12V connection from (CD-ROM) *PICtutor's* power input connector to the +12V pin on Toolkit. Do not connect this +12V supply to any other Toolkit pin!

For workbench convenience, it is preferable to keep the interconnecting wires short-ish (see photograph), although the author has often had programming connection leads of as long as a metre without experiencing problems.

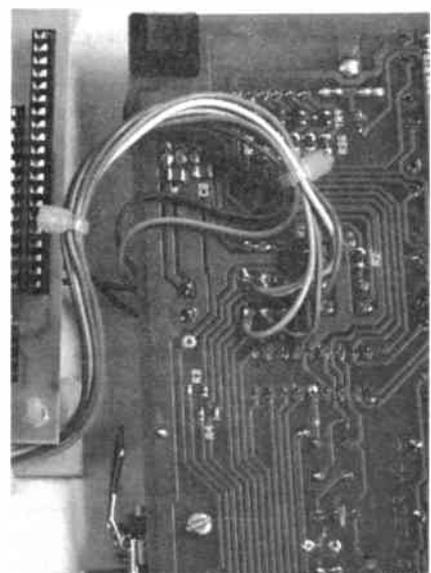Note that the program sending aspect of the Toolkit Mk2 software can be used directly with either of the *Tutor* p.c.b.s., without them being connected to the Toolkit p.c.b., just plugging the computer connector into the *Tutor* board as normal.



Trackside detail of the PICtutor board connections to Toolkit.

However, there is no screen advice given about when the *Tutor* board switches S1 to S4 should be used. You must remember to use them in the order discussed in the *Tutor* text when you are asked if you want to Process this Program.

Carry out the switching procedure and then press <Enter>. When advised that the sending is complete, again use the switches to terminate programming.

Verification and disassembly are never available when the *PIC Tutor* boards are used on their own without the Toolkit p.c.b. connected, irrespective of your computer's ability to actually read from its printer port.

COMPUTER LEAD

It is strongly recommended that a proper ready-made printer connecting cable (normal – Centronics) with integral connectors is used to couple Toolkit to the computer.

It is, though, permissible to make your own simpler connecting lead, referring to Fig.6 for the pins involved.

Here now, we must reiterate the correction we previously published to Fig.7 of *Toolkit Mk1* which showed the use of printer port pin 11 instead of the correct pin 10 (as now shown in *Toolkit Mk2*'s Fig.6). The error was compounded by both the text and the drawing referring to the computer's Busy line being used to read data from the PIC. In fact, the term *Acknowledge* should have been used instead of *Busy* and, as some readers pointed out, Busy is on pin 11, and Ack is on pin 10.

We now categorically re-state that both versions of *PIC Toolkit* use Acknowledge on pin 10 and the software for both is written to read pin 10 via its respective port register. Contrary to the assertion of a few readers, there are no errors on the *Mk1* p.c.b.

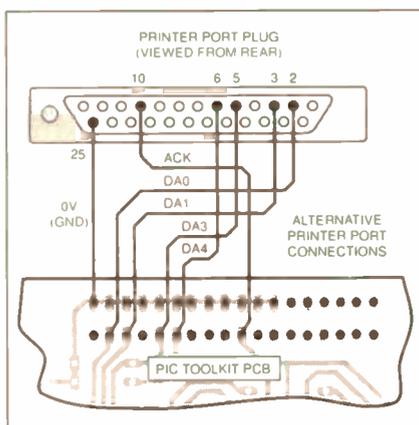


Fig.6. Alternative connections between Toolkit Mk2 and the computer.

SOFTWARE LOADING

Software for Toolkit Mk2 is available on 3.5-inch disk and from the *EPE* web site (see later). Although originally written in QuickBASIC, it has been compiled as an independent suite of programs (.EXE) that run without the need to have

QuickBASIC on your computer.

(The author's original .BAS source code files – in text fashion – are also on the same disk for the benefit of those who wish to examine them through a text editor (e.g. EDIT) or QuickBASIC/QBasic. Unless you really know about writing such .BAS programs, do not try to amend or run them. If you do run them, you will need to do so from the same directory in which your Basic resides and amend the TK.BAT file creation in TKSET06.BAS accordingly.)

The stand-alone (.EXE) files are installed into directory C:\PIC which, if it does not exist already, is created automatically by the installation routine. All operations within Toolkit depend on this directory as being the "home" directory and no other can be used.

The recommended installation is intended to be done with the disk in Drive A, and the operating system in DOS mode. If you are already in Windows, exit from it back to the MS-DOS prompt (via Program Manager for Win 3.1 or the Shutdown facility for Win 95). The DOS prompt is likely to look like C:\> or C:\WINDOWS>. From this prompt type A: to enter Drive A.

Now type TKINSTAL. This auto-installation routine creates the C:\PIC directory (if necessary) and copies the relevant files into it. Once that has been done, the installation routine calls the main program (TKMAIN02).

At this point (and for reasons unknown) the instruction "Hit any key to return to SYSTEM" might appear. Do as it says and hit any key.

On entry, TKMAIN02 checks whether file C:\PIC\TKFACTS.TXT exists. If the answer is false, the software assumes that it has not been run on this computer before, and calls up (Chains to) the Setup program TKSET06.

Many functions are performed by this program. For starters, an opening screen welcomes you and describes what takes place next. The first of these actions occurs via the next screen and asks you to press various keyboard keys and check what voltage readings (using a multimeter) are obtained on various parts of the Toolkit board (and *PIC Tutor* board if connected). Toolkit must, of course, be connected to the computer and to a suitable power supply. Any PIC in Toolkit or *PIC Tutor* should be removed before the power is switched on.

PORT TESTING

Now, it's possible that your computer may not have its printer port register set



The setup screen. It is interactive and allows you to fully check the connections between the computer and Toolkit, and ascertain if the port allows data to be read back.

to 0378 hex (as many consider to be the norm), it may be set to 0278 or 03BC hex. Initially, the Toolkit software is set to output via the 0378 register. You will only get the correct responses from the DA0 to DA4 pins if this is the register address set into the computer.

If you get no response, press P (for port) to change the register being examined by the software to 0278, and try again. If still no response, again press P to change to 03BC. A third press of P will return you to 0378.

If none of the register values produce the correct voltage reading on your meter, thoroughly recheck the connections between the computer and Toolkit.

Once you have found the register that produces a response, do not press P again.

During this process, the software assesses whether, with DA4 high, the logic on DA0 is readable via the ACK line. If at least five matches occur in sequence, it is assumed that the ACK pin can be read. The computer now beeps at you and an asterisk statement informs that Verifying is OK on that port.

If this statement refuses to appear, even though your voltage readings show that you are on the correct register, then your computer cannot read the data on pin 10. Regretfully, this means that it can neither verify nor disassemble from a PIC. It will be able to program the PIC, though, if you've found the correct responses through the meter readings.

When the beep occurs, or when you find that it's not going to, press <Enter> to continue the setting up.

Incidentally, it is permissible to run Setup with a PIC in the socket. You must ensure, though, that one of the earliest keys you press is that which resets the PIC. Failure to do so could result in incorrect responses from the output line back to the computer, and its ability to read back not recognised by Toolkit's software.

FILES SETUP

Stage two of setting up involves the creation of many files which are called periodically by the various routines.

Amongst them are some test files (.ASM and .MSG).

All these files are created within the C:\PIC directory and are prefixed by the letters "TK", e.g. TKTEST1.ASM.

This stage of setting up is very quick, the author's various computers taking between about two and four seconds. When the screen tells you it's complete, pressing any key returns you to program TKMAIN02, which now displays the main menu of options available.

Each option is prefixed by a number or letter, and pressing that key selects that option. Alongside many of the options is a list of default file names. You will see, for example, alongside "A Assemble TASM Text To Binary", the default is C:\PIC\TKTEST1.ASM, others have the statement NONE YET. The latter will be updated in due course, depending on what other actions are subsequently taken.

If the port test has revealed that the computer cannot read data from Toolkit, three options will be "greyed" and the word Unavailable will be shown in the default column. It means what it says – you cannot access these functions, nor will the software try to verify code that has been sent to the PIC.

In writing this software, much emphasis has been placed on its ease of use, and where possible default choices are offered which merely require the pressing of a single key (frequently just the <Enter> key). Also, default file names are kept updated to suit circumstances, but remain unchanged where appropriate. This means, for example, that you can repeatedly return to a particular routine and still have immediate use of the same file name that you used last time you entered that routine.

PROGRAM ASSEMBLY

Let's show you an example of using defaults. You have seen that C:\PIC\TKTEST1.ASM is the Assembly default name. This means that this file is ready to be assembled from a

.ASM file to a .OBJ file suitable for sending to the PIC. (Note that it is only .ASM files using TASM grammar that can be assembled by this routine. MPASM files need translating through another menu option to make them suitable.)

First, switch off Toolkit, insert a PIC16C84 or PIC16F84 into the correct socket on Toolkit (or that on PIC Tutor if it's being used – but never have more than one PIC anywhere in the Toolkit/Tutor system), and switch on. We shall now assume that this PIC has never been used before and that you will not find any response from any of the PIC's data pins on a meter (or on the Tutor I.e.d.s).

From the main menu, press A to enter the Assembly program (a separate chained program named TKPROG02). The screen will confirm that you are in the Assembly routine and that you have several choices: pressing M <Enter> will return you to the main menu and D <Enter> will call up the directory. Any file selected from the directory will then become the default file (more on this later, and on the other statements now shown on screen).

You will also see that C:\PIC\TKTEST1.ASM is shown as the default file now available and that pressing <Enter> on its own will cause it to be assembled. You also have the choice of entering your own file name, pressing <Enter> to complete it (should you enter a name that does not exist, you will be told so and offered the chance to enter another name).

For now, just press <Enter> on its own. The routine then opens the file you have called, loads and assembles it. While it's doing so, progress statements appear on the screen plus the current time at which they occur (this is only for interest). You will see that it has taken about two seconds for this file.

Also shown is the byte count (actually the number of 14-bit commands) of the assembled code (14) and the number of

lines in the original source code (28). An error count is shown too – the program has been checking your code while assembling it, seeing if there's anything that it doesn't recognise and if so incrementing the error count on each occasion. An error file (.ERR) is also written to with the details. On this occasion the count is 0.

If errors are found, you can exit to DOS EDIT to correct them. More on the use of the EDIT facility in Part 2.

Now, though, since the code has been assembled successfully, it is ready to be sent to the PIC. Following the screen instruction, press any key to return to the main menu.

Back in the main menu you will see that option 2, Program PIC with TASM Binary, now has a default file name beside it whereas before it just said NONE YET. The file name is basically the same as that just used, but now with a .OBJ ending instead of the .ASM, i.e. C:\PIC\TKTEST1.OBJ. The original Assemble default name is still shown as previously.

The .OBJ file is now ready to be sent to the PIC. But on this occasion, because we are assuming the PIC itself has never been used before, we must configure it to suit the application in which it is to be used.

During assembly, three other files are created as well, with extensions of .ERR (containing assembly error information if applicable), .REF (used only during assembly and of no user value), and .LST (showing the original .ASM text, hex values of the assembled codes, the PIC addresses at which they will be placed plus a text line count). At the end of the file, any error information is repeated, plus the values/names for all "equates" and labels.

NEXT MONTH

In Part 2 we reveal the rest of the sophisticated PIC programming options provide by Toolkit Mk2. The author's finding it to be a Dream Machine to work with!

(In the meantime – to exit the software, press Q from main menu. To restart from DOS type TK from the PIC directory.)


RESOURCES

Software for PIC Toolkit Mk2 is available on 3.5-inch disk from the Editorial office and as a free download from the EPE web site – see Shop Talk column in this issue.

Data sheets for PIC devices are available from Microchip's web site at <http://www.microchip.com>.

Back Issues of Toolkit Mk1 (July '98), the PIC16F87x Review (Apr '99) and reprints (back issues now all sold) of the PIC Tutorial articles of Mar-May '98 are available from the EPE Editorial office (see Back Issues page 385).

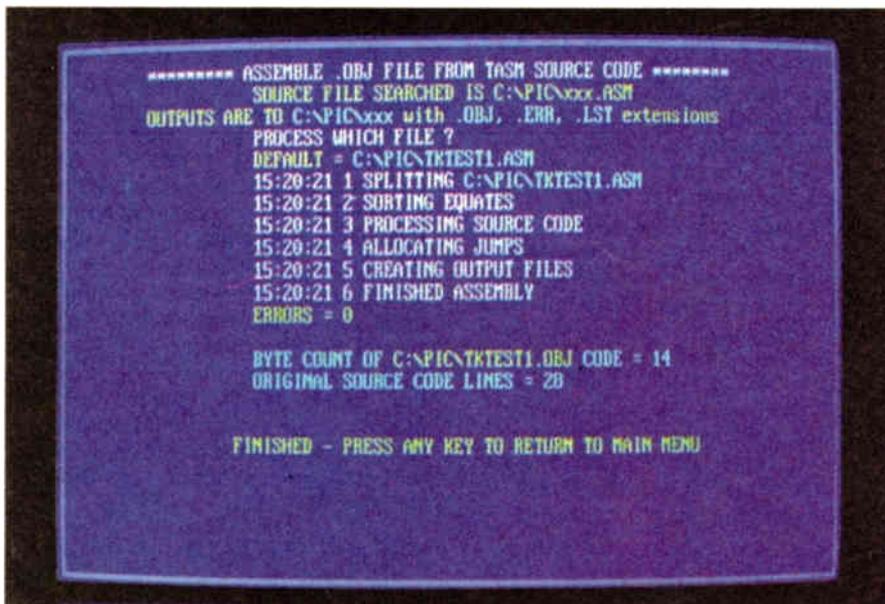For details of the PICutor CD-ROM see our CD-ROMs for Electronics page 364.



A typical screen display following assembly of a source code file to an object file.

PIC BASIC

Write your PICmicro programs in BASIC!

Quicker and easier than "C" or assembler Expanded BASIC Stamp I compatible instruction set. True compiler provides faster program execution and longer programs than BASIC interpreters. 12CIN and 121COUT instructions to access external serial EEPROMs. More user variables Peek and Poke instructions to access any PICmicro register from BASIC. Serial speeds to 9600 baud. In-line assembler and Call support (call your assembly routines). Supports PIC12C57x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 92x and PIC16F8x microcontrollers. Use in DOS or Windows Compatible with most PICmicro programmers.

The low-cost PicBasic Compiler (PBC) makes it easy to write programs for the last Microchip PICmicro. PBC converts these programs into hex or binary files that can be programmed directly into a PICmicro microcontroller. The easy-to-use BASIC language makes PICmicro programming available to everyone with its English-like instruction set. No more scary assembly language!

The **PicBasic Pro** Compiler runs on PC compatibles. It can create programs for the PIC12C57x, PIC12C67x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 92x, PIC16CE66x and PIC16F8x microcontrollers. The PicBasic Pro Compiler instruction set is upward compatible with the BASIC Stamp II and Pro uses B52 syntax. Programs can be compiled and programmed directly into a PICmicro, eliminating the need for a BASIC Stamp module. These programs execute much faster than their Stamp equivalents. They may also be protected so no one can copy your code!


Pic Basic - £49.95

Pic Basic Pro - £149.95

Supplied with full documentation
Free PIC MACRO compiler
and
sample basic programs

EPIC™

- Low-cost programmer for PIC12Cxxx, PIC12CExxx, PIC14Cxxx, PIC16C505, 55x, 6xx, 7xx, 84, 92x, PIC16CE62x and PIC16F8xx microcontrollers
- ZIF adapters available for 8/18- and 40/28-pin DIP, 8-, 18- and 28-pin SOIC, 44-pin MQFP and 44- and 68-pin PLOC PICmicro
- Runs off two 9-volt batteries or optional AC adapter
- Connects to PC parallel printer port
- Software upgradeable for future PICmicro
- Includes "8051" style PICmicro micro emulator
- Available assembled and tested or as bare board with diskette

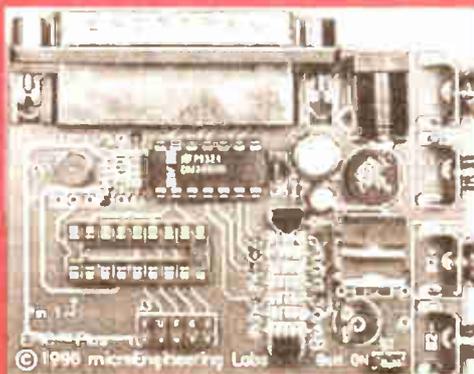

SUPPORTS THE NEW PIC16C87x
Available from CROWNHILL

EPIC Programmer £49.95
or **£35** if purchased with
PIC BASIC or Pro
25-pin cable £5.95
PIC16F84 £1.90

Call Now for a brochure and full list of Basic Instructions
or <http://www.crownhill.co.uk/picbasic/home.html>

Alli plus £5 P&P and 17.5% VAT


Join the world wide PIC Basic mail list and access the PIC Basic Knowledge Base via FTP
E-mail: majordomo@qunox.net with "subscribe picbasic-1" in the message

PIC16F84-04P	£1.90 each
PIC12C50B-509	£0.85 each
24LC16	£0.75 each
24LC65	£1.50 each
PIC16C620	£1.95 each
PIC16C821	£2.25 each
PIC16C622	£2.50 each

LCD DISPLAYS

Various types available from
£7.50 (2x16 line)
Ideal for use with PIC Basic.
Example code supplied

with every unit

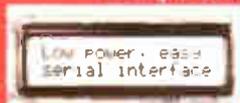

Serial LCD Display
Drivers (PIC16F84)
£2.00

PIC PROGRAMMER KIT

Programs the Popular PIC 16C84, 16F84, 24xx series serial memory devices. Connects to the serial port of a PC and requires NO EXTERNAL power supply. The kit includes instructions for assembly, circuit diagrams and component layout.

This handy kit programmer is easy to use, taking no more than 20 minutes to assemble and test. The Professional quality PCB is double sided, through plated with 35mm holes and comes pre-drilled for PC-board assembly. It is supplied with drive software for use in DOS or a 32-bit PC, powered and used with a 25-pin cable, a 9V battery and a Disk for all necessary drivers, test and data files for PIC devices, including FREE Assembly and Simulator.

Only £15.00 including Delivery and VAT

(includes 4x 9V 500mAh 9V battery cable to connect to serial port of PC)

CABLE £5.95 VAT AND DELIVERY



PIC Micro CD ROM (packed with 100MB of information) all current data sheets, Programs and Diagrams, Applications notes, PDF Views, includes TRIS, PIND and TETRIS and many other routines for a PIC 84 BASIC language ASSEMBLY routines.
£10 inc P&P & VAT

AMAZING LOW PRICES

Crownhill Associates Limited

The Old Bakery, New Barns Road, Ely, Cambridge, CB7 4PW

Tel: 01353 666709

Fax: 01353 666710

www.crownhill.co.uk

E-mail: sales@crownhill.co.uk

Transform your PC.... Into an oscilloscope, spectrum analyser and multimeter...

The ADC-200 range of PC based oscilloscopes offer performance only previously available on the most expensive 'benchtop' scopes. By intergrating several instruments into one unit, the ADC-200 is both flexible and cost effective.

Connection to a PC gives the ADC-200 the edge over traditional oscilloscopes: the ability to print and save waveforms is just one example. Units are supplied with PicoScope for Windows which is powerful, yet simple to use, with comprehensive on line help.



Applications

- ▼ Video
- ▼ Automotive
- ▼ Electronics design
- ▼ Production line tests
- ▼ Fault finding
- ▼ Education

All units are supplied with software, cables and power supply. Prices exclude VAT.

Features

- ▼ A fraction of the cost of comparable benchtop oscilloscopes
- ▼ Up to 100 MS/s sampling
- ▼ Advanced trigger modes- capture one off events.
- ▼ Up to 50 MHz spectrum analyser
- ▼ Large buffer memory

<i>ADC-200/100</i>	£499
<i>ADC-200/50</i>	£399
<i>ADC-200/20</i>	£299



A scope at your fingertips.....

Once oscilloscopes were heavy and clumsy to handle, but over the years they have become smaller and smaller. The latest development in this field has just arrived: a digital storage oscilloscope in a handy slim housing, scarcely longer than a pencil and about as thick as your thumb. Despite its small size, its performance can match that of a service oscilloscope.



ONLY £80

- ### Applications
- ▼ On-the-spot measurements
 - ▼ Hobby electronics
 - ▼ Measurements in amplifiers
 - ▼ Production line tests

- ▼ Can use PC display
- ▼ Sample rates from 50ns to 1ms
- ▼ Up to 20 MS/s

Prices exclude VAT


Call for a FREE software demonstration disk or visit our web site

Fax: +44 (0)1954 211880 Tel: +44 (0)1954 211716

E-mail: post@picotech.co.uk Web: www.picotech.com


PICO
Technology Limited

INGENUITY UNLIMITED

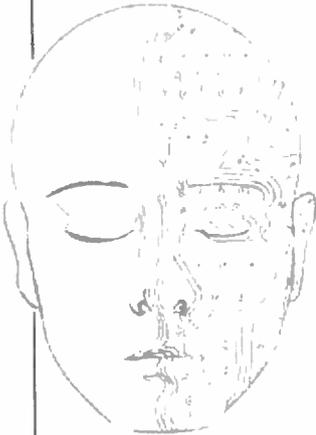

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit tips, not simply mechanical or electrical ideas. Ideas *must be the reader's own work and not have been submitted for publication elsewhere*. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should preferably be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. **Please draw all circuit schematics as clearly as possible.**

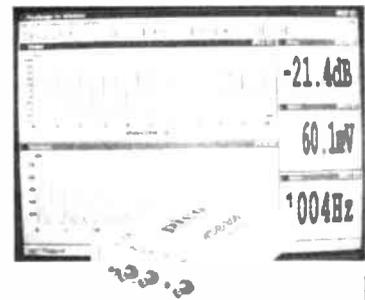Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. They could earn you some real cash and a prize!



WIN A PICO PC BASED OSCILLOSCOPE

- 50MSPS Dual Channel Storage Oscilloscope
- 25MHz Spectrum Analyser
- Multimeter
- Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours.

Every six months, Pico Technology will be awarding an ADC200-50 digital storage oscilloscope for the best IU submission. In addition, two single channel ADC-40s will be presented to the runners up.

Photo Slave Flash Unit

— *Flash Pictures*

THE USE of a second "slave" flash as the main light enables the use of creative lighting effects in flash photography. By placing a second flash at, say, 45 degrees to the subject, shadows are formed to show its texture and form, and dramatic effects such as backlighting, strong side light etc. are also possible.

The flash on the camera fills in or softens the shadows made by the secondary flash. Using the circuit described in Fig.1, the camera flash also triggers the slave flash.

Firing of the camera flash is detected by a photo diode or phototransistor TR1. Capacitor C1 blocks the effect of A.C.-generated ambient light and allows only the pulse caused by firing the camera flash to reach the amplifier formed by transistor TR2 and resistors R3 and R4.

The amplified pulse is fed to the monostable formed by IC1, R5, C2 and C3. The fixed-length pulse produced by this is passed through resistor R6 and triggers thyristor CSR1. This shorts the two switch terminals of the secondary flash which fires.

The circuit works reliably in ambient light conditions ranging from full sunlight to a darkened room, and also responds to bounced flash. In practice that it is not necessary to

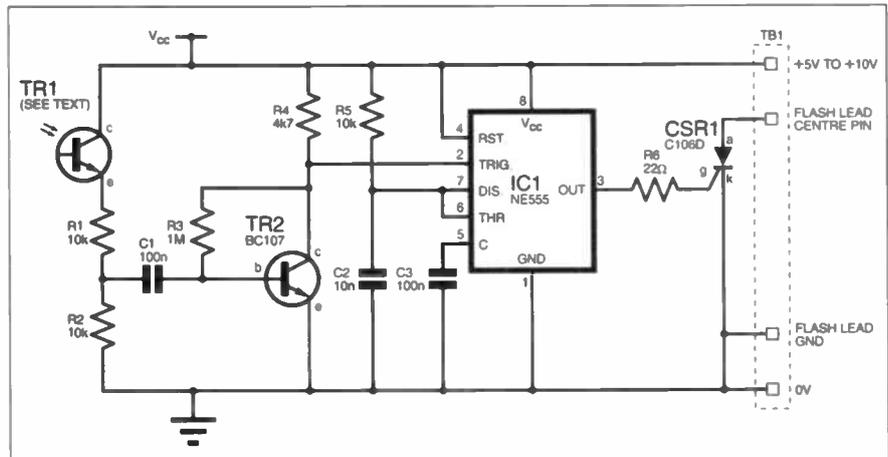


Fig.1. Photo Slave Flash Unit circuit diagram.

point the sensor at the primary flash, giving greater scope for positioning the slave to give the best lighting effect.

Component choice is not critical. TR1 has been tested using a variety of surplus photo diodes and phototransistors with consistent results. TR2 could be any general purpose *npn* silicon transistor. The circuit could either be powered from a 6V to 9V battery or from the flash gun's battery.

For further ideas, if TR1 were replaced by a microphone and amplifier the secondary flash could be triggered by sound. This would allow dramatic photographs of such things as breaking glass. A security camera could be developed to photograph burglars if the output from an intruder alarm replaced the photo sensor.

Peter Taylor,
Mickleover, Derby.

Siren Sounder — *Trako Model*

A SIMPLE alarm circuit which is fun to build and will find many uses, perhaps as a warning device or as a novelty, is shown in Fig.2. The alarm is built around two 555 timers, which act as oscillators to produce a distinct two-tone effect. Note that only one resistor and capacitor is used on each oscillator.

Oscillator IC1 runs at a lower frequency than IC2. The low frequency signal generated by IC1 modulates the frequency of IC2 which changes the audio tone.

The output from IC2 at pin 3 is fed to the base of *pnp* transistor TR1, which amplifies the sound and drives the speaker, LS1. Resistor R4 limits the collector current.

The frequency and timing of each oscillator is dependent on R1 and C1 for IC1, and R3 and C2 for IC2 and these components could be changed to alter the note.

P. Graham,
Yate, Bristol.

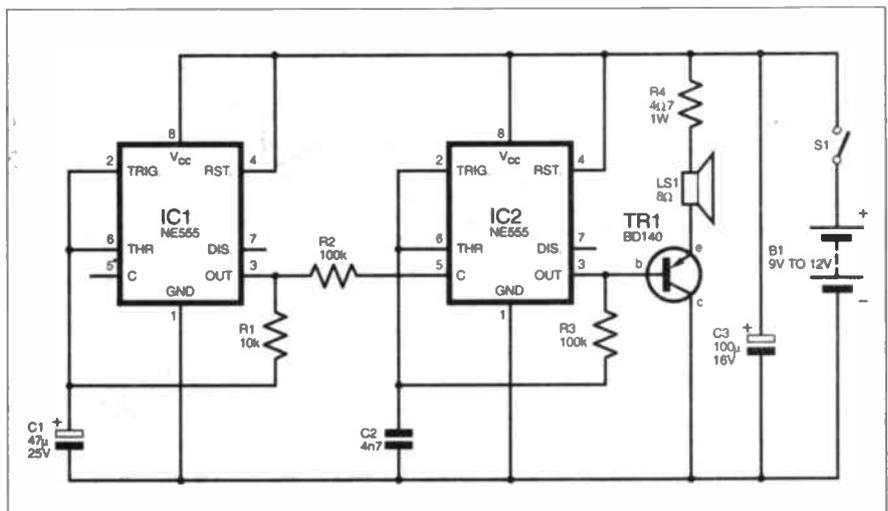


Fig.2. Circuit diagram for a simple Siren Sounder.

Space Case Alarm -

By Rev. Thos. Scarborough

SCHOOL pupils often use a strong plastic "space case" to house their ruler, pencils, etc. My young son wanted me to rig his space case with an alarm, so that it would go off when any other pupil opened the case without his permission. In the circuit diagram of Fig.3, IC1 is an inexpensive CMOS LSI melody generator, which comes in different versions (Christmas Jingles, Happy Birthday, etc.).

When a battery is connected, IC1 plays a melody once, then stops. While the sound is not very loud, it is certainly enough to attract the attention of a teacher! Switch S2 is a miniature slide switch which enables the

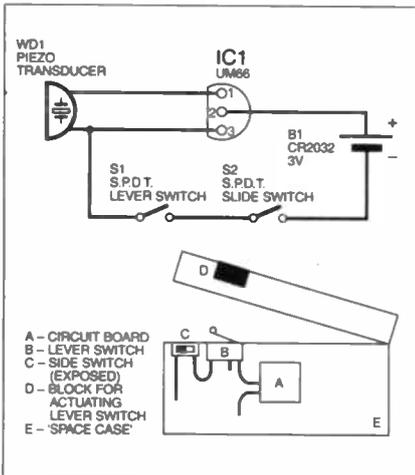


Fig.3. Space Case Alarm.

PICO PRIZE WINNERS

It's time to decide the winners of superb PICO Technology PC-based oscilloscopes, once again generously donated by PICO (www.picotech.com) for three lucky entrants whom in our judgment submitted the best ideas published in the past six months. As always, every entry was judged on a number of criteria including the extent of "lateral thinking" or novelty, technical merit, resourcefulness, appropriateness, and overall completeness.

After careful consideration, *EPE* Editor Mike Kenward and *Ingenuity Unlimited* host Alan Winstanley finally selected the following winners:

WINNER - receives an impressive PICO ADC200-50 PC Digital Storage Oscilloscope, worth over £450!

Naseer Ahmad - Using Solenoid Valves in Place of Motorised Valves (January 1999). An ingenious design based around a switched mode chip adapted for use in this control application.

RUNNERS-UP - both are lucky recipients of PICO ADC-40 Single-Channel PC-Based Oscilloscopes.

Duncan Boyd - Audio Limiter (April 1999). We felt this was a novel application for a limiting circuit which used a transconductance amplifier for the front end.

J. D. Gray - AF Sweep Signal Generator (February 1999). This design was thoroughly worked and presented.

pupil to set the alarm and is mounted inconspicuously in the side of the case, or even inside. Microswitch S1 triggers the alarm when the case is opened.

The battery is a small 3V lithium manganese cell which would probably give a year of use or more. Leads may be soldered directly to the battery but this must be done very rapidly, taking care to avoid excess heating. Use anti-static precautions when handling IC1 with care.

As simple as the design is, "dad" is delighted to report that other pupils were offering to pay my son's dad to construct a similar alarm for them, too!

*Rev. Thos. Scarborough,
Fresnaye, Cape Town, RSA.*

INGENUITY UNLIMITED

BE INTERACTIVE
IU is *your* forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize!

Electronic Rotary Switch - A Goox!

Substitute

IN THE circuit of Fig.4, a novel approach has been adopted for replacing mechanical rotary switches used in many types of circuit. A momentary push-to-make switch together with some electronics offers an option of making an electronic rotary switch to replace a mechanical one.

At power-on, a reset signal is applied by IC3a/b to reset IC1 and IC2. The output will be selected sequentially from Q0 to Q9 of IC2 and the selection will be advanced every time S1 is closed.

The R-S latch IC1 is used for switch debouncing and is set high every time S1 is pressed and reset after a delay generated by resistor R1 and capacitor C1. Hence it provides a debounced pulse, as a clock input to IC2.

The circuit acts similarly to a multi-way switch action for which a 4017 counter/divider has been used. The selection will be valid until the next switching action occurs.

When any Q output of IC2 is selected, it will be at a high state (logic 1). This can be used to activate a control pin of IC4 and turn a corresponding bilateral switch on. A 4016 Quad Bilateral Switch is used for this purpose.

At the bilateral switch output, the user's circuit can be interfaced as required, so that

this circuit will offer a multi-way selection to the circuit. This could be useful in case of the selection of analogue signals which the 4016 can also handle. Digital circuits may be connected directly to the output of IC2.

A maximum of nine steps' selection is offered by the 4017. On every tenth switching, it will reset itself through IC3b and the cycle will repeat from Q0 onwards.

To provide fewer selections you can select Q outputs of your choice to reset the circuit. For instance, if you need only four selections, then connect Q4 (pin 10) to the OR gate IC3b pin 6 and now on every fifth selection' the circuit will reset and start from Q0.

B. D. Mehta, Ahmedabad, India.

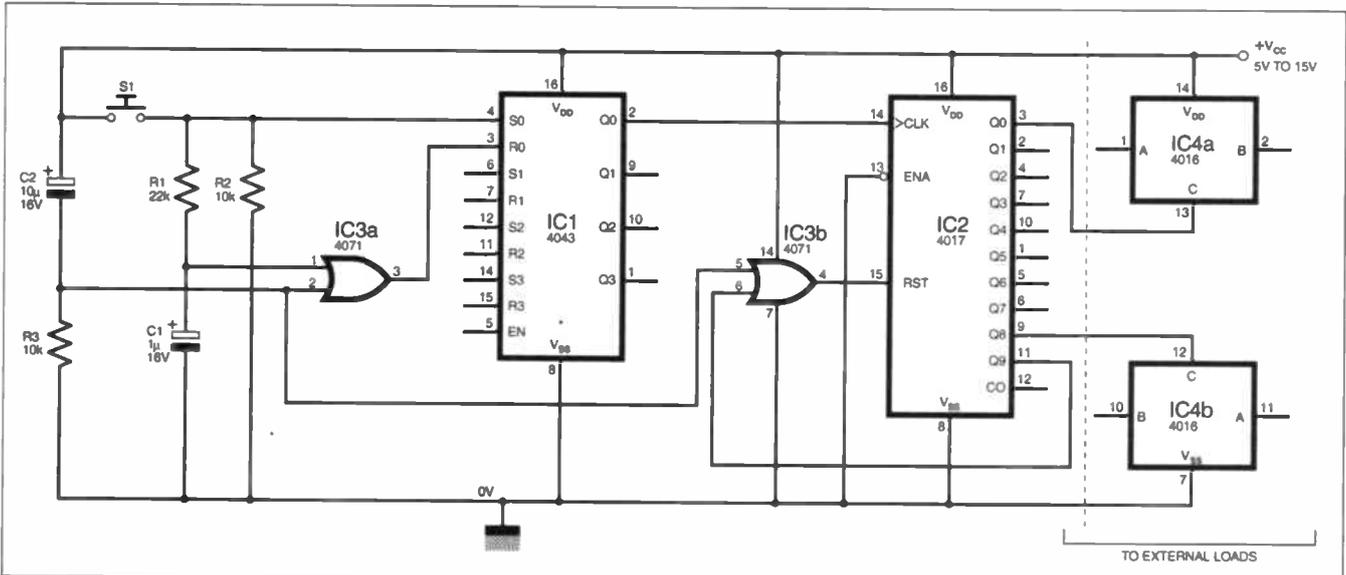


Fig.4. Circuit diagram for an electronic rotary switch.

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3V-12V operation. 500m range..... **£16.45**

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter. Just 17mm x 17mm including mic. 3V-12V operation. 1000m range..... **£13.45**

STX High-performance Room Transmitter

High performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6V-12V operation. 1500m range. **£15.45**

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9V-12V operation. 3000m range..... **£16.45**

VXT Voice-Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range. **£19.45**

HVX400 Mains Powered Room Transmitter

Connects directly to 240V A.C. supply for long-term monitoring. Size 30mm x 35mm. 500m range..... **£19.45**

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range..... **£22.95**

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range..... **£23.95**

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9V-12V operation..... **£22.95**

ATR2 Micro-Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line..... **£13.45**

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range..... **£15.95**

TLX 700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range..... **£13.45**

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range..... **£16.45**

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation..... **£22.95**

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation..... **£30.95**

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation..... **£50.95**

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range..... **£40.95**

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range..... **£40.95**

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m..... **£35.95**

QRX 180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as pre-built and aligned module ready to connect on board so no difficulty setting up. Output to headphones. 60mm x 75mm. 9V operation..... **£60.95**

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £2.00 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send Sterling Bank Draft and add £5.00 per order for shipment. Credit card orders welcomed on 01827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

★★★ Specials ★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way d.i.l. switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits)..... **£50.95**

Individual Transmitter DLTX..... **£19.95**

Individual Receiver DLRX..... **£37.95**

MBX-1 HI-FI Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your HI-FI, tape or CD and transmits HI-FI quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle.

Size 27mm x 60mm. 9V operation. 250m range..... **£20.95**

**SUMA
DESIGNS**

DEPT. EE
THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY, NEAR ATHERSTONE,
WARWICKSHIRE CV9 2LE
VISITORS STRICTLY BY APPOINTMENT ONLY



Tel/Fax:
01827 714476

DIRECT BOOK SERVICE

EPE BOOKS

ELECTRONICS TEACH-IN 88/89 INTRODUCING MICROPROCESSORS Mike Tooley B.A. (published by *Everyday Practical Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Microprocessors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering popular microprocessors.

And excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment.
80 pages **Order code TI-88/89** £2.45

TEACH-IN No. 7, plus FREE SOFTWARE ANALOGUE AND DIGITAL ELECTRONICS COURSE (published by *Everyday Practical Electronics*)

Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE
This highly acclaimed *EPE Teach-In* series, which included the construction and use of the *Mini Lab* and *Micro Lab* test and development units, has been put together in book form. Additionally, EPT Educational Software have developed a GCSE Electronics software program to complement the course and a FREE DISK covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The *Mini Lab* and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way; you will both see and hear the electron in action! The *Micro Lab* microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.
160 pages **Order code T17** £3.95



ELECTRONIC PROJECTS BOOK 1 (published by *Everyday Practical Electronics* in association with Magenta Electronics)

Contains twenty projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesizer, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three-Channel Sound to Light, BBC 16K sideways RAM, Simple Short Wave Radio, Insulation Tester, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser, Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider - (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccanear Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.
128 pages **Order code EP1** £2.45

The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

FOR A FURTHER SELECTION OF BOOKS SEE THE NEXT TWO ISSUES OF EPE.

Note our UK postage costs just £1.50 no matter how many books you order!

RADIO / TV VIDEO

ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS R. A. Penfold

This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.
109 pages **Order code BP356** £4.95

SETTING UP AN AMATEUR RADIO STATION I. D. Poole

The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aerials to use; Methods of construction; Preparing for the licence.

An essential addition to the library of all those taking their first steps in amateur radio.
86 pages **Order code BP300** £3.95

EXPERIMENTAL ANTENNA TOPICS H. C. Wright

Although nearly a century has passed since Marconi's first demonstration or radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.
72 pages **Order code BP278** £3.50

25 SIMPLE INDOOR AND WINDOW AERIALS E. M. Noll

Many people live in flats and apartments or other types of accommodation where outdoor aerials are prohibited, or a lack of garden space etc. prevents aerials from being erected. This does not mean you have to forgo shortwave listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aerials that the author has proven to be sure performers.

Much information is also given on shortwave bands, aerial directivity, time zones, dimensions etc.
50 pages **Order code BP136** £1.75

PROJECT CONSTRUCTION

PRACTICAL REMOTE CONTROL PROJECTS Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infrared, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.
160 pages **Order code BP413** £5.99

PRACTICAL ELECTRONIC MODEL RAILWAY PROJECTS R. A. Penfold

The aim of this book is to provide the model railway enthusiast with a number of useful but reasonably simple projects that are easily constructed from readily available components. Stripboard layouts and wiring diagrams are provided for each project. The projects covered include: constant voltage controller; pulsed controller; pushbutton pulsed controller; pulsed controller with simulated inertia, momentum and braking; automatic signals; steam whistle sound effect; two-tone horn sound effect; automatic two-tone horn effect; automatic chuffer.

The final chapter covers the increasingly popular subject of using a computer to control a model railway layout, including circuits for computer-based controllers and signalling systems.
151 pages **Order code BP384** £4.99

A PRACTICAL INTRODUCTION TO SURFACE MOUNT DEVICES Bill Mooney

This book takes you from the simplest possible starting point to a high level of competence in handworking with surface mount devices (SMDs). The wider subject of SM technology is also introduced, so giving a feeling for its depth and fascination.

Subjects such as p.c.b. design, chip control, soldering techniques and specialist tools for SM are fully explained and developed as the book progresses. Some useful constructional projects are also included.

Whilst the book is mainly intended as an introduction, it is also an invaluable reference book, and the browser should find it engrossing.
120 pages **Order code BP411** £4.99

FAULT-FINDING ELECTRONIC PROJECTS R. A. Penfold

Starting with mechanical faults such as dry joints, short-circuits etc, coverage includes linear circuits, using a meter to make voltage checks, signal tracing techniques and fault finding on logic circuits. The final chapter covers ways of testing a wide range of electronic components, such as resistors, capacitors, operational amplifiers, diodes, transistors, SCRs and triacs, with the aid of only a limited amount of test equipment.

The construction and use of a Tristate Continuity Tester, a Signal Tracer, a Logic Probe and a CMOS Tester are also included.
136 pages **Order code BP391** £4.99

TEST EQUIPMENT CONSTRUCTION R. A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:- AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe.

The designs are suitable for both newcomers and more experienced hobbyists.
104 pages **Order code BP248** £3.99

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books, and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.
66 pages **Order code BP121** £3.99

ELECTRONIC PROJECT BUILDING FOR BEGINNERS R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including the following topics:

Component identification, and buying the right parts; Resistor colour codes, capacitor value markings, etc; Advice on buying the right tools for the job; Soldering, with advice on how to produce good joints and avoid "dry" joints; Making easy work of the hard wiring; Construction methods, including stripboard, custom printed circuit boards, plain matrix board, surface mount boards and wire-wrapping; Finishing off, and adding panel labels; Getting "problem" projects to work, including simple methods of fault-finding; In fact everything you need to know in order to get started in this absorbing and creative hobby.
135 pages **Order code BP392** £4.95

TWO EXCITING NEW BOOKS

Specially imported by *EPE*

Bebop To The Boolean Boogie


By Clive (call me Max) Maxfield

ORDER CODE BEB1 £24.95

An Unconventional Guide to Electronics Fundamentals, Components and Processes

The Foreword by Pete Waddell, Editor, *Printed Circuit Design*, reads:

"Personally, I think that the title of this tome alone (hmmm, a movie?) should provide some input as to what you can expect. But, for those who require a bit more: be forewarned, dear reader, you will probably learn far more than you could hope to expect from *Bebop to the Boolean Boogie*, just because of the unique approach Max has to technical material. The author will guide you from the basics through a minefield of potentially boring theoretical mish-mash, to a Nirvana of understanding. You will not suffer that fate familiar to every reader: re-reading paragraphs over and over wondering what in the world the author was trying to say. For a limey, Max shoots amazingly well and from the hip, but in a way that will keep you interested and amused. If you are not vigilant, you may not only learn something, but you may even enjoy the process. The only further advice I can give is to 'expect the unexpected'."

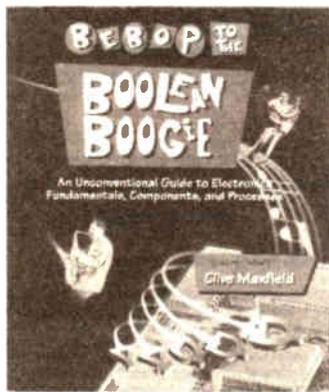

This book gives the "big picture" of digital electronics. This indepth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean Algebra and Karnaugh Maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more (including a recipe for a truly great seafood gumbo!).

Hundreds of carefully drawn illustrations clearly show the important points of each topic. The author's tongue-in-cheek British humor makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. A great reference for your own shelf, and also an ideal gift for a friend or family member who wants to understand what it is you do all day. . . .

By importing these books ourselves we have managed to make them available in the UK at an exceptional price.

Audio and Music

VALVE & TRANSISTOR AUDIO AMPLIFIERS

John Linsley Hood

This is John Linsley Hood's greatest work yet, describing the milestones that have marked the development of audio amplifiers since the earliest days to the latest systems. Including classic amps with valves at their heart and exciting new designs using the latest components, this book is the complete world guide to audio amp design.

Contents: Active components; Valves or vacuum tubes; Solid-state devices; Passive components; Inductors and transformers; Capacitors, Resistors, Switches and electrical contacts; Voltage amplifier stages using valves; Valve audio amplifier layouts; Negative feedback; Valve operated power amplifiers; Solid state voltage amplifiers; Early solid-state audio amplifiers; Contemporary power amplifier designs; Preamplifiers; Power supplies (PSUs); Index.

250 pages

Order code NE24

£19.99

AUDIO AMPLIFIER PROJECTS

R. A. Penfold

A wide range of useful audio amplifier projects, each project features a circuit diagram, an explanation of the circuit operation and a snipboard layout diagram. All constructional details are provided along with a shopping list of components, and none of the designs requires the use of any test equipment in order to set up properly. All the projects are designed for straightforward assembly on simple circuit boards.

Circuits include: High impedance mic preamp, Low impedance mic preamp, Crystal mic preamp, Guitar and GP preamplifier, Scratch and rumble filter, RIAA preamplifier, Tape preamplifier, Audio limiter, Bass and treble tone controls, Loudness filter, Loudness control, Simple graphic equaliser, Basic audio mixer, Small (300mW) audio power amp, 6 watt audio power amp, 20/32 watt power amp and power supply, Dynamic noise limiter.

A must for audio enthusiasts with more sense than money!
116 pages

Order code PC113

£9.95

MAKING MUSIC WITH DIGITAL AUDIO

Ian Waugh

In this practical and clearly-written book, Ian Waugh explains all aspects of the subject from digital audio basics to putting together a system to suit your own music requirements. Using the minimum of technical language, the book explains exactly what you need to know about: Sound and digital audio, Basic digital recording principles, Sample rates and resolutions, Consumer sound cards and dedicated digital audio cards.

On a practical level you will learn about: sample editing, digital multi-tracking, digital FX processing, integrating MIDI and digital audio, using sample CDs, mastering to DAT and direct to CD, digital audio and Multimedia.

This book is for every musician who wants to be a part of the most important development in music since the invention of the gramophone. It's affordable, it's flexible, it's powerful and it's here now! It's digital and it's the future of music making.

256 pages

Order code PC114

£14.95

Bebop Bytes Back

By Clive "Max" Maxfield and Alvin Brown

ORDER CODE BEB2 £29.95

An Unconventional Guide To Computers

Plus FREE CD-ROM which includes: Fully Functional Internet-Ready Virtual Computer with Interactive Labs

The Foreword by Lee Felsenstein reads:


"1. The more time you spend with this book and its accompanying CD-ROM, the more you'll get out of it. Skimming through it won't take you where you want to go. Paying serious attention, on the other hand, will teach you more about computers than you can imagine. (You might also see a few beautiful sunrises.)

2. The labs work on two levels: on and under the surface. When you're performing the labs you'll need to look for patterns that build up from individual events.

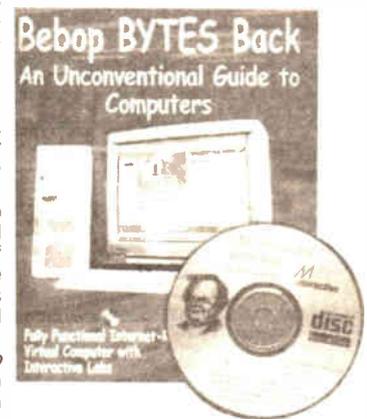3. When you're done, you won't look any different. You won't get a trophy or a certificate to hang on your wall. You'll have some knowledge, and some skill, and you'll be ready to find more knowledge and develop more skill. Much of this will be recognisable only to someone who has the same knowledge and skill."

This follow-on to *Bebop to the Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop I" left off, guiding you through the fascinating world of computer design . . . and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the accompanying CD-ROM (for Windows 95 machines only) contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the book contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers.

If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this one!



POSTAGE

You only pay

£1.50

per order
(UK postage)

NO MATTER HOW
MANY BOOKS
YOU ORDER

Overseas Readers see
ORDERING DETAILS on the
next page for overseas
postage prices

CIRCUITS AND DESIGN

AN INTRODUCTION TO PIC MICROCONTROLLERS

Robert Penfold

Designing your own PIC based projects may seem a daunting task, but it is really not too difficult providing you have some previous experience of electronics. The PIC processors have plenty of useful features, but they are still reasonably simple and straightforward to use. This book should contain everything you need to know.

Topics covered include: the PIC register set; numbering systems; bitwise operations and rotation; the PIC instruction set; using interrupts; using the analogue to digital converter; clock circuits; using the real time clock counter (RTCC); using subroutines; driving seven segment displays.

166 pages

Order code BP394

£5.99

PRACTICAL OSCILLATOR CIRCUITS

A. Flind

Extensive coverage is given to circuits using capacitors and resistors to control frequency. Designs using CMOS, timer i.c.s and op.amps are all described in detail, with a special chapter on "waveform generator" i.c.s. Reliable "white" and "pink" noise generator circuits are also included.

Various circuits using inductors and capacitors are covered, with emphasis on stable low frequency generation. Some of these are amazingly simple, but are still very useful signal sources.

Crystal oscillators have their own chapter. Many of the circuits shown are readily available special i.c.s for simplicity and reliability, and offer several output frequencies. Finally, complete constructional details are given for an audio sinewave generator.

133 pages

Order code BP393

£4.99

PRACTICAL ELECTRONIC CONTROL PROJECTS

Owen Bishop

Explains electronic control theory in simple, non-mathematical terms and is illustrated by 30 practical designs suitable for the student or hobbyist to build. Shows how to use sensors as input to the control system, and how to provide output to lamps, heaters, solenoids, relays and motors.

Computer based control is explained by practical examples that can be run on a PC. For stand-alone systems, the projects use microcontrollers, such as the inexpensive and easy-to-use Stamp BASIC microcontroller. These projects are chosen to introduce and demonstrate as many aspects as possible of the programming language and techniques.

196 pages

Order code BP377

£5.99

PRACTICAL ELECTRONICS HANDBOOK -

Fourth Edition. Ian Sinclair

Contains all of the everyday information that anyone working in electronics will need.

It provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Discrete component circuits, Sensing components, Linear I.C.s, Digital I.C.s, Microprocessors and microprocessor systems, Transferring digital data, Digital-analogue conversions, Computer aids in electronics, Hardware components and practical work, Standard metric wire table, Bibliography, The HEX scale, Index.

440 pages

Order code NE21

£14.99

COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages

Order code 160

£3.99

OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston

A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages

Order code NE14

£14.99

OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold

The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA preamplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages

Order code BP335

£4.95

A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and other logic "building blocks"; CMOS logic i.c. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

The emphasis is on a practical treatment of the subject, and all the circuits are based on "real" CMOS devices. A number of the circuits demonstrate the use of CMOS logic i.c.s in practical applications.

119 pages

Order code BP333

£4.95

AUDIO AND MUSIC

INTRODUCTION TO DIGITAL AUDIO

(Second Edition)

Ian Sinclair

Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and

methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages

Order code PC102

£7.95

PROJECTS FOR THE ELECTRIC GUITAR

J. Chatwin

This book is for anyone interested in the electric guitar. It explains how the electronic functions of the instrument work together, and includes information on the various pickups and transducers that can be fitted. There are complete circuit diagrams for the major types of instrument, as well as a selection of wiring modifications and pickup switching circuits. These can be used to help you create your own custom wiring.

Along with the electric guitar, sections are also included relating to acoustic instruments. The function of specialised piezoelectric pickups is explained and there are detailed instructions on how to make your own contact and bridge transducers. The projects range from simple preamps and tone boosters, to complete active controls and equaliser units.

92 pages

Order code BP358

£4.95

MIDI SURVIVAL GUIDE

Vic Lennard

Whether you're a beginner or a seasoned pro, the MIDI Survival Guide shows you the way. No maths, no MIDI theory, just practical advice on starting up, setting up and ending up with a working MIDI system.

Over 40 cabling diagrams. Connect synths, sound modules, sequencers, drum machines and multitracks. How to budget and buy secondhand. Using switch, thru and merger boxes. Transfer songs between different sequencers. Get the best out of General MIDI. Understand MIDI implementation charts. No MIDI theory.

104 pages

Temporarily out of print

PRACTICAL ELECTRONIC MUSICAL EFFECTS UNITS

R. A. Penfold

This book provides practical circuits for a number of electronic musical effects units. All can be built at relatively low cost, and use standard, readily available components. The projects covered include: Wah-Wah Units; Distortion Units; Phaser; Guitar Envelope Shaper; Compressor; Tremolo Unit; Metal Effects Unit; Bass and Treble Boosters; Graphic Equaliser; Parametric Equaliser. The projects cover a range of complexities, but most are well within the capabilities of the average electronics hobbyist. None of them require the use of test equipment and several are suitable for near beginners.

102 pages

Order code BP368

£4.95

LOUDSPEAKERS FOR MUSICIANS

Vivan Capel

This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages

Order code BP297

£4.99

BOOK ORDERING DETAILS

Our postage price is the same no matter how many books you order, just add £1.50 to your total order for postage and packing (overseas readers add £3 for countries in the EEC, or add £6 for all countries outside the EEC, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to Direct Book Service or credit card details, Visa or Mastercard - minimum credit card order is £5 - to: DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET BH21 1RW (mail order only).

Books are normally sent within seven days of receipt of your order but please allow 28 days for delivery (more for overseas orders). Please check price and availability (see latest issue of Everyday Practical Electronics) before ordering from old lists.

For a further selection of books see the next two issues of EPE.

DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD. Tel 01202 881749

Fax 01202 841692. Due to the cost we cannot reply to overseas orders or queries by Fax.

E-mail: editorial@epemag.wimbome.co.uk

BOOK ORDER FORM

Full name:

Address:

.....

..... Post code: Telephone No:

Signature:

I enclose cheque/PO payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard £ Card expiry date

Card Number

Please send book order codes:

.....

.....

Please continue on separate sheet of paper if necessary

EVERYDAY

PRACTICAL ELECTRONICS

BACK ISSUES



We can supply back issues of *EPE* and *ETI* (see panel) by post, most *EPE* issues from the past five years are available. An *EPE* issue for the last five years is also available - see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price.

DID YOU MISS THESE?

DEC '97

PROJECTS • Safe and Sound - Security Bleeper • Active Microphone • Car Immobiliser • Mini Organ.
FEATURES • TEACH-IN '98 - An Introduction to Digital Electronics-2 • Circuit Surgery • Interface • B² Spice Review • Ingenuity Unlimited • Alternative and Future Technologies-1 • Net Work - The Internet • Free Giant Data Chart - Formulae.

JAN '98 Photostats Only

PROJECTS • Disco Lights Flasher • Simple M.W. Radio • EPE Virtual Scope-1 • Surface Thermometer.
FEATURES • TEACH-IN '98 - An Introduction to Digital Electronics-3 • Circuit Surgery • Ingenuity Unlimited • Alternative and Future Technologies-2 • Net Work - The Internet • Free - Giant PIC Data Chart.

FEB '98

PROJECTS • Water Wizard • Kissometer • Waa-Waa Effects Pedal • EPE Virtual Scope - 2.
FEATURES • TEACH-IN '98 - 4 • Ingenuity Unlimited • Techniques-Actually Doing It • Circuit Surgery • Net Work - The Internet • Chip Special - HT7630 PIR Controller.



MAR '98 Photostats Only

PROJECTS • Lighting-Up Reminder • The Handy Thing • Switch-Activated Burglar Alarm • Audio System Remote Controller.
FEATURES • TEACH-IN '98 - 5 • Ingenuity Unlimited • Interface • Stripboard Magic Review • Circuit Surgery • Net Work • EPE PIC Tutorial Supplement 1

APRIL '98 Photostats Only

PROJECTS • Simple Metal Detector • Single or Dual Tracking Power Supply • Experimental Piezo-Cable Projects - Distributed Microphone - Vibration Alarm • RC-Meter.
FEATURES • Ingenuity Unlimited • Patent Your Invention • TEACH-IN '98 - 6 • Circuit Surgery • Net Work • Techniques - Actually Doing It • EPE PIC Tutorial Supplement 2

MAY '98 Photostats Only


PROJECTS • Dice Lott • Security Auto-Light • Stereo Tone Control plus 20W Stereo Amplifier • Improved Infra-Red Remote Repeater.
FEATURES • TEACH-IN '98 - 7 • Net Work • EPE PIC Tutorial Supplement 3

JUNE '98

PROJECTS • EPE Mood Changer • Simple SW Receiver • Atmel AT89C2051/1051 Programmer • Reaction Timer.
FEATURES • 8051-based EEPROM Microcontrollers • TEACH-IN '98 - An Introduction to Digital Electronics - 8 • Circuit Surgery • Techniques - Actually Doing It • Ingenuity Unlimited

JULY '98

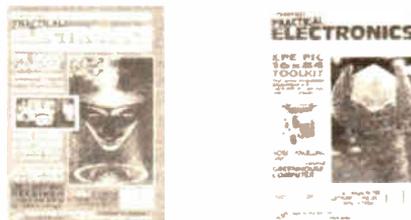PROJECTS • PIC16x84 Toolkit • Noise Cancelling Unit • Low Battery Indicator • Greenhouse Computer - 1.
FEATURES • Using the L200CV Voltage Regulator • TEACH-IN '98 - 9 • Ingenuity Unlimited • Circuit Surgery • Net Work.



AUG '98

PROJECTS • Lightbulb Saver • Float Charger • PC Transistor Tester • Greenhouse Computer - 2 • Time Machine Update.
FEATURES • TEACH-IN '98 - 10 • Circuit Surgery • Techniques - Actually Doing It • Ingenuity Unlimited • New Technology Update • Net Work • IVEX PCB Cad Review.

SEPT '98

PROJECTS • Mains Socket Tester • Personal Stereo Amplifier • Greenhouse Radio Link • PIC Altimeter.
FEATURES • TEACH-IN '98 - 11 • Ingenuity Unlimited • Circuit Surgery • Interface • Net Work • Crocodile Clips Review.

OCT '98

PROJECTS • Voice Processor • Digiserv R/C Channel Expander • Reliable Infra-Red Remote Control • PC Capacitance Meter.
FEATURES • Easy PCB Making • Using LM335 and LM35 Temperature Sensors • Circuit Surgery • Ingenuity Unlimited • Net Work • Electronics Principles 5.0 Review.

NOV '98

PROJECTS • PIC Tape Measure • T-Stat Electronic Thermostat - 1 • PhizzyB Computers - 1 • 15-way Infra-Red Remote Control.
FEATURES • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work - The Internet • Easy PC for Windows 95 Review • FREE EPE CD-ROM No.1.

DEC '98 Photostats Only

PROJECTS • EPE Mind PICKler-1 • Fading Christmas Lights • Handheld Function Generator • Damp Stat Electronic Thermostat • PhizzyB Computers-2.
FEATURES • PhizzyB Computers-2 Understanding Computers • Circuit Surgery • Ingenuity Unlimited • Index • FREE 48-page Understanding Passive Components booklet.

JAN '99

PROJECTS • Alternative Courtesy Light Controller • Twinkle Twinkle Reaction Game • Volume Compressor • PhizzyB Computers-3 • EPE Mind PICKler-2.
FEATURES • New Technology Update • From Russia With Love • Circuit Surgery • PhizzyB Computers-3 • Net Work.



FEB '99

PROJECTS • PIC MIDI Sustain Pedal • Light Alarm • Wireless Monitoring System-1 • PhizzyB Computers-4.
FEATURES • Ingenuity Unlimited • Sclar Project • PhizzyB Computers-4.

MAR '99

PROJECTS • Smoke Absorber • Auto Cupboard Light • PhizzyB Computers-5 • Time and Date Generator • Wireless Monitoring System-2.
FEATURES • Ingenuity Unlimited • I/ITSEC Show Report • PhizzyB Computers-5 • Practically Speaking • Circuit Surgery • Net Work.

APRIL '99

PROJECTS • Mechanical Radio • Voice Record/Playback Module • Versatile Event Counter • PhizzyB Computers-6 • Ironing Board Saver.
FEATURES • Ingenuity Unlimited • PIC16F87x Microcontrollers • PhizzyB Computers-6 • MAX761 D.C. to D.C. Converter • Interface • Circuit Surgery • Net Work • FREE 48-page Basic Soldering Guide booklet.

BACK ISSUES ONLY £2.75 each inc. UK p&p.

Overseas prices £3.35 each surface mail, £4.35 each airmail.

We can also supply issues from earlier years: 1992 (except March, April, June to Sept. and Dec.), 1993 (except Jan. to March, May, Aug., Dec.), 1994 (except April, May, June, Nov.), 1995 (except Jan., May to Sept., Nov., Dec.), 1996 (except Feb., April, May, July, Aug., Nov.), 1997.

We can also supply back issues of *ETI* (prior to the merger of the two magazines) for 1998/9 - Vol. 27 Nos 1 to 13 and Vol. 28 No. 1. We are not able to supply any material from *ETI* prior to 1998. Please put *ETI* clearly on your order form if you require *ETI* issues.

Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM - BACK ISSUES - PHOTOSTATS - INDEXES

- Send back issues dated
- Send photostats of (article title and issue date)
- Send copies of last five years indexes (£2.75 for five inc. p&p - Overseas £3.35 surface, £4.35 airmail)

Name

Address

- I enclose cheque/PO./bank draft to the value of £.....
- Please charge my Visa/Mastercard £.....

Card No. Card Expiry Date

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.
SEND TO: **Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.**
Tel: 01202 881749. Fax: 01202 841692. (Due to the cost we cannot reply to overseas queries or orders by Fax.)
E-mail: orders@epemag.wimborne.co.uk

Payments must be in sterling - cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.
Send a copy of this form, or order by letter if you do not wish to cut your issue.

M5/99

VIDEOS ON ELECTRONICS

A range of videos selected by EPE and designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.



BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.


Order Code VT201

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

Order Code VT202

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

Order Code VT203

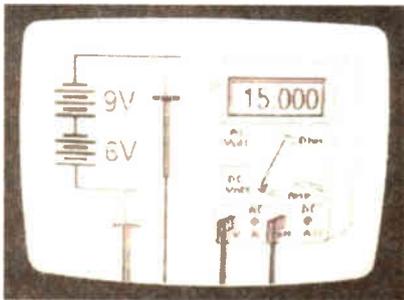

VT204 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply.

Order Code VT204

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

Order Code VT205

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

Order Code VT206

£34.95 each
inc. VAT & postage

Order 8 or more get one extra FREE
Order 16 get two extra FREE

VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

Order Code VT102

VT103 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

Order Code VT103

DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

Order Code VT301

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

Order Code VT302

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc.

Order Code VT303

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits.

Order Code VT304

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

Order Code VT305

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

Order Code VT306


RADIO

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

Order Code VT401

VT402 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver.

Order Code VT402

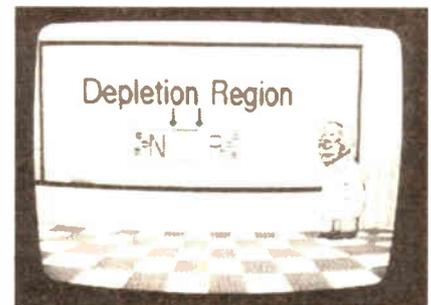

VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

Order Code VT403


MISCELLANEOUS

VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

Order Code VT501

VT502 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO₂ gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning.

Order Code VT502

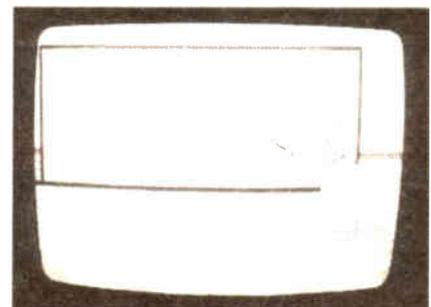

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier. (All videos are to the UK PAL standard on VHS tapes)

ORDERING: Price includes postage to anywhere in the world.

OVERSEAS ORDERS: We use the VAT portion of the price to pay for airmail postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank).

Visa and Mastercard orders accepted – please give card number, card expiry date and cardholder's address if different from the delivery address.

Orders are normally sent within seven days but please allow a maximum of 28 days – longer for overseas orders.

Send your order to: Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)

Direct Book Service is a division of Wimborne Publishing Ltd., Publishers of EPE
Tel: 01202 881749. Fax: 01202 841692

Due to the cost we cannot reply to overseas orders or queries by Fax.

E-mail: editorial@epemag.wimborne.co.uk

SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

NET WORK is our monthly column written for readers having access to the Internet. Don't forget that we maintain our own web site at <http://www.epemag.wimborne.co.uk>, and by using our Secure Server at <https://secure.tcp.co.uk/epemag>, readers can subscribe or renew their subscription on-line using Visa or Mastercard. The *EPE* Back Issues secure order form is a popular and convenient way of ordering reprints, issues and printed circuit boards.

New on the *EPE* web site is a web version of the history of both *Everyday Electronics* and its former sister magazine *Practical Electronics*, founded back in 1964. In his on-line article, Editor Mike Kenward describes how the magazines progressed from their early roots to merge into the leading UK hobby and educational magazine.

A separate illustrated section includes some fascinating screen shots of old issues and advertisements, also it shows some original cover shots of *Everyday Electronics*, and describes how the advent of affordable home computers in the mid 1980s was to have a profound impact in the future direction of the magazine. We hope you enjoy the feature.

THE WORMS HAVE TURNED

Regular Internet users may have heard of the "Happy99" Windows "worm" which has been circulating the Internet. This month's *Net Work* looks at some of the risks faced by its users when fetching files from remote sites using E-mail, FTP or the web.

A worm first appeared on American networks on 2 November, 1988, when a student in Cornell University created what he thought was a harmless code which would replicate and grow on any susceptible Unix host computer. The worm would then seek to spread to other computers by exploiting the inherent weaknesses that existed at that time in government and research communications networks.

When the worm was unleashed the result was that American network systems – both military and academic – were eventually brought crashing to a halt, devastated by the way the worm propagated itself through the entire system, growing and choking up every computer in its path until the entire system locked up. Initial attempts to restore systems following this new form of attack were not entirely successful, because a "disinfected" system could soon be attacked again by other networks which were still under siege from what was later to be known as *The Internet Worm*.

UNDER ATTACK


Many users are very casual about the risks involved in transmitting or receiving files by Internet. There are three forms of malicious code attack which computer users ought to be aware of, since the risks of becoming "infected" are now greater than ever given that file transmission via the Internet is commonplace.

A worm propagates itself from one host computer to another. The idea is simply that it copies itself at every opportunity. A worm is simply *there* but normally doesn't try to attack your system *per se*.

Trying to eliminate a worm may be difficult but usually a cure is found. **Happy99.exe** is a good example, discussed shortly. It can be propagated by being encoded into an E-mail, or can be transmitted via a Usenet post.

As reflected in its name, a Trojan Horse is a program which looks inviting and alluring: its perpetrators are trying to fool you into opening it and running it. Note that a Trojan Horse is not the same as a computer virus attack. The device may pretend to be a game or innocent-looking program, but behind the scenes it is busy itself by damaging the host computer setup.

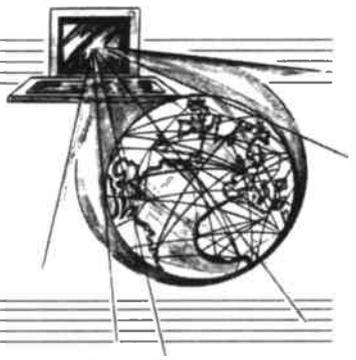How do you really know for definite that the file you just fetched from the Internet is really what it purports to be? Recently a Trojan Horse entitled **Picture.exe** was released which, amazingly, could sniff out and send AOL usernames and passwords from the host system to a particular remote E-mail address.



A computer virus can be intended to inflict deliberate damage on its host system. Virii can latch themselves on to genuine-looking program files, like bacteria infecting healthy tissue: the main program might continue to work but the virus can grow invisibly within the system and be transmitted to others – e.g. by residing on the hard disk or by infecting floppy disks – without the users' knowledge.

As to what happens after a virus attack, well it depends. There are thousands of viruses in circulation and when a host system contracts one of them, any number of effects can be observed, from the computer gradually slowing down because its memory is being filled, to files becoming corrupted, a system behaving bizarrely on a particular day (e.g. Friday the 13th) or – worst case scenario – a complete trashing of a hard disk. (You do back up important data every day, don't you?)

DON'T PANIC

Probably the most common virus I come across is *Form*, which tends to be introduced on dubious-looking floppy disks. Some variants wake up on the eighteenth of every month and display a "Don't Panic" message. Other attempted virus attacks include an innocent one (I assume) contained in a reader's floppy disk that arrived in the post. Fortunately my anti-virus software detected the presence of *Tan Pro 524* immediately.

Occasionally, a figment called the *Good Times* virus springs up, appearing in the form of a "damaging" E-mail message. This can cause novices great concern. The subject line of the E-mail threatens that the virus will harm the host system if it is opened and read.

Good Times is a hoax. If anything, it's the actual propagation of the E-mail message by worried users which is the "virus". Let me emphasise one thing: *you can't damage your system or introduce a virus merely by reading an E-mail message. You can, however, introduce a worm or a damaging virus by "running" an attached executable code.*

The worm **Happy99** (Happy New Year, right?) may appear as an attachment called **happy99.exe** in E-mail messages and it is very tempting to run the Windows executable file just to see what happens. This has actually struck uncomfortably close to home, since an E-mail message from an "official" software support technician to my brother did indeed have the **Happy99** worm attachment. The software vendor had been attacked by the worm and an employee must have run it, thereby propagating the worm onto its customers' systems. Worried Windows users can check for its presence by looking for a file called **ska.exe** or **wsock32.ska**. (The Symantec web site offers a cure.)

UPDATE

The best defence in this warfare is to keep updated with an anti-virus package such as Symantec's *Norton Anti Virus*, which was one of the first to carry details of **Happy99**. Subscribe to updates if you value your data: Norton permits a series of monthly updates which can be obtained by a "Smart Update" direct modem transfer (no Internet connection being used necessarily, you notice). You can also submit suspicious program files to Norton for examination.

There are several good anti-viral (AV) resources on the web. The first is www.symantec.com/avcenter, the leading Symantec site with lots of data, including information on **Happy99**. Other respected vendors of AV protection include www.mcafee.com, www.drsolemon.com, www.av.ibm.com (an IBM-Symantec joint venture) and www.datafellows.com. Macintosh users could try www.macvirus.com. If your work depends on the Internet or dealing with files from external sources, you should sign up to an anti-virus update system today.

As usual the URLs mentioned above (and more besides) are already enabled on the *EPE* web site – go straight to my *Net Work* page and click. Suggestions for good electronics-related web resources are always welcome – please E-mail yours to alan@epemag.demon.co.uk.

NOW AVAILABLE

RANGER 2

for Windows 95™

Demo Software - available from our Web Address

The Complete, Integrated Schematic & PCB Layout Package

Windows Ranger 2

For Windows 95 & NT

- New Hierarchical Circuit
- Split Devices • Gate & Pin Swap
- New Edit Devices in Circuit
- Copper Fill • Power Planes
- Autorouter • Back Annotation

£250

Ranger 2 Outputs:

Full Windows Outputs
Plus - HP-GL
Gerber
NC Drill
AutoCad DXF

Windows Ranger 2 with Spectra SP2

Ranger & Spectra Autorouter provide the most cost effective PCB Design system available. A powerful, intuitive system at an outstanding price!

£600

Windows Ranger 2 Upgrade

Upgrade your existing PCB Package to Windows Ranger 2.

£150

SPECIAL OFFER Ranger 2 Lite £35 (Prices exc VAT/P&P)

Demo Software - download from <http://biz.ukonline.co.uk/seetrax>

Call 01730 260062

Fax 01730 267273

Old Buriton Lameworks, Kiln Lane,
Buriton, Petersfield, Hants. GU31 5SJ



SEETRAX

Advanced Systems & Technology for PCB Manufacture

PCBs FROM PAST ISSUES OF ETI

(prior to the merger of EPE and ETI in March 99). See opposite page for ordering details.

Name and Issue of project	Unit code	Price			
ETI PCB Service Issue 1 1999			Surface Mount Diagnostic Interface	E/798/2	£5.09
Stress and Skin Temperature Meter	E/0199/1	£14.55	Surface Mount Logic probe	E/798/3	£5.09
'Short Cut' Continuity Tester	E/0199/2	£5.09	Mains Monitor	E/798/4	£12.33
R.F. Probe	E/0199/3	£5.09	Aquaprobe	E/798/5	£5.50
Switch Volt PSU	E/0199/4	£5.09			
ETI PCB Service Issue 13 1998			ETI PCB Service Issue 6 1998		
Programmable Logic Microcontroller Board	E/1398/1	£7.32	PIC Development Board	E/698/1	£5.50
Programmable Logic Simulator Board	E/1398/2	£5.09	Signal Generator	E/698/2	£8.99
Regulated Battery PSU	E/1398/3	£5.09	Headlight Delay Unit	E/698/3	£5.50
Audio Power Meter	E/1398/4	£7.32	6-Interval Games Timer	E/698/4	£5.09
Car Vigilante	E/1398/5	£5.64			
Millivolt Meter	E/1398/6	£6.77	ETI PCB Service Issue 5 1998		
Wobbulator	E/1398/7	£6.22	UHF Transmitter (DS)	E/598/1	£5.07
			UHF Transmitter Encoder	E/598/2	£5.09
ETI PCB Service Issue 12 1998			UHF Receiver Front End (DS)	E/598/3	£5.07
Beerstat	E/1298/1	£5.09	UHF Receiver I.F. stage (DS)	E/598/4	£5.07
Fishbiter	E/1298/2	£5.09	Fridge Thermometer	E/598/5	£5.50
Smooth Fuzz	E/1298/3	£5.09	AVR Controller	E/598/6	£5.50
			27C16 Eprom Programmer	E/598/7	£7.87
ETI PCB Service Issue 11 1998			Guardian Light	E/598/9	£6.22
Loop Alarm	E/1198/1	£5.09			
Ricky Sound (Music Lovers)	E/1198/2	£5.09	ETI PCB Service Issue 4 1998		
			LED Voltmeter	E/498/1	£5.64
ETI PCB Service Issue 10 1998			BB Ranger Control Board	E/498/2	£6.22
Ionisation Chamber	E/1098/1	£5.09	BB Ranger Score Board	E/498/3	£22.89
Ionisation Chamber (SMD)	E/1098/2	£5.09	Line-Up Oscillator with Glitch	E/498/4	£8.99
PIC Development Board: see also issue 6 below	E/698/1	£5.50	Tic-Tac-Toe	E/498/5	£8.44
ETI PCB Service Issue 9 1998			ETI PCB Service Issue 3 1998		
Q Meter	E/998/2	£5.09	Medium Wave Loop	E/398/1	£5.64
Bath Duck	E/998/3	£5.09	AA Cell Eliminator	E/398/2	£7.32
			PIC Based Double Bass Tuner	E/398/3	£5.64
ETI PCB Service Issue 8 1998			5-range Capacitor Meter	E/398/4	£6.77
PIC Electronics Security Switch	E/898/1	£5.09	MIDI Drum Pads	E/398/5	£5.64
PIC Multiplexed LED Display	E/898/2	£5.09			
PIC Non-multiplexed LED Display	E/898/3	£5.09	ETI PCB Service Issue 2 1998		
Easy Parker	E/898/4	£6.77	Smartcam main board	E/298/1	£5.09
Tiny Traffic Lights	E/898/5	£5.09	Smartcam opto-sensor board	E/298/2	£5.09
Q Meter	E/898/6	£5.09	Both smartcam boards	E/298/1&2	£7.00
Bath Duck	E/898/7	£5.50	Switched Mode Internal Power Supply	E/298/5	£7.87
			Auto Cupboard light	E/298/3	£5.64
ETI PCB Service Issue 7 1998					
PIC 16C74 Development Board	E/798/1	£5.09	ETI PCB Service Issue 1 1998		
			Control Centre Desk-Top unit	E/198/1	£8.99
			Control Centre Main Section	E/198/2	£7.87

PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749; Fax 01202 841692 (NOTE, we cannot reply to orders or queries by Fax); E-mail: orders@epemag.wimborne.co.uk. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required – see the Back Issues page for details.

Please check price and availability in the latest issue. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
★PIC Digital/Analogue Tachometer DEC'96	127	£7.23
Stereo Cassette Recorder		
Playback/PSU	128	£7.94
Record/Erase	129	£9.04
★Earth Resistivity Meter JAN'97		
Current Gen. – Amp/Rect.	131/132 (pr)	£12.70
Theremin MIDI/CV Interface (double-sided p.t.h.)	130 (set)	£40.00
Mains Failure Warning	126	£6.77
Pacific Waves FEB'97		
PsiCom Experimental Controller	136	£9.00
Oil Check Reminder	125	£7.16
Video Negative Viewer	135	£6.75
Tri-Colour NiCad Checker	138	£6.45
Dual-Output TENS Unit (plus Free TENS info.)	139	£7.20
★PIC-Agoras – Wheelie Meter APRIL'97		
418MHz Remote Control – Transmitter	141	£6.90
– Receiver	142	£5.36
Puppy Puddle Probe	143	£6.04
MIDI Matrix – PSU	145	£6.10
– Interface	147	£5.42
– Interface	148	£5.91
Quasi-Bell Door Alert MAY'97		
2M F.M. Receiver	133	£6.59
★PIC-A-Tuner	144	£7.69
Window Closer – Trigger	149	£7.83
– Closer	150	£4.91
– Closer	151	£4.47
Child Minder Protection Zone JUN'97		
– Transmitter	153	£6.58
– Receiver	154	£6.42
Pyrotechnic Controller	155	£6.93
★PIC Digilogue Clock	156	£7.39
Narrow Range Thermometer	158	£6.37
Micropower PIR Detector – 1 JULY'97		
Infra-Red Remote Control Repeater	152	£6.69
(Multi-project P.C.B.)	932	£3.00
Karaoke Echo Unit – Echo Board	159	£6.40
– Mixer Board	160	£6.75
Computer Dual User Interface	161	£6.70
★PEST Scarer	162	£6.60
Variable Bench Power Supply AUG'97		
Universal Input Amplifier	932	£3.00
Micropower PIR Detector – 2 Controller	146	£6.55
★PIC-OLO	163	£6.72
Active Receiving Antenna	164	£7.02
Soldering Iron Controller	140	£6.59
★PIC Noughts & Crosses Game	157	£6.63
Micropower PIR Detector – 3	165	£7.82
Alarm Disarm/Reset Switch	166	£5.72
Ironing Safety Device	167	£5.12
Remote Control Finder OCT'97		
Rechargeable Handlamp	168	£6.32
★PIC Water Descaler	169	£6.23
★EPE Time Machine	170	£6.90
Auto-Dim Bedlight	171	£8.34
Portable 12V PSU/Charger	172	£6.63
Car Immobiliser	173	£6.61
Safe and Sound (Security Bleeper) DEC'97		
Surface Thermometer	175	£7.00
Disco Lights Flasher	179	£7.32
Waa-Waa Pedal (Multi-project PCB) JAN'98		
★Virtual Scope – Digital Board	174	£7.64
Analogue Board (per board)	178	£8.30
★Water Wizard	932	£3.00
Kissometer	176	£14.49
★EPE PIC Tutorial FEB'98		
The Handy Thing (Double-Sided)	177	£7.34
Lighting-Up Reminder	180	£7.69
★Audio System Remote Controller – PSU	181	£7.67
Main Board	182	£7.99
Simple Metal Detector MAR'98		
(Multi-project PCB)	183	£6.58
Single or Dual-Tracking Power Supply	184	£5.90
★RC-Meter	185	£7.05
Security Auto-Light APR'98		
Stereo Tone Control plus 20W Stereo Amplifier	186	£8.29
Tone Control	932	£3.00
20W Amplifier	187	£7.90
★Dice Lott	188	£7.66
Security Auto-Light MAY'98		
Stereo Tone Control plus 20W Stereo Amplifier	189	£8.10
Tone Control	190	£7.78
20W Amplifier	191	£8.58
★Dice Lott	192	£8.05

PROJECT TITLE	Order Code	Cost
EPE Mood Changer JUNE'98	193	£7.75
★AT89C2051/1051 Programmer		
Main Board	194	£8.50
Test Board	195	£8.69
★Reaction Timer Software only	–	–
★PIC16x84 Toolkit JULY'98		
★Greenhouse Computer	196	£6.96
Control Board	197	£9.08
PSU Board	198	£8.10
Float Charger AUG'98		
Lightbulb Saver	199	£6.59
Personal Stereo Amplifier	202	£3.00
(Multi-project PCB) SEPT'98		
★Greenhouse Radio Link	932	£3.00
★PIC Altimeter	200	£8.32
Voice Processor	201	£8.15
★Digiserv R/C Expander OCT'98		
IR Remote Control	203	£7.18
Transmitter	204	£7.69
Receiver	205	£3.00
★PIC Tape Measure NOV'98		
Electronic Thermostat	206	£3.50
T-Stat	207	£6.82
PhizzyB	208	£4.00
A-PCB B-CD-ROM C-Prog. Microcontroller	209	£4.50
15-Way IR Remote Control	210	£4.00
Switch Matrix	211	£5.16
15-Way Rec/Decoder	212	£3.95
Damp Stat DEC'98		
Handheld Function Generator	213	£4.00
★Fading Christmas Lights	215	£5.16
PhizzyB I/O Board (4-section)	216	£3.95
Twinkle Twinkle Reaction Game JAN'99		
★EPE Mind PICKler	217	£7.55
PhizzyB I/O Board (4-section)	214	£6.30
Alternative Courtesy Light Controller	216	£3.95
Light Alarm FEB'99		
★Wireless Monitoring System – Transmitter	218	£6.78
Receiver	219+a	£9.92
★PIC MIDI Sustain Pedal Software only	220+a	£8.56
★Wireless Monitoring System-2 MAR'99		
F.M. Trans/Rec Adaptors	219a/220a	See Feb'99
★Time and Date Generator	221	£7.37
Auto Cupboard Light	222	£6.36
Smoke Absorber	223	£5.94
Ironing Board Saver APR'99		
Voice Record/Playback Module	224	£5.15
Mechanical Radio (pair)	225	£5.12
★Versatile Event Counter	226A&B	£7.40 pr.
PIC Toolkit Mk 2 MAY'99	207	£6.82
A.M./F.M. Radio Remote Control	227	£8.95
Transmitter	228	£3.00
Receiver	229	£3.20

EPE SOFTWARE

Software programs for EPE projects marked with an asterisk * are available on 3.5 inch PC-compatible disks or free from our Internet site. Three disks are available: PIC Tutorial (Mar-May '98 issues); PIC Disk 1 (all other software Apr '95–Dec '98 issues); EPE Disk 2 (Jan '99 issue to current cover date). The disks are obtainable from the *EPE PCB Service* at £2.75 each (UK) to cover our admin costs (the software itself is free). Overseas (each): £3.35 surface mail, £4.35 each airmail. All files can be downloaded free from our Internet FTP site: <ftp://ftp.epemag.wimborne.co.uk>.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

.....

Name.....

Address.....

.....

I enclose payment of £.....(cheque/PO in £ sterling only) to:

Everyday Practical Electronics

Access (MasterCard) or Visa No. Minimum order for credit cards £5



Signature..... Card Exp. Date.....

Please supply name and address of cardholder if different from the address shown

NOTE: You can order p.c.b.s via our Internet site on a secure server: <http://www.epemag.wimborne.co.uk>

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics/ETI Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
 Up to 20 volts d.c. at 1 amp continuous, 1.5 amps peak, fully variable from 1 to 20 volts. Twin Voltage and Current meters for easy read-out. 240 volt a.c. input. Fully smoothed, size 23cmx14cmx8cm.

£45 inc. VAT
 Post £4

RADIO COMPONENT SPECIALISTS
 337 WHITEHORSE ROAD, CROYDON SURREY, CR0 2HS. Tel: 0181-684 1665

Lots of transformers, high volt caps, valves, output transformers, speakers, in stock. Phone or send your wants list for quote.

ELECTRONIC KITS

- 88-108MHz FM transmitters from under £5
- Many educational and hobby electronic kits covering all technical abilities, from beginners' circuits to MCU/MPU designs
- Low cost PCB services and equipment
- Send 4x1st class stamps for catalogue

DTE MICROSYSTEMS, 112 SHOBNALL ROAD, BURTON-ON-TRENT, STAFFS DE14 2BB
 PHONE or FAX: 01283 542229
<http://www.btinternet.com/~dtemicrosystems>

BRAND NEW SINCLAIR SPECTRUM & QL PARTS

ZX MICRODRIVES £15, INTERFACE ONE £20, CARTRIDGES 10 FOR £15, 50 FOR £50.
 QL BOARDS 5, 6 & 7, POPULATED WITH JS ROMS, £30; UNPOPULATED, £12; MICRODRIVES £10 EACH. TOP & BOTTOM CASES £15. MEMBRANES £15.

THE P.C., MAC and QL's "Little Friend" MAC LINK £10 - P.C. LINK £25 - QL LINK £12

CAMBRIDGE 288 A4 NOTEBOOK COMPUTER AVAILABLE AGAIN £99, RECONDITIONED £60

ONLY 1" THICK, 4xAA BATTs, 20 HOURS WORK, LCD SCREEN, 72 Crs, 6 LINES, 32K RAM, EXTRA RAMS & EPROMS, 9 pin D SERIAL PORT, ROM HAS BBC BASIC, W/PROCESSOR, SPREADSHEET, DATA BASE, IMP/EXPORT TO PC etc, V52 TERMINAL.

W.N. RICHARDSON & CO.
 PHONE/FAX 01494 871319
 6 RAVENSMEAD, CHALFONT ST PETER, BUCKS, SL9 0NB.

BTEC ELECTRONICS TECHNICIAN TRAINING

GNVQ ADVANCED ENGINEERING (ELECTRONIC) - PART-TIME
 HND ELECTRONICS - FULL-TIME
 B.Eng FOUNDATION - FULL-TIME

Next course commences
Monday 13th September 1999
 FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
 (Dept EPE) 20 PENYWERN ROAD
 EARLS COURT, LONDON SW5 9SU
 TEL: 0171-373 8721

THE BRITISH AMATEUR ELECTRONICS CLUB

exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter. For membership details, write to the Secretary:

Mr. M. R. Moses, 5 Park View, Cwmaman, Aberdare CF44 6PP

Space donated by Everyday Practical Electronics

Miscellaneous

X-10® Home Automation
We put you in control™
WHY TOLERATE WHEN YOU CAN AUTOMATE?

An extensive range of 230V X-10 products and starter kits available. Uses proven Power Line Carrier technology, no wires required. Products Catalogue available online. Worldwide delivery.

Laser Business Systems Ltd.
 E-Mail: info@laser.com
<http://www.laser.com>
 Tel: (0181) 441 9788
 Fax: (0181) 449 0430

ASTRA Desk Top Accounting™

Are you worried that your customers will insist on using the Euro and so leave you off their list of suppliers?

see www.AstraAccounts.co.uk for a Pan-European solution to help you with this looming problem

S&S Systems Ltd., Bretton Court, S26 5PS, UK

G.C.S.E. ELECTRONIC KITS, at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB.

EX-EQUIPMENT BARGAINS!! 10 watt amplifier module + V/C, selector, £3.00; 10 watt stereo, includes p.s.u. & controls, £5.00. K.I.A., 1 Regent Road, Ilkley LS29 9EA.

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Hove, Sussex BN3 8GR, or phone Brighton 883871, fax 01273 706670.

VALVE ENTHUSIASTS: Capacitors and other parts in stock. For free advice/lists please ring, Geoff Davies (Radio), Tel. 01788 574774.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and Production. Artwork raised from magazines or draft designs at low cost. PCBs also designed from schematics. Production assembly also undertaken. For details send to P. Agar, Unit 5, East Belfast Enterprise Park, 308 Alberbridge Road, Belfast, BT5 4GX, or phone/fax 01232 738897.

NEW AND USED COMPUTERS, spares, etc. at keenest prices. e.g.: 386 min 2MB RAM, 20MB HDD, desktop case, keyboard and cables, 12in. VGA mono monitor, £55. 486 DX33 min. 8MB RAM, 120MB HDD, desk top case, keyboard and cables, 14in. VGA colour monitor, £165. Many other systems available. Whatever you need, Phone/Fax 0181 853 3374 for prices.

FREE CATALOGUE: Moreton Alarm Supplies/CCTV 2000, unbeatable prices! Board cameras from £29.00. Telephone 0151 630 0000.

PIC PROTOTYPING KIT. Eurocard size. On-board RS232, voltage regulation and protection, in-circuit programming. Large prototyping area. Kit includes serial and programming cables. For details send an A5 s.a.e. to: Frank Cembrola, 93/B St. Johns Road, Biddulph, Staffs, ST8 6LL, UK. <http://www.a-f-u-net.com/main.htm>. Tel. 01782 518356.

EPE NET ADDRESSES

EPE FTP site: <ftp://ftp.epemag.wimborne.co.uk>
 Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:

PIC-project source code files: /pub/PICS
 PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. Do not try to download the folder itself!

EPE text files: /pub/docs
 Basic Soldering Guide: solder.txt
 EPE TENS Unit user advice: tens.doc and tens.txt
 Ingenuity Unlimited submission guidance: ing_unlit.txt
 New readers and subscribers info: epe_info.txt
 Newsgroups or Usenet users advice: usenet.txt
 Ni-Cad discussion: nicadfaq.zip and nicad2.zip
 UK Sources FAQ: uksource.zip
 Writing for EPE advice: write4us.txt

Ensure you set your FTP software to ASCII transfer when fetching text files, or they may be unreadable.

Note that any file which ends in .zip needs unzipping before use. Unzip utilities can be downloaded from :
<http://www.winzip.com> or
<http://www.pkware.com>

On-line readers! Try the new EPE Chat Zone - a virtually real-time internet "discussion board" in a simple to use web-based forum!
<http://www.epemag.wimborne.co.uk/wwwboard>
 Or buy EPE Online: www.epemag.com

TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for **FREE INFORMATION** on the course of your

Electrical Contracting & Installation
Electrical Engineering
C&G Basic Electronic Engineering
C&G Basic Mechanical Engineering
TV and Video Servicing
Radio and Hi-Fi Servicing
Refrigeration Heating & Air Conditioning
Motorcycle Maintenance

FREEPHONE 0500 581 557

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Claydon Way Skypark Glasgow, G3 8BR. Tel. 0500 581 557 or Tel/Fax, Ireland 01 285 2533

Please send me my Free Information on your Electronics Courses.


Mr/Mrs/Ms/Miss (BLOCK CAPITALS PLEASE) _____ Date of Birth _____
Address _____
Postcode _____
Occupation _____ Tel. No. _____

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box Dept. ZEE010499

Professional 88-108MHz FM Broadcasting Kits

Detailed Instructions with Schematics
High Quality Screen Printed PCBs
High Quality Components

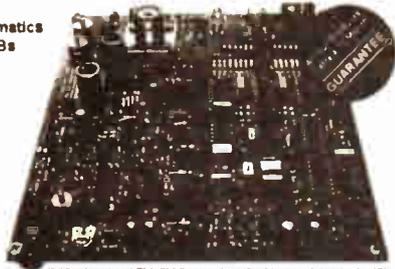Transmitters from 0.05W to 35W
FM Stereo Coders
Audio Compressor Limiters
Antennas
RF Power Amps



MasterCard VISA

WE DELIVER WORLD WIDE AND ACCEPT MAJOR CREDIT CARDS

Visit our Website at <http://www.veronica.co.uk>

Contact Us Now For A Free Brochure


Tel 01274 883434 Fax 01274 428665

email info@veronica.co.uk

Unit 5/6 1A Sandbeds/ Albert Rd Queensbury BRADFORD BD13 1AA



C.C.T.V. BOARD CAMERAS FROM £19.95

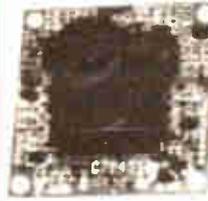

ONLY 29mm x 29mm

LOTS OF 10 (Each) **£19.95**
LOTS OF 5 **£21.50**
LOTS OF 2 **£23.95**
SAMPLE **£25.95**
Add P&P £3 ANY ORDER
VAT INCLUDED

MINIATURE C.C.T.V. CAMERAS FROM TOP USA MAKER. IDEAL FOR COVERT SURVEILLANCE OR SECURITY USE IN SHOPS, OFFICES AND PRIVATE HOMES. CONNECTS TO ANY TV OR VIDEO IN SECONDS - OPTIONAL CABLE ETC. AVAILABLE. OUR 1993 PRICE FOR THIS CAMERA WAS £385!! HUGE RECESSION IN ELECTRONIC INDUSTRY HAS SLASHED THESE PRICES TO RIDICULOUS LEVELS! THESE ARE USA MADE - NOT CHEAP CHINESE MODELS. READY BUILT WITH LENS ETC. BRAND NEW 1999 STOCK - FULL 12 MONTH GUARANTEE WORKS FROM 9V-PP3 BATTERY OR OUR CAMERA PSU AND CABLE KIT SHOWN BELOW.

Audio Model add **£5.00**
1/3in. image sensor with 288 x 352 pixels. Auto ins. 270 lines. 6V to 12V D.C. 30MA. Includes 3-6mm wide angle lens. Pinhole Lens add **£2.**

APPLICATIONS
SECURITY SURVEILLANCE. MACHINE MONITORING. NANNY WATCHING. STAFF THEFT. BIRD OBSERVATION. ETC.
BRITISH PAL SYSTEM

SECRET SPY CAMERAS MICRO SIZE 16mm x 16mm



PINHOLE 3-6MM

JAPANESE CCTV TECHNOLOGY REDUCES THE SIZE FOR EASY CONCEALMENT.

PLEASE ADD £2 TO ABOVE 29 x 29mm PRICES



NIGHT VISION CCTV CAMERA 37mm x 38mm

HIGH SPECIFICATION SHARP JAPANESE CAMERA MODULES FITTED WITH SIX INFRARED LEDs TO SEE IN TOTAL DARKNESS UP TO 12FT. 400 LINE RESOLUTION WITH FANTASTIC 0.2 LUX LEVEL. SENT INSIDE CLEAR PERSPEX CUBE. SAMPLE **£36 + £3 P&P LESS FOR QUANTITY**

Camera PSU and Cable Kit



A total solution for powering and connecting to our range of board camera modules and covert cameras. The kit contains a quality plug-in mains adaptor and a 20m pre-wired cable. One end of the cable has a SCART plug, an audio phono plug, a video phono plug and a DC power socket. The lead from the mains adaptor is plugged into the DC socket and either the SCART plug or audio and video phono plugs are plugged into your TV, monitor or VCR.

MAPLINS PRICE **£24.99**. OUR PRICE **£12.50**
NO EXTRA P&P IF ORDERED WITH CAMERA BOARD.



SMART CAMERA CASINGS TO ACCEPT ANY OF OUR BOARD CAMERAS £3.00

LASER POINTERS

Professional model fires a small red laser dot over 250 metres. Built into luxury executive presentation ballpoint pen with case and batts.

LIST **£39.95** NOW **£15.00**

Gold-plated Keyfob model

LIST **£29.95** **£13.00**


Add **£3 p&p** any quantity.

(Only sold to schools or tradesmen - no minors under 21)



1/4in. COLOUR CCD CAMERAS

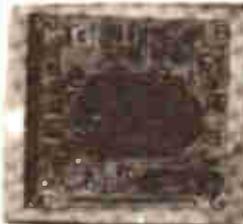Japanese Twinboard 1/4in. CCD and DSP (digital signal processor) colour CCTV boards with popular 3-6mm wide angle lens. High specification 290,000 pixels, electronic iris, 330 TV lines and LUX level 2. 12 volt DC. Use with our camera PSU and cable kit (see above).



LOWEST PRICE IN EEC

£59.00

Please add **£5** Audio model + **£3** p&p

VISONIC RADIO TRANSMITTER/RECEIVER SETS

Comprises smart remote control normally used as a panic button or medical alert for the elderly. Causes receiver to open or close a circuit thereby triggering a siren, automatic garage door or other device until button is released. Range 35m indoors, 100m outdoors. 9V PP3 batt. included. DTI approved 1340 licence exempt. MRP **£47.85** set.

SAMPLE SET **£15.90**

LOTS 10 **£12.90** set. LOTS 5 **£13.90**. LOTS 2 **£14.90**.
P&P **£3** any quantity


ALL GOODS ARE BRAND NEW AND PERFECT. BULK BUYERS PLEASE ASK FOR JOHN PRICES INCLUDE VAT.



A.S.A. (Est. 1979)
51 Cambridge Road
Middlebrough
TS5 5NL

Order Hotline
01642 850912
Fax:
01642 823173

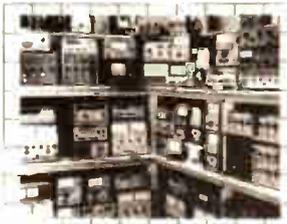SUPPLIER OF QUALITY USED TEST INSTRUMENTS



CONTACT

Cooke International
Unit Four, Fordingbridge Site, Barnham
Bognor Regis, West Sussex, PO22 0HD, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457
Web: <http://www.cooke-int.com>
E-mail: info@cooke-int.com

OPERATING & SERVICE MANUALS



CONTACT

Cooke International
Unit Four, Fordingbridge Site, Barnham
Bognor Regis, West Sussex, PO22 0HD, U.K.
Tel: (+44)01243 545111/2 Fax: (+44)01243 542457
Web: <http://www.cooke-int.com>
E-mail: info@cooke-int.com

★★ BACK TO BASICS ★★

RESISTORS		DIODES	
0-25W 5% CARBON E24 values 1R0 to 10M	each 2p	1N4148, 2p each (100 for £1), 1N914 5p (50 for £1)	
(Also E12 3R9 to 10M, 10 for 10p, 100 for 45p)		1N4001/2/3/4/6/7, 4p, 1N5401/2/4/6/8, 9p	
0-25W 1% METAL FILM E12 values 10R to 1M	each 3p	ZENERS 2V7 to 33V 400mW, 7p, 1R3W, 12p	
Price per value: 10 for 20p, 100 now only £1.79			
0-5W 5% CARBON E12 values 10R to 10M	each 2 1/2p		
(Also E12 4R7 to 4M7, 10 for 15p, 100 for 99p)			
0-6W 1% METAL FILM E12 values 10R to 1M	each 5p		
Price per value: 10 for 39p, 100 now only £1.99			
Development Packs available, send SAE for lists			
CAPACITORS		INTEGRATED CIRCUITS	
Radial Aluminium Electrolytics (µF/Volts)		CMOS 4000/12/11/12UB/23/25/30/69/72/73/75, 19p	
1R3, 2, 2.2, 2.5, 4.7/25V, 10/16, 22/16	5p	74LS00, 27p, 74LS02, 17p, 74LS04, 24p, 74LS05, 17p	
2.2/63, 4.7/63, 22/50, 33/25	6p	74LS08, 19p, 74LS14, 25p, 74LS17, 37p, 74LS244, 38p	
22/63, 33/63, 47/16, 47/25, 100/25	7p	TTL 7400/1/2/4/6/10/12/20/30, 19p	
47/63, 220/10, 220/16, 330/10, 470/10	8p	TIMERS 555, 24p, 556, 42p, ICM7555, 34p, ICM7556, 109p	
100/35, 220/25, 470/16, 470/25	9p	OP-AMPS LM324, 28p, LF351, 49p, LM358, 29p, 741, 23p	
100/63, 12p, 220/63, 19p, 470/63, 29p		CA3080E, 79p, CA3130E, 99p, CA3140E, 49p, CA3240E, 129p	
1000/16, 17p, 1000/25, 22p, 1000/35, 40p		LINEAR LM348, 31p, LM380, 39p, LM381, 164p, LM382, 149p	
Axial types available - please send SAE for lists		LM386, 58p, LM387, 105p, LM389, 119p, LM391, 90p, 189p	
		LM567, 58p, LM747, 39p, LM748, 38p, LM3908, 84p	
		MC709, 69p, MC1307, 89p, MC1310, 89p, MC13100, 79p	
TRANSISTORS		LEDs	
BC107/8/9, 17p, BC182/182U/183/183L, 9p		3mm or 5mm, Red, Yellow, Green, Amber	each 10p
BC184/184L/212/212L/212L/212L/37/547/8/9, 9p		10mm L.E.D.s, Red, Green, Yellow, Amber	each 29p
BC557/558/559, 9p, BCY70/71/72, 19p		Low current L.E.D.s: 1mA, 3mm or 5mm, R, G or Y	19p
BC135/8/7/8/9/140, 24p, BFY50/1/2, 29p		Bicolour L.E.D.s: 3mm or 5mm, R/G, R/Y or G/Y	36p
BF180/182, 36p, BF184/185, 59p		Tn-colour L.E.D.s: 3mm or 5mm, R/G/Y	each 39p
TIP31A/31C/32A/34/41A/42A, 39p		RED flash L.E.D. 9 to 12V, 3mm or 5mm	each 69p
TIP47, 56p, TIP122, 49p, TIP2955, £1.09		DISCOUNTS 5 + 5%, 10 + 10%, 25 + 15%, 100 + 20%	
ZTX107/8/9/212/34/300/1/2/34/110/13, 19p		Send SAE for list of 1997/98/99 EPE KITS	
WANT MORE? PLEASE SEND SAE FOR LISTS		P&P £1 NO VAT. Send SAE for COMPONENT lists	
		ALL MAJOR CREDIT CARDS, CHEQUES & POs ACCEPTED	
		FBI ELECTRONICS, THE BUSINESS CENTRE	
		FRIDGE STREET, BEDALE, NORTH YORKSHIRE DL8 2AD	
		TEL: 01677 425840	

COVERT VIDEO CAMERAS

Black and White Pin Hole Board Cameras with Audio. Cameras in P.I.R., Radios, Clocks, Briefcases etc. Transmitting Cameras with Receivers (Wireless). Cameras as above with colour. Audio Surveillance Kits and Ready Built Units, Bug Detector etc.

A.L. ELECTRONICS

Please phone 0181 203 0161 for free catalogue.

Fax 0181 201 5359

New DTI approved Video Transmitters and Receivers (Wireless)

N. R. BARDWELL LTD (EPE)

100	Signal diodes 1N4148	£1.00	200	Assid disc ceramic capacitors	£1.00
75	Rectifier Diodes 1N4001	£1.00	50	Assid Skel Presets (sm stand cermet)	£1.00
50	Rectifier Diodes 1N4007	£1.00	50	Assid RF chokes (inductors)	£1.00
10	W01 Bridge Rectifiers	£1.00	50	Assid grommets	£1.00
10	555 Timer I.C.s	£1.00	80	Assid solder tags p.conns terminals	£1.00
4	741 Op Amps	£1.00	10	Assid crystals - plug in	£1.00
50	Assorted Zener Diodes 400mW	£1.00	24	Assid coil formers	£1.00
12	Assorted 7-segment Displays	£1.00	8	Assid di switches	£1.00
25	5mm I.e.d.s. red green or yellow	£1.00	20	Miniature slide switches spico	£1.00
25	3mm I.e.d.s. red green or yellow	£1.00	10	Standard slide switches op dt	£1.00
50	Axial I.e.d.s. 2mcd red Diode Package	£1.00	30	Assid if transformers	£1.00
25	Assid High Brightness I.e.d.s. var cols	£1.00	100	Assid beads (ceramic teflon fish spine)	£1.00
20	BC182L Transistors	£1.00	80	Assid small stand offs I throughs etc	£1.00
25	BC212L Transistors	£1.00	30	Assid di sockets up to 40 way	£1.00
30	BC237 Transistors	£1.00	10	TV coax plugs plastic	£1.00
20	BC327 Transistors	£1.00	20	Small spring loaded terminals	£1.00
30	BC328 Transistors	£1.00	40	metres very thin connecting wire red	£1.00
30	BC547 Transistors	£1.00	20	1in glass reed switches	£1.00
30	BC548 Transistors	£1.00	20	Magnetic ear pps with lead and plug	£1.00
30	BC549 Transistors	£1.00	100	Any one value 1/4W 5% of resistors range	£0.45
25	BC557 Transistors	£1.00	1R to 10M		£1.00
30	BC558 Transistors	£1.00	10	7812 Voltage Regulators	£1.00
30	BC559 Transistors	£1.00			
20	2N3904 Transistors	£1.00			
100	50v wkg Axial Capacitors 1nF	£1.00			
100	50v wkg Axial Capacitors 4n7	£1.00			
12	1uF 250v encapsulated radial plastic cased capacitors	£1.00			
80	Assid capacitors electrolytic	£1.00			
80	Assid capacitors 1nF to 1µF	£1.00			

Prices include VAT, postage £1.25. 31p stamp for Lists

288 Abbeydale Road, Sheffield S7 1FL

Phone (0114) 2552886 Fax (0114) 2500689

E-mail sales@bardwells.co.uk

Web site: http://www.bardwells.co.uk

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1	15 x 5mm Red Leds	SP133	20 x 1N4004 diodes
SP2	12 x 5mm Green Leds	SP134	15 x 1N4007 diodes
SP3	12 x 5mm Yellow Leds	SP135	6 x Min slide switches
SP6	15 x 3mm Red Leds	SP136	3 x BFY50 transistors
SP7	12 x 3mm Green Leds	SP137	4 x W005 1-5A bndge rectifiers
SP10	100 x 1N4148 diodes	SP138	20 x 2-2.63V radial elect. caps
SP11	30 x 1N4001 diodes	SP140	3 x W04 1-5A bndge rectifiers
SP12	30 x 1N4002 diodes	SP142	2 x Cmos 4017
SP18	20 x BC182 transistors	SP143	5 Pairs min crocodile clips (Red & Black)
SP20	20 x BC184 transistors	SP145	6 x ZTX300 transistors
SP21	20 x BC212 transistors	SP146	10 x 2N3704 transistors
SP23	20 x BC549 transistors	SP147	5 x Stripboard 9 strips x 25 holes
SP24	4 x Cmos 4001	SP151	4 x 8mm Red Leds
SP25	4 x 555 timers	SP152	4 x 8mm Green Leds
SP26	4 x 741 Op amps	SP153	4 x 8mm Yellow Leds
SP28	4 x Cmos 4011	SP154	15 x BC548 transistors
SP29	3 x Cmos 4013	SP156	3 x Stripboard, 14 strips x 27 holes
SP31	4 x Cmos 4071	SP160	10 x 2N3904 transistors
SP36	25 x 10.25V radial elect. caps	SP161	10 x 2N3906 transistors
SP37	15 x 100/35V radial elect caps	SP165	2 x LF351 Op.amps
SP39	10 x 470/16V radial elect. caps.	SP167	6 x BC107 transistors
SP40	15 x BC237 transistors	SP168	6 x BC108 transistors
SP41	20 x Mixed transistors	SP175	20 x 1.63V radial elect. caps
SP42	200 x Mixed 0.25W C.F. resistors	SP177	10 x 1A 20mm quick blow fuses
SP47	5 x Min PB switches	SP182	20 x 4.7-63V radial elect. caps.
SP102	20 x 8-pin DIL sockets	SP183	20 x BC547 transistors
SP103	15 x 14-pin DIL sockets	SP187	15 x BC239 transistors
SP104	15 x 16-pin DIL sockets	SP191	3 x Cmos 4023
SP105	4 x 74LS00	SP192	3 x Cmos 4066
SP109	15 x BC557 transistors	SP193	20 x BC213 transistors
SP111	15 x Assorted polyester caps	SP194	8 x OA90 diodes
SP112	4 x Cmos 4093	SP195	3 x 10mm Yellow Leds
SP115	3 x 10mm Red Leds	SP197	6 x 20 pin DIL sockets
SP116	3 x 10mm Green Leds	SP198	5 x 24 pin DIL sockets
SP118	2 x Cmos 4047		
SP120	3 x 74LS93		
SP124	20 x Assorted ceramic disc caps		
SP130	100 x Mixed 0.5W C.F. resistors		
SP131	2 x TL071 Op amps		

RESISTOR PACKS - C.Film

RP3	5 each value - total 365 0.25W	£2.80
RP7	10 each value - total 730 0.25W	£4.00
RP10	1000 popular values 0.25W	£5.80
RP4	5 each value-total 365 0.5W	£3.75
RP8	10 each value-total 730 0.5W	£6.35
RP11	1000 popular values 0.5W	£8.10

1999 Catalogue now available £1 inc. P&P or FREE with first order.

P&P £1.25 per order. NO VAT

Orders to:

Sherwood Electronics,
7 Williamstown St., Mansfield,
Notts. NG19 6TD.

Millions of quality components at lowest ever prices!

Plus anything from bankruptcy - theft recovery - frustrated orders - over production etc.

Send 45p stamped self addressed label or envelope for clearance lists.

Brian J Reed

**6 Queensmead Avenue, East Ewell
Epsom, Surrey KT17 3EQ**

Tel: 07775 945386

Mail order UK only.

Lists are updated and only 40 are sent out every 2 weeks. This normally ensures that orders can be fulfilled where only a few thousand of an item is available. (Payment is returned if sold out. I do not deal in credit notes). This will sometimes entail a delay of up to eight weeks - but the prices will be worth the wait!

ADVERTISERS INDEX

A.L. ELECTRONICS.....	392
ANTEX.....	352
A.S.A.....	391
N. R. BARDWELL.....	392
BELL COLLEGE OF TECHNOLOGY.....	355
B.K. ELECTRONICS.....	Cover (iii)
BRIAN J. REED.....	392
BULL ELECTRICAL.....	Cover (ii)
COOKE INTERNATIONAL.....	391
CROWNHILL ASSOCIATES.....	377
DANNELL ELECTRONICS.....	333
DISPLAY ELECTRONICS.....	314
EPT EDUCATIONAL SOFTWARE.....	330
ESR ELECTRONIC COMPONENTS.....	322
FML ELECTRONICS.....	391
FOREST ELECTRONIC DEVELOPMENTS.....	368
GREENWELD.....	316
ICS.....	391
JEM ELECTRONICS.....	355
J&N FACTORS.....	318
JPG ELECTRONICS.....	355
LABCENTER ELECTRONICS.....	329
MAGENTA ELECTRONICS.....	320/321
MILFORD INSTRUMENTS.....	355
NATIONAL COLLEGE OF TECH.....	343
PICO TECHNOLOGY.....	378
QUASAR ELECTRONICS.....	343
QUICKROUTE SYSTEMS.....	Cover (iv)
RADIO-TECH.....	352
RAYDON ELECTRONICS.....	343
SEETRAX CAE.....	388
SERVICE TRADING CO.....	316
SHERWOOD ELECTRONICS.....	392
SLM (MODEL) ENGINEERS.....	352
SQUIRES.....	337
STEWART OF READING.....	333
SUMA DESIGNS.....	381
TECHNOLOGY EDUCATION INDEX.....	316
TELNET.....	317
VANN DRAPER ELECTRONICS.....	366
VERONICA FM.....	319
VERONICA KITS.....	391

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS,

MILL LODGE, MILL LANE, THORPE-LE-SOKEN,

ESSEX CO16 0ED.

Phone/Fax: (01255) 861161

For Editorial address and phone numbers see page 323.

**OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK**

1000's
SOLD
TO
PRO
USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)


ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN
FEATURES: • Independent power supplies with two toroidal transformers • Twin LED Vu Meters
• Level controls • Illuminated on/off switch • Jack/XLR inputs • Speakon outputs • Standard 775mV
inputs • Open and short circuit proof • Latest Mos-Fets for stress free power delivery into virtually any
load • High slew rate • Very low distortion • Aluminium cases • MXF600 & MXF900 fan cooled with D.C
loudspeaker and thermal protection

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-
MXF200 W19" D11" H3 1/2" (2U)
MXF400 W19" D12" H5 1/2" (3U)
MXF600 W19" D13" H5 1/2" (3U)
MXF900 W19" D14 1/2" H5 1/2" (3U)

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15

SPECIALIST CARRIER DEL. £12.50 EACH

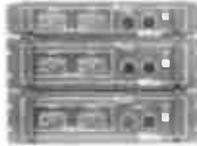

**FLIGHTCASED
LOUDSPEAKERS**

A new range of quality loudspeakers, designed to take advantage of the latest loudspeaker technology and enclosure designs. All models utilize high quality studio cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands. The FC15-300 incorporates a large 16 X 6 inch horn. All cabinets are fitted with the latest Speakon connectors for your convenience and safety. Five models to choose from.

WEDGE
MONITOR



PLEASE NOTE:- POWER RATINGS
QUOTED ARE IN WATTS R.M.S. FOR
EACH INDIVIDUAL CABINET.
ALL ENCLOSURES ARE 8 OHM.

15-15 inch speaker
12-12 inch speaker

ibl FC15 300 WATTS Freq Range 35Hz-20KHz, Sens 101dB, Size H695 W502 D415mm
PRICE:- £299.00 per pair

ibl FC12-300 WATTS Freq Range 45Hz-20KHz, Sens 96dB, Size H600 W405 D300mm
PRICE:- £249.00 per pair

ibl FC12-200 WATTS Freq Range 40Hz-20KHz, Sens 97dB, Size H600 W405 D300mm
PRICE:- £199.00 per pair

ibl FC12-100 WATTS Freq Range 45Hz-20KHz, Sens 100dB, Size H546 W380 D300mm
PRICE:- £179.00 per pair

ibl WM12 200 WATTS Freq Range 40Hz 20KHz, Sens 97dB, Size H418 W600 D385mm
PRICE:- £125.00 EACH

SPECIALIST CARRIER DEL:- £12.50 per pair, Wedge Monitor £7.00 each

Optional Metal Stands PRICE:- £49.00 per pair Delivery:- £6.00

OMP XO3-S STEREO 3-WAY ACTIVE CROSS-OVER SWITCHABLE 2-WAY



BASS MID TOP BASS/MID TOP BASS MID/TOP
CONFIGURED 3 WAY 2 WAY BASS/MID COMBINED 2 WAY MID/TOP COMBINED

FEATURES:

Advanced 3-Way Stereo Active Cross-Over (switchable two way), housed in a 19" x 1U case. Each channel has three level controls: Bass, Mid & Top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass Mid 125-250 500Hz, Mid Top 1.8-3.5Hz at 24dB per octave. The 2/3 way selector switches are also accessed by removing the front fascia. Each stereo channel can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mV input/output. Fully compatible with OMP Rack Amplifier and Modules.

PRICE:- £117.44 + £5.00 P&P

ibl IN-CAR AUDIO BASS BOX 10/100

INCREDIBLE VALUE



The new ibl In-Car Audio Bass Box has been designed with a sloping front to reduce internal standing waves. The bass box incorporates a 10 inch 4 ohm loudspeaker with a genuine 100 watts R.M.S. output resulting in powerful and accurate bass reproduction.

FEATURES:- • Cabinet manufactured from MDF and sprayed in a durable black shiny HAMMERITE finish. • Fitted with a 10 inch loudspeaker with rolled rubber edge and coated cone assembly • The top of the cabinet incorporates gold plated connection terminals. SPECIFICATION:- 100Watts R.M.S. 200 Watts Peak (Music). Ported reflex, critically tuned. Size: H405 W455 D305mm.

PRICE:- £79.00 + £6.00P&P

SOUNDLAB CDJ1700 CD PLAYER

VARIABLE SPEED



The new CDJ1700 now offers a tough build quality boasting an all new shockproof transport mechanism, frame accurate cueing and wide range pitch control. The CDJ1700 looks after the CD's while the operator looks after the sound.

FEATURES:

•19"X2U RACK MOUNTING •FULLY VARIABLE PITCH CONTROL PLUS/MINUS 16% •PITCH BLEND •3 BEAM LASER PICKUP •1 BIT 8 X OVERSAMPLING DAC •CUE AND LOOP FACILITY •TRACK SKIP WITH FF/REV •DIGITAL AND ANALOGUE OUTPUTS •CONTINUOUS/SINGLE TRACK PLAY •CLEAR BACKLIT MULTIFUNCTION DISPLAY •10 TRACK PROGRAM PLAY •TRACK ELAPSED TRACK REMAINING AND DISC REMAINING TIME DISPLAYS

SPECIFICATION:- Freq response 20Hz-20KHz S/N ratio >80dB THD <0.09%(1KHz) Channel separation >80dB(1KHz) Max output voltage 2Vrms Power 220 240Vac 50 60Hz Size W 482 H 88 D 250mm Weight 4.18Kg PRICE:-£225.00 + £5.00 P&P

STEREO DISCO MIXER MPX-7700

ECHO & SOUND EFFECTS



- * 4 STEREO INPUT CHANNELS
- * 2 DJ MIC INPUT CHANNELS
- * 2X7 BAND GRAPHIC EQUALISERS
- * HEADPHONE MONITOR WITH PFL
- * ASSIGNABLE CROSSFADE
- * DIGITAL ECHO

STEREO DISCO MIXER WITH:- •2X7 GRAPHIC EQUALISERS •2 MONO MIC INPUTS •DJ MIC WITH FADER, TALKOVER AND VOICE CHANGER •4 STEREO CHANNELS WITH INDIVIDUAL FADERS AND ASSIGNABLE CROSSFADE •CHANNELS SWITCHABLE, TURNTABLE (MAG CARTRIDGE), CD, LINE, TAPE, ETC. •ECHO WITH BALANCE, REPEAT AND DELAY •HEADPHONE MONITOR WITH PREFADE LISTEN •CHOICE OF 6 SOUND EFFECTS •STEREO MONO SWITCH •2 X LED VU METERS •MASTER FADER •OUTPUT 775mV

•SIZE:- 482X240X115mm •POWER:- 230V AC 50/60Hz. PRICE:- £169.00 + £5.00 P&P

SOUNDLAB MINI STROBE • IDEAL FOR USE IN DISCO'S / RAVES

• EDUCATIONAL EXPERIMENTS ETC.

A top quality mini strobe with high light intensity for its size and variable flash rate adjustment. Housed in a silver/black steel case with adjustable mounting bracket. • Flash Rate: Adjustable from zero to ten flashes per second • Mains Powered complete with plugged lead • 230V AC 50/60Hz • Size:- 125 X 84 X 52mm PRICE:- £19.99 + £2.20 P&P



OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices NOTE that all models include toroidal power supply, integral heat sink, glass fibre PCB and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS

OMP/MF 100 Mos-Fet Output power 100 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110dB. Size 300 x 123 x 60mm. PRICE:- £42.85 + £4.00 P&P

OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110dB. Size 300 x 155 x 100mm. PRICE:- £66.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110dB. Size 330 x 175 x 100mm. PRICE:- £83.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm. PRICE:- £135.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm. PRICE:- £261.00 + £12.00 P&P

NOTE MOS FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD INPUT SENS 500mV, BAND WIDTH 100KHz. OR PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC

B.K. ELECTRONICS

UNIT 1 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR.

TEL.: 01702 527572 FAX.: 01702-420243

Web:- <http://www.bkelec.com> E-mail:- Sales@bkelec.com




DELIVERY CHARGES PLEASE INCLUDE AS ABOVE TO A MAXIMUM AMOUNT £30.00 OFFICIAL ORDERS FROM SCHOOLS COLLEGE GOVT BODIES PLCs ETC PRICES INCLUSIVE OF V.A.T. SALES COUNTER CREDIT CARD ORDERS ACCEPTED BY POST PHONE OR FAX





THE QUICKROUTE

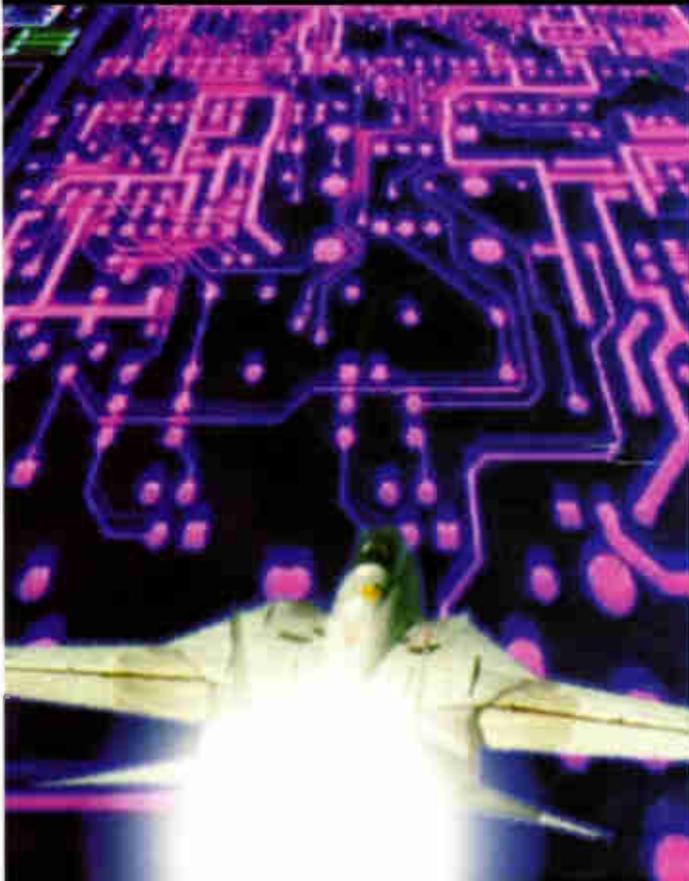

Simulation Circuit Capture PCB Autorouting CAD/CAM

Imagine an electronics design system that lets you draw schematics onto the screen and then simulate them at the touch of a button. Now imagine pressing another button and seeing the schematic replaced with a PCB rats-nest. Pressing another button starts the autorouter, and finally you can click on File then Save As to create a complete set of CAD/CAM files.

Too easy? We hope so. Quickroute has always been designed first and foremost to be easy to use. That's why simulation, circuit capture, PCB autorouting and CAD/CAM support are all integrated into **one** package. So that you only have to learn **one** package.

But it doesn't end there. We have included a wide range of features in Quickroute to help you work effectively. For example our Gerber import facility lets you check your CAD/CAM files before sending them to your manufacturer.

We have also introduced a major new PLUGIN module called the SymbolWizard that actually creates custom symbol designs for you. Simply select a template, specify pad and spacing properties and SymbolWizard creates the schematic and PCB symbols for you!

If you would like to find out more about Quickroute, why not call us on FREEphone 0800 731 28 24, or visit our web site on www.quickroute.co.uk. Prices start at under £100 including UK P&P and VAT for a complete system.

**"modern, powerful
and easy to use"**

Elektor Electronics 97



FREEphone

0800 731 28 24

Int +44 161 476 0202 Fax 0161 476 0505

Web www.quickroute.co.uk

30 DAY MONEY BACK GUARANTEE

