

EVERYDAY

SEPTEMBER 1999

PRACTICAL

ELECTRONICS

With



Starter Project

£2.65

LOOP AERIAL SW RECEIVER

Easy to build and use.
4.5MHz to 14MHz coverage



CHILD GUARD


Helps protect from heat sources

8 CHANNEL DATA LOGGER - 2


Uses the new PIC 16F877

FROM PIPELINES TO PYLONS - 2

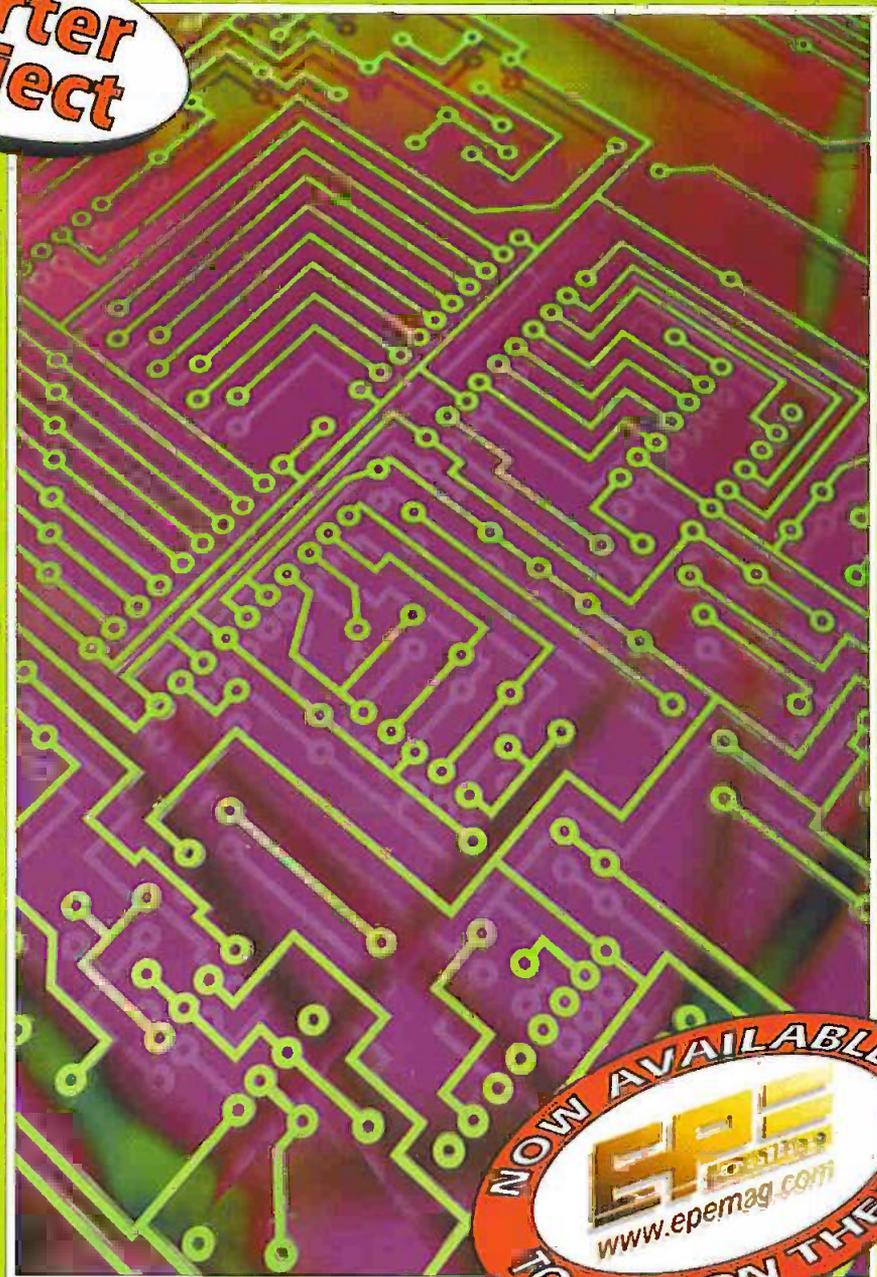The high tech behind our electricity supply



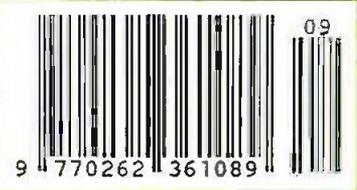THE No.1 MAGAZINE FOR
ELECTRONICS TECHNOLOGY
& COMPUTER PROJECTS



PLUS Ingenuity Unlimited • Circuit Surgery
New Technology Update • Net Work

<http://www.epemag.wimborne.co.uk>

ECG MACHINES 7.6v 10AH BATT/24V 8A TX Ex government ECG machines! Measures 3500/3500/120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear including video out etc. On the front panel are two DIN sockets for connecting the body sensors to. Sensors not included. Inside 2 x 6V 10AH sealed lead acid battery (generally not in good condition), PCB's and a 2A/2.24V toroidal transformer (means in). Sold as seen, may have one or two broken knobs etc due to poor storage. **£195.99** ref VP2

HYDROPONICS DO YOU GROW YOUR OWN? We have a full colour hydroponics catalogue available containing nutrients, pumps, fittings, environmental control, light fittings, plants, test equipment etc Ring for your free copy.

PC COMBINED UPS AND PSU The unit has a total power of 252 watts, standard mother board connections and 12 peripheral power leads for drives etc. Inside is 3 12v 7.2Ah sealed lead acid batteries. Backup time is 8 mins at full load or 30 mins at half load. Made in the UK by Magnum. 110 or 240Vac input, 15v at 35A, 5v at 5A, 12v at 9A, 12v at 5A outputs. 170x250x220mm, new and boxed. **£29.99** Ref: PCUP52

WINDOWS 95 CD As supplied with Hewlett Packard PC's these CDs have all the window files on them and were intended to be used to restore windows on a PC after a crash etc. **£15** REF: SX06

ALTERNATIVE ENERGY CD, PACKED WITH HUNDREDS OF ALTERNATIVE ENERGY RELATED ARTICLES, PLANS AND INFORMATION ETC **£14.50** REF: CD56

aerial photography kit This rocket comes with a built in camera & flies up to 500 feet (150 m) turns over, and takes an aerial photograph of the ground below. The rocket then returns safely with its film via its built in parachute. Takes standard 110 film. Supplied complete with everything including a launch pad and 3 motors (no film). **£29.99** ref: astro

SATELLITE MODULATOR MODULES prices from just 9p. Surface mount modulators full of components. Fitted with an F type connector and a UHF type connector. Pack of 100 **£9.95** ref: SS20

PROJECT BOXES Another bargain for you are these smart ABS project boxes, smart two piece screw together case measuring approx 6" x 4" x 2" complete with panel mounted LED. Inside you will find loads of free bits, tape heads, motors, chips, resistors, transistors etc. Pack of 20 **£19.95** ref: MD2

REMOTE HEATING CONTROLLERS WITH 30A MAINS RELAY from just 99p. These units were designed to be plugged into a telephone socket. You then called the phone and some new bit turned the heating on. Each box contains lots of bits including 3 mains 30A relay. pack of 20 **£20** ref: SS34

PIR CAMERA Built in CCTV camera (composite output) IR strobe light PIR detector and battery backup. Designed to 'sneak' pictures down the phone line but works well as a standalone unit. Bargain price **£39.95** ref: SS81.1. These units are brand new models designed to take 'pictures' of intruders and then transmit the pictures down the telephone line. The PIR detects the intruder, fires the strobe light this ensures a perfect picture even in total darkness. The picture is stored in memory inside the module and then sent by modem (not included) down the telephone line. The units also have a nicad battery pack included presumably to maintain operation in the event of mains power failure. Output from the camera is standard B/W composite. 320x240 pixels with a 60x65 degree field of view, the picture quality is excellent. Each PIR also contains a video capture and compression unit. The infra red strobe has a range of 15m. The PIR has a range of 12m. Power requirements are 12v dc 400mA. Power supplies available at **£5** ref: SS30. The units are supplied with connection details etc but we do not have any information on using the compression and capture unit or interfacing to modems etc. The units do have operational PIR's, strobes and camera's (camera is 12vdc and gives out standard composite 1v p-p video) how you adapt these to work together is entirely up to you. Retail price for the units was in excess of £200 each sale price **£39.95** ref: SS81.1. Power supplies **£5** ref: SS80

TELEPHONES Just in this week is a huge delivery of telephones, all brand new and boxed. Two piece construction with the following features: illuminated keypad, tone or pulse (switchable), recall, redial and pause, high/low and off ringer switch and quality construction finished in a smart off white colour and is supplied with a standard international lead (same as US or modems) if you wish to have a BT lead supplied to convert the phones these are also available at **£1.55** each ref: BTX. Phones **£4.99** each ref: PH2 10 off **£30** ref: SS2

3HP MAINS MOTORS Single phase 240v, brand new, 2 pole, 340x180mm, 2550 rpm, built in automatic reset overload protector, keyed shaft (40x16mm). Made by Leeson. **£99** each ref: LEE1

BUILD YOUR OWN WINDFARM FROM SCRAP New publication gives step by step guide to building wind generators and propellers. Armed with this publication and a good local scrap yard could make you self sufficient in electricity! **£12** ref: LOT181

CHEFTANTANK DOUBLE LASERS 9 WATT + 3 WATT + LASER OPTICS Could be adapted for laser listener, long range communications etc. Double beam units designed to scan the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment. 7 mile range, no circuit diagrams due to MOD, new price **£50,000?** us? **£199**. Each unit has two gallium Arsenide injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 20vdc, 600KHz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets. **£199** Ref: LOT14

MAGNETIC CREDIT CARD READERS AND ENCODING MANUAL **£9.95** Cased with flyzoids, designed to read standard credit cards, complete with control electronics PCB and manual covering everything you could want to know about what's hidden in that magnetic strip on your card! just **£9.95** ref: BAR31

Hipower 12v xenon strobe variable rate flasher modules and tubes. CRUseful! 12v PCB fitted with control electronics and a powerful Xenon tube! just apply 12v DC to the input and the tube will flash. On the board is a small potentiometer which can be used to vary the flash rate. PCB measures just 70x55mm and could be incorporated into many interesting projects! **£5** ref: FLS14. Pack of 10 is **£45** ref: FLS2

Hydrogen fuel cells now in stock

Our new Hydrogen fuel cells are 1v at up to 1A output. Hydrogen input, easily driven from a small electrolosis assembly or from a hydrogen source, our demo model uses a solar panel with the output leads in a glass of salt water to produce the hydrogen. Each cell is designed to be completely taken apart, put back together and expanded to what ever capacity you like, (up to 10watts and 12v per assembly. Cells cost **£79** ref: HFC11

We get over 8,000 hits a day..... check us out!

<http://www.bullnet.co.uk>

PHILIPS VP406 LASER DISC PLAYERS, SCART OUTPUT, RS232 CONTROLLED **£24.95** REF: VP406

SMOKE ALARMS Mains powered, made by the famous Gent company, easy fit next to light fittings, power point. Pack of 5 **£15** ref: SS23, pack of 12 **£24** ref: SS24

4AH D SIZE NICADs pack of 4 **£10** ref: 4AHPK

ELECTRIC FENCE KIT Everything you need to build a 12vdc electric fence, complete with 200m of fence wire. **£49** ref: AR2

SENDER KIT Contains all components to build a AM transmitter, complete with case. **£35** ref: VSX02

10 WATT SOLAR PANEL Amorphous silicon panel fitted in a anodized aluminum frame. Panel measures 3' by 1' with screw terminals for easy connection. 3' x 1' solar panel **£55** ref: MAG45. Unframed 4 pack (3'x1') **£58.99** ref: SOLX

12V SOLAR POWERED WATER PUMP Perfect for many 12v DC uses, ranging from solar fountains to hydroponical! Small and compact yet powerful, works direct from our 10 watt solar panel in bright sun. Max flow 17 fl. oz. Max flow = 8 lpm. 1 SA Ref: ACB. **£18.99**

SOLAR ENERGY BANK KIT 50x 6"x12" 6v solar panels (amorphous) + 50 diodes **£99** ref: EF112

PINHOLE CAMERA MODULE WITH AUDIO! Super board camera with on board sound! extra small just 28mm square (including microphone) ideal for covert surveillance. Can be hidden inside anything, even a matchbox! Complete with 15 metre cable, psu and i/over connectors. **£49.95** ref: CCGU

SOLAR MOTORS Tiny motors which run quite happily on voltages from 3-12vdc. Works on our 6v amorphous 6' panels and you can run them from the sun! 32mm dia 20mm thick. **£1.50** each

WALKIE TALKIES 1 MILE RANGE **£37/PAIR** REF: MAG30

LIQUID CRYSTAL DISPLAYS Bargain prices, 20 character 2 line, 83x19mm **£3.99** ref: SMC2024A

16 character 4 line, 62x25mm **£5.99** ref: SMC1640A

4D character 1 line 154x16mm **£6.00** ref: SMC4D11A

YOUR HOME COULD BE SELF SUFFICIENT IN ELECTRICITY! Comprehensive plans with loads of info on designing systems, panels, control electronics etc. **£7** ref: PV1

LOW COST CORDLESS MIC 500 range, 90-105mhz, 11.5g, 193 x 26 x 39mm, 9v PP3 battery required. **£17** ref: MAG15P1

AUTO SUNCHARGER 155x600mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. **£12.99** REF: AUC10P3

SOLAR POWER LAB SPECIAL 2x 6v 6v 133mA cells, 4 LEDs, wire, buzzer, switch, 1 relay or motor. **£7.99** REF: SA27

SOLAR NICAD CHARGERS 3 x AA size **£9.99** ref: 6P476, 2 x C size **£9.99** ref: 6P477

5.25" FLOPPY DISKS pack of 500 disks **£25** ref: FD.

REGISTER FOR OUR ELECTRONIC NEWSLETTERS BULL-ELECTRICAL.COM

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS **£4.00** P & P PLUS VAT.

24 HOUR SERVICE **£6.50** PLUS VAT.

OVERSEAS ORDERS AT COST PLUS **£3.50**

(ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

phone orders : **01273 203500**

FAX **01273 323077**

Sales@bull-electrical.com

30 WATTS OF SOLAR POWER for just **£69.94** panels each one 3'x1' and producing 8w, 13v. **PACK OF FOUR** **£69** ref: SOLX

200 WATT INVERTERS plugs straight into your car cigarette lighter socket and is fitted with a 13A socket so you can run your mains operated devices from your car battery. **£49.95** ref: SS66

THE TRUTH MACHINE Tests if someone is lying by micro tremors in the voice, battery operated, works in general conversation and on the phone and TV as well. **£42.49** ref: TD3

INFRA RED FILM 6" square piece of flexible infra red film that will only allow IR light through. Perfect for converting ordinary torches, lights, headlights etc. to infra red output only using standard light bulbs. Easily cut to shape. 6" square **£15** ref: IRF2

33 KILO LIFT MAGNET Neodymium, 32mm diameter with a fixing bolt on the back for easy mounting. Each magnet will lift 33 kilos, 4 magnets bolted to a plate will lift an incredible 132 kilos! **£15** ref: MAG33

HYDROGEN FUEL CELL PLANS Loads of information on hydrogen storage and production. Practical plans to build a hydrogen fuel cell (good workshop facilities required) **£5** set ref: FCP1

STIRLING ENGINE PLANS Interesting information on pack covering all aspects of Stirling engines, pictures of home made engines made from an aerosol can running on a candle! **£12** ref: STIR2

ENERGY SAVER PLUGS Saves up to 15% electricity when used with fridges, motors up to 2A, light bulbs, soldering irons etc. **£9** ea ref: LOT71, 10 pack **£69** ref: LOT72

12V OPERATED SMOKE BOMBS Type 3 is a 12v trigger and 3 smoke canisters, each canister will fill a room in a very short space of time! **£14.99** ref: SB3. Type 2 is 20 smaller canisters (suitable for simulated equipment fires etc) and 1 trigger module for **£29** ref: SB2. Type 1 is a 12v trigger and 20 large canisters. **£49** ref: SB1

HIPOWER ZENON VARIABLE STROBES Use! 12v PCB fitted with hi power strobe tube and control electronics and speed control potentiometer. Perfect for interesting projects etc. 70x55mm 12vdc operation. **£5** ea ref: FLS1, pack of 10 **£49** ref: FLS2

NEW LASER POINTERS 4.5mw, 75 metre range, hand held unit runs on two AA batteries (supplied) 670nm. **£29** ref: DEC48J

HOW TO PRODUCE 35 BOTTLES OF WHISKY FROM A SACK OF POTATOES Comprehensive 270 page book covers all aspects of spirit production from everyday materials. Includes construction details of simple stills. **£12** ref: M53

NEW HIGH POWER MINI BUG With a range of up to 800 metres and a 3 axis use from a PP3, this is our top selling bug! less than 1" square and a 10m voice pickup range. **£28** ref: LOT102

IR LAMP KIT Suitable for CCTV cameras, enables the camera to be used in total darkness! **£6** ref: EF136

INFRA RED POWERBEAM Handheld battery powered lamp, 4 inch reflector, gives out powerful pure infrared light! perfect for CCTV use, nightlights etc. **£29** ref: PB1

SUPERWIDEBAND RADAR DETECTOR Detects both radar and laser, XK and KA bands, speed cameras, and all known speed detection systems. 360 degree coverage, front & rear waves/guides. 1.1x2.7x4.6" fits on visor or dash. **£149**

LOPTX Made by Samsung for colour TV. **£3** each ref: SS52

LAPTOP LCD SCREENS 240x170mm, **£12** ref: SS51

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have compiled 140 business manuals that give you information on setting up different businesses, you purchase these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! **£14** ref: EP74

HIGH POWER DC MOTORS, PERMANENT MAGNET 12 - 24v operation, probably about 1/4 horse power, body measures 103mm x 75mm with a 60mm x 5mm output shaft with a machined flat on it. Fixing is simple using the two threaded bolts protruding from the front. **£22** ref: MOT4

INFRA RED REMOTE CONTROLS made for TVs but may have other uses pack of 100 **£39** ref: IREM



Online
web catalogue
bull-electrical.com

ELECTRONIC SPEED CONTROLLER KIT For the above motor is **£19** ref: MAG17. Save **£5** if you buy them both together. 1 motor plus speed controller rrp is **£41**, offer price **£36** ref: MOT5A



SONY STEREO TV CHASSIS assemblies comprising complete TV PCB excluding tube and scan coils. Nearm stereo, mains input. Appear to be unused but sold as seen. Would probably be good for spares or as a means stereo TV PCB sound receiver and amplifier. Fax: **KV29F1U** and **KV29F1U(BE30)** PCB nos: 1-659-827-12 1-859-826-14 1-741-600-11 **£30** ref: STV1

RCB UNITS In line IEC lead with fitted RC breaker. Installed in seconds.

Pack of 3 **£9.98** ref: LOT5A

RADIO CONTROLLED CARS etc. No remotes but good strippers for servos motors and receivers. Sold as is, no returns, mixed types. **£3** each ref: ROC2

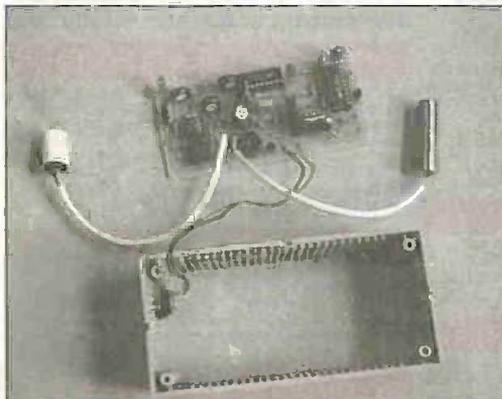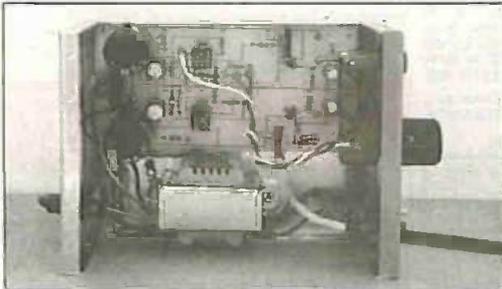VOICE CHANGERS Hold one of these units over your phone mouth piece and you can adjust your voice using the controls on the unit! Battery operated **£15** ref: CC3



© Wimborne Publishing Ltd 1999. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS/ETI is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our October '99 Issue will be published on Friday, 3 September 1999. See page 627 for details.

Everyday Practical Electronics/ETI, September 1999

Projects and Circuits

- LOOP AERIAL SW RECEIVER** by Robert Penfold **636**
Discover the thrill of making your own radio with this simple Starter Project!
- VARIABLE DUAL POWER SUPPLY** by Tony Sercombe **646**
Fully variable from $\pm 3V$ to $\pm 15V$ up to 500mA, and short-circuit proof*
- CHILD GUARD** by Tom Webb **662**
Helping to protect your loved ones, an audible warning sounds if children (or others) approach a fire
- INGENUITY UNLIMITED** hosted by Alan Winstanley **668**
Theatrical Cue Light; Morse Practice Oscillator; Keypad Code Controller; Intercom/Baby Listener; TV Test pattern Generator
- 8-CHANNEL ANALOGUE DATA LOGGER - 2** by John Becker **688**
How to use this highly versatile PIC16F877 micro-controlled design

Series and Features

- NEW TECHNOLOGY UPDATE** by Ian Poole **640**
Optical phase-shifting helps photolithography reduce chip sizes
- POWER GENERATION FROM PIPELINES TO PYLONS - 2**
by Alan Winstanley **652**
Concluding our on-site tour of electrical power generation and delivery
- PRACTICALLY SPEAKING** by Robert Penfold **660**
A novice's guide to capacitor types and choices
- PRACTICAL OSCILLATOR DESIGNS - 3.** Armstrong, Meissner, Franklin and Butler, plus R.F. probes by Raymond Haigh **678**
Worked examples and circuit info for hands-on constructors
- CIRCUIT SURGERY** by Alan Winstanley and Ian Bell **693**
Transducer User; Photo-sensor; R.M.S. - Stand by for the Maths; Powerless to Help
- NET WORK - THE INTERNET PAGE** surfed by Alan Winstanley **699**
Desoldering Guide; Zoom through the Hayes; Big-Footed E-mail for Life; Virus Updates

Regulars and Services

- EDITORIAL** **635**
- NEWS** - Barry Fox highlights technology's leading edge **643**
Plus everyday news from the world of electronics
- READOUT** John Becker addresses general points arising **649**
- SHOPTALK** with David Barrington **672**
The essential guide to component buying for EPE projects
- ELECTRONICS VIDEOS** Our range of educational videos **675**
- CD-ROMS FOR ELECTRONICS** **676**
Parts Gallery + Electronic Circuits and Components; Digital Electronics; Analogue Electronics; plus PICtutor, plus Modular Circuit Design; see also Direct Book Service pages
- BACK ISSUES** Did you miss these? **686**
- DIRECT BOOK SERVICE** **696**
A wide range of technical books available by mail order, plus more CD-ROMs
- PRINTED CIRCUIT BOARD AND SOFTWARE SERVICE** **700**
PCBs for EPE projects - some at "knockdown" prices! Plus EPE software
- ADVERTISERS INDEX** **704**

Readers Services • Editorial and Advertisement Departments **635**

625

Visit our website
www.distel.co.uk

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always
wanted for cash!

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND &
VIDEO TUNER
CABLE COMPATIBLE*

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors or AV equipment which are fitted with a composite video or SCART input. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tunable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. Ideal for desktop computer video systems & PC (picture in picture) setups. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard. Brand new - fully guaranteed.

TELEBOX ST for composite video input type monitors £36.95
TELEBOX STL as ST but fitted with integral speaker £39.50
TELEBOX MB Multiband VHF/UHF/Cable/hyperband tuner £69.95
For overseas PAL versions state 5.5 or 6 MHz sound specification.
*For cable / hyperband signal reception Telebox MB should be connected to a cable type service. Shipping on all Teleboxes, code (B)

NEW State of the art PAL (UK spec) UHF TV tuner module with composite TV pp video & NICAM hi fi stereo sound outputs. Micro electronics all on one small PCB only 73 x 160 x 52 mm enable full tuning control via a simple 3 wire link to an IBM pc type computer. Supplied complete with simple working program and documentation. Requires +12V & +5V DC to operate. **BRAND NEW - Order as MY00. Only £49.95 code (B)**
See www.distel.co.uk/data_my00.htm for picture & full details

FLOPPY DISK DRIVES 2 1/2" - 8"

All units (unless stated) are **BRAND NEW** or removed from other brand new equipment and are fully tested, aligned and shipped to you with a full 90 day guarantee. Call or see our web site www.distel.co.uk for over 2000 untested drives for spares or repair.

- 3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only £25.95(B)
- 3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop £18.95(B)
- 5 1/4" Teac FD-55GF 1.2 Meg (for IBM PCs) RFE £18.95(B)
- 5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's etc) RFE £29.95(B)
- 5 1/4" BRAND NEW Mitsubishi MF501B 350K £22.95(B)
- Table top case with integral PSU for HI 5 1/4" Floppy / HD £29.95(B)
- 8" Shugart 800/501 B SS refurbished & tested £120.00(E)
- 8" Shugart 810 B SS HI Brand New £195.00(E)
- 8" Shugart 851 B double sided refurbished & tested £260.00(E)
- 8" Mitsubishi M2894-63 double sided NEW £295.00(E)
- 8" Mitsubishi M2896-63-02U DS slimline NEW £295.00(E)
- Dual 8" cased drives with integral power supply 2 Mb £499.00(E)

HARD DISK DRIVES 2 1/2" - 14"

- 2 1/2" TOSHIBA MK1002MAV 1.1Gb laptop(12.5 mm H) New £79.95
 - 2 1/2" TOSHIBA MK2101MAN 2.16 Gb laptop (19 mm H) New £89.50
 - 2 1/2" TOSHIBA MK4309MAT 4.3Gb laptop (8.2 mm H) New £105.00
 - 2 1/2" TOSHIBA MK4409MAV 6.1Gb laptop (12.7 mm H) New £190.00
 - 2 1/2" to 3 1/2" conversion kit for PCs, complete with connectors £14.95
 - 3 1/2" FUJI FK-309-26 20mb MFM U/F RFE £59.95
 - 3 1/2" CONNER CP3024 20 mb IDE U/F (or equiv.) RFE £59.95
 - 3 1/2" CONNER CP3044 40 mb IDE U/F (or equiv.) RFE £69.00
 - 3 1/2" QUANTUM 405 Prodril ve 42mb SCSI U/F, New RFE £49.00
 - 5 1/4" MINISCRIIBE 3425 20mb MFM U/F (or equiv.) RFE £49.95
 - 5 1/4" SEAGATE ST-238R 30 mb RLL U/F Refurb £69.55
 - 5 1/4" CDC 94205-51 40mb HI MFM U/F RFE tested £69.95
 - 5 1/4" HP 97549 850 Mb SCSI RFE tested £99.00
 - 5 1/4" HP C3010 2 Gbyte SCSI differential RFE tested £195.00
 - 5 1/4" NEC D2246 85 Mb SMD interface. New £199.00
 - 8" FUJITSU M2322K 160Mb SMD U/F RFE tested £195.00
 - 8" FUJITSU M2392K 2 Gb SMD U/F RFE tested £345.00
- Many other drives in stock - Shipping on all drives is code (C1)

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK
10,000,000 items EX STOCK
For MAJOR SAVINGS
CALL OR SEE OUR WEB SITE www.distel.co.uk

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see -
At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PCs in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features. Eached facplate, test switching and LOW RADIATION MPR specification. Fully guaranteed. In EXCELLENT little used condition.

Tilt & Swivel Base £475
VGA cable for IBM PC included.
Only £119 (B) Order as MITS-SVGA
External cables for other types of computers available - CALL

Ex demo 17" 0.28 SVGA Mitsubishi Diamond Pro monitors, Full multisync etc.
Full 90 day guarantee. Only £199.00 (E)

Just In - Microvitec 20" VGA (800 x 600 res), colour monitors. Good SH condition - from £299 - CALL for info

PHILIPS HCS35 (same style as CM8533) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed
Dimensions: W14" x H12 3/4" x 15 1/2" D.
Only £99.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen blem). In attractive square black plastic case measuring W10" x H10" x 1 1/2" D. 240 V AC mains powered.
Only £79.00 (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 khz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only £125 (E)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. Fill all solid state colour monitors, complete with composite video & optional sound input. Attractive leak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185 (F)

We probably have the largest range of video monitors in Europe. All sizes and types from 4" to 42" call for info.

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock
Call or see our web site.

19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!




Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting, plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays. Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:

OPT Rack 1 Complete with removable side panels. £345.00 (G)
OPT Rack 2 Rack. Less side panels £245.00 (G)

Over 1000 racks, shelves, accessories
19" 22" & 24" wide 3 to 46 U high.
Available from stock !!

32U - High Quality - All steel RakCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of integral fans to the sub panel etc. Other features include: fitted casters and floor levers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour, Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 1/2" W)

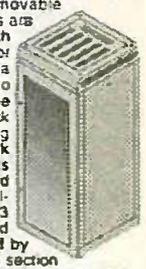

Sold at LESS than a third of makers price !!

A superb buy at only £245.00 (G)
42U version of the above only £345 - CALL

12V BATTERY SCOOP - 60% off !!


A special bulk purchase from a cancelled export order brings you the most amazing savings on these ultra high spec 12v DC 14 Ah rechargeable batteries. Made by Hawker Energy Ltd, type SBS15 featuring pure lead plates which offer a far superior shelf & guaranteed 15 year service life. Fully BT & BS6290 approved. Supplied BRAND NEW and boxed. Dimensions 200 wide, 137 high, 77 deep. M6 bolt terminals. Fully guaranteed. Current makers price over £70 each
Our Price £35 each (C) or 4 for £99 (E)

RELAYS - 200,000 FROM STOCK

Save ££££'s by choosing your next relay from our Massive Stocks covering types such as Military, Octal, Cradle, Hermetically Sealed, Continental, Contactors, Time Delay, Relay, Mercury/Wetted, Solid State, Printed Circuit Mounting etc. CALL or see our web site www.distel.co.uk for more information. Many obsolete types from stock. Save ££££'s

COLOUR CCD CAMERAS

Undoubtedly a miracle of modern technology & our special buying power! A quality product featuring a fully cased COLOUR CCD camera at a give away price! Ultra features full auto light sensing for use in low light & high light applications. A 10 mm fixed focus wide angle lens gives excellent focus and resolution from close up to long range. The composite video output will connect to any composite monitor or TV (via SCART socket) and most video recorders. Unit runs from 12V DC so ideal for security & portable applications where mains power not available. Overall dimensions 66 mm wide x 117 deep x 43 high. Supplied BRAND NEW & fully guaranteed with user data. 100's of applications including Security, Home Video, Web TV, Web Cams etc, etc.
Web ref = LK33 ONLY £99.00 or 2 for £180.00 (B)

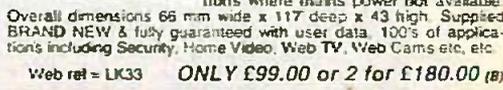

SOFTWARE SPECIALS

NT4 WorkStation, complete with service pack 3 and licence - OEM packaged. ONLY £89.00 (B)
ENCARTA 95 - CDROM, Not the latest - but at this price!! £7.95
DOS 5.0 on 3 1/2" disks with concise books c/w CBasic £14.95
Windows for Workgroups 3.11 + Dos 6.22 on 3.5" disks £55.00
Wordperfect 6 for DOS supplied on 3 1/2" disks with manual £24.95
shipping charges for software is code B

TEST EQUIPMENT & SPECIAL INTEREST ITEMS

- MITS. FA3415ETKL 14" Industrial spec SVGA monitors £245
- FARNELL 0-60V DC @ 50 Amps, bench Power Supplies £995
- FARNELL AP3080 0-30V DC @ 80 Amps, bench Supply £1850
- 1kW to 400 kW - 400 Hz 3 phase power sources - ex stock £1850
- IBM 8230 Type 1, Token ring base unit driver £760
- Wayne Kerr RA200 Audio frequency response analyser £2500
- IBM 53F501 Token Ring ICS 20 port lobe modules £750
- IBM MAU Token ring distribution panel B228-23-5050N £95
- AIM 501 Low distortion Oscillator 9Hz to 330KHz, IEEE £550
- ALLGON 8360, 11805-1680 MHz hybrid power combiners £250
- Trend DSA 274 Data Analyser with G703(2M) 64 Wb EPOA £6500
- Marconi 6310 Programmers 2 to 22 GHz sweep generator £1550
- Marconi 2022C 10KHz-1GHz RF signal generator £4995
- Marconi 2030 opt 03 10KHz-1 GHz RF signal generator New £3750
- HP1650B Logic Analyser EPOA
- HP3781A Pattern generator & HP3782A Error Detector EPOA
- HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts £1800
- HP6264 Rack mount variable 0-20V @ 20A metered PSU £675
- HP54121A DC to 22 GHz low channel test set EPOA
- HP8130A opt 020 300 MHz pulse generator, GPIB etc £7900
- HP AT, AD 8 pen HPGL high speed drum plotters - from £550
- HP DRAFTMASTER 1 8 pen high speed plotter £750
- EG-G Brookdeal 55035C Precision lock in amp £1800
- View Eng. Mod 1200 computerised inspection system EPOA
- Sony DXC-300GA High quality CCD colour TV camera £995
- Kelthley 590 CV capacitor / voltage analyser EPOA
- Rascal ICR40 dual 40 channel voice recorder system £3750
- Fiskers 45KVA 3 ph On Line UPS - New batteries £9500
- Emerson AP130 2.5KVA industrial spec UPS £2100
- Mann Tally MT645 High speed line printer £2200
- Intel SBC 486/335SE Multibus 486 system, 8Mb Ram £945
- Siemens K4400 64Kb to 140Mb demux analyser £2950

- HP6030A 0-200V DC @ 17 Amps bench power supply £1950
- Intel SBC 486/125C08 Enhanced Multibus (MSA) New £1150
- Nikon HFX-11 (Ephiphot) exposure control unit £1450
- PHILIPS PM5518 pro. TV signal generator £1250
- Motorola VME Bus Boards & Components List, SAE / CALL £1250
- Trio 0-18 vdc linear, metered 30 amp bench PSU. New £550
- Fujitsu M3041R 600 LPM high speed band printer £1950
- Fujitsu M3041D 600 LPM printer with network interface £1250
- Perkin Elmer 299B Infrared spectrophotometer £500
- Perkin Elmer 597 Infrared spectrophotometer £3500
- VG Electronics 1035 TELETEXT Decoding Margin Meter £3250
- LightBand 60 output high spec 2u rack mount Video VDA's £495
- Sekonic SD 150H 18 channel digital Hybrid chart recorder £1995
- B&K 2633 Microphone pre amp £300
- Taylor Hobson Talysurf amplifier / recorder £750
- ADC SS200 Carbon dioxide gas detector / monitor £1450
- BBC AM20/3 PPM Meter: (Ernest Turner) - drive electronics £75
- ANRITSU 9654A Optical CD-2.5Gb/wavelorn meter £5650
- ANRITSU MS9001B1 0.6-1.7 uM optical spectrum analyser EPOA
- ANRITSU ML93A optical power meter E990
- ANRITSU Fibre optic characteristic test set EPOA
- R&S FT0Z Dual sound unit E650
- R&S SBUF-E1 Vision modulator E775
- WILTRON 6630B 12.4 / 20GHz RF sweep generator £5750
- TEK 2445 150 MHz 4 trace oscilloscope £1250
- TEK 2465 300 MHz 300 MHz oscilloscope rack mount £1955
- TEK TDS360 400MHz digital realtime - disk drive, FFT etc £2900
- TEK TDS524A 500MHz digital realtime - colour display etc £5100
- PH3585A Opt 907 20Hz to 40 Mhz spectrum analyser £3950
- PHILIPS PW1730/10 60KV XRAY generator & accessories EPOA
- CLAUDE LYONS 12A 240V single phase auto. volt. regs. £325
- CLAUDE LYONS 100A 240/415V 3 phase auto. volt. regs. £2900

DISTEL on the web !! - Over 16,000,000 items from stock - www.distel.co.uk



ALL MAIL TO
Dept PE, 29/35 Osborne Rd
Thornton Heath
Surrey CR7 8PD
Open Mon - Fri 9.00 - 5:30

LONDON SHOP
Open Mon - Sat 9:00 - 5:30
215 Whitehorse Lane
South Harwood
On S&A Bus Route
N Thornton Heath &
Salthurst Park SR Rail Stations

NEW DISTEL
Visit our web site
www.distel.co.uk
email = admin@distel.co.uk

ALL ENQUIRIES
0208 653 3333
FAX 0208 653 8888

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bank Fin. account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00, (B)=£5.50, (C)=£8.50, (D)=£2.50, (E)=£5.00, (F)=£20.00, (G)=CALL. Allow approx 6 days for shipping - later CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top Cash prices paid for surplus goods. All trademarks, tradenames etc acknowledged © Display Electronics 1999. E & O.E 07/99

NEXT MONTH


PIC16F87x MINI TUTORIAL

As we explained in the 8-Channel Analogue Data Logger of Aug/Sept '99, the PIC16F87x family of microcontrollers are much more powerful than the familiar '84 devices: up to eight channels of ADC; serial communications I/O at controllable baud rates; enlarged program and on-chip EEPROM memories; 20MHz maximum clock rate; external serial data memory read/write.

In this Mini Tutorial we take a closer look at how the PIC16F87x family can be programmed to implement the type of functions offered by the Data Logger. Knowledge of how and why these routines are written will greatly assist you in writing similar functions for other applications. The discussions have the emphasis placed on the PIC16F877 device, but in principle they equally apply to the PIC16F873, '874 and '876 devices as well.

Some of the author's investigations were clouded by ambiguities in the PIC16F87x data sheet and took considerable experimental research to understand how to implement some functions. By reading this article, you could be saved much time and heart-ache when attempting to use the functions in your own designs.

THE QWL LOUDSPEAKER

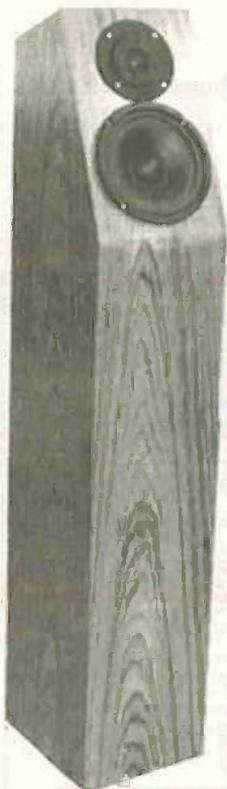

The design and construction of a Quarter Wave Loaded loudspeaker system.

This article was written originally in 1988 for ETI, and a modified version is presented describing the incorporation of improved drivers and a matching crossover. It is hoped that the design will appeal to existing owners of the QWL in terms of an upgrade, as well as to new constructors looking for a wide frequency range loudspeaker occupying a reasonable floor space.

The choice of loudspeaker is often a very personal decision and this design is the result of hours of measurement and listening. Over the years friends have been invited to audition these speakers and, as their performance received very favourable comments by even the most candid listener, it is felt that the majority of readers will not be disappointed with the results of this project.

These loudspeakers are relatively cheap for the performance obtained (as a useful rule of thumb they compare very favourably with commercial designs costing in the order of three times the cost of the speaker units and crossovers in this design) and are fairly simple to build. They occupy very little floor space, are easily moved to a desired position for serious listening, and are of the right height to preclude the need for stands. The overall design has been carefully selected on the basis of a combination of good measured frequency response, stereo imaging, sound quality and efficiency.

MAINS CABLE DETECTOR

Probably most do-it-yourself enthusiasts are aware of the dangers of drilling into the walls of practically any building, and use some form of pipe/cable detector to check that it is safe prior to doing any work of this type. Such precautions should ensure that there are no nasty surprises, but some types of cable can be difficult to detect. Most pipe and cable locators are actually metal locators that are optimised for this application. They are quite good at finding things like nails in doors and plasterwork, locating metal pipes, and finding cables in metal conduits. They tend to be less effective at finding electric cables that are in plastic conduits. The problem seems to be that there is simply not that much metal in an electric cable, especially a lighting type that is only designed to carry modest currents. This makes such cables difficult to detect unless they are close to the surface of a wall.

The project featured here uses an alternative approach to finding cables, which is to pick up the 50-hertz mains "hum" signal produced by the cable. This signal is relatively easy to locate even with a small cable that is buried deep in a wall.

**PLUS:
ALL THE
REGULAR
FEATURES**

NO ONE DOES IT BETTER

EVERYDAY
PRACTICAL
ELECTRONICS

ETI
ELECTRONICS
TODAY INTERNATIONAL

DON'T MISS AN
ISSUE - PLACE YOUR
ORDER NOW!
Demand is bound to be high

OCTOBER ISSUE ON SALE FRIDAY, SEPTEMBER 3

Computer Controlled Robotics

Bring Electronics to Life

	3 Axis Arm	£115		Carpet Rover	£89
	5 Axis Arm	£139		Mobile Arm	£179
	Hexapod Walker	£110		Micro Mouse	£79

Technology Education Index

Telephone for our catalogue or visit our web site for further details

40 Wellington Road, Orpington, Kent BR5 4AQ

Telephone - (01689) 876880

Web Site - <http://www.technologyindex.com>

Prices exclude VAT and £5.00 next day carriage



PLASTIC BOXES & ENCLOSURES

Contact us for your free catalogue

S.L.M. (Model) Engineers Ltd
Chiltern Road
Prestbury
Cheltenham
GL52 5JQ

Telephone 01242 525488
Fax 01242 226288

HOW DOES YOUR EQUIPMENT MEASURE UP? AT STEWART OF READING THERE'S ALWAYS 'SCOPE' FOR IMPROVEMENT!

PHILIPS PM3217 - Dual Trace 50MHz Delay
VERY GOOD OSCILLOSCOPE incl. 2 probes, Touch & Front cover. Only version not incl. probes, etc. FROM **£200** **£300**

GOULD OS300 Dual Trace 20MHz. Light weight. Very good value. **ONLY £160**

THIS IS THE BEST CHEAP SCOPE YOU WILL EVER BUY!!!

GOULD OS1100 - Dual Trace, 30MHz Delay. Very bright, supplied with manual and two probes. **£200**

TEKTRONIX 2215 - Dual Trace 50MHz
Sweep Delay Includes 2 probes **ONLY £350**

TEKTRONIX 400 SERIES

468 Digital Storage Dual Trace 100MHz Delay	£500
466 Analogue Storage Dual Trace 100MHz Delay	£280
465 Dual Trace 350MHz Delay Sweep	£750
478 Dual Trace 200MHz Delay Sweep	£450
468 Dual Trace 100MHz Delay Sweep	£350

HC3502 Dual Trace 20MHz 5mV-20V Div 0-2s. Acc. 0-5 Sec/Div. X-Y: X5 Magnifier, TV-type etc. **UNUSED £180**

OSCILLOSCOPES

PHILIPS PM3002 2+2 ch., 100MHz delay, etc.	£300
TEKTRONIX T45465 dual trace, 100MHz delay, etc.	£250
TEKTRONIX T4554 4 ch., 350MHz delay, etc.	£250
TEKTRONIX 24158 dual trace, 150MHz delay, etc.	£150
TEKTRONIX 2255 dual trace, 20MHz	£300
KIKUSUI 6100 5-trace, 100MHz delay	£25
TEKTRONIX 2430 dig storage dual trace, 150MHz	£1200
TEKTRONIX 2212 dig storage dual trace, 50MHz	£750

THESE TWO HAVE NEVER BEEN SO CHEAP

TEKTRONIX 2445, 4-ch. delay sweep, cursors, readout. ONLY £700

MARCONI 2019A synthesised AM/FM signal gen 80kHz-1040MHz. Led. display, keyboard entry. ONLY £750
ALL FULLY TESTED - IN GOOD CONDITION

MARCONI 5211 drop sweep gen. 10kHz-20GHz **£4000**
HP 8657A syn sig gen. 100kHz-100MHz **£2500**
HP 8652B syn sig gen. 100kHz-800MHz **£1500**
HP 8656A syn sig gen. 100kHz-500MHz **£1250**
MGATRONIC 7100 syn sig gen. 10MHz-200GHz **£6000**
MARCONI 2107 AM/FM phase locked sig gen. 100kHz-100MHz **£2000**

HP 4275A LCR meter, 10kHz-10MHz **£750**
HP 41182A LF impedance analyser, 5Hz-10MHz **£900**
MARCONI 2206 mod meter, 500Hz-20GHz. **£800**
FARNELL JUM2000 auto read meter, 10Hz-2.4GHz, unused. **£1250**
STABLELOCK 4018 radio counter test set **£2250**
HP 5352B freq counter, 20GHz **£3000**
HP 342B noise source, 10MHz-10GHz **£500**
HP 11622D dual dir coupler, 20Hz-10GHz **£1500**
HP 11691D dual dir coupler, 20Hz-10GHz **£1250**

H.P. 6640A AM/FM Signal Gen 500kHz-1024 MHz 500kHz-512 MHz version. £450 £250

SPECTRUM ANALYSERS

H.P. 8592E 90kHz-5.50GHz with Ops 004011/0211/05/11/0. **£3000**
55717A Gen and 8502A high freq probe **£2250**
H.P. 8592A 90kHz-1.8GHz (75% duty) **£2250**
H.P. 8555B with main frame 100kHz-1500MHz **£1250**
H.P. 8532A (dig frame) with 8556A 100kHz-21GHz **£2750**
H.P. 3522A dual channel 250kHz **£2000**
MARCONI 2382 100Hz-400MHz high resolution **£2250**
B&K 2202SR signal analyser **£3000**
ADVANTEST TR4111 50kHz-2.5GHz **£3000**
MARCONI 2370 30kHz-12MHz **From £500**
H.P. 841 Systems: **From £500**
8533 110Hz-110MHz **From £750**
8534 500kHz-1250MHz **From £1000**
8552 10MHz-10GHz

MARCONI TF2015 AM/FM Sig Gen 10-520MHz £175

RACAL 9008 Automatic mod meter 1-5MHz-2GHz £200

WATHE KERR induction analyser 3245 **£2000**
H.P. 8112A pulse generator 50MHz **£1250**
DATRON AutoCh multimeter, 20-7th digit, 10651081A/1071 **£300-£250**

SONEIMBERGER 7081 precision voltmeter, 8+1-digit **£1500**
RACAL 1958 freq counter, 100kHz-10MHz, IEEE etc. **£400**
MARCONI 2440/2443 freq counter, 200kHz-250GHz. **From £1250**
PHILIPS FM5228 sig gen. 100kHz-180MHz, with built-in 200 MHz freq counter, IEEE **£650**
MARCONI 6500 amplitude analyser **£2000**
FARNELL PSU type AP10030 **£1000**
FARNELL PSU type AP7000 **£500**
B&K Accutronmeter type 4355 **£300**
TEKTRONIX probes PE1029, 100MHz readout, unused **£50**
TEKTRONIX probes PE106A 250MHz readout, unused **£25**

GOULD J38 Sine Square Oscillator 100kHz-100kHz. Low distortion **ONLY £95**

FLUKE MULTIMETERS Type 805A 4+1/2 digit, 2A True RMS **£100**
Type 801A 3+1/2 digit, 10A **£75**
Type 8012A 3+1/2 digit, 2A **£50**

FARNELL L302 Bench Power Supply 0-30 Volts, 0-2 Amps. Constant D.C. outputs/Constant current. **ONLY £80**

MANY OTHER POWER SUPPLIES AVAILABLE

SPECIALS - Limited Quantity

MARCONI 2022E Syn AM/FM SIG GEN, 10 KHz-1.01z Up to 100dBm output, phase mod. Led. display, keyboard entry, etc., small, lightweight **ONLY £525**

FLUKE SCOPEMETERS Models: 53-96/99, dual trace, 50MHz plus digital storage, etc. Unused from **£400 to £850**

POWER SUPPLY Model HSP3012, 0-30V, 0-12 Amps current limiting 2 meters. Used **£150** Unused **£200**

GOODWILL GYT67 DUAL CHANNEL A.C. MILLIVOLTMETER 10mV-30V in 11 ranges Frequency 10Hz-1MHz Used **£100** Unused **£125**

FARNELL LF1 Sine Sq Oscillator 10Hz-1MHz **ONLY £75**

LEVELL TC2000MP PIC Oscillator 1Hz-1MHz Sine Square, meter, battery operated (Batteries not supplied) **£50**

Solatron 7045 - 4.5 Dg Bench Multimeter with leads **£45**

Solatron 7150 DMM 6.5 digit True RMS IEEE **£225**

WAYNE KERR AMM255 Automatic Modulation Meter AM/FM 1-5MHz-20Hz 2.5 digit Unused **£500**

GOODWILL GFC 80102 FREQUENCY COUNTER, Range 1Hz-120MHz, 8-Digit Display, 15mV RMS Sensitivity. Unused **£75**

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS. RG6 1PL
Telephone: (0118) 9268041. Fax: (0118) 9351696
Callers welcome 9am-5.30pm Monday to Friday (other times by arrangement)

Used Equipment - GUARANTEED. Manuals supplied
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for lists. Please check availability before ordering.
CARRIAGE on units £15. VAT to be added to Total of Goods and Carriage

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3V-12V operation. 500m range. £16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter. Just 17mm x 17mm including mic. 3V-12V operation. 1000m range. £13.45

STX High-performance Room Transmitter

High performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm, including mic. 6V-12V operation, 1500m range. £15.45

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9V-12V operation. 3000m range. £16.45

VXT Voice-Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range. £19.45

HVX400 Mains Powered Room Transmitter

Connects directly to 240V A.C. supply for long-term monitoring. Size 30mm x 35mm. 500m range. £19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range. £22.95

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range. £23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9V-12V operation. £22.95

ATR2 Micro-Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line. £13.45

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 500m range. £15.95

TLX 700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range. £13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range. £16.45

TKX900 Signalling Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation. £22.95

CD400 Pocket Bug Detector/Locator

LED and piezo beeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation. £30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate beeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation. £50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range. £40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range. £40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m. £35.95

QRX 180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as pre-built and aligned module ready to connect on board so no difficulty setting up. Output to headphones. 60mm x 75mm. 9V operation. £60.95

★★★ Specials ★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output; momentary or alternate, 8-way d.I.L. switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits) £50.95

Individual Transmitter DLTX £19.95

Individual Receiver DLRX £37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great ideal. Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle.

Size 27mm x 60mm. 9V operation. 250m range. £20.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £2.00 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send Sterling Bank Draft and add £5.00 per order for shipment. Credit card orders welcomed on 01827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

**SUMA
DESIGNS**

DEPT. EE
THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY, NEAR ATHERSTONE,
WARWICKSHIRE CV9 2LE
VISITORS STRICTLY BY APPOINTMENT ONLY



**Tel/Fax:
01827 714476**

£9 BARGAIN PACKS

VIBRATING REED FREQUENCY METER, 55-65Hz. Order Ref: 9P8.
 BUMP 'N GO SPACESHIP KIT. Order Ref: 9P9.
 10 TDK AUDIO TAPES. Order Ref: 9P12.
 2-TONE HORN KIT. Order Ref: 9P15.
 TV REMOTE CONTROL, made by Philips, this will control almost every TV receiver or video. Order Ref: 9P20.

£10 BARGAIN PACKS

100A TIME SWITCH, ex-electricity board, reconditioned. Order Ref: 10P14.
 MAXIMUM DEMAND INDICATOR, 230V AC. Order Ref: 10P15.
 TANGENTIAL BLOWER FAN, 28in. long fan with motor in middle. Order Ref: 10P16.
 POWER STATION TYPE VOLTMETER in 6in. diameter metal case. Order Ref: 10P25.
 ALUMINIUM CASE, 19 1/2x12 1/2x8, very good condition. Order Ref: 10P40.
 POWERFUL WATER PUMP, operated by heavy duty mains motor. Order Ref: 10P76.
 DOUBLE BLOWER, mains operated, suit greenhouse or workshop. Order Ref: 10P84.
 FLUORESCENT CONVERTER by Philips for 3x9in. tubes. Order Ref: 10P89.
 COMPUTER DRIVER, MS-DOS 4.01. Order Ref: 10P99.
 MOTORISED DISPLAY, 12x10A micro mains switches, driven by mains motor. Order Ref: 10P101.
 CRT ref. SE5J31, 6in. Order Ref: 10P104.
 HOT WIRE PANEL METER, 6in. Order Ref: 10P106.
 DATA RECORDER, Sharp ref. IT400. Order Ref: 10P110.
 AMSTRAD MODEM SM2400, may need attention. Order Ref: 10P111.
 SOLENOID WATER VALVE, Danfoss, 12V DC or 24V AC. Order Ref: 10P118.
 POWER RELAY, 4x10A changeover contacts. Order Ref: 10P136.
 10A AMMETER for RF. Order Ref: 10P144.
 BENCH SOLDERING IRON on base, little storage soiled. Order Ref: 10P145.
 PRECISION VOLTAGE PANEL METER for exact reading between 100 and 125V AC. Order Ref: 10P146.
 SHARP DISK DRIVE M21F11. Order Ref: 10P147.
 FULLY ENCLOSED CROMPTON PARKINSON MAINS MOTOR, 1.6 h.p. 875 r.p.m. Order Ref: 10P149.
 12 COPPER CLAD BOARDS, various sizes from 6x3 to 12x12. Order Ref: 10P150.
 ALARM FOR HOUSE OR CAR, ultrasonic, neatly cased, ready-to-use when battery fitted. Order Ref: 10P155.

EVEN BIGGER BARGAINS

9in. MONITOR by Philips, new, made to work with OPD computer. £15. Order Ref: 15P1.
 METAL CASE for 9in. monitor, supplied as a flat pack, £12. Order Ref: 12P3.
 9in. TUBE by Philips, as used in our monitor, £12. Order Ref: 12P7.
 BIG AMPLIFIER BOX, 256x178x120mm. £12. Order Ref: 12P30.
 AMSTRAD 3in. DISK DRIVES, 2 with differing faults, should be possible to make one good one, £15. Order Ref: 15P46.
 ULTRASONIC ALARM for house or car, complete with external horn speaker and 12V power supply, £18. Order Ref: 18P3.
 100 ASSORTED COMPUTER GAMES, no more than 5 of any one type, ideal for remaking, £20. Order Ref: 20P12.
 MULLARD 14in. COLOUR TUBE, ref. AQ37590X. £15. Order Ref: 15P76.
 MAINS STEP DOWN TO 115V TRANSFORMER, this is 1000W as auto but has a separate winding to give 500W 115V isolated, £25. Order Ref: 25P18.
 3in. DISK DRIVE, £29. Order Ref: 29P6.
 SUPER 8 CINE PROJECTOR without sound. Order Ref: 39P1.
 SUPER 8 CINE PROJECTOR with sound, £49. Order Ref: 49P1.
 PSU CASE, size 255x115x210mm, black case with labeled silver front and fitted carrying handles. Smart kit reference 5096 or 5007, £12. Order Ref: 12P20.
 8in. FLUORESCENT TUBES, brand new, in maker's wrappings, box of 12, £12, but you must collect. Order Ref: 12P11.
 DIGITAL PANEL METER, comes complete with details of how to use it to display amps or volts, £11.50. Order Ref: 11P2.
 250m TWIN 5A EXTENSION LEAD, this is ideal for most gardening tools, rubber but treated so that it can't perish through sunlight, etc., £20. Order Ref: 20P35.
 EMERGENCY LIGHTING UNIT with perspex cover, contains rechargeable batteries and an inverter unit to power the internal fluorescent tube, regular price over £30, our price £15. Order Ref: 15P32.
 SOIL HEATER, 100W transformer and wire, £12. Order Ref: 12P33.
 SPEED CONTROLLER for 12V DC motors up to 1/6 h.p., kit of parts £12. Order Ref: 12P34, or made up £20, Order Ref: 20P39.
 SOLAR PANEL, 15V so will trickle charge car battery, £15. Order Ref: 15P72.
 CAMCORDER BATTERY CHARGER, suits most camcorders, £15. Order Ref: 15P73.

SPECIAL 12V RECHARGEABLE BATTERY. This is the Jap made Yuasa. It is sealed so can be used in any position. £3.50 each or 5 for £15. Order Ref: 3.5P11. The batteries have a capacity of 2.3AH which may be a bit low for some jobs but remember you can join them in parallel to give a high amperage.

RECHARGEABLE NICAAD AA BATTERIES. You can have these at a bargain price of 50p each, but you have to buy a pack of 10 which would give you a 12V rechargeable battery. However, it is quite easy to divide into 2 x 6V rechargeables or 10 x 1.2V rechargeables. Order Ref: 5P287. Made by Varta.

CHARGER FOR YUASA BATTERY. This battery charger plugs into a 13A socket, charges at approximately 1/4A so it would charge it at the correct rate. Complete with croc clips, ready to go, £5. Order Ref: 5P269.

FOR QUICK HOOK-UPS. You can't beat leads with a croc clip each end. You can have a set of 10 leads, 2 each of 5 assorted colours with insulated crocodile clips on each end. Lead length 35cm, £2 per set. Order Ref: 2P459.

BIG 12V TRANSFORMER. It is 55VA so over 4A. Beautifully made and well insulated. Live parts are in a plastic frame so cannot be accidentally touched, £3.50. Order Ref: 3.5P20.

TWIN 13A SWITCHED SOCKET. Good British make, white, quite standard size so suitable for flush mounting or in a surface box. £1.50. Order Ref: 1.5P51.

1mA PANEL METER. Approximately 80mm x 50mm, front engraved 0-100, price £1.50. Order Ref: 1/16R2.

BUY ONE GET ONE FREE

ULTRASONIC MOVEMENT DETECTOR. Nicely cased, free standing, has internal alarm which can be silenced. Also has connections for external speaker or light. Price £10. Order Ref: 10P154.

VERY POWERFUL BATTERY MOTOR. Intended to operate portable screwdriver. It is 2 1/2in. long and 1 1/2in. diameter. Has a good length spindle. Will operate with considerable power off any voltage between 6V and 12V d.c. Price £2. Order Ref: 2P456.

D.C. MOTOR WITH GEARBOX. Size 60mm long, 30mm diameter. Very powerful, operates off any d.c. voltage between 6V and 24V. Speed at 6V is 200 rpm but higher with higher voltages of course. Price £3. Order Ref: 3P108.

MOTOR SPEED CONTROLLER. For d.c. motors up to 24V and any power up to 1/6 h.p. They reduce by intermittent full voltage pulses so there should be no loss of power. In kit form £12. Order Ref: 12P34. Or made up and tested, £20. Order Ref: 20P39.

VERY THIN DRILLS. 12 assorted sizes vary between 0.6mm and 1.6mm, price £1. Order Ref: 12P128.
EVEN THINNER DRILLS. 12 that vary between 0.1 and 0.5mm, price £1. Order Ref: 12P129.

BT TELEPHONE EXTENSION WIRE. This is proper heavy-duty cable for running around the skirting board when you want to make a permanent extension. 4 cores properly colour coded, 25m length, only £1. Order Ref: 1067.

A MUCH LARGER PROJECT BOX. Size 216mm x 130mm x 65mm with lid and 4 screws. This is an ABS box which normally retails at around £6. All brand new, price £2.50. Order Ref: 2.5P28.

LARGE TYPE MICROSWITCH with 2in. lever, changeover contacts rated at 15A at 250V, 2 for £1. Order Ref: 1/21R7.

BALANCE ASSEMBLY KITS. Japanese made, when assembled ideal for chemical experiments, complete with tweezers and 6 weights 0.5 to 5 grams. Price £2. Order Ref: 2P444.

CYCLE LAMP BARGAIN. You can have 100 6V 0.5A MES bulbs for just £2.50 or 1,000 for £20. They are beautifully made, slightly larger than the standard 6.3V pilot bulb so they would be ideal for making displays for night lights and similar applications.

DOORBELL PSU. This has a.c. voltage output so is ideal for operating most doorbells. The unit is totally enclosed so perfectly safe and it plugs into a 13A socket. Price only £1. Order Ref: 1/30R1.

FLASHING BEACON. Ideal for putting on a van, a tractor or any vehicle that should always be seen. Uses a Xenon tube and has an amber colour dome. Separate fixing base is included so unit can be put away if desired. Price £5. Order Ref: 5P267.

MOST USEFUL POWER SUPPLY. Rated at 9V 1A, this plugs into a 13A socket. Is really nicely boxed, £2. Order Ref: 2P733.

1.5-6V MOTOR WITH GEARBOX. Motor is mounted on the gearbox which has interchangeable gears giving a range of speeds and motor torques. Comes with full instructions for changing gears and calculating speeds. £7. Order Ref: 7P26.



EVEN BIGGER BARGAINS

200W WOOFER by Challenger, 8in., 4 ohm, £18. Order Ref: 18P9.

250W WOOFER by Challenger, this is 10in., £29. Order Ref: 29P7.

365-DAY TIME SWITCH, has two 16A channels, £35. Order Ref: 35P7.

FIELD TELEPHONE, ex-GPO, just needs a pair of wires to join together, £16 each. Order Ref: 16P8.

1,000 CYCLE LAMP BULBS, 6V 0.5A, £20. Order Ref: 20P38.

SOUND SWITCH, can be operated by clapping hands, shouting or almost any other noise. Comes complete with instructions, assembled and ready to work, but needs casing. Price only £3. Order Ref: 3P46.

LIGHT ALARM, could be used to warn when a cupboard door is opened, light shining on the unit makes the bell ring, completely built and neatly cased, requires only a battery, £3. Order Ref: 3P155.

WATER LEVEL ALARM, be it bath, sink, cellar, sump or any other thing that could flood, this device will tell you when the water has risen to the preset level, adjustable over quite a useful range. Really cased for wall mounting, ready to work when battery fitted, £3. Order Ref: 3P156.

BIKE RADIO, in fact, it's more than a radio, it's an alarm and a spotlight, the radio is battery operated, of course, and needs 3 AA cells, only one band but this is the FM band so will receive Radio 1 and 2, comes complete with handlebar fixing clips, price £4. Order Ref: 4P72.

ULTRA VIOLET-VIEWING UNIT, this is a very neat metal enclosure about the size of a 6in. cube, the lamp and control gear are in the top compartment and an open space with a platform below allows you to inspect paper or other objects under the UV light, intended for 230V mains operation, price £12. Order Ref: 12P35.

4-SOCKET MAINS ADAPTOR, we would say that this is ideal for the handyman, but no doubt many of you will say it's also for the handywoman! Will take up to a load of 13A and 4 units can be used at one time, has a neon indicator to show the power is on, price £4. Order Ref: 4P102.

MODERN TELEPHONE HANDSET, ideal home or office extension, £2. Order Ref: 2P84.

CASED POWER SUPPLY FOR MODELS, mains operated, gives variable voltage from 6V to 12V and reversible, ideal model trains, etc., £12. Order Ref: 2P3.

INSULATION TESTED WITH MULTIMETER, internally generates voltages which enable you to read insulation directly in megohms, the multimeter has four ranges, A.C./D.C. volts, 3 ranges DC milliamps, 3 ranges resistance and 5 amp range, these instruments are ex-British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50 with leads, carrying case £2 extra. Order Ref: 7.5P4.

REPAIRABLE METERS, we have some of the above testers but slightly faulty, not working on all ranges, should be repairable, we supply diagram, £3. Order Ref: 3P176.

SUPERIOR 12V PSU. This is special in that the output is regulated 12V DC at 600mA. It is in a normal type plastic container with prongs to go into a 13A socket, has an indicator on/off light. Price £22.50. Order Ref: 22.5P25.

SOLAR EDUCATIONAL KIT, a kit comprising 400mA solar module, sun power DC motor, connecting lead, fan impeller and selection of turnable discs. Supplied complete with booklet explaining the principles and applications of solar energy. This kit is an ideal educational introduction to solar power, price £5. Order Ref: 5P160.

EQUIPMENT COOLING BLOWER, near enough 5in. square and 1 1/2in. thick, but a really good mover, mains operated, price £4. Order Ref: 715L.

SOLDERING IRON, super mains powered with long-life ceramic element, heavy duty 40W for the extra special job, complete with plated wire stand and 245mm lead, £3. Order Ref: 3P221.

SOLAR POWERED NICAAD CHARGER, 4 Nicad batteries AA (HP7) in about 10 hours or 2 in only 4 hours, 1 in about 2 hours. It is a complete boxed unit which you can easily carry about, price £6. Order Ref: 6P3.

MINI BLOW HEATER, 1kW, ideal for under desk or airing cupboard, etc., needs only a simple mounting frame, price £5. Order Ref: 5P23.


TERMS

Send cash, PO, cheque or quote credit card number - orders under £25 add £3.50 service charge.

J & N FACTORS

Pilgrim Works (Dept. E.E.)
 Stairbridge Lane, Bolney,
 Sussex RH17 5PA


Telephone: 01444 881965

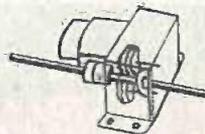

Transform your PC... Into an oscilloscope, spectrum analyser and multimeter...

The ADC-200 range of PC based oscilloscopes offer performance only previously available on the most expensive 'benchtop' scopes. By integrating several instruments into one unit, the ADC-200 is both flexible and cost effective.

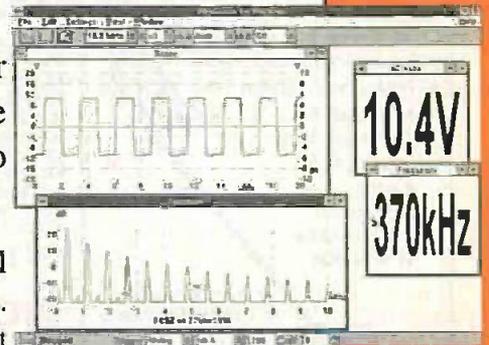Connection to a PC gives the ADC-200 the edge over traditional oscilloscopes: the ability to print and save waveforms is just one example. Units are supplied with PicoScope for Windows which is powerful, yet simple to use, with comprehensive on line help.



Applications

- ▼ Video
- ▼ Automotive
- ▼ Electronics design
- ▼ Production line tests
- ▼ Fault finding
- ▼ Education

All units are supplied with software, cables and power supply. Prices exclude VAT.

Features


- ▼ A fraction of the cost of comparable benchtop oscilloscopes
- ▼ Up to 100 MS/s sampling
- ▼ Advanced trigger modes- capture one off events.
- ▼ Up to 50 MHz spectrum analyser
- ▼ Large buffer memory

<i>ADC-200/100</i>	£499
<i>ADC-200/50</i>	£399
<i>ADC-200/20</i>	£299



A scope at your fingertips.....

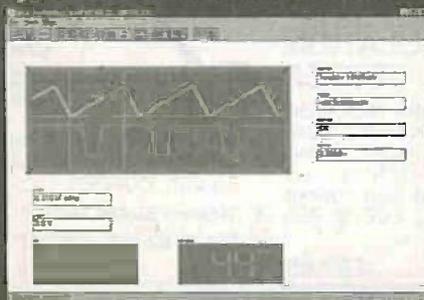Once oscilloscopes were heavy and clumsy to handle, but over the years they have become smaller and smaller. The latest development in this field has just arrived: a digital storage oscilloscope in a handy slim housing, scarcely longer than a pencil and about as thick as your thumb. Despite its small size, its performance can match that of a service oscilloscope.



ONLY £80



Applications

- ▼ On-the-spot measurements
- ▼ Hobby electronics
- ▼ Measurements in amplifiers
- ▼ Production line tests

- ▼ Can use PC display
- ▼ Sample rates from 50ns to 1ms
- ▼ Up to 20 MS/s

Prices exclude VAT

Call for a **FREE** software demonstration disk or visit our web site

Fax: +44 (0)1954 211880 Tel: +44 (0)1954 211716

E-mail: post@picotech.co.uk Web: www.picotech.com

PICO
Technology Limited



MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with I.C. control of all timing functions and advanced pulse separation techniques.

- New circuit design 1994
- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater



- Detects gold, silver, ferrous & non-ferrous metals

- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware

KIT 847.....£63.95

PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

SUPER ACOUSTIC PROBE

Our very popular project - with probe components and diecast box. Picks up vibrations amplifies, and drives headphones. Sounds from engines, watches, and speech through walls can be heard clearly. Useful for mechanics, instrument engineers and nosy parkers! A very useful piece of kit.

KIT 865.....£29.95

DC Motor/Gearboxes

Our Popular and Versatile DC motor/Gearbox sets. Ideal for Models, Robots, Buggies etc. 1-5 to 4-5V Multi ratio gearbox gives wide range of speeds.



LARGE TYPE - MGL £6.95
 SMALL - MGS - £4.77

Stepping Motors

MD38...Mini 48 step...£8.65
 MD35...Std 48 step...£9.99
 MD200...200 step...£12.99
 MD24...Large 200 step...£22.95



PIC PIPE DESCALER

- SIMPLE TO BUILD
- HIGH POWER OUTPUT
- AUDIO & VISUAL MONITORING
- SWEPT FREQUENCY

An affordable circuit which sweeps the incoming water supply with variable frequency electromagnetic signals. May reduce scale formation, dissolve existing scale and improve lathering ability by altering the way salts in the water behave. Kit includes case, PCB, coupling coil and all components. High coil current ensures maximum effect. L.E.D. monitor



KIT 868£22.95 POWER UNIT.....£3.99

MICRO PEST SCARER

Our latest design - The ultimate scarer for the garden. Uses special microchip to give random delay and pulse time. Easy to build reliable circuit. Keeps pets/pests away from newly sown areas, play areas, etc. Uses power source from 9 to 24 volts.



- RANDOM PULSES
- HIGH POWER
- DUAL OPTION

Plug-in power supply £4.99

KIT 867.....£19.99

KIT + SLAVE UNIT.....£32.50

WINDICATOR

A novel wind speed indicator with LED readout. Kit comes complete with sensor cups, and weatherproof sensing head. Mains power unit £5.99 extra.

KIT 856.....£28.00

★ TENS UNIT ★

DUAL OUTPUT TENS UNIT

As featured in March '97 issue.

Magenta have prepared a FULL KIT for this excellent new project. All components, PCB, hardware and electrodes are included. Designed for simple assembly and testing and providing high level dual output drive.

Set of 4 spare electrodes £6.50

KIT 866.... Full kit including four electrodes £32.90

1000V & 500V INSULATION TESTER



Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms. Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95

MOSFET MkII VARIABLE BENCH POWER SUPPLY 0-25V 2-5A.

Based on our Mk1 design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.



Kit No. 845.....£64.95

EPE PROJECT PICs

NOW £5.90

Programmed PICs for all EPE Projects
 Now one price
£5.90 each

(*some projects are copyright)

ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS



- UP TO 4 METRES RANGE
- LOW CURRENT DRAIN

KIT 812.....£14.81

SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube plus instructions for message loading.

KIT 849.....£16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMs at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£28.51

SUPER BAT DETECTOR



1 WATT O/P, BUILT IN SPEAKER, COMPACT CASE
 20kHz-140kHz

NEW DESIGN WITH 40kHz MIC.

A new circuit using a 'full bridge' audio amplifier i.c., internal speaker, and headphone/tape socket. The latest sensitive transducer, and 'double balanced mixer' give a stable, high performance superheterodyne design.



KIT 861.....£24.99

ALSO AVAILABLE Built & Tested£39.99

E.E. TREASURE HUNTER P.I. METAL DETECTOR MKI

Magenta's highly developed & acclaimed design. Quartz crystal controlled circuit MOSFET coil drive. D.C. coupled amplification. Full kit includes PCB, handle, case & search coil.

- KIT INC. HEADPHONES
- EFFICIENT CMOS DESIGN
- POWERFUL COIL DRIVE

- DETECTS FERROUS AND NON-FERROUS METAL - GOLD, SILVER, COPPER ETC.
- 190mm SEARCH COIL
- NO 'GROUND EFFECT'

KIT 815.....£45.95



SIMPLE PIC PROGRAMMER

INCREDIBLE LOW
PRICE!

Kit 857 **£12.99**

INCLUDES 1-PIC16F84 CHIP
SOFTWARE DISK, LEAD
CONNECTOR, PROFESSIONAL
PC BOARD & INSTRUCTIONS

Power Supply £3.99

EXTRA CHIPS:
PIC 16F84 £4.84

Based on the design in February '96 EPE article, Magenta have made a proper PCB and kit for this project. PCB has 'reset' switch, Program switch, 5V regulator and test L.E.D.s. There are also extra connection points for access to all A and B port pins.

PIC16C84 LCD DISPLAY DRIVER

INCLUDES 1-PIC16F84
WITH DEMO PROGRAM
SOFTWARE DISK, PCB,
INSTRUCTIONS AND
24-CHARACTER 2-LINE
LCD DISPLAY

Kit 860 **£19.99**

Power Supply £3.99

FULL PROGRAM SOURCE
CODE SUPPLIED—DEVELOP
YOUR OWN APPLICATION!

Another super PIC project from Magenta. Supplied with PCB, industry standard 2-LINE x 16-character display, data, all components, and software to include in your own programs. Ideal development base for meters, terminals, calculators, counters, timers—Just waiting for your application!

★ Chip is pre-programmed with demo display ★

PIC16C84 MAINS POWER 4-CHANNEL CONTROLLER & LIGHT CHASER

- WITH PROGRAMMED 16F84 AND DISK WITH SOURCE CODE IN MPASM
- ZERO VOLT SWITCHING – 10 CHASE PATTERNS
- OPTO ISOLATED
- 4 X 3 KEYPAD CONTROL
- SPEED CONTROL POT.
- HARD FIRED TRIACS
- 4 CHANNELS @5 AMPS

Now features full 4-channel chaser software on DISK and pre-programmed PIC16F84 chip. Easily re-programmed for your own applications. Software source code is fully 'commented' so that it can be followed easily.

Kit 855 **£39.95**

LOTS OF OTHER APPLICATIONS

PhizzyB

ALL PARTS FOR SERIES INCLUDING PCBs, PROGRAMMED CHIP, CD-ROM AND DISPLAYS

MAIN BOARD – FULL KIT ... **£131.95** BUILT ... **£149.95**

I/O PORTKIT **£16.99** BUILT **£24.99**

L.C.D. **£12.49** POWER SUPPLY **£3.99**

8-BIT SWITCH/LATCH **£7.95** INT. MODULE **£10.45**

68000 DEVELOPMENT AND TRAINING KIT

KIT 621
£99.95

8 MHz 68000 16-BIT BUS
MANUAL AND SOFTWARE
2 SERIAL PORTS, PIT,
AND I/O PORTS



PSU £6.99
SERIAL LEAD £3.99

Mini-Lab & Micro Lab Electronics Teach-In 7

As featured in EPE and now published as Teach-In 7. All parts are supplied by Magenta. Teach-In 7 is £3.95 from us or EPE

Full Mini Lab Kit – £119.95 –
Power supply extra – £22.55
Full Micro Lab Kit – £155.95
Built Micro Lab – £189.95



EPE PIC Tutorial

NEW!

At Last! A Real, Practical, Hands-On Series
3-Part Series – Starting March '98

- Learn Programming from scratch
- Uses Re-Programmable PIC16F84 Chip
- Start by lighting an l.e.d. and work up through over 30 tutorials to Sound Generation, Data Display, and a Security System
- PIC TUTOR Board has Input Switches, Output l.e.d.s, and on board programmer

PIC TUTOR BOARD KIT

Includes: PIC16F84 Chip, TOP Quality PCB printed with Component Layout and all components* (*not ZIF Socket or Displays). Included with the Magenta Kit is a disk with Test and Demonstration routines.

KIT 870 **£27.95, Built & Tested £42.95**

Optional: Power Supply – **£3.99**, ZIF Socket – **£9.99**

LCD Display – With Software and Connection details **£7.99**

LED Display – Including Software..... **£6.99**

PIC TOOLKIT

- PROGRAMS PIC16C84 and 16F84
- ACCEPTS TASM AND MPASM CODE

Full kit includes PIC16F84 chip, top quality p.c.b. printed with component layout, turned pin PIC socket, all components and software* *Needs QBASIC or QUICKBASIC

KIT 871 . . . **£13.99. Built and tested £21.99**

SUPER PIC PROGRAMMER

- READS, PROGRAMS, AND VERIFIES
- WINDOWS™ SOFTWARE
- PIC16C6X, 7X, AND 8X
- USES ANY PC PARALLEL PORT
- USES STANDARD MICROCHIP • HEX FILES
- OPTIONAL DISASSEMBLER SOFTWARE (EXTRA)
- PCB, LEAD, ALL COMPONENTS, TURNED PIN SOCKETS FOR 18, 28, AND 40 PIN ICs.

- SEND FOR DETAILED INFORMATION – A SUPERB PRODUCT AT AN UNBEATABLE LOW PRICE.

Kit 862 **£29.99**

Power Supply £3.99

DISASSEMBLER
SOFTWARE **£11.75**

PIC STEPPING MOTOR DRIVER

INCLUDES: PCB,
PIC16F84 WITH
DEMO PROGRAM,
SOFTWARE DISK,
INSTRUCTIONS
AND MOTOR.

Kit 863 **£18.99**

FULL SOURCE CODE SUPPLIED.
ALSO USE FOR DRIVING OTHER
POWER DEVICES e.g. SOLENOIDS.

Another NEW Magenta PIC project. Drives any 4-phase unipolar motor – up to 24V and 1A. Kit includes all components and 48 step motor. Chip is pre-programmed with demo software, then write your own, and re-program the same chip! Circuit accepts inputs from switches etc and drives motor in response. Also runs standard demo sequence from memory.

MAGENTA

All prices include VAT. Add £3.00 p&p. Next Day £6.99

Tel: 01283 565435 Fax: 01283 546932 E-mail: sales@magenta2000.co.uk



Station Road, Cullercoats, Tyne & Wear, NE30 4PQ

All Major Credit cards Accepted... Prices Exclude Vat @17.5%. Add £1.25 carriage & Vat to all orders.

See Next / Last Months Ad. for COMPONENT ACCESSORIES

DIL Sockets

- Stamped Pin 8 Pin DIL 0.3... 14 Pin DIL 0.3... 18 Pin DIL 0.3... 20 Pin DIL 0.3... 24 Pin DIL 0.6... 28 Pin DIL 0.6... 40 Pin DIL 0.6... 48 Pin DIL 0.3... 14 Pin DIL 0.3... 16 Pin DIL 0.3... 18 Pin DIL 0.3... 20 Pin DIL 0.3... 24 Pin DIL 0.6... 28 Pin DIL 0.6... 40 Pin DIL 0.6... 48 Pin DIL 0.3... 14 Pin DIL 0.3... 16 Pin DIL 0.3... 18 Pin DIL 0.3... 20 Pin DIL 0.3... 24 Pin DIL 0.6... 28 Pin DIL 0.6... 40 Pin DIL 0.6... 48 Pin DIL 0.3...

0.1" Pin Header Strip

- 1 x 36 Way Straight £0.38 1 x 36 Way Straight £0.56 1 x 36 Way 90° £0.54 2 x 36 Way 90° £0.80 Available in 2, 3, 4, 5 & 10 ways. Also female PCB sockets & jumper links. 20 Way Socket Strip £0.48

Transistor Sockets

- T016-4 Base Socket £0.24 T05 Base Socket £0.24

IDC Cable Sockets

- 10 Way Socket £0.25 14 Way Socket £0.35 16 Way Socket £0.37 20 Way Socket £0.37 26 Way Socket £0.38 34 Way Socket £0.39 40 Way Socket £0.55 50 Way Socket £0.60

PCB Box Headers

- 10 Way Straight £0.27 14 Way Straight £0.36 16 Way Straight £0.36 20 Way Straight £0.32 26 Way Straight £0.37 34 Way Straight £0.37 40 Way Straight £0.63 50 Way Straight £0.96 10 Way 90° £0.33 16 Way 90° £0.42 20 Way 90° £0.53 26 Way 90° £0.70 34 Way 90° £0.81 40 Way 90° £0.83 50 Way 90° £0.95

PCB Latch Headers

- 10 Way Straight £0.50 16 Way Straight £0.70 20 Way Straight £0.78 26 Way Straight £0.81 34 Way Straight £0.86 40 Way Straight £1.29 50 Way Straight £1.29 10 Way 90° £0.58 16 Way 90° £0.78 20 Way 90° £0.82 26 Way 90° £1.06 34 Way 90° £1.14 40 Way 90° £1.26 50 Way 90° £1.74

DIL Headers

- 14 Way DIL £0.54 16 Way DIL £0.59 24 Way DIL £0.90 40 Way DIL £1.02

Transistor Headers

- 10 Way Transistor £0.49 14 Way Transistor £0.47 16 Way Transistor £0.47 20 Way Transistor £0.54 26 Way Transistor £0.62 34 Way Transistor £0.67 40 Way Transistor £0.90 50 Way Transistor £1.02

D Type Connectors

- Solder Bucket 9 Way Male Plug £0.26 9 Way Female Socket £0.27 15 Way Male Plug £0.34 15 Way Female Socket £0.39 15 Way H.D. Plug £0.47 15 Way H.D. Socket £0.78 23 Way Male Plug £0.49 23 Way Female Socket £0.49 25 Way Male Plug £0.36 25 Way Female Skt £0.39

IDC Ribbon Mounting

- 9 Way Male Plug £1.08 9 Way Female Socket £1.08 25 Way Male Plug £1.18 25 Way Female Socket £1.13

Right Angled PCB

- 9 Way Male Plug £0.37 9 Way Female Socket £0.35 15 Way H.D. Socket £0.77 25 Way Male Plug £0.53 25 Way Female Socket £0.51

Plastic D Covers

- 9 Way Cover - Grey £0.30 9 Way Cover - Black £0.30 15 Way Cover - Grey £0.33 25 Way Cover - Grey £0.36 25 Way Cover - Grey £0.34 25 Way Cover - Black £0.37 9 to 9 Cover / Case £0.96 25 to 25 Cover / Case £0.84 9 to 25 Cover / Case £0.94

Audio Connectors

- 2.5mm Jack Plug £0.21 2.5mm Line Socket £0.14 2.5mm Chassis Socket £0.20 3.5mm Mono Plug £0.30 3.5mm Mono Line Skt £0.14 3.5mm Stereo Plug £0.36 3.5mm Stereo Line Skt £0.37 3.5mm Stereo Chassis Skt £0.34 Mono Plug £0.34 Mono Line Socket £0.35 Mono Chassis Skt £0.35 Mono Plug £0.40 Mono Line Socket £0.38 Mono Chassis Skt £0.40 Stereo Spakon Plug £2.81

DIN Series

- 2 Pin Line Plug £0.19 2 Pin Chassis Socket £0.15 3 Pin Line Plug £0.27 3 Pin Chassis Socket £0.28 4 Pin Line Plug £0.24 4 Pin Chassis Socket £0.26 5 Pin Line Plug £0.30 5 Pin Chassis Skt £0.30 5 Pin Line Plug 240° £0.24 5 Pin Chassis Skt 240° £0.32 5 Pin Line Plug 360° £0.24 5 Pin Chassis Skt 360° £0.32 6 Pin Line Plug £0.34 6 Pin Chassis Socket £0.35 7 Pin Line Plug £0.37 8 Pin Line Plug £0.44 8 Pin Chassis Socket £0.36

Phono Series

- Red Line Plug £0.20 Black Line Plug £0.20 White Line Plug £0.20 Red Line Socket £0.20 Black Line Socket £0.20 Yellow Line Socket £0.20 White Line Socket £0.20 Red Chassis Socket £0.20 Black Chassis Socket £0.20 Gold Plated Plug Red £0.66 Gold Plated Plug Black £0.66

XLR Series - metal

- 3 Pin Line Plug £1.26 3 Pin Line Socket £1.71 3 Pin Chassis Plug £1.50 3 Pin Chassis Socket £1.49 Neutrik Line Plug £1.68 Neutrik Line Socket £1.99 Neutrik Chassis Plug £2.13 Neutrik Chassis Socket £2.37

RF Connectors

- BNC Plug 50Ω Solder £0.99 BNC Plug 50Ω Crimp £0.68 BNC Plug 75Ω Solder £0.95 BNC Plug 75Ω Crimp £0.68 BNC Chassis Socket £0.81 F Plug - Twist £0.24 F Plug - Crimp £0.26 TNC Plug 50Ω Solder £1.24 TNC Plug 50Ω Crimp £0.85 TNC Plug 75Ω Solder £1.40 TNC Plug 75Ω Crimp £1.16 UHF Plug 5mm Cable £0.63 UHF Plug 9.1mm Cable £0.73 UHF Chassis Skt - Sqr £0.50 UHF Chassis Skt - Rnd £0.70

Terminals

- Colours Red, Black, Green, Blue, White or Yellow 2mm Solder Plugs £0.18 2mm Chassis Sockets £0.26 4mm Solder Plugs £0.35 4mm Stackable Plugs £0.40 4mm Chassis Sockets £0.23 4mm Binding Posts £0.63 33mm Crocodile Clips £0.13

Power Connectors

- DC Low Voltage DC Plug 0.7ID 2.35OD £0.47 DC Plug 1.3ID 3.4OD £0.32 DC Plug 1.7ID 4.0OD £0.47 DC Plug 1.7ID 4.75OD £0.47 DC Plug 2.1ID 5.0OD £0.25 DC Plug 2.5ID 5.0OD £0.24 DC Plug 3.1ID 6.3OD £0.46 DC Line Socket 2.1mm £0.57 DC Chassis Skt 2.1mm £0.40 DC Chassis Skt 2.5mm £0.41

IEC Mains 6A 250Vac

- 3 Pin IEC Line Socket £1.08 3 Pin IEC Line Plug £1.78 3 Pin Chassis Socket £0.55 3 Pin Chassis Plug £0.72

8 Way Bulgin

- 8 Pin Line Plug P551 £4.09 8 Pin Chassis Skt P552 £1.39

Toggle Switches

- Sub-Miniature 3A 125V 1A 250V 3mm Ø Mounting Hole SPST 3 x 10mm £0.58 SPST 3 x 18mm £0.60 SPDT c/o 5 x 10mm £0.80 SPDT c/o 5 x 10mm £0.80 DPDT 9.2 x 10mm £0.66

Miniature

- 3A 125V 3A 250V 6.2mm Ø Mounting Hole SPST 8 x 13mm £0.65 SPDT 8 x 13mm £0.60 SPDT c/o 8 x 13mm £0.60 SPDT c/o Biased 2 way £0.97 SPDT c/o Biased 1 way £1.04 DPDT 12 x 13mm £0.72 DPDT c/o 12 x 13mm £0.80 DPDT c/o Biased 2 way £1.28 DPDT c/o Biased 1 way £1.28

Standard

- 10A 250V Push on terminals 12mm Ø Mounting Hole SPST 18 x 30mm £1.28 SPDT 18 x 30mm £1.30 SPDT c/o 18 x 30mm £1.43 DPDT 21 x 32mm £1.25 DPDT c/o 21 x 30mm £1.68

Slide Switches

- Miniature 300mA 125V 7 x 15mm Mounting Hole DPDT 7 x 23mm £0.20

Standard

- 1A 125V 5.5 x 12mm Mounting Hole DPDT 12 x 35mm £0.25 DPDT c/o 12 x 35mm £0.27

Rotary Switches

- 150mA 250V Make before Break 22mm Ø 1 Pole 12 Way £0.84 2 Pole 4 Way £0.84 3 Pole 4 Way £0.84 4 Pole 3 Way £0.84

Push Switches

- Miniature Round 230mV 125V 28 x 10mm 7.0mm Ø Mounting Hole Non Latching Push to Make Black PTM £0.23 Red PTM £0.23 Yellow PTM £0.23 Green PTM £0.23 Blue PTM £0.23 White PTM £0.23 Non Latching Push to Break Black PTB £0.24

Standard Square

- 1A 250V 39 x 15MM 12mm Ø Mounting Hole Non Latching Push to Make Black PTM £0.60 Red PTM £0.60 White PTM £0.60 Latching - push On push Off Black £0.65 Red £0.65 Blue £0.65 White £0.65

Rocker Switches

- Miniature 6A 250V Solder Tags SPST 21 x 14 x 16mm £0.69 DPDT 21 x 24 x 22mm £0.96 SPST - Red Neon £1.02 SPST - Green Neon £1.02 SPST - Amber Neon £1.02

Standard

- 15A 250V Push on Tags SPST 30 x 11 x 22mm £0.58 DPDT 30 x 25 x 22mm £1.12 Illuminated 15A 250V Push on Tags SPST 30x14mm Red £0.84 SPST 30x25mm Red £1.40 DPST 30x25mm Amber £1.40 DPST 30x25mm Green £1.40

Relays

- PCB Mounting 1A 24Vdc DPDT 5V £1.28 1A 24Vdc DPDT 12V £2.00 3A 110V SPDT 6V £0.58 3A 110V SPDT 12V £0.58 5A 110V SPDT 6V £0.72 5A 110V SPDT 12V £0.72 5A 110V DPDT 6V £0.93 5A 110V DPDT 12V £0.93 5A 240V DPDT 6V £1.76 5A 240V SPDT 12V £1.25 10A 240V SPDT 6V £1.44 10A 240V SPDT 24V £1.44

Computer Accessories Adaptors

- 9M Gender Changer £2.18 9F Gender Changer £2.29 25M Gender Changer £2.60 25F Gender Changer £2.80 9 Male - 25 Female £1.90 9 Male - 25 Male £1.90 9F - 4 Mini Din Female £2.40 5M Din - 6F Mini Din £2.08 5F Din - 6M Mini Din £2.08

Testers / Patch Boxes

- Mini Tester 7 LEDs £4.72 Check Tester 18 LEDs £6.32 Enhanced + Switches £15.25 13 Jumper Box M.F. £2.90 25D Patch Box M.F. £2.78 Anti-Static Wrist Strap £4.76 RS232 Surge Protector £5.43 Mains Surge Protector £11.99 4 Gang Surge Block £15.50

Leads & Cables

- 1.5m Printer Lead £3.40 5m Printer Lead £9.38 10m Printer Lead £8.75 Serial Printer 25M-9F £4.50 Serial Printer 25M-25F £4.45 Null Modem Leads 9 Female - 9 Female £3.16 25 Female - 25 Female £4.63 9 Female - 25 Female £5.16 9F25F to 9F25F £5.52 Modem Leads 25Male to 9Female £4.08 25Male to 25Female £4.75 PC Link Leads Interlink 25M to 25M £4.38 Patch Lead 25Male to 25Male £4.50 25Male to 25Male £2.60 Internal Leads Floppy Cable A/B £3.00 Hard Disk 2xIDE £1.65 Power 3W-2 x 3W £1.88 Power 5W-2 x 3W £1.50 Power 5W-2 x 3W £2.24 Power 5W-3W, 5W £2.24

Networking

- BNC T Piece MIF £1.71 BNC T Piece FFF £2.40 BNC Coupler F £0.95 BNC Coupler M £1.65 BNC Batches Crimper £17.44 50Ω BNC Terminator £1.24 Thinner Cable per m £0.39

Boxes & Cases

- Many more sizes available General Purpose Plastic 75 x 56 x 25mm £0.99 75 x 51 x 22mm £0.99 111 x 57 x 22mm £1.10 79 x 61 x 40mm £1.12 100 x 76 x 41mm £1.79 118 x 98 x 45mm £2.08 150 x 100 x 60mm £2.77 50 x 80 x 50mm £2.72

Diecast Aluminium

- 50 x 50 x 31mm £2.57 100 x 50 x 25mm £2.98 112 x 62 x 31mm £3.55 120 x 65 x 40mm £3.05 150 x 80 x 50mm £5.36 121 x 95 x 61mm £5.99

Two Piece Aluminium

- 133 x 70 x 37mm £2.08 102 x 102 x 37mm £1.94 102 x 70 x 37mm £1.98 102 x 63 x 50mm £1.34 76 x 51 x 25mm £1.39 152 x 102 x 58mm £2.82 178 x 127 x 63mm £3.64 203 x 152 x 76mm £4.84 102 x 102 x 63mm £2.15 133 x 102 x 63mm £2.57 152 x 102 x 76mm £3.23

Steel/Aluminium

- Plastic coated steel top, Aluminium base 152 x 114 x 44mm £3.04 203 x 127 x 51mm £3.80 229 x 127 x 63mm £3.04 114 x 63 x 57mm £3.04

Wire & Cable

- Ribbon Cable Price per 300mm (1ft) 10 Way Grey Ribbon £0.11 16 Way Grey Ribbon £0.17 20 Way Grey Ribbon £0.24 25 Way Grey Ribbon £0.28 34 Way Grey Ribbon £0.38 40 Way Grey Ribbon £0.48 50 Way Grey Ribbon £0.53 60 Way Grey Ribbon £0.64

Enamelled Copper Wire

- Per 50g (2oz) Reel 500g reels available 14 SWG Enamelled £0.97 16 SWG Enamelled £0.97 18 SWG Enamelled £0.97 20 SWG Enamelled £0.97 22 SWG Enamelled £1.12 24 SWG Enamelled £1.14 26 SWG Enamelled £1.22 28 SWG Enamelled £1.24 30 SWG Enamelled £1.25 32 SWG Enamelled £1.27 34 SWG Enamelled £1.29 36 SWG Enamelled £1.31 40 SWG Enamelled £1.35 48 SWG Enamelled £1.64

Tinned Copper Wire

- Per 50g (2oz) Reel 500g reels available 14 SWG Tinned £0.97 16 SWG Tinned £0.97 18 SWG Tinned £0.97 20 SWG Tinned £1.01 22 SWG Tinned £1.01 24 SWG Tinned £1.03 26 SWG Tinned £1.03 28 SWG Tinned £1.03 30 SWG Tinned £1.03

Equipment Wire

- Colours Black, Brown, Red, Orange, Yellow, Green, Blue, Purple, Grey & White Per 100m Reel/Sold 1/0.6mm £2.72 Stranded 7/0.2mm £2.53

Opto Electronics

- LEDs 3mm Red Led £0.08 3mm Green Led £0.09 3mm Yellow Led £0.10 3mm Orange Led £0.10 5mm Red Led £0.08 5mm Green Led £0.08 5mm Yellow Led £0.08 5mm Orange Led £0.10 5mm Red Flashing £0.44 5mm Green Flashing £0.50 5mm Yellow Flashing £0.54 5mm Br-Colour Led £0.33 5mm Tri-Colour Led £0.28

7 Segment Displays

- 0.51" Red Cathode £0.78 0.51" Red Cathode £0.78 0.51" Red Cathode £0.78

Infra Red Devices

- 3mm IR Emitter £0.23 5mm IR Emitter £0.39 3mm Photo-Transistor £0.76 3mm Photo-Transistor £0.64 4N25 Opto-Coupler £0.36 4N26 Opto-Coupler £0.36 4N29 Opto-Coupler £0.45 6N135 Opto-Coupler £1.30 6N136 Opto-Coupler £0.85 6N137 Opto-Coupler £0.90 6N138 Opto-Coupler £1.30 6N139 Opto-Coupler £0.90 CNY17-1 O. Coupler £0.47 CNY17-2 O. Coupler £0.47 IS-74 Opto-Coupler £0.45 ISD-74 Opto-Coupler £0.96 MOC3020 Opto-Triac £0.52 MOC3041 Opto-Triac £0.96 ORP12 LDR £0.89

Solar Coils

- 0.45V Screw Terminals £0.85 100mA 25 x 46mm £1.19 250mA 25 x 56mm £1.19 400mA 45 x 75mm £1.70 800mA 66 x 95mm £2.96 1000mA 75 x 95mm £3.52

Crystals

- DT-38 5 Small Can £0.42 1.8432MHz £1.49 2.04MHz £1.49 2.4576MHz £1.24 3.2768MHz £0.96 3.579545MHz £0.81 3.6864MHz £0.81 4.0MHz £0.81 4.194304MHz £0.81 4.433619MHz £0.81 4.9152MHz £0.81 6.0MHz £0.81 6.144MHz £0.81 7.3728MHz £0.81 8.0MHz £0.81 8.67238MHz £0.81 10.0MHz £0.66 11.0MHz £0.81 11.0592MHz £0.81 12.0MHz £0.83 14.2456MHz £0.83 16.0MHz £0.83 20.0MHz £0.90

Everday Practical Electronics Projects

- Discounted Component Kits Now Available Full details on our Web site http://www.esr.co.uk Pulsed Peizo Sounder High output peizo sounder with flying leads, built in driver & pulsed circuit. 3-20Vdc, 18mA, 65dB (Min 9Vdc), 42mmØ. £0.85 on £0.79 (25+) Normal Price £1.60

DM830 Digital Multimeter

- A sturdy well designed 3 1/2 digit LCD multimeter ideal for hobby or professional use. Covering five functions with 18 ranges including 10Aac Current - DC Volts, AC Volts, DC Current, Resistance, Diode Test and a simple function generator output. Supplied complete with battery, test leads, operating instructions. CE Approved. Only £6.73 +vat

AC Volt

- 0-200-750V £1.65 DC Volts £1.88 0-200mV-2-20-200-1000V £1.50 DC Current 0-200µA-2-20-200mA-10A Resistance 0-200Ω-2-20-200kΩ-2MΩ Diode Test Dimensions 126 x 70 x 24mm

PCB Material & Equipment and Soldering

- FREE Fully illustrated catalogue, send A4 SAE (add SASE)

VOL. 28 No. 8 SEPTEMBER '99

FUDGE

The mains supply in the UK, as everyone now knows (don't they?), is 230V a.c., changed some years ago to fall into line with the rest of Europe. Why? Who knows! However, if you measure it you will find that it is actually 240V plus or minus a few per cent, carefully controlled by the generating companies.

Most of the time it does not worry us editorially, we quote 230V because someone in authority somewhere says that is the standard; we know it's actually 240V but when you are part of Europe you get to a point where you let these things wash over you. This month, however, we have had to make it clear that 230V and 240V are actually the same thing!

In Alan Winstanley's excellent *Pipelines To Pylons* feature, Alan explains how the mains is derived and how we get to 240V (oops, sorry, 230V) from the 400kV that is originally transmitted. Of course, if we call the mains voltage 230V none of the explanations in Alan's article make any sense. So, please forgive us Mr. EU, we have had to tell the truth this month and let readers know that 230V is just a fudge - what we in the UK actually get is a very good, highly reliable, 240V a.c. 50Hz mains supply. But, of course, in future we will do as we are told and call it 230V, unless of course at some other time in the future we have to tell the truth to make the maths work.

Perhaps someone somewhere can give us a reason why we need to standardise with the rest of Europe and call 240V 230V. It's not as if we have actually changed anything except what we call it. We still exchange power with France across the English Channel and appliances still work happily in any country in Europe. And, as Alan said to us in an E-mail "either value is still enough to give you a frizzy hairdo" (or much worse).

DANGER

On a more serious note, Alan's article covers all the points readers have been querying over the past months about earthing of the supply, etc. Although I know the basics of supply from my training back in the distant past, the article has clarified a number of points for me and made me realise how complex power generation now is.

It also underlines some of the dangers, particularly of high voltage installations and I must admit that I did not realise how far power could jump at these voltages. Such installations are fenced off for good reason - the message is to stay well away. Don't ever think that you will be safe simply because you won't touch anything; at the high voltages concerned you don't need to touch anything to be killed.

Mike Kenward

AVAILABILITY

Copies of EPE/ETI are available on subscription anywhere in the world (see right), from all UK newsagents (distributed by Seymour) and from the following electronic component retailers: Omni Electronics and Maplin in S. Africa. EPE can also be purchased from retail magazine outlets around the world. An Internet on-line version can be purchased from www.epemag.com



SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £26.50. Overseas: £32.50 standard air service, £50 express airmail. Cheques or bank drafts (in £ sterling only) payable to Everyday Practical Electronics and sent to EPE Sub. Dept., Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Fax: 01202 841692. E-mail: subs@epemag.wimborne.co.uk. Also via the Web at: <http://www.epemag.wimborne.co.uk>. Subscriptions start with the next available issue. We accept MasterCard or Visa. (For past issues see the Back Issues page.)

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 p&p (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). Normally sent within seven days but please allow 28 days for delivery - more for overseas.

Payment in £ sterling only please. Visa and MasterCard accepted, minimum credit card order £5. Send, fax or phone your card number and card expiry date with your name, address etc. Or order on our secure server via our web site. Overseas customers - your credit card will be charged by the card provider in your local currency at the existing exchange rate.

Editor: MIKE KENWARD

Secretary: PAM BROWN

Deputy Editor: DAVID BARRINGTON

Technical Editor: JOHN BECKER

On-Line Editor: ALAN WINSTANLEY

Business Manager: DAVID J. LEAVER

Subscriptions: MARILYN GOLDBERG

Editorial: Wimborne (01202) 881749

Advertisement Manager:

PETER J. MEW, Frinton (01255) 861161

Advertisement Copy Controller:

PETER SHERIDAN, Wimborne (01202) 882299

READERS' ENQUIRIES

E-mail: techdept@epemag.wimborne.co.uk
We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. Due to the cost we cannot reply to overseas queries by Fax.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers (see *Shoptalk*). We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

ADVERTISEMENTS

E-mail: adverts@epemag.wimborne.co.uk
Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS/ETI take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are bona fide, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; overseas readers should check local laws.



LOOP AERIAL SW RECEIVER

ROBERT PENFOLD

You don't have to surf-the-net to capture the world. Just build this low-budget receiver and be amazed!

THERE have been electronic projects for just about everything imaginable published in recent years, but a simple shortwave (SW) receiver is still one of the most interesting electronic devices that you can build.

Commercial shortwave sets are now highly sophisticated pieces of electronics, and it is probably not feasible for the home constructor to compete with these. However, at the other end of the scale it is possible to produce simple and inexpensive receivers that are fun to build and will pick up numerous stations from around the world.

IN RANGE

The design featured here is intended for broadcast band reception at frequencies from about 4.5MHz to 14MHz. This provides coverage of the popular 49, 41, 31, 25, and 22 metre bands. It does not require an elaborate aerial or an earth connection, and the aerial is a form of loop antenna.

The term "loop" is perhaps not entirely appropriate in this case, because the aerial is actually about 2.5m of 300 ohm impedance ribbon feeder. This form of loop antenna has the advantage of being easy to accommodate, and it seems to provide quite strong output signals.

The loop is, in fact, about two or three metres on one dimension and only about 10mm on the other, rather than a circle of around two metres in diameter, but this does not seem to have a drastic effect on performance. The output of the set is adequate to drive either a crystal earphone or a pair of medium impedance headphones.

This is a very simple design using just three transistors. There are no unusual coils to wind or buy because the loop aerial also acts as the tuning coil, so it is very easy to build.

TUNED CIRCUIT

The block diagram of Fig.1 shows the simple arrangement used in this SW Receiver. Conventionally, the aerial is a long piece of wire which has one end connected to the receiver and the other end left unconnected. The aerial provides signals over a wide range of frequencies and a filter must remove all except those signals that

are close to the required reception frequency.

A sophisticated receiver has complex circuits to provide this filtering, but a simple receiver such as the one featured here has to rely on one simple filter. This is invariably a parallel tuned circuit, which is merely a capacitor connected in parallel with an inductor.

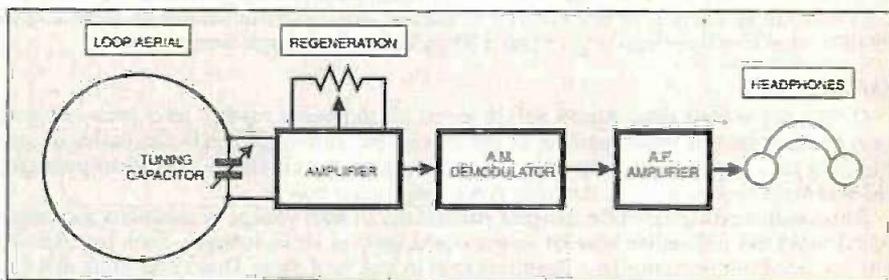


Fig.1. Block diagram for the simple Loop Aerial SW Receiver.

At a certain frequency, called the "resonant frequency", this type of circuit has infinite impedance. Away from the resonant frequency the impedance falls away rapidly to a low level. In effect, signals at or close to the resonant frequency are allowed to pass through to the subsequent stage while signals at other frequencies are short-circuited to earth.

In this design the aerial and the inductor in the tuned circuit are one and the same. The aerial is a large single-turn inductor, and the size of the aerial determines its inductance. The capacitor in the tuned circuit is a variable type, and this permits the reception frequency to be varied over a wide frequency range. The aerial only operates efficiently at its resonant frequency and at nearby frequencies, and this gives much the same result as using a separate long-wire aerial and tuned circuit.

The output from the aerial feeds a two-stage amplifier that has a buffer stage to provide a high input impedance. This is essential, as loading on the tuned circuit would otherwise reduce its efficiency to the point where it would not give adequate bandpass filtering. The second stage of the amplifier provides a substantial amount of voltage amplification.

This very simple form of receiver has two main shortcomings, which are a lack of sensitivity and inadequate selectivity. A receiver's selectivity is its ability (or lack of it) to pick out just one transmission from several stations on similar frequencies. Without some help a single tuned circuit does not provide adequate selectivity.

POSITIVE FEEDBACK


This help is in the form of positive feedback from the output of the amplifier to the tuned circuit at the input. As one would

expect, this recycling of some of the signal provides an effective boost in gain, and improved sensitivity.

Less obviously, it also provides a great improvement in selectivity. This is due to the fact that there is more feedback at the centre of the passband than there is away from resonance where the receiver operates less efficiently. This feedback, or "regeneration" as it is normally called in this context, therefore provides a much higher boost in sensitivity at the centre of the passband, narrowing the passband in the process.

There is a definite limit to the amount of feedback that can be used, and exceeding this limit results in the circuit breaking into oscillation. Optimum results are obtained with the regeneration control set just below the point at which oscillation occurs.

The output from the amplifier is fed to a conventional a.m. demodulator that recovers the audio signal from the received r.f. (radio frequency) carrier wave. Even on strong signals the output level from the demodulator will be quite low, and an audio amplifier is therefore used to boost this signal to a more usable level. Good volume is obtained from a crystal earphone or medium impedance headphones.

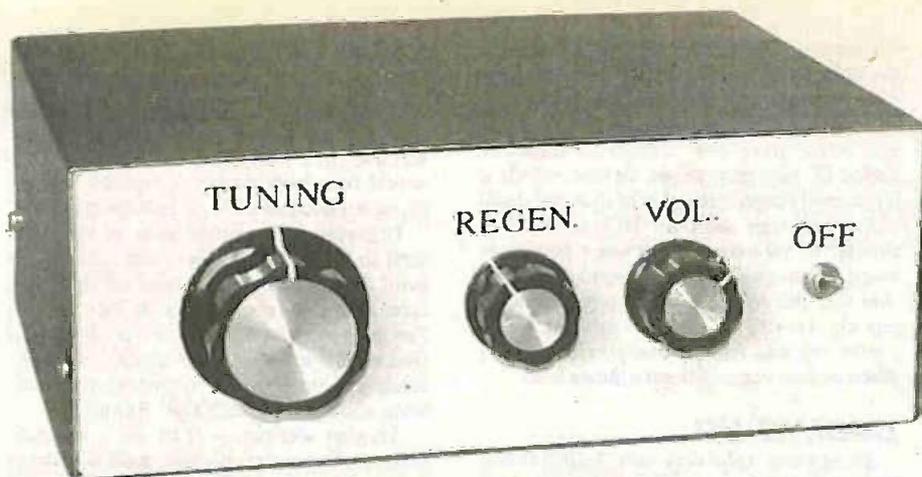

CIRCUIT OPERATION

The complete circuit diagram for the Loop Aerial SW Receiver is shown in Fig.2. L1 is the loop aerial itself, and VC1 is the tuning capacitor. TR1 is a junction gate field effect transistor (j.f.e.t.) which is used here in the common source mode. Unlike an ordinary bipolar transistor, a j.f.e.t. requires a reverse bias in order to provide linear amplification.

Resistor R2 results in the source(s) of TR1 being taken to about 0.5 volts or so positive, while aerial coil L1 biases the gate (g) input to the 0V rail and provides the small reverse bias. Bypass capacitor C2 removes the negative feedback that would otherwise be introduced by R2.

Transistor TR1 provides a certain amount of voltage gain, but its main purpose is to provide a high load impedance for the tuned circuit. A high input impedance is a natural characteristic of a j.f.e.t. and other field effect devices.

GAIN

Most of the voltage gain is provided by *pnp* transistor TR2, which operates as a simple common emitter amplifier. Regeneration control VR1 enables a controlled amount of feedback to be provided over the entire amplifier via capacitor Cx. The value of Cx is extremely low, and it is not actually a "proper" capacitor. It is simply two short pieces of insulated wire twisted together.

Capacitor C3 couples the output of TR2 to a conventional diode demodulator, which has D1 and C4 to respectively provide the rectification and the smoothing. The amplitude of the carrier wave is proportional to the audio signal voltage.

On the face of it, simply using some low-pass filtering will give an output signal that is equal to the average signal level, and therefore provides the required audio output signal. In practice this would not happen because the carrier wave is an a.c. signal, and the positive half cycles balance the negative half cycles to give an average output voltage of zero. Removing one set of half cycles eliminates this balancing, and gives the required demodulation.

Potentiometer VR2 is the "load resistor" for the demodulator and is also the volume control. From here the signal is coupled, via C5, to a common emitter amplifier based on transistor TR3. The output power available from TR3 is not very great, but it is sufficient to drive a crystal earphone. It will also drive medium impedance headphones if the phones are connected in series. Other types of headphone and earphone are unlikely to provide acceptable results.

The current consumption of the circuit is around 12mA or so. A good quality PP3 size battery is adequate to power the set, but if it is likely to receive a great deal of use it would be more economic to use six AA-size cells in a holder.

COMPONENTS

Resistors

R1	1k
R2	560Ω
R3	470k
R4	5k6
R5	1M
R6	2k2

See
**SHOP
TALK**
page

All 0.25W 5% carbon film

Potentiometers

VR1	1k rotary carbon, lin
VR2	4k7 rotary carbon, log

Capacitors

C1, C3	1n Mylar (2 off)
C2, C4	10n ceramic (2 off)
C5	1μ radial elect. 50V
C6, C7	100μ radial elect. 10V (2 off)
VC1	365p variable (see Shoptalk)
Cx	twisted lead, see text

Semiconductors

D1	OA91 germanium signal diode
TR1	BF244A <i>n</i> -channel j.f.e.t.
TR2	BC559 <i>pnp</i> silicon transistor
TR3	BC549 <i>nnp</i> silicon transistor

Miscellaneous

S1	s.p.s.t. min toggle switch
B1	9V (PP3) battery, see text
SK1, SK2	2mm or 4mm socket (2 off)
SK3	3.5mm jack socket (see text)
PL1, PL2	2mm or 4mm plug, to match sockets SK1, SK2 (2 off)
L1	300 ohm ribbon feeder (approx 2.5m) for aerial loop (see text)

Metal instrument case, see text; 0.1 inch pitch stripboard, size 31 holes x 20 copper strips; control knob (3 off); crystal earphone or headphones (see text); battery connector; wire; solder pins; solder, etc.

Approx. Cost
Guidance Only

£11

excl. batt. & variable cap

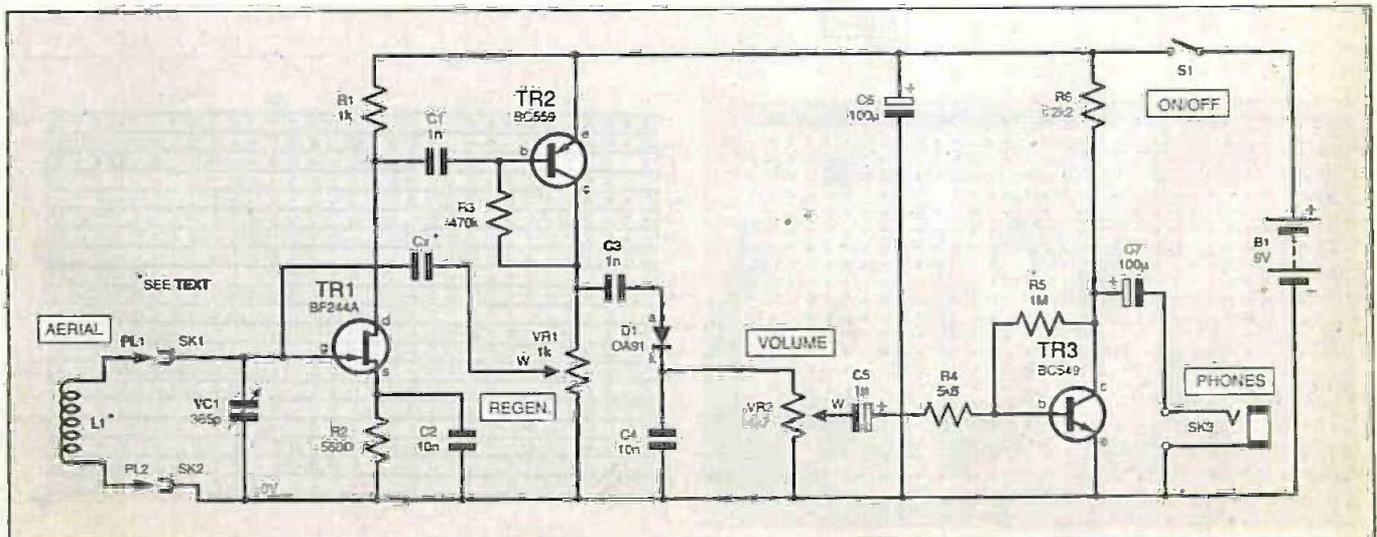


Fig.2. Complete circuit diagram for the Loop Aerial SW Receiver. The loop aerial is a single "loop" of about 2.5m of 300 ohm feeder cable and full details can be found in Fig.3

CONSTRUCTION

This simple receiver circuit is built up on stripboard and the component layout and wiring, together with the underside view showing breaks in the copper tracks, are shown in Fig.4. The board measures 31 holes by 20 copper strips, but it is not sold in this size.

Commence construction by cutting a larger piece of board to size using a hacksaw, cutting along the rows of holes. This produces some rough edges but they are easily filed to a neat finish.

Next the two 3mm diameter mounting holes are drilled in the board and the three breaks in the copper strips are made. A special tool for cutting copper strips is available, but a handheld twist drill of about 5mm in diameter does the job quite well. Whatever tool you use, make sure that the strips are broken across their full width.

The board is now ready for the components to be fitted. Fit the resistors and capacitors first, making sure that the three electrolytic capacitors have the correct

orientation. Use single-sided solder pins at the points where connections to the sockets, controls, and battery clip will be made.

Finally, fit the semiconductors, making sure they have the correct orientation. Diode D1 is a germanium device, which is more easily damaged by heat than the usual silicon devices such as TR1 to TR3. It should not be necessary to use a heatsink when connecting this component, but make sure that the soldered joints are completed quickly. Having connected one lead, allow a few seconds for the component to cool down before connecting the other lead.

CASING-UP

Shortwave receivers are traditionally built into metal cases, but this design does not rely on the case to carry any connections and it can be housed in a plastic case if preferred. It is important to keep the wiring reasonably short, and it is probably best not to depart too far from the general layout used for the prototype (see photographs).

VARIABLES

It is advisable to use a large control knob on tuning control VC1 because this makes accurate tuning easier, but it will necessitate the use of a fairly tall case. Ideally, VC1 would be a high quality air-spaced variable capacitor such as a 365pF Jackson type "O".

Unfortunately, components of this type tend to be very expensive, and some of the solid dielectric types (as used on the prototype) are not much better in this respect. Probably the best low-cost option, if you can find one, is to use a good quality "surplus" air-spaced component. Any maximum value from about 250pF to 500pF will do.

Another alternative is to use a low cost solid-dielectric component, such as used in "transistor radios". These usually have two "a.m." sections, which are used in parallel (i.e. wire the two non-earth terminals together). Any low value "f.m." sections can be wired in parallel with the "a.m." sections or just left unused.

Some variable capacitors require the usual 10mm diameter mounting hole, but

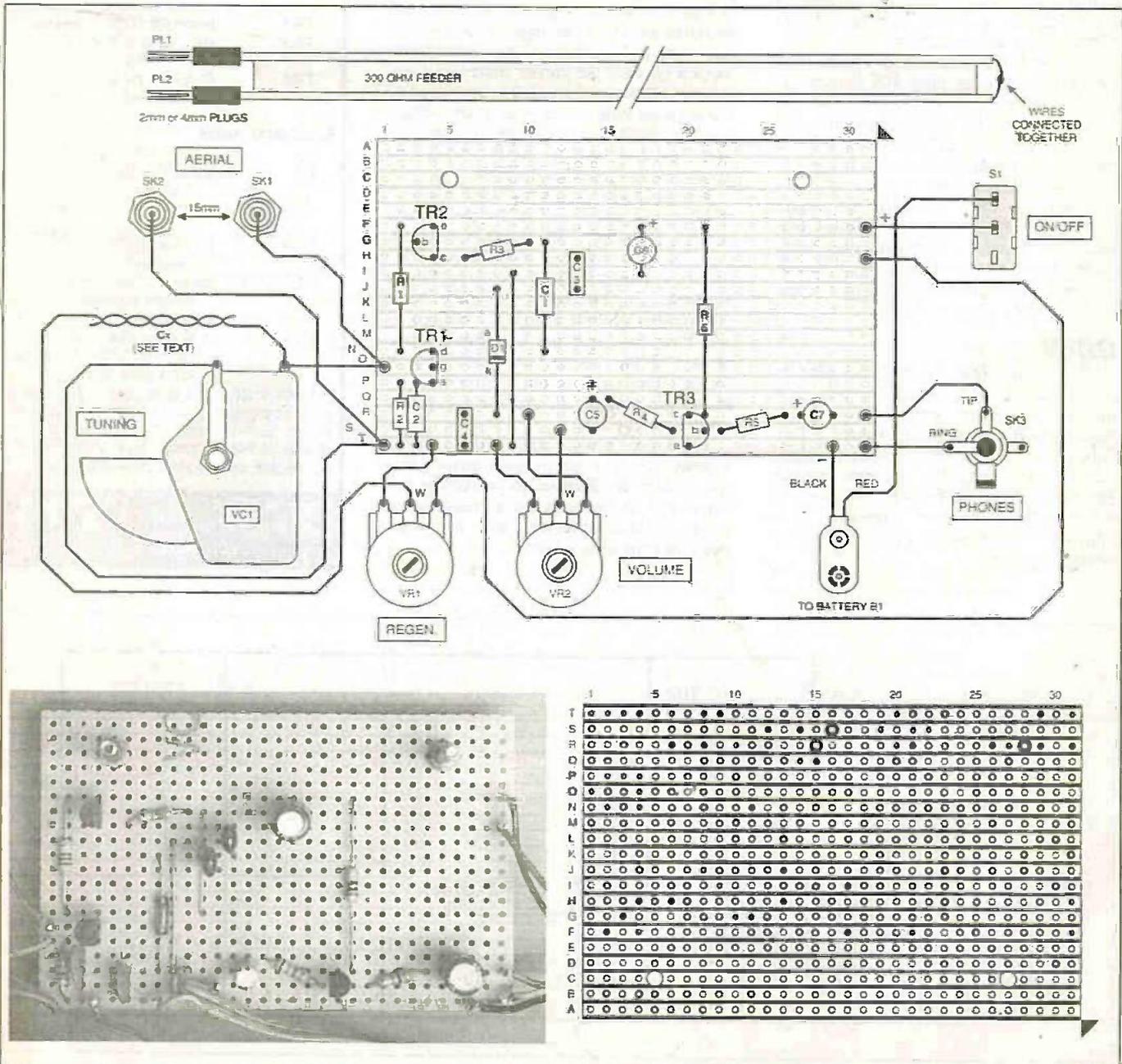


Fig.3. Stripboard component layout, off-board interwiring and board underside showing breaks in copper tracks. "Loop" aerial details are shown at the top and the completed board above.

most are fixed to the front panel using two or three short screws that fit into threaded holes in their front plates. With this second type it is often easier to glue them in place using a good quality adhesive such as an epoxy type. If longer fixing screws are used, make sure they do not penetrate so far into the front plate that they damage or foul the vanes.

SOCKETS

Sockets SK1 and SK2 are mounted on the rear panel of the case, and they must be quite close together (a gap of 15mm is about right). If the set will be used with a crystal earphone SK3 must be a 3.5mm jack socket, which matches the plugs normally fitted to this type of earphone. The switch contact fitted to open style sockets of this type is not required in this case, and one tag is therefore left unused.

A 3.5mm stereo socket is required for medium impedance headphones of the type sold as replacements for use with "Walkman" style units. These sockets are available in several styles, and the retailer's literature should include connection information. The 'phones are used in series, which means that the common earth tag is left unconnected and the board is wired to the other two tags.

The circuit board is mounted on the base panel of the case using metric M2.5 screws. Include spacers about 6mm long between the board and the case.

The wiring is perfectly straightforward, see Fig.3, apart from capacitor Cx. Ideally this would be made from two pieces of single-strand insulated wire, but ordinary multi-core connecting wire will do. Simply twist the ends of the wires together so that they are entwined over a length of about 50mm. If you use multi-core wire it is advisable to wrap some tape around the wires to ensure that everything stays in place.


AERIAL

Details of the aerial are also provided in Fig.3. A 2.5 metre length of 300 ohm ribbon feeder provides the approximate frequency coverage specified previously. Alternatively, you can use two aerials of different lengths to give the receiver two bands, and broaden its frequency coverage.

Band changing is then achieved by unplugging one aerial and connecting the other instead. This is a rather crude way of doing things, but is essentially the same as the plug-in coil method that has traditionally been used for simple shortwave receivers.

Realistically, the receiver is unlikely to perform well at very high frequencies, and there are relatively few a.m. broadcast stations to be found on the low frequency bands. One aerial about 1.5 metres long and one about 3.5 metres in length will provide coverage of the broadcast bands from 60 metres to 13 metres. Using 300 ohm ribbon feeder is not particularly expensive, so you might like to experiment with aerials of various lengths to see what, if anything, can be received at higher and lower frequencies.

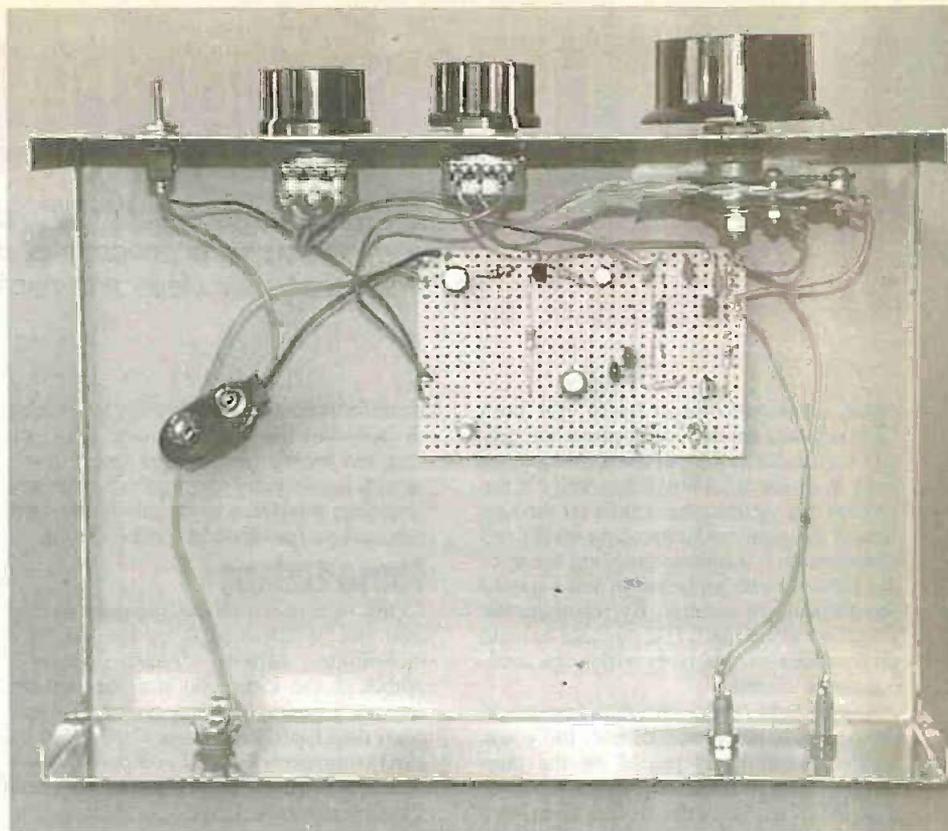It is very easy to make the aerial. Start by removing about 25mm of the plastic "ribbon" at each end of the cable using a sharp modelling knife, taking due care not to cut either yourself or the wires in the cable.



Suggested component layout and wiring inside the prototype metal case. The aerial and headphone sockets are mounted on the rear panel. Space must be allowed for a 6-cell AA-size battery pack if the receiver is to be used regularly.

Using ordinary wire strippers remove a few millimetres of insulation from each end of both wires, and "tin" the exposed ends with solder. At one end of the cable solder the two wires together to close the loop. At the other end of the cable fit two 2mm or 4mm plugs to match the type of socket used for SK1 and SK2.

IN USE

After a final check of the wiring it is time to connecting everything together and test the receiver. The aerial will not work well if it is left in a crumpled heap, but on the other hand it does not have to be kept perfectly straight. The prototype worked well with the aerial at about 30 degrees to the horizontal with the far end fixed to a cupboard with a piece of Bostik Blu-Tack.

With Regeneration control VR1 fully backed-off in a counter clockwise direction and Volume control VR2 well advanced it will probably be possible to receive a few stations, but not very well. Accurate adjustment of the Regeneration control is crucial if good results are to be obtained. Advancing this control should give much improved results with better sensitivity and selectivity.

However, as explained previously, advancing the Regeneration control too far results in the set breaking into oscillation. This will be heard as increased noise in the headphones, and a tone of varying pitch as the set is tuned across a station.

Optimum results are obtained with the Regeneration control

backed off just far enough to bring the set out of oscillation. Any large changes in the setting of tuning control VC1 will probably require some readjustment of the Regeneration control in order to maintain good results.

RECEPTION

The main shortwave broadcast bands will provide a range of interesting stations at practically any time of the day. Bear in mind though, that reception is at the mercy of the upper atmosphere, and is affected by factors such as the weather, sunspot activity, and the time of year. At times reception may be exceptionally good, while at other times the bands might provide few signals at all.

Normally, in the UK, it will be possible to receive stations from all over Europe, plus perhaps a few stations in North Africa, the Middle East, etc. When conditions are favourable it is possible to receive stations from much further afield.

You do not have to be a linguist to follow some of the programmes, as many countries put out programmes in English. For example, one of the first transmissions heard when testing the prototype was an English language broadcast from Turkey. □



New Technology Update

Ian Poole investigates the problems facing the photolithography process of producing today's i.c.s and finds that new ideas and techniques need to be explored.

THE semiconductor industry has been predicting the demise of photolithography for almost as long as the technique has been in existence. Photolithography is the process that defines the details on the surface of the semiconductor using masks and photoresistive solutions enabling areas of the surface to be protected or left exposed for diffusion or etching. By repeating the processes many times it is possible to build up the different structures within the semiconductor circuit.

As the sizes of the different features in the i.c.s have been reduced over the years, so the requirements placed on the photolithography process have increased. Over a period of ten years the feature sizes have fallen dramatically. Now manufacturers have to support sub-micron sizes for all their new products. Sizes of 0.1 microns are being talked about for production although the procedures for achieving this are not easily available at the moment.

Not only does this push the manufacturing tolerances right to the limit, but it also means that the photolithographic process requires further development. To achieve this the process needs to be optimised to enable it to cope with the minute sizes that are required, and a greater problem is that the sizes are now below the wavelength of light itself and this places a physical limit on the ultimate performance of the technique.

Problems Unmasked

Despite these problems the sizes have continued to shrink. New methods of overcoming problems have now been found although a few years ago they appeared to be insurmountable. This has enabled today's i.c.s to become a reality. Further developments are now required if the sizes are to fall even further.

Whilst photolithography is a technology that has been used for very many years, it is one that is likely to remain for some time yet. With the huge investments required to enable new technologies to be introduced, and the enormously competitive nature of the industry, it is essential that manufacturers quickly see a return for their money.

This has given the impression that companies may appear to be very conservative when it comes to revolutionary new technologies that require completely new lines to be installed. As a result methods of significantly improving techniques based on lithography have continued to surface.

As feature sizes started to shrink towards the limits of conventional light, ultra-violet with its shorter wavelengths was used. This approach is now used in the production of many of the i.c.s being

manufactured today. However, to be able to achieve the feature sizes that are required for the new designs being developed it is necessary to progress further and introduce new ideas to be able to meet the required performance in manufacturing.

Phase Shifting

One way in which the required definition can be obtained is by the use of a technique called "phase-shifting". Although the technique has been known for many years it is only now that it has been developed to a stage that it can be used commercially by a company named Numerical Technologies based in Santa Clara, California, USA.

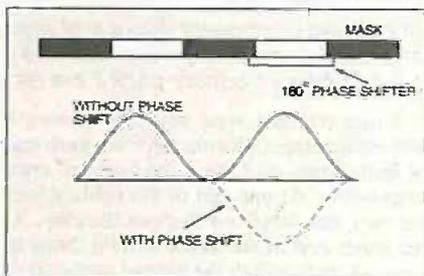


Fig. 1. Phase shifting technique.

The new patented approach basically uses a software package to generate masks to phase-modulate the light in a two pass process. As shown in Fig. 1, phase shifting selectively modulates the phase of light as it passes through the photomask. The high-quality image produced by this process greatly improves resolution and depth of focus so that the tiny features in designs can "print" accurately on a wafer.

One of the advantages of the new system is that it is compatible with existing industry standards. The software package takes inputs from industry standard i.c. layout files and then automatically configures them for phase-shifting photomasks. The phase-shifting masks will print polygate lengths as small as 0.09 microns, about half the length in today's leading-edge i.c.s, using the standard 248nm wavelength light.

The new system is being well received in the market. Early this year Motorola indicated they are to deploy the system in their production to enable them to manufacture PowerPC processors with increased speed for communication applications. This was undertaken as a joint venture between NumeriTech and Motorola and will allow them to shrink the gate lengths to 0.10 micron with the existing manufacturing processes.

Optical Correction

In addition to using a phase-shifting mask it is possible to further enhance the images by using a process named optical proximity correction (OPC). The process, it is claimed, resolves the distortion that results from a variety of factors including optical proximity as well as diffusion and the effects associated with etching and the resist itself.

It is found that as the shapes progress from the original design through the reduction to the final mask and then into the manufacture of the silicon, they become less well defined. This is witnessed by effects such as the rounding of corners or the shortening of lines.

There are a variety of techniques that are used to achieve improvements. The outside corners can be enhanced by the addition of small squares. The inside corners can be trimmed so that excessive rounding or line shortening is reduced or prevented.

The corrections also make the final wafer image match the designer's layout more closely, preventing short and open circuits. It also means that the final chip more accurately matches the original simulations.

Alternatives

As might be expected phase-shifting and optical correction are not the only techniques that are being developed. Other techniques have their place as well.

One, known as electron beam lithography, uses the same basic techniques as photolithography, but instead of using light to expose the photo-resist, it utilises an electron beam. Naturally a different photo-resist must be used — one that is sensitive to an electron beam.

As these beams have a much shorter wavelength it is possible to achieve higher degrees of definition. The system effectively writes directly onto the wafer, and the performance is highly dependent upon the beam forming optics.

One of the main drawbacks of this system is that because it uses an electron beam, rather than light, this process must take place in an evacuated chamber. This makes throughput much lower and this is a critical aspect of any semiconductor manufacturing process these days.

Whatever techniques are used, it can be seen that there are still plenty of options to reduce the feature sizes within integrated circuits still further. However, a point will eventually come when it is not possible to use photolithographical methods. Even now research is being invested in possible methods of overcoming these problems, and it will be interesting to see what arises in the coming years.

SAVE OVER 60%
 QR4 FULL ACCESS
 JUST £99
 (Normal price £249)
 Offer ends 31st October 1999
 (Price includes post & packing and VAT)

QR4™

QUICKROUTE



Quickroute Makes it Easy



SPECIFICATION

- Modern user interface with dockable toolbars & active buttons
- Multi-sheet schematic capture at the press of a button.
- Power rail & data bus support
- 32 Bit mixed mode analogue & digital simulation
- Support for a range of SPICE .MODEL statements
- Copper flood fill
- Netlist import & export
- CAD/CAM file import/export. Gerber Viewer.
- PCB Design with 18 layer autorouter
- WMF, DXF, & SPICE file export
- 1000+ Library Symbols
- Engineering Change & Design Checking



FREE DEMO


Download a free demonstration version from our web site at <http://www.quickroute.co.uk>

30 DAY MONEY BACK GUARANTEE

It's not hard to see why Quickroute is so easy to use! We've integrated mixed mode simulation, schematic capture, PCB design with autorouting and CAD-CAM support into one integrated environment. Best of all, prices start at just £99.88 inclusive* for the complete system with support for 300 pins - less than the price of some simulators alone!

Quickroute 4.0 features a modern user interface with active buttons and dockable tool bars. Frequently used tools can appear on floating tool pallettes for quick access, and with tool-tips and on-line help you can be sure of getting information on Quickroute's features fast.

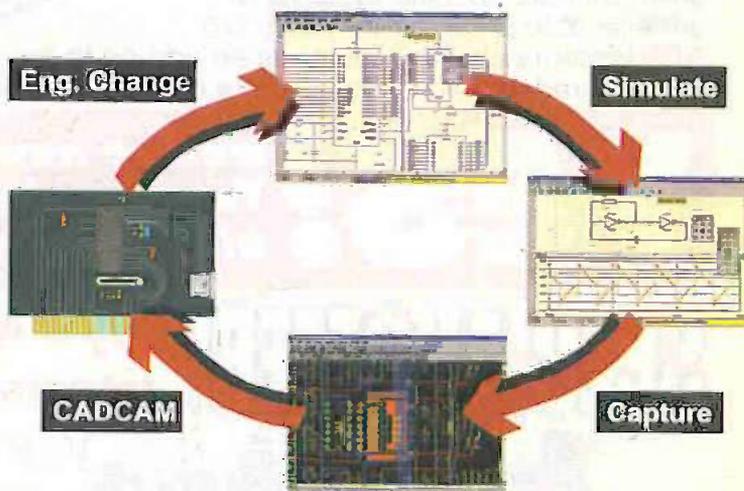To create a schematic in Quickroute 4.0, simply click on the symbol browser and select and place symbols onto the design area. Use the 'intelligent' wires, power rails and data bus elements to quickly wire up your schematic and simulate the design as required. When completed, simply press a button to capture the schematic, a PCB rats nest will then appear (no messy netlists required!).



Use the multi layer autorouter, and/or manual routing to complete your PCB together with copper fill, etc as required. Finally print your design, or create CAD/CAM files suitable for manufacture (we even include a Gerber viewer for checking).

But it doesn't end there! Quickroute 4.0 includes engineering change for automatic updating of your PCB from the schematic, netlist import & export so that you can link to other EDA packages (including many simulators), DXF, SPICE, and WMF file export together with over 1000 library symbols.

Call us now and find out why Quickroute 4.0 Makes it Easy!

	Price	UK Inclusive Price*
QR4 300 Pin	£79.00	£99.88
QR4 800 Pin	£149.00	£182.13
QR4 Full	£249.00	£299.63

*Includes UK P&P and VAT. Phone for EC/World prices.
 **Design cycle figure shows screen shots from different projects.
 Prices & specification subject to change without notice.

FREEphone Ref 411
0800 731 28 24


FAX 0161 476 0505 TEL 0161 476 0202
 Quickroute Systems Ltd Regent House
 Heaton Lane Stockport SK4 1BS UK
 Copyright (C) 1998 Quickroute Systems Ltd. All rights reserved. All trademarks are the property of their respective owners.

88-108MHz FM stereo Radio Transmitters and kits

FM radio transmitter kits from as little as
£13.95 professionally built systems
from only **£19.95**

Powerful systems: kits up to
35-Watts power professional
systems up to **220-Watts
power**

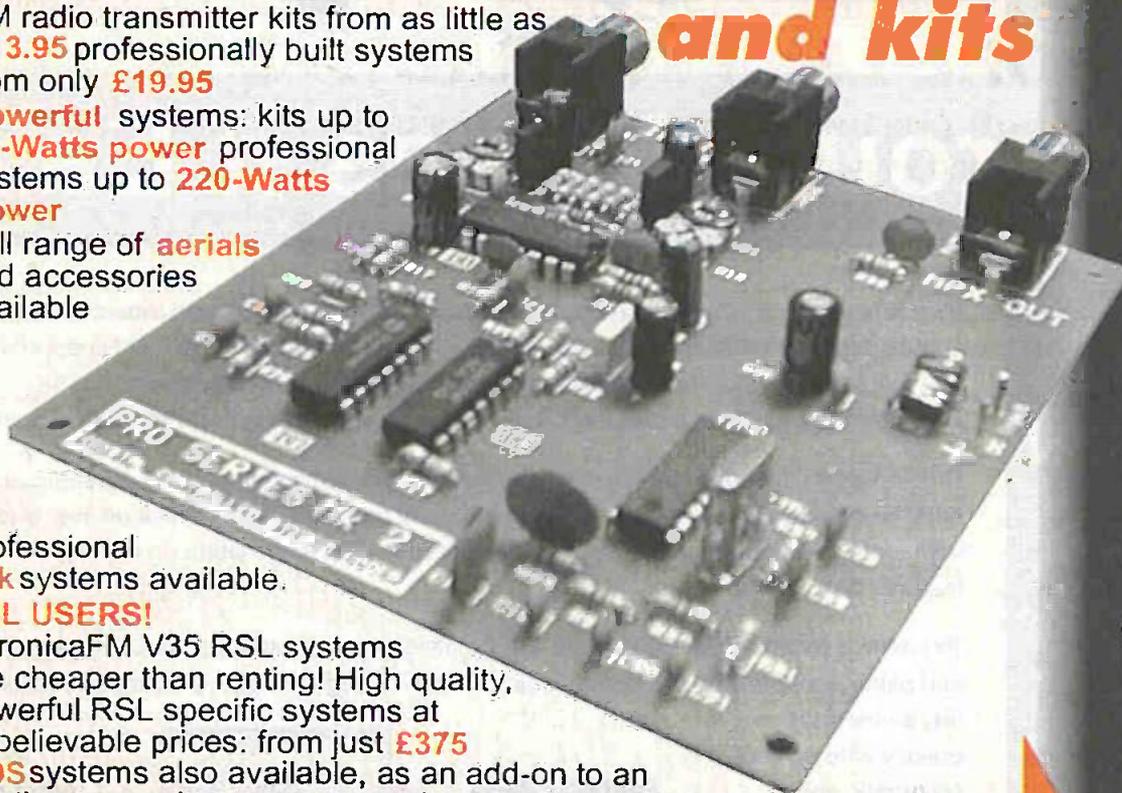Full range of **aerials**
and accessories
available



Professional
link systems available.

RSL USERS!

VeronicaFM V35 RSL systems
are cheaper than renting! High quality,
powerful RSL specific systems at
unbelievable prices: from just **£375**

RDS systems also available, as an add-on to an
existing transmitter, or as part of a complete system

YES! we are now on the internet!
You can view and buy
all our products online!

SPECIAL OFFER! Buy a **NEW PLL Pro II**
transmitter kit and
you will receive the
ALL NEW Pro II
Stereo encoder
(pictured above)
FREE!



CONTACT US NOW! for more information
and a free brochure

E-mail: info@veronicafm.co.uk

 **01274 816200** (fax same
number)

VeronicaFM, 18 Victoria Street, Queensbury, Bradford, West Yorks, BD13 1AR

WWW.VERONICAFM.CO.UK

PHONE-LESS INTERACTIVE TV

Irish viewers will soon be able to participate in TV programs while at home, and without a phone-link. Barry Fox reports.

SOUTHERN Ireland will pioneer the use of a new digital TV system that lets viewers interact with the broadcaster, without needing a phone, cellphone or cable connection. The service will be launched next year by Digico, a private company now being spun off from state broadcaster RTE, Radio Telefis Eireann. Digico will offer teleshopping and let millions of viewers vote on quiz questions or political issues without overloading the country's phone system.

Digico will compete head on with Ireland's Cablelink cable system, bought recently by NTL, and with Rupert Murdoch's Sky satellite service which already transmits digital services into Eire but needs a phone line for interaction.

WINDS in the Rigging

RTE is developing the technology, called WINDS or Wireless Interactive Network for Digital Services, with EU funds. Digital terrestrial TV signals are broadcast in the usual way, using Europe's Digital Video Broadcasting standard. But the home receiver also works as a low power transmitter, sending data signals back to Digico's masts from an existing UHF rooftop or set-top aerial.

The Irish government has allocated 1MHz slices of the UHF spectrum to carry the return path signals. Each slice is split into 1000 very narrow channels and the receiver can hop between channels until it finds one in its area that is clear.

WINDS borrows from GSM digital cellphone technology to keep transmission powers at a minimum, and so let the system re-use the same frequencies in closely neighbouring areas. The receiver transmits and receives test signals, and automatically optimises its transmission strength. Urban areas will have more 1MHz slices and use relay stations to let the receivers transmit at very low power, in very small cell zones.

Wide Range Coverage

Because Ireland has spare UHF frequencies and is a long way from other countries' transmitters, 30 masts will be able to transmit digital TV programmes at high power and reach 98 per cent of homes. Up to 20,000 receivers can transmit back to one broadcast mast at the same time.

The return path bit rate changes depending on what data has to be transmitted, and the data is packaged like a TC/IP Internet signal to make it error-resistant. Recent tests with CCETT, the Centre Commun d'Etudes de Telediffusion et Telecommunications, at Rennes in France, have shown that a home receiver can return a data signal 30 kilometres with transmission powers of well under the one watt licensed by the Irish government.

Although Digico will only have airspace for six broadcast channels, carrying less than 40 programmes, the company plans to launch in September 2000 with a receiver that houses a 25 gigabyte hard disk. This will let the viewer store up to 10 movies for later viewing.

Says Peter Branagan, Director of Digital Planning at RTE, "Interactivity is the new paradigm. WINDS can provide a wireless return path that is free to use and adds less than 30 Euros to the cost of the receiver. And viewers will be able to interact even when their teenagers are on the phone"

HEADBAND MAGNIFIER



APART from a good selection of test equipment and a wealth of enthusiasm, the intrepid electronics enthusiast needs one other vital workshop aid, good eyesight. Sadly, good vision is not necessarily an attribute always readily available and the miniature size of so many of today's components can make a fair number of enthusiasts feel inadequately equipped! Where funds permit, some enthusiasts faced with this problem emulate professional workshop engineers and have a large bench-mounted angle-poise magnifier complete with its own light source. Such things are not cheap, however.

Readers who would like to inexpensively improve their ability to view fine detail might care to consider Sheshto's new versatile Headband Magnifier Kit. It really is an astonishingly simple yet ingenious approach to the problem. It comprises an adjustable headband, four interchangeable pairs of lenses, and a spotlight!

Sheshto say that it provides the complete answer for achieving the best results when doing close-up work and offers the ideal way to work on any craft, hobby or DIY project, leaving your hands free to get on with the job. We salute our irons to that belief!

The four precision-ground optical lenses are designed to cover all focal lengths needed from semi-close-up to very close-up and are easily changed over with the simple clip-in slots on the headband. The lenses can be pushed up out of the line of vision when not required. The magnifications and working distances are: 1.2x 520-620mm (20-24in), 1.8x 230-320mm (9-12in), 2.5x (150-25mm (5-10in), 3.5x 80-120mm (3-5in).

As can be seen in the photo, the battery operated adjustable spotlight is very neatly incorporated on the top of the headband. It can be switched on for those extra delicate close-up jobs. Those of us whose eyesight is no longer 20-20 will know that just increasing the illumination on a subject can on its own help the eyes to focus better.

The price of £34.95 plus £3.00 p&p is a very small outlay for something that could well enhance your ability to take a closer view of the world, and especially your hobby.

Sheshto state that for 90 years they have specialised in tools, supplies and equipment for technicians and craftsmen. They say that their Essential Tool and Reference Guide is packed with useful information and features over 2000 hard to find tools and references; its price £5.

For more information, contact Sheshto Ltd., Dept EPE, Unit 2, Sapcote Trading Centre, 374 High Road, Willesden, London NW10 2DH. Tel: 0181 451 6188. Fax: 0181 451 5450. (No web site or E-mail quoted.)

HEAR, HEAR!

Barry Fox, with ear to the ground, hears whispers about a new amplifying system.

TECHNOLOGY is now available to help judges hear people who are nervous in court, and let the world hear MPs who mumble in Parliament. After developing a system to help audiences hear what was going on in a local children's theatre, Philips of the Netherlands is using its Profecta Acoustic Feedback Suppressor to let a public address system sound four times louder than is usually possible without "howlround" feedback.

Audio systems howl because the microphones pick up stray sound from the loudspeakers, and feed it to the amplifier and back to the loudspeakers. So the sound goes round in circles, getting louder all the time and finally resonating like an organ pipe at whatever frequency the system is most efficient at reproducing.

Early feedback suppressors worked by filtering out the resonant frequency. This kills the howl but makes the reproduced sound very unnatural.

More modern systems de-correlate the input and output sound by shifting the frequency of all the sound from the speakers by around 5Hz. So the microphones do not reinforce the same frequencies in a vicious circle. This limits feedback but adds a myriad of faint echoes to the sound, all with slightly different pitch, like an acoustic hall of mirrors. So a single voice starts to sound like a choir.

If a de-correlation system adds more than 3dB gain over the level at which feedback would normally start, the echo effect becomes offensive and makes speech

unintelligible. As the human ear needs an increase of 10dB to register a subjective doubling of loudness, a 3dB improvement is hardly noticeable.

Philips Communication and Security Systems division has now programmed digital signal processing chips to shift the frequency of the sound while predicting what the added echoes will be like. Profecta AFS then generates signals which exactly match the predicted echoes in pitch and level, and subtracts them from the microphone input. So the shifted sounds coming from the speakers never reach the amplifier.

This lets the amplifier add around 20dB more gain than would normally cause feedback howl, and without a choir effect.

Philips first tried Profecta AFS at a children's theatre called de Schalm near its laboratory at Eindhoven in the Netherlands. The theatre had to sling the stage microphones high to stop the children hitting their heads when they skipped and jumped around the stage. The high microphones were then unable to pick up the performers' voices without feedback. Since AFS was installed the audience has for the first time been able to hear what is being said and sung.

Philips then packaged AFS in a rack mount for sale to PA firms, at around £2500. Units have already been installed in the Dutch and Spanish Parliaments, and were recently demonstrated to the UK's Houses of Parliament and Royal Courts of Justice.

GREENWELD RE-LIVES!

IT'S always heart-warming to be able to report good news about a situation that had previously seemed depressing. In our July issue we reported that Greenweld Electronics had ceased trading, but that a purchaser for the business was being sought. We are delighted to report that a purchaser has indeed been found and that the name Greenweld will soon reappear.

The name and assets of this renowned electrical and mechanical surplus company have just been bought by a new company run by two brothers with a science background.

By the time you read this, the company will have started operations from their new base in Essex and a catalogue will be mailed out at the beginning of September to all those on the database. The new company will continue to supply the same range of goods which it hopes to supplement with additional items of a general scientific and technical nature.

We have received this information just as we go to press with this issue and do not yet know details of what is happening with the previous Greenweld site at Southampton, nor do we know details of the new location in Essex. We hope to publish information on both matters in the next issue. Hopefully we shall also be able to tell you a bit more about the company which has resurrected Greenweld.

All too often over the years we have seen the demise of enterprising electronics businesses. It is really good to know that Greenweld has been saved and wish the venture every success.

Until we can provide more details, you can contact Greenweld as follows: E-mail: greenweld@aol.com. Fax: 01992 613020. Web: www.greenweld.co.uk. (Phones had not been installed at the time of writing.)

DIGITAL TV COLLEGE

WE were extremely interested to learn that the College of North West London has started courses on servicing digital TV equipment. Their press release comments that bridging the gap between old and new technology is the challenge that faces all training establishments. Whilst digital TV was launched last year to a mixed reaction, it is now taking off in a big way and the College says that it is streets ahead of the field in offering the latest state-of-the-art servicing facilities.

The College has invested £20,000 on installing 20 digital TV workstations, fully equipped with digital storage oscilloscopes, spectrum analysers and logic probes, to allow students to test and fault-find using digital TV receivers, both satellite and terrestrial. It has a selection of digital set-top decoders from various major manufacturers, including Philips, Nokia and Pace, and trains students to service all of them.

It is still the only FE college in the UK to provide digital TV training courses, because the technology is so new. This means that it attracts lecturers and engineers from employers all over Britain, including the BBC, IBM, the Comet chain and other FE colleges.

Deputy Head of Department John Raynard says that "Our intention is to bridge the gap between analogue/digital technology and microprocessor-based systems. We offer one-day courses for the servicing industry, either on college premises or on site. They can be either off-the-shelf or customised for service engineers who need a specific updating or upgrading programme."

The College offers three current one-day courses, held approximately once a month, leading to college certificates, which are: Digital TV Broadcasting and Reception, Servicing Digital TV Decoders, Microprocessors for TV Service Engineers.

Additionally, the College has received accreditation to offer the City & Guilds course on Digital TV at Level 3 of the Electronic Servicing 2254 from September '99. The College will set the exams, but students who pass will get a C&G certificate - the first college-devised unit of this type in the UK.

For further information contact Kay Shelley, College of North West London, Dudden Hill Lane, London NW10 2XD. Tel: 0181 208 5196. Fax: 0181 208 5151. Web: www.cnwl.ac.uk. (Say that EPE has told you about the College.)

Hi-Fi Show '99

THE Hi-Fi Show, Europe's biggest hi-fi and home entertainment exhibition, will be staged at the newly refurbished Novotel Hotel, Hammersmith, London on 23-26 September '99. This huge show has outgrown its previous venue and the city-centre move will provide further expansion with more rooms, exhibitors and products to be launched.

The Hi-Fi Show '99 will be a pivotal event in the history of home entertainment. As the final show of the Millennium, it will be a celebration of familiar and traditional technologies and a reception for the formats that will shape our listening and viewing pleasure in the future. Over 200 of the world's leading hi-fi companies will demonstrate and launch their latest equipment.

Exclusively at the show, the BBC will provide hands-on demonstrations of the new Digital Radio Broadcast (DAB). This will take over from FM, giving improved quality and reception.

Tickets for the Hi-Fi Show '99 are available from the ticket hot-line 0181 774 0790. Adult admission is £4 in advance, £5 on the day. Under 14's go free. The show is open 10am to 6pm.

NET MUSIC PROTECTION

Barry Fox reports on the initiative for tighter copyright protection for Net-sourced music and games.

THE music and electronic industries' Secure Digital Music Initiative has now agreed the framework for copyright control on portable players that can download music from the Internet (see SDMI's website www.sdmi.org). Leonardo Chiariglione, the SDMI's Executive Director, is not bothered that some companies, including Thomson and subsidiary RCA, have jumped the gun by launching proprietary systems.

"They are all downstairs helping to write the standard" he said during a 3-day meeting of 200 representatives from 150 member companies in London. "Sometimes different people inside the same company have different strategies. Niche products will not succeed because consumers need the assurance that they are not tied to a proprietary source of music. People must be able to get what they want from anywhere that has it".

The SDMI was formed last December when the music industry failed to block the sale of Diamond Multimedia's Rio solid state portable. Chiariglione, who heads the

TV Technologies division at Telecom Italia, has for the past 11 years chaired the committees which set the MPEG digital video compression standards.

SDMI builds on technology used in the MPEG-2 standard for digital video disc and TV, and MPEG-4 for video on the Internet. The bitstream carries keys which can be used, with extra keys in the player, to unlock encrypted content. When an SDMI-compliant PC downloads music from the Internet, or copies it from a CD, it will encrypt the music so that it can only be used in one portable player which is electronically locked to the PC.

By 31 March 2000 the SDMI will extend this protection framework to cover the entire delivery chain, whether the Internet or broadcast airwaves.

Says Chiariglione "SDMI will then protect movies, games and TV. It's a fundamental step which lets the seller and buyer agree on a contract. This opens the way for an infinite number of new business models".

RAE COURSE

THE Hilderstone Radio Amateurs' Examination Course commences on 23 Sept '99 in the Sandwich area of East Kent (exact location not yet advised). Tutor Ken Smith G3JIX advises that this is the usual course for the Amateur Radio Licence Exam, but also much of the content covers a very good grounding for general electronics interests (including some of the history as well).

This course has been run at intervals for many years, with eminent success. Ken says that we have exciting times ahead for Amateur Radio and that "wireless" methods are growing amazingly throughout the professional and commercial world. Furthermore, Amateur Radio continues to be central to a stimulating, fun-based and entertaining introduction to modern technology.

"It is", says Ken, "one of those pastimes that increases your circle of friendships greatly - and on a world-wide basis. All interested people, whatever their age etc., are most welcome to explore with us this remarkable technology with a very human face; and the Exam does not have to be sat, of course!"

For more information contact Ken Smith via G3JIX, or tel: 01304 813175, or via ken.smith@saqnet.co.uk.

LOW ENERGY FOOD

NO, we are not about to advocate yet another slimming diet, but to compliment Sainsbury's for the energy saving concepts being embodied into their new store at the Millennium site in London.

The refrigeration system, for example, will be partly cooled by the lower lying ground water that remains at a constant 10°C throughout the year. The heat output by this system will be used to heat the store. Earth banks around the building will help insulate against temperature changes, while the reinforced concrete walls act as a giant storage heater, absorbing heat in the day and releasing it at night. Wind turbines and solar cells generate power which is stored in batteries and used to light the building at night. There will also be free recharge points for customers' electrically powered cars. It all seems very forward looking.

The store will open in September.

CIRKIT JOINS DELTRON

IF you use coils in your electronics designs, the chances are that Cirkit Distribution will be one of the companies who come to mind when you are thinking about which supplier to use. You will probably use Cirkit for other electronic components as well. It will, therefore, be of interest to you to know that Circuit Distribution has been acquired by Deltron Electronics.

Cirkit has been trading since 1984 and has been part of the Bulgin Group since its creation. Deltron is a growing public company primarily focussed on distribution activities in the UK and abroad. The business of Cirkit will operate as part of the Roxburgh Electronics subsidiary of Deltron.

FASTER PHONE LINES

BETWEEN now and next spring, BT will be installing equipment that will transform ordinary phone lines into digital channels which operate up to ten times faster. Initially, 400 exchanges around the UK, covering nearly six million households and businesses, will be upgraded.

The ADSL (Asymmetric Digital Subscriber Line) technology can boost existing local copper networks by using sophisticated electronics at the exchange and in customers' premises, without digging up streets and pavements.

ADSL works by transmitting and receiving digital signals across the cop-

per pair of wires connecting each customer to the exchange. It operates on a frequency band higher than that used by the voice line operating in the same copper pair, so that the two services do not interfere with each other.

At the customer's end the equipment consists of two principal items. A filter, or "splitter", provides separate physical sockets for the digital service and the voice service. A normal telephone plugs into the phone socket on the splitter. An ADSL modem plugs into the digital port on the splitter and is then plugged into appropriate digital consumer equipment, e.g. a PC or digital TV.

LISTEN TO THE ECLIPSE

By Barry Fox

The Rutherford Appleton Laboratory at Chilton in Oxfordshire has a plan to let people research the solar eclipse on August 11, without travelling to Cornwall, France, Germany or Romania. All they need is a simple Medium Wave radio to log the reception of distant stations.

Radio waves usually travel in straight lines, and cannot reach past the horizon. They also reflect off the upper (E and F) layers of the ionosphere, some 300km up, to "skip" long distances. But during the day, the lower (D) level of the ionosphere, at around 100km, absorbs radio waves. So distant radio stations can be heard at night but not in the day.

RAL wants to use this effect to track what happens to the ionosphere when the eclipse effectively turns off the sun's ionising radiation and the lower level decays after a few seconds.


The last time the UK saw a total eclipse was in 1927, when radios were a luxury and ionospheric science was a novelty. Now virtually everyone has an MW radio and a tape deck to record reception.

RAL has checked all suitable frequencies and found two MW stations, *Radio La Coruna* in Spain on 639kHz and *Radio Marseilles* on 675kHz, which are ideal for the test. Both can normally be heard only at night in the UK. If they can be heard on the morning of the eclipse it signifies a dramatic change in the lower level of the ionosphere which is letting waves through for reflection instead of absorbing them.

Anyone interested should tune to the station on a night before the eclipse, leave the radio set to that frequency and tell RAL their post code and what they heard or did not hear during the eclipse. RAL will then log the effect over the whole country.

Further details are available from RAL's web site at www.wda.rl.ac.uk.

VARIABLE DUAL POWER SUPPLY

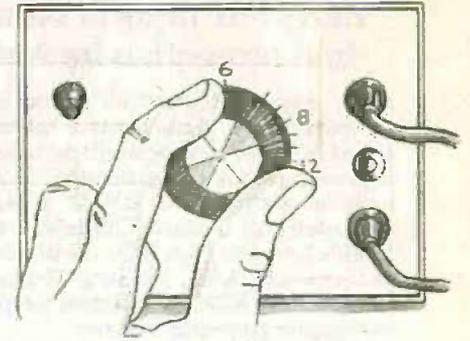

TONY SERCOMBE

Fully variable from $\pm 3V$ to $\pm 15V$, this 500mA workshop tool is short-circuit proof, and highly useful!

SOME time ago the author urgently needed a split level power supply and for quickness copied a previously published circuit. It worked well, with one exception, that it had no protection against accidental short circuits.

In the author's case, these could happen with the negative output, mainly due to the fact that on most of his printed circuit boards the negative and earth lines were in close proximity. The slightest contact between the two would cause instant destruction of the negative feed transistor. So, on the last occasion this occurred, it was decided to revisit the circuit, and the design described here is the result of that investigation.

CIRCUIT DESCRIPTION

As can be seen from the circuit diagram in Fig.1, a centre-tapped transformer (T1) is used so that both positive and negative voltages may be obtained from the bridge rectifier (REC1). Capacitors C1 and C2 smooth the rectified voltage. Resistors R1 and R2 provide a discharge path when the power supply is switched off.

Two LM301 op.amps are used as the controlling elements, the negative controller (IC2) being slaved from the positive

controller (IC1), the latter acting as the master in conjunction with potentiometer VR1, which sets the output voltages.

A reference supply voltage for the op.amps is obtained from Zener diodes D1 and D2, which set it at $\pm 18V$. Variable d.c. feedback is applied to pin 2 of IC1 via VR1. Thus, as the feedback is increased the output drops, and when decreased it rises. IC2 is controlled by the output of IC1 and thus adjusts the negative line accordingly.

The outputs of each of the op.amps feed the bases of Darlington transistors TR1 and TR3, via resistors R12 and R9 respectively. The outputs from the transistors are then fed via low value (1Ω) resistors to the power output sockets. Capacitors C7 to C10 help to smooth any high-frequency spikes or noise at the output sockets. Resistors R15 and R16 provide a discharge path when the unit is switched off.

CURRENT LIMITING

The purpose of transistors TR2 and TR4 is to limit the current that can be drawn should an excessive load be presented to the unit's outputs. As more current is drawn, an increasing voltage drop occurs across resistors R13 and R14, so driving the base of TR2 more positive than its emitter, and the base of TR4 more negative.

These transistors now start to turn on, so shunting the bases of TR1 and TR3, having the effect of turning them off in extreme cases. The current drawn by TR2 and TR4 is restricted to a safe maximum limit by resistors R12 and R10 in series with the outputs of the op.amps. The resistors also serve to prevent the op.amp outputs being sunk almost to ground in the event of a complete short circuit.

The power supply will stand a total short circuit at its outputs, with no damage being caused to them, or to the transformer or rectifier.

It should be noted that resistors R10 and R11 across the output and feedback connections of the op.amps should be matched to at least one per cent to maintain sensible tracking between the two outputs. It may well be worth measuring several samples with a multimeter to get identically matching values.

A wirewound potentiometer is recommended for VR1 since the resolution is likely to be better in this application.

CONSTRUCTION

Since this unit is mains powered, great care should be exercised in its construction. If in any doubt about constructing it, consult a qualified electrician. Mains voltages can be lethal if abused.

Details of the printed circuit board component positions and track layout are shown in Fig.2. This board is available from the EPE PCB Service, code 242.

It is a wise precaution to use sockets for the op.amps as they would otherwise be very difficult to remove without damaging the p.c.b., should this become necessary.

Although not used in the prototype, a 0V to 20V moving coil meter could be wired across the outputs, with a changeover switch to select which output is monitored. However, these are quite expensive and the prototype used a calibrated scale drawn around the knob for potentiometer VR1. If done with care, this method can have a very neat appearance, and is probably accurate enough for most purposes. Otherwise, the output may be monitored with a multimeter.


A metal case should be used to house the power supply, and this should be connected to the mains supply earth via the power cable. The mains fuse can be of the cartridge type mounted on the back panel. A cable clamp must be used for the mains input cable.

For the prototype, 4mm single sockets were used as the d.c. power output connectors. Other types of socket may be used to suit individual requirements.

TESTING

Once the p.c.b. has been assembled, fully check for any mistakes, and for the good quality of the soldering. On the prototype, the mains transformer was pop-riveted close to the edge of the long side of the case, and the p.c.b. was secured to the base with self-adhesive p.c.b. supports. However, it is best not to fully fix the p.c.b. until testing is complete.

A piece of insulating plastic sheet should be cut to just under the size of the p.c.b. and placed between it and the case floor. These sheets are readily obtainable from model shops.

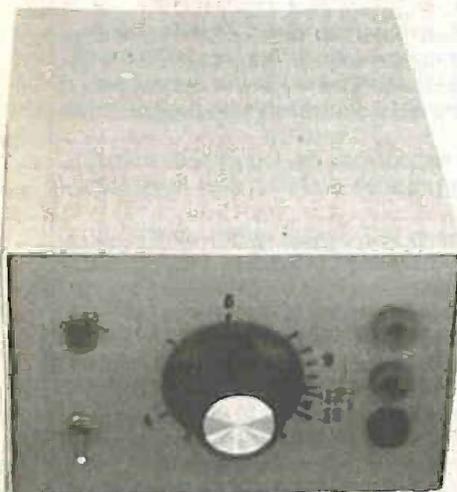


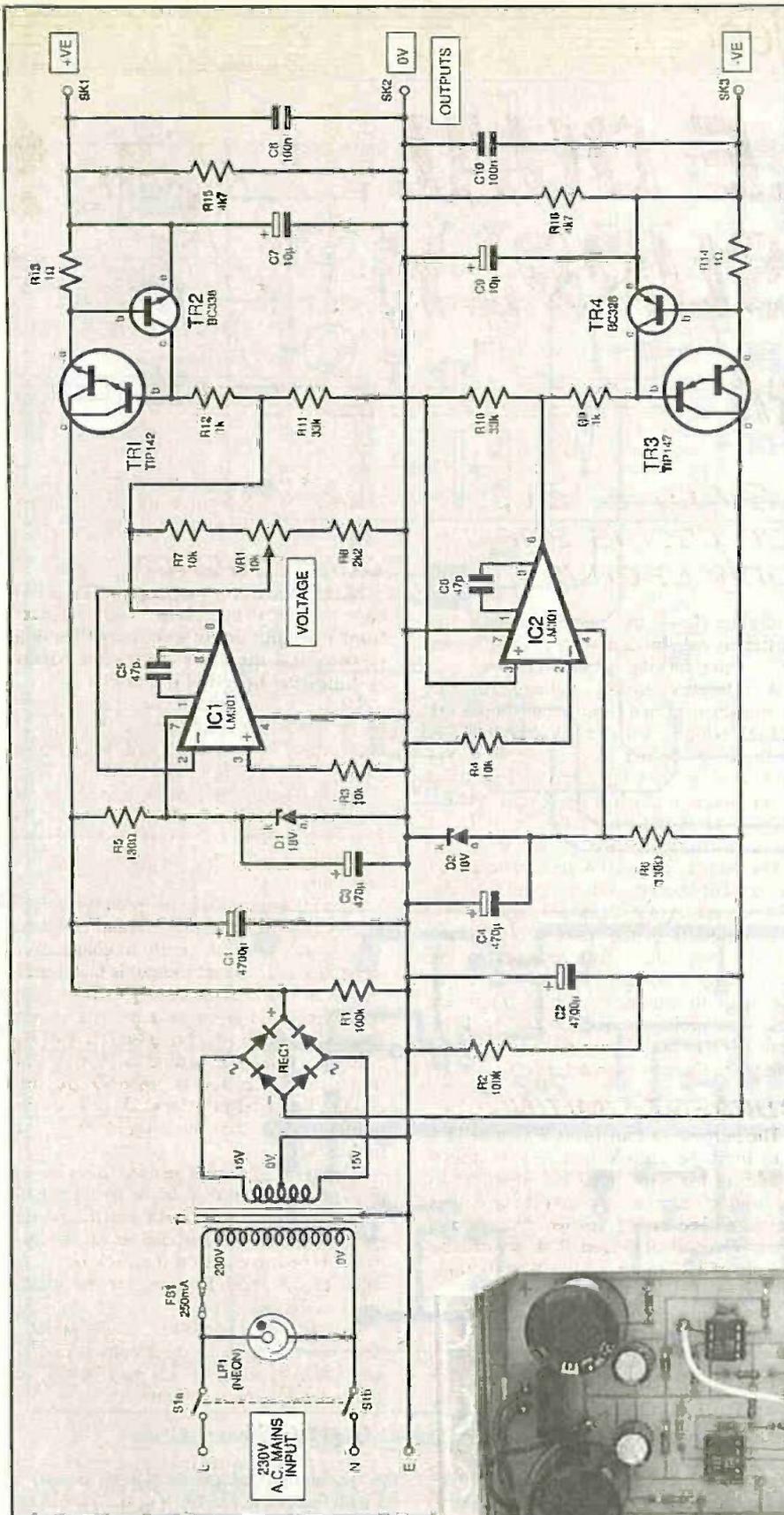


Fig.1. Complete circuit diagram for the Variable Dual Power Supply.

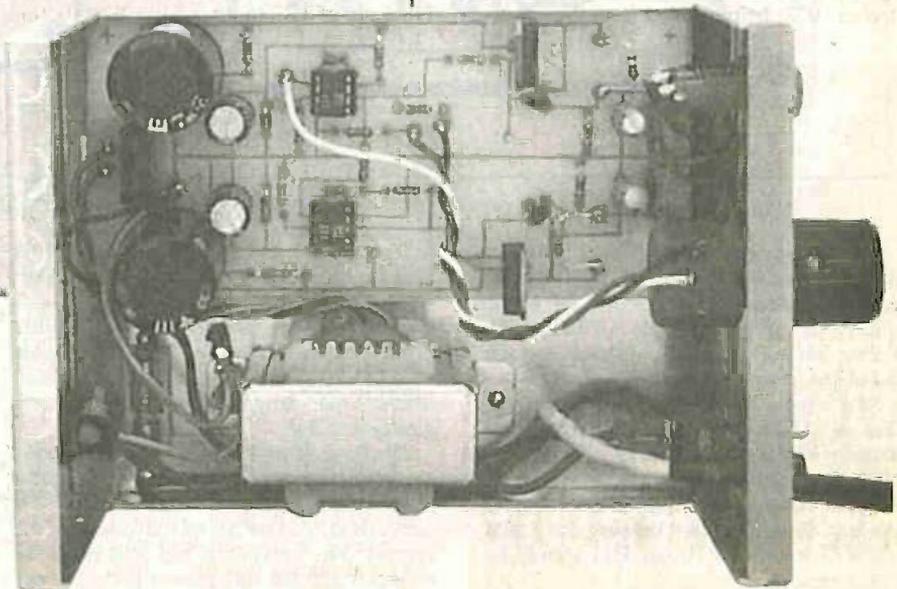When all the connections to the board from the control panel have been completed and checked, and the mains cable fitted, the unit is ready for testing. Connect a voltmeter, set to a range of about 20V d.c., across the positive output and 0V, and switch on the power supply.



COMPONENTS

Resistors
 R1, R2 100k (2 off)
 R3, R4, R7 10k (3 off)
 R5, R6 130Ω (2 off)
 R8 2k2
 R9, R12 1k (2 off)
 R10, R11 33k 1% (see text) (2 off)
 R13, R14 1Ω 0.6W (2 off)
 R15, R16 4k7 (2 off)
 All 0.25W 5% carbon film unless stated.

See
**SHOP
 TALK**
 page

Potentiometer
 VR1 10k wirewound

Capacitors
 C1, C2 4700µ radial elect. 35V (2 off)
 C3, C4 470µ radial elect. 25V (2 off)
 C5, C6 47p ceramic (2 off)
 C7, C9 10µ radial elect. 25V (2 off)
 C8, C10 100n ceramic (2 off)

Semiconductors
 TR1 TIP142 npn Darlington transistor
 TR2 BC338 npn transistor
 TR3 TIP147 pnp Darlington transistor
 TR4 BC328 pnp transistor
 IC1, IC2 LM301 op.amp (2 off)

Miscellaneous
 FS1 250mA fuse, anti-surge, 20mm
 LP1 mains rated neon lamp; panel mounting
 REC1 bridge rectifier, 50V 1A (in-line pins)
 S1 s.p.s.t. mains rated toggle switch
 SK1 to SK3 4mm single socket (see text) (3 off)
 T1 mains transformer, 15V-0-15V sec, 500mA

Printed circuit board, available from the EPE PCB Service, code 242; metal case, size to suit; cable clamp; 20mm panel mounting fuseholder; knob; printed circuit board supports, self-adhesive (4 off); plastic insulating sheet (see text); connecting wire; solder, etc.

Approx. Cost
 Guidance Only

£31
 excluding case

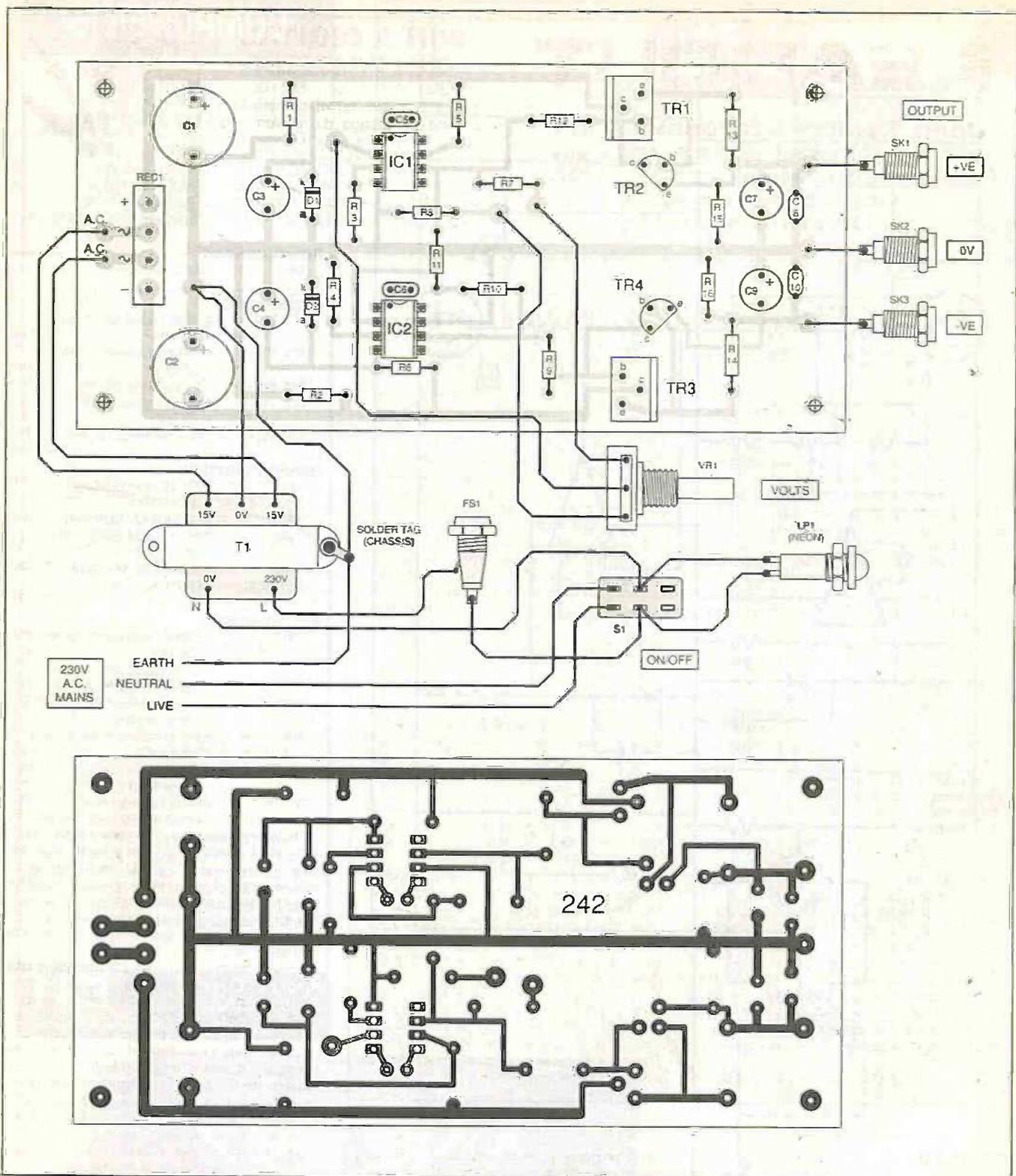


Fig.2. Component layout and full size copper foil master track pattern, plus off-board connection details.

The minimum setting (fully counter-clockwise) of potentiometer VR1 should result in reading of about 3V (2.8V in the prototype). If about 15V is indicated, reverse the outer connecting leads at each end of the potentiometer track.

Now check the negative voltage output. This should (inversely) match the positive output within a few millivolts. Component tolerances will inevitably have some effect here, but the outputs should track together sensibly. Should this not happen, the actual values of resistors R10 and R11 should be re-examined.

If all is well, and assuming that a built-in panel meter is not being used, the Voltage scale for VR1 may now be marked. Use as large a knob as possible with a pointer printed on, so that an easily readable scale may be drawn. Set the control at minimum rotation and, using a water-based pen, mark a reference dot.

Using your multimeter across the positive output, note this voltage at the minimum scale setting. Do similarly at 1V intervals around the arc of movement of the control. The maximum end will get a bit cramped and for this reason perhaps only

the "standard" voltages need to be annotated with figures, at 5V, 6V, 9V, 12V and 15V positions.

A spirit-based pen can now be used to draw small freehand lines to indicate all points at 1V intervals. Next remove the knob and the potentiometer, and gently rub the water-based dots away with a moist cloth.

Now apply rub-down figures, burnish and lacquer. The control potentiometer can then be refitted, setting the knob to the start mark, with the control fully counter-clockwise. The power supply is now ready for use. □

READOUT

John Becker addresses some of the general points readers have raised. Have you anything interesting to say? Drop us a line!

WIN A DIGITAL MULTIMETER

The DMT-1010 is a 3½ digit pocket-sized I.c.d. multimeter which measures a.c. and d.c. voltage, d.c. current and resistance. It can also test diodes and bipolar transistors.

Every month we will give a DMT-1010 Digital Multimeter to the author of the best *Readout* letter.



★ LETTER OF THE MONTH ★

OUT OF AFRICA

Dear EPE,
I have been an avid follower of your magazine for many years under its various titles. Unfortunately, coming from the Third World country of Zimbabwe I could not always get it, what with import restrictions and currency devaluations. Whenever I could get my hands on a copy (old or new) I read it from cover to cover, absorbing all the informative articles and drooling over the supplies available from your advertisers.

However, now that I am resident in England, a subscription to your magazine was top of my birthday wishes list, and thanks to my wonderful wife, I am now a proud subscriber to *EPE*.

Unfortunately I missed out on a large chunk of your publication and am therefore not up-to-date with the new technology which features prominently in *EPE* these days. My main concern is for PIC technology, what does PIC stand for? Programming is obviously involved, is this through a PC? If so what programs and hardware are needed?

Thanks to *EPE*, I have built and fitted two car alarms to my wife's vehicle and pitrié in Zimbabwe. They were invaluable there as car theft is rife and not once did we have a problem. I also built an amplifier for my mother-in-law who is rather deaf and could not hear the TV without it being turned up so loud as to annoy everyone around. The amplifier plugged into the A.V. audio output on the TV and fed a pair of headphones. All this being achieved with a lot of patience and only an analogue multimeter for testing.

Thank you for an excellent magazine. By the way, novelty circuits such as your *Musical Sundial* (June '99) are always welcome.

P.S. What did the resistor sing when it fell onto the multimeter's dial? *an ohm, ohm on the range!*

Brian Cornish, Ringwood, Hants

We are delighted to hear from you and welcome you as a full-time reader!

The word PIC in this context is a proprietary term owned by Arizona Microchip and used to describe their range of microcontrollers. It probably stands for Programmable In-Circuit microcontroller, although we cannot confirm this. Note that there are other devices which have the prefix PIC as part of their identity coding, but these should not be confused with the Microchip PICs.

Your best low-cost initial route into understanding PIC microcontrollers is through my PIC Tutorial series of March to May 1998. We have run out of back issues for this, but photocopies of the three parts are available, as stated on our Back Issue page. If funds permit, a more sophisticated approach can be taken via our PICtutor CD-ROM; see our CD-ROMs for Electronics pages.

We are surprised that you experienced import restrictions over EPE. We have a number of readers in Zimbabwe who subscribe and regularly renew their subscription. Currency valuation we have no control over, but in UK terms taking out a subscription is an economically viable way of ensuring you receive EPE each month (and here begins the "Sponsor's Message"). Subscription details are always printed on the Editorial page, and order forms are published from time-to-time (but you do not need to use a form - any sheet of paper will do, or use any other of the multitude of ways in which you can communicate with us.)

Another way in which you can obtain EPE, of course, is through our Internet EPE Online site at <http://www.epemag.com>. (Commercial Break now over!)

Brian, we can't think of anything to comment on your 'ohmly joke, let alone cap it, so we won't try! We wish you continued success with your designing (and Mother-in-Law)! Hope you find your multimeter reward a good addition to your tools range.

RACEY WIRELESS MONITOR

Dear EPE,
Hello from New Zealand. I'm involved in dirt track Stock Car racing, and we have been having problems lap scoring 25+ cars round the track. Then seeing your Feb '99 issue on the *Wireless Monitoring System* I have a few questions:

1. Can the transmitters send up to 300 different identity codes continuously and for how long? i.e. one per car that comes each race night, and up to five hours before recharging.

2. Can the receiver pick up 25+ different I.D. codes in order, which will pass by at 100km/hour, to allow the PC to display the cars' order over the finish line. 1st/2nd/3rd/etc?

3. How many receivers can a PC monitor? i.e. can we place 10+ around so we can plot the cars' progress around the track?

Frank Korver, New Zealand, via the Net

We passed Frank's E-mail on to the designer, James Humphris, for his comments. He replies:

1. The transmitters presently are limited to 255 different identifying codes i.e. encoded by an 8-bit binary word. However, with an alteration to the source and destination software, this could be increased to 16 bits fairly easily (i.e. 65535 codes).

2. This is the tricky one! Firstly each receiver can only pick up a transmission from a single transmitter at once. This is because all transmitters operate on the same frequency and as such any simultaneous transmissions are ignored (fully explained in the article). This being the case, let's assume that under the conditions of operation, a useful range of 10m can be achieved. Let's also assume that the cars pass the transmitter half-way so we have an effective range of 20m. Let's also assume that the transmission begins as soon as the car enters this useful range.

Each transmission from each transmitter takes 330ms, so each car needs to be in the effective range for at least this time. 100km/h equates to 100,000m/3600s = 27.7m/s, or approximately 28m/s. So, in 330ms, the car would travel 28 × 0.33 = 9.24m. Considering these constraints, theoretically it would be possible to register cars passing the finishing line as long as they were separated by at least 10m, otherwise all information would be lost. The other point is, you would have to ensure that all transmissions began at a specific point. I don't know how you would achieve this.

The transmitter-to-receiver link has only ever been tested in a fairly static environment, i.e. walking pace only, so the effect of 100km/h motion has not been investigated. Possibly a better idea would be to put receivers in the cars, and a single transmitter continuously transmitting. However, the accuracy of this idea would have to be investigated.

The other point is that most modern motor cars are fully EMI compliant, and I don't know if stock cars would be as such. What I mean is that the RFI from the ignition system may well interfere with the r.f. between transmitter and receiver. Have you considered an optical system instead? This could be far more accurate.

3. The receiver can monitor an infinite number of different transmitters as long as all transmissions are independent in time (explained in the article).

James Humphris, via the Net

OU AGAIN

Dear EPE,
Can I add to your answer to Matthew Stuart re TV programs about electronics. The BBC2 programmes (not programs by the way!) post-midnight are called *The Learning Zone* and although much is, not all the content is produced by the OU (Open University), for example *Science in Action*.

Many years ago I asked an OU presenter why they didn't give more publicity to their output as this might encourage more people to think about taking an OU course. His reply was that the programmes weren't designed for the casual viewer and the OU wasn't in the entertainment business! I would hope this attitude has changed but don't bother to contact OU because there's a far easier way.

If Matthew gets in touch with BBC Education Information he can register, as I did a couple of years ago, to receive a free quarterly guide listing

every programme under separate categories e.g. Computing, Maths and Number, Music, History etc. along with VIDEOplus+ numbers. Contact info: Tel: 08700 100222. CEEFAX: Pages 630-636. Web: www.bbc.co.uk/education/zone.

Hope this helps Matthew find what he wants. By the way, there is an OU maths programme called *Modelling Turkeys* which, if it is ever shown, is a wonderful demo using a logarithmic scale to produce a linear graph of turkey weight vs. cooking time. This is followed by more serious applications of the principles which I have made use of from time to time as an electronics hobbyist.

Barry Taylor, via the Net

Thank you Barry, yes the Learning Zone is TV well-worth watching and caters for many interests. You do need (usually) to get up a bit early or stay up late to watch them (I still don't trust preset video recording timers!).

PIC TOOLKIT V2.2

Last month in *Readout*, I answered a letter from Dave Buck whose PIC programming problem had been caused by his "illegally" using the TAB key when writing .ASM code for use with PIC Toolkit Mk2. We had thought it was general knowledge that when writing in TASM grammar, text formatting control keys were not allowed to be used. It is a point very strongly emphasised in our PIC Tutorial (*Mar-May '98*), and on the PICtutor CD-ROM. Erroneously, I had believed DOS EDIT (which is my preferred/suggested text editor) to be free of text formatting control commands, and overlooked the potential threat of the TAB key being used.

As it happens, Dave was not the only one who used the TAB key instead of spaces, a few other readers reported assembly problems which turned out to be caused by inclusion of the TAB control character (ASCII 9). From Toolkit's point of view, it was looking for space characters (ASCII 32) from which to make decisions about which columns the program code statements should belong - Labels in column 1, action commands column 2, source/destination column 3, etc. Whereas on-screen TABbed commands look like spaces, Toolkit was seeing ASCII 9 instead of 32, and so overlooking the desired column splits. The result was chaos! Virtually every single command line could thus cause an error situation because things were not where they should be!

However, whilst I could have been hard-hearted and simply left it that text format commands are not allowed with Toolkit, and that this restriction included ASCII 9 from DOS EDIT, I succumbed to yet another challenge - to allow Toolkit Mk2 to accept TABs. This it now does and the revised software version, PIC Toolkit Mk2 V2.2, has become the version on our Internet FTP site and on the Toolkit disk available from the Editorial office (as detailed on the EPE PCB Service page).

The files have the same names as the original V2.0 versions, and should be copied to your directories to replace the existing files of the same name. Readers loading the Toolkit software for the first time need not concern themselves with this matter, the original V2.0 files have been replaced by V2.2 on the disk and FTP site.

Interestingly, Dave's original .ASM file that he had sent, also showed up a few other matters which I had not anticipated. He was inserting a space immediately following the comma in bit-related command statements. Toolkit looks for commas in this situation and treats them as another column separator, but because it also uses the spaces as column delineators, the intended bit source/destination that followed the comma was being overlooked. Version V2.2 now allows a single space (but no more than one space otherwise you'll have an assembly problem) following the comma in bit-related commands. However, you do not need to use a space, the bit statement can immediately follow the comma.

Additionally, another matter not expected was Dave's occasional use of hexadecimal values to indicate bit values. Toolkit V2.0 was seeing a non-decimal value (in this case a statement preceded by a \$ sign) and was thus thinking that it should now look for an equated (.EQU) value of the same form as listed with the other specified equates - and not finding one, reporting this an error situation. This has been rectified in V2.2, and hex values may now be used to specify bit values.

As a point of my own making, when extensive-ly using the Send Message to EEPROM routine in connection with another design being worked on, I regretted not having allowed comments to be added on the same line as the message data. The Message routine has now been amended in V2.2 to allow this to be done (preceded by a semicolon, of course).

Dave's just E-mailed "Thanks for the revised program files, I've got them up and working and it's 100%".

PERPETUAL CALENDAR

Dear EPE,

Re the letter from Lloyd Kirk in *Readout* of August '99, using my Sinclair microdrive cartridge Calendar program provides evidence that the calendar of 1972 is the same as that for the year 2000.

R.L.A. Latham, Weeping Cross, Stafford

Many thanks Mr Latham for kindly sending printouts which prove the truth of Lloya Kirk's suggestion. The calendars included on my several PCs also confirm this and, moreover, that $1972 = 2000 = 2028 = 2056 = 2084 = \dots$? On this short timescale, it seems that the calendar repeats every 28 years. However, on a much greater timescale does anyone know if this continues ad infinitum, or do extra leap days at strategic intervals upset the cyclic uniformity?

As a spin-off from this question, I have found that while my computers are supposed to be Millennium Compliant (as confirmed by a message box on start-up), they are not Millennium 2.1 Compliant! That is, the calendar baulks at going beyond 2099, and reverts back to 1970!

So what? some of you might exclaim, believing that it won't affect you or most of us around now. Ah, but wasn't similar thinking in earlier years partly responsible for us having a Millennium Bug problem now? Shall our descendants inherit a Y2K1 Bug from us?

DIY PCB PRINTS

Dear EPE,

I have been a very keen follower of *Practical Electronics*, *Everyday Electronics* and *Everyday Practical Electronics* for the past 30-odd years or so, going back to the early 1960s and have built many of your projects over the years. By studying your projects, and in particular the circuits of *Ingenuity Unlimited*, I have been inspired to investigate and build all sorts of novel and useful devices. I have derived much pleasure in trying many different ways of producing my own p.c.b.s, they have normally been successful although I have not always been totally satisfied with the result.

In the past few years, I have obtained several inexpensive computers, gradually working my way up to a PC. In each case I have attempted to produce (with the aid of a drawing program) printed circuits resembling professional quality. Recently, with the use of the PC and a decent printer, I felt I could be getting close to reaching my final goal, but when I come to print out the results of my work on acetate film to produce a negative, I find that the ink seems to refuse to dry and is very pale, could you suggest a special ink for this purpose?

Another idea I might suggest is, would it not be possible to print out a circuit design onto a backing sheet with some special etch resistant ink, so as to be able to iron the image directly onto plain copper laminated board, therefore doing away with the need for expensive resist-coated board and also the production of an inter-negative, similar to the production of T-shirt motifs. Awaiting with interest any comments you may make in a forthcoming magazine.

N. Dyson, Glossop, Derbys SK13 8EP

Even in the days when I was professionally manufacturing p.c.b.s, I used positive resist-coated material for prototypes, and continue to do so. However, I never did fully solve the problem of achieving 100 per cent quality when using a dot-matrix printer (with inked ribbon) as the image producer.

Since acquiring an ink-jet printer however, I now obtain perfect images when printing onto acetate drafting film (to the "coarser" side). These images are suitable for use directly with photoresist board and a UV exposure unit.

Yes, there is an iron-on material available from some major component suppliers. It's called Press-n-Peel, but I have never used it and cannot comment on its effectiveness.

WELL WEATHERED

Dear EPE,

Referring to *Readout* of August '99 and your question about other reader's projects from past years, I wish to share my experience with two EPE projects that I have constructed.

After reading the *Weather Station* of Feb-Apr '90, I started constructing it and finished all the circuits in August '90 and installed it on my roof that same month. From then on, it has worked continuously with accurate readings and has seen wind strengths of Force 9, and still it goes well.

The other is the *Digital Car Tachometer* of June '91. After I had prepared the circuit and a metal box for it, I removed the dashboard of my Fiat 127 car, to place the i.e.d.s and the 8-digit display near the speedometer. I fitted everything in place and it is still working fine. Also, it survived a head-on collision that I had with another car five years ago. I rearranged the components and the metal box and after a while it was working as new on my repaired car.

I am very proud of the above projects. As a result I always refer your magazine to other people as it gives me what I want, and the know-how to continue in the hobby.

Would it be possible for the author of the *Weather* project to design additional circuits that can be added to it so that I can connect the data signals to a computer for logging the parameters, showing the readout out on the monitor, while still using the original display? This idea has been in my mind for years now, but I have not mastered design techniques yet.

I want this extra facility so that I can utilise my old 8086 or 386 computer. Also, I wish to have an audible signal from the anemometer, adjustable to sound a buzzer when Force 3 or Force 5 is in effect, using a switch to select the wind force alarm.

Joseph Vella, Pieta, Malta

We are no longer in contact with the author of the *Weather Station* and so cannot offer additional interface circuits specifically designed for it. However, you might consider the *Data Logger* of Aug/Sept '99 for monitoring the data. It can input up to eight simultaneous analogue signals, and store them as digital values for subsequent output and display on a computer screen.

Taking a quick look at the original *Wind Speed* circuit (Fig.8 Feb '90), it seems that you might be able to tap the rotation pulse signal at the output of IC1 and feed it into an AND or NAND gate additionally controlled by the signal line connected to one of the bargraph i.e.d.s. The output from the gate could then be fed via a suitable resistor and capacitor to the input of any ordinary amplifier of any size, even a simple amplifier module such as are sold by various of our advertisers. You could use a switch to select which bargraph output is the gating source.

Great to know of the "impact" that the Tachometer has had with you!

PIC ROUTINES

Dear EPE,

Over the past year or two I have become very familiar with the use of the PIC16C84 and have designed several projects around it. However, I feel a series which discusses programming techniques on an algorithmic level would be very useful. I am sure that most people find trawling through someone else's source code extremely tedious.

A series on subjects such as encoding, decoding, pulse width measurement, serial data transfer etc., would be beneficial and a logical follow-up to your PIC Tutorial series.

Richard Cox, via the Net

A very useful suggestion Richard, which we are investigating.

Prices include VAT
and free delivery (UK only)

Vann Draper Electronics Ltd

Unit 5, Premier Works, Canal St, South Wigston, Leicester LE18 2PL
Tel 0116 277 1400 Fax 0116 2773945
E-mail sales@vanndraper.co.uk Home page www.vanndraper.co.uk

Valid until
31st Oct 1999

EPE reader offers

SL30

Soldering station £31.03 £65.00



- Digital readout of set & actual temp
- Powerful 24V 48W iron
- Adjustable between 160°C to 480°C
- Earthed tip for static sensitivity
- Includes base station, iron and tip
- Spare tip 0.8, 1.6, 3.2mm £1.65 ea

APPA201

Bench multimeter £129.83 £99.00



- 3.5 digit back lit display
- Auto & manual ranging
- Battery & mains operation
- AC/DC voltage & current
- Resistance to 20Mohm
- Diode & continuity test
- Carrying strap & tilt stand

SG4160B

Rf signal gen £151.58 £99.00



- 0.1-150MHz (450MHz 3rd H)
- 100mV output (no load)
- Output high/low switch
- Int mod 1kHz (AM) 30%
- Ext mod 50Hz-20kHz
- Crystal checker facility
- 115/230Vac 50/60-Hz

H6000

10MHz function gen £198.58 £149.00



- 0.1Hz-10MHz range
- Sine, square & triangle
- 50ohm output
- TTL output
- 20mVpp to 20V pp o/p
- 0, -20, -40dB o/p control
- Ext freq mod/sweep

305LDD

Power supply £178.08 £139.00



- 0-30V 5A output
- Twin LCD displays
- Coarse & fine adjustment
- Short circuit protection
- Audible & visual over current alarm
- Ripple <10mV
- Optional service manual £15.00

MX450

Multimeter £41.13 £29.00



- AC and DC voltage
- AC and DC current to 20A
- Resistance to 20Mohm
- Capacitance to 20µF
- Diode, Hfe & continuity test
- 10Mohm input
- Includes holster & test leads

AG2601

1MHz Audio gen £151.58 £99.00



- 10Hz-1MHz in 5 ranges
- Sine and square outputs
- 600ohm output impedance
- 0, -20, -40dB output control
- Sync input
- Distortion <0.05%
- 115/230Vac 50/60 Hz

DT830B

Multimeter £12.56 £8.00



- AC & DC volts
- DC current to 10A
- Transistor test
- Diode test
- Basic accuracy 0.5%
- Incl. probes & battery
- Soft carry case £3.50

Full technical data sheets for all products are available as hard copies either by post or from our web site at www.vanndraper.co.uk and all equipment is supplied ready to use complete with operating manuals, accessories, mains leads and a 12-month guarantee.

Ex-demonstration units of Grundig equipment are also available. These are unmarked, in virtually new condition and have mostly only been used once for exhibitions/demonstrations. All models include accessories and a 12-month guarantee. prices as follows:

MO30	30MHz 2ch oscilloscope	£499.38	£369.00	RF1000	Rf millivoltmeter	£527.58	£359.00
UZ2400	2.4GHz frequency counter	£386.58	£275.00	FG100	20MHz function generator	£581.63	£429.00
RLC100	LCR meter	£445.33	£325.00	DM100	4.5 digit bench multimeter	£515.83	£369.00

Use this coupon for your order

or phone, fax or E-mail quoting S311099

Name Address Tel No

Model	Description	Quantity	Price each	Total

Cheques payable to Vann Draper Electronics Ltd, or debit my Visa, Mastercard or Switch:

Card No Exp date Switch Iss No Signature

POWER GENERATION FROM PIPELINES TO PYLONS



ALAN WINSTANLEY

Part Two

Supported by the expertise of the international power generation company National Power plc, Alan describes some of the high technology involved in generating power – from a gas pipeline to the turbines and generators and then to the electricity pylon and beyond!

WE CONCLUDE our in-depth look at power generation by examining some of the techniques related to the provision of a 230V a.c. supply to our housing and industry.

Power to the People

Let us return to the process of electrical power generation and examine it in greater detail. Previously it was mentioned that each of the three gas turbines in our adopted power station drives an a.c. generator; a steam turbine drives a fourth.

A power generator consists of an electromagnet (*rotor*) which is rotated directly by the turbine shaft. Each revolution of the turbine turns over the generator once. The rotor is surrounded by stator coils in which the moving rotor induces a voltage that will ultimately be delivered to the consumer.

Power Spin

If a simple two-pole rotor is used, this could be likened to a simple electromagnet

having a North and a South Pole. The spinning electromagnet induces a voltage in the stator coils each time it passes by, and the stator voltage will therefore reverse polarity with every half-revolution of the rotor. The voltage level generated in the stator coil depends on how far the rotor has travelled during one revolution (its rotational angle).

How a sinewave is generated with this setup is depicted in Fig.9. Because it delivers alternating voltage, this generator is more correctly called an *alternator*. (A *dynamo* produces a d.c. voltage instead.)

To get the most out of each revolution of the rotor, several stator coils are deployed so that multiple sine wave voltages are generated per revolution. In fact, three coils are spaced at 120 degrees apart (see Fig. 10) and the coils are designated by a colour code which will be familiar to every electrician: they are Red, Yellow and Blue. The generator windings produce 15.75kV between the phases.¹

The overall result can be plotted as a three-phase voltage, see Fig. 11. It can be seen that the voltage in the red phase is 120 degrees behind the yellow phase, which lags 120 degrees behind the blue phase.

By increasing the rotor's speed, the frequency can be increased, although the three phases will always be 120 degrees apart. This simplified approach assumes that there is only one pair of magnetic poles on the spinning rotor as shown, and this is normally the case in practice.

If the rotor spins once per second, then the a.c. voltage generated in each phase will have a frequency of one Hertz (Hz).

¹ For reasons which will be clarified later, it is usual in the power industry to talk of "line voltages" as phase-to-phase voltages, rather than the voltage which is generated in a single-phase circuit with respect to a "common" or "earth" reference. In a three-phase generator, the voltage which is generated in an individual phase is 9.1kV, which is $15.75kV/\sqrt{3}$. This produces 15.75kV between phases. ARW.

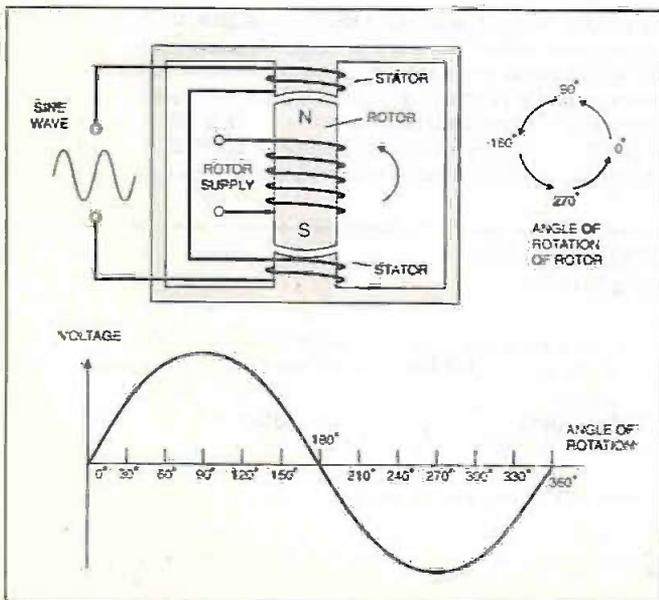


Fig.9. A sinewave is produced in the stator coil by the spinning rotor. The voltage level depends on the rotor's angle of rotation, and it reverses polarity every 180 degrees.

Fig.10 (right). A three-phase generator has three fixed stator windings, placed 120 degrees apart around a spinning rotor, which itself is an electromagnet, having a North and South pole.

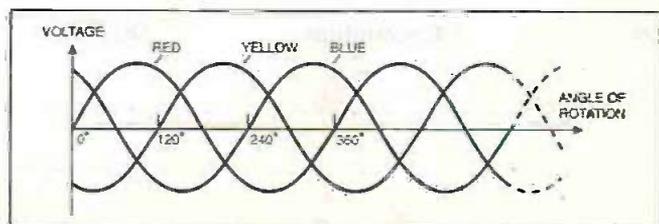
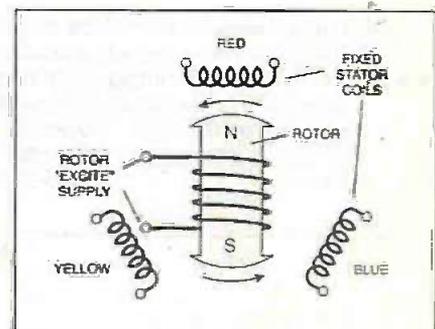


Fig.11. Three-phase electricity generated by the alternator of Fig.10. The three phases are 120 degrees apart.

changing polarity every half second. The frequency of the generated voltage is calculated by:

$$\text{frequency} = \frac{\text{no. of pairs of poles} \times \text{revs. per minute}}{60}$$

From the above formula, a generator with one pair of poles as illustrated must rotate at 3,000r.p.m. to produce electricity at 50 Hertz, which is the *declared system frequency*. The statutory limits defined in the Electricity Supply Regulations of 1937 are 50Hz. \pm 1% (i.e. 49.5 – 50.5Hz) although the National Grid (NGC) strives for a variation of no more than 0.1% as best practice. The turbines operate at this speed, 24 hours a day for months on end.

In the mid 1920's before electrical power generation was standardised, several frequencies could be used – anything from what was probably a migraine-inducing 25Hz and must have been murder to read by, all the way up to 80Hz. The Electricity Supply Act of 1926 resulted in a standardisation of supply frequency across Great Britain, at 50Hz, although in the USA and some other countries the supply has been set at 60Hz.

In fact most generators tend to have two poles although certain types e.g. hydro-electric generators may have four or more poles. This allows for a slower rotor speed of 1,500 r.p.m for a four-pole machine which is more appropriate for the medium involved, whilst still generating a 50Hz sinewave.

Frequency Control

The actual method of controlling the supply frequency ultimately boils down to speeding up or slowing down all the generators on the system, by increasing or decreasing their load.

Great effort is made to maintain this value and to eliminate cumulative errors in the consumer's supply, which might otherwise affect electric clocks, time switches, audio equipment etc. Any minor change in frequency is compensated for later on, in order to enable frequency-sensitive equipment to catch up (or slow down).

All power plants interconnected by the National Grid can be considered as part of an enormous "pool" of electricity hooked together on an "infinite busbar", which runs at a set frequency.



A circuit breaker unit connected to the gas turbine. Notice the colour coding "spots".

Every power station thus connected operates at this frequency. If at this time a small isolated power station was *not* connected to the busbar, but was then hooked in later, the frequency of the existing "pool" would easily dominate the generator of the newly-connected power plant. The net result is that *all parts of an interconnected system operate at the same frequency*.

The operating frequency of the rest of the grid is thus physically applied to an individual generator, in what is effectively a contest of wills. Since a generator's stator is synchronised to its rotor (and turbine shaft), it is necessary to ensure that a gas turbine runs at a speed which enables the generator's frequency to be matched to the rest of the grid. Hence, the challenge is to supply just enough fuel to the turbines so that the generator runs at the prevailing system frequency adopted by the rest of the grid.

Any increase in the fuel supply will *not* necessarily cause the turbine to run any faster, because the generator is already synchronised or locked to the frequency of the grid: instead the turbine will simply be "loaded", which is undesirable. The system frequency can be best controlled by ensuring that the generator's MW output constantly matches the consumer MW (megawatts) demand.

Test Run

The best analogy of this is to consider a car which is being driven at a fixed speed. If the car encounters a hill it will slow

down, making it necessary to open the throttle to maintain engine speed. If the hill levels out, the throttle can be closed again. If it goes downhill, the engine can be used as a brake to slow the car.

The other key parameter is, of course, *voltage*. For consumers, the statutory limits on their 230V supply is \pm 6%. Unlike the system frequency, the voltage levels can vary in different parts of the transmission system. The voltage output of a generator is directly related to the rotor voltage – the excitation voltage, which is controlled by a complex automatic voltage regulation (AVR) system. Every aspect of the generator and the turbine's performance is constantly monitored by the power plant's fully computerised control room.

Down-the-Line

The next part of the electricity generation process relates to the way in which the power generated in the stator coils is transmitted to the user. Typically, the generator outputs 15-75kV and is rated for more than two hundred megawatts (MW).

The three phases – red, yellow and blue – are carried outdoors from the generator by cables using large ducts which resemble pipelines. These pipes are pressurised in order to prevent corrosion or water ingress. The ducts are also colour coded to identify the phases, and this same theme is used all the way through to the end-user's premises.

One major problem is, how to actually switch such high magnitudes of voltage?

Leaps and Volts

All of the high voltage areas at National Power's Killingholme "A" station – just like every other high voltage installation – are surrounded by a perimeter fence or wall. Such areas are padlocked and it is *strictly forbidden* to enter the area – even to pick a weed – without the relevant safety permit.

Although much of the equipment is safely earthed, many high tension wires and terminals are of necessity uninsulated. *High voltages can flash over and strike a human being with deadly effect if they stray too close to high voltage power lines, transformers or other electrical equipment.*

For high voltage operations, the industry-standard minimum safe working distances are:

400kV	3.1 metres	66kV	1.0 metres
275kV	2.4 metres	33kV	0.8 metres
132kV	1.4 metres		

Remember that the human body is a walking 3 kilohm resistor and is effectively grounded at one end. If a person unwittingly encroaches within the safe working distance then there is a very serious risk of arcing and flashing over. That person may suffer devastating electrical

burns as well as risking death. There may also be an explosion and fire.

It would be impossible for anyone to rescue a person from such a dire predicament because of the same risks *they* would face from arcing by the same high voltages, so any attempt to mount a rescue near to high voltages would be *highly dangerous*.

If you should see a person next to high voltage power lines or equipment whom you suspect may have suffered electrocution or burns, there is nothing you can do except stay a safe distance away and call for help. All rescue attempts must be left to the experts who will insist on making the area safe before entering it. (The separate box-out "Heartfelt Shock" is a timely reminder of emergency first aid procedure which can be undertaken for persons who may have received a shock from the domestic 230V supply.)

Every year many people lose their lives by electrocution purely through carelessness and ignorance. Children must never be permitted to play anywhere near an electricity substation, and must never attempt to retrieve, say, a lost ball from within a fenced-off substation compound.

Playing near overhead power lines (including electric train overhead wires) should also be strongly discouraged, so the flying of kites and model aircraft in these areas is exceedingly dangerous.

The dangers of death caused by flashing over are very real and are ignored literally at one's peril.

Since these extremely high potential voltages can arc across considerable distances (see the box out entitled "Leaps and Volts"), one can imagine the nightmarish problems which exist in the power plant when trying to switch thousands of volts.

The switchgear concerned must be able to withstand not only their full loads but six-fold overloads which occur when motors are starting. They must also be capable of carrying or interrupting fault currents and must also cope with 17,500 volts peak across the contact terminals. Evidently, we are not talking 6mm (1/4in.) toggle switches here!

The solution lies in the use of special gas-filled circuit breakers. These are spring-loaded and motor driven and are designed to quench the high tension arc which develops between opening contacts. The compound sulphur hexafluoride (SF₆) is used and this is six times less conductive than air. Earlier types used oil-filled contacts or compressed air to snuff out the arc.

The 15-75kV (phase-to-phase) generator voltages are stepped up to 400kV by an external transformer – one per generator – for onwards transmission to the National Grid.

Stay Cool

Many readers will be aware that large transformers are oil-cooled in order to aid heat dissipation. With the largest types, the oil will be circulated by pumps and heat will be exchanged with a water-filled coolant circuit.

In the event of a transformer internal failure (e.g. winding shorts, or contacts starting to burn out), hydrogen is one of the

first gases to be produced, so by testing for this gas any trends can be spotted early. A device known as a Buchholz relay is used as an automatic switch that responds to increasing levels of gas build-up in the oil.

More accurate tests of oil samples are also undertaken by National Power and other gases such as acetylene can be measured over, say, a month and a good estimate made of the nature of an internal fault. Ultimately the oil can be drained and then the fault can be repaired.

Also worthy of mention is a small digital counter near to the transformer's perimeter steel fence. It displayed "20": when this was queried, the author was cheerfully told that this meant the transformer had been hit by lightning twenty times... Er, quite.


Quite a Buzz

A compound area called the "banking compound" adjacent to the main power transformers contains an array of insulators and busbar isolating switches. Usually, when Killingholme "A" is in full swing, the crackle of high tension voltages fills the air around this bus-bar area. The same compound contains current transformers which monitors the station's output.

From there, the 400kV supply is fed underground to a nearby sub-station, before finding its way on to a transmission tower, the very first in a series of many hundreds which will be used to distribute the power around the countryside.

Super Grid!

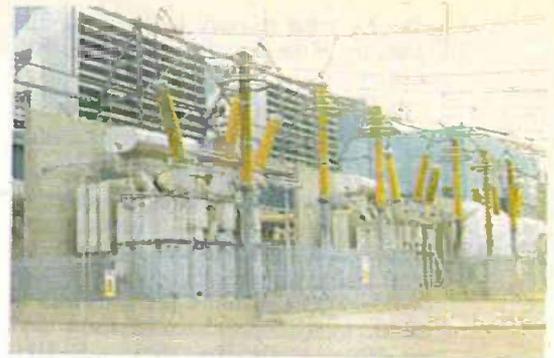The enormous 400kV supply – known as the Super Grid (275kV in certain



Four 400kV transformers connected to the outputs of the four generators.



A gas-filled circuit breaker, rated at 17.5kV 10,000A, connected to the gas turbine generator.



A Buchholz safety switch, relay is fitted on oil-cooled transformers and detects any build-up of gases in the oil.

Pylon on the Power

The electricity pylon – more correctly called a suspension or transmission tower – carries overhead three-phase electricity between substations in all weathers. Terminal towers are located at each end of the route, whilst deviation towers enable the wire route to be realigned.

These "lattice" towers are significantly more economical to construct and repair than attempting to bury high voltage insulated cables underground, and the ambient air also acts as a natural cooling system to help with heat dissipation on the wires. Larger towers provide a greater span, needing fewer towers to suspend cables over a distance, but variations in design are used depending on local conditions (e.g. aircraft or natural landscape considerations).

The largest Super Grid towers support wires operating at 400,000V. Fibre optical cables are wrapped around many cables to carry Internet traffic: the light signals are unaffected by the high voltages. The smaller towers seen in the countryside or near towns and villages are usually owned by the Regional Electricity Companies (RECs) rather than the National Grid.

Power cables are uninsulated and usually made of aluminium alloy, which is lighter than comparable conductors so that slimmer, smaller towers can be used. The towers are inherently earthed, and an individual earth conductor wire can often be seen connecting the tops of towers together.


To ensure that the high voltage cable and the earthed tower are separated from each other, chains of porcelain or toughened glass insulators are used. A 132kV wire might use just nine insulators, whilst a

400kV Super Grid power line may demand twin chains of 24 insulators. Atmospheric pollution is another factor which determines how many insulators are needed, because fall-out from industry and salts in the atmosphere can degrade the insulating effect.


Each insulator is actually a capacitor having metal end caps separated by the dielectric material of the insulator. This produces

a series of air-spaced capacitors between the metal caps and the tower, resulting in an uneven distribution of voltages across the insulators. Hence the power line voltage will be unevenly dropped across the capacitances, but the one nearest the power cable could operate near its maximum voltage breakdown limit.

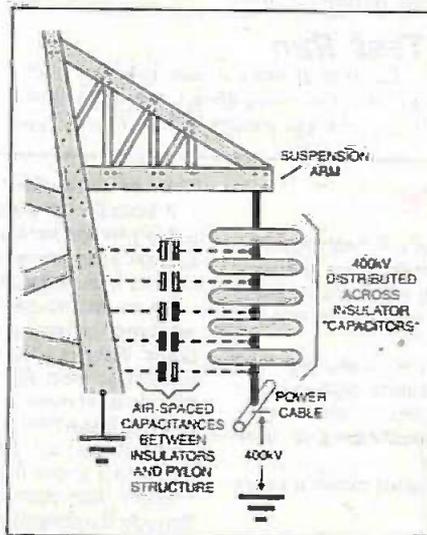The addition of a guard ring helps relieve the stress on the insulator



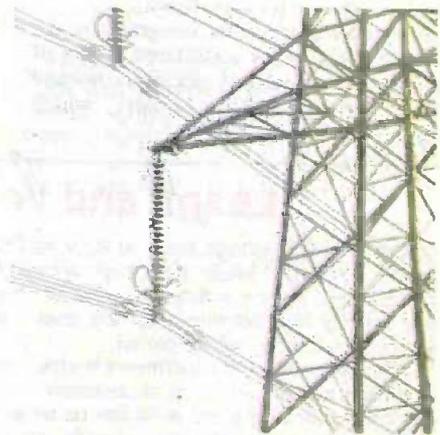Porcelain or toughened glass insulators are used in chains to prevent contact with the earthed transmission tower. The voltage on the power line is distributed across all insulators as shown; which have metal caps and therefore form capacitors.



Typical pylon insulator set-up carrying 400kV supplies. Note the guard ring nearest the cable.

dielectrics nearest the power cable by shunting their capacitance, and it also ensures that any possible flashover is diverted away from the insulator surfaces to prevent damage, see diagram. Insulators have a undulating cross section to increase their surface area, useful in wet weather.

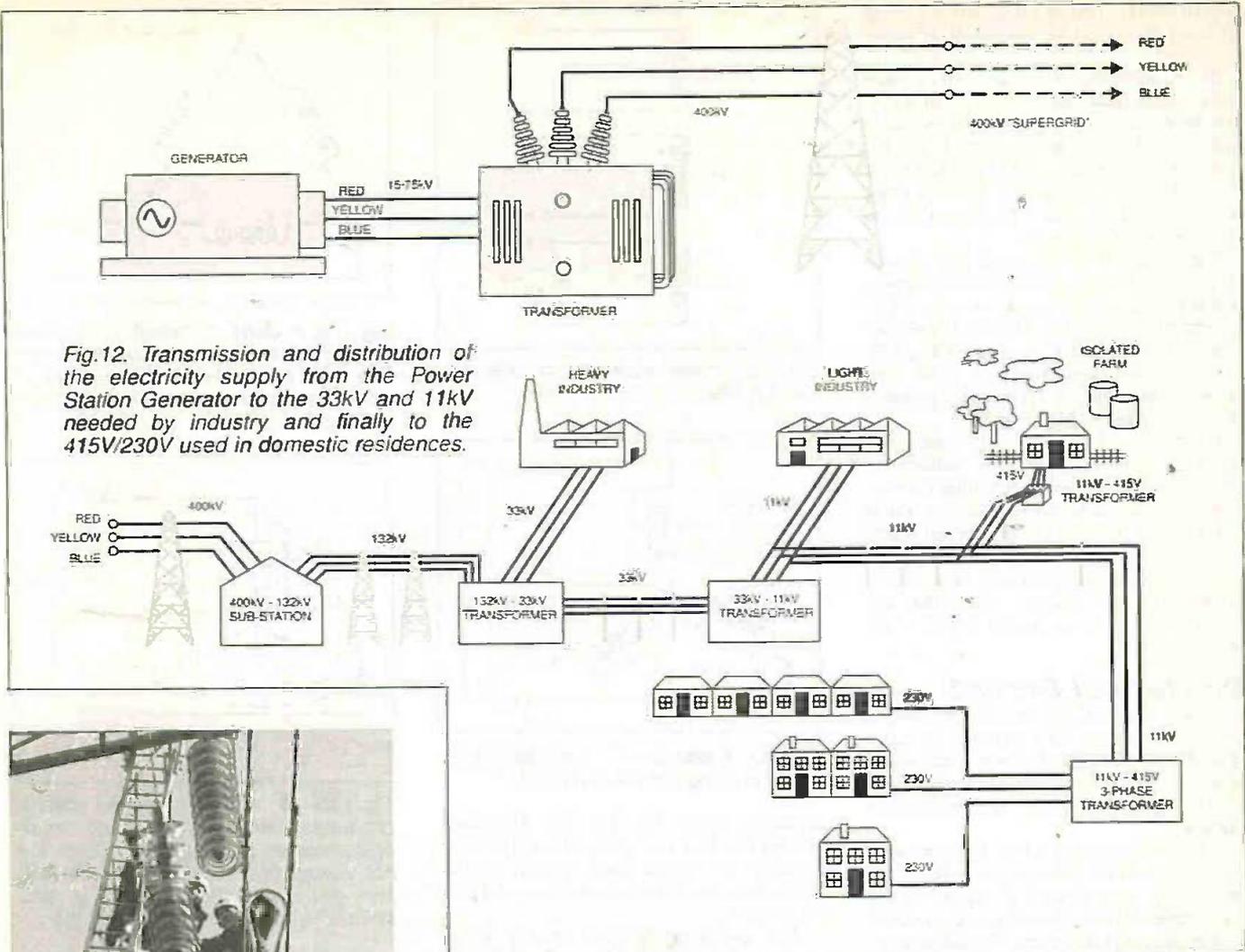


Fig.12. Transmission and distribution of the electricity supply from the Power Station Generator to the 33kV and 11kV needed by industry and finally to the 415V/230V used in domestic residences.



National Grid engineers installing glass insulators on an overhead cable.

regions) will be found hanging off the largest of pylons (as a general rule, the larger the pylon, and the bigger the insulators, then the higher the voltage being carried). The same pylons also carry Super Grid voltages generated by neighbouring power stations.

If ever one wondered why there are three arms to each side of a pylon, the answer is suddenly blindingly obvious: there is one wire per phase, with each tower usually carrying two circuits. Sometimes, wires may be paralleled, which will be witnessed by two wires running next to each other to share the load. (See the separate box out, "Pylon on the Power".)

These extremely high voltages are transmitted over considerable distances to regional sub-stations, where they are progressively stepped down by transformers (auto transformers are usually used on the Super Grid). Outline structure of the electricity distribution system is shown in Fig.12.

The Super Grid is first reduced to a 132kV grid system and then to 33kV for use by industrial estates and heavy industries. Light industries may require an 11kV supply which is provided by a sub-station. The final reduction occurs in


residential areas, where the 11kV is stepped down to three-phase 415V from which single phase 230V a.c. is produced, as we shall see later.

(Officially, UK domestic supplies have been "harmonised" at 230V a.c. for reasons best understood by the European Union. In reality, UK supplies are 240V a.c. just as they always have been, evidenced by taking a quick measurement of 243V!).

In many cases, the customer (say, a farm in a remote locality) will have his own 11kV-to-415V step-down transformer and these are a common site in the English countryside, perched on top of a wooden pole. It is the job of the Regional Electricity Boards to distribute power to commercial and residential properties, and sub-stations with suitable step-down transformers will be used as appropriate. From Fig.12 it can be seen how the Super Grid voltage is systematically stepped-down as the end users' locality is approached.

More on Three-Phase

The red, yellow and blue colour code of the 3-phase system applies from the generator outputs of Killingholme "A" all the way through to the 415V transformer found by residential properties. One could be forgiven for thinking that the use of three very large stator coils to generate three-phase power would demand six wires to conduct the current, as shown in Fig. 13a, noting the direction of each winding (or the start/end of the coil) is denoted with a spot symbol.

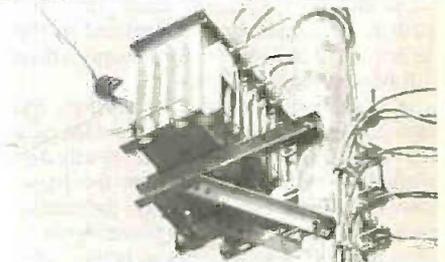

A typical 3-phase transformer, mounted on a wooden pole. It has an 11kV primary and a 415V secondary, from which 230V a.c. is produced.

After all, a single-phase load requires two supply wires to power it: normally known as Live (or "hot") and Neutral, though the live is more correctly called the *Line* voltage.

However, a three-phase system is able to transmit three times the power of a single phase design without the need for six wires, simply by arranging the windings as shown in Fig. 13b. The start of one winding is connected to the end of another, and the three connections are brought out as shown. Because of its shape, this "triangular" configuration is known as a delta (or mesh) connection. Three wires can be used to transmit a three-phase supply in this way.

The alternative arrangement of windings shown in Fig. 14a is called a star connection (or Y connection), and the central connection is called the "star point" (or the

neutral point). This is used universally by National Power on the output of all of its generators.

By commoning the "starts" of each phase together as shown, a four wire-system (three "line" voltages or phases, and a neutral conductor) can be created. The net current flowing into or out of the star point is zero because each phase uses the other two for its return path. The net voltage is also zero at the star point.

The principles of delta and star circuits are relevant throughout the power transmission network, all the way down to the 230V a.c. supply delivered to a home. In the case of a three-phase 415V supply, see Fig. 14b, a step-down transformer is used (not shown) which has a 11kV delta primary and a star-wired 415V secondary.

Therefore, 415V is supplied between any two lines as shown. A voltage of $415V/\sqrt{3} = 240V$ will be developed across a "load" placed between the star point and a single phase. This is precisely how a domestic 230V is derived -- connected to the star/neutral point and any of the (nominally) 415V phases. (Note that our "230V" supply is in reality 240V -- see previous page.)

On Neutral Ground

Having outlined the overall process of power generation, let's explore in more depth further aspects of power distribution which will be familiar to us all: the need for a neutral wire, and also the requirement for earthing.

In order to provide a 230V domestic supply from a 415V three-phase supply, the "live" 230V wire is taken from one of the transformer's 415V phases and the neutral is taken from the star point. The star or neutral point is also physically connected to the earth at the transformer, as depicted by the earth symbol in Fig. 14b, for reasons which will become apparent later.

In a typical residential installation, the three 230V supplies which are provided by a 415V three-phase transformer are evenly distributed to balance the load on the transformer. This is achieved by, say, connecting every third house to the same phase. A whole street of small 2 to 3 bedroom houses may have one phase whilst a small development of much larger houses -- which will demand more power -- might use a different phase to try to balance the loading, and so on.

A significant side effect of this arrangement is that neighbouring premises, whilst each enjoying a 230V supply, may endure a potential of 415V between their respective live supplies: it can be seen in Fig. 14b how 415V exists between any two phases or lines. For this reason, the 230V "live" of one residence should never be used in neighbouring installations because they might not share the same phase.

Each house drawn in Fig. 15 is connected to one of the 3-phase "lines", and the diagram shows how all three houses have their neutral wires commoned together to the star/neutral point of the 415V supply transformer. That same star point is also connected to the earth.

Quite how an individual house will be connected in practice depends on several factors, but assuming that an underground supply is taken to the property, then usually a 230V supply will be routed there using an

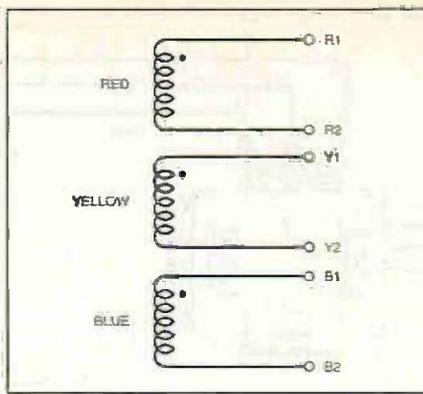


Fig. 13a. Three separate phases require a total of six connections.

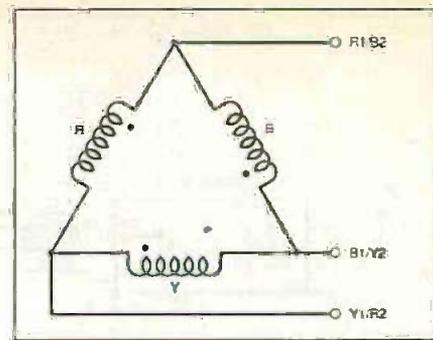


Fig. 13b. A delta or "mesh" connection for a 3-phase supply dispenses with the need for six wires. The net sum of voltages around the delta configuration is zero.

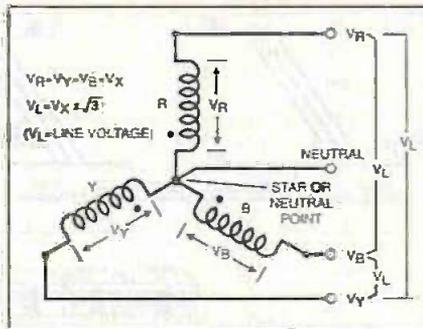


Fig. 14a. A star (or "Y") connection with the star being the neutral point.


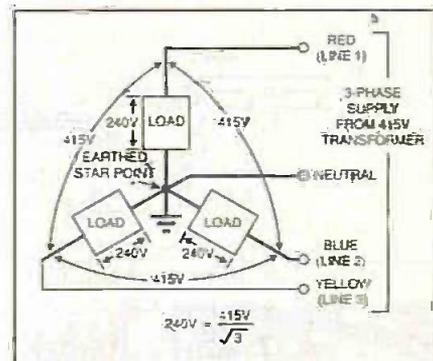



Fig. 14b. A 415V 3-phase voltage produces 240V across each "load" connected to the star point. Since the net voltage is zero in the 3-phase system, the star point is neutral, or zero volts. It is connected to the ground.

armoured cable, see Fig. 16. The steel armour is wired as a "protective earth" and connects the house earth system to the earthed star/neutral point of the local 415V transformer.

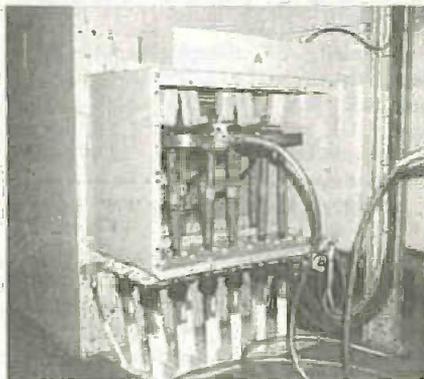This completes a good quality metal earthing connection between the domestic earth system and the star/neutral point of the 415V transformer. All exposed domestic



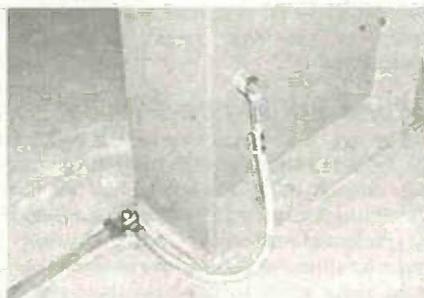
Exposed equipment with safety earth wires fitted during maintenance.




How all exposed steel framework is soundly interconnected with copper bars and also earthed.

copper water pipes and other metal work which could possibly become live through a fault, are hardwired together by "equipotential bonding", which ensures that no individual route to earth will be more resistant to a fault current than any other.

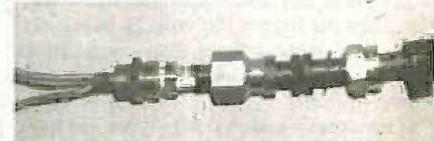Incidentally, the consumer's neutral may also be directly connected to an earth stake at their incoming supply, but usually this only occurs if the existing earth connection path is found to be inadequate, or if no



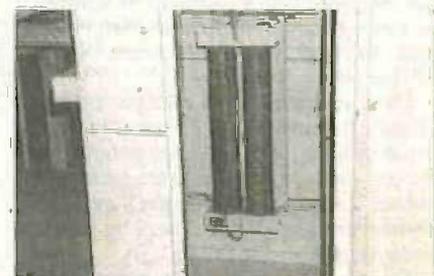A typical armoured-cable terminator, note the steel armour which is the "protective earth".



The "neutral resistor" is designed to limit fault currents in the generator. It connects between the star point and earth.

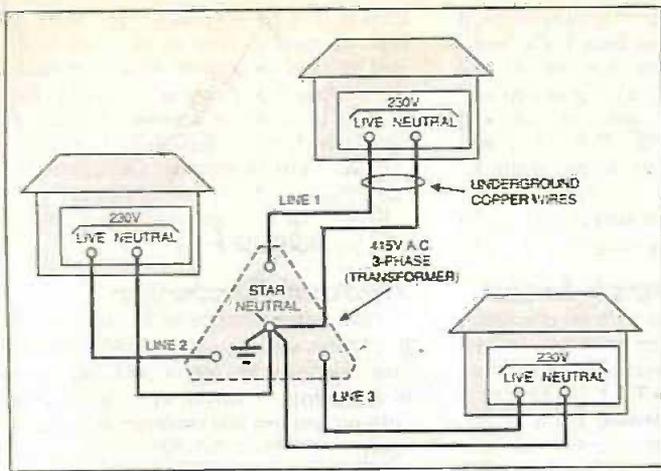


Fig. 15. How a 415V 3-phase system is utilised to distribute 230V to the end user. Each "house" uses one phase in order to balance the loading on the substation (ref. Fig. 14b).

earth has been provided at all by the electricity supply authority. There are other variations on house wiring as defined in the *IEE Regulations* with which a competent electrician will be familiar, and who should be consulted if individual doubts exist. In the case of overhead domestic supplies, the earth terminal of the property might only be connected to earth but not to neutral.

Getting Down to Earth

We have now shown how a 230V a.c. supply is derived from a 3-phase 415V transformer, noting also that a consumer's neutral wire connects to the transformer's star/neutral point. A separate "protective" earth (the steel armour of the underground cable) runs between the consumer's earth terminal and the (earthed) star point of the transformer as well. What is the point of all this "earthing"?

It is widely understood that the need for "earthing" (or "grounding" in the USA/Canada) is a safety measure designed to prevent electric shock due to wiring faults or insulation breakdowns. More accurately, earthing is used as a method of ensuring that no open or exposed metal-

work can accidentally become "live" should an internal insulation fault arise. This aspect is now examined in greater detail, and it's useful to start (courtesy of National Power) by seeing what happens in our adopted power station, Killingholme "A", before we look at the situation in a domestic residence.

In the field of electricity generation any voltages expressed are always understood to be *between phases* rather than with respect to earth or "ground". A 415V three-phase supply has 415V *between phases*, not between a phase and ground (between which, 230V a.c. exists). Recall how a 9.1kV generator coil produces 15.75kV between phases, and it is this latter voltage which everyone talks about.

However, the ground or earth plays a fundamental safety-related role. Remembering that the power generator's output takes the form of a star connection, the star point has a net voltage and current of zero. In practice, the generator's star point is connected to earth via a "neutral" resistor.

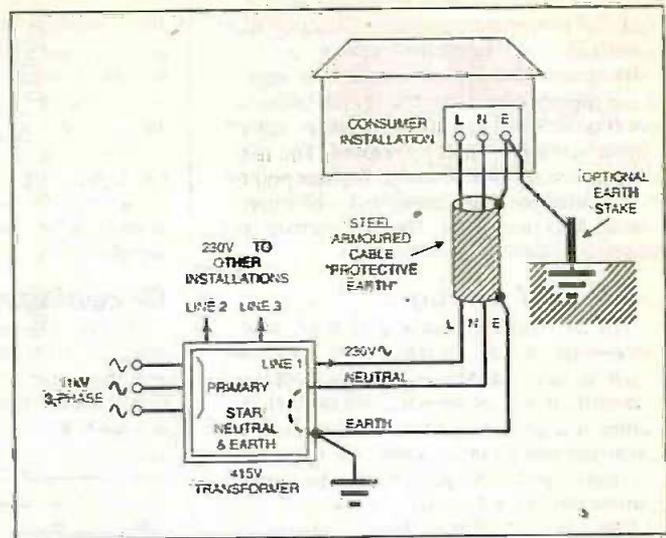


Fig. 16. How an earth connection is routed through to a consumer installation. The steel armoured cable ensures a good earth continuity between the installation and the transformer star/neutral earth. It is connected via a brass cable gland which terminates the cable.

In the case of the generators used at Killingholme "A", this resistor fills a metal cabinet (see photo), but in older plants the resistor can actually be in liquid form, made from a tankful of potash and capable of handling kilo-amperes of current. However, it should be realised that the *only currents which ever flow to earth are fault currents*.

All exposed metal work, instrument racking, chassis, cabinets and even the metal girders of the power station's buildings are heavily interconnected with straps and bonding wires and also physically connected to the earth. This "ring of steel" ties all of the open metalwork together to form the escape route down which fault currents can flow. It means also that all earthed parts are at the same potential – zero or very nearly so.

If any fault develops in the generator – such as a failure in insulation – then if any part of the exposed metal work becomes "live" there will be an immediate short to

Heartfelt Shock and First Aid

THE HUMAN BODY is a water-filled resistor of approximately 3 kilohms value, and is a good conductor of electricity. Since one side of the mains power supply is grounded, then it is possible to receive fatal electric shocks if your body comes into contact with high voltages – the body will complete a circuit and current will flow through the body back to earth.

The human heart is a muscle which happens to be most susceptible to stimulation at a frequency of 50Hz. Perversely, this is also the frequency of the UK mains supply.

The effects of shock depend on the level of current which flows from a device (and where it flows through the body). Once a certain threshold is reached, you will have no control over the actions of muscles, which means that you may be unable to release your grip on a device and may suffer electrocution.

A list of effects which would arise if you grasped a "live" apparatus or wire is as follows:

1mA	Tingling
9mA	Probably still able to release the device
16mA	Borderline on ability to release the device
20mA	Unable to release the device
16mA to 50mA	Pain, possible unconsciousness. Heart and respiratory functions probably continue.
> 100mA	Heart tremor, asphyxia due to respiratory paralysis. Severe shock and burns. Possible death.

Burns are caused when current passes through the skin tissue, and because of their penetrating action, electric burns can be much

deeper than their size might suggest. Extremely serious burns can result from contact with high voltage power lines.

First Aid

In the event of a person receiving a suspected electric shock from the domestic mains supply, you should act quickly and calmly to help the victim, without exposing yourself to the same risk of electrocution.

- Avoid touching the victim if he or she may still be in contact with the mains. Switch off and unplug, or use an insulating wooden pole or wooden chair to push the victim clear of the supply.
- If the victim has stopped breathing, you should apply artificial respiration immediately.
- Then treat burns immediately. Relieve pain and reduce tissue damage by cooling the affected area with plenty of clean cold running water, or apply ice, frozen produce etc.
- Remove any items of a constrictive nature (rings, watchstraps, bracelets) before swelling starts.
- Apply a sterile dressing for protection from infection. Do not apply lotions, creams or ointments nor prick blisters.
- Seek medical attention.

No attempt should be made to help victims of high voltage electrocution unless it is certified that the power source has been completely isolated. See the section "Leaps and Volts" for more information.

earth, because the star point is connected to earth as well. The neutral resistor will limit the current and prevent a serious failure.

Although a fault current will now flow, this will be detected by earth fault relays, current transformers, circuit breakers or other devices. In the case of a major generator fault, the neutral resistor is capable of withstanding many tens of amperes for five seconds, at a potential of some 10kV or more.

Ground Force

In the simple example of Fig.17, a generator phase has shorted to an imaginary steel girder, one end of which is connected to earth. It will be seen that the neutral limiting resistor now forms the load for the winding and a fault current will flow down to earth and through the resistor, which limits the current.

In his several days on-site at Killingholme "A", the author saw countless examples of all kinds of earth straps and leads which are designed to ensure high tension fault currents find their way directly to earth. It clearly makes a great deal of sense to make it easy for fault currents to flow through a massive conductor - the ground - and trip a circuit breaker in the process to disconnect the supply. A similar form of protection is used in the home.

Remembering that the power station also

uses electricity itself for its own systems, it is interesting to note that even if the worst happened and power was lost entirely, the power station has a Battery Room containing several very large banks of lead-acid accumulators which offer 48V, 110V and 220V d.c., sufficient to power auxiliary equipment for many hours. Safety regulations (danger caused by sparks) prevented any photography in this area.

Greetings, Earth Links

We can draw parallels with the preceding principles to examine the need for earthing at a domestic or commercial installation. The "neutral" wire of a 230V a.c. supply is provided by the star/neutral point of the transformer and is therefore always close to zero volts with respect to the incoming "live". The star/neutral point is also earthed as shown in Fig.14b and Fig.15. A separate good quality metal earth connection usually runs between the installation's earth circuit back to the transformer (e.g. to its metal body, which is also earthed).

The arrangement for domestic/commercial installations is virtually identical to that used by the power station generators to isolate failures in the insulation or other faults. If every piece of exposed non-live metal is earthed,

then it will be very easy for "escaping" fault current to flow to earth as well; it will strive to complete the circuit back to the earthed star point of the 415V transformer. In so doing, a massive current will flow which will melt an in-line fuse or operate a circuit breaker. (A separate box out "Fuses - The Race to Protect" gives a little more background to domestic circuit breakers and fuses.)

Heated Exchange

Taking the example of an ordinary electric heater (see Fig.18), its metal casing is connected to the earth terminal of the mains plug. Alternating current flows between the live and neutral wires when the heater functions normally.

If a live wire should come adrift within the heater and touch the metal cabinet, then a heavy current will flow to earth which will melt the fuse in the mains plug, thereby disconnecting the supply. Such action prevents the user from being able to touch a "live" metal cabinet and acquire a potential, because he or she could be fatally injured by the fault current flowing through the human body en route to earth.

Fuses - The Race To Protect

Fuses are the "last gasp" and sometimes the only protection found in most domestic electric appliances as well as electronic circuits. A fuse is primarily used in a mains plug-top to oversee the mains cable (power cord) and will "melt" if the cable is severed or damaged, when an excessive current could flow. The fuse is also intended to disconnect the mains supply should an insulation fault, such as a short to earth, arise within the apparatus.

Fuses are the most rudimentary type of over-current protection and rely on a wire melting to interrupt the supply. They offer little protection to human beings in preventing electric shock, other than to disconnect the supply if an overload condition (e.g. a short to earth) occurs.

Old open-type fuses found in some fuseboards contain bare wire which will melt if the rated current is exceeded. However, fuse wire can eventually start to oxidise which may cause premature failure. An HRC (High Rupture Capacity) fuse uses a sand-filled ceramic cartridge to prevent oxidation and also to extinguish the arc. These are typically found in UK mains plugs but larger versions are used in industry. Continental fuseboards use such ceramic cartridge fuses as well.

Electronic equipment often utilises a variety of glass-bodied cartridge fuses: 20mm x 5mm for up to 10A current, whilst larger 32mm (1 1/4 in.) types are produced with ratings exceeding 25A. Some types are anti-surge, meaning that they will not "nuisance trip" when equipment surges during first powered up. It is always very important that fuses are replaced with the same type, size and rating. Failure to do so may cause both a fire and an electrocution hazard.

The miniature circuit breaker (or MCB) is a resettable form of fuse or "trip switch" which will act to open the circuit when an excessive current is drawn by the load. The best form of protection though is Residual Current Device or RCD, also known as an earth leakage circuit breaker (ELCB) or Ground Fault Circuit Interrupter (GFCI) in the United States.

These devices "look for" an imbalance between the currents flowing in the live and the neutral wires. If any difference arises, any losses must be due to current leaking to earth, and an RCD will typically trip within 40ms of detecting an earth leakage current of 30mA.

Not to be confused with an MCB, a Residual Current Device offers the best personal protection against electrocution and is a wise investment when using outdoor power tools. Most RCDs now offer "double-pole" protection which disconnects both the Live and the Neutral wires to ensure total isolation, and feature a test button. Fuseboards fitted with RCDs are now quite common.

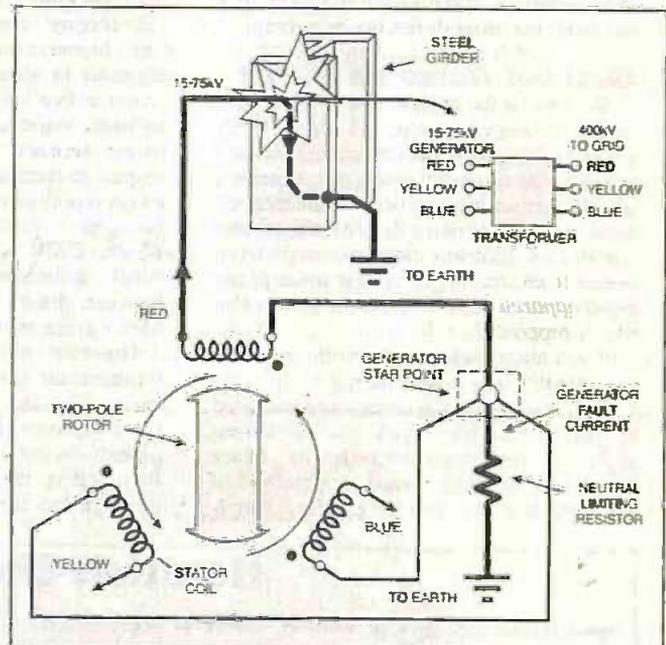


Fig.17. A "neutral" resistor connects the generator star point to the earth to limit any fault currents. Here, the Red phase has shorted to earth, via a steel girder in this simple example.

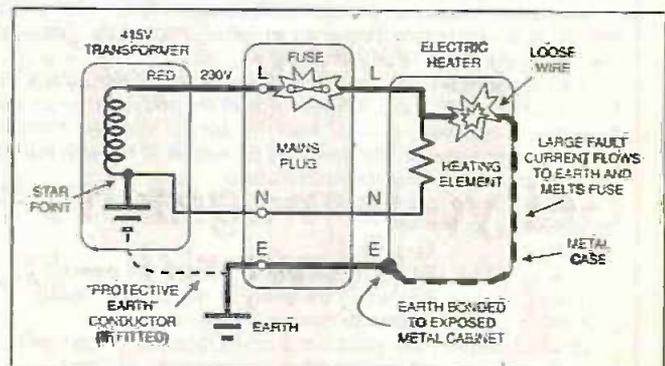


Fig.18. How earthing ensures that any insulation breakdowns will cause a fuse to melt, thereby disconnecting the supply. A large fault current flows to earth, when a loose wire shorts the 230V live wire to earth, via the earthed metalwork.

PRACTICALLY SPEAKING

Robert Penfold looks at the Techniques of Actually Doing It!

CAPACITORS must rank as just about the simplest form of electronic component, and a capacitor is basically just two metal plates with a layer of insulation in-between. The Insulating layer is called the dielectric.

Practical components are usually in the form of two strips of thin metal foil interleaved with two strips of plastic foil. The strips are rolled or folded up to produce small components that have a large plate area. This enables high values of capacitance to be condensed into small physical volumes.

Although capacitors are fundamentally quite simple, they seem to cause more confusion than all other types of component combined. Supposedly, the reason for this is that there are so many different types available. If you look in one of the larger component catalogues for a 1nF capacitor you will probably have about 15 to 20 components of this value to choose from! So how do you select the right one?

Square Pegs Into . . .

When dealing with capacitors you have to take into account the physical characteristics of the components as well as their electrical ratings. Capacitors come in a variety of shapes and sizes, and it might be impossible to fit a component into the available space on the circuit board if you do not choose carefully. Taking a 1nF capacitor as an example, they are readily available in printed circuit mounting versions with various lead spacings, axial versions, and even leadless surface mount versions.

Printed circuit mounting (pcm) capacitors are usually box-shaped components, but they are sometimes disc-like, cylindrical, or even globular in appearance. Whatever the shape, they have what are usually very short lead-out wires emanating from the same side of the component. This makes it easy to fit the capacitor onto a printed circuit board, but only if the spacing of the leads matches that of the corresponding holes in the circuit board.

With the early printed circuit mounting capacitors any attempt to manoeuvre them into a layout having the wrong lead spacing usually resulted in one of the leads breaking off. Modern capacitors of this type are much tougher, but it still pays to be very careful when dealing with the open construction type. Due care needs to be exercised when soldering them in place, since the heat from the iron tends to weaken the joints that hold the leads in position.

The types that are encased in plastic are much tougher, and can usually be manipulated into place without too much difficulty. However, this is only likely to work if you are moving up or down by 2.5mm (0.1in.). Using components having the wrong spacing gives

physically weaker results and could compromise reliability.

Axial capacitors are tube-shaped components with a leadout wire at each end, like ordinary resistors. It is sometimes possible to fit an axial component in place of a printed circuit mounting type, but it may be necessary to mount it vertically. This again gives a physically weak construction and is best avoided.

Printed circuit mounting capacitors are unlikely to fit into a layout intended for axial components. It can sometimes be achieved with the aid of soldered-on extension leads, but this type of thing gives scrappy looking results and very poor reliability. This is all right as a stop-gap solution to get a project "up and running" until the proper component can be obtained, but it is not viable as a normal construction method.

Modern component layouts tend to be quite compact, and the amount of space available for each component is usually very limited. The fact that a capacitor has the right lead spacing or the required axial case style does not necessarily mean that it will fit into the layout. Particularly with axial components and the higher value printed circuit mounting types, there are enormous variations in size.

Some capacitors have an overall length that is about the same as the lead spacing, while with others the overhang at each end is so great that they are about 50 per cent longer than the lead spacing. If space on the circuit board is limited it is advisable to check the maximum dimensions of the capacitors in the component catalogue, and to make some measurements to check that they will fit into the layout.

Foiled Again

Having found a capacitor that will fit into the layout correctly, how do you know whether or not it is suitable electrically? The components list should give some basic guidance, and for any out of the ordinary capacitors it should be specific.

In components lists and catalogues you will normally find capacitors referred to as something like "ceramic", "Mylar", or "polyester". This is the material used as the dielectric. The best dielectric depends on the application for the capacitor.

Ceramic capacitors operate well at high frequencies, but their tolerance ratings are usually quite high and their values can change quite dramatically with changes in temperature and the passage of time. Capacitors

having a plastic foil such as polyester or Mylar are generally more accurate and stable, but do not work efficiently at very high frequencies. Silvered mica (also known as just plain "mica") capacitors are used where the ultimate in stability is required, but these are only available at low values of up to about 1nF.


Letters from readers having problems with projects sometimes point out that certain capacitors they are using are not the correct type, and query whether this could be the cause of the problem. Using capacitors of the wrong type is definitely not a good idea, but it is unlikely to prevent a project from working at all.

If a filter requires expensive plastic foil capacitors having a tolerance rating of 5 per cent, but you use lower quality plastic foil or ceramic components, it will still work after a fashion. However, the filter frequency could be well away from the required figure and there could be other anomalies in the frequency response obtained.

If plastic foil capacitors are used instead of ceramic types the circuit could operate inefficiently, and in some cases there is a risk of it becoming unstable. If a radio design requires mica capacitors but inexpensive ceramic plate capacitors are used instead, the frequency coverage could be incorrect, and the tuning could drift.

In many circuits the exact type of capacitor used is not critical, but unless you know exactly what you are doing it is best to use only the specified type. If an unusual capacitor is required the components list should make this clear, and there will probably an explanatory note somewhere in the article as well.

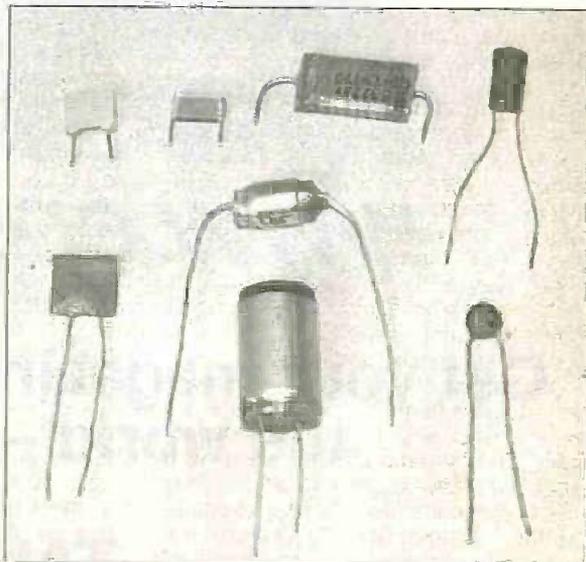For example, most capacitors can work safely at potentials of 100V or



Eight varied types of capacitor of 1 μ F or so in value. The disc ceramic one (bottom right) is physically the smallest, but has the highest value.

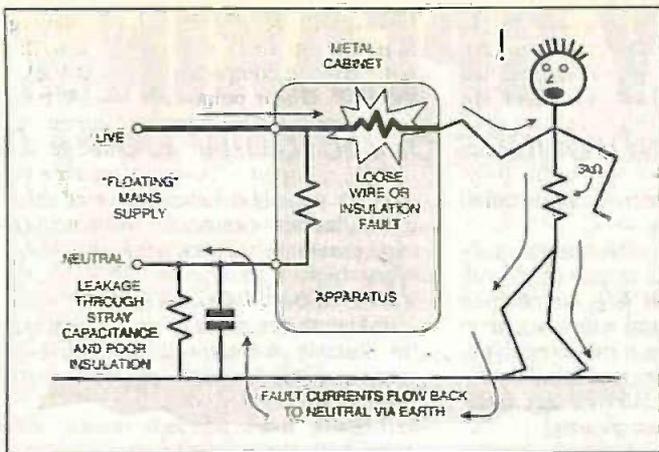


Fig.19. A "floating" (unearthed) supply can still give rise to electrocution risks caused by stray capacitance or poor insulation completing a path back to neutral. (Adapted from Guide to IEE Wiring Regulations (15th Edition) - J. F. Whitfield.)

There is a counter-argument which states that if no earth were installed, then even if a human being *did* accidentally touch a live terminal, no ill effects could arise because there would be no reason for current to flow through the body to earth. The body would merely be "floating" at the live voltage but no potential difference would exist across him or her, and no harm would be done.

Anyone who has suffered at the hands of a very cheap open-type mains transformer will know that standards of electrical insulation are sometimes less than 100 per cent, and leakage currents can occur. This means that the earth (or, say, the chassis of an apparatus) could still *not* be completely isolated from the supply even if the supply has no *apparent* direct connection to earth and is supposed to be "floating". Poor insulation allows a leakage current to flow given a suitable opportunity.

There are other ways in which the earth can form a return path for fault currents, even if the supply is supposed to be "floating". As IEE guidelines state, electrical insulation can itself be thought of as a capacitor dielectric, with the live wiring forming one "plate" and the earth forming the other.

This *stray capacitance* could form an adequate route for an a.c. fault current to pass, should a human body accidentally contact a live wire (see Fig.19). There is thus the prospect of receiving an electric shock from earth fault currents even if it is thought that the mains supply is floating and supposedly unearthed.

In Shock

Still on the subject of accidental electrocution, the human body, being full of water, is the walking equivalent of a 3 kilohm resistor and it only takes a current of 20mA to pass through a muscle to

Acknowledgements

The author is extremely grateful to those at National Power Killingholme "A" without whose assistance this article would not have succeeded in its objective of exploring the world of electricity from pipelines to pylons. Thanks again to Station Manager Keith Ulyett and Richard Power for their valuable and enthusiastic support. The National Grid PLC kindly permitted reproduction of several photos.

Several readers contributed technical information to this feature when the subject of mains earthing was raised in our *Circuit Surgery* (Oct. 1997) pages. The author is grateful to J. Goldfinch, B. J. Taylor and R. H. Ogilvie for their input.

Internet users can view the National Power PLC web site at www.national-power.com. The National Grid web site at www.ngc.co.uk offers more background information, data, real video clips and more. The web site of the Yorkshire Electricity Group at www.yeg.co.uk contains a considerable amount of material which will be of general interest to the public, teachers and youngsters.

cause uncontrollable spasms and render the body unable to release a live wire. A separate box out entitled "Heartfelt Shock" explains some things about the human body and its reaction to electric shock, and there is also some useful first aid advice to help with cases of suspected electrocution.

There are various earthing configurations permitted under the UK Institute of Electrical Engineers' Wiring Regulations, but how earthing is achieved in an installation depends on whether the incoming supply is via underground cables or from an overhead supply. Due consideration is also paid by installers to the method by which earthing has been implemented in the locality by the supply authorities.

It should be again emphasised that the domestic electricity supply should NEVER be interfered with except under expert guidance. □



Get your magazine "instantly" anywhere in the world - buy from the web.

TAKE A LOOK,
A FREE ISSUE IS AVAILABLE


more, whereas most circuits operate at 15V or less. Consequently, maximum operating voltages are not always specified in component lists because they are irrelevant. If a circuit requires a high voltage capacitor then the operating voltage will be specified, and there will probably be a warning note in the text of the article as well.

High Values

Ordinary capacitors are only available in values of up to about 1 μ F or so. Higher values tend to be rather bulky and expensive to manufacture. Many circuits do actually require higher values though, and these values are available in the form of polarised capacitors.

By far the most common form of polarised capacitor is the *electrolytic* type. Internally an electrolytic capacitor is not much different to a plastic foil type, and it mainly differs in that the dielectric is in the form of a paper like material impregnated with an electrolyte. This enables small components having values of hundreds or even thousands of microfarads to be produced at low cost.

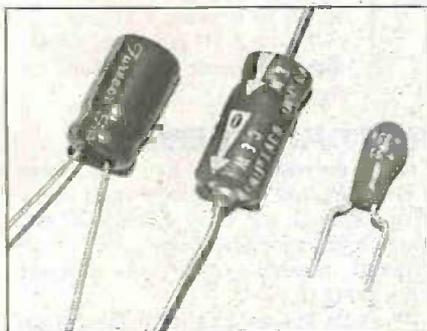Unlike ordinary capacitors, the electrolytic variety only works properly when supplied with a d.c. potential of the correct polarity. You therefore have to be careful to connect them the right way round. If an electrolytic capacitor is connected with the wrong polarity the circuit will probably fail to work and in many cases there will be a real danger



From left to right, radial electrolytic, axial electrolytic and tantalum capacitors. Although it has a value of 22 μ F, the tantalum has a maximum diameter of just 3mm.

of a high current flowing and the capacitor literally exploding.

Always be careful to fit electrolytic capacitors with the correct polarity, especially when dealing with high value components. The polarity is indicated by "+" and (or) "-" marks on the components themselves, and on the layout diagrams. With the axial versions there is also an indentation around the end of the body that has the positive leadout wire.

As pointed out previously, maximum operating voltage is not normally a consideration when dealing with capacitors. The situation is different with electrolytic capacitors though, as they often have quite low maximum voltage ratings. Component lists, therefore, usually indicate a suitable "working" voltage rating for each electrolytic capacitor.

From the electrical point of view there is no problem in using a component having a *higher* voltage rating than the one specified. Physical size is again an issue here though, and higher voltage rating normally translates into increased bulk. An electrolytic capacitor having a grossly excessive voltage rating is likely to be far too big to fit into the available space on the circuit board.

Making the Grade

There are alternatives to electrolytic capacitors, but the only common one is the tantalum variety. These are also known as "tantalum beads", due to their round and bead-like appearance.

Electrolytic capacitors provide high values in small physical volumes, but they tend to have high tolerances, high leakage currents, poor high frequency performance, and poor stability. Tantalum capacitors, on the other hand, offer much better performance, but at what is usually a much higher cost.

Like electrolytics, the tantalum variety is polarised and must be connected the right way round. Tantalum capacitors are very intolerant of polarising voltages of the wrong polarity, so be very careful to fit them the right way round.

Most component catalogues now list some superior grade electrolytic capacitors that give improved performance over "bog standard" components. If a component list specifies a tantalum component or an "improved" electrolytic type it is essential to use a high quality component here.

Sometimes an ordinary electrolytic capacitor will not work in place of a superior grade component or a tantalum capacitor. A timing circuit may fail to time-out, or a low frequency oscillator might fail to oscillate. In a less extreme case operation may be erratic, with a timing circuit producing elongated and variable delay times.

If a superior grade electrolytic is needed for a switch-mode power supply there is a risk of the circuit coming to expensive grief if a cheap electrolytic is used instead. If a high quality capacitor is specified in a component list, it has been specified for a reason.

Some polystyrene capacitors look as though they are polarised, because they have one end of the body tinted red (sometimes yellow). In some high frequency circuits it is better if the component is connected one way round or the other, and this is where it would not be a good idea to have the outer plate of the capacitor connected to a sensitive part of the circuit. These capacitors are not polarised though, and in most circuits they can be connected either way round.


Variable Capacitors

Variable capacitors are little used outside the realm of radio where they act as the tuning controls for radio receivers, signal generators, and so on. Strictly speaking a variable capacitor has two values, which are its *maximum* and *minimum* values. In practice it tends to be only the maximum value that is specified. The values available are quite low, and 500pF is the highest value you are likely to encounter.

There are two main types, which are the air-spaced and solid dielectric varieties. Air-spaced variable capacitors are the most expensive, and use air as the dielectric. There are two sets of metal vanes, one fixed and one that can be rotated via the spindle. Moving the rotating vanes into the fixed ones increases the capacitance of the component, and separating them reduces the capacitance.

It is essential to use the "kid glove" approach with air-spaced capacitors since the slightest distortion of any vane is likely to cause a short circuit at some settings of the component. Some careful straightening will usually redeem the component, but could significantly change its value.

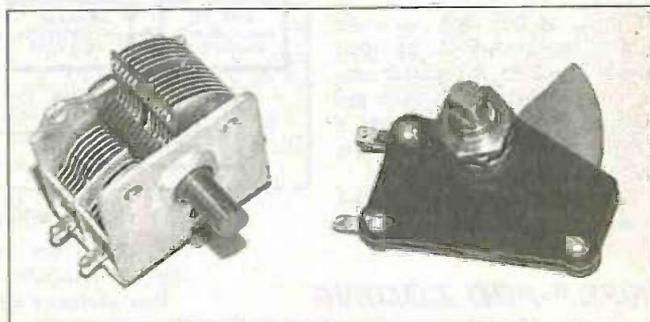Solid dielectric capacitors are much the same as air-spaced components, but have thin sheets of plastic to ensure



The fixed and moving vanes can be clearly seen on the air-spaced component (left). The variable capacitor on the right is a large solid-dielectric type.

that the two sets of vanes cannot short-circuit. This makes it possible to produce smaller and cheaper components, but with reduced stability. It is tempting to use a cheap solid dielectric variable in place of an air-spaced type, but results are likely to be poor.

Read the "fine print" before buying one of the very cheap solid dielectric variable capacitors. Some of these have very short spindles of a non-standard diameter.

There are preset versions of variable capacitors, or "trimmers" as they are often called. Some are basically just scaled down versions of variable types.

Compression trimmers are a form of solid dielectric variable capacitor, where the vanes are made from a springy metal. By adjusting a screw the vanes can be forced closer together to give increased capacitance.

Trimmers vary greatly in size and shape, and it will usually be necessary to seek out the exact component specified in the component list. Otherwise physical considerations may make the component unusable.

CHILD GUARD

TOM WEBB



Provides an audible warning if children (and others) approach a fire.

CHILD Guard is a design intended to help prevent young children from burning themselves. It does so by means of an audible warning if the child approaches a hot fire. The circuit may be used with any equipment designed to produce heat, e.g. electric, gas or coal fire.

The design produces a coded infra-red beam which detects the proximity of a person by bouncing infra-red off them as they approach, yet without being confused by other infra-red sources. A separate sensor detects the random infra-red radiation being emitted from a hot fire. If anyone approaches the fire, a warning buzzer sounds.

The block diagram in Fig.1 shows how the circuit is split up into separate sections.

INFRA-RED CODING

A system based on a *continuous* infra-red signal would not work in this application, since the receiving circuit would be heavily influenced by stray background infra-red emission from lights etc. A coded infra-red signal is better since the receiver can be set up to respond to a specific code.

There are a number of encoding and decoding devices available but two from Holtek are used for this circuit. An HT12B transmitter encodes the signal and adds a 38kHz carrier signal for greater reliability. A separate demodulating sensor detects the coded signal and provides a clean output waveform with the 38kHz carrier removed. An HT12D receiver then decodes the signal to give a steady output.

The HT12B and HT12D devices were discussed in detail in the *Reliable Infra-Red Remote Control* article in EPE October '98, to which readers are referred for more detailed information.

CIRCUIT DIAGRAM

The complete circuit diagram for the Child Guard is shown in Fig.2.

The circuit around transmitter IC6 is designed to produce the coded infra-red beam. The 455kHz oscillation frequency required by IC6 is generated across pins 15 and 16 by the ceramic resonator X1, in conjunction with resistor R15 and capacitors C6 and C7.

The HT12B allows for a binary code of between 0 and 255 to be set via its pins A0 to A7. The pins are internally biased high but any may be taken to the 0V line to set a different code. In this application, only pins A0 and A1 are connected to the 0V line.

The DOUT pin provides the coded output superimposed on a 38kHz carrier signal.

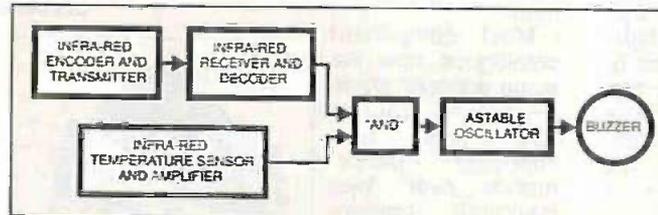


Fig.1. Block diagram for the Child Guard.

This drives the infra-red diode D5 via Darlington transistor TR3.

Potentiometer VR3 is in series with D5, allowing the transmission power to be varied. Ballast resistor R16 prevents a power supply short circuit through D5 and TR3 when VR3 is set to minimum resistance.

Infra-red detector IC4 only responds to infra-red signals that are modulated by a 38kHz carrier signal. When it detects a signal having this frequency, it outputs it to transistor TR1, via resistor R8, which inverts and supplies it to the decoder IC5.

The code to which IC5 responds is set by its pins A0 to A7. Since pins A0 and A1 on the transmitter (IC6) are connected to 0V,

the same pins on IC5 are also connected to 0V.

When IC5 receives a correctly coded signal, its pin 17 (VT) goes high. This causes transistor TR2 to conduct, which turns on the reed relay (RLA) and l.e.d. D4. The high output from IC5 pin 17 also causes capacitor C5 to charge up, to provide a delay before TR2 turns off again following the end of the signal from IC5. This ensures that the relay does not go on and off too quickly. Diode D2 prevents C5 discharging into the VT pin.


Resistor R10 sets the oscillation frequency for IC5 to the required rate of 150kHz. The value is chosen to suit a power supply of between 4.5V and 5V.

The l.e.d. D4 is used to indicate that the circuit has received the signal.

HEAT/FIRE SENSOR

When the reed relay is turned on, power is now supplied to the temperature sensor circuit through the relay contacts RLA1. Power is conserved by keeping this circuit switched off when a coded infra-red signal is not being received.

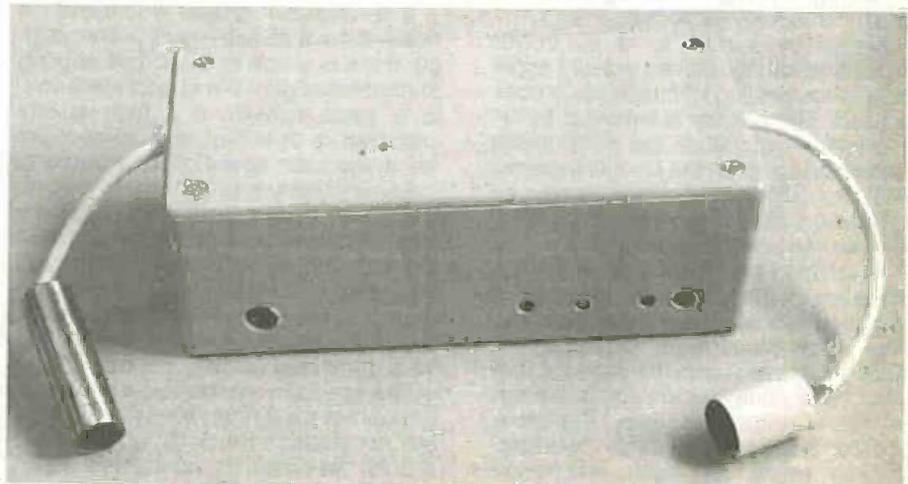Two heat sensors are used in this circuit, IC1 and IC7. They are TSL260 devices, chosen because they are sensitive to lower frequency infra-red, in the spectral range of 350nm to 1050nm, such as that radiated from hot fires. The intention of allowing for two heat sensors is in case there are two heat sources to be watched.



Completed Child Guard with two heat sensors.

The heat sensor outputs are jointly fed to the op.amp comparator stage formed around IC2a and IC2b. The bias voltage at the non-inverting input of IC2b is controlled by preset VR1, which is used to compensate for differences in d.c. output from the sensors. Preset VR2 adjusts the op.amp's gain.

The output from IC2b feeds into IC2a, which acts as an inverting comparator. When the voltage at pin 2 reaches the threshold voltage set on its pin 3 by resistors R3 and R4, the output from pin 1 switches from almost +5V to almost 0V. This triggers the astable IC3, which now starts oscillating, causing warning beeps to be output from the buzzer, WD1.

The output frequency of IC3 is set by the

components on its pins 2 and 6. Capacitor C1 charges up through a small value resistor, R5, and then discharges through a larger value resistor, R6. Diode D1 allows the capacitor to charge up quickly, bypassing R6, but discharge slowly via R6. This causes an uneven mark-space ratio so the buzzer (an "active" type) generates a short beep with a big pause, to reduce irritation to the user.

The beep length is calculated as $0.7 \times 100k\Omega \times 4.7\mu F = 0.329$ seconds. The pause length is calculated as $0.7 \times 1M\Omega \times 4.7\mu F = 3.29$ seconds.

ALTERNATIVE PIR OPTION

The use of a passive infra-red sensor

(PIR) is another option if you want the device to be triggered more easily, detecting the motion of someone moving near to it. The PIR's own normally-closed internal relay contacts are wired to transistor TR2 via resistor R11. When the PIR detects motion TR2 is turned on, activating relay, RLA and its contacts.

Note that R11 is only required if a PIR detector is fitted – if a PIR is not included it is essential to omit R11. It is assumed that the PIR contacts are normally-closed, hence TR2 is normally switched off. When the proximity of someone is detected, the contacts open and TR2 is switched on, due to the current flowing via resistors R11 and R12.

If a PIR is used, IC5 is not required (nor

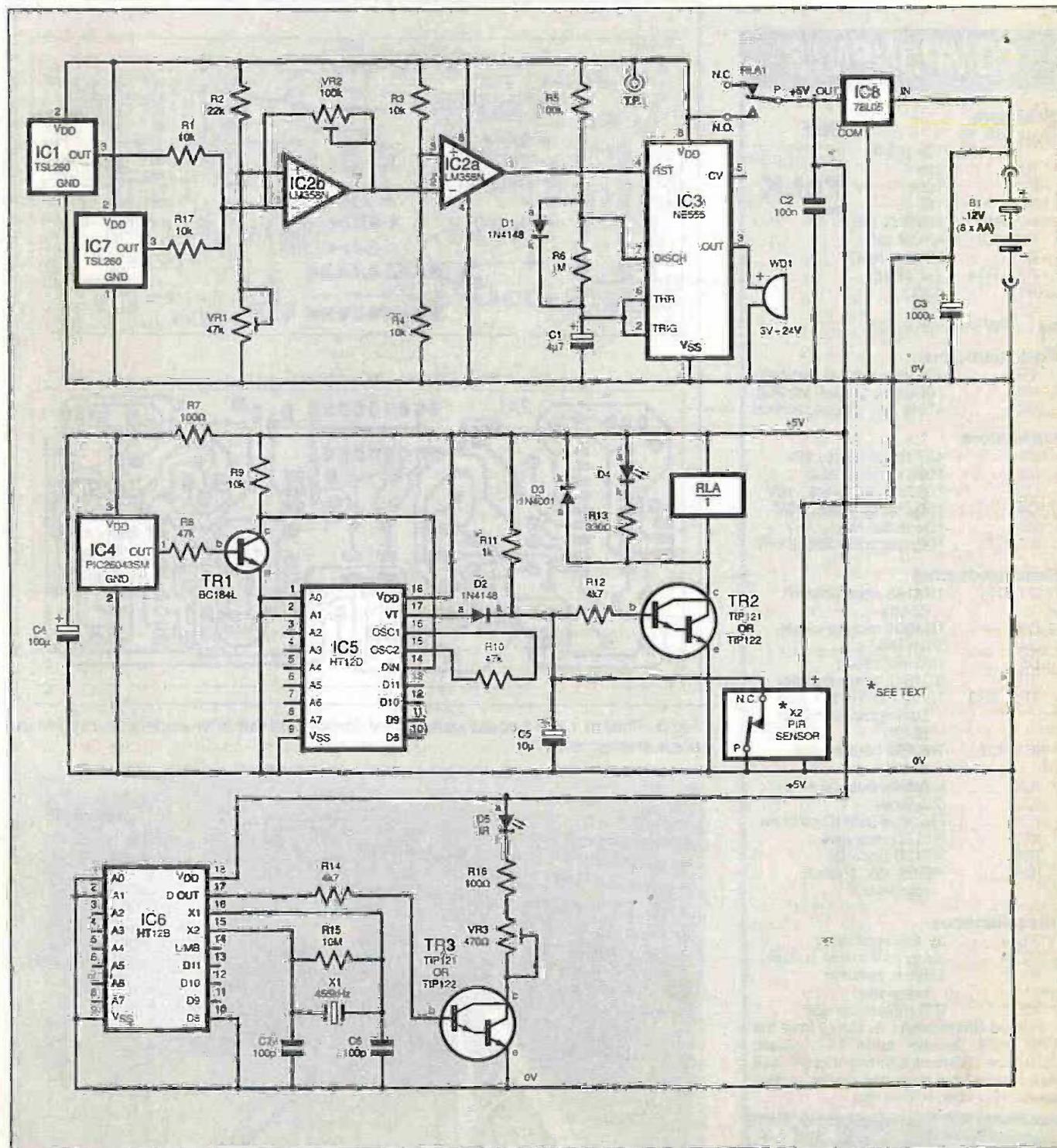


Fig.2. Complete circuit diagram for the Child Guard. The optional PIR sensor is shown in-circuit and is designated X2.

can it be used), i.e. the PIR is an *alternative* to the other infra-red detection circuitry. Consequently, IC4, IC5 and IC6 and all their associate components should be omitted in this application.

POWER SUPPLY

Power to the Child Guard is intended to be from a 12V battery. This is suited to powering the PIR sensor if used. The battery supply is regulated down to +5V by IC8 to suit the rest of the circuit.

Since the standby current is 10mA and the "on" current is 50mA, a battery pack containing eight AA-size 1.5V cells could be used. A 12V d.c. mains adaptor is a suitable alternative. Typically, the latter can supply 300mA.

If a PIR is not used, a lower voltage supply source may be used, such as a 9V battery. Alternatively, a d.c. power supply of 5V (4.5V) could be used by inserting a wire link in the place of IC8.

Note that IC5 and IC6 *must not* be supplied with a voltage greater than +5V.

C2 and C3 are decoupling capacitors to help smooth the supply lines.

CONSTRUCTION

Apart from the two temperature sensors, all the components are contained on a single printed circuit board (p.c.b.). The topside component layout and full size underside copper foil track master are shown in Fig.3. This board is available from the *EPE PCB Service*, code 241.

Begin construction by soldering in the resistors and wire links, noting that one link is under the socket for IC2 and another under the buzzer WD1. Ensure that the electrolytic capacitors (C1, C3, C4, C5), transistors, diodes and the buzzer are connected the right way around. Note that on the IR diode (D5) the long leg may be the cathode (k) - check with your component supplier's catalogue. Do not insert the dual-in-line i.c.s until construction has been completed and fully checked.

If a PIR sensor is not being used then R11 must be omitted. If a PIR is being used then be sure to connect its power pins to the +12V supply rather than the +5V regulated supply. Four-core wire can connect the PIR sensor to the circuit.

COMPONENTS

Resistors

R1, R3, R4,	
R9, R17	10k (5 off)
R2	22k
R5	100k
R6	1M
R7, R16	100Ω (2 off)
R8, R10	47k (2 off)
R11	1k (see text)
R12, R14	4k7 (2 off)
R13	330Ω
R15	10M

All 0.25W 5% carbon film.

Potentiometers

VR1	47k min. preset, vertical
VR2	100k min. preset, vertical
VR3	470Ω min. preset, vertical

Capacitors

C1	4μ7 radial elect., 16V
C2	100n ceramic disc
C3	1000μ radial elect., 16V
C4	100μ radial elect., 16V
C5	10μ radial elect., 16V
C6, C7	100p ceramic disc (2 off)

Semiconductors

D1, D2	1N4148 signal diode (2 off)
D3	1N4001 rectifier diode
D4	5mm red l.e.d.
D5	infra-red diode
TR1	BC184L npn transistor
TR2, TR3	TIP122 or TIP121 npn Darlington transistor (2 off)
IC1, IC7	TSL260 heat sensor (2 off)
IC2	LM358N dual op.amp
IC3	555 timer
IC4	PIC26043SM IR receiver
IC5	HT12D decoder
IC6	HT12B encoder
IC8	78L05 +5V 100mA regulator

Miscellaneous

RLA1	5V SIL reed relay
WD1	3V to 24V active buzzer
X1	455kHz ceramic resonator
X2	PIR motion sensor

Printed circuit board, available from the *EPE PCB Service*, code 241; plastic case, size 130mm x 64mm x 42mm, (see text); single-hole insulated power socket-connecting wire; solder, etc.

Approx. Cost
Guidance Only

£30

excl. PIR sensor & Case

See
**SHOP
TALK**
page


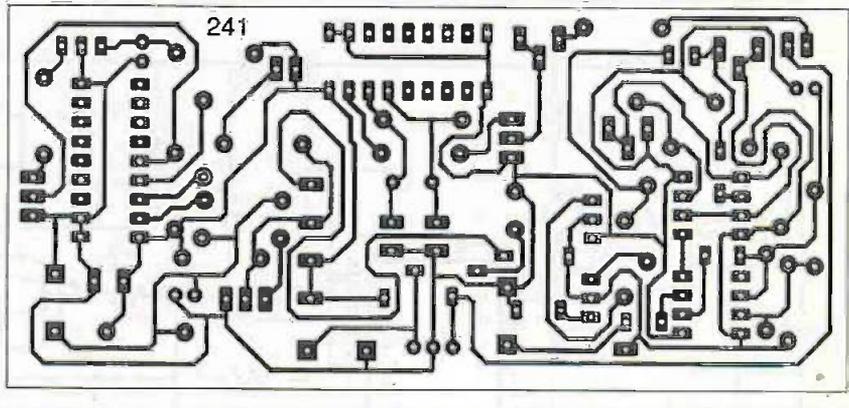
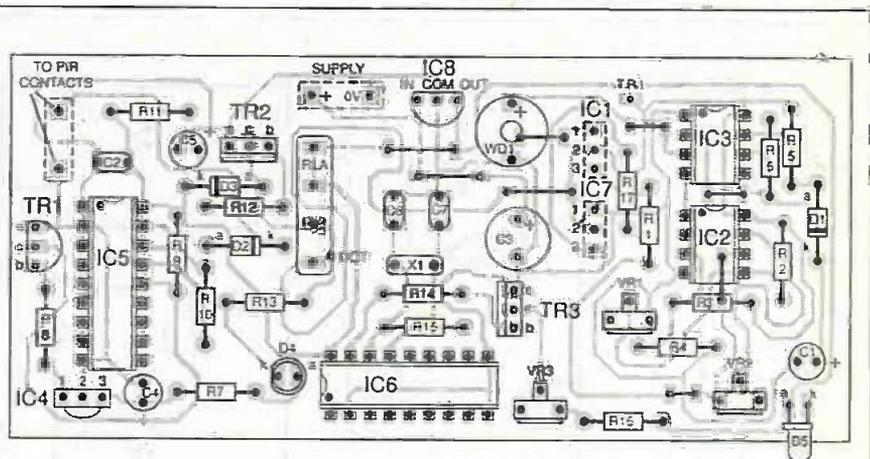


Fig.3. Printed circuit board component layout and full size underside copper foil track master pattern.

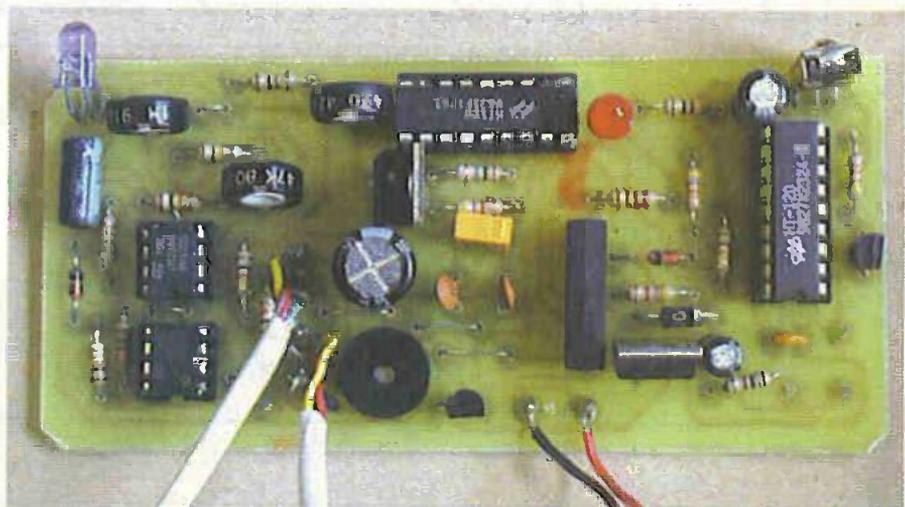

Components mounted on the prototype circuit board.

The IR receiver IC4 has a "dome" on its sensitive side, this faces outwards from the p.c.b.

Ultimately, if it is found that the beam from the IR transmitter, D5, is being detected by the IR receiver, IC4, through stray reflection inside the case, the transmitter and receiver devices could be partially surrounded by Blu-Tack, or even a small tube could be used.

CASING

A metal box should be used if the device is to be positioned very close to the heat source, but otherwise a plastic case is suitable. If using a metal case, the p.c.b. should be mounted so that it cannot come into contact with it, which could cause a short circuit across the copper tracks.

Drill holes in the case to suit the positions of the IR receiver and IR diode. Suitable holes are also needed for the power supply input, and the cables to the heat sensors. Additionally, three holes in the case are required to allow adjustment access to the three preset potentiometers, using a small screwdriver.

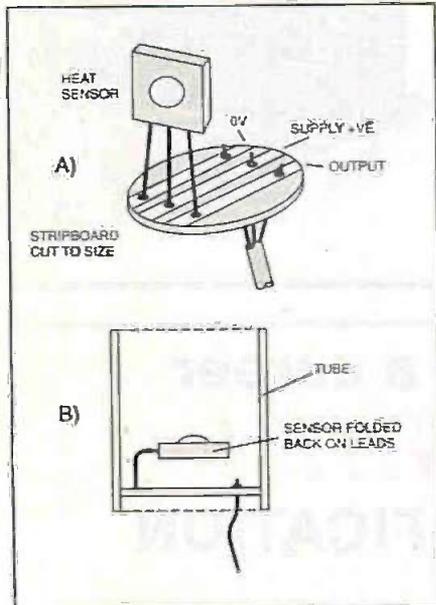


Fig.5. Suggested assembly technique for the heat sensors.

It is advisable to use an input socket for the power supply, plus a switch, although the latter was not used on the prototype. Suitable holes for these should also be drilled. All holes should be drilled accurately to correspond with their respective components.

Position the p.c.b. so that the IR receiver and diode are as close as possible to their case holes, as shown in Fig.4, to prevent any loss in range.

You can either have the heat sensors mounted on the outside of the box or in a separate box attached to 4-core wire. This enables two separate heat sources to be detected.

The heat sensors are each mounted on small pieces of stripboard, as shown in Fig.5a. Since they could receive interference from surrounding lights, causing the circuit to be active all the time, they need to be partially enclosed. One option is to surround them by a metal tube, otherwise a piece of plastic tube may be used if it is

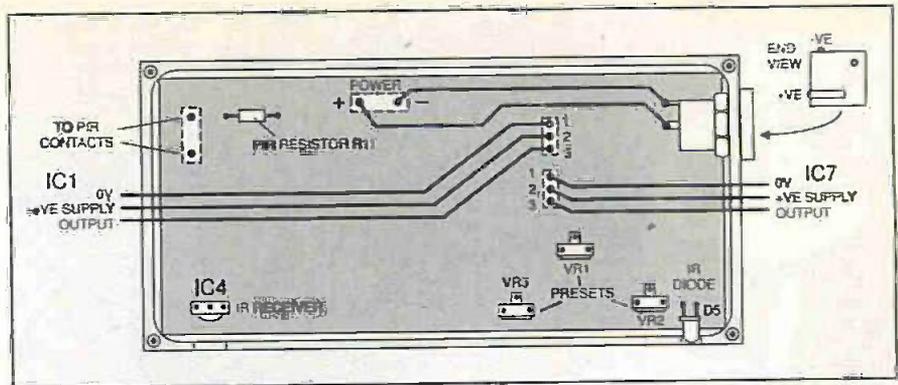


Fig.4. Child Guard p.c.b. and its connections within the case.

covered by some white insulating tape.

The stripboard should be cut to the right size to fit into the tube. Construction of the sensor tubes is shown in Fig.5b. Use small-diameter 3-core cable to attach the sensors to the circuit (or use 4-core cable and trim off the fourth wire at each end).

TESTING

The first check is to make sure voltage regulator IC8 is the correct way round. Connect the circuit to the battery and then check that +5V is present on the output pin of IC8. If it is, disconnect the power and then insert the remaining chips, correctly orientated.

Testing of the infra-red modules presents a problem as if one does not work then the other will seem not to be working as well. If in doubt use a voltmeter or oscilloscope as follows:

Test the voltage on the VT pin (pin 17) on IC5 (receiver). It should be normally at 0V but change to about 5V when a signal is received. If the VT test fails then check that IC4 is fitted the right way round, with its "dome" facing the outside edge of the p.c.b.

Now check three voltages on the pins of IC4. Pin 3 should be +5V and pin 2 at 0V. When a signal is not received, pin 1 (the output pin) should be at just under 4V. When a signal is received this voltage should fall by about 1V.

Note that as the signal is oscillating, a voltmeter provides a rather approximate guide to voltage. If an oscilloscope is avail-

able it should be possible to view the encoded signal, in which case the trace will rise and fall between 4V and 0V.

If this test fails then try sending a signal from a TV remote control unit. The signal will not be decoded, but you will at least know if the receiver device is working, and hence determine if the fault lies in the transmitter, or the receiver, or both.

If the output from IC4 is working, test the signal at the Data In (pin 14) of IC5. It should be at about 0V when no signal is received, rising to about 1.3V on a voltmeter when a signal is being received. An oscilloscope will show that the signal actually pulses to about 5V.


If the VT pin on the receiver is working then simple voltmeter tests should establish the position of any other faults.

While testing the temperature sensing part of the circuit, connect the +5V supply to test point TP1, as this will give that part of the circuit a constant +5V supply, rather than being cut off by the reed relay whenever you move out of the range of the infra-red beam. Use a torch to provide a source of infra-red to the sensors.


SETTING-UP

All the presets can be adjusted to suit the user's own particular needs. The following is a summary of their functions:

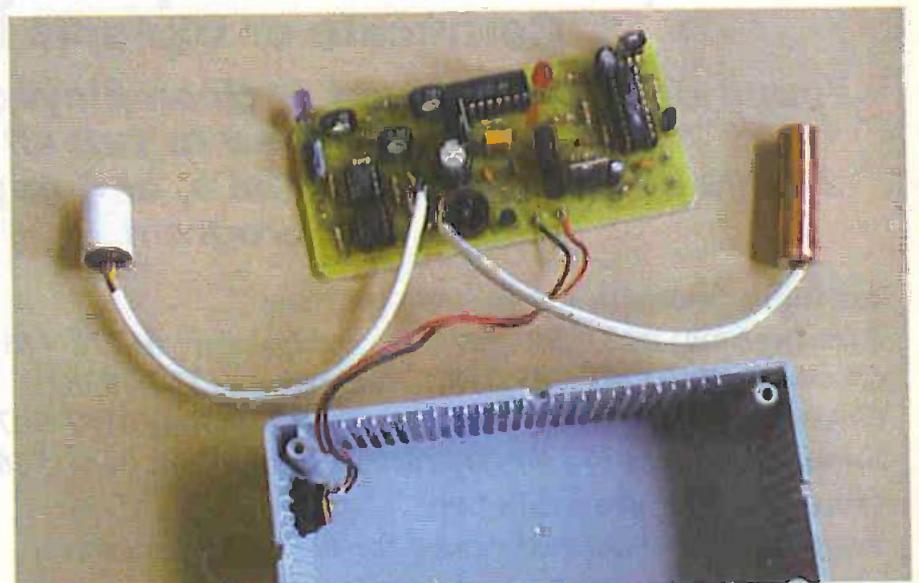VR1 is in a potential divider circuit which sets the voltage at which the comparator (IC2a) is triggered. Reducing the resistance lowers the voltage being looked



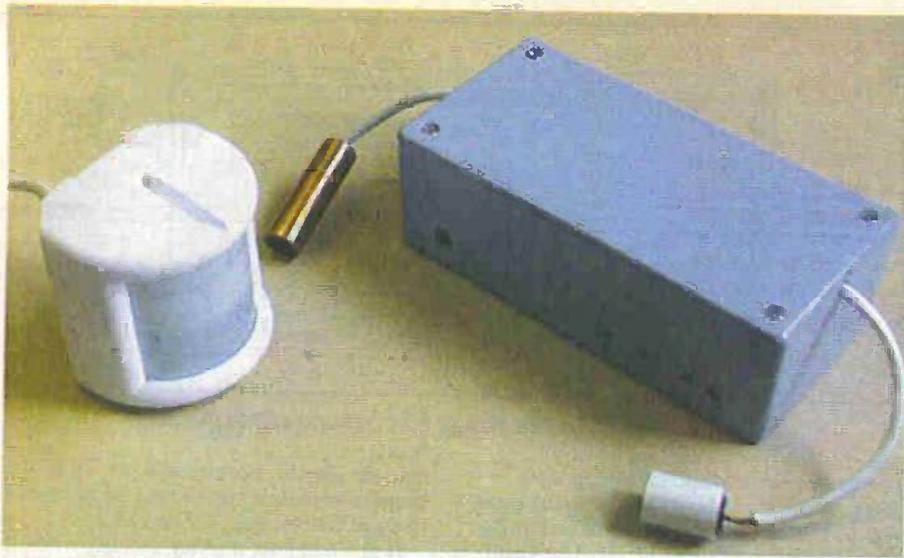Completed Child Guard showing the heat sensors and power socket wired to the p.c.b.



Finished Child Guard together with a miniature PIR Sensor. The heat sensors are encased in tubes. Note the holes for setting the presets and the transmitter/receiver "windows".

for, which increases the sensitivity. Note that if the resistance is lowered too much, the circuit will pick up background IR radiation.

VR2 sets the feedback resistance for op.amp IC2b, thus setting its gain. If the resistance is increased, the gain is increased, along with the sensitivity. If the resistance is increased too much, the circuit will pick up background radiation.

VR3 adjusts the range of the infra-red beam by decreasing or increasing the power going through IR diode D5.

Reducing the resistance extends the range.

COMMON PROBLEMS

Typical construction mistakes include dry joints and bridged pads i.e. adjacent pads accidentally joined together with solder. Other potential problems might include failure to insert wire links, especially the one under IC2 and the buzzer.

Also check that the components are correctly placed, and the correct way round. Note again that some IR l.e.d.s are unusual in that the longer lead denotes the cathode.


If the PIR sensor is not working, then check that you have connected it to the 12V supply.

IN USE

The system can be used in many ways, but the main intention is to give a parent a warning if their child approaches a heat source, such as a fire. It is especially useful if they have inquisitive babies who are beginning to walk.

Another use could be to warn blind or partially sighted people if they are about to touch something dangerously hot, such as a stove.

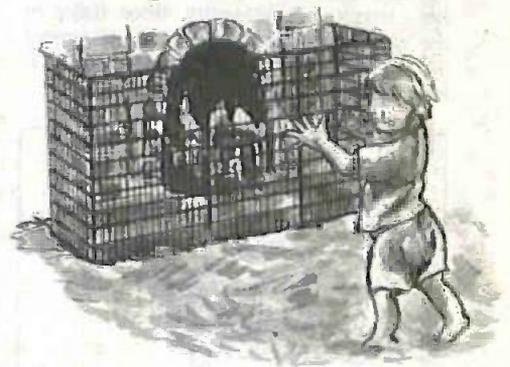The Child Guard could be placed above the heat source (e.g. fire) to be monitored, with both sensors facing it, and the IR diode or PIR detector facing into the room. Another location could be above a stove, this time with the heat sensors pointing towards the hobs. □



Start To Turn a hobby into a career

FREE TRAINING!!!!

CITY & GUILDS 7261 QUALIFICATION

in

Electronics & Computing systems

Certificate or Diploma levels

Young or old, Employed or Unemployed these courses are designed to suit all

2 days per week for 30 weeks, or 4 days if on a New Deal program

Training rooms in the following areas:

Birmingham; 0121 200 2646

Bridgwater; 01278 445 210

Chelmsford; 01245 345 218

Derby; 01332 202828

Gravesend; 01474 535034

East London; 0181 507 1377


South London; 0171 274 4106

West London; 0181 566 5252

Other courses are available:

Telephone your nearest centre for more information

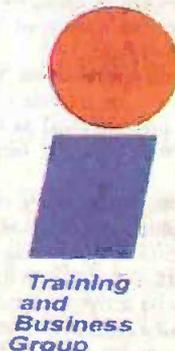We are an Equal Opportunities organisation



PIC BASIC

Write your PICmicro programs in BASIC!

Quicker and easier than "C" or assembler Expanded BASIC Stamp I compatible instruction set. True compiler provides faster program execution and longer programs than BASIC interpreters. 12CIN and 121COUT instructions to access external serial EEPROMs. More user variables Peek and Poke instructions to access any PICmicro register from BASIC. Serial speeds to 9600 baud. In-line assembler and Call support (call your assembly routines). Supports PIC12C67x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 92x and PIC16F8x microcontrollers. Use in DOS or Windows Compatible with most PICmicro programmers.

The low-cost PicBasic Compiler (PBC) makes it easy to write programs for the fast Microchip PICmicros. PBC converts these programs into hex or binary files that can be programmed directly into a PICmicro microcontroller. The easy-to-use BASIC language makes PICmicro programming available to everyone with its English-like instruction set. No more scary assembly language!

The **PicBasic Pro** Compiler runs on PC compatibles. It can create programs for the PIC12C67x, PIC12CE67x, PIC14Cxxx, PIC16C55x, 6xx, 7xx, 84, 9xx, PIC16CE62x and PIC16F8x microcontrollers. The PicBasic Pro Compiler instruction set is upward compatible with the BASIC Stamp II and Pro uses BS2 syntax. Programs can be compiled and programmed directly into a PICmicro, eliminating the need for a BASIC Stamp module. These programs execute much faster than their Stamp equivalents. They may also be protected so no one can copy your code!

Pic Basic - £49.95

Pic Basic Pro - £149.95

Supplied with full documentation

Free PIC MACRO compiler


and

sample basic programs

Download the full PICBASIC instruction set with sample programs
<http://www.crownhill.co.uk>

EPIC™

- Low cost programmer for PIC12Cxxx, PIC12CExxx, PIC14Cxxx, PIC16C505, 55x, 6xx, 7xx, 84, 9xx, PIC16CE62x and PIC16F8xx microcontrollers
- ZIF adapters available for 8/18- and 40/28-pin DIP, 8-, 18- and 28-pin SOIC, 44-pin MQFP and 44- and 68-pin PLCC PICmicros
- Runs off two 9-volt batteries or optional AC adapter
- Connects to PC parallel printer port
- Software upgradeable for future PICmicros
- Includes "8051" style PICmicro macro assembler
- Available assembled and tested or as bare board with diskette

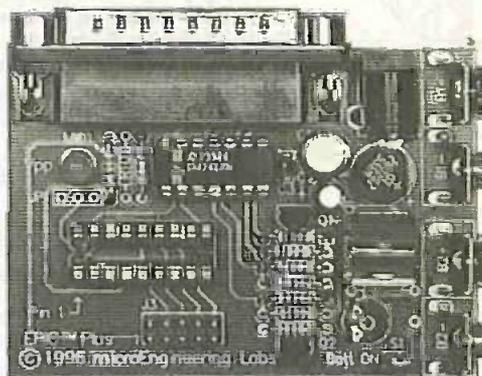

SUPPORTS THE NEW PIC16C87X
Available from CROWNHILL

EPIC Programmer £49.95

or **£35** if purchased with

PIC BASIC or Pro

25-pin cable £5.95

PIC16F84 £1.90

All plus £5 P&P and 17.5% VAT

Join the world wide PIC Basic mail list and access the PIC Basic Knowledge Base via FTP
E-mail: majordomo@quos.net with "subscribe picbasic-1" in the message

PIC16F84/04P	£1.90 each
PIC12C508/509	£0.65 each
24LC16	£0.75 each
24LC65	£1.50 each
PIC16C620	£1.95 each
PIC16C621	£2.25 each
PIC16C622	£2.50 each

LCD DISPLAYS

Various types available from
£7.50 (2x16 line)

Ideal for use with PIC Basic.

Example code supplied

with every unit



Serial LCB Display
Drivers (PIC16F84)
£2.00

AMAZING LOW PRICES

PIC PROGRAMMER KIT


Programs the Popular PIC 16C84, 16F84, 24xx series serial memory devices. Connects to the serial port of a PC and requires NO EXTERNAL power supply. The kit includes instructions for assembly, circuit diagram and component layout.

This handy little programmer is easy to build, taking no more than 30 minutes to assemble and test. The Professional quality PCB is double-sided, through-plated with solder resist and screen printing to aid efficient assembly. It is supplied with driver software to run in DOS on a 286 PC upwards and under Windows 95 on 486 or Pentium and a Disk full of interesting projects, tips and data sheets for PIC devices, including FREE Assembler and Simulator.

Only £15.00 including Delivery and VAT

(requires 9-pin D-type to 9-pin D-type cable to connect to serial port of PC)

CABLE £5 INC VAT AND DELIVERY

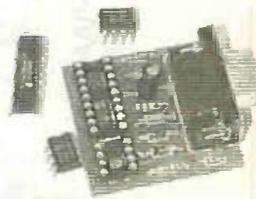

PIC Micro CD ROM

Packed with 600Mb of information, all current data sheets, Programs and Diagrams, Application notes, PDF Viewer, Includes PING-PONG and TETRIS with video and sound out of a PIC84 BASIC language ASSEMBLY routines!

£10 inc P&P & VAT

Crownhill Associates Limited

The Old Bakery, New Barns Road, Ely, Cambridge, CB7 4PW


Tel: 01353 666709

Fax: 01353 666710

www.crownhill.co.uk

E-mail: sales@crownhill.co.uk

INGENUITY UNLIMITED

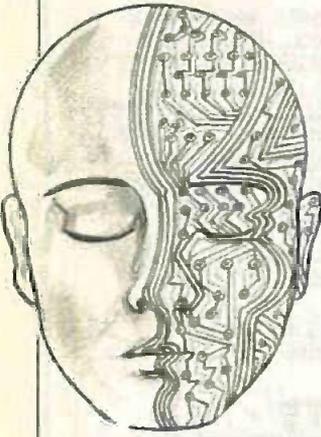

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit tips, not simply mechanical or electrical ideas. Ideas *must be the reader's own work* and not have been submitted for publication elsewhere. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should preferably be typed or word-processed, with a brief circuit description (between 100 and 500 words maximum) and full circuit diagram showing all relevant component values. Please draw all circuit schematics as clearly as possible. Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BS21 1PF. They could earn you some real cash and a prize!



WIN A PICO PC BASED OSCILLOSCOPE

- 50MSPS Dual Channel Storage Oscilloscope
- 25MHz Spectrum Analyser
- Multimeter • Frequency Meter
- Signal Generator

If you have a novel circuit idea which would be of use to other readers then a Pico Technology PC based oscilloscope could be yours. Every six months, Pico Technology will be awarding an ADC200-50 digital storage oscilloscope for the best IU submission. In addition, two single channel ADC-40s will be presented to the runners-up.

Theatrical Cue Light - In the Spotlight

THE CIRCUIT diagram presented in Fig. 1 will provide a simple but effective means of communication between a theatre stage manager and lighting operator so that the stage manager can "cue" lighting changes. The stage manager controls the "Master Station" and the lighting operator has a "Slave Station". Both stations have a red and green l.e.d. and a pushswitch and are linked by three-core cable.

Communication is initiated when the stage manager presses the "Call" or "Master" pushswitch S2. The red l.e.d.s on both units flash, warning the lighting operator that a lighting change is pending. This "Standby" call must be acknowledged - the operator

presses the "Slave" pushswitch S3, and the red l.e.d.s become steady.

An unacknowledged call may be cancelled by a further press on the "Call" switch. When the lighting change is required, the stage manager presses the "Call" switch again. Both red l.e.d.s extinguish and the green l.e.d.s light to give a "Go" cue.

To reset the system ready for further cues, the "Slave" switch is pressed; however, a timer has been incorporated to perform the reset approximately three seconds after the "Go cue" has been issued.

The main circuit is, essentially, a state machine; each state is determined by the two JK flip-flops within IC1. Table 1 explains

each state; the order shown depicts normal use with alternate presses of the Master (S2) and Slave (S3) switches. If the Master switch is pressed during state 2, the system will return to state 1.

Flip-flops IC1a and IC1b are clocked by the Master and Slave Station switches respectively. The former is debounced by capacitor C2 and resistors R4 and R5. The Slave switch S3 simply shorts the 'B' and 'C' interconnections; when closed, transistor TR1 will conduct providing a high clock pulse for IC1b. Capacitor C1 removes unwanted spikes when the red l.e.d.s are flashing.

The flip-flops are connected so that their state preceding a clock pulse depends upon the state of their partner. When IC1b is reset, IC1a works in toggle mode, changing state

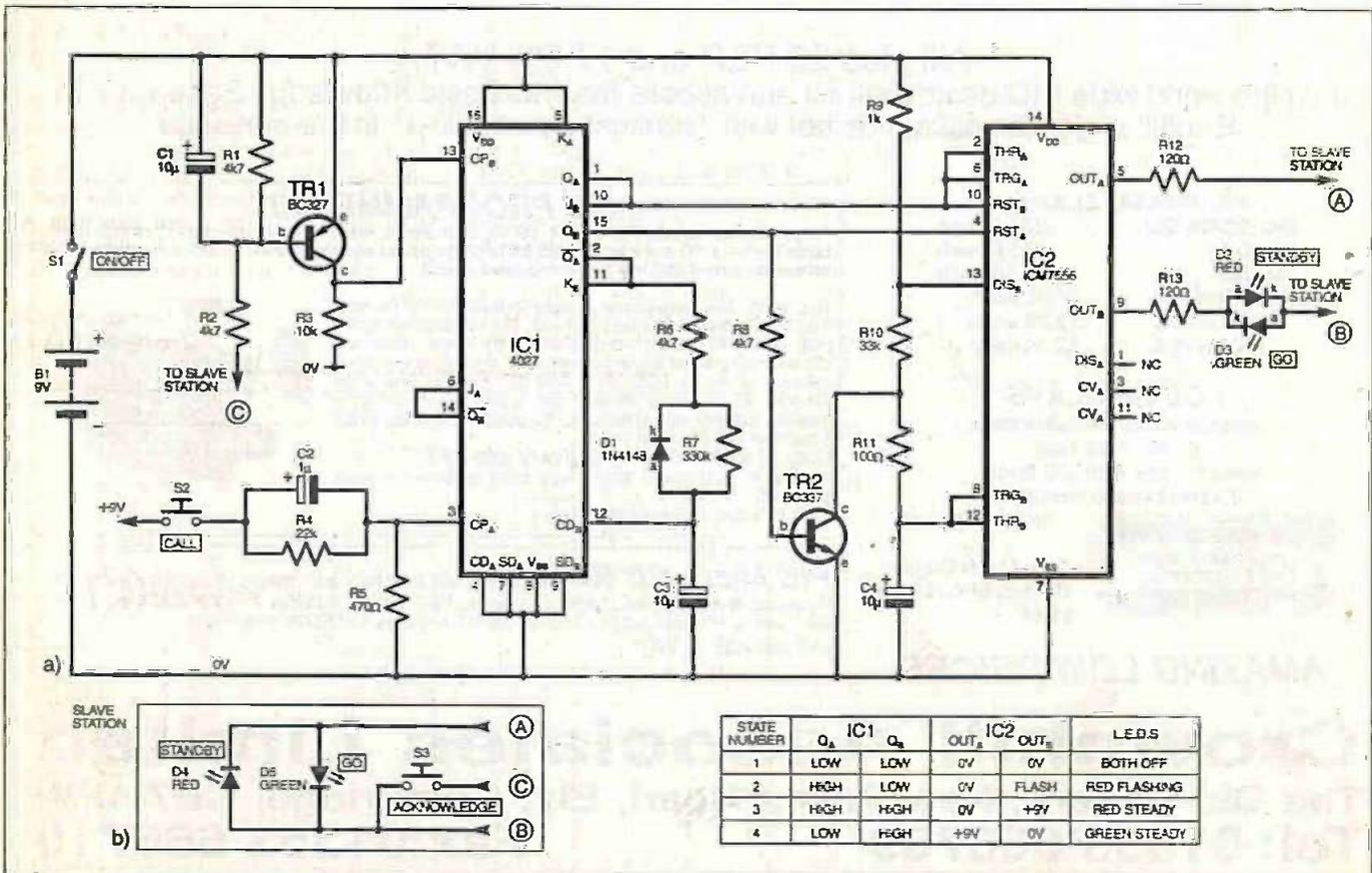


Fig. 1. Circuit diagram for a Theatrical Cue Light.

Keypad Code Controller - Fingertip Control

with every clock pulse. When IC1b is set, IC1a will reset when clocked. IC1b is configured to act as a D-type flip-flop, adopting the state of IC1a after a clock pulse.

The timer circuit is based around the reset pin of IC1b (pin 12). When the green l.e.d.s light, the inverted output of IC1a (pin 2) will go high, and capacitor C3 charges via resistors R6 and R7. After about three seconds IC1b will reset, so the system reverts to state 1. Diode D1 ensures a speedy discharge path for C3, as soon as the inverted output IC1a goes low.

The l.e.d.s are driven by the dual timer IC2. Which l.e.d. is lit depends on which of IC2's outputs is high. When they are both low, neither l.e.d. is lit. IC2b is connected in an astable mode which flashes the red l.e.d.s. The reset input (pin 10) is connected to the output of IC1a which when low, forces the timer's output low. With a high output from IC1b, transistor TR2 will prevent capacitor C4 from charging, which inhibits IC2b. This will result in a steady +9V output.

The other half of IC2 provides a push-pull drive, with the addition of a logic function. The output (pin 5) is at 0V at all times except when the reset (pin 4) is high and the trigger and threshold inputs (pins 2 and 6) are low; i.e. during state 4.

Both sets of l.e.d.s are connected in series. Each pair of l.e.d.s could be replaced with a single bi-coloured l.e.d. and the circuit can be powered by a 9V PP3 type battery.

Steve Teal,
Witney, Oxon.

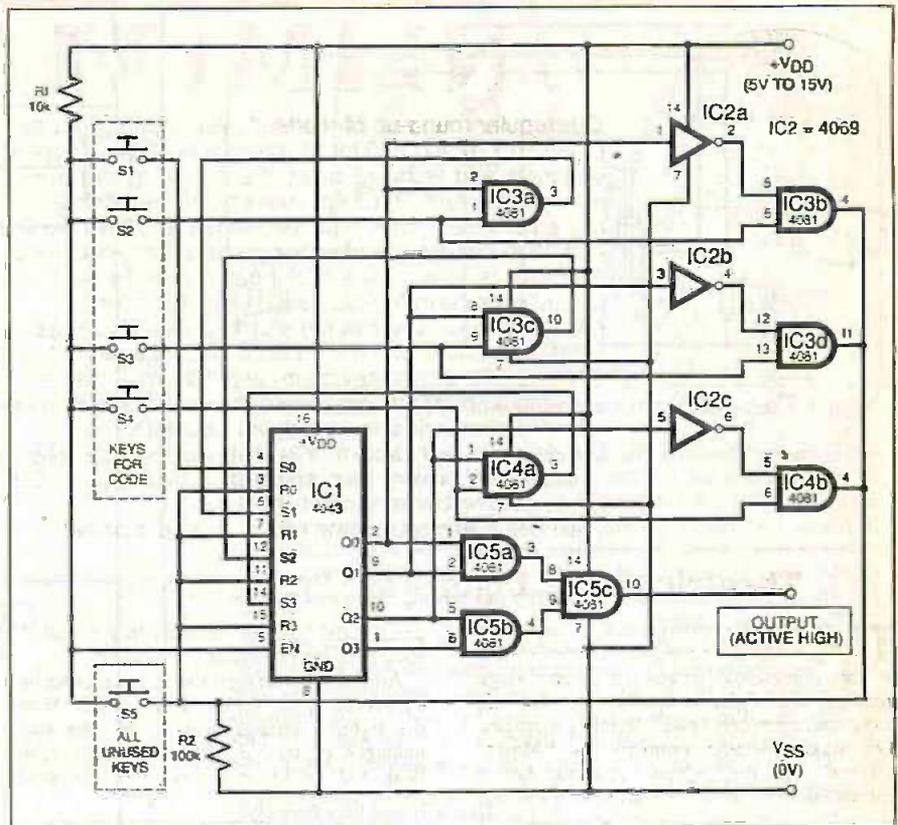


Fig.3. Circuit diagram for the Keypad Code Controller.

Morse Practice Oscillator -

Get Keyed Up

ALTHOUGH there is a vast amount of Morse tutoring software available, a small Morse Practice Oscillator is handy for occasions where a little spare time is on hand, and the circuit of Fig.2 was produced for a simple battery-operated device to assist with Morse practice sessions.

The oscillator, centred around IC1, is a phase-shift type, the frequency of which is determined by components C1, C2, R4 and R6. (The equation to determine the actual frequency is $f=1/2\pi RC$.) A split supply is produced by the voltage divider resistors R1 and R2 and is decoupled by capacitor C3. To make the output a sine wave the gain of IC1a has to be kept at around $\times 3$ and this is accomplished by the feedback resistors R3 and R5.

As the circuit was to be powered by a battery and also drive a loudspeaker, a way to minimise the current consumption was needed and the output stage centred around IC1b was the result. Transistors TR1 and TR2 are a complementary pair which has no base bias; therefore when the key is not pressed the stage consumes practically no current.

Usually, operating a complementary pair in this way would produce severe crossover distortion but as the output is fed back to IC1b inverting input, the heavy negative feedback here almost completely eliminates distortion. None of the device types are critical and those shown could be readily substituted.

Stephen Forsyth,
Gormouth,
Morayshire.

THE circuit diagram shown in Fig.3 provides a CMOS active high signal at the output following the correct entry of a four digit code on a standard 10-digit keypad. It may be used to control many different circuits and devices.

Assuming that pushswitches S1 to S4 are wired for a code of 1234 for example, the circuit functions as follows: upon the press of "1" the first flip-flop in IC1 is set and its Q0 output (pin 2) goes high. Consequently this sends one input of IC3a high together with one input of IC5a, wired as a 4-input AND gate.

When switch-pad 2 is pressed, the second input of IC3a is brought high, generating a high output and setting the second flip-flop of IC1. This brings the second input of IC5a high and one input of IC3c. When pad 3 is pressed, pin 9 of IC3c goes high thus setting

the third flip-flop of IC1. Output Q2 goes high, which brings the third input of IC5 and one input of IC4a high.

Finally, when pad 4 is pressed this brings the second input of IC4a high, setting Q3 of IC1, and bringing the last input to IC5 high. This causes the circuit output to go high at IC5e pin 10, which can be used to control external circuitry.

The circuit is protected from incorrect key-presses because all unused keys (represented by S5) are tied to the Reset inputs of all the flip-flops. Also, in the example, if 4 is pressed instead of 3, this brings the second input of IC4b high, hence its output goes high. All flip-flops will then reset. All other incorrect keypresses will reset the circuit in the same way.

Damien Maguire,
Greystones, Ireland.

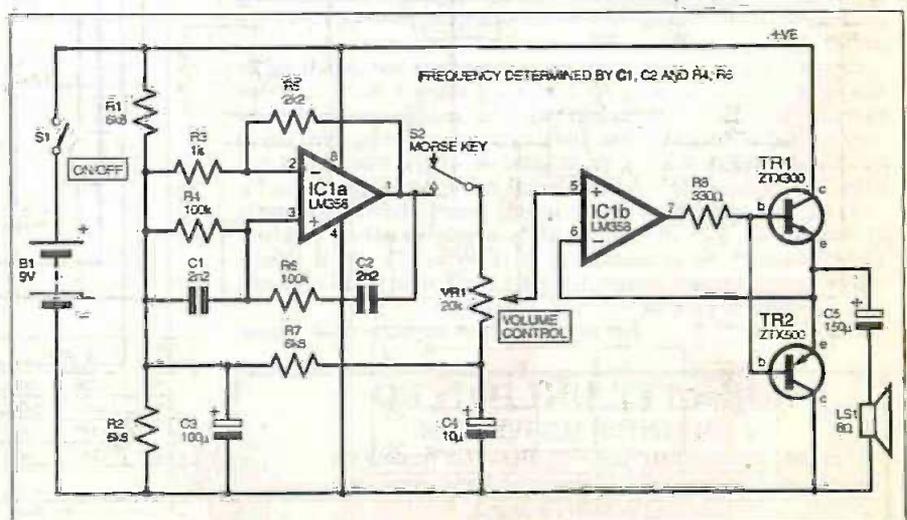


Fig.2. Morse Practice Oscillator circuit diagram.

Intercom/Baby Listener - Baby Talk

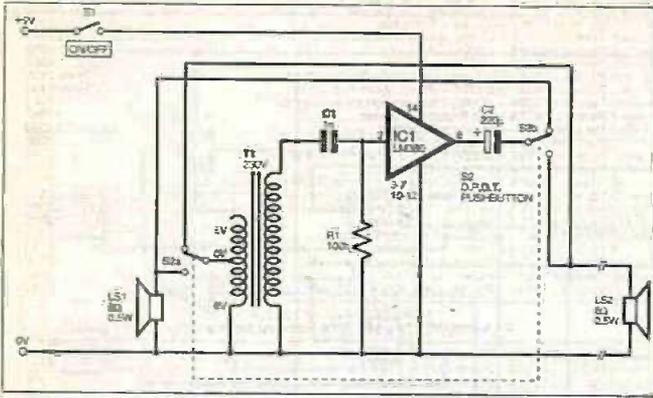


Fig.4. Circuit diagram for an Intercom/Baby Listener unit.

THE simple Intercom/Baby Listener circuit design shown in Fig.4 is based around the LM380. The intercom delivers good tone, and around 500mW (1/2W) of power. It functions best when one speaks directly into the loudspeaker, but will reproduce sounds a few metres away.

Pushbutton switch S2 switches the intercom from "Listen" to "Talk" mode by reversing the positive connections of the loudspeakers. Therefore, the intercom is normally in listening mode and may be used as a "Baby Listener".

Only a twin-core cable is required to connect the "remote station", LS2. The transformer T1 provides impedance matching between the loudspeakers and the amplifier. (A small mains transformer was used, as audio transformers were hard to come by locally). The intercom draws around 10mA current on standby, and should, with a 9V PP9 battery, give more than a fortnight's continuous service, alternatively rechargeable batteries could be utilised.

Rev. Thomas Scarborough,
Fresnaye, Cape Town, Republic of South Africa.

TV Test Pattern Generator - Colour Bands

A LOW-COST solution to testing colour TVs and monitors without having to resort to expensive kits or custom i.c.s is shown in circuit diagram Fig.5. It should satisfy the majority of repair and alignment tasks. The circuit consists of a sync generator, IC1, followed by buffer amplifier transistors TR2 to TR4 and a colour encoder IC2.

A teletext timing chain i.c. (IC1) is used as a sync generator and is driven by a 6MHz master clock source from oscillator TR1. IC1 produces several outputs, including composite sync from pin 5 and field rate signals from pins 19 to 23, which are used for the test patterns.

Unfortunately, these field rate signals mean that the bars are horizontal instead of vertical, but provided one remembers to trigger the oscilloscope at field rate instead of line rate, no problems should occur. Transistor TR5 is a logic inverter which is used to send pins 19 to 23 into a high impedance state during blanking, and for slightly longer because of the teletext border. Switch S2 is the pattern selector.

The buffer amplifiers TR2 to TR4 match the high impedance outputs of IC1 with the low impedance input requirements of IC2, and they also reduce the 5V logic level outputs to standard 1V peak-to-peak video levels. Presets VR1 to VR3 can be adjusted with an oscilloscope for 1V p-p at their outputs, or by using a TV or monitor for correct colours.

Crystal X2 is the colour subcarrier oscillator reference which can be fine-tuned via timer capacitor VC1 to obtain colour lock on the TV or monitor. The usual 4.433MHz bandpass filter and luminance delay line were omitted to conserve space. The CVBS signal is output from pin 20 of IC2 and fed to the monitor via the video output or to a modulator such as the UM1233 via VR4, which is adjusted for correct contrast on the TV.

If constructing the circuit on stripboard, since the circuit operates at r.f. frequencies, join all unused tracks to ground and no problems should be found. An unregulated p.s.u. of 9V to 12V d.c. at 100mA can be used as a power source. The CXA1145P used for IC2 is available from CPC in Preston.

Lee Archer, Ashton-in-Makerfield, Wigan.


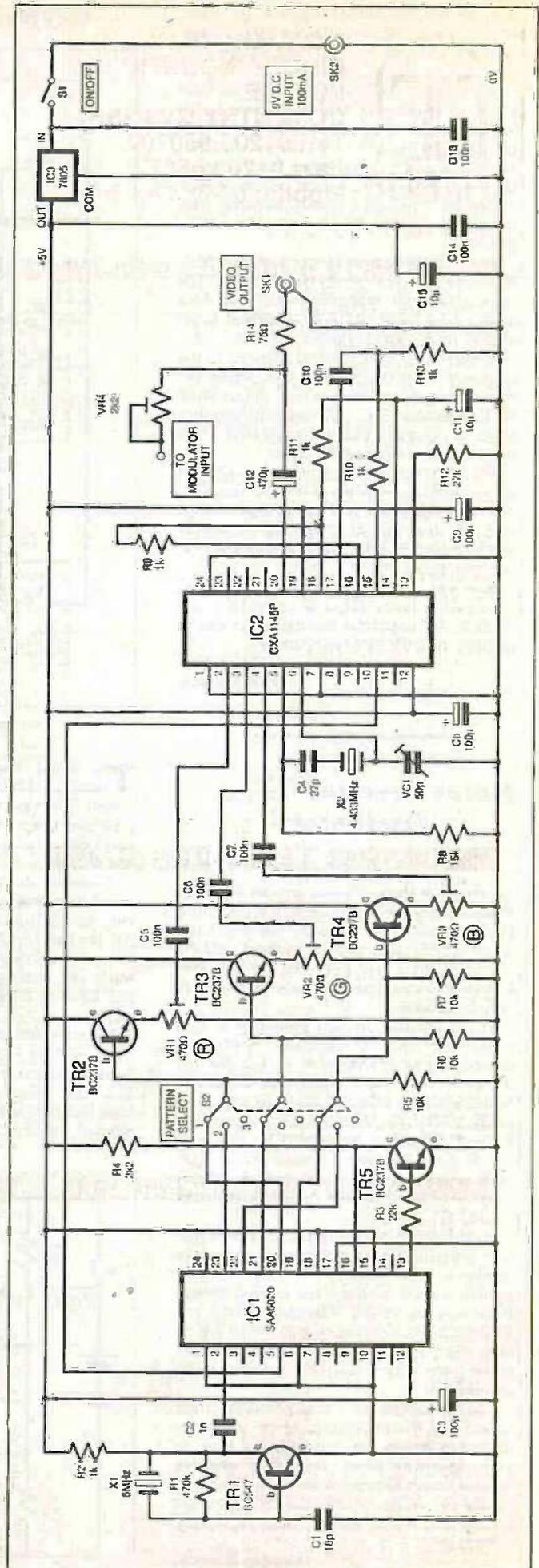


Fig.5. TV Test Pattern Generator circuit diagram.

INGENUITY UNLIMITED

BE INTERACTIVE

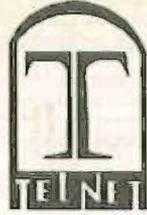IU is your forum where you can offer other readers the benefit of your Ingenuity. Share those ideas, earn some cash and possibly a prize!



8 CAVANS WAY,
BINLEY INDUSTRIAL
ESTATE.
COVENTRY CV3 2SF
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M59)

OSCILLOSCOPES

Beckman 9020 - 25MHz - Dual Channel	£150
Gould OS 245A/250/255/300/3351/4000	from £125
Hewlett Packard 180A/180C/181A/182C	from £150
Hewlett Packard 1745A, 1741A, 1744A, 100MHz Dual Channel	from £300
Hewlett Packard 541100 - 1GHz Digitizing	£1250
Hewlett Packard 54200A - 50MHz Digitizing	£500
Hewlett Packard 54201A - 300MHz Digitizing	£1250
Hewlett Packard 54512B - 300MHz - 1 GS/s 4-Channel	£2250
Hewlett Packard 54501A - 100MHz - 100 Ms/s 4-Channel	£1250
Hitachi V152/V302B/V302F/V353F/V350B/V650F	from £105
Hitachi V650F - 60MHz Dual Channel	£200
Hitachi W1100A - 100MHz 4-Channel	£200
Intron 2020 - 20MHz Digital Storage (NEW)	£450
Iwatsu SS5710/SS5722 - 20MHz	from £125
Meguro - MSO 1270A - 20 MHz Digital Storage (NEW)	£450
Lecroy 9304 AM - 200MHz - 100 Ms/s 4-Channel	£3000
Lecroy 5450A - 300MHz/400 Ms/s D.S.O. 2-Channel	£2250
Philips PM 3075 - 100MHz Dual Channel	£450
Philips PM 3211 PM 3212 PM 3214 PM 3217 PM 3234 PM 3240 PM 3245 PM 3244 PM 3261 PM 3262 PM 3263 PM 3240	from £125
Philips PM 3295A - 400MHz Dual Channel	£1600
Philips PM 3335 - 500MHz/200 Ms/s D.S.O. 2-Channel	£950
Tektronix 435 - 50MHz Dual Channel	£200
Tektronix 464 425 - 100MHz 2-Channel	from £300
Tektronix 465 455B - 100MHz Dual Channel	from £300
Tektronix 466 - 100MHz D.S.O.	£500
Tektronix TAS 475 - 100MHz - 4-Channel	£995
Tektronix 475M75A - 200MHz/250MHz Dual Channel	from £400
Tektronix 485 - 50MHz - 2-Channel	£750
Tektronix 2211 - Digital Storage - 50MHz	£250
Tektronix 2213 - 60MHz Dual Channel	£350
Tektronix 2215 - 60MHz Dual Trace	£375
Tektronix 2220 - 60MHz Dual Channel D.S.O.	£950
Tektronix 2221 - 60MHz Digital Storage 2-Channel	£950
Tektronix 2225 - 50MHz Dual Channel	£350
Tektronix 2235 - 100MHz Dual Trace	£500
Tektronix 2235 - Dual Trace 100MHz (portable)	£900
Tektronix 2240 - 300MHz/500 Ms/s D.S.O. 2-Channel	£2900
Tektronix 2245 - 150MHz - 4-Channel + DMM	£900
Tektronix 2445A - 100MHz - 4-Channel	£900
Tektronix 2475B - 400MHz - 4-Channel	£2500
Tektronix 5403 - 60MHz - 2 or 4 Channel	from £150
Tektronix 7313, 7603, 7623, 7633 - 100MHz 4-Channel	from £225
Tektronix 7704 - 250MHz 4 Channel	from £350
Tektronix 7904 - 500MHz	from £400
Trio GS-1022 - 20MHz - Dual Channel	£125

Other scopes available too

SPECIAL OFFER

HITACHI V212 - 20MHz DUAL TRACE	£160
HITACHI V222 - 20MHz DUAL TRACE - ALTERNATE VAG/MPY	£150

SPECTRUM ANALYSERS

Anco AC8211 - Spectrum Analyser 17GHz	£1995
Anritsu MS62B - 10kHz-470MHz	£1995
Anritsu MS3401A + MS3401B - (10kHz-200MHz)	£3500 / £3995
Anritsu MS610B - 10kHz-2GHz - (Mini)	£4500
Anritsu MS710F - 100kHz-20GHz Spectrum Analyser	£5500
Anrocom PS4555 - 1000MHz - portable	£950
Hainig 6078/6079 - Spectrum Analyser/Tracking Gen + 100MHz Oscilloscope	£1900
Hewlett Packard 182T - 855A (10MHz-21GHz)	£2750
Hewlett Packard 182T - 855B - 0-1 to 1500MHz	£1250
Hewlett Packard 853A - 855B - 0-1 to 1500MHz	£2250
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£5750
Hewlett Packard 3560A - 9Hz-50MHz	£800
Hewlett Packard 3562A - 0-2Hz to 25 9Hz (Dual Channel)	£2000
Hewlett Packard 435A - 20GHz-400MHz	£4000
Hewlett Packard 8569B - (0-1 to 22GHz)	£4250
Hewlett Packard 85045A - S' Parameter Test Set	£2500
Hewlett Packard 8753A - Network Analyser	from £3000
Hewlett Packard 8753B - Network Analyser	from £4500
IFR 7730 - 10kHz-1GHz	£2000
Meguro MSA 4901 - 300GHz (AS NEW)	£750
Meguro MSA 4912 - 1-1GHz (AS NEW)	£1000
Rohde & Schwarz - SWOB 5 Polystop 0-1-1300MHz	£1500
Takada Riken 4122 - 1 GHz Spectrum Analyser	£2100
Tektronix 7L18 with mainframe (1.5-50GHz with external mixers)	£2000
Tektronix 455P - 100Hz-1.6GHz programmable	£4500
Tektronix 456P - 1Hz-1.6GHz Spectrum Analyser	£4250

MISCELLANEOUS

Adret 740A - 100kHz-1120MHz Synthesised Signal Generator	£800
Anritsu MG 3601A Signal Generator 0-1-1040MHz	£1250
Anritsu ME 462B DFQ Transmission Analyser	£2500
Anritsu MG 643B Signal Generator 0-05-1050MHz	£750
Boonton 92C R.F. Multimeter	£185
Boonton 93A True RMS Voltmeter	£195
Dranzet 625 - AC/DC - Multifunction Analyser	£900
EIP 331 - Frequency Counter 18GHz	£450
EIP 545 - Frequency Counter 18GHz	£1250
EIP 575 - Frequency Counter 18GHz	£1450
Eltek SMP5 - Power Supply 50V/30V	£380
Farnell DSQ-1 Synthesised Signal Generator	£125
Farnell AP 30250A Power Supply 3V - 252A	£1750
Feedback PFG 605 Power Function Generator	£1950
Fluke 1100A - Calibrator	£1500
GH ELM EPR1 PCM Signalling Recorder	£2000
Guidline 9152 - 1/2 Battery Standard Cell	£550
Hewlett Packard 16300 - Logic Analyser (43 Channels)	£500
Hewlett Packard 16500A/B and C - Fitted with 16510A/1651A/16520A/16531A - Logic Analyser	from £2000
Hewlett Packard 331A - Distortion Analyser	£300
Hewlett Packard 333A - Distortion Analyser	£300
Hewlett Packard 334A - Distortion Analyser	£300
Hewlett Packard 3392A - 21MHz Synthesised Function Generator	£900
Hewlett Packard 3335A - Synthesised Signal Generator (200Hz-81MHz)	£2750
Hewlett Packard 3336C - Synthesised Signal Generator (10Hz-21MHz)	£800
Hewlett Packard 3455A - 8 1/2 Digit Multimeter (Autocon)	£500
Hewlett Packard 3456A - Digital Voltmeter	£550
Hewlett Packard 348A - HP - 1B Switch Control Unit (various Plug-ins available)	£1750
Hewlett Packard 35600A - Dual Channel Dynamic Signal Analyser	£600
Hewlett Packard 3566A - Selective Level Meter	£1500
Hewlett Packard 3711A/3712A/3718/3793B - Microwave Link Analyser	£900
Hewlett Packard 3746A - Selective Measuring Set	£200
Hewlett Packard 377A - PCM Terminal Test Set	£400
Hewlett Packard 3779A/3779C - Primary Mux Analyser	from £400
Hewlett Packard 3784A - Digital Transmission Analyser	£5000

Hewlett Packard 3785A - Jitter Generator + Receiver	£1250
Hewlett Packard 3790C - Signalling Test Set (No. 7 and ISDN)	£4250
Hewlett Packard P392A - Variable Attenuator	£250
Hewlett Packard 4192A - LF Impedance Analyser	£6500
Hewlett Packard 4252A - Digital LCR Meter	£350
Hewlett Packard 432A - C Meter	£900
Hewlett Packard 435A or B Power Meter (with 9481A/9484A)	from £400
Hewlett Packard 436A and 437B - Power Meter and Sensor	from £900
Hewlett Packard 4918A - (TIMS) Transmission Impairment M. Set	£1000
Hewlett Packard 4972A - Lan Protocol Analyser	£1250
Hewlett Packard 5183 - Waveform Recorder	£1250
Hewlett Packard 5288A - Frequency Counter 100MHz	£250
Hewlett Packard 5314A - (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5315A - Universal Counter (IEEE)	£400
Hewlett Packard 5335A - 200MHz High Performance Synthesizer Counter	£600
Hewlett Packard 5324A - Microwave Frequency Counter (500MHz-18GHz) Opts 1 + 3	£600
Hewlett Packard 5359A - High Resolution Time Synthesiser	£2000
Hewlett Packard 5370B - Universal Time Counter	£2000
Hewlett Packard 5384A - 225MHz Frequency Counter	£500
Hewlett Packard 5385A - Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005	£750
Hewlett Packard 6033A - Power Supply Autorange (20V - 30A)	£750
Hewlett Packard 6253A - Power Supply 20V - 3A Turn	£200
Hewlett Packard 6255A - Power Supply 40V - 1.5A Turn	£200

HEWLETT PACKARD 6251B
Power Supply 20V - 50A 3000 Discount for Quantities

Hewlett Packard 6264B - Power Supply (0-20V, 0-25A)	£300
Hewlett Packard 6271B - Power Supply 40V - 3A	£220
Hewlett Packard 6271B - Power Supply 50V - 3A	£220
Hewlett Packard 6634A - Quad Power Supply	£2000
Hewlett Packard 6632A - Power Supply (20V - 5A)	£800
Hewlett Packard 6612A - 20V - 25A System P.S.U.	£750
Hewlett Packard 7475A - 6 Pin Ploper	£280
Hewlett Packard 7580A - 8 Pin Ploper	£350
Hewlett Packard 7760 - Coax Dual Directional Coupler	£500
Hewlett Packard 8015A - 50MHz Pulse Generator	£500
Hewlett Packard 8165A - 50MHz Programmable Signal Source	£1250
Hewlett Packard 8180A - Data Generator	£1500
Hewlett Packard 8182A - Data Analyser	£1500
Hewlett Packard 8350A - Sweep Oscillator Mainframe (various plug-in options available)	£2500
Hewlett Packard 8355A - Wave Source Module 25.5 to 403Hz	£500
Hewlett Packard 8355A - Millimeter Wave Source Module 33-50GHz	£4250
Hewlett Packard 8405A - Vector Voltmeter	£350
Hewlett Packard 8620C - Sweep Oscillator Mainframe	from £550
Hewlett Packard 8640B - Signal Generator (512MHz - 1024MHz)	from £550
Hewlett Packard 8642A - Signal Generator (0-1 to 1050MHz) High Performance Synthesiser	£6500
Hewlett Packard 8656A - Synthesised Signal Generator (90MHz)	£650
Hewlett Packard 8656B - Synthesised Signal Generator	£1450
Hewlett Packard 8657A - Signal Generator (100MHz-1040MHz)	£1900
Hewlett Packard 8656D - Synthesised Signal Generator (10kHz-2600MHz)	£3250
Hewlett Packard 8750A - Storage Normaliser	£295
Hewlett Packard 8750A - Scalar Network Analyser	£1500
Hewlett Packard 8757A - Scalar Network Analyser	£2250
Hewlett Packard 8901A - Modulation Analyser	£1000
Hewlett Packard 8901B - Modulation Analyser	£2000
Hewlett Packard 8903E - Distortion Analyser	£1600
Hewlett Packard 8930B - Distortion Analyser (Mini)	£1500
Hewlett Packard 8930C - Distortion Analyser (Mini)	£2500
Hewlett Packard 8922B (RH) - Radio Comms Test Set (G.S.M.)	from £900
Hewlett Packard 9958A - Cellular Radio Interface	£1000
Keytek MZ-15/EC - Minizap 15V Hand-Held ESD Simulator	£1750
Kroh-Hite 2200 - Lin Log Sweep Generator	£995
Kroh-Hite 4024A - Oscillator	£250
Kroh-Hite 5200 - Sweep Frequency Generator	£250
Kroh-Hite 6500 - Phase Meter	£250
Leader LDM-170 - Signal Generator	£350
Leader 2216 - Signal Generator (100kHz-140kHz) AMP/CMW with built-in FM stereo modulator (mini)	£995
Marconi 1065B - Demultiplexer and Frame Alignment Monitor (new)	£90A
Marconi 2019 - 80kHz-1040MHz Synthesised Signal Generator	£750
Marconi 2019A - 80kHz-1040MHz Synthesised Signal Generator	£1000
Marconi 2111 - UHF Synthesiser (new)	£90A
Marconi 2185 - 1.5GHz Programmable Attenuator (new)	£90A
Marconi 2305 - Modulation Meter	£1750
Marconi 2337A - Automatic Distortion Meter	£1150
Marconi 2510 - True RMS Voltmeter	£700
Marconi 2871 - Data Comms Analyser	£500
Marconi 2955 - Radio Comms Test Set	£2000
Marconi 6310 - Sweep Generator - Programmable - new (2-20GHz)	£3500
Marconi 6550/6960 - Power Meter & Sensor	from £500
Marconi 6960 - Power Meter & Sensor	from £350
Marconi 891 - A/F Power Meter	£400
Philips PM5167 MHz Function Generator	£400
Philips 5160 - LF Synthesiser (G.P.I.B.)	£500
Philips 5518 - Synthesised Function Generator	£1500
Philips PM5519 - TV Pattern Generator	£350
Philips PM5716 - 50MHz Pulse Generator	£525
Primo 4000 - Sig. Dist. Meter (NEW)	£150
Quartzlock 2A - 0.1Hz Frequency Standard	£200
Racal 1992 - 1.5GHz Frequency Counter	£700
Racal 6111/6151 - GSM Radio Comms Test Set	£600
Racal Dana 9081/9092 - Synthesised Signal Generator 520MHz	from £400
Racal Dana 9094 - Synthesised Signal Generator 104MHz	£450
Racal Dana 9304 - True RMS RF Multimeter	£350
Racal Dana 9304A - R/E Multimeter (new version)	£375
Racal Dana 9303 - R/F Level Meter & Head	£650
Racal Dana 9917 - UHF Frequency Meter 560MHz	£175
Rohde & Schwarz LFM2 - 60MHz Group Delay Sweep Generator	£350
Rohde & Schwarz CMTA 94 - GSM Radio Comms Analyser	£695
Schaffner NSG 202A - Line Voltage Variation Simulator	£750
Schaffner NSG 222A - Interference Simulator	£700
Schaffner NSG 223 - Interference Generator	£700
Schlumberger 2720 - 1250MHz Frequency Counter	£400
Schlumberger 4031 - 1GHz Radio Comms Test Set	£4995
Schlumberger Stablock 4040 - Radio Comms Test Set	£1995
Schlumberger 7050/7055/7075 - Multimeters	from £350
Stanford Research DS 340 - 15MHz Synthesised Function (NEW) and Arbitrary Waveform Generator	£1200
Syston Donner 6030 - Microwave Frequency Counter (25-5GHz)	£1995
Tektronix AM503 - TM501 - PE302 - Current Probe Amplifier	£995
Tektronix PG505 - T8501 - SG503 - TM503 - Oscilloscope Calibrator	£1995
Tektronix 577 - Curve Tracer	£1150
Tektronix 1240 - Logic Analyser	£500
Tektronix 141A - PAL Test Signal Generator	£250
Tektronix AA5001 & TM5005 MF - Programmable Distortion Analyser	£1995
Tektronix TM5003 - APG 5101 - Arbitrary Function Generator	£1500
Tektronix - Plug-ins - many available such as SC504, SW503, SG502, PC505, FG504, FG501, TG501, TR503 - many more	
Time 9811 - Programmable Resistance	£400
Time 9814 - Voltage Calibrator	£550
Valhalla Scientific - 272A Programmable Resistance Standard	£500
Wandel & Goltermann PFJ-8 - Error Meter Test Set	£1500
Wandel & Goltermann PCM44 (4 options)	£950
Wandel & Goltermann MU30 - Test Point Scanner	£1500
Wayne Kerr 4225 - LCR Bridge	£500
Wavetek 171 - Synthesised Function Generator	£250
Wavetek 172B - Programmable Signal Source (0-0001Hz-13MHz)	£90A
Wavetek 184 - Sweep Generator - 5MHz	£390
Wavetek 3010 - 1-1GHz Signal Generator	£1250
Willtron 6405 - RF Analyser (1MHz-2GHz)	£90A
Willtron 6620S - Programmable Sweep Generator (3-6GHz-6-50Hz)	£950
Willtron 6747-20 - Sweep Frequency Synthesiser (10MHz-20GHz)	£950
Yokogawa 3535 - Analyser Recorder	£90A

MANY MORE ITEMS AVAILABLE -
SEND LARGE SAE FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED -
WITH 90 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING -
CARRIAGE & VAT TO BE ADDED TO ALL GOODS

Child Guard

Quite a few items for the *Child Guard* project took some running down and certain parts will be hard to find amongst your local suppliers' stocks. This applies particularly to the "semiconductor" devices, and possibly the heat sensors.

Starting with the 3-pin infra-red receiver chip type PIC26043SM (no, it is not a microcontroller), this is available from Farnell (☎ 0113 263 6311), code 139-877. Interestingly, the model was built using the PIC12043 but on checking for supplies it was found to be obsolete and we were advised of the suggested "substitute". If you have any PIC12043s you can certainly use these.

In a previous article, the HT12D decoder and HT12B encoder I.C.s were called for and we highlighted F.M.L. Electronics (☎ 01677 425840), who bought-in stocks especially. They still have stocks and they cost £1.49 each, plus £1 p&p. The TSL260 heat sensor came from Electromail (☎ 01536 204555), code 176-387.

The "active" buzzer (code 35-0030) and the single in-line (SIL) relay (code 60-0650) were both purchased from Rapid (☎ 01206 751166). The neat little 2-1mm power d.c. socket can be purchased, for the inclusive sum of £1, from Harrogate Electronic Services, 25 Regent Parade, Harrogate, N. Yorks, HG1 5AZ (☎ 01423 564353), quote code DCS21R. They can also supply a matching plug.

The internal PIR motion detector, with closed relay contacts, caused a small problem but you might find your local DIY store can help here. The one with the model is a Micromark (MM9466A) type, but they have failed to come back to us with a source. CPC of Preston (☎ 01772 654455) list a similar one and you could contact them for a price and handling charge, quote code SR00090.

The printed circuit board is available from the *EPE PCB Service*, code 241.

Variable Dual Power Supply

First sighting of the parts listing for the *Variable Dual Power Supply* project looked fairly straightforward and we were not expecting any supply problems, until we started looking-up the preferred wirewound potentiometer. This component used to be widely stocked and be reasonably priced, not anymore! We found one listed by Electromail (code 812-853) for just over £7. So, it may be wise to rethink and revert to a carbon or conductive polymer track type for about £1 to £2, even though they are rated with a 20% tolerance.

Just in time to get us out of a fix came the welcome news that Greenweld Electronics is to continue trading – see News page 644. They did carry quality surplus components, including wirewound pots, and it might pay to contact them by Fax on 01992 613020 or E-mail: greenweld@aol.com. Other companies you could try are: Bull Electrical (☎ 01273 203500), J&N Factors (☎ 01444 881965) and WCN Supplies (☎ 01763 226522).

The mains transformer in the prototype originally came from Circuit, but this company has now been absorbed by the Deltron Group into their subsidiary

Roxburgh, who do not run a mail order operation for small orders. We have not found a 15V-0V-15V 500mA type replacement, but advertisers should be able to offer a suitable alternative rated at around 1A to 2A. Provided it is chassis mounting, will fit in the case and has "tying" leads or wiring tags for connection to the p.c.b., it should do the job.

The same situation applies to the in-line bridge rectifier. You will probably be offered a 1A to 2A at 100V to 200V version. Any of these will work in this circuit.

The printed circuit board is available from the *EPE PCB Service*, code 242 (see page 700).

Loop Aerial SW Receiver

One of the major problems with selecting the components for the *Loop Aerial SW Receiver* project will be the final choice of the tuning capacitor. The price differentials can be quite staggering, ranging from the level of £18 (precision engineered) down to about £2.50 for the "transistor radio" type. So, it is definitely a case of shopping around for the "best buy".

Ideally, the tuning capacitor would be a quality 365pF single-gang, air-spaced, Jackson type "O". Unfortunately, this one tends to be expensive (approx. £18) and the solid-dielectric (Difaco) types, as used in the model, do not fair much better at £13.50 approx.

A low-cost option in this case (if there is one) is to purchase a quality "surplus" air-spaced item. To this end, you could try contacting the likes of Greenweld, Bull Electrical and J&N Factors who sometimes offer these as "bargain buys of the month" – see *Variable Dual Power Supply* section above. Any maximum value from 250pF to 500pF will do. Another option is to go for a miniature "transistor radio" solid-dielectric type. This will only set you back about £2.50. Don't forget to check the mounting arrangement before purchase.

Finally, you will have to purchase a larger than needed piece of stripboard and cut it down to size.

Data Logger-2

As promised, last month, the latest updated news on the supply of "specials" for the *Data Logger* project is that stocks of the new F87x family micro-controllers should now be appearing. In fact, an unprogrammed 40-pin PIC16F877, 4MHz version is available now from Forest Electronic Developments for the sum of £9.50, plus £3 for p&p. Phone 01425 274068 or check their web site at: <http://dSPACE.dial.pipex.com/robin.abbot/FED> for more details.

We also understand Farnell (☎ 0113 263 6311) will be receiving supplies around mid-August and have quoted us code 300-2690. They also have stocks of the 24LC256 serial EEPROM memory chip, code 300-1696.

The latest news from Magenta Electronics (☎ 01283 565435 or <http://magenta2000.co.uk>) is that they are now producing a complete kit, inclusive of case, eight 24LC256 EEPROM memory chips and a ready-programmed PIC, for the all-in figure of £49.95. The price of £10 for a pre-programmed PIC16F877 quoted last month is correct.

!! New from FED, PIC 16F877 Chips and Support !! PIC Programmers, Development Kit and C Compiler

PIC 16F877 Chip – now in stock!

Microchip's latest EEPROM device – 40-pin, 10-bit A/D converters, master/slave IIC bus, full duplex USART, 8K ROM, 352 bytes file registers, 256 bytes internal EEPROM, upwardly compatible with 16C74/16C77, but instant erase and rewrite. Supported by our programmers, PICDESIM and our new C Compiler.

PIC 16F877 devices, 4MHz, 40-pin DIP device £9.50

The FED PIC C Compiler

Supports all PIC16Cxx, 12C6xx devices

Integrated Compiler Environment includes FED's PICDE for simulation and debugging

Ring/Write for details or visit our Web Site:

£100 CD-ROM, £120 with printed manuals

<http://dSPACE.dial.pipex.com/robin.abbot/FED>

PIC & AVR Programmers

PIC Serial – Handles serially programmed PIC devices in a 40-pin multi-width ZIF socket. 16C55X, 16C6X, 16C7X, 16C8x, 16F8X, 12C508, 12C509, PIC 14090 etc. Also In-Circuit programming. Price: £45/kit, £50/built & tested.
PIC Introductory – Programs 8 & 18-pin devices: 16C505, 16C55X, 16C61, 16C62X, 16C71, 16C71X, 16C8X, 16F8X, 12C508/9, 12C671/2 etc. £25/kit.
AVR – 1200, 2313, 4144, 8515 in ZIF. Price: £40 kit £45 built & tested.
Scenix – SX18/SX28 in a 40-pin ZIF. Price: £40 kit £45 built & tested.

Programmers operate on PC serial interface. No hard to handle parallel cable swapping! Programmers supplied with instructions, + Windows 3.1/95/98/NT software. Upgrade Programmers from our web site!

AVR, PIC, Scenix – Windows Development

Assembler/Simulator allows development of your AVR, PIC or Scenix projects in one Windows program. Incorporate multiple files, view help file information directly from code, edit within project, build/track errors directly in source, then simulate. Many breakpoint types, follow code in source, set breakpoints in source. Run, single step, or-step over. **Logic Analyser Display!** Input stimuli includes clocks, direct values and serial data.
Profiler – examine and time frequently called routines use the information to optimise out bottle necks. PIC Version Simulates up to 50 times faster than MPSIM!
Cost £20.00. Specify PICDESIM (Includes Scenix) or AVRDESIM version

PIC BASIC Products – See our web site for details

16C74 version – 4 & 20MHz
£30.00 Kit, £35.00 Built & Tested
(Add £3.00 for 20MHz version)



Forest Electronic Developments
60 Walkford Road, Christchurch, Dorset, BH23 5QG
E-mail – robin.abbot@dSPACE.dial.pipex.com
Web Site – <http://dSPACE.dial.pipex.com/robin.abbot/FED>
01425-274068 (Voice/Fax)

Prices are fully inclusive. Add £3.00 for P&P and handling to each order. Cheques/POs payable to Forest Electronic Developments, or phone with credit card details.



ADD £2.60 P&P to all orders (Europe £3.50 Rest of World £5.00). We accept all major credit cards. Make cheques payable to Quasar Electronics. Prices include 17.5% VAT MAIL ORDER ONLY FREE CATALOGUE with order or send 2 x 1st class stamps (refundable) for details of our 150 kits & publications.

PROJECT KITS

OUR HIGH QUALITY PROJECT KITS ARE SUPPLIED WITH ALL COMPONENTS, PCBs & DETAILED INSTRUCTIONS

- **10W STEREO AMPLIFIER MODULE** Uses TDA2009 class AB audio power amp IC designed for quality stereo applications. 3068-KT £9.95
- **2 x 25W CAR BOOSTER AMPLIFIER** - suitable for use with an existing car stereo system. Connects to the output of the car stereo. Features stereo CD player or radio. Headrests included. PCB 75mm x 75mm. 124-KT £14.95
- **IR REMOTE TOGGLE SWITCH** Use any remote control unit to switch on/off relay on/off. 3058-KT £8.95
- **SPEED CONTROLLER** for any common DC motor up to 10715mA. Pulse width modulation gives maximum torque at all speeds. 3027-KT £9.95
- **PC 16C71 FOUR SERVO MOTOR DRIVER** Simultaneously control up to 4 servo motors (not supplied). Only 50mm x 70mm. 3102-KT £14.95
- **IMPULSION STEPPER MOTOR DRIVER** for any 5, 6 or 8 lead motor. 3 run modes. 3109-KT £12.95
- **PC BASED STEPPER MOTOR DRIVER** Connects to parallel port. Drives two stepper motors up to 5A each. 3113-KT £15.95
- **TRANSMITTER RECEIVER PAIR 2** - action key fob style. 300-375MHz Tx with 30m range. Receiver analogue module with extended decoder IC. 30A15 £13.75
- **STEREO VU METER** shows peak music power using 2 rows of 10 LEDs (green, yellow, red) moving bar display. 3030-KT £10.95
- **NEGATIVE POSITIVE ION GENERATOR** Standard Cockcroft-Walton multiplier circuit. Makes voltage experience required. 3057-KT £9.95
- **AM RADIO KIT** Tuned Radio Frequency front end and single strip AM radio IC & 2 stages of audio amplification. All components inc. speaker provided. PCB 22 x 102mm. 3053-KT £9.95
- **LED DICE CLASSIC** into electronics & circuit analysis. 7 LEDs simulate dice roll, score down & land on a number at random. 555 IC circuit. 3003-KT £7.95
- **STAIRWAY TO HEAVEN** Tests hand-eye co-ordination. Press switch when green segment of LED lights to climb the stairway - miss & start again! Good intro to several basic circuits. 3005-KT £7.95
- **ROULETTE LED** Roll some round the wheel, stores down & drops into a slot. 10 LEDs, CMOS decade counter & Op-Amp. Educational & fun! 3008-KT £9.95
- **DUAL LED DICE PC 16C54** circuit performs similar function to 3003-KT but two dice. Good intro to micro-computer. Software code supplied on disk. 3071-KT £11.95
- **AUDIO TO LIGHT MODULATOR** Controls intensity of one or more lights in response to an audio input. Safe, modern optoisolator design. Meets voltage experience required. 3018-KT £8.95
- **5V NEON TUBE FLASHER** Transistor circuit uses up 5V battery supply to flash the 25mm long neon tube. Adjustable flash rate (0.25-2 Secs). 3022-KT £10.95
- **LED FLASHER 5** ultra bright red LEDs flash in sequence or randomly. Ideal for model railways. 3052-KT £11.95
- **16C84 PC PROGRAMMER** Reads, programs & verifies. Uses any PC parallel port. All hardware, software & documentation needed to learn & test this IC provided. 3061-KT £21.95
- **SERIAL PC PROGRAMMER** for 8 & 16, 28 and 48 pin DIP serial programmed PICs. Third party software supplied expires after 21 days and costs US\$23 to register. 3098-KT £8.95

- **12-BIT PC DATA ACQUISITION SYSTEM** Use your PC to monitor and control external events and devices through its parallel port. 3118-KT £6.95
- **3V1.5V TO 5V BATTERY CONVERTER** Replace expensive 5V batteries with economic 1.5V batteries. IC based circuit steps up 1 or 2 'AA' batteries to give 3V1.5V. 3036-KT £8.75
- **LIGHT ALARM** Protect your valuables. Alarm sounds if circuit detects smallest amount of light. Price in each box set. 3026-KT £4.50
- **PIEZO SCREAMER** 110db of ear piercing noise. PCB fits in box with 2 x 35cm piezo elements built into their own resonant cavity. Use as an alarm siren or just for fun! 8-PIN. 3115-KT £6.95
- **COMBINATION LOCK** Versatile electronic lock combining main circuit & separate keypad for remote opening of lock. Relay supplied. 3029-KT £8.95
- **ULTRASONIC MOVEMENT DETECTOR** Crystal locked oscillator frequency for near 100% detection. High return stability and reliability. PCB 75 x 40mm houses all components. 4-7m range. Adjustable sensitivity. Output will drive internal relay/circuit. 3040-KT £12.95
- **PIR DETECTOR MODULE** 3-head assembled unit just 25x30mm as used in commercial burglar alarm systems. 3076-KT £8.25
- **TRAIN SOUNDS** 4 selectable sounds - whistle blowing, level crossing bell, chugging & chimey chime. All components inc. speaker supplied. 3001 £8.50
- **ANIMAL SOUNDS** Cat, dog, chicken and cow. Ideal for kids terrified bys and schools. All components inc. speaker supplied. 3010 £8.95
- **MUSIC BOX** Activated by light. Plays eight Christmas songs and 5 other tunes. All components inc. speaker supplied. 3104-KT £9.95
- **ROBOT VOICE EFFECT** Make your voice sound similar to a robot or Ewok, real fun for discos, school plays, theatre productions, radio stations and playing jokes on your friends when you answer the phone! PCB 60mm x 70mm. 1314-KT £7.95
- **FUNCTION GENERATOR** Quad Op-Amp oscillator & wave shaper circuit generates audio range square waves (5Hz-50kHz), triangle & pseudo sine outputs. 3002-KT £4.95
- **LOGIC PROBE** tests CMOS 3 TTL circuits & detects test pulses. Visual & audio indication of logic state. Full instructions supplied. 3024-KT £7.25
- **POCKET SAMPLER/DATA LOGGER** Sample analogue inputs from 0-2V and 0-20V. Unit fits into D-29H case supplied. PC powered. Software supplied. 3112-KT £18.95

SURVEILLANCE

High performance surveillance bugs. From assemblies supplied with sensitive electret microphone & battery instructions. All transmitters can be received on an ordinary VHF FM radio. Available in kit form (KIT) or assembled and tested (AST)

- **ROOM SURVEILLANCE KIT - MINIATURE SV TRANSMITTER** Easy to build & guaranteed to transmit 3000m. 2V Long battery life. 3-5V operation. Only 45x18mm. 3007AKT £4.95 or AS3007 £9.95
- **MKIT - MINIATURE SV TRANSMITTER** Our best selling bug. Super sensitive, high power - 500m range. 6V (over 110m with 12V supply and better range). 45x19mm. 3007BKT £5.95 or AS3018 £11.95
- **HPTX - HIGH POWER TRANSMITTER** High performance, 2 stage transmitter gives greater capability & higher quality reception 1000m range. 6-12V operation. Size 70x15mm. 3023AKT £8.95 or AS3032 £18.95
- **MKIT - MICRO-MINIATURE SV TRANSMITTER** The ultimate bug for its size, performance and price. Just 15x25mm. 500m range @ 9V. Good stability. 6-12V operation. 3015AKT £7.95 or AS3011 £14.95
- **VTX - VOICE ACTIVATED TRANSMITTER** Operates only when sounds detected. Low standby current. Variable trigger sensitivity, 500m range. Peaking circuit supported for maximum TX output. On/off switch. 6V operation. Only 60x35mm. 3026AKT £7.95 or AS3028 £14.95
- **HARD-WIRED BUG-TWO STATION INTERCOM** Each station has its own amplifier, speaker and mic. Can be set up as either a hard-wired bug or two-station intercom. 10m x 2-core cable supplied. 3021KIT £11.95 (KIT form only)
- **TWRX - TAPE RECORDER VOX SWITCH** Used to automatically create a tape recorder (not supplied) via its REMOTE socket when sounds are detected. All conversations recorded. Adjustable sensitivity & turn-off delay. 115x19mm. 3013KIT £8.95 or AS3013 £18.95
- **TELEPHONE SURVEILLANCE KIT - MINIATURE TELEPHONE TRANSMITTER** Attaches anywhere to phone line. Requires only a phone if used. Useful in your car and near both parties. 300m range. Uses line as serial & power source. 20x45mm. 3015KIT £4.95 or AS3016 £19.95
- **TRI - TELEPHONE RECORDING INTERFACE** Automatically record all conversations. Connects between phone line & tape recorder (not supplied). Operates recorders with 1.5-12V battery systems. Powered from line. 50x30mm. 3003KIT £5.95 or AS3003 £15.95
- **TFA - TELEPHONE PICK-UP AMPLIFIER WIRELESS PHONE BUG** Place pickup coil on the phone line or near phone handset and hear both sides of the conversation. 3052KIT £12.95 or AS3055 £19.95
- **1 WATT FM TRANSMITTER** Easy to construct. Delivers a crisp, clear signal. Two-stage circuit. Kit includes microphone and requires a simple open dipole aerial. Supply: 6-30V DC. PCB 42mm x 45mm. 1019-KT £24.95
- **4 WATT FM TRANSMITTER** Combines three RF stages and an audio pre-amplifier. Professional microphone supplied or you can use a separate pre-amplifier circuit. Antenna can be an open dipole or Ground Plane. Ideal project for those who wish to get started in the fascinating world of FM broadcasting and want a good basic circuit to experiment with. Supply: 12-18V DC. PCB 44mm x 148mm. 1029-KT £19.95

X FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X FACTOR PUBLICATIONS can be found in our catalogue. All minimum order charges for reports and plans is £5.00 PLUS names! P&P

- **SUPER-EAR LISTENING DEVICE** Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £14.50
- **TELEPHONE BUG PLANS** Build your own state-of-the-art telephone bug. Suitable for any phone. Requires over 250 metres - more with good receiver. Made from easy to obtain, cheap components. R006 £22.50
- **LOCKS** - How they work and how to pick them. The fact based report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Priced with information and illustrations. R008 £3.50
- **RADIO & TV JOKER PLANS** We show you how to build three different circuits for distracting TV picture and sound plus FM radio! May upset your neighbours & the authorities! DISCRETION REQUIRED. R017 £3.50
- **INFINITY TRANSMITTER PLANS** Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just call the target phone's address the unit will hear all room sounds. Great for burglarized security. R015 £2.95
- **THE ETHER BOX CALL INTERCEPTOR PLANS** Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! R025 £3.00
- **20 MHz FUNCTION GENERATOR** Coarse and fine-tuning TTL output. 2V p.p. Uses MAX933 IC. Full assembly and operating instructions and box provided. 3101-KT £48.95

CASH CREATOR BUSINESS REPORTS Need ideas on how to make some hard cash? We'll tell you just what you need! You get 40 reports (approx. 600 pages) on floppy disk that give you information on setting up different businesses. You also get valuable reproduction and duplication rights so that you can set the manuals as you like. R030 £7.50

Bell College of Technology
Almada Street
Hamilton ML3 0JB
Tel: 01698 283100
Fax: 01698 459790



Make your expertise pay!

In today's world you need qualifications to obtain and keep employment. Our open learning courses make obtaining those qualifications as convenient as possible.

Choose from our dozens of SOA accredited units, either singly to update your skills or as a group to obtain a Higher National Certificate.

- Learn at your own pace in your own home
- Support from professional engineers via phone, FAX and the Internet
- Courses from Introductory Bridging Modules to HNC Electronics
- Units from Programmable Logic Controllers to Engineering Computing

DONT DELAY - we are waiting to hear from you.

Contact: Laura Murdoch, Open Learning Co-ordinator
Tel: 01698 283100 extension 214.

E-mail: l.murdoch@bell.ac.uk

Web: <http://floti.bell.ac.uk/openlearning>

Member of the British Association for Open Learning
Prestew Centre for Financial Times Management



Bell College of Technology is a registered charity No. SC 021176, providing quality Higher Education and training opportunities for all.



SQUIRES

MODEL AND CRAFT TOOLS
A comprehensive range of Miniature Hand and Power Tools
and now an extensive range of
ELECTRONIC COMPONENTS
featured in a fully illustrated

336-page Mail Order Catalogue

1999 Issue

SAME DAY DESPATCH
FREE POST & PACKING

Catalogue free of charge to addresses in United Kingdom.

For overseas send 6 International Reply Coupons to:

Squires, 100 London Road,
Bognor Regis, West Sussex
PO21 1DD

Tel: 01243 842424

Fax: 01243 842525

SHOP NOW OPEN




SURVEILLANCE KITS

Sepia Technologies Ltd specialise in the production of top quality surveillance kits designed to operate on either FM/Air band frequencies. All kits are supplied with easy to follow instructions. Circuit diagrams and high quality components and pc.b.s

TRANSMITTING PEN KIT

PTX

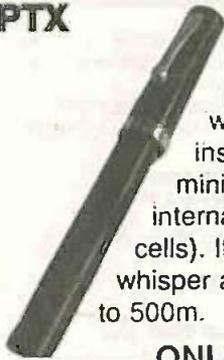


A breakthrough. When assembled this quality Sheaffer pen appears just like any other working pen, yet concealed inside is a fully working micro miniature transmitter with its own internal power supply (3 x button cells). It will pick up the slightest whisper and transmit over a range of up to 500m.

ONLY £27.95 inc. P&P
All parts included except batteries.

ADAPTOR BUG KIT

ADT

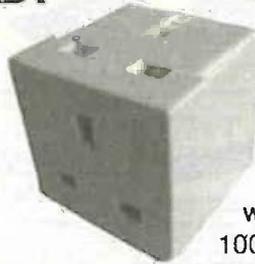

When assembled this appears just like any other fully functioning two-way mains adaptor, yet concealed inside is a powerful mains powered transmitter which will pick up the slightest whisper and transmit up to 1000m. Ideal bugging device – just plug in and go.

ONLY £24.95 inc. P&P
All parts required included.

ROOM MONITORING KITS

UMTX ULTRA MICRO ROOM TRANSMITTER
ONLY £14.95 inc. P&P

Without a doubt the smallest transmitter kit in the world – only 10mm x 16mm, powered by 3V-12V. Range up to 1000m.

SMTX SUPER MICRO ROOM TRANSMITTER KIT
ONLY £12.95 inc. P&P

Micro-sized transmitter kit, only 20mm x 20mm – the most popular by far. Range up to 1200m, powered by 3V-12V.

HPTX HIGH POWERED ROOM TRANSMITTER KIT
ONLY £14.95 inc. P&P

A high powered micro transmitter kit, yet still only 24mm x 24mm. Range up to 1800m, powered by 6V-12V.

UPTX ULTRA HI-POWER ROOM TRANSMITTER KIT
ONLY £17.95 inc. P&P

Ultra high power transmitter kit with a superb range of 3000m, yet still only measures 16mm x 38mm, powered by 9V-12V.

VTX VOICE-ACTIVATED ROOM TRANSMITTER KIT
ONLY £18.95 inc. P&P

A variable sensitivity controlled Vox circuit which activates its own transmitting circuit from the slightest whisper. Only 20mm x 65mm. Range up to 1200m, powered by 9V-12V.

MPTX MAINS POWERED ROOM TRANSMITTER
ONLY £18.95 inc. P&P

A powerful transmitter kit measuring only 30mm x 40mm including power supply circuit. Range up to 1000m. Can be concealed anywhere!!! 110V/240V.

COUNTER SURVEILLANCE KITS

RFD BUG DETECTOR
ONLY £29.95 inc. P&P

A pocket-size kit only 40mm x 50mm which will locate all those hidden bugs. L.E.D. and sounder with gain control to pinpoint devices. 9V required.

RFD II BUG DETECTOR
ONLY £44.95 inc. P&P

A professional unit with multi L.E.D. readout, sounder and audio

confirm. Will also locate most telephone devices. 9V required. Only 60mm x 100mm.

TELEPHONE MONITORING KITS

MTTX MICRO TELEPHONE TRANSMITTER KIT
ONLY £14.95 inc. P&P

Smallest kit available – only 10mm x 18mm, powered by the telephone line. Transmits only when phone is in use. Range up to 1000m.

STTX MINIATURE TELEPHONE TRANSMITTER KIT
ONLY £12.95 inc. P&P

Measures only 20mm x 15mm. Powered by line, with a range up to 1500m. Transmits only when phone is in use.

HTTX HI-POWER TELEPHONE TRANSMITTER KIT
ONLY £15.95 inc. P&P

The most powerful available, up to 3000m – yet still only 20mm x 30mm. Transmits only when phone is in use. Line powered.

ATS TELEPHONE RECORDING INTERFACE KIT
ONLY £12.95 inc. P&P

Connects between telephone line and cassette recorder. Automatically switches on tape when phone is used. Powered by line. Only 15mm x 25mm.

TRACKING TRANSMITTER KIT

TTX II TRACKING TRANSMITTER KIT
ONLY £19.95 inc. P&P

Ideal for tracking applications, gives out a continuous signal – fully variable. Range up to 3000m, yet only 25mm x 55mm. 9V-12V power. Complete with details of how to adapt a receiver to locate/trace.

ROOM/TELEPHONE TRANSMITTER KIT
RTTX ROOM AND TELEPHONE TRANSMITTER KIT
ONLY £24.95 inc. P&P

A breakthrough – this line-powered unit will transmit all telephone conversations when phone is in use, then when the call ends it will monitor and transmit all room conversations. 35mm x 35mm. Range up to 1200m.

HOW TO ORDER

BY POST

Please send cheque or money order (cash by registered post). Overseas customers please add £5.00 per order.

BY PHONE

7.30 am to 9 pm – 7 days

We accept all major credit cards.
Immediate despatch

VISITORS BY APPOINTMENT ONLY

SEPIA TECHNOLOGIES LTD

2 DUKE STREET
SUTTON GOLDFIELD
WEST MIDLANDS
B72 1RJ

TEL: 0121 362 1862

FAX: 0121 362 1881

E-MAIL: sepiatek@aol.com

WE EXPORT WORLDWIDE

VIDEOS ON ELECTRONICS

A range of videos selected by *EPE* and designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc



BASICS

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more.


Order Code VT201

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits.

Order Code VT202

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained.

Order Code VT203

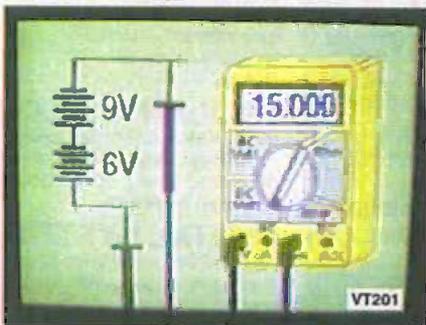

VT204 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply.

Order Code VT204

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc.

Order Code VT205

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits.

Order Code VT206

£34.95 each
inc. VAT & postage

Order 8 or more get one extra FREE
Order 16 get two extra FREE

VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output.

Order Code VT102

VT103 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path.

Order Code VT103

DIGITAL

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation.

Order Code VT301

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc.

Order Code VT302

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc.

Order Code VT303

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits.

Order Code VT304

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices.

Order Code VT305

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work.

Order Code VT306


RADIO

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system.

Order Code VT401

VT402 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver.

Order Code VT402

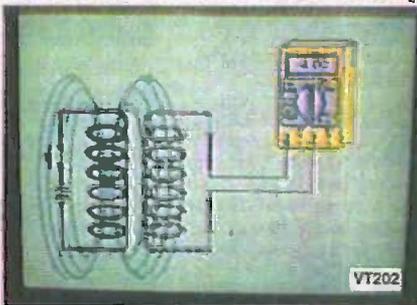

VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding.

Order Code VT403


MISCELLANEOUS

VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers.

Order Code VT501

VT502 57 minutes. Laser Technology A basic introduction covering some of the common uses of laser devices, plus the operation of the Ruby Rod laser, HeNe laser, CO₂ gas laser and semiconductor laser devices. Also covers the basics of CD and bar code scanning.

Order Code VT502

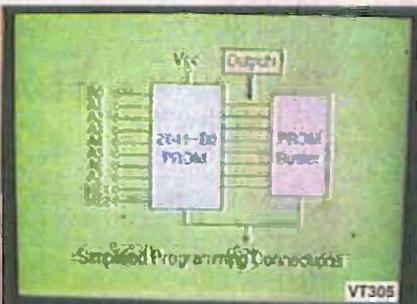

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co., an American supplier. We are the worldwide distributors of the PAL and SECAM versions of these tapes. (All videos are to the UK PAL standard on VHS tapes unless you specifically request SECAM versions.)

ORDERING: Price includes postage to anywhere in the world.

OVERSEAS ORDERS: We use the VAT portion of the price to pay for airmail postage and packing, wherever you live in the world. Just send £34.95 per tape. All payments in £ sterling only (send cheque or money order drawn on a UK bank).

Visa and Mastercard orders accepted - please give card number, card expiry date and cardholder's address if different from the delivery address.

Orders are normally sent within seven days but please allow a maximum of 28 days, longer for overseas orders.

Send your order to: Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)

Direct Book Service is a division of Wimborne Publishing Ltd., Publishers of *EPE*

Tel: 01202 881749. Fax: 01202 841692

Due to the cost we cannot reply to overseas orders or queries by Fax.

E-mail: editorial@epemag.wimborne.co.uk

Everyday Practical Electronics are pleased to be able to offer all readers these

ELECTRONICS CD-ROMS

NEW ANALOGUE ELECTRONICS by Mike Tooley

Analogue Electronics is a complete learning resource for this most difficult branch of electronics. The CD-ROM includes a host of virtual laboratories, animations, diagrams, photographs and text as well as a SPICE electronic circuit simulator with over 50 pre-designed circuits.

FUNCTIONS


The component values on all circuits can be edited and the user can use the simulation engine to see how the value of each component affects circuit performance. You can, for instance, alter frequency and phase angle and plot outputs on a virtual oscilloscope or show load line graphs etc.

COVERAGE


Sections on the CD-ROM include: Fundamentals -- Analogue Signals (5 sections), Transistors (4 sections), Waveshaping Circuits (6 sections); Op.Amps -- 17 sections covering everything from Symbols and Signal Connections to Differentiators; Amplifiers -- Single Stage Amplifiers (8 sections), Multi-stage Amplifiers (3 sections); Filters -- Passive Filters (10 sections), Phase Shifting Networks (4 sections), Active Filters (6 sections); Oscillators -- 6 sections from Positive Feedback to Crystal Oscillators; Systems -- 12 sections from Audio Pre-Amplifiers to 8-Bit ADC plus a gallery showing representative p.c.b. photos.

- Includes SPICE circuit simulator with over 50 circuits
- Unique virtual laboratories
- Editable assignments
- Design parameters for circuits included
- Complete hi-fi amplifier case study

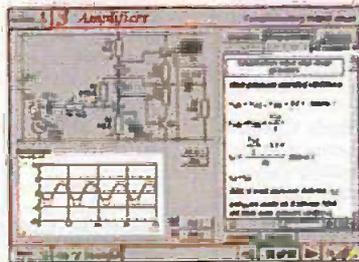Prices for each of the two CD-ROMs above are:



Complimentary output stage.

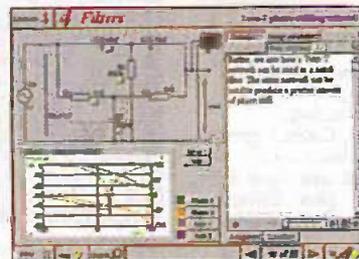

Twin-T phase shifting network



Gallery -- Wideband Amplifier

DIGITAL ELECTRONICS by Mike Tooley

Digital Electronics builds on the knowledge of logic gates covered in *Electronic Circuits & Components* (below), and takes users through the subject of digital electronics up to the operation and architecture of microprocessors. The virtual laboratories allow users to operate many circuits on screen.

FUNDAMENTALS

Fundamentals introduces the basics of digital electronics including binary and hexadecimal numbering systems, ASCII, basic logic gates and their operation, monostable action and circuits, and bistables -- including JK and D-type flip-flops.

COMBINATIONAL LOGIC

Multiple gate circuits, equivalent logic functions and specialised logic functions such as majority vote, parity checker, scrambler, half and full adders. Includes fully interactive virtual laboratories for all circuits.


SEQUENTIAL LOGIC
Introduces sequential logic including clocks and clock circuitry, counters, binary coded decimal and shift registers.

DIGITAL SYSTEMS


A/D and D/A converters and their parameters, traffic light controllers, memories and microprocessors -- architecture, bus systems and their arithmetic logic units.

GALLERY

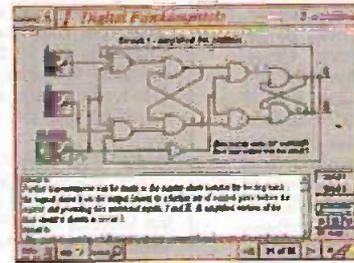
A catalogue of commonly used IC schematics taken from the 74xx and 40xx series. Also includes photographs of common digital integrated circuits and circuit technology.



Virtual laboratory -- Flip-Flops

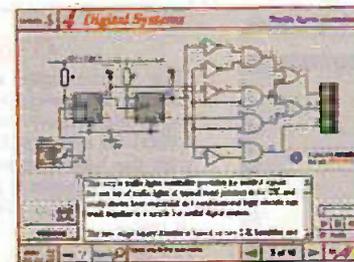

Virtual laboratory -- Traffic Lights

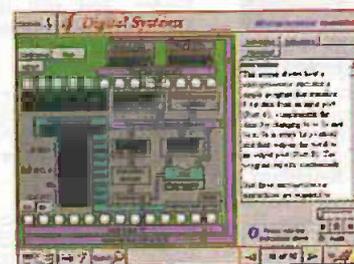

Microprocessor

Hobbyist/Student£45 inc VAT
Institutional (Schools/HE/FE/Industry).....£99 plus VAT
Institutional 10 user (Network Licence)£199 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

ELECTRONIC CIRCUITS & COMPONENTS + THE PARTS GALLERY by Mike Tooley

Electronic Circuits & Components provides an introduction to the principles and application of the most common types of electronic components and shows how they are used to form complete circuits. The virtual laboratories, worked examples and pre-designed circuits allow students to learn, experiment and check their understanding as they proceed through the sections on the CD-ROM. Sections on the disk include: **Fundamentals:** units & multiples, electricity, electric circuits, alternating


circuits. Passive Components: resistors, capacitors, inductors, transformers.
Semiconductors: diodes, transistors, op.amps, logic gates. **Passive Circuits . Active Circuits**

The Parts Gallery -- many students have a good understanding of electronic theory but still have difficulty in recognising the vast number of different types of electronic components and symbols.

The Parts Gallery helps overcome this problem; it will help students to recognise common electronic components and their corresponding symbols in circuit diagrams. Sections on the disk include: **Components , Components Quiz, Symbols, Symbols Quiz, Circuit Technology**

Hobbyist/Student£34 inc VAT
Institutional (Schools/HE/FE/Industry)£89 plus VAT
Institutional 10 user (Network Licence)£169 plus VAT

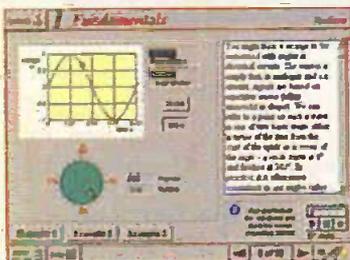(UK and EU customers add VAT at 17.5% to "plus VAT" prices)




Virtual laboratory -- sinusoids



Circuit technology screen

TWO APPLICATIONS ON ONE CD-ROM

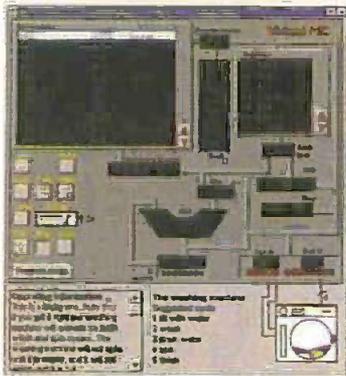Interested in programming PIC microcontrollers? Learn with **PICtutor** by John Becker



The Virtual PIC

Developed from John's *EPE* series, this highly acclaimed CD-ROM, together with the PICtutor experimental and development board, will teach you how to use PIC microcontrollers with special emphasis on the PIC16x84 devices. The board will also act as a development test bed and programmer for future projects as your programming skills develop. This interactive presentation uses the specially developed Virtual PIC Simulator to show exactly what is happening as you run, or step through, a program. In this way the CD provides the easiest and best ever introduction to the subject. Nearly 40 Tutorials cover virtually every aspect of PIC programming in an easy to follow logical sequence.

HARDWARE

Whilst the CD-ROM can be used on its own, the physical demonstration provided by the PICtutor Development Kit, plus the ability to program and test your own PIC16x84s, really reinforces the lessons learned. The hardware will also be an invaluable development and programming tool for future work once you have mastered PIC software writing.

Two levels of PICtutor hardware are available – Standard and Deluxe. The Standard unit comes with a battery holder, a reduced number of switches and no displays. This version will allow users to complete 25 of the 39 Tutorials.

The Deluxe Development Kit is supplied with a plug-top power supply (the Export Version has a battery holder), all switches for both PIC ports plus l.c.d. and 4-digit 7-segment l.e.d. displays. It allows users to program and control all functions and both ports of the PIC and to follow the 39 Tutorials on the CD-ROM. All hardware is supplied fully built and tested and includes a PIC16F84 electrically erasable programmable microcontroller.



Deluxe PICtutor Hardware

PICtutor CD-ROM

Hobbyist/Student£45 inc. VAT
 Institutional (Schools/HE/FE Industry)£99 plus VAT
 Institutional 10 user (Network Licence).....£199 plus VAT

HARDWARE

Standard PICtutor Development Kit£47 inc. VAT
 Deluxe PICtutor Development Kit£99 plus VAT
 Deluxe Export Version£96 plus VAT
 (UK and EU customers add VAT at 17.5% to "plus VAT" prices)

MODULAR CIRCUIT DESIGN by Max Horsey and Philip Clayton


Developed from Max Horsey's *Teach-In* series *A Guide to Modular Circuit Design* (*EPE* Nov '95 to Aug '96). This highly acclaimed series presented a range of tried and tested analogue and digital circuit modules, together with the knowledge to use and interface them. Thus allowing anyone with a basic understanding of circuit symbols to design and build their own projects.

Essential information for anyone undertaking GCSE or "A" level electronics or technology and for hobbyists who want to get to grips with project design. Over seventy different Input, Processor and Output modules are illustrated and fully described, together with detailed information on construction, fault finding and components, including circuit symbols, pinquits, power supplies, decoupling etc.

Single User Version £19.95 inc. VAT
 Multiple User Version £34 plus VAT

(UK and EU customers add VAT at 17.5% to "plus VAT" prices)

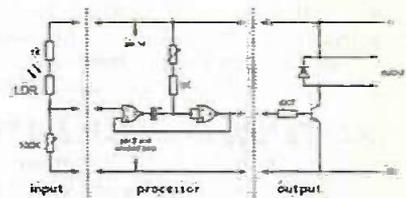designing your circuit
 simply select your modules from the wide choice available,
 read how they work and join them up to make your circuit



"I found that I could design a circuit without my teacher's help. And it worked! Everything was to hand – which chips to use – and which pins did what." Andrew Preston (GCSE student)

A Web Browser is required for Modular Circuit Design – one is provided on the *EPE CD-ROM No. 1* (see below) but most modern computers are supplied with one.

Minimum system requirements for these CD-ROMs: PC with 486/33MHz, VGA+256 colours, CD-ROM drive, 8MB RAM, 8MB hard disk space. Windows 3.1/95/98/NT, mouse, sound card (not required for *PICtutor* or *Modular Circuit Design*).

CD-ROM ORDER FORM

Please send me:

- Electronic Circuits & Components +The Parts Gallery
 Analogue Electronics
 Digital Electronics
 PICtutor

- Hobbyist/Student
 Institutional
 Institutional 10 user

Note: The software on each version is the same, only the licence for use varies.

- PICtutor Development Kit – Standard
 PICtutor Development Kit – Deluxe Deluxe Export

Note: The PICtutor CD-ROM is not included in the Kit prices.

- Modular Circuit Design – Single User
 Modular Circuit Design – Multiple User

Full name:

Address:

Post code: Tel. No:

Signature:

I enclose cheque/PO in £ sterling payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard: £ Card expiry date:

Card No:

Please supply name and address of cardholder if different to the delivery address.

ORDERING

ALL PRICES INCLUDE UK POSTAGE

Student/Single User/Standard Version price includes postage to most countries in the world. EU residents outside the UK add £5 for airmail postage per order.

Institutional, Multiple User and Deluxe Versions – overseas readers add £5 to the basic price of each order for airmail postage (do not add VAT unless you live in an EU country, then add 17½% VAT or provide your official VAT registration number).

Send your order to:

Direct Book Service
 33 Gravel Hill, Merley, Wimborne
 Dorset BH21 1RW
 (Mail Order Only)


Direct Book Service is a division of Wimborne Publishing Ltd. To order by phone ring

01202 881749. Fax: 01202 841692

We cannot reply to overseas orders by Fax. Goods are normally sent within seven days.

Demos (not Modular Circuit Design) available on the *EPE CD-ROM No. 1* (Free with the November '98 issue) – send £2 for this CD-ROM if you require the demos. Minimum order for credit card payment is £5.

PRACTICAL OSCILLATOR DESIGNS

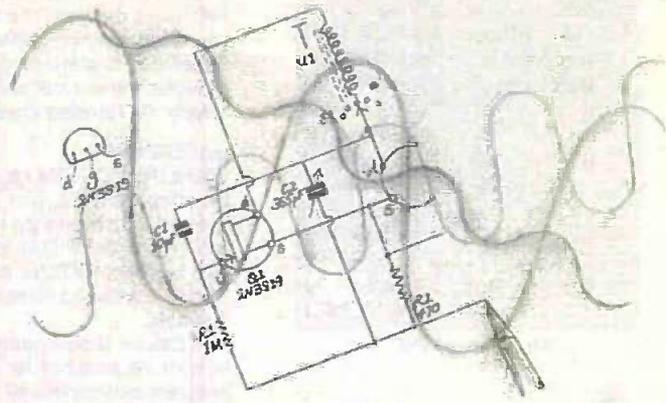

RAYMOND HAIGH

Most text books deal with oscillators in a theoretical way. This series, prepared with the electronics enthusiast and experimenter very much in mind, is intensely practical. Tried and tested circuits are fleshed out with component values, and their vices and virtues are exposed.

PART THREE – THE ARMSTRONG, MEISSNER, FRANKLIN AND BUTLER OSCILLATORS, PLUS PROBES FOR R.F. VOLTAGE MEASUREMENTS.

EARLIER articles covered the Hartley and Colpitts oscillators, and their variants, in some detail. This month, circuits attributed to Armstrong, Meissner, Franklin and Butler will be considered.

With the Hartley circuit, feedback is applied to a tapping in the tuning inductor: with the Colpitts, the tuning capacitor is tapped. Quite apart from questions of performance, these circuits are convenient because of the way they simplify coil design.

ARMSTRONG OSCILLATORS

Oscillators attributed to E. H. Armstrong, the great American radio pioneer, involve more complicated inductor arrangements. Two of his designs rely on a separate winding to feed maintaining energy back to the tuned circuit. Another has a pair of tuned circuits with feedback via the anode/grid capacitance of a coupling valve.

Conceived during the decade following Lee De Forest's invention of the triode, the circuits were of crucial importance to the emerging radio industry and, from 1917 to 1924, there was much acrimonious patent litigation between De Forest and Armstrong. The American courts decided in De Forest's favour on the basis of a legal technicality. However, in Britain, the validity of Armstrong's patents, and of his claim to be the true originator, has generally been upheld.

GETTING IN TUNE

In their original form, with triode valves as the maintaining devices, the circuits became known as tuned grid, tuned anode, and tuned grid/tuned anode. Clearly, the circuits take their names from the way the frequency determining components are connected to the valve.

The tuned grid circuit came to be adopted almost universally as the local oscillator in valve superhet receivers. (The superhet receiver was invented by Armstrong whilst he was a US Army Signals Officer stationed in France during the First World War.) No doubt the ability to connect coil and capacitor to ground made it the natural choice for this purpose.

With the growing use of bipolar transistors during the 1960's, the valve tuned grid circuit fell from use as it did not adapt well to the new low-impedance devices, or to the type of mixer/oscillator stages which became standard in mass produced radios. It was, however, replaced by another very early oscillator circuit, the Meissner; more on this later.

The subsequent development of field-effect transistors, with their more valve-like characteristics, saw its resurrection as the local oscillator in simple, wide coverage communications receivers. A typical application of the tuned gate oscillator stage of the radio receiver front-end is shown in Fig. 1a.

OSCILLATORS IN SUPERHET RECEIVERS

Superhet oscillators operate at a higher frequency than that of the incoming signals. This higher frequency is combined with the incoming signal in a mixer (see Fig. 1b), and the difference between the two, the intermediate frequency, or i.f., is selected by tuned circuits and amplified.

Domestic radios have an i.f. of between 455kHz and 470kHz. Older, high-performance valve sets had an i.f. of 1.6MHz, and modern communications receivers have multiple i.f.s which can include 40MHz, 10MHz, 455kHz and lower frequencies.

Tuning of the signal frequency and oscillator stages is via a dual-ganged tuning capacitor, and some provision must be made, therefore, for this frequency difference to be constantly maintained over the tuning capacitor swing. Taking the medium wave band as an example, and assuming an i.f. of 460kHz, the signal frequency tuned circuit will sweep from 1600kHz down to 530kHz, whilst the oscillator must cover 2060kHz (1600+460) to 990kHz (530+460).

The different coverage is achieved by making the oscillator coils of lower inductance than the signal frequency or r.f. coils, and by placing a capacitor in series with the oscillator gang of the tuning capacitor in order to reduce its value when fully meshed. The series capacitor is called a "padder". By this means, the oscillator circuits can be made to track the signal frequency circuits almost perfectly, and the 460kHz difference is maintained over the full swing of the variable tuning capacitor. (Strictly speaking, absolutely perfect tracking is achieved at three points on the dial.)

ARMSTRONG OSCILLATOR – Tuned Gate F.E.T. Version

We can now consider the functions of the various components of the Armstrong oscillator stage (Fig. 1a) in our receiver "front-end" circuit of Fig. 1, where the tuned circuit formed by L2 and variable capacitor VC1a determines the frequency of oscillation. The swing reducing padder capacitor C2 is connected in series with the coil L2

PLEASE NOTE

In the "Tuned Circuit Calculations" panel in Part 1 (July '99 issue) page 522, the third and fourth equations for f should be as follows and not as printed:

$$f = \frac{5.033}{\sqrt{LC}}$$

$$f = \frac{159.155}{\sqrt{LC}}$$

to simplify band switching (this has virtually the same effect as connecting it directly in series with VC1a). Trimmer capacitor VC2 permits the precise matching of the minimum capacitance in the r.f. and oscillator circuits, and fixed capacitor C3 is required to optimise tracking only on the longwave band.

Coupling or "reaction" winding L1 must be connected so that the feedback is in-phase, and the correct arrangement is indicated on the circuit diagram. Resistor R1, capacitors C1 and C7 decouple the oscillator from the supply rail, and the tuned circuit is connected to the gate (g) of transistor TR1 via capacitor C5. Gate resistor R3 ensures correct biasing.

Valve and f.e.t. versions of this circuit are prone to "squegging", i.e., the transistor goes in and out of oscillation, usually at a low radio frequency. Resistor R2 is included to inhibit this. If the problem is encountered despite the inclusion of R2, modify the time constant of the gate input circuit by reducing the value of C5 and/or R3. Increasing the value of R1 may also effect a cure.

BIASING

Biasing has to be optimised or the circuit will not oscillate over the full swing of a 365pF tuning capacitor on the highest shortwave range (10MHz to 30MHz). The source bias resistor is, therefore, made up of R4 and preset potentiometer VR1. If such extensive coverage is not required, a single fixed resistor of around 2.2 kilohms can be substituted when 2N3819 transistors are used, or 4.7 kilohms when J310s are wired into circuit.

The output is taken from the "hot" end of the tuning coil via a low value capacitor C4. It must be fed into a high impedance load or oscillation will be inhibited. Output voltage is reasonably constant over the full swing of a 365pF variable capacitor, and the waveform is of excellent quality.

Connecting a diode from gate to ground/0V (diode cathode (k) to ground) to limit forward conduction of the j.f.e.t.'s gate makes oscillation weak and erratic on the highest shortwave range, and, for this reason, it has been omitted. If extended high frequency coverage is not required, connecting a diode will limit oscillation amplitude and prevent a slight flattening of the waveform which can occur at low frequencies.

ARMSTRONG INDUCTORS

The feedback or reaction winding L1 must be tightly coupled to the tuned winding L2. The rule-of-thumb adopted for valve versions of the circuit was to make the number of turns on the feedback coil between 30

per cent and 50 per cent of the turns on the tuned winding. It was also recognised that the capacitance across the feedback winding had to be kept to an absolute minimum in order to avoid "squegging" and other forms of erratic operation.

With the f.e.t. version of the circuit, a ratio of 10 per cent up to 2MHz, then progressively increasing to 50 per cent on the highest shortwave range, should ensure reliable oscillation. Wind feedback windings over the "earthy" end of tuned windings, separating the two by a layer of insulating tape: coupling must be tight or oscillation may not be maintained over the full tuning range.

MOSFET MIXER

A well tried mixer circuit completes our receiver circuit and is illustrated in Fig.1b, where incoming signals, tuned by L4 and VC1b, are applied to gate 1 (g1) of the dual-gate MOSFET TR2. The oscillator voltage is fed to TR2 gate 2 (g2).

For best results, mixers of this kind require an oscillator injection of at least 1V, and preferably close on 2V r.m.s. Clearly, therefore, the output voltage of the tuned gate oscillator, and the high input impedance of the MOSFET mixer, make this an effective combination. The whole arrangement is reminiscent of the old triode-hexode valve frequency changers, where the grid of the triode section was extended into the electrode stream of the hexode mixer in order to inject the local oscillation.

ARMSTRONG'S OSCILLATORS

Three early valve oscillators are attributed to Edwin Howard Armstrong: the tuned grid, the tuned anode and the tuned grid/tuned anode. They were all used in transmitters, and the tuned grid circuit was adopted, almost universally, as the local oscillator in superhet receivers until bipolar transistors began to take the place of valves.

When field-effect transistors (f.e.t.s), with their more valve-like characteristics, were introduced, it saw a revival in receivers with some pretensions to high performance. A typical circuit is given in Fig.1.

The f.e.t. version of Armstrong's circuit oscillates readily from audio up to 50MHz or more. A near perfect sinewave is produced, and output is reasonably constant over the tuning capacitor swing. On the downside, a separate feedback winding is required on the tuning coil, and output impedance, with this particular circuit, is high.

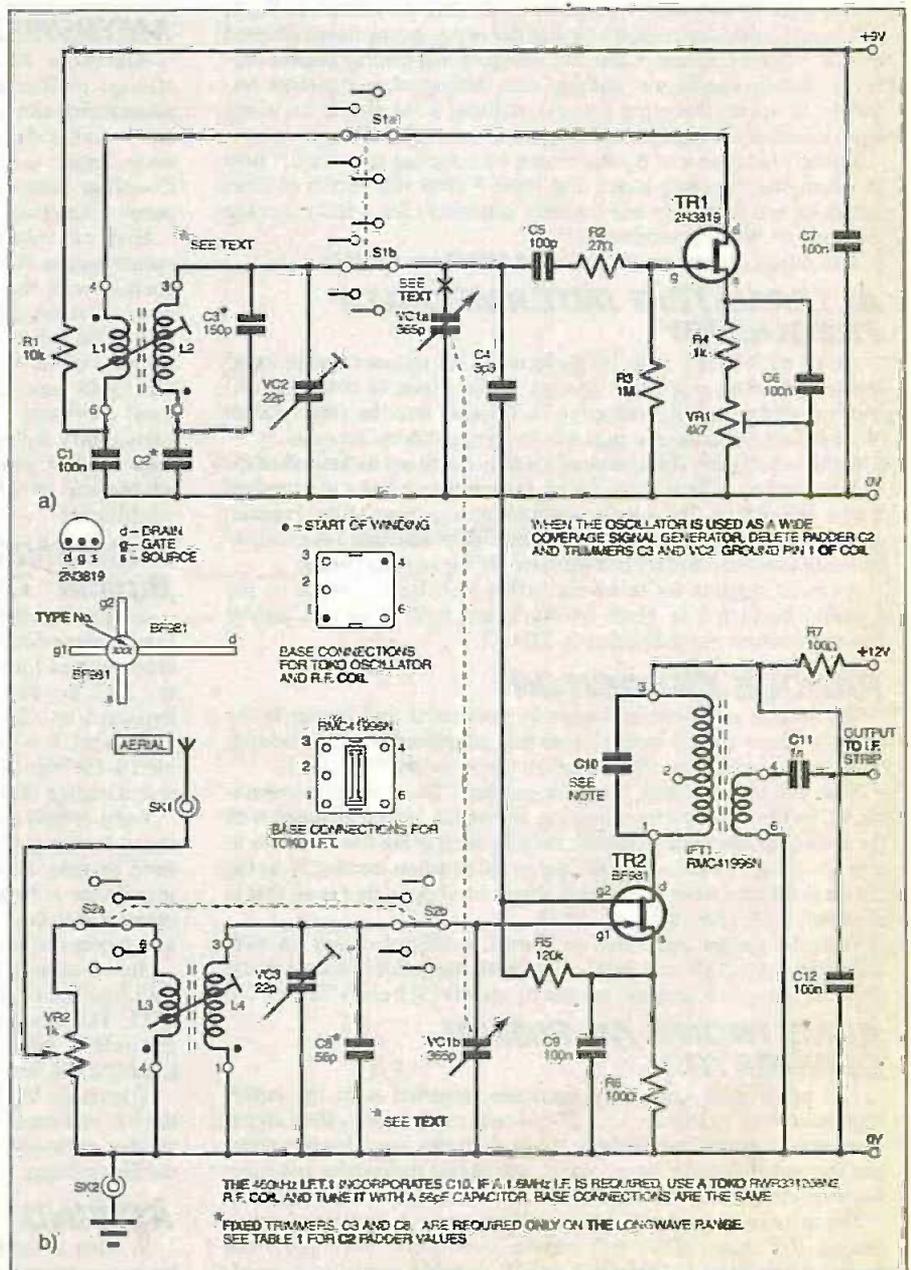


Fig.1. Radio receiver "front-end" using an f.e.t. version of an Armstrong oscillator. Suitable for receivers covering 150kHz to 30MHz. See Table 2 for details of tuning coils and capacitors.

Here the two circuits are coupled by means of capacitor C4. Readers who have coil packs from old valve receivers will find that they usually work well with this dual f.e.t. arrangement.

INPUT CIRCUIT

The aerial is coupled to the r.f. tuned circuit by means of coil L3 and potentiometer VR2 acts as a simple, but effective, input attenuator to prevent strong signals causing cross modulation. Trimmer capacitor VC3 matches the minimum capacitance in the r.f. tuned circuit to that of the oscillator section. Capacitor C8 is required only on the longwave band to ensure good oscillator tracking.

Source (s) bias for TR2 is provided by resistor R6, which is bypassed by capacitor C9. Bias on TR2 gate 2 is fixed at around 1V (the optimum level when MOSFETs are used as mixers) by connecting it to the source via resistor R5. If difficulty is encountered in securing oscillation at the maximum tuning capacitor setting on the highest shortwave range, try increasing the value of this resistor to about 220 kilohms.

Supply line decoupling is effected by R7 and C12, and the mixer output is taken from the secondary of IFT1, at pin 4. The primary of this r.f. transformer forms the drain load of TR2 and is, of course, tuned to the intermediate frequency. In practice, the setting of the adjustable core, within the coil former, is very broad.

MIXER/OSCILLATOR COMBINATION

Our receiver front-end, formed by combining the circuits in Fig. 1, will significantly out-perform the bipolar or i.c. arrangement adopted in most domestic radios. Correctly set up, it will display greater sensitivity, reduced oscillator "pulling" (the shifting of the oscillator frequency by strong incoming signals), reduced noise and, if the aerial input attenuator is used judiciously, lower cross-modulation.

Readers may wish to try the circuit by coupling it to the i.f. strip in a domestic transistor radio, and Table 1 gives full details of Toko inductors and trimming and padding capacitors for a full coverage (150kHz to 30MHz) receiver.

The values quoted are for an i.f. of 450kHz to 470kHz.

ALTERNATIVE INTERMEDIATE FREQUENCY

An i.f. of 1.6MHz is to be preferred. This reduces image interference (spurious responses spaced, in the main, at twice the i.f.) and it would permit the output to be injected into the aerial socket of a car radio or domestic portable to form a double superhet.

Unfortunately, the Toko range of inductors does not include all of the double-winding coils required for an Armstrong oscillator in a receiver with a 1.6MHz i.f. The simpler inductor arrangement of the Franklin oscillator does, however, permit the windings of standard Toko coils to be series connected to produce inductors of the required value.

A circuit suitable for receivers with a 1.6MHz i.f., based on the Franklin oscillator, is given in Fig. 3, and coil types and padder capacitor values are scheduled in Table 3.

PADDER CAPACITOR

The padder capacitor is invariably connected into circuit in the manner shown for C2 in Fig. 1a, as this simplifies range switching. (Coil and capacitor are controlled by the same switch bank.)

With this arrangement, however, padder C2 and variable capacitor VC1a form a capacitive tapping across L2, which changes with the setting of the tuning control, thereby increasing the variation in output voltage. Locating the padder in the position marked X on the circuit diagram avoids this, and if single band operation is all that is required, this is the preferred option.

With the padder connected as shown, oscillator output on MW varies between 2.5V and 3.6V r.m.s. With the padder located in the alternative position, output changes by only 0.1V from 3.5V to 3.6V.

ARMSTRONG AS SIGNAL GENERATOR

The tuned gate Armstrong oscillator, together with the buffer stage described in Part 2 (Aug '99), would make an excellent signal generator. Constructors wishing to use it in this way should substitute the coils listed for the r.f. stage, and delete the padder and trimmer capacitors (C2, C3, and VC2).

The bottom end of coil L2 should, of course, be connected to ground (0V line). This will ensure continuous coverage from around 150kHz to 30MHz if a 365pF variable capacitor is used. Output coupling capacitor, C4, will have to be kept very small, and attenuation circuitry may have to be provided, in order to prevent the overloading of the buffer stage.

TABLE 1:
Tuned-Gate F.E.T. Version of Armstrong Oscillator
Tuned circuit components for r.f. and oscillator stages of a superhet receiver with a 460kHz i.f. (See Fig. 1)

Band	R.F. Coil L3/L4 Fig.1b	Oscillator Coil L1/L2 Fig.1a	Padder C2 (pF) Fig.1a	Range MHz
LW	CAN1A350EK	RWR331208N2	150	0.14 - 0.3
MW	RWR331208N2	YMRS80046N	330	0.53 - 1.6
SW1	154FN8A6438EK	154AN7A6440EK	680	1.5 - 4
SW2	154FN8A6439EK	154AN7A6441EK	1500	3.5 - 12
SW3	KXNK3767EK	KXNK3766EK	2000	10 - 30

Notes:

(1) The quoted tuning ranges are approximate. The tuning capacitor should have a minimum capacitance of not much more than 10pF and a maximum capacitance of at least 300pF.

(2) To improve tracking on the LW band only, a 56pF capacitor is connected across the r.f. stage tuned winding, L4. (C8 in Fig.1b).

(3) To improve tracking on the LW band only, a 150pF capacitor is connected across the oscillator stage tuned winding, L2. (C3 in Fig.1b).

(4) The coil reference numbers are for Toko Inductors.

MEISSNER OSCILLATOR

Alexander Meissner's valve oscillator represented an early attempt to increase the isolation of the tuned circuit from the maintaining device. In its original valve form, coil windings in the anode and grid circuits provide the necessary feedback, and a separate tuned winding determines the frequency of oscillation. Coupling between the valve and the tuned circuit is, therefore, purely inductive.

High r.f. voltages are developed across the tuned circuit in the output stages of transmitters, and the elimination of a direct connection with the valve reduces the risk of inter-electrode break down. Despite this advantage, the circuit fell out of use before the end of the valve era.

Once again, the gradual shift from valves to transistors during the 1960s saw the re-introduction of Meissner's circuit in the local oscillator stage of radio receivers. It seems to have been particularly suited to the then new, low impedance devices with their modest gains. Single transistor mixer/oscillators, using an adaptation of Meissner's feedback system, became standard world-wide.

MEISSNER OSCILLATOR - Bipolar Transistor Version

Simple superhets invariably incorporate the front-end shown in Fig. 2, where coils L3 and L4 couple transistor TR1 to the oscillator tuned circuit formed by L5 and tuning capacitor VC1b. Base bias for TR1 is provided by resistors R1 and R2; and resistor R3, bypassed by C2, sets the bias voltage on the emitter (e). Signal input, via L1, is tuned by the combination of L2 and VC1a, and coupled to the base of TR1 via a low impedance tapping to avoid excessive damping on the resonant circuit.

Long aerials are connected to the receiver via L1, again to minimise damping. (The input attenuator VR2 shown in Fig. 1b could be used to great advantage here.) Short whip aerials present a high impedance at frequencies up to 30MHz or so, and they are usually connected to the "hot" end of L2, through socket SK2. Connections to a ferrite rod aerial are shown in Inset A.

Signal mixing (strictly speaking combining) takes place within TR1, and the required 460kHz output is selected by i.f. transformer IFT1. The tuned primary of this transformer is tapped to ensure a reasonable match with the collector circuit. Resistor R4 and capacitor C4 decouple the circuit from the supply line.

Trimmers, VC2 and VC3, enable the minimum capacitances in the r.f. and oscillator tuned circuits to be matched, and C5 is the padder capacitor which modifies the frequency coverage of the oscillator stage.

REWIND

In order to simplify coil production, the emitter of TR1 is sometimes connected to a tapping on the tuned winding. Whilst this arrangement compromises the best feature of Meissner's oscillator, the feedback paths are the same. Commercially produced three winding coils are no longer available to the home constructor, and

readers who wish to experiment with this circuit will have to either wind their own coils or adopt the emitter tapping modification so that standard Toko inductors can be used.

Base connections for Toko coils are also given in Fig.2, and type numbers and padder values are scheduled in Table 2. Readers who wish to wind their own coils should give the collector winding 10 per cent of the number of turns on the tuned winding up to 2MHz or so, then gradually increase the ratio to 25 per cent on the coils for the highest shortwave range.

The emitter winding should have between two and three turns on all ranges. The three windings must be tightly coupled, and connected as shown in Fig.2.

PERFORMANCE

The circuit is effective in simple transistor radios where the swing of the tuning capacitor VC1 is usually less than 300pF and shortwave coverage does not extend much above 18MHz. However, oscillation is not likely to be maintained on the shortwave ranges when the tuning capacitor setting approaches 300pF. On the highest range (10MHz to 30MHz), oscillation will probably fade when the tuning capacitor is set above 150pF.

To avoid these problems, the oscillator in some early transistor radios ran at half the normal frequency on the highest shortwave range, and the second harmonic was used for mixing purposes.

TABLE 2:


Bipolar Transistor Version of the Meissner Oscillator
Tuned circuit components for r.f. and oscillator stages of a simple superhet receiver with a 460kHz i.f. (See Fig.2 with Inset B for circuit diagram)

Band	R.F. Coil L1/L2	Oscillator Coil L3/L5	Padder C5 (pF)	Range MHz
LW	CAN1A350EK	RWR331208N2	150	0.14 - 0.3
MW	RWR331208N2	YMRS80046N	330	0.53 - 1.6
SW1	BKANK3333R	BKANK3426R	680	1.5 - 4
SW2	BKANK3334R	KANAK3337R	1500	3.5 - 12
SW3	BKXN3335R	MKANK3428R	2000	10 - 30

Notes:

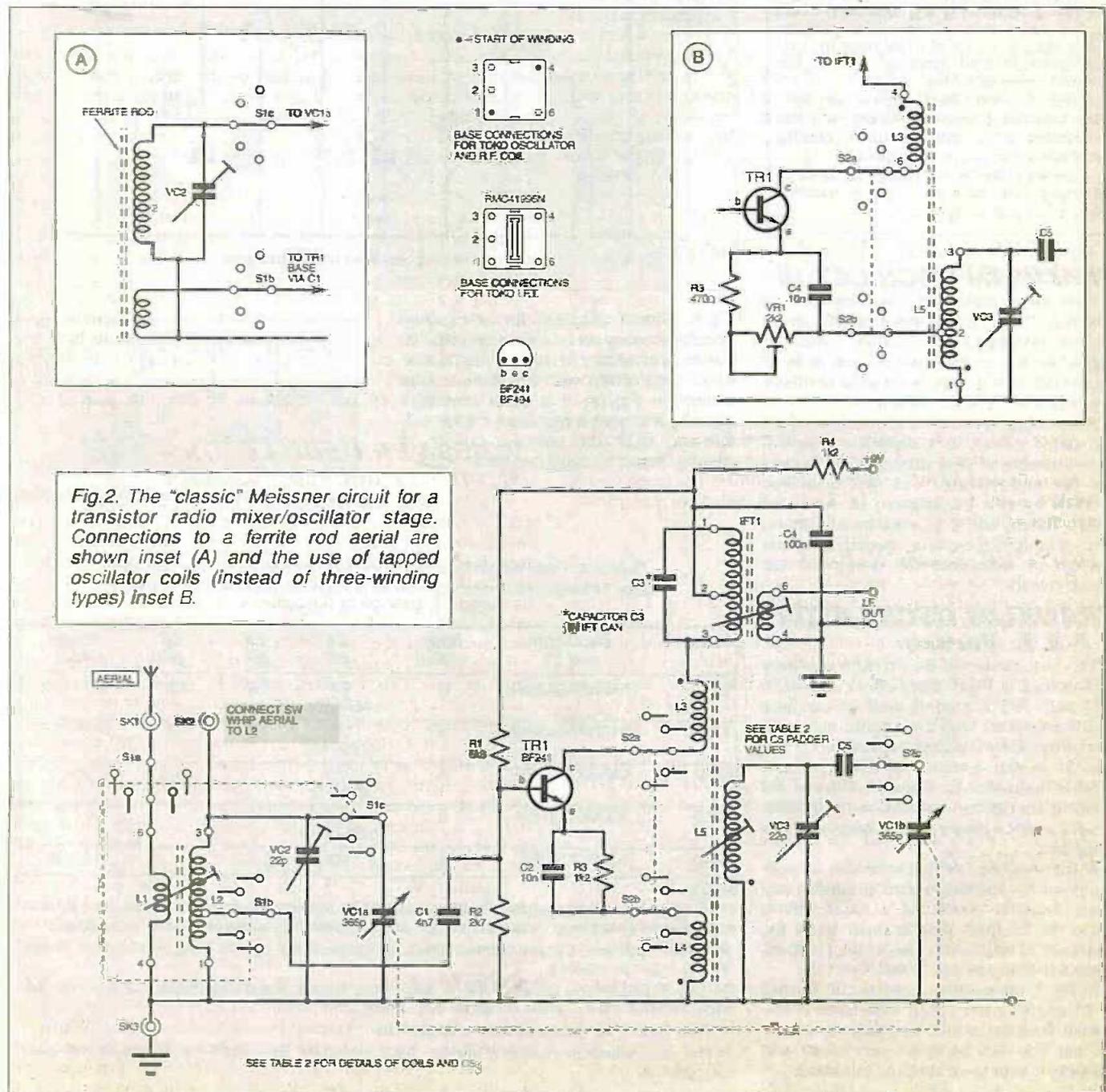- (1) The quoted tuning ranges are approximate. The tuning capacitor should have a minimum capacitance of not much more than 10pF and a maximum capacitance of at least 300pF. A miniature polythene dielectric capacitor would be appropriate for this circuit.
- (2) The coil reference numbers are for Toko inductors.

Even this modest level of performance may prove difficult to achieve if TR1 emitter resistor R3 is not selected to suit the transistor used. In the modified emitter circuit given in Inset B, the



value of R3 has been reduced and a preset potentiometer, VR1, has been added in series with it so that the biasing can be optimised.

Only one low cost transistor is used, and it is probably this, more than anything else, that has made the circuit so popular with radio manufacturers for almost 40 years. Readers who wish to experiment with simple superhets would be well advised to adopt the circuit based on the Armstrong oscillator, shown in Fig.1, or the adaptation of the Franklin given in Fig.3.

Although field-effect transistors are more expensive, these circuits are more willing to oscillate with adverse LC ratios, band switching is simpler, and performance is superior.

FRANKLIN OSCILLATOR

British radio engineer, Charles S Franklin, added an LC tuned circuit to Abraham and Bloch's multivibrator and produced his oscillator. The tuning inductor comprises an untapped single winding, and range switching is considerably simplified.

Waveform quality is acceptable for radio receivers and simple signal generators, but the output voltage varies with the setting of the tuning capacitor to a greater extent than is the case with some other circuits. Measures can be taken to regulate the output, but this is at the expense of more complicated range switching.

Loading on the tuned circuit is very light, even with the transistor version, and this contributes to the good frequency stability for which the circuit is renowned.

Operation below 100kHz or so tends to be erratic. The circuit will, however, oscillate up to 60MHz and beyond.

FRANKLIN OSCILLATOR

Involved for much of his working life with Marconi, C. S. Franklin was a prolific inventor. He originated the variable capacitor, ganged tuning, coaxial feeders and, of more direct interest to us here, a versatile oscillator that is renowned for its stability.

His design involves the addition of an LC tuned circuit to a capacitor coupled, i.e. an astable or free running, multivibrator. The multivibrator was first described in 1918 by two Frenchmen, H. Abraham and E. Bloch, and it is a matter of conjecture whether Franklin modified their concept or independently developed the whole circuit.

FRANKLIN OSCILLATOR - F.E.T. Version

The f.e.t. version of the Franklin oscillator is illustrated in Fig.3. Field-effect transistors TR1 and TR2 are configured as common source amplifiers with their drains and gates cross coupled by feedback capacitors, C3 and C4/C5, in the manner of Abraham and Bloch's multivibrator. Resistors R1 and R4 are the drain (d) load resistors and gate resistors R2 and R3 ensure correct biasing of the transistors.

A free running multivibrator can be synchronised by injecting pulses at almost any point. Franklin connected a tuned circuit across the feedback path in order to fix the frequency of oscillation, one of the feedback capacitors being tapped to facilitate this.

In Fig.3, the parallel tuned circuit formed by L1 and VC1 has a high impedance at resonance. Because of this, feedback capacitors, C4 and C5, can be made very small and damping is kept to an absolute minimum.

In the original valve version, these capacitors were no more than 1pF, and the oscillator was renowned for its low level of drift. To ensure reliable oscillation down to 150kHz with this wide-range f.e.t. version, the value of C4 and C5 has to be increased to 10pF. If the circuit is to be used exclusively at higher frequencies and maximum frequency stability is important, these components should be reduced in value until oscillation is only just maintained.

This circuit is decoupled from the power supply by resistor R5 and capacitor C8. Signal output is taken from the drain (d) of TR2 via d.c. blocking capacitor C7. If the oscillator is to be used in a radio receiver, the output should be applied to gate 2 of the dual-gate MOSFET TR2 shown in the mixer stage in Fig.1b.

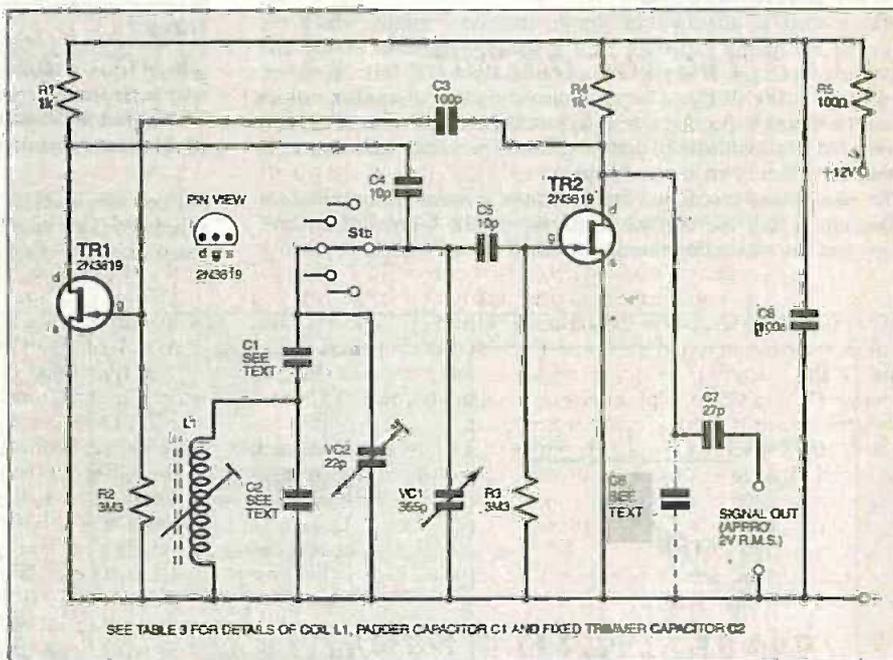


Fig.3. Circuit diagram for a Franklin oscillator using an f.e.t. Can be used as the local oscillator in a superhet receiver in conjunction with the mixer stage shown in Fig.1b. If a wide coverage signal generator is required, delete C1, C2 and VC2 and connect coil(s) L1 directly across tuning capacitor VC1.

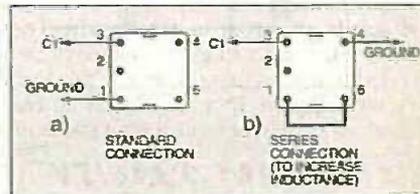


Fig.4. Connections to Toko coils listed in Table 3.

TABLE 3: Field-Effect Transistor Version of the Franklin Oscillator
Table of tuned circuit components for a superhet radio with a 1.6MHz I.F.
(See Fig.3 for circuit diagram).

Band	Oscillator coil L1	Base wiring	C1 pF	C2 pF	C6 pF	Range MHz
LW	154FN8A6438EK	B	74 (47+27)	39	220	0.16 - 0.45
MW	154FN8A6438EK	B	110 (100+10)	18	82	0.53 - 1.6
SW1	KANSK4960EG	A	335 (330+5)	-	6.8	1.6 - 5
SW2	KXNK3767EK	B	950 (680+270)	-	-	4 - 13
SW3	KXNK3766EK	A	1500	-	-	10 - 30

Notes:

- (1) The quoted tuning ranges are approximate. The tuning capacitor should have a minimum capacitance of not much more than 10pF and a maximum capacitance of at least 300pF.
- (2) Fixed capacitors, C2, are connected across the oscillator coil, on Long and Medium Waves only, to improve tracking.
- (3) See Fig.1b for the circuit of the r.f. and mixer stages. Fixed capacitors, C2, are not connected across the r.f. tuned circuit on any range.
- (4) See Table 1 for details of the r.f. stage coils.
- (5) The coil reference numbers are for Toko inductors. See Fig.4 for details of the base connections.

It should be noted that J310 transistors will not work in this circuit: 2N3819s should be used.

FRANKLIN SUPERHET OSCILLATOR

The tuning arrangements depicted in Fig.3 enable the circuit to be used as the local oscillator in a superhet receiver. Tuning coil L1 has a single winding, and this makes it possible to series connect coils in the Toko range to create inductance values appropriate to the production of a 1.6MHz intermediate frequency.

Padder capacitor C1 limits the swing of tuning capacitor VC1. Trimmer VC2 permits the matching of minimum capacitances in the r.f. and oscillator circuits, and C2 is required to ensure correct tracking only on the long and medium wave bands. Suitable Toko inductors and capacitor values are listed in Table 3. Oscillator coil connections are shown in Fig.4.

REGULATING THE OUTPUT

The output from Franklin's circuit varies with the setting of the tuning capacitor to a greater extent than the Armstrong or Butler oscillators and, with swings of 10pF to 365pF, the variation can be significant. (The impedance of the tuned circuit falls as the capacitance ratio is increased, and this reduces the level of feedback from the drain of TR1 to the gate of TR2, especially at low frequencies.)

Output can be made more constant between 150kHz and 5MHz by connecting capacitor C6 (shown dashed) between TR2 drain and ground (0V). The improvement is particularly noticeable between 150kHz and 450kHz, where the variation is from 1.25V to 4V r.m.s. without the capacitor, and 2.9V to 3.1V with the component in circuit. If this capacitor is not provided, it may be necessary to increase C4 and C5 to 27pF to ensure oscillation down to 150kHz when the circuit is used as a signal generator.

Including capacitor C6 will, of course, necessitate another switch bank, and this detracts from the extreme simplicity of the arrangement. However, the circuit will function perfectly well with the mixer stage shown in Fig.1b without this component. Used in a radio receiver with a 1.6MHz i.f., the lowest oscillator frequency is 1750kHz when tracking a signal input of 150kHz. Fade at low frequencies is not, therefore, a problem.

I.F. TRANSFORMER FOR 1.6MHz

Toko do not list a 1.6MHz i.f. transformer, but one can be contrived by tuning a medium wave r.f. coil with an external capacitor. The details are given in Fig.1b. The 1.6MHz i.f. output can be injected, via a short length of coaxial cable, into the aerial socket of a car radio tuned to the extreme h.f. end of the medium wave band. This combination forms a double superhet which, if properly aligned, is capable of quite a high standard of performance.

WAVEFORM QUALITY

Waveform quality varies with the setting of the tuning capacitor VC1. A perfect sinewave can be obtained when the values of C4 and C5 are as low as possible, consistent with reliable oscillation. A fairly high ratio of capacitance to inductance in the tuned circuit will make the selection of the feedback capacitors less critical.

Only spot-frequency or narrow-band versions of the oscillator can be made to produce a perfect waveform in this way. Fortunately, radio receivers are tolerant of a measure of local oscillator waveform distortion.

FRANKLIN SIGNAL GENERATOR

If Fig.3 is to be used as a simple signal generator, the output should be buffered; the amplifier described last month would be suitable. In view of the output level at low frequencies (approximately 3V r.m.s.), it would be prudent to locate a switched attenuator between oscillator and buffer and gang it with the range switch. By this means a reasonably constant output could be ensured.

Use the tuned windings of the coils listed for the r.f. stage when the circuit forms a signal generator. Readers who like to wind their own coils should refer to the first part of the series for details of a suitable range of inductors.

EXTENDING THE RANGE

Operation of the circuit becomes erratic below 100kHz. It will, however, oscillate above 100MHz with the appropriate tuned circuits.

Constructors can hand-wind self-supporting coils for these frequencies, or purchase S18 type coils from the Toko range. Toko inductors for v.h.f. working were scheduled in connection with the Colpitts oscillator, and a Jackson 25pF C809 type variable capacitor would be suitable for tuning purposes.

The circuit displays an increasing reluctance to oscillate above 35MHz unless a 22pF capacitor is wired in the C6 position.

BUTLER OSCILLATOR

Also known as the cathode-coupled oscillator, Frederick Butler developed his circuit whilst he was serving with the RAF during World War Two. He published details of it in 1944.

The original design was, of course, based on the use of valves. It shares the advantage, with the Franklin, of only requiring a single winding, untapped coil. The tuned circuit is not, however, isolated from the active devices to the same degree.

Variants of Butler's circuit sometimes form the basis of the oscillator stage in domestic radio i.c.s in order to simplify coil design and switching (e.g., the CA3123E and the TDA1083).

BUTLER OSCILLATOR - Series Fed F.E.T. Version

The Butler oscillator can be configured in either the series or shunt fed modes and a typical series fed arrangement, with field-effect transistors (f.e.t.s) as the active devices, is given in Fig.5.

Configured as a source follower, f.e.t. TR1 has a high input impedance at the gate, and a low output impedance at the source. Grounded gate stage TR2 has a low input impedance at the source and a high output impedance at the drain. In this way, the circuit ingeniously ensures a good match for the direct coupling of the active devices and imposes minimum damping on the tuned circuit formed by L1 and VC1.

The frame and moving vanes of VC1 are grounded for convenience, and the tuner is connected across the coil via bypass capacitor C3. Output from the drain (d) of TR2 is coupled to the gate (g) of TR1 via feedback capacitor C1. Signal output is developed across source resistor R2 and C2 acts as a d.c. blocking capacitor.

Despite the indirect connection of the tuning capacitor, which places the supply voltage across its vanes, this circuit is to be preferred to the shunt fed version depicted in Fig.6, which is more reluctant to oscillate at range extremes.

Substituting J310s for the 2N3819 field-effect transistors increases the output but biasing is more critical and operation can be erratic. Readers wishing to try J310s should reduce the common source resistor R2 to 150 ohms.

Output is pretty constant from 150kHz to 10MHz, but falls at higher frequencies when the ratio of tuning capacitance is high, and when 2N3819s are used. This fall in output is avoided when J310s are the active devices.

Shunt Fed - F.E.T. Version

The shunt fed Butler oscillator circuit depicted in Fig.6 is usually adopted when there is a need to ground the tuning coil. With this version, the tuned circuit is connected to the high impedance gate of

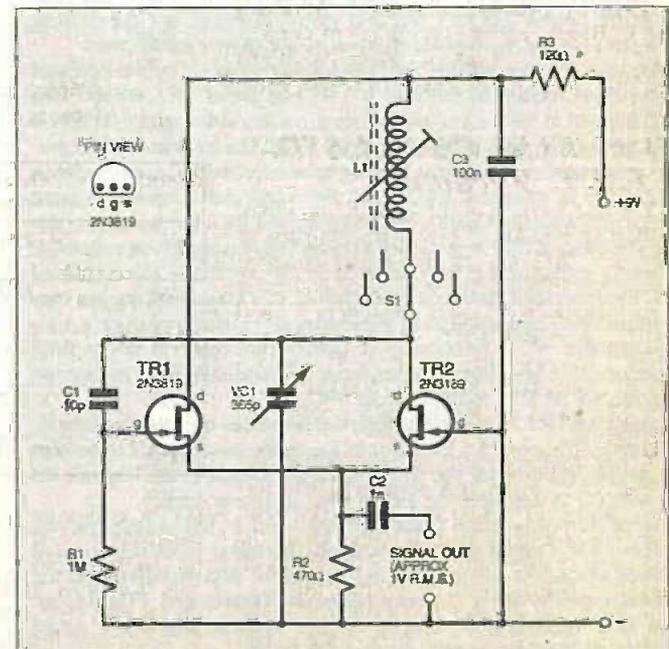


Fig.5. Circuit diagram for a field-effect transistor (f.e.t.) version of the series fed Butler oscillator.

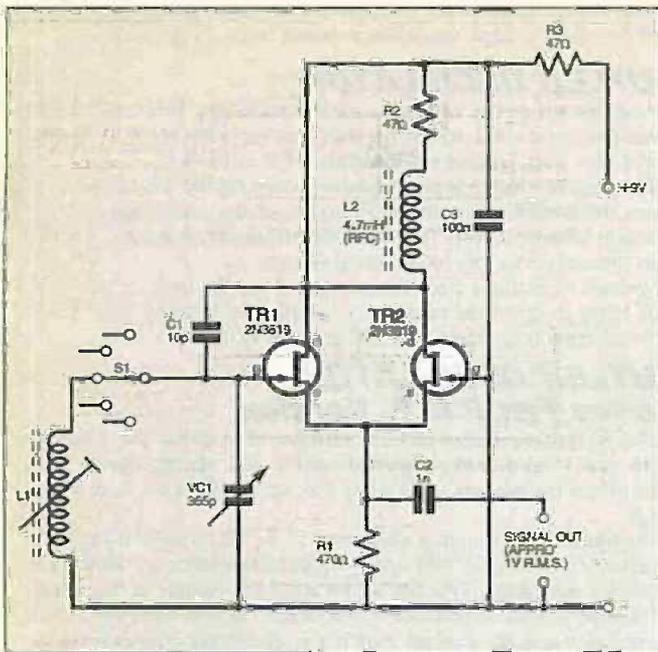


Fig.6. Circuit for a parallel (shunt) fed f.e.t. version of the Butler oscillator.

TR1 and feedback is developed across an r.f. choke, L2, which acts as the drain load for TR2.

Resistor R2 is a "Q" spoiler to prevent the internal resonances of the choke triggering erratic operation. Even when this precaution is taken, there is a tendency for the oscillator to malfunction below 500kHz or so, and the circuit will not oscillate over the full swing of a 365pF capacitor on the 10MHz to 30MHz shortwave range.

Unless there is a compelling need to connect the tuning inductor to ground, the series fed circuit given in Fig.5 is much to be preferred. However, between 500kHz and 15MHz, the shunt fed circuit works well, providing a reasonably constant output with a tolerable waveform.

Series Fed - NPN Transistor Version

Butler's ingenious combination of a grounded grid (grounded gate or base with transistors) and a cathode follower stage (source or emitter follower) makes it possible for bipolar transistors to function well in this circuit. Configuring bipolar transistors in this way increases their normally low base and modest collector impedances, thereby limiting damping on the tuned circuit to the point where oscillation can be maintained, over a wide frequency range, and with reasonably large ratios of capacitance to inductance in the tuned circuit.

A design based on npn transistors is given in Fig.7. It is very similar to the series fed f.e.t. version given in Fig.5, but the biasing arrangements for the bipolar transistors are more complicated.

The base (b) bias voltage for both transistors is set by the potential divider chain formed by resistors R1, R2 and preset VR1, the d.c. bias being applied to TR2 via signal isolating resistor R4. Emitter (e) bias is developed across resistor R3 and preset VR2. The inclusion of the preset potentiometers enables the biasing to be adjusted to accommodate a wide range of transistor types, and the compromise between output voltage and waveform purity can be optimised for a particular application. The base of TR1 is grounded at radio frequencies by capacitor C1.

Tuning inductor L1 is connected in the collector (c) circuit of TR1, the grounded base configuration of this stage making the output impedance high enough to avoid excessive damping. Again, tuning capacitor VC1 is connected across the coil via decoupling capacitor C3. Capacitor C2 completes the feedback loop by linking the collector of TR1 to the base of TR2.

Arranging TR2 as an emitter follower increases the base impedance of the stage. This enables the value of feedback capacitor C2 to be kept low, thereby minimising the damping on the tuned circuit. Resistor R5 acts with C3 to decouple the circuit from its power supply.

Signal output is taken from the "hot" end of the tuning coil via capacitor C4. Output can, alternatively, be taken from the coupled emitters via a low value blocking capacitor. Signal voltage at the emitters remains fairly constant between 500kHz and 15MHz, but there is a reduction in output on the highest shortwave range (10MHz to 30MHz) and below about 500kHz.

Moreover, the quality of the waveform at the emitters is poor: a chain of rounded pulses which cannot be improved by adjusting the bias potentiometers.

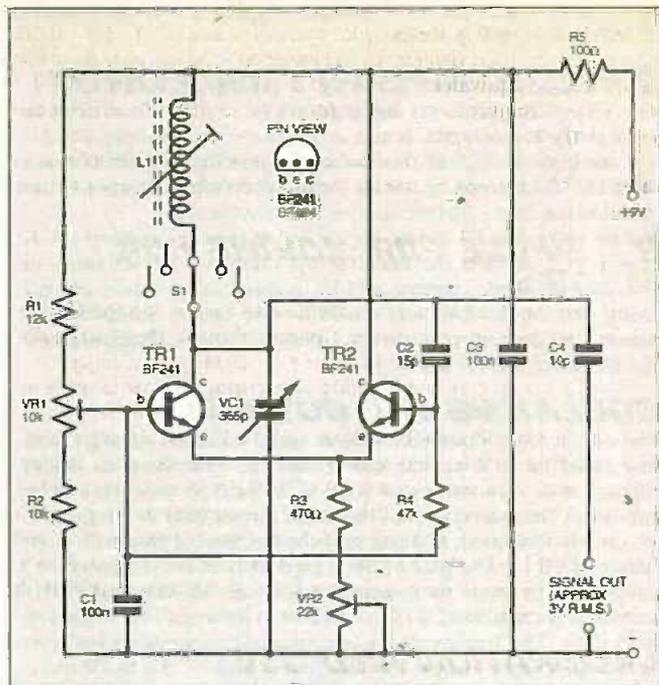


Fig.7. Bipolar npn transistor version of the series fed Butler oscillator.

Series Fed - PNP Transistor Version

By substituting pnp transistors, it is possible to invert the circuit and connect the tuning inductor to a negative ground. Most small signal pnp transistors with a high enough f_T will work in this circuit, but some, particularly medium power types, have high internal capacitances, and this limits the high frequency coverage for a given output voltage. (Coverage can be maintained by adjusting VR2, but signal output falls.) BC557s work well, and pnp transistors designed for r.f. working should be particularly suitable.

Biasing, feedback and decoupling arrangements are identical to those adopted in the circuit using npn transistors.

With appropriate tuned circuits, the bipolar transistor versions of Butler's oscillator will function from 20kHz to above 60MHz. Purity of waveform is excellent if the bias potentiometers are adjusted to hold the output below 1V r.m.s. (approximately 3V peak-to-peak).

MEASURING R.F. VOLTAGES

Some means of detecting the presence, and assessing the magnitude, of r.f. voltages, is essential when conducting experiments with oscillators.

Conventional digital or analogue test meters will not measure voltages alternating at much above a few hundred Hertz. The addition of a simple and inexpensive diode probe will, however, enable basic test meters to be used for the detection and measurement of r.f. voltages into the u.h.f. region.

SEMICONDUCTOR DIODES

Semiconductor signal diodes, which rectify the r.f. and produce a d.c. voltage which can be measured by conventional meters, are used in probes of this kind. Germanium diodes begin to conduct heavily at a lower voltage than their silicon counterparts (0.2V as opposed to 0.6V), and they are to be preferred for this purpose.

If a probe is to be used with a moving coil meter, OA47 diodes will be found to produce a marginally greater output at very low voltages, but any germanium or Schottky diode should prove suitable. Silicon signal diodes, e.g., the 1N4142, can be used successfully if their reduced small-signal sensitivity is taken into account.

R.F. PROBE FOR DIGITAL TEST METERS

The circuit given in Fig.8a shows how the diode is connected in probes to be used with high input resistance digital or electronic test meters. The input resistance of instruments of this kind is usually 10 megohms, and the diode must be shunt connected in order to maintain sufficient current flow for the rectifying action to take place.

The d.c. voltage developed at the diode's cathode (k) is approximately equal to the peak value of the applied a.c. voltage (i.e., 1.414



We can supply back issues of *EPE* and *ETI* (see panel) by post, most *EPE* issues from the past five years are available. An *EPE* index for the last five years is also available - see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one* article (or *one* part of a series) can be purchased for the same price.

DID YOU MISS THESE?

APRIL '98 Photostats Only

PROJECTS • Simple Metal Detector • Single or Dual Tracking Power Supply • Experimental Piezo-Cable Projects - Distributed Microphone - Vibration Alarm • RC-Meter.
FEATURES • Ingenuity Unlimited • Patent Your Invention • TEACH-IN '98 - 6 • Circuit Surgery • Net Work • Techniques - Actually Doing It • *EPE* PIC Tutorial Supplement 2

MAY '98 Photostats Only

PROJECTS • Dice Lott • Security Auto-Light • Stereo Tone Control plus 20W Stereo Amplifier • Improved Infra-Red Remote Repeater.
FEATURES • TEACH-IN '98 - 7 • Net Work • *EPE* PIC Tutorial Supplement 3

JUNE '98

PROJECTS • *EPE* Mood Changer • Simple SW Receiver • Atrnel AT89C2051/1051 Programmer • Reaction Timer.
FEATURES • 8051-based EEPROM Microcontrollers • TEACH-IN '98 - An Introduction to Digital Electronics - 8 • Circuit Surgery • Techniques - Actually Doing It • Ingenuity Unlimited



JULY '98

PROJECTS • PIC16x84 Toolkit • Noise Cancelling Unit • Low Battery Indicator • Greenhouse Computer - 1.
FEATURES • Using the L200CV Voltage Regulator • TEACH-IN '98 - 9 • Ingenuity Unlimited • Circuit Surgery • Net Work.

AUG '98

PROJECTS • Lightbulb Saver • Float Charger • PC Transistor Tester • Greenhouse Computer - 2 • Time Machine Update.
FEATURES • TEACH-IN '98 - 10 • Circuit Surgery • Techniques - Actually Doing It • Ingenuity Unlimited.

SEPT '98

PROJECTS • Mains Socket Tester • Personal Stereo Amplifier • Greenhouse Radio Link • PIC Altimeter.
FEATURES • TEACH-IN '98 - 11 • Ingenuity Unlimited • Circuit Surgery • Interface • Net Work • Crocodile Clips Review.

OCT '98

PROJECTS • Voice Processor • Digiserv R/C Channel Expander • Reliable Infra-Red Remote Control • PC Capacitance Meter.
FEATURES • Easy PCB Making • Using LM335 and LM35 Temperature Sensors • Circuit Surgery • Ingenuity Unlimited • Net Work.

NOV '98

PROJECTS • PIC Tape Measure • T-Stat Electronic Thermostat - 1 • PhizzyB Computers - 1 • 15-way Infra-Red Remote Control.
FEATURES • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work - The Internet • Easy PC for Windows 95 Review • *FREE* *EPE* CD-ROM No.1.

DEC '98 Photostats Only

PROJECTS • *EPE* Mind PICKler-1 • Fading Christmas Lights • Handheld Function Generator • Damp Stat Electronic Thermostat • PhizzyB Computers-2.
FEATURES • PhizzyB Computers-2 Understanding Computers • Circuit Surgery • Ingenuity Unlimited • Index • *FREE* 48-page Understanding Passive Components booklet.

JAN '99

PROJECTS • Alternative Courtesy Light Controller • Twinkle Twinkle Reaction Game • Volume Compressor • PhizzyB Computers-3 • *EPE* Mind PICKler-2.
FEATURES • New Technology Update • From Russia With Love • Circuit Surgery • PhizzyB Computers-3 • Net Work.



FEB '99

PROJECTS • PIC MIDI Sustain Pedal • Light Alarm • Wireless Monitoring System-1 • PhizzyB Computers-4.
FEATURES • Ingenuity Unlimited • Scholar Project • PhizzyB Computers-4.

MAR '99

PROJECTS • Smoke Absorber • Auto Cupboard Light • PhizzyB Computers-5 • Time and Date Generator • Wireless Monitoring System-2.
FEATURES • Ingenuity Unlimited • MTSEC Show Report • PhizzyB Computers-5 • Practically Speaking • Circuit Surgery • Net Work.

APRIL '99

PROJECTS • Mechanical Radio • Voice Record/Playback Module • Versatile Event Counter • PhizzyB Computers-6 • Ironing Board Saver.
FEATURES • Ingenuity Unlimited • PIC16F87x Microcontrollers • PhizzyB Computers-6 • MAX761 D.C. to D.C. Converter • Interface • Circuit Surgery • Net Work • *FREE* 48-page Basic Soldering Guide booklet.



MAY '99

PROJECTS • MIDI Handbells • A.M./F.M. Radio Remote Control • PhizzyB Computers-7 • PIC Toolkit Mk2-1.
FEATURES • PC Engines - From 4004 to Pentium III • Ingenuity Unlimited • Practically Speaking • PhizzyB Computers-7 • Circuit Surgery • New Technology Update • Net Work • *FREE* pull-out 7400 series Pinout Data Chart.

JUNE '99

PROJECTS • Clipping Video Fader (Starter Project) • PC Audio Frequency Meter • Musical Sundial • PIC Toolkit Mk2-2.
FEATURES • Alan Dower Blumlein • Circuit Surgery • Interface • PhizzyB Computers-8 • Ingenuity Unlimited • Edison 3 Review • Net Work - The Internet.

JULY '99

PROJECTS • 12V Lead-acid Battery Tester • L.E.D. Stroboscope • *EPE* Mood Picker • Intruder Deterrent.
FEATURES • Practical Oscillator Designs-1 • Practically Speaking • Circuit Surgery • Ingenuity Unlimited • New Technology Update • Net Work - The Internet.

AUG '99

PROJECTS • Ultrasonic Puncture Finder • Magnetic Field Detective • Freezer Alarm • 8-Channel Analogue Data Logger-1 • Sound Activated Switch.
FEATURES • Practical Oscillator Designs-2 • Power Generation from Pipelines to Pylons-1 • Ingenuity Unlimited • Circuit Surgery • New Technology Update • Interface • Net Work - The Internet.

BACK ISSUES ONLY £2.75 each inc. UK p&p.

Overseas prices £3.35 each surface mail, £4.35 each airmail.

We can also supply issues from earlier years: 1992 (except March, April, June to Sept. and Dec.), 1993 (except Jan. to March, May, Aug., Dec.), 1994 (except April, May, June, Nov.), 1995 (except Jan., May to Sept., Nov., Dec.), 1996 (except Jan., Feb., April, May, July, Aug., Nov.), 1997, 1998 (except Jan., March to May, Dec.).

We can also supply back issues of *ETI* (prior to the merger of the two magazines) for 1998/9 - Vol. 27 Nos 1 to 13 and Vol. 28 No. 1. We are not able to supply any material from *ETI* prior to 1998. Please put *ETI* clearly on your order form if you require *ETI* issues.

Where we do not have an issue a photostat of any *one* article or *one* part of a series can be provided at the same price.

ORDER FORM - BACK ISSUES - PHOTOSTATS - INDEXES

- Send back issues dated
- Send photostats of (article title and issue date)
- Send copies of last five years Indexes (£2.75 for five inc. p&p - Overseas £3.35 surface, £4.35 airmail)

Name

Address

I enclose cheque/PO/bank draft to the value of £.....

Please charge my Visa/Mastercard £.....

Card No. Card Expiry Date

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.

SEND TO: Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.

Tel: 01202 881749. Fax: 01202 841692. (Due to the cost we cannot reply to overseas queries or orders by Fax.)

E-mail: orders@epemag.wimborne.co.uk

Payments must be in £ sterling - cheque or bank draft drawn on a UK bank. Normally supplied within seven days of receipt of order.

Send a copy of this form, or order by letter if you do not wish to cut your issue.

M9/99



**Ravensbourne College
of Design and Communication**

Courses in Broadcast Technology

The television industry needs qualified broadcast engineers to fill the large number of jobs available in the industry. The practical courses offered at Ravensbourne can give your career in television a kick-start.

Edexcel NC Broadcast Engineering

If you are 16 or over, this 1 year NC course provides a unique route into HE courses in broadcast technology.

Edexcel HND Digital Technology

A 2 year HND for students over 18, which prepares you for a career in broadcast engineering with a TV company or facilities house.

Places still available for September 1999

**Call now for an information pack
and application form
0181 289 4970**



**NATIONAL
COLLEGE OF
TECHNOLOGY**


DISTANCE LEARNING COURSES in:

Analogue and Digital Electronics
Circuits, Fibres & Opto-Electronics
Electronic Testing & Fault Diagnosis
Programmable Logic Controllers
Mechanics and Mechanisms
GCSE and BTEC Mathematics

- Courses to suit *beginners* and those wishing to *update* their knowledge and practical skills
- Courses are delivered as self-contained kits
- No travelling or college attendance
- Learning is at your own pace
- Courses may have BTEC Certification and Tutoring

For information contact:
NCT Ltd., P.O. Box 11
Wendover, Bucks HP22 6XA
Telephone 01296 624270; Fax 01296 625299
Web: <http://www.nct.ltd.uk>

C.C.T.V. BOARD CAMERAS FROM £19.95

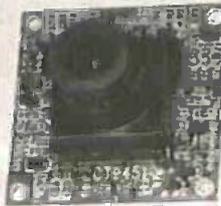

ONLY 29mm x 29mm

MINIATURE C.C.T.V. CAMERAS FROM TOP USA MAKER IDEAL FOR COVERT SURVEILLANCE OR SECURITY USE IN SHOPS, OFFICES AND PRIVATE HOMES. CONNECTS TO ANY TV OR VIDEO IN SECONDS - OPTIONAL CABLE ETC. AVAILABLE OUR 1993 PRICE FOR THIS CAMERA WAS £385!! HUGE RECESSION IN ELECTRONICS INDUSTRY HAS SLASHED THESE PRICES TO RIDICULOUS LEVELS! THESE ARE USA MADE - NOT CHEAP CHINESE MODELS. READY BUILT WITH LENS ETC. BRAND NEW 1999 STOCK - FULL 12 MONTH GUARANTEE. WORKS FROM 9V-PP3 BATTERY OR OUR CAMERA PSU AND CABLE KIT SHOWN BELOW.

LOTS OF 10 (Each) **£19.95**
LOTS OF 5 **£21.50**
LOTS OF 2 **£23.95**
SAMPLE **£25.95**
Add P&P £3 ANY ORDER
VAT INCLUDED

Audio Model add £5.00
1/3in. image sensor with 288 x 352 pixels. Auto iris. 270 lines. 6V to 12V D.C. 30mA. Includes 3-6mm wide angle lens. Pinhole Lens add £2.

APPLICATIONS:
SECURITY
SURVEILLANCE,
MACHINE MONITORING,
NANNY WATCHING,
STAFF THEFT,
BIRD OBSERVATION,
ETC.
BRITISH PAL SYSTEM.



SECRET SPY CAMERAS MICRO SIZE 16mm x 16mm

JAPANESE CCTV TECHNOLOGY REDUCES THE SIZE FOR EASY CONCEALMENT.
PLEASE ADD £2 TO ABOVE 29X29MM PRICES




HIGH QUALITY EXTRA SMALL B&W CAMERA

1/3in. CCD BOARD CAMERA WITH AUTO BACKLIGHT COMPENSATION
128 STEP ELECTRONIC IRIS AND 380 TV LINES RESOLUTION.
320,000 PIXELS AND 0-2 LUX LEVEL GIVES REMARKABLE CRYSTAL CLEAR PICTURES
32mm (h) x 32mm (l) x 23mm (t)
MAPLINS PRICE £79.99
OUR PRICE **£35.95**
3-6mm WIDE ANGLE LENS
ADD £5 AUDIO

Camera PSU and Cable Kit

A total solution for powering and connecting to our range of board camera modules and covert cameras. The kit contains a quality plug-in mains adaptor and a 20m pre-wired cable. One end of the cable has a SCART plug, an audio phono plug, a video phono plug and a DC power socket. The lead from the mains adaptor is plugged into the DC socket and either the SCART plug or audio and video phono plugs are plugged into your TV, monitor or VCR.
MAPLINS PRICE £24.99. OUR PRICE **£12.50**

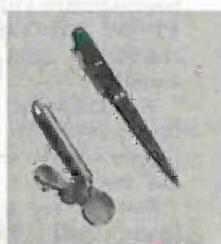CAMERA CASING WITH SWIVEL WALL BRACKET TO TAKE ANY OF OUR BOARD CAMERAS **£3.50**



LASER POINTERS

Professional model fires a small red laser dot over 250 metres. Built into executive ballpoint pen with case and batts.


LIST £39.95 NOW **£10.00**

Gold-plated Keyfob model
LIST £29.95 NOW **£9.00**

Multi Keyfob with 5 tips fires a dot, horizontal line, star, arrows and circle

LIST £41.25 NOW **£12.00**
Add £3 p&p any quantity.

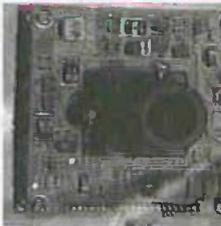(Only sold to schools or tradesmen - no minors under 21)



1/4in. COLOUR CCD CAMERAS

Japanese Twinboard 1/4in. CCD and DSP (digital signal processor) colour CCTV boards with popular 3-6mm wide angle lens. High specification 290,000 pixels, electronic iris, 330 TV lines and LUX levels 2, 12V DC. Use with our camera PSU and cable kit (see above). Size 32mm x 32mm.

LOWEST PRICE
IN EEC

£59.00

Audio model
add £5.00

VISONIC RADIO TRANSMITTER/RECEIVER SETS

Comprises smart remote control normally used as a panic button or medical alert for the elderly. Causes receiver to open or close a circuit thereby triggering a siren, automatic garage door or other device until button is released. Range 35m indoors, 100m outdoors. 9V PP3 batt. Included. DTI approved 1340 licence exempt. MRP £47.85 set. Boxed with full instructions.

SAMPLE SET **£15.90**, 2 SETS **£29**, 5 SETS **£62**

ULTRAGUARD POLYCARBONATE BELLBOXES.

White. 15in. x 10in. lassoo-proof shape with crime prevention label. 118 decibel horn siren, flashing Xenon strobe. Nicad back-up batteries and full anti-tamper system all factory fitted and sealed. 12V PSU supplied. Can be triggered by simple bell-push, any alarm panel or the Visonic set shown above.

MRP £41.87. NOW **£16** + £3 P.P.


ALL GOODS ARE BRAND NEW AND PERFECT. BULK BUYERS PLEASE ASK FOR JOHN. PRICES INCLUDE VAT. £3 P.P. ANY SIZE ORDER



A.S.A. (Est. 1979)
51 Cambridge Road
Middlesbrough
TS5 5NL

Order Hotline
01642 851256
Fax:
01642 823173

8-CHANNEL ANALOGUE DATA LOGGER

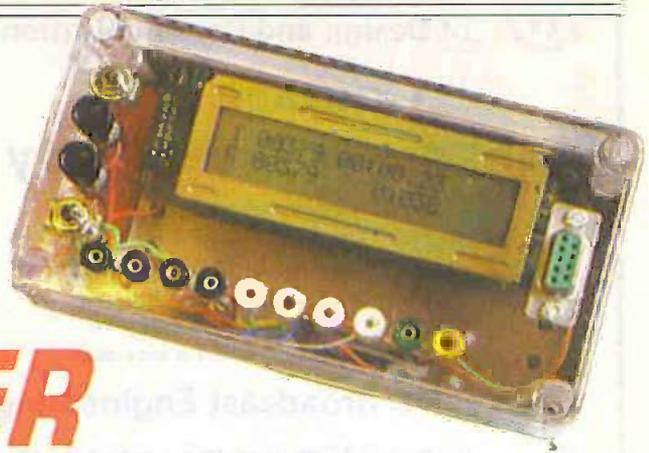

JOHN BECKER

Part 2

The new PIC16F877 microcontroller offers versatile analogue data logging opportunities.

HAVING discussed the circuit and constructional details last month, we now describe how to use the Data Logger and view its recordings.

PROGRAMMING THE PIC

To program IC1 using *PIC Toolkit Mk2* (May and June '99 issues), connect the CLK, DATA, MCLR and 0V pins on the Data Logger board (near top centre as shown in Fig.2 – last month) back to the RB6, RB7, MCLR and 0V pins (in that order) on the *Toolkit Mk2* board.

Switch on power to both units. From the *Toolkit Mk2* software, select main menu Option 1 – Configure PIC Factors.

Accept the first three default options (XT, WDT no, POR yes), select the 'F87x option instead of the '84 option, then accept the remaining defaults, through to and including sending the configuration data to the PIC.

The PIC's configuration register bits affected are shown in Table 2. The data is read from left to right, bit 13 to bit 0. A full explanation of the bit functions is given in the PIC16F877 data sheet.

Now call up *Toolkit Mk2* main menu Option 2 (Program PIC with TASM Binary code), key in DATLOG01 and send the data to the PIC as instructed on screen.

Note that *PIC Toolkit Mk1*, *PIC Tutorial* and *PICtutor* cannot supply the full configuration data required by the PIC16F87x devices and that their program handling capacity is 1023 bytes (the Data Logger program is in excess of that length).

SECOND CHECKS

With the programmed PIC in-situ, and with the power off, insert all the remaining i.c.s. As said last month, not all the memory chips IC5 to IC11 need to be used, just insert those you want in ascending numerical order position. Connect the l.c.d. and set the wiper of preset VR1 fully anti-clockwise. Switch off S1 (Run/Stop).

If you have a signal generator (one that can output a waveform whose min-max peaks lie between 0V and +5V – even a square wave will do), couple it into channel 1 (SK1). Set the generator for its lowest possible rate, ideally of much less than the 1Hz sampling rate about to be selected.

Alternatively, you could connect a potentiometer (10kΩ lin, say) across the +5V/0V rails and connect its wiper to channel 1, adjusting the rotation while sampling.

As a last resort, just connect a temporary link between the Data Logger's +5V supply and channel 1.

Switch on power again, and double check that +5V still exists on the output of regulator IC2. Look at the l.c.d. and check that seemingly meaningful data is shown on its screen – never mind the actual content at the moment just check that something is there on both lines. Adjust VR1 to change the contrast if preferred.

Switch off the power again, and wait a few seconds before following the actions for the next stage – Reset.

RESET

Sample Counter Reset

With switch S3 (Reset) pressed, switch on the power and look at the l.c.d. Now release S3 (but don't touch any of the switches again until we've explained matters a bit further).

Note that the Data Logger's Reset mode can only be entered in this fashion, i.e. at switch on.

(Actually, if the Data Logger is connected to the *PIC Toolkit Mk2* board at this time, Reset mode can be entered by just pressing and releasing *Toolkit's* Reset switch (S1) while Data Logger S3 is pressed, which avoids having to power down and then up again. The action resets the PIC's internal program counter, as also occurs when power is switched on.)

Immediately power is switched on, the software should recognise that S3 is pressed and the l.c.d. should display the information shown in Photo 1.



Photo 1. Reset mode screen, phase 1.

The l.c.d. screen should show RATE=.5 on the top line. This is the default rate at which samples will be taken unless you set it otherwise (as in a moment). It means that all eight data channels will be sampled as a group once every half-second.

In the lower l.c.d. line, the words COUNTER RESET will be seen. It means exactly what it says, the sample counter has been reset, to zero.

Sample Rate Changing

At this point in the Reset procedure, you can change the sampling rate. Press switch S2 (Up) once; the rate will be seen to change to 1 – one sample group (all eight channels) per second. Press again to show a Rate of 2 – one sample group every two

Table 2. Configuration setting for the PIC16F877.

CP1	CP0	DBG	NIL	WRT	CPD	LVP	BOR	CP1	CP0	POR	WDT	OS1	OS0
1	1	1	1	1	1	0	0	1	1	0	0	0	1

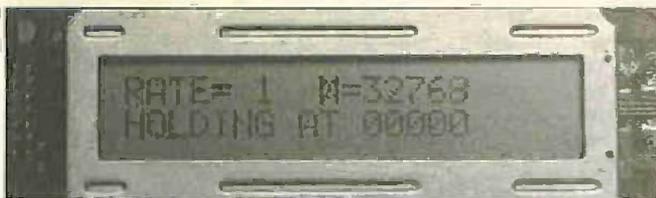


Photo 2. Typical I.C.D. display following Reset.



Photo 3. Typical I.C.D. display during sampling.

seconds. Keep pressing a few times more and note that each press increases the period between each batch of eight samples by one second. The maximum period between samples is 62 seconds, about 10 days-worth of continuous data sampling, if you wish it and have the 24LC256 chips installed!

The Rate counter setting is bi-directional — up or down. Down-counting is controlled by switch S3 (Down). Press it and observe the sampling rate descending. Once you reach RATE=.5 again, the next press of S3 will roll the internal counter over to 63, but instead of seeing RATE=63, you will see the statement RATE=EXT. In this mode the sampling rate is determined not by the software's controlling clock routines, but by any digital signal (+5V/0V) fed into the Data Logger at socket SK10.

For the moment, return the sample rate to show RATE= 1.

Maximum Sample Quantity Setting

Even though you may have installed memories of considerable data storage capacity, there are times when you might wish to leave the Data Logger running unattended but want to restrict the number of samples that it can take before you return.

This is where the next phase of the setting up will be useful, setting the maximum count limit. Switch S1 (Run/Stop) on to enter this phase.

To the right of I.C.D. line 1, the message M= followed by a value will be seen. Letter M stands for Memory and the value is likely to be 16384 (although this may differ the first time the program is run). The value is the maximum count that can occur on this setting before the sampling is automatically ceased.

To reduce the count limit, press S3 (Down). At each press, the count limit will be lowered by a factor of two. The order is 16384, 8192, 4096, 2048, 1024, 512, 256, FREE RUN, and then rolls over back to 16384 etc. In reality, the actual limit for the first seven values is always one byte less than that shown — the software is written to detect when the counter, which is incremented after each sample, reaches the limit set, and then refuses to take any more.

Pressing switch S2 increases the count limit selected.

Be especially aware that if you set a count limit which is greater than the capacity of the memory chips you have used, once the sample count has reached the chip's capacity, the chip's own counter will roll over to zero and start over-writing the previously recorded data. This, though, could be beneficial in some sampling situations where the signal data you want to record could occur at any unexpected time.

This is the purpose of the FREE RUN setting, which does not impose a maximum limit and sampling goes on and on indefinitely until you stop it.

Leave the count limit set on 16384. Now switch off S1.

When in Reset mode, if you do not want to change any of the parameters but just reset the sample counter, simply switch S1 through its two-phase sequence, returning to the Run/Hold mode.

Note that the Reset function does not actually reset the serial memory chips to hold zero values. This action would seriously shorten the lifetime of the devices, which is about 100,000 write cycles (there is no limit to the number of read cycles).

RUN/HOLD MODE

The act of switching off S1 when in Reset mode phase 2 terminates the Reset mode and puts the Data Logger into its Run/Hold mode. Had you not entered the Reset mode by pressing S3 while switching on power, Run/Hold is the mode that would have been entered instead.

The I.C.D. screen now shows the Rate and count limit on the top line, and line 2 shows the message HOLDING AT 00000, the zeros confirming that the sample counter has been reset. Photo 2 shows the I.C.D. in this condition.

Simultaneously with S1 being switched off, the new rate, sample limit and count values are stored in the PIC's internal EEPROM memory. The first two are retained there until you initiate the Reset sequence at some future date. (The count value will be updated from time to time as described shortly.)

To start sampling, just switch on S1 (Run/Hold).

After a very brief pause, sampling starts and its progress is displayed on the I.C.D. On the far left of the top line is shown the channel number whose sampled data is displayed immediately to the right of it. On the right of the top line the elapsed time is shown in HH:MM.SS format, on a 24-hour basis. It increments at one second intervals, irrespective of the sample rate selected (except in EXT CLK mode, see later).

The elapsed time counter is always reset when power is first switched on.

The sample data value shown on the top line is that immediately received from the analogue-to-digital converter, prior to it being stored in the serial memory. If a signal generator is being used the value could be any between 0 and 1023. If a +5V link provides the data voltage, the value will be about 1023.

The value of 1023 is the maximum value that the 10-bit ADC sampling will produce when the channel is at the same voltage as the ADC's internal upper reference voltage. The minimum possible value is zero, for a 0V input.

READ BACK

Following storage of the data, it is read back and displayed on line 2, prefixed by the letter R (for Read). Provided that a memory chip has been installed for the channel on display, this number should be the same as the one on the top line.

However, if the channel does not have a memory chip installed, the value displayed on line 2 will be 65535. This is because the memory routine has found nothing but logic 1 on the data line when each bit for that memory location is read. It is the presence of resistor R22 that causes this result, pulling the data line high.

At the moment, with channel 1, you should see identical sample and replay values on the top and bottom lines.

You will also observe that the clock counter is busy incrementing, as is the sample counter at the right of line 2. A typical screen display is shown in Photo 3.

To stop the sampling, switch off S1. If you watch carefully, when you switch off S1, the sample counter fairly rapidly increments by five counts. This action places zeroes in the next five memory locations, an aid to later determination (when the data has been transferred to the computer) of where sample batches start and end.

When the five zeroes have been written, the sampling process for this batch has ended and I.C.D. line 2 shows the message HOLDING AT, followed by the current count number.

Additionally at this point, the software stores the current count value in the PIC's own internal EEPROM memory, and this value is retained even after the Data Logger has been switched off. It is recalled when the Logger is switched on again, although the value shown then will be one higher than that on display at the moment of power switch off.

Switch off the power, wait a few seconds and switch on again. The software now retrieves the last-used Rate, count limit and sample count values from its EEPROM memory, and displays them on the I.C.D. The message that should greet you on this occasion is RATE= 1 M=16384 on the top line, with line 2 showing HOLDING AT followed by the count value retrieved. Photo 4 shows a typical screen.

To start sampling once more, switch on S1, switching it off again when you want to



Photo 4. Typical I.C.D. display when first switching power on after a previous batch of data has been sampled.



Photo 5. Typical l.c.d. screen during data transfer to PC, the baud rate is confirmed as 9600.

stop sampling. Try it. Then we'll tell you about viewing the other channels.

CHANNEL VIEWING

With the Logger running, briefly press switch S2. Within one second (the rate of sampling) the switch status will be read and the channel number on display will be incremented. Release S2 when the number changes to indicate channel 2.

On the top line, the sample value should show zero since this channel does not have a signal source connected, only the 0V connection via its pull-down resistor.

If you have a memory in location IC5, the bottom line should show a value of zero. If the location is empty, though, a value of 65535 will be seen (as explained earlier).

Press S2 again, but this time keep it pressed. Each time a sample occurs, the channel displayed will increment, up to 8 and roll over to 1. Pressing S3 instead will decrement the channel number.

It is important to note that all eight channels are always sampled as a batch, irrespective of which channel is on display.

Note also that the current channel number on display is not stored in EEPROM memory and will always default to channel 1 when power is first applied.

When you have finished sampling, switch off S1.

MEMORY FULL

When a limit has been imposed on the sampling count and that limit has been reached, sampling ceases and the l.c.d. advises on line 2 that a MEM FULL condition exists.

The only action that can be performed when the memory is full is to transfer the data to the PC. When you see the message, switch off S1. You may also switch off the power, since even on power-up the full memory condition is recognised.

To clear the full memory condition, the Reset sequence has to be performed during power up.

TRANSFER TO PC

Data can be transferred to the PC computer at any time that S1 is switched off (except in Reset mode).

The Data Logger's serial data acquisition program that is run on the computer is centred around a machine code routine the author has written specifically for the Logger. It is accessed from Basic (QBasic or QuickBASIC), which also does all the formatting and sending of the processed data to the hard disk.

The machine code configures and reads the computer's internal serial registers via interrupt calls. Its source code can be read as a text file, DATLOG01.J. It was written for the shareware A86/D86 (8086 et al) assembler, which generated the loadable

DATLOG01.COM binary file.

(There are additional notes as a text file with the software - these should be read through your text editor.)

The 10-bit data samples are transmitted by the Data Logger as two 8-bit bytes each limited

to a maximum value of 127, plus Stop bit. The computer's internal interrupt routine receives the data as an inverted byte of twice the value transmitted. The software inverts and reformats the data to its original value as stored in the serial memory chips.

From the MS-DOS screen, enter the directory in which your QBasic or QuickBASIC software is held.

If you are using QuickBASIC, type QB/L to load QuickBASIC complete with its library routine that allows Basic programs to be run with the associated machine code program.

With QBasic (which has its own machine code access facility built in), just type QB.

From within the loaded Basic, load the Data Logger program DATLOG01.BAS.

COM PORT SETTING

Near the head of the program you have the option to set which PC COM port is to be used. Find the statement in which the variable COMPORT% is given a value (COMPORT% =). To use COM port 1 set COMPORT% = 0. To use COM port 2 set COMPORT% = 1. If you now resave the program, that same COM port value will be the one selected each time you run the program.

Immediately the program is run (starting it in the usual way for Basic), the author's serial-reading machine code routine is automatically loaded. The Basic program then enters that routine and waits for the serial data from the PIC to start being sent.

To start sending data to the PC, press switch S2 (Up/Send) - S1 must be switched off for the software to recognise that S2 is pressed.

Once S2 has been pressed, the PIC's software first sends six zero value bytes and then proceeds to read and transmit all the stored data from each memory in turn, starting at channel 1 (see Photo 5). The double-byte (word)

data for each sample is sent as LSB (least significant byte) first, with each bit being sent in ascending order from bit 0 to 7.

ALL EIGHT CHANNELS

All eight channels will be read even though some may not have memories installed. However, when the software detects the value of 65535 (as produced from an empty memory location, the routine for reading that channel is terminated).

Normally, for installed memories, the same quantity of samples will be sent as the number of samples taken since the Data Logger was last reset (i.e. from sample 0 upwards). When FREE RUN is selected, the software attempts to read back from 16383 memory locations, but terminates that channel if a memory is uninstalled. If memories having a lesser capacity than 16384 samples (less than 256 kilobits) are installed, their contents will be read more than once - intelligent inspection of their PC files must be applied to find the start of duplication.

TERMINATION CODE

When the last sample from each channel has been sent, a termination code is sent, consisting of two bytes each having a value of 127. The next channel is then transmitted, until all eight have been dealt with.

Each time the machine code recognises the termination code of a channel, the routine returns to Basic and the block of sampled data is output to the hard disk as a binary data file named CAPICLOG\DATLOGx.DAT, where x is the channel number. (Directory CAPICLOG is created during program installation.)

When each channel has been read, the computer screen shows the values of the first nine samples received for that channel. When all eight channel blocks have been saved to disk, they are each recalled and their first and last ten samples are displayed. Photo 6 shows a typical display.

TEXT FILES

Next, the same .DAT binary files are again recalled in turn and eight new files are created, each holding the sample values as individual numbers expressed in text format. The files are named CAPICLOG\DATLOGx.TXT, where again x is the channel number.

A third stage follows in which all eight .TXT files are opened simultaneously and a composite single file, CAPICLOG\DATLOG10.TXT, is created in which the values of each channel are combined into lines of eight columns separated by a TAB character (ASCII 9). This suits the file for input to Microsoft Excel for subsequent graphing and analysis (more on this later).

The .TXT files can (probably) also be read by any word-processing program. MS-DOS EDIT is well suited to this.

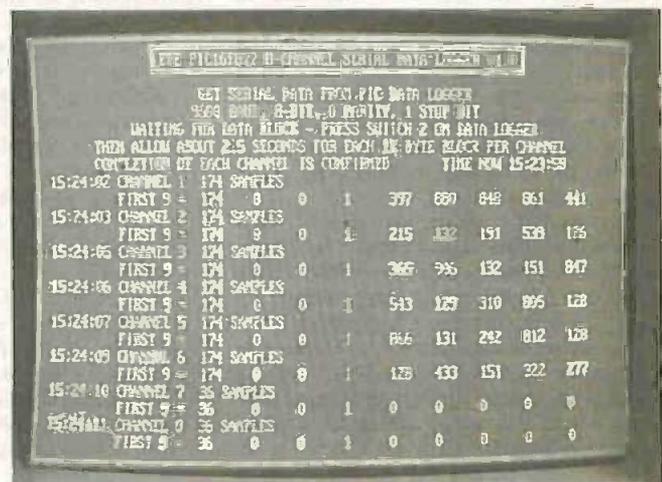


Photo 6. Typical PC screen display during serial data input from the Data Logger.

V-SCOPE FORMAT

That's not all – four more files are now created, suited for display using the *Virtual Scope* (Jan. and Feb. '98) software (you only need the software, the hardware is not required).

Each file holds the data for two channels, the pairs are 1/2, 3/4, 5/6, 7/8 and the files are named 0110000x.Y00 where x is a value of 0 to 3 in order of each pair of channels. These files are stored in the same directory in which your Basic program resides.

The apparently unusual file names (originally intended to be date and time related) allow the files to be accessed and viewed as oscilloscope-type traces through the V-Scope's Directory facility. They may be manipulated in the same way as any other V-Scope files.

Once the V-Scope files have been created, the transfer process is complete and you can come out of Basic in your usual way.

So, then, if that selection of data file options doesn't suit you, nothing will! (But do tell the author via *EPE* if he's wrong on this point, and make practical suggestions.)

A final point on the files, however: the file names used are fixed in the software. It is suggested, though, that in normal use of the Data Logger, you rename the recorded files to those of your choice, allowing fresh batches of sampled data to be imported without overwriting the previous batch. It is preferable that the same extension names should be retained (especially with the V-Scope files).

VIEWING VIA EXCEL

Microsoft's Excel software offers an excellent way in which the Data Logger data can be examined and graphically displayed. The following is one way in which it can be used (determined from the author's Excel 7).

From the Windows desk-top display ("main menu") perform the following steps (all "clicks" are left-hand mouse button clicks unless stated):

- Open My Computer (double-click)
 - Open [C:] drive (double-click)
 - Open MS Office (double-click)
 - Open Microsoft Excel (double-click)
 - In Excel, open File menu (top left)
 - Click Open
 - Click arrow to right of My Documents panel
 - Click on [C:]
 - Open PICLOG directory (double-click)
 - Click arrow to right of Files of Type panel
 - Click Text Files
 - Select DATLOG10 (double-click)
- The file is now loaded and Text Import Wizard screen displayed
- Click Finish (bottom right)

This last action formats and displays the DATLOG10.TXT file as eight columns of numerical data with a row count corresponding to the sample count. At the head of each column is also displayed some textual information. Box 1 states the number of samples ($N =$) for that column. Boxes 2 and 3 just show zeros. Box 4 states the Logger channel number. Box 5 shows the sample rate that applied when the recording was made. The final box in the column simply states END. Now do the following:

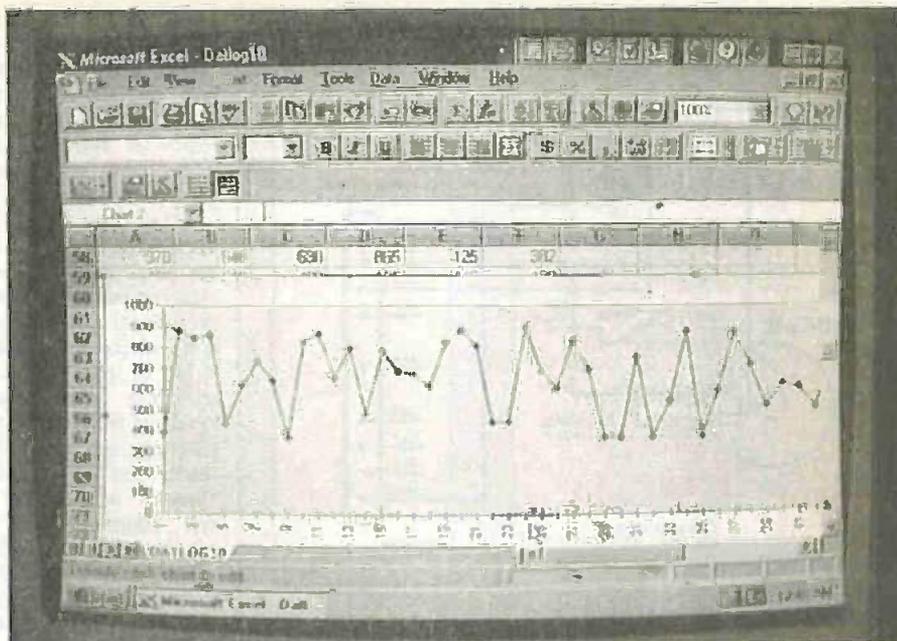


Photo 7. Typical Excel graph display of data recorded during first examination of the Data Logger.

- Click box in column 1 row 5 (box 5A)
- Hold down shift key
- Press cursor down arrow
- Allow cursor to scroll down the rows, with the selected boxes being highlighted
- Stop scrolling on last box before the word END (if you go too far, press cursor up key instead)
- Release cursor key but keep shift key pressed
- Press cursor right key once to highlight column 2 as well
- Release shift key

In one of the panels above the tabulated data an icon showing a graph should be seen – its position and style has been found to be slightly different between computers. (If it is not on display, click on View in the top line then click on Chart to make a tick mark. Click OK then proceed as now described.)

- Click the small arrow immediately to the right of the graph symbol.
- From the graph selection revealed, click on the waveform-like image
- Shift the cursor arrow (which now looks like a graph symbol) over the highlighted data area and click to reveal the Chart Wizard box
- Click on Finish

A coloured graph of the data in columns 1 and 2 now appears, representing the values of the first two channels of data you have recorded.

Only the line for channel 1 should show waveform changes, representing the instantaneous values captured from the signal generator waveform (or just a straight line near the top if a +5V link was used). Photo 7 shows a typical example.

Channel 2 should be represented by a constant value of zero (this should be the case whether or not channel 2 has a memory chip installed).

The height and width of the graph can be changed by positioning the mouse cursor on one of the corners of the graph box so

that a "diagonal" cursor appears. Hold down the mouse left-hand button and drag the cursor in any direction, the box size and shape will change accordingly.

All four box corners can be used in this way, plus midway-points on the box sides. The box can be extended way beyond the limits of the screen area. To end the resizing, release the mouse button. Keyboard scroll and pan keys can now be used to examine various parts of the graph. The graph can also be moved around by click/hold somewhere within it and dragging to a new position.

The data and graph can be jointly printed to paper via the Print option of the File menu (top left). Just the graph on its own can be printed too – explore the tool bar options to find out how.

To clear the graph, right-click the mouse over it and select Clear from the revealed menu.

There are many functions that Excel can perform, including all sorts of manipulations of the data and displays. But this mini intro to Excel is not going any further. Explore for yourself!

SUNDIAL MONITORING

If you have built the *Musical Sundial* (June '99), it is an ideal subject on which to use the Data Logger in a real-life situation. Although not stated in the *Sundial* text, it can be very easily coupled to the Logger and monitored either at a rate set by the Logger, or as triggered by the *Sundial* itself.

Hopefully, you will have seen in *Sundial's* Fig.4 (bottom right) the reference to its test switches being used with the Logger. In which case you simply make connections between *Sundial* switches and Logger as shown now in Fig.3.

When *Sundial's* switches S4 and S5 are switched off, two voltage sources are routed to the Logger. S5 routes the l.d.r. voltage (relative to the level of sunlight illuminating the sensor) at the output of the multiplexers IC1 and IC2 to Logger channel 1. S4 routes one of the multiplexer selector lines (DA7) to channel 3 and provides a

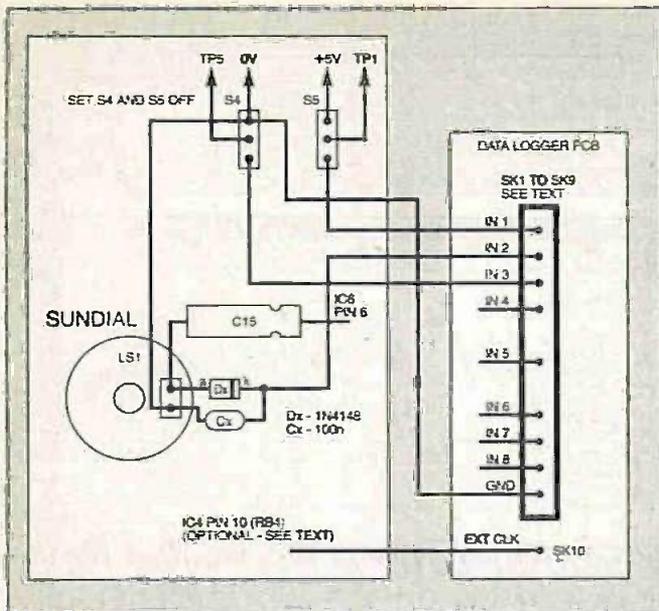


Fig.3. Connections between the Musical Sundial and Data Logger.

sync marker relative to *Sundial's* 16-step cycle.

Monitoring of when *Sundial* goes into one of its several musical modes can be monitored directly from the speaker LS1, but requires the temporary addition of a 1N4148 diode (Dx) and a 100nF capacitor (Cx), as shown in Fig.3. These two components rectify the signal level present on the speaker when an audio signal is being output. The rectified signal is input to Logger channel 2.

AFTER-THOUGHT

After *EPE* went to press with *Sundial*, the author decided to allow its software to generate a trigger pulse on RB4 suited to use as the Logger's external clock. To this end, an RB4 pulse is generated at the start of each of *Sundial's* 16 sampling steps, allowing each sensor's voltage to be synchronously monitored through the full cycle.

It is recognised that you may have already sealed your *Sundial's* p.c.b. and can no longer gain access to its pin RB4 (IC1 pin 10), in which case this synchronous monitoring option is not available to you. However, if you can get to RB4, link it to the Logger at its external clock input (SK10).

To monitor *Sundial* synchronously, set the Logger's rate value to EXT. When running, the positive-going pulses from *Sundial* RB4 will cause the Logger to sample the respective l.d.r. voltage at each cycle step, plus the voltage present on the multiplexer control line. The start of this pulse going high signifies the start of *Sundial's* cycle. *Sundial's* audio output is not monitored in this mode.

For non-synchronous monitoring of *Sundial*, set the Logger's sampling rate to any value you fancy, but a one-second rate is probably best for a trial run through. In this mode, it can never be accurately determined which l.d.r. is actually being monitored at the point of sampling, but the data can still provide a good indication of

prevailing sunlight conditions. The multiplexer pulse voltage will be recorded at each sample but is really of little value when you come to analyse the recording.

What does become interesting, though, is the recording of the audio output in relation to sunlight conditions. It is even possible (with a bit of practice) to recognise when the hours are being marked (chimes, pips and full tune), and when the "Sun's brightening" and "Sun's going" mini-themes are played.

The time at which these events occur can be calculated from the sample count value at that point on the graph in relation to the known

inclusive CD-ROM (all products data and applications info), or as individual booklets.

For further information contact Arizona Microchip Technology, Microchip House, 505 Eskdale Road, Winnersh Triangle, Woking, Berks RG41 5TU. Tel: 0118 921 5858. Fax: 0118 921 5835. Web: <http://www.microchip.com>.

ACKNOWLEDGEMENT

We express our gratitude to Arizona Technologies Ltd for their helpful co-operation in connection with our introduction to and use of the PIC16F87x microcontrollers and associated serial EEPROM devices. The willing assistance of Gordon MacNee is greatly appreciated.

MINI PIC TUTORIAL

Those of you who are interested in programming PICs are recommended to read the *Mini PIC16F87x Tutorial* which is to be published next month. It discusses how to use some of the options offered by the PIC16F877 and, by implication, the other three PICs in this family, the '873, '874 and '876. All four devices were discussed in the *PIC16F87x Review*. □

sampling rate.

When graphing the recording through Excel, highlight columns 1, 2 and 3. If your recording is very lengthy it might be best to examine it in sections.

An example display of data recorded from the *Sundial* is shown in Photo 8.

DATA SHEETS

The full data sheets for the Microchip devices used in the Data Logger are available from Microchip: PIC16F87x family, code DS30292A, serial EEPROM memories: DS21203D (24LC256), DS21191C (24LC128), DS21189B (24LC64), DS21162C (24LC32). There are three ways to obtain them from Microchip: as downloads from their web site, from their fully


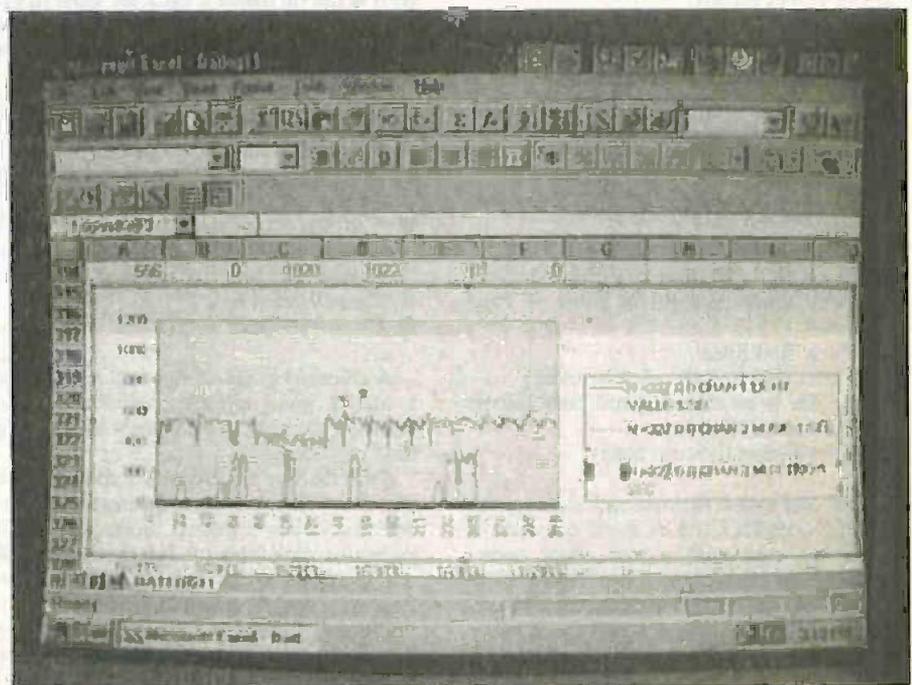
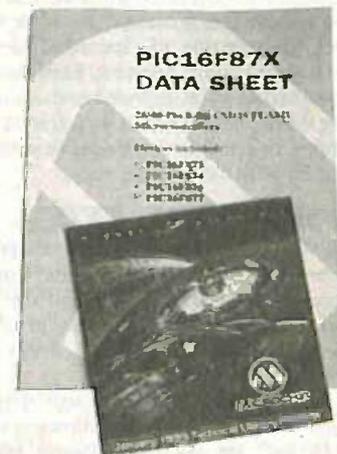


Photo 8. Example of data recorded from the *Sundial* and graphed by Excel.

CIRCUIT SURGERY

ALAN WINSTANLEY
and IAN BELL

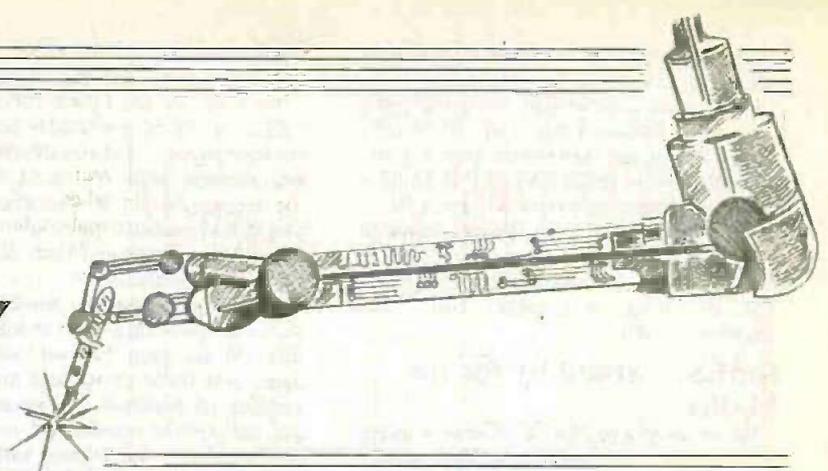

An interesting photo-sensitive amplifier comes under scrutiny in this month's round-up of readers' queries. Our resident team offers a new definition of P.M.P.O. ratings and a maths-intensive approach to R.M.S. values.

THIS month's column is somewhat maths-intensive but we hope there's something for everyone, starting with a straightforward query from a reader involved with car electrical systems.

Transducer User

I'm more of a car mechanic than an electronics engineer and need help using piezo sounders in various car projects. I understand these sounders need a "driver" circuit, could you explain?

I would also like to use 3mm and 5mm l.e.d.s on the 12V supply but I am unable to find the correct resistor. I have a good understanding of car electrics but am a bit lost with some electronics! John Learmonth, Catrine, Ayrshire.

Piezo (pronounced either "peeet-zo" or "pee-ayt-zo") sounders are solid-state transducers which can be used as alarm tone generators as well as high-impedance microphones. They fall into two categories: a piezo transducer is nothing more than a disk of piezo ceramic material, and it is this which requires a separate driver circuit (in the same way, a loudspeaker will not make a warning sound unless you drive it with a suitable audio signal.)

What you need is a piezo buzzer, or piezo siren, which is a completely self-contained unit that will generate a warning tone as soon as a supply is connected. It already contains the driver circuit, and some will produce an ear-splitting sound. They are readily available from good mail-order vendors, but be sure to choose a buzzer and not a "dumb" transducer. There are some practical details in *Circuit Surgery*, May 1997.

Light Work

Typically, a "forward voltage" of about 2V appears across a correctly-biased l.e.d. when illuminated. You must, therefore, "drop" the remaining 10V (of your car electrics supply) by using a series resistor, which must be of a suitable value to limit the current to the required level (say, 10mA to 25mA) as well. How this is achieved is explained in Fig.1.

However, the most practical way of utilising l.e.d.s for what you're doing is to buy the type which has a built-in series resistor. They can be bought for 5V and 12V operation from some mail-order suppliers. Light-emitting diodes are not always much use on car dashboards, though, as they can be "washed out" by direct sunlight. (ARW.)

Photo-sensor

Some time ago I used the 2N5777 photo-Darlington transistor which now seems to be obsolete. Is an equivalent available? P. Jenkins, Liverpool.

Yes it does appear to be obsolete - I have one in stock and I'm hanging on to it! It has a completely transparent TO92 body and was a popular choice of photo-sensor ten years ago.

An old 1995 Cricklewood Electronics catalogue lists them at £5.50 even then! An alternative would be the MEL12 photo Darlington transistor (Maplin) which has a high gain and will probably be every bit as good.

Photo-Darlington transistors are

extremely sensitive, relying on the energy imparted by incidental light onto the semiconductor junction to "trip" the device into conduction. (Old germanium transistors performed the same way, whether you liked it or not. The glass-bodied OC71 transistor was painted black and could be converted into a simple phototransistor by

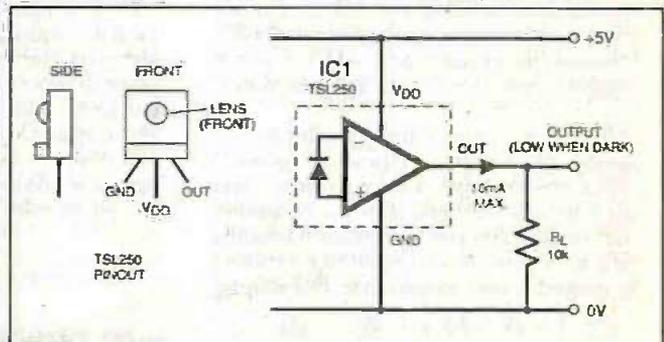


Fig.2. Simple light-to-voltage converter circuit using the Texas TSL250 visible light sensor chip.

scraping away the paint! Hence, I think, the OCP71, a very early photo-transistor.)

Texas Instruments offers an interesting range of CMOS light-to-voltage converters including the TSL250 (for visible light - the TSL260s are tuned for infra-red). They are housed in transparent single-in-line three-pin packs containing a 1mm square photodiode and amplifier behind a lens, all on a single monolithic i.c. The output voltage is directly proportional to the incidental light level. They are very easy to set up and they operate from 2.7V to 5.5V at 10mA absolute maximum load.

A practical light sensor circuit, which outputs a voltage that is proportional to ambient light, is shown in Fig.2. I measured about 3.4V output at maximum brightness, down to 300mV in near darkness.

All that is needed is, say, a comparator or Schmitt trigger and you have an instant snap-action switch without the trial-and-error biasing arrangement that is often associated with photo-Darlington circuits. The TSL250 range is also useful for data reception systems, or by using them to measure

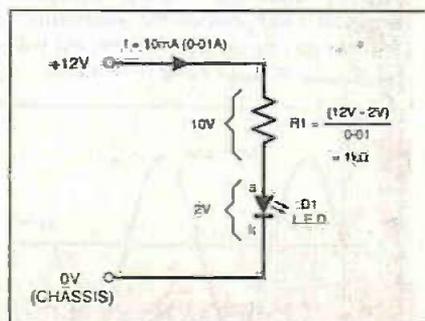


Fig.1. Calculation of a typical series resistor if using an l.e.d. on a 12V car electrical supply, assuming 10mA forward current.

light reflected from an object, a simple proximity sensor may be constructed.

Data sheets can be had from Farnell's free data sheet service (tel. 0113 231 0160). Farnell also sell the devices, e.g. the TSL250 I tested (code 460-898) is £1.87 + VAT, minimum credit card order is £10.

Another product from Texas seems to have gone the same way as your 2N5777, Mr. Jenkins - I couldn't find the useful TSL220 voltage-to-frequency chip listed anywhere. (ARW)

R.M.S. - Stand by for the Maths

We received a number of queries relating to the subject of audio amplifier power output and volume. We hope the following covers most of the concerns addressed by these readers - our reply gets a bit mathematical in places but we have aimed to describe the concepts so that readers who dislike maths can just ignore the equations!

If you have any difficulties understanding it please let us know and we will try to help. There are also some nifty little maths books available from bookstores, including the *Collins Pocket Gem* series which act as a useful memory aid for rusty mathematicians everywhere.

How can I make the output of a 555 timer, drive an 8 ohm 11W speaker at full power from a 12V rail without any complex audio amplifier i.c. or circuitry? The output from pin 3 of the 555 is a short-duration (3 second) tone of about 300Hz. The maximum I can obtain is 5V a.c. which equates to roughly 3 watts. P. Male, Worcs.

Before we answer this specifically we need to discuss what we mean by "power" when dealing with a.c. waveforms, and also make some comments on measuring a.c. signals. The power in watts dissipated in a resistor when a constant (d.c.) voltage is applied is easy to calculate. It is simply:

$$P = IV = IR = V^2/R \quad (1)$$

This calculates the dissipation in watts for a resistor R (ohms) with a voltage V (volts) across it and a current I (amps) flowing through it. Any of the three equations can be used, depending on which circuit values are known.

When we have any form of varying voltage or current (that is, an a.c. waveform) the situation is more complicated. The case usually considered is that of a sinusoidal varying voltage, or sine wave. This is a signal which changes in time in accordance with the mathematical sine function (see Fig. 3).

On Average

The power dissipated in a resistor driven by a sine wave varies from instant to instant in accordance with the equations given above. However, we often need to know what the average power dissipated over a period of time actually is.

This is not simply a matter of taking the average voltage or current - it is zero for a sine wave, but practical experience quickly demonstrates that a resistor will get hot if an a.c. source of sufficient magnitude is connected across it - so the resistor's average power is obviously *not* zero! In fact, the heating effect produced in a resistor

traditionally forms the basis of how we define power for non-d.c. signals.

To work out the power for an arbitrary cyclic waveform, we need to add up all the "contributions" for instantaneous power and average them over the cycle. To find the average height of a number of people you would measure the height of each, add up all the heights and then divide by the number of people.

To find the average power of an a.c. waveform, it would seem to follow that we take I^2R for each "instant" of the waveform, add them all up and divide by the number of instants. Unfortunately, there are an infinite number of instantaneous power values - the current varies continuously, unlike our "people example" where there are a finite number of individuals. So we have to use a special mathematical technique called integration to find our average power.

The average power dissipated in a resistor, R , for a cyclically varying current, i , over the cycle time T of a waveform is given by the equation below. We integrate (indicated by the symbol \int) the waveform over one cycle (0 to T) to add up all the "instantaneous contributions" and divide by T to get the average. The dt in the equation represents an instant of time (t).

$$P = \frac{1}{T} \int_0^T R i^2 dt \quad (2)$$

If we compare this formula with $P=I^2R$ for a d.c. signal we can find a value of d.c. current which would give the same heating effect (power dissipation) as i averaged over one cycle. This is obtained by dividing the above equation by R and taking a square root (if this is hard to follow note we would get I if we did the same to I^2R , which is our d.c. power value). The result is:

$$I_{DC\text{equivalent}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} \quad (3)$$

This means that $P = R \times I_{DC\text{equivalent}}^2$. This equivalent current is called the Root Mean Square or r.m.s. value of the a.c. current. Observe that the current is being squared (i^2 in the equation), averaged by integration and division by T (hence mean) and square-rooted (the $\sqrt{\quad}$ in the equation) - which is where the name comes from. We can define an r.m.s. voltage in the same way.

If we have a sine wave then $i = I_{\text{peak}} \sin(2\pi t/T)$ where t is time and I_{peak} is the peak value of the a.c. current. Now we have to do some more maths - substitute the sinusoidal current equation in equation 3 and perform the integration. We will not go into the details here, but we get $I_{DC\text{equivalent}} = I_{\text{peak}} / \sqrt{2}$ or $0.707 I_{\text{peak}}$.

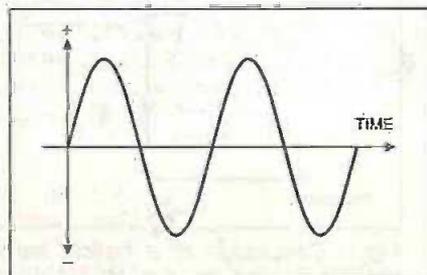


Fig.3. A sine wave, so called because of its mathematical sine function.

This is a formula that may be well known to many readers - to find the r.m.s. value of an a.c. voltage or current, divide peak value by the square root of 2. The ratio of a waveform's peak value to its r.m.s. value is known as the crest factor. The crest factor is $\sqrt{2}$ for sine wave.

At this point it is worth noting that mains electricity voltages are usually quoted as r.m.s. values. For example, an actual 230V a.c. (the UK mains voltage) implies a peak value of 325V a.c. or 650V peak-to-peak. The r.m.s. value is quoted because people are usually interested in heating effect, light output, or power consumption in general when dealing with the mains.

From our equations it should be evident (even if the actual calculation is a bit difficult) that if the waveform is *not* a sine wave, then when we apply equation 3 to get the equivalent current we will not get the same answer. The formula $I_{RMS} = 0.707 I_{\text{peak}}$ is only true for pure sine waves. For any other wave shape we have to apply equation 3 from scratch.

Watts On

This brings us back to the problem posed by the reader. Let us assume that the output of the 555 (or the driver circuit) is a 50 per cent duty-cycle square wave switching between 0V and 12V (this may be not be exactly the case, but it will serve our purposes). This waveform is nothing like a sine wave, so what is the r.m.s. value of the voltage?

Fortunately, in this case (now we understand the principles involved) the situation is simple enough to bypass equation 3. The average heating effect of the waveform is intuitively half that of 12V d.c. - our square wave is like a 12V d.c. signal which is only on for half of the time. So the r.m.s. voltage is 6V. If this was applied directly to an 8 ohm load the power would be $6^2/8$ or 4.5W.

It is also worth noting that a 6V peak sine wave (i.e. 12V peak-to-peak) would dissipate 2.25W in 8 ohms. A 12V peak sine wave (you would need a dual rail $\pm 12V$ supply to handle this) would deliver 9W into 8 ohms. These figures should indicate why the reader is having difficulty, and why power amplifiers often have large supply voltages. For a given maximum drive voltage, the power can be increased by reducing the load resistance (e.g. using a 4 ohm speaker instead of 8 ohm) if the drive circuit is able to cope.

It is not clear how the values were measured in the circuit. Measuring a.c. signals using meters poses some problems. Traditional moving-coil a.c. meters respond to the average of the absolute value of the current (known as the rectified mean) but are calibrated to show the r.m.s. value for a pure sine wave. (An "absolute" value simply means ignoring the sign, for example, the absolute values of +2 and -2 are both 2.)

Such meters will not give accurate readings for signals other than pure sine waves, however, it is possible to calculate correction factors for other waveshapes. Particular care must be taken if measuring a.c. waveforms with d.c. components (i.e. containing a d.c. offset voltage - perhaps an a.c. signal swinging around a d.c. bias voltage rather than 0V) as the d.c. part may influence the measurement.

It is also possible to use a "true r.m.s." converter, and these may be incorporated into digital multimeters. You can purchase r.m.s. to d.c. converter chips which give a d.c. output proportional to the true r.m.s. value of the input waveform. Some of these chips are quite expensive (over £20), but the SSM2110 from Analogue Devices is only around £7, for example.

Measuring Up

Returning again to the reader's query, our calculations above assumed a 12V square wave (equal to the supply) signal applied to the load, however it was stated that only 5V a.c. was obtained. We do not know how this was measured (i.e. if this is a meter reading, or the peak value of a square wave). The low value may be due to measurement error as the waveform is not sinusoidal, or due to the driver-circuit, or a combination of the two.

For the driver circuit we basically need a switching device capable of handling 1.5A (12V into 8 ohms) so a typical low voltage power transistor should do the job. A suitable Darlington driver should be able to achieve this, particularly as the 555 timer can sink or source up to 200mA. It therefore seems likely that the problem is with the measurement of the output power or interpretation of the power available. (IMB).

Powerless to Help

At the same time, we received a related query from a Malaysian reader asking: "Can you tell me the differences between the P.M.P.O. and r.m.s.? I found the first terms on most hi-fis and the

latter used in the 20W Stereo Amplifier published in May, 1998. It seems that both words are related to the output power of an amplifier, but I don't understand the differences between them and how to calculate the P.M.P.O." N. J. How, Malaysia (by E-mail).

The term P.M.P.O. stands for *Peak Music Power Output* and is often seen emblazoned on consumer electronics – stereo systems, CD players etc. – sold in the High Street. The problem with p.m.p.o. figures is that they only indicate the maximum power that can be output for a very short time (usually less than one second) so the figure does not really relate to sustained loudness over normal listening periods. Multimedia loudspeakers are a good example, with 240W to 300W p.m.p.o. being quoted.

On the other hand, the r.m.s. figure for an audio amplifier or loudspeakers gives the *continuous* power that can be handled – which *does* directly relate to "perceived loudness". Although p.m.p.o. figures sound impressive and manufacturers love to quote them, they do not really mean much.

There is no agreed industry standard for p.m.p.o. nor is there an accurate way to relate it to r.m.s. figures. A rule of thumb some people use is to divide p.m.p.o. by a factor to get an approximate r.m.s. figure, but we have seen values from 2 to 20 quoted for this factor!

Quoting p.m.p.o. figures can be very dubious, and may be measured at unacceptably high distortion levels, and more impressive-looking still, "total p.m.p.o."


ratings can be classed as the sum of the two stereo channels combined (usually r.m.s. per channel is quoted on stereo amplifiers). Furthermore, what does "music power" mean? Music signals are very variable. R.M.S. is usually (and should be) quoted for a pure sine wave at a low output distortion value.

In general, if audio equipment specifications quote a p.m.p.o. figure and no r.m.s. value you should be wary. Maybe p.m.p.o. should stand for *Pretty Meaningless Power Over-exaggeration*. (RMS – *Rated More Sensibly?* – ARW). (IMB.)

* In August 1999 *Circuit Surgery*, P. 614, fourth paragraph, the text should read: "The value of R2 must be large enough to prevent excessive current flowing in TR1's collector."


CIRCUIT THERAPY

Circuit Surgery is your column. If you have any queries or comments, please write to: Alan Winstanley, *Circuit Surgery*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset, BH21 1PF, United Kingdom. E-mail: alan@epemag.demon.co.uk. Please indicate if your query is not for publication. A personal reply cannot always be guaranteed but we will try to publish representative answers in this column.

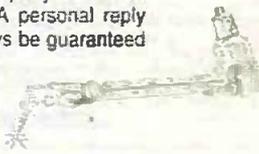

EPE BINDERS

KEEP YOUR MAGAZINES SAFE – RING US NOW!

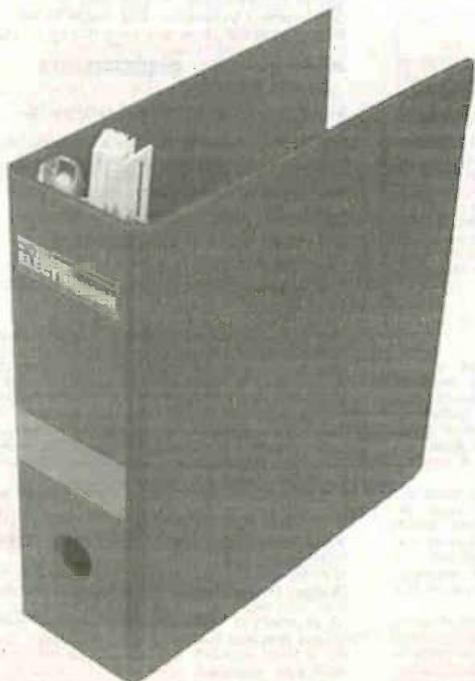

This ring binder uses a special system to allow the issues to be easily removed and re-inserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard-wearing royal blue p.v.c. with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £5.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge (overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by credit card), to Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Fax: 01202 841692. E-mail: editorial@epemag.wimborne.co.uk.

Web site: <http://www.epemag.wimborne.co.uk>


(We cannot reply to queries or confirm overseas orders by Fax due to the cost.)



We also accept credit card payments. Mastercard or Visa (minimum credit card order £5). Send your card number and card expiry date plus cardholder's address.

DIRECT BOOK SERVICE

Circuits and Design

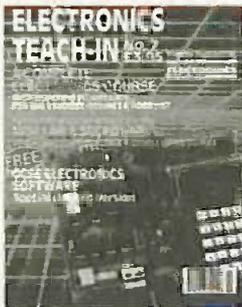

ELECTRONICS TEACH-IN No. 7. ANALOGUE AND DIGITAL ELECTRONICS COURSE

FREE SOFTWARE

(published by *Everyday Practical Electronics*)
Alan Winstanley and Keith Dye B.Eng(TECH)AMIEE
This highly acclaimed *EPE Teach-In* series, which included the construction and use of the *Mini Lab* and *Micro Lab* test and development units, has been put together in book form. Additionally, EPT Educational Software have developed a GCSE Electronics software program to complement the course and a FREE DISK covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The *Mini Lab* and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way; you will both see and hear the electron in action! The *Micro Lab* microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.

160 pages **Order code N17**

£3.95

ELECTRONICS PROJECTS USING ELECTRONICS WORKBENCH plus FREE CD-ROM

FREE CD-ROM

M. R. Horsey
This book offers a wide range of tested circuit modules which can be used as electronics projects, part of an electronics course, or as a hands-on way of getting better acquainted with Electronics Workbench. With circuits ranging from 'bulbs and batteries' to complex systems using integrated circuits, the projects will appeal to novices, students and practitioners alike.

Electronics Workbench is a highly versatile computer simulation package which enables the user to design, test and modify their circuits before building them, and to plan PCB layouts on-screen. All the circuits in the book are provided as runnable Electronic Workbench files on the enclosed CD-ROM, and a selection of 15 representative circuits can be explored using the free demo version of the application.

Contents: Some basic concepts; Projects with switches, LEDs, relays and diodes; Transistors; Power supplies; Op-amp projects; Further op-amp circuits; Logic gates; Real logic circuits; Logic gate multivibrators; The 555 timer; Flip-flops, counters and shift registers; Adders, comparators and multiplexers; Field effect transistors; Thyristors, triacs and diacs; Constructing your circuit; Index.

227 pages

Order code NE23

£14.99

A BEGINNER'S GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor.

170 pages

Order code BP285

£4.99

PRACTICAL REMOTE CONTROL PROJECTS

Owen Bishop

Provides a wealth of circuits and circuit modules for use in remote control systems of all kinds; ultrasonic, infrared, optical fibre, cable and radio. There are instructions for building fourteen novel and practical remote control projects. But this is not all, as each of these projects provides a model for building dozens of other related circuits by simply modifying parts of the design slightly to suit your own requirements. This book tells you how.

Also included are techniques for connecting a PC to a remote control system, the use of a microcontroller in remote control, as exemplified by the BASIC Stamp, and the application of ready-made type-approved 418MHz radio transmitter and receiver modules to remote control systems.

160 pages

Order code BP413

£5.99

DISCOVERING ELECTRONIC CLOCKS

W. D. Phillips

This is a whole book about designing and making electronic clocks. You start by connecting HIGH and LOW logic signals to logic gates. You find out about and then build and test bistables, crystal-controlled astables, counters, decoders and displays. All of these subsystems are carefully explained, with practical work supported by easy to follow prototype board layouts.

Full constructional details, including circuit diagrams and a printed circuit board pattern, are given for a digital electronic clock. The circuit for the First Clock is modified and developed to produce additional designs which include a Big Digit Clock, Binary Clock, Linear Clock, Andrew's Clock (with a semi-analogue display), and a Circle Clock. All of these designs are unusual and distinctive.

This is an ideal resource for project work in GCSE Design and Technology, Electronics Product, and for project work in AS-Level and A-Level Electronics and Technology.

194 pages, A4 spiral bound

Order code NE24

£16.50

DOMESTIC SECURITY SYSTEMS

A. L. Brown

This book shows you how, with common sense and basic do-it-yourself skills, you can protect your home. It also gives tips and ideas which will help you to maintain and improve your home security, even if you already have an alarm. Every circuit in this book is clearly described and illustrated, and contains components that are easy to source. Advice and guidance are based on the real experience of the author who is an alarm installer, and the designs themselves have been rigorously put to use on some of the most crime-ridden streets in the world.

The designs include all elements, including sensors, detectors, alarms, controls, lights, video and door entry systems. Chapters cover installation, testing, maintenance and upgrading.

192 pages

Order code NE25

£12.99

MICROCONTROLLER COOKBOOK

Mike James

The practical solutions to real problems shown in this cookbook provide the basis to make PIC and 8051 devices really work. Capabilities of the variants are examined, and ways to enhance these are shown. A survey of common interface devices, and a description of programming models, lead on to a section on development techniques. The cookbook offers an introduction that will allow any user, novice or experienced, to make the most of microcontrollers.

240 pages

Order code NE26

£19.99

A BEGINNER'S GUIDE TO TTL DIGITAL ICs

R. A. Penfold

This book first covers the basics of simple logic circuits in general, and then progresses to specific TTL logic integrated circuits. The devices covered include gates, oscillators, timers, flip-flops, dividers, and decoder circuits. Some practical circuits are used to illustrate the use of TTL devices in the 'real world'.

142 pages

Order code BP282

£4.95

ELECTRONIC MODULES AND SYSTEMS FOR BEGINNERS

Owen Bishop

This book describes over 60 modular electronic circuits, how they work, how to build them, and how to use them. The modules may be wired together to make hundreds of different electronic systems, both analogue and digital. To show the reader how to begin building systems from modules, a selection of over 25 electronic systems are described in detail, covering such widely differing applications as timing, home security, measurement, audio (including a simple radio receiver), games and remote control.

200 pages

Temporarily out of print

PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

F. A. Wilson, C.G.J.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and 'cut-and-try' methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias - tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages

Temporarily out of print

The books listed have been selected by *Everyday Practical Electronics/ETI* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

FOR ANOTHER SELECTION OF BOOKS SEE THE NEXT TWO MONTH'S ISSUES.

Note our UK postage costs just £1.50 no matter how many books you order!

Computing

WINDOWS 95 EXPLAINED

P. R. M. Oliver and N. Kantaris

If you would like to get up and running, as soon as possible, with the new Windows 95 operating system, then this is the book for you.

The book was written with the non-expert, busy person in mind. It explains the hardware that you need in order to run Windows 95 successfully, and how to install and optimize your system's resources. It presents an overview of the Windows 95 environment.

Later chapters cover how to work with programs, folders and documents; how to control Windows 95 and use the many accessories that come with it; how to use DOS programs and, if necessary, DOS commands and how to communicate with the rest of the electronic world.

170 pages

Order code BP400

£5.95

INTERFACING PCs AND COMPATIBLES

R. A. Penfold

Once you know how, PC interfacing is less involved than interfacing many eight-bit machines, which have tended to use some unusual interfacing methods.

This book gives you: A detailed description of the lines present on the PC expansion bus. A detailed discussion of the physical characteristics of PC expansion cards. The I/O map and details of the areas where your add-on can be fitted. A discussion of address decoding techniques. Practical address decoder circuits. Simple TTL 8-bit input and output ports. Details of using the 8255 parallel interface adaptor. Digital to analogue converter circuits. In fact everything you need to know in order to produce successful PC add-ons.

80 pages

Temporarily out of print

EASY PC INTERFACING

R. A. Penfold

Although the internal expansion slots of a PC provide full access to the computer's buses, and are suitable for user add-ons, making your own expansion cards requires a fair amount of expertise and equipment. The built-in ports provide what is often a much easier and hassle-free way of interfacing your own circuits to a PC. In particular, a PC printer port plus a small amount

of external hardware provides a surprisingly versatile input/output port. The PC 'games' port is less useful for general interfacing purposes, but it can be useful in some applications.

This book provides a number of useful PC add-on circuits including the following: Digital input/output ports; Analogue-to-digital converter; Digital-to-Analogue Converter; Voltage and Current measurement circuits; Resistance meter; Capacitance meter; Temperature measurement interface; Biofeedback monitor; Constant voltage model train controller; Pulsed model train controllers; Position sensor (optical, Hall effect, etc.); Stepper motor interface; Relay and LED drivers; Triac mains switching interface.

179 pages

Order code BP285

£4.99

INTRODUCTION TO MICROPROCESSORS

John Crisp

If you are, or soon will be, involved in the use of microprocessors, this practical introduction is essential reading. This book provides a thoroughly readable introduction to microprocessors, assuming no previous knowledge of the subject, nor a technical or mathematical background. It is suitable for students, technicians, engineers and hobbyists, and covers the full range of modern microprocessors.

After a thorough introduction to the subject, ideas are developed progressively in a well-structured format. All technical terms are carefully introduced and subjects which have proved difficult, for example 2's complement, are clearly explained. John Crisp covers the complete range of microprocessors from the popular 4-bit and 8-bit designs to today's super-fast 32-bit and 64-bit versions that power PCs and engine management systems etc.

Contents: The world changed in 1971; Microprocessors don't have ten fingers; More counting; Mathematical micros; It's all a matter of logic; Registers and memories; A microprocessor based system; A typical 8-bit microprocessor; Programming; High level languages; Micros are getting bigger and faster; The pentium; The PowerPC; The Alpha 21164 microprocessor; Interfacing; Test equipment and fault finding.

222 pages

Order code NE21

£16.99

Theory and Reference

Bebop To The Boolean Boogie

By Clive (call me Max)
Maxfield
ORDER CODE BEB1

£24.95

470 pages. Large format

*Specially imported by EPE –
Excellent value*

An Unconventional Guide to
Electronics Fundamentals,
Components and Processes

This book gives the "big picture" of digital electronics. This in-depth, highly readable, up-to-the-minute guide shows you how electronic devices work and how they're made. You'll discover how transistors operate, how printed circuit boards are fabricated, and what the innards of memory ICs look like. You'll also gain a working knowledge of Boolean algebra and Karnaugh maps, and understand what Reed-Muller logic is and how it's used. And there's much, MUCH more (including a recipe for a truly great seafood gumbo!). Hundreds of carefully drawn illustrations clearly show the important points of each topic. The author's tongue-in-cheek British humor makes it a delight to read, but this is a REAL technical book, extremely detailed and accurate. A great reference for your own shelf, and also an ideal gift for a friend or family member who wants to understand what it is you do all day....

470 pages – large format

Order code BEB1

£24.95

DIGITAL ELECTRONICS – A PRACTICAL APPROACH
With FREE Software: Number One Systems – EASY-PC
Professional XM and Pulsar (Limited Functionality)

Richard Monk

Covers binary arithmetic, Boolean algebra and logic gates, combination logic, sequential logic including the design and construction of asynchronous and synchronous circuits and register circuits. Together with a considerable practical content plus the additional attraction of its close association with computer-aided design including the FREE software.

There is a "blow-by-blow" guide to the use of EASY-PC Professional XM (a schematic drawing and printed circuit board design computer package). The guide also conducts the reader through logic circuit simulation using Pulsar software. Chapters on p.c.b. physics and p.c.b. production techniques make the book unique, and with its host of project ideas make it an ideal companion for the integrative assignment and common skills components required by BTEC and the key skills demanded by GNVQ. The principal aim of the book is to provide a straightforward approach to the understanding of digital electronics.

Those who prefer the "Teach-In" approach or would rather experiment with some simple circuits should find the book's final chapters on printed circuit board production and project ideas especially useful.

250 pages

Order code NE28

£16.99

DIGITAL GATES AND FLIP-FLOPS

Ian R. Sinclair

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages

Order code NE105

£8.95

FREE
SOFTWARE

Bebop Bytes Back

By Clive "Max" Maxfield
and Alvin Brown

ORDER CODE BEB2

£29.95

Over 500 pages. Large
format

*Specially imported by
EPE – Excellent value*

An Unconventional Guide
To Computers

Plus FREE CD-ROM which includes:
Fully Functional Internet-Ready
Virtual Computer with Interactive
Labs

This follow-on to *Bebop To The Boolean Boogie* is a multimedia extravaganza of information about how computers work. It picks up where "Bebop!" left off, guiding you through the fascinating world of computer design... and you'll have a few chuckles, if not belly laughs, along the way. In addition to over 200 megabytes of mega-cool multimedia, the accompanying CD-ROM (for Windows 95 machines only) contains a virtual microcomputer, simulating the motherboard and standard computer peripherals in an extremely realistic manner. In addition to a wealth of technical information, myriad nuggets of trivia, and hundreds of carefully drawn illustrations, the book contains a set of lab experiments for the virtual microcomputer that let you recreate the experiences of early computer pioneers. If you're the slightest bit interested in the inner workings of computers, then don't dare to miss this one!

Over 500 pages – large format

Order code BEB2

£29.95

Bebop BYTES Back
An Unconventional Guide To
Computers



NEWNES INTERACTIVE ELECTRONIC CIRCUITS CD-ROM
Edited by Owen Bishop

An expert adviser, an encyclopedia, an analytical tool and a source of real design data, all in one CD-ROM. Written by leading electronics experts, the collected wisdom of the electronics world is at your fingertips. The simple and attractive Circuits Environment™ is designed to allow you to find the circuit or advice notes of your choice quickly and easily using the search facility. The text is written by leading experts as if they were explaining the points to you face to face. Over 1,000 circuit diagrams are presented in a standardised form, and you are given the option to analyse them by clicking on the Action icon. The circuit groups covered are: Amplifiers, Oscillators, Power, Sensing, Signal Processing, Filters, Measurement, Timing, Logic Circuits, Telecommunications.

The analysis tool chosen is SpiceAge for Windows, a powerful and intuitive application, a simple version of which automatically bursts into action when selected.

Newnes Interactive Electronic Circuits allows you to: analyse circuits using top simulation program SpiceAge; test your design skills on a selection of problem circuits; clip comments to any page and define bookmarks; modify component values within the circuits; call up and display useful formulae which remain on screen; look up over 100 electronic terms in the glossary; print and export netlists.

System Requirements: PC running Windows 3.x, 95 or NT on a 386 or better processor, 4MB RAM, 8MB disk space.

CD-ROM

Order code NE-CD1

£49.99

NEW
CD-ROM

Audio and Music

AN INTRODUCTION TO LOUDSPEAKERS AND
ENCLOSURE DESIGN

V. Capel

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him- or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the Kapellmeister loudspeaker enclosure.

148 pages

Order code BP255

£3.99

PRÉAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent

performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases). The preamplifier circuits featured include: Microphone preamplifiers (low impedance, high impedance, and crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include: Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and low-pass). Scratch and rumble filters. Loudness filter. Audio mixers. Volume and balance controls.

92 pages

Order code BP309

£3.99

HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold

Practical construction details of how to build a number of audio power amplifiers ranging from about 50 to 300/400 watts r.m.s. includes MOSFET and bipolar transistor designs.

96 pages

Order code BP277A

£3.99

ACOUSTIC FEEDBACK – HOW TO AVOID IT

V. Capel

Feedback is the bane of all public address systems. While feedback cannot be completely eliminated, many things can be done to reduce it to a level at which it is no longer a problem.

Much of the trouble is often the hall itself, not the equipment, but there is a simple and practical way of greatly improving acoustics. Some microphones are prone to feedback while others are not. Certain loudspeaker systems are much better than others, and the way the units are positioned can produce a reduced feedback. All these matters are fully explored as well as electronic aids such as equalizers, frequency-shifters and notch filters.

The special requirements of live group concerts are considered, and also the related problem of instability that is sometimes encountered with large set-ups. We even take a look at some unsuccessful attempts to cure feedback so as to save readers wasted time and effort duplicating them.

Also included is the circuit and layout of an inexpensive but highly successful twin-notch filter, and details on how to operate it.

92 pages

Order code BP310

£4.99

Testing, Theory, Data and Reference

SCROGGIE'S FOUNDATIONS OF WIRELESS AND ELECTRONICS - ELEVENTH EDITION

S. V. Amos and Roger Amos
Scroggie's Foundations is a classic text for anyone working with electronics, who needs to know the art and craft of the subject. It covers both the theory and practical aspects of a huge range of topics from valve and tube technology, and the application of cathode ray tubes to radar, to digital tape systems and optical recording techniques.

Since Foundations of Wireless was first published over 60 years ago, it has helped many thousands of readers to become familiar with the principles of radio and electronics. The original author Sowerby was succeeded by Scroggie in the 1940s, whose name became synonymous with this classic primer for practitioners and students alike. Stan Amos, one of the fathers of modern electronics and the author of many well-known books in the area, took over the revision of this book in the 1980s and it is he, with his son, who have produced this latest version. 400 pages **Order code NE27** £19.99

ELECTRONICS MADE SIMPLE

Ian Sinclair
Assuming no prior knowledge, Electronics Made Simple presents an outline of modern electronics with an emphasis on understanding how systems work rather than on details of circuit diagrams and calculations. It is ideal for students on a range of courses in electronics, including GCSE, C&G and GNVQ, and for students of other subjects who will be using electronic instruments and methods.

Contents: waves and pulses, passive components, active components and ICs, linear circuits, block and circuit diagrams, how radio works, disc and tape recording, elements of TV and radar, digital signals, gating and logic circuits, counting and correcting, microprocessors, calculators and computers, miscellaneous systems. Page 169 (large format) **Order code NE23** £12.99

TRANSISTOR DATA TABLES

Hans-Günther Steidle
The tables in this book contain information about the package shape, pin connections and basic electrical data for each of the many thousands of transistors listed. The data includes maximum reverse voltage, forward current and power dissipation, current gain and forward transmittance and resistance, cut-off frequency and details of applications.

A book of this size is of necessity restricted in its scope, and the individual transistor types cannot therefore be described in the sort of detail that maybe found in some larger and considerably more expensive data books. However, the list of manufacturers' addresses will make it easier for the prospective user to obtain further information, if necessary.

Lists over 8,000 different transistors, including f.e.t.s. 200 pages **Order code NE24** £12.99

MORE ADVANCED USES OF THE MULTIMETER

R. A. Penfold

This book is primarily intended as a follow-up to BP239, (see below), and should also be of value to anyone who already understands the basics of voltage testing and simple component testing. By using the techniques described in Chapter 1 you can test and analyse the performance of a range of components with just a multimeter (plus a very few inexpensive components in some cases). Some useful quick check methods are also covered.

While a multimeter is supremely versatile, it does have its limitations. The simple add-ons described in Chapter 2 extended the capabilities of a multimeter to make it even more useful. 64 pages **Order code BP265** £2.95



ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of the instruments are also examined.

Everything from Oscillators, through R, C & L measurements (and much more) to Waveform Generators and testing Zeners. 206 pages **Order code PC109** £8.95

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects. 90 pages **Order code BP259** £2.95

NEWNES ELECTRONICS TOOLKIT - SECOND EDITION

Geoff Phillips

The author has used his 30 years experience in industry to draw together the basic information that is constantly demanded. Facts, formulae, data and charts are presented

to help the engineer when designing, developing, evaluating, fault finding and repairing electronic circuits. The result is this handy workmate volume: a memory aid, tutor and reference source which is recommended to all electronics engineers, students and technicians.

Have you ever wished for a concise and comprehensive guide to electronics concepts and rules of thumb? Have you ever been unable to source a component, or choose between two alternatives for a particular application? How much time do you spend searching for basic facts or manufacturer's specifications? This book is the answer, it covers resistors, capacitors, inductors, semiconductors, logic circuits, EMC, audio, electronics and music, telephones, electronics in lighting, thermal considerations, connections, reference data. 158 pages **Order code NE20** £12.99

PRACTICAL ELECTRONIC FAULT FINDING AND TROUBLESHOOTING

Robin Pain

This is not a book of theory. It is a book of practical tips, hints, and rules of thumb, all of which will equip the reader to tackle any job. You may be an engineer or technician in search of information and guidance, a college student, a hobbyist building a project from a magazine, or simply a keen self-taught amateur who is interested in electronic fault finding but finds books on the subject too mathematical or specialized.

The book covers: Basics - Voltage, current and resistance; Capacitance, inductance and impedance; Diodes and transistors; Op-amps and negative feedback; Fault finding - Analogue fault finding, Digital fault finding;

Memory; Binary and hexadecimal; Addressing; Discrete logic; Microprocessor action; I/O control; CRT control; Dynamic RAM; Fault finding digital systems; Dual trace oscilloscope; IC replacement. 274 pages **Order code NE22** £18.99

AN INTRODUCTION TO LIGHT IN ELECTRONICS

F. A. Wilson

This book is not for the expert but neither is it for the completely uninitiated. It is assumed the reader has some basic knowledge of electronics. After dealing with subjects like Fundamentals, Waves and Particles and The Nature of Light such things as Emitters, Detectors and Displays are discussed. Chapter 7 details four different types of Lasers before concluding with a chapter on Fibre Optics. 161 pages **Order code BP359** £4.95

UNDERSTANDING DIGITAL TECHNOLOGY

F. A. Wilson C.G.I.A., C.Eng., F.I.E.E., F.I. Mgt.

This book examines what digital technology has to offer and then considers its arithmetic and how it can be arranged for making decisions in so many processes. It then looks at the part digital has to play in the ever expanding Information Technology, especially in modern transmission systems and television. It avoids getting deeply involved in mathematics.

Various chapters cover: Digital Arithmetic, Electronic Logic, Conversions between Analogue and Digital Structures, Transmission Systems. Several Appendices explain some of the concepts more fully and a glossary of terms is included. 183 pages **Order code BP376** £4.95

Project Building

ELECTRONIC PROJECT BUILDING FOR BEGINNERS

R. A. Penfold

This book is for complete beginners to electronic project building. It provides a complete introduction to the practical side of this fascinating hobby, including:

Component identification, and buying the right parts; resistor colour codes, capacitor value markings, etc; advice on buying the right tools for the job; soldering; making easy work of the hard wiring; construction methods, including stripboard, custom printed circuit boards, plain matrix boards, surface mount boards and wire-wrapping; finishing off, and adding panel labels; getting "problem" projects to work, including simple methods of fault-finding.

In fact everything you need to know in order to get started in this absorbing and creative hobby. 135 pages **Order code BP362** £4.95

45 SIMPLE ELECTRONIC TERMINAL BLOCK PROJECTS

R. Babbington

Contains 45 easy-to-build electronic projects that can be constructed by an absolute beginner, on terminal blocks using only a screwdriver and other simple hand tools. No soldering is needed.

Most of the projects can be simply screwed together, by following the layout diagrams, in a matter of minutes and readily unscrewed if desired to make new circuits. A theoretical circuit diagram is also included with each project to help broaden the constructor's knowledge.

The projects included in this book cover a wide range of interests under the chapter headings: Connections and Components, Sound and Music, Entertainment, Security Devices, Communication, Test and Measuring. 163 pages **Order code BP373** £4.95

30 SIMPLE IC TERMINAL BLOCK PROJECTS

R. Babbington

Follow on from BP378 using ICs. 117 pages **Order code BP379** £4.99

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.S

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s. 80 pages **Order code BP121** £3.99

BOOK ORDERING DETAILS

Our postage price is the same no matter how many books you order, just add £1.50 to your total order for postage and packing (overseas readers add £3 for countries in the EEC, or add £6 for all countries outside the EEC, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to Direct Book Service or credit card details, Visa or Mastercard - minimum credit card order is £5 - to: DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET BH21 1RW (mail order only).

Books are normally sent within seven days of receipt of order but please allow a maximum of 28 days for delivery - more for overseas orders. Please check price and availability (see latest issue of Everyday Practical Electronics/ETI) before ordering from old lists.

For a further selection of books see the next two issues of EPE/ETI.

DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD. Tel 01202 881749

Fax 01202 841692. Due to the cost we cannot reply to overseas orders or queries by Fax.

E-mail: dbs@epemag.wimborne.co.uk

BOOK ORDER FORM

Full name:

Address:

Post code: Telephone No:

Signature:

I enclose cheque/PO payable to WIMBORNE PUBLISHING LTD for £

Please charge my Visa/Mastercard £ Card expiry date:

Card Number:


Please send book order codes:

Please continue on separate sheet of paper if necessary

SURFING THE INTERNET

NET WORK

ALAN WINSTANLEY

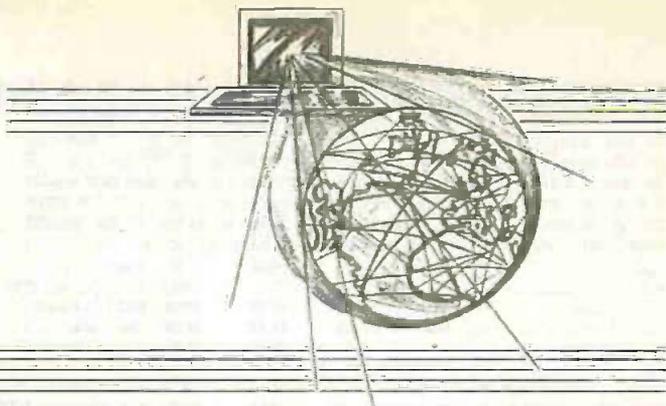

THERE are several new uploads to the *EPE* web site (www.epemag.wimborne.co.uk), including a new series of pages devoted to the *Modern Electronics Manual* and the *Electronics Service Manual*. Both Manuals are constantly updated A4 ring binders designed for students or hobbyists, or those seeking training or re-training in basic electronics. The web pages provide a comprehensive listing of each Manual's contents, and there is also a new facility for secure on-line ordering with world-wide shipping. You can view these pages by going to [manuals.htm](#) on the *EPE* web site, or follow the links.

DESOLDERING GUIDE

The author has finally created the sequel to the popular *Basic Soldering Guide*, an on-line resource which is used by colleges, students and technicians. The "BSG" is linked by the Edinburgh Engineering Virtual Library and is a well-established educational resource. The new follow-up is the *Basic Desoldering Guide*, which illustrates simple techniques of using desoldering pumps as well as copper braid. There is also the new *Black Museum of Bad Soldering* which depicts some real-life examples of poor soldering technique (the author is collecting more). You can catch up with all of this – fourteen colour photos in all – at [desolderpix.htm](#).

ZOOM THROUGH THE HAYES

If you're out looking for a new modem, read the box carefully! One classed as a "Winmodem" relies on the processor power of a Windows PC instead of its own built-in signal processing. They will only work in Windows. The giveaway is that they are usually cheaper than "fully blown" modems by £10 or £20 or more. 3COM/US Robotics is the best known brand of Winmodem which appear as OEM internal modems favoured by Dell and others.

An alternative type of Winmodem uses the Lucent chipset and is manufactured under many brands: Zoom (www.zoomtel.com) produces such a PCI card (hence the telltale "LT" Winmodem label). Look closely in the specifications or ads for talk of "using the power of Windows" or "only works in Windows" – sure signs that you're holding a cheaper Winmodem rather than a completely stand-alone device.

A Winmodem will be perfectly adequate for many users, but some brands are evidently more highly regarded than others. One major advantage of the budget Zoom PCI internal Winmodem, apart from the fact that unlike a traditional ISA card it will happily share Interrupts, is that it is easy to upgrade the Windows driver without needing to "flash" the modem firmware. It may simply require copying over a new .vxd driver file into Windows. Unlike a firmware flash upgrade, which is a one-way street, this means that the old drivers can be restored by the user if desired, so you can experiment to obtain the best overall performance. The most comprehensive resource on Lucent chipset modems and others is available on <http://808hi.com/56k/x2-lucent.htm>

Hayes Corporation is usually the name associated with computer modem technology, and many experienced users will have grappled with the arcane delights of the Hayes Command Set when trying to coax a modem into operation at one time or another. Modem settings can be customised with the addition of the appropriate command in the "init string" – the chain of Hayes commands which initialises the modem each time it dials. Windows 95/98 users can add extra settings by going to Device Manager/Modems (*select yours*)/Properties/Connection/Advanced. Modem handbooks often quote the available Hayes command switches.

In April, Zoom announced that it had acquired much of Hayes Communications' modem assets. This includes well-known brands such as Hayes and Accura. Bundled into the deal was the entire assets of Hayes Europe along with Hayes' UK headquarters.

I have been pretty encouraged by my own experiences with Zoom modems. Close examination inside a recent desktop PC

revealed its modem was actually an old US Robotics X2 Winmodem, a 33.6K version at that, "flashed" up to 56K. I decided to "flash" it further to V.90 using the latest patch from USR (now 3COM) to see if it would improve its negotiation. Doing so can be a nerve-wracking experience, because applying the wrong patch can render a modem totally unusable. Since ISP's V.90 compatibility standards are gradually being refined, it is wise to get in the habit of checking for the latest modem driver or firmware upgrades, the latter usually being "flashed" into the modem's PROM chip using a simple on-screen procedure. In my case the upgrade didn't make much difference to reliability. Time for a change.

I decided to experiment with a Zoom Dual-Standard 56K/X2 flash-upgradeable internal modem. The Zoom has a five-year guarantee with improved built-in lightning protection and it installed immediately without hesitation. Performance and negotiation was generally more reliable than the USR, although this could partly be due to the type of modem racks in use at the other end: perhaps they didn't like my USR card much.

Later I handed the Zoom over to another user along with a V.90 flash upgrade file, which somehow turned out to be the wrong one. After running the upgrade the modem was crippled, but praise goes to Zoom UK who graciously provided another (V.90) PROM chip, and now it works fine. Rather than revert to the earlier ISA modem, though, I settled for another off-the-peg Zoom, this time a 56K/V.90 Dual Standard PCI Winmodem. This also installed easily, and it will have to do until ISDN2e or ADSL comes along, as wireless modems and cable modems are frustratingly out of reach. In the meantime I can busy myself fiddling with different version of Windows drivers.

BIG FOOTED E-MAIL FOR LIFE

If you have several E-mail addresses, or indeed if you keep changing your Internet Service Provider, one useful way to keep things under control is to use an E-mail re-direction service. One which has been running for a couple of years now is Bigfoot (www.bigfoot.com), an unfortunate name perhaps but a proven and reliable service!

One drawback to changing ISPs is the often longwinded task of informing everybody of your change of address. Bigfoot has several free options to help make life a little easier. Mail can be forwarded to a single E-mail address or forwarded on to a maximum of five addresses, the latter is useful if you travel and use CompuServe or AOL to log in whilst abroad.

The addresses to which you would like your mail redirected are set up through the members' page at Bigfoot's web site, and when you need to alter any of the addresses it is a straightforward task to input a new E-mail address. After registering you are given an address in the form of yourname@bigfoot.com which you then hand out to all and sundry, safe in the knowledge that your true address can change whenever you like.

For those people who post messages to Usenet (newsgroups) the Bigfoot service also offers a Spam (unsolicited E-mail) blocking option so that mail from known sources of Spam is not forwarded. Something to check out next time you are on-line.

VIRUS UPDATES

Much has been written about Windows viruses, especially Melissa (June '99 *Net Work*) and Worm.Explore.Zip (first unleashed in Israel in June '99, also see August '99 *Net Work*). Microsoft has posted a fix which discourages Outlook users from opening a possibly harmful E-mail attachment, thereby also reducing the virus' propagation to the addresses contained in the Address Book. Go to officeupdate.microsoft.com for the patches (Outlook 97, 98, 2000).

Don't forget to check the *Net Work* page of the *EPE* web site for this month's round up of suggested URLs. My E-mail address is alan@epemag.demon.co.uk

BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or the next two issues of *Everyday Practical Electronics* (all books with a BP prefix to the order code are Babani books). Many readers have asked us to also supply various other Babani books, which have a reputation for value for money.

Our customers tell us they appreciate our speedy service and low postage charge and they would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (1.50p for UK p&p no matter how many books you buy). We are pleased to be able to respond; we are now able to meet *all* your requirements for Babani books - if it's in print we can supply it.

Code	Title	Price	Code	Title	Price	Code	Title	Price
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	£1.95	BP326	An Introduction to Satellite Communications	£5.95	BP338	Sage Instant Accounting Explained	£5.95
BP37	50 Projects using Relays, SCRs and TRIACs	£2.95	BP327	DOS One Step at a Time (covers Version 6.2)	£4.99	BP399	Windows '95 One Step at a Time	£4.95
BP44	IC 555 Projects	£3.99	BP328	Sage Explained	£5.95	BP403	The Internet and World Wide Web Explained	£5.95
BP76	Power Supply Projects	O.O.P.	BP329	Electronic Music Learning Projects	£4.95	BP404	How to Create Pages for the Web Using HTML	£5.99
BP125	25 Simple Amateur Band Aerials	£1.95	BP331	A Beginners Guide to MIDI	£4.95	BP405	MS Works for Windows 95 explained	£5.95
BP132	25 Simple SW Broadcast Band Aerials	£1.95	BP334	Magic Electronics Projects	£4.95	BP406	MS-Word 95 Explained	£6.99
BP144	Further Practical Electronics Calculations & Formulae	£4.95	BP337	A Concise Users Guide to Lotus 1-2-3 for Windows	£5.95	BP407	Excel 95 Explained	£6.99
BP145	25 Simple Tropical and MW Band Aerials	£1.75	BP341	MS-DOS Explained (covers V6.2)	£6.99	BP408	Access 95 - One Step at a Time	£5.99
BP162	MIDI Projects	£2.95	BP345	Getting Started in Practical Electronics	£4.99	BP409	MS Office 95 One Step at a Time	£6.99
BP164	An Introduction to 68000 Assembly Language	£2.95	BP346	Programming in Visual BASIC for Windows	£6.95	BP410	35 Opto-Display Terminal Block Projects	£4.99
BP192	More Advanced Power Supply Projects	£2.95	BP349	Practical Opto-Electronic Projects	£4.95	BP412	A Practical Approach to Excel for Windows 95	£4.99
BP258	Learning to Program in C	£4.95	BP350	Electronic Board Games	£4.95	BP415	Using Netscape on the Internet	£6.95
BP259	A Concise Introduction to UNIX	£4.95	BP352	Excel 5 Explained	£5.95	BP416	Practical Alarm Projects	£4.99
BP261	A Concise Introduction to Lotus 1-2-3 (Revised Edition)	£3.95	BP355	A Guide to the World's Radio Stations (1995/6 Edition)	£5.95	BP417	Explaining Microsoft Publisher for Windows 95	£5.99
BP262	A Concise Introduction to Wordperfect (Revised Edition)	£3.95	BP362	Access One Step at a Time	£4.95	BP418	Word 95 Assistant	£6.99
BP273	Practical Electronic Sensors	£4.99	BP363	Practical Electronic Music Projects	£4.95	BP419	Using Microsoft Explorer on the Internet	£6.99
BP275	Simple Short Wave Receiver Construction	£3.95	BP367	Electronic Projects for the Garden	£4.95	BP420	E-Mail on the Internet	£6.99
BP281	An Introduction to UHF/VHF for Radio Amateurs	£4.99	BP370	The Superhet Radio Handbook	£4.95	BP421	Windows 95 Assistant	£6.99
BP284	Programming in QuickBASIC (revised edition)	£5.99	BP373	An Introduction to Networks for PC and Mac Users	£5.95	BP422	Essentials of Computer Security	£5.99
BP292	Public Address Loudspeaker Systems	£4.99	BP375	The Novice Radio Amateurs Examination Handbook	£4.95	BP424	Microsoft Exchange for Business and Home Use	£6.99
BP293	An Introduction to Radio Wave Propagation	£3.95	BP380	Advanced Projects For The Electric Guitar	£4.99	BP425	Microsoft Internet Explorer Assistant	£5.99
BP301	Antennas for VHF and UHF	£4.95	BP383	Understanding the Mathematics of Electronics	£5.99	BP426	MS Office 97 Explained	£6.99
BP303	Preamplifier and Filter Circuits	£4.99	BP387	Windows One Step at a Time	£4.95	BP427	Netscape Internet Navigator Assistant	£6.99
BP311	An Introduction to Scanners and Scanning	£4.99	BP388	Why Not Personalise Your PC	£4.99	BP428	MS Word 97 Explained	£6.99
BP312	An Introduction to Microwaves	£3.95	BP389	Power Point for Windows Explained	£5.95	BP429	MS Excel 97 Explained	£6.99
BP315	An introduction to the Electromagnetic Wave	£4.95	BP390	An Introduction to the World Wide Web for PC and Mac Users	£6.99	BP430	MS Access 97 - One Step at a Time	£5.99
SP316	Practical Electronic Design Data	£5.99				BP432	Simple Series Terminal Block Projects	£4.99
BP317	Practical Electronic Timing	£4.95				BP434	PC Hardware Assistant	£6.99
BP320	Electronic Projects for Your PC	£3.99				BP435	Programming in C++	£6.99
BP324	The Art of Soldering	£3.99						
BP325	A Concise Users Guide to Windows 3.1	£4.95						

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749; Fax 01202 841692 (NOTE, we cannot reply to orders or queries by fax); E-mail: orders@epemag.wimborne.co.uk. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required - see the *Back Issues* page for details.

Please check price and availability in the latest issue.
Boards can only be supplied on a payment with order basis.

Special KNOCK DOWN SALE of PCBs.

We have a few p.c.b.s left from past projects these are being offered at the knock down price of £2.00 each - no matter what size they are (some of these boards are worth over £15.00 each) while stocks last. This price includes VAT and UK post - overseas orders please add 50p postage (or £1 per board for airmail postage).

£2.00 EACH inc. VAT and p&p

Print Timer, 874; Stereo HiFi Controller - Power Supply, 886 - Main Board, 887 - Expansion/Display Boards, (pair) 888; Power Controller, 905; Active Guitar Tone Control, 907; TV Off-er (pair), 908/909; Video Modules - 1 Simple Fader, 910; Video Enhancer, 912; 12V 35W PA Amplifier, 930; ★National Lottery Predictor, 935; MIDI Pedal, 938; Club Vote Totaliser, 939; Ramp Generator - Logic Board (double-sided p.t.h.), 944 - Analogue board, 945; Microcontrolled 3-Digit Timer, 933; Low-Range Ohmmeter Adaptor, 926; Vandata - Boot Control Unit, 953 - Display Unit, 954; Capacitor Check, 955.

Any of the above for just £2 each inc. VAT and p&p.

Back numbers or photostats of articles are available see the *Back Issues* page for details.

PROJECT TITLE	Order Code	Cost
Digital Delay Line	958	£8.04
50Hz Field Meter	959	£8.32
Temperature Warning Alarm (Teach-In '96)	960	£6.15

PROJECT TITLE	Order Code	Cost
Stereo "Cordless" Headphones	DEC 95	
Transmitter	961	£8.04
Receiver	962	£7.66
★EPE Met Office - Sensor/Rainfall/Vane	963/965	£11.33
Spiral transparency free with above p.c.b.		
★EPE Met Office -	JAN 96	
Computer Interface (double-sided)	964	£7.69
Audio Signal Generator	959	£6.58
Automatic Camera Panning (Teach-In '96)	972	£6.63
Printer Sharer	973	£9.93
Van-Speed Dice (Teach-In '96)	FEB 96	
Mains Signalling Unit - 2 12V Capacitive PSU	974	£5.69
	975	£6.07
Multi-Purpose Mini Amplifier	MAR 96	
High Current Stabilised Power Supply	976	£6.12
Mind Machine Mk III - Sound and Lights	979	£6.62
Infra-Zapper Transmitter/Receiver (Teach-In '96)	980	£7.39
Bat Band Converter/B.F.O.	APR 96	
Hearing Tester	984a/b	£5.80
Event Counter (Teach-In '96)	985	£6.87
	986	£8.39
B.F.O. and Bat Band Converter	MAY 96	
Versatile PIR Detector Alarm	984a/b	£5.80
Mind machine Mk III - Tape Controller	988	£6.76
Midi Analyser	989	£6.70
Countdown Timer (Teach-In '96)	992	£6.74
	993	£9.44
Sarah's Light	JUNE 96	
Home Telephone Link	996	£7.17
★PulStar	997 (pr)	£10.72
VU Display and Alarm	998	£6.60
	999	£7.02
Ultra-Fast Frequency Generator	JULY 96	
and Counter - Oscillator/L.C.D. Driver	994/995 (pr)	£12.72
Timed NiCad Charger	100	£6.99
Single-Station Radio 4 Tuner	101	£7.02
Twin-Beam Infra-Red Alarm - Transmitter/Receiver	102/103 (pr)	£10.50
★Games Compendium	104	£6.09
Mono "Cordless" Headphones	AUG 96	
- Transmitter/Receiver	990/991 (pr)	£10.16
Component Analyser (double-sided p.t.h.)	105	£12.18
Garden Mole-Ester	106	£6.07
Mobile Miser	107	£6.36
Bike Speedo	108	£6.61
★PIC-Tock Pendulum Clock	SEPT 96	
Power Check	109	£6.31
Analogous Delay/Flanger	110	£6.42
Draught Detector	111	£7.95
Simple Exposure Timer	112	£6.22
	113	£6.63

PROJECT TITLE	Order Code	Cost
Video Fade-to-White	114	£6.98
Direct Conversion 80m Receiver	116	£7.52
Vehicle Alert	117	£6.55
10MHz Function Generator - Main Board	118	£7.33
- PSU	119	£5.39
Tunable Scratch Filter	115	£7.83
*Central Heating Controller	120	£7.85
D.C. to D.C. Converters - Negative Supply Generator	122	£5.96
- Step-Down Regulator	123	£6.01
- Step-Up Regulator	124	£6.12
*PIC Digital/Analogue Tachometer	127	£7.23
Stereo Cassette Recorder	128	£7.94
Playback/PSU	129	£9.04
*Earth Resistivity Meter	131/132 (pr)	£12.70
Current Gen. - Amp/Rect	130 (set)	£40.00
Theremin MIDI/CV Interface (double-sided p.h.)	126	£6.77
Mains Failure Warning	135	£9.00
Pacific Waves	137	£6.78
Ps/Com Experimental Controller	125	£7.16
Oil Check Reminder	135	£6.75
Video Negative Viewer	138	£6.45
Tri-Colour N/Cad Checker	139	£7.20
Dual-Output TENS Unit (plus Free TENS info)	141	£6.90
*PIC Agoras - Wheelie Meter	142	£5.35
418MHz Remote Control - Transmitter	143	£6.04
- Receiver	145	£6.10
Puppy Puddle Probe	147	£5.42
MIDI Matrix - PSU	148	£5.91
- Interface	133	£6.59
Quasi-Bell Door Alert	144	£7.69
2M F.M. Receiver	149	£7.83
*PIC A-Tuner	150	£4.91
Window Closer - Trigger	151	£4.47
- Closer	153	£6.58
Child Minder Protection Zone	154	£6.42
- Transmitter	155	£6.93
- Receiver	156	£7.39
Pyrotechnic Controller	158	£6.37
*PIC Dialogue Clock	152	£6.69
Narrow Range Thermometer	932	£3.00
Micropower PIR Detector - 1	159	£6.40
Infra-Red Remote Control Repeater	160	£6.75
(Multi-project P.C.B.)	161	£6.70
Karaoke Echo Unit - Echo Board	162	£6.60
- Mixer Board	932	£3.00
Computer Dual User Interface	146	£6.55
*PEST Scarer	163	£6.72
Variable Bench Power Supply	164	£7.02
Universal Input Amplifier	140	£6.59
Micropower PIR Detector - 2 Controller	157	£6.63
*PIC-OLO	165	£7.82
Active Recarving Antenna	166	£5.72
Soldering Iron Controller	167	£5.12
*PIC Noughts & Crosses Game	168	£6.32
Micropower PIR Detector - 3	169	£6.23
Alarm Disarm/Reset Switch	170	£6.90
Ironing Safety Device	171	£6.34
Remote Control Finder	172	£6.63
Rechargeable Handlamp	173	£6.61
*PIC Water Descaler	175	£7.00
*EPE Time Machine	176	£14.49
Auto-Dim Bedlight	177	£7.34
Portable 12V PSU/Charger	178	£6.61
Car Immobiliser	179	£7.32
Safe and Sound (Security Bleeper)	174	£7.64
Surface Thermometer	178	£8.30
Disco Lights Flasher	932	£3.00
Waa-Waa Pedal (Multi-project PCB)	176	£14.49
*Virtual Scope - Digital Board	177	£7.34
Analogue Board (per board)	180	£7.69
*Water Wizard	181	£7.67
Kissometer	182	£7.99
*EPE PIC Tutorial	183	£6.58
The Handy Thing (Double-Sided)	184	£5.90
Lighting-Up Reminder	185	£7.05
*Audio System Remote Controller - PSU	186	£8.29
Main Board	932	£3.00
Simple Metal Detector	187	£7.90
(Multi-project PCB)	188	£7.66
Single or Dual-Tracking Power Supply	189	£8.10
*RC-Meter	190	£7.78
Security Auto-Light	191	£8.58
Stereo Tone Control plus 20W Stereo Amplifier	192	£8.05
Tone Control	193	£7.75
20W Amplifier	194	£8.50
*Dice Loit	195	£8.69
EPE Mood Changer	196	£6.96
*AT89C2051/1051 Programmer	197	£9.08
Main Board	198	£6.10
Test Board	199	£6.59
*Reaction Timer Software only	202	£3.00
*PIC16x84 Toolkit	932	£3.00
*Greenhouse Computer	200	£6.32
Control Board	201	£8.15
PSU Board	203	£7.18
Float Charger	204	£7.69
Lightbulb Saver	205	£3.00
Personal Stereo Amplifier	206	£3.50
(Multi-project PCB)	205	£3.00
*Greenhouse Radio Link	206	£3.50
*PIC Altimeter	205	£3.00
Voice Processor	206	£3.50
*Digitary P/C Expander	205	£3.00
IR Remote Control	206	£3.50
Transmitter	205	£3.00
Receiver	206	£3.50

PROJECT TITLE	Order Code	Cost
*PIC Tape Measure	207	£6.82
Electronic Thermostat	208	£4.00
T-Stat	211	£3.00
PhizzyB	212	£4.00
A-PCB B-CD-ROM C-Prog. Microcontroller	209	£4.50
15-Way IR Remote Control	213	£4.00
Switch Matrix	215	£5.16
15-Way Rec/Decoder	216	£3.95
Damp Stat	210	£7.55
Handheld Function Generator	214	£6.30
*Fading Christmas Lights	216	£3.95
PhizzyB I/O Board (4-section)	217	£6.72
Twinkle Twinkle Reaction Game	218	£6.78
*EPE Mind PICKer	219+a	£9.92
PhizzyB I/O Board (4-section)	220+a	£8.56
Alternative Courtesy Light Controller	218	£6.78
Light Alarm	219+a	£9.92
*Wireless Monitoring System - Transmitter	220+a	£8.56
Receiver	-	-
*PIC MIDI Sustain Pedal Software only	219a/220a	Feb'99
*Wireless Monitoring System-2	221	£7.37
F.M. Trans/Rec Adaptors	222	£6.36
*Time and Date Generator	223	£5.94
Auto Cupboard Light	224	£5.15
Smoke Absorber	225	£5.12
Ironing Board Saver	226A&B	£7.40 pr.
Voice Record/Playback Module	207	£6.82
Mechanical Radio (pair)	227	£8.95
*Versatile Event Counter	228	£3.00
*PIC Toolkit Mk 2	229	£3.20
A.M./F.M. Radio Remote Control	231	£9.51
Transmitter	232	£8.79
Receiver	233	£6.78
*Musical Sundial	234	£6.72
PC Audio Frequency Meter	235	£7.10
*EPE Mood PICKer	932	£3.00
12V Battery Tester	236	£5.00
Intruder Deterrent	237	£8.88
L.E.D. Stroboscope	238	£6.96
(Multi-project PCB)	239	£6.77
Ultrasonic Puncture Finder	240	£6.53
*8-Channel Analogue Data Logger	932	£3.00
Buffer Amplifier (Oscillators Pt 2)	241	£7.51
Magnetic Field Detector	242	£7.64
Sound Activated Switch	-	-
Freezer Alarm (Multi-project PCB)	-	-
Child Guard	-	-
Variable Dual Power Supply	-	-

EPE SOFTWARE

Software programs for EPE projects marked with an asterisk * are available on 3.5 inch PC-compatible disks or free from our Internet site. Four disks are available: PIC Tutorial (Mar-May '98 issues); PIC Toolkit Mk2 (Mar-Jun '99 issues); PIC Disk 1 (Apr '95-Dec '98 issues); EPE Disk 2 (Jan '99 issue to current cover date). The disks are obtainable from the EPE PCB Service at £2.75 each (UK) to cover our admin costs (the software itself is free). Overseas (each): £3.35 surface mail, £4.35 each airmail. All files can be downloaded free from our Internet FTP site: <http://ftp.epemag.wimborne.co.uk>.

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name.....

Address.....

I enclose payment of £..... (cheque/PO in £ sterling only) to:

Everyday
Practical Electronics
MasterCard or Visa No.
Minimum order for credit cards £5



Signature..... Card Exp. Date.....

Please supply name and address of cardholder if different from the address shown

NOTE: You can order p.c.b.s via our Internet site on a secure server:
<http://www.epemag.wimborne.co.uk>

PRACTICAL ELECTRONICS



Everyday Practical Electronics/ETI reaches twice as many UK readers as any other independent monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading independent monthly magazine in this market for the last fourteen years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics/ETI Advertisements, Mill Lodge, Mill Lane, Thorpe-le-Soken, Essex CO16 0ED. Phone/Fax (01255) 861161.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
Up to 20 volts d.c. at 1 amp continuous. 1.5 amps peak, fully variable from 1 to 20 volts. Twin Voltage and Current meters for easy read-out. 240 volt a.c. input. Fully smoothed, size 23cmx14cmx8cm.



£45 inc. VAT
Post £4

RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON SURREY, CR0 2HS. Tel: 0181-684 1665
Lots of Transistors, High watt coils, valves, output transformers, sockets, in stock. Phone or send your wants list for quote.

ASTRA Desk Top Accounting™
Are you worried that your customers will insist on using the Euro and so leave you off their list of suppliers?
See www.AstraAccounts.co.uk for a Pan-European solution to help you with this looming problem
S&S Systems Ltd, Bretton Court, S26 5PS, UK

BRAND NEW SINCLAIR SPECTRUM & QL PARTS
ZX MICRODRIVES £15, INTERFACE ONE £20, CARTRIDGES 10 FOR £15, 50 FOR £50.
QL BOARDS 5, 6 & 7, POPULATED WITH JS ROMS, £30, UNPOPULATED, £12; MICRODRIVES £10 EACH, TOP & BOTTOM CASES £15, MEMBRANES £15
THE P.C., MAC and QL's "Little Friend" MAC LINK £10 - P.C. LINK £25 - QL LINK £12
CAMBRIDGE Z88 A4 NOTEBOOK COMPUTER AVAILABLE AGAIN! £99, RECONDITIONED £60
ONLY 1" THICK, 4AAA BATT'S, 20 HOURS WORK, LCD SCREEN, 72 Ch, 6 LINES, 32K RAM, EXTRA RAMS & EPROMS, 9 pin D SERIAL PORT, ROM HAS BBC BASIC, W/PROCESSOR, SPREADSHEET, DATA BASE, IMP/EXPORT TO PC etc, V32 TERMINAL
W.N. RICHARDSON & CO.
PHONE/FAX 01494 5713195
RAVENSMOOR, CHALFONT ST PETER, BUCKS, SL9 0NB

BTEC ELECTRONICS TECHNICIAN TRAINING

GNVQ ADVANCED ENGINEERING (ELECTRONIC) - PART-TIME
HND ELECTRONICS - FULL-TIME
B.Eng FOUNDATION - FULL-TIME
Next course commences
Monday 13th September 1999
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 BENYVERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: 0171-373 8724

**THE BRITISH AMATEUR
ELECTRONICS CLUB**
exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.
For membership details, write to the Secretary:
Mr. M. P. Moses,
5 Park View, Cwmaman,
Aberdare CF44 6PP
Space donated by
Everyday Practical Electronics

Miscellaneous

G.C.S.E. ELECTRONIC KITS, at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 52 Severn Road, Clacton, CO15 3RB.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and Production. Artwork raised from magazines or draft designs at low cost. PCBs also designed from schematics. Production assembly also undertaken. For details send to P. Agar, Unit 5, East Belfast Enterprise Park, 308 Albertbridge Road, Belfast, BT5 4GX, or phone/fax 01232 738897.

VALVE ENTHUSIASTS: Capacitors and other parts in stock. For free advice/lists please ring Geoff Davies (Radio), Tel. 01788 574774.

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poyning Drive, Hove, Sussex BN3 8GR, or phone Brighton 883871, fax 01273 706670.

SINGLE BOARD COMPUTER: PIC16F84 89C2051, ACR90S1200 and 68HC11 with real time clock, 12C EEPROM, RS232, RS485, 128 KB-1MB EPROM Emulator. Fax 852 29522558 (Hong Kong), <http://www.wvtek.com>.

SECOND USER TEST EQUIPMENT FOR SALE: Scopes, generators, dmms, etc. HP, Tektronix, Datron, Hameg, Marconi, Fluke, etc. Low prices. Also some non-working equipment for parts, experiments, etc. Ring or E-mail for list. 07930 144803 or bford@mitectelcom.com.

FREE CATALOGUE: New company offers surplus stock to the public, components, tools and anything that comes along. Phone or write to: WCN Supplies, 61 Millbrook Road East, Southampton SO15 1HN. Tel. 01703 226522.

WANTED: Probes for Bell Model 640 Gaussmeter or would consider complete unit. Phone/Fax 0121 357 9909.

ENTERPRISING PERSON with knowledge and capability of making alarms wanted for a great idea I have. Fifty-fifty split is guaranteed for this genuine proposition, I'm definite we will get a result. Please contact: Dean Felix, 19 Eastland Walk, Bramley, Leeds LS13 2HA.

MICROCHIP PICMASTER EMULATOR complete with PIC16C71 module, psu and leads, etc., used once only, £225. Tel. Leeds 0113 252 4186.

PART-TIME ELECTRONICS OR ELECTRICAL ENTHUSIAST wanted for work on electronic project, must be a real whizz kid. Apply with all relevant details to Eng Group Services Ltd., Unit 10 Fazeley Street Ind. Estate, Birmingham B5 5RS.

REPLACEMENT LAMPS at the lowest prices, all types supplied, e.g. standard, pygmy, reflector, coloured, disco, stage, low energy, halogen, sodium, metal halide. We also supply decorative fibre optic lamps, bubble tubes, lava lamps etc.; quantity discounts. Phone/Fax 01260 271573.

DISCO AND PA EQUIPMENT at discount prices. Radio mics from £100, twin CD player £289, 2 x 160W amplifier £185, 2 x 400W amplifier £329, 3-disc karaoke player £209, mixing packages from £229, Par56 inc. lamp £26. Phone/Fax for price list: 01260 271573.

40 x SIEMENS V23102 24V SSR, £50 ono;
50 x Gen. Semiconductor MBR1060 power Schottky diodes, £40 ono; 3 x Hitachi monochrome display (120mm x 90mm display), £40 each ono; 1 x Raaco professional pcb repair kit, £100 ono; 1 x Cliff solder fume extractor, £50 ono; 1 x wrist strap test point, £40 ono. All items brand new and boxed/tubed. Tel. 01535 600726

EPE NET ADDRESSES

EPE FTP site: <ftp://ftp.epemag.wimborne.co.uk>

Access the FTP site by typing the above into your web browser, or by setting up an FTP session using appropriate FTP software, then go into quoted sub-directories:

PIC-project source code files: /pub/PICS

PIC projects each have their own folder; navigate to the correct folder and open it, then fetch all the files contained within. Do not try to download the folder itself!

EPE text files: /pub/docs

Basic Soldering Guide: solder.txt

EPE TENS Unit user advice: tens.doc and tens.txt

Ingenuity Unlimited submission guidance: ing_unlt.txt

New readers and subscribers info: epe_info.txt

Newsgroups or Usenet users advice: usenet.txt

Ni-Cad discussion: nicadfaq.zip and nicad2.zip

UK Sources FAQ: uksource.zip

Writing for EPE advice: write4us.txt

On-line readers! Try the new EPE Chat Zone - a virtually real-time Internet "discussion board" in a simple to use web-based forum!
<http://www.epemag.wimborne.co.uk/wwwboard>
Or buy EPE Online: www.epemag.com

Ensure you set your FTP software to ASCII transfer when fetching text files, or they may be unreadable.

Note that any file which ends in .zip needs unzipping before use. Unzip utilities can be downloaded from:
<http://www.winzip.com> or
<http://www.pkware.com>

TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice.

Electrical Contracting & Installation
Electrical Engineering
C&G Basic Electronic Engineering
C&G Basic Mechanical Engineering
TV and Video Servicing
Radio and Hi-Fi Servicing
Refrigeration Heating & Air Conditioning
Motorcycle Maintenance

FREEPHONE 0500 581 557

Or write to: International Correspondence Schools, FREEPOST 882, 8 Elliot Place, Croydon Skyrack, Glasgow, G3 8BR. Tel: 0500 581 557 or Tel/Fax: Ireland 01 265 2533

Please send me my Free Information on your Electronics Courses.

Name/Ms/Miss (BLOCK CAPITALS PLEASE) _____ Date of Birth _____

Address _____

Postcode _____

Occupation _____ Tel. No. _____

From time to time, we permit other carefully screened organisations to write to you about products and services. If you would prefer not to hear from such organisations please tick box Dept. ZEEE 050699

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220V/240V AC 50/60HZ OUTPUT 0V-260V

PANEL MOUNTING	Price	P&P
0.5KVA 2.5 amp max	£33.00	£6.00
	(£45.84 inc VAT)	£7.00
	(£61.39 inc VAT)	
SHROUDED		
0.5KVA 2.5 amp max	£34.00	£6.00
	(£47.00 inc VAT)	£7.00
	(£62.57 inc VAT)	
1KVA 5 amp max	£46.25	£7.00
	(£63.50 inc VAT)	
2KVA 10 amp max	£55.00	£8.50
	(£66.35 inc VAT)	
3KVA 15 amp max	£66.50	£8.50
	(£111.63 inc VAT)	
5KVA 25 amp max	£150.00	(£ Carriage & VAT)

Buy direct from the Importers. (lowest prices in the country)

500VA ISOLATION TRANSFORMER
Input lead 240V AC. Output via 3-pin 13A socket. 240V AC continuously rated, mounted in fibreglass case with handle internally. Used Price £35.00 carriage paid + VAT (£41.13)

TOROIDAL L.T. TRANSFORMER
Primary 0-240V AC. Secondary 0-30V + 0-30V 600VA. Primary coil supplied. Price £25.00 carriage paid + VAT (£29.38)

COMPREHENSIVE RANGE OF TRANSFORMERS - LT-ISOLATION & AUTO
110V-240V Auto transfer either cases with American socket and mains lead or open frame type. Available for immediate delivery.

ULTRA VIOLET BLACK LIGHT BLUE FLUORESCENT TUBES

4ft. 40 watt £14.00 (callers only)	(£16.45 inc VAT)
2ft. 20 watt £9.00 (callers only)	(£10.59 inc VAT)
1ft. 8 watt £4.90 + 75p p&p	(£5.32 inc VAT)
5ft. 6 watt £3.95 + 50p p&p	(£4.24 inc VAT)
6in. 4 watt £3.95 + 50p p&p	(£4.24 inc VAT)

230V AC BALLAST KIT
For either 6in. 4in or 12in tubes £8.95-£14.43 p&p
The above tubes are 3000 4000 approx. 3500-4000µsec for desecrating security markings, access systems & Criminal applications.
Other Waveforms of UV/TUBE suitable for Geospatial & Photo Sensible applications. Please telephone your enquiries.

400 WATT BLACK LIGHT BLUE UV LAMP
GES Mercury Vapour lamp suitable for use with a 400W P.F. Ballast.
Only £39.95 incl. p&p & VAT

5 KVA ISOLATION TRANSFORMER
As New. Ex Equipment. Fully shrouded. Line Noise Suppression. Ultra Isolation Transformer with terminal covers and knock-out cable entries. Primary 110V/240V. Secondary 120V/240V. 50/60Hz. 0.005µF Capacitance. Size: L37cm x W15cm x H15cm. Weight: 42 kilos. Price £120 + VAT. Ex-warehouse. Carriage on request.

24V DC SIEMENS CONTACT
Type 3TH6022-08 2.7A/20 and a TC 230V AC 10A. Contacts Silver or Silver Plating. Size H 120mm x W 45mm x D 75mm. Brand New Price £7.53 incl. p&p and VAT.

240V AC WESTCOOL SOLENOIDS
TT2 Mod 1 Rat. 1 Max. stroke 7mm. Base mounting. Main stroke 50s pull approx. TT8 Mod 1 Rat. 1 Max. stroke 11mm. Base mounting. 1/2in. stroke 150g pull approx. TT10 Mod 1 Rat. 1 Max. stroke 150g pull approx. Price incl. p&p & VAT TT5 £5.38. TT6 £6.81. SERIES 400 £7.54.

AXIAL COOLING FAN
230V AC 120mm square x 38mm D blade 10 watt Low Noise Fan. Price £7.29 incl. p&p and VAT.
Other voltages and sizes available. Heavy stock. Please telephone your enquiries.

INSTRUMENT CASE
Brand new. Manufactured by Inhol. L 31cm x H 16cm x D 19cm Deep. Removable front and rear panel for easy assembly of your components. Grey leather finish, complete with case feet. Price £16.45 incl. p&p and VAT. £2 off £20.00 inclusive.

DECAST ALUMINIUM BOX
with internal PCB guides. Internal size 65mm x 165mm x 50mm deep. Price £9.90 incl. p&p & VAT. £2 off £17.50 incl.

230V AC SYNCHRONOUS GEARED MOTORS
Brand new. Output Gearbox Couplet type motor. H 65mm x W 55mm x D 35mm. 40mm dia. Shaft x 10mm dia. RPM and gear. Output 40mm. £11.18 incl. p&p & VAT.

SOLID STATE EHT UNIT
Input 225V/240V AC. Output 200kV. 15kV. Producing 10mm spark. Built in 10 sec timer. Easily modified for 20 sec. 30 sec. to continuous. Designed for boiler ignition. Covers all uses in the field of physics and electronics. e.g. Super-physics neon or argon tubes etc. Price base case £3.50. £2.40 P&P (£12.31 inc VAT) P&S.

EPROM ERASURE KIT
Build your own EPROM Erasure Kit for a fraction of the cost of a made-up unit. Kit of parts less case includes 12in. Beest 2537. Argon Tube Ballast unit, pair of 6-pin leads, neon indicator, on/off switch, safety resistor and circuit £15.00/£2.00 p&p. £19.99 inc VAT.

WASHING MACHINE WATER PUMP
Brand new 240V AC fan cooled. Can be used for a variety of purposes. Inlet 1 1/2in., outlet 1in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

SUPPLIER OF QUALITY USED TEST INSTRUMENTS

CONTACT
Cooke International
Unit Four, Forthampton Six, Barnham, Dogger Road, West Sussex, PO23 0AQ, UK
Tel: (+44) 01243 543112. Fax: (+44) 01243 543257
Web: <http://www.cooke-int.com>
E-mail: info@cooke-int.com

OPERATING & SERVICE MANUALS

CONTACT
Cooke International
Unit Four, Forthampton Six, Barnham, Dogger Road, West Sussex, PO23 0AQ, UK
Tel: (+44) 01243 543112. Fax: (+44) 01243 543257
Web: <http://www.cooke-int.com>
E-mail: info@cooke-int.com

Professional 88-108MHz FM Broadcasting Kits

All Our Kits include:
Detailed Instructions with Schematics
High Quality Screen Printed PCBs
High Quality Components

Our Product Range includes:
Transmitters from 0.05W to 35W
FM Stereo Coders
Audio Compressor Limiters
Antennas
RF Power Amps

Our Kits Are Also Available Fully Assembled And Tested

Veronica KITS

Visit our Website at <http://www.veronica.co.uk>

Contact Us Now For A Free Brochure
Tel 01274 883434 Fax 01274 428665
email info@veronica.co.uk
Unit 5 & 1A Sandwicks Albert Rd Queensbury BRADFORD BD15 1AA

N. R. BARDWELL LTD (EPE)

100 Signal Diodes 1N4148	£1.00	200 Ass'd. disc ceramic capacitors	£1.00
75 Rectifier Diodes 1N4001	£1.00	50 Ass'd. SMD Presets (pm. stand. ceramic)	£1.00
50 Rectifier Diodes 1N4007	£1.00	50 Ass'd. RF chokes (inductors)	£1.00
10 W01 Bridge Rectifiers	£1.00	50 Ass'd. grommets	£1.00
555 Timer I.C.s	£1.00	Ass'd. solder leads, proximal terminals	£1.00
741 Op Amps	£1.00	Ass'd. crystals - plug in	£1.00
Assorted Zener Diodes 400mW	£1.00	24 Ass'd. coil formers	£1.00
Assorted 7-segment Displays	£1.00	8 Ass'd. diodes	£1.00
5mm LEDs, red, green or yellow	£1.00	20 Miniature slide switches (open)	£1.00
3mm LEDs, red, green or yellow	£1.00	10 Standard slide switches (open)	£1.00
4-pin LEDs, 2000 red Diode Package	£1.00	Ass'd. 0.1 transformers	£1.00
Ass'd. High Brightness LEDs, var. sizes	£1.00	Ass'd. toggle (keramic, nylon, fish spine)	£1.00
BC122 Transistors	£1.00	80 Ass'd. small stand offs, through hole	£1.00
BC212 Transistors	£1.00	Ass'd. oil sockets up to 40 way	£1.00
BC237 Transistors	£1.00	10 TV coil plugs, plastic	£1.00
BC328 Transistors	£1.00	20 Small spring loaded terminals	£1.00
BC547 Transistors	£1.00	40 Ass'd. various thin connecting wires, red	£1.00
BC548 Transistors	£1.00	10 In. glass reed switches	£1.00
BC549 Transistors	£1.00	20 Magnetic ear pins with lead and plug	£1.00
BC557 Transistors	£1.00	100 Any one value 1/4W 5% of resistor range	£1.00
BC558 Transistors	£1.00	1R to 10M	£0.45
BC559 Transistors	£1.00	7812 Voltage Regulators	£1.00
2N3054 Transistors	£1.00		
100 1W 50V Wkg Axial Capacitors	£1.00		
100 4W 50V Wkg Axial Capacitors	£1.00		
12 1uF 250V encapsulated radial plastic	£1.00		
Ass'd. capacitors electrolytic	£1.00		
Ass'd. capacitors electrolytic	£1.00		
Ass'd. capacitors 1W to 1/4W	£1.00		

288-290, Albert Road, Sheffield S7 1PL
Phone 0114 252666 Fax 0114 250068
E-mail enquiries@bardwell.co.uk
Web site: <http://www.bardwell.co.uk>

NEW SPECIAL OFFERS

Arriva pentaback pcb (uncoated) for using videos it has a 23pin D lead to plug into the computer and pcb pins for composite video in and out. When no video input is connected the normal computer display is shown on the composite video out when the video input is added the whole screen on the screen is replaced by the video image. The pcb is powered from the computer. £19.99

WATCH SLIDES ON TV "Lesegang" electronic automatic slide viewer with built in high quality colour tv camera, composite video output with a BNC plug. In very good condition with few signs of use. £108.00

Board camera with 512x582 pixels 4.4x3.3mm sensor with composite video out. All need to be housed in your own enclosure and have fragile exposed surface mount parts and require 10V to 12V dc power supply.

47MM size 60x32x7mm with 6 infra red leds (gives the same illumination as a small torch with 650.00 watt-£58.75

UP size 39x38x23mm spy camera with a fixed focus pin hole lens for hiding behind a very small hole. £37.00 watt-£36.98

40MC size 39x38x23mm camera for 1/2 mount lens. This gives a much clearer picture than with the small lens. £68.75

Standard 1/2 mount lens F1.6 16mm for 40MC £26.43 watt-£21.06

Waterproof camera with stylish 02 & silver case £82.78 watt-£129.00 for 10x280 1/2 watt-£104.95

DIA30 Handheld transistor analyzer IC test, you which lead is the base, the collector and emitter and is a NPN or PNP or faulty. HMA20 handheld MOS-TEF analyzer identifies gate drain and source and P or N condition. DIA30 & HMA20 £38.34 each

DCAS3 computer analyzer with led readout identifies transistors, mostly, diodes & LEDs lead connections. £69.95

Speaker cabinet 2-way speaker systems with Motorola tweeters speaker dia 15" 12" 8"

power rating 250W RMS 170W RMS 100W RMS

microphone 40m 20m

red range 40m-25m 40m-20m 40m-20m

sensitivity (VPM) 30m 94dB 20dB

size in mm 500x700x340 450x540x315 514x620x230

weight 21.0kg 16.2kg 7.4kg

price each for back

w/pcoding £125.95 £99.95 254.04

grey led coding £159.97 £119.97 £64.99

(*not normally in stock above 1 week for delivery)

Power amplifiers 1W each mount with gain controls

STAN50 2x160Watts 140mm load 14kg £200.00

STAN300 2x190Watts (Alpha level) 11kg £230.00

STAN500 2x450Watts (Alpha load) 15kg £550.00

LEDs 5mm or 5mm red or green. 75 each value 11p each

Cable ties up to £3.95 per 1000 £48.50 per 10,000

Rechargeable Batteries

AA(P7) 500mAh £10.95 AA 500mAh with solder tags £15.50

AA 800mAh £11.75 AA 800mAh with solder tags £16.25

C 24H with solder tag £16.00 D 24H 1.2AH £22.00

D 44H with solder tag £19.95 P7 2.4V 100mAh £4.95

12Ah with solder tag £15.50 Sub C with solder tag £2.50

AAA (N18) 100mAh £1.75 US AA with tags (Phillips) C7E1.95

Notes: *Metal Hydroxide AA cells high capacity with no memory if charged at 100mA and discharged at 250mA or less 1300mAh capacity (lower capacity for high discharge rates) £2.95

Special offers, please check for availability stock of 4 40x16mm Nicad batteries 17 terminals dia with red & black leads 4.8V £5.95

5 button cell 5V 280mAh battery with wires (Varta) S2520mg £2.45

Optical 866 battery pack 12V 1.60AH contains 10 Sub C cells with solder tags (the size most commonly used in cordless screwdrivers and drills 22 elements) only a £1.50 to crack open and was manufactured in 1994

£3.77 each or £10.50 per box of 14

50 pin 190x106x20mm with slots to house a pcb the id connector an edge connector (12 way item) (part and serial terminals to connect in wires and 5 slots in cable blank) £2.55

7-segment common anode led display 12mm £0.45

GAAS PBT low leakage current 58873 1295 each

£3.95 10x £7.95 100x BC547A transistor 20 for £1.00

1555 UHF timing amplifier LC 15 surface mounting package with test sheet £1.50

DC-DC converter Reliability model V12P6 12V 1W 200mA output 300V input to output isolation with 0.025 £4.95 each or pack of 10 £38.50

Alphas A82903-C range stepping motor 14V 7.5 amp 27mm 68mm dia body 6.3mm shaft £3.95 or £20.00 for a box of 30

Polyester capacitors box type 2200µF lead pitch 0.5in 250V dc 18c each, 14c 100µ, 30 1000µ, 14c 250Vdc 20p each, 15c 100µ, 10p 1000µ

Polypropylene 1uF 400V dc (Wing M9P10) 27.5mm pitch 32x28x17mm case 75p each 600 100µ

Phillips 125 series solid aluminium axial leads 20x1F 10V & 2.2-40V 40c each, 25c 100µ

Solid carbon resistors very low inductance date for IC circuits 27ohm 2W, 20ohm 2W 25c each 15c each 100µ, we have a range of 0.25W 0.5W 1W and 2W solid carbon resistors, please see 54 for list

LM189 Digital motoriser 17 ranges 1000V dc 750V ac 2000mAh 200mA transistor 18c 9V and 1.5V battery lead £3.95

Head held ultrasonic remote control £3.95

CY746 gate relay 30x10mm dia with 3 wire terminals will also work as a relay 18c

20p each or £3.50 per 100

Veronica R0000H Synchronizer top normally used on no machines and printing presses etc. It looks like a normal cabinet with a slot out of the top £4.95 each (£3.75 100x)

Highest compound tube

HV3240-45 5.2kV 50mA regulated at 18.5kV 100µA output 8 pin DIL package £5.49 each 100x £2.25

All products advertised are new and unused unless otherwise stated. We range of CMOS TTL 74HC 74F Linear Transistors, ICs, rechargeable batteries, capacitors, tools etc always in stock.

Please add £1.95 towards P&P (orders from the South Highlands, Northern Ireland, Isle of Man, Isle of Wight and overseas may be subject to higher P&P for heavy items). VAT included in all prices.

JPG ELECTRONICS
276-278 Chatsworth Road
Chesterton S40 2BH
Access/Visa orders
Tel: (01246) 211202 Fax: (01246) 558959
Callers welcome 9.30 am to 5.30 pm
Monday to Saturday



POWER AMPLIFIER MODULES-LOUDSPEAKERS-MIXERS *PRICES INCLUDE V.A.T.*PROMPT DELIVERIES
19 INCH STEREO AMPLIFIERS-ACTIVE CROSS/OVERS. *LARGE [A4] S.A.E. 60p STAMPED FOR CATALOGUE

OMP MOS-FET POWER AMPLIFIERS
HIGH POWER, TWO CHANNEL 19 INCH RACK



1000's
 SOLD
 TO PRO
 USERS

THE RENOWNED MXF SERIES OF POWER AMPLIFIERS

FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
 MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS ARE R.M.S. INTO 4 OHMS, WITH BOTH CHANNELS DRIVEN
 FEATURES: • Independent power supplies with two toroidal transformers • Twin LED Vu Meters
 • Level controls • Illuminated on/off switch • Jack/XLR inputs • Speaker outputs • Standard 775mV
 inputs • Open and short circuit proof • Latest Mos-Fets for stress free power delivery into virtually any
 load • High slew rate • Very low distortion • Aluminium cases • MXF600 & MXF900 fan cooled with D.C
 loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC

SIZES:-

MXF200 W19"	D11"	H31"	(2U)
MXF400 W19"	D12"	H51"	(3U)
MXF600 W19"	D13"	H51"	(3U)
MXF900 W19"	D14 1/2"	H51"	(3U)

PRICES:- MXF200 £175.00 MXF400 £233.85
 MXF600 £328.00 MXF900 £449.15

SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03'S STEREO 3-WAY ACTIVE CROSS-OVER SWITCHABLE 2-WAY



FEATURES:
 Advanced 3-Way Stereo Active Cross-Over (switchable two way), housed in a 19" x 1U case. Each channel
 has three level controls: Bass, Mid & Top. The removable front fascia allows access to the programmable DR
 switches to adjust the cross-over frequency. Bass-Mid 125/250/500Hz, Mid-Top 15/3/5Hz, all at 24dB per
 octave. The 2/3 way selector switches are also accessed by removing the front fascia. Each stereo channel
 can be configured separately. Bass Invert Switches are incorporated on each channel. Nominal 775mV
 input/output. Fully compatible with OMP Rack Amplifier and Modules.
PRICE:- £117.44 + £5.00 P&P

SoundLAB SPM 12 AND 16 CH.MIXERS

The 12 and 16 Channel SPM Series Of Studio Quality Mixers
 Are Ideal For Fixed Installation Stage And Mobile Use.

- * 48V PHANTOM POWER
- * BUILT IN POWER SUPPLY
- * 230V AC/50Hz
- * PEAK INPUT LEVEL LEDS
- * PRE FADE LISTEN (PFL)
- * SUB MASTER OUTPUT
- * COMBINED XLR/1/4" JACK
- * 60mm FADERS * CH.MUTE
- * 2 STEREO AUX.SEND/RETURNS
- * CONSTANT PAN CONTROL
- * 3 BAND EQ WITH MID SWEEP
- * HEADPHONE/CONTROL ROOM O/P
- * CD/TAPE INPUTS & OUTPUTS
- * BALANCED INPUTS & OUTPUTS
- * BUS ASSIGN SWITCH
- * MONITOR SEND



PRICES:- SPM1202 4MONO MIC/LINE,4STEREO INPUTS £299.00 FREE
 SPM1602 8MONO MIC/LINE,4STEREO INPUTS £395.00 UK P&P

STEREO DISCO MIXER MPX5700



STEREO DISCO MIXER WITH:- *2X7 GRAPHIC EQUALISERS *2 MONO MIC INPUTS *DJ MIC
 WITH FADER, TALKOVER AND VOICE CHANGER *4 STEREO CHANNELS WITH INDIVIDUAL
 FADERS AND ASSIGNABLE CROSSFADE *CHANNELS SWITCHABLE, TURNABLE (MAG
 CARTRIDGE), CD, LINE, TAPE, ETC. *ECHO WITH BALANCE, REPEAT AND DELAY
 *HEADPHONE MONITOR WITH PREFADE LISTEN *CHOICE OF 6 SOUND EFFECTS *STEREO
 MONO SWITCH *2 X LED VU METERS *MASTER FADER *OUTPUT 775mV
 *SIZE:- 482X240X115mm *POWER:- 230V AC 50/60HZ **PRICE:- £169.00 + £5.00 P&P**

ECHO & SOUND EFFECTS

- * 4 STEREO INPUT CHANNELS
- * 2 DJ MIC INPUT CHANNELS
- * 2X7 BAND GRAPHIC EQUALISERS
- * HEADPHONE MONITOR WITH PFL
- * ASSIGNABLE CROSSFADE
- * DIGITAL ECHO

RADIO MICROPHONE CYBERWAVE FMM 1000

* IDEAL FOR:- LIVE BANDS, PUBLIC ADDRESS & KARAOKE ETC.
 * ON/STANDBY/OFF SWITCH MOUNTED ON MIC BARREL FOR EASE OF USE
 * 100 HOURS BATTERY RUNNING TIME, 1PP3 (NOT SUPPLIED)
 * SINGLE CHANNEL RF MICROPHONE 174.23 OR 174.56MHz
 * MAINS ADAPTOR FOR RECEIVER SUPPLIED * FM LOCK INDICATOR
 & VOL CONTROL ON RECEIVER. **PRICE:- £119.99 FREE UK P&P**



FLIGHTCASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take
 advantage of the latest loudspeaker technology and
 enclosure designs. All models utilize high quality studio
 cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant
 directivity horns, extruded aluminium corner protection and steel ball corners,
 complimented with heavy duty black covering. The enclosures are fitted as standard
 with top hats for optional loudspeaker stands. The FC15-300 incorporates a large
 16 X 6 inch horn. All cabinets are fitted with the latest SpeakerConnectors
 for your convenience and safety. Five models to choose from.

WODGE
 MONITOR



PLEASE NOTE:- POWER RATINGS
 QUOTED ARE IN WATTS R.M.S. FOR
 EACH INDIVIDUAL CABINET.
 ALL ENCLOSURES ARE 3 OHM.

- ib1 FC15 300 WATTS Freq Range 35Hz-20KHz, Sens 101dB, Size H695 W502 D415mm
PRICE:- £299.00 per pair
- ib1 FC12-300 WATTS Freq Range 45Hz-20KHz, Sens 96dB, Size H600 W405 D300mm
PRICE:- £249.00 per pair
- ib1 FC12-200 WATTS Freq Range 40Hz-20KHz, Sens 97dB, Size H600 W405 D300mm
PRICE:- £199.00 per pair
- ib1 FC12-100 WATTS Freq Range 45Hz-20KHz, Sens 100dB, Size H546 W380 D300mm
PRICE:- £179.00 per pair
- ib1 WM12 200 WATTS Freq Range 40Hz-20KHz, Sens 97dB, Size H418 W600 D385mm
PRICE:- £125.00 EACH

SPECIALIST CARRIER DEL:- £12.50 per pair, Wodge Monitor £7.00 each
 Optional Metal Stands **PRICE:- £49.00 per pair Delivery:- £6.00**

FANE COLOSSUS POWER

VERY HIGH POWER LOUDSPEAKERS.

THE COLOSSUS RANGE OF LOUDSPEAKERS
 ARE DESIGNED FOR USE IN SUPERIOR HIGH
 POWER OUTPUT SYSTEMS. ALL MODELS ARE 2 OHM
 COLOSSUS 12MB:- * 12 INCH * 450WATT R.M.S.
 * 900 WATTS PEAK * Sens 98 dB * Res Freq.55 Hz.
 * Frequency Range 40 Hz-3.5KHz **PRICE £129.00**
 COLOSSUS 15XB:- * 15 INCH * 600WATTS R.M.S.
 * 1200 WATTS PEAK * Sens 99 dB * Res Freq.35 Hz.
 * Frequency Range 30 Hz-1.0KHz **PRICE £159.00**
 COLOSSUS 18XB:- * 18 INCH * 600WATTS R.M.S.
 * 1200 WATTS PEAK * Sens 100dB * Res Freq.30 Hz.
 * Frequency Range 27 Hz-1.0Kz **PRICE £183.00**
 ALL MODELS ARE DELIVERED CARRIAGE FREE(UK ONLY)



OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED

These modules now enjoy a world wide reputation for quality, reliability and performance at a realistic price. Four
 models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and
 Hi Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre
 P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 100 watts
 R.M.S into 4 ohms, frequency response 1Hz - 100KHz -
 -30dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D
 typical 0.002%, Input Sensitivity 500mV, S.N.R. -
 -110dB Size 300 x 123 x 60mm
PRICE:- £42.85 + £4.00 P&P



OMP/MF 200 Mos-Fet Output power 200 watts
 R.M.S into 4 ohms, frequency response 1Hz - 100KHz
 -30dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D
 typical 0.001%, Input Sensitivity 500mV, S.N.R. -110dB,
 Size 300 x 155 x 100mm.
PRICE:- £66.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts
 R.M.S into 4 ohms, frequency response 1Hz - 100KHz
 -30dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D
 typical 0.001%, Input Sensitivity 500mV, S.N.R. -110dB,
 Size 330 x 175 x 100mm
PRICE:- £83.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts
 R.M.S into 4 ohms, frequency response 1Hz - 100KHz
 -30dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D
 typical 0.001%, Input Sensitivity 500mV, S.N.R. -110dB, Fan
 Cooled, D.C. Loudspeaker Protection, 2
 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE:- £135.85 + £6.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts
 R.M.S into 2 ohms, 725 watts R.M.S into 4 ohms,
 frequency response 1Hz - 100KHz -30dB, Damping
 Factor >300 Slew Rate 75V/uS, T.H.D. typical
 0.002%, Input Sensitivity 500mV, S.N.R. -110dB, Fan
 Cooled, D.C. Loudspeaker Protection, 2 Second
 Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE:- £261.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS
 STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHZ OR
 PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) INPUT SENS
 775mV, BAND WIDTH 50KHZ. ORDER STANDARD OR PEC

B.K. ELECTRONICS

UNIT 1 COMET WAY, SOUTHEND-ON-SEA,
 ESSEX, SS2 6TR.

TEL.: 01702 527572 FAX.: 01702-420243


Web:- <http://www.bkelec.com> E-mail:- Sales@bkelec.com

DELIVERY CHARGES:- PLEASE INCLUDE AS ABOVE TO A MAXIMUM
 AMOUNT £30.00. OFFICIAL ORDERS FROM SCHOOL, COLLEGES,
 GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES
 COUNTER, CREDIT CARD ORDERS ACCEPTED BY POST PHONE OR FAX



Electronics, Electrical & Mathematics Principles V6

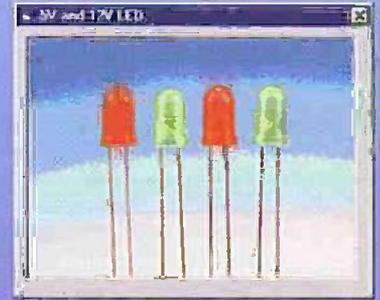If you are looking for an easy and enjoyable way of studying or improving your knowledge of electronics and maths then this is the software for you.



£99.95*

Multi-user site licence
additional £500*

CD-ROM for Windows '95, '98 & NT

Topics range from Ohm's law and simple DC through AC theory to the latest PIC16F84 and PIC16C71 microcontrollers where the architecture and complete instruction set can be explored through the interactive graphics. Mathematics are developed from simple number systems to solving linear equations.

Additions to V6 include: Circuit theorems, Norton, Thevenin's & Superposition, Magnetism & Electromagnetism, Motors, Generators & Transformers, Three phase systems, More on complex numbers, A beginners introduction to PIC's, Statistics, Single page colour printing, Faster graphics... PLUS: all the Electronics Toolbox routines, along with an Illustrated Components, Tools & Equipment Dictionary. A total of over 900 main menu selections.

Please telephone or visit our web site for more information.

COMPLETE PC BASED ELECTRONICS, ELECTRICAL AND MATHEMATICS COURSE where the colourful interactive graphics make it ideally suited for both personal study and a more enjoyable way of revising.

Currently used in hundreds of UK and overseas schools and colleges to support GCSE, A Level, City and Guilds, BTEC, GNVQ's and University courses.

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex, UK, CM8 2BJ.

Tel/Fax: 01376 514008; sales@eptsoft.demon.co.uk www.eptsoft.demon.co.uk

*UK and EC countries add £2 per order for post & packing. VAT should be added to the total.

Outside Europe £3.50 for air mail postage by return.

Switch: Delta, Visa and Mastercard orders accepted - please give card number and expiry date. Cheques & Postal Orders should be made payable to EPT Educational Software.