

**EVERYDAY**

MAY 1990

# ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

£1.40

**AMSTRAD SPEECH  
SYNTHESISER**

---


**QUIZMASTER**

---

**ELECTRONIC  
BAROMETER**

---

**FREE INSIDE!**

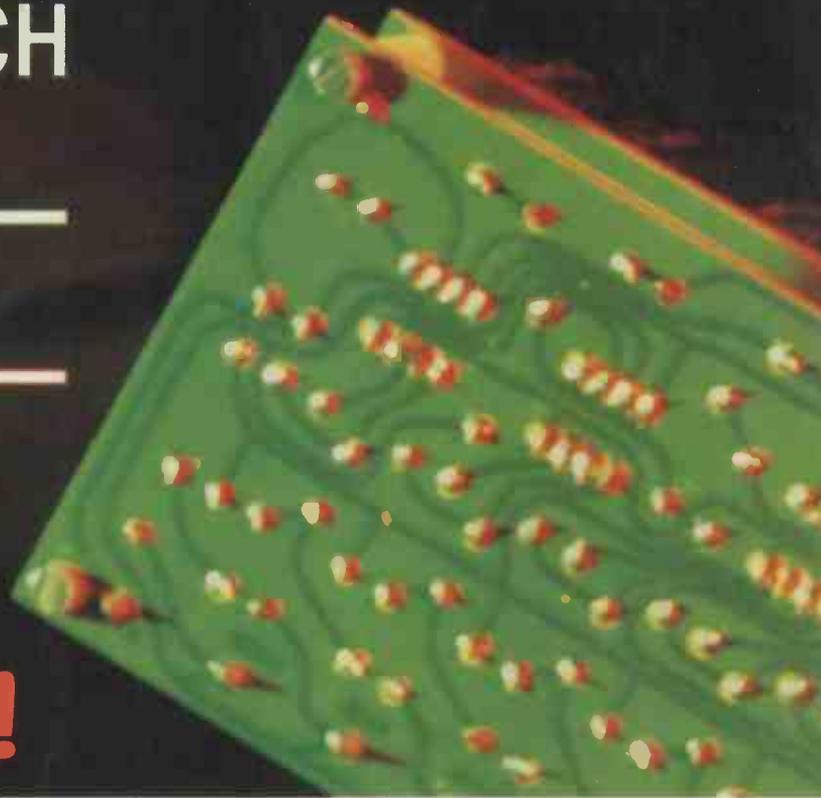

**SPECIAL  
AMATEUR RADIO  
SUPPLEMENT**

**SHORT WAVE  
RECEIVER**

---

**DIY AERIALS**



ISSN 0262-3617



9 770262 361003

The Magazine for Electronic & Computer Projects



### ONE POUND PACKS



All packs are £1 each. Note the figure on the extreme left of the pack ref number and the next figure is the quantity of items in the pack, finally a short description.

- BD2 5 13A spurs provide a fused outlet to a ring main where devices such as a clock must not be switched off.
- BD9 2 6V 1A mains transformers upright mounting with fixing clamps.
- BD11 1 6 1/2in speaker cabinet ideal for extensions, takes our speaker. Ref BD137.
- BD13 12 30 watt reed switches, it's surprising what you can make with these—burglar alarms, secret switches, relay, etc., etc.
- BD22 2 25 watt loudspeaker two unit crossovers.
- BD30 2 Nicad constant current chargers adapt to charge almost any nicad battery.
- BD32 2 Humidity switches, as the air becomes damper the membrane stretches and operates a microswitch.
- BD42 5 13A rocker switch three tags so on/off, or change over with centre off.
- BD45 1 24hr time switch, ex-Electricity Board, automatically adjust for lengthening and shortening day. original cost £40 each.
- BD49 5 Neon valves, with series resistor, these make good night lights.
- BD56 1 Mini uniselector, one use is for an electric jigsaw puzzle, we give circuit diagram for this. One pulse into motor, moves switch through one pole.
- BD67 1 Suck or blow operated pressure switch, or it can be operated by any low pressure variation such as water level in water tanks.
- BD103A 1 6V 750mA power supply, nicely cased with mains input and 6V output leads.
- BD120 2 Stripper boards, each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of condensers, etc.
- BD128 10 Very fine drills for pcb boards etc. Normal cost about 80p each.
- BD132 2 Plastic boxes approx 3in cube with square hole through top so ideal for interrupted beam switch.
- BD134 10 Motors for model aeroplanes, spin to start so needs no switch.
- BD139 6 Microphone inserts—magnetic 400 ohm also act as speakers.
- BD148 4 Reed relay kits, you get 16 reed switches and 4 coil sets with notes on making c/o relays and other gadgets.
- BD149 6 Safety cover for 13A sockets—prevent those inquisitive little fingers getting nasty shocks.
- BD180 6 Neon indicators in panel mounting holders with lens.
- BD193 6 5 amp 3 pin flush mounting sockets make a low cost disco panel.
- BD199 1 Mains solenoid, very powerful, has 1in pull or could push if modified.
- BD201 8 Keyboard switches—made for computers but have many other applications.
- BD211 1 Electric clock, mains operated, put this in a box and you need never be late.
- BD221 5 12V alarms, make a noise about as loud as a car horn. Slightly soiled but OK.
- BD242 2 6in x 4in speakers, 4 ohm made from Radiomobile so very good quality.
- BD252 1 Panostat, controls output of boiling ring from simmer up boil.
- BD259 50 Leads with push-on 1/4in tags—a must for hook-ups—mains connections etc.
- BD263 2 Oblong push switches for bell or chimes, these can mains up to 5 amps so could be foot switch if fitted into pattress.
- BD268 1 Mini 1 watt amp for record player. Will also change speed of record player motor.
- BD283 3 Mild steel boxes approx 3in x 3in x 1in deep—standard electrical.
- BD305 1 Tubular dynamic mic with optional table rest.
- BD400 4 Books, useful for beginners, describes amplifiers equipment and kits sets.
- BD653 2 Miniature driver transformers. Ref. LT44. 20k to 1k centre tapped.
- BD548 2 3.5V relays each with 2 pairs changeover contacts.
- BD667 2 4.7 µf non-polarised block capacitors, pcb mounting.

There are over 1,000 items in our Catalogue. If you want a complete copy please request this when ordering.

TOASTERS 2 slice toasters — may need slight attention. Only £3.00 each. Ref 3P84.

PERSONAL STEREOs Again customer returns but complete and with stereo head phones. A bargain at only £3.00 each. Our ref 3P83.

MICROWAVE CONTROL PANEL Mains operated, with touch switches. This unit has a 4 digit display with a built in clock and 2 relay outputs — one for power and one for pulsed power level. Could be used for all sorts of timer control applications. Only £6.00. Our ref 6P18.

EQUIPMENT WALL MOUNT Multi adjustable metal bracket ideal for speakers, lights, etc. 2 for £5.00. Our ref 5P152.

NEW MAINS MOTORS 25 watt 3000 rpm made by Framco. Approx 6" x 3" x 4". Priced at only £4.00 each. Our ref 4P54.

SHADED POLE MOTORS Approx 3" square. Available in 24V and 240V AC. Both with threaded output shaft and 2 fixing bolts. Price is £2.00 each. 24V Ref 2P65, 240V Ref 2P66.

SUB-MIN TOGGLE SWITCH Body size 8mm x 4mm x 7mm SBDT with chrome dolly fixing nuts. 3 for £1. Our ref BD649.

COPPER CLAD PANEL for making PCB. Size approx 12in long x 8 1/2in wide. Double-sided on fibreglass middle which is quite thick (about 1/16in) so this would support quite heavy components and could even form a chassis to hold a mains transformer, etc. Price £1 each. Our ref BD683.

### POWERFUL IONISER

Generates approx. 10 times more IONS than the ETI and similar circuits. Will refresh your home, office, workroom etc. Makes you feel better and work harder — a complete mains operated kit, case included. £12.50. Our ref 12P51.

**REAL POWER AMPLIFIER** for your car, it has 150 watts output. Frequency response 20Hz to 20KHz and signal to noise ratio better than 60dB. Has built in short circuit protection and adjustable input level to suit your existing car stereo, so needs no pre-amp. Works into speakers ref. 30P7 described above. A real bargain at only £57.00. Order ref: 5P71.

**REAL POWER CAR SPEAKERS.** Stereo pair output 100W each. 4-Ohm impedance and consisting of 6 1/2" woofer, 2" mid range and 1" tweeter. Each set in a compact purpose built shelf mounting unit. Ideal to work with the amplifier described above. Price per pair £30.00. Order ref: 30P7.

**STEREO CAR SPEAKERS.** Not quite so powerful — 70w per channel. 3" woofer, 2" mid range and 1" tweeter. Again, in a super purpose built shelf mounting unit. Price per pair £30.00. Order ref: 28P1.

**VIDEO TAPES** These are three hour tapes of superior quality, made under licence from the famous JVC Company. Offered at only £3 each. Our ref 3P63. Or 5 for £11. Our ref 11P3. Or for the really big use 10 for £20. Our ref 20P20.



### ELECTRONIC SPACESHIP.

Sound and impact controlled, responds to claps and shouts and reverses when it hits anything. Kit with really detailed instructions. Ideal present for budding young electrician. A youngster should be able to assemble but you may have to help with the soldering of the components on the pcb. Complete kit £10. Our ref. 10P81

**COMPUTER KEYBOARDS** Brand new, uncased. £3.00 each. ref 3P69.

**12" HIGH RESOLUTION MONITOR** Amber screen, beautifully cased for free standing, needs only a 12v 1.5 amp supply. Technical data is on its way but we understand these are TTL input. Brand new in makers' cartons. Price: £22.00. Order ref: 22P2.

### SINCLAIR C5 WHEELS

Including inner tubes and tyres. 13" and 16" diameter spoked poly carbonate wheels. Finished in black. Only £6.00 each. 13" Ref 6P10, 16" Ref 6P11

**COMPOSITE VIDEO KITS** These convert composite video into separate H sync, V sync and video. Price £8.00. Our ref 8P39.

**BUSH RADIO MIDI SPEAKERS** Stereo pair. BASS reflex system, using a full range 4in driver of 40hms impedance. Mounted in very nicely made black fronted walnut finished cabinets. Cabinet size approx 8 1/2in wide, 14in high and 3 1/2in deep. Fitted with a good length of speaker flex terminating with a normal audio plug. Price £5 the pair. Our ref 5P141.

**3 1/2in FLOPPY DRIVES** We still have two models in stock: Single sided, 80 track, by Chicon. This is in the manufacturers metal case with leads and IDC connectors. Price £40, reference 40P1. Also a double sided, 80 track, by NEC. This is uncased. Price £59.50, reference 60P2. Both are brand new.

**10 MEMORY PUSHBUTTON TELEPHONES** These are customer returns and "sold as seen". They are complete and may need slight attention. Price £6.00. Ref. 6P16 or 2 for £10.00. Ref. 10P77. BT approved.

**REMOTE CONTROL FOR YOUR COMPUTER** With this outfit you can be as much as 20 feet away as you will have a joystick that can transmit and a receiver to plug into and operate your computer and TV. This is also just right if you want to use it with a big screen TV. The joystick has two fire buttons and is of a really superior quality, with four suction cups for additional control and one handed play. Price £15 for the radio controlled pair. Our ref 15P27.

**ASTEC PSU.** Mains operated switch mode, so very compact. Outputs +12v 2.5A, +5v 6A, ±5v 5A, ±12v 5A. Size: 7 1/2in long x 4 1/2in wide x 2 1/2in high. Cased ready for use. Brand new. Normal price £30+, our price only £13.00. Order ref 13P2.

**VERY POWERFUL 12 VOLT MOTORS.** 1/2HP Horsepower. Made to drive the Sinclair C5 electric car but adaptable to power a go-kart, a mower, a rail car, model railway, etc. Brand new. Price £20. Our ref 20P22.

### PHILIPS LASER

This is helium-neon and has a power rating of 2mW. Completely safe as long as you do not look directly into the beam when eye damage could result. Brand new, full spec. £35. Our ref. 35P1. Mains operated power supply for this tube gives 8kv striking and 1.25kv at 5mA running. Complete kit with case £15. As above for 12V battery. Also £15. Our ref 15P22.

**PANEL METERS** 270 deg movement. New. £3.00 each. Our ref 3P89.

**SURFACE MOUNT KIT** Makes a super high gain snooping amplifier on a PCB less than an inch square! £7.00. Our ref 7P15.

**CB CONVERTERS** Converts a car radio into an AM CB receiver. £4.00. Our ref 4P48.

**GEIGER COUNTER KIT** Includes PCB, tube, loudspeaker, and all components to build a 9v battery operated geiger counter. Only £39. Our ref 39P1.


**12V TO 220V INVERTER KIT** This kit will convert 12V DC to 220v AC. It will supply up to 130 watts by using a larger transformer. As supplied it will handle about 15 watts. Price is £12. Our ref 12P17.

**FULL RANGE OF COMPONENTS** at very keen prices are available from our associate company SCS COMPONENTS. You may already have your catalogue, if not request one and we will send it FOC with your order.

**HIGH RESOLUTION MONITOR** 9in black and white, used Philips tube M24360W. Made up in a lacquered frame and has open sides. Made for use with OPD computer but suitable for most others. Brand new. £20. Our ref 20P26.

**12 VOLT BRUSHLESS FAN.** Japanese made. The popular square shape (4 1/2in x 4 1/2in x 1 1/4in). The electronically run fans not only consume very little current but also they do not cause interference as the brush type motors do. Ideal for cooling computers, etc., or for a caravan. £8 each. Our ref 8P26.

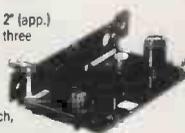**MINI MONO AMP** on p.c.b. size 4" x 2" (app.) Fitted Volume control. The amplifier has three transistors and we estimate the output to be 2W rms. More technical data will be included with the amp. Brand new, perfect condition, offered at the very low price of £1.15 each, or 13 for £12.00.



### J & N BULL ELECTRICAL

Dept. EE 250 PORTLAND ROAD, HOVE, BRIGHTON, SUSSEX BN3 5QT.

MAIL ORDER TERMS: Cash, PO or cheque with order. Monthly account orders accepted from schools and public companies. Please add £2.50 postage to orders. Access and B/Card orders accepted — minimum £5. Phone (0273) 734648 or 203500. Fax No. (0273) 23077.

### POPULAR ITEMS — MANY NEW THIS MONTH

**MAINS FANS** Small type construction. Approx. 5" x 4" mounted on a metal plate for easy fixing. New. £5.00 each. Our ref 5P166.

**MICROWAVE TURNABLE MOTOR** Complete with weight sensing electronics that would have varied the cooking time. Ideal for window displays, etc. Only £5.00. Our ref 5P165.

**JOYSTICKS** for BBC Atari, Dragon Commodore, etc. All £5.00 each. All brand new, state which required.

**TELEPHONE TYPE KEYPAD.** Really first class rear mounting unit. White lettering on black buttons. Has conductive rubber contacts with soft click operation. Circuit arranged in telephone type array. Requires 70mm by 55mm cutout and has a 10 IDC connector. Price £2.00. Ref. 2P251.

**SUB-MIN PUSH SWITCHES** Not much bigger than a plastic transistor but double pole PCB mounting. 3 for £1.00. Our ref BD688.

**AA CELLS** Probably the most popular of the rechargeable NICAD types. 4 for £4.00. Our ref. 4P44.

**20 WATT 4 OHM SPEAKER** With built in tweeter. Really well made unit which has the power and the quality for hi-fi 6 1/2" dia. Price £5.00. Our ref. 5P155 or 10 for £40.00 ref. 40P7.

**MINI RADIO MODULE** Only 2in square with ferrite aerial and solid dia. tuner with own knob. It is superb and operates from a PP3 battery and would drive a crystal headphones. Price £1.00. Our ref. BD716.

**BULGIN MAINS PLUG AND SOCKET** The old and faithful 3 pin with screw terminals. The plug is panel mounted and the socket is cable mounted. 2 pairs for £1.00 or 4 plugs or 4 sockets for £1.00. Our ref. BD715, BD715P, or BD715S.

**MICROPHONE** Low cost hand held dynamic microphone with on/off switch in handle. Lead terminates in 1.35mm and 1.25mm plug. Only £1.00. Ref. BD711.

**MOSFETS FOR POWER AMPLIFIERS AND HIGH CURRENT DEVICES** 140v 100watt pair made by Hitachi. Ref. 2SK413 and its complement 2SJ118. Only £4.00 a pair. Our Ref. 4P42.

Also available in H pack Ref 2S139 and 2SK343 £4.00 a pair. Ref. 4P51.

**TIME AND TEMPERATURE LCD MODULE A** 12 hour clock a Celsius and Fahrenheit thermometer a too hot alarm and a too cold alarm. Approx 50x20mm with 12.7mm digits. Requires 1AA battery and a few switches. Comes with full data and diagram. Price £6.00. Our ref. 6P12.

**REMOTE TEMPERATURE PROBE FOR ABOVE.** £3.00. Our ref. 3P60.

**A REAL AIR MOVER** Circular axial fan moves 205 cubic foot per min which is about twice as much as our standard 4 1/2" fans. Low noise mains operated 6 1/2" dia. brand new. Regular price over £30.00. Our price only £10.00. Our ref 10P71.

**600 WATT AIR OR LIQUID MAINS HEATER** Small coil heater made for heating air or liquids. Will not corrode, lasts for years. Coil size 3" x 2" mounted on a metal plate for easy fixing. 4" dia. Price £3.00. Ref. 3P78 or 4 for £10.00. Our ref. 10P76.

**EX-EQUIPMENT SWITCHED MODE POWER SUPPLIES** Various makes and specs but generally +5, +12v ideal bench supply. Only £8.00. Our ref. 8P36.

**ACORN DATA RECORDER** Made for the Electron or BBC computer but suitable for others. Includes mains adaptor, leads and book. £12.00. Ref. 12P15.

**PTFE COATED SILVER PLATED CABLE** 19 strands of .45mm copper will carry up to 30A and is virtually indestructible. Available in red or black. Regular price is over £120 per reel. Our price only £20.00 for 100m reel. Ref. 20P21 or 1 of each for £35.00. Ref 35P2. Makes absolutely superb speaker cable!

**NEW PIR SENSORS** Infra red movement sensors will switch up to 500w mains, UK made. 12 month manufacturers warranty, 15-20m range with a 0-10min timer, adjustable wall bracket. Only £20.00. Ref. 20P24.

**MITSUBISHI 3 1/2" DISC DRIVES** Brand new drives, 1/2 height double sided, double density warranted. Our price £60.00. Ref. 60P5.

**NON-MEMORY PUSHBUTTON TELEPHONES.** Same condition as 10 Memory with redial £3.00. Our ref. 3P79. BT approved.

**SPECTRUM PRINTER INTERFACE** Add a centronics interface to your Spectrum complete with printer cable for only £4.00. Our ref. 4P52.

**SPECTRUM SOUND BOX** Add sound to your Spectrum with this device. Just plug in. Complete with speaker, volume control and nicely boxed. A snip at only £4.00. Our ref. 4P53.

**BBC JOYSTICK INTERFACE** Converts a BBC joystick port to an Atari type port. Price £2.00. Our ref. 2P261.

**TELEPHONE EXTENSION LEAD** 5m phone extension lead with plug on one end, socket on the other. White. Price £3.00. Our ref. 3P70 or 10 leads for only £19.00. Ref. 19P2.

**LCD DISPLAY** 4 1/2" digits supplied with connection data £3.00. Ref. 3P77 or 5 for £10. Ref. 10P78.

**CROSS OVER NETWORK** 8 Ohm 3 way for tweeter midrange and woofer nicely cased with connections marked. Only £2.00. Our ref. 2P255 or 10 for £15.00. Ref. 15P32.

**BASE STATION MICROPHONE** Top quality uni-directional electret condenser mic 600r impedance sensitivity 16-18KHz — 68db built in chime complete with mic stand bracket. £15.00. Ref. 15P28.

**MICROPHONE STAND** Very heavy chromed mic stand, magnetic base 4" high. £3.00 if ordered with above mic. Our ref. 3P80.

**SOLAR POWERED NICAD CHARGER** 4 Nicad AA battery charger. Charges 4 batteries in 8 hours. Price £6.00. Our ref. 6P3.

**MAINS SOLDERING IRON** Price £3.00. Our ref. 3P65.

**SOLDERING IRON STAND** Price £3.00. Our ref. 3P66.

**MAINS SOLDERING IRON** Price £3.00. Our ref. 3P65.

**SOLDERING IRON STAND** Price £3.00. Our ref. 3P66.

**PIR SENSORS** Suitable for alarm systems etc. Nicely boxed. Priced at only £10.00. Our ref. 10P79.

**SHARP PLOTTER PRINTER** New 4 colour printer originally intended for Sharp computers but may be adaptable for other machines. Complete with pens, paper etc. Price £16.00. Our ref. 16P3.

**CENTRONICS ADAPTER KIT** Converts the above plotter/printer to Centronics compatible. Price £4.00. Our ref. 4P57.

**CAR IONIZER KIT** Improve the air in your car, clears smoke and helps prevent fatigue. Case req. Price £12.00. Our ref. 12P8.

**NEW FM BUG KIT** New design with PCB embedded coil 9v operation. Priced at £5.00. Our ref. 5P158.

**NEW PANEL METERS** 500uA movement with three different scales that are brought into view with a lever. Price only £3.00. Ref. 3P81.

**STROBE LIGHTS** Fit a standard edison screw light fitting 240V 40/min. flash rate available in yellow, blue, green and red. Complete with socket. Price £10 each. Ref. 10P80 (state colour required).

**ELECTRONIC SPEED CONTROL KIT** Suitable for controlling our powerful 12v motors. Price £17.00. Ref. 17P3 (heatsink required).

**EXTENSION CABLE WITH A DIFFERENCE** It is flat on one side making it easy to fix and look tidy. 4 core, suitable for alarms, phones etc. Our price only £5.00 for 50m reel. Ref. 5P153.

**METAL PROJECT BOX** Ideal for battery charger, power supply etc. Sprayed grey size 8" x 4" x 4 1/2". Louvered for ventilation. Price £3.00. Ref. 3P75.

# EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY



ABC

VOL 19 No 5 MAY 1990

The Magazine for Electronic & Computer Projects

ISBN 0262-3617

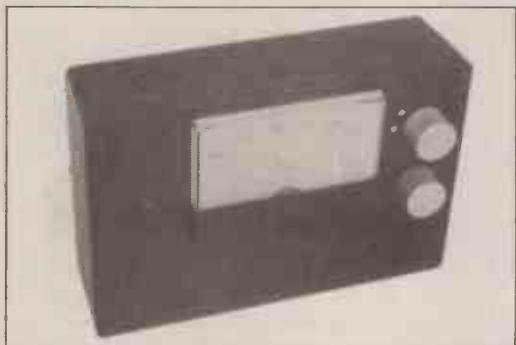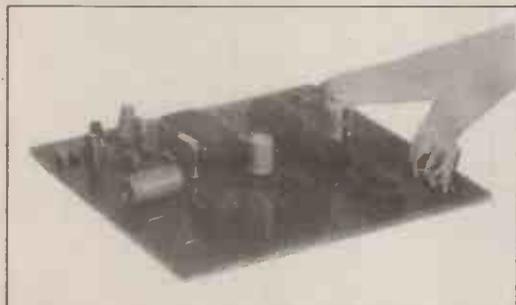PROJECTS ... THEORY ... NEWS ...  
COMMENT ... POPULAR FEATURES ...



Cover photograph by Reflections of Bournemouth

© Wimborne Publishing Ltd 1990. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduced or imitations in whole or in part are expressly forbidden.

Our June '90 Issue will be published on Friday, 4 May 1990. See page 295 for details.

Everyday Electronics, May 1990

## Projects

- AMSTRAD CPC SPEECH SYNTHESISER** 304  
by Robert Penfold  
If only your Amstrad could talk!
- ELECTRONIC BAROMETER** 310  
by Owen Bishop  
Take some of the guesswork out of local "weather forecasting"
- AZIMUTH ADJUSTMENT AID** 322  
by T. R. de Vaux-Balbirnie  
You don't have to scrap your old tape recorder — bring it back to life!
- S. W. RADIO** 7  
by Robert Penfold  
"Tweak" and "Twiddle" your way around the world **Supp-**
- QUIZMASTER** 328  
by Adrian Galea  
A question of logic
- AUTO MEMO** 342  
by Owen Bishop  
Get your message across loud and clear

## Series

- MICRO IN CONTROL — PART 6** 316  
by John Hughes  
Counting circuits and control logic
- ROBOT ROUNDUP** 326  
by Nigel Clark  
Investigating the world of robots
- ON SPEC** 334  
by Mike Tooley  
The place for Spectrum and Sam miro owners
- ACTUALLY DOING IT** 346  
by Robert Penfold  
Considering mains power
- AMATEUR RADIO** 348  
by Tony Smith G4FA1  
Mouse Decoders and Keyboards; Alternative Test
- BBC MICRO** 350  
by Robert Penfold  
Communications applications

## Features

- EDITORIAL** 303
- SHOPTALK** 319  
by David Barrington  
Product news and component buying
- FOR YOUR ENTERTAINMENT** 320  
by Barry Fox  
Hot Tip; Lap-Top Rambo; DATs Music
- MARKET PLACE** 333  
Free readers buy, sell and swop spot
- POWER SUPPLIES FOR PROJECTS** 336  
by Vivian Capel  
Pitfalls to look out for when designing mains power supplies
- DOWN TO EARTH** 340  
by George Short  
Valves past and future
- DIRECT BOOK SERVICE** 352  
Selected technical books by mail order
- PRINTED CIRCUIT BOARD SERVICE** 356
- ADVERTISERS INDEX** 360

**FREE** between pages 326 and 327

**AMATEUR RADIO SUPPLEMENT (12-pages)**  
Shortwave Reception — Crystal Set — DIY Aerials — T.R.F. Receiver

Readers Service • Editorial and Advertisement Departments 303

## RESISTORS

Carbon Film 0.25W E12 or E24 series 1p each (min quantity 10 per value), 80p per 100, £6.00 per 1000.

### \*\* Special Offer \*\*

Mixed Pack, of 1000 Carbon Film resistors, 1R to 10M, 100 different values all separately packed and labeled only £5.90

Metal Film 0.25/0.5 W E96 series 10R to 1M0 4p each (min quantity 10 per value), £3.00 per 100.

Ceramic/wirewound  
4W OR1-10K 35p each  
7W OR33-12K 37p each  
11W OR68-10K 40p each  
17W 1R-10K 44p each  
5% discount on 10+, 10% on 25+, 20% on 100+

Skeleton Pre-Sets  
E3 series 100R-1M 20% Horizontal or vertical 18p each.  
5% discount on 10+, 10% on 25+, 20% on 100+

Enclosed Pre-Sets  
100R-10M 20% Horizontal or Vertical 24p each. 5% discount on 10+, 10% on 25+, 20% on 100+

20 Turn 3/4" Cermet Pots  
10% tolerance 10R-2M 90p each, 5% discount on 10+, 10% on 25+, 20% on 100+

## CAPACITORS

Radial Aluminium  
Electrolytic 20% tolerance

10/16/25/35 Volt  
4.7, 10, 22, 33, 47, 100 12p  
220, 330, 470 20p  
1000 30p  
2200 48p  
3300 65p  
4700 85p

50/63/ Volt  
0.47, 1, 2.2, 3.3, 4.7, 10 12p  
22, 33, 47 20p  
100, 220 30p  
470 50p  
1000 90p

100 Volt  
0.47, 1, 2.2, 4.7 12p  
10, 22 20p  
47 30p  
100 50p

Ultra miniature Aluminium electrolytic radial 20% tolerance

4 V 18p  
220

6.3 Volt 18p  
22, 100

16 Volt 18p  
10, 22, 47

25 Volt 18p  
10, 22, 33

35 Volt 18p  
4.7, 10, 22

50 Volt 18p  
0.1, 0.22, 0.33, 0.47, 1, 2.2, 3.3, 4.7, 10

## CAPACITORS

Disc Ceramic 5% tolerance 150Volt values in pF  
15, 22, 33, 47, 68, 100, 150, 220, 330, 470 4p  
6p

10% tolerance value in pF  
220, 330, 470, 680, 1000, 1500, 2200 6p  
3300, 4700, 6800 8p

+80%-20% tol. value pF  
4700, 10000 6p  
22000, 47000 9p

Tant. Bead resin dipped 20% tolerance value in uF  
6.3 Volt 15p  
10, 22 25p  
47

10 Volt 15p  
3.3, 4.7, 6.8 25p  
10, 15 35p  
22, 33, 47

16 Volt 15p  
2.2, 3.3, 4.7, 6.8 25p  
10, 15 35p  
22, 33

25 Volt 15p  
1, 2.2, 3.3 25p  
4.7, 6.8 35p  
10, 15

35 Volt 15p  
0.1, 0.22, 0.33, 0.47 20p  
0.68, 1, 2.2, 3.3 30p  
4.7, 6.8, 10

## CMOS

4000	17p	4106	34p
4001	17p	4160	40p
4002	17p	4161	40p
4006	37p	4162	40p
4007	17p	4163	40p
4008	37p	4174	37p
4011	17p	4175	40p
4012	17p	4194	42p
4013	25p	4501	27p
4014	37p	4502	40p
4015	37p	4503	37p
4016	28p	4504	120p
4017	37p	4506	76p
4018	37p	4508	99p
4020	37p	4510	37p
4021	37p	4511	37p
4022	37p	4512	37p
4023	17p	4513	99p
4024	35p	4514	85p
4025	17p	4515	80p
4027	34p	4516	37p
4028	37p	4517	99p
4029	37p	4518	37p
4032	56p	4519	26p
4034	95p	4520	37p
4035	44p	4521	85p
4038	65p	4522	44p
4040	37p	4526	44p
4042	37p	4527	44p
4043	37p	4528	44p
4044	37p	4529	50p
4046	47p	4530	99p
4049	27p	4531	44p
4050	27p	4532	80p
4051	37p	4534	240p
4052	37p	4536	120p
4053	37p	4538	54p
4060	37p	4539	45p
4066	20p	4541	50p
4067	99p	4543	54p
4068	17p	4544	130p
4069	17p	4547	130p
4070	17p	4549	400p
4071	17p	4551	85p
4072	17p	4553	120p
4073	17p	4554	320p
4075	17p	4555	50p
4076	17p	4556	50p
4077	17p	4557	120p
4078	17p	4558	120p
4081	17p	4559	440p
4082	17p	4560	110p
4093	27p	call sales for 4500 series above 4560	
4094	48p		
4097	99p		
4099	46p		

## DIODES

1N914 5p  
1N4148 4p  
1N4001 3p  
1N4002/3/4/5/6 4p  
1N5401 7p  
1N5402/4/6/8 11p

### Zener Diodes


500 mW  
2.4, 2.7, 3.3, 3.9, 4.7, 5.1, 5.6, 6.2, 6.8, 8.2, 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91  
All above voltages at 5p each

1.3 W  
3.3, 3.9, 4.3, 4.7, 5.1, 5.6, 6.2, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13, 15, 16, 18, 20, 22, 24, 27, 30, 33, 36, 39, 43, 47, 51, 56, 62, 68, 75, 82, 91  
All above voltages at 16p each

2.5W, 20W & 75W versions available
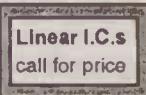
### Bridges

W005 23p  
W02 25p  
W04 30p  
W06/08 35p  
2A 200V 65p  
2A 400V 72p  
2A 600V 90p  
6A 200V 78p  
6A 400V 84p  
6A 600V 99p



## TRANSISTORS

BC107B 20p  
BC108B 20p  
BC109C 22p  
BC184C 6p  
BC212B 6p  
BC239C 4p  
BC307C 4p  
BC548C 4p  
BC558C 4p  
ZTX300 17p

The above are a few examples from the 1000's of transistor types we have. We cover all ranges and types including JFET, SIPMOS, TMOS, TIP plastic & metal, FET & Darlington.

## REGULATORS

7805 5V @ 1.5A 30p  
7812 12V @ 1.5A 30p  
7815 15V @ 1.5A 30p  
7905 -5V @ 1.5A 30p  
7912 -12V @ 1.5A 30p  
7915 -15V @ 1.5A 30p

## KITS KITS KITS

ALL KITS ARE SUPPLIED WITH MAINS TRANSFORMER, HIGH QUALITY GLASS FIBRE SILK SCREENED PCB, FULL INSTRUCTIONS, HEATSINK, SOLDER ETC. CASE NOT SUPPLIED BUT AVAILABLE

**CONSTANT CURRENT NI-CAD CHARGER** Charge your Ni-Cads safely, can be left on indefinitely without damage, batteries fully charged from flat in approx. 18 hours. Charge up to 12 batteries in series (except PP3). **£7.50**

**FAST NI-CAD CHARGER** Rapidly charge your Ni-Cad racing pack from mains or 12Volts. Charger guarantees a full charge every time, making maximum use of your pack. **£10.50**

**BENCH POWER SUPPLY 2.5 - 35 Volt @ 2 Amps** The following spec ensures excellent value for money for this most essential of workshop equipment. Line Reg. 0.03%, Load Reg. 0.1% Ripple Rejection 70 dB, Output Res. 1.5 milliOhm, Output Noise 80uV. **£8.00**

**10 Amp BENCH POWER SUPPLY 5 - 33 Volt** Use for powering C.B./ Ham Radios, or a very high powered bench power supply. Spec as 2A version above. **£32.00**

HUNDREDS OF KITS AVAILABLE - SEND FOR LIST

## 1990 CATALOGUE

OUR NEW CATALOGUE LISTS THOUSANDS OF COMPONENTS, SWITCHES, RELAYS, BUZZERS, SOUNDERS, FIXINGS, CHEMICALS, PCB MATERIAL, CABLE, MODULES, METERS, SOLDER, CONNECTORS, PLUGS, SOCKETS, TRANSFORMERS, INDUCTORS, PLASTIC & METAL BOXES, AND LOTS, LOTS MORE - IN FACT EVERYTHING YOU NEED

£2.50 (INCLUDING 5 £1 DISCOUNT VOUCHERS)

## ADVANCED ELECTRONIC PRODUCTS LTD

P.O. BOX 10, Newton Abbot, Devon. TQ12 1JP

Tel: (0626) 332091 Fax: (0626) 332381

MAIL ORDER TERMS: POSTAL ORDER OR CHEQUE WITH ORDER. PLEASE ADD 75p POST & PACKING TO ORDER VALUE AND THEN 15% VAT. ACCESS & VISA HOLDERS PLEASE PHONE ORDER BEFORE 4.45PM FOR SAME DAY DESPATCH. ALL ORDERS UNDER 750 Grms SENT BY FIRST CLASS POST. OVERNIGHT CARRIER £9

# MAINS APPLIANCE REMOTE CONTROL

*The dream of controlling any appliance from your armchair comes much closer with our Mains Appliance Remote Control. It employs an infra-red remote control and the standard house mains wiring to switch most mains appliances or to adjust a digital room thermostat. Its uses are limited by your imagination and ingenuity!*



## DIRECT CONVERSION RECEIVER

*Designed for the 80 metre amateur band this set has a performance that is not far short of a full superhet circuit. The receiver and the chosen frequency band provide an excellent introduction to amateur radio for those with some constructional experience.*

## MINI BRIDGE AMPLIFIER

*This simple audio power amplifier is a general purpose type which could be used in a number of applications. Its design was prompted by a reader's request for a small but reasonably powerful amplifier suitable for use with video equipment. The unit should be equally suitable for operation with a guitar pick-up or as a general purpose test amplifier. It is powered by four HP7 size batteries.*



## CHOOSING AND USING TEST EQUIPMENT

*This is the first part of a short series of self contained articles looking at the various items of test gear available, giving consideration to how useful they are, how to use them and what to look for when buying them. Unless you own all the test gear you could ever need these articles are for you.*

# EVERYDAY ELECTRONICS

JUNE ISSUE ON SALE FRIDAY MAY 4 1990



# MARCO trading

ELECTRONIC COMPONENTS & EQUIPMENT

24HR  
ANSAPHONE

**MARCO TRADING**  
THE MALTINGS, HIGH STREET, WEM.  
SHROPSHIRE SY4 5EN DEPT 5  
Tel: (0939) 32763 Telex: 35565  
Fax: (0939) 33800  
ELECTRICAL & ELECTRONIC  
COMPONENT SUPPLIERS



**NEW CATALOGUE**  
200+ PAGE ELECTRONIC  
COMPONENT CATALOGUE  
(INCLUDING DISCOUNT  
TICKETS) SEND £1.00


BRANCHES: SUPERTRONICS, 65 HURST STREET, BIRMINGHAM. 021 6666504  
WALTONS, 55A WORCESTER STREET, WOLVERHAMPTON. 0902 22039

ALL  
PRICES  
INCL. VAT

## MAY SPECIAL OFFER



**BOTH PACKS FOR £15.00**

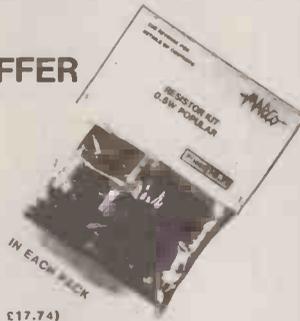

(TOTAL CATALOGUE PRICE - £17.74)

### DRILL PRESS



**£85**  
Plus £5.00 carriage.

5 speed single phase, 1/2 hp motor drives 13mm chuck belt

### RIFLE MICROPHONE

Super-directive sound collecting microphone. High sensitivity super cardioid electret condenser. Tubular element with foam windshield. Built-in amplifier and earphones



Type..... Uni-directional. Electret condenser  
Impedance..... 2Kohms  
Response..... 200-15000Hz  
Sensitivity: Mic..... -45dB  
Headphones..... -5dB

ORDER CODE MIC/RIFLE PRICE **£34.95**

### PERSONAL CASSETTES

#### SPECIAL OFFER

**AIWA - HS-P12**

Features: Auto-Stop, Metal Selector. Our Price **£8.99**

**AIWA - HS-G35 Mk II**

Features: Auto-Reverse, 3-Band Graphic Equalizer, CrO<sub>2</sub>/Metal Selector. Our Price **£16.99** or 2 for **£30.00**

### FULL RANGE OF BABANI BOOKS IN STOCK

### ANTEX IRONS

C-15W IRON	£7.65
CS-17W IRON	£7.75
XS-25W IRON	£7.85
XS KIT 25W	£10.85
CS KIT 17W	£10.75
C-KIT 15W	£10.75
ALL BITS FOR IRONS - £1.60	
ELEMENTS £3.95 STANDS £2.99	

**ORYX PORTASOL GAS SOLDERING IRON**  
**£18.75 TIPS £5.50**

### 4-WAY - WITH LEAD & PLUG

A 4-way 13A socket, fused and with neon indicator. Fitted with 3 meters of cable terminating in a 13A fused plug. White.

PRICE **£5.75** each




### 4-WAY EX SOCKET

Without above.  
PRICE **£3.99**

### 12V CHARGER

Please add £1.50 P&P unless stated.

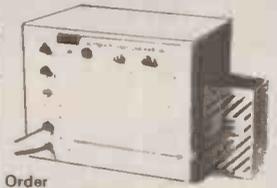

Order Code: SO/135  
Price - **£11.50** (+£2.00 P&P)

### 12V RECHARGEABLE UNITS

10 x 'D' size ni-cads (4ah) encapsulated in a black plastic case. Fuse holder. Gives 12V output when charged. Ex-equipment. Fully guaranteed. Dimensions: 245x75x75mm

\* This unit is supplied, depending on availability. Either in 4-pin version or 6-pin version. The price is the same for either version.



Order Code: SO/132  
Price: 1+ **£9.20** (+ £2.12 P&P)  
10+ **£8.05** (P&P £4.50 per 10)

### 12V TWIN FLUORESCENT LAMP 12" DOUBLE TUBES

ONLY **£5.99**



ATTRACTIVE WHITE FITTING, RIBBED PERSPEX DIFFUSER, ON/OFF SWITCH, 3FT CABLE, TRANSISTORISED CIRCUITRY, KEYHOLE FIXING 12V DC 8W TUBES. DIMENSIONS: 368 x 67 x 43MM. IDEAL FOR BOATS, CARAVANS, VANS ETC.

### QUARTZ HALOGEN SPOT-LIGHT

Hand-held or hanging. 12ft. Curly cable. 5 times normal headlamp intensity. On/off switch. Simply plugs into cigar lighter socket.

**£5.99**



### ELECTRET MICROPHONE INSERT

10mm diam. 6.5mm thick 3V-10V (9V typ.) 600ohm. 20-12000Hz  
Order Code: AUD/MIC/1 **65p**  
Also AUD/MIC/2



Full range of BABANI Books on TV/RADIO/AERIALS etc. e.g.  
INTRODUCTION TO SATELLITE T.V. **£5.95**  
Fane Loudspeaker enclosure Design & Construction - 54 pages **£3.99**  
Full range of WIREWOUND RESISTORS now in stock - 2.5W/4W/7W/11W/17W/25W/50W - see our new catalogue


### OSCILLOSCOPES

TEKTRONIX D755 - 50 meg. Solid State  
Price **£295.00** incl. V.A.T. Carriage **£12.00**

### BOOKS

DATA VOLUME 1 - Trans. data & drawings	£3.99
A-BUY	£10.75
DATA VOLUME 2 - as above C-Z	£10.29
DATA VOLUME 3 - 2N-2N6735	£42.00
Set of 4	£13.50
DATA VOLUME 4 - 2SA & on	£10.75
DIODES VOLUME 1	£10.65
DIODES VOLUME 2	£20.60
Both Volumes	£8.95
I.C. CMOS	£8.95
I.C. TTL	£19.50
I.C. LIN VOLUME 1	£8.95
I.C. LIN VOLUME 2	£8.99
Both Volumes	£13.00
THYRISTORS A to Z	£10.45
TRANSISTORS A to Z	£8.90
TRANSISTORS 2N-3N	£7.00
Both Volumes	£13.00

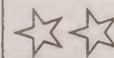Full range of Transistors, 74LS, CMOS, Meters, TOOLS, Boxes, Vero, Valves, PCB, Audio, Aerials, etc., etc.



SEE OUR CATALOGUE

### HOME ALARM PACKAGE

includes:

- \* Optima Alarm Control Panel
- \* External Red Bell Box
- \* 2 x 1 Internal Passive I.R.
- \* 2 x Door Contacts
- \* Siren for bell box
- \* 100 mtrs. cable and clips
- \* Full fitting instructions

ONLY **£115** + £2.50 CARRIAGE  
(Phone for further details)

### POWER AMPLIFIER

High power stereo in-car amplifier, 2 x 75W stereo or mono (switchable). Input selector switch permits connections to normal and high power car stereo players. Power will ON/OFF automatically from remote connection to car stereo power lead. Input sensitivity selector. Supplied complete with fitting instructions.

ORDER CODE CAR/PA  
PRICE **£39.99**



### "CLOSED-CIRCUIT" TELEVISION SYSTEM

1 x CAMERA    1 x MONITOR    1 x CAMERA BRACKET

USED    USED    NEW

PRICE: **£175** Plus £12.00 carriage

### SURVEILLANCE EQUIPMENT

TYPE 1: Camera, Monitor, Camera bracket, 40m lead - ready to use. Price: **£149.99** Carriage: **£15.00**  
TYPE 2: Identical to the above camera but with built-in intercom. Price: **£199.00** Carriage: **£15.00**

### DESOLDERING PUMP

**£2.99** ORDER CODE TOOL/D/SOL

STAR BUY

### PROBES - X1, X10

Useful set of X1 and X10 probes. One unit which is switchable. BNC connectors.  
Price **£14.95**

### MAINS ADAPTOR

3-4, 5-6-7, 5-9-12V  
300 - A

**£3.50** ..  
**£3.00** .. 10+

### 22SWG RESIN SOLDER

500gm. REEL    1+    10+    100+

**£4.99**    **£4.75**    **£3.99**

ALSO 18SWG at **£4.95** 500gm.

Orders of 5 or more reels please add a further 75p P&P

### FM TRANSMITTER

Very High Quality 'MINI-BUG' - Ideal for Baby Alarm etc.!!  
A very good range is obtainable - we have obtained over 1/2 mile, but it does depend on conditions. Simply remove cover - insert battery - and you're ready to go. Reception can be obtained on any FM radio. Frequency: 105-108 MHz FM. Power: PP3 9V battery (not included). Dimensions: 4.25" x 2.25" x 0.75". Order Code - SO.004. Price: **£9.99**



### MARCO KITS

Ceramic 50V (125)	£3.99
Electrolytics Rad. (100)	£8.50
Fuse 20mm Q B (80)	£4.75
Fuse 20mm A S (80)	£8.50
Pre-set Pots. Horiz. (120)	£7.75
Pre-set Pots. Vert. (120)	£7.75

### RESISTORS

0.25W Popular (1000)	£6.99
0.25W 5 off (305)	£3.75
0.25W 10 off (610)	£5.10
0.5W Popular (1000)	£10.75
0.5W 5 off (365)	£5.40
0.5W 10 off (730)	£8.75
1W5 off (365)	£15.25
2W5 off (365)	£25.00
Zener Diodes 5 off (55)	£3.99

We deliver from stock - The fastest way to order is a fax !

### ULTRASONIC CAR ALARM




Complete kit including case  
44.367BKL ..... £ 30.40

This system is specially designed to protect your car and its contents against potential thieves. Low current consumption and high noise immunity are just two of its distinguishing features.

In addition the system has a voltage sensing device i.e. the alarm is also triggered if appliances are switched on by an unauthorised person (e.g. the interior lighting when the door is opened).

### PC Radio (Elektronics February 1990)

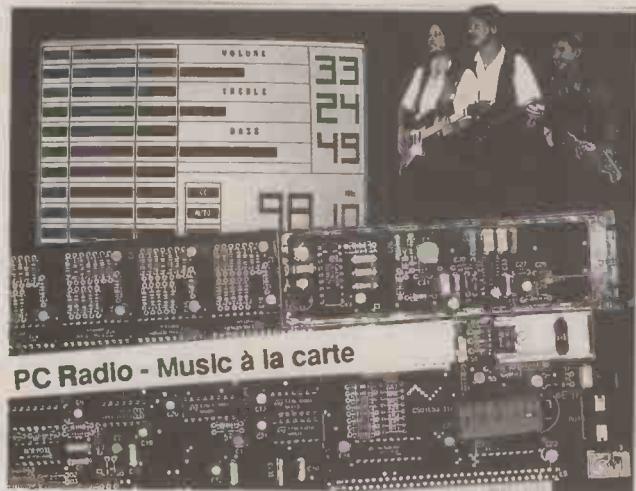

PC Radio - Music à la carte

### DIGITAL PROFESSIONAL ECHO 1000

(Elektronics June 89)

This low cost echo unit is certain to impress music lovers - amateur and professional - everywhere. Excellent specification and top performance make the EU 1000 a winner and despite meeting professional requirements the unit will not make too big a hole in your pocket. Working on the delta modulation prin-

ciple on a digital base, delay times up to one second are possible at full bandwidth and large signal to noise ratio.

Complete kit  
44.255BKL ..... £ 99.50

Ready assembled module  
44.255F ..... £ 134.50



#### Specification

Input sensitivity:  
Input 1 : 2 mV  
Input 2 : 200 mV

Delay Time:  
variable from 60 ms to 1 s

Bandwidth :  
100 Hz to 12 kHz

#### Additional features:

- inputs mixable
- single and multiple echo
- adjustable delay level
- switchable vibrator
- switch-controlled noise suppression

This FM radio consists of an insertion card for IBM PC-XTs, ATs and compatibles and is available as a kit or a ready-built and aligned unit. The radio has an on-board AF power amplifier for driving a loudspeaker or a headphone set, and is powered by the computer. A menu-driven program is supplied to control the radio settings.

Complete kit  
44.544BKL ..... £ 82.75

Ready assembled module  
44.544F ..... £ 137.30

### VM 1000 Video-Modulator

(Elektronics March 90)



Many inexpensive or older TV sets lack a SCART or other composite video input, and can only be connected to a video recorder or other equipment via an RF modulator. The modulator operates at a UHF TV channel between 30 and 40. Use is made of a single-chip RF modulator that couples low cost to excellent sound and picture quality.

Complete kit  
44.546BKL ..... £ 36.90

#### Ordering and payment:

- all prices excluding V.A.T. (french customers add 18.6%T.V.A.)
- send Euro-cheque, Bank Draft or Visa card number with order. Please add £ 3.00 for p & p (up to 2 kg total weight)
- postage charged at cost at heigher weight Air/Surface -
- we deliver worldwide except USA and Canada
- dealer inquiries welcome

### RFK 700 RGB-CVBS Converter

(Elektronics October 89)

Nearly all computers supply as an output signal for colour monitors RGB signals. With the help of the RFK 7000 it is possible to record this signals with a videorecorder or to give them onto a colour TV (This is only possible, if the

computer delivers a vertical sync. of 50 Hz and a horizontal sync. of 15.625 Hz).

The voltage supply is gained from a 12V/300mA-DC voltage mains adaptor.

Complete kit  
44.525BKL ..... £ 66.50

Ready assembled module  
44.525F ..... £ 119.50

### FRK 7000 CVBS-RGB Converter

With the help of the FRK 7000 e.g. it is possible to use a cheap clour monitor with RGB input on a video recorder. The voltage supply is gained from a 12V/300mA-DC voltage mains adaptor.

Complete kit  
44.509BKL ..... £ 66.50


Ready assembled module  
44.509F ..... £ 119.50



We deliver from stock - The fastest way to order is a fax !

LPS 8000 / LC 7000 Low Cost Show Laser

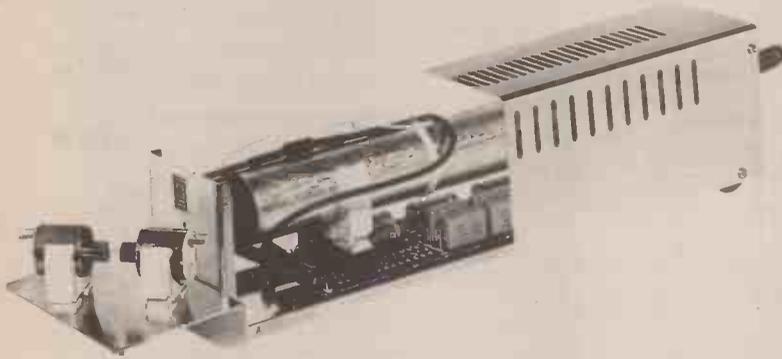(Electronics The Maplin Magazine Dec 88 + Feb-Mar 90)



An almost infinite number of circular patterns can be projected onto a wall or ceiling with this super laser show equipment.

The complete project includes a laser tube and accompanying power supply, housed in a metal case, and a laser controller, LC 7000. The laser controller drives the accompanying deflection unit, fixed onto the laser power supply case, which produces the numerous configurations.

Naturally the laser tube, together with the power supply, can produce beams without the laser controller and the controller can be used with other, similar lasers.

LPS 8000 Laser Power Supply, complete kit  
Version 240 Volts AC  
44.428BKL220 ..... £ 86.90  
Version 220 Volts AC  
44.428BKL240 ..... £ 86.90

LC 7000 Laser Controller, complete kit  
Version 12 Volts DC  
44.427BKL ..... £ 60.80

H-N Laser Tube 2 mW  
44.428LR ..... £ 60.80

LPS 8000 Laser Power Supply, ready assembled module  
Version 240 Volts AC  
44.428F240 ..... £ 156.50  
Version 220 Volts AC  
44.428F220 ..... £ 156.50

LC 7000 Laser Controller, ready assembled module  
Version 12 Volts DC  
44.427F ..... £ 104.30


Laser Motor-Mirror Set, complete kit  
44.506M ..... £ 22.95

VIDEO RECORDING AMPLIFIER

(Elektor Electronics April 89)

Losses can easily occur when copying video tapes resulting in a distinct reduction in quality. By using this video recording amplifier, with no less than four (!) outputs, the modulation range is enlarged and the contrast range of the copy increases.

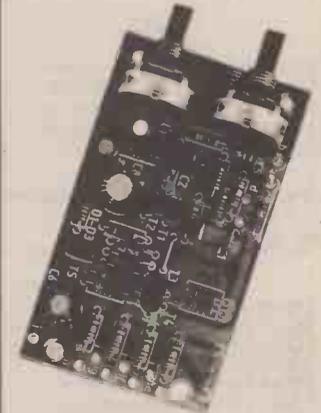Two level controllers for edge definition (contour) and amplification (contrast range) allow individual and precise adaptation.




Complete Kit  
(including Box, PCB and all parts)  
44.324BKL ..... £ 14.75

IBM PC Service Card

(Elektor Electronics May 1990)

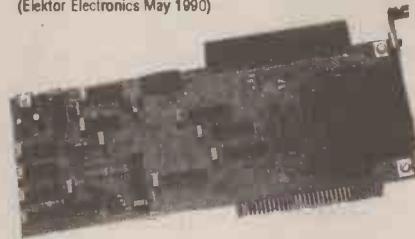This card was developed for assistance in the field of service, development and test. The card is used as a bus-extension to reach the measurement points very easy. It is also possible to change cards without having a "hanging computer".



Complete kit  
44.517BKL ..... £ 77.95


Ready assembled module  
44.517F ..... £ 137.95

TA 1000 Telephone Answering Unit

(Elektor Electronics January 1990)

This automatical telephone answering unit uses a 256-kbit voice recording circuit to store and replay your spoken message of up to 15 seconds. Noteworthy features are that it is available as a complete kit, provides a battery back-up facility and does not require alignment. No provision is made, however, to record incoming calls.

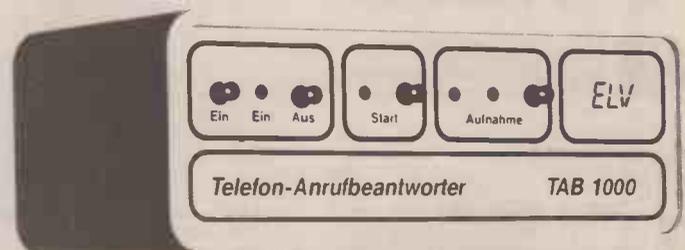Complete kit  
44.433BKL ..... £ 45.65  
Ready assembled module  
44.433F ..... £ 87.25




IC TESTER for IBM-PC-XT/AT

(Electronics The Maplin Magazine Jun-Jul 89 +

Elektor Electronics December 89)

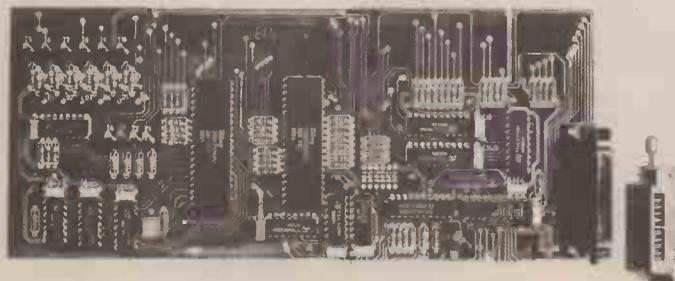With the ELV IC tester logic function tests can be carried out on nearly all CMOS and TTL standard components, accommodated in DIL packages up to 20 pin. The tester is designed as an insertion card for IBM-PC-XT/AT and compatibles. A small ZIF test socket PCB is connected via a flat band cable. Over 500 standard components can be tested using the accompanying comprehensive test software.



Complete Kit including Textool socket, connectors, sockets, Flat band cable, PCB, Software  
44.474BKL ..... £ 60.85

Ready Assembled Module  
4.474F ..... £ 113.00

Software, single  
44.474SW ..... £ 17.85

# MAGENTA ELECTRONICS LTD

MAIL ORDER AND SHOP:  
EE88 135 Hunter Street,  
Burton-on-Trent,  
Staffs. DE14 2ST  
Tel: 0283 65435  
Fax: 0283 46932



All prices include VAT  
Shop open 9-5 Mon-Fri;  
9-2 Saturday  
Official orders welcome

Add £1  
p&p to  
all orders

## SUPERHET BROADCAST RECEIVER


### EE MAR '90

At last, an easy to build SUPERHET A.M. radio kit. Covers Long and medium Wave bands, built in loudspeaker with 1 watt output. Excellent sensitivity and selectivity provided by ceramic I.F. filter. Simple alignment and tuning without special equipment. Kit available less case, or with pre-cut and drilled transparent plastic panels and dial for a striking see-through effect.

KIT REF 835

£15.99

## D.C. MOTOR GEARBOXES

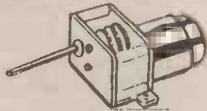

Ideal for Robots and Buggies. A miniature plastic reduction gearbox coupled with a 1.5-4.5 Volt mini motor. Variable gearbox reduction ratios are obtained by fitting from 1 to 6 gearwheels (supplied). Two types available:

**SMALL UNIT TYPE MGS** £3.99  
Speed range 3-2200 rpm. Size 37x43x25mm

**LARGE UNIT TYPE MGL** £4.55  
Speed range 2-1150 rpm. Size 57x43x29mm

*Supplying Electronics  
for Education,  
Robotics, Music,  
Computing and much,  
much more!*

Send NOW for our  
illustrated  
**CATALOGUE**  
Only £1.00!

## STEPPING MOTORS

A range of top quality stepping motors suitable for driving a wide range of mechanisms under computer control using simple interfacing techniques.

**ID35 PERMANENT MAGNET MOTOR** — 48 steps per rev. £16.50

**MD200 HYBRID MOTOR** — 200 steps per rev. £16.80

**MD35 1/4 PERMANENT MAGNET MOTOR** — 48 steps per rev. £12.70

**MD38 PERMANENT MAGNET MOTOR** — 48 steps per rev. £8.95

## MICRO IN CONTROL NEW SERIES STARTED EE DEC '89 STARTER KIT £21.95

ALL PARTS LISTED IN TABLE 1  
INCLUDING 5V 250mA SUPPLY  
AND K12 840 PIN BREADBOARD

## EDUCATIONAL BOOKS & BOOK PROJECTS

### ADVENTURES WITH ELECTRONICS

The classic Easy to Follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-DEC breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-DEC breadboard and all the components for the series.

ADVENTURES WITH ELECTRONICS £4.75  
COMPONENT PACK (less book) £22.35

### FUN WITH ELECTRONICS

From the USBORNE Pocket Scientist series — An enjoyable introduction to electronics. Full of very clear full colour pictures accompanied by easy to follow text. Ideal for all beginners — children and adults. Only basic tools are needed. 64 full colour pages cover all aspects — soldering — fault finding — components (identification & how they work). Also full details of how to build 6 projects — burglar alarm, radio, game, etc. Requires soldering — 4 pages clearly show you how.

The components supplied in our pack allows all the projects to be built and kept. The book is available separately.  
FUN WITH ELECTRONICS Book £2.25  
COMPONENT PACK (less book) £17.55

### 30 SOLDERLESS BREADBOARD PROJECTS

A book of projects by R. A. Penfold covering a wide range of interests. All projects are built on a Verobloc breadboard. Full layout drawings and component identification diagrams enable the projects to be built by beginners. Each circuit can be dismantled and rebuilt several times using the same components. The component pack allows all projects in the book to be built one at a time.

Projects covered include amplifiers, light actuated switches, timers, metronome, touch switch, sound activated switch, moisture detector, M.W. Radio, Fuzz unit, etc.

**30 SOLDERLESS BREADBOARD PROJECTS Book 1** £2.95  
**COMPONENT PACK** £27.15  
**VEROBLOC** £7.49

### ENJOYING ELECTRONICS

A more advanced book which introduces some arithmetic and calculations to electronic circuits. 48 chapters covering elements of electronics such as current, transistor switches, flip-flops, oscillators, charge, pulses, etc. An excellent follow-up to Teach-in or any other of our series. Extremely well explained by Owen Bishop who has written many excellent beginners' articles in numerous electronics magazines.

**ENJOYING ELECTRONICS Book** £3.60  
**COMPONENT PACK** £14.31  
**VEROBLOC** £7.49

Note — A simple multimeter is needed to fully follow this book. The M102 BZ is ideal. £13.98

### A FIRST ELECTRONICS COURSE

A copiously illustrated book that explains the principles of electronics by relating them to everyday objects. At the end of each chapter a set of questions and word puzzles allow progress to be checked in an entertaining way. An S-DEC breadboard is used for this series — soldering is not required.

**A FIRST ELECTRONIC COURSE BOOK** £3.75  
**PACK** £22.35

## EVERYDAY ELECTRONICS KIT PROJECTS

ALL KITS HERE HAVE BEEN FEATURED IN EE. IF YOU DO NOT HAVE THE MAGAZINE WITH THE ORIGINAL ARTICLE, YOU WILL NEED TO ORDER THE REPRINT FOR 80p EXTRA. REPRINTS ALSO AVAILABLE SEPARATELY. KITS INCLUDE CASES, PCB'S, HARDWARE AND ALL COMPONENTS (UNLESS STATED OTHERWISE) CASES ARE NOT DRILLED, LABELS ARE NOT SUPPLIED.

Ref	Price	Ref	Price
835		578	
SUPERHET BROADCAST RECEIVER Mar 90		SPECTRUM I/O PORT less case Feb 87	£10.05
With drilled panels and dial	£15.99	569	CAR ALARM Dec 86
Without above	£12.99	563	200MHz DIG. FREQUENCY METER Nov 86
834	£9.69	561	LIGHT RIDER LAPEL BADGE Oct 86
QUICK CAP TESTER Feb 90		560	LIGHT RIDER DISCO VERSION
833	£29.95	559	LIGHT RIDER 16 LED VERSION
EE 4 CHANNEL LIGHT CHASER Jan 90		556	INFRA-RED BEAM ALARM Sept 86
815	£39.95	544	TILT ALARM July 86
EE TREASURE HUNTER Aug 89		542	PERSONAL RADIO June 86
814	£19.98	528	PA AMPLIFIER May 86
BAT DETECTOR Jun 89		523	STEREO REVERB Apr 86
812	£13.80	513	BBC MIDI INTERFACE Mar 86
ULTRASONIC PET SCARER May 89		512	MAINS TESTER & FUSE FINDER Mar 86
807	£22.71	497	MUSICAL DOOR BELL Jan 86
MINI PSU Feb 89		493	DIGITAL CAPACITANCE METER Dec 85
806	£10.28	481	SOLDERING IRON CONTROLLER Oct 85
CONTINUITY TESTER Feb 89		464	STEPPER MOTOR INTERFACE FOR THE BBC
803	£31.93		COMPUTER less case Aug 85
REACTION TIMER Dec 88			1D35 STEPPER MOTOR EXTRA
800	£28.72		OPTIONAL POWER SUPPLY PARTS
SPECTRUM EPROM PROGRAMMER Dec 88		461	CONTINUITY TESTER July 85
796	£26.61	455	ELECTRONIC DOORBELL June 85
SEASHELL SYNTHESIZER Nov 88		453	GRAPHIC EQUALISER June 85
790	£26.57	444	INSULATION TESTER Apr 85
EPROM ERASER Oct 88		430	SPECTRUM AMPLIFIER Jan 85
786	£7.44	392	BBC MICRO AUDIO STORAGE SCOPE INTERFACE
UNIVERSAL NICAD CHARGER July 88			Nov 84
780	£16.35	387	MAINS CABLE DETECTOR Oct 84
CABLE & PIPE LOCATOR April 88		386	DRILL SPEED CONTROLLER Oct 84
769	£52.95	362	VARICAP AM RADIO May 84
VARIABLE 25V-2A BENCH POWER SUPPLY Feb 88		337	BIOLOGICAL AMPLIFIER Jan 84
	£14.53	263	BUZZ OFF Mar 83
763	£22.31	242	INTERCOM no case July 82
AUDIO SIGNAL GENERATOR Dec 87		240	EGG TIMER June 82
739	£18.65	205	SUSTAIN UNIT Oct 81
ACCENTED BEAT METRONOME Nov 87		108	IN SITU TRANSISTOR TESTER June 78
740	£31.03	106	WEIRD SOUND EFFECTS GEN Mar 78
ACCOUSTIC PROBE Nov 87 (less bolt & probe)		101	ELECTRONIC DICE Mar 77
744	£18.29		
VIDEO CONTROLLER Oct 87			
743	£15.24		
AUTOMATIC PORCH LIGHT Oct 87			
728	£14.45		
PERSONAL STEREO AMP Sept 87			
720	£40.89		
BURST-FIRE MAINS CONTROLLER Sept 87			
724	£28.25		
SUPER SOUND ADAPTOR Aug 87			
718	£71.43		
3 BAND 1.6-300MHz RADIO Aug 87			
719	£12.93		
BUCCANEER LB. METAL DETECTOR inc. coils and case, less handle and hardware July 87			
720	£13.41		
DIGITAL COUNTER/FREQ METER (10MHz) inc. case July 87			
722	£16.54		
FERMOSTAT July 87			
715	£37.97		
MINI DISCO LIGHT Jun 87			
707	£8.94		
EQUALIZER (IONISER) May 87			
700	£22.28		
ACTIVE I/R BURGULAR ALARM Mar 87			
581			
VIDEO GUARD Feb 87			
584			
SPECTRUM SPEECH SYNTH. (no case) Feb 87			

## INSULATION TESTER

EE APRIL 85



A reliable electronic tester which checks insulation resistance of wiring appliances etc., at 500 volts. The unit is battery powered simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. One of our own designs and extremely popular.

KIT REF 444

£20.85

## PET SCARER

EE MAY 89

Produces high power ultrasound pulses. L.E.D. flashes to indicate power output and level. Battery powered (9V-12V or via Mains Adaptor).

KIT REF 812

Mains Adaptor £1.98

£13.80

## DIGITAL FREQUENCY 200 MHz METER

EE NOV 86

An 8 digit meter reading from AF up to 200 MHz in two ranges. Large 0.5" Red LED display. Ideal for AF and RF measurements. Amateur and C.B. frequencies.

KIT REF 563

£62.98

## DIGITAL CAPACITANCE METER

EE DEC 85

Simple and accurate (1%) measurement of capacitors from a few pF up to 1,000  $\mu$ F. Clear 5-digit LED display indicates exact value. Three ranges - pF, nF, and  $\mu$ F. Just connect the capacitor, press the button and read the value.

KIT REF 493

£44.25

## 3 BAND SHORT WAVE RADIO

EE AUG 87

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

KIT REF 718

£28.25

## MOSFET VARIABLE BENCH 25V 2.5A POWER SUPPLY

EE FEB 88

A superb design giving 0.25V and 0-2.5A. Twin panel meters indicate Voltage and Current. Voltage is variable from zero to 25V. A Toroidal transformer MOSFET power output device, and Quad op-amp IC design give excellent performance.

KIT REF 769

£52.96

## MINI STROBE

EE MAY '86

A hand held stroboscope which uses 6 "ultra bright" LEDs as the light source. Designed to demonstrate the principles of stroboscope examination, the unit is also suitable for measuring the speed of moving shafts etc. The flash rate control covers 170-20,000 RPM in two ranges.

KIT REF 529

£14.76

## ACOUSTIC PROBE

EE NOV '87

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers and nosey parkers!

KIT REF 740

£18.65

## 4 CHANNEL LIGHT CHASER

EE Jan '90

A 1000W per channel chaser with zero volt switching, hard drive, inductive load capability, mic sound sensor and sophisticated 'beat' detector. Chase steps to music or auto when quiet. Variable speed and mic. sens. LED mimic on front panel. Switchable for 3 or 4 channels. P552 output. Ideal for rope lights, pin spots, disco and display lighting.

KIT REF 833

£29.95

## EE EQUALISER

EE MAY '87

A mains powered ioniser with an output of negative ions that give a refreshing feeling to the surrounding atmosphere. Negligible current consumption and all-insulated construction ensure that the unit is safe and economical in use. Easy to build on a simple PCB.

KIT REF 707

£16.54

## MUSICAL DOORBELL

EE JAN '86

This project uses a special I.C. pre-programmed with 25 tunes and 3 chimes. A Magenta design, the circuit is battery powered and only draws current whilst producing sounds. Two rotary switches select the tune required. Provision is made for three bell pushes, each of which sounds a different tune, so that three points of entry can be identified.

KIT REF 497

£19.95

## EPROM ERASER

EE OCT '88

Safe low-cost unit capable of erasing up to four EPROM's simultaneously in less than twenty minutes. Operates from a 12V supply. Safety interlock. Convenient and simple to build and use.

KIT REF 790

£26.57

## LIGHT RIDERS

EE OCT '86

Three projects under one title - all simulations of the Knight Rider lights from the TV series. The three are a lapel badge using six LEDs, a larger LED unit with 16 LEDs and a mains version capable of driving six main lamps totalling over 500 watts.

KIT REF 559 CHASER LIGHT

£14.52

KIT REF 560 DISCO LIGHTS

£20.89

KIT REF 561 LAPEL BADGE

£10.86

## EE TREASURE HUNTER

EE AUG '89

A sensitive pulse induction Metal Detector. Picks up coins and rings etc., up to 20cms deep. Low "ground effect". Can be used with search-head underwater. Easy to use and build, kit includes search-head, handle, case, PCB and all parts as shown.

KIT REF 815

Headphones

£39.95  
£1.99

## STEPPING MOTOR INTERFACE

EE AUG '85

This interface enables 4 phase unipolar stepping motors to be driven from four output lines of any computer user port. The circuit is especially suitable for the ID35 motor and our MD200 which are commonly used in buggies and robot arms. Supplied complete with ribbon cable and connector for the BBC user port.

KIT REF 464

£8.95

# TK FOR KITS

## GUARD DOG KIT



One of the best burglar deterrents is a guard dog and this kit provides the barking without the bite! Can be connected to a doorbell, pressure mat or any other intruder detector and produces random threatening barks. Includes mains supply and horn speaker. **XK125** £24.95

## DISCO LIGHTING KITS




**DL8000K** 8-way sequencer kit with built-in opto-isolated sound to light input. Only requires a box and control knob to complete .... £39.95  
**DL1000K** 4-way chaser features bi-directional sequence and dimming 1kW per channel .. £23.95  
**DLZ1000K** Uni-directional version of the above. Zero switching to reduce interference ..... £13.95  
**DLA1** (for DL & DLZ1000K) Optional op-to input allowing audio 'beat/light response ..... 95p  
**DL3000K** 3-channel sound to light kit, zero voltage switching, automatic level control and built-in mic. 1kW per channel ..... £19.55

## POWER STROBE KIT

Produces an intense light pulse at a variable frequency of 1 to 15Hz. Includes high quality PCB, components, connectors, 5Ws strobe tube and assembly instructions. Supply: 240V ac. Size: 80x50x45. **XK124 STROBOSCOPE KIT.** £17.25



## PROGRAMMABLE ELECTRONIC LOCK KIT

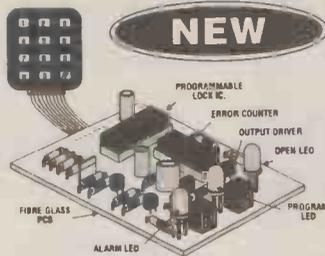

Keys could be a thing of the past with this new high security lock. Secure doors to sheds, garages, even your home or prevent the unauthorised use of computers, burglar alarms or cars. One 4-digit sequence will operate the lock while incorrect entries will sound an alarm. The number of incorrect entries allowed before the alarm is triggered is selected by you. Further entries will be ignored for a time also set by you. Only the correct sequence will open the lock and switch off the alarm. The sequence may easily be changed by entering a special number and code on the supplied keyboard. Kit includes; keyboard, alarm buzzer, high quality PCB and all electronic components. Supply 5-15V DC. Will drive our Latch Mechanism (701 150 @ £18.98) or relay directly. **XK131** £19.95

## SIMPLE KITS FOR BEGINNERS


Especially aimed at the beginner. Have fun with your project even after you have built it and also learn a little from building it. These kits include high quality solder resist printed circuit boards, all electronic components (including speaker where used) and full construction instructions with circuit description.



**SK1 DOOR CHIME** plays a tune when activated by a pushbutton £4.50  
**SK2 WHISTLE SWITCH** switches a relay on and off in response to whistle command £4.50  
**SK3 SOUND GENERATOR** produces FOUR different sounds, including police/ambulance/fire-engine siren and machine gun £4.50

**XK118 TEN EXCITING PROJECTS FOR BEGINNERS** this kit contains a solderless breadboard, components and a booklet with instructions to enable the absolute novice to build ten fascinating projects including a light operated switch, intercom, burglar alarm and electronic lock. Each project includes a circuit diagram, description of operation and an easy to follow layout diagram. A section component identification and function is included, enabling the beginner to build the circuits with confidence .... £17.25

## SUPER-SENSITIVE MICROBUG

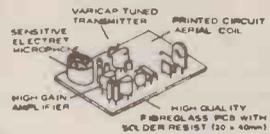


Only 45x25x15mm, including built-in mic. 88-100MHz (standard FM radio). Range approx. 300m depending on terrain. Powered by 9V PP3 (7mA). Ideal for surveillance, baby alarm etc. **XK128** £6.35

## VERSATILE REMOTE CONTROL KIT




Includes all components (+ transformer) for a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc details supplied) can switch up to 16 items of equipment on or off remotely. Outputs may be latched to the last received code or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits. Supply: 240V AC or 15-24V DC at 10mA. Size: (exc. transformer) 9x4x2 cms. Companion transmitter is the MK18 which operated from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available - MK9 (4-way) and MK10 (16-way).  
**MK12 IR Receiver** (inc. transformer) ..... £19.55  
**MK18 Transmitter** ..... £8.95  
**MK9 4-way Keyboard** ..... £2.75  
**MK10 16-way Keyboard** ..... £7.95  
**601133 Box for Transmitter** .. £2.95

## ELECTRONIC WEIGHING SCALE

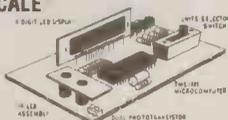


Kit contains a single chip microprocessor. PCB, displays and all electronics to produce a digital LED readout of weight in Kgs or Sts/Lbs. A PCB link selects the scale-bathroom/two types of kitchen scales. A low cost digital ruler could also be made. **ES1** £8.25

## VOICE RECORD/PLAYBACK KIT

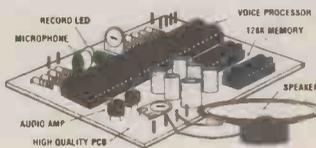

This simple to construct and even simpler to operate kit will record and playback short messages or tunes. It has many uses - seatbelt or light reminder in the car, welcome messages to visitors at home or at work, warning messages in factories and public places. In fact anywhere where a spoken message is announced and which needs to be changed from time to time. Also suitable for toys - why not convert your daughter's £8 doll to an £80 taking doll!!  
 Size ..... 76 x 60 x 15mm  
 Message time ..... 1-5 secs normal speed, 2-10 secs slow speed  
**XK129** £25.95
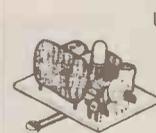
## PROPORTIONAL TEMPERATURE CONTROLLER KIT



Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine making, etc.  
 Maximum load 3kW (240V AC). Temperature range up to 90°C. Size: 7x4x2.5cms. **MK4** ..... £8.95

# TK ELECTRONICS

## TK ELECTRONICS

13 Boston Road  
 London W7 3SJ  
 Tel: 01-567 8910  
 Fax: 01-566 1916

ORDERING INFORMATION All prices INCLUDE VAT. Free P & P on orders over £60 (UK only), otherwise add £1.15. Overseas Customers divide total order by 1.15 then add P & P: Europe £3.50, elsewhere £10.00. Send cheque/PO/Visa/Access No. with order. Giro No. 529314002. Local Authority and educational institutions orders welcome. Shop Open: Tuesday-Thursday 10 am - 5 pm. Saturday 10 am - 4 pm.



**ORDERS: 01-567 8910 24 HOURS**

# EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

The Magazine for Electronic & Computer Projects

VOL. 19 No. 5

May '90

## Editorial Offices

EVERYDAY ELECTRONICS EDITORIAL,  
6 CHURCH STREET, WIMBORNE,  
DORSET BH21 1JH  
Phone: Wimborne (0202) 881749  
FAX: (0202) 841692

See notes on **Readers' Enquiries** below—we regret that lengthy technical enquiries cannot be answered over the telephone

## Advertisement Offices

EVERYDAY ELECTRONICS ADVERTISEMENTS  
HOLLAND WOOD HOUSE, CHURCH LANE,  
GREAT HOLLAND, ESSEX CO13 0JS.  
Frinton (0255) 850596

## MISSING MORSE

This issue has been bumped up in size with the inclusion of the *Amateur Radio Supplement*. Amateur radio is a fascinating hobby, closely allied to electronics and of course totally dependent on electronics.

Before I go on about radio I must make an apology – we have been unable to publish the *Morse Tutor* announced last month, due to circumstances beyond our control – will Mr D. Virden (the designer) please contact us with regard to this project! Providing we can re-establish contact and sort out some minor technical points we hope to publish the design in a few months' time – as they say, watch this space.


As far as we can tell this is the first time in the history of EE that we have been unable to publish an "advertised" project. I hope we can put this right in due course.

Getting back to radio I must say that it was listening to short wave transmissions that originally got me interested in electronics. Building and using your own receiver adds that extra something which makes the hobby even more interesting. Please let us know of your experiences and interest in this subject. It is not an area that we cover in any depth but should there be a high level of interest among readers we will consider more amateur radio projects.
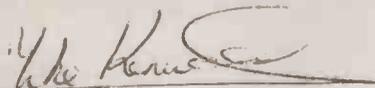
## B.A.E.C. FOUNDER

It is with regret that we must report the death of Cyril Bogod. Well known to many readers, Cyril was the founder of the British Amateur Electronics Club, an organisation which has helped many hobbyists over the years. Cyril was always interested in helping anyone with their hobby and no doubt there are many readers who have much to thank him for.

His organisational abilities and enthusiasm ensured that the B.A.E.C. survived through many years. His generosity has insured it will continue. A short obituary appears on page 347. The last time I spoke to Cyril he was 'phoning from his hospital bed to see if I could help find someone to assist with the B.A.E.C. in future years, such was his dedication.



## SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £16.00. Overseas: £19.50 (£37 airmail). Cheques or bank drafts (in £ sterling only) payable to Everyday Electronics and sent to EE Subscriptions Dept., 6 Church Street, Wimborne, Dorset

BH21 1JH. Subscriptions can only start with the next available issue. For back numbers see below.

## BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS are available price £1.50 (£2.00 overseas surface mail—£ sterling only please—inclusive of postage and packing per copy. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. In the event of non-availability one article can be photostatted for the same price. Normally sent within seven days but please allow 28 days for delivery. We have sold out of Sept. Oct. & Dec. 85, April, May, Oct. & Dec. 86, Jan., April, May & Nov. 87, Jan., March, April, June & Oct. 88.

## BINDERS

Binders to hold one volume (12 issues) are available from the above address for £4.95 (£6.95 to European countries and £9.00 to other countries, surface mail) inclusive of post and packing. Normally sent within seven days but please allow 28 days for delivery. Payment in £ sterling only please.

Editor MIKE KENWARD

Secretary PAMELA BROWN

Deputy Editor

DAVID BARRINGTON

Business Manager

DAVID J. LEAVER

Editorial: WIMBORNE (0202) 881749

Advertisement Manager

PETER J. MEW Frinton (0255) 850596.

Classified Advertisements

Wimborne (0202) 881749

## READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a **stamped self-addressed envelope** or a **self-addressed envelope and international reply coupons**.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

## COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data or answer queries on projects that are more than five years old.

## ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should address them to the advertiser or should consult a local trading standards office, or a Citizen's Advice Bureau, or a solicitor.


## TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the U.K. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.



# AMSTRAD CPC SPEECH SYNTHESISER

## ROBERT PENFOLD

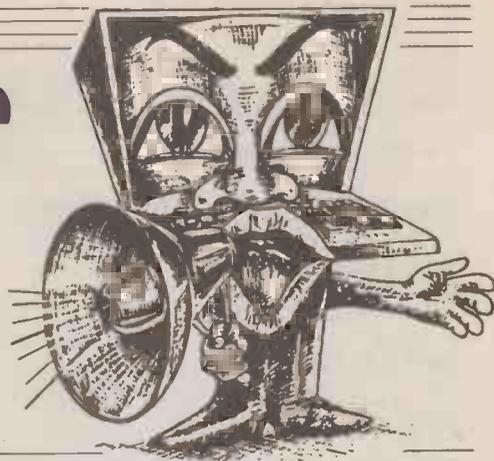

*Low-cost voicing for your Amstrad. Based on the popular SPO256 "speech" chip.*

ALTHOUGH they rank as one of the most popular computer ranges, the number of published add-on projects for the Amstrad CPCs seems to be relatively small. Possibly this is due to the fact that Amstrad launched these computers after the main home computer boom, when interest in computer projects had waned somewhat. Anyway, this article describes an add-on speech synthesiser for any computer in the CPC range, and helps to rectify the lack of projects for these machines.

The unit fits onto the CPC expansion port, and provides its speech output via the computer's built-in loudspeaker. The circuit is based on the popular SPO256 speech synthesiser chip. This is a relatively cheap speech chip, but is one which gives an unlimited vocabulary.

Unlike some methods of speech synthesis, the one used by the SPO256 does not require large amounts of the computer's memory in order to store a few words. In fact a dozen long sentences would probably require no more than about 1K of memory. The speech quality is

not as good as some systems, but is quite acceptable. Considering the simplicity of the system used in this method of speech synthesis, the speech quality is remarkably good.

### ALLOPHONES

There is a slight drawback in using the SPO256 speech chip, and this is simply that it is relatively difficult to program well. It produces words by stringing together a number of "allophones", which are the basic sounds of speech. For example, "shhhh", "arr", and "ow" are the sort of simple sounds that can be fitted together to make up the more complex sounds of complete words. These words, separated by pauses where necessary, can then be put together to make complete sentences, or even a number of sentences if required.

For this system to be successful you must have at your disposal all the sounds needed to make up all the words in the language. Apparently the sounds required vary significantly from one language to another, and the sounds for a particular language are called "phonemes". The SPO256 contains sixty four phonemes (including pauses) that permit any English word to be produced.

For this system to work well the allophones need to be chosen very carefully, and the obvious ones are not necessarily the ones that give the best results. However, with a little experience it is possible to put together some intelligible sentences in a reasonably short space of time, perhaps with a little "fine tuning" being needed in order to get things just right.

### SYSTEM OPERATION

The block diagram of Fig.1 shows the basic arrangement used in this speech synthesiser. The speech synthesiser chip is at

the heart of the unit, and this includes a 2K by 8 ROM that contains all the allophones. It has provision for operation with up to three external ROMs, giving a maximum capacity of 256 allophones. However, in most circuits (including this one) no external ROMs are used. There are 64 allophones available to the user, and these are selected via six address inputs.

Rather than a true audio output, the SPO256 provides a pulse width modulated output signal. In other words, the output signal is a high frequency pulse signal, with the pulse width being varied to give the required audio output voltage. A high mark-space ratio gives a high average output voltage, a low mark-space ratio gives a low average output potential, and a 1 to 1 ratio gives an intermediate average output level.

By varying the pulse width the average output voltage can therefore be made equal to the required audio output potential. In order to decode this type of signal it is merely necessary to pass it through a lowpass filter. This filters out the pulses and leaves a potential equal to the average voltage of the pulse signal. The output signal from the lowpass filter is too low to drive the audio input of the CPC computers properly, and so the signal is boosted by an amplifier before being fed to the computer.

### INTERFACING


Interfacing the SPO256 to the buses of a computer is reasonably straightforward. In order to produce a series of allophones from the chip it must first be fed with a 6-bit allophone address. Then, in order to get the chip to produce the selected allophone, a pulse must be applied to the chip's "ALD" (allophone load) input.

It is important that the next allophone is not sent to the SPO256 until it has completed the current one. Otherwise, each allophone, apart from the final one, is cut short to make way for the subsequent one, giving what is just a brief burst of noise from the loudspeaker.

The SPO256 provides a sort of "handshake" output in the form of its "LRQ" (load request) output. This is normally low, but it goes high when the chip is producing an allophone.

The flow of data can be correctly controlled by using a software routine to send an allophone address to the SPO256, wait until "LRQ" goes low, send another allophone address, monitor "LRQ" again, and so on, until all the allophones have

Fig. 1. The Amstrad CPC Speech Synthesiser block diagram.

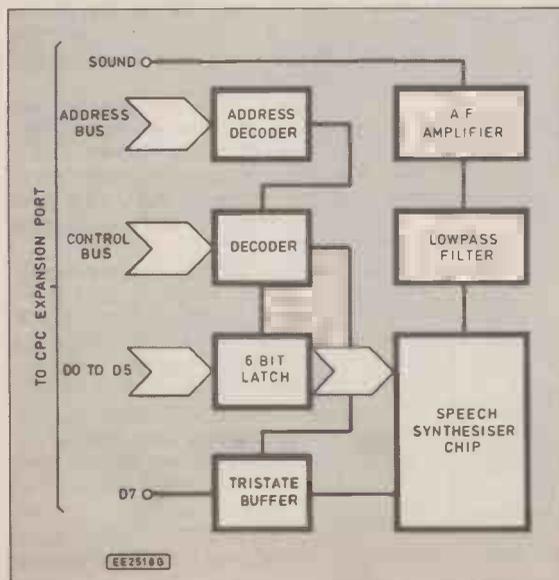

been produced. Timing loops are not really a viable alternative as the allophones have various durations from 10ms to 420ms. An accurately timed flow of data is essential if a good quality output is to be achieved.

In my experience at any rate, feeding the address inputs of the SPO256 direct from one of the computer's buses is not likely to be successful. More reliable results are usually obtained if it is fed from a latching output port. In this case it is driven from a 6-bit latching output derived from data lines D0 to D5.

The "ALD" input of the speech chip is driven from the "write" output of the address/control bus decoder circuit. Consequently, writing an allophone address to the SPO256 results in that allophone being automatically produced by the device.

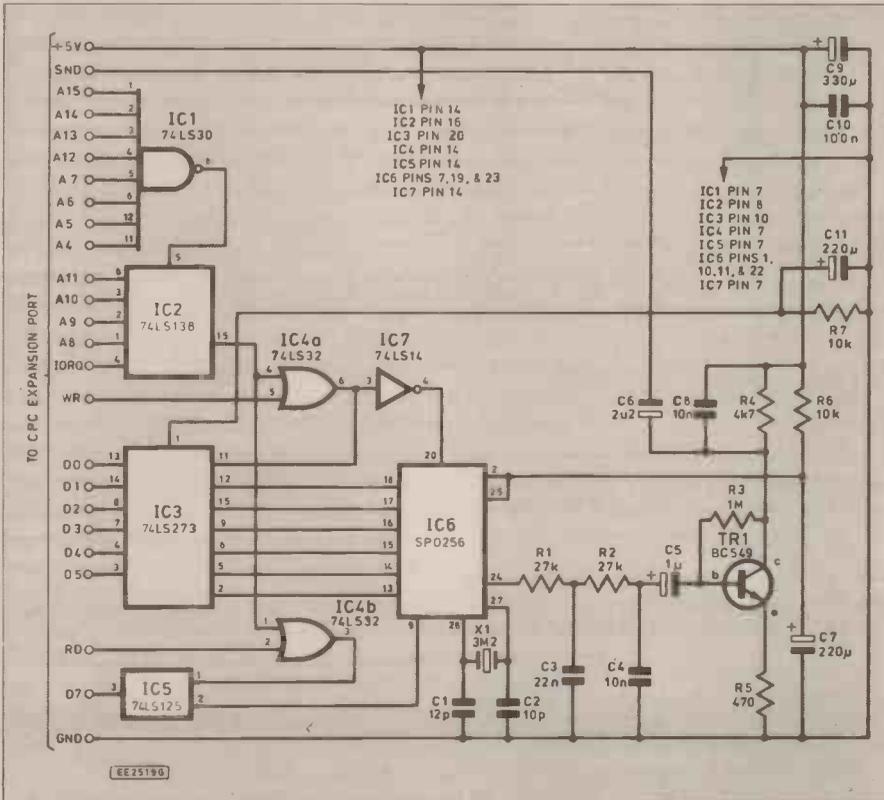


Fig. 2. Complete circuit diagram for the Amstrad CPC Speech Synthesiser.

The "LRQ" output of the SPO256 is fed to D7 of the data bus via a tristate buffer. Note that data line D6 is not required by the speech synthesiser, and that this line of the computer's expansion port is left unconnected.

## DECODING

With an unexpanded CPC464 it is possible to utilize a very simple form of address and control bus decoding, which more or less consists of activating the interface when A10, IORQ, and either RD or WR are all low. With expanded or disk based CPCs the situation is a little more tricky, and much more precise decoding is required if interactions between the user add-on and other hardware (particularly the disk drivers) are to be avoided.

In this circuit all the address lines from A4 to A15 are decoded so that the speech synthesiser is placed in the input/output map at address &F8F0. In fact it appears at "echoes" from &F8F0 to &F8FF, and can be accessed by way of any address in this range.

This range of addresses is specified as being free for user add-ons in the Amstrad CPC manuals, and there should be no danger of any conflicts between the speech synthesiser and any official Amstrad add-ons or the computer's internal hardware. However, other add-ons might use the same address range, and might not be compatible with this unit.

The address/control bus decoder provides separate "read" and "write" outputs. Address &F8F0 is therefore used for sending allophone addresses to the SPO256, and for monitoring its "LRQ" output.

## CIRCUIT OPERATION

Refer to Fig.2 for the full circuit diagram of the Amstrad CPC Speech Synthesiser. IC6 is the SPO256 speech chip, and this has a built-in clock oscillator. It requires a discrete crystal and two capacitors (X1, C1, and C2), and the clock frequency recommended by the speech manufacturer is 3.12MHz.

Crystals having this operating frequency do not seem to be very easily obtained, and I opted for a 3.2768MHz component. This is a readily available and inexpensive type intended for use in "quartz" clocks.

The increased clock frequency merely results in a slight increase in the pitch of the audio output, and a marginal increase in the speed with which words are "spoken" by the unit. Perfectly satisfactory results should be obtained using any crystal frequency from about 3MHz to 3.3MHz.

The SPO256 requires a negative reset pulse at switch-on, and this is provided by R6 and C7. The pulse code modulated output is filtered by R1/C3 and R2/C4 to leave the decoded audio frequency signal which is fed to a common emitter amplifier based on TR1. This has a large amount of local negative feedback provided by R5, and this reduces its voltage gain to about 20dB (10 times). This gives an audio output of more than adequate strength to drive the CPC's audio input. C8 provides some additional lowpass filtering which helps to give a low ripple output signal.

## ADDRESS DECODING

Address decoding is provided by IC1 and IC2. IC1 is an eight input NAND gate, and it decodes A4 to A7 and A12 to A15. The output of IC1 only goes low when all eight of these address lines are high, which is when an address which has "F" (hex) as the first and third digits is accessed.

IC2 decodes address lines A8 to A11. IC2 is a three-to-eight line decoder, but in this case only output "0" of the device is utilized. A8 is connected to its positive enable input, while A9 to A11 are coupled to its three address inputs.

Output 0 to IC2 goes low when an address having "8" (hex) as its second digit is accessed. However, the output of IC1 couples to one of the negative enable inputs of IC2, so that output 0 of IC2 only goes low when an address in the range &F8F0 to &F8FF is accessed.

This almost gives all the required decoding, but there are a couple of mild complications. One is simply that the Z80A microprocessor used in the CPC machines has separate input/output and memory maps.

The microprocessor indicates to the rest of the system that it is undertaking an input/output instruction by taking the IORQ line low. Thus, the speech synthesiser must ignore addresses in the relevant range unless IORQ is low. This is achieved by connecting IORQ to a second negative enable input of IC2.

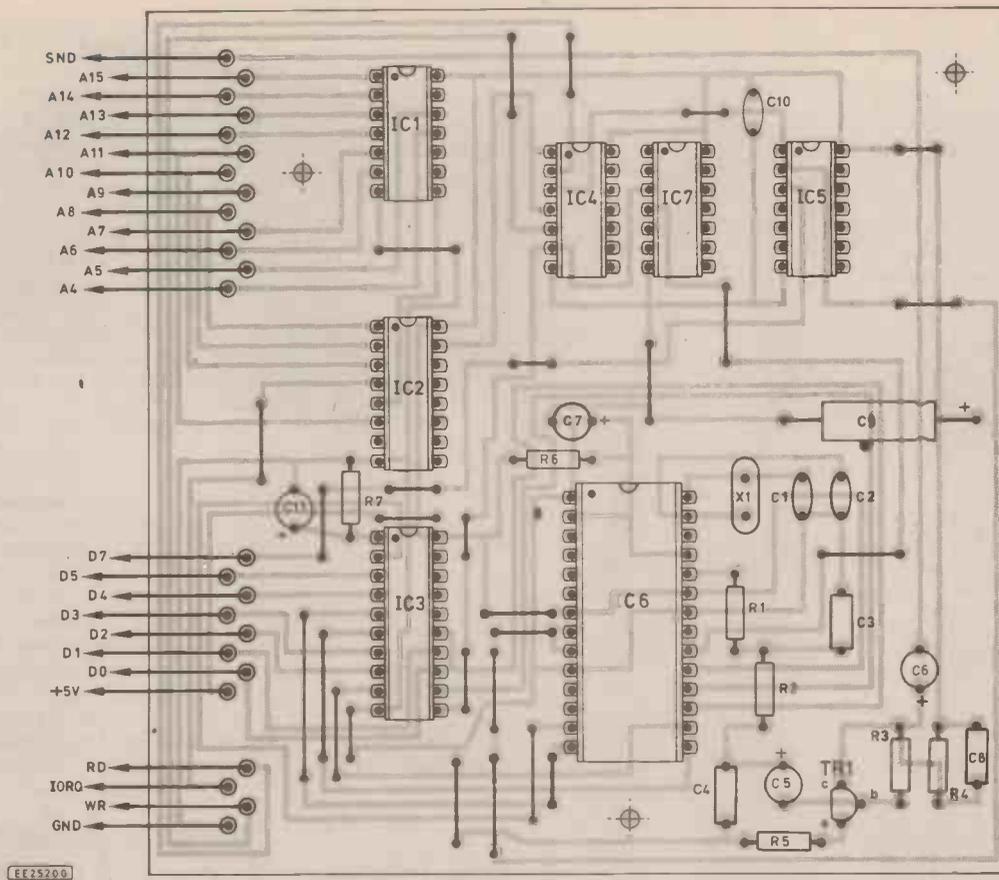


Fig. 3. (above) Printed circuit board component layout and wiring details. (below) Full size printed circuit copper foil master pattern.

The second complication is that we require separate outputs for read and write operations. This is achieved by gating the output of IC2 with the RD (read) and WR (write) lines of the CPC expansion bus, using a separate OR gate for each of these two lines. This gives a negative read pulse from IC4b, and a negative write pulse from IC4a.

A positive pulse is needed for the ALD input of the speech chip, and this is derived from the write output via inverter IC7. The six bit latching output for IC6 is provided by IC3, which is actually an octal D type flip/flop. In this case only six of the flip/flops are used, with the two "spares" just being ignored. IC4a provides a negative pulse to the "clock pulse" input of IC3 during write operations to the interface, and this latches the outputs of the flip/flops.

At switch-on a negative reset pulse is supplied to IC3 by C11. This ensures that IC3 commences with all its outputs low, and that the speech chip does not produce any output until the user activates it. R7 ensures that C11 is rapidly discharged when the computer is switched off, so that a fresh reset pulse is produced when it is switched on again.


IC5 is a quad tri-state buffer, but in this circuit only one buffer is used and no connections are made to the other three. It interfaces the LRQ output of IC6 to D7 of the CPC expansion bus, and it is set to the active state by the output pulses from IC4b during read operations to the speech synthesiser.


Power for the speech synthesiser is obtained from the +5 volt supply output of the CPC expansion port. C9 provides smoothing which helps to give a low noise level on the audio output of the unit.
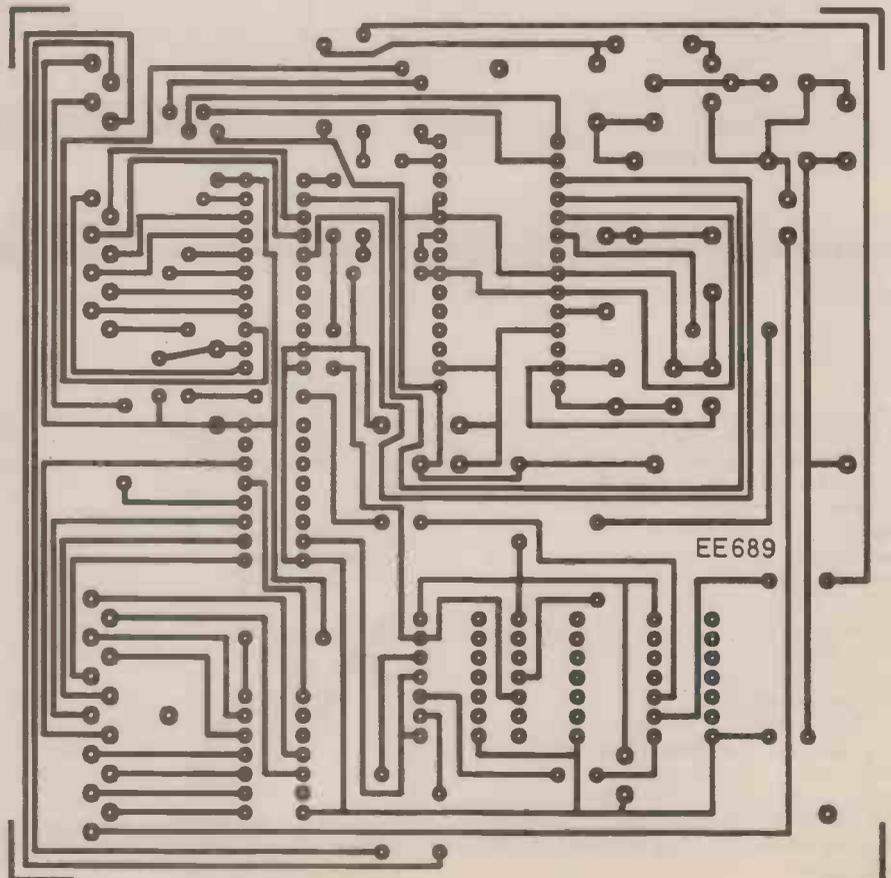
## CONSTRUCTION

Details of the printed circuit board are provided in Fig.3. Crystal X1 must be a miniature wire-ended type with 0.2 inch

lead spacing if it is to fit easily onto the board. Try to complete the soldered joints reasonably rapidly when fitting this component as some crystals are relatively easily



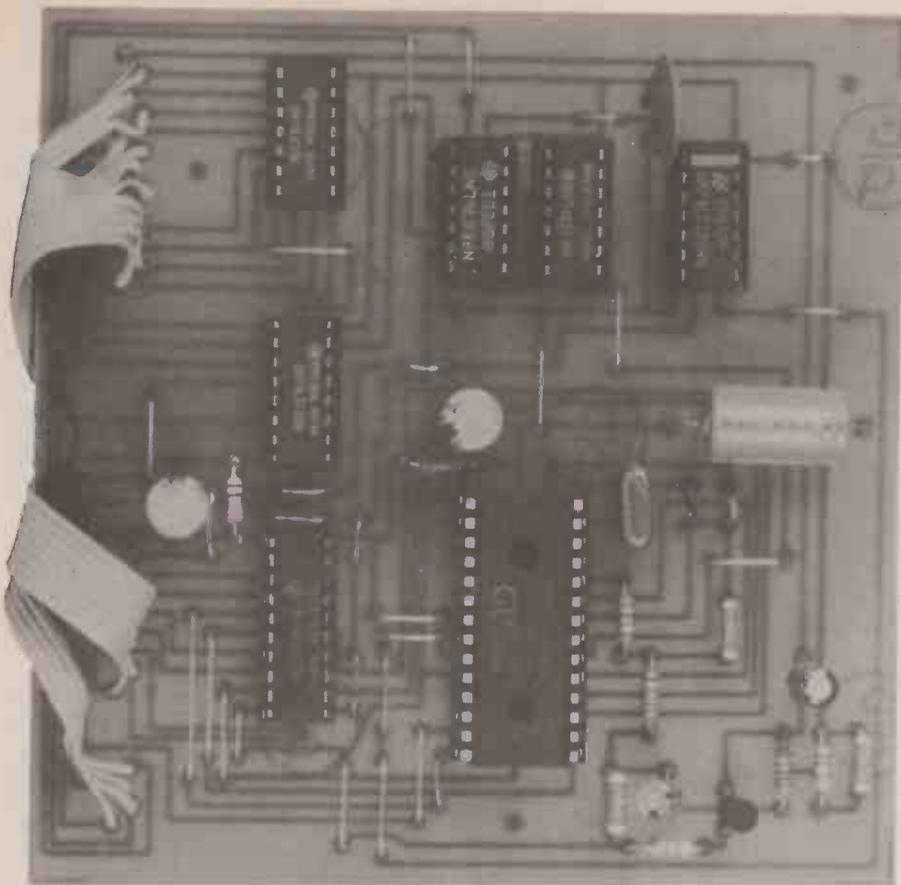

Completed circuit board showing all the i.c.s. mounted in i.c. holders.

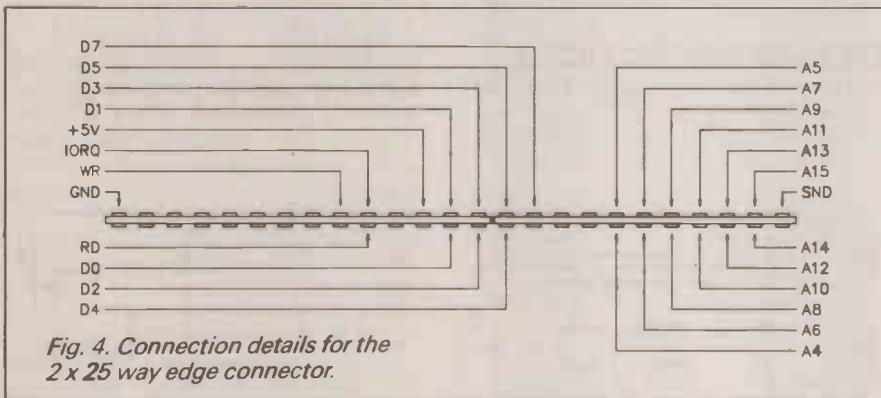


Fig. 4. Connection details for the 2 x 25 way edge connector.

damaged by heat. IC6 is a MOS integrated circuit, and as such it is vulnerable to damage by static charges.

Leave this component in its anti-static packaging until, in all other respects, the unit is finished. Then fit this component onto the board, handling it as little as possible, avoiding touching the pins and fitting it into a holder already fitted to the board so that there is no need to make any direct soldered connections to this chip.

With a fairly large integrated circuit of this type, IC6 can be a bit difficult to fit a into its socket. Usually the pins have to be carefully bent inwards slightly. Be careful not to buckle any of its pins when fitting IC6 into its socket. Although none of the other integrated circuits are static sensitive types, it is recommended that they should be fitted in holders.

There should be no difficulties in fitting the other components onto the board provided the correct types of capacitor are used. In particular, the polyester types should have a lead spacing of 7.5 millimetres (0.3 inches). Be careful to fit the electrolytic capacitors with the cor-

rect polarity. A number of link wires are required, and these can be made from 22s.w.g. tinned copper wire, or the leads trimmed from the resistors and capacitors might be sufficient.

## CONNECTIONS

The board is connected to the computer via a 25-way ribbon cable which is fitted with a 2 by 25-way 0.1 inch pitch edge connector at the computer end. At the other end it is either connected directly to the board, or via pins if preferred.

Both ends of the cable should be prepared by separating all the wires, stripping a few millimetres of insulation from each one, and tinning them all with solder. The terminals of the edge connector (or the twenty five that are used anyway) should be tinned with solder, as should the pins on the board if this method of connection is adopted.

In my experience the CPC computers are not tolerant of long connecting leads on their expansion bus. It is therefore recommended that the connecting cable should be no more than about 0.6 metres long.

The edge connector connection details are given in Fig.4. The board has been designed so that the order of the connections on the board matches up well with that of those on the edge connector. There is no need for any crossing over of wires, but you still need to be very careful to get each lead connected to the right terminal of the edge connector.

The multi-coloured "rainbow" ribbon cable is better for this sort of thing, but grey ribbon cable is usable if you take extra care. If you are using a connector fitted with the appropriate polarising key, make quite sure that you have the connector the right way up before making the connections to it.

If the connector is not fitted with a polarising key, clearly mark the top and bottom edges such as to minimise the risk of fitting it to the expansion port up-side-down. Once this wiring has been completed, check it very thoroughly at least once before connecting the unit to the computer and trying it out.

Projects of this type are often left as uncased boards, as was the prototype. However, it should not be difficult to fit the unit into a small plastic case if preferred. This does have the advantages of being a bit neater, and keeping dust etc. off the circuit board.

## COMPONENTS

### Resistors

R1, R2	27k (2 off)
R3	1M
R4	4k7
R5	470
R6, R7	10k (2 off)

All 0.25W 5% carbon

### Capacitors

C1	12p ceramic plate
C2	10p ceramic plate
C3	22n polyester (7.5mm pitch)
C4, C8	10n polyester (7.5mm pitch) (2 off)
C5	1µ radial elect. 63V
C6	2µ2 radial elect. 63V
C7, C11	220µ radial elect. 10V (2 off)
C9	330µ axial elect. 10V
C10	100n disc ceramic

### Semiconductors

IC1	74LS30 8-input NAND gate
IC2	74LS138 3-to-8 line decoder
IC3	74LS273 octal flip/flop
IC4	74LS32 quad 2-input OR gate
IC5	74LS125 quad tristate buffer
IC6	SP0256 speech synthesiser
IC7	74LS14 hex inverting trigger
TR1	BC549 silicon npn

### Miscellaneous

X1	3.2768MHz miniature wire-ended crystal (see text)
----	---

Printed circuit board available from the EE PCB Service, order code EE689; case (see text); 2 x 25 way 0.1 inch pitch edge connector; 25 way ribbon cable; 14 pin d.i.l. i.c. holder (4 off); 16 pin d.i.l. i.c. holder; 20 pin d.i.l. i.c. holder; 28 pin d.i.l. i.c. holder; connecting wire; etc.

Approx cost.  
Guidance only

**£20**

## IN USE

With any add-on project that connects to a computer's buses it is essential to connect it to the computer *prior* to switch-on. Otherwise the computer is likely to crash when the add-on is connected, and the computer and (or) add-on could be damaged. Once switched on, the computer should go through its start-up routine in the normal way. Switch off at once and recheck all the wiring if there is any hint of anything out of the ordinary at switch-on.

To test the unit you can try this example program, which should result in the speech unit saying a couple of words that will be familiar to all readers!

### 5 REM SPEECH ROUTINE

```
10 READ a
20 OUT &F8F0,a
30 IF a = 64 THEN END
40 WHILE INP(&F8F0) > 127
50 WEND
60 GOTO 10
70 DATA 7, 7, 35, 52, 19, 0, 33, 20, 3, 19,
45, 7, 42, 17, 39, 24, 11, 12, 41, 55, 64
```

Line 10 reads data from line 70, and at line 20 each read value is sent to the speech synthesiser. Line 30 is used to detect the end of the speech data, and terminate the routine.

This is achieved by using a number of 64 as the last allophone value. This value is sent to the speech unit, but as it does not respond to the two most significant bits, the value it is sent is effectively zero. This is important, because most of the allophones do not cut off after the appropriate length of time, but will continue indefinitely if allowed to do so. Using 0 as the last allophone address finishes the sequence of allophones with a short pause, and ensures that there is then silence from the speech unit until it is activated again.

A WHILE...WEND loop at lines 40 and 50 halts the progress of the program until

the current allophone has been completed. The test used is whether or not the value returned from the speech unit is greater than 127. It must be more than 127 while an allophone is being produced, since D7 will be taken high by the status output of the SPO256, giving a returned value of at least 128. However, once an allophone has been completed, and D7 is taken low, the returned value can be no more than 127. Logic ANDing could be used to mask D0 to D6, but the method used in the demonstration program is probably faster and easier.

The allophone values used in the example program are the obvious ones, and they give reasonable results. In some cases the obvious allophones give something far removed from the desired result, but a little experimentation will often resolve matters.

Sometimes what may seem like a sound that requires just one allophone needs to be put together from two or even three allophones. The accompanying list of allophones, addresses (in hex and decimal),

plus example words to clarify the sounds they produce, should aid the selection of likely allophones for your own phrases.

## ALLOPHONE ALTERATION AND USE

Note that in most cases you cannot produce elongated versions of allophones simply by using the same one two or three times in succession. In most cases this just gives a sort of echo effect. It is possible with some though, as indicated in the list.

With a few of these it is acceptable to duplicate them at the beginning of a word, but not if they are used at the end or in the middle. However, I am only giving guidelines rather than rigid rules here. It does no harm to experiment a little, and the invalid use of allophones sometimes gives the best results.

In a number of instances there are what seems to be duplications of allophones. This is where the lengths of the sounds and the emphasis is different. In general, it is the longer and "harder" versions of sounds that are used at the beginnings of words, with shorter and "milder" versions being used at the end or in the middle.

The example words indicate the normal position in a word that each allophone should occupy, although I must again emphasise that there are no hard and fast rules here. Where there are alternative sounds, it is worthwhile trying them all to determine which one sounds best.

Some of the shorter and "sharper" sounds work best if they are preceded by silence. As many of these are often used at the beginnings of words, this preceding silence will be provided anyway. However, where necessary a strategically placed brief pause (allophone 0 or 1) will improve results. The sounds which benefit from this are the B, D, and G ones (which only need short pauses), and the P, T, and K ones (which require longer pauses, possibly even allophone 2 instead of 1).

Pauses in general tend to be problematical. There is a natural tendency to assume that there are short pauses between words, longer ones between sentences, and no pauses anywhere else. In fact there are often few pauses between words, and some in between syllables of the words that do not easily trip of the tongue. When selecting pauses, or any allophones come to that, you should think in terms of what the phrase sounds like, rather than how it appears in written form. □

TABLE 1: List of Allophones, their addresses and sample words

Dec Address	Hex Address	Allo- phone	Example Word	Dec Address	Hex Address	Allo- phone	Example Word
0	0	PA1*	10ms pause	32	20	AW	OUr
1	1	PA2*	30ms pause	33	21	DD2	Down
2	2	PA3*	50ms pause	34	22	GG3	fiG
3	3	PA4*	100ms pause	35	23	VV	VerticAl
4	4	PA5*	200ms pause	36	24	EG1	GUest
5	5	OY	boY	37	25	SH	SHone
6	6	AY	frY	38	26	ZH	aZure
7	7	EH*	End	39	27	RR2	tRain
8	8	KK3	Come	40	28	FF*	Find
9	9	PP	Poster	41	29	KK2	sKy
10	A	JH	dodGe	42	2A	KK1	Can
11	B	NN1	tiN	43	2B	ZZ	Zoo
12	C	IH*	plT	44	2C	NG	bANk
13	D	TT2	Top	45	2D	LL	Love
14	E	RR1	Rattle	46	2E	WW	Wood
15	F	AX*	sUcceed	47	2F	XR	Rain
16	10	MM	Mint	48	30	WH	WHere
17	11	TT1	porT	49	31	YY1	Yell
18	12	DH1	THem	50	32	CH	CHoose
19	13	IY	sEA	51	33	ER1	fIR
20	14	EY	cAge	52	34	ER2	buRR
21	15	DD1	shoulD	53	35	OW	bOW
22	16	UW1	io	54	36	DH2	THey
23	17	AO*	tAUght	55	37	SS*	veSt
24	18	AA*	IOt	56	38	NN2	Now
25	19	YY2	YEs	57	39	HH2	How
26	1A	AE*	tAp	58	3A	OR	sORe
27	1B	HH1	Hat	59	3B	AR	aLARm
28	1C	BB	BUsy	60	3C	YR	reaR
29	1D	TH*	THen	61	3D	EG2	Got
30	1E	UH*	bOOk	62	3E	EL	saddLE
31	1F	UW2	bOOt	63	3F	BB2	Bottle

Where allophones are marked with a "\*" it is possible to use the same one two or more times in a row in order to give an elongated version of the sound.

A selection of products from our **BARGAIN LISTS**: Ring or write for a free copy of our latest list + 32 page Spring Supplement.

**Z4295** Error Correction Card, made by Tulse-data Ltd, this 130x86mm board contains a 80C85A microprocessor, 82C51x3, 5864-15, 2764-15, + 9 other chips, a 10 way DIL switch R's C's etc... There's a 14 way ribbon cable to a small PCB with 2x1489. Originally cost over £70.00. Our low price £10.00

**Z4300** Nice panel 330x170mm with 3 chunky heatsinks 47x36x32mm, each with TO220 voltage reg. Also 56x74 series IC's including L+LS, 3x40W IDC plugs, few tants etc... Attached to the board are 2x0.5 metre long twisted and flat ribbon cables terminated in 50 way IDC sockets. £4.00

**K575** Plastic Power Pack, mainly TO126 & TO220 transistors, SCR's, Triacs etc. All new full spec marked devices offering fantastic value. Lots of TIP & BD types. 50 for £7.50

**Z4299** Hourmeter. This has a 12-24V quartz movement and measures to 99999.99 hours (11 and a half years!). Face 52x52mm, depth 50mm. £4.60

**Z8884** Acoustic coupler for use with Liberator. Made by Sendata, 700F series. One end has PCB with lots of chips plus 4xAA Nicads to power. Other end has socket to take mains power supply (supplied). Also included is a communications cartridge and a comprehensive 46 page manual. New. £20.00

**Z4279** Interesting little panel (75mmx40mm) with 16 position BCD channel switch (24 pins), two dual green seven seg displays, two min keyboard switches, and a short a 4093. Attached by a short length of ribbon cable is a second panel (same size) with 4518, 4019 and two x 5068 chips. Supplied with circuit. Only £2.20

### KEYBOARDS



**Z8852** Keyboard: Superb brand new keyboard 392 x 181 with LCD displaying 1 line of 10 characters and a further line with various symbols. 100 keys, inc. separate numeric keypad. Chips on board are 2 x 74HC05, 80C48. LCD + driver chips are easily removable from board. £15.00

**Z8857** High quality Alphanumeric keyboard on aluminium frame 314 x 150mm. Contactless keys good for 20 million operations. Originally sold at over £100 each, they were used in a 'Printoom' portable terminal. Fully ASCII encoded output. Power supply +5V and -12V @ 35mA. Supplied with comprehensive data. £14.95

**Z8856** Cherry computer keyboard. Very slim model 340 x 130 by only 14mm deep, including keys. Matrix output. 67 keys in pale/dark brown. £4.00

**Z8863** Keyboard. High quality unit made by Micro Switch. 69 pale grey and blue keys. 6 red 5mm LED's, 15 various LS chips and socketed D8048 by Intel. Output via 7 way plug and there is a 4 way edge connector too. Keyboard frame is 317 x 128mm. PCB on which it's mounted is 285 x 170mm. Price..... Excellent value at £12.00

### DISPLAYS

**Z4243** Display panel 152 x 112mm with NEC 8 digit display (Z1731); 8279-5, MC146818, 3 x uPA80C, & a couple of LS chips, crystal, etc. £2.90

**Z1731** NEC Vacuum Fluorescent Display FIP8B11. 8 digit multiplexed output 10mm high. Heater voltage 2V, grid/anode voltage 24V. £2.00

**Z4115** 8 digit 12.7mm high LCD and holder. These are 14 segment devices allowing alphanumeric display. Normally costing over £15.00 we are offering these for just £4.50

**Z4148** LCD as Z4115 but 6 digit, 50 pins. Like RS588-601. Their price 10.86. £3.00

**Z1732** Epson LCD 4 digit 8mm high. £2.00

**Z1637** LCD Display - Direct drive 3 1/2 digit similar to RS 588-572. 12.7mm high digits. Op voltage 4-12 RMS @ 32Hz typ. Supplied with data. £2.00; 10+ / £1.75; 25+ / £1.50; 100+ / £1.00

**Z1560** 7 seg display, 20mm high. Common anode. Only 70p! 25+ / 50p; 100+ / 42p

**DL1416** Alphanumeric 4 character intelligent display 0.16" £7.00

**DL3416** 4 digit intelligent alphanumeric display with built-in drive and memory. ASCII ROM and multiplexing circuitry. TTL compatible inputs. +5V. Supplied with data. List price £41.50. £8.00

# 1990 CATALOGUE

128 PAGES OF ELECTRONIC COMPONENTS AND EQUIPMENT. HUGE RANGE! AMAZING VALUE! DON'T MISS OUT - GET YOUR COPY NOW - ONLY £1.50 POST FREE!!!

## HIGH QUALITY TEST EQUIPMENT

HITACHI OSCILLOSCOPES FOR QUALITY AND VALUE



**V223** DC-20MHz, dual Channel, single time-base delayed sweep, DC offset, alternate magnifier, 6in screen, 5mV/div vert. sensitivity 0.2µs/div-0.2s/div sweep time. Complete with 2 probes, manual, mains lead. £475 Other models from £339 - full details in catalogue. Ask for colour brochure.

### METEX METERS

8 different models in our catalogue!

- ★ 4 1/2 digit 12mm LCD display
- ★ 30 ranges incl 20A ac/dc
- ★ Frequency counter
- ★ Capacitance test with zero adjust
- ★ Data hold switch
- ★ Diode test
- ★ Transistor test
- ★ Continuity test M4650
- ★ Test leads with 4mm plugs £94.00
- ★ Rugged yellow case
- ★ Carrying case



Battery and instruction manual included. AC volts 0-200m-2-20-200-750Vac ±0.5% DC volts 0-200m-2-20-100-1000Vdc ±0.5% AC current 0-2m-200m-20Aac ±1.0% DC current 0-200µ-2m-200m-20Aac ±0.5% Resist 0-200 2k-20k-200k-2M-20MΩ ±0.15% Capacitance 0-20p-200n-20µF ±2.0% Frequency 0-20k-200kHz ±2.0% Transistor hFE 0-1000 NPN/PNP Dims 176 x 90 x 36mm

### FREQUENCY COUNTER



**FC5250** 7 digit frequency counter for frequencies between 10Hz and 150MHz. Power on/off, x1/x10 gate time and VHF/HF switches. Inputs via BNC sockets. Supplied complete with instruction manual and test lead. Requires an external 9Vdc nom 200mA power supply. Price..... £65.00

DIGITAL CAPACITANCE METER



**CM3300** High accuracy AUTORANGING 3 digit capacitance meter. High resolution measurement in the range 0.1pF to 99900µF with 10 auto ranges. Range hold switch for batch testing capacitors. Range zero control. Inputs via spring terminals or test leads (supplied). Complete with leads and instruction manual. Price..... £65.00

## GREENWELD ELECTRONIC COMPONENTS

All prices include VAT; P&P £2.00 per order. Min Credit Card £5. No CWO min. Official Orders from Education welcome & min invoice charge £10.00. Our shop has enormous stocks of components and is open from 9-5.30 from Mon-Sat. Come and see us!

HOW TO CONTACT GREENWELD: By Post: Use the address below: By Phone: (0703) 772501/783740 (ansaphone out of business hours): By Fax: (0703) 787555: By Email: MAG36026: By Telex: 94081101 GWELD Payment is accepted by cheque, postal order, cash inc. foreign currency bank notes/book tokens/Access/Visa/Connect.

443D MILLBROOK ROAD, SOUTHAMPTON, SO1 0HX.

### AF GENERATOR/COUNTER



**AG2603AD** A combined audio frequency signal generator and frequency counter. A six character LED display allows direct reading of internally generated signal or signals from an external source. The frequency generator has a range of 10Hz to 1MHz with either square or sine waveforms and adjustable output level. The frequency counter has a range of 10Hz to 150MHz. Frequency range controlled by a 5-step selector and fine control. Adjustable output level with 0/20/40dB attenuator.

### AUDIO GENERATOR

Frequency range ..... 10Hz to 1MHz  
Output impedance ..... 600Ω unbalanced  
Output control ..... 0-20-40dB and fine adjuster  
Output control:  
Sine ..... 8V rms max square ..... 10V p-p max

### FREQUENCY COUNTER

Frequency range ..... 10Hz to 150MHz  
Input voltage ..... Less than 50mV  
Max input voltage ..... 3V  
Input impedance:  
High frequency ..... 1MHz VHF ..... 50Ω  
Power ..... 240Vac 50Hz  
Dims ..... 215 x 150 x 200mm  
Price ..... £175.00

### RF GENERATOR/COUNTER

Similar in appearance to above with same frequency counter. Spec:

Frequency range ..... 100kHz to 150MHz  
RF Output ..... 100mV rms (up to 35MHz)  
Output control ..... 0/20dB and fine adj.  
Modulation ..... Internal 1kHz, external 50kHz-20kHz at less than 1V rms  
Price ..... £179.00

## AMSTRAD SPEECH SYNTHESISER

As featured in this month's issue!

All components inc. PCB, edge conn., etc., for just **£10.95!**

+ FREE! An extra SP0256 chip with every kit!  
Suitable Case **£3.00**  
SP0256 Speech Chip **£2.50**

### SIGNAL TRACER/INJECTOR



**Y133** For fault finding on Audio & RF Equip, VU meter and speaker. Level controls, 0-60dB atten. switch, I/P, O/P, ext spkr, and injector skts on Front panel. Size 200x140x96mm. Uses PP3. £55.00

## MSDOS PACK


- Z4305** Epson PCe disk pack  
Contents:  
1) 364 page MSDOS 3.20 reference manual showing all commands, etc.  
2) 100 page book "Everyday with MS-DOS" - an excellent introduction, starting from basics.  
3) 95 page book "Setting up and getting started".  
4) 61 page book "Diagnostics Users Guide".  
5) Pack of 3 5.25" disks - 2 MSDOS 3.20 system/utilities disks and a system dependent utilities disk.

All books are spiral bound. Everything brand new in original carton.

Cost new £55. Our price **£10.00**

### POWER SUPPLIES

#### (a) SWITCH MODE

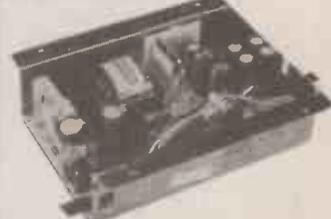

#### ASTEC Model AA12531

I/P: 115/230V ac 50/60Hz. O/P: V1 + 5V 5A; V2 + 12V 0.15A. Size: 160 x 104 x 45mm. Partially enclosed panel with fixing holes in steel case on 120 x 125mm centres. Inputs and Outputs are on colour coded leads; there is also an EEC socket on a flying lead. £6.95

#### Z660 Astec switched mode PSU Type AA7271.

This small PCB, just 50 x 50mm will accept 8-24V input and give a stable 5V DC at up to 2A output. The 6 transistor circuit provides current overload protection, thermal cut-out and excellent filtering. Offered at the remarkably low price of just £5.00

#### (b) CONVENTIONAL

**Z4215** Siliconix mains input, 4.5V DC 150mA output to 3.5mm jack plug on 2m lead. Built-in continental 2-pin plug. Size 62 x 46 x 35mm £1.50

**Z4170** Plug in power supply. Built in 13A plug. Output 6V DC 300mA on 2m long lead terminated in a 3mm power plug. British made to BS415 £1.50

**Z4208** Onic Power Supply. Moulded plastic case with built in 13A plug. Output 9Vdc at 600mA delivered to 2m lead with 2.5mm power plug £3.50

### BREADBOARDS

FREE, if requested, with every breadboard sold this month! K574 wire link pack with about 250 links for use with breadboard or PCB's!

#### PROTOBLOC 1

G708 Protobloc 1 has a total of 400 tie points consisting of two sets of 30 rows of 5 interconnected sockets plus 4 rows of interconnected sockets running alongside, suitable for use as power supply rails. All contact positions are clearly defined on an alphanumeric grid. ABS polymer board mounted on an adhesive foam base. Will accommodate up to three 16 pin devices. An ideal introduction to solderless circuit development systems. Size 80 x 60mm. £2.50

#### PROTOBLOC 2

G711 Protobloc 2 has a total of 840 tie points. Will accommodate up to seven 16 pin devices. Size 172 x 64mm £3.95

#### PROTOBLOC 2A

G712 As above, but mounted onto a rigid base plate complete with three 4mm terminals for power connections. A mounting bracket which clips into the base is also provided to accept a variety of components including switches and potentiometers, etc. Price..... £8.95

#### PROJECT BOARD GL24

G724 2 of type G711 mounted onto a rigid baseplate with 3 coloured terminals, for power connections. Overall size 225 x 150mm. Price..... £13.95

#### PROJECT BOARD GL36

G736 3 of type G711 and an additional strip of 100 tie points mounted onto a rigid base plate with 4 coloured terminals. Overall size 242 x 195mm. Price..... £19.95

# ELECTRONIC BAROMETER

OWEN N. BISHOP

*How to become your local Ian McCaskill and confound the experts.*

**T**HIS article describes how to build an instrument for measuring atmospheric pressure and how to use it for making forecasts of local weather conditions. It is based on the cheapest of the electronic pressure sensors currently available.

Readings are in millibars, over the range 950mb to 1050mb; with a precision of 2-3mb. This covers the whole normal range of atmospheric pressure. The Electronic Barometer has a memory circuit to retain the value of the previous pressure reading.

## MEASURING PRESSURE

There are several units that are used for expressing atmospheric pressure. The oldest reliable technique for determining atmospheric pressure is to measure the height of the column of mercury in a mercury barometer. The height is usually expressed in inches, centimetres or millimetres. On these scales, atmospheric pressure is in the region of 30 inches or 76cm of mercury. Barometers of the aneroid pattern are often graduated on these scales, even though they work on entirely different principles and they have no mercury column.

Pressure may also be measured in pounds per square inch. This unit was more often used in engineering than in everyday

life, though you may occasionally find a pressure-cooker with a gauge graduated in this unit. Average atmospheric pressure is about 14.7lb/in<sup>2</sup>.


Nowdays all these units have been largely replaced by the scientific unit of pressure, the Pascal (Pa). A Pascal is a pressure of one Newton per square metre. On this scale, average atmospheric pressure is about 100000Pa, or 100kPa.

However, in meteorology, the Pascal has not replaced an earlier pressure unit, the Bar. A pressure of one bar is equivalent to a pressure of 100kPa. Average atmospheric pressure is thus about one bar.

For convenience, atmospheric pressure is usually expressed in thousandths of a bar, or millibars. This is the unit used on the daily weather maps in the newspapers and on TV. This is the unit shown on the display of the Electronic Barometer.

Atmospheric pressure at a given location varies continuously, and this variation is usually associated with changes in the weather. At sea level, the pressure is unlikely to fall below 950mb. Pressure can fall lower than this during severe hurricanes but, with buildings collapsing around them, nobody is likely to be interested in reading barometers at such a time. Similarly, there is an upper limit of pressure at sea level which is about 1050mb.

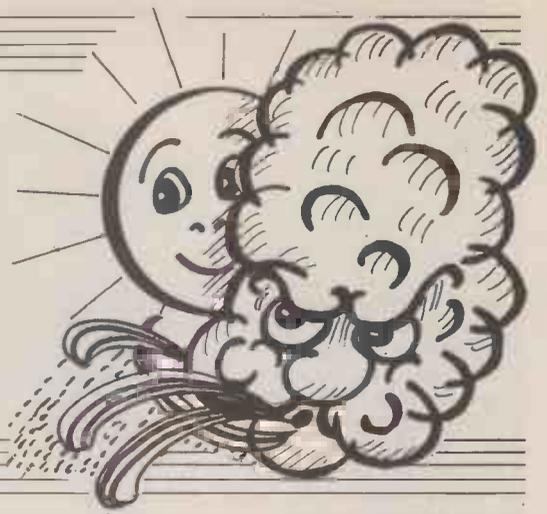If you live on a hill or a mountain, pressures are lower than those at sea level. This



is because, as we go higher, there is less atmosphere above us. In addition, the density of the atmosphere decreases with altitude.

The reduction of pressure with altitude is therefore a complicated relationship. At lower altitudes, pressure falls by approximately 0.12mb for every metre above sea level. Thus pressures are 30mb lower at 250m above sea level.

You may need to take this into account when comparing readings taken with the barometer against pressures shown on weather maps, since the latter are usually corrected to what they would be at sea level. If you need to, it is easy to set the barometer to operate over a slightly lower range of pressures to allow it to be used at altitudes above sea level.

For weather-forecasting, the most important information a barometer provides is whether the pressure is relatively high or low, whether it is rising or falling, and whether it is changing rapidly or slowly. The exact level is not so important. If you intend to use the Electronic Barometer for local forecasting, it is unnecessary to calibrate it precisely or to allow for your height above sea level.


## PRESSURE SENSOR

The pressure sensor used in this instrument is the Motorola MPX100A. Its action depends on a piezo-electric transducer, with a reference vacuum on one side of it and atmospheric (or other) pressure on the opposite side. Differences of pressure on either side of the transducer cause strain, resulting in a difference of potential across the transducer.

This potential difference appears across the two output terminals of the device ( $V+$  and  $V-$ ) and is referred to as the output ( $V_{out}$ ) of the transducer. The difference of potential (or output) is linearly related to the difference in pressure. Typically, a pressure difference of 1000mb gives an output of 60mV.

Unfortunately there are some complications that must be overcome before this output can be used as an indicator of pressure. When the pressure difference is zero (0mb on both sides of the transducer) the output is about 10mV. This *offset voltage*, has to be subtracted from the output voltage before the pressure can be calculated.

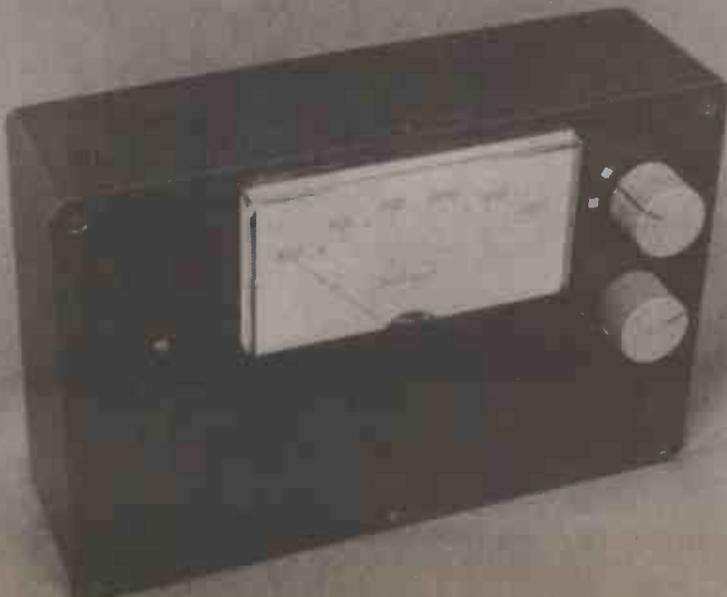Another complication is that the output voltage is dependent not only on pressure but on temperature. Typically the output drops by 0.19 per cent for every degree Celsius rise in temperature.



This may not sound much but it must be remembered that, when measuring atmospheric pressure, we are concerned only with relatively small variations of pressure. A temperature rise of, say, 10°C causes a drop of output of 1.9 per cent. In terms of pressure, this is equivalent to an error of 19mb in 1000mb.

As we are concerned with measuring pressure over a range of 950mb to 1050mb, a range of 100mb. Over this relatively small range an error of 19mb is very serious. A change of temperature due to a change of weather conditions could easily swamp any corresponding change in pressure rendering the readings of the instrument useless.

Temperature-compensated sensors are available but these are far more expensive than the MPX100A. One method of compensating for temperature with the MPX100A is by using suitable circuits incorporating a temperature sensor. This is not as easy to do, since the offset voltage is also temperature-dependent. Adjusting the circuit using this method becomes complicated.

The output from the sensor ( $V_{out}$ ) is passed to a chain of three operational amplifiers which perform the calculations necessary to convert it into a voltage ( $V_C$ ) suitable to drive the meter. The prototype uses a 50 $\mu$ A f.s.d. meter, with a series resistor to convert it to a 1V f.s.d. (approx.) voltmeter. The calculation performed by the circuit must therefore have three stages:

- 1) Find  $V_{out}$ , using an amplifier as a subtractor, to subtract  $V_-$  from  $V_+$ . The result is  $V_A$ , which is very close to  $V_{out}$ , but may include small errors due to tolerances in components and the input offset voltage of the amplifier. The circuit compensates for these error at the next stage.
- 2) Add an offset voltage to compensate for the offset output of the pressure sensor at zero pressure (about 10mV), and for any small offset errors in the operational amplifiers. We also need a large offset voltage to allow for the fact that, when the pressure is 950mb, the output to the meter is to be zero. The total offset required is in the region of -67mV,

The following table shows the voltages at the two ends of the pressure range:

	Low end	High end	Difference
Pressure (mb)	950	1050	100
$V_A$ (typical, mV)	67	73	6
$V_B$ (mV)	0	-6	-6
$V_C$ (mV)	0	1000	1000

To sum up, the equation that these amplifiers have to solve is:

$$V_C = 167(V_A - 0.067) \text{ volts}$$

Individual sensors vary to the extent that  $V_A$  may increase only 4.5mV or as much as 9mV for pressure increase of 100mb, so it must be possible to adjust the gain anywhere between 111 and 222.

## MEMORY

As already mentioned, it is important to know whether and how fast the pressure is rising or falling. The old-fashioned aneroid barometer usually has a pointer mounted on its front glass, that can be turned

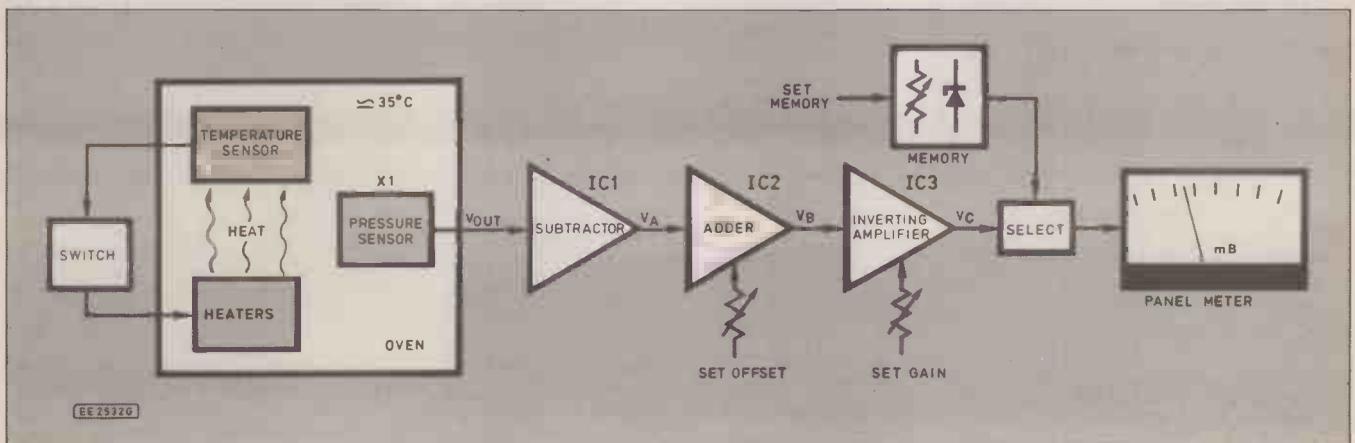


Fig. 1. System block diagram for the Electronic Barometer

In our instrument we adopt a much simpler technique. The sensor is enclosed in a "oven" in which it is held at constant temperature by a simple thermostat circuit. This eliminates the need for temperature compensation.

A third source of error is hysteresis. The effect of this is that, if pressure is increasing, the output for a given pressure is higher than it would be if pressure was decreasing.

Fortunately, this effect is manifest only for relatively large changes of pressure. When measuring atmospheric pressure we are dealing with only small pressure changes and hysteresis can be ignored.

Another factor that must be taken into account is that the magnitude of the output depends on supply voltage. In this circuit we regulate the supply voltage at +5V.

## HOW IT WORKS

The system block diagram, Fig.1, shows the pressure sensor enclosed in its oven. There it is held at a constant temperature of about 35°C. The exact temperature does not matter provided that it is constant and that it is slightly higher than any temperature that the instrument may become exposed to during normal operation.

Owing to the heat generated by the transformer and circuit components, the temperature inside the instrument case will be a few degrees above room temperature. The temperature in the oven must be a few degrees above that.

though we must be able to allow for manufacturing tolerances when setting up the circuit.


Addition is performed using an operational amplifier connected as an adder, with output  $V_B$ . Since the adder also inverts the sum, the output of the second amplifier is a negative voltage.

3) Amplify  $V_B$  so that while  $V_B$  changes from 0V to -6mV, the input to the panel meter increases from 0 to 1V. For this we need an operational amplifier connected as an inverting amplifier with a gain of 167. The output of this amplifier is referred to as  $V_C$ .

manually to set it to the present pressure. On returning a few hours later, it can be seen what pressure change has occurred since the pointer was last set.

We have a similar facility in the Electronic Barometer. A variable potential divider is connected to the panel meter in place of the operational amplifier chain. The potential divider receives a stabilised voltage of 1.26V from a band-gap voltage reference.

The potential divider is adjusted manually until the meter shows the same reading as is currently being obtained from the amplifiers. The potential divider thus acts as a memory. When the barometer is

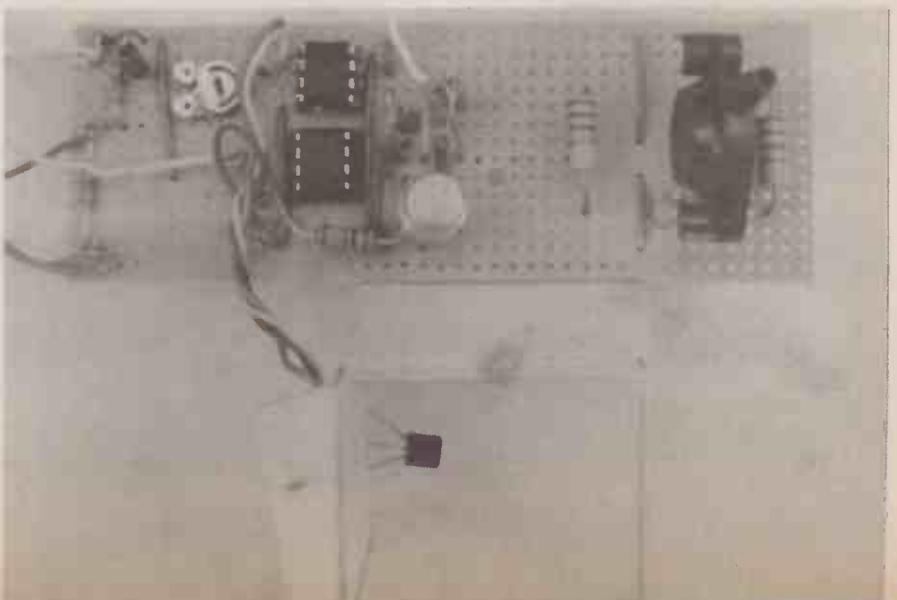

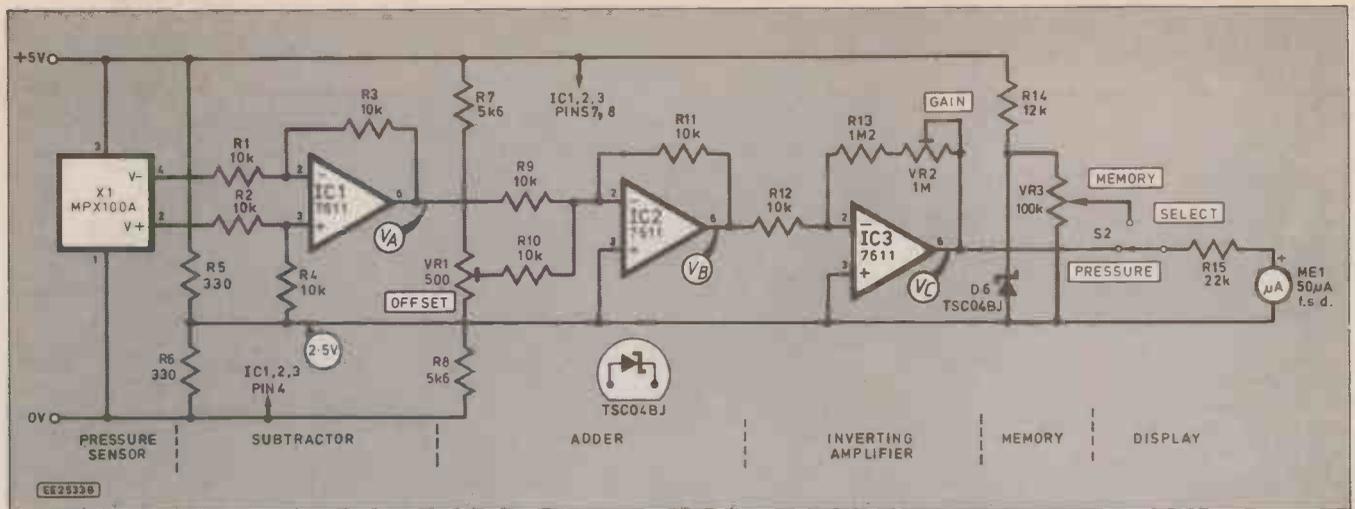


Fig. 2. Pressure-sensing and amplifying circuit diagram for the Electronic Barometer

next used, the reading from the potential divider will not have altered and may be compared with the new reading obtained from the amplifiers.

### CIRCUIT DETAILS

The pressure-sensing and amplifying circuit for the Electronic Barometer is shown in Fig.2. IC1 calculates  $V_A$ . IC2 adds this to the voltage at the wiper of potentiometer VR1. This preset resistor is adjusted so that the voltage at its wiper is  $-67\text{mV}$ , or whatever value is needed to produce the required offset. A multiturn preset potentiometer is used for VR1, so as to allow this voltage to be set precisely.

The output  $V_B$  from IC2 is the invert of the sum,  $-(V_A - 0.067)$ . IC3 amplifies and inverts  $V_A$ . For a "typical" sensor, VR2 is set so as to make the total of VR2 and resistor R13 equal to  $1.67\text{M}$ , giving a gain of 167. Thus the output  $V_C$  is  $167(V_A - 0.067)$ .

The output from IC3 passes through switch S1, and resistor R15 to the positive terminal of the panel meter. Since all voltages are referenced to the 2.5V line (Fig.2) the negative terminal of the meter is connected to this line.

The meter used in the prototype was a microammeter with  $50\mu\text{A}$  full scale deflection (f.s.d.). Resistor R15 converts it to a voltmeter with a f.s.d. of approximately 1V.

When 1V is applied, the current through the combined resistance of R15 and the meter coil ( $1.5\text{k}$ ) is  $42\mu\text{A}$ . Thus the voltage required for f.s.d. is a little more than 1V in practice. This discrepancy is taken care of by slightly increasing the gain of the inverting amplifier (IC3). Thus there is no need to use an expensive precision resistor for R15.

If you have a ready-made 1V f.s.d. voltmeter, use this instead and omit R15. If you have a microammeter with a different f.s.d., calculate the value of R15 from:

$$R = 1/(\text{f.s.d.}) - \text{resistance of meter coil.}$$

### ANCILLARY CIRCUITS

The thermostat circuit for the oven appears in Fig. 3. The sensor gives an output voltage of  $0.01\text{V}$  for each degree Celsius, above  $0^\circ\text{C}$ . IC5 compares this with a standard voltage set by preset VR4.

For a temperature of  $35^\circ\text{C}$ , the voltage at the sensor output is  $0.35\text{V}$ . If the wiper of VR4 is set to produce the same voltage, the

output of IC5 rises every time the temperature falls below  $35^\circ\text{C}$ . This turns on transistor TR1 and current flows through R18 and R19.

These resistors are rated at  $0.5\text{W}$  and act as the heater elements. Note that the resistor current comes from a 12V source, so increasing the heating effect. This circuit maintains the temperature of the oven constant to less than half a degree Celsius.

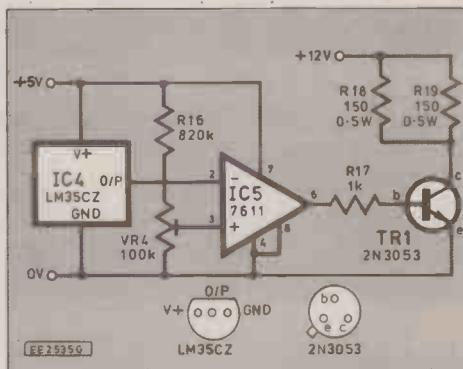


Fig. 3. Thermostat circuit diagram for the "oven".

The suggested power supply circuit is a conventional 5V regulated supply and is shown in Fig.4. It also supplies an unregulated 12V to the heater resistors.

The main circuit and display take about  $50\text{mA}$  and the heaters take about  $170\text{mA}$ . Other supply circuits giving similar output may be used instead. A heatsink is needed for the 5V regulator, IC6.

### CONSTRUCTION

If you do not have a suitable bench power pack, begin by building the power supply circuit. Fig. 5 shows a suitable stripboard component layout and details of underside breaks in the copper strips. Alternatively, purchase a ready-made p.c.b. and the necessary components. The completed power supply must be safely enclosed to prevent the danger of accidentally touching parts at mains potential while building and testing the remainder of the circuit.


Begin the main circuit construction by building the sensor board, Fig. 6. This holds the thermostat circuit, the pressure sensor and the first of the op amps, IC1.

The oven consists of a cubical box made from stiff cardboard, Fig. 7. It has no bottom as it rests on the stripboard. Note that the oven must NOT be made air-tight! A flap along the bottom of the left side of the box has a hole in it so that the box can be secured by a bolt passing through the hole at I24.

Three pinholes are made in the left side near the top of the box. The three terminal wires of IC4 are threaded through these and bent as shown, so as to hold the body of the i.c. just above the heater resistor R18. Using a heatshunt, flexible leads are soldered to the three terminal wires of IC4 to connect it to the board at the points shown in Fig.6.

Test the heater circuit by switching on both the +5V and +12V supplies. The oven and temperature sensor should be in place over the pressure sensor and heater resistors. Adjust VR4 so that the voltage at its wiper is  $0.35\text{V}$ .

Fig. 4. Suggested power supply circuit using a 5V regulator i.c.

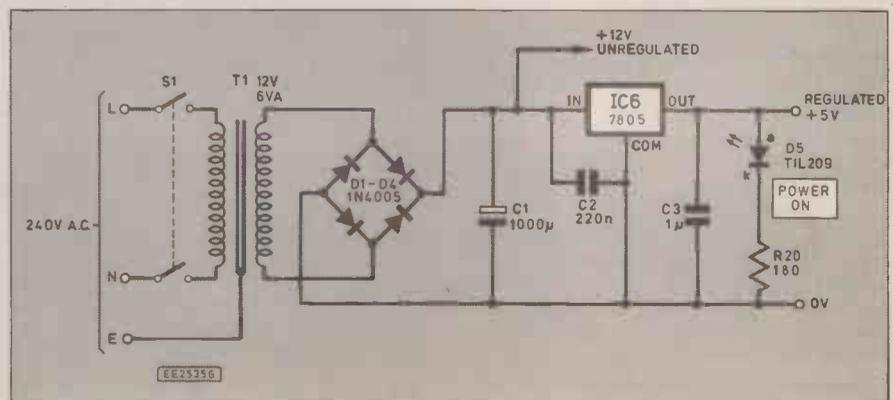

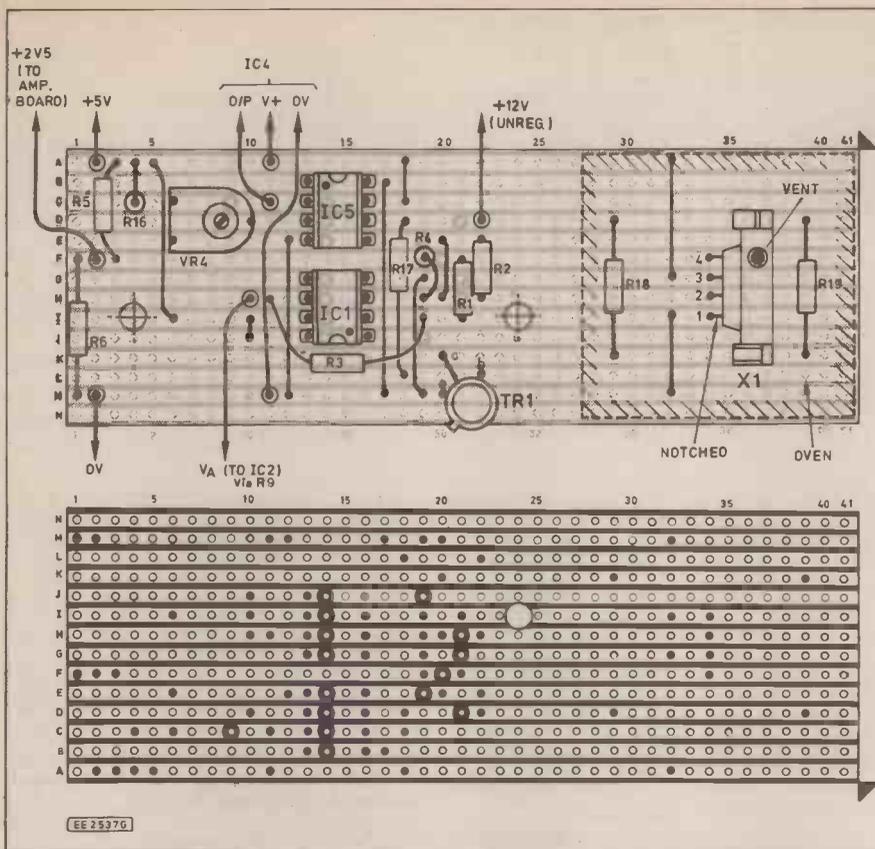


Fig. 6. Component layout and breaks in the underside copper tracks of the pressure sensing/amplifier board.

Use a voltmeter to monitor the output of IC4 (at pin C11 on the sensor board). This rises steadily until it reaches about 0.35V and then remains virtually constant. It may take five minutes or more to reach this state.

The functioning of the heaters can be checked by measuring the p.d. across them. Connect a voltmeter between the 12V supply and the collector of TR1. When the circuit is first switched on, the p.d. should be about 11V, indicating a current of just over 150mA. When the required temperature is reached, the p.d. falls and, from then on, ranges slowly between 0V and 11V.

The output from the pressure sensor X1 may now be checked. There was little point in checking it before because, even under constant temperature, it takes about five minutes after power is applied to reach a steady output state.


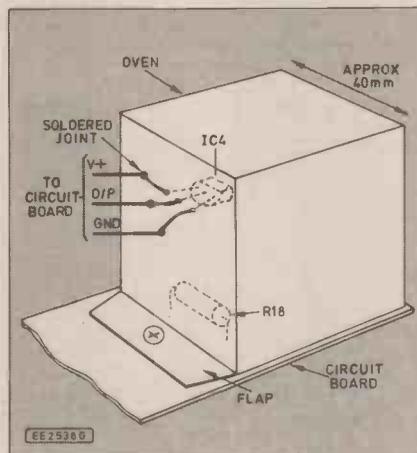


Fig. 7. Mounting the temperature sensor in the "oven".

Fig. 5. Stripboard component layout for the power supply. There are no breaks in the copper tracks. A small heatsink is required for IC6.

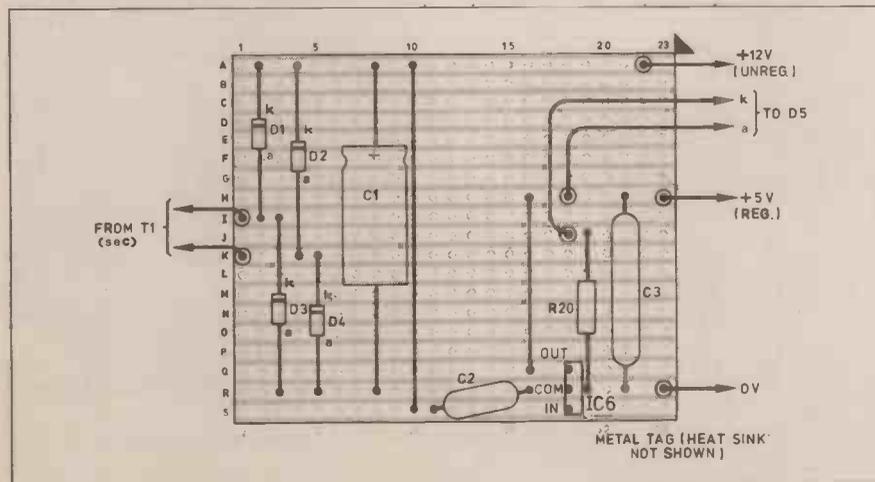

A voltmeter connected between the resistor lead at H22 (positive) and the resistor lead at F21 shows a voltage difference of about 50mV to 120mV, depending upon the characteristics of the individual sensor. A voltage equal to this voltage difference appears at the output (pin 6) of IC1, measured relative to the +2.5V line (pin F2).

## COMPONENTS

### Resistors

R1-R4, R9-R12	10k 0.6W metal film 1% (8 off)
R5, R6	330 0.6W metal film (2 off)
R7, R8	5k6 (2 off)
R13	1M2
R14	12k
R15	22k
R16	820k
R17	1k
R18, R19	150 0.5W carbon 5% (2 off)
R20	180

All 0.25W 5% carbon,  
except where stated

**Shop  
Talk**

See  
page 319

### Potentiometers

VR1	500 multturn cermet preset
VR2	1M sub-min. skeleton preset, horiz.
VR3	100k rotary
VR4	100k sub-min. skeleton preset, horiz.

### Capacitors

C1	1000µ elec. 16V
C2	220n polyester
C3	1µ polyester

### Semiconductors

D1-D4	1N4005 rect diode (4 off)
D5	TIL209 l.e.d. (or similar)
D6	TSC04BJ 1.2V band-gap voltage reference
TR1	2N3053 n.p.n. silicon
IC1-IC3, IC5	7611 CMOS op. amp (4 off)
IC4	LM35CZ temp. sensor
IC6	µA7805UC +5V 1A voltage regulator
X1	MPX100A pressure sensor

### Miscellaneous

T1	12V 6VA mains transformer
ME1	50µA f.s.d. moving coil panel meter
S1	DPDT mains toggle switch
S2	2-pole 6-way rotary or s.p.d.t. toggle switch

Stripboard, 0.1 in. matrix 41 holes x 14 strips, 25 holes x 17 strips and 23 holes x 19 strips; 8-pin d.i.l. sockets (4 off); 1mm solder pins (20 off); metal diecast case, size 220mm x 150mm x 65mm; stick-on feet (4 off) knobs (2 off); card for making oven; nuts and bolts for mounting T1 and circuit boards; connecting wire; mains lead and plug; heatsink; solder etc.

Approx cost.  
Guidance only

**£52**

## ADDER/ INVERTING BOARD

The other two amplifiers are built on a separate board (Fig.8) which is later mounted on the back panel of the instrument case. Holes bored in the back panel allow screwdriver access to VR1 and VR2 so that the circuit may be adjusted while the case is closed.

After mounting the components on this board, make the necessary inter-board connections. (+5V supply, 0V line, +2.5V line,  $V_A$ ). Switch on the power and wait five minutes for the sensor to stabilise. Check the value of  $V_A$  at pin B3 (on the amplifier board), relative to the +2.5V line. Adjust VR1 until the voltage at its wiper is -0.067V (relative to the +2.5V line). The output of IC2 now shows the value of  $V_B$ , which is between 0mV and -6mV.

### TESTING

To convince yourself that the circuit is working, remove the oven temporarily and attach a length of plastic tubing (e.g. aquarium air-tubing) to the vent of the pressure sensor. Connect a voltmeter to measure  $V_A$  and then blow gently into the tube.

A small but appreciable increase of voltage should be indicated. Conversely, sucking gently on the tube causes a decrease in  $V_A$ . Repeat this, measuring  $V_B$ , which should show a decrease with increased pressure and an increase with decreased pressure.

Now connect the voltmeter to measure  $V_C$  (pin G25). Adjust VR2 so that the output is about 0.5V, to give a mid-scale reading. Blowing and sucking now causes the needle to swing rapidly across the voltmeter scale.

### CASE

Bore holes in the rear of the case for the bolts supporting the amplifier board and to allow access to VR1 and VR2. For the type of panel meter specified, cut a circular aperture in the front panel for the body of the meter and four holes for the fixing bolts.

Drill holes in the front panel for the switch S2, the potentiometer VR3, and l.e.d. D5. Mount S2, VR3 and D5 on the front panel. Mount the panel meter and complete the off-board wiring connections as shown in Fig. 9.

Remove the graduated scale from the meter and paint out the numerals and the legend "microamperers", using Tippex typewriter fluid or other "liquid paper". Re-number the scale from 950 to 1050, using rub-down lettering. Add the legend "Millibars". Replace the scale in the meter.

### BENCH TEST

Switch on, select "Pressure", and allow at least 20 minutes for the heaters to warm the oven and for the pressure sensor to stabilize. Set VR2 to the centre of its track. If you have access to a reliable Barometer, read the pressure in millibars. Calculate what  $V_A$  should be:

$1013\text{mb} = 760\text{mm of mercury} = 29.9\text{in of mercury}$

$$V_C = (\text{pressure} - 950)/100 \text{ volts}$$

Adjust VR1 until  $V_C$  (relative to the +2.5V line) equals this value.

If you do not have access to a barometer, estimate your local pressure from a weather map (on TV). The display shows the pressure you have just set in millibars.


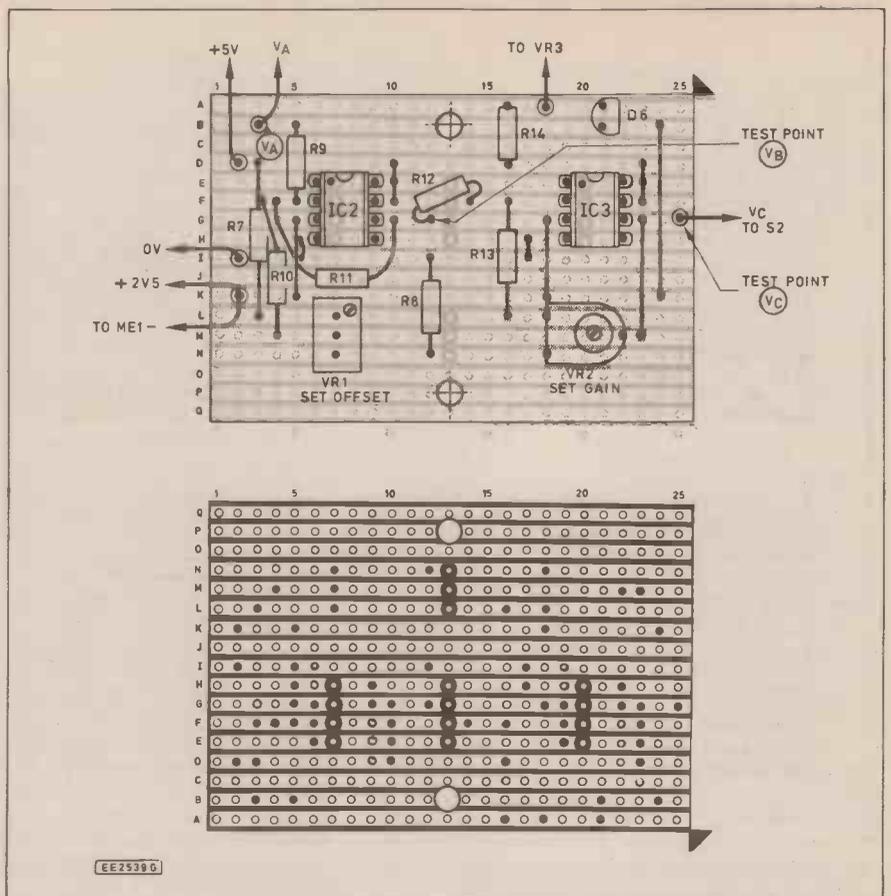


Fig. 8. Component layout and details of breaks in the underside copper tracks of the adder/inverter board.

Fig. 9. Interwiring to the three boards and off-board components.

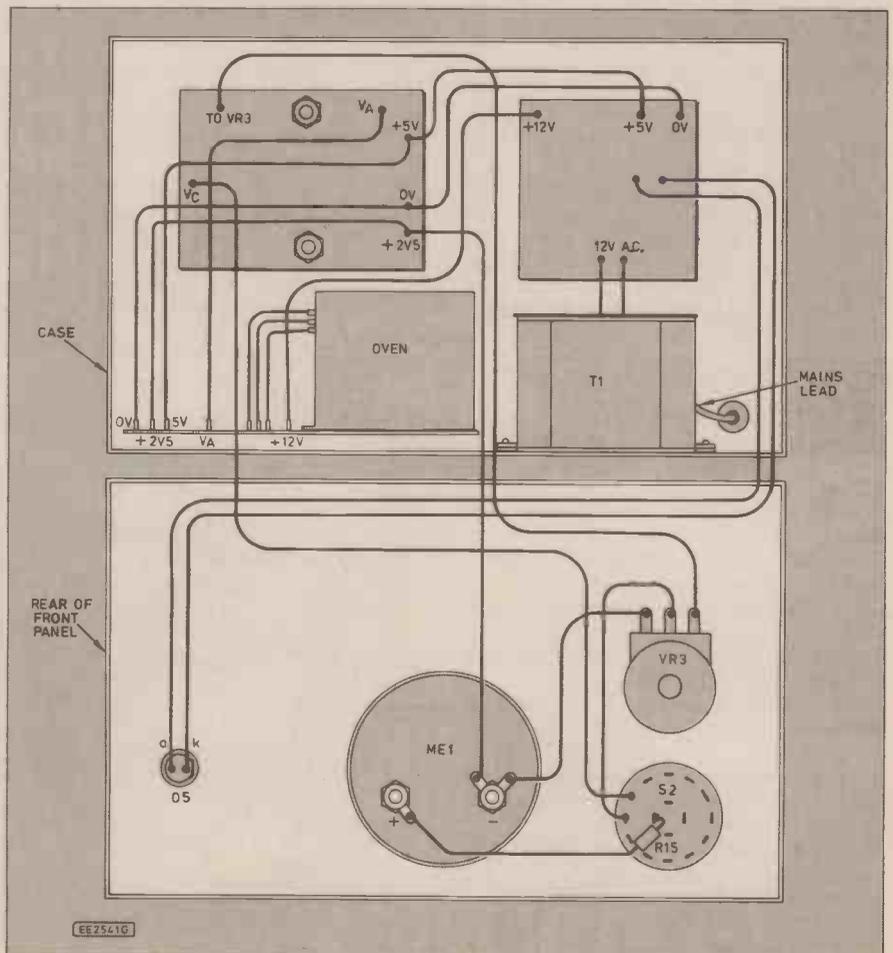

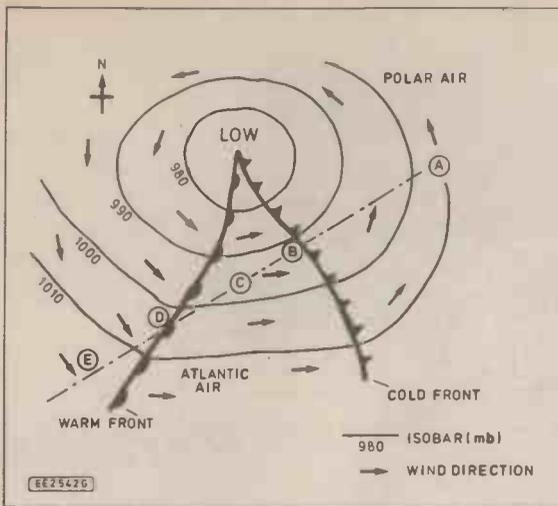


Fig. 10 (left). Example "weather map" showing low pressure or depression region.

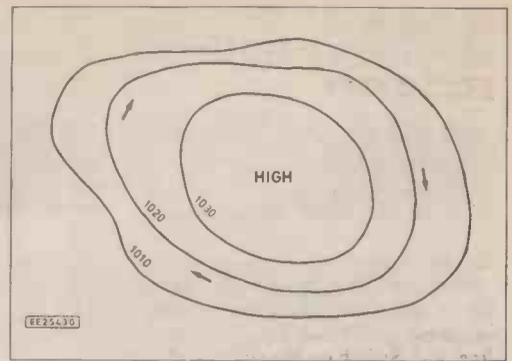


Fig. 11 (right). Example of high pressure or anticyclone region.

Turn switch S2 to "Memory". As you turn preset VR4 it is possible to make the display change over the full scale from 950mb to 1050mb.

Keep the barometer switched on permanently for the next few days. Make records of its readings at given times and compare these with those you obtain from another barometer or from weather maps.

You will probably find that the gain setting is too high or too low. The effect of this is that, for example, pressure increases by 20mb, as shown by the other barometer, but the readings of the Electronic Barometer increase by only 16mb. The gain is too low: adjust VR2 accordingly, turning it slightly clockwise. Or maybe the barometer shows an increase of 27mb; in this case the gain is too high and VR2 must be turned anti-clockwise.

At this point you may find that, with VR2 turned fully one way or the other, it is not possible to set the gain to the required amount. This is due to manufacturing variations between individual sensors. If so, remove resistor R13 and replace it with a resistor of higher or lower value.

After these adjustments, the barometer may now be showing the right amount of change, but its readings may be overall too high or too low. Adjust VR1 to offset the readings by the right amount. You may need to adjust VR2 and possibly VR1 again slightly over the next few days but, after that, the barometer will have been calibrated sufficiently closely for normal use.

## LOCAL WEATHER FORECASTING

Although one can not hope to compete with the vast technological resources of the official meteorologists, a barometer can provide a remarkably reliable forecast of local weather in the short term. As mentioned before, it is the changes in pressure that count most.

First of all, here are some simple forecasts:

**Pressure falling** — expect cloud, rain (snow or sleet in winter).

**Pressure rising** — expect fine weather (possibly clear weather with frosty nights in winter)

**Slowly changing pressure (or no change)** — weather continuing as at present, light winds or calm.

**Rapid change in pressure (rise or fall)** — forecasts strong winds and rapid changes from the existing weather.

The rules above do not apply in all circumstances and, for a more reliable

forecast, we need to take wind direction into account. There are two types of weather system in the region of the British Isles, the depression and the anticyclone.

## DEPRESSION

A depression is a region of low pressure and is associated with a region of warm moist Atlantic air being partly surrounded by cold dry Polar air (Fig 10). The borders between the two air masses are referred to as a warm front and a cold front. Depressions vary in size — a large one is more-or-less the same size as the British Isles. Normally they move across the country from south-west to north-east. On occasions, though, they may change direction, halt, or even move in the opposite direction, which unpredictability may result in somewhat red faces among the weather-people.

Assuming normal behaviour, if you are at a point A (Fig 11) you may expect the following weather sequence over the next several hours as the depression passes by (the diagram shows you travelling SW through the depression - which gives the same sequence):

- A Pressure falling, becoming cloudier, clouds becoming lower, wind becoming stronger and veering (i.e. changing direction clockwise) from SE or SW to westerly.
- B The warm front arrives, warmer but "muggy", pressure still falling, winds veer abruptly, rain (snow or sleet in winter).
- C Pressure reaches a minimum and starts to rise again. Clouds may clear but then reappear.
- D The cold front arrives, cooler but less

"muggy", winds stronger and veering again, to NW or N, rain, though possibly less than before.

E Pressure rising, clouds clearing, dry fine weather.

With a little guidance from recent weather maps, you should be able to work out where you are in relation to the next depression and to forecast what weather to expect next. One of the big problems of the weather forecasters is that depressions behave erratically and do not always reach the predicted location at the expected time.


This is why rain often comes before or after it is officially forecast. Using your barometer you are able to watch the actual progress of the depression and to know more exactly when the predicted weather changes will occur, if at all.

## ANTICYCLONE

An anticyclone is a region of high pressure (Fig 11). Weather is usually good in such conditions. Clear skies, and bright sunny days in summer — with cold frosty nights in winter. Winds are usually none or light.

Anticyclones often stay around for several days at a time before they finally move away and the weather changes. The winds circulate in a clockwise direction so, by observing your local wind direction and the changes in pressure, you will be able to work out your position within the system and which way the anticyclone is moving. This will tell you if the good weather is likely to continue and for how long.

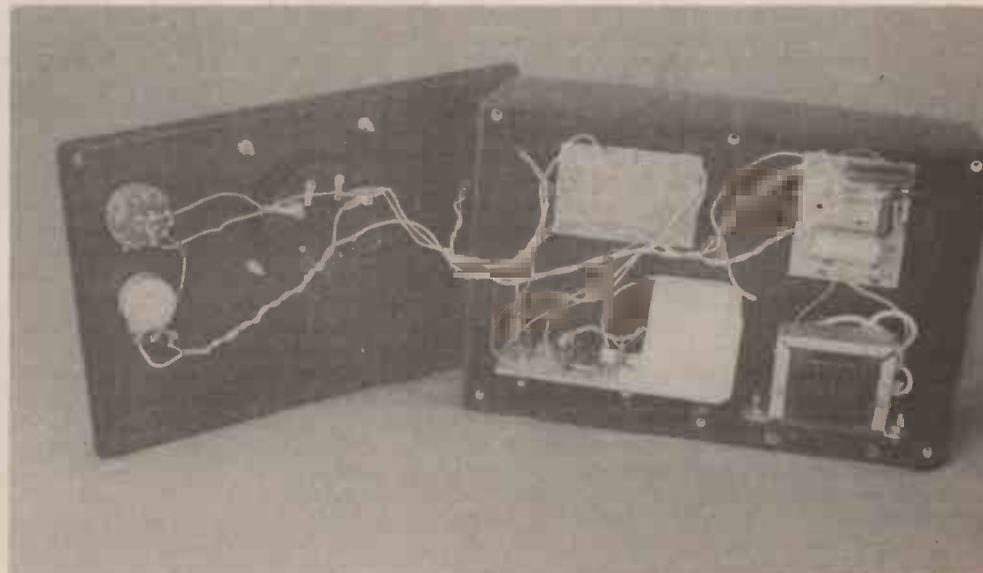The description above is over-simplified but it will help you to get started with the fascinating hobby of predicting your local weather. There are several popular books available that will take you further in this direction. □



# MICRO IN CONTROL

JOHN HUGHES

Part Six



Starting from very basic principles this series quickly builds through logic to simple microprocessor control.

Now we are starting to get close to the real microprocessor area — let's look at counting circuits and control logic.

## EXERCISE 13

### Dividers and Counters

Look carefully at the relationship between INPUT and OUTPUT pulses for the 7476 flip-flop. Each input pulse only causes HALF an output pulse, in our case DOWN, then UP. Because of this, a flip-flop like this is sometimes called a BINARY DIVIDER circuit, because it takes two input pulses to produce each output pulse (Fig. 6.1).

**S** That's why we need binary arithmetic.

**T** Right again. We work in steps of two because the chips do so. Most of you are probably familiar with binary numbers, but just in case, we'll write them down as we go along. We've already seen that there are only the two DIGITS 0 and 1 that we can use. They can represent 0 volts and 5 volts respectively, also OFF and ON. They could be made to represent any TWO-STATE system, couldn't they?

Let's get on with our exercise, and bring the second 7476 flip-flop into use. We'll just take the output of the first one to the clock input of the second (leave the indicator connected and add an extra indicator to the new output. Let's label the outputs QA and QB. OK?

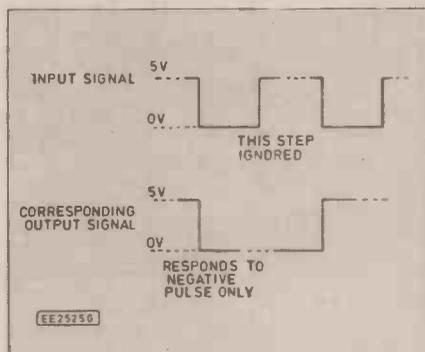


Fig. 6.1. Behaviour of binary divider

**S** And ignore "NOT QA" and "NOT QB"?

**T** For now, yes. Now wire it up and send it some pulses as before from the de-bouncer (Fig. 6.2).

**S** It's dividing by two again | by four now.

**T** That's right. Our two indicators (remove the one from the 7400 now) are counting "nought . . one . . two . . three . . nought" if you watch them, thus (writes table):

Counting Pulses		
ordinary (denary numbers)	BINARY numbers QB QA	
0	0	0
1	0	1
2	1	0
3	1	1
4 (same as 0)	0	0

**T** It makes sense now to start with column A on the RIGHT as this is how we normally deal with numbers. Then the right-hand column is UNITS, the next (B) is TWOS, and so on.

**S** They keep going round and round.

**T** Yes. Could we go beyond 3?

**S** Only with more flip-flops.

**T** Right. If you wish you could add another 7476 and link it in to count up to . . . ?

**S** (eventually) 16. No, 15.

**T** Right again. However, guess what? The chip makers got there before us and made chips with four or more stages in them. We'll now look at a "four bit counter" the 7493.

**S** This will give Fours and Eights | C and D columns.

**T** Exactly. Let's see the pin-out for the 7493 (Fig. 6.3). Having spotted the power pins 5 and 10, notice that there are four output pins, as expected, but only two in-

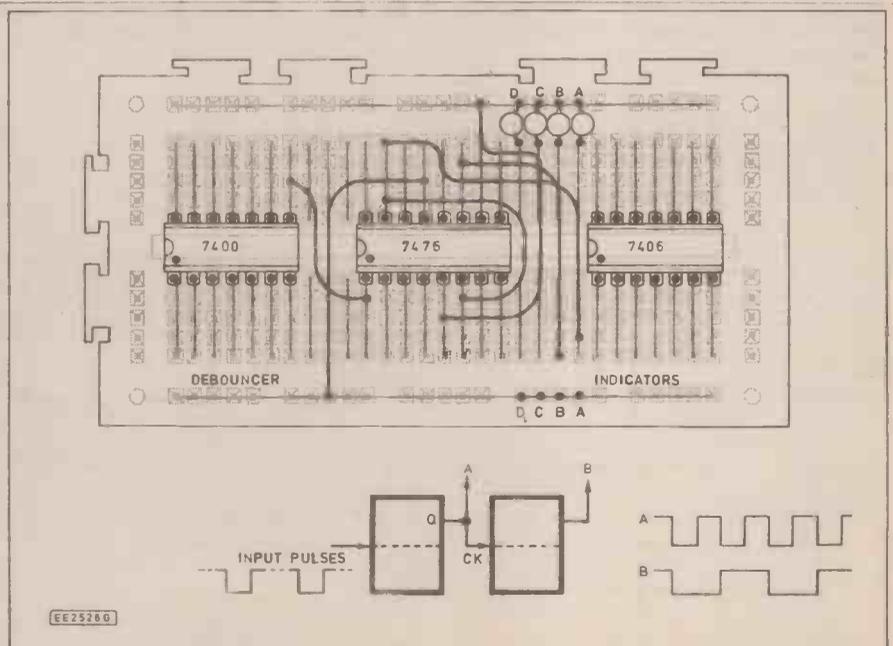


Fig. 6.2. Adding the second J-K.

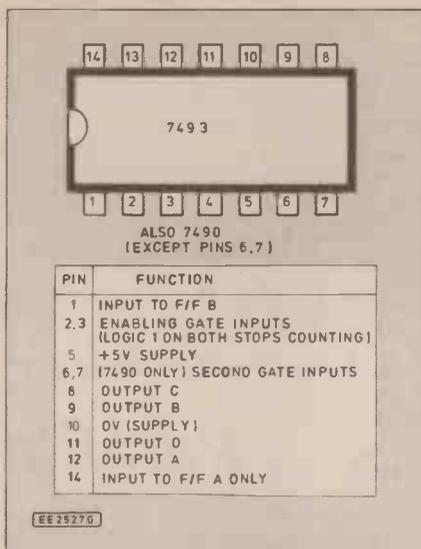


Fig. 6.3. The 4-bit binary counter.

put pins. There are also a couple of "gate" pins (2 and 3).

The chip is labelled as "divide-by-two and divide-by-eight", which means that, to increase its usefulness, the makers have put into it a single binary divider (input pin 14, output 12), and three more dividers linked internally together, so that only the first input, B, is needed (pin 1). The outputs B, C and D are marked as pins 9, 8 and 11 respectively.

**S** Does "NC" stand for "no connection"?

**T** Yes, there are some unused pins.

Now insert the chip carefully as usual in the space I hope you left in the middle of your board (Fig. 6.4) and add the links as shown. Thus we take our pulse input from our debounced switch to pin 14. (A "biased" switch, one which springs back when released, or a push-button, is easier to use here).

**S** What about input B? Does this go to the output of A?

**T** Yes. It can also be taken to indicator A, and you can link outputs B, C and D to their indicators.

**S** Inputs C and D are presumably connected already, inside the chip.

**T** Right. Don't forget power links, by the way.

**S** Do we need to connect the "gates" you mentioned?

**T** They are alternatives, so we'll need to connect either one of them in order to "enable" the chip. They provide a valuable facility in that we can stop the chip by means of these gates if we need to. For now, link one of them to logic 0 (the 0V line, as shown).

Now we're ready to switch on and go. Try a few pulses to see what happens. Is it as you'd expect?

**S** (mostly) Yes, it seems to be counting in binary.

**T** We'd better write down the patterns to make sure:

Number of input pulses	Output pattern D C B A
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1

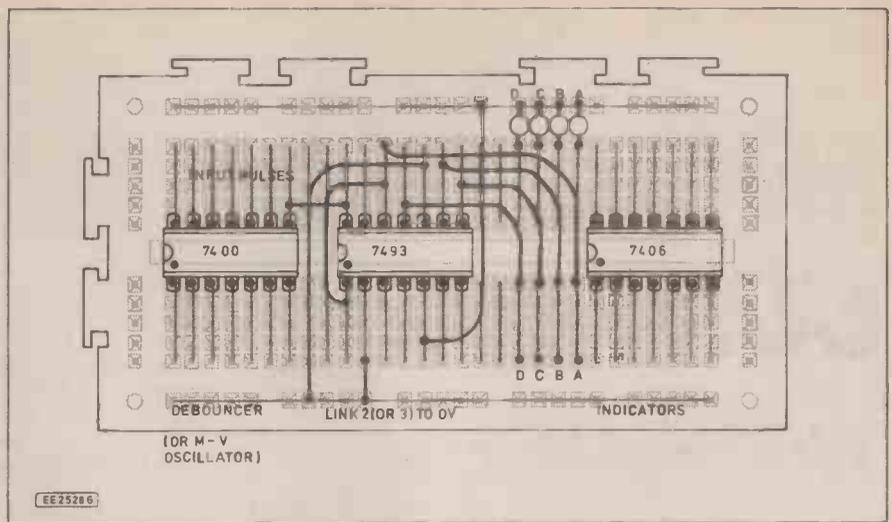


Fig. 6.4. Checking the binary counter.

Number of input pulses	Output pattern D C B A
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1
10	1 0 1 0
11	1 0 1 1
12	1 1 0 0
13	1 1 0 1
14	1 1 1 0
15	1 1 1 1
16 (same as 0)	0 0 0 0 ...and so on

**S** It goes round as before. We could add more stages to count further, I suppose.

**T** Quite. Practical circuits would clearly need to do this, wouldn't they? However, there are a few points worth noting at this stage.

The first is that, in order to represent ALL the common digits (0 to 9) of our familiar denary system, we MUST have all four columns A, B, C and D. Three columns would only get us up to ...?

**S** Seven (I nearly said eight).

**T** Yes. Of course, nought to seven is eight numbers, if we count zero, as we must.

Now, if we were designing a pocket calculator, for example, we would need counters for each digit which stop at nine, wouldn't we?

**S** Yes. Could we use the gates to stop it at that point?

**T** Exactly. In fact, let's try. Add the links shown in Fig. 6.5. Can you see what they do (we hope)?

**S** (after some thought) They remove the logic 0 on both gates when the counter reaches ten, and stop it moving on beyond nine.

**S** (another), Because of the logic 1 on pins B and D.

**T** Spot on. I see some of you have it working now. This kind of counter is called a BCD counter. It stands for "binary-coded-denary" (or decimal) and is widely used.

**S** I suppose there's a chip for this, too.

**S** (another) I've found one in the data sheet, 7490. They call it a decade counter.

**T** OK. There's also a divide by twelve counter. But let's proceed. In computers, there's no need to limit the chip in this way (at least, not until it needs to talk to us humans) and the full counter is quicker for long calculations. This brings us to HEX notation.

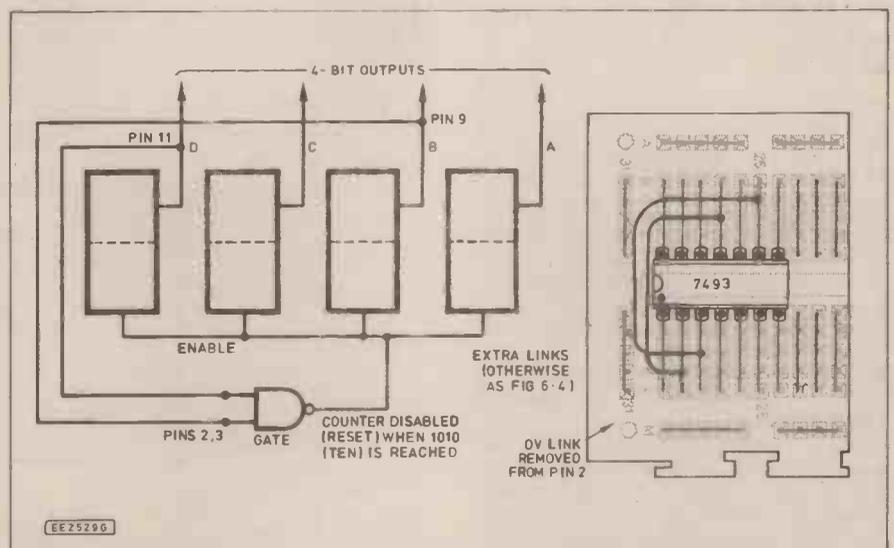


Fig. 6.5. Using the built-in NAND gate to count in TENS.

**S** Sounds like witchcraft.

**T** Behaves like it, too, at times! The point is, we have a four bit chip available, and the idea of this new and useful notation is to keep all its possible output values in a single "column", by introducing extra symbols for the last six values (the ten, eleven, etc., which get two columns in ordinary notation).

**S** I could suggest some smashing new symbols.

**T** I bet. Unfortunately, the mathematicians who work in this area got there first, and just used the first six letters of the alphabet. Thus A represents ten, B eleven, and so on.

**S** Up to F for fifteen, then?

**T** You might like to write them down. You could fill in an extra column in the earlier table, reading "1,2,3,4,5,6,7,8,9... then?"

**S** "ten, el... NO. A,B,C,D,E,F"

**T** Good. We may find HEXADECIMAL (hex for short) arithmetic useful from time to time. Don't forget it.

**S** Are there any more special counter chips?

**T** Many. It's easy to make a counter count backwards. By linking the NOT Q outputs instead of the Q outputs to the next stages, for example. A "down counter" has many uses in calculating circuits. Switching by gates between up and down counting is also useful. And they can have more than four bits, of course.

**S** Some computers use 16 or 32 bits nowadays.

**T** Sure. For control purposes we won't need so many. In fact we'll probably find an eight-bit micro is plenty to cope with.

**S** Can we connect our clock to the counter?

**T** Why not, indeed. You could spend some time now re-checking some of the circuits we've just discussed, and perhaps trying some of the other counter chips we mentioned.

## EXERCISE 14

### Logic Control Examples

**T** It's time we tried to apply our grasp of logic to a control system example. Let's start with an easy one. Do you still have the small motor and battery that we used to test the relay circuit?

**S** Yes, and mine still works. Look.

**T** Good. Now what I'd like you to consider is this: Can you make the motor run only after a number of buttons or switches have been pressed in the right order?

**S** I could do the first part (without the "right order") by using AND gates. | or NANDs

**S** (another) With a bistable, to keep it ON when the buttons have been released.

**T** That sounds OK to me. I assume you could draw a diagram of your system.

**S** Yes, but I'd need to have more details, such as:

- How many buttons, and in what order?
- Does the motor run on logic 0 or logic 1?

**S** (another) That second one doesn't matter. It's up to you, isn't it. You choose in your design.

**T** Well, you both seem to be clear about starting. Perhaps we should set ourselves a specific task as a starter. Let's say THREE buttons or switches (and don't forget you can "dab" a wire to logic 0 for testing), and let's say A has to be pressed first, then B and C TOGETHER, to start the motor.

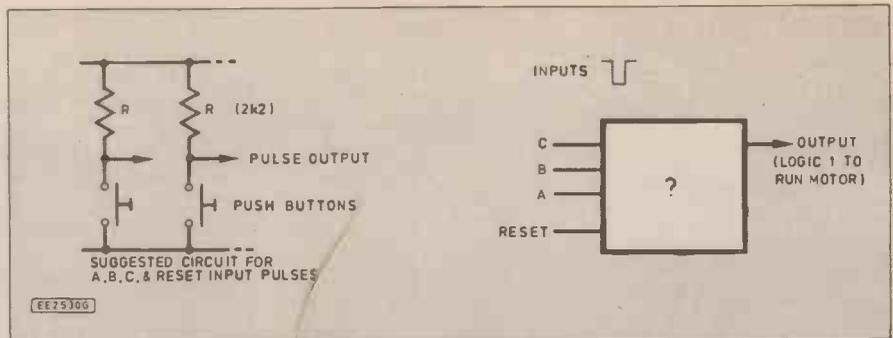


Fig. 6.6. Motor control example. To start the motor, A must be pressed first, then B and C together.

**S** The letters don't matter. We could re-label them.

**T** Quite, though in a real system, the same buttons might be used for many functions.

**S** Like a telephone dialling pad.

**T** Just so. Let's suppose, too, that our motor drive circuit (the one with the relay in it, OK?) switches the motor ON when it receives an input at logic 1 (at 5V).

Then we could start as we did with the electronic lock, by drawing a box and seeking to work out what to put in it (Fig. 6.6).

**S** Will the inputs be normally at 0 or 1?

**T** As one of you said, it's up to us. I suggest we adopt a widely-used method of having them all at logic 1, with a button to pulse each to logic 0 when pressed (momentarily, that is).

**S** We'll need debouncers, then.

**T** It's possible, though a simple bistable, as we've seen, does its own debouncing. It's only when actually counting (using the clock pin) that we need "clean" pulses. I'll leave it to you for now.

**S** We'll need an AND (or NAND) for B and C.

**S** (another) and a flip-flop to hold the output ON.

**S** (another) What about a "reset" button to stop it?

**T** That sounds like something we should add to our specification, doesn't it? Right, we'll have a fourth one. Can you try filling in the box, now? I'll add my version, and we can compare them (Fig. 6.7).

Now I think we could try it out.

**S** We don't really have to use the motor. One of the l.e.d. indicators would do.

**S** (others) A motor's more fun | lazy so-and-so | etc.

**T** You're probably right, and most systems are tried out using bread-board tech-

niques at first. But there does come a time when the system has to work in the real world. Then we MAY find extra difficulties, such as unexpected pulses from interference sources, mechanical time delays, and other snags.

I agree with those who think it's fun to use a real motor if you have one handy, but most of the time we may be stuck with indicators only. Either way, carry on and check it now.

**S** (later) Can we discuss how it works?

**T** I agree, we should. Anyone start us off?

**S** I started by realising that a bistable is needed to keep the motor on... and off.

**S** (another) Yes, and it has to be SET by a logic 0 pulse, and this has to be controlled by a gate. It took me some time to see which kind, though.

**T** Yes. You will have realised that, in a sense, an OR gate behaves like an AND for logic 0, doesn't it? You ONLY get logic 0 out when both A AND B inputs are also 0. Some designers use such "inverse logic" a great deal.

**S** (others) Then we need a second bistable to make it necessary to follow the correct sequence. | and another OR gate. | the RESET button puts the motor flip-flop OFF.

**S** And the second flip-flop needs resetting, using the pulse from buttons B and C | the one that starts the motor.

**T** You seem to have it well sorted out. Bear in mind that all the pulses are to logic 0, and notice that the Q output gives logic 1, so we use the complementary output of the second bistable.

**S** I used the other output, but swapped the SET and RESET signals.

**T** Again, there are more ways... Well done.

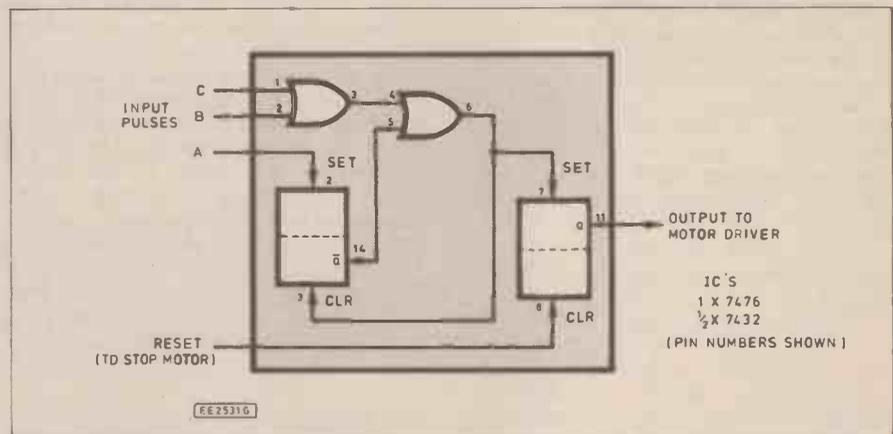


Fig. 6.7. Suggested logic system for motor exercise. It may be preferable to use reset signal to clear both bistables. (Remember power supply links to i.c.s.)

## EXERCISE 15

### Going up? (or down?)

**T** The control of a lift provides an excellent example for us. It can be more complex than might at first appear, and we may wish to go back to the days of the lift operator! However, let's see how far we can get.

As before, we need an exact specification, then we must agree on details of input and output signals. Both these, in practice, would naturally reflect the "state-of-the-art" in both electronic and mechanical design, including the vital considerations of safety and of cost.

**S** And appearance, noise, and so on.

**T** Yes, and even whether the stairs would be better for our physical well-being! Fortunately, we can limit our design features to keep life fairly simple today. Let's start with the lift spec.

**Specification:** It should work between two floors to start with, but provide for a third (or more) afterwards. Each floor will have a CALL BUTTON, and, of course, the lift must not move unless all doors are closed.

**S** Do we need buttons inside the lift?

**S** (another, after thought) No, because they only do what the external buttons do and could have the same circuits.

**T** I agree. Perhaps, on our model, we can also do without internal doors. In fact, the model lifts we have knocked up to give you

something to work on are virtually "two-dimensional" as you'll see.

**S** Because we don't need to carry a real load?

**T** Quite. But we shall need call buttons. Anything else?

**S** We'll need some sort of sensors to detect when the lift reaches each floor. | and if the doors are closed | and if the lift goes too high or too low | or too quickly for safety | signal lights | etc.

**T** Good points, all of them. Duly noted. Our next task (next month) will be to list the INPUT and OUTPUT SIGNALS required. And, if some of you wish to build your own lift model (a challenging and worthwhile project), I'll describe some of the features of our version (and how it might be improved).



with David Barrington

### Amstrad CPC Speech Synthesiser

No matter what permutation we tried when pricing up the parts for the *Amstrad CPC Speech Synthesiser* we were unable to come anywhere near the price being offered by **Greenweld** (☎ 0703 772501) for a complete kit (including p.c.b. but excluding case). We think that at £10.95 (plus £2 p&p) it's got to be a bargain. This price includes an extra Free speech chip!

A suitable case will only cost £3 and the SP0256-AL speech chip £2.50 when purchased separately. (The nearest price for the speech i.c. we found was £5). **Greenweld Electronics**, Dept EE, 443D Millbrook Road, Southampton, SO1 0HX.

The 3.2768MHz crystal is to be found in most catalogues under the "Timing" Crystals" section for timekeeping or use in quartz clocks. Satisfactory results should be obtainable from crystals using a frequency from 3MHz to 3.3MHz.

The printed circuit board for the Amstrad CPC Speech Synthesiser is available through the *EE PCB Service*, code EE689 (see page 356).

### Electronic Barometer

Quite a few of the components used in the *Electronic Barometer* can be classed as special items, and therefore most likely to cause purchasing problems locally.

The only source to date that we have been able to find for the TC04JB band-gap voltage reference is from **Electromail** (☎ 0536 204555), code 283-564. If constructors experience any difficulty in locating the ICL7611 CMOS i.c.s, the same company carry stocks. Also **Grandata** are able to supply this CMOS op. amp.

The heart of the barometer circuit is the "pressure sensor" and this device was purchased from **Maplin**, code UH37S (MPX100AP). The MPX100AP sensor cost £13.95 so care should be exercised when handling and soldering this device on the stripboard. Double check that it is the correct way round before finally soldering it in position.

When ordering the LM35CZ temperature sensor i.c. it is important to ask for the Centigrade version, designated with the letters CZ. The one in the prototype was obtained from **Maplin**, code UF51 (LM35CZ) £5.25.

Provided the meter movement is rated at 50µA full scale deflection (f.s.d.), practically any moving coil meter will do here. It is, of course, better to use as large a meter as possible for ease of reading and the 4in. movement, code RX54J (50µA Lrge Pan Meter) £8.25 from **Maplin** was used in our model.

### TRF Receiver

The main items that push up the cost of the *TRF Receiver* (*Amateur Radio Supplement*) are the variable capacitors. However, although a value of 300p is quoted for the capacitor VC1, in practice you can, if you wish, choose any value between 250p and 500p and it should work satisfactory.

But try to avoid inexpensive tuning capacitors which have miniature spindles. It could prove difficult to locate a suitable control knob for these types.

The Jackson series "0" quality tuning capacitors are currently stocked by **Cirkit** (☎ 0992 444111). They are also the main distributor for Toko coils and stock a good range of r.f. chokes.

For maximum output, loudspeaker LS1 should have an impedance of 8 ohms, however speakers having an impedance up to about 80 ohms should give a reasonable performance in this circuit. When purchasing potentiometer VR2 be sure to ask for a "log" law type.

If constructing the simple "crystal set", keep in mind that germanium diodes are more susceptible to heat damage than silicon types. So take extra care when soldering this device in circuit.

### Quizmaster

Looking down the list of components for the *Quizmaster* project, we cannot foresee any component purchasing difficulties.

For those readers who do experience troubles, **Robinswood Electronics** are selling a complete kit, including case, for the sum of £25.95 plus £1 post and packing.

They also claim that if any constructor runs into troubles and cannot get their kit to work they will repair it Free of charge.

The offer only applies provided the kit is returned within 30 days of purchase. They will, of course, charge for return postage and replacement parts. **Robinswood Electronics**, Dept EE, 33 Cotteswood Road, Gloucestershire, GL4 9RQ. (*Mail Order Only*).

The printed circuit board is available from the *EE PCB Service*, code EE690 (see page 356).

### Auto Memo

All the components called up in the *Auto Memo* parts list appear to be off-the-shelf items and should not cause local sourcing problems.

The p.c.b. type warning device (**Electromail** (No. 249-794) ☎ 0536 204555) used in the model seems fairly expensive for this simple circuit and one of the many cheaper piezo transducers on the market should work here. Most are rated at about 4V to 12V plus and range in price from approximately 70p to £2.

The "click switch" or a suitable alternative, such as a microswitch, should be available from most component advertisers. The one used in the prototype is the **Maplin** non-locking click-effect switch, code FF87K (Click Switch).

### Azimuth Adjustment Aid

We do not expect any component buying problems for readers undertaking the *Azimuth Adjustment Aid*. The dual, p.c.b. mounting potentiometer is a standard line and should be stocked by most component suppliers.

If you do find that you require a new tape head for your machine, we can recommend the excellent range stocked by **Hart Electronic Kits** (☎ 0691 652894). They will be only too pleased to advise you on your requirements.

PLEASE MENTION  
EVERYDAY ELECTRONICS  
WHEN REPLYING TO  
ADVERTISEMENTS

# FOR YOUR ENTERTAINMENT

BY BARRY FOX

## Lap-top Rambo

Recently the Dell Computer Corp. of Texas launched a new computer, a high specification lap-top with a 386 processor, hard disk and back lit i.c.d. screen. It's a nice piece of kit at a good price (under £3,000). They boast its weight as "under fifteen pounds".

Whatever that looks like on paper, I can tell you it's darned heavy when you actually lift it. What's more, the big and heavy re-chargeable nickel-cadmium battery only runs for two hours. "Computing time for the Dell portable is limited only by the number of spare battery packs the user can carry", says Dell. To work on the move you need to carry several spare batteries, and end up looking like Rambo with a bandolier of heavy hardware.

"Why call it a lap-top?", I asked the Dell people. "Have any of you ever actually tried using it on a long plane journey?"

Their answer is that computers like this are not intended to be used for steady work on long plane journeys. They are intended to be dumped in the back of a car and moved between home, office and hotel room.

"Why not call it transportable then?"

Because, says Dell, people think that a "transportable" needs to be plugged into the mains. The trade term for a computer that works on batteries as well as mains is "lap-top". Toshiba started it, says Dell.

The common sense fact that people don't use heavy computers on their laps does not, it seems, count for anything.

## Back-up

What for many people will be a real benefit of a "lap-top" isn't even mentioned in the publicity material.

Anyone who has suffered a power cut while working with a desk top PC, and either lost data from memory or had disks corrupted, ends up wanting a UIPS, or Uninterruptible Power Supply. A UIPS has low voltage batteries which are continually charged by the mains. At the same time the battery voltage is stepped up to mains voltage to run the computer.

The power supply for the computer thus floats independently of the mains. If there is a short failure, the batteries just bridge the gap; if the failure is long term the batteries keep the computer running for a few minutes, which is long enough to save all data from memory onto disk.

But add-on UIPS units cost several hundred pounds.

A lap-top that can run on either mains or battery power has the equivalent of a "free" UIPS built-in. In most designs, if the mains supply fails the computer just goes on running off its batteries.

But even the normally smart Dell people haven't spelled this obvious benefit out in their publicity material. Instead they make much of a long-life lithium battery buried inside the lap top which keeps the memory powered up for two minutes while the roving user changes batteries.

How long, I wonder, before a computer

firm cottons on to the value of free UIPS as a selling feature for lap tops? And how long, I wonder, before firms making portable computers, and video camcorders, start selling what many users would welcome — a battery pack that takes expendable cells.

Camcorders, like portable computers, rely on rechargeable NiCads. If one thing in life is certain, it is that a NiCad will always go flat when you most need power. Working on a long journey, or shooting video in deep country, you cannot charge flat batteries. The simple answer is a battery pack, the same size as

the NiCad pack, but with slots inside to take standard alkaline batteries. Alkaline cells can be bought virtually anywhere in the world.

Of course, it's far more expensive to use alkaline cells than rechargeable batteries, but if you are stuck with no mains supply, wanting either to work on a computer or shoot video, £10 on alkaline cells for a couple of hours power will seem cheap at the price. In any case business people who work on the move, can claim back the price of batteries. But so far I know of no dummy NiCad packs, which take alkaline cells.

## Hot Tip

This may save a lot of people a lot of wasted time.

Over the years, I've many times cursed battery-powered soldering irons, which always seem to run down just before you have finished the last joint. And they are next to useless in cold weather, for instance working outside on a car.

So I jumped at the chance of buying one of the Flame Master hot gas soldering tools widely advertised in the electronics press by *Maplin Electronics*. After a few muddles over the order I got the iron — but couldn't use it because it comes empty, and without a source of gas to fill it. The instruction manual simply says "powered by butane gas", with no identification of what kind of butane can or cylinder to use, and where to buy them.

The butane cylinders sold in hardware stores have a wide range of proprietary nozzle fittings. So I carried the Maplin tool round several shops and finally found a cylinder, made by Braun, which seemed to fit. But I had great difficulty getting enough gas from the cylinder into the tool to keep it running for anything like the claimed "up to two hours continuous use".

So I wrote to Maplin asking what make of gas cylinder they recommended. Maplin replied that their service department tested the tools with "Newport purified butane gas". This, said Maplin, is available from branches of *Woolworths* or direct from the suppliers, *Keen World Marketing*, of Ridgeway, Iver Bucks.

I then tramped round every Woolworths I could find. But not one stocked, or had even heard of, Newport cylinders. So

I wrote to Keen, who said that Maplin were wrong, and they do not offer a mail order service.

But at last the trail was getting as warm as the soldering tool should be. Keen says that Newport is "available from most independent retail confectioner, tobacconist and newsagents in the UK".

The key point is that the Newport cylinder is intended to refill *cigarette lighters*, and it comes with a cap which has eight different nozzle fittings loosely mounted as a push fit. This, says Keen, provides a safe fit with any of the 2,000 or more different brands of re-fillable gas lighters available worldwide. You need a good fit to get the gas into the tool, without spillage — which is an obvious fire risk.

By trial and error I found that several nozzles, e.g. the white one, would do the trick of filling the Maplin iron.

Hopefully this piece of information will help any readers who have bought what is actually a very neat little tool. But surely it would make sense for Maplin now to add a note to the instructions that go with the soldering iron, naming the Newport cylinder, explaining where it can be bought and saying which of the eight coloured nozzles Maplin's service department have found best able to load gas without risk of leaks around the nozzle.

*Maplin tell us that a variety of different types of butane refill can be used with the iron. They are generally available from tobacconist and many other retailers who sell cigarettes.*

*Maplin do not sell the gas due to the problems of supplying it by mail order. (Ed).*

## DATs Music

A music journalist told recently how he often gets music from new bands sent to him on DAT cassette. Small independent record companies find it far cheaper to produce small runs of DAT real-time copies, than to press CDs.

Apart from producing a CD master tape (at around £350 a time), a master disc for pressing (another £350) and then

paying between £1 and £2 each for pressed discs (depending on volume), most pressing plants won't press less than 500 CDs. So it's far easier and cheaper for a record company to send out DAT cassettes of new bands to the press.

There is only one snag. Many of the magazines receiving these cassettes, do not have DAT players.

## THE RTC MONITOR II

100 WATT SPEAKER KIT £60.00 + £3.50 P&P (pair)

RESPONSE: 55Hz-20kHz

BASS POLYMER CONE D: 22cm

DOVE TWEETER: 14mm

OVERALL SIZE (HWD): 382,252,204mm

RECOMMENDED AMP POWER: 10-100 watts per channel

The performance standard achieved in this compact design is distinctively superior to anything else available at the price. The drive units used are of sophisticated design and have been carefully integrated with a Complex Crossover.

Stereo performance is exceptionally good with a well focussed sound stage and sharp resolution of detail. Distortion throughout the frequency range is low even at quite high power input and this gives a great sense of dynamic range and openness especially when used in bi-wired mode.

Supplied with:— 2 READY CUT BAFFLES, ALL CROSSOVER COMPONENTS, 2 BASS MID-RANGE, 2 DOME TWEETERS, HOOK UP WIRE, GRILLE CLOTH, SCREW TERMINALS AND SCREWS.



## GOODMANS 60W CAR GRAPHIC



As new condition but have been returned by customers or shops, so they may need some attention. Hence the price of only £8.00 each. Order six of these units and you get the seventh one free. Postage £2.90

## LCD DIGITAL MULTI TEST METER AC DC

Volts resistance and DC Amps. Most of these units are new but have been returned or rejected by the store and sold with all faults at £11.00 each. Postage £1.00. (Made by Ross Electronics).

## ROSS PUSH BUTTON RADIO

Mains and battery operated. High quality VHF/FM, Medium and Long Wave reception, 6 pushbutton selected preset stations. Fully retractable telescopic aerial. Headphone/earphone jack socket.



Size 230H x 150W x 65D.  
Ref RE-5500.  
Brand new.  
Listed price over £30.00.

Price £14.95  
+ £2.80 P&P

## SHURE HIFI STEREO MAGNETIC CARTRIDGE

Fitted with an elliptical diamond stylus supplied with fitting kit and instructions. A good quality unit made to sell for well over twenty pounds due to scoop purchase, we are able to offer these at a fraction of the manufacturers price. All units are brand new and boxed. £7.20 each. If you order in multiples of five you get one free. Postage £1.30 (Made in U.S.A.)

## KOSS STEREO HEADPHONES

High quality light weight stereo headphones fitted 3.5mm jack with adaptor to 6.4mm jack. Ideal use Hifi or personal stereos-made to sell for nine pounds. Our price for this unit £4.25. Postage 60p.

## TV SOUND TUNER KIT



In the cut-throat world of consumer electronics, one of the questions designers apparently ponder over is "Will anyone notice if we save money by chopping this out?" In the domestic TV set, one of the first casualties seems to be the sound quality. Small speakers and no tone controls are quite common and that really is quite sad, as the TV companies do their best to transmit the highest quality sound. Given this background a compact independent TV tuner that connect direct to your Hi-Fi is a must for quality reproduction. The unit is mains operated. This TV SOUND TUNER offers full UHF coverage with 4 pre-selected tuning controls. All parts including Varicap tuner, mains transformer, PCB with IC's, capacitors and coils etc., to build the unit illustrated above; without case and scale.

£11.50 + £2.30 P&P

Case as illustrated £6.90 + £2.00 P&P

## MAIL ORDER £1 BARGAIN PACKS BUY 20 GET 1 FREE

Please state pack(s) required

No.	Qty. per pack
BP015B	1 30W dome tweeter. Size 90x66mil JAPAN made
BP016	6 2200µf can type Electrolytic 25V d.c. computer grade made in UK by PHILIPS
BP017	3 33000µf 16V d.c. electrolytic high quality computer grade UK made
BP019	20 20 ceramic trimmers
BP020	4 Tuning capacitors, 2 gang dielectric a.m. type
BP021	10 3 position, 8 tag slide switch 3 amp rated 125V a.c. made in USA
BP022	5 Push-button switches, push on push off, 2 pole change over. PC mount JAPAN made
BP023	6 2 pole 2 way rotary switch
BP024	2 Right angle, PCB mounting rotary switch, 4 pole, 3 way rotary switch UK made by LORLIN
BP025	4 4 pole, 3 way miniature rotary switch with one extra position off (open frame YAXLEY type)
BP026	4 4 pole, 2 way rotary switch UK made by LORLIN
BP027	30 Mixed control knobs
BP029	6 Stereo rotary potentiometers
BP030	2 10k wire wound double precision potentiometers UK made
BP031	6 Single 100k multitune pots, ideal for varicap tuners UK made by PHILIPS
BP032	4 UHF varicap tuner heads, unboxed and untested UK made by PHILIPS
BP033	2 FM stereo decoder modules with diagram UK made by PHILIPS
BP033A	4 6"x3/4" High grade Ferrite rod. UK made
BP034	3 AM IF modules with diagram PHILIPS UK made
BP034A	2 AM-FM tuner head modules. UK made by Mullard
BP034B	1 Hi-Fi stereo pre-amp module inputs for CD, tuner tape, magnetic cartridge with diagram. UK made by MULLARD
BP035	6 All metal co-axial aerial plugs
BP036	6 Fuse holders, panel mounting 20mm type
BP037	6 In line fuse holders 20mm type UK made by BULGIN
BP038	20 5 pin din, 160° chassis socket
BP039	6 Double phono sockets, Faxolin mounted
BP041	3 2.8m lengths of 3 core 5 amp mains flex
BP042	2 Large VU meters JAPAN made
BP043	30 4V miniature bulbs, wire ended, new untested
BP044	2 Sonotone stereo crystal cartridge with 78 and LP styl JAPAN made
BP045A	2 Mono Cassette Record and play heads
BP046	4 6-0-6 4VA mains transformers, PC mount UK made
BP047	1 24V 0.3VA mains power supply. Brand new boxed UK made by MULLARD
BP049	10 OC44 transistors. Remove paint from top and it becomes a photo-electric cell (ORP 12) UK made by MULLARD
BP050	30 Low signal transistors n.p.n., p.n.p. types
BP051	6 14 watt output transistors. 3 complimentary pairs in T066 case (Ideal replacement for AD161 and 162s)
BP052A	1 Tape deck pre-amp IC with record/replay switching No LM1818 with diagram
BP053	5 5 watt audio ICs. No TBA800 (ATEZ)
BP054	10 Motor speed control ICs, as used with most cassette and record player motors
BP055	1 Digital DVM meter I.C. made by PLESSEY as used by THANDAR with diagram
BP056	4 7 segment 0.3 LED display (red)
BP057	8 Bridge rectifiers, 1 amp, 24V
BP058	200 Assorted carbon resistors
BP059	1 Power supply PCB with 30V 4VA transformer. MCT818CT IC & bridge rectifier. Size 4"x2 1/2"
BP061	5 6.35mm Mono jack plugs
BP063	5 6.35mm stereo switched jack sockets
BP064	12 Coax chassis mount sockets
BP065	1 3mtr Euro-mains lead with chassis socket

## MULTIBAND RADIO

VHF 54-176 MHz + AM CB BANDS 1-80

Listen to: AIR TRAFFIC CONTROL, AIRCRAFT, RADAR PUBLIC UTILITIES RADIO AMATEURS AND MANY MANY MORE

£17.95  
POSTAGE  
£2.85

SQUELCH CONTROL  
"RUBBER DUCK AERIAL"

## HAND HELD WALKIE TALKIES



Ideal for sports or any outdoor activities. Built-in call button and separate volume control. Range 1.2km maximum. 49MHz crystal control superhet circuit with built-in condenser mic. and speaker. Unit supplied with vinyl carrying case and personal earphone.

£32.90 a pair  
+ £2.60 P&P


## RADIO AND TV COMPONENTS ACTON LTD

21 HIGH STREET, ACTON, LONDON W3 6NG

MAIL ORDER TERMS, POSTAL ORDERS and CHEQUES with orders Orders under £20 add £3.00 service charge. Nett monthly accounts to Schools, Colleges and P.L.C. only ACCESS VISA. Phone orders between 9.30 & 12pm please Overseas readers write for quote on delivery. Phone: 01-723 8432 or 01-992 8430

Callers 323 Edgware Road London W2 Closed Sun. 21 High St, Acton, London W3 closed Sun, Mon & Wed

## 30+30 WATT AMPLIFIER KIT

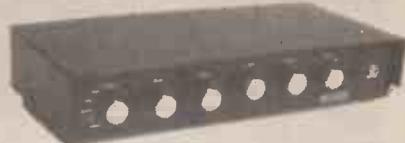

An easy to build amplifier with a good specification. All the components are mounted on the single P.C.B. which is already punched and backprinted.

- 30W x 2 (DIN 4 ohm)
  - CD/Aux, tape I, tape II, tuner and phono inputs.
  - Separate treble and bass
  - Headphone jack
  - Size (H.W.D.) 75x400x195mm
- Kit enclosed: case, P.C.B., all components, scale and knobs £36.80. post £3.50 (Featured project in *Everyday Electronics* April 1989 issue). Reprint Free with kit.

## AMPHONIC 125+125 POWER AMPLIFIER




125 watt per channel stereo power amplifier with independent volume controls, professional 19" rack mount and silent running cooling fan for extra reliability.

Output power .... 125W RMS max. per channel  
Output impedance ..... 4 to 16 ohms  
(max. power into 4 ohms)

Sensitivity ..... 450V at 22K ohms  
Protection .... Electronic short-circuit and fuses  
Power ..... 220-240V a.c. 50Hz  
Chassis dim ..... 435x125x280mm

£142 + £7.00 p&p

## STEREO DISCO MIXER MX7770

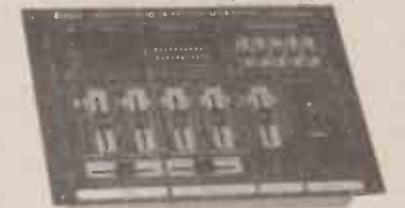

4-channel stereo disco mixer with built-in 5-band graphic equalizer capable of mixing a total of 8 line, phono or mic inputs, switchable on the front panel. Controls include cross fade between channels 1 and 2, headphone cue, DJ mic talkover, channel level markers and stereo/mono switch. Twin 12 LED bargraph display. Output to amp, tape and headphones.

Input sensitivity ..... Mic. 0.3mV, Phono 3mV, Line 150mV  
Input impedance ..... Mic. 600Ω, Phono 47kΩ, Line 47kΩ  
Max. input level ..... Mic. 30mV, Phono 140mV, Line 5V  
Output impedance ..... 600Ω  
Rated output ..... >3mV  
Hum and noise ..... >3mV  
Frequency response: Mic. .... 50-20000Hz  
Phono ..... 50-20000Hz  
Line ..... 20-30000Hz

Equalizer section:  
Control frequencies ..... 60Hz, 250Hz, 1kHz, 3.5kHz, 12kHz  
Control range ..... ±12dB, boost or cut  
Power ..... 240Vac  
Dims ..... 380 x 270 x 96mm

£86.95 + £5.80 p&p

## BELT-DRIVE QUICKSTART VARISPEED DISCO TURNTABLE

- ★ Quick start ideal for scratching
- ★ Pitch control
- ★ Pop-up target lamp
- ★ Strobe lamp
- ★ Counterweighted tubular tone arm with plug-in headshell
- ★ Full manual control
- ★ Remote start/stop
- ★ 7.5kg



£112.00  
+ £7.00 P&P



# AZIMUTH ADJUSTMENT AID

T.R. de VAUX-BALBIRNIE

*"As new" performance from ageing cassette players.*

**M**OST HOMES have at least one cassette player. As well as the family stereo unit, there may be others in children's bedrooms, cars, and perhaps for computer data storage. Personal stereos of the "Walkman" variety and cassette players combined with portable radios and televisions add to the list.

It is wrong to assume that these will continue to work at peak performance without servicing. Regular cleaning of the heads and tape transport mechanism is essential. This can be done using a cleaning cassette in accordance with the manufacturer's instructions.

If this is not done, deposits of oxide rubbed from the tape surface will build up on the record/playback head and spoil high-frequency performance. The sound will then be muffled and there may be incomplete "wiping off" when the erase head is involved.

In severe cases, ordinary cleaning will be inadequate and more extensive manual cleaning required. Further servicing requires head demagnetising and the most

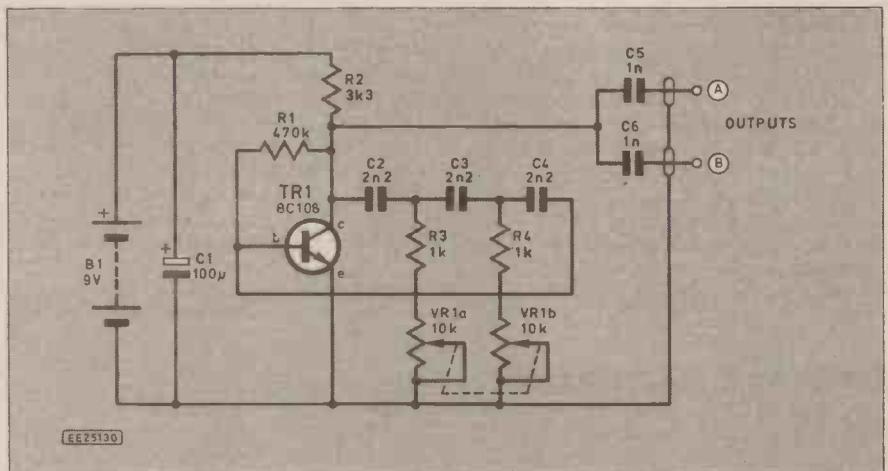


Fig. 1. Complete circuit diagram for the Azimuth Adjustment Aid.

convenient way of doing this is to use an electronic demagnetising cassette. This is necessary since, over a period of time, the

record/playback head can become magnetised - again, resulting in poor high-frequency response.

## REPLACEMENT


Unfortunately, even with regular servicing, there will come a time when the heads become excessively worn and reach the end of their useful life. The above measures will then fail to restore sound quality.

Many a cassette player is discarded for this reason when there are still years of life left in it. It is a relatively inexpensive job to replace worn out heads and restore "as new" performance. Advertisers in this magazine supply replacement heads which will fit virtually all machines.

However, the new record/playback head will need to be adjusted so that the gap, over which the tape passes, is accurately aligned to be at right angles to the direction of tape travel - this is called "azimuth adjustment".

Adjustment is simply a matter of turning one small screw. However, if this is not done properly, high-frequency response will, once again, suffer.

Accurate adjustment needs a tape on which is recorded a high frequency tone. This is listened to as the azimuth adjustment is made. When playback reaches maximum volume, the adjustment is cor-

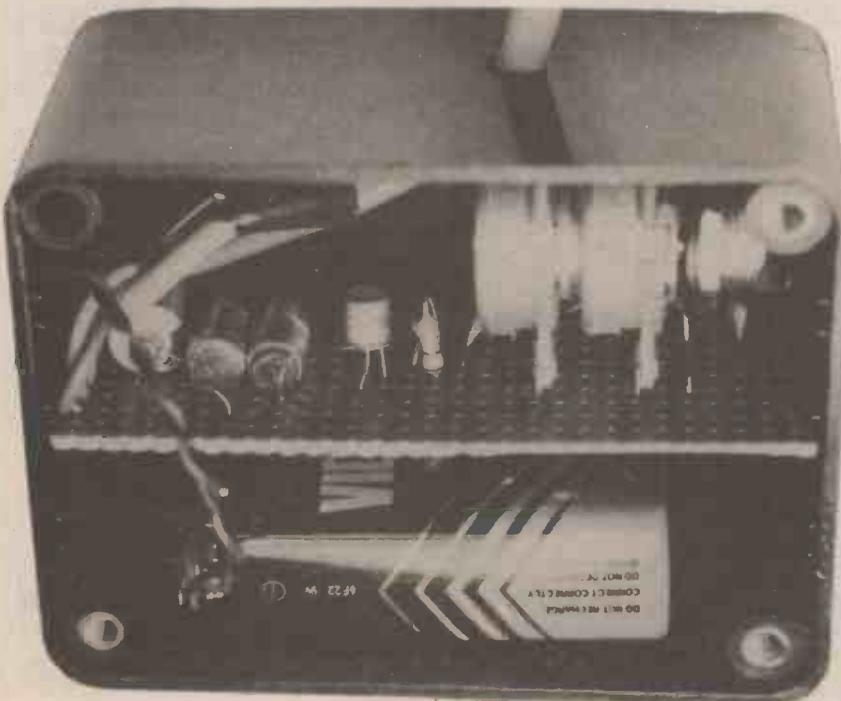

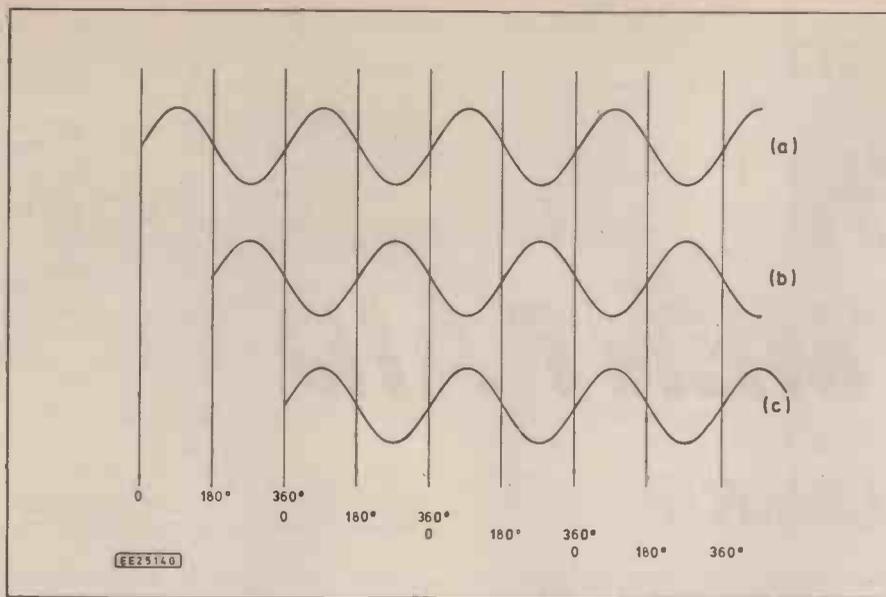


Fig. 2. Waveforms showing phase-shift differences in the circuit.

rect. It often happens that azimuth adjustment will give a new lease of life to the machine even when the record/replay head is slightly worn.

The present project is a sine-wave oscillator which produces a tone of approximately 8kHz which is a very high pitched whistle. The unit is plugged into the input socket of a tape recorder known to be in good condition and a recording made. The recording is then preserved and used as a master tape in making the azimuth adjustment on other machines.

### CIRCUIT DESCRIPTION

The complete circuit for the Azimuth Adjustment Aid is shown in Fig. 1. This is a phase-shift oscillator and works in the following way.

Consider for a moment an a.c. signal at transistor TR1 collector (c). Furthermore, imagine that a complete wave occupies 360 degrees (see Fig. 2a). Each of circuit elements C2 and R3/VR1a, C3 and

R4/VR1b together with capacitor C4 introduce a change of phase to this signal.

This means that the wave falls out of step with the original. The amount by which it is out of phase is specified as a number of degrees (remembering that a complete wave occupies 360 degrees). Thus, the wave would be totally out of step if the phase difference were 180 degrees – that is, one half of a wave (see Fig. 2b).

With any particular component values in the circuit elements above, there will be one particular frequency where the phase change is exactly 60 degrees per stage. The effect of the three circuit elements in cascade, is therefore to produce a phase difference of 180 degrees.

The output from capacitor C4 is directly coupled to TR1 base (b) which amplifies it and introduces a further phase change of 180 degrees due to its own action. The overall effect is that the new signal arrives at the collector with a phase difference of 360 degrees compared with the original – that is, the waves are in step with one another (see Fig. 2c).

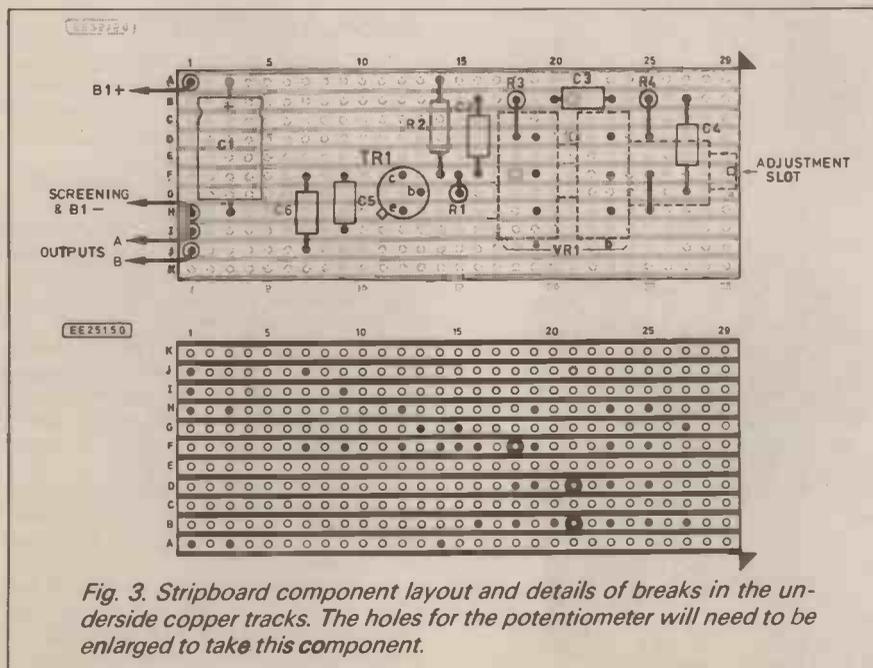


Fig. 3. Stripboard component layout and details of breaks in the underside copper tracks. The holes for the potentiometer will need to be enlarged to take this component.

The new signal now matches the original and re-inforces it. Each circuit element introduces quite a lot of signal loss so TR1 needs to be a high-gain transistor to give sufficient "boost" and maintain oscillation.

The output appears as a sine wave between TR1 collector and emitter (e). At first sight, there seems no reason why the circuit should begin oscillating in the absence of an initial signal on which the transistor can operate. However, in practice, stray noise and pick-up provide sufficient input for the process to begin. The circuit then works selectively on the frequency which gives the necessary 360 degree phase change. By altering the setting of potentiometer VR1, the required frequency may be selected. VR1a and VR1b comprise both sections of a dual potentiometer so adjustment of one automatically adjusts the other. In the prototype unit, this provides adjustment between limits of 3 kHz and 14 kHz approximately. At the end of construction it will be set to deliver a frequency of 8kHz approximately. Resistor R1 applies base bias and R2 acts as a load resistor for TR1. Capacitors C5 and C6 allow the a.c. signal from TR1 collector to pass to each channel of the stereo output.

### CONSTRUCTION

Construction is based on a circuit panel made from a piece of 0.1 in. matrix strip-board size 11 strips x 29 holes (see Fig. 3). Cut this to size and file it carefully to fit the slots of the specified plastic box.

Make the inter-strip link and track breaks as indicated then solder the on-board components into position as shown in Fig. 3, except for VR1. Before fitting the dual-ganged potentiometer VR1, cut the spindle to a length of 3mm and make a cross cut using a hacksaw – this will enable it to be adjusted with a screwdriver at the end of construction.

Note that VR1 fits the stripboard matrix but the holes occupied by the tags will need to be drilled slightly larger. When doing

### COMPONENTS

#### Resistors

R1 470k  
R2 3k3  
R3, R4 1k (2 off)

All 0.25W 5% carbon

#### Potentiometer

VR1 10k dual-track p.c.b. mounting, lin.

#### Capacitors

C1 100µ axial elec. 16V  
C2, C3, C4 2n2 ceramic (3 off)  
C5, C6 1n polystyrene (2 off)

#### Semiconductor

TR1 BC108 npn silicon

#### Miscellaneous

Stripboard 0.1in. matrix, size 11 strips x 29 holes; plastic case, size 76mm x 58mm x 38.5mm internal; B1 PP3 battery and connector to suit; miniature twin screened wire, approx. 50cm; connectors to suit tape recorder input; adhesive fixing pad; connecting wire; solder etc.

Approx cost.  
Guidance only

£8

this, take care to avoid breaking any tracks – if you do, solder a short bridging wire across any gap. Solder a 10cm piece of light-duty stranded connecting wire to copper strip A and a 2cm piece of similar wire to Strip H.

Drill a hole in the rear of the box for the output lead to pass through. With the circuit panel in place, measure the position of VR1 spindle and mark this on the inside of the box. Remove the circuit panel and drill the marked position with a hole 4mm in diameter through which VR1 may be adjusted with a small screwdriver.

Mount remaining components and, referring to Fig. 4, complete the internal wiring. Use a piece of light-duty twin screened wire for the output lead – 50 cm. will probably be found sufficient. Solder the inner conductors to copper strips I and J. Twist the screening, sleeve 2cm of it and trim off any excess. Solder this and the negative battery connector wire to the “free” end of the wire already soldered to strip H. Insulate the bare ends with p.v.c. tape (see photograph).

Pass the signal wire through the hole in the case already drilled for the purpose and tie a piece of string tightly around it on the inside so that it cannot pull free in use. Adjust VR1 to approximately mid-track position and replace the circuit panel. Connect the battery and secure it to the side of the box using a double-sided adhesive fixing pad.

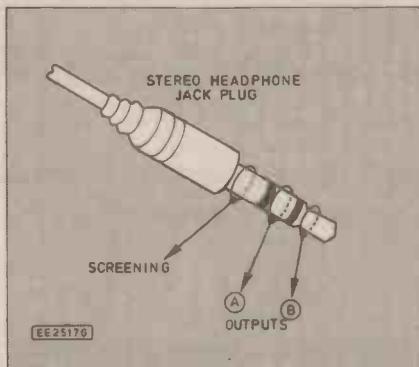


Fig. 5. Test set-up using a pair of stereo headphones.

## TESTING

Make a basic test by connecting a pair of stereo headphones to the output lead as shown in Fig. 5. Twisted connections are in order here since short circuits will cause no harm.

When the unit is switched on, a whistle should be heard whose pitch depends on VR1 adjustment – clockwise rotation increases the frequency. Adjust VR1 so that the whistle is very high-pitched – about 1/16th turn of VR1 anticlockwise from the highest pitch which can be heard.

The exact frequency is unimportant but should lie in the range 7kHz to 10kHz. Readers having access to an oscilloscope can use this to adjust frequency.

The master tape is made on a tape machine known to be in good condition. A high-quality recorder will give best results. Attach connector(s) to the ends of the output wires to suit the recorder input. The microphone input will be found most convenient to use because this is easily accessible.

If there are manual recording level controls set them to zero. Before switching the amplifier on, turn the volume control to

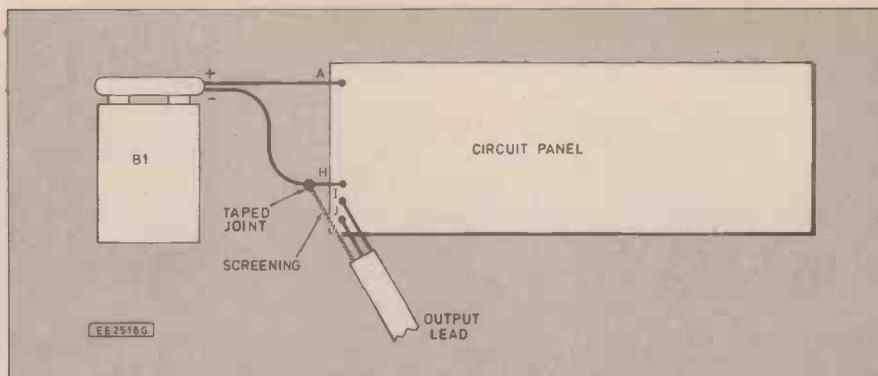


Fig. 4. Interwiring from the circuit battery board to the screened output lead and battery.

zero – this is very important. Switch off any noise reduction system.

Start recording and advance the level controls until the VU meters show the correct signal strength. This will be found with the controls only slightly advanced.

With automatic machines, try a test recording. Turn the amplifier volume control up gently to listen to the test signal. If the recording level is too high, use a less sensitive input – the phono input, for example.

On playback the high pitched whistle should be clearly heard although quite a lot of background noise (tape hiss) is to be expected. If no signal is heard, perhaps the frequency has been set too high for the recorder to handle. Try reducing it a little by anti-clockwise adjustment to VR1.

## AZIMUTH ADJUSTMENT

With all adjustments made, make a recording lasting for at least two minutes. Now, working on the suspect machine, locate the azimuth adjustment screw on the record/playback head (the one with the spring under it). In many machines this screw is easily accessible – sometimes through a small hole. A mirror may be needed and in some case limited dismantling is necessary.

Clean the tape heads before proceeding. If there are any stubborn deposits on the heads and transport mechanism, clean


them off gently using a cotton bud and proprietary cleaning fluid. If a demagnetising cassette is available, use this too.

Now play the test tape and listen carefully. Adjust the azimuth adjustment screw very slowly one way and the other until the whistle is as loud as possible. Even in severe cases, only very small adjustments are needed. With luck, performance will now be restored.

If results are poor and further cleaning does not improve the sound, the fault is likely to be a worn record-playback head. Usually replacement is simply a matter of fitting a new one after any necessary dismantling. Obviously, this is a job which needs patience and care. Be sure to use a head of at least as good a quality as the one being replaced or results will be disappointing.

Solder the wires to the new head cautiously, avoiding excessive heat. Make sure the connections do not touch one another or the surrounding metalwork. The head must then be aligned as previously described. After re-assembling, the tape recorder should sound brand new again!

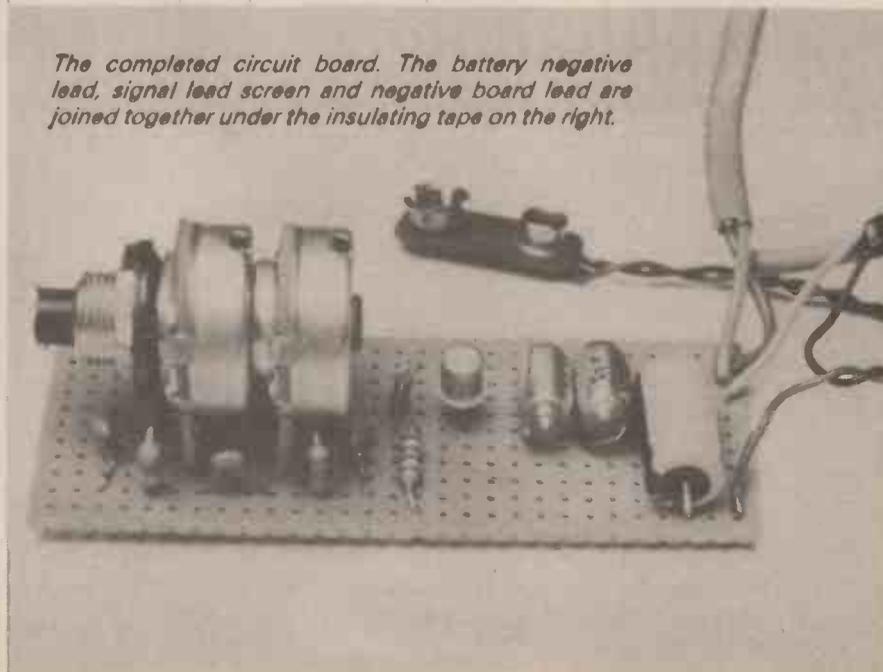Note that no on-off switch has been included. It is therefore necessary to disconnect the battery after use. A switch could be placed in the battery positive wire but this was not thought worthwhile in the prototype. □





# The New Cirkuit Summer Catalogue

- 100s new products
- £10 worth discount vouchers
- Latest books
- Low cost multimeters
- 184 pages
- Only £1.60 available from larger newsagents or directly from Cirkuit



**Cirkuit Distribution Ltd.**  
Park Lane, Broxbourne, Herts EN10 7NQ  
Telephone (0992) 444111

**OUT NOW! OUT NOW! OUT NOW!**



## HART AUDIO KITS — YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HIGH QUALITY REPLACEMENT CASSETTE HEADS

HART KITS give you the opportunity to build the very best engineered hi-fi equipment there is, designed by the leaders in their field, using the best components that are available.

With a HART KIT you have direct access to the friendly HART service, you are not dealing through, or paying for, any middlemen.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

Telephone or write for our FREE LISTS giving full details of all our Kits, components and special offers. Here are a few selected items.

### AUDIO DESIGN 80 WATT POWER AMPLIFIER

This fantastic amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. Featured on the front cover of the May issue of 'Electronics Today International' this complete stereo power amplifier offers World Class performance with the option of a stereo LED power meter and a versatile passive front end giving switched inputs, volume and balance controls. Tape, CD players, or indeed any 'flat' input may therefore be directly connected to bypass tone controls or give a 'stand-alone' facility. The amplifier can also be supplied in 'slave' and 'monobloc' versions without the passive input stage and power meter.

All versions fit within the standard 420x260x75mm case to match our 400 Series Tuner range. ALL power supplies are stabilised, the heavy current supplies using the same most-fit devices as the amplifier. The power supply, using a toroidal transformer, is in fact a complete module contained within a heavy gauge aluminium chassis/heat sink and fitted with IEC mains input and output sockets. All the circuitry is on a proper printed circuit with low-resistance blade connectors for the six stabilised DC outputs. HART KITS don't leave you to fasten a few capacitors to the floor of the main chassis and wire the power supply the hard way! Remember with a HART KIT you get the performance you want at the price quoted through proper engineering design and the right components. We do not insult your intelligence by offering a kit at what seems a fair price and then tell you that you have to spend three times as much to get an upgraded model!

K1100 Complete Stereo Amplifier Kit with LED Power Meter and 3-input Passive Stage. Total cost of all parts is £418.88

Our Discount Price for the Complete Kit ..... £365.98  
K1100S Stereo Slave Version, with plain Front Plate ..... £309.43  
K1100M 'Monobloc' mono version, with plain Front Plate ..... £224.15  
RLH10 Reprints of latest 'Audio Design Amplifier' articles ..... £2.70  
K1100CM HART Construction Manual with full parts lists ..... £4.50

Reprints and construction manual can be purchased separately and their cost credited against subsequent kit purchase.

All versions are supplied with dual primary mains transformers for use on 220/240v or 110/115v mains. Monobloc price does not include the construction manual.

SPECIAL OFFER until the end of February the K1100 kit will be supplied with the new ALPS low noise precision pots at NO EXTRA CHARGE.

### LINSLEY-HOOD 400 SERIES SUPER HIGH QUALITY AM/FM TUNER SYSTEM

This is the ideal companion tuner to the 80W Audio Design Amplifier in any ultimate hi-fi system with case size, front plate layout and even control pitches unified for stacking. Like the 80W Audio Design Amplifier this is your route to DX+ performance for a few tenths of the cost! Two designs by John Linsley Hood make up this combination of his ultra high quality FM tuner and stereo decoder described in 'Electronics Today International' and the Synchrondyne AM receiver described in 'Wireless World'. Novel circuit features in the FM section include ready built pre-aligned front end, phase locked loop demodulator with a response down to DC and advanced sample and hold stereo decoder together making a tuner which sounds better than the best of the high-priced exotics but, thanks to HART engineering, remains very easy to build and set up. The Synchrondyne section with its selectable band width provides the best possible results from Long and Medium wave channels, so necessary in these days of split programming. If you want the very best in real HI-FI listening then this is the tuner for you. Since all components are selected by the designer to give the very best sound this tuner is not cheap, but in terms of its sheer sound quality, it is incredible value for money. To cater for all needs AM only and FM only versions are available as well as the full AM/FM model, with any unit being upgradeable at any time. For further details see our fully illustrated lists.

K400 FM Only version, total cost of all parts is £211.90.  
Our special discount price for complete kit only ..... £189.52  
K400 AM/FM version, Discount Price for complete kit ..... £249.08

### STUART TAPE RECORDER CIRCUITS

Complete stereo record, replay and bias circuit system for reel-to-reel recorders. These circuits will give studio quality with a good tape deck. Separate sections for record and replay give optimum performance and allow a third head monitoring system to be used where the deck has this fitted. Standard 250mV input and output levels. These circuits are ideal for bringing that old valve tape recorder back to life. Suitable stereo heads are available at very reasonable prices.

K900W Stereo Kit with Wound Coils and Twin Meter Drive ..... £90.68  
RJS1 Reprints of Original Descriptive Articles ..... £2.80

### LINSLEY-HOOD CASSETTE RECORDER CIRCUITS

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are suitable for use with any high quality cassette deck. Switched bias and equalisation to cater for chrome and ferric tapes. Very versatile and easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit ..... £57.80  
VU Meters to suit ..... £3.99 each  
RLH1 & 2 Reprints of Original Articles ..... £2.70

Our latest lists also give details of our ranges of specialist high quality AUDIO CONNECTORS and LEADS, cassette decks and seasonal special offers. Write or telephone for your FREE copy. (Overseas 2 IRCs Please, or 5 for Airmail).

Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex. stock. We also stock a wide range of special heads for home construction and industrial users.

HS16 Sendust Alloy Stereo Head. High quality head with excellent frequency response and hyperbolic face for good tape contact. £17.86  
HC40 NEW RANGE High Beta Permalloy Stereo head. Modern space saver design gives excellent high-frequency response with easy fitting and lower cost. Suitable for chrome, metal and ferric tapes, truly a universal replacement head, with ample quality for Hi Fi decks and cheap enough for car players! ..... £6.65  
HX100 Special Offer Stereo Permalloy Head ..... £2.86  
HRP373 Downstream Monitor Stereo Combination Head ..... £44.39  
HQ551 4-Track Record & Play Permalloy Head for auto-reverse car players or quadraphonic recording ..... £16.79  
HS24 Standard Erase Head ..... £2.59  
SM166 2/4 AC Erase Head, Standard Mount ..... £12.60  
HS9510 2/4 Stereo DC Erase Head ..... £8.70  
HQ761E 4/4 AC Erase Head, tracks compatible with HQ551 ..... £57.06

We can supply card reader heads for OEMs at very keen prices.

### REEL TO REEL HEADS

999R 2/4 Record/Play 110mH. Suits Stuart tape Circuits ..... £13.34  
998E 2/4 Erase Head 1mH. Universal Mount. Suits Stuart ..... £11.96

### TAPE RECORDER CARE PRODUCTS

HART TC1 TEST CASSETTE Our famous triple purpose test cassette. Sets tape azimuth, VU level and tape speed ..... £5.36  
DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation ..... £4.08  
DEM115 Electronic, Cassette Type, demagnetizer ..... £8.61

Our new Winter '89 price list is FREE. Send for your copy now. Overseas customers welcome, please send 2 IRCs to cover surface post, or 5 for Airmail.


We now accept inland and overseas orders by post or telephone on all Access, Master and Visa Credit Cards. Please add part cost of carriage and insurance as follows: INLAND: Orders up to £20 — £1; Orders over £20 — £2.50; Next day — £9. OVERSEAS: Please see the ordering information with our lists.

QUALITY AUDIO KITS

24hr SALES LINE  
(0691) 652894

ALL PRICES INCLUDE VAT

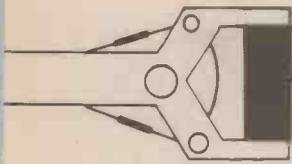**HART**  
HART ELECTRONIC KITS LTD.  
6 PENYLAN MILL  
OSWESTRY, SHROPSHIRE  
SY10 9AF



# Robot Roundup

NIGEL CLARK

## ROBOT OLYMPICS

Wednesday and Thursday, September 26 and 27 should be kept free in the diaries of all robotophiles. The Turing Institute in Glasgow is holding a Robot Olympics which it is hoped will attract all the latest creations of schools, colleges, companies and individuals throughout the world.

Dr Peter Mowforth, who is organising the event, said the idea behind it was to provide a physical forum for the latest robot developments.

At the moment the only way for researchers to find out what other roboticists are doing is to read the journals or speak to each other at conferences. They exchange notes and plans and if they are lucky they might be able to see a video.

But as Mowforth said the video might have taken weeks to prepare and what the researchers want is to see the mistakes as well as the successes. He added that at a recent conference in Japan one of the most popular events had been a collection of video "out-takes" of robot mistakes.

The best way of assessing a robot was to see it operating. Mowforth said that robotics was going through a very interesting phase at the moment. In the last five years, and particularly the last two, there had been a change in thinking about what makes a robot.

Before that most developments concerned the expansion of uses of industrial arms, such as adding sensors and improving software. But now there was a greater concern about the behaviour of robots with a search for intelligent connections between perceptions and actions or inputs and outputs.

There had also been a fall in the cost of components which meant that much worthwhile work was being done outside the traditional academic areas.

Mowforth hoped the event would attract more worldwide interest in the work being done in this country, which 20 years ago led the world in robotics, and in particular the work at the Turing. Finally he wanted it to be fun.

## COMPETITION

There will be a competitive element with a prize for the best robot overall. The judging will be based on the quality and precision of the building of the device, the sophistication of its behaviour and its novelty.

If there are a number of similar robots, hexapods for example, it is intended to have a competition between them.

Anyone is welcome to enter provided their machines conform to the definition of being an autonomous device showing an intelligent link between perception and action. They also had to agree with most people's general prejudices about what constitutes a robot. Automatic washing machines do not qualify.

The interest which had already been generated can be judged from the fact that the event has had to be put back. Originally it

was intended to be held in April for only one day but many potential entrants said that they would be unable to have their projects ready by then.

Anyone interested in participating can contact Dr. Peter Mowforth at: *Turing Institute, 36 North Hanover Street, Glasgow G1 2AD. (Fax: 041 552 6400)*

## TREKKER

An attempt to gauge the value of *Clwyd Technics'* move into the primary school market with an extension pack for its Trekker mobile resulted in more questions than answers. I asked teachers at my local infants and junior schools in St. Albans to assess how useful the two-wheeled vehicle would be in trying to meet the criteria laid down in the craft and technology section of the National Curriculum.

It was quickly apparent that the infants, aged between five and seven, would not benefit from Trekker. It was too complex and sophisticated. Young small hands need something that is simple and robust.

Lights, sensors and fancy dancing are not needed. An ability to show off what the computer is capable of without having components broken off the control board are.

The teachers said that the children found Trekker exciting while running through its demonstration programs and many made suggestions for ways in which the various sensors could be used. It was thought that the use of heat sensors and the magnet might be possible with the infants.

However, there were a number of drawbacks which severely limited its use by children of that age. The switches were too small for their fingers, they could not see the end of the pen, which on the Trekker is held in a holder in the centre of the mobile, so that they had difficulty estimating line length and angle size. It was also thought to be too fragile.

Perhaps it was a little unfair to test Trekker on infants as the extension pack was not intended for children so young. However, it did point to areas which needed to be kept in mind when providing equipment for infants particularly in relation to its ability to withstand a large amount of less-than-careful use.

Shirley Harwood at the junior school was more positive about its possible assistance in the teaching of technology to the older children. She was able to see areas in which Trekker could be used in developing projects to increase the children's understanding of various technical problems.

However, she did not feel she had been able to give it a thorough testing, not because of any difficulties with the equipment or its accompanying documentation, but because of organisational arrangements which had already been made.

Preparing projects for the children to undertake takes time and must be based around the facilities and equipment available at the time. It is difficult to incorporate new unexpected pieces of equipment, particularly ones which need to be worked on without the children so that the teacher can assess how they can be incorporated into the classroom work.

Time is the great enemy in achieving an understanding of a new piece of equipment. Harwood felt that she would need to be able to work with Trekker through the summer holidays to be able to assess how best to use it.

## TEACHER SUPPORT

This raises a number of questions about how to ensure that children have the best resources available to help them in their learning about and understanding of the subject. For once money is not the problem, directly anyway.


If teachers do not have time to assess all the equipment available and how it can best be used, all the money in the council's budget would not make any difference.

It is here that the teacher support, provided by the local authority, is important in providing the necessary advice and training. But even this cannot guarantee success if teachers do not have time to go on courses or properly assimilate the information given. We are now back to money and staffing.

It will be some time before the craft and technology section of the National Curriculum is functioning properly. Today's schoolchildren will be the guinea pigs.



# AMATEUR RADIO SUPPLEMENT

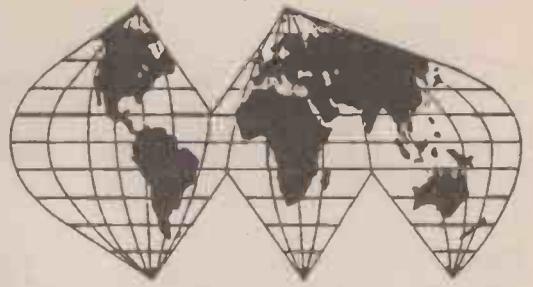

*In this supplement we will consider some of the basic principles of short wave radio, together with two practical projects for you to build. The projects range from the most basic of sets suitable for the absolute beginner, through to a Direct Conversion Receiver (to be published next month) more appropriate for constructors with a reasonable amount of experience at electronics construction. We start with the most basic possible receiver, the crystal set.*

## **Short Wave Reception**

**by Robert Penfold**



### **Radio Signals**

In order to understand the principles of radio you need to know what is meant by a radio signal. A radio signal is just an ordinary a.c. (alternating current) type, very much like the mains supply or an audio signal. The voltage rises from zero in a positive direction, reaches a peak and then falls back to zero again. The voltage then rises and falls again, but is negative in value.

Each pair of positive and negative excursions constitutes one complete cycle. A repetitive a.c. signal has a frequency, which was once expressed as so many cycles per second. These days the term "Hertz" (often just abbreviated to "Hz") is used instead. One cycle per second is the same as one Hertz (1Hz).

The mains frequency is 50 Hertz, which is quite low, at something approaching the lower limit of the audio range (20Hz to 20kHz). High audio frequencies are often expressed in kilohertz (kHz) incidentally, and one kilohertz equals one thousand Hertz. Radio signals are at frequencies above

the audio range, and more or less carry on where the audio spectrum leaves off. The short wave bands lie within the range 1.6MHz to 30MHz. A megahertz (MHz) is equal to one million Hertz, or one thousand kilohertz, and so we are talking here about frequencies that are well beyond the audio range.

Exactly why a high frequency signal fed into a length of wire acting as an aerial results in a radio signal being radiated is one of those things for which there is no easy answer. At this stage it is best just to accept it as a fact. Radio signals are a form of electromagnetic radiation, and they will induce corresponding voltages into any aerial wires that they reach. The strength of these voltages is not likely to be very great in practice.

As the radio signals move outwards from the transmitting aerial they cover an ever wider area, but become weaker. This is just like the light from a bulb or candle becoming weaker further from the light source. Each doubling of distance reduces the signal by a factor of four.

### **Aerials**

It is possible to focus the radio signals into a beam to limit the spreading effect, and enable the energy to be concentrated in one particular direction, like a torch focuses the light from its bulb into a narrow beam. Aerials of this type can be very effective for reception as well. Interference from unwanted stations is reduced as they are mostly out of the aerials field of "view".

Directional aerials almost invariably provide so-called gain, giving stronger signals. Rather than true gain, what they are actually doing is gathering up signals over a relatively large area and concentrating them onto the main receiving element. This gives greater pick-up than the unaided main element can provide.

With short wave signals, especially on the lower frequency bands, it requires some pretty massive aerial arrays in order to achieve even a moderate amount of directivity and gain. Unless you get deeply into short wave radio a simple wire antenna is the order of the day, and the receivers described in this series will

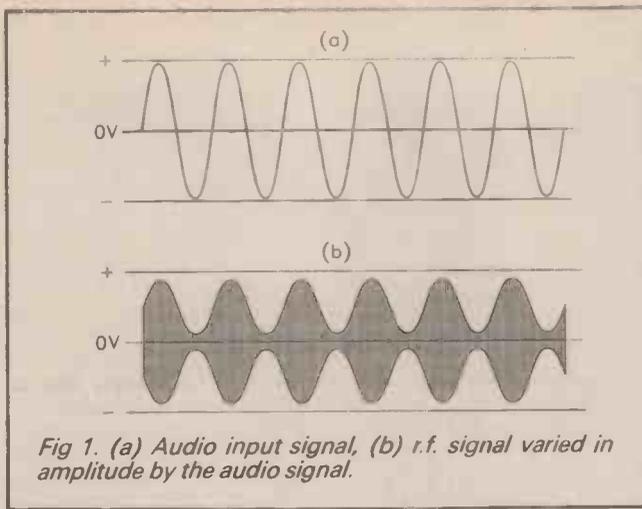


Fig 1. (a) Audio input signal, (b) r.f. signal varied in amplitude by the audio signal.

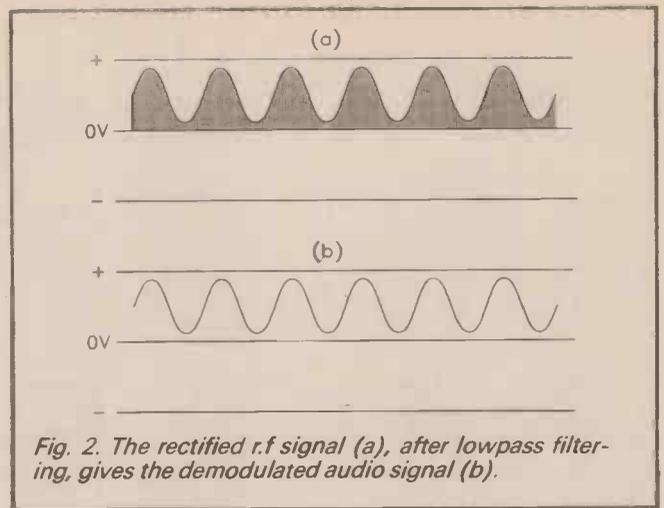


Fig. 2. The rectified r.f. signal (a), after lowpass filtering, gives the demodulated audio signal (b).

give good results when used with simple aerials.

## Modulation

Transmitting a signal from point A to point B is one thing — getting the signal to convey some useful information is another. The most simple method of putting useful information onto a radio signal is simple on/off switching, which is the system used to send messages using Morse code. For communications on the short wave bands the other forms of modulation used are mostly forms of amplitude modulation (a.m.). Frequency modulation of various types is used to a significant extent, but mainly for specialised types of communications such as FAX and tele-type.

In this article we will only be concerned with ordinary a.m. signals, which are the only type used to a significant extent by short wave broadcast stations. It is in fact the same form of modulation that is used by medium and long wave broadcast stations.

I suppose that Morse code sent via radio could be regarded as a very basic form of amplitude modulation. In order to send audio frequency signals a considerably refined form of amplitude modulation is needed. Instead of just on and off switching, proper amplitude modulation has the ability to vary the strength of the signal to any level between these two extremes. The strength of the radio signal is varied in sympathy with the audio input signal. The waveform diagrams of Fig.1 explain this process far better than any words from me. The modulated radio signal is usually termed the "carrier wave" (or just "carrier") incidentally.

## Demodulation

With the transmitter having placed the audio signal onto the carrier wave as variations in strength, the receiver must demodulate the signal to recover the original audio signal. A simple filtering process to produce a signal equal to the average signal level might seem like a viable method of demodulation, but matters are not quite as simple as this. The signal is an a.c. type, and the negative half cycles exactly match the positive ones, giving an average signal level of zero regardless of the modulation level.

In order to recover the audio mod-

ulation the radio frequency signal must be rectified (Fig.2(a)) and then filtered using a simple C — R lowpass filter. The effect of rectification is to give a signal that is always of the same polarity. It does not matter whether it is the positive or negative half cycles that are removed. In either case, the two sets of half cycles will no longer be there to cancel each other out, and the average signal strength will vary in sympathy with the amplitude of the carrier wave.

The lowpass filter has the effect of smoothing out the rectified carrier signal to give an output signal equal to the average carrier level. This is the required audio signal (Fig.2(b)).

## Crystal Set

A crystal set is the most simple of radio receivers, and is actually devoid of any active devices. It does not need a battery — it is the received signal that directly drives the earphone. Obviously this approach does not give very good performance, and I would not suggest that a crystal set is suitable for those wishing to seek out rare and difficult radio stations (or "DXing" as it is known in short wave radio terminology).

On the other hand, a short wave crystal set represents a very simple, inexpensive, but interesting constructional project for beginners and more advanced constructors. It is one of those things that every electronics enthusiast should give a try some time.

It is a real achievement if you manage to pick up a few distant stations from time to time, and it reveals to you just how strong some signals can get. This is an important point, as with any short wave receiver the problem is often not so much one of achieving high enough sensitivity, but one of sorting out the very weak signals from amongst a plethora of strong ones. This is another respect in which a crystal set is not very good. If there are two strong transmissions only a few kilohertz apart, a crystal set will receive them simultaneously. It is up to your hearing mechanisms to sort out one from the other!

## Crystal Set Circuit

This crystal set design is entirely conventional, and has the circuit shown in Fig.3. The first task the circuit must perform is to sort out the required signal from the mass of signals at various frequencies that will be picked up by the

aerial. This is achieved using a parallel tuned circuit which is comprised of VC1 and L1. These provide a low impedance at most frequencies, and effectively short circuit input signals to earth. However, at and around a certain frequency the tuned circuit is at resonance, and will have an extremely high impedance.

Signals at or close to the resonant frequency can pass through to the next stage, while signals at other frequencies are filtered out. VC1 enables the resonant frequency of the tuned circuit to be varied, and it is an ordinary tuning control.

A single tuned circuit does not provide particularly sharp filtering, and this gives a crystal set the poor selectivity mentioned earlier. The Q of an inductor is a measure of its efficiency, and in theory using a high Q coil for L1 will give improved selectivity. In practice matters are not as simple as this.

In order to make optimum use of the limited signal level from the aerial it must be directly coupled to the tuned circuit. Similarly, the detector stage must take the signal direct from the tuned circuit if it is to give a usable output level. Both these factors result in damping of the tuned circuit and an effective lessening of L1's Q value. A high Q coil will optimise results, but in practice, is not likely to provide a degree of selectivity that is noticeably higher than a component having a more modest Q value.

Diode D1 is the demodulator rectifier which in this case passes the positive half cycles and blocks the negative ones. Connecting D1 round the other way so that it is the negative half cycles that are passed will result in the unit still work-

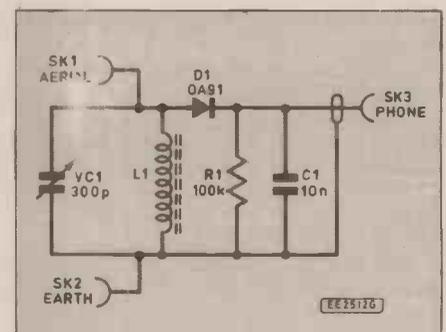


Fig. 3. The circuit diagram of the crystal set. It is purely passive — no battery is needed.

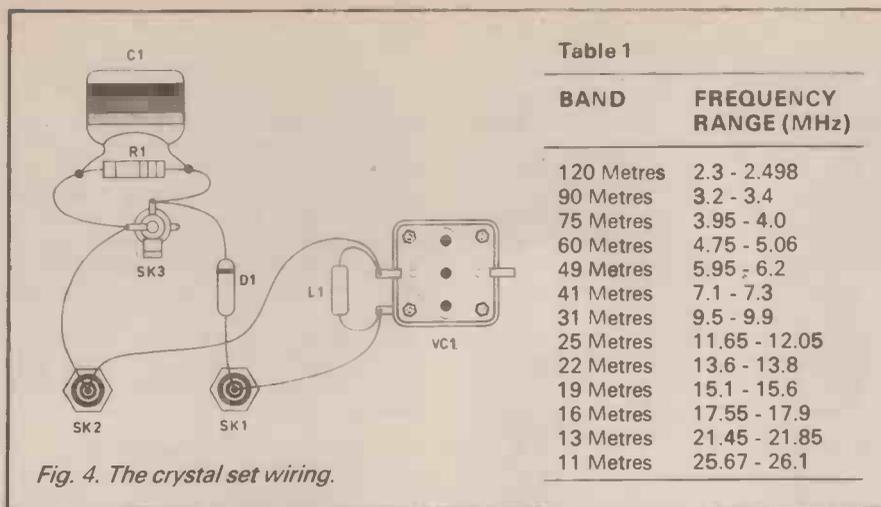


Fig. 4. The crystal set wiring.

Table 1

BAND	FREQUENCY RANGE (MHz)
120 Metres	2.3 - 2.498
90 Metres	3.2 - 3.4
75 Metres	3.95 - 4.0
60 Metres	4.75 - 5.06
49 Metres	5.95 - 6.2
41 Metres	7.1 - 7.3
31 Metres	9.5 - 9.9
25 Metres	11.65 - 12.05
22 Metres	13.6 - 13.8
19 Metres	15.1 - 15.6
16 Metres	17.55 - 17.9
13 Metres	21.45 - 21.85
11 Metres	25.67 - 26.1

ing exactly the same. D1 is a germanium diode and not a modern silicon type.

The problem with a silicon diode is that it does not begin to conduct until the forward voltage reaches about 0.5 volts or so. In many cases the input voltage to the detector will not reach this level, and a silicon diode would give no output at all in such cases. Germanium diodes are well suited to this application as they operate reasonably efficiently at low input voltages. C1 is the filter capacitor which smooths out the rectified radio frequency signal to leave the audio modulation.

## Headphones

Traditionally a crystal set is used with a pair of high impedance (about 4k) magnetic headphones of good sensitivity. Headphones of this type are little used these days, and you would probably find it difficult to obtain a pair. Those that are available tend to be rather expensive. Such headphones represent the best option as far as performance considerations are concerned, but a crystal earphone is much cheaper, readily available, and will provide good results.

Electrically, a crystal earphone appears to be a capacitor of a few nanofarads in value. There is no discharge path for C1 through the earphone, and as a result of this C1 tends to charge up to the peak input voltage and hold that charge. Resistor R1 provides a discharge path for C1 so that the required demodulator action is obtained. R1 is not required if the output of the unit will only be fed to high impedance magnetic headphones. These do have a fairly low resistance that will provide the necessary discharge path for C1. The set is unlikely to work at all using any low or medium impedance earphone or headphone.

## Construction

With a unit as simple as this there is little point in bothering with a circuit board. It is an easy matter to hard-wire the project. Virtually any small metal or plastic case should suffice for this unit. I used a plastic type having an aluminium front panel and approximate outside dimensions of 130 by 68 by 40 millimetres. The layout of the front panel is not too important, but try to choose one that will avoid any long wires.

Variable capacitor VC1 can be an air spaced component, but I found that using an inexpensive plastic dielectric type gave results that were not noticeably different to those obtained using a high quality component. A Jackson "Type O" 365p air spaced component requires three short 4BA countersunk mounting screws which fit into the threaded holes in the front plate of the component. These screws must be quite short (no more than about 6 millimetres in length) or they might protrude too far into the capacitor and damage its plates.

If you use an inexpensive plastic dielectric component it might be supplied with suitable fixing screws. Often the easiest way of mounting these components is to glue them in place using a good quality adhesive such as an epoxy type. Although a value of 300p is quoted for VC1 in the components list, in practice any value of between about 250 and 500p should be suitable. Try to avoid inexpensive variable capacitors which have miniature spindles. It could prove difficult to locate a control knob to fit one of these!

## Coverage

For L1 the prototype has an ordi-

nary r.f. choke having a value of 2.2 microhenries. This gives coverage from about 5.5Mhz to 16MHz, which includes several of the popular short wave broadcast bands (see Table 1). Using a component of suitable value for L1 the unit can be made to cover any band from the long wave band through to the upper end of the short wave spectrum.

The bands covered with the specified value are those which are most likely to furnish some interesting stations. Although the receiver can be made to cover other bands it might not receive any signals at a strength which will provide an audible output. You might like to experiment with other values though.

You can try winding your own inductors. Half a dozen turns of 22 s.w.g. enamelled copper wire on a piece of 10 millimetre diameter ferrite rod will provide good results. Use fewer turns to move the coverage higher in frequency, or more turns in order to shift the coverage in the low frequency direction. Even coils wound on wooden or plastic formers with no ferrite core seem to give quite good results.

## Wiring

Details of the crystal set wiring are shown in Fig.4. This is mostly straightforward, but there are a couple of points to bear in mind. D1 is a germanium diode, and as such it is more vulnerable to heat damage than the more familiar silicon devices. The risk of damaging this device when soldering it in place is not severe since its leadout wires will probably be left quite long. However, try to complete the soldered joints to this component reasonably quickly.

Probably the best way of fitting R1 and C1 is to first twist the leads of C1 around those of R1, then solder C1 onto R1, and finally fit this little assembly onto SK3. Making connections to VC1 and the sockets should be easy provided you tin all the tags and the ends of wires prior to attempting to complete any joints.

## A Suitable Aerial

At one extreme, the aerial can simply consist of some ordinary p.v.c. connecting wire dangled out of an upstairs window, strung around a picture rail or loft, or something of this type. At the opposite extreme, it can be made from proper aerial wire, strung outside between two trees, aerial masts, or whatever, with an overall length of 40 metres or more. About 5 metres or so of wire mounted as high as possible indoors will provide better results than you might expect. When initially testing the prototype I received the English service of Helsinki Radio using an aerial of this type. Obviously an outdoor aerial will give better results, especially when propagation conditions are poor.

The main point to note if you are using an outdoor aerial are that the antenna is installed as high as possible, and as far away from buildings as possible. The wire needs to be insulated from any earthed objects, which means any building, tree, mast, etc. For a receiving aerial there is no real need to resort to anything particularly elaborate though. Use some plastic twine to connect the far end of the aerial to its support for instance. Protect the insulation on the aerial wire with some added sleeving at

## COMPONENTS

### Resistor

R1 100k 5% carbon film

### Capacitors

C1 10n polyester  
VC1 300p variable (see text)

### Semiconductors

D1 0A91 germanium diode

### Miscellaneous

L1 2μ2 r.f. choke (see text)  
SK1 red 4mm socket  
SK2 black 4mm socket  
SK3 3.5mm jack socket

Control knob; crystal or high impedance earphone; case approx 130 x 68 x 40mm; plugs and wire for aerial and earth connections — see text; connecting wire; 100p capacitor — optional, see text.

Approx cost.  
Guidance only

£6

any points where there is a risk of it chafing and wearing through.

When using a long aerial with any very simple receiver there is a risk that loading effects will reduce selectivity to an unusable level, with a jumble of stations being received simultaneously. If you use a long aerial with this receiver, you might find that under most conditions results are better if the aerial is connected to SK1 by way of a capacitor of around 100p in value. This will give reduced signal strengths, but the volume should still be quite good, and selectivity will be much improved.

## Earth

An earth connection merely consists of


a piece of metal which is buried in the ground and connected to the receiver via a piece of wire that should be kept as short as possible. The most popular form of earth connection is a piece of metal pipe pushed into the ground.

The benefit of an earth connection depends to a large extent on the frequency in use. On the lower frequency bands it can substantially boost signal strengths, whereas it is likely to make no noticeable difference at all on the high frequency bands.

Using the set is very easy, since there is only the tuning control to contend with. The bandwidth of the receiver is wide enough to make slow motion tuning drives unnecessary. The main require-

ment is patience on the part of the user. Interesting stations will appear, often to fade out again soon after, then reappear, and so on.

If you have the patience you can usually identify a station, since most short wave broadcast stations put out frequent station identification messages. This station fading is not due to deficiencies in the receiver, but is caused by the vagaries of the atmosphere and the propagation of radio signals. Even if you have the best short wave radio in the world, fading will still be a problem, and you will still need to exercise patience in order to find and identify weak DX stations. □

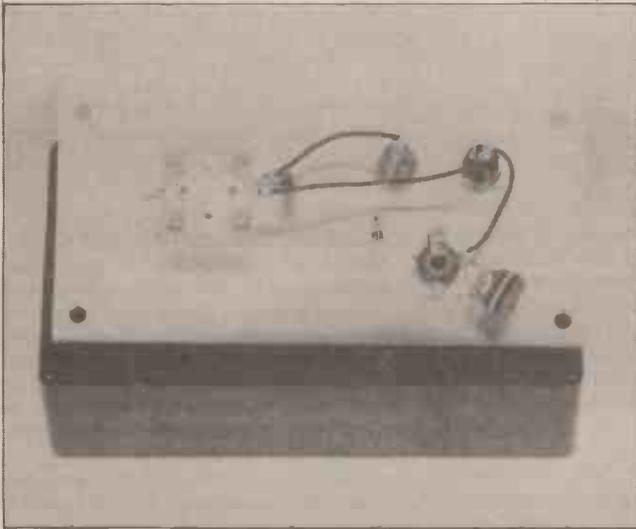

# DIY Aerials

by George Hylton



**T**HE sunspot cycle is now near its maximum. Short-wave broadcasts from distant lands can be picked up. Ideally, a nice long outdoor aerial should be used, but if like me you live in a flat with no garden this may not be possible. Here are some hints and tips which can often help to improve reception at little cost.

Because receivers differ in design, and no two receiving locations are identical it will pay to experiment. Remember too, that even in the best conditions short-wave reception is usually worse than reception on long and medium waves, and much worse than v.h.f./f.m. But you may still find the effort rewarding, because short waves provide a window on a range of human activities which runs from political propaganda and religious exhortation, to exotic music, information about little known places, and even special programmes for listeners with some knowledge of electronics.

## Interference

There are two sorts of interference;

local electrical noise from the mains and from appliances inside the house, and interference from more distant sources that arrives through the air along with the radio broadcasts. Inside-the-house interference can obviously be reduced by fitting an outside aerial, that is, by removing the aerial, or at least part of it, from the interference.

For the flat-dweller or similarly restricted listener probably the most that can be done in the way of an external aerial is to mount a whip aerial (Fig.1a) on the wall by a window, or on the window sill, or simply to hang a wire from the window. The lead-in ("downlead") can pass through a (slightly open) window, or through a hole in the window frame or in some cases the wall.

If drilling holes is forbidden and the window must be firmly closed it is possible to couple the aerial through the glass by sticking one metal pad to the outside and another to the inside. The glass pane in between forms the dielectric of a capacitor and the metal

pads the plates. A cheap and easy metal pad is a piece of aluminium cooking foil. For a single-glazed window it can be quite small (say the size of a small saucer or the top of a teacup). Wires can't be soldered to aluminium (at least not with ordinary solder) but a line-contact connection formed by laying a few centimetres of bared wire across the foil and sticking it down with tape will serve.

A wall-mounting bracket for a whip can be made by bending a piece of metal pipe, or stout plastic pipe, and fixing it with nails or screws (Fig.1b). (Masonry nails if it must be fixed to the wall). If the whip is a push-fit into the pipe the bared end of the downlead can be wedged in as shown to form a connection.

If you have a TV aerial on the roof you might try using its downlead as a short-wave aerial. With the usual co-axial cable a connection to the "outer" only should suffice, so that the normal use of the aerial for TV is not affected. It must be remembered, however, that TVs themselves create interference in the form of line-timebase harmonics. You may only

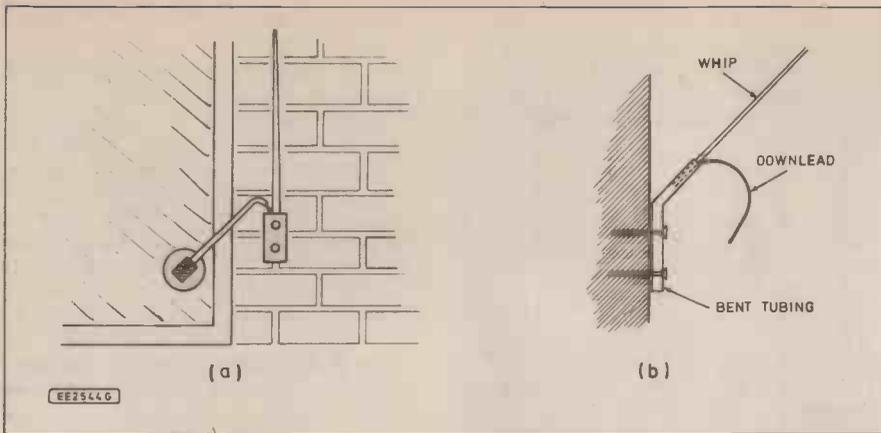


Fig. 1(a). External whip aerial with capacitive coupling through the window glass. (b) Simple mounting bracket.

be able to use the downlead when the TV is off.

## Aerial-to-Receiver Connections

The more expensive types of commercial receiver have special aerial (antenna) terminals. The cheaper ones usually don't. They have a pull-out whip for a SW aerial, and no earth terminal. Don't despair! Connections are easily improvised, without doing any modifications to the receiver circuitry.

The SW performance can often be improved significantly simply by standing the receiver on a metal surface. This increases the efficiency of the whip aerial. If you have no ready-made metal surfaces, use a metal tray, or a large piece of aluminium foil. It may work better if the receiver is laid on its back on the foil.

The foil acts as a sort of r.f. earth, even though it isn't physically earthed. For an aerial connection, the simplest arrangement is to wrap the insulated downlead a few times round the base of the built-in whip (Fig.2). Note that the insulation is not removed. The connection is a capacitive one, using the insulation as a dielectric. The capacitance so formed is small, and this is important.

In the cheaper sort of receiver the whip is connected directly (Fig.3) to the aerial tuned circuit L1/C1. Here C1 is the tuning capacitor and the capacitance to "earth" of the whip adds to it. Making a

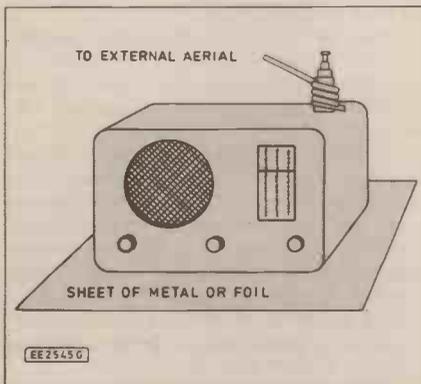


Fig. 2. Where no aerial terminals exist an external aerial can be coupled by wrapping its insulated downlead round the built-in whip aerial. Note that no direct connection is made. Placing the receiver on a sheet of metal often improves reception.

direct connection to an external whip can easily throw enough extra capacitance across C1 to upset the tuning. This is likely to wipe out any advantage gained from increased signal strength.

## Indoor Aerials

The trouble with indoor aerials is that they are guaranteed to pick up the maximum amount of mains-borne interference. Also, since most buildings attenuate the incoming radio signals to some extent (steel-framed blocks of flats worst of all) the signal-to-noise ratio is degraded. Nevertheless, indoor aerials can work.

It nearly always pays to experiment to find the best position for the aerial, but near an outside wall is a good bet, and so is in front of a window. If you know where electrical wiring runs in the walls, keep your aerial well clear.

For a receiver with no special aerial terminals practically the only simple indoor aerial worth trying is just a few metres of insulated wire, coupled capacitively to the built-in whip as already described (Fig.2).

The trouble with this type of aerial, however, is that it has a relatively high impedance. This makes it rather good at picking up local interference by capacitive coupling to the mains wiring of the house. If you are greatly troubled by this sort of interference (usually generated by anything that arcs or sparks, such as

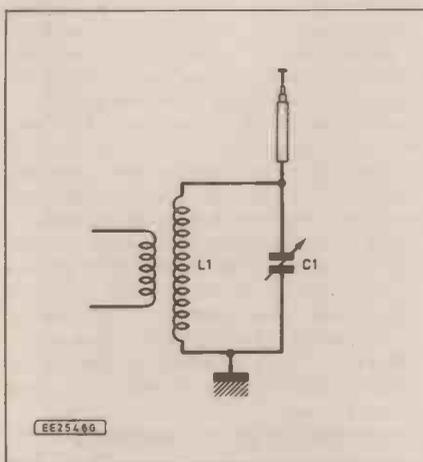


Fig. 3. In many receivers the built-in whip is connected directly to the live side of the signal-frequency tuned circuit L1/C1.

the brushes of motors in domestic appliances, also fluorescent lamps) you may find it worthwhile to use a low-impedance loop aerial.

## Mains Leads

Before describing the loop aerial a point about battery versus mains operation is worthwhile. The mains circuits are apt to be full of interference of the type just described. The mains connecting lead brings this to the receiver. Purpose-built short-wave receivers may have mains filters to reduce this. Ordinary receivers don't. Their mains leads are a pathway which brings interference straight into the heart of the receiver.

Mains leads also act as aerials, bringing to the receiver signals picked up by the house wiring. For this reason they have occasionally been deliberately used (taking precautions against shock) as aerials. The results, in general, are poor, and the practice has died a natural death.

It will be clear that interference may be reduced by dispensing with the mains lead and operating the receiver from internal batteries.

## Short-Wave Loops

The ferrite rod aerials now almost universally used for medium and long wave reception are a special form of loop aerial. The "loop" in this case is the little coil of wire wound round the ferrite rod. The function of the rod is to concentrate the magnetic field of the incoming radio wave so that the amount of signal voltage induced in the loop is increased.

There is no reason, in principle, why ferrite rod aerials should not be used for short-wave reception. Unfortunately, practical considerations get in the way. The amount of voltage induced in a loop depends on the number of turns: a short-wave coil needs to have a low inductance, so it has few turns. Ferrite material has losses (i.e. it dissipates energy) which increase with frequency. Special high-frequency ferrite can be made, but it is less good at concentrating the field than the lower-frequency kind. The result is that in practice ferrite short-wave loop aerials are less efficient than another sort of loop.

## One-Turn Loops

The single-turn tuned loop (Fig.4) is the better alternative. As mentioned previously the amount of signal voltage increases with the number of turns. On this

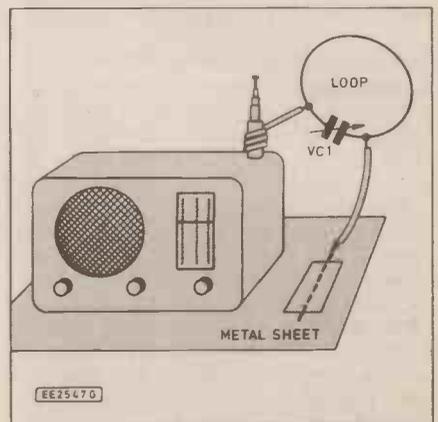


Fig. 4. Coupling arrangements for a tuned loop aerial.

basis a one-turn loop seems a poor bet. Fortunately, pickup is also proportional to the area of the loop, and this compensates for the reduction in turns.

Practical indoor loops can have diameters up to about a metre, which gives about 10,000 times the area of one turn on a ferrite rod. Loops of any shape (e.g. square) may be used, but long thin shapes are inefficient.

If you have a receiver with built-in terminals for an external aerial connection you can try an untuned one-turn loop as an indoor aerial. For ordinary receivers (and often for special SW receivers too), a tuned loop gives better results. Fig.4 shows one method of coupling to an ordinary receiver, using the capacitive wrap-around coupling to the whip for one leg and a taped-down direct connection to the metal or foil base sheet as the other. Variable capacitor VC1 (which can be a "medium-wave" type salvaged from an old receiver) is used for tuning. Tuning is fairly broad and should hold good over any one SW broadcast band.

A circular loop of one metre diameter made from any sort of wire (hookup wire, mains flex, etc.) has an inductance in the region of  $4\mu\text{H}$ . A tuning capacitor of 250pF maximum (typical for a miniature foil-dielectric type as used in MW receivers) gives a lowest tuned frequency of about 5MHz.

The highest tunable frequency depends on the minimum value of the tuning capacitance. This depends on the setting of the trimming capacitor (which is normally part of the tuning capacitor assembly), plus the input capacitance of the receiver (which depends on the number of turns wrapped round the whip) plus the stray capacitance between the two downleads (which can be minimised by keeping them short and well apart). In practice it is generally possible to achieve a 2:1 tuning ratio (e.g. 5 to 10MHz) and by minimising the strays, setting the trimmer to minimum, and using fewer coupling turns you might get a 3:1 ratio (e.g. 5 to 15MHz).

Tuning capacitors from radios are normally two-gang capacitors, so the capacitance can be increased by connecting the two sections in parallel. Air-spaced tuning capacitors from old valve radios usually have higher capacitance, such as  $365 + 365\text{pF}$  or  $450 + 450\text{pF}$ . These high values give a greater tuning ratio, but may need a smaller loop, which is less efficient as an aerial. They are, however, good for use with our next kind of aerial.

## Low-Impedance Loops

Although wire loops often work well indoors they do have fairly high impedance. This can be reduced by reducing the inductance and increasing the capacitance. With wire as a constructional material the only simple way of reducing the inductance is to reduce the loop area, but this reduces sensitivity. The answer is to abandon wire in favour of broad strips of metal. These act in effect as if they were several wires in parallel and the inductance falls even though the loop diameter is unchanged or even increased, within reason.

Metal strip is expensive, but for loop materials use can be made of the fact that at high frequencies the currents flow

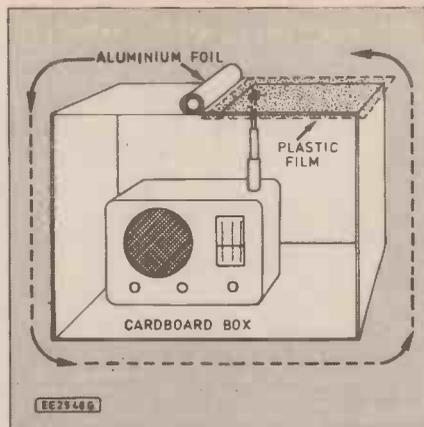


Fig. 5. Box loop. This is tuned by rolling the loose end of the foil over the plastic film.

only on the outer skin of a conductor. So very thin strip can be used, and this is available in handy rolls in the form of aluminium kitchen foil. (At the time of writing this article I bought a roll, 330mm wide and 50m long for £1.80.)

## Box Loop

The simplest and cheapest broad-strip loop aerial doesn't even require a tuning capacitor. It's made (Fig.5) by taping the end of a roll of foil to the top of a large cardboard box, and unrolling the foil round the box and back to where it started. To prevent the loose end from shorting to the taped-down end a sheet of thin plastic film (e.g. from a shopping bag) is placed over the foil as shown. When the loose end is rolled over this foil the resulting sandwich forms a capacitor. Tuning is carried out by rolling or unrolling the foil to vary the overlap.

The receiver can be coupled by standing it inside the box and extending the whip to touch the underside near the gap in the top foil. Coupling capacitance can if necessary be increased by giving the top of the whip a "hat" of foil to increase its area.

Tuning is sharp, but unstable. Stability can be increased, once the approximate tuning point is found, by placing a book on either side of the roll. The roll can be inched along by sliding the books.

The box loop is very effective in reducing breakthrough by powerful local signals (e.g. the local TV transmitter) as well as giving good sensitivity to the wanted signals. Clearly, a large box is desirable, and indeed necessary if the lowest short-wave bands are to be tunable. The box can be of any non-conducting material (wood, plastic) and structures such as wooden cupboards and bookshelves can be used. Avoid having large areas or loops of metal (saucepans etc) in the field of the loop; these reduce sensitivity.

Foil of almost any width can be used with roller tuning, because the reduction in inductance caused by using a wider foil is offset by the increased capacitance due to the greater overlap area.

## Loop Orientation

So far nothing has been said about the positioning of a loop, though it will be obvious that the best position should be found by trial and error. It is well known that loops are directional. They give maximum response to signals arriv-

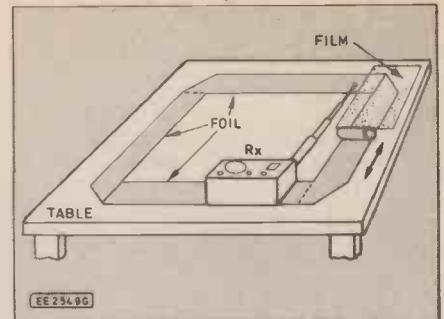


Fig. 6. Horizontal foil loop. The whip aerial must not make contact with the foil but should be extended over it as shown.

ing edge-on and minimum to signals arriving broadside on. This directional property can be used to reduce interference from strong local transmitters. But when a distant transmission is tuned in it is found that rotating the loop often makes little difference to signal strength. The reason is that the same signal often arrives simultaneously from several slightly different directions, having been reflected from different parts of the ionosphere.

For the same reason, the original polarization of the waves is blurred. A vertical aerial radiates a vertically polarized signal and this calls for a vertically orientated receiving aerial. However, reflection by the ionosphere usually results in some of the signal arriving with horizontal polarization.

## Table-Top Loop

The table-top loop is useful to the short-wave listener because it enables a flat, horizontal loop to be used if this is more convenient. This leads to the arrangement shown in Fig.6. The table must be of a non-conducting material and must embody no large loops of metal such as an all-round-the-edge metal trim or a metal frame.

## Unobtrusive Loops

Loops in general are not compatible with domestic elegance. Having convinced yourself by experiment that a loop aerial is worth having you may well want to hide it from view. It is often quite easy to hide the loop itself.

For example, a wire loop might be run round (or behind) a picture frame. It still has to be coupled to the receiver, however, and this can make its presence obvious.

One trick which can help makes use of the fact that if a second, smaller loop is placed in the field of the loop aerial signal from the aerial is coupled to the smaller loop. A small loop (Fig. 7) can take the form of one or two turns of insulated wire run round the cabinet of the receiver or taped to the back. A wrap-around coupling to a whip aerial can be made as before.

In the absence of a metal-plate base the "earth" connection can be made to a sheet of foil taped to the base of the cabinet or to battery negative. This gives a completely indirect form of coupling, enabling the receiver, when not being used with a loop, to be picked up and carried about the house. The presence of the coupling loop does not interfere with

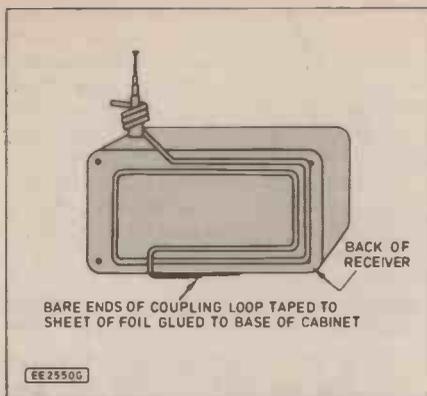


Fig. 7. How to attach a coupling loop to the receiver.

normal reception of medium and long wave and V.H.F. transmissions.

The tuning capacitor (or roll) of the main loop can be hard to hide. One possibility is to run a horizontal loop round the underside of a table top. A conventional tuning capacitor may be fixed where it is accessible but hidden by the table-top.

This is difficult when a rolling-foil tuner is used. One possible way out (Fig.8a) is to lay a gapped foil loop on the table then cover it with a thin tablecloth, not shown, (preferably of a low-loss material such as nylon). A metal tray (or wooden tray with foil stuck to its bottom) is placed on the cloth so as to straddle the hidden gap. there are now two capacitances from foil to tray, in series across the gap (Fig.8b). Moving the tray changes the overlaps and so tunes the loop.

The receiver is fitted with a coupling coil round its base, capacitively coupled

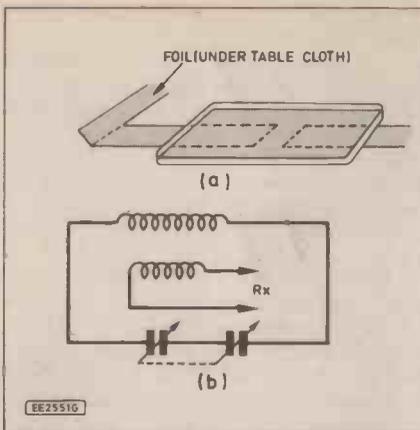


Fig. 8(a). Concealed table-top loop. A thin table cloth (not shown) conceals the foil, and provides a dielectric. A metal tray moved over the gap in the foil tunes the loop. (b) Equivalent loop circuit plus receiver coupling coil.

to the whip in the usual way. the "earth" connection can be either to a foil pad on the back of the set or a direct connection to battery negative (or, in some cases, to the loudspeaker grille if this is metal). With this arrangement you can amaze your friends by boosting short wave signals by moving the tea-tray about!

### Setting Up

When experimenting with aerials you need some way of find out whether signals are really being boosted by your aerial as opposed to being just picked up directly by the receiver itself. It is essential to use battery operation so as to eliminate pickup by the mains lead. The built-in whip aerial should be retracted into the

set as far as possible. When your aerial is working efficiently it should make no difference to the received signal strength when you touch the top of the whip with your finger. Use weak signals when making tests.

It is quite likely, when a tuned loop is being set up, that you will find a perceptible lift in signal as the loop is tuned in but that you still get a louder signal when you touch the whip. This indicates that the coupling between the loop and the receiver is incorrect: probably too weak. Try increasing it by wrapping more turns of insulated wire round the whip or putting more turns on the coupling coil. You can also increase coupling by using a larger coupling coil.

With some receivers, tuning the loop may affect the tuning of the receiver itself. This can happen in two ways. First, the coupling of the loop may be strong enough to pull the receiver off tune in some way. You may still be able to find a loop tuning setting which boosts the signal without too much pulling. If not, the only way out is to slacken off the coupling.

The other tuning effect has quite a different cause. You may well find that some weak signals, often associated with whistles which change pitch as the tuning is adjusted, disappear when the loop is tuned in. These are in fact spurious signals which occur at "image" frequencies.

An image frequency differs from the true tuned frequency by twice the intermediate frequency of a superhet receiver. A strong signal on an image frequency may get through the receiver's own built-in aerial tuning, which is not very selective on short waves. A tuned aerial provides some extra selectivity and so attenuates image frequencies. □


# TRF Receiver

by Robert Penfold



THESE days t.r.f. (tuned radio frequency) receivers seem to be out of fashion, and few designs for them appear in the electronics press. This contrasts with the situation ten or twenty years ago when simple t.r.f. designs for the home constructor appeared quite frequently.

Technology may have moved on, but sets of this type surely remain as much fun to build and use as they ever were. Their performance may not equal that of a good superheterodyne (superhet) receiver, but they can still provide some good results. They have the advantage of being simple, relatively inexpensive, and once constructed require no alignment (and hence require no test gear to aid with their alignment). Their main disadvantage is that they are relatively difficult to use, and require a lot of careful adjustment of the feedback control if they are to provide good results.

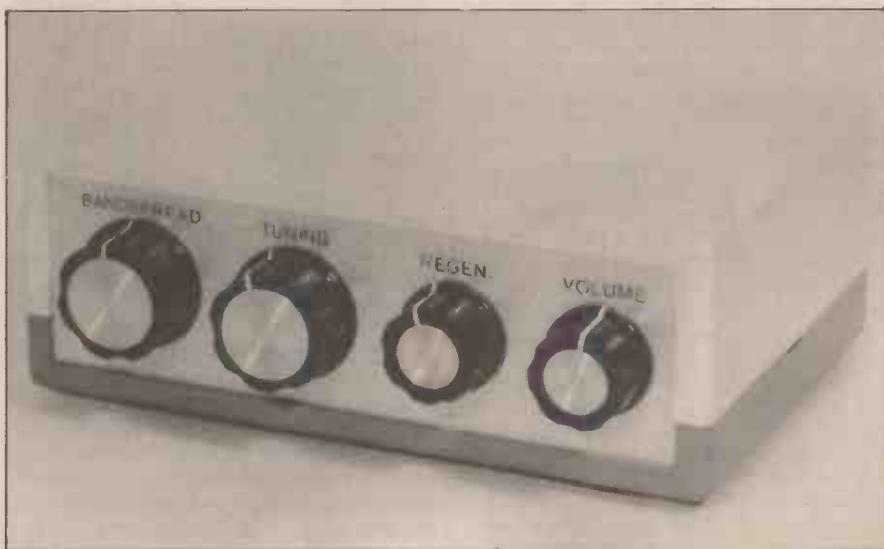

## Regeneration

A t.r.f. or "straight" receiver as it is also known, amplifies the incoming radio signal and then demodulates it without any conversion to an intermediate frequency (as used in a superhet receiver). The problem with this approach is that it is difficult to obtain high gain and selectivity at the high frequencies involved in short wave reception. In order to combat this virtually all t.r.f. receivers use a process called "regeneration", usually in the form of a regenerative detector.

Regeneration is a form of feedback, and is in fact just ordinary positive feedback. In other words, some of the output signal of an r.f. amplifier is fed back to the input, and the circuit is arranged so that the feedback signal is in-phase with the input signal. It therefore tends to reinforce it, and give increased gain.

There is a limit to the amount of feedback that can be used successfully. If this threshold is exceeded, the result is a signal being continuously fed around the amplifier, giving oscillation at the frequency where the amplifier has peak gain. The boost in gain just below this threshold level is quite substantial, and in order to obtain good results the feedback level must be set quite accurately just below the oscillation point.

Unfortunately, even fairly small changes to the setting of the tuning control can necessitate minor adjustments to the regeneration level in order to maintain optimum results. This can be a bit irksome when you first start using a t.r.f. receiver, but you soon get used to this way of doing things.

## Selectivity

A more than slightly useful side effect of regeneration is that it vastly improves selectivity. The reason this occurs is that there is relatively little feedback away from the frequency where the amplifier has its peak response. The more feedback that is applied to the circuit, the greater the disparity between the feedback level

at the centre of the passband and just a little offset from it.

Compared to a superhet receiver having an expensive crystal or mechanical filter the selectivity of a t.r.f. receiver is still relatively poor, but it is vastly better than a crystal set (such as the one described earlier). The improvement in selectivity obtained by using optimum feedback is much greater than one might expect.

Many receivers which utilize positive feedback do not have a diode demodulator. Instead they use some form of regenerative detector. These mostly make use of what is normally an undesirable characteristic of transistors. This is their variations in gain with changes in collector current (or drain current in the case of field effect devices). In general, the gain of a transistor increases with rises in collector current, and decreases with reductions in collector current. This gives what is a rather crude and ineffective form of rectification.

Using regeneration over an amplifier tends to heighten the difference in the amount of amplification on positive and negative half cycles. With the regeneration level optimised, the difference between the peak negative and positive levels is very large, giving very effective rectification of the signal. Simply applying lowpass filtering to the output of the amplifier therefore gives a demodulated signal of good strength. The audio quality is likely to be something less than hi-fi, but is more than adequate for present purposes.

## Coverage

This t.r.f. receiver has been designed primarily for simplicity and cheapness, but it nevertheless provides a useful level of performance. It covers three wavebands, giving coverage from about 1.4MHz to 25MHz. The ranges covered are as follows:

- Range 1 1.4 - 4MHz
- Range 2 4 - 12MHz
- Range 3 8 - 25MHz

The unit does not quite cover up to the 30MHz limit of the short wave range, although it can be adjusted to do so if the wiring to the coil units is kept short enough. This slight lack of coverage is not of any great importance though, since the 13 metre broadcast band is covered by the unit, and is the highest frequency band that is likely to prove worthwhile with a receiver of this type.

In order to avoid the complications of waveband switching the unit uses the alternative of plug-in coils for waveband selection. The Denco plug-in coils that were once the standard choice for a receiver of this type would seem to be no longer available. The coils are therefore ordinary Japanese metal canned types for printed circuit mounting, but fitted onto DIN plugs to facilitate plug-in band changing.

## Circuit

The circuit (Fig. 1) is based on the amplifier formed by TR1 and TR2. These operate as common source and common base stages respectively. This unusual configuration is a form of cascode circuit, and is one which gives good high frequency performance. As the amplifier operates both as an r.f. amplifier and as the detector it must handle both r.f. and a.f. signals. Consequently, it has both a.f. and r.f. bypass capacitors in its source circuit (C3 and C4 respectively).

On the face of it, C3 should operate properly at both audio and radio frequencies. In practice it is better to include C4 as many electrolytic capacitors are not designed for operation at high frequencies, and do not perform properly at these frequencies.

An advantage of using a field effect transistor at the input of the circuit is that it has an extremely high input impedance. This helps to minimise loading on the tuned winding of T1, which aids good selectivity. The tuned winding of T1 acts as the gate bias resistor for TR1 — Resistor R1 ensures that TR1's gate is not left floating during coil changes.

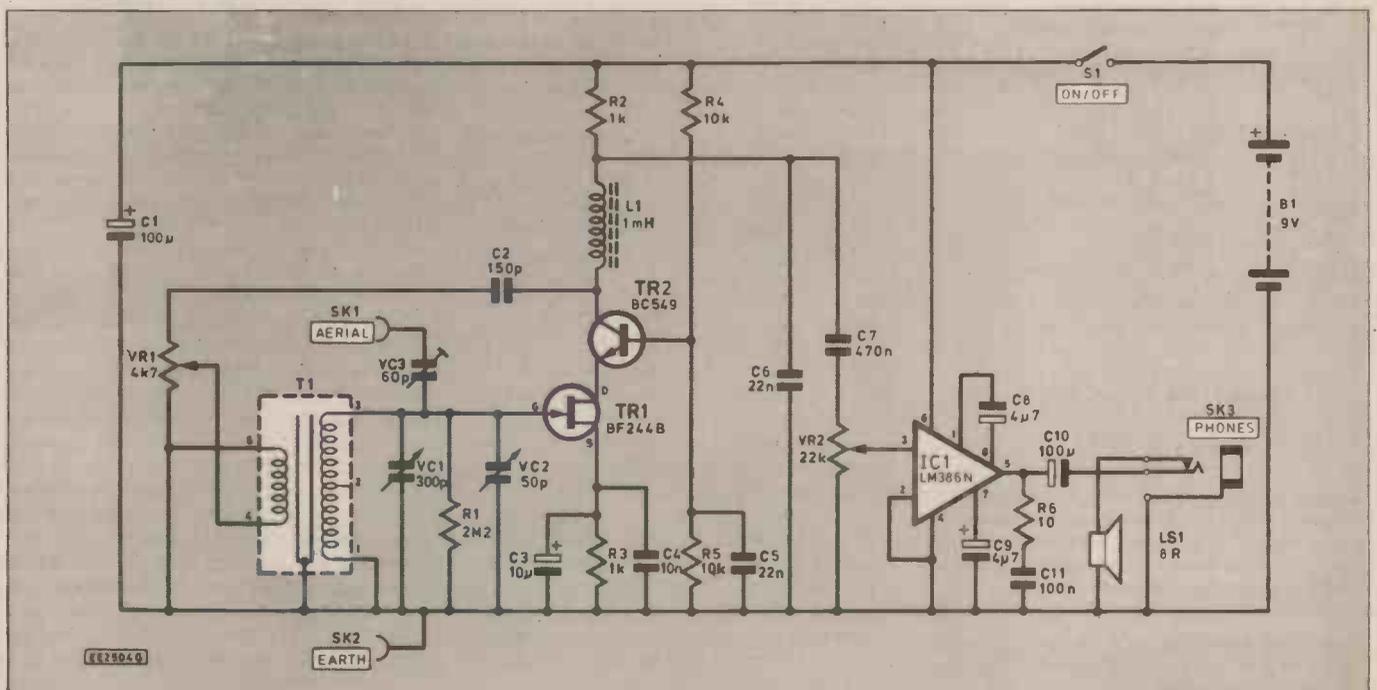


Fig 1. Full circuit diagram of the T.R.F receiver

## Variable Capacitor

VC1 is the main tuning control, and VC2 is the bandspeed control. Due to its low value VC2 only covers a small part of each tuning range. It is used for fine tuning, and it avoids the complication of fitting a slow motion drive to the main tuning control. The aerial signal is coupled into the tuned circuit via trimmer VC3. This trimmer must be set at a compromise value that gives a good signal transfer, but does not load the tuned circuit to the point where selectivity becomes inadequate.

The positive feedback is obtained by tapping off some of the output signal via C2 and VR1. The latter is connected as a volume control style attenuator and enables the amount of regeneration to be controlled. The input and output of the amplifier are out-of-phase, but T1 is connected to give signal inversion so that the feedback is of the positive variety.

For a regenerative receiver to give good results it is important that the feedback level can be accurately controlled. With some circuits there is a tendency for them

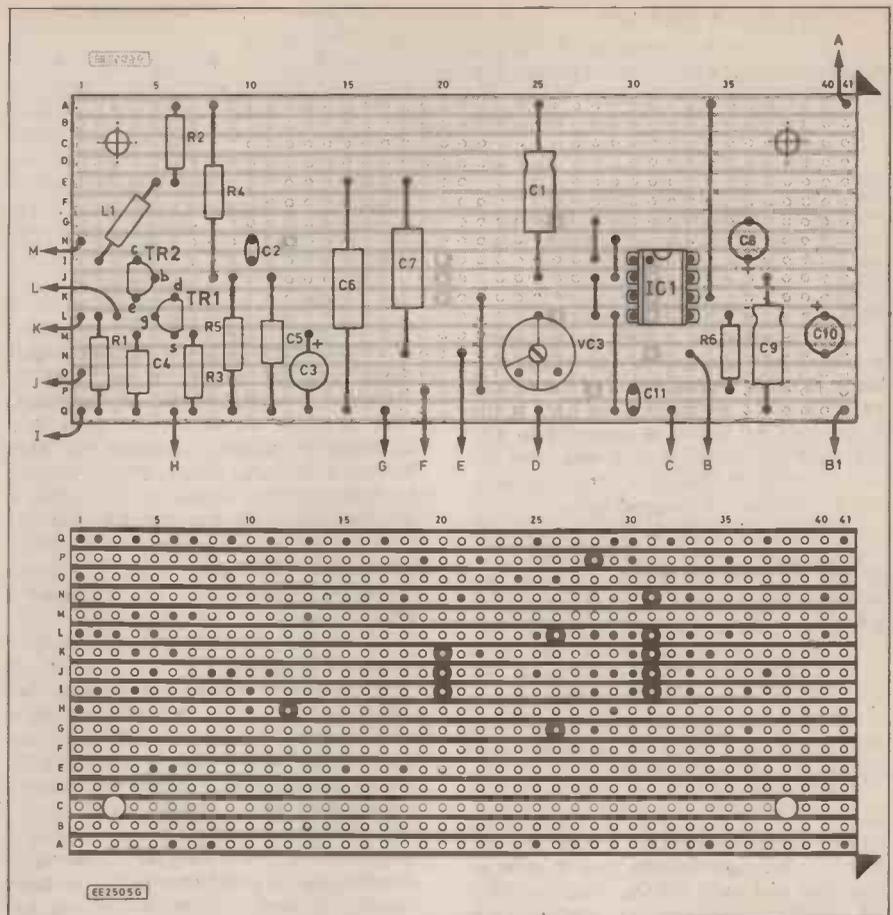


Fig. 2. Stripboard layout details

## COMPONENTS

### Resistors

R1	2M2
R2, R3	1k (2 off)
R4, R5	10k (2 off)
R6	10

**Shop  
Talk**

See  
page 319

### Potentiometers

VR1	4k7 lin.
VR2	22k log, with switch (S1)

### Capacitors

C1	100µ axial elect. 10V
C2	150p ceramic plate
C3	10µ radial elect. 25V
C4	10n polyester
C5, C6	22n polyester (2 off)
C7	470n polyester
C8	4µ7 radial elect. 63V
C9	4µ7 axial elect. 63V
C10	100µ radial elect. 10V
C11	100n ceramic
VC1	365p air spaced Jackson type "O" (see text)
VC2	50p air spaced (Jackson C804)
VC3	60p plastic foil trimmer

### Semiconductors

IC1	LM386N audio power amp
TR1	BF244B Jfet
TR2	BC549 silicon <i>n.p.n.</i>

### Miscellaneous

LS1	8ohm loudspeaker
SK1	red 4mm socket
SK2	black 4mm socket
SK3	3.5mm switched jack socket
L1	1mH r.f. choke
T1	(range 1) Toko KANK3333R
	(range 2) Toko KANK3334R
	(range 3) Toko KANK3335R
B1	9 volt (6 x HP7 in holder)

Case about 180 x 65 x 120mm; control knob (4 off); 0.1 inch stripboard 41 holes by 17 strips; 3-way DIN socket; 3-way DIN plug (3 off); battery connector (PP3 type); 8 pin d.i.l. holder; Veroplns; wire; etc.

Approx cost.  
Guidance only

**£29**

to snap into oscillation with the feedback level only moderately advanced. This makes it impossible to set the feedback level just fractionally short of the oscillation level. Quite good control of the regeneration level is possible with this circuit, and good results can be obtained if VR1 is adjusted carefully.

## Choke

L1 acts as the load for r.f. signals, while R2 is the load for demodulated audio signals. C6 is the r.f. filter capacitor. C7 couples the demodulated audio signal to volume control VR2. From here the signal is coupled to a small audio power amplifier built around IC1.

By connecting C8 directly across pins 1 and 8 the amplifier is used with a minimum of negative feedback, and therefore provides maximum gain. This gives sufficient output to drive the loudspeaker at good volume on any reasonably strong station. For maximum output power LS1 should have an impedance of 8 ohms, but loudspeakers having an impedance of up to 80 ohms will work quite well in the circuit.

For DXing the use of headphones is strongly recommended. For reasons I do not pretend to understand, comprehending speech or Morse code signals through a lot of noise seems to be noticeably easier when using headphones rather than listening via a loudspeaker. Headphone socket SK3 has a pair of break contacts that automatically switch out the internal loudspeaker when the headphones are in use.

The current consumption of the circuit is about seven milliamps under quiescent


conditions. As IC1 has a class B output stage the current drain can be several times higher than this at high output levels. A medium capacity battery such as six HP7 size cells in a plastic holder represent a good choice as the power source.

## Construction

Most of the components are fitted on a 0.1 inch pitch stripboard which has 17 copper strips by 41 holes. Details of the board are provided in Fig.2. The board is not sold in this particular size, and you must trim a larger piece down to the correct size using a hacksaw. Cut along rows of holes rather than trying to cut between them. This will leave rough edges, but they can be smoothed using a small flat file.

The dozen breaks in the copper strips can be made using the special spot face cutter tool, or a hand held twist drill bit of about 4mm in diameter will do the job quite well. The two mounting holes for the board are 3.3 millimetres in diameter, and will take 6BA or M3 bolts. Note that short spacers (about 6 millimetres long) must be used over the mounting bolts, between the case and the board. If you use plastic stand-offs instead, the size of the mounting holes must be varied to suit the particular stand-offs used.

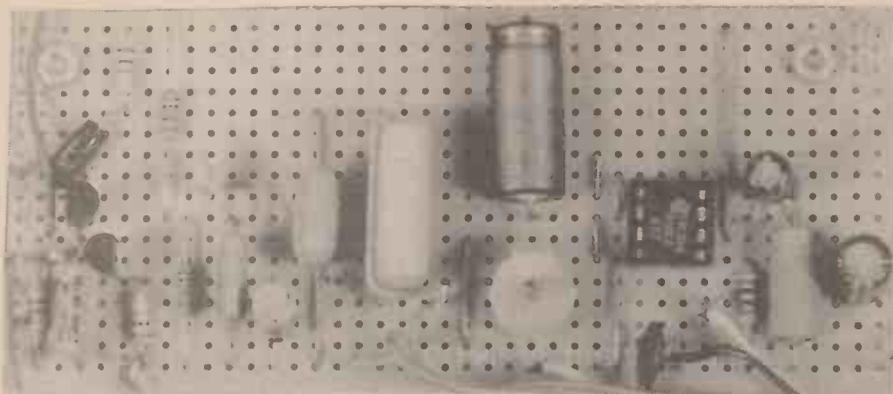Fitting the components on the board is largely straightforward. Start with the resistors, capacitors, and link wires, and then fit L1 and the semiconductors. Be careful to fit the electrolytic capacitors and semiconductors the right way round. Be especially careful with IC1, since it would be difficult to remove it once it has



been soldered in place it is best to use a holder for this component.

The link wires can be made from 22 s.w.g. tinned copper wire, or trimmings from resistor leadout wires will probably suffice. VC3 may or may not fit directly onto the board, depending on the exact type you obtain. If it will not plug into the correct holes, probably the best course of action is to fit pins into the board, and to then mount VC3 on these, using stout connecting wires to bridge any gaps from the pins to the tags if necessary. Pins are fitted to the board at all the points where connections to off-board connections will be made.

### Case

The unit requires a plastic or metal case having approximate outside dimensions of 180 by 120 by 65 millimetres or more. The four controls are mounted on the front panel, with VC1 and VC2 towards the left, and the two potentiometers on the right hand section of the panel. SK1 and SK2 are mounted on the rear panel, well towards the right end (as viewed from the rear). A three way DIN socket for the coils should be mounted close to SK1 and SK2. SK3 is mounted towards the opposite end of the panel.

The 365p air spaced capacitor specified for VC1 has an unusual mounting arrangement. It needs a central hole of about 8 millimetres in diameter for its spindle, plus three holes of about 4mm

in diameter for the countersunk 4BA mounting screws. These screws fit into threaded holes in the front plate of VC1, and they must be no more than about 6mm long. Otherwise there is a strong risk of them penetrating VC1 too far and damaging its metal plates.

A simple way of marking the positions of the three small mounting holes is to make a card template with the aid of VC1 itself. Alternatively you might simply prefer to glue VC1 in place using a good quality adhesive such as an epoxy type. Any variable capacitor of reasonable quality and having a value of about 300p to 500p should be suitable for VC1.

The prototype used a switched potentiometer for VR2 and S1, giving a conventional combined volume control and on/off switch. Obviously a separate potentiometer and switch could be used if preferred.

The three-way DIN socket requires a main 15mm diameter hole, plus two 3.3mm diameter holes for the 6BA or M3 mounting bolts. Drill the large hole first and then use the socket as a template so that the positions of the smaller mounting holes can be marked.

A grille for the speaker is needed in the top panel of the case, and this can consist of a pattern of small holes of around 4mm in diameter drilled in the panel. Take due care when drilling these holes, since making a neat job of this is not as easy as you might think. Drilling very small holes

first and then drilling them out to the required size often gives the best results.

Miniature loudspeakers do not normally have any built-in mounting bracket, and LS1 will probably have to be glued in place. Any good general purpose adhesive should do the job, but try not to smear any over the diaphragm.

### Wiring

The wiring is shown in Fig.3, which should be used in conjunction with Fig.2 (point "A" in Fig.2 connects to point "A" in Fig.3 for example). Before commencing the wiring tin the tags of all the controls and sockets with solder. Provided the ends of leads are similarly tinned, there should be no difficulty in completing the joints. Try to keep all the wiring as short and direct as possible, especially the wiring to VC1, VC2, the coil holder, and other wiring around the input section of the circuit.

Fitting the coils onto their three-way DIN plugs is not too difficult, and the correct method of connection is shown in Fig.4. One of the tags on the coil which connects to its metal can must be bent outwards slightly so that it can be soldered to the middle pin of the plug. Do not overlook the link wire which connects together the three tags on the other side of the coil.

It is unlikely the plastic casing of the plug will fit back in place once the coil has been soldered in position. Trying to fit it in place could easily damage the coil or plug. The assembly is quite tough and does not actually need an outer casing, but you can bind round the plug and coil with insulation tape if you want to give the coil assemblies a neater appearance.

### In Use

The unit requires a long wire aerial, and the notes on aerials for the crystal set apply equally to this receiver. An earth connection will give better reception on the lower frequency bands, and it can also be beneficial for reception on the higher frequency bands. On these bands there can be problems with hand capacitance effects, which means a slight shift in the tuning when you place your hand near the tuning control or take it away. An Earth connection, even if it is not a very efficient one, should totally remove any slight problems of this type. It is best to use the range two coil when initially trying out the receiver.

Initially set VC3 at about half maximum capacitance. If there are problems with

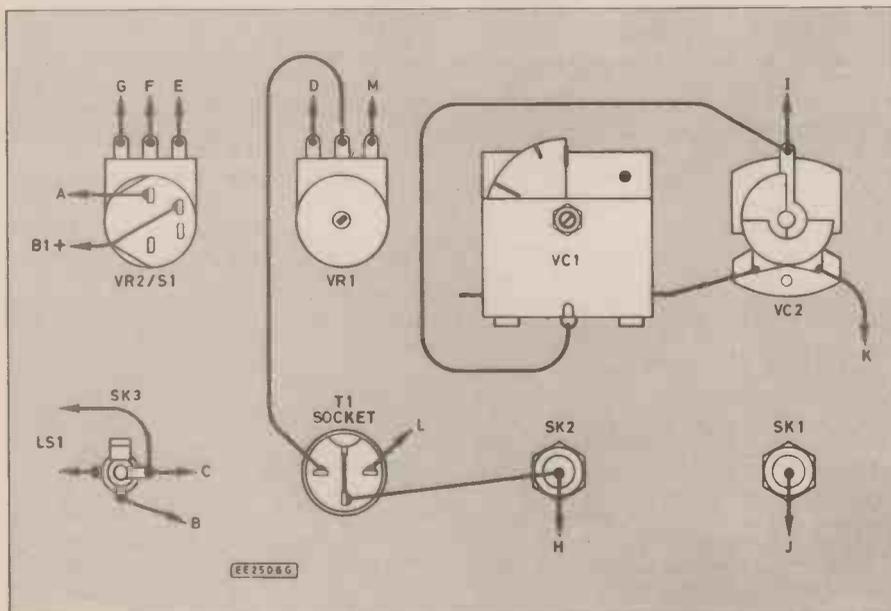


Fig. 3. Details of the wiring (use in conjunction with Fig. 2.).


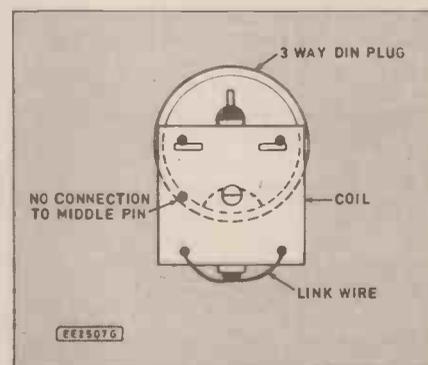


Fig. 4. Method of fitting the Toko coils to three-way DIN plugs

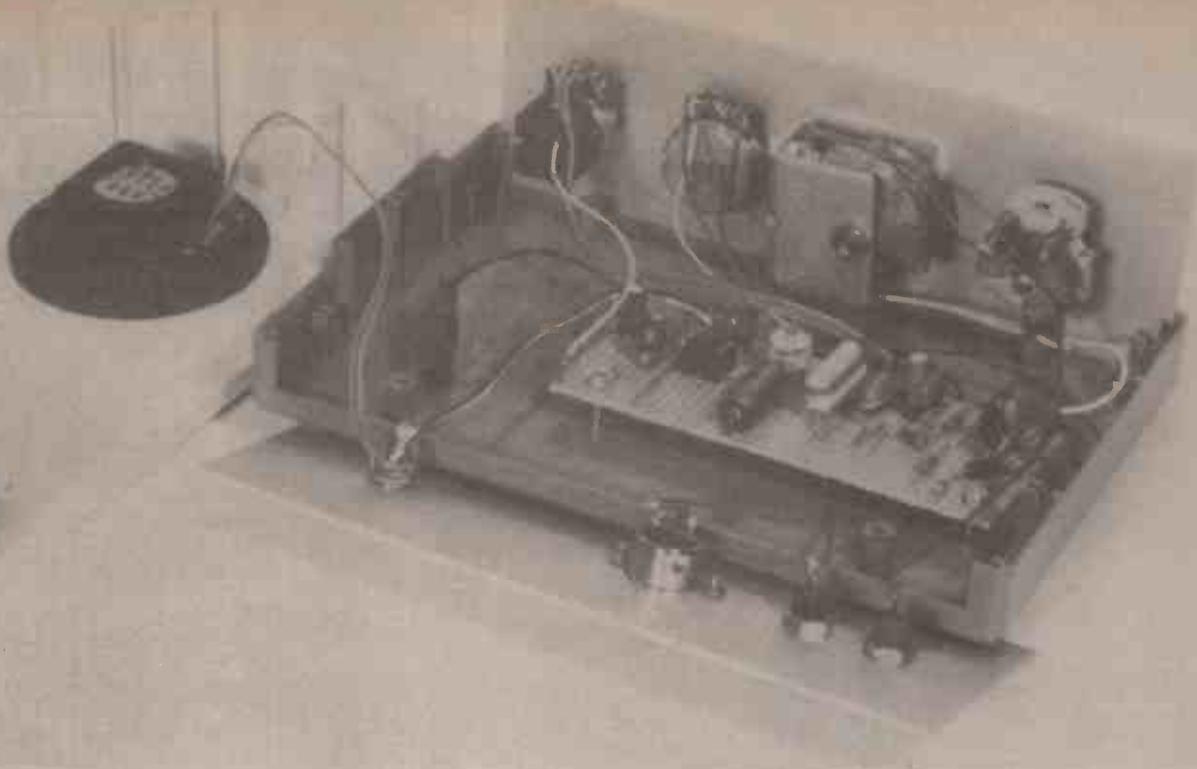

overloading and a lack of selectivity, try using a slightly lower value. Also use a lower setting for VC3 if it is not possible to obtain adequate regeneration at some settings of the tuning control. If, on the other hand, selectivity and regeneration are satisfactory, but sensitivity seems to be lacking, try a higher setting. With a little trial and error over a period of time you should be able to obtain a good compromise setting.

Capacitor VC1 is used to tune the receiver to the desired band, and then VC2 is used to scan that band for stations. Broadcast stations generally provide by far the strongest signals in the short wave spectrum, and there should be little difficulty in locating these bands.

The cores of the coils can be adjusted (using a proper trimming tool) to give the correct frequency coverage for their respective ranges. However, unless you have access to suitable test equipment it is probably best to simply leave the cores in their initial positions unless the coverage of a range seems to be seriously amiss.

Careful adjustment of the regeneration control (VR1) is essential if the receiver is to provide good results. It must be set just below the point at which oscillation occurs. It is usually pretty obvious when the set has broken into oscillation, since the background noise level will change suddenly, and a tone of varying pitch will be heard as the set is tuned across an a.m. station. Any large changes in the settings of the tuning and bandspread controls will almost certainly necessitate slight readjustment of VR1 in order to maintain optimum performance.

## Propagation

When short wave listening it is more than a little useful if you understand some of the basics of radio wave propagation. As many readers will probably be aware, radio waves travel in straight lines, but can overcome the curvature of the earth by bouncing off the upper atmosphere and back to earth. In fact there can be a multiple bounce effect with signals bouncing from the atmos-

phere down to the ground, being reflected back up into the atmosphere again, and so on. This enables signals to reach the other side of the world.

This is only possible at suitable frequencies, and when conditions in the atmosphere are favourable. On the lower frequency bands the ground wave signal (i.e. the direct signal) provides communications over distances of up to a few hundred miles. It is therefore highly unusual for these bands to go completely "dead". After dark, and sometimes during daylight hours in the winter, reflections from the atmosphere permit communications over greater distances. The reflections are from a relatively low layer of the atmosphere though, and this makes communications over really long distances very difficult (but not impossible).

The high frequency bands are a very different prospect. The ground wave tends to be absorbed by the earth, and it gives very limited range. If the atmosphere is not favourable for long distance communications, the high frequency bands are likely to be completely devoid of signals!

When the atmosphere does reflect signals at these frequencies, they are reflected from a relatively high layer, and even signals at quite shallow angles will be affected. This enables vast distances

to be covered by a single hop. The lack of interference from local stations, plus the long distances easily covered by these signals, makes the high frequency bands the best ones for long distance reception.

Propagation conditions on the high frequency bands are best during the hours of daylight, and during the summer months when there are long days. Sunspot activity is a crucial factor on the highest frequency bands, and in general, the more sunspots the better reception will be. Sunspots rise and fall on an eleven year cycle, and at the moment we are more or less at a peak of activity. The DX prospects of the high frequency bands are therefore excellent at the present time.

The main mode of operation used on the amateur bands for voice communications is single sideband (s.s.b.). It is possible to resolve s.s.b. signals on a t.r.f. receiver by advancing the regeneration control just beyond the threshold of oscillation. However, this could result in the set radiating illegal interference, and the general level of the set's performance when used in this way is likely to leave something to be desired. Better results on the amateur bands can be obtained using a direct conversion receiver, which is the subject of an article in the next issue of *Everyday Electronics*. □



# SHORTWAVE HANDBOOK

# EVERYDAY ELECTRONICS DATA BOOK

NEWNES  
Short Wave  
Listening  
HANDBOOK




## NEWNES SHORTWAVE LISTENING HANDBOOK

Written by Joe Pritchard G1UQW this book will be of value to anyone interested in shortwave listening.

Part One covers the "science" side of the subject, going from a few simple electrical "first principles", through a brief treatment of radio transmission methods to simple receivers. The emphasis is on practical receiver designs and how to build and modify them, with several circuits in the book.

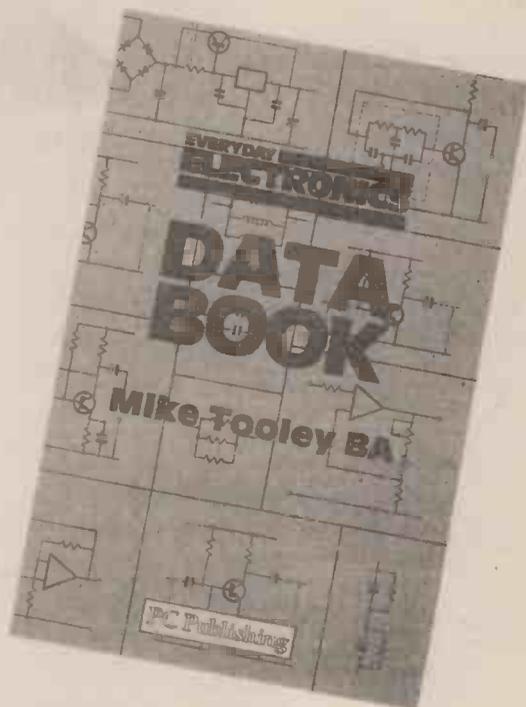Part Two covers the use of sets, what can be heard, the various bands, propagation, identification of stations, sources of information, QSLing of stations and listening to amateurs. Some computer techniques, such as computer morse decoding and radio teletype decoding are also covered.



## EVERYDAY ELECTRONICS DATA BOOK

Written by Mike Tooley for EE and published in association with PC Publishing, this book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but it also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available 'industry standard' components and devices.

A must for everyone involved in electronics!

See the Direct Book Service pages for ordering details.


## AIR IONISERS

By means of points raised to a very high voltage, ionisers re-structure the air you breathe, turning ordinary air molecules into potent negative ions. The effects of breathing in these ions can be quite startling. Almost everybody reports that it makes them feel good, and there is now strong evidence that it can also improve your concentration, make you more healthy and alert, make you sleep better, and even raise your IQ.
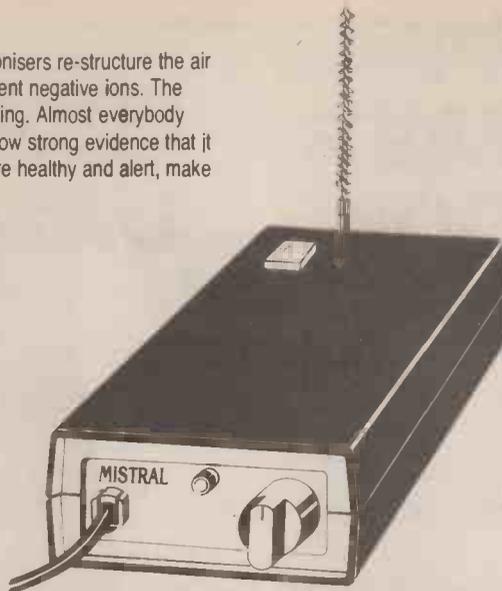
### THE MISTRAL AIR IONISER

The ultimate air ioniser. The Mistral has variable ion drive, built-in ion counter and enough power to drive five multi-point emitters with ease. Its nine main drive stages, five secondary drives and four booster stages give an immense 15 billion ions per minute output – enough to fill the largest room in a matter of seconds.


The parts set contains everything you need to build the Mistral: components, PCB, case, emitter and full instructions. If you're keen to increase the output still further, there's an optional eight-point internal emitter set to give extra ionising capability, and an almost silent piezo-electric ion fan to drive the ions away from the emitter and into the room.



MISTRAL IONISER PARTS SET **£32.66**

INTERNAL EMITTER PARTS SET  
(optional) **£3.22**

ION FAN (optional) **£11.27**

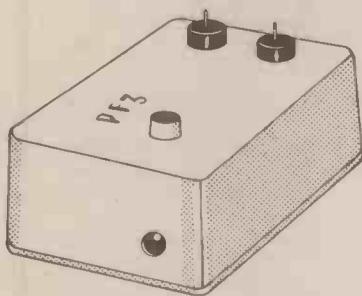

### PROPHET PF3



The Prophet performs its own special miracle on the dashboard of your car. First reports are most impressive: driving becomes a positive pleasure, easier to stay alert on long motorway journeys, a child cured of travel sickness. The ion effect is not to be underestimated. Don't forget the experiments either: there's the smoke trick, truffids, the living emitter, and more. The Prophet can be used anywhere with a supply of 9V to 12V DC, so don't restrict it to the car alone!

PROPHET PF3 PARTS SET **£21.39**

### THE Q-ION

Check out the ion levels around your house. The Q-Ion will measure the output of any ioniser, test the air to see where the ions are concentrating, help you set up fans and position your ioniser for best effect, and generally tell you anything you want to know about ion levels in the air. The readout is in the form of a bar graph which moves up and down as the Q-Ion sniffs the air in different parts of the room. Readings up to  $10^{10}$  ions per second, positive or negative.

Q-ION COMPLETE PARTS SET **£21.16**

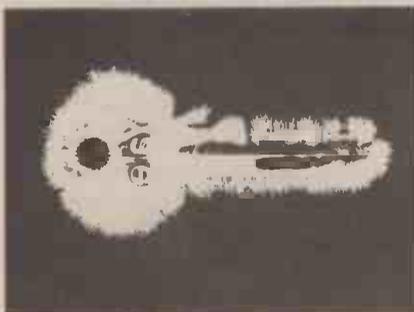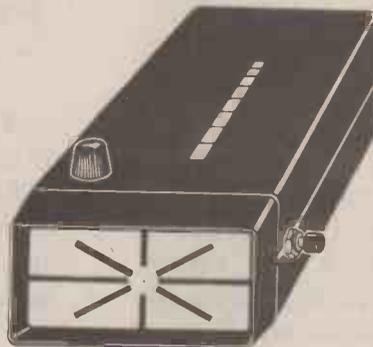

### KIRLIAN CAMERA

Bioplasmic fields, auras, or just plain corona discharge? No matter how you explain them, the effects are strange and spectacular. Can you really photograph the missing portion of a torn leaf? Can you really see energy radiating from your finger tips? Most researchers would answer 'yes' to both questions.

Our Kirlian photography set contains everything you need to turn the Mistral into a Kirlian camera, your bedroom or spare room into a darkroom, and to expose, develop and print Kirlian photographs (photographs made with high voltage electricity instead of light). The set includes exposure bed, safelight bulb, developing and fixing chemicals, trays, imaging paper and full instructions. A Mistral ioniser parts set is also required.

KIRLIAN CAMERA SET **£19.78**

## IONISER EXPERIMENTS

### \* The Vanishing Smoke Trick

Light up a cigarette and gently puff smoke into a glass jar until the air inside is a thick, grey smog. Carefully invert the jar over the ioniser so that the emitter is inside. Within seconds the smoke will vanish! This is one of the best demonstrations of an ioniser's air cleaning action and with a large jar the effect is quite dramatic.

### \* Triffids

Connect a length of wire from the ioniser emitter to the soil in the pot of a houseplant. One with sharp, pointy leaves is best. Hold your hand close to the plant and the leaves will reach out to touch you! In the dark you may see a faint blue glow around the leaf tips – this works better with some plants than with others, so try several different types. The plants don't object to this treatment at all, by the way, and often seem to thrive on it.

### \* The Electric Handshake

Wear rubber soled shoes. Touch the ioniser emitter for a few seconds until your body is thoroughly charged up. When your hair stands on end, that's just about enough. Then give everyone you meet a jolly electric handshake. Just think, you could lose all your friends in a single evening! (A meaner trick still is to charge up a glass of water or a pint of beer. Even your family won't speak to you after that!)

*Specialist*  
**SEMICONDUCTORS**

Tel: (0600) 3715 LIMITED  
SALES DEPT., ROOM 111, FOUNDERS HOUSE, REDBROOK, MONMOUTH, GWENT.

#### ORDERING

All prices include VAT  
UK orders: please add £1.15 postage and packing.  
Eire and overseas: please deduct VAT and add  
£5.00 carriage and insurance.



#### ACCESS

Phone 0600 3715 for immediate  
attention to your Access order.

# QUIZMASTER

**ADRIAN GALEA**

*An unbiased "umpire" for team quiz games. Indicates to the Quizmaster who pressed their button first.*


**T**HE Quizmaster is a "first to press" indicator which was originally designed to be used in a team quiz game similar to the TV programme "Blockbusters". It can be used with up to eight contestants, each contestant having his or her own pushbutton which controls a corresponding l.e.d. on the quizmaster control module.

The unit is operated by the questionmaster who begins the round by pressing the Reset button on the control console. This starts an internal clock which limits the amount of time the contestants have to answer the question; the questionmaster then starts to read aloud the question and the contestants race to press their individual buttons when they feel they know the answer.

If any contestant's button is pressed, the Quizmaster control module lights the corresponding l.e.d., sounds the buzzer and, more importantly, locks out all the other pushbuttons so that only one l.e.d. can be lit at any one time. However, should no button be pressed before the clock times out, the buzzer sounds and all the pushbuttons are locked out.
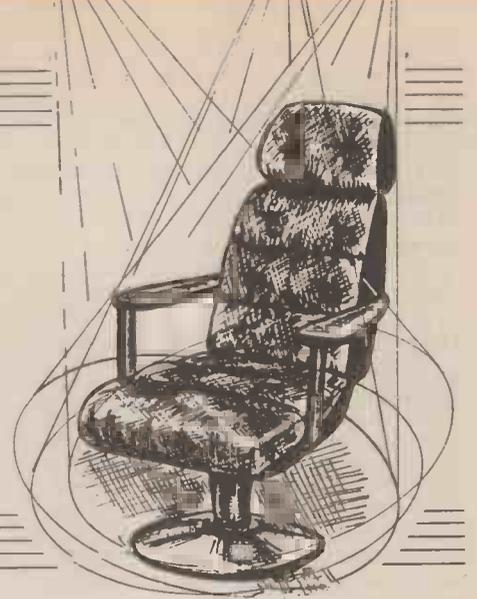
## CIRCUIT DESCRIPTION

The complete circuit for the Quizmaster is shown in Fig.1. It can be broadly divided into two sections, the "Logic Circuit" (comprising IC1 to IC5 and their associated components, diodes D9, D10 and resistor R14) and the "Timing Circuit"



(IC6 and its associated components, including the buzzer WD1).

The logic circuit monitors the pushbutton switches S1 to S8 and when one is pressed, lights one of the l.e.d.s (D1 to D8) and drives an internal signal (the "GATE" signal) low as described below; this latter action locks out all the other pushbuttons and initiates the buzzer.

The timing circuit is made up of two individual monostable timers IC6a (T1) and IC6b (T2) contained in the same i.c. package. The first monostable (T1) provides the length of time for the question to be asked and the contestants to think about their answer. The second monostable (T2) drives the buzzer and can be initiated by either the first time period ending or by the "GATE" signal going low.

*The completed Quizmaster control console and the eight contestant's "answer" buttons.*

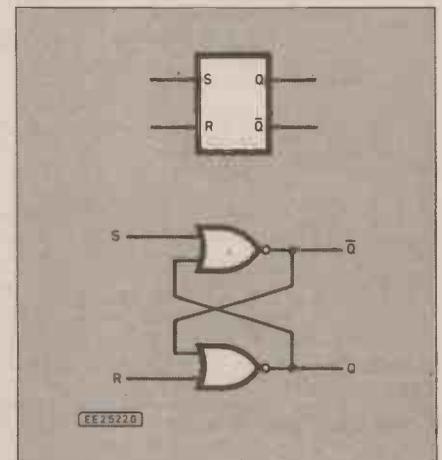
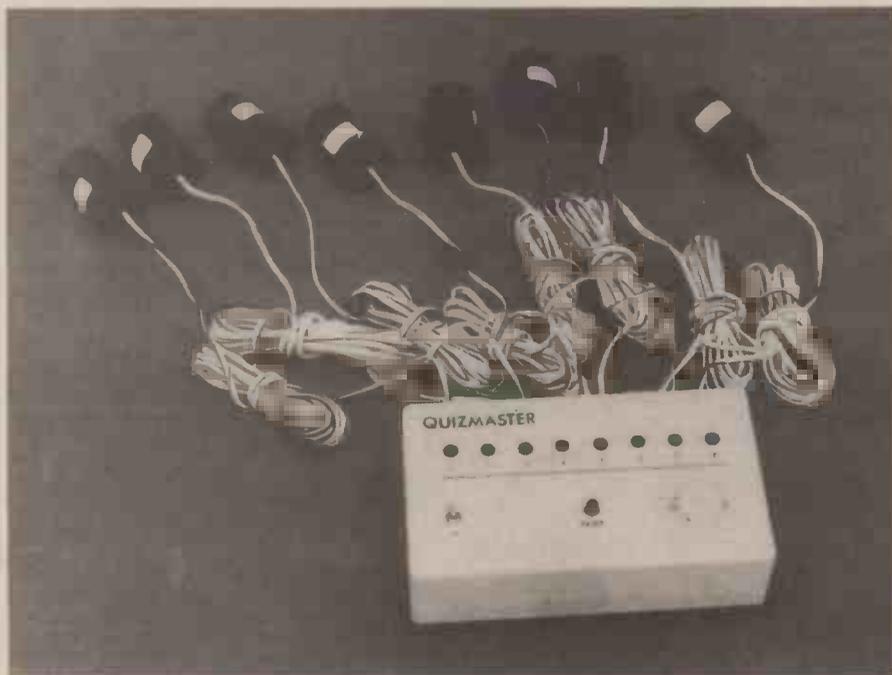


Fig. 2. Block and circuit schematic for the RS latch.

## LOGIC CIRCUIT

The operation of the logic circuit is based on a device known as an RS latch (see Fig.2). This is a type of flip-flop or bistable, the operation of which can be summarised as follows:

The RS latch has two inputs (R and S) and two outputs (Q and  $\bar{Q}$ ); the outputs are complementary so that when Q is at logic 1,  $\bar{Q}$  must be at logic 0 and vice versa. The output Q is set to logic 1 by a pulse applied to the S input and reset to logic 0 by a pulse applied to the R input; however, once Q has been set or reset then further pulses applied to that same input have no further effect on the outputs.

RS latch circuits can themselves be built up using either NAND gates or NOR gates; if they are based on NAND gates then the inputs are normally held high and are taken low (i.e. a negative-going pulse is applied) to change the outputs over. On the other hand, if they are based on NOR gates the inputs are normally held low and are taken high (i.e. a positive-going pulse is applied) to cause the outputs to change.

The RS latches used in this circuit (IC3 and IC4) are based on NOR gates. These particular i.c.s are tri-state devices which means that apart from the outputs either being high or low, they can also be "disconnected" from the rest of the circuit; this is achieved by taking the Enable pin low (pin 5 on IC3 and IC4). As the disconnecting facility is not required in this application, the Enable pin *must* be tied high.

Returning now to the circuit diagram Fig.1, on pressing the Reset button (S9) two things happen; firstly, a logic 1 is applied to the R inputs of all the RS latches (IC3 and IC4), resetting each of the Q outputs to logic 0 and thereby setting the NOR gate output (IC5, pin 13) to logic 1 (see Fig.3). Secondly, monostable T1 (IC6a) is initiated (see "Timing Circuit") and so its output (pin 5) is also high.

The outputs of the NOR gate and Monostable T1 are combined together into the "GATE" signal by means of diodes D9, D10 and resistor R14 which form a "hard wired" AND gate. Thus, so long as all the RS latches are reset (i.e. NOR gate output is at logic 1) and Monostable T1 is initiated, the GATE signal is at logic 1.

This GATE signal is fed back to the individual "input AND gates" (IC1 and IC2), each of which has its other input tied down to 0V (i.e. held at logic 0) via resistors R1 to R8. The output of each of the AND gates is therefore at logic 0.

If any of the contestants' pushbuttons is now pressed, both inputs to that AND gate will be at logic 1, setting its output high. This change of output is seen by the RS latch as a positive-going pulse on its S input which sets its Q output to logic 1; current now flows through the l.e.d. and limiting resistor R10. Even if the pushbutton is subsequently released (resetting the output of the AND gate to logic 0), the Q output of the RS latch will remain at logic 1 and so the l.e.d. stays lit.

Each of the l.e.d.s D1 to D8 share the same current limiting resistor; this is because during normal operation of the circuit only one l.e.d. should be lit at any one time. However, when the unit is first switched on it is possible for more than one l.e.d. to be lit; in this case, the current flowing through the limiting resistor stays roughly the same but it is provided by a number of routes, i.e. through each of the l.e.d.s that are turned on. Thus the current flowing through each of the l.e.d.s is only a fraction of that which would be flowing if it alone were the only current path. The l.e.d.s therefore glow dimly.

As can be seen from the short form truth table for the NOR gate (Fig.3.), when at least one of its inputs is high its output is at logic 0; hence the RS latch Q output going high resets the NOR gate output low, thus

SHORT FORM TRUTH TABLE FOR 8 INPUT NOR GATE								O/P
INPUTS								
0	0	0	0	0	0	0	0	1
X	X	X	X	X	X	X	1	0
X	X	X	X	X	X	1	X	0
X	X	X	X	X	1	X	X	0
X	X	X	X	1	X	X	X	0
X	X	X	1	X	X	X	X	0
X	X	1	X	X	X	X	X	0
X	1	X	X	X	X	X	X	0
1	X	X	X	X	X	X	X	0

X = don't care

EE2523G

Fig. 3. Short form Truth Table.

turning off the GATE signal.

This has two effects; it prevents the output of any of the AND gates going high, thus inhibiting the action of any of the contestants' pushbuttons (including the one that has already been pressed!) and secondly, it initiates Monostable T2 (IC6b) which sounds the audible alarm WD1.

However, should no contestant press his or her button, Monostable T1 times out and its output (IC6a, pin 5) goes low; this turns the GATE signal off, again lock-


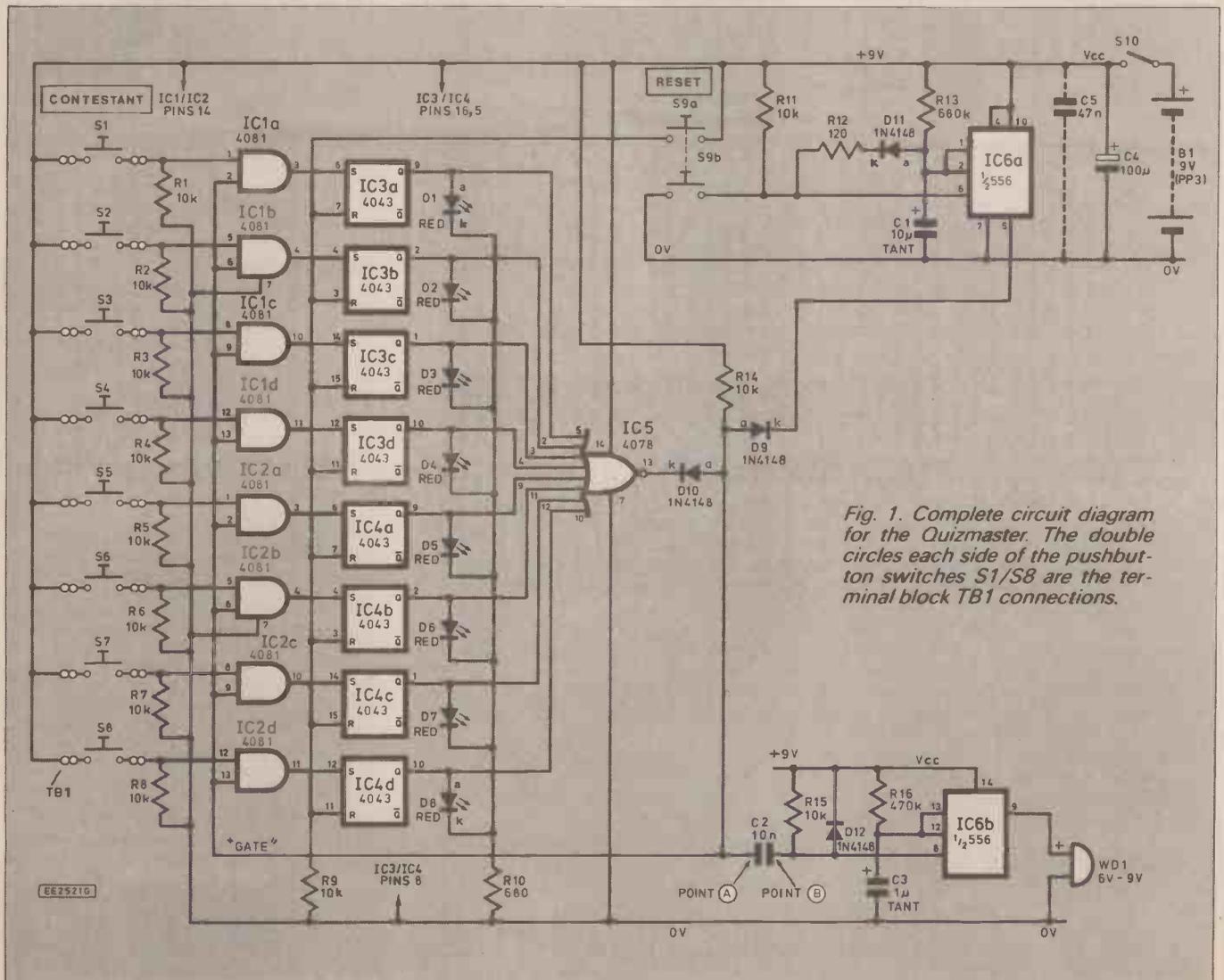


Fig. 1. Complete circuit diagram for the Quizmaster. The double circles each side of the pushbutton switches S1/S8 are the terminal block TB1 connections.

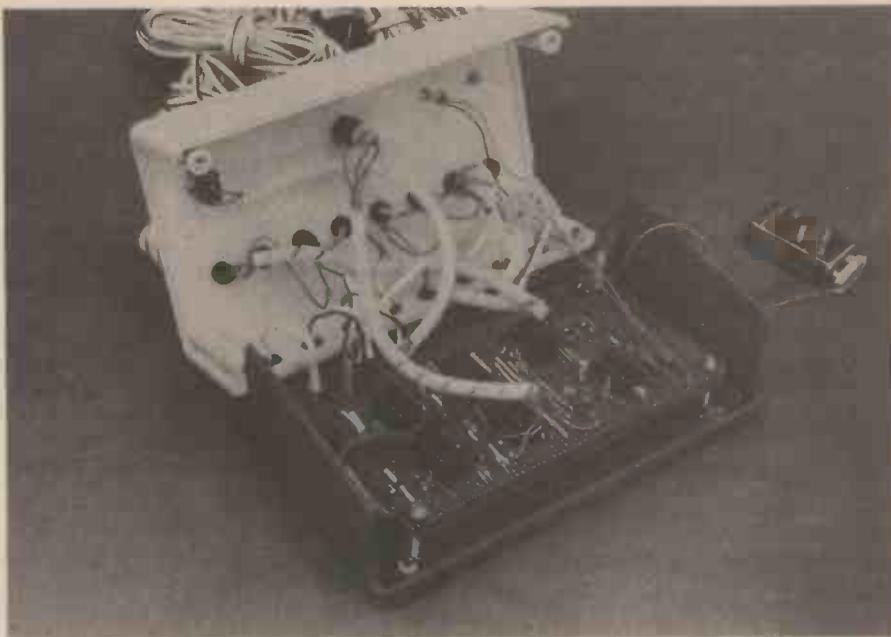

The early stripboard prototype version showing the "wiring looms" to the i.e.d.s.

ing out all pushbuttons and sounding the buzzer.

You may think it is possible for two i.e.d.s to be lit at the same time if a second button is pressed immediately after the first but before the "GATE" signal has had the chance to go low; however, to put this in perspective, using the component manufacturers' literature, the resolution of the circuit is calculated to be about  $1/4\mu\text{s}$ . To illustrate this point, rope in a few helpers and try and deliberately get more than one i.e.d. on at same time; I doubt you'll ever succeed.

## TIMING CIRCUIT

The timing circuit is provided by IC6 (and its associated components) which is a 556 timer; this is really two independent 555 timers in one package. The first timer (IC6a) provides the preset time for each question and is set to about eight seconds; the second timer (IC6b, set to about one second) is used to drive the audible alarm, sounded either when a contestant presses his button or when the time allowed has elapsed.

The "on time",  $T$ , for each monostable is set by the resistor/capacitor connected to the Threshold pin (e.g. R13 and C1 for Monostable T1) according to the formula:  $T = 1.1 \times R \times C$  where  $T$ ,  $R$  and  $C$  are in seconds, Ohms and Farads respectively.

Notice that both timers have very different triggering circuits; in order to understand why, a brief explanation of the operation of the i.c. is required.

Each timer contains a resistor chain that it uses to derive two reference voltages of  $1/3V+$  and  $2/3V+$ . These voltages are applied (internally) to comparators which "monitor" the input voltages on the Trigger and Threshold pins. It also contains a transistor that it uses to apply a "short circuit" between the Threshold pin and ground, thus discharging the timing capacitor and preventing it from charging up.

To initiate the device, the voltage on the Trigger input (normally held high) is taken below  $1/3V+$ . Once initiated, the output voltage goes high and the internal transistor is turned off; this allows the timing capacitor to begin to charge up.

When the voltage across the timing capacitor (i.e. the voltage on the threshold pin) reaches  $2/3V+$ , the timer is turned off (i.e. its output goes low) and the internal transistor is turned on again, thus discharging and shorting out the timing capacitor. The monostable is not normally retriggerable, i.e. once initiated it does not respond to further pulses applied to the trigger. However, after using the original Quizmaster unit a few times it was found that it would be preferable if Monostable T1 were retriggerable.

This is because on odd occasions a contestant would interrupt the questionmaster but give a wrong answer; the questionmaster would then press the reset button and start to read the next question. However pressing the reset button merely cleared the i.e.d.s; it did not retrigger the monostable. The monostable would then time out before the questionmaster finished reading the next question.

Consider now Monostable T1 trigger circuit, IC6a. The trigger is normally held high via resistor R11 but is momentarily connected to the 0V rail when the Reset button (S9b) is pressed; the monostable is now initiated and capacitor C1 starts to charge up via resistor R13. Should the Reset button be pressed again before the timing period has elapsed, the capacitor is discharged almost completely via diode D11 and resistor R12; the timing period starts again from scratch. Thus operating the Reset button in effect retriggers monostable T1.

Turning now to Monostable T2 (IC6b), its Trigger input cannot be connected directly to the GATE signal because it is a requirement of the timer i.c. that once initiated, the voltage on the Trigger pin must return to a voltage greater than  $1/3V+$  before the end of the timing period otherwise the device will be inhibited and the output will remain high (until the trigger voltage rises above  $1/3V+$ ). However, once the GATE goes low (either because the NOR gate output goes low indicating that a contestant has pressed his button or Monostable T1 output goes low indicating the end of the time allowed) it will remain so until the Reset button is pressed.

This problem is overcome by means of capacitor C2. When the GATE signal is high both plates of capacitor C2 are held at  $V+$  via resistors R14 and R15; capacitor C2 is therefore discharged. When the GATE goes low, one side of the capacitor (Point A) is effectively connected to the 0V rail; as the voltage across a capacitor cannot change instantaneously, the voltage on the other plate (point B) also momentarily dips to 0V before the capacitor begins to charge up via resistor R15. The voltage on point B therefore rises to  $V+$ .

However, when the Reset button is pressed and the GATE goes high again, point A immediately rises to  $V+$  and point B would theoretically momentarily rise to twice  $V+$  (if the capacitor were fully charged) before starting to discharge through resistor R15 to  $V+$ . This potentially destructive spike is eliminated by diode D12 which begins to conduct when point B rises to 0.6V above  $V+$ .

## CONSTRUCTION

The i.c.s used in this project are CMOS types; care must be taken not to damage these static-sensitive devices during han-

## COMPONENTS

### Resistors

R1-R9, R11	
R14, R15	10k (12 off)
R10	680
R12	120
R13	680k
R16	470k

All 0.25W 5% carbon film

### Capacitors

C1	10 $\mu$ tantalum bead, 16V
C2	10n polyester
C3	1 $\mu$ tantalum bead, 16V
C4	100 $\mu$ radial elec., 25V
C5	47n disc ceramic

### Semiconductors

D1-D8	5mm red i.e.d.s (8 off)
D9-D12	1N4148 signal diode (4 off)
IC1, IC2	4081 CMOS quad 2-input AND gate (2off)
IC3, IC4	4043 CMOS quad 3-state NOR R/S latch (2 off)
IC5	4078 CMOS 8-input NOR gate
IC6	556 dual timer

### Miscellaneous

S1-S8	Min. push-to-make switch (8 off)
S9	Min. 2-pole push-to-make switch
S10	Min. On/Off toggle switch
B1	9V PP3 battery, with connectors

Printed circuit board available from *EE PCB Service*, code EE690; case, Verobox 103; 14-pin i.c. socket (4 off); 16-pin i.c. socket (2 off); TB1 12-way screw terminal block; buzzer; i.e.d. bezels (8 off); twin-core bell wire (about 16m, i.e. 2m per "contestant button"); rubber grommets; solder pins; connecting wire; nuts and bolts; solder etc.

Approx cost.  
Guidance only

**£26**

ding and soldering. Because of this, it is preferable if the i.c.s are mounted in sockets rather than being soldered directly to the printed circuit board.

It is suggested that after building the circuit board it is thoroughly tested before the complete unit is assembled in the master control case together with the contestant pushbutton switches. In order to do this (and to facilitate construction), the flying leads from the circuit board for the


contestants' pushbuttons are connected to a terminal strip TB1 which will later be fixed to the side or bottom of the case. The reasons for doing this will become apparent when testing the unit.

### CIRCUIT BOARD

Construction of the printed circuit board is fairly straightforward and the component layout and full size copper foil master pattern is shown in Fig.4. This

board is available through the EE PCB Service, code EE690.

It is suggested that the i.c. sockets be soldered in position first followed by the link wires, terminal pins, resistors, capacitors and then diodes. The flying leads to the l.e.d.s (D1 to D8), on/off switch S10, reset button (S9) and contestants' pushbuttons 12-way terminal strip (TB1) can then be soldered in place along with the battery connector and miniature buzzer.

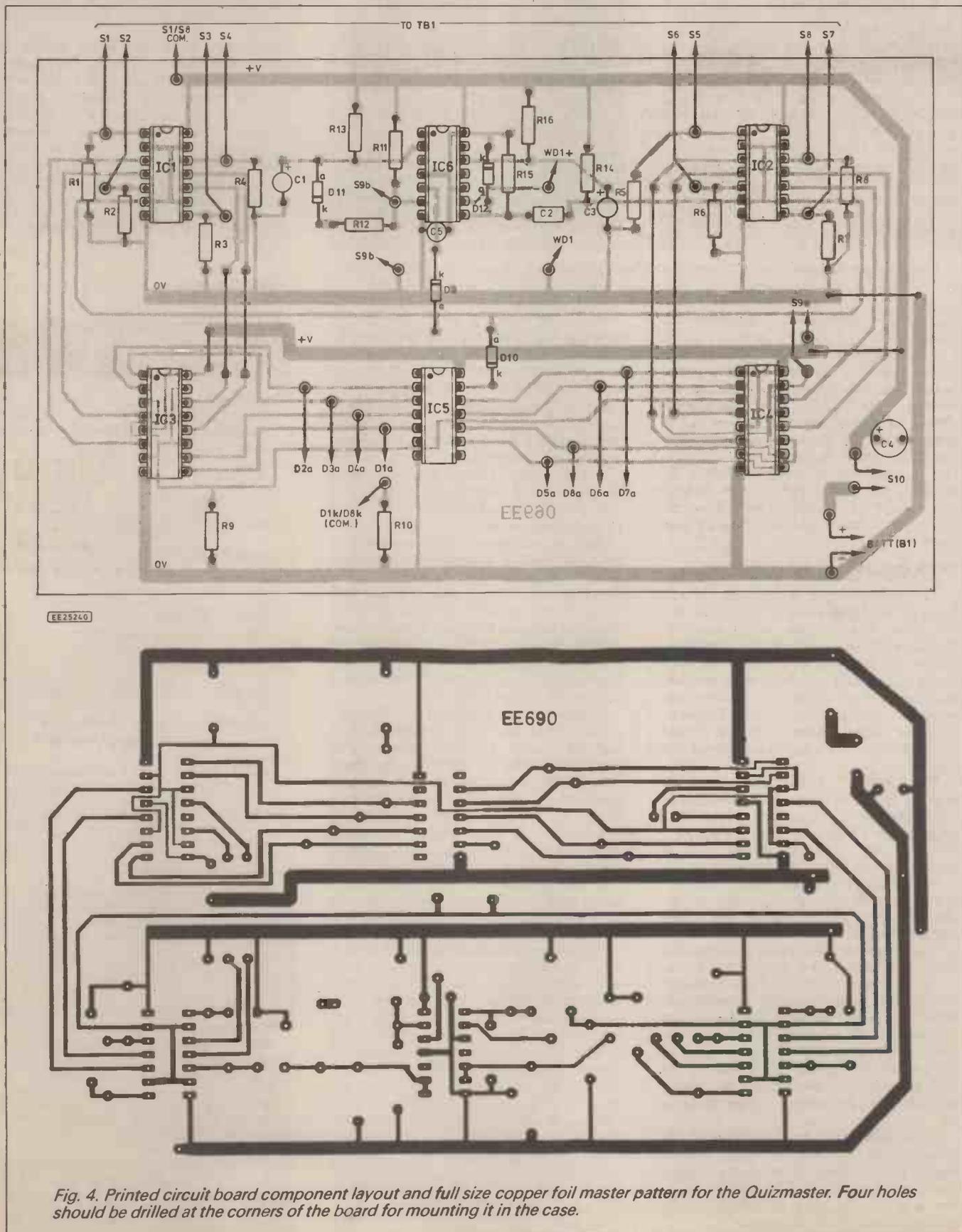

EE25240

Fig. 4. Printed circuit board component layout and full size copper foil master pattern for the Quizmaster. Four holes should be drilled at the corners of the board for mounting it in the case.

## WIRING UP

Single strand light-duty wire was used for the flying leads; for the on/off switch and reset button, 203mm (8in.) lengths were found to be suitable. For the contestants' pushbuttons and l.e.d.s longer lengths 255mm - 305mm (10-12in.) were used; the leads can be bundled together into a "wiring loom" using cable ties or spiral cable wrapping and the ends cut to the required length to suit.

The other ends of the flying leads can then be connected as required; note that the cathodes (k) of the l.e.d.s are all linked together as shown in Fig. 5. The i.c.s can now be inserted.

At this stage carefully check the circuit board over once more; if all appears to be correct, insert the i.c.s taking care that they are oriented correctly (and inserted in the right socket!) and avoid touching the pins. The operation of the circuit may now be tested before assembling the rest of the unit.



Control console front panel layout showing the contestant's l.e.d.s.

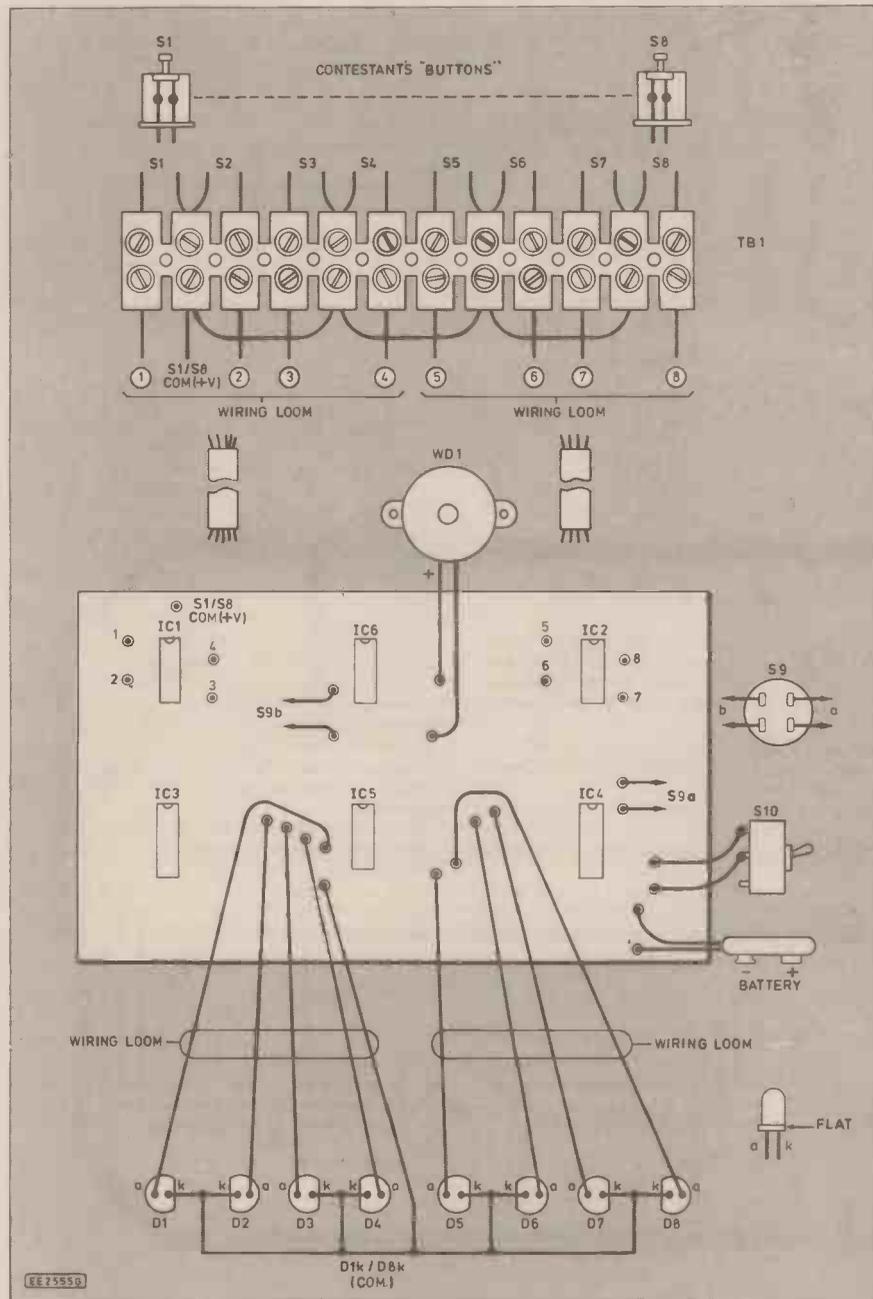


Fig. 5. Interwiring from the printed circuit board to the l.e.d.s, terminal block and contestant switches.

## TIMING

The times set for Monostables IC6a and IC6b were those that most suited the author's own use; if it is required, they may be changed by adjusting the values of the timing resistors or capacitors. The type of capacitor used is not important so long as it can physically fit in the space provided. However, it is recommended that electrolytic and ceramic disc capacitors are avoided.

The 556 timer i.c. is available as a CMOS or bipolar device; if a bipolar version is used it is recommended that a 47nF decoupling capacitor (C5) is fitted close to the supply pins (shown dotted in Fig.1). This is not necessary with the CMOS device.

## TESTING

Plug the battery into its holder and switch on; some (or all) of the l.e.d.s should now be lit though they may be glowing very dimly indeed. Immediately press the Reset button S9 and all the l.e.d.s should now be extinguished; if not, switch off and carefully check the circuit board before continuing.

If all is well, wait for approximately eight seconds and the buzzer should sound for about one second. Now, using a short length of wire, dab each of the flying leads to the pushbuttons in turn to the positive supply on the terminal strip; nothing should happen!

Press the Reset button again and this time dab the "short" from the positive supply on to one of the pushbutton flying leads before the Monostable T1 times out; this time the corresponding l.e.d. should light (quite brightly) and the buzzer sound immediately. Dab the short on to each of the other flying leads to the pushbuttons in turn; nothing further should happen.

Repeat this test with all the other pushbutton leads in turn. Finally, press the Reset button, wait for a couple of seconds and then dab a short on any pushbutton flying lead; immediately press the reset button and time how long it takes before the buzzer sounds. This time interval should not have changed (it should be about 8s).

If any difficulties are experienced, it is suggested that the unit is switched off and one side of the diode D9 is unsoldered and lifted clear of the circuit board. The logic

circuit has now effectively been separated from the timing circuit and can be functionally tested on its own (ignoring the buzzer which should sound every time the GATE signal goes low). Once any faults are cleared, diode D9 can be resoldered and one side of diode D10 unsoldered to allow testing of the timing circuit.

## ASSEMBLY

The circuit board has been designed to fit in a type 100 "Verobox" (110mm x 190mm x 60mm) although any other case of at least similar dimensions may be used. At first site it might appear as though the case is rather large and that a smaller size could have been used; however, there are a lot of flying leads to be accommodated and the size of case quoted is probably the minimum that could be used.

Mark the lid of the box and drill the required holes for the l.e.d.s, Reset button, on/off switch and buzzer. Fit the mounting bezels for the l.e.d.s. Drill the base of the

box for the circuit board mounting pillars and terminal strip for the pushbuttons. Mount the terminal strip in position and then pass the leads for the switches through the grommets, secure with cable clamps and connect to the terminal strip as shown in Fig.5. Fit the circuit board mounting pillars and connect the pushbutton flying leads to the terminal strip before installing the board in position. Mark and drill the side of the box for the pushbutton cables and fit rubber grommets. Fit the buzzer, on/off switch and reset button in position before pushing each of the l.e.d.s into its mounting bezel.

Solder the pushbuttons to the other ends of the cables and fit them in suitable containers such as plastic 35mm film cases. It is handy if each pushbutton is identified with a number corresponding to the l.e.d. position on the Quizmaster control unit.

## FINAL TESTING

Once the unit has been assembled it can be tested in much the same way as before;

as a final check you could try "racing" the buttons, operating one slightly before the other.

Before using the Quizmaster in earnest, it is always best to begin by fully testing the unit; this is done by asking each contestant in turn to press his or her button (after pressing the Reset button) to ensure that the corresponding l.e.d. lights and the rest of the contestants then press theirs to ensure that they are locked out.

## OPERATING

When in use, you may get the odd complaint (usually from the losing team) that the unit is "rigged" or that a particular button does not respond as fast as some one else's. You may counter these arguments by offering to swop the buttons around or lapse into a detailed description of the circuit operation to demonstrate that their fears are unfounded. Threatening to deduct a point for arguing with the questionmaster is usually far more effective.

*Happy quizzing!*

# MARKET PLACE

**WANTED** Galanti X310 organ manual, handbook or other information to help senior citizens club. Tel. (0460) 62361.

**WANTED** for Apple 11E printer and any extension cards. Tel. (0203) 450476.

**WANTED** roger bleep, power echo mike cct diagrams. Write Douglas Kinneer, P.O. Box 40, Glenrothes, Fife.

**PK88** packet radio controller with all leads and operating manual £90. Postage paid. Tel. (0704) 892088 — ask for Mike.

**CROTECH** 3132 dual trace 20MHz scope with leads and probe unused £220. Tel. (0480) 811654 Eves.

**FOR SALE** 1 mixed box of 25 large and small heat sinks £15. Send SAE P. Howard, 9, Park Meadow, Doddinghurst, Brentwood, Essex CM15 0TT.

**TOSHIBA** HX10 MSX computer home micro kit with cassettes games and books £60 o.n.o. Mr William Wilson, 7 Alexander St., Cowdenbeath, Fife KY4 9AA Tel. (0383) 512963.

**COMMUNICATIONS** receiver wanted. Medium, shortwave. Adjustable bandwidth filter. Will consider valve model. Collect Easter. Please write. A.G. Swan, Odenwaldring 22, D6101 Brensbach, West Germany.

**AVO MULTIMINOR** £16. Fluke digital multimeter £50. HV probes £10. Clampmeter £15. Tel. 01-554-2913. 6-8pm.

**SCOPE** Hitachi V.212 20MHz. As new. Manual and twin set of leads. Offers. Tel. (0875) 811816.

**WANTED** parallel interface for Star NL-10 printer. Tel. 01-656-1568.

**SPECTRUM** Beta disk users interested in ex-

changing hardware, data. Contact Taylor, 15 Lindsay Road, Bristol BS7 9NP. Tel. 516353.

**OFFERS** for vintage Bush l.w./m.w./s.w. valve radio. Fully working. Good condition. Tel. (0922) 691795.

**MEMORY** chips 32 NEC PD43256 C-12L SRAM £10 each or £8 each for 8+ (RS635-498). Tel. Adam (0707) 268177.

**WANTED** radio and television servicing 81/82, 82/83, 83/84, 84/85 volumes. Good condition. £17 each including p & p. Tomlinson, 24, Kelmscott Gardens, Leeds LS15 8HL.

**ULTRA VIOLET** light box for p.c.b. etching cost £180 sell £80 with timer. Tel. Basildon 417775 (Essex).

**FOR SALE** sound to light unit three channel. 1000W each channel, sound input. £15 post paid. L.T. Hill, 29 Stead Lane, Bedlington, Northumberland.

**RACAL** digital frequency meter type SA 520H. £45 o.n.o. or exchange for Spectrum 48K computer s.a.e. David Wood, 57 Willis Pearson Avenue, Bradley, Bilston, West Midlands WV14 8DA.

**WANTED** any info on the Philips BDX96 pnp transistor. Mark Timlin, 4, Belgrave Street, Ossett, West Yorks WF5 0AD.

**200+ COMPONENTS** for £3. Contains transistors. l.c.s, l.e.d.s, resistors etc. All new. 1000+ for £10. D. Simpson, 42 Wareham Way, Sunnybrow Crook, Co. Durham DL15 0NG.

**WANTED** ready made working v.h.f./f.m. micro transmitter. Prepared to pay up to £2. Please write to Mr. J.J.P. Townsend, Loveday House, Cranleigh School, Cranleigh, Surrey GU6 8PZ.

### FREE READERS ADS.

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Pen pals or items related to electronics only. No computer software. EE cannot accept responsibility for the accuracy of ads, or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut-out valid "date corner". Ads. will not appear (or be returned) if these rules are broken.

**SWAP** R7000 25 to 2000 MHz as new for R71E in like order. G. Meil, St. Clair Cottage, Holm, Orkney KW17 2RZ.

**WANTED** "Fun With Short Waves" circa 1960 Author Gilbert Davey or "Fun With Radio" circa 1957. Mr. J. Maughan, 40 Windsor Drive, New Silksworth, Sunderland, Tyne and Wear SR3 1JQ. **VINTAGE** Rx/Tx aircraft 1155 valve Tx/Rx Type 38.RAM chips 4116. Attache case radios — offers. Tel. Leicester 787503.

**WANTED** Dragon 64 computer cash/exchange VOX Jaguar keyboard, Godwin 4S Drummaker with 2 octave keyboard. Ivan Comisky, 33D North Clarence Street Flats, Dublin 1, Ireland.

**C64C COMPUTER.** Tape, joystick, games, utilities, "action replay" Mk.5P speech synth. Mouse + art software £150 + p & p. E.J.A. Dumbill, Church Farm, Church St., Foston, Nr. Grantham, Lincs. NG32 2LG.

**DUAL** 8" disc drives ex. Intel equipment including power supply £100 o.n.o. Tel. (0784) 457949.

**ELECTRONICS** and computing JULY 1981 — JAN 1986 complete. Good cond. £5 offers, exchanges. Tel. 01-647-2633.

**HAS ANYONE** got either to work Heart Rate Monitor Interface, September 1988 ECG Interface November 1988. Barrie Hanstead, 115 Avon Road, Uppingham, Essex RM14 1QX.

Name & Address:			

BLOCK CAPITALS PLEASE

Please read the **RULES** then write your advertisement here — one word to each box. Add your name, address and/or phone no. Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a cut-out valid date corner.

Signature ..... Date .....

**COUPON VALID FOR POSTING BEFORE 2 FEBRUARY '90**

(One month later for overseas readers)

**SEND TO: EE MARKET PLACE, EVERYDAY ELECTRONICS, 6 CHURCH STREET, WIMBORNE, DORSET BH21 1JH.**

(For readers who don't want to ruin the issue send a photostat or a copy of the coupon (filled in of course) with a cut-out valid "date corner"



*a regular feature for the Spectrum Owner...*

by Mike Tooley BA

LAST MONTH we showed how readers can make maximum use of the powerful Philips SAA1099 stereo sound generator chip fitted to the MGT SAM Coupé. This month, we have an interesting demonstration software routine which puts some of the facilities offered by this chip to the test. We begin, however, by attempting to catch up with a bumper crop of problems, hints and tips sent in by readers.

### Changing Times

Ben Howe writes from Ormskirk to let me know about an error which crept into the Clock/Timer Program (*Everyday Electronics Dec '89*). Ben has been using the program but has found that the clock advances from 23.59 to 24.00 rather than the expected 00.00.

Unfortunately, this was an oversight on my part so, for Mr Howe (and others) who may be using the Spectrum as a clock, here is the solution:

1. Add a line 4055 as follows:  
4055 IF hour = 24 THEN LET  
hour = 0

2. Add an extra space between the last pair of quotes in line 2120.

Several other readers have commented on the Clock/Timer program and seem to have put this to good use. M. Sharpe has written to ask if there is any way that the Spectrum can be made to issue a "tick" every second using the BEEP command.

Whilst a BEEP statement could easily be included within the main timing loop (which starts at line 2100), this would have the effect of slowing the clock down as the BEEP command monopolises the CPU! An alternative solution might be that of flashing the border, alternately between red and green, every second. If this will suffice, the following lines can be added in order to produce this "visual tick":

```
2125 IF sec/2 = INT (sec/2) THEN BOR-
DER 2
```

```
2126 IF sec/2 <> INT (sec/2) THEN
BORDER 4
```

### Under the Microscope

Andy Scott is a regular reader of this column and he writes from Avon to request details of sources of information concerning the Ferranti uncommitted logic array (ULA) chip fitted to the Spectrum. In particular, Andy would like some details con-

cerning the internal logic of the device (particularly in the area of the clock and video signal processing).

The "official" Spectrum Service Manual provides little information on the ULA device which is presumably quite deliberately kept "under wraps". Has anyone got any further information which might be worth passing on?

### Illogical Logic

Tony Preston, from Cardiff, thinks he may have discovered a problem with the ROM in his Plus-Two. Tony writes:

"Can anyone throw some light on a problem which I have come across when using the Boolean operators, AND, OR etc. Why does Sinclair BASIC produce strange results with these functions? Is there an error in the ROM or have I missed something?"

In short, Tony, the answer is that ZX-BASIC handles the logical operators in a somewhat different manner from that which is employed in several other popular microcomputers. As an example, the following results are obtained:

Logical Operation	Result
1 AND 1	1
1 AND 0	0
2 AND 2	2
2 AND 1	2 (!)
2 AND 0	0

Despite the somewhat surprising outcome (in the case of "2 AND 1" there is some logic behind the Spectrum's handling of Boolean operations which, whilst unconventional, is at least consistent in all versions of the ROM. For the benefit of those who may have had their curiosity aroused by this apparent anomaly, I shall attempt to explain this in a future "On Spec".

### Machine Code Revisited

Mike Short has requested some details of books which will help him learn to program in Z80 code. Mike writes:

"Like many people, I would like to be able to make my programs more efficient and also more compact. I am a reasonably proficient BASIC programmer. Can you please recommend something which will help me make the quantum leap into machine code? I have a Plus-Two and a Plus-D with 3.5in. disk drive."

Mike's request is fairly common as most serious users of the Spectrum eventually realise the need for something more powerful than ZX-BASIC. Two books worth looking at are *Spectrum + 2 Machine Language for the Absolute Beginner* by Joe Pritchard (published by Melbourne House, ISBN 0-86161-209-4) and *Spectrum Machine Language for the Absolute Beginner* by William Tang (also published by Melbourne House, ISBN 0-86161-110-1). Despite the similarity of their titles, these two books are completely different and both can be recommended.

As far as software is concerned, *Hisoft's* DEVPAC is probably the most widely used development tool which provides powerful editing, assembly and debugging facilities. This package can be used to enter, test and debug assembly language programs ranging from the trivial to the most complex.

### Mission Control

Stephen Villiers teaches Design and Realisation and his pupils are experimenting with a Spectrum-controlled buggy.

Stephen needs an interface which can control four d.c. motors (each rated at 12V, 1A) and provides inputs for six sensors (all of which employ TTL level signals). Stephen writes:

"The interface needs to be fairly cheap to construct (we may have to build several of these!) and must also use a minimum of chips. We would like to have a small keypad with four switches to control the direction of the buggy.

With the four motor drive signals and six inputs, this makes a grand total of ten input signals and four output signals. Can this be achieved using a single Z80-PIO or would you recommend another integrated circuit?"

Fortunately, the solution to this problem appeared in March 1988 *Everyday Electronics* and takes the form of our "On Spec" Add-on I/O Port. The interface uses only three chips (including an 8255 programmable parallel I/O device) and costs in the region of £16 to build.

Since the 8255 has three 8-bit I/O ports (rather than the two available from the Z80-PIO) there should be no problem with the configuration suggested. Hope it all works well, Stephen!

### Play It Again Sam!

Readers of this column will be only too well aware that the MGT SAM Coupé offers some remarkably powerful facilities in the area of sound generation. Last month, I promised a routine which would put the SAA1099 through its paces. Here it is:


```
10 REM SAM Coupe only
20 SOUND 28,1
30 SOUND 8,11
40 SOUND 9,4
50 SOUND 20,3
60 FOR x=1 TO 4
70 SOUND 21,0
80 FOR y=5 TO 1 STEP -1
90 SOUND 16,y
100 FOR z=255 TO 128 STEP -8
110 SOUND 8,z
120 SOUND 0,16
130 PAUSE x
140 NEXT z
150 NEXT y
160 SOUND 21,1
170 FOR y=1 TO 5
180 SOUND 16,y
190 FOR z=128 TO 255 STEP 8
200 SOUND 8,z
210 SOUND 0,16
220 PAUSE x
230 NEXT z
240 NEXT y
250 NEXT x
260 SOUND 28,2
```

The program uses only two of the SAA1099's tone generators. Tone sequences of descending frequency (lines 80 to 150) are produced without noise (line 70 disables the noise source) whilst tone sequences of ascending frequency (lines 170 to 240) are coloured with noise (line 160 enables the noise source). Output from the sound generator is enabled by means of line 20 and disabled by means of line 260 which places the chip in the reset state.

NEXT MONTH: We shall be taking a look at MGT's "Communications Interface" for the SAM Coupé. In the meantime, if you have any problems, queries or suggestions for inclusion in *On Spec*, please don't hesitate to drop me a line: Mike Tooley, Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey. KT13 8TT.
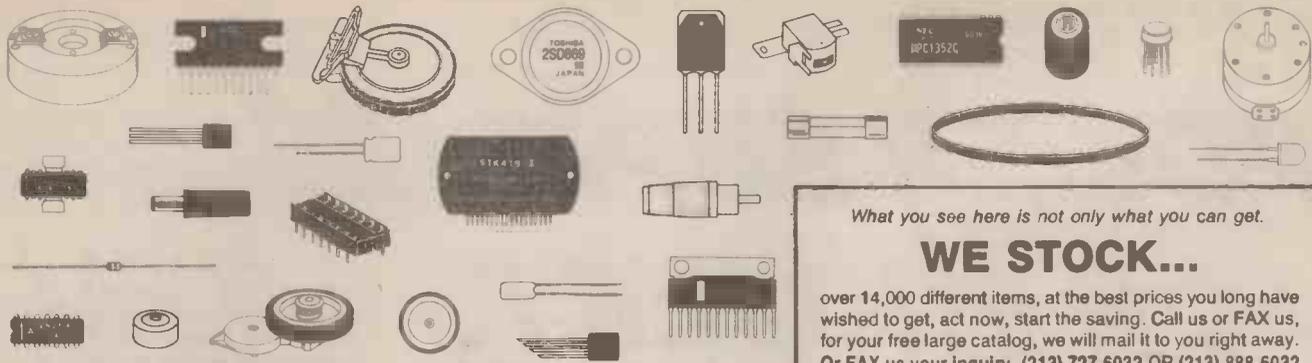
### THE COUPÉ

A new SAM coupé User Group and PD library has been formed. Anyone interested in joining a should contact them at 10 Ricardo Rd., Old Windsor, Berkshire. SL4 2NU



What you see here is not only what you can get.

## WE STOCK...

over 14,000 different items, at the best prices you long have wished to get, act now, start the saving. Call us or FAX us, for your free large catalog, we will mail it to you right away. Or FAX us your inquiry. (213) 727-6032 OR (213) 888-6032

## YOUR RELIABLE ELECTRONIC COMPONENTS SUPPLY

- HIGH QUALITY PRODUCTS
- BEST PRICES YOU LONG HAVE WISHED TO GET
- FOR IMMEDIATE DELIVERY & RAPID SHIPMENT
- ORIGINAL REPLACEMENT PARTS
- ASK FOR YOUR FREE COPY CATALOG
- AGENTS & DISTRIBUTORS (IMPORT & EXPORT)
- WE REPLY TO YOUR INQUIRY IN THE SAME DAY
- COMPETITIVE PRICES, DISCOUNTS FOR WHOLESALE QUANTITIES

- WE SHIP YOUR ORDER ON THE DATE OF YOUR CONFIRMATION WITH FAST COURIER
- SO ACT NOW AND START SAVING
- IF YOU DON'T SEE IT, ASK FOR IT
- SPECIALIST IN EXPORT

We are continuously updating our inventory, let us hear from you of things we do not have, we will give it a study.

TO ORDER: INFORM US YOUR INQUIRY, OR ASK FOR YOUR FREE FULL CATALOG AND PRICES.

**DALBANI CORPORATION  
OF AMERICA**

2733 CARRIER AVENUE  
LOS ANGELES, CALIFORNIA 90040  
UNITED STATES OF AMERICA

Tel: (213) 727-0054  
Fax: (213) 727-6032  
Fax: (213) 888-6032  
Tlx: 3722489

ALL SALES IN U.S. DOLLARS



WE ACCEPT VISA / MASTERCARD

Remember  
The Cricklewood  
Service is Fast  
and Efficient

# CRICKLEWOOD ELECTRONICS

**BIGGER  
AND BETTER**

**1990 COMPONENTS  
CATALOGUE**

- ONE OF THE LARGEST RANGES OF COMPONENTS IN THE UK
- FAST AND EFFICIENT SAME DAY PERSONAL SERVICE
- VERY COMPETITIVE PRICES; QUANTITY DISCOUNTS AVAILABLE
- DISCOUNT VOUCHERS INCLUDED
- NO MINIMUM ORDER

JUST LIKE A NEW CAR! YOU CAN ONLY JUDGE THE 1990 CATALOGUE BY LOOKING UNDER THE COVER. WITH OVER 13,000 STOCK LINES, CRICKLEWOOD ARE ABLE TO SUPPLY MOST OF THE COMPONENTS NEEDED FOR E.E. PROJECTS. PHONE US FOR YOUR SPECIAL NEEDS.

FILL IN THE COUPON AND POST IT WITH YOUR CHEQUE, PO ETC FOR £1.50 TO RECEIVE YOUR 1990 CRICKLEWOOD ELECTRONICS CATALOGUE AND VOUCHERS WHICH YOU CAN USE AGAINST YOUR NEXT PURCHASE

**Cricklewood Electronics Ltd**  
40 CRICKLEWOOD BROADWAY, LONDON, NW2 3ET  
Tel: 01-450 0995/452 0161  
Fax: 01-208 1441 Telex: 914977



TELEPHONE ORDERS OUR SPECIALITY

## CRICKLEWOOD ELECTRONICS 1990 COMPONENTS CATALOGUE

PLEASE SEND ..... COPIES OF THE 1990  
CRICKLEWOOD ELECTRONICS CATALOGUE AT  
£1.50 TO:

NAME .....

ADDRESS .....

.....

.....

.....

Remittance enclosed £..... **E**

# POWER SUPPLIES FOR PROJECTS

VIVIAN CAPEL



*A straightforward introduction to the design of simple mains power supplies:*

**M**OST PROJECTS have one thing in common, they need a power supply. In many cases a suitable battery is all that is required, but if the circuit takes more than a few mA, or operates for more than a few minutes, battery powering can be expensive.

A mains power supply unit (PSU) is easy to design and build – but there are pitfalls. We hope to point out some of these pitfalls and not only give circuits but examine principles and show how to design your own to suit that special project.

The simplest circuit consists of a diode to rectify the a.c., a resistor to drop the voltage to the required value and a reservoir capacitor to smooth the result (Fig. 1). The main snag with this circuit is *safety*. One side of the mains supply is connected directly to the negative of the d.c. output which usually in turn is connected to the chassis, case, and flying leads. While you may ensure that the mains plug is fitted so that the neutral is connected to the d.c. negative, the plug could later be removed and replaced incorrectly.

Another snag is that most modern circuits use semiconductors which require only a low voltage. The resistor thus needs to be of high value to drop from the 240V mains, and most of the power is wasted in heating it.

Furthermore, the voltage drop depends on the value of the current taken, if it varies, so does the voltage. If the current ceases due to a malfunction of the project, the voltage rises to well above the mains voltage (why it goes higher we will explain later). If then the capacitor has a low voltage rating, it will object most vigorously, get very hot under the collar, and most likely explode!

One way of reducing the effect of current variation or cessation, is to fit a bleeder resistor across the circuit. To be effective it must pass at least two or three times the current taken by the load, which is even more wasteful and generates more heat.

Has this circuit no practical applications at all then? Yes it has, in fact it was the standard method of powering valved TV receivers for a couple of decades. With these, the bleeder was provided by a series chain of valve heaters, and the d.c. supply needed was in the region of 200V so not much had to be dropped. Even so, large wire-wound resistors were used that got very hot.

The circuit should thus be used only when a large constant current is required at near mains voltage. Even then, precautions must be taken to isolate it so that no external leads or metalwork are connected to the mains.

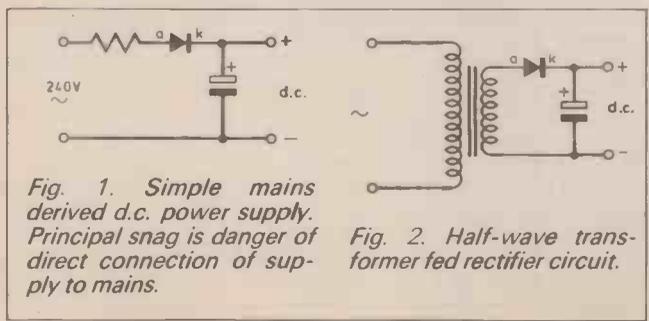


Fig. 1. Simple mains derived d.c. power supply. Principal snag is danger of direct connection of supply to mains.

Fig. 2. Half-wave transformer fed rectifier circuit.

The value of any resistors used can be easily calculated by Ohms law from the voltage drop required and current taken ( $R = V/I$ ). Use the same values to calculate their wattage rating ( $W = VI$ ), the current in both cases being in amps.

## TRANSFORMERS

The circuit we have just considered is more usually fed from a transformer as shown in Fig. 2, so first of all a few relevant points about transformers. A simple transformer as shown has a *primary* (pri.) winding and *secondary* (sec.) winding that are in close proximity and sharing a common iron core. The magnetic coupling between them induces a voltage across the secondary which is proportional to their turns ratio in relation to the voltage applied to the primary. So, a turns ratio of 1:10 produces 24 volts from a primary voltage of 240V.

It follows from this that a choice of voltages can be obtained by arranging for tappings on the secondary to provide different ratios. Usually the most common is a centre tap (ct.) which gives two equal voltages but in opposite phase, that is the end of one section goes negative as the other is going positive. This has its main application in full-wave rectifiers and split polarity systems as we shall see. Many transformers have several secondaries each having a different voltage and current rating.

Transformers are rated in VA which is volt-amps. This specifies the maximum power that can be taken without overloading. The current rating for a particular winding is the maximum for that winding, but it does not follow that the maximum can be taken from *all* windings at the same time. The products of the voltage and current in amps taken from all windings when added must not exceed the VA figure for the transformer.

So for example, a transformer with a 6V 1A and a 12V 0.5A winding is rated at 6VA. Either of those secondaries can be fully loaded but not both. Alternatively, 0.7A could be taken from the 6V winding (4.2VA) as well as 0.15A from the 12V (1.8VA), or any other combination that added up to 6VA.

The power flowing in all secondary windings is equal to that in the primary minus a few per cent due to various losses. So, ignoring losses, in the mains primary the current is only a tenth of what it is in a single 24V secondary. Thus it can be wound with much thinner wire.

This is useful when identifying unmarked windings. The thin wires are the high voltage ones which in most cases is the mains primary, and the thick ones are the low-voltage wires. If the wires are concealed by sleeving right up to the tags, they can be identified by resistance measurements, the high resistance one being the primary.

When measuring any winding that is centre-tapped it will be found that one half has a higher resistance than the other. This may give rise to doubts as to whether the centre-tap is true. There is no need to worry though. The reason for the unequal resistance is that the windings are wound on a bobbin which gets thicker as more turns are added, so the outer half will have more wire than the inner, although both have the same number of turns. As it is the number of turns that matter, the resistance difference can be disregarded.

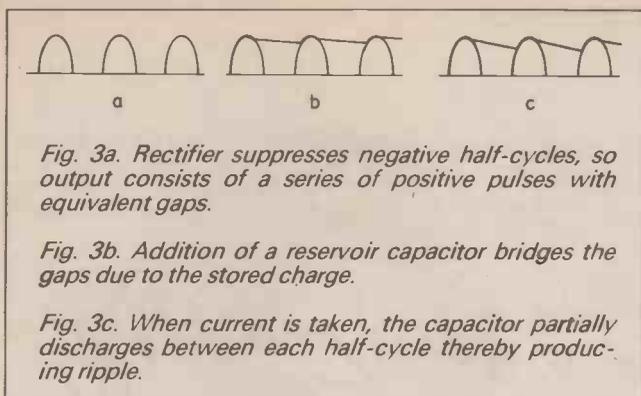


Fig. 3a. Rectifier suppresses negative half-cycles, so output consists of a series of positive pulses with equivalent gaps.

Fig. 3b. Addition of a reservoir capacitor bridges the gaps due to the stored charge.

Fig. 3c. When current is taken, the capacitor partially discharges between each half-cycle thereby producing ripple.

When the full rated current is being taken from the secondary the resistances of both primary and secondary cause a voltage drop, and there are also magnetic losses. The result is that the voltage at full load is less than it is off load.

The difference is given by the *regulation* figure which is quoted as a percentage. For large transformers the figure is typically 5 per cent, but in the case of miniature ones it can be as high as 25 per cent. For medium-sized units, 10 to 15 per cent is normal. Transformers are usually wound to give their rated voltage at full load.

This means that for a 10 per cent regulation, the voltage off load will be 10 per cent higher than the full-load rating: If the load fluctuates, so also will the voltage between the two limits. This may be important with some circuits.

For the mathematically inclined, the formula for regulation is:

$$\text{Regulation} = \frac{V_{OL} - V_{FL}}{V_{OL}} \times 100\%$$

In which  $V_{OL}$  is the off-load voltage, and  $V_{FL}$  is the full-load voltage.

Toroidal transformers are of particular interest for powering audio equipment especially where low-level signals are present. They have a doughnut shaped construction which gives a very low flux leakage, hence a low hum field.

Care though must be taken in mounting them. They are usually secured by a single bolt through a metal clamping disc at the top, down to the chassis. No earthed strut or other member should be fixed to the top of the bolt as this would form a single shorted turn which would overload the transformer.

## RESERVOIR CAPACITOR

The "reservoir capacitor" is a much misunderstood component, it is generally believed to just smooth the hum from the d.c. Well it does that, but there is much more to it.

Without this capacitor the output from a half-wave rectifier using a single diode as in Fig. 2 is a series of positive humps with a gap in between them where the suppressed negative half cycle should be, Fig. 3a. Half of the time the volts are zero, and for the rest, are somewhere between zero and peak. A meter connected across the circuit gives about 0.45 of the transformer voltage rating.

With the capacitor connected, the reading jumps dramatically. The capacitor charges to the value of the first peak, and drops only slightly due to capacitor leakage and the current taken by the meter, until the next peak which restores it to full value again, Fig. 3b. The voltage reading is thus that of the a.c. voltage peak.

Now a.c. voltages and currents are not specified by their peak values as these would be of little real use when the values are just as often zero as they are at peak. An average value which is 0.636 of the peak, may therefore be considered more useful, but is still not right.

Instead, the practical value chosen to describe an a.c. sine wave, is that of a d.c. voltage current which would produce the same heating effect in a wire element. This is known as the root-mean-square (r.m.s.) value and is 0.707 the value of the peak.

So all ordinary meters read the r.m.s. value, and transformers are rated at it. The peak value is the reciprocal of 0.707 which is 1.414, so when we take a reading after adding a reservoir capacitor, it indicates the peak value and therefore jumps from 0.45 to 1.414 times the transformer rating.

This gives the rather surprising effect of a 9V transformer producing  $9 \times 1.414 = 12.7$  volts d.c. off load. It gives us an important rule when designing a power supply with a reservoir, the transformer must be chosen to be about three-quarters that of the required d.c. voltage.

When a load is applied, the reservoir capacitor discharges through it as soon as the peak has passed, but is recharged on the

next peak. The effect is illustrated in Fig. 3c. Now the greater the current drawn, the faster the discharge and the steeper the discharge curve. This produces a more pronounced ripple on the d.c. supply, which is evident when comparing Fig. 3b in which there is very little current, with Fig. 3c.

This incidentally, can give a clue to excess current in an audio amplifier. If a hum suddenly develops it can be the result of heavy current, usually due to a fault in the output stage, causing a steep discharge of the reservoir capacitor between peaks, thereby increasing the ripple.

There can of course be other causes of hum, but if it appears suddenly in a previously hum-free amplifier, this is a very likely cause. It is as well to switch off quickly before wisps of smoke from the output stage confirm it!

But back to the reservoir capacitor. If we fit a higher value it will take longer to discharge so producing shallower discharge curves and less ripple. So, the value of the reservoir capacitor should be chosen in relation to the required load current. High values are needed for high currents if ripple is to be kept low.

## SURGE LIMITER

When using high values though, it means that a high current flows into the capacitor in a short space of time near the tip of each peak. In addition a high current flows into it at switch-on from the fully discharged state. To reduce this surge a small-value resistor termed a *surge limiter* may be wired in series with the rectifier either on the a.c. or d.c. side.

This short-duration high current at each positive peak is some  $3\frac{1}{2}$  times that of the load current, and is supplied by the transformer which must be capable of delivering it. Therefore the available load current is only 0.28 of the transformer a.c. current rating.

The reservoir capacitor, as all other capacitors, must be of adequate voltage rating for the intended circuit. It is always wise to use one with a good safety margin, at least 25 per cent higher than the applied voltage. It has been found that reliability is closely related to the difference between the rated and applied voltage; those with a large safety margin rarely give trouble.

One factor with potentially disastrous results that is often overlooked in the selection of a reservoir capacitor, is the *ripple current rating*. From our investigation of the function of the reservoir capacitor, it is evident that current equal to that of the total d.c. load is constantly flowing into and out of it.

It must therefore be capable of passing that current which is why reservoir capacitors in high current circuits are physically large. If it is not, it will get hot and can explode. Be in no doubt, an exploding reservoir capacitor is a fearful sight to behold!

The rule is that the ripple current rating of the reservoir capacitor must be equal to or greater than the maximum load current likely to be drawn from the circuit. Physically small capacitors, although of adequate voltage rating and capacitance rarely have a sufficient ripple current specification unless the required load current is small. Most reputable suppliers can give the ripple current rating of capacitors they stock even if it does not appear on the capacitor itself, so be sure to check it before using one.

## RECTIFIERS

Silicon rectifiers are now universally used because of their small size and big current ratings. They are a far cry from the rectifiers of a few years ago which were large and had an array of cooling fins that had to be mounted vertically to allow a free flow of air through them. They frequently deteriorated resulting in a lowered supply voltage, and commonly developed a short-circuit to the earthed-fixing bracket with spectacular results and a dreadful smell that hung around for days.

All those little pleasantries are fortunately in the past and the present devices are comparatively trouble-free if they are treated properly. Current ratings must not be exceeded, but this is no problem as rectifiers are available up to very high currents. Choose one with a generous current safety margin as the cost difference is minimal.

The point to watch is the Peak Inverse Voltage rating (PIV). If we take a look at Fig. 4, we shall see what happens on the negative half-cycle when the rectifier is non-conducting. The transformer winding is negative at the top end and positive at the bottom, while the reservoir capacitor is negative at the bottom and positive at the top. The combined voltage, in series, of the winding and the capacitor thereby add together and is applied across the rectifier. As the capacitor and transformer winding each have the peak voltage appearing across them, the total reverse voltage applied to the rectifier is twice that peak. This amounts to 2.8 times the r.m.s. voltage.

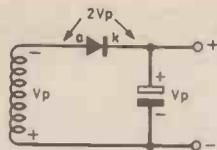


Fig. 4. During negative half-cycles when rectifier is non-conducting, the peak voltage stored in the capacitor in series with the negative voltage in the transformer winding imposes a reverse voltage of twice the peak or 2.8 times the r.m.s. across the rectifier.

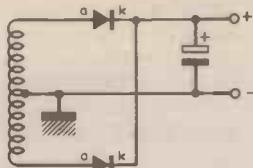


Fig. 5. A full-wave rectifier circuit using a centre-tapped winding.



Fig. 6. Both half-cycles are positive with a full-wave circuit, so the capacitor discharge is less and ripple is reduced.

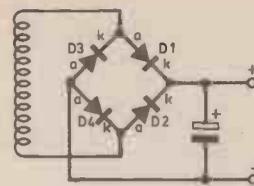


Fig. 7. A bridge circuit provides full-wave rectification without a transformer centre tap.

So the PIV rating of the rectifier must be greater than about three times the r.m.s. voltage of the transformer secondary. If it is not, the rectifier will fail prematurely. Overlooking this point is a common cause of rectifier failures.

Silicon rectifiers drop about 0.6V irrespective of the load current so that must be allowed for in low voltage PSUs. Should this cause a problem an alternative is to use a *germanium* diode as these drop only about 0.15V to 0.2V. A useful one is the OA47 which has a current rating of 110mA and PIV of 25V.

If by the way, you are one of the many folk who can never remember which way round a rectifier goes, a good mnemonic is to remember *pp*, which reminds us that the arrow points to the positive. The physical shape of most rectifiers is also pointed at the positive end, so the same aid applies.

## FULL-WAVE RECTIFIER

The circuit we have so far considered is known as a "half-wave rectifier" because it rectifies only the positive halves of the a.c. cycle. A "full-wave" circuit rectifies both halves. The transformer secondary winding has a centre tap, or more usually two separate windings, which can be connected end-to-end. Having separate windings means that they can be used for separate isolated functions if required and so are more versatile.

The important thing with twin windings is to ensure they are connected the right way round. The start of one must be connected to the finish of the other, if two starts or two finishes are connected together there will be zero voltage output. Two diodes are used, one at each end of the winding, and their cathodes (k) are connected together to the positive of the reservoir capacitor. The centre tap of the windings is the negative and is usually earthed, Fig. 5.

As the reservoir capacitor is being topped up at each half-cycle instead of alternative ones its capacity can be less and also the ripple is less, Fig. 6. It is still supplying the whole load current at the a.c. zero points though, so the same ripple current applies as for the half-wave circuit.

The d.c. voltage produced is the same as for the half-wave circuit if we consider each half of the winding and its diode as a separate half-wave rectifier. Thus the d.c. voltage is 1.4 times the a.c. rating of the half of a single centre-tapped winding, or of one of a pair. If the rating of the whole winding is used, then the d.c. voltage is half that, which is 0.7 times the a.c.

Current is supplied on both half-cycles, so the d.c. current is equal to the a.c. flowing in the secondary. This is a big improvement on the half-wave system in which it is only 0.28 times the a.c. Smaller windings can thus be used, although there must be the equivalent of two secondaries. As each diode behaves as a half-wave rectifier, the same peak inverse voltage limits apply.

## BRIDGE RECTIFIER

The bridge is also full-wave, but is usually so called to distinguish it from the circuit already described. As shown in Fig. 7, it has four diodes in a diamond configuration and is fed from a single untapped transformer winding. Two anodes are taken to the negative d.c. line, while the two cathodes of the other pair are connected to the positive. The two anode/cathode junctions then go to the ends of the winding.

If you have problems remembering the diode connections for the other circuits this may seem a lot worse. However, the same *pp* rule applies as before; all arrows point toward the positive, even D3 and D4, the ones nearest the winding because they point through D1 and D2.

The bridge works as follows: When the top of the winding is positive and the bottom negative, diode D1 conducts the posi-

tive charge to the positive line and diode D4 conveys the negative charge to the negative line. Diodes D2 and D3 are non-conducting. When the polarity reverses and the top of the winding becomes negative, D3 conducts the charge to the negative line, while D2 connects the bottom of the winding which is now positive to the positive line. Thus the diodes that are diagonally opposite conduct together on alternate half cycles.

This arrangement halves the amount of wire in the transformer secondary because the whole winding is conducting at both half cycles whereas with the full-wave circuit each half of the winding conducts only on alternate ones. The transformer yoke can be made smaller and there are also fewer winding lead-outs and terminal tags. So, the transformer is cheaper for the cost of two extra inexpensive diodes. The net saving may not be spectacular for a one-off, but for a production run of several thousand is considerable. Hence the popularity of the bridge circuit with equipment manufacturers.

D.C. voltage is 1.4 times the a.c. rating of the whole winding in contrast to the 0.7 times of the whole winding of the centre-tapped circuit. Current though is lower, being 0.62 times the a.c.

## SPLIT-POLARITY FULL-WAVE

Many i.c.s require both negative and positive supplies relative to a central "earth" or 0V point. In some cases they will work with a pair of resistors across a single-pole supply, the centre connection going to the 0V point, but not all will. A split supply circuit is shown in Fig. 8. At first glance it looks like a bridge circuit but it is not, it is in fact a *dual* polarity full-wave p.s.u.

If you ignore diodes D3 and D4, it can be seen that diodes D1 and D2 comprise a normal full-wave rectifier circuit with transformer centre-tap the same as Fig. 5. Diodes D3 and D4 make up another full-wave circuit using the same transformer but with their anodes taken to the output which is therefore negative. The reservoir capacitor for this section has its negative connected to the supply line and its positive to earth or 0V.

Just as with a single pole full-wave circuit, a transformer with twin secondaries can be used in place of a single centre-tapped winding.

The d.c. voltage is the same for each section as that of the single full-wave circuit, that is 0.7 of the whole winding, or 1.4 times the half, or one of a pair. As the same secondary is supplying both circuits, the d.c. current for each is half that of a single full-wave circuit, which is also half the a.c. rating.

## REGULATORS

If a *constant voltage* is required that will not vary in spite of wide variations in load current, a *regulator* can be included in the power circuit. One important bonus with a regulator is that because it keeps the voltage constant, it also reduces ripple to a low order. Ripple can cause many unexpected snags with otherwise trouble-free circuits, and it produces hum or buzz in audio circuits.

A regulator should be included as a matter of course with all low level audio circuits such as microphone mixers and moving-coil gram stages as it provides a super-smooth supply to a degree that is difficult to attain by RC decoupling. It also gives a high rejection of signal coupling via the supply and so reduces the possibility of instability.

Fortunately all these advantages can be obtained quite easily, as there is a wide range of regulator integrated circuit (i.c.) chips available that are inexpensive and easy to use, most have only three connections, an "in", "out", and "common" earth. They are also available in positive or negative versions.

All regulators reduce the applied voltage to the specified output value, so unlike a capacitor they cannot maintain the voltage if it

dips below it. If there is any chance of this happening, a suitable capacitor should be connected to the input side to maintain the voltage during such lows, leaving the regulator to smooth out the voltage variations above it. The supplied data thus specifies a minimum input voltage which is a few volts above the regulated output. There is also a maximum.

A popular regulator i.c. which has built-in overload, thermal and short-circuit protection is the 78, and 79 series. The 78L is rated at 100mA, positive output, the 79L at 100mA negative output, the 78 and 79 give 1A positive and negative respectively, and the 78S, 2A positive output. There are many other types but these are perhaps the most useful for general work. Each type has a suffix which denotes the output voltage.

The devices are encapsulated with a three-pin lead-out which is the same for the 78 and 78S series, but not the 79 which has the same encapsulation but different pin connections. The 78L and 79L are housed in TO92 type cases.

A heatsink is required for the 78, 79 and 78S but not the 78L and 79L. In most cases heat sinking can be achieved by bolting the device to a main member of a metal case. A little heatsink grease smeared on the back of the mounting lug before it is fitted will improve the heat-transfer.

### Regulator Data

Device	Output Voltage	Input Voltage	Equivalents
7805	+5V ( $\pm 0.2V$ )	7.0-25V	$\mu A7805UC$ ; LM340T-05; MC7805CP; SN72905.
7812	+12V ( $\pm 0.5V$ )	14.5-30V	$\mu A7812UC$ ; LM340T-12; MC7812CP; SN72912.
7815	+15V ( $\pm 0.6V$ )	17.5-30V	$\mu A7815UC$ ; LM340T-15; MC7815CP; SN72915.
7824	+24V ( $\pm 1.0V$ )	27.0-38V	
78L05	+5V ( $\pm 5\%$ )	7.0-30V	
78L12	+12V ( $\pm 5\%$ )	14.5-35V	
78L15	+15V ( $\pm 5\%$ )	17.5-35V	
78L24	+24V ( $\pm 5\%$ )	27.0-35V	
7905	-5V ( $\pm 0.2V$ )	7.0-25V	
7912	-12V ( $\pm 0.5V$ )	14.5-30V	
7915	-15V ( $\pm 0.6V$ )	17.5-30V	$\mu A7915UC$ ; LM320T-15; MC7915CP.
7924	-24V ( $\pm 1.0V$ )	27.0-38V	
79L05	-5V ( $\pm 10\%$ )	7.0-30V	
79L12	-12V ( $\pm 5\%$ )	14.5-35V	
79L15	-15V ( $\pm 5\%$ )	17.5-35V	
79L24	-24V ( $\pm 5\%$ )	27.0-35V	
78S05	+5V ( $\pm 0.2V$ )	8.0-35V	
78S12	+12V ( $\pm 0.5V$ )	15.0-35V	
78S15	+15V ( $\pm 0.6V$ )	18.0-35V	
78S24	+24V ( $\pm 1.0V$ )	27.0-40V	

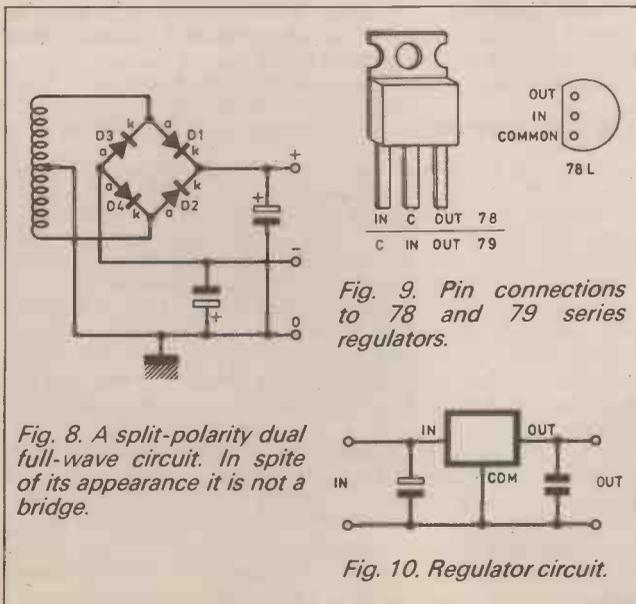


Fig. 8. A split-polarity dual full-wave circuit. In spite of its appearance it is not a bridge.

Fig. 9. Pin connections to 78 and 79 series regulators.

Fig. 10. Regulator circuit.

The pin configurations are shown in Fig. 9. The metal fixing lug is connected to the common earthed pin with the 78 and 78S regulators and so for most circuits can be bolted directly to an earthed metal chassis or case without insulating it. A regulator circuit is shown in Fig. 10.

### LAYOUT

There are not many problems in laying out a power supply circuit providing a few simple rules are observed. The components should be physically separated from any low-level signal circuits as far as reasonably possible. This is especially so if the transformer is not toroidal.

If there are separate modules or printed circuit boards in the project being powered, separate negative wires should be brought from each to the same earth tag as the negative of the reservoir capacitor. The same applies to the positives which should be brought back individually to the reservoir positive.

This is an example of preventive fault elimination. In many cases it isn't really necessary, and the supply leads can be looped from one unit to another, but common impedances are thereby introduced. These can cause coupling between circuits which can produce quite baffling symptoms. So, it is usually better to play safe.

If the power supply components are all mounted on a printed circuit board, connect the negative print or pad from the reservoir capacitor to an earth point and do not connect anything else to that print. It may be tempting to earth some other nearby circuit to a convenient point on this print or to the negative of the capacitor itself. However, high ripple current travels along the print from capacitor negative to the earth point and any circuit connected thereto will certainly have ripple voltage fed to it.

### DESIGNING A PSU

From the information given we should now be in a position to design a PSU for any specific requirement. We will now go through the steps for a particular case as an example. The project is a Stereo Power Amplifier 30 watts per channel, requiring a 35V supply, but with a pre-amp needing 12V.

The first stage is to find a suitable transformer from those locally available and then design the circuit around it. To supply 60W of audio power, the mains transformer must be able to provide that and an extra margin to allow for losses. If the amplifiers are class A, a much higher power would be needed as losses are greater, but these are rare and we can assume that the amplifiers are class B. A transformer with an 80VA rating should be about right.

The a.c. voltage required is 0.7 of the d.c. output so we need a winding giving 25V. We find that most transformers offer twin windings so we can connect them end-to-end to give full-wave rectification using only two diodes.

An alternative which may appeal to hi-fi enthusiasts is to drive each amplifier from a separate power supply, which is said to improve sound quality and stereo separation. In this case each winding can be connected to a bridge circuit of four diodes so needing eight in all.

Next, comes the reservoir capacitor. The working voltage should provide a margin over the 35V supply, so 50V should be chosen. On peaks at full power, the amplifiers will be taking  $60W \div 35V = 1.7A$ , so the ripple current must be at least this. Usually, large value electrolytics at high working voltage have a high ripple current rating. A typical example of  $4,700\mu F$  at 50V has a ripple current of 4.1A. It is at lower voltages and capacitances that the ripple current must be watched.

For the diodes, we need a PIV of  $35 \times 2.8 = 98V$  minimum, and a current rating of 1.7A minimum. The *1N5402* has a PIV rating of 200V and a current rating of 3A, so it should do nicely.

Now we have to provide the 12V supply for the pre-amp which has a current drain of 20mA. A 12V regulator, the *78L12* will take up to 100mA and does not require a heatsink. Its maximum input voltage is 35V which could just about work off the 35V supply. However, the maximum load on the transformer occurs only on the peaks in the music; during quiet passages and silences, the power amplifier current is minimal. Assuming a 10 per cent transformer regulation, the d.c. voltage will then rise some 3.5V to 38.5V.

A resistor in series with the input to the regulator will drop the voltage to a safe level below the maximum. At 20mA, a 470 ohm drops 9.4V, so the input voltage will then range from about 26V - 29V. The regulator also gives a 55dB ripple rejection, which is highly desirable for a pre-amp.

This example illustrates how the various factors we have described can be applied to produce a correctly designed PSU for any project. □

# DOWN TO EARTH

BY GEORGE HYLTON

IF YOU'RE interested in the ways things are invented, the radio valve provides both information and amusement. It may have lessons for today. The man who made the pioneering discovery didn't realise its significance. The man who did realise it got the credit. And the man who turned it into the amplifying device which started the first electronic revolution didn't know how it worked.

## EDISON EFFECT

Edison was one of the pioneers of filament lamps. (He's often credited with inventing them, but in fact the earliest examples were made by a Brit called Swan.) Anyway, in the course of experimenting with lamps, Edison discovered that if a metal plate is placed near the filament (Fig 1), current flows as shown if this plate is made positive, but not if made negative.

This was a very interesting discovery. It showed that current can flow through a vacuum (the early lamps were vacuum lamps, not inert-gas-filled ones as now). Since a vacuum is empty space, with nothing in it to conduct current, this was surprising. It might have been expected to act as a perfect insulator. Since substantial current flowed only when the plate was made positive with respect to the filament, this suggested that negatively charged particles ("thermions") were being thrown off the hot filament and attracted to the positive charge on the plate.

## FLEMING

Edison was a busy man and didn't

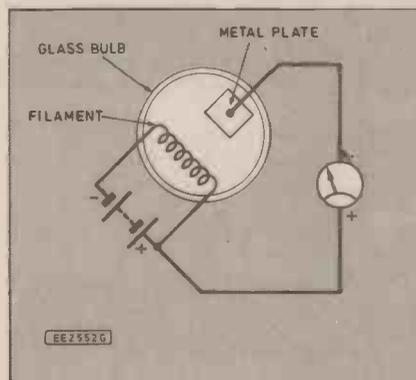


Fig. 1 Edison Effect.

follow up his discovery. About 20 years later, in Britain, Ambrose Fleming realised that the Edison Effect, as it was called, could be put to use as a means of "detecting" the radio waves which were then being vigorously promoted for communications by Marconi.

Fleming patented his "thermionic diode" detector in 1905. By then, the nature of the negatively charged particles was known. In Britain, one physicist J.J. Thompson, had identified the electron in 1899. Another, O. W. Richardson, saw that electron flow explained the Edison Effect.

The "thermions" were electrons, given enough thermal energy to leave the filament. Fleming's diode was called a valve by analogy with fluid engineering. It acted as a one-way gate for current. This enabled it to rectify a.c. signals, including radio waves (Fig. 2). Rectifiers were called detectors because, in their various forms, they enabled radio waves to be "detected"; i.e. turned into d.c. to operate some sort of indicator such as a galvanometer.

In fact, the diode valve (or vacuum tube as the Americans said) wasn't a very good detector of feeble signals. Other detectors were more sensitive. The diode really came into its own much later, after it had become possible to amplify radio signals.

## LEE DE FOREST

An American physicist, Lee de Forest, became interested in the diode. There was a problem in using it — Fleming held the patent. So de Forest set about modifying the diode to get round the patent protection. He was hampered by a firm belief that diode detection required the presence of a thin gas inside the envelope.

The important change made by de Forest was to add a third electrode (Fig. 3). The signal was applied between filament and the extra electrode. Output was taken at the plate, which was given a strong positive bias. It was found that the triode detector worked better if the signal electrode had the form of a wire grid.

Looking at Fig. 3 with our modern knowledge of transistors and f.e.t.s. it seems incredible that de Forest didn't immediately recognise that he had constructed an amplifying device. To us, with hindsight, the filament is an emitter or source of electrons. The plate is a collector. The grid is a gate, controlling the flow between emitter and collector.

Yet, although de Forest patented his grid triode detector in 1907, it wasn't until 1912 that he (in common with several other workers in other places)

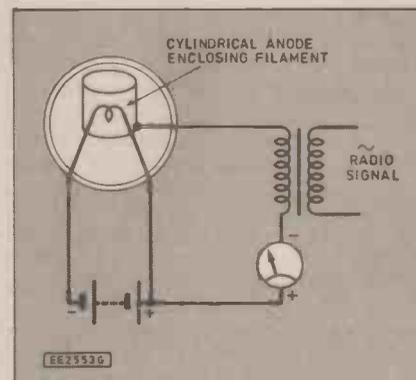


Fig. 2 Diode valve.

discovered that it could be made to amplify as well as detect. The ensuing legal battle over patents was won, in the USA, by de Forest.

As to the exploitation of the triode, that was done by more competent workers who disregarded de Forest's quaint ideas about the need for gas and designed efficient triodes which used a hard vacuum.

## LESSONS

Perhaps the most significant lesson to emerge from this bizarre story is the usefulness of publishing discoveries. Making known the Edison Effect laid the foundation for other work. But the story also shows the benefits of simply playing about with things. Adding a third electrode to the diode was just playing about but its consequences were momentous.

Of course, if de Forest had ceased believing that the presence of gas was necessary, and instead had looked at his triode in terms of electron flow he might well have discovered the amplifying ability much earlier. But he didn't. Playing about is fine, but playing about plus careful thought is finer. As Pasteur said, chance favours the prepared mind.

## TRANSISTORS

The search for the transistor was more purposeful. It took longer because the materials technology was very difficult, but at least the researches at Bell Telephone laboratories knew what they were after; a solid equivalent of the triode valve. It's said that the first transistor (the point-contact transistor) was really discovered accidentally in the course of experiments which aimed to produce what we know as the field-effect transistor. Maybe, but its significance was understood at one, and soon led to the invention of the junction transistor which paved the way to the micro-electronic revolution.

## VALVE REBORN?

It's just possible that the valve, now used for only special applications, may be reborn, but in a new form. Vacuum devices have one property which has become very important as computing speed has risen. Electrons, once launched into a vacuum, can move freely. In transistor language they have very high mobility, which is what you want for high-speed computing circuits.

There are two drawbacks. One is that traditional valves are too large. The other is that relatively enormous amounts of

Continued on page 344

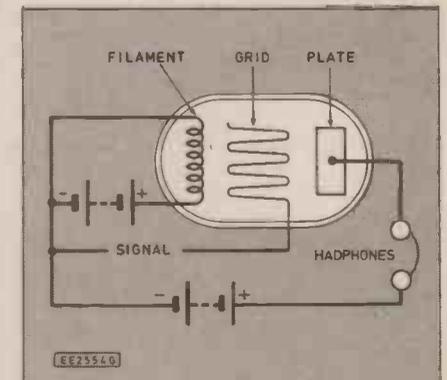


Fig. 3 De Forest's Triode Detector

## BUILD IT YOURSELF!

### MOTHERBOARDS

**XT TURBO**  
12MHz, V20, 0k, 8 slots. Small size, takes 256k x 4 DIL.  
**£62.10 (+ £4.50 P&P)**

**AT TURBO**  
12MHz, 0k, up to 4 M on board. Seven slots, takes 256k x 1, or 256k x 4, or 1M x 1.  
**£158.00 (+ £4.50 P&P)**

**AT TURBO PLUS**  
12MHz, up to 4 M on board. Eight slots, takes 256k x 4 or SIPs. EMS fitted.  
**£188.00 (+ £4.50 P&P)**

### STARTER SYSTEMS

Both include a full 1Mbyte of RAM, 101/102 key keyboard, a 12" mono monitor, Hercules graphics, DR-DOS and a parallel port. Both run at 12MHz clock speed and have eight slots.

**AT mini-tower £749**  
**XT system £459**  
Delivery Included

### CASES

**XT/AT CASE**  
Space for three 5.25" floppy/hard disk drives and one 3.5" drive.  
**£44.50 (+ £6 P&P)**  
**180W PSU £44.85 (+£3 P&P)**

**DE-LUXE CASE**  
Same disk space but prettier! Speed display.  
**£65.00 (+ £6 P&P)**

**MINI TOWER CASE**  
AS DE-LUXE case but desk-top tower style.  
**£72.50 (+ £6 P&P)**  
**200W PSU £69 (+ £3 P&P)**

### PC-DIY BOOK

If you are more sure how to go about building your own PC, this book is for you. 112 pages full of DIY tips for £7.95 including postage.

**VAT is INCLUDED in all our prices.**  
Why not telephone or write for our free catalogue?

### DISPLAY ADAPTERS

**UNIVERSAL VGA**  
This board auto-switches between 8 and 16 bit, drives mono, EGA and VGA monitors, (in native mode) and supports all standard VGA modes. Easy upgrade to extended VGA to give 1024 by 768.

**£137.00 (+ £2 P&P)**  
**DUAL CGA/HERC**  
Auto-switch, plus port for printer.  
**£38.00 (+ £2 P&P)**  
**102 keyboard £46 (+£5 P&P)**

### I/O ADAPTERS

**RS232 short card.**  
**£16.10 (+ £2 P&P)**

**AT SERIAL/GAME/ PARALLEL CARD**  
Sockets for serial 2.  
**£11.50 (+ £2 P&P)**

**FLOPPY controller for XT or AT, 360, 720, 1.2, 1.44. Two drives 3.5" or 5.25".**  
**£24 (+ £2 P&P)**

## BLACKMORE ELECTRONICS LTD

4 THE PLOCKS, BLANDFORD FORUM,  
DORSET DT11 7AA


Tel: (0258) 451347 Fax: (0258) 456046

ALL MAJOR CREDIT CARDS ACCEPTED BY POST, TELEPHONE OR FAX

When you need

## COMPONENTS

(C.W.O. Post Free U.K.)

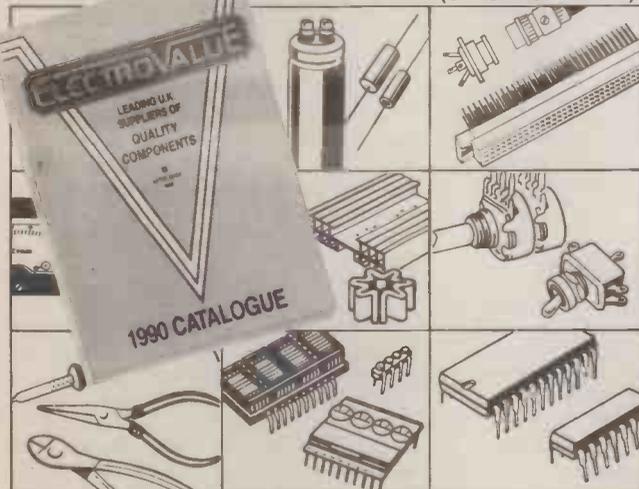

You need

## ELECTROVALUE

for **FREE CATALOGUE** write phone or call

ELECTROVALUE LTD, FREEPOST, 28b St. Jude's Rd., Englefield Green, Egham, Surrey TW20 8BR  
(No stamp required). Phone 0784 433 603. Fax 0784 435 216. Telex 264475.

Shop hours 9.0-5.30pm (Sat 9.0-1.0pm)

NORTHERN BRANCH 680 Burnage Lane, Manchester M19 1NA. Phone 061-432 4945. Fax 061-432 4127.

## PUBLIC ADDRESS AND DISCO EQUIPMENT

# YOU PAY TRADE PRICES!



### MIXERS

Choose from 25 models ■ Mixers for home use, disco's, public address and studio use ■ From 4 to 16 channels  
■ Also 6 and 8 ch midi systems  
■ Equalizer mixers MRT60 and many more.

### ECHO'S

■ VC1 analogue ■ 6040 stereo amplifier ■ 8040 digital echo  
■ Also mini echo's.

### DIGITAL DELAY/REVERB

■ 19" rack systems ■ Digital reverb with 63 user programs ■ Digital delay up to infinite repeat ■ Also multi-effects programmable unit.

### GRAPHICS

■ 19" rack systems ■ 31 band single channel ■ 2 x 15 band two channel, and 2 x 31 band two channel.

### CHASSIS SPEAKERS/ CABINETS

■ PA speakers 5 1/4" to 12" ■ Twin cone from 40 to 100 Watts ■ Various models disco/group speakers 10" to 18" various types ■ Bass speakers ■ Bass mids and mids ■ Also Rexine cabinets 10", 12" & 15" ■ Plus range of cabinet fittings and portable speaker stands and brackets.

### PIEZO TWEETERS

■ 10 models stocked from £2.95 to £7.95 ■ Square piezo £4.95.

### PUBLIC ADDRESS SPEAKERS

■ For PA and background music system with and without 100 volt line  
■ **OUTDOOR.** Range of weatherproof systems at various power ratings  
■ **INDOOR.** Columns for speech, columns for music ceiling speakers, suspension speakers, corridor speakers, wall speakers, music speakers - various sizes and types.



### DECKS

3 models heavy duty top quality with plinth/cover.  
■ DLP1 belt drive quick start.  
■ DLP2 direct drive system.  
■ DLP3 quartz controlled quickstart direct drive.



### POWER AMPLIFIERS

■ Power boosters single channel: 100W, 175W and 2kW. 2-ch/stereo: 135 + 135W, 160 + 160 Watt and 1500 + 1500 Watt.

### AMPLIFIERS

■ With preamps ■ 240V AC models and 12V DC/240V AC or 24V DC/240V AC ■ From 15 Watts up to 175 Watts  
■ Also background music tape amplifiers and paging amplifiers.  
■ Plus range of mixer-amplifiers.  
■ Choose from 25 models.

### MOBILE AMPLIFIERS

■ Range of 12 volt amplifiers up to 100 Watts ■ Also portable megaphones stocked and 12 volt power boosters.

### MICROPHONES/ STANDS

■ XLR/Jack etc ■ Mics for disco, public address and Hi-Fi ■ Good quality at low cost ■ Also stands, booms etc. and wireless microphone system

### OUTDOOR HORNS

■ Various models up to 12" with or without 100 volt line with drivers  
■ Also range of horns with choice of drive units.  
■ Accessories: Leads ■ Plugs  
■ Adaptors ■ Transformers etc, for all PA requirements.

### HORN/ CROSSOVERS

■ 100 Watt midrange and tweeter horns ■ Also matching crossovers and filters up to 300 Watts.

CALL IN OR PHONE FOR BEST PRICES  
OPEN 6 DAYS A WEEK

## HENRY'S AUDIO ELECTRONICS

404 Edgware Road, London W2 1ED

Telephone: 01-724 3564

Fax: 01-724 0322

Sales Office: 01-258 1831

TRADE/EDUCATION/EXPORT SUPPLIED

PA - DISCO CATALOGUE WITH DISCOUNT VOUCHERS Ref PA1  
Send A4 SAE (£1.00 UK) or £2 UK full products catalogue

# AUTO MEMO

**OWEN BISHOP**



*Make sure your memo's are seen and inwardly digested with this neat attention getting note pad.*

**H**AVE YOU ever left a message for someone and they did not notice it? There is little chance of this happening with the Auto-Memo. This electronic memo pad insists on being noticed. Its l.e.d. flashes in a eye-catching way and its distinctive-sounding bleeper demands the attention of the ear. The only way to stop it is to pick it up and turn it face down (but read the message first!)

The circuit is housed in a small plastic case, one side of which has a panel of plastic laminate suitable for accepting messages in pencil or felt-tip pen. When finished with, messages are wiped off with a damp cloth. In one corner of the message panel is a large l.e.d. mounted in a chrome bezel. From within the case comes the sound made by an audible warning device.

The switch is a non-locking click-key on the underside of the case. The Auto-Memo rests on this key and its weight keeps the key depressed.

You write the message on the "pad" and put the Memo firmly down on the table. The switch clicks on and the Memo is in action. It remains active until it is picked up and turned over.

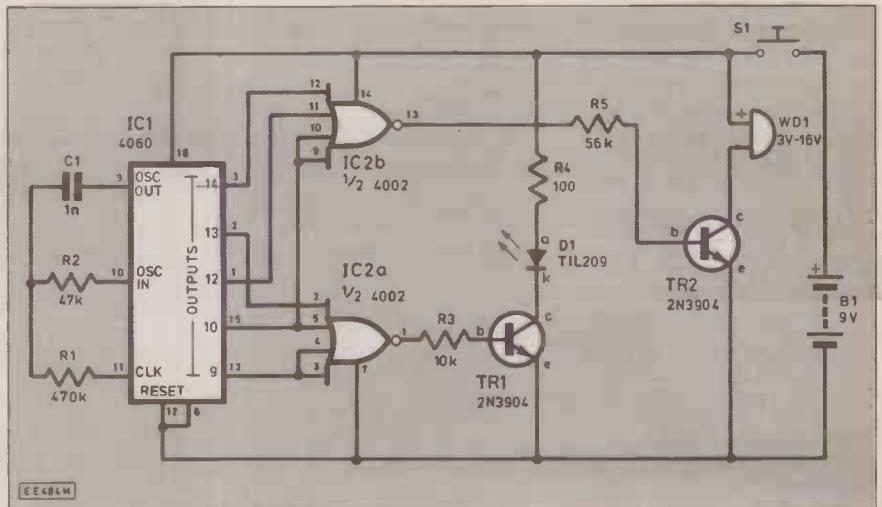


Fig. 1. Circuit diagram of the Auto Memo

The circuit is specially designed for low current consumption. The average current is only 7mA, so it operates for about 70 hours on a PP3 battery.

## HOW IT WORKS

The circuit for the Auto-Memo is based on a CMOS 14-stage counter i.e., the 4060 (Fig 1). This has its own in-built clock circuit, so all we need to supply are the timing capacitor C1 and resistors R1 and R2.

The clock runs at high frequency (8kHz), which is divided down by the counter to give a range of output frequencies. In this circuit we use five of these frequencies:

Output	Frequency (Hz)
9	16
10	8
12	2
13	1
14	0.5

Outputs 10, 12 and 14 are fed to a NOR gate IC2b. The gates

have four input terminals so one of the signals goes to two input terminals. These frequencies each differ by a factor of 4.

The output of the NOR gate IC2b goes high only when all four of its inputs are low. This output is used to turn on a transistor TR2 which operates the audible warning device WD1. This is a ready-made unit having its own internal oscillator running at 3.7kHz. It emits a piercing high-pitched tone when switched on.

The effect of the logic is to turn on the WD1 for two short bursts, followed half a second later by two more bursts. The sequence is repeated every two seconds. The result is an intermittent and attention-catching chirping sound, easily distinguished from the sounds of microwave cookers, alarm watches, warbling phones and other hi-tech products that assail the ears in the modern home.

The warning buzzer takes about 10mA when operating but, since the logic switches it on for only one eighth of the time, the average current is only 1.25mA. This saves battery power yet gives an effective alerting sound.

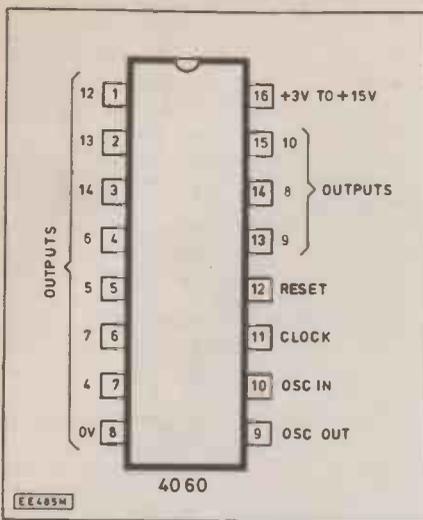


Fig. 2. Pin-out of the 4060

The flashing l.e.d. D1 is also controlled by feeding three counter outputs to NOR gate IC2a. This time we use outputs 9, 10 and 13. Since output 9 runs twice as fast as output 10, while output 13 runs *eight* times slower than output 10, the gate produces a rather different output signal from that used for operating the buzzer.

The l.e.d. is switched on and off eight times in rapid succession, taking one second for this. Then there is a pause of one second before the flashing is repeated. The series resistor R4 is only 100 ohms to give high-intensity illumination.

The l.e.d. takes around 30mA when on but, since the pattern of flashing results in


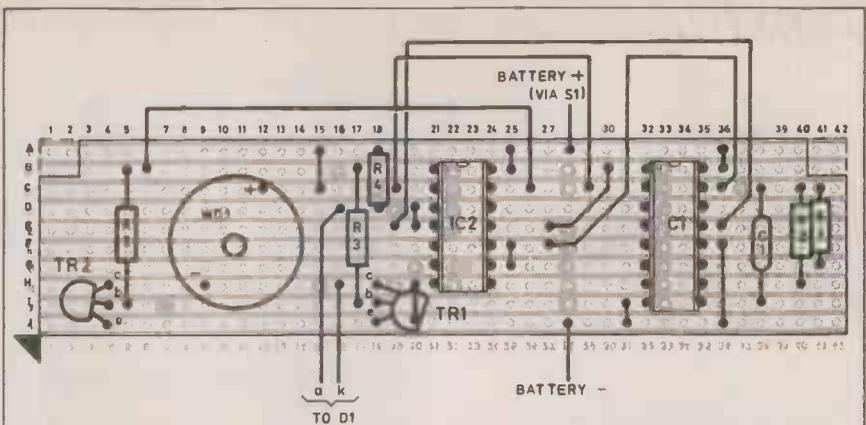
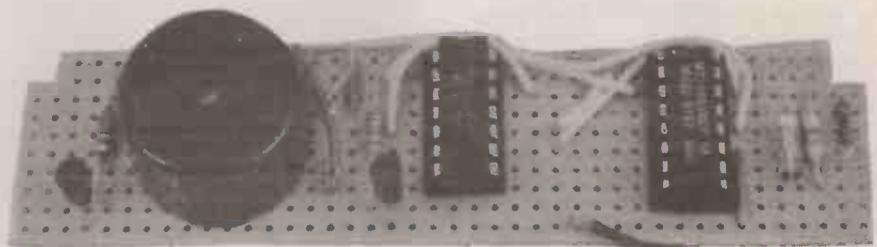


Fig. 3. Veroboard layout and wiring for the Auto Memo.

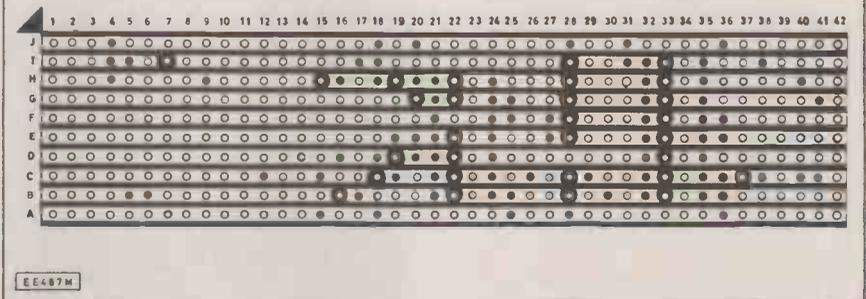

the l.e.d. being on for only an eighth of the time, average current consumption is only around 3.75 mA. this is an attention-getting but economical display.

puts. Fig.2 shows the pinout of the 4060. Note that stages 1 to 3 and stage 11 are not available.

### OPTIONS


There is plenty of scope for playing around with the logic of this device. By varying the connections, a wide range of different audible and visible signals may be produced.

The prototype NORs three outputs for each type of signal but you can NOR two, three or four outputs from IC1 if you wish. You can also make use of the other out-
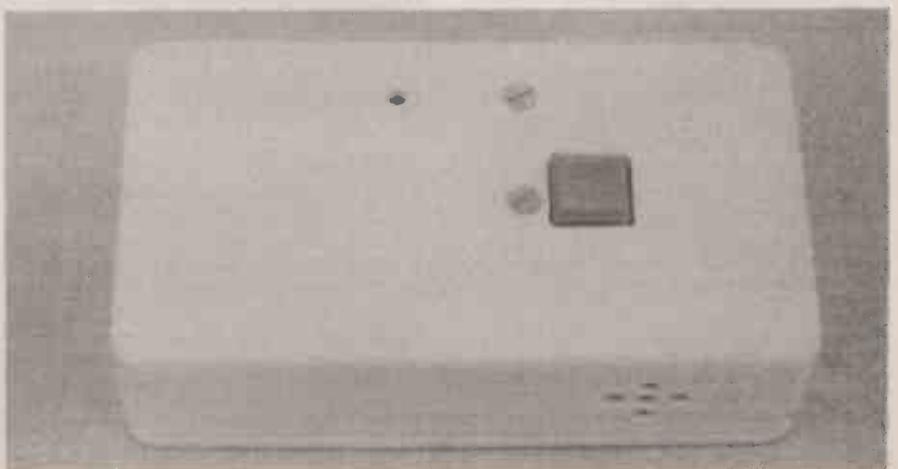
### CONSTRUCTION

The case used in the prototype has internal slots which hold the main circuit-board which is built on a piece of strip-board (42 holes x 10 strips) running the length of the case.

The component layout and details of cuts required in the underside copper strips is shown in Fig. 3. The rest of the components are packed tightly into the case, as can be seen in the photographs.



## COMPONENTS

### Resistors

R1	470k
R2	47k
R3	10k
R4	100
R5	56k

All 0.25W 5% carbon

**Shop  
Talk**

See  
page 319

### Capacitors

C1	1n, polystyrene
----	-----------------

### Semiconductors

D1	TIL209 l.e.d. (or similar), with chrome mounting bezel
TR1, TR2	2N3904 <i>npn</i> silicon
IC1	4060 CMOS 14-stage counter
IC2	4002 CMOS dual 4-input NOR gate

### Miscellaneous

WD1	3V-16V buzzer, p.c.b. mounting
S1	Click-effect push to make switch (or microswitch), p.c.b. mounting.

Stripboard, 0.1in matrix 10 strips x 42 holes and a small off-cut piece for mounting S1; 1mm solder pins (4 off); 14-pin i.c. socket; 16-pin i.c. socket; PP3 battery and connector; plastic case, 122mm x 63mm x 32mm; plastic laminate, 70mm x 55mm; contact adhesive; connecting wire; solder etc.

Approx cost.  
Guidance only

**£6**

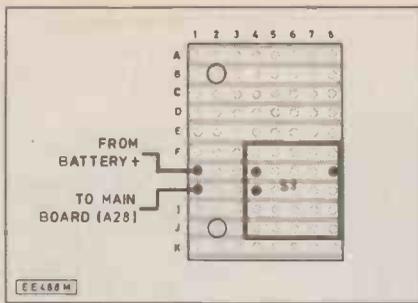


Fig. 4. Circuit board for S1.

If the case used is the same as that used in the prototype, it is necessary to cut the top corners of the board as shown in Fig 3, to allow the lid to drop into position. Note that one of the strips beneath IC2 (across pins 5 and 10) is *NOT* cut, but is used as a connection to simplify the wiring. The same applies to the connection between IC1 pin 3 and IC2 pin 12.

The circuit is powered by a 9V "transistor" battery (PP3). Off-board wiring runs to the battery connector with the click-key S1 in the positive lead. The battery fits comfortably in the space shown in the photographs and does not need any special retaining clip.

The audible warning device is a type that operates on any voltage between 3V and 16V d.c. It has two pins at its rear, suitable for soldering directly to the circuit board. The board is held in slots so that the buzzer comes close to the front of the case. Holes are cut in the case to allow the sound to escape.

The l.e.d. used in the prototype has a threaded chromium-plated bezel. This is mounted in a hole drilled in the top corner of the case. The photographs show where the l.e.d. is situated when the lid is in position.

The message panel is cut from a scrap of Formica or similar plastic laminate, preferably white or any other light colour.

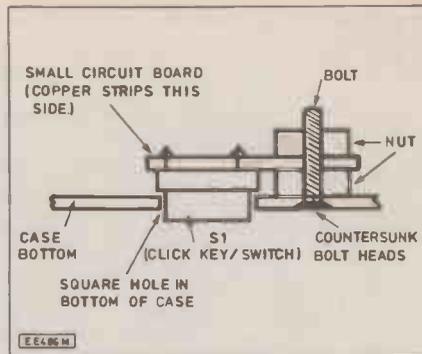


Fig. 5. S1 mounting details.

This is fixed to the lid of the case, using impact adhesive.

The key-switch S1 is mounted on the small circuit board, (Fig.4 and Fig. 5). The board has two holes drilled in it so that it may be supported by two bolts. A square aperture is cut in the bottom of the case, as well as two holes for the bolts.


The key-switch should protrude through the aperture so that the surface of the key-top is about 2mm below the bottom sur-

face of the case. Check that the key contacts close when the key-top is pressed flush with the bottom of the case. If necessary, additional nuts or washers can be threaded on to the bolts to bring the key to the correct position.

It is important to check that the weight of the case and its contents (including battery) is sufficient to hold the key-switch S1 depressed. If it is not, put some ballast in the case. A large metal nut (preferably wrapped in insulating tape) or similar compact but massive object should do what is required. A small plastic bag full of small nails can be shaped to fit between the hardware in the region just around the switch.

The positive lead from the battery clip goes to one terminal of S1. Wire a lead from the other terminal of S1 to the pin at A28 on the board. The negative lead from the battery clip goes to the pin at J28. Run twin leads from the pins at D16 and H16 to the l.e.d. taking care to observe the correct polarity.

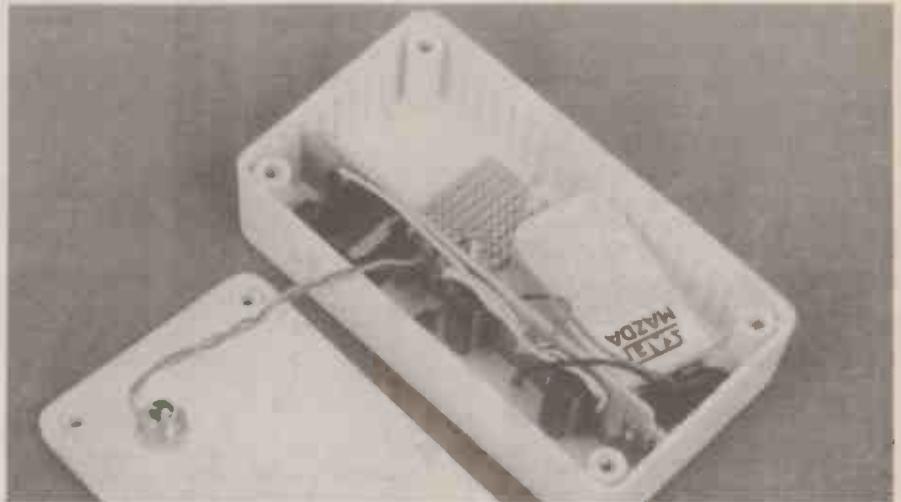When the lid has been bolted down, the Auto-Memory is ready for leaving messages for the family, your friends and — if you are as absent-minded as the author — for yourself! □



# DOWN TO EARTH

CONTINUED FROM PAGE 340

heat are needed to make electrons leave the filament (or cathode). Some research sponsored a few years ago by the US Navy suggests that both drawbacks might be avoided.

It proved possible to use the sort of fabrication methods used in i.c. manufacture to make arrays of tiny vacuum diodes. These diodes did not have heated cathodes. Instead, they made use of a process called field emission. This, in a nutshell, consists of subjecting a cathode not to heat but to a high voltage stress. If the stress is great enough electrons are pulled out of the unheated surfaces.

The effect is well known and is the basis of an instrument, the field emission microscope, used by physicists to enlarge surfaces to the point where single atoms are visible. What is needed for field emission is not high voltage as such but a high voltage-gradient be-

tween cathode and anode. You can get a high gradient by applying a relatively low voltage to anodes and cathodes spaced very close together. This is where the new fabrication techniques come in handy; electrodes can be made which are only a few microns apart.

## HEMTs

It's one thing to make field emission diodes and quite another to make triodes. We may never see "vacuum tube integrated circuits". New types of f.e.t. may render them unnecessary. These "high electron mobility" transistors (HEMTs) are based on the idea that solid matter is mostly empty space. An electron, released into the space between atoms, can move with perfect freedom - until it hits something.

In a perfect crystal, where the atoms

are arranged in nice straight lines, an electron ought to be able to travel long distances without hitting anything. Unfortunately, in order to make ordinary transistors work, the crystal has to be doped with impurities. These scatter the electrons, reducing their mobility. In the HEMT, the electrons do most of their travelling in an undoped region where collisions are minimal.

The HEMT exists, but it's hard to make. At present it's used as a discrete device in microwave amplifiers. It's just possible that somebody may hit upon a way of making vacuum micro-triodes more easily than HEMTs. In that case, the radio valve will make its comeback, though in a form undreamed of by Fleming and de Forest.

## Reference:

Scientific American March 1965

## ONE POUND PACKS



All packs are £1 each. Note the figure on the extreme left of the pack ref number and the next figure is the quantity of items in the pack, finally a short description.

- BD152 1 Gas or liquid shut off valve, clockwork dial, setting can be on for up to 12 hours.
- BD153 1 Same as BD152 but thermostatically operated.
- BD154 1 12v operated drip proof relay, ideal for outdoor or in-car operation
- BD158 4 12 way 5 amp screw down polythene bodied connector strips. Used to be called choc blocks when made of Bakelite.
- BD159 2 12 way 25 amp connector blocks.
- BD160 1pr Plug together 12 way connector bolts. Ideal for quick joints in leads.
- BD168 2 Component mounting tag strips each with 50 stand-up tags.
- BD169 4 Short wave air spaced trimmers 3-30pF. Screwdriver operated.
- BD170 4 Assorted neon type numeric tubes made by HIVAC.
- BD175 1 2 watt mains motor driving gearbox, final speed 200rpm
- BD177 5 12v Lilliput bulbs
- BD178 3 Panel mounting slim line indicator lights with amber lens. These take Lilliput bulbs.
- BD179 3 Oblong mains neon indicator lights, approx 1inx1/2in.
- BD181 100 PVC grommets for insulation through 1/4th hole
- BD182 1 25pF air spaced tuning capacitor, small hole fixing with 1/4in spindle.
- BD189 1 20 amp double pole switch on flush plate which fits standard 3x3 electrical box, illuminated when on.
- BD190 1 20 amp dp switch but surface mounting, oblong shape.
- BD191 6 Lamp holder adaptors which takes two pin plug, also supplied
- BD193 6 5 amp 3 pin flush sockets brown.
- BD197 2 Thermostats, spindle setting — adjustable range for ovens etc.
- BD199 1 Mains operated solenoid with plunger 1in travel.
- BD201 8 Computer keyboard switches with knobs, pcb or vero mounting.
- BD205 1 Very small 12v operated relay with one pair change-over contacts.
- BD211 1 Electric clock, mains driven, always right time — not cased.
- BD212 1 Mains transformer 230v primary and two 8v 1/2amp secondaries.
- BD213 2 5 core curly leads, tinsel wire for phones, etc.
- BD214 2 Sub-min toggle switches double pole double throw.
- BD215 4 Mini dpdt slides switches with chrome dolly instead of the usual plastic toggle.
- BD216 1 Stereo pre-amp Mullard EP9001.
- BD217 100 Standard wire ending push-ons for standard 1/4in tags.
- BD218 100 Ditto, but right angled.
- BD219 100 Soldercon tags. With these you can make your own sockets for ICs etc.
- BD224 1 Battery operated motor made for 9v cassette players but speed controllable by lowering voltage.
- BD227 4 50k quad pots. Standard 1/4in spindle single hole fixing.
- BD228 1 Ice stat thermostat. Ideal for controlling water pipe antifreeze coils.
- BD229 1 Instrument buzzer, variable low, medium or soft.
- BD233 2 Eagle educational kits. One makes chemical balance with weights and the other has electricals for experiments.
- BD237 1 Computer grade electrolytic 3150µF at 40v.
- BD243 2 6x4 16 ohm loudspeakers permanent magnet, 5 watts.
- BD245 4 Standard size pots. 1/2 meg with dp switch.
- BD248 1 A noise suppressor/mains filter.
- BD249 1 13A socket on plate with spur, fits normal electrical box.
- BD253 1 Open thermometer — bimetal type, reads 200-500 deg F.
- BD266 1 Mains transformer 9v 1/2A secondary split primary so ok also for 115V.
- BD267 1 Mains transformer 15v 1A secondary p.c.b. mounting.
- BD291 1 Ten turns 3 watt pot 1/4in spindle 100ohm.
- BD298 1 15 amp round pin plug.
- BD300 1 Mains solenoid with plunger compact type.
- BD303 1 12 pole 3 way ceramic wave charge switch.
- BD310 2 Oven thermostats.
- BD316 1 Round pin kettle plug with moulded on lead.
- BD453 2 2kΩ, 60ohm loudspeakers.
- BD454 2 2kΩ, 80ohm loudspeakers.
- BD465 3 5A round pin plugs will fit item BD193.
- BD466 4 7 segment l.e.d. displays.

**EPSON DISC DRIVE** Ref no SP540. 5 1/4in double sided, double density, supplied with data. Brand new. £55.00. Our ref 55P1.




Ex-Electricity Board. Guaranteed 12 months.

## VENNER TIME SWITCH

Mains operated with 20 amp switch. One on and one off per 24 hours, repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95 without case, metal case — £2.95, adaptor kit to convert this into a normal 24hr time switch but with the added advantage of up to 12 on/off's per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30

## SOUND TO LIGHT UNIT

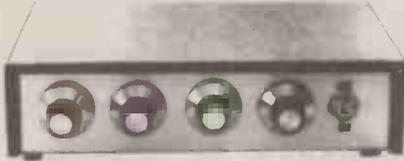

Complete kit of parts of a three channel sound to light unit controlling over 2,000 watts of lighting use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two tone metal case and has controls for each channel, and a master on/off. The audio input and outputs are by 1/4in sockets and three panel mounting fuse holders provide thyristor protection. A four pin plug and socket facilitate ease of connecting lamps. Special price is £16

## 12v MOTOR BY SMITHS

Made for use in cars, etc, these are very powerful and easily reversible. All 3in dia. They have a good length of spindle — 1/4hp £4.00 1/2hp £5.00 3/4hp £8.00



## 25A ELECTRICAL PROGRAMMER

Learn in your sleep. Have radio playing and kettle boiling as you wake — switch on lights to ward off intruders — have a warm house to come home to. You can do all these and more. By a famous maker with 25 amp on/off switch. A beautiful unit at £2.50



## PRINTER PLOTTER

prints on plain paper in four selectable colours, made by the famous Jap SHARP company for use with their PC MZ700/800, but with a simple interface details of which we expect to have shortly. This will in all probability work with your computer. We have to clear a store room so you can have this at only a fraction of its proper price, brand new with leads and makers instruction data, yours for only £16, but act quickly or you may miss the superb bargain order ref is 16P3

**15 WATT WOOFER** 8in circular with separate matching 3in tweeter. 8ohm coils. £3.00 a pair. Our ref 3P98.

**RE-CHARGEABLE NICADS 'D' SIZE 4 AMP** These are tagged for easy joining together but tags, being spot welded, are easy to remove. Virtually unused, tested and guaranteed £2.00 Our ref 2P141 or 6 wired together for £10.00 Our ref 10P47.

**RECORD PLAYER DECK.** 12 volt operated, belt driven with an 11in turntable, stereo cartridge. Will play 7in-10in or 12in individually at either 45rpm or 33rpm. Fitted speed selector and pick-up cueing lever. Price £12 plus £3 postage. Our ref 12P4.

**ATARI 65XE COMPUTER** We have a few of these left. New and perfect but less handbook and PSU. Real bargain at £39.00. Our ref 39P2.

**PAPST AXIAL FAN**—Manufacturers Ref No. TYP4580N. This is mains operated. 15 watt rating and in a metal frame with metal blades so OK in high temperatures. Body size approx 4 1/4in square x 1 1/4in thick. £6.00 each, plus £1.00 postage. Our ref 6P6.

**VERY POWERFUL MAGNETS.** Although only less than 1in long and not much thicker than a pencil, these are very difficult to pull apart. Could be used to operate embedded reed switches etc. Price 80p each. 2 for £1.00. Our ref 80P42.



**ORGAN MASTER** is a three octave musical keyboard. It is beautifully made, has gold plated contacts and is complete with ribbon cable and edge connector. Brand new, only £15 plus £3 postage. Our ref 15P16.

**ULTRASONIC TRANSMITTER-RECEIVER** Small, nicely cased, will detect movement in a room up to 10mx10m. Ingenious construction makes it independent of the mains; cannot be switched off, even with its on/off switch, until you know the secret, has delayed action enabling you to switch it on and leave the room; it has an inbuilt piezo sander which is very penetrating and high pitched and would frighten away most intruders. Has internal switching and could be coupled to an outdoor alarm if required.

It is the basis of a very efficient burglar alarm, or has other uses. For instance: you could disconnect the internal sander and using the internal switches you would know when somebody arrives without that person being aware that you know. Similarly, the unit could be used to operate other equipment ultrasonically. It is brand new, guaranteed OK, complete but less battery (PP3 alkaline type). Price is £18. Our ref 18P3

**110 DECIBEL HORN** For use with the ultrasonic intruder detector. Ideal for external positioning to attract the attention of neighbours should you have an intruder. This unit has its own mounting bracket and comes complete with good length of lead. Price £4. Our ref 4P60. Incidentally, this could also be used as a loudspeaker.

## DON'T MISS THESE



**20V-0-20V** Mains transformers 2 1/2 amp (100 watt) loading, tapped primary. 200-245 upright mounting £4, Our ref 4P24.

**HIGH-VOLT CAPS.** Not ceramic, but the much more reliable foil type. Good range from 1nf to 35µ at voltages 1kv to 2.5v. Keen prices, good quality discounts. Request list.

**BATTERY OPERATED TRAVEL MECHANISM** On a plastic panel measuring approx 9in x 3 1/2in is driven by a reversible 12v battery motor, fitted with pulley and belt which rotates a threaded rod and causes a platform to travel backwards and forwards through a distance of approx 5in. Price £5. Our ref 5P140

**MAINS OPERATED WATER VALVE** with hose connection for inlet and outlet suitable for low pressure. Auto plant watering, etc. Only £1 each. Our ref 8D370.

**20 VOLT 4AMP MAINS TRANSFORMER** Upright mounting with fixing feet. price £3. Our ref 3P59.

**12 VOLT SOLENOID.** Has good 1/2in pull or could be made to push if fitted with a rod. Approx. 1 1/2in long by 1in square. Price £1. Our ref 8D232A.

**16OHM PM SPEAKERS.** Approx 6in x 4in. 5 watts. Offered at a very low price so you can use two in parallel to give you 10 watts at 8 ohms. £1 for the two. Our ref 8D684.

**EHT TRANSFORMER** 4kv 2mA Ex-unused equipment. £5. Our ref 5P139.

**VERY USEFUL MAGNETS.** Flat, about 1in long, 1/2in wide and 1/4in thick, very powerful. 6 for £1. Our ref 8D274A.

**CLEAR LAQUER.** Quick drying for the protection of transfers, markings, maps, etc. Also protects wood and metal. Exceptionally clear. Large can for £1. Our ref 8D660.

**CASE WITH 13A PRONGS.** To go into 13A socket, nice size and suitable for plenty of projects such as battery trickle charger, speed controller, time switch, night light, noise suppressor, dimmers etc. Price 2 for £1. Our ref 8D565.

**ALPHA-NUMERIC KEYBOARD.** This keyboard has 73 keys giving trouble free life and no contact bounce. The keys are arranged in two groups, the main area is a QWERTY array and on the right is a 15 key number pad, board size is approx. 13in x 4in. Brand new but offered at only a fraction of its cost, namely £3, plus £1 post. Our ref 3P27.

**4-CORE FLEX CABLE.** Cores separately insulated and grey PVC covered overall. Each copper core size 7/0.2mm. Ideal for long telephone runs or similar applications even at mains voltage. 20 metres £2. Our ref 2P196 or 100 metres coil £8. Our ref 8P19.

**METAL PROJECT BOX.** Ideal for battery charger, power supply etc. sprayed grey, size 8in x 4 1/2in x 4in high, ends are louvred for ventilation other sides are flat and undrilled. price £3. Our ref 3P75.

**CAPACITOR BARGAIN.** Axial ended — 4700µF at 25V. Jap made. Normally 50p each, but you will get 4 for £1. Our ref 613

**SINGLE SCREENED FLEX.** 7.02 copper conductors, pvc insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m for £1. Our ref 8D668.

**3 CORE FLEX BARGAIN No. 1.** Core size 5mm so ideal for long extension leads carrying up to 5 amps or short leads up to 10 amps. 15m £2. Our ref 2P189.

**3 CORE FLEX BARGAIN No. 2.** Core size 1.25mm so ideal for long extension leads carrying up to 13 amps or short leads up to 25 amps. 10m £2. Our ref 2P190.

**DISPLAY 16 CHARACTER 2 LINE** As used in telephone answering and similar machines. Screen size 85mm x 36mm x 9.3mm. Alpha-numeric, dot matrix module with integral CMOS micro processor, LCD display. Made by the EPTSON Company, reference 16027AR. Price £10 Our ref 10P50.

**SUPER 8mm CINE PROJECTOR.** 600ft film capacity, reel to reel loading and governor controlled projection speeds of 18 and 24 f/s. Sound output 3.5 watts, complete with zoom lens, recording microphone and handbook. Price £39.50. Our ref 39P2.

**THERE IS GOING TO BE A BURIAL!** For several years now we have been offering mains operated clocks at only £1 each. These are cooker clocks which in addition to telling you the time would also switch things on and off at pre-set times. However, despite this silly price these have been very slow sellers and as we have still almost 10,000 of them in a store which we have to clear we are making one even sillier final offer before burying them. You can have 16 brand new clocks still in original packing for only, £5. Our ref 5P151. Add £3 post if not collecting.

**CAMERAS.** Three cameras, all by famous makers, Kodak, etc. One disc and two different instant cameras. All in first class condition, believed to be in perfect working order but sold as untested. You can have three for £10, which must be a bargain if only for the lenses, flash gear, etc. Our ref 10P50.

**FLIP-OVER DIGITAL CLOCK.** Quite an eye-catcher, this is mains operated. The figures flip-over per minute and per hour and give a larger than usual visual display. Supplied complete with front and perspex panels to glue together to make its case. £2.00 each. £2.20P5.

**BT HANDSET.** With curly lead terminating with flat BT plug. Colour cream. Price £5. Our ref 5P123.

**SINGLE SCREENED FLEX.** 7.02 copper conductors, pvc insulated then with copper screen, finally outer insulation. In fact quite normal screened flex. 10m for £1. Our ref 8D668. Ditto, but solid conductor. 10m for £1. Our ref 8D668a.

**WHITE CEILING SWITCH.** 5 amp 2 way surface mounting with cord and tassel. Made by the famous Crabtree Company. Price £1 each. Our ref 8D528. Ditto but brown. 2 for £1. Our ref 528B

**EHT TRANSFORMERS.** Normal primary, secondary 3kv at 3mA continuous or 20mA intermittent. Ideal as a spark generator for boiler lighting, etc., or with a simple voltage doubler circuit would make a good ioniser. Price £7. Our ref 7P7. 8kv secondary 3mA. Price £10. Our ref 10P56.

**MAINS TRANSFORMER.** Upright mounting. Normal mains input, gives 28V at 3.5A so should be ideal for big amplifier, variable P.S.U., etc. Price only £4. Our ref 4P24, please add £1 postage.

**TRANSFORMER IN WATERPROOF METAL CASE.** 24V 5A output. Ideal for garden lighting or to operate pond pump etc. Case has cable glands for mains in and low voltage output leads. Price £8. Our ref 8P17.

**MAINS RELAY.** With transparent plastic cover. Could be p.c.b. or dip mounted, has single 8-10A c/o contact. Real bargain 2 for £1. Our ref 8D486.

**PANEL METERS.** Engraved Vu approximately 1 1/4" square. Luminare these from behind and you will have a really super looking panel. Real bargain 2 for £1. Our ref 8D366.

**TRANSMITTER TUNING CONDENSATOR.** 160pF made for a very famous RAF transmitter, only £1 each. Unused but mounting brackets will need a bit of cleaning up due to storage. Our ref 8D424.

# J & N BULL ELECTRICAL

Dept. EE, 250 PORTLAND ROAD, HOVE  
EAST SUSSEX BN3 5QT

MAIL ORDER TERMS: Cash, PO or cheque with order. All orders add £2.50 service charge. monthly account orders accepted from schools and public companies. Access and Visa orders accepted — minimum £5.00.  
Phone (0273) 734648 or 203500. Fax No. (0273) 23077

# ACTUALLY DOING IT!

by Robert Penfold

I HAVE often advised beginners to electronics construction to steer well clear of mains powered projects, and make no apologies for giving the same advice again here. Projects powered from a humble PP3 battery enable you to make mistakes and learn from them, with little risk to the components in the project, and none to yourself.

With a mains powered project a mistake could easily result in some expensive components (literally) going up in smoke, and any carelessness on the part of the constructor would be potentially fatal. Leave mains powered projects until you have gained enough experience to tackle them confidently.

## PRIMARY CONSIDERATIONS

Sooner or later, and preferably later, you will no doubt wish to build a mains powered project of some description. This will probably not present too many difficulties, since the wiring around the mains transformer and on/off switch is likely to be pretty basic stuff. However, there are a few possible problems, and these mainly revolve around correctly identifying and connecting the transformer's windings. Many manufacturers seem to employ some unusual arrangements in what is presumably an attempt to make their transformers as versatile as possible.

The primary winding is unlikely to give too much difficulty, as in many cases there will simply be two tags. These will probably be marked something like "0V" and "240V", or they may simply be marked with a common "240V" marking. Either way, the mains input is applied to these two tags, and it does not matter which way round they are connected.

It is not uncommon for mains transformers to have tapped primary windings, so that they can be used with several mains voltages. The standard U.K. mains supply potential is 240 volts, and the mains input should therefore be con-

nected across the tags marked "0V" and "240V". Ignore any other tags associated with the primary winding.

The convention is to have the "N" mains lead connected to the "0V" tag, and the "L" lead connected to the "240V" tag. The opposite method of connection is perfectly satisfactory though, and the transformer will provide isolation between the primary and secondary windings with either method of connection.

Some mains transformers have twin primary windings. These are usually in the form of two 120 volt mains supplies using the two windings connected in parallel, or a 240 volt supply if they are series connected.

Obviously series connection is required for use on the 240 volt U.K. mains supply, and Fig. 1(a) shows the correct method of connection. Note that in this case the phasing of the two windings is important, and that they must be connected as in Fig. 1(a), and not as in Fig. 1(b) or Fig. 1(c). Getting the phasing of the windings incorrect will probably not cause any damage, but one winding will cancel out the other to give zero output from the secondary winding(s).

I have encountered one or two mains transformers which have twin 240 volt secondary windings. These must be connected in parallel, as shown in Fig. 2 (the same basic method of connection is used if twin 120 volt secondary windings are to be used with a 120 volt mains supply)

I am not sure why a transformer should have twin 240 volt primary windings since, as far as I am aware, there are no 480 volt mains supplies for operation with series connection. I can only assume that for some reason it is cheaper and easier to manufacture them this way. Fortunately, these rather awkward components seem to be something of a rarity.

## SECONDARY CONSIDERATIONS

The secondary winding or windings of

mains transformers are potentially more confusing, as there are often centre tapplings, multiple tapplings, and multiple windings to contend with. With the most basic of transformers there is a single secondary winding marked "0V" and "9V" in the case of a 9 volt component for example. With a transformer of this type it does not normally matter which way round the secondary winding is connected.

Mains transformers having a single untapped winding are something of a rarity. Some have multiple tapplings and can provide numerous output voltages. A typical transformer of this type would have outputs at 0V, 10V, 12V, 15V and 17V. Normally such a transformer would be used by taking the output from across the 0V tag and the one corresponding to the required output voltage (the "0V" and "15V" tags for an output of 15 volts for example).



The output voltage is equal to the difference between the voltage figures for the two tags used, and it is quite possible to obtain (say) 5 volts by using the 15 volt and 10 volt tags ( $15V - 10V = 5V$ ). However, using a multi-tapped transformer to provide an output voltage that is well below its full secondary rating is very inefficient. You would be using a component that was physically much larger than really necessary, as well as being relatively expensive.

## CENTRE TAPPED

Many power supply circuits utilize push-pull rectification (the type which has two rectifiers), and these need a centre tapped transformer. The central ("0V") tapping connects to earth, while the other two tags connect to their respective rectifiers. Note that some power supply circuits use bridge rectification (the four rectifier type) with the centre tap on the secondary winding then being ignored. The output potential of the transformer is then double the normal voltage rating (e.g. a 9V-0V-9V type effectively becomes an 18 volt untapped type).

Mains transformers having centre tapped secondary windings seem to be getting rather scarce in the component catalogues, apart from the ever popular 6, 9, and 12 volt miniature types. Instead, many suppliers now seem to offer mains transformers having twin secondary windings. These can be used as centre-tapped types using the method of connection shown in Fig. 3(a). In this example the transformer is a 9 volt type, but obviously the same basic method of connection can be used for components having different voltage ratings.

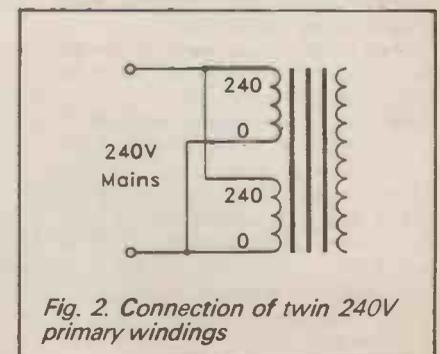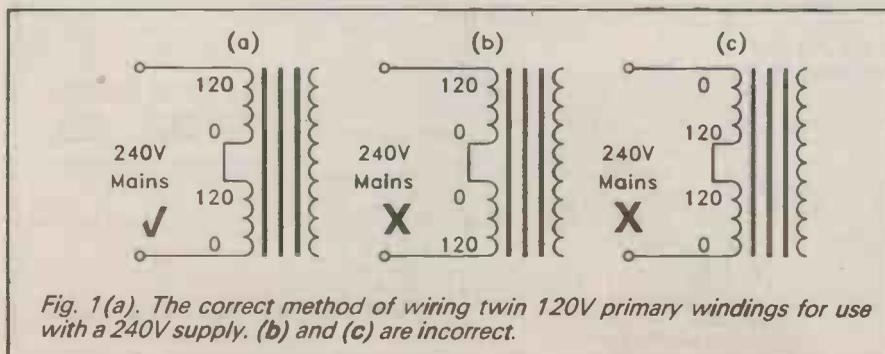Some constructors run into difficulty when using a twin secondary component





# ...REPORTING AMATEUR RADIO...

TONY SMITH G4FAI

## MORSE DECODERS AND KEYBOARDS

I was interested to read Mike Tooley's comments on Morse decoders in *On Spec* in the February issue. For those who don't know Morse, these enable the text of coded signals to be read as plain language on a computer screen. Add a Morse keyboard, which enables typed letters and figures to be transmitted as good quality code, and you have a modern Morse teleprinter.

However, the use of such aids to Morse operation in amateur radio is the subject of controversy among Morse enthusiasts. Purists say that true enjoyment of Morse operation can only be achieved by using a personal knowledge of the code to send and receive it. They also fear an erosion of traditional skills.

Nevertheless, many high speed operators do use keyboards, sending Morse much faster than is possible with other instruments, at the same time reading the Morse coming back at them by ear. Dr Gary Bold ZL1AN, in *The Morseman* column in *BREAK-IN*, journal of New Zealand's national radio society, May 1988, described the evolution of the Morse keyboard, "... Two types of Hams were mainly responsible. One group were just experimenters, obsessed (as all good Hams should be) in pushing back the frontiers, seeing the production of a Morse keyboard as a challenge to be overcome.

## HIGH SPEED OPERATORS

"The other group had found that their code reading ability had so far outstripped their sending skill that slow, frustration-filled, 35 words per minute QSOs grew increasingly unsatisfying. I became friendly with a group of such operators in 1977. They were predominantly non-technical and had bought commercial keyboards simply to have more enjoyable chats with each other. Their standard conversational speed (reading, of course, in their heads) was about 65 w.p.m., but on good nights some would go up to 80.

"At first their Morse sounded like the high speed twittering of conversing robots, but after repeated listening I copied some call signs. When I called them individually they readily changed down to 35 w.p.m. to talk to me. Although I felt rather as if I was conversing with creatures from some higher existence they did not think they were doing anything particularly clever.

"One... told me that after he had bought his keyboard his receiving speed had gone from 35 w.p.m. to 65 w.p.m. in three months... these people were from that small, exceptionally 'Morse-talented', group who find code reading comes easily and have difficulty understanding why others can't do it..."

## LITTLE ENJOYMENT

It can be seen from the above that while some Morse enthusiasts may use keyboards for sending they are not likely to use decoders for receiving. For someone who knows and likes using Morse there can be little enjoyment in having the code deciphered by a "machine" which, in any case, is not too efficient for radio work.

For satisfactory decoding, the incoming Morse has to be perfectly formed and received as a strong, interference free signal. Keyboards send the quality of Morse required, but few operators of manual or electronic keys do, and conditions on the radio bands are typified by QSB (fading) and QRM (interference).

So what good are decoders? They are of interest to computer buffs who like experimenting with new ways of using their computers. They may interest short-wave listeners who want to decipher the unintelligible code signals they can hear across the bands from a variety of sources. They may even encourage an interest in acquiring the skill to read Morse "in the head".

For learning to send Morse properly the decoder offers a valuable facility for self-tuition. Unlike the trained human ear, which can often decipher a wrongly sent letter correctly, the computer displays exactly what has been transmitted.

Properly sent, for example, the letter H is four dots with identical spaces between each dot. If an operator using a conventional hand key hesitates slightly after the first dot the decoder picks up one dot followed by a group of three dots, and displays the letters E and S instead of the intended letter H.

The learner is thus able to practice sending to a decoder checking constantly on the accuracy of individual letters or numbers, and concentrating on those which cause problems until they can be sent and received perfectly.

## CHANGING CIRCUMSTANCES

At present discussion about Morse learning is of great interest to most UK amateurs because it is necessary to pass a Morse code test in order to obtain a class A licence to operate on the amateur bands up to 30MHz - although there is no Morse test to qualify for a class B (v.h.f. only) licence.

The test arises from a requirement of the International Radio Regulations that operators on frequencies below 30MHz should have a knowledge of Morse. They need to understand instructions to close down or move frequency if they interfere with official or emergency transmissions, a requirement going back to the early days of radio when virtually all transmissions were in Morse.

Circumstances have changed over the years and from 1992 ships at sea will begin to phase in new emergency/safety

arrangements using satellites and other systems without a Morse code requirement. Because of this, pressure is building up within the amateur radio movement for the Morse test to be abolished.

This can be seen in the USA which at present requires all types of licensee to pass a Morse test. According to the W5YI REPORT, the Federal Communications Commission, having received twelve petitions including one from the national society (ARRL), announced proposals in February to create a new amateur licence class, for frequencies of 222MHz and higher, which will not require a Morse test. This will be a beginner's licence and will replace the existing Novice and Technician licences. It is likely to be introduced at the end of 1990.

## ISRAEL PROPOSES ALTERNATIVE TEST

One comment made on the need to abolish the Morse test is that young computer enthusiasts, who are seen by many national societies to represent the future for amateur radio, are not willing to learn Morse to get an amateur licence.

On these lines, Israel's national radio society (Israel Amateur Radio Club) has made a formal proposal to be considered at the International Amateur Radio Union Region 1 Conference in Spain on 1-6 April. This suggests that in view of the new maritime radio arrangements the Morse test for amateurs should be replaced "by some form of operating proficiency test more suitable to the present day data operating modes of amateur radio." It goes on to suggest that the ITU be asked to revise the International Radio Regulations to give effect to this.

The proposal says "It is felt that introduction of the measures proposed... will prove attractive to the 'Computer Generation'...". Whether the prospect of having to take a test in computer operating proficiency will appeal to non-computer enthusiasts thinking of taking up amateur radio is not discussed!

What existing radio amateurs think of the proposal is not known as for some reason it has not been publicised by the Radio Society of Great Britain in advance of sending its delegates to the conference. It will be interesting to see how the conference deals with this suggestion. The idea of abolishing the Morse test will undoubtedly be popular, but there are bound to be reservations about adopting an alternative as most societies are committed to the idea of making entry to amateur radio much easier than it is at present.

**Build your own  
SHORT WAVE RECEIVER  
... see the supplement**

# SURVEILLANCE PROFESSIONAL QUALITY KITS

A range of high quality kits as supplied to leading UK security companies, all in-house designed and produced, not to be confused with cheap imports. All kits come fully documented with concise assembly and setting-up details, fibreglass PCB and all components. All transmitters are fully tuneable and can be monitored on a normal VHF radio or tuned higher for greater security. Build up service available if required.

MTX. Micro-miniature audio transmitter. 17mm x 17mm. 9V operation. 1000m range	£12.95
VT500. Hi-power audio transmitter. 250mW output. 20mm x 40mm 9-12V operation. 2-3000m range	£15.95
VOX75. Voice activated transmitter. Variable sensitivity. 30mm x 40mm. 9V operation. 1000m range	£18.95
CTX900. Sub-carrier scrambled audio transmitter. Cannot be monitored without decoder fitted to radio. 30mm x 40mm. 9V operation. 1000m range	£21.95
DSX900. Sub-carrier decoder unit for monitoring CTX900. Connects to radio earphone socket. Provides output for headphones. 35mm x 50mm. 9-12V operation	£21.95
HVX400. Mains powered audio transmitter. Connects directly to 240V AC supply. 30mm x 35mm. 500m range	£18.95
XT89. Crystal controlled audio transmitter. High performance. 100mW output. Supplied with xtal for 108MHz. Others available to 116MHz. 85mm x 28mm. 9V operation. 2-3000m range	£36.95
TKX900. Tracker/Beeper transmitter. Transmits continuous stream of audio pulses. Variable tone and rate. Powerful 200mW output. 63mm x 25mm. 9V operation. 2-3000m range	£21.95
ATR2. Micro size telephone recording interface. Connects between telephone line (anywhere) and cassette recorder. Tape switches automatically with use of phone. All conversations recorded. Powered from line 10mm x 35mm	£12.95
TLX700. Micro miniature telephone transmitter. Connects to line (anywhere) switches on and off with phone use. All conversations transmitted. 20mm x 20mm. Powered from line 1000m range	£12.95
XML900. RF bug detector. Variable sensitivity. Triggers LED and beeper when in presence of RF field. Detects MTX 15-20 feet. 55mm x 55mm. 9V operation	£26.95
XL7000. Professional bug detector locator. Variable sensitivity. Twin mode ten segment LED readout of signal strength with variable rate beeper. Second mode AUDIO CONFIRM distinguishes between localised bug transmission and normal legitimate signal such as pagers, cellular etc. 70mm x 100mm. 9V operation	£54.95

UK customers please send cheques, PO's or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft or Eurocheque and add £5.00 per order for shipment. Credit card orders accepted on 0827 714476. Trade enquiries welcome.

Send 28p stamp for New 1990 Full Catalogue



The Workshops, 95 Main Rd  
Baxterley, Nr. Atherstone  
Warks CV9 2LE



0827 714476

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60 OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£26.50	£3.75 (£34.79 inc VAT)
1KVA 5 amp max	£34.00	£4.25 (£43.99 inc VAT)
2KVA 10 amp max	£49.00	£5.50 (£62.68 inc VAT)
3KVA 15 amp max	£65.00	£6.25 (£81.94 inc VAT)
5KVA 25 amp max	£115.00	Carriage on request

## VOLTAGE CHANGING TRANSFORMER

1250 Watt auto. Tepped 0-90V, 100, 110, 115, 120, twice to obtain voltages between 90 and 240V. Fitted in heavy duty louvered metal case. Fused input. Price incl VAT & p&p £39.50

COMPREHENSIVE RANGE OF TRANSFORMERS-LT. ISOLATION & AUTO (110-240V Auto transformer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

## ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 40 watt £10.44 (£12.00 inc VAT) Caller only
2ft 20 watt £7.44 + £1.25 p&p (£9.99 inc VAT)
13in 10 watt £5.80 + 75p p&p (£7.53 inc VAT)
12in 8 watt £4.80 + 75p p&p (£6.38 inc VAT)
9in 6 watt £3.96 + 50p p&p (£5.12 inc VAT)
6in 4 watt £3.96 + 50p p&p (£5.12 inc VAT)
230V AC BALLAST KIT for either 6in, 9in or 12in tubes £5.50 + 55p p&p (£6.96 inc VAT)
For 13in tubes £6.00 + 75p p&p (£7.75 inc VAT)

## 400 WATT UV LAMP

Only £34.00 + £2.50 p&p (£41.98 inc VAT)  
175 WATT SELF BALLASTED BLACK LIGHT MERCURY BULBS Available with BC or ES fitting. Price incl VAT & p&p £19.84.



## 12 VOLT BILGE PUMPS

Buy direct from the Importers  
500 GPH 15ft head 3 amp £16.00 inc.  
1750 GPH 15ft head 9 amp £20.18 + £2.00 p&p (£25.50 inc VAT)



## EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angstrom Tube Ballast unit pair of bi-pin leads neon indicator on/off switch safety microswitch and circuit £14.00 + £2.00 p&p (£18.40 inc VAT)

## SUPER HY-LIGHT STROBE KIT

Designed for Disco, Theatrical users etc.  
Approx 16 joules. Adjustable speed £48.00 + £2.00 p&p (£57.50 inc. VAT)  
Case and reflector £22.00 + £2.00 p&p (£27.60 inc VAT)  
SAE for further details including Hy-Light and Industrial Strobe Kits.



## SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

081-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

Showroom open Monday/Friday

## Hobby Kit Electronics

### JUST A SMALL SELECTION OF KITS FROM OUR EVER INCREASING RANGE

Kit No.	Description	Price (each) £ (incl. VAT)
1001	0.2 WATT FM TRANSMITTER	4.16
1004	LIGHT SWITCH	5.83
1006	800 WATT MUSIC TO LIGHT	4.99
1009	1 WATT FM TRANSMITTER	5.42
1013	AM-FM-VHF RECEIVER	13.33
1018	GUITAR TREMOLO	7.08
1020	0-5 MINUTE TIMER	5.42
1022	METAL DETECTOR	4.16
1026	RUNNING LIGHTS	8.33
1027	NI CAD BATTERY CHARGER	7.08
1029	4 SOUNDS ELECTRIC SIREN	4.99
1034	CAR BATTERY CHECKER	2.92
1036	TRANSISTOR TESTER	3.75
1038	AM-FM AERIAL AMPLIFIER	2.92
1044	GRAPHIC EQUALIZER	12.91
1045	SOUND EFFECT GENERATOR	6.66
1047	SOUND SWITCH	9.58
1055	RM RECEIVER USING TDA 7000	12.49
1059	TELEPHONE AMPLIFIER	8.33
1065	INVERTER 12V DC TO 220V AC	20.82
1069	12V DC FLUORESCENT TUBE UNIT	5.42
1073	VOICE ACTIVATED SWITCH	6.24
1075	ELECTRONIC DICE WITH LED'S	6.66
1091	GUITAR PRE-AMPLIFIER	7.50
1098	DIGITAL THERMOMETER WITH LCD DISPLAY	20.82
1114	ELECTRONIC LOCK	7.50
1117	TV PATTERN GENERATOR	9.17
1119	TELEPHONE LINE RECORDING	4.16
1122	TELEPHONE CALL RELAY	6.66
1124	ELECTRONIC BELL	4.99
1125	TELEPHONE LOCK	6.66
1129	NEGATIVE ION GENERATOR	14.16
1131	ROBOT VOICE	6.66
1133	STEREO SOUND TO LIGHT	9.52
1203	MINI FM TRANSMITTER WITH MICROPHONE	4.16

All kits are supplied complete including Silk Screened pcb, Components, Solder, Wire and full instruction sheet. Purpose built boxes with silk-screened front panels are available for some of the above. Please consult our catalogue.

★ ★ ★ ★ ★ ★ ★ ★  
LARGE STOCKS OF INTEGRATED CIRCUITS, SEMI'S, OTPO ELECTRONICS, CAPACITORS, RESISTORS, SWITCHES AND OTHER MISCELLANEOUS PRODUCTS ARE ALSO AVAILABLE FROM - **Hobbykit**

★ ★ ★ ★ ★ ★ ★ ★  
For latest kit catalogue and price list send a large 45p S.A.E. to:

# Hobbykit Ltd.



CREDIT CARD HOTLINE  
01-205 7485



UNIT 19, CAPITOL INDUSTRIAL PARK  
CAPITOL WAY,  
LONDON NW9 0EQ  
FAX NO: 01-205 0603

# eb...Beeb...Beeb...Beeb...Beeb...Beeb

... Morse ... Computer Communications ... Radio Teletype ...

IN LAST month's *Beeb Micro* article we looked at the ways in which CW and RTTY signals can be interfaced to a computer such as a BBC model B. This month we will continue on this theme, and a couple of practical interface circuits will be described.

These are reasonably simple and straightforward to build, but it is only fair to point out that in order to set them up ready for use you should ideally have access to suitable test gear. An audio signal generator and an oscilloscope or a.c. millivoltmeter are particularly useful. The alternative is an inordinate amount of trial and error.

## PLL Decoder

As explained last month, a simple but effective tone decoder can be built around a phase locked loop integrated circuit such as the NE567N. A simple decoder circuit of this type appears in Fig.1. TR1 and TR2 act as an input buffer stage and a simple bandpass filter. Although a phase locked loop decoder has good immunity to noise, better results are possible if some filtering is used to reduce the noise content on the input signal.

Some short wave receivers have a built-in CW filter with a bandwidth of a few hundred hertz. With a receiver of this type there is little point in using the input stages of this circuit. Instead, the signal could be coupled straight into IC1 via d.c. blocking capacitor C5 (but note that the polarity of C5 should be reversed if you adopt this method). Also, the centre frequency of the phase locked loop would have to be set up to match the centre frequency of the receiver's CW filter.

The input stages consist of a common emitter amplifier based on TR1, feeding into an emitter follower buffer stage which utilizes TR2. TR1 has a substantial amount of negative feedback introduced by R2, plus built-in bandpass filtering due to the use of a parallel tuned circuit (L1/C4) as its collector load. The latter provide a centre frequency of a little over 1kHz. Transistor TR2 prevents loading of the tuned circuit damping it to the point where a useful level of filtering is no longer provided.

Note that L1 must be a type that will operate efficiently at audio frequencies, and should not be an r.f. choke (these are not normally available in such a high value anyway). On the other hand, it does not need to be an expensive type based on a very high quality potcore. I used a Cirkut type 10RB, which seems to work well in this application.

IC1 is the NE567N phase-locked-loop tone decoder. This has C8, R6 and VR1 as the timing circuit for its v.c.o., and VR1 is adjusted to provide a centre frequency that matches that of the input filter. C6 and C7 are the filter capacitors in the smoothing circuit and lowpass filter. The open-

collector output is at pin 8 of IC1, and R5 acts as the collector load for this. D1 is an optional l.e.d. indicator which has R4 to provide current limiting. In practice this l.e.d. is virtually essential, as without it the task of tuning signals so that the decoder locks onto them is difficult. With the indicator included, it is obvious when lock is achieved, as the l.e.d. will flash on and off in sympathy with the CW signal.

Power is provided by a 9 volt battery. The standby current consumption is about 10 milliamps, but it is very much higher than this when lock is achieved. A fairly high capacity battery should therefore be used, such as a PP9 size or six HP7 size cells in a plastic holder.

Although it is very simple, this circuit will work quite well as a CW tone decoder. It is certainly a good one to try if you wish

nuisance, and it could be overcome by including D1 and R4, but connecting the anode of D1 to the +5 volt supply of the computer rather than the +9 volt supply of the tone decoder. However, a more practical solution might be to have software provide an on-screen indication of the output level from the decoder.

## Two Tone Circuit

Although the circuit of Fig.1 is very good for CW reception, it is less well suited to RTTY decoding. This is generally handled more efficiently using more sophisticated tone decoders, such as the twin filter type that was broadly described in last month's *Beeb Micro* article. The circuit for a decoder of this type is provided in Fig.2.

IC1 simply acts as a buffer stage at the input. It drives two bandpass filters that

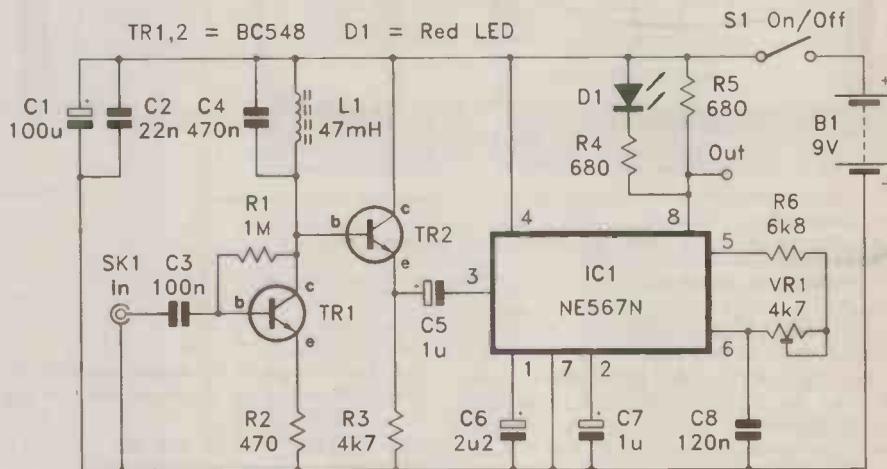


Fig. 1. A simple CW Tone Decoder based on a phase-locked-loop i.c.

to experiment with this type of equipment. In order to set up VR1 correctly, temporarily wire a resistor of about 470k to 1M in value between pin 5 of IC1 and the input of the unit. Then adjust VR1 for maximum output level at the emitter of TR1. Use an a.c. millivolt meter or an oscilloscope to measure the signal level here.

## Interfacing

It is probably best to get the unit operating satisfactorily before it is interfaced to a computer. Its output should not be directly connected to a computer input port (such as a line of the BBC computer's user port) as it is not at standard logic levels.

One method of interfacing is to use some form of level shifter circuit. Another option is to omit D1, R4, and R5, and to connect the open collector output to the input line of the computer. As the BBC computer's user port inputs have internal pull-up resistors, this method should be perfectly satisfactory.

The lack of an indicator l.e.d. is a slight

are based on IC2 and IC3, and are of a well known design. These must have frequencies that match those of the RTTY signal. RTTY signals are normally transmitted in the form of a carrier wave switched between two frequencies, rather than a carrier wave which is amplitude modulated by a two-tone input signal.

In order to provide a two-tone audio output from the receiver it must be set to the s.s.b. mode (assuming no mode specifically for RTTY is included), so that the input signal is heterodyned with the beat frequency oscillator (b.f.o.). Within reason, the receiver can then be tuned to obtain any desired audio frequencies having a spacing that is set at the transmitter. For amateur RTTY transmissions the standard tone spacing is 175Hz.

Accordingly, it does not matter too much what centre frequencies are used for the two filters, provided they are 175Hz apart. The frequency of the filter based on IC2 is preset at about 1.1kHz. The centre frequency of the filter based on IC3 can be adjusted by means of VR1, and can be set

175Hz higher or lower than the other filter frequency, as desired. I set it 175Hz lower in frequency, but setting it 175Hz higher would probably make no noticeable difference to the performance of the decoder.

The outputs of the filters feed into separate rectifier and smoothing circuits, which in turn feed into voltage comparator IC4. This has a small amount of hysteresis provided by R15. This ensures that the output switches cleanly from one logic level to the other, and also reduces the risk of problems with "jitter" on noisy input signals. TR1 is a common emitter output stage of the open collector variety. This will drive any logic input which has a pull-up resistor, including one of the BBC computer's user port input lines.

The circuit is powered from a 9 volt battery, and the current consumption is only about 6.5 milliamps. Even a small (PP3 size) battery should be adequate as the power source. A larger type would probably prove to be more economic though, if the unit will receive a great deal of use.

Having located the peak frequency, set the audio signal generator 175Hz lower in frequency. Use the a.c. millivoltmeter or oscilloscope to monitor the output level at pin 6 of IC3, or use the multimeter to measure the voltage across R14. Then adjust VR1 for the highest possible output level. It should provide a pronounced peak, and must be adjusted very carefully. The unit is then ready for use.

In the absence of a calibrated signal generator, a short wave radio tuned to a carrier wave and having the b.f.o. switched on will provide a variable audio tone. This can be adjusted to the centre frequency of the filter based on IC2, and adjusted for a slightly lower pitch. VR1 is then adjusted to peak this lower frequency signal. This is obviously a bit hit and miss, and you will probably need to experiment a little in order to obtain the right shift frequency.

The filters have quite narrow bandwidths in order to give good performance. An unavoidable consequence of this is that the unit needs to be adjusted quite accurately if it is to operate properly.

impossible. Some form of tuning indicator is essential.

The ideal method is one which uses an oscilloscope set to the mode where the timebase is switched out, and signals can be fed to the X and Y amplifiers. The X input monitors the voltage across R8, while the Y input is fed with the voltage from R14. Both inputs should have the same sensitivity.

Using the oscilloscope in this way you do, of course, get it to draw lissajous figures. In this case it will draw some quite interesting ones, with something like Fig.3(a) if a signal is tuned correctly. If the tuning is slightly off in one direction, the display will look more like Fig.3(b), while Fig.3(c) shows the sort of display to be expected if the tuning is amiss in the opposite direction.

If the tuning is well out, the display is likely to be just a total jumble of lines, but there is usually no difficulty in getting close using the tuning "by ear" method. With this type of tuning indicator it is then very easy to get the tuning absolutely spot-on.

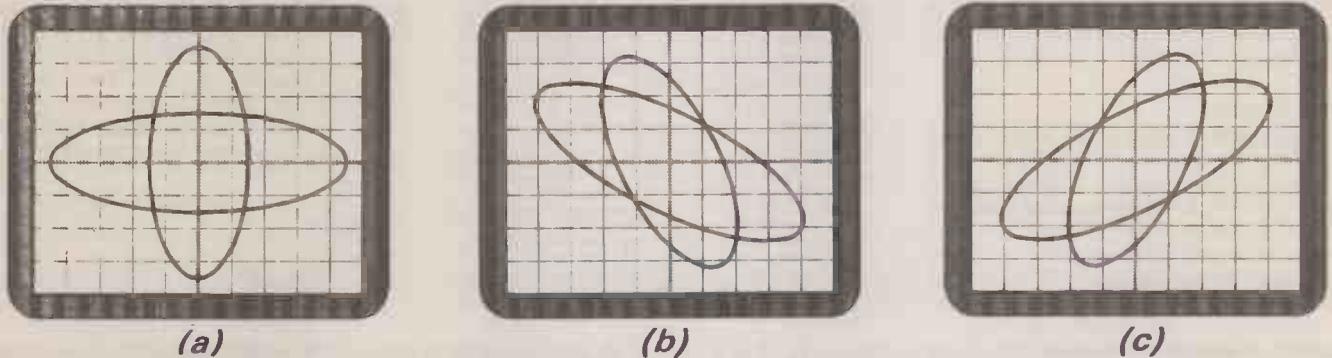


Fig. 3. Using an oscilloscope as a timing indicator. (a) indicates correct timing. While (b) and (c) show tuning errors in opposite directions.

### Setting Up

In order to accurately set up the unit ready for use a calibrated audio signal generator and an oscilloscope, a.c. millivoltmeter, or multimeter are required. The output of the audio signal generator is fed to the input of the unit, and the millivoltmeter or oscilloscope is used to monitor the output level at pin 6 of IC2. A multimeter set to read about 10 volts d.c. full scale can effectively monitor the output level from IC2 if it is used to measure the voltage across R8.

Adjust the frequency control of the audio signal generator to find the frequency at which the filter based on IC2 has its peak response. Be careful not to use an excessive input level, as this will prevent a definite peak frequency from being obtained.

The unit will work well with the "tape" output of a receiver. If overloading seems to occur, a resistor of about 100k in series with the input should rectify matters. The unit can also be fed from a "phone" output, but changes in the volume control setting will then alter the input level to the filter. Obviously the volume control must then be given settings that will provide a suitable input level for the decoder.

### Tuning


The narrow bandwidth of the filters and the small frequency shift used for amateur RTTY not only makes units of this type difficult to set up properly, but also makes accurately tuning in stations quite tricky. Even if you have a really good sense of pitch, accurately tuning the warbling sound of an RTTY signal "by ear" is virtually

Note that in practice there will often be noise and fading of one or both tones, and that the traces may not be quite as perfect as depicted in Fig.3. Tuning signals is still reasonably easy, and if things are not perfect at first, during the periods when signals come through strongly you can do some readjustments to get things just right.

It is surprising just how bad the input signal can get, with a well decoded output still being produced. If the horizontal and vertical sections of the trace are not at right angles to one another, either the transmission has the wrong tone spacing, or the tunable filter of the decoder is not set up correctly.

Next month: We will consider a more simple form of tuning indicator, and using a UART to give decoded parallel data that can be read by the user port.

Fig. 2. A twin filter type decoder suitable for RTTY reception.

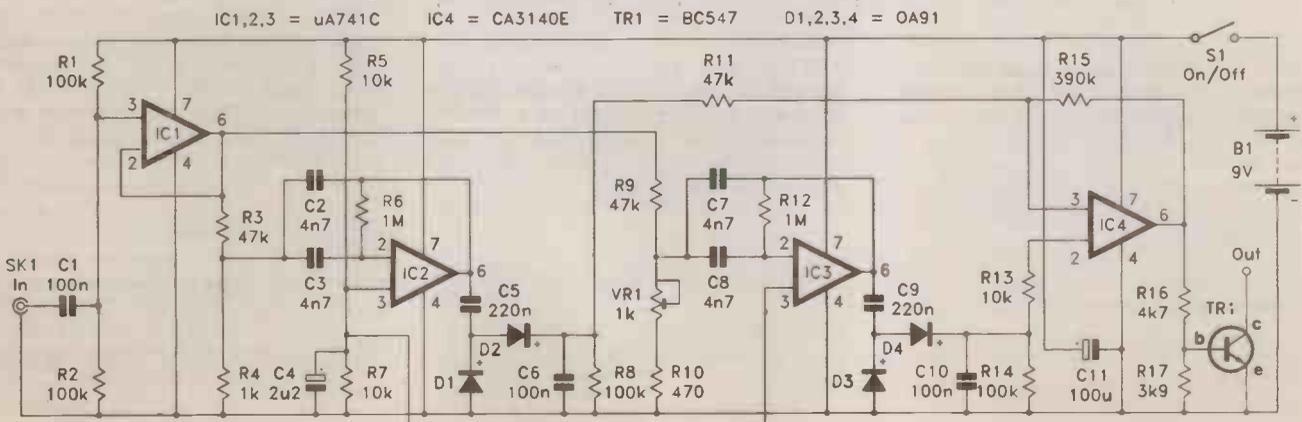

# DIRECT BOOK SERVICE

The books listed have been selected as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page.

## MORE BOOKS NEXT MONTH—MORE BOOKS NEXT MONTH

### AUDIO & MUSIC

#### SYNTHESIZERS FOR MUSICIANS

**R. A. Penfold**  
Modern synthesizers are extremely complex, but they mostly work on principles that are not too difficult to understand. If you want to go beyond using the factory presets or the random poking of buttons, this is the book for you.

It covers the principles of modern synthesis—linear arithmetic as used by Roland, phase distortion (Casio), Yamaha's frequency modulation, and sampling—and then describes how the instruments are adjusted to produce various types of sound—strings, brass, percussion, etc. The theoretical side of synthesis is treated in an easy to understand way—the technical information being restricted to what you need to know to use your instrument effectively.

168 pages Order code PC105 £6.95

#### AUDIO

**F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.**

Analysis of the sound wave and an explanation of acoustical quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapter on audio systems—amplifiers, oscillators, disc and magnetic recording and electronic music.

320 pages Temporarily out of print

#### INTRODUCTION TO DIGITAL AUDIO

**Ian Sinclair**  
Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring digital audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages Order code PC102 £5.95

#### MAKE MONEY FROM HOME RECORDING

**Clive Brooks**  
Now that you've spent a fortune on all that recording gear, MIDI and all, wouldn't it be nice to get some of it back? Well here's the book to show you how.

It's packed with money making ideas, any one of which will recoup the price of the book many times over. Whether you have a fully fledged recording studio at home, or just a couple of stereo cassette recorders and a microphone, you'll be able to put the ideas in this book into practice and make money.

105 pages Order code PC104 £5.95

### TESTING & TEST GEAR

#### HOW TO TEST ALMOST EVERYTHING ELECTRONIC—2nd EDITION

**Jack Darr and Delton T. Horn**  
Describes electronic tests and measurements—how to make them with all kinds of test equipment, and how to interpret the results. New sections in this edition include logic probes, frequency counters, capacitance meters, and more. (An American book.)

190 pages Order code T2925 £9.05

#### GETTING THE MOST FROM YOUR MULTIMETER

**R.A. Penfold**  
This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages Order code BP239 £2.95

#### MORE ADVANCED USES OF THE MULTIMETER

**R.A. Penfold**  
This book is primarily intended as a follow-up to BP239, (see above), and should also be of value to anyone who already understands the basics of voltage testing and simple component testing. By using the techniques described in chapter 1 you can test and analyse the performance of a range of components with just a multimeter (plus a very few inexpensive components in some cases). Some useful quick check methods are also covered.

While a multimeter is supremely versatile, it does have its limitations. The simple add-ons described in chapter 2 extend the capabilities of a multimeter to make it even more useful. The add-ons described include an active r.f. probe, a high resistance probe, an a.c. sensitivity booster, and a current tracer unit.

84 pages Order code BP265 £2.95

### TEACH-IN THEORY & REFERENCE



#### EVERYDAY ELECTRONICS DATA BOOK

**Mike Tooley BA**  
(published by EE in association with PC Publishing)  
This book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but it also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available "industry standard" components and devices.

A must for everyone involved in electronics!  
256 pages Order code DATA £8.95

#### ELECTRONICS TEACH-IN 88/89—INTRODUCING MICROPROCESSORS

**Mike Tooley BA** (published by *Everyday Electronics*)  
A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Microprocessors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering the most popular microprocessor chips.

An excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment.  
80 pages (A4 size) Order code TI-88/89 £2.45

#### THE ILLUSTRATED DICTIONARY OF ELECTRONICS—4th EDITION

**Rufus P. Turner and Stan Gibilisco**  
With more than 27,000 terms used in electronics today, this collection is THE most comprehensive dictionary available. Including all practical electronics and computer terms, it is as up-to-date as the latest advances in the field itself! Tables and data on subjects most often consulted for projects and experiments are included. Other conversion tables include English/metric and metric/English conversions for units of measurement of energy, power and volume, and Fahrenheit/Celsius temperature conversion charts.

Setting this edition apart from other electronic dictionaries is its emphasis on illustration. Featuring more than complete definitions, this fourth edition includes over 450 detailed drawings and diagrams.

All entries are listed in alphabetical order. Abbreviations and initials are listed in sequence with whole words. All terms of more than one word are treated as one word. (An American book.)  
648 pages Order code TI2900 £23.65

#### MICROPROCESSING SYSTEMS AND CIRCUITS

**F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.**

A truly comprehensive guide to the elements of micro-processing systems which really starts at the beginning. Teaches the reader the essential fundamentals that are so important for a sound understanding of the subject.  
256 pages Temporarily out of print

#### ELECTRONICS TEACH-IN No. 3 — EXPLORING ELECTRONICS (published by *Everyday Electronics*)

**Owen Bishop**  
Another EE value for money publication aimed at students of electronics. The course is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

Exploring Electronics contains more than 25 useful projects, assumes no previous knowledge of electronics and is split into 28 easily digestible sections.  
88 pages (A4 size) Order code TI3 £2.45

#### ELECTRONICS—A "MADE SIMPLE" BOOK

**G. H. Olsen**  
This book provides excellent background reading for our *Introducing Digital Electronics* series and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity.  
330 pages Order code NE10 £4.95

#### PRACTICAL ELECTRONICS CALCULATIONS AND FORMULAE

**F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.**

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias—tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-current Circuits, Passive Components, Alternating-current Circuits, Networks and Theorems, Measurements.  
256 pages Order code BP53 £3.95

#### MICROELECTRONIC SYSTEMS N2 CHECKBOOK

**R. Vears**  
The aim of this book is to provide a foundation in microcomputer hardware, software and interfacing techniques. Each topic is presented in a way that assumes only an elementary knowledge of microelectronic systems and logic functions. The book concentrates on 6502, Z80 and 6800 microprocessors and contains 60 tested programs, 160 worked problems and 250 further problems.  
Order code NE04N £6.95

**ELECTRONICS-BUILD AND LEARN**

**R. A. Penfold**  
The first chapter gives full constructional details of a circuit demonstrator unit that is used in subsequent chapters to introduce common electronic components—resistors, capacitors, transformers, diodes, transistors, thyristors, fets and op amps. Later chapters go on to describe how these components are built up into useful circuits, oscillators, multivibrators, bistables and logic circuits.  
At every stage in the book there are practical tests and experiments that you can carry out on the demonstrator unit to investigate the points described and to help you understand the principles involved. You will soon be able to go on to more complex circuits and tackle fault finding logically in other circuits you build.

120 pages Order Code PC103 £5.95

**PRACTICAL ELECTRONICS HANDBOOK**

**Ian Sinclair**  
Ian Sinclair has now revised this useful and carefully selected collection of standard circuits, rules-of-thumb, and design data for professional engineers, students and enthusiasts involved in radio and electronics. Covering passive and active components, discrete component circuits (such as amplifiers, filters and oscillators) and linear and digital i.c.s., the book includes many items which are not elsewhere available in a single handy volume. The operation and functions of typical circuits are described, while mathematics is limited to that necessary for deciding component values for any application.  
This revised edition contains more details on computers and microprocessors and has been brought up to date throughout.

199 pages Order Code NE06 £7.95

**TRANSISTOR SELECTOR GUIDE**

This unique guide offers a range of selection tables compiled so as to be of maximum use to all electronics engineers, designers and hobbyists.  
Section 1: Covers component markings, codings and standards, as well as explaining the symbols used.  
Section 2: Tabulates in alpha-numeric sequence the comprehensive specifications of over 1400 devices.  
Section 3: Tabulates the devices by case type.  
Section 4: Considers particular limits to the electrical parameters when compiling the tables.  
Section 5: Illustrates package outlines and leadouts.  
Section 6: Consists of a surface mounting device markings conversion list.

192 pages Temporarily out of print


**CIRCUITS & DESIGN**

**ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF MODEL RAILWAYS**

**R.A. Penfold**  
Home computers may easily be applied to the control of model railways and really quite sophisticated control, which needs only simple programming, is not too difficult to achieve. The main problem lies in interfacing the computer to the layout, but fortunately it is not too difficult or expensive to build suitable interfaces, and this book shows you how.

The projects consist of various types of controller, including a high quality pulse type, as well as circuits for train position sensing, signal and electric points control etc. The use of computers does not have to be restricted to massive layouts. Something as simple as an oval of track with a single siding can be given a new dimension by adding computer control and much fun can be had from these relatively simple set-ups.

88 pages Order code BP180 £2.95

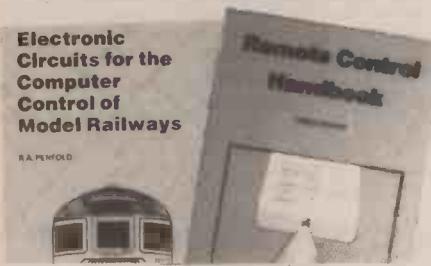

**ELECTRONIC CIRCUITS HANDBOOK**

**Michael Tooley BA**  
This book aims to explode two popular misconceptions concerning the design of electronic circuits: that only those with many years of experience should undertake circuit design and that the process relies on an understanding of advanced mathematics. Provided one is not too ambitious, neither of these popularly held beliefs is true.

Specifically, this book aims to provide the reader with a unique collection of practical working circuits together with supporting information so that circuits can be produced in the shortest possible time and without recourse to theoretical texts.

Furthermore, information has been included so that the circuits can readily be modified and extended by readers to meet their own individual needs. Related circuits have been grouped together and cross-referenced within the text (and also in the Index) so that readers are aware of which circuits can be readily connected together to form more complex systems. As far as possible, a common range of supply voltages, signal levels and impedances has been adopted.

As a bonus, ten test gear projects have been included. These not only serve to illustrate the techniques described but also provide a range of test equipment which is useful in its own right.

277 pages Order code NE05 £14.95

**DIGITAL IC EQUIVALENTS AND PIN CONNECTIONS**

**A. Michaels**  
Shows equivalents and pin connections of a popular selection of European, American and Japanese digital i.c.s. Also includes details of packaging, families, functions, manufacturer and country of origin.

256 pages Temporarily out of print

**INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE**

**A. Michaels**  
Helps the reader to find possible substitutes for a popular selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.

320 pages Order code BPB5 £3.50

**CHART OF RADIO, ELECTRONIC, SEMICONDUCTOR AND LOGIC SYMBOLS**

**M. H. Banani, B.Sc.(Eng.)**  
Illustrates the common, and many of the not-so-common, radio, electronic, semiconductor and logic symbols that are used in books, magazines and instruction manuals, etc., in most countries throughout the world.

Chart Order Code BP27 £0.95

**AUDIO IC CIRCUITS MANUAL**

**R. M. Marston**  
A vast range of audio and audio-associated i.c.s. are readily available for use by amateur and professional design engineers and technicians. This manual is a guide to the most popular and useful of these devices, with over 240 diagrams. It deals with i.c.s. such as low frequency linear amplifiers, dual pre-amplifiers, audio power amplifiers, charge coupled device delay lines, bar-graph display drivers, and power supply regulators, and shows how to use these devices in circuits ranging from simple signal conditioners and filters to complex graphic equalizers, stereo amplifier systems, and echo/reverb delay line systems etc.

168 pages Order code NE13 £11.95

**HOW TO DESIGN ELECTRONIC PROJECTS**

**R. A. Penfold**  
The aim of this book is to help the reader to put together projects from standard circuit blocks with a minimum of trial and error, but without resorting to any advanced mathematics. Hints on designing circuit blocks to meet your special requirements are also provided.

128 pages Order code BP127 £2.25

**50 CIRCUITS USING GERMANIUM SILICON AND ZENER DIODES**

**R. N. Soar**  
Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most simple and inexpensive of components—the diode. Includes the use of germanium and silicon signal diodes, silicon rectifier diodes and Zener diodes, etc.

64 pages Order Code BP36 £1.50

**KEY TECHNIQUES FOR CIRCUIT DESIGN**

**C. G. Loveday C.Eng MIERE**  
Deals with designing electronic circuits from scratch covering concepts such as target specifications, component selection (passive, discrete and i.c.s.), the design cycle, derating and so on. Numerous design examples are given and several reader exercises all with fully worked solutions. The approach is essentially non-mathematical.

128 pages Order code BM1 £6.95

**DESIGNING WITH LINEAR ICs**

**G.C. Loveday**  
A book that deals with the design of the vital area of analog circuitry covering design with modern linear integrated circuit devices. The first chapter introduces the reader to important design techniques, test strategies, layout, and protection and also includes a section on the use of a typical CAD tool. There are separate chapters that cover in depth the use of op-amps, comparators and timers each with detailed design examples and reader exercises. A final chapter brings all the previous work together in a number of complete design problems with fully worked solutions. The text is essentially non-mathematical and is supported by many diagrams.

180 pages Order code BM3 £8.75

**OPTOELECTRONICS CIRCUITS MANUAL**

**R. M. Marston**  
A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s. and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages Order code NE14 £12.95



**A MICROPROCESSOR PRIMER**

**E. A. Parr, B.Sc., C.Eng., M.I.E.E.**  
Starts by designing a small computer which, because of its simplicity and logical structure, enables the language to be easily learnt and understood. The shortcomings are then discussed and the reader is shown how these can be overcome by changes and additions to the instruction set. In this way, such ideas as relative addressing, index registers, etc., are developed.

96 pages Order code BP72 £1.75

**POPULAR ELECTRONIC CIRCUITS**

—BOOK 1

POPULAR ELECTRONIC CIRCUITS

—BOOK 2

**R. A. Penfold**  
Each book provides a wide range of designs for electronic enthusiasts who are capable of producing working projects from just a circuit diagram without the aid of detailed construction information. Any special setting-up procedures are described.

BOOK 1 160 pages Order code BP80 £2.95

BOOK 2 160 pages Order code BP98 £2.95

**CMOS CIRCUITS MANUAL**

**R. M. Marston**  
Written for the professional engineer, student or enthusiast. It describes the basic principles and characteristics of these devices and includes over 200 circuits. All the circuits have been designed, built and fully evaluated by the author; all use inexpensive and internationally available devices.

pages Order code NE12 £9.95

**REMOTE CONTROL HANDBOOK**

**Owen Bishop**  
Remote control systems lend themselves to a modular approach. This makes it possible for a wide range of systems, from the simplest to the most complex, to be built up from a number of relatively simple modules. The author has tried to ensure that, as far as possible, the circuit modules in this book are compatible with one another. They can be linked together in many different configurations to produce remote control systems tailored to individual requirements. Whether you wish simply to switch a table lamp on and off, or to operate an industrial robot, this book should provide the circuit you require.

226 pages Order code BP240 £3.95

**COIL DESIGN AND CONSTRUCTION MANUAL**

**B. B. Babani**  
A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now rather old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages Order Code 160 £2.50



**30 SOLDERLESS BREADBOARD PROJECTS - BOOK 1**

**R. A. Penfold**  
Each project, which is designed to be built on a "Verobloc" breadboard, is presented in a similar fashion with a brief circuit description, circuit diagram, component layout diagram, components list and notes on construction and use where necessary. Wherever possible, the components used are common to several projects, hence with only a modest number of reasonably inexpensive components, it is possible to build in turn, every project shown. Recommended by BICC-Verobloc.

160 pages Order Code BP107 £2.95

BOOK 2 - All projects use CMOS i.c.s but the items on component identification etc., are not repeated from Book 1  
160 pages Order code BP113 £2.25

**ELECTRONIC PROJECTS — BOOK 1**

Published by *Everyday Electronics* in association with *Magenta Electronics*.

Contains twenty of the best projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesiser, *EE* Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16k Sideways Ram, Simple Short Wave Radio, Insulation Tester, Visual Guitar/Instrument Tuner, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, *EE* Equaliser Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider — (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, *EE* Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.

128 pages(A4 size) Order Code EP1 £2.45

**HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s**

R. A. Penfold

Deals with the simple methods of copying printed circuit

board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.  
80 pages Order code BP121 £2.50

**HOW TO GET YOUR ELECTRONIC PROJECTS WORKING**

R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.

96 pages Order code BP110 £2.50

**ELECTRONIC SCIENCE PROJECTS**

O. Bishop

These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained.

144 pages Order code BP104 £2.95

**BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS**

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also includes examples in the form of simple projects.

112 pages Order code No. 227 £1.95

**TEST EQUIPMENT CONSTRUCTION**

R.A. Penfold

This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:- AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Millivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe. The designs are suitable for both newcomers and more experienced hobbyists.

104 pages Order code BP248 £2.95

**RADIO, TV, SATELLITE**

**BEGINNER'S GUIDE TO RADIO—9th EDITION**

Gordon J. King

Radio signals, transmitters, receivers, antennas, components, valves and semiconductors, CB and amateur radio.

266 pages Order code NE08 £6.95

**AN INTRODUCTION TO RADIO DXING**

R. A. Penfold

Anyone can switch on a short wave receiver and play with the controls until they pick up something, but to find a particular station, country or type of broadcast and to receive it as clearly as possible requires a little more skill and knowledge. The object of this book is to help the reader to do just that, which in essence is the fascinating hobby of radio DXing.

112 pages Order code BP91 £1.95

**A TV-DXERS HANDBOOK**

R. Bunney

Roger Bunney is probably one of the leading authorities in this country on the subject. Includes many units and devices which have been designed and used by active enthusiasts, and often, considerable ingenuity and thought have gone into the development of such units to overcome individual problems. A practical and authoritative reference to this unusual aspect of electronics.

128 pages Order code BP176 £5.95

**SATELLITE TELEVISION INSTALLATION GUIDE—**

2nd EDITION

John Breeds

This book is now firmly established as a leading study manual for satellite TV installers, technical colleges who run City & Guilds courses, and training schools in major companies. It will be invaluable to anyone who wants to set up a dish receiver.

It covers all aspects of satellite dish installation: Installation of indoor unit, Geostationary satellites, Site survey, Dish assembly, Signal polarisation, Setting up the dish, Polar mount dish, TV download and relay cable and F-connectors, EIRP footprint contours, Trouble-shooting guide, Glossary of terms and Useful addresses.

56 pages (large format) Order code JB1 £11.95

**NEWNES SHORTWAVE LISTENING HANDBOOK**

Joe Pritchard G1UQW

Part One covers the "science" side of the subject, going from a few simple electrical "first principles", through a brief treatment of radio transmission methods to simple receivers. The emphasis is on practical receiver designs and how to build and modify them, with several circuits in the book.

Part Two covers the use of sets, what can be heard, the various bands, propagation, identification of stations, sources of information, QSLing of stations and listening to amateurs. Some computer techniques, such as computer morse decoding and radio teletype decoding are also covered.

224 pages Order code NE16 £12.95

**DIRECT BOOK SERVICE**

(A Division of Wimborne Publishing Ltd.)

**TO ORDER**

Please state the title and order code clearly, print your name and address and add the required postage to the total order.


Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.00 for all countries outside Europe, surface mail postage) and send a PO, cheque or international money order (£ sterling only) made payable to *Direct Book Service* quoting your name and address, the order code and quantities required to *DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET, BH21 1RW* (mail order only).

See next month's issue for another three page selection of books.

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of *Everyday Electronics*) before ordering from old lists.

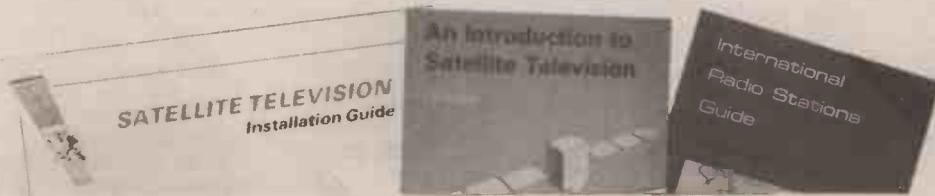Note — our postage charge is the same for one book or one hundred books!



**COMPUTING**

**SERVICING PERSONAL COMPUTERS—2nd EDITION**

Mike Tooley BA

The revised and enlarged second edition contains a new chapter on the IBM PC, AT, TX and compatibles. It is essential for anyone concerned with the maintenance of personal computer equipment or peripherals, whether professional service technician, student or enthusiast.

240 pages (hard cover) Order code NE15 £25

**AN INTRODUCTION TO PROGRAMMING THE BBC MODEL B MICRO**

R. A. & J. W. Penfold

Written for readers wanting to learn more about programming and how to make best use of the incredibly powerful model B's versatile features. Most aspects of the BBC micro are covered, the omissions being where little could usefully be added to the information provided by the manufacturer's own manual.

144 pages Order code BP139 £1.95

**AN INTRODUCTION TO COMPUTER COMMUNICATIONS**

R. A. Penfold

Provides details of the various types of modem and their suitability for specific applications, plus details of connecting various computers to modems, and modems to the telephone system. Also information on common networking systems and RTTY.

96 pages Order code BP177 £2.95

**AN INTRODUCTION TO COMPUTER PERIPHERALS**

J. W. Penfold

Covers such items as monitors, printers, disc drives, cassette recorders, modems, etc., explaining what they are, how to use them and the various types and standards. Helps you to make sure that the peripherals you buy will work with your computer.

80 pages Order code BP170 £2.50

**HOW TO GET YOUR COMPUTER PROGRAMS RUNNING**

J. W. Penfold

Have you ever written your own programs only to find that they did not work? Help is now at hand with this book which shows you how to go about looking for your errors, and helps you to avoid the common bugs and pitfalls of program writing. Applicable to all dialects of the BASIC language.

144 pages Order code BP169 £2.50

**AN INTRODUCTION TO 6502 MACHINE CODE**

R. A. & J. W. Penfold

No previous knowledge of microprocessors or machine code is assumed. Topics covered are: assembly language and assemblers, the register set and memory, binary and hexadecimal numbering systems, addressing modes and the instruction set, and also mixing machine code with BASIC. Some simple programming examples are given for 6502-based home computers like the VIC-20, ORIC-1/Atmos, Electron, BCC and also the Commodore 64.

112 pages Order code BP147 £2.95

**THE PRE-BASIC BOOK**

F. A. Wilson, C.G.J.A., C.ENG., F.I.E.E., F.I.E.R.E., F.B.I.M.

Another book on BASIC but with a difference. This one does not skip through the whole of the subject and thereby leave many would-be programmers floundering but instead concentrates on introducing the technique by looking in depth at the most frequently used and more easily understood computer instructions. For all new and potential micro users.

192 pages Order code BP146 £2.95

# HIGH GRADE COMPONENT PARCELS

**EVERYTHING  
MUST  
GO!**

Unless otherwise stated, all the clearance parcels we offer contain brand new, top grade components. If some of the offers look too good to be true, all I can say is that the optimists will get some stunning bargains, the cynics will never know what they've missed, so everybody will be happy! All offers apply only while current stocks last - watch out for next month's parcels or, better still, be the first to hear about any new offers by putting your name on our mailing list.


**Access Orders:  
Tel: 0600 3715**

## SEMI CONDUCTORS

What a selection! Every single parcel will contain: ICs, signal diodes, rectifiers, zeners, semiconductor VDRs, transistors, FETs, high voltage transistors, power transistors, triacs, voltage regulators, and a good deal more. Did I mention the varicap tuning diodes? The VHF transistors? The Schottky rectifiers? All the semiconductors you've ever wanted, but could never afford. This has to be one of the finest parcels we have ever offered. Don't miss it!

**PARCEL 9A:  
200 SEMICONDUCTORS  
for £10! + VAT**

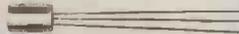**PARCEL 9B:  
1000 SEMICONDUCTORS  
for £40! + VAT**



## PRESETS

An attractive and very functional pack of preset pots. The parcels contain a high proportion of top quality cermet, both single and multi-turn. In fact they outnumber the carbon types! All styles and types are represented: open, enclosed, vertical, horizontal, square, round, 3/4" and 1 1/4" multi-turns, and so on. All values from a few ohms to several megs.

**PARCEL 11A:  
200 PRESETS for £6 + VAT**

**PARCEL 11B:  
1000 PRESETS for £25 + VAT**



## SWITCHES

Take a rocker switch in one hand, a roller microswitch in the other, and have yourself a rock 'n' roll party! OK, the jokes aren't up to much, but the switches are superb. Lots of rocker switches - ideal as spares for household gadgets. Some, so I'm told, fit the dashboard cut-outs on Ford cars, so just think of the extra lights and stuff you could fit! Then there are the toggles, the push switches, the rotaries and the sliders. All tucked up snugly, bless their cotton socks, in our switch parcels. And all for 10p each or less - it's enough to make you explode with joy. Well, nearly enough.

**PARCEL 14A: 100 ASSORTED  
SWITCHES for £10! + VAT**

**PARCEL 14B: 300  
ASSORTED  
SWITCHES  
for £25! +  
VAT**



## MONSTER OPTO PARCELS

If it has anything to do with light, it's in here. There are LEDs of all shapes, sizes and colours, seven segment displays, infra-red senders and receivers, bar graph assemblies, opto switches, and who knows what else. The larger parcels have LCDs too. An excellent selection of top quality devices.

**PARCEL 12A:  
100 OPTO DEVICES for £10 + VAT**

**PARCEL 12B:  
300 OPTO DEVICES  
for £25 + VAT**



## H.V. POLYESTERS

Above 100n or so the price of non-electrolytic caps starts to rise steeply. To get one above 1µF will cost the earth, or at least a major planet. And not even an asteroid for change. These parcels contain caps to at least 4µF.

Replace those nasty non-polar electrolytics in your speaker crossovers, connect them across electrolytic smoothing and coupling caps in your hi-fi, stop using back-to-back tants in your projects. The larger caps will easily cost several ££s each from normal suppliers. We've got too many, so...

**PARCEL 15A:  
200 HV POLYESTERS  
for £10 + VAT**

**PARCEL 15B:  
600 HV POLYESTERS  
for £25 + VAT**



## CONNECTORS

If you ever again need to connect anything to anything else, the chances are you'll find the plugs and sockets for it in this parcel. Computers?

There are D connectors, printer connectors, RS232 connectors, and so on. PCBs? There are edge connectors and pin connectors. RF connectors?

No problem. Audio? There are speaker plugs and sockets, DIN connectors and much more.

And all for 10p or less apiece! How can you resist it?

**PARCEL 10A:  
100 ASSORTED CONNECTORS for £10! + VAT**

**PARCEL 10B:  
300 ASSORTED CONNECTORS  
for £25! + VAT**

## RESISTORS

Supplied to you as they arrive with us: some bagged, some banded, some reeled, some loose. The mixture has 1/4W resistors in every single E12 value, with some E24 and an assortment of E96 precision types. Then there are 1/2W resistors and a nice selection of

power types to 5W and above. The proportions vary from parcel to parcel, but you'll certainly have an excellent range of types and values.

I have absolutely no intention of counting out tens of thousands of resistors, so these are sold by weight. As a rough guide 1000 1/4W resistors weigh about 240g, so there are over 4000 of these to the Kg.

**PARCEL 13A:  
10Kg RESISTOR  
PARCEL £30  
+ VAT**

## JUNK!

Bits of equipment, PCBs, components, hardware, mags, books, data, everything electronic turns up at some time or other in our legendary JUNK parcels.

There's so much unsorted stuff around the place we hardly know what goes in there ourselves! The components won't be neatly packed - once we've combed their hair and dressed them in their Sunday best, they go onto one of lists. In the JUNK parcel you see them in the raw state.

The first 10Kg is yours for £18 + VAT. After that, the price is £1 per Kg, so 11Kg will be £19 + VAT, 12Kg will be £20 + VAT, and so on. Have as much as you like!

**JUNK SPECIAL:  
1 cwt for £50!  
+ VAT**

**UK Orders:**  
Please add £2.50 towards postage and packing and 15% VAT to the total

**Europe and Eire:**  
Please add £6.00 carriage and insurance. No VAT

**Outside Europe:**  
Please add £12.00 carriage and insurance. No VAT

# HIGHGRADE COMPONENTS LTD

Unit 111, 8 Woburn Road, Eastville, Bristol BS5 6TT  
Tel: 0600 3715 Fax: 0600 72262

H5

# PCB SERVICE

Printed circuit boards for certain constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for overseas airmail. Remittances should be sent to **The PCB Service Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH.** Cheques should be crossed and made payable to **Everday Electronics (Payment in £ sterling only).**

*Boards for some older projects – not listed here – can often be obtained from Magenta Electronics, 135 Hunter St., Burton-on-Trent, Staffs DE14 2ST. Tel: 0283 65435 or Lake Electronics, 7 Middleton Close, Nuthall, Nottingham NG16 1BX. Tel: 0602 382509.*

**NOTE:** While 90% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery – overseas readers allow extra if ordered by surface mail. Please check price and availability in the latest issue before ordering. We can only supply boards listed in the latest issue. Boards can only be supplied on a payment with order basis.

PROJECT TITLE	Order Code	Cost
Video Guard	FEB '87 556	£3.80
Spectrum I/O	557	£5.35
Computer Buffer/Interface	MAR '87 560	£3.32
Fridge Alarm	MAY '87 565	£3.00
Mini Disco Light	JUNE '87 567	£3.00
EE Buccaneer Metal Detector	JULY '87 570	£4.10
Monomix	571	£4.75
Noise Gate	SEPT '87 577	£4.41
Electronic Analogue/Digital Multimeter	579	£6.40
Transtest	OCT '87 580	£3.32
BBC Sideways RAM/ROM	NOV '87 585	£4.10
Twinkling Star	DEC '87 588	£3.00
Audio Sine Wave Generator	589	£3.03
Capacitance Meter	JAN '88 590	£4.10
Transistor Curve Tracer	592	£3.00
Game Timer	FEB '88 583	£3.55
Semiconductor Tester	MAR '88 594	£3.19
SOS Alert	595	£3.00
Guitar/Keyboard Envelope Shaper	596	£4.23
Stereo Noise Gate	APR '88 597	£6.65
Pipe & Cable Locator	598	£3.00
Inductive Proximity Detector	574	£3.00
Multi-Chan Remote Light Dim	MAY '88 599	£3.00
Transmitter	600	£3.07
Receiver	605	£3.00
Door Sentinel	606	£5.91
Function Generator – Main Board	607	£4.19
Function Generator – Power Supply		
Multi-Chan Remote Light Dim	JUNE '88 601	£4.86
Relay/Decoder	602	£3.07
Dimmer Board	603	£3.00
Power Supply	604	£7.76
Mother Board	611	£3.00
Headlight Reminder		
Video Wiper	JULY '88 612	£6.75
Isolink	613	£4.21
Tea Tune	AUG '88 609	£3.00
Time Switch	614	£4.84
Suntan Timer	610	£3.07
Car Alarm	615	£3.12
Breaking Glass Alarm	SEPT '88 617	£4.27
Amstrad PIO	618	£6.77
Eprom Eraser	OCT '88 620	£4.07
Doorbell Delay	NOV '88 616	£3.56
Micro Alarm	621	£3.12
Infra-Red Object Counter	622	£4.61
Trans Receiver	623	£3.23
Display	624	£3.05
Seashell Sea Synthesiser	625	£4.84
Reaction Timer Main Board	DEC '88 626	£3.46
Display Board	627	£3.00
Downbeat Metronome	629	£4.84

EPROM Programmer (On Spec)	DEC '88 630	£8.29
Phasor	631	£5.64
Monkey/Hunter Game	JAN '89 634	£3.36
Continuity Tester	FEB '89 619	£2.67
4-Channel Light Dimmer	635	£7.67
Mini PSU	636	£3.23
Sound-to-Light Interface	MAR '89 637	£6.24
Midi Pedal	639	£7.00
Midi Merge	640	£3.00
Audio Lead Tester	641	£5.77
Light Sentinel	APR '89 632	£9.20
Main Control Board	633	£4.59
Remote Interface (4 boards)	638	£6.64
Electron User Port	642	£6.80
4-Channel Auto-Fader Interface		
Pet Scarer	MAY '89 644	£3.00
Electron A/D Interface	645	£4.84
Spectrum EPROM Programmer	JUNE '89 628	£7.87
Bat Detector	647	£4.95
Programmable Pocket Timer	JULY '89 648	£3.82
Electronic Spirit Level	AUG '89 649	£3.85
Distance Recorder	651	£5.23
Treasure Hunter	652	£3.73
Xenon Beacon	SEPT '89 650	£4.13
Probe Pocket Treasure Finder	653	£4.12
Power Supplies { – Fixed Voltage	654	£4.08
{ – Variable Voltage	655	£4.48
Music on Hold	OCT '89 646	£3.85
Power Supplies – 25V 700mA	656	£4.35
– 30V 1A	657	£4.55
EE Seismograph – Control	658	£4.08
– Detector	659	£4.22
Lego/Logo & Spectrum	660	£6.49
Wash Pro	NOV '89 643	£3.83
Biofeedback Monitor – Front End	661	£4.52
– Processor	662	£4.56
Power Supplies – 1.5V–25V 2A	663	£4.78
Lego/Lego & Spectrum Interface	664	£5.60
EEG Electrode Impedance Meter	DEC '89 665	£3.98
Biofeedback Signal Generator	JAN '90 666	£4.08
Four-Channel Light Chaser	667	£6.70
Quick Cap Tester	FEB '90 668	£3.92
Weather Station		
Anemometer – Freq/Volt Board	670	£3.94
– Optional Display	669	£3.73
Wind Direction	673/674	£4.22
System Power Supply	675	£3.59
Prophet In-Car Ioniser	676	£3.18
EE Weather Station	MAR '90 671	£4.47
Display Driver	672 & 678	£4.22
Display & Sensor Boards	677	£4.28
Fermostat Mk2		
Superhet Broadcast Receiver	679/680	£4.22
Tuner/Audio Amp		
Stereo Noise Generator	APR '90 681	£4.24
Digital Experimenter's Unit		
Pulse Generator	682	£4.46
Power Supply	683	£3.66
Enlarger Timer	684	£4.28
EE Weather Station		
Rainfall/Sunlight Display	685	£4.27
Rainfall Sen(687)/Sunlight Sen(686)	686/687	£4.16
Amstrad Speech Synthesiser	MAY '90 689	£4.68
Quizmaster	690	£4.74

Please note it is important to give project title as well as order code.

## EE PRINTED CIRCUIT BOARD SERVICE

Please send me the following p.c.b.s.

**Order Code Project Quantity Price**

.....

.....

.....

I enclose cheque/PO for £.....

Name.....

Address.....

.....

.....

Please allow 28 days for delivery (see note above)

BLOCK CAPITALS PLEASE

# QUALITY... SECURITY SUPPLIES

FOR  
DIY &  
TRADE

...AT LOWEST PRICES

## CONTROL UNITS

- Automatic
- Modular
- Lighting
- Timer

## SENSORS

- Passive Infra-Red
- Ultrasonic
- Infra-Red Beam

## ACCESSORIES

- Contacts
- Pressure Pads
- Security Lighting
- Cable Etc. Etc.

CARS &  
VANS

HOMES &  
FACTORIES

## PRODUCT OF THE MONTH

### CPU 9000 SELF-CONTAINED ALARM

**SYSTEM** Immediate Security Without Installation  
For homes storerooms, clubhouses, caravans etc...

- Detects intruders up to 30ft
- Penetrating 103db Siren with auto reset.
- Compact size only 203x180x78mm.
- Easily extended for coverage of additional rooms or large areas.
- Operates from 240V ac and 12V dc. Priced **£67.72 +VAT**



TELEPHONE  
OR SEND FOR  
FREE  
LITERATURE  
TODAY


## The Security Specialist RISCOMP LIMITED

Dept. EE5, 51 Poppy Road,  
Princes Risborough, Bucks.  
HP17 9DB

Callers by Appointment  
Office hours Mon-Fri  
9am-5pm



(084 44) 6326

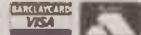

## electronize Car Electronics

### MICRO-PRESSURE CAR ALARM

This new type of alarm is triggered by a unique pressure sensing system. As any vehicle door is opened, air is drawn out, causing a minute drop in air pressure. A sensor detects this sudden pressure change and sets off the alarm.

A sophisticated arrangement of electronic filters and timers provide features to match ultra-sonic systems but at a fraction of the cost.

- ★ 1 Micro-Pressure intruder detection.
- ★ 2 Operates on all doors and tailgate.
- ★ 3 No door switches needed.
- ★ 4 Automatically armed 1 minute after leaving vehicle.
- ★ 5 10 second entry delay with audible warning.
- ★ 6 Sounds horn intermittently for 1 minute.
- ★ 7 Easy fitting - only 3 wires to connect - no holes to drill.
- ★ 8 Compact design can be hidden below dashboard.
- ★ 9 All solid state Power MOSFET output - no relays

MICRO-PRESSURE ALARM KIT £12.95  
ASSEMBLED READY TO FIT £18.95

### VOLT DROP CAR ALARM

Our latest alarm using the popular voltage drop method of triggering. Based on the timers of the micro-pressure alarm it offers features 4 to 9 above but relies on the existing door switch operation for triggering.

VOLT DROP ALARM KIT £11.75  
ASSEMBLED READY TO FIT £17.75

### TOTAL ENERGY DISCHARGE IGNITION

Our long established Extended CDI system retains the contacts to allow easy fitting whilst the electronics removes the adverse effects. The unique spark generating system still out performs the latest all electronic systems.

TOTAL ENERGY DISCHARGE IGNITION £18.95  
ASSEMBLED READY TO FIT £24.90


All Electronize kits include clear, easy to follow instructions, quality components and everything needed, right down to solder and heatsink compound.

Order direct (Please quote Ref. CO6 and add  
or send for more details from:- £1 post and packing per item.)

**ELECTRONIZE DESIGN** tel. 021 308 5877  
2 Hillside Road, Four Oaks, Sutton Coldfield, B74 4DQ


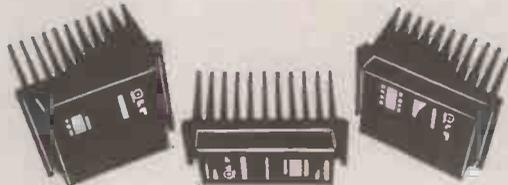
## The UK Distributor for the complete ILP Audio Range



### BIPOLAR AND MOSFET MODULES

The unique range of encapsulated amplifier modules with integral heatsink.

HY30	15W	Bipolar amp.	£11.50	HY248	120W	Bipolar amp (8ohm)	£25.20
HY60	30W	Bipolar amp	£11.50	HY364	180W	Bipolar amp (4ohm)	£39.25
HY6060	30W	Stereo Bipolar amp	£24.45	HY368	180W	Bipolar amp (8ohm)	£39.25
HY124	60W	Bipolar amp (4ohm)	£19.00	MOS128	60W	Mosfet amp	£40.70
HY128	60W	Bipolar amp (8ohm)	£19.00	MOS248	120W	Mosfet amp	£46.35
HY244	120W	Bipolar amp (4ohm)	£25.20	MOS364	180W	Mosfet amp	£75.75

### PLATE AMPLIFIERS

Bipolar and Mosfet modules with the same electronics as above amplifiers housed in a different extrusion without heatsink.

HY6060P	30W	Stereo Bipolar amp.	£20.10	HY364P	180W	Bipolar amp (4 ohm)	£25.99
HY124P	60W	Bipolar amp (4 ohm)	£14.85	HY368P	180W	Bipolar amp (8 ohm)	£25.99
HY128P	60W	Bipolar amp (8 ohm)	£14.85	MOS128P	60W	Mosfet amp.	£36.60
HY244P	120W	Bipolar amp (4 ohm)	£20.10	MOS248P	120W	Mosfet amp.	£39.95
HY248P	120W	Bipolar amp (8 ohm)	£20.10	MOS364P	180W	Mosfet amp.	£66.65

Note: These modules require additional heatsinks

### POWER SUPPLIES

Comprising toroidal transformer and DC board to power the ILP amplifier modules.

PSU30	Pre-amplifier	£10.80	PSU542	HY248	£27.40
PSU212	1 or 2 HY30	£19.25	PSU552	MOS248	£29.60
PSU412	HY6060, HY124, 1or2 HY60	£21.45	PSU712	HY244 (2)	£31.75
PSU422	HY128	£23.70	PSU722	HY248 (2)	£32.80
PSU432	MOS128	£24.75	PSU732	HY364	£32.80
PSU512	HY244, HY128 (2)	£26.35	PSU742	HY368	£34.95
PSU522	HY124 (2)	£26.35	PSU752	MOS364, MOS248 (2)	£34.95
PSU532	MOS128 (2)	£27.40			

### PRE-AMP and MIXER MODULES

These encapsulated modules are supplied with in-line connectors but require potentiometers, switches etc.


HY6	Mono pre-amp with bass and treble	£9.30
HY66	Stereo pre-amp with bass and treble	£15.50
HY83	Guitar pre-amp with special effects	£18.95
B6	Mounting board for HY6	£1.15
B66	Mounting board for HY66 or HY83	£1.75

### POWER SLAVES

These cased amplifiers are supplied assembled and tested in 60 and 120 watt Bipolar or Mosfet versions.

US12	60 watt Bipolar (4ohm)	£77.50	US32	60 watt Mosfet	£105.95
US22	120 watt Bipolar (4ohm)	£85.95	US42	120 watt Mosfet	£115.95

Prices include VAT and carriage

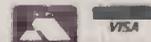

Quantity prices available on request  
Write or phone for free Data Pack

## Jaytee Electronic Services

143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL  
Telephone: (0227) 375254 Fax: 0227 365104

**AGE A & G ELECTRONICS LTD.**  
ELECTRONIC COMPONENTS MAIL ORDER COMPANY.  
Electronic components, I.C.'s, diodes, LED's, capacitors, potentiometers, solar chargers, computer disks, video tapes, aerosols, etc.  
Brand new quality components at unbeatable prices.  
1990 catalogue is out now

ACCESS (SEND £1 FOR YOUR COPY) (refundable with first order) VISA

100 Park Avenue, London E6 2SR. Tel: 01-552 2386

**WALTONS OF WOLVERHAMPTON**  
Established since 1947 - offering a complete range - I.C.s, transformers, switches, pots, capacitors, resistors, kits, speakers, test equipment, books and lots, lots more!  
COME AND SEE US AT: MON-SAT 9-6.00 pm  
55A WORCESTER STREET, WOLVERHAMPTON TEL: 0902 22039

**ELECTRONIC COMPONENTS**  
EVERYTHING FOR YOUR NEXT PROJECT  
THE BIGGEST DISPLAY IN THE SOUTH IS AT  
**FRASER ELECTRONICS**  
42 ELM GROVE ★ SOUTHSEA ★ HANTS  
Telephone 0705-815584

**NEW VHF MICROTRANSMITTER KIT**  
Tuneable 80-115 MHz, 500 metre range, sensitive electret microphone, high quality PCB, SPECIAL OFFER complete kit ONLY £5, assembled and ready to use £8.95 post free. Access/Visa orders telephone 021 411 1821 (24hrs).  
Cheques/P.O.s payable to:  
**QUANTEK ELECTRONICS LTD**  
(Dept. EE), 45a Station Road Northfield, Birmingham B31 3TE

**VISA SERVICE MANUALS**  
Available for most Video Recorders, Colour & Mono Televisions, Cameras, Test Equipment, Amateur Radio, Vintage Valve Wireless, Any Audio, Music Systems, Computers, Kitchen Appliances, etc.  
Equipment from the 1930's to the present and beyond.

Over 100,000 models stocked, originals & photostats.  
FREE Catalogue Repair & Data Guides with all orders.  
**MAURITRON TECHNICAL SERVICES (EE)**  
8 Cherry Tree Road, Chinnor, Oxfordshire OX9 4QY.  
Tel: (0844) 51694. Fax: (0844) 52554

**240V AC POWER SUPPLIES**  
LARGE STOCKS - QUANTITY DISCOUNTS  
P.S.U.'s HAVE MANY OTHER USES  
SINCLAIR PSU £9.95  
48K 9VDC 1.4 AMP - 128K 2.1 AMP QL £22.95  
BROTHER PRINTER PSU £12.95  
TYPE 'C' 6VDC 2 AMP - TYPE 'D' 8.5VDC 1 AMP OBERON £14.95  
REGULATED 12VDC 1 AMP  
EEC LTD Prices incl. VAT. Please add £2 P&P  
12 HIGH ST. WATLINGTON OXON OX4 5PS TEL 049 161 3294

**MAN ELECTRONIC SERVICES**

H52-2961	Alt Flashing Signal.....	£2.99
H52-2963	Electrifying Apparatus.....	£8.45
H52-2967	IC Radio.....	£9.45
H52-2968	Fog Horn.....	£5.95
H52-2971	Moving Light Tube.....	£28.95
H52-2976	Apple Radio.....	£8.45
H52-2982	Metal Detector.....	£5.95
H52-2988	Antenna Amp.....	£4.95
H52-2989	Speed Control.....	£18.95
H52-2994	Diode Receiver.....	£10.99
H52-2998	Lie Detector.....	£5.95
H52-3002	Electronic Dice.....	£10.95
H52-3005	Antenna Amp 30-850Mhz.....	£9.45
H52-3006	VHF Receiver.....	£10.95
H52-3021	MW Testing Transmitter.....	£4.99
H52-3022	Electronic Barking Dog.....	£13.45
H52-3033	Microwave Leak Detector.....	£6.95
H52-3112	Traffic Lights.....	£5.75
H52-3214	Test Oscillator.....	£6.75
H52-3236	Robot Voice.....	£9.49

SEND S.A.E. 9x6(24p) for catalogue. P&P per kit 60p  
**12B HIGH ST, MILDENHALL, SUFFOLK IP28 7EQ**  
Tel: 0638 713329

**REG VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY**  
1 to 24 volts up to 1/2 amp. 1 to 20 volts up to 1 amp. 1 to 16 volts up to 1 1/2 amps A.C. Fully stabilised. Twin panel meters for instant voltage and current readings. Overload protection.  
Fully variable.  
Operates from 240V AC.  
Compact Unit, size 9 x 5 1/2 x 3in.  
**£42 inc. VAT** + Post £2

**RADIO COMPONENT SPECIALISTS**  
337 WHITEHORSE ROAD, CROYDON SURREY, U.K. Tel: 081-684 1665  
List, Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

**TECHNICAL INFO SERVICES (EE)**  
76 Church St, Larkhall, Lanarkshire ML9 1HE  
Phone 0638 824585 Mon-Fri, 9-5  
any other time 0638-823334, FOR FAST QUOTES  
WORLD'S LARGEST COLLECTION SERVICE MANUALS - Most unobtainable elsewhere. Prices range from only £4.50 - large s.a.e. any quotation, no obligation to buy.  
WORLD'S SOLE Suppliers of TV & Video Repair manuals etc. from TV TECHNIC, also such publishers as Henemann, Newsas, TV Technic, Thorn etc. Every published service sheet in stock, supplied full size, not bits & pieces. CTV's or any combination £3.50 plus 1sae. any other single item £2.50 plus 1sae. Complete Circuit Sets for most Videorecorders only £7 s.a.e. (no very thin made).  
LSAE for QUOTATIONS plus GIANT CATALOGUE - NEWSLETTERS - BARGAINS - FREE S/SH as available.  
Comprehensive TV Repair Manual £3.50. Complete Radio Service and Repair Course £9.50. Complete Repair & Service Manuals - Mono TV £12.50. CIV £17.00. Video £19.50. Complete Repair Data with circuit - Mono TV £9.50. CIV £12.50. Video £10.50.  
£3.00 plus 1sae BRINGS THE ONLY COMPREHENSIVE SERVICE SHEETS & MANUALS, CATALOGUES plus FREE CHASSIS GUIDE and £4.00 OF VOUCHERS

**SINCLAIR COMPUTER SPARES**  
KEYBOARD MEMBRANES. Spectrum 48K. £2.96. 128K or + (5 Layer). £6.89. QL £6.96  
ULA's 6C001E/7C010/7K010E5 all £10.46 ea. many other parts available. Including: Case Parts, Manuals, PSU's, Modulators, Cass/Disc Drive Parts.  
WE CAN SUPPLY A VAST RANGE OF SPECIFIC SPARES for many makes of TV, Video & Audio Equipment. Also SINCLAIR, AMSTRAD & COMMODORE Computers. So whether it's a Custom Chip or maybe just a Remote Control Handset you require... GIVE US A TRY!!!  
We also stock a range of Electrical/Telephone Accs., Aerials, Tools, Batteries, Soldering Equipment and MUCH MORE for our catalogue/lists, please send a LSAE (9x6min) or 40p stamps/PO etc. MAIL ORDER ONLY. Please add 75p P&P to above orders.  
MARPET (EES) 1 Hornbeam Mews, Gloucester GL2 0UE  
TEL 0452 26883

**N. R. BARDWELL LTD**

200 - Signal diodes 1N4148.....	£1.00
100 - Rectifier diodes 1N4001.....	£1.00
100 - Zener diodes 6V8 400mW.....	£1.00
30 - Assorted DIL sockets up to 40 pin.....	£1.00
30 - Assorted Sockets/Cons. Dil, Edge, I.D.C., Header etc.....	£1.00
30 - Transistors BC478.....	£1.00
20 - Miniature SP/CO Slide switches.....	£1.00
20 - Magnetic ear pips + lead and Plug.....	£1.00
75 - Electrolytics 4.7uf 63V.....	£1.00
1 - 10watt stereo amplifier - 4 controls + data.....	£2.95

Prices include VAT, postage 60p. All items new.  
Many other lines in stock.  
Shop open Mon/Sat 9.30-5.30. Lists S.A.E.  
288 ABBEYDALE ROAD, SHEFFIELD S71 1FL  
Tel: (0742) 552886. Fax: (0742) 500689

**ROBINSWOOD "QUIZMASTER"**  
Are you new to project building?  
Why not "cut your teeth" on the Quizmaster (see Everyday Electronics issue May '90)  
Too difficult?  
Not at all! It's easy to build and fun to use. We will supply you with a kit of parts (inc case) for only £25.95 (+ £1.00 P&P)  
And, to prove how simple it really is, if you can't get your Quizmaster to work, send it back (within 30 days of purchase) and we will repair it  
FREE OF CHARGE (postage and parts extra).  
You just can't go wrong!!  
This is an opportunity not to be missed, your RISK FREE start to electronics!  
Order your Quizmaster NOW! Cheques payable to: Robinswood Electronics, 33 Cottswold Rd, Gloucester GL4 9RQ

The prepaid rate for semi-display space is £8.00 (plus VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified advertisements is 30 pence (plus VAT) per word (minimum 12 words).  
All cheques, postal orders, etc., to be made payable to Everyday Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749.

**Kits**  
KITS. Microtransmitter, VHF/FM, 14x25mm, including free microphone, £4.50. VHF/FM bleeper tracking transmitter, £7.99. Voice operated switch, £8.99. Telephone transmitter, VHF/FM, £4.99. Automatic telephone recording switch, £7.99. SAE list. ACE(EE). 99 Greenheath, Hedgesford, Staffs. Access orders 05438 71902 (24 hrs).  
G.C.S.E. ELECTRONICS KITS. Ten different £10.50 (+70p, p&p) or SAE for details. SIR-KIT ELECTRONICS, 70 Oxford Road, Clacton CO15 3TE.

**Miscellaneous**  
PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B.M.A. Circuits, 38 Poyning Drive, Sussex BN3 8GR, or phone Brighton 720203.  
FOR SALE Jackson NiCad battery chargers. Output d.c. 2-4V and 9V. £5.25 inc p&p. A.C.W. Computer Repairs, 2 Forge Cottages, High Street, Welme, Wallingford, Oxon OX10 6HQ.  
KIA AMAZING MAYDAY GIVEAWAY!! 50 ASTD Polyesters & Electrolytics FREE!! Return ad + £1 P&P to: 8 Cunliff Road, Ilkley. Reg-PSU 5/12/24V, £1.90, Poweramps 100 watt + TO3 Heatsink, £6.95.  
£1 SELECTION BAGS containing resistors, capacitors, diodes, etc. Send SAE, cash to Mr S. Berry, 6 Celtic Steet, Liverpool L8 8AJ.  
SHARP MZ80A: Integral screen, tape deck, interfaced printer, double disk drive. Offers, Mr Husbands, 34 Pleasant Street, Blackpool FY1 2HU.  
SPARES AND REPAIR. Spares, service manuals and repair service available for all makes of test equipment (scopes, DMM's, generators, PSU's, etc) at very reasonable prices. Distance no object. Hesing Technology, 41 Bushmead Road, Eaton Socon, Cambs PE19 2RW. Tel: 0480 214488/216870.

**BLACK FOX AUDIO SYSTEMS**  
18 Rugeley Road, Chase Terrace, Walsall, West Midlands WS7 8AQ  
MOSFET POWER AMPLIFIERS  
STEREO PFA25 25W + 25W in to 8 ohms..... £60.00  
STEREO PFA30 30W + 30W in to 8 ohms..... £65.00  
Modules include two regulated power supplies one for each amplifier plus AC output 15-0-15 1A variable gain heatsinks.  
PFA50 50 watts in to 8 ohms..... £25.00  
PFA140 140 watts in to 8 ohms..... £30.00  
Modules include heatsinks variable gain, voltage regulators on driver stage.  
POWER SUPPLIES AVAILABLE BUILT TO ORDER NOT MASS PRODUCED ALL HAVE 5 YEAR GUARANTEE

**B.C.E. ELECTRONICS**  
Unit 3, Chasewood Park Business Centre, Hedgesford Road, Heath Hayes, Cannock, Staffs WS12 5HL  
Electronic Components, Service aids, Test gear and much more for the electronics enthusiast.  
Lists and E.E. Kits available soon  
Mon, Tues, Wed, Fri, Sat  
10.00 - 6.00  
Closed Thursday  
(0543) 77572

## MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 9 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	TV, video & Hi-Fi Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Refrigeration & Air Conditioning	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCSE/CCE/SCE over 40 examination subjects to choose from <input type="checkbox"/>			

Name \_\_\_\_\_ Address \_\_\_\_\_

# ICS

International Correspondence Schools, Dept. ECS 90  
Telephone: 01-643 9568 or 041-221 2926 (24 hours) 312/314 High Street, Sutton, Surrey SM1 1HR.

## CAMBRIDGE COMPUTER SCIENCE LIMITED

★10MByte Winchester, used, 3 months Wty	£42.00 each
★5.25" Disk Drives, 80 Tk, DSDD	£34.00 each
★5.25" drive cases, room for drive, PSU & fan	£10.00 each
★5.25" Disk Drives, 80 Tk, DSDD Used, No Wty	£15.00 each
(The £15.00 drives are sold on a strictly "as is" basis)	
★5.25" Disks, DSDD, 48tpi boxes of 10	£3.00 box
★50W PSU 5V 6A, 12V 2.5A, -5V 0.5A, -12V 0.5A	£16.00 each
★40W PSU 5V 3.75A, 12V 1.5A, -12V 0.4A, cased with on/off switch	£10.00 each
★Gold PSU 0-30V @5A Limited quantity only at	£45.00 each
★Dual Data lead (BBC Micro to 2 Disk Drives)	£4.00 each
★Power lead (BBC Micro to Disk Drive)	£2.00 each
★Dual power lead (BBC Micro to 2 Disk Drives)	£4.00 each
★68000 CPUs (The first orders get 10MHz chips)	£3.50 each
★280A CPU, CTC, PIO £1.20 each; DMA £2.00	£4.50 all 4
★74LS TTL, pick and mix, buy 10 or more for	£0.12 each
Types available: '00 '02 '04 '08 '11 '13 '15 '20 '21 '26 '27 '30 '32 '33 '38 '42 '74 '83 '96 '107 '109 '122 '132 '136 '139 '145 '151 '153 '157 '158 '163 '164 '165 '191 '193 '298 '385 '670	
★EPROMS 27C128-25	£2.50 each
★EPROMS 27C256-25	£3.50 each
★256K Byte DRAM Modules, removed from equipment	£6.00 each
★6254 8K Byte SRAM	£12.30 each
★65256 32K Byte rams	£7.00 each
★8K Byte NV ram chips £3.00 each	£10.00 four
★Keyboard, 100 keys on board LCD & micro I/O	£8.00 each
★Toroidal mains transformer, 12V 4A & 0.4A, 12-0-12 1A & 2A, 9-0-9 2A	£4.00/1, £6.00/2, £8.00/3
★Video Tapes, £180 VHS	£2.50 each

Prices include postage. Add 50p (plus VAT) to orders below £5.00.  
All items new unless stated. Add 15% VAT to all prices. (Please note mail order only)  
Send an SAE for our latest list or for more info.  
Dept EE, 374 Milton Road, Cambridge CB4 1SU  
Tel: 0223 424602 or 0831 430496

## Professional quality Typesetting and page make-up on your own computer for just £150

Typefit is a desk top publishing program which runs on IBM PC's and compatibles. It is ideal for producing all forms of typesetting including magazines, books, catalogues, price lists, leaflets, brochures, advertisements, etc.

Typefit is now being used by major book and magazine publishers, colleges and universities, print shops, estate agents, and many small companies.

- ★ WYSIWYG system with on-screen typefaces.
- ★ Easy to learn and use.
- ★ Over 200 Typefaces.
- ★ On screen and telephone help available.

For more information ring us NOW

# Typefit

PC Page make-up Software and Typesetting Bureau

First Floor 28-30 Southampton Road, Ringwood, Hants BH24 1JD.  
Tel: (0425) 480880. Fax: (0425) 470069  
Datalinx Box ANTONY  
Document Exchange 45711 RINGWOOD

'Everyday Electronics' is produced entirely on Typefit



NATIONAL COLLEGE OF TECHNOLOGY

## PACKAGED SHORT COURSES

The National College of Technology (NCT Ltd) offers a range of packaged short courses in analogue electronics, digital electronics and fibres & optoelectronics for study at home or at work. The advantages are that you may,

- commence at any time
- work at your own pace
- have a tutor (optional)

and there is no travelling involved. BTEC certificates are available subject to the conditions of the award. These highly popular packed courses contain workbooks, a cassette tape, circuit board and components necessary to provide both theoretical and practical training.

Whether you are a newcomer to electronics or have some experience and simply need updating, there is probably a packaged short course ready for you. Write or telephone for details, quoting Everyday Electronics, to:

**NCT Ltd, Bicester Hall,  
5 London Road, Bicester  
Oxon OX6 7BU**

or telephone (0296) 613067 Ext. 202

Carbon Film resistors 1/4W 5% E24 series 0.51R to 10MΩ	1p
100 off per value—75p, even hundreds per value totalling 1000	£6.00p
Metal Film resistors 1/4W 10R to 1MΩ 5% E12 series—2p, 1% E24 series	3p
Mixed metal/carbon film resistors 1/2W E24 series 1R0 to 10MΩ	11/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 4M7 E6 series	7p
<b>Miniature polyester capacitors 250V working for vertical mounting</b>	
.015, .022, .033, .047, .068-4p, 0.1-5p, 0.12, 0.15, 0.22-6p, 0.47-8p, 0.68-8p, 1.0-12p	
<b>Mylar (polyester) capacitors 100V working E12 series vertical mounting</b>	
1000p to 8200p - 3p, .01 to .068 - 4p, 0.1 - 5p, 0.12, 0.15, 0.22-6p, 0.47/50V-8p	
<b>Submin ceramic plate capacitors 100V wkg vertical mountings, E12 series</b>	
2% 1.8pf to 47pf - 3p, 2% 56 pf to 330pf - 4p, 10% 390p - 4700p	4p
Disc/plate ceramics 50V E12 series 1P0 to 1000P, E6 Series 1500P to 47000P	2p
<b>Polystyrene capacitors 63V working E12 series long axial wires</b>	
10pf to 820pf - 3p, 1000 pf to 10,000pf - 4p, 12,000 pf	5p
741 Op Amp - 20p, 555 Timer	22p
cmos 4001 - 20p, 4011 - 22p, 4017	40p
<b>ALUMINIUM ELECTROLYTICS (Mfds/Volts)</b>	
1/50, 2, 2/50, 4, 7/50, 10/25, 10/50	5p
22/16, 22/25, 22/50, 47/16, 47/25, 47/50	6p
100/16, 100/25 7p; 100/50 12p; 100/100	14p
220/16 8p; 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
<b>Submin, tantalum bead electrolytics (Mfds/Volts)</b>	
0.1/35, 0.22/35, 0.47/35, 1.0/35, 3.3/16, 4.7/16	14p
2.2/35, 4.7/25, 4.7/35, 6.8/16 15p; 10/16, 22/6	20p
33/10, 47/6, 22/16 30p; 47/10 35p; 47/16 60p; 47/35	80p
<b>VOLTAGE REGULATORS</b>	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V	55p
<b>DIODES (piv/amps)</b>	
75/25mA 1N4148 2p, 800/1A 1N4006 6p, 400/3A 1N5404 14p, 115/15mA OA91	6p
100/1A 1N4002 4p, 1000/1A 1N4007 7p, 60/1.5A S1M1 5p, 100/1A bridge	25p
400/1A 1N 4004 5p, 1250/1A BY127 10p, 30/1.5A OA47	8p
Zener diodes E24 series 3V3 to 33V 400 mW - 8p, 1 watt	12p
Battery snaps for PP3 - 6p for PP9	12p
L.E.D.'s 3mm, & 5mm. Red, Green, Yellow - 10p, Grommets 3mm - 2p, 5mm	2p
Red flashing L.E.D.'s require 5V supply only	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A 0/blow 5p, A/surge 8p, Holders pc or chassis	5p
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0m - 30p, Machines 12V dc	£7.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£3.50p
AA/HP7 Nicad rechargeable cells 80p each, Universal charger unit	£6.50p
Glass reed switches with single pole make contacts - 8p, Magnets	12p
0.1" Stripboard 2 1/2" x 1" 9 rows 25 holes - 20p, 3/4" x 2 1/2" 24 rows 37 holes	60p
<b>TRANSISTORS</b>	
BC107/8/9-12p, BC547/8/9-8p, BC557/8/9-8p, BC182, 182L, BC183, 183L, BC184, 184L, BC212, 212L-10p, BC327, 337, 337L-12p, BC727, 737-12p, BD135/6/7/8/9-25p, BCY70-15p, BFY50/51/52-20p, BFY88-15p, 2N3055-50p, TIP31, 32-30p, TIP41, 42-40p, BU208A-£1.20, 8F195, 197-12p	
All prices are inclusive of VAT. Postage 25p (free over £5). Lists Free.	

## THE CR SUPPLY CO

127 Chesterfield Rd., Sheffield S8 0RN  
Tel: 0742 557771 Return posting

# OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX · 031 667 2611

## A COMPREHENSIVE RANGE WITH SERVICE SECOND TO NONE

OUR MUCH EXPANDED, BETTER ILLUSTRATED CATALOGUE WILL COST £1.50 - TO INCLUDE VOUCHERS TO USE AGAINST FUTURE PURCHASES. TO RECEIVE A COPY AS SOON AS THEY ARE READY, PLEASE SEND YOUR REMITTANCE WITH THE VOUCHER BELOW.

New 1990/1 OMNI Catalogue available soon

Please send me a copy of the 1990/91 OMNI catalogue as soon as it is ready. Payment of £1.50 enclosed.

NAME: \_\_\_\_\_  
 ADDRESS: \_\_\_\_\_  
 TELEPHONE: \_\_\_\_\_



Open: Monday-Friday 9.00-6.00  
 Saturday 9.00-5.00



## ADVERTISERS INDEX

ADVANCED ELEC. PRODUCTS	294
BARRIE ELECTRONICS	360
BK ELECTRONICS	Cover (iii)
BLACKMORE ELECTRONICS	341
BULL J & N	Cover (ii)/345
CAMBRIDGE COMP. SCIENCE	359
CIRKIT DISTRIBUTION	325
CRICKLEWOOD ELECTRONICS	335
CR SUPPLY COMPANY	359
DALBANI CORPORATION	335
ELECTRONIZE DESIGN	357
ELECTROVALUE	341
ELV FRANCE	298/299
GRANDATA	296
GREENWELD ELECTRONICS	309
HART ELECTRONIC KITS	325
HENRY'S AUDIO ELECTRONICS	341
HIGHGRADE COMPONENTS	355
HOBBYKIT	349
ICS	359
JAYTEE ELECTRONIC SERVICES	357
LONDON ELECTRONICS COLLEGE	360
MAGENTA ELECTRONICS	300/301
MAPLIN ELECTRONICS	Cover (iv)
MARCO TRADING	297
NATIONAL COLLEGE OF TECH	359
OMNI ELECTRONICS	360
RADIO & TV COMPONENTS	321
RISCOMP	357
SERVICE TRADING CO.	349
SHERWOOD ELEC. COMP.	360
SPECIALIST SEMICONDUCTORS	327
SUMA DESIGNS	349
TK ELECTRONICS	302
TYPEFIT	359

## BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

**2 YEAR BTEC National Diploma (OND) ELECTRONIC & COMMUNICATIONS ENGINEERING**  
 (Electronics, Computing, Television, Video, Testing & Fault Diagnosis)

**1 YEAR BTEC National Certificate (ONC) ELECTRONIC ENGINEERING 1-INFORMATION TECHNOLOGY**  
 (Electronics, Satellite TV, Networks, Telecomms)

**2-ELECTRONIC EQUIPMENT SERVICING**  
 (Electronics, Television, Video Cassette Recorders, CCTV, Testing and Fault Diagnosis)

**3-SOFTWARE ENGINEERING**  
 (Electronics, Assembler, BASIC, Pascal, CAD/CAM)

**4-COMPUTING TECHNOLOGY**  
 (Electronics, Computing Software/Hardware, Microelectronics)

**10 MONTHS BTEC Higher National Certificate (HNC) COMPUTING TECHNOLOGY & ROBOTICS**  
 (Microprocessor Based Systems, Control, Robotics)

These courses include a high percentage of college based practical work to enhance future employment prospects. No additional fees for overseas students. Shortened courses of from 3 to 6 months can be arranged for applicants with previous electronics knowledge.

THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME

**O.N.C. and O.N.D. Next Course Commences Monday 17th September 1990 FULL PROSPECTUS FROM**

**LONDON ELECTRONICS COLLEGE (Dept. EE), 20 PENYWERN ROAD EARLS COURT, LONDON SW5 9SU Tel: 01-373 8721**

## TRANSFORMERS EX STOCK

<b>MAINS ISOLATORS</b> Pri 120V x 2 or 220/240V or 415/440V. Sec 440 or 240V or 110V Centre Tapped				<b>30/15V or 15-0-15V</b> 2x 15V Tapped Secs. Volts available: 3, 4, 5, 6, 8, 9, 10, 15, 18, 20, 27, 30V or 15-0-15V				<b>60/30V or 30-0-30V</b> 2x 30V Tapped Secs Volts available: 16, 18, 36, 40, 60V or 24-0-24 or 30-0-30V												
20 VA	£8.33	2.51	0.5	1	4.55	1.81	0.5	1	6.72	2.09	60V	30V	£	P&P						
60	13.60	2.70	1	2	6.19	1.98	1	2	10.25	2.21	2	A	4	13.17	2.53					
100	15.87	P 2.92	2	A	10.01	2.20	2	A	13.17	2.53	3	M	6	19.05	2.64					
200	22.49	& 3.52	3	M	11.60	2.42	4	P	8	21.72	2.75	5	S	10	27.46	3.19				
250	29.20	P 3.62	4	P	8	13.84	2.53	6	12	31.32	3.41	6	12	19.41	2.92	6	12	31.32	3.41	
500	41.91	4.24	5	S	10	17.72	2.74	5	S	10	27.46	3.19	8	16	25.94	3.02	8	16	44.04	3.93
1000	76.01	5.33	6	12	19.41	2.92	6	12	31.32	3.41	10	20	29.94	3.24	10	20	51.28	4.40		
1500	98.04	6.54	8	16	25.94	3.02	8	16	44.04	3.93	12	24	34.82	3.35	12	24	59.09	5.22		
2000	117.96	7.64	10	20	29.94	3.24	10	20	51.28	4.40	<b>96/48V or 48-0-48V</b> 2x 0-36-48V Secs to give 60, 72, 84, 96V, or 36-0-36V or 48-0-48V.									
3000	165.41	O/A	12	24	34.82	3.35	12	24	59.09	5.22	96V	48/36V	£	P&P						
6000 VA	353.43	D/A	15	30	37.43	4.01	15	30	41.10	5.54	0.5	1	£7.16	1.76						
			20	40	51.10	6.54	20	40	51.10	6.54	1	2	12.80	2.31						

<b>24/12V or 12-0-12V</b> 2x 12V Secs				<b>50/25V or 25-0-25V</b> 2x 25V Tapped Secs to give 7, 8, 10, 13, 17, 20, 25, 33, 40, 50V or 20-0-20V or 25-0-25V				<b>TOOL TRANSFORMERS</b> 2KVA £71+£5.33					
24V	12V	£	P&P	50V	25V	£	P&P	<b>CONSTANT VOLTAGE TRANSFORMERS</b> For Spike-free Stable Mains					
0.15	0.3	3.44	1.87	0.5	1	5.91	2.09	<b>INVERTERS</b> 12/24V DC to 240V AC Square or Sine Wave					
0.25	0.5	3.64	1.90	1	2	7.19	2.21	<b>TRANSFORMERS WOUND TO SPEC</b> Batch Winding 3VA to 15KVA					
0.5	1	4.36	1.98	2	A	12.81	2.75	<b>TOROIDALS</b> Batches Wound to Order 30VA to 4KVA					
1	2	6.08	2.09	3	M	14.82	2.92	<b>AVO's &amp; MEGGERS</b> Full range available					
2	A	4	7.01	2.20	4	P	8	20.30	3.24	<b>Also Valve Mains &amp; Output Transformers</b>			
3	M	6	12.08	2.36	6	S	12	25.81	3.41	Please add 15% V.A.T. to all items after P&P Send SAE for Lists			
4	P	8	12.87	2.42	8	16	36.52	4.12					
6	S	12	15.62	2.64	10	20	43.34	4.41					
8	16	18.59	3.08	12	24	51.87	5.22						
10	20	25.02	3.52										
15	30	31.10	3.63										
20	40	44.40	4.12										
30	60	63.75	4.89										
41	83	73.41	6.32										

PO BOX 70, ILFORD ESSEX, IG5 0AP  
**BARRIE ELECTRONICS LTD**  
 TELEPHONE: 01-551 8454

## SHERWOOD ELECTRONIC COMPONENTS 45 Rutland Street, Mansfield, Notts NG18 4AP SPECIAL PACKS — All at £1.00 each

SP1 12x5mm Red LEDs	SP32 4xCmos 4077
SP2 12x5mm Green LEDs	SP33 4xCmos 4081
SP3 12x5mm Yellow LEDs	SP34 2xCmos 4510
SP4 10x5mm Amber LEDs	SP35 2xCmos 4511
SP5 36x6mm 1 part LED clips	SP36 20x10µF/25V Rad.Elec.Caps.
SP6 12x3mm Red LEDs	SP37 15x10µF/35V Rad.Elec.Caps.
SP7 12x3mm Green LEDs	SP38 20x47µF/25V Rad.Elec.Caps.
SP8 10x3mm Yellow LEDs	SP39 12x47µF/16V Rad.Elec.Caps.
SP9 40x3mm 1 part LED clips	SP40 15xBC237 Transistors
SP10 50x1N4148 signal diodes	SP41 25xmixed Transistors
SP11 25x1N4001 rectifier diodes	SP42 2xLM1458
SP12 25x1N4002 rectifier diodes	SP43 12x5mm Led's 4 each, Red, Green Yellow
SP13 25xRad.Elec.Caps. (1-1000µF)	SP44 25x1N4000 series rect. diodes
SP18 15xBC182 Transistors	SP45 16x400mW zeners — assorted values
SP19 15xBC183 Transistors	SP47 5xminiature push button switches
SP20 15xBC184 Transistors	SP101 15 metres of 22SWG 60-40 solder
SP21 15xBC212 Transistors	SP102 15x8 pin DIL sockets
SP22 15xBC214 Transistors	SP103 12x14 pin DIL sockets
SP23 15xBC549 Transistors	SP104 12x16 pin DIL sockets
SP24 5xCmos 4001	SP105 5x74L50 I.C.s
SP25 5x555 Timer	SP106 5x74LS02 I.C.s
SP26 5x741 Op-Amp	SP107 20xmixed presets — Hor. + Vertical
SP27 5xCmos 4002	SP108 15xBC382 Transistors
SP28 5xCmos 4011	SP109 15xBC557 Transistors
SP29 3xCmos 4013	SP110 4x74LS13 I.C.s
SP30 5xCmos 4025	
SP31 4xCmos 4071	

1 pack of your choice FREE when you buy any 10 of the above £1.00 packs.

<b>ADDITIONAL PACKS</b>		<b>RESISTOR PACKS</b>	
SP50 25x5mm Red LEDs	£2.00	0.25W Carbon Film resistors 10R-10M	
SP51 25x5mm Green LEDs	£2.00	5 each value — total 365	£2.75
SP52 50xRad. Elec. Caps.	£1.95	10 each value — total 730	£4.50
SP53 30xDIL sockets 8, 14, 16	£2.00	1000 popular values	£6.00
SP54 1xTIL38+1xTIL100	£1.80	Individual resistors	2p ea.
SP57 100x1N4148 diodes	£1.75	10+ one value	1p ea.
SP65 60x3mm+5mm Led's	£4.80	100 one value	75p

<b>CMOS</b>		<b>I.C.s</b>		<b>V. REGS.</b>	
4000 25p	4070 27p	555	22p	78L05	25p
4001 25p	4071 27p	556	75p	78L12	25p
4002 25p	4072 27p	741	22p	78L15	26p
4001 25p	4073 27p	747	70p	78L05	30p
4012 27p	4075 27p	CA3140E	45p	79L12	30p
4013 38p	4077 32p	CA3240E	£1.25	7815	36p
4017 55p	4081 27p	LM339	55p	79L05	30p
4023 30p	4093 27p	LM380-14	£1.25	79L12	30p
4025 25p	4510 65p	LM723	60p	7805	35p
4027 50p	4511 65p	LM1458	55p	7815	36p
4040 70p	4514 £1.25	TL071	60p	7905	36p
4047 65p	4515 £1.30	TL072	60p	7815	36p
4049 40p	4516 65p	TL081	40p	7912	35p
4066 40p	4528 70p	TL082	55p	7915	38p

Cheques or P.O. to: **SHERWOOD ELECTRONIC COMPONENTS**  
 Please add £1 P&P to orders under £20.00

This only a small sample of components stocked, send 75p for new 1990 catalogue, contains vouchers redeemable against orders over £5.00. NO VAT



**POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS**

**OMP POWER AMPLIFIER MODULES**

Supplied ready built and tested.

**OMP POWER AMPLIFIER MODULES** Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, integral heat sink, Glass fibre P.C.B. and Drive circuits to power compatible Vu meter. Open and short circuit proof.

**THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS**



**OMP100 Mk 11 Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz - 3dB, T.H.D. 0.01%, S.N.R. - 118dB, Sens. for Max. output 500mV at 10K, Size 355 x 115x65mm. PRICE £33.99 + £3.00 P&P.**

**NEW SERIES II MOS-FET MODULES**

**OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. - 125dB. Size 300 x 123 x 60mm. PRICE £39.99 + £3.00 P&P.**

**OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. - 130dB. Size 300 x 155 x 100mm. PRICE £62.99 + £3.50 P&P.**

**OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz - 3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. - 130dB. Size 300 x 175 x 100mm. PRICE £79.99 + £4.50 P&P.**

NOTE.— MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS, STANDARD — INPUT SENS. 500mV BAND WIDTH 100KHz, PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) — INPUT SENS. 775mV, BAND WIDTH 50KHz, ORDER STANDARD OR PEC



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. PRICE £8.50 + 50p P&P.

**LOUDSPEAKERS**



**LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE S.A.E. (30p STAMPED) FOR COMPLETE LIST.**

**McKENZIE:— INSTRUMENTS, P.A., DISCO, ETC.**

- ALL MCKENZIE UNITS 8 OHMS IMPEDENCE**
- 8" 100 WATT C8100GPM GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID. DISCO. RES, FREQ. 80Hz. FREQ. RESP. TO 14KHz. SENS. 99dB. PRICE £29.30 + £2.00 P&P
  - 10" 100 WATT C10100GP GUITAR, VOICE, ORGAN, KEYBOARD, DISCO, EXCELLENT MID. RES, FREQ. 70Hz. FREQ. RESP. TO 6KHz. SENS. 100dB. PRICE £35.58 + £2.50 P&P
  - 10" 200 WATT C10200GP GUITAR, KEYBOARD, DISCO, EXCELLENT HIGH POWER MID. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 103dB. PRICE £48.67 + £2.50 P&P
  - 12" 100 WATT C12100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 7KHz. SENS. 98dB. PRICE £37.59 + £3.50 P&P
  - 12" 100 WATT C12100TC TWIN CONE) HIGH POWER WIDE RESPONSE. P.A., VOICE, DISCO. RES, FREQ. 45Hz. FREQ. RESP. TO 14KHz. SENS. 100dB. PRICE £38.58 + £3.50 P&P
  - 12" 200 WATT C12200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 100dB. PRICE £65.79 + £3.50 P&P
  - 12" 300 WATT C12300GP HIGH POWER BASS LEAD GUITAR, KEYBOARDS, DISCO, ETC. RES, FREQ. 45Hz. FREQ. RESP. TO 5KHz. SENS. 100dB. PRICE £87.51 + £3.50 P&P
  - 15" 100 WATT C15100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 98dB. PRICE £55.05 + £4.00 P&P
  - 15" 200 WATT C15200BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. PRICE £75.10 + £4.00 P&P
  - 15" 250 WATT C15250BS VERY HIGH POWER BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 99dB. PRICE £82.54 + £4.50 P&P
  - 15" 400 WATT C15400BS VERY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 40Hz. FREQ. RESP. TO 4KHz. SENS. 102dB. PRICE £96.47 + £4.50 P&P
  - 18" 400 WATT C18400BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. RES, FREQ. 27Hz. FREQ. RESP. TO 3KHz. SENS. 99dB. PRICE £172.06 + £5.00 P&P

**EARBENDERS:— HI-FI, STUDIO, IN-CAR, ETC.**

- ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)**
- SURROUND**
- 8" 50 WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 7KHz. SENS. 97dB. PRICE £8.90 + £2.00 P&P
  - 10" 50 WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. RES, FREQ. 40Hz. FREQ. RESP. TO 5KHz. SENS. 99dB. PRICE £12.00 + £2.50 P&P
  - 10" 100 WATT EB10-100 BASS, HI-FI, STUDIO. RES, FREQ. 35Hz. FREQ. RESP. TO 3KHz. SENS. 96dB. PRICE £27.76 + £3.50 P&P
  - 12" 60 WATT EB12-60 BASS, HI-FI, STUDIO. RES, FREQ. 28Hz. FREQ. RESP. TO 3KHz. SENS. 92dB. PRICE £21.00 + £3.00 P&P
  - 12" 100 WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. RES, FREQ. 26Hz. FREQ. RESP. TO 3KHz. SENS. 93dB. PRICE £38.75 + £3.50 P&P
- FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
- 5 1/4" 60 WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 63Hz. FREQ. RESP. TO 20KHz. SENS. 92dB. PRICE £9.99 + £1.50 P&P
  - 6 1/2" 60 WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 38Hz. FREQ. RESP. TO 20KHz. SENS. 94dB. PRICE £10.99 + £1.50 P&P
  - 8" 60 WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 40Hz. FREQ. RESP. TO 18KHz. SENS. 89dB. PRICE £12.99 + £1.50 P&P
  - 10" 60 WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. RES, FREQ. 35Hz. FREQ. RESP. TO 12KHz. SENS. 86dB. PRICE £16.49 + £2.00 P&P

**TRANSMITTER HOBBY KITS**

**PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS**

**3W FM TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP, PRICE £14.49 + £1.00 P&P**

**FM MICRO TRANSMITTER (BUG) 100-108MHz VARICAP TUNED COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATT, PRICE £8.82 + £1.00 P&P**



3 watt FM Transmitter



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS WELCOME FROM SCHOOLS, COLLEGES, GOVT. BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA ACCESS ACCEPTED BY POST, PHONE OR FAX.



\* PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE S.A.E., 30p STAMPED FOR CURRENT LIST.

**OMP VARISPEED TURNTABLE CHASSIS**



\* MANUAL ARM \* STEEL CHASSIS \* ELECTRONIC SPEED CONTROL 33 & 45 \* VARI PITCH CONTROL \* HIGH TORQUE SERVO DRIVEN DC MOTOR \* TRANSIT SCREWS \* 12" DIE CAST PLATTER \* NEON STROBE \* CALIBRATED BAL WEIGHT \* REMOVABLE HEAD SHELL \* 1/2" CARTRIDGE FIXINGS \* CUE LEVER \* POWER 220/240V 50/60Hz \* 390x305mm \* SUPPLIED WITH MOUNTING CUT-OUT TEMPLATE.

PRICE £59.99 + £3.50 P&P.

**OPTIONAL MAGNETIC CARTRIDGES**

STANTON AL500  
PRICE £16.99 + 50p P&P

GOLDRING G850  
PRICE £6.99 + 50p P&P

**OMP MOS-FET POWER AMPLIFIERS, HIGH POWER, TWO CHANNEL 19 INCH RACK**

**THOUSANDS PURCHASED BY PROFESSIONAL USERS**



**NEW MXF SERIES OF POWER AMPLIFIERS**

THREE MODELS:— MXF200 (100w + 100w) MXF400 (200w + 200w) MXF600 (300w + 300w)

All power ratings R.M.S. into 4 ohms.

**FEATURES:** \* Independent power supplies with two Toroidal Transformers \* Twin L.E.D. Vu meters \* Rotary indexed level controls \* Illuminated on/off switch \* XLR connectors \* Standard 775mV inputs \* Open and short circuit proof \* Latest Mos-Fets for stress free power delivery into virtually any load \* High slew rate \* Very low distortion \* Aluminium cases \* MXF600 Fan Cooled with D.C. Loudspeaker and Thermal Protection.

**USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.**

**SIZES:—** MXF 200 W19" x H3 1/2" (2U) x D11" MXF 400 W19" x H5 1/2" (3U) x D12" MXF 600 W19" x H5 1/2" (3U) x D13"

MXF200 £171.35

MXF400 £228.85

MXF600 £322.00

SECURICOR DELIVERY £12.00 EACH

**OMP LINNET LOUDSPEAKERS**

THE VERY BEST IN QUALITY AND VALUE



MADE ESPECIALLY TO SUIT TODAY'S NEED FOR COMPACTNESS WITH HIGH OUTPUT SOUND LEVELS. FINISHED IN HARDWEARING BLACK VINYL WITH PROTECTIVE CORNERS, GRILLE AND CARRYING HANDLE. INCORPORATES 12" DRIVER PLUS HIGH FREQ. HORN FOR FULL FREQ. RANGE: 45Hz-20KHz BOTH MODELS 8 OHM, SIZE H18" x W15" x D12"

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET

OMP 12-100 (100W 100dB) PRICE £159.99 PER PAIR

OMP 12-200 (200W 102dB) PRICE £209.99 PER PAIR

SECURICOR DEL.— £12.00 PER PAIR

**IN CAR STEREO BOOSTER AMPLIFIER**



**TWO SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS**

150 WATTS (75+75) INTO 4 OHMS

300 WATTS (150+150) INTO 4 OHMS

FEATURES:—

\* HIGH & LOW INPUT IMPEDANCES

\* HIGH & LOW INPUT SENSITIVITIES

\* VARIABLE INPUT GAIN CONTROL

\* SHORT CIRCUIT OUTPUT PROTECTION

\* POWER REQUIREMENT 12V. D.C.


PRICES: 150 WATT £43.00

300 WATT £95.00 + £3.00 P&P EACH

**PIEZO ELECTRIC TWEETERS-MOTOROLA**

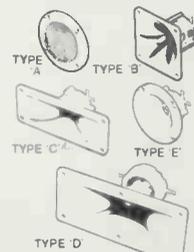**PIEZO ELECTRIC TWEETERS — MOTOROLA**

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 each + 50p P&P.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 50p P&P.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £6.99 each + 50p P&P.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 each + 50p P&P.

TYPE 'E' (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 each + 50p P&P.

LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £3.99 + 50p P&P.

**STEREO DISCO MIXER**

**STEREO DISCO MIXER** with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features 5 inputs with individual faders providing a useful combination of the following:—

3 Turntables (Mag). 3 Mics. 4 Line including CD plus Mic with talk over switch Headphone Monitor. Pan Pot L & R. Master Output controls. Output 775mV. Size 360x280x90mm. Supply 220-240v.

Price £134.99 — £4.00 P&P



**B. K. ELECTRONICS** Dept EE

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR

TEL: 0702-527572 FAX: 0702-420243

# Double Tops

DUAL BAND VHF (45W)/UHF (35W)

FM MOBILE TRANSCIEVER

When only the best is good enough – and

you still want something better . . .

- ★ Cross Band Full Duplex
- ★ 4 Scanning Modes
- ★ 10 Function Memory Channels
- ★ Highly Visible Colour LCD Display
- ★ Illuminated Front Panel Controls
- ★ 5 Channel Spacing Steps
- ★ Built-in Duplexer
- ★ Function Keys have Unique Audible Tone
- ★ Bell Function
- ★ Compact & Lightweight

#### Accessories Included:

- ★ Hand-held microphone
- ★ Mobile mounting bracket
- ★ Mounting hardware
- ★ Power cable



**ALINCO**  
from MAPLIN  
the authorised  
distributor

This very high quality 2m/70cm FM dual band mobile transceiver has been specially designed to provide maximum performance and operating convenience in an ultra compact package. An impressive array of features gives maximum flexibility in mobile installations. The transceiver has an output power of 45W (VHF) 35W (UHF) and incorporates a high/low power switch. The unit is provided with 10 programmable memories. Channel spacing is in 5, 10, 12.5, 20 and 25kHz steps. There are four scanning modes:

1. VFO scanning of the entire band.
2. Memory scanning of selected memories.
3. Programmed band scanning of a selected segment of the band.
4. Priority scanning allows selection of a frequency, in VFO or memory, to serve as a priority frequency.

A duplexer is built-in so that when an antenna for both bands is in use, only one feeder cable for the transceiver is necessary.

The unit is supplied with a comprehensive instruction manual. It is illegal to transmit with this unit unless you hold a Radio Amateur's Class B (or A) licence.


Quote Reference DBT20 **£499.95**

#### VHF/UHF FM Dual Band Handheld Transceiver

- ★ 6W VHF/5W UHF Output Power (with optional 12V battery pack)
- ★ Cross Band Full Duplex Operation
- ★ Frequency selection by Direct Keyboard Entry or Step Up/Step Down
- ★ Automatic Battery Save Function
- ★ 20 Memory Channels
- ★ Built-in DTMF Keypad and Encoder
- ★ Amazing Compact Size Only 3×6×19 cm approx.

This unit is very compact and is one of the smallest dual band transceivers currently available. With the battery pack supplied output power is 2.5W for VHF and 2W for UHF. Frequency selection is either by direct keypad entry of the required frequency or by using step up/step down buttons in increments/decrements of 5kHz, 100kHz and 1MHz. An automatic battery save (ABS) function will extend battery life considerably. There are 20 memories (10 VHF and 10 UHF) for storing operating, offset and tone frequencies. The scanning facility has a priority function which has the ability to scan between chosen VHF and UHF frequencies. A 10dB RF attenuator is switch selectable and can be used in areas of high RF saturation.

Quote Reference DHT20 **£369.95**

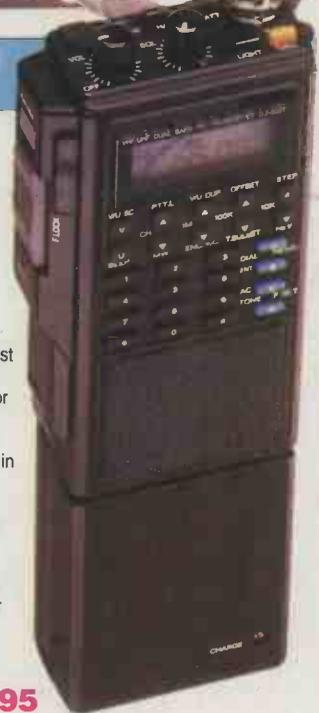

#### PLUS TOP VALUE AMATEUR RADIO VHF FM Handheld 2m Transceiver

- ★ Ultra compact, lightweight design
- ★ 6.5W Output Power (with optional 12V battery pack)
- ★ Simple Operation
- ★ Easy to See LCD Display
- ★ 10 Channel Memories
- ★ Battery Save
- ★ Function Lock
- ★ Tone Burst
- ★ Amazing Compact Size Only 3×6×17 cm approx.


A very high quality, lightweight, 2m handheld transceiver, incorporating many useful features. This transceiver is extremely simple to operate, most functions can be performed with one hand!

Quote Reference AHT20 **£219.95**
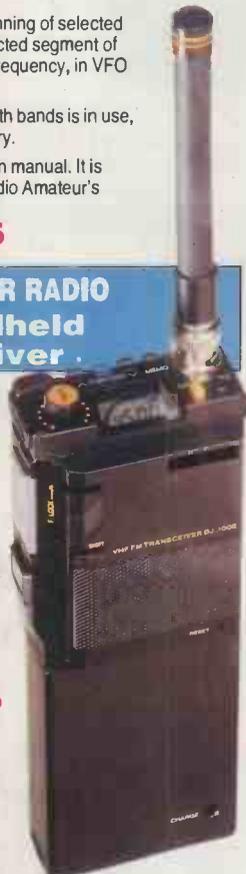
#### 12V Ni-Cad Battery Pack

For use with either above hand-held transceivers. A 12V 700mAh battery pack with integral DC-DC converter which allows the transceiver to be powered from a car cigarette lighter socket.

A charger is also available for use with this pack. Battery Pack NBP20 **£59.95** Charger NBC20 **£14.95**



**Maplin** ELECTRONICS

P.O. Box 3, Rayleigh, Essex SS6 8LR.

**CREDIT CARD HOTLINE**

**0702 554161**



**PHONE BEFORE 5PM FOR SAME DAY DESPATCH**

or call in at a Maplin store in Birmingham, Bristol, Leeds, Hammersmith, Edgware, Manchester, Nottingham, Newcastle-upon-Tyne, Reading, Southampton and Southend-on-Sea.

Add 75p for carriage on all mail orders. If only ordering a catalogue, just add 50p carriage.

Subject to availability. Prices may change after May 1st 1990.

**SEE THE COMPLETE RANGE OF TRANSCIEVERS AND LOTS MORE IN OUR BUMPER 580-PAGE CATALOGUE ON SALE NOW AT ALL BRANCHES OF WHSMITH – PRICE £2.25!**