

EVERYDAY

MAY 1996


PRACTICAL

ELECTRONICS

FULLY S.O.R. £2.45

MIDI ANALYSER

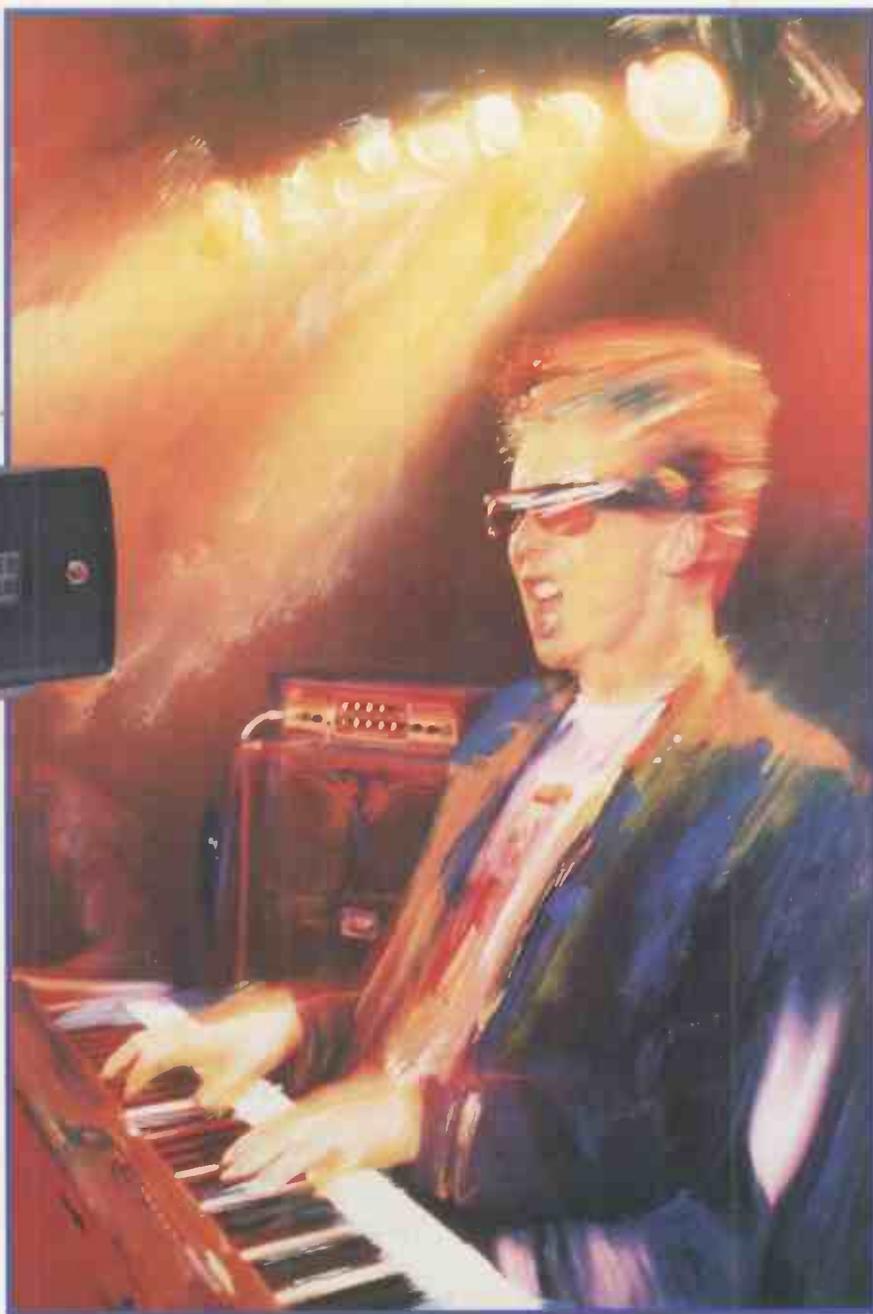'See' the commands coming from your MIDI instrument - note value, octave number, key velocity, etc.



PIR DETECTOR

Protect your property, indoors or out

COUNTDOWN TIMER

Versatile l.e.d. readout timer - a Teach-In '96 project

The history and present day uses of

CATHODE RAY TUBES

INGENUITY

UNLIMITED

Readers' Circuit Ideas

**THE NO. 1 INDEPENDENT
MAGAZINE FOR
ELECTRONICS TECHNOLOGY
& COMPUTER PROJECTS**



SURVEILLANCE TELESCOPE Superb Russian zoom telescope adjustable from 15x to 60x! complete with metal tripod (impossible to use without this on the higher settings) 66mm lens, leather carrying case £149 ref BAR69

RADIATION DETECTOR SYSTEM Designed to be wall mounted and connected into a PC, ideal for remote monitoring, whole building coverage etc. Complete with detector, cable and software. £19.95 ref BAR75.

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4" long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours use. £99 REF EP79. (probably not licensable!)

CCTV CAMERA MODULES 46X70X29mm, 30 grams, 12v 100mA. auto electronic shutter, 3.6mm F2 lens, CCIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EF137.

IR LAMP KIT Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EF138.

REMOTE CONTROL AND DATA TD1400 MODEM/VIEWDATA Complete system comprising 1200/75 modem, auto dialler, infra red remote keyboard, (could be adapted for PC use?) psu, UHF and RGB output, phone lead, RS232 output, composite output. Absolute bargain for parts alone! £9.95 ref BAR33.

9 WATT CHIEFTAN TANK LASERS

Double beam units designed to fit in the gun barrel of a tank, each unit has two semi conductor lasers and motor drive units for alignment, 7 mile range, full circuit diagrams, new price £50,000? us? £349. Each unit has two gallium Arsenide Injection lasers, 1 x 9 watt, 1 x 3 watt, 900nm wavelength, 28vdc, 600hz pulse frequency. The units also contain an electronic receiver to detect reflected signals from targets, five or more units £299 ea, £349 for one. Ref LOT4.

TWO WAY MIRROR KIT Includes special adhesive film to make two way mirror(s) up to 60"x20". (glass not included) Includes full instructions. £12 ref TW1.

NEW HIGH POWER RF TRANSMITTERS

AMPLIFIERS Assembled PCB transmitters, 4 types available, 12.6vdc 90 watt 1.5-30mhz 75 ohm in/out FM/AM £75 ref RF1 12.6vdc 40 watt 50-200mhz 50 ohm in/out FM/AM £65 ref RF2 28vdc 125 watt 1.5-30mhz 75 ohm in/out FM/AM £85 ref RF3 28vdc 100 watt 50-200mhz 50 ohm in/out FM/AM £75 ref RF4 A heat sink will be required, nng for price and availability. If you intend using these as audio transmitters you will need a also need a preamp. Complex module available at £40 ref RF5.

COMPUTER/WORKSHOP/HIFI PCB UNITS Complete protection from faulty equipment for every body! Inline unit fits in standard IEC lead (extends it by 750mm), fitted in less than 10 seconds, reset/test button, 10A rating. £9 each ref MM5.

RADIO CONTROLLED CARS FROM £6 EACH!!!!

All returns from famous manufacturer, 3 types available, single channel (left, right, forwards, backwards) £6 ref LOT1. Two channel with more features £12 ref LOT2. Two channel proportional (plug in crystals etc) £35 ref LOT3.

THOUSANDS AVAILABLE RING/FAX FOR DETAILS!

MAGNETIC CARD READERS (Swipes) £9.95 Cased with flyleads, designed to read standard credit cards! they have 3 wires coming out of the head so they may write as well? complete with control electronics PCB. just £9.95 ref BAR31

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is the certificate enabling you to reproduce (and sell) the manuals as much as you like! £14 ref EP74

PANORAMIC CAMERA OFFER Takes double width photographs using standard 35mm film. Use in horizontal or vertical mode. Complete with strap £7.99 ref BAR1

COIN OPERATED TIMER KIT Complete with coin slot mechanism, adjustable time delay, relay output, put a coin slot on anything you like! TV's, videos, fridges, drinks cupboards, HIFI, takes 50p's and £1 coins, DC operated, price just £7.99 ref BAR27.

ZENITH 900 X MAGNIFICATION MICROSCOPE Zoom, metal construction, built in light, shrimp farm, group viewing screen, lots of accessories. £29 ref ANAYLT.

AA NICAD PACK Pack of 4 tagged AA nicads £2.99 ref BAR34

PLASMA SCREENS 22x310mm, no data hence £4.99 ref BAR87

NIGHTSIGHTS Model TZS4 with infra red illuminator, views up to 75 metres in full darkness in infrared mode, 150m range, 45mm lens, 13 deg angle of view, focussing range 1.5m to infinity. 2 AA batteries required. 950g weight. £199 ref BAR61. 1 years warranty

LIQUID CRYSTAL DISPLAYS Bargain prices, 16 character 2 line, 99x24mm £2.99 ref SM1623A 20 character 2 line, 83x19mm £3.99 ref SM2020A 16 character 4 line, 62x25mm £5.99 ref SMC1640A

TAL-1 110MM NEWTONIAN REFLECTOR TELESCOPE Russian. Superb astronomical scope, everything you need for some serious star gazing! up to 169x magnification. Send or fax for further details £249 ref TAL-1

GOT AN EXPENSIVE BIKE? You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

GOT AN EXPENSIVE ANYTHING? You need one of our cased vibration alarms, keyswitch operated, fully cased just to fit it to anything from videos to caravans, provides a years protection from 1

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

PP3 battery, UK made. SALE PRICE £4.99 REF SA33

DAMAGED ANSWER PHONES These are probably beyond repair so just £4.99 each. BT response 200 machines. REF SA30.

COMPUTER DISC CLEAROUT We are left with a lot of software packs that need clearing so we are selling at disc value only! 50 discs for £4, that's just 8p each! (our choice of discs) £4 ref EP66

IBM PS2 MODEL 160Z CASE AND POWER SUPPLY Complete with fan etc and 200 watt power supply. £9.95 ref EP67

DELL PC POWER SUPPLIES 145 watt, +5,-5,+12,-12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP55

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5.25" drives but returns so they will need attention SALE PRICE NOW ONLY £3.50 ref EP69

PP3 NICADS Unused but some storage marks. £4.99 ref EP52

DELL PC POWER SUPPLIES (Customer returns) Standard PC psu's complete with fly leads, case and fan. +12v, -12v, +5v, -5v SALE PRICE £1.99 EACH worth it for the bits alone! ref DL1. TRADE PACK OF 20 £29.95 Ref DL2.

GAS HOBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

RED EYE SECURITY PROTECTOR 1,000 watt outdoor PIR switch SALE PRICE £6.99 ref EP57

ENERGY BANK KIT 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EF112.

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses, includes word processor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (0345-326009 try before you buy) Current retail price is £129, SALE PRICE £9.95 ref SA12. SAVE £120!!!

COMPLETE PC 200 WATT UPS SYSTEM Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. LAST FEW TO CLEAR AT £49 SAVE £30 ref LOT61

BIG BROTHER PSU Cased PSU, 6v 2A output, 2m o/p lead, 1.5m input lead, UK made, 220v. SALE PRICE £4.99 REF EP7



Check out our
WEB SITE

<http://www.pavillon.co.uk/bull-electrical>

RACAL MODEM BONANZA! 1 Racal M1223 1200/75 modem, telephone lead, mains lead, manual and comms software, the cheapest way onto the net! all this for just £13 ref DEC13.

4.5mw LASER POINTER. BRAND NEW MODEL NOW IN STOCK! supplied in fully built form (looks like a nice pen) complete with handy pocket clip (which also acts as the on/off switch.) About 60 metres range! Runs on 2 AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. just £39.95 ref DEC49 TRADE PRICE £28 MIN 10 PIECES

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 REF TEN/1

RUSSIAN MONOCULARS Amazing 20 times magnification, coated lenses, carrying case and shoulder strap £29.95 REF BAR73

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and s/ware. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

EMERGENCY LIGHTING UNIT Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased, 6v 8AH lead acid req'd. (secondhand) £4 ref MAG4P11.

YUASHA SEALED LEAD ACID BATTERIES Two sizes currently available this month. 12v 15AH at £18 ref LOT8 and 6v 10AH (suitable for emergency lights above) at just £6 ref LOT7.

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. £8.99 REF SA25.

ECLATRON FLASH TUBE As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. £6.99 REF SA15B.

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3 P&P PLUS VAT.
PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS
WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500
FAX 01273 323077

E-mail bull@pavillon.co.uk

24v AC 96WATT Cased power supply. New. £9.99 REF SA40

MICRODRIVE STRIPPERS Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, s/wich plus 1 relay or motor. Superb value kit SALE PRICE JUST £4.99 REF SA27

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back ordered metal case. SALE PRICE £49 REF SA16B

PLUG IN ACORN PSU 19v AC 14w. £2.99 REF MAG3P10

13.8V 1.9A PSU cased with leads. Just £9.99 REF MAG10P3

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the C5 motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

PHONE CABLE AND COMPUTER COMMUNICATIONS PACK Kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PCs over a long distance utilizing the serial ports. Complete kit £8.99. Ref comp1.

VIEWDATA SYSTEMS made by Phillips, complete with internal 1200/75 modem, keyboard, psu etc RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

AIR RIFLES. 22As used by the Chinese Army for training purposes, so there is a lot about! £39.95 REF EF78. 500 pellets £4.50 ref EF80.

PLUG IN POWER SUPPLY SALE FROM £1.50 Plugs in to 13A socket with output lead. three types available, 9vdc 150mA £1.50 ref SA19, 9vdc 200mA £2.00 ref SA20, 6.5vdc 500mA £2 ref SA21.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2.

***MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range up to 2kmin open country. Units measure 22x52x155mm. Including cases and ear pieces. 2xPP3 req'd. £30.00 pr. REF: M AG30

***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EF62 (dit) Transmits to any FM radio.

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER COMPLETE WITH COIN SLOT MECHANISMS originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EF82B extra pellets (500) £4.50 ref EF80.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 Ideal for experimenters! 30 m for £12.99 ref MAG13P1

MIXED GOODIES BOX OF
MIXED COMPONENTS WEIGHING 2 KILOS
YOURS FOR JUST £5.99

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R/7.

RATTLE BACKS Interesting things these, small piece of solid perspex like material that if you try to spin it on the desk it only spins one way in fact if you spin it the 'wrong' way it stops of its own accord and go's back the other way! £1.99 ref GIJ01.

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc £6 ref EP70

HYPOTHERMIA SPACE BLANKET 215x150cm aluminised foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirror! £3.99 each ref O/L041.

LENSTATIC RANGER COMPASS Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying viewer. 50mm dia, 86gm. £10.99 ref O/K604.

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are recharged, automatically rejects unsuitable cells, complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

TALKING WATCH YES, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities. micro size just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

SANYO NICAD PACKS 120mmx14mm 4.8v 270 mA suitable for cordless phones etc. Pack of 2 just £5 ref EP78.

3" DISCS As used on older Amstrad machines, Spectrum plus 3's etc £3 each ref BAR400.



STEREO MICROSCOPES BACK IN STOCK Russian, 200x complete with lenses, lights, filters etc etc very comprehensive microscope that would normally be around the £700 mark, our price is just £299 (full money back guarantee) full details in catalogue. Ref 95/300.

WE BUY SURPLUS STOCK FOR CASH

BUYERS DIRECT LINE 0860 425692
FREE CATALOGUE

100 PAGE CATALOGUE NOW
AVAILABLE, 50P STAMP OR FREE

ON REQUEST WITH ORDER.

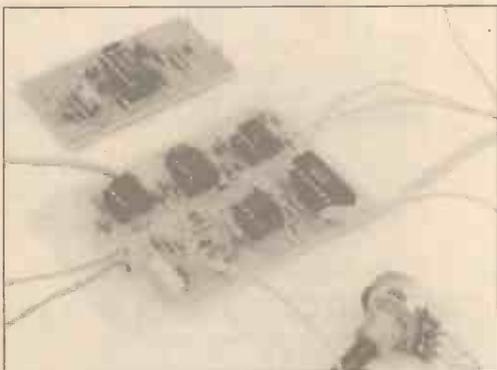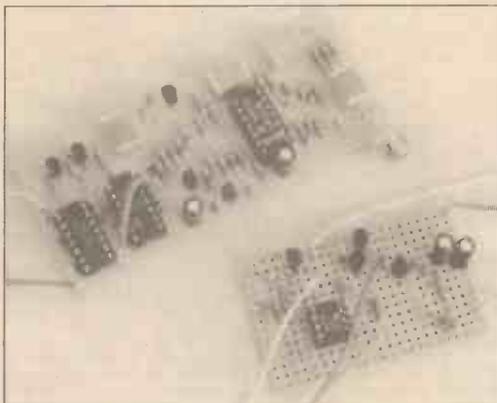

© Wimborne Publishing Ltd 1996. Copyright in all drawings, photographs and articles published in EVERYDAY PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our June '96 Issue will be published on Friday, 3 May 1996. See page 331 for details.

Everyday Practical Electronics, May

Projects

- MIDI ANALYSER** by Julian Ilett and Brett Gossage 342
The secrets of MIDI really revealed!
- MIND MACHINE Mk III - 3 • TAPE CONTROLLER** by Andy Flind 360
Build up a library of stress-reducing tapes for use with our low cost Mind Entrainment unit. Has many other applications
- VERSATILE PIR DETECTOR ALARM** by Andy Flind 366
Reliably and discretely detect intruders anywhere within your domain
- COUNTDOWN TIMER** by Max Horsey 378
Switch-selectable countdown for any period below 100 minutes, with buzzer and optional relay. A *Teach-In '96* project
- BAT BAND CONVERTER B.F.O.** by Bill Mooney 396
Translates bat-chat down to our audio range when used with last month's radio-coupled converter

Series

- TEACH-IN '96 - A Guide to Modular Circuit Design - 7** 374
by Max Horsey
Showing how simple modules can be used as the building blocks for larger designs. Crystal controlled and a.c. clock pulse generators, counters, 7-segment decoder/drivers and displays
- INTERFACE** by Robert Penfold 386
More about serial interfacing - the 6402 UART with its receiver and transmitter functions
- INGENUITY UNLIMITED** hosted by Alan Winstanley 389
D.C. Lamp Dimmer; Infra-Red Headphone Link; Remote Handset Tester; Programmable Timer/Sequencer
- AMATEUR RADIO** by Tony Smith G4FAI 404
Frequency clash for radio-operated car keys; RSGB survey; Millennium Committee; Role of the IARU

Features

- EDITORIAL** 341
- NEW TECHNOLOGY UPDATE** by Ian Poole 351
Who says the age of steam is over? - a new breed of micro-machine runs on it!
- INNOVATIONS** 352
Everyday news from the world of electronics
- VALVES TODAY - 2 • The C.R.T.** by Ian Poole 354
In oscilloscopes, radar systems and cash tellers, cathode ray tubes keep thermionic valve technology to the fore
- FOX REPORT** by Barry Fox 358
Hotly hifi - more revitalising for the valve; BT and the Superhighway; Are there holes in BT's Net?
- SHOPTALK** with David Barrington 371
Component buying for *EPE* projects
- ELECTRONICS VIDEOS** 372
Our range of educational videos
- BACK ISSUES** Did you miss these? 391
- FAX ON DEMAND** 392
Need a recent *EPE* article today? Try our new "instant" service!
- OHM SWEET OHM** by Max Fidling 395
Galvanised into action, Max and Piddles risk neighbourly molestation!
- DIRECT BOOK SERVICE** 399
A wide range of technical books available by mail order
- PRINTED CIRCUIT BOARD SERVICE** 402
PCBs for *EPE* projects - some at "knockdown" prices!
- ADVERTISERS INDEX** 408

Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's -

SPECIAL BUY

AT 286

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k + 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!
Order as HIGRADE 286 **ONLY £129.00** (E)

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/2" floppy disk drive (instead of 1.2 Mb)	£19.95
NE2000 Ethernet (thick, thin or twisted) network card	£39.00

LOW COST 486DX-33 SYSTEM

Limited quantity of this 2nd user, superb small size desktop unit. Fully featured with standard simm connectors 30 & 72 pin. Supplied with keyboard, 4 Mb of RAM, SVGA monitor output, 256k cache and integral 120 Mb IDE drive with single 1.44 Mb 3.5" floppy disk drive. Fully tested and guaranteed. Only **£399.00** (E)
Many other options available - call for details.

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" or 3 1/2" from only £18.95!

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from other brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (if 3 1/2" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent RFE	£24.95(B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only	£25.95(B)
3 1/2" Mitsubishi MF355C-D. 1.4 Meg. Non laptop	£18.95(B)
5 1/4" Teac FD-55F/9 1.2 Meg (for IBM PC's) RFE	£18.95(B)
5 1/4" Teac FD-55F-03-U 720K 40/80 (for BBC's) etc RFE	£22.95(B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)
Table top case with integral PSU for HH 5 1/4" Floppy or HD	£29.95(B)
8" Shugart 800/801 8" SS refurbished & tested	£195.00(E)
8" Shugart 810 8" SS HH Brand New	£195.00(E)
8" Shugart 851 8" double sided refurbished & tested	£250.00(E)
Mitsubishi M286-63 8" double sided NEW	£275.00(E)
Mitsubishi M286-63-02U 8" DS slimline NEW	£285.00(E)
Dual 8" cased drives with integral power supply 2 Mb	£499.00(E)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte drive with industry standard **SMI Interface**. Ultra hi speed data transfer and access times, replaces Fujitsu equivalent model. Complete with full manual. Only **£299.00** or 2 for **£525.00** (E)

3 1/2" FUJI FK-309-26 20mb MFM I/F RFE	£59.95(C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv) RFE	£59.95(C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv) RFE	£69.00(C)
3 1/2" RODIME R03057S 45mb SCSI I/F (Mac & Acorn)	£99.00(C)
3 1/2" WESTERN DIGITAL 850mb IDE I/F Brand New	£185.00(C)
5 1/4" MINISCRIBE 3425 20mb MFM I/F (or equiv) RFE	£49.95(C)
5 1/4" SEAGATE ST-238R 30 mb RLL I/F Refurb	£69.95(C)
5 1/4" CDC 94205-51 40mb HH MFM I/F RFE tested	£69.95(C)
8" FUJITSU M2232K 160Mb SMD I/F RFE tested	£195.00(E)

Hard disc controllers for MFM, IDE, SCSI, RLL etc. from **£16.95**

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!



TV SOUND & VIDEO TUNER CABLE COMPATIBLE

The TELEBOX is an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop computer video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi Fi audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£36.95
TELEBOX STL as ST but fitted with integral speaker	£39.50
TELEBOX MB Multiband VHF/UHF/Cable/Hyperband tuner	£69.95

For overseas PAL versions state 5.5 or 6 mHz sound specification.
*For cable / hyperband reception Telebox MB should be connected to a cable type service. Shipping code on all Teleboxes is (B)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call for info / list.

IC's - TRANSISTORS - DIODES

OBSOLETE - SHORT SUPPLY - BULK

6,000,000 items EX STOCK

For MAJOR SAVINGS - CALL FOR SEMICONDUCTOR HOTLIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync colour monitor with fine 0.28 dot pitch tube and resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features. Etched landscape, text switching and LOW RADIATION MPR specification. Fully guaranteed, supplied in EXCEL-

LENT little used condition. Order as MITS-SVGA
Tilt & Swivel Base £4.75
VGA cable for IBM PC included.
Only **£119** (E)
External cables for other types of computers CALL

5000 Monitors from stock !!!
HERCULES, EGA, CGA, VGA, SVGA - 6 to 26"
+ Many special items - CALL with your needs !

Just in - Microvitec 20" VGA (800 x 600 res.) colour monitors. Good SH condition - from **£299** - CALL for info

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all video monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed flap controls, VCR correction button etc. Good used condition - fully tested - guaranteed.
Dimensions: W14" x H12 1/2" x 15 1/2" D.
Only **£95** (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested & guaranteed (possible minor screen burn). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. 240 V AC mains powered.
Only **£79.00** (D)

KME 10" 15M10009 high definition colour monitors with 0.28" dot pitch. Superb clarity and modern styling. Operates from any 15.625 KHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Good used condition.
Only **£125** (E)

20" 22" and 26" AV SPECIALS


Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound input. Attractive leak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT little used condition with full 90 day guarantee.

20"£135 22"£155 26"£185 (F)

.....SPECIAL INTEREST ITEMS

MITS FA3445ETKL 14" Industrial spec SVGA monitors 2Kw to 400 Kw - 400 Hz 3 phase power sources - ex stock	£245
Broadcast Electronics Inc FX30 FM exciter 80-108 MHz	£750
Stanelco STA15 15Kw RF induction heater system	£950
IBM 8230 Type 1, Token ring base unit driver	£750
IBM 53F5501 Token Ring ICS 20 port lobe modules	£95
IBM MAU Token ring distribution panel 8228-23-5050N	£550
AIM 501 Low distortion Oscillator 9Hz to 330KHz. IEEE	£1800
Trend DSA 274 Data Analyser with G703(2M) 64 Vo	£950
HP APOLLO RX700 system units	£675
HP6621A Dual Programmable GPIB PSU 0-7 V 160 watts	£1850
HP6264 Rack mount variable 0-20V @ 20A metered PSU	£1200
HP54121A DC to 22 GHz four channel test set	£1850
HP7580A AT 8 pen HPGL high speed drum plotter	£6500
Marconi 6310 Programmable 2 to 22 GHz sweep generator	£850
EG-NG Brookdale 95035C Precision lock in amp	£250
OTC Ltd 1550 SM Stabilised IR laser calibration source	£125
Link Dynamics 2Kw programmable vibration test system	£3750
Computer 16mm CTV auto iris lenses 'C' mount - NEW	£1200
Kelthley 590 CV capacitor / voltage analyser	£2200
Racal ICR40 dual 40 channel video recorder system	£1200
Roken 80-250 240v single phase flow solder machine	£1950
ICI R5030UV34 Cleanline ultrasonic cleaning system	£1250
Mann Talley MT645 High speed line printer	£3750
INTEL SBC 486/133SE Multibus 486 system. 8Mb Ram	£950
Zeta 3220-05 A0 4 pen HPGL fast drum plotters	£1150
Nikon HFX-11 (Ephiphot) exposure control unit	£1450
Motorola VME Bus Boards & Components List. SAE / CALL	£1500
Trilo 0-18 vdc linear, metered 30 amp bench PSU. New	£950
Fujitsu M3041R 600 LPM band printer	£1250
Fujitsu M3041D 600 LPM printer with network interface	£1250
Perkin Elmer 2998 Infrared spectrophotometer	£3750
VG Electronics 1035 TELETEXT Decoding Margin Meter	£950
Andrews LARGE 3.1 M Satellite Dish & mount (For Voyager)	£1995
Thurlby LA 1608 logic analyser	£1995
Denon SD 150H 16 channel digital Hybrid chart recorder	£575
Delecto MUD 0185AH 1KVA UPS system with batts NEW	£485
System Video 1152 PAL waveform monitor	£300
Test Lab - 2 mtr square quietised acoustic test cabinets	£650
Kenwood 9601 PAL Vectorscope - NEW	

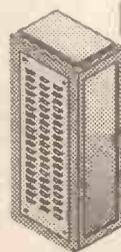Please call for further details on the above items



19" RACK CABINETS

Superb quality 6 foot 40U
Virtually New, Ultra Smart
Less than Half Price!

Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and louvered removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 pin socket switched mains distribution strip make these racks some of the most versatile we have ever sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in multiple bays.

Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:	
OPT Rack 1 Complete with removable side panels	£335.00 (G)
OPT Rack 2 Rack, Less side panels	£225.00 (G)

32U - High Quality - All steel RackCab

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer style' smoked acrylic front panel to enable status indicators to be seen through the panel, yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre punched for standard 'cage nuts'. A mains distribution panel internally mounted to the bottom rear, provides 8 x IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvers. The top panel may be removed for fitting of Integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, prepunched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions mm=1625H x 635D x 603 W. (64" H x 25" D x 23 3/4" W)
Call at LESS than a third of makers price !!



A superb buy at only **£195.00** (G)

Over 1000 racks - 19" 22" & 24" wide
3 to 44 U high. Available from stock !!
Call with your requirements.

TOUCH SCREEN SYSTEM

The ultimate in 'Touch Screen Technology' made by the experts - MicroTouch - but sold at a price below cost !! System consists of a flat translucent glass laminated panel measuring 29.5 x 23.5 cm connected to an electronic controller PCB. The controller produces a standard serial RS232 or TTL output which continuously gives simple serial data containing positional X & Y co-ordinates as to where a finger is touching the panel - as the finger moves, the data instantly changes. The X & Y information is given at an incredible matrix resolution of 1024 x 1024 positions over the entire screen size !! A host of available transition software enables direct connection to a PC for a myriad of applications including: control panels, pointing devices, POS systems, controllers for the disabled or computer un-trained etc etc. Imagine using your finger with 'Windows', instead of a mouse !! (a driver is indeed available !!) The applications for this amazing product are only limited by your imagination!! Complete system including Controller, Power Supply and Data supplied at an incredible price of only: **£145.00** (B)
Full MICROTUCH software support pack and manuals for IBM compatible PC's £29.95 RFE - Tested

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disks supplied. RFE. Fully tested and guaranteed. Windows compatible. **£59.95** (A1)
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 64k DOS limit. Complete with data.
Order as: XT RAM UG. 256K. £34.95 or 512K £39.95 (A1)

SIMM SPECIALS

1 MB x 9 SIMM 3 chip 120ns	Only £19.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£23.50 or 70ns £24.95 (A1)
1 MB x 9 SIMM 9 chip 80 ns	£22.50 or 70ns £24.00 (A1)
4 MB 70 ns 72 pin SIMM - with parity	Only £95.00 (A1)
8 MB 70 ns 72 pin SIMM - no parity	£159.00 (A1)
INTEL 486-DX33 CPU £55.00	INTEL 486-DX66 CPU £69.00 (A1)

FANS & BLOWERS

EPSON D0412 40x40x20 mm 12V DC	£7.95 / £55
PAPST Type 612 60x60x25 mm 12V DC	£8.95 / £75
MITSUBISHI MMF-D6D12DL 60x60x25 mm 12V DC	£4.95 / £42
MITSUBISHI MMF-08C12DM 80x80x25 mm 12V DC	£5.25 / £49
MITSUBISHI MMF-09B12DH 92x92x25 mm 12V DC	£5.95 / £53
PANCAKE 12-3.5 92x92x18 mm 12V DC	£7.95 / £69
EX-EUJIP AC fans. ALL TESTED 120 x 120 x 38 mm specily 110 or 240 v £6.95. 80 x 80 x 38 mm - specily 110 or 240 v £5.95	
IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240V NEW	£79.95

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

DISPLAY
-ELECTRONICS-


ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept PE. 32 Bliggin Way
Upper Norwood
LONDON SE19 3XF

LONDON SHOP
Open Mon - Sat 9.00 - 5.30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Selhurst Park SR Rail Stations

NEW DISTEL©
The Original
FREE On line Database
Info on 20,000 + stock items!
RETURNING SOON!

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bona Fide account orders accepted from Government, Schools Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)=£3.00, (A1)=£4.00 (B)=£5.50, (C)=£8.50, (D)=£12.00, (E)=£15.00, (F)=£18.00, (G)=CALL. Allow approx 6 days for shipping - faster CALL. Scotland surcharge CALL. All goods supplied to our Standard Conditions of Sale and Discounts guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1996. E & O.E. 01/5

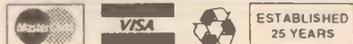

ULTRA-FAST FREQUENCY GENERATOR & COUNTER

Improve your workshop facilities with this high-speed, multi-frequency item of test gear. Designed in response to the need for a frequency generator and 8-digit counter which can cope with frequencies well in excess of 40MHz and with more than one signal generator, it's a real freq-out!

'SCOPES

Every picture tells a story and a "picture" of an electronic signal can tell you much more than a voltage, current or frequency measurement. Starting next month this short series of articles looks at the equipment that can provide the "picture" – the cathode ray oscilloscope. The series covers 'Scope Basics, Measurements, Experiments, Applications and Digital Storage 'Scopes. Don't miss this excellent insight into a very versatile piece of test gear.

TELEPHONE LINK

Build yourself a simple 'phone link for use in and around your home, workshop, etc. This project describes a neat, easy to build 'phone that can operate over distances of up to one kilometre.



SARAH'S LIGHT

So you're not afraid of the dark? Imagine the scene: It's the middle of a winter's night when you're woken up by the sound of a creaking floorboard. Pulse racing, you try to get out of your bed, but find that you can't. The hairs on the back of your neck stand up as you consider that from where you are there's no way you can turn on the light. So you crouch, trapped, staring into the darkness while your imagination parades a host of frightening possibilities. Sounds like a nightmare? It's a situation faced nightly by children who sleep in a cot – and then we wonder why kids are afraid of the dark! So the idea for Sarah's light was born, to banish fears of the dark by giving the child control over it.

EVERYDAY

PRACTICAL

ELECTRONICS

JUNE ISSUE ON SALE FRIDAY, MAY 3


Everyday Practical Electronics, May

NEXT MONTH



Integrated PCB & Schematic Design System for Windows™

New Version 3.5

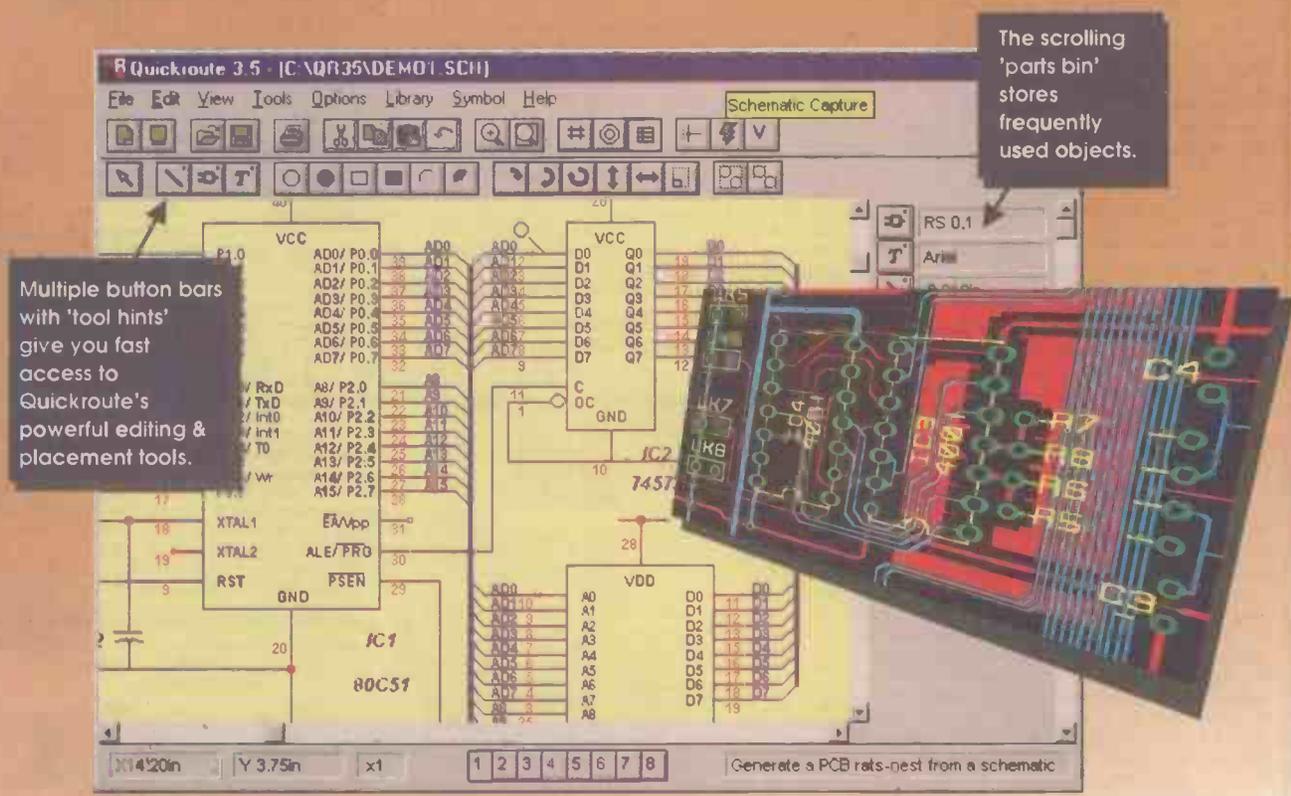

Multiple button bars with 'tool hints' give you fast access to Quickroute's powerful editing & placement tools.

The scrolling 'parts bin' stores frequently used objects.

"..of all the products included here, this is my personal favourite... Really, thats all I have to say about Quickroute - it certainly gets my vote!"

Review of QR 3.0 & other products
Computer Shopper Nov 95

EASY TO USE

Quickroute 3.5 is a powerful, affordable and easy to use integrated schematic & PCB design system for Windows. With its multiple button bars, 'tool hints' and 'parts bin', Quickroute helps you to design quickly and efficiently

POWERFUL

There are four different versions of Quickroute giving you a choice of features & price. Quickroute is available with multi-sheet schematic capture, auto-routing, 'engineering change' (modification of a PCB from a schematic), copper fill, and a range of file import/export options. See the table for a selection of features.

AFFORDABLE

Prices are Designer (£149), PRO (£249) and PRO+ (£399). The Personal edition is available for just £68, but has the manual provided on disk as on-line help. Post & Packing is £5 (UK), £8 (EC), £12 (World). VAT must be added to the total price.

	Personal	Designer	PRO	PRO+
PCB & Schematic Design	✓	✓	✓	✓
Schematic Capture		✓	✓	✓
Auto router			✓	✓
Design Rule Checking			✓	✓
Export WMF & Tango			✓	✓
Export Gerber/NC-Drill			✓	✓
Extended Libraries			✓	✓
Tango + Gerber Import				✓
Update PCB from schematic				✓
DXF & SPICE Export				✓
Copper Fill				✓

Tel/Fax 0161 449 7101



Quickroute Systems Ltd., 14 Ley Lane, Marple Bridge, Stockport, SK6 5DD, U.K.

email info@quicksys.demon.co.uk



Phone now for more information

Prices and specifications subject to change without notice. All trade marks are acknowledged & respected.

HART

HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART KITS give you the opportunity to build the very best engineered hi-fi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase. Our list will give you full details of all our Audio Kits, components and special offers.

INTRODUCING

The Hart "Chiara"

Single-Ended Class "A" Headphone Amplifier.

Most modern high fidelity amplifiers either do not have a headphone output facility, or this may not be up to the highest standard.

The new Hart "Chiara" has been introduced as an add-on unit to remedy this situation, and will provide two ultra high quality headphone outlets. This is the first unit in our 2000 Range of modules to be introduced through the year. Housed in the neat, black finished, Hart Minibox it features the wide frequency response, low-distortion and "musicality" that one associates with designs from the renowned John Linsley Hood.

Both outputs will drive any standard high quality headphones with an impedance greater than 30 ohms and the unit is ideal for use with the Sennheiser range. A signal link-through makes it easy to incorporate into your system and two extra outputs, one at output level and one adjusted by the Volume control are available on the back panel. The high level output also makes a very useful long-line driver where remote mounted power amplifiers are used. Power requirements are very simple and can be provided by either of our new "Andante" power supplies. Use the K3565 to drive the "Chiara" on its own, K3550 if driving other modules as well.

Volume and Balance controls are provided and as befits any unit with serious aspirations to quality these are the ultra high quality Alps "Blue Velvet" components.

Very easily built, even by beginners, since all components fit directly on the single printed circuit board and there is no conventional wiring whatsoever. The kit has very detailed instructions, and even comes with a roll of Hart audiograde silver solder. It can also be supplied factory assembled and tested.

Selling for less than the total cost of all the components, if they were bought separately, this unit represents incredible value for money and makes an attractive and harmonious addition to any hi-fi system.

K2100 The total cost of a complete set of all components to build this unit is £126.37. Our special discount price for all parts bought together as a kit is.....£109.50

K2100SA Series Audiophile, with extra selected components.....£112.46

HART TC1D Triple Purpose TEST CASSETTE

Now available again and even better than before! Our famous triple purpose test cassette will help you set up your recorder for peak performance after fitting a new record/play head. This quality precision Test Cassette is digitally mastered in real time to give you an accurate standard to set the head azimuth, Dolby/VU level and tape speed, all easily done without test equipment.

TC1D Triple Purpose Test Cassette.....£9.99

Send or 'phone for your copy of our FREE List of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows: -INLAND Orders up to £20 - £1.50, Orders over £20 - £3.50. Express Courier, next working day £10.

OVERSEAS - Please see the ordering information with our lists.

NEW BOOK

"Audio Electronics"

And now, hot off the press, yet another classic from the pen of John Linsley Hood. Following the ongoing enormous success of his "Art of Linear Electronics" the latest offering is the all-new edition of "Audio Electronics", now entirely re-written by the master himself.

Underlying audio techniques and equipment is a world of electronics that determines the quality of sound. For anyone involved in designing, adapting or using digital or analogue audio equipment understanding electronics leads to far greater control over the reproduced sound.

The subjects covered include tape recording, tuners, power output stages, digital audio, test instruments and loudspeaker crossover systems. John's lifetime of experience and personal innovation in this field allow him to apply his gift of being so familiar with his subject that he can write clearly about it and make it both interesting and comprehensible to the reader.

Containing 240 pages and over 250 line illustrations this new book represents great value for money at only £18.99 plus £2.50 postage. Send or telephone for your personal copy now.

ALPS "Blue Velvet"

Precision Audio Controls



To fulfil the need for ultra high quality controls we import a special range of precision audio pots in values to cover most quality amplifier applications. All in 2-gang stereo format, with 20mm long 6mm diam. steel shafts, except for the 50K Log which is 25mm x 6mm. Overall size of the manual pot is 27W x 24H x 27Deep, motorised versions are 72-4mm Deep from the mounting face. Mounting bush for both types is 8mm diameter.

Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability.

The motorised versions use a 5V DC motor coupled to the normal control shaft with a friction clutch so that the control can be operated manually or electrically. The idea of having electrically operated pots may seem odd, archaic even, but it is in fact the only way that remote control can be applied to any serious Hi-Fi system without loss of quality. The values chosen are the most suitable available for a low loss passive volume and balance control system, allowing armchair control of these two functions.

Our prices represent such super value for pots of this quality due to large purchases for our own kits.

MANUAL POTENTIOMETERS

2-Gang 100K Lin.....£15.67
2-Gang 10K, 50K or 100K Log.....£16.40
2-Gang 10K Special Balance, zero crosstalk and zero centre loss.....£17.48

MOTORISED POTENTIOMETERS

2-Gang 20K Log Volume Control.....£26.20
2-Gang 10K RD Special Balance, zero crosstalk and less than 10% loss in centre position.....£26.98

REEL TO REEL HEADS

999R 2/4 R/P 100mH.....£16.84
We have a few erase heads to suit which can only be supplied when 2 R/P heads are purchased £36.80

TAPE RECORDER CARE PRODUCTS

DEM1 Mains Powered Tape Head
Demagnetizer, prevents noise on playback due to residual head magnetisation.....£4.08
DEM115 Electronic, Cassette Type, demagnetizer.....£8.61

LINSLEY HOOD 'SHUNT FEEDBACK' RIAA MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIERS



The HART K1450 Magnetic pickup preamplifier kit features a totally discrete component implementation with a specially designed low input impedance front end and the superior sound of the Shunt Feedback circuitry. High quality components fitting to an advanced double-sided printed circuit board make this a product at the leading edge of technology that you will be proud to own. Nevertheless with our step by step instructions it is very easy and satisfying to assemble. The higher current consumption of this unit means that it is best powered by our new Andante Audio Power Supply, itself an advanced piece of technology in a matching case. This supplies the superbly smoothed and stabilised supply lines needed by any sensitive preamplifier and features a fully potted Hi-grade toroidal transformer along with a special limited shift earth system for hum free operation. The K1450 is suitable for all moving coil and moving magnet transducers this unit is especially recommended for, and will extract the very best from the modern generation of low output high quality moving coil transducers.

K1450 Kit, complete with all parts ready to assemble inside the fully finished 228mm x 134mm x 63mm case. Kit includes full, easy to follow, assembly instructions as well as the Hart Guide to PCB Construction, we even throw in enough Hart Audiograde Silver Solder to construct your kit!.....£111.58

K1450SA Series Audiophile version with selected components.....£133.94

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. For top performance cassette recorder heads should be replaced every 1,500 hours. Fitting one of our high quality replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines (Sony are special dimensions, we do not stock) and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex-stock. We also stock a wide range of special heads for home construction and industrial users.

HC80 NEW RANGE High Beta Permalloy Stereo head. Modern space saver design for easy fitting and lower cost. Suitable for chrome, metal and ferric tapes, truly a universal replacement head for everything from hi-fi decks to car players and at an incredible price too!.....£11.70
HRP373 Downstream monitor combi head.....£62.59
HQ551A 4-Track R/P.....£8.75
HQ551S Sony Mount 4-Tr. R/P.....£14.90
HQR560 Rotary Base 12.5mm R/P/E.....£21.90
HQR570 Rotary Base 15mm R/P/E.....£22.59
HQR580 Rotary Base 12.5mm R/P.....£14.29

HART Classical CD's.

Top quality, Full Digital (DDD), over 100 titles from only £1.99! Ring or send for your list!

TECHNICAL BOOKSHELF

We stock a good range of books of interest to the electronics and audio enthusiast, including many reprinted classics from the valve era. Some were in last month's advertisement, but see our list for the full range.

New this month is the GEC Valve designs book at £18.95, and the VTL Book, a modern look at valve designs, £17.95.

QUALITY AUDIO KITS

24 hr. SALES LINE (01691) 652894

ALL PRICES INCLUDE UK/EC VAT

HART ELECTRONIC KITS LTD. 6 PLYMOUTH ROAD, OSWESTRY, CHESHIRE SV10 3AF

SURVEILLANCE PROFESSIONAL QUALITY KITS

No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

Genuine SUMA kits available only direct from Suma Designs. Beware inferior imitations!

UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3-12V operation. 500m range.....£16.45

MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter
Just 17mm x 17mm including mic. 3-12V operation. 1000m range.....£13.45

STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....£15.45

VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range.....£16.45

VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range..£19.45

HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range.....£19.45

SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range.....£22.95

SCLX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range.....£23.95

SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation.....£22.95

ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....£13.45

UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use. All conversation transmitted. Powered from line. 500m range.....£15.95

TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range.....£13.45

STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm. 1500m range.....£16.45

TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation.....£22.95

CD400 Pocket Bug Detector/Locator

LED and piezo bleeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation.....£30.95

CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate bleeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation.....£50.95

QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range.....£40.95

QLX180 Crystal Controlled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range.....£40.95

QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m.....£35.95

QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Outpt to headphones. 60mm x 75mm. 9V operation.....£60.95

A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.

★★★ Specials ★★★

DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way dill switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits).....£50.95

Individual Transmitter DLTX.....£19.95

Individual Receiver DLRX.....£37.95

MBX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range.....£20.95

**SUMA
DESIGNS**

DEPT. EE

THE WORKSHOPS, 95 MAIN ROAD,
BAXTERLEY, NEAR AHERSTONE,
WARWICKSHIRE CV9 2LE

VISITORS STRICTLY BY APPOINTMENT ONLY



Tel/Fax:
01827 714476



**27D Park Road
Southampton SO15 3UQ
Tel 01 703 236363
Fax 01 703 236307**

E-Mail 100014, 1463 Internet http://www.herald.co.uk/clients/G/Greenweld.html

**Our 200 page 1996 Catalogue is
£2.00, but will be sent free with
any order.**

One off and pack prices in bold include VAT; qty prices don't. Number in brackets after order code is approx qty available. P&P £300 per order. Pay by cheque, PO, Cash, Book tokens, Visa, Access or Switch. We are open for callers from 8.5-30 Mon-Sat.

Semiconductors

Some memory chips, found in a parcel purchased a while ago but only just surfaced.

As far as we can ascertain, they're all DRAMs.

X3919 (1429) TMS4256FML-12 256k x 1 18 pin surface mount. 50p; 100+ 0.30

X4083 (130) 41256-12 18 pin surface mount. 50p; 100+ 0.30

X4091 (31) TMS4416-15 18 pin surface mount. 50p.

X4089 (93) TMS4464-12 (few -15) 18 pin surface mount. 50p.

X3920 (74) 81257-12 256k(?) 18 pin surface mount. 50p.

X3921 (400) D41464-12 64k x 4 18 pin surface mount. 50p; 100+ 0.30

X4088 (64) D41464-15 (we'll supply these when -12 is sold out) 64k x 4 18 pin surface mount. 50p.

X3924 (274) M5M4256L-12 256k 18 pin DIL 0.1" pitch. 50p; 100+ 0.30

X4087 (35) M5M4256L-12 256k 24 pin DIL 0.1" pitch. 50p.

X4084 (198) D41264-12 24 pin DIL 0.1" pitch. 50p; 100+ 0.30

X3922 (112) TMS4C1024D-12 1M x 1 20 pin surface mount. £1.50; 100+ 0.90

X3923 (17) 42C4064Z-12 (M?) 24pin DIL 0.1" pitch. £1.50

X4085 (78) 1259Z-15 16 pin DIL 0.1" pitch 50p

X4092 (37) 1259EJ-12 18 pin surface mnt. 50p

X4086 (65) 1257Z-15 16 pin DIL 0.1" pitch 50p

X4090 (23) M5M4256-15 16 pin DIL 0.1" pitch 50p

X4093 (24) M5M4256J -15 18 pin surface mount. 50p.

X4094 (34) M8B1256-12 16 pin DIL 0.1" pitch 50p

X4095 (7) M8B1464-12 16 pin DIL 0.1" pitch 50p

X3936 (6) Texas 256k x 9 bit SIMM, uses 3 x 14C256-80. £5.00

X3935 (8) Epsom 256k x 9 bit 3 chip SIMM. £5.00

68B19 (200) 78H12ASC TO3 steel case 12V 5A voltage regulator. List 9.34 Our Price £3.00; 100+ 2.00

X3903 (70) ZNREF040CI TO18 case 4.0V precision reference diode. £1.00

X3909 (54) 7905 TO220 voltage reg. -5V 1A /£1.00; 100+ 0.14

X3751 (5500) 1N4003 preformed and cropped for vertical PCB mntg. 100/£1.00; 1000+ 0.006

X3732 (1600) A PNP darlington TO92 transistor with life of 100. (Not marked) 25/£1.00; 1000+ 0.025

X3763 (2200) E-line NPN transistor UGN3078U. Hfe 40. 100/£2.50; 1000+ 0.015

X3902 (22) Extraordinary device - Petier effect thermo-electric module. Acts like a heat pump (18W max) - when voltage is applied, one surface heats and the other cools. Max temp difference of about 70°C size 30x30x4.7. List Price £35.00 Supplied with data sheet. Our Price £12.00

Phone Index Clock X6825 (70) Natty little gadget. Case 115x80 has quick find index and contained within the top is a pop-up LCD clock with large display, alarm and snooze facility. £3.00

JPTO First a couple of LCD modules: (4096 29) These are ex-equip. 24x2 dot matrix text with short ribbon cable with 14 way header skt. £6.00

(4097 15) As above, but with back light. £8.00

(6764 18) Complete vacuum fluorescent display assembly. 16 digit 6x7 dot display + drivers and DC-DC converter all on PCB 162x56. 5V supply. Supplied with comprehensive data £20

X3762 (1400) 5mm high brightness green LED. clear case with cropped leads. right angle mntg. 10/£1.00; 1000+ 0.025

REFERENCE BOOKS

(6777 (41) Third Generation TMS320 User's Guide 1989) 624pp 210x150mm £3.00

(6774 (3) 2 volumes - BA481 to SAA197; AA199B to TDA4680. (1992) Size 227x 177 /10.00

(6773 (25) Philips data handbook - Semiconductors or Television and Video Systems Vol 1 only - BA481 to SAA197 £4.00

X6778 (78) Optoelectronics and Image-Sensor Data Book. All Texas Instruments devices (1987) £4.00

X6771 (14) National Semiconductor DRAM Management Handbook. Size 227x 177 (1989) £8

X6772 (97) National Semiconductor RAM Databook. Size 227x 177 (1987) £2

HANDS FREE KITS For using portable cellular phones in cars

X9085 (84) For the Motorola MicroTAC, contains hands-free cradle with adaptor, speaker, microphone, and glass mounted antenna. £15

X9084 (100) For the Motorola 8000/9000 series, contains hands-free cradle with adaptor, speaker, microphone, and glass mounted antenna £15

X9083 (120) For the NEC P200/P300, P201/P301 and Kenwood KMP-H700 contains hands-free cradle with adaptor, speaker, microphone, and glass mounted antenna £15

X9082 (120) As X9084, but also 8800X LED and LCD versions, contains hands-free cradle with adaptor, speaker, microphone, and glass mounted antenna £15

X9081 (120) As X9084, contains hands-free cradle with adaptor, speaker & microphone. £10

X6815 (200) Electric stapler mechanism, as fitted to some Xerox copiers. This is a nice solid bit of machinery with a 12V motor and external gear chain. It also has a hopper loaded with 5000 staples. £6.00; 100+ 4.00

Personal Mobile Car Adaptors

These consist of a curly cord with car plug one end (fused with LED indicator) and battery shaped moulding the other. Ask for illustrated list

Personal Mobile Cases

Good quality leather cases. Ask for illustrated List

X6714 fits Nokia Orange phone. £3.00

X6756 (180) MTS600 phone cradle made from steel with rubber lining for Motorola phone. Size 117x52x45mm £1.50; 100+ 0.85

X6754 (400) Plastic mobile phone cradle for in car use £1.00; 100+ 0.60

Rabbit Mobile Phone Chassis

Another mobile phone disaster! This one could be used indoors as a normal phone, and also as a mobile, providing there was a transmitter in close proximity, but only for making, not receiving calls

X6757 (400) Consists of two panels that clip together. Panel A has LCD 42x18mm with 10 digit display + several icons: min mic and earpiece; mostly s/m components, batt holder, 16.84 xtal; Panel B has 4 xtal - 50.00, 6.4, 149.5 and another; again, lots of s/m. Both panels for £3.00

X6758 (2000) Panel B only. £1.00

MOTORS & SOLENOIDS

X3945 (3000) Geared 16V DC reversible motor (works well on 12V) size 61x33 dia 10mm dia gear on spindle. Final drive speed 200RPM. £3.00; 100+ 2.00

X6660 (2000) Another motor to add to those on the front page of the Winter Supplement. This one is 12V. 4000RPM. 500mA (7.5A stall), body 75x52mm, spindle 20x4mm, weight 335g £5.00; 100+ 3.00

X6665 (150) A most excellent Japanese mains (220V 0.12A) induction motor with integral gearbox giving a final drive speed of 180RPM to the 48x6mm spindle. Supplied with 5µF starting cap. Solid diecast alloy frame 90x70x70mm £8.00; 100+ 5.00

X6666 (240) Crozet synchronous 28V ac 7W motor 47mm dia x 21mm deep with easily removed gearbox giving final drive speed of 8RPM to 114x4mm spindle. The list price on motor + gearbox is over £43! Our Price £4.00; 100+ 2.80

X6667 (350) Neat 12V stepper motor 44x42x42mm 24 step (15°) £1.50; 100+ 0.80

X6668 (450) Heavy duty solenoid 53x38x32mm Plunger 14mm dia has slot 4mm wide, 20mm travel. 24V dc continuously rated. £2.00; 100+ 1.40

POWER SUPPLIES

X6816 (1500) Plug in ac adaptor, 1.8m lead with 2.5mm power skt. Output 24V ac 200mA £2.00; 100+ 1.20; 1k+ 0.90

X6863 (64) DC adaptor - 110V in on 1m long lead with US 2 pin plug. Output 9V 300mA on 1.8m lead with 2.5mm jack plug. Series two together and use on mains! Price for TW0: £3.00

MISCELLANEOUS

X6762 (160) Set of 3 shrink wrapped disk cases by Esselte. Each takes up to five 3.5" disks. £2.00

X6813 (96) Panoramic camera. Fixed focus 35mm camera that uses standard film New and boxed. £5

X6812 (24) Lottery number selector. 49 coloured balls inside a clear plastic globe. Shake them up, invert the globe and 6 balls appear in a trench £2.50

X3939 (200) Piezo sounder 35dia x 25.5. 12V operation. Like our A385, but mounting lugs cut off 80p; 100+ 0.40

X6814 (6) Large 500µA panel meter 110x80mm face, needs 60mm hole. £5

X3834 (75) Allac edge connector transfer. 0.1" pitch 69 way. Pack of 10 strips. £1.00

X6664 (188) Calculator HL812E 8 digit with %, sq root and memory. 125x70x18mm. £3.00; 100+ 2.00

SWITCHES - Rotary

X3843 (540) 8 pin DIL mntg BCD 10 way switch by EECO. 11x11x11. £1.50; 100+ 0.85

FEME 5950 series for PCB or panel mntg. 10mm bush, spindle 17x6dia, (Farnell 480-472 etc)

X6759 (150) 1pole 12way List 9.45 Our Price £2

X6761 (200) 2pole 6way List 9.94 Our Price £2

X6760 (65) 4pole 6way List 13.87 Our Price £3

Digital

X3946 (220) Pico sub min push button 0-9 BCD 16x7x26 £1.00; 100+ 0.50

X3849 (245) Min clip in type SPCO rated 2A 250V ac. 2/£1.00; X3943 (150) Std on off rocker rated 16A 250V ac. Black 3/£1.00; X3931 (100) Std DP on off rocker rated 10A 250V ac. Black. 2/£1.00; 100+ 0.30

X3859 (900) Sub min PCB mntg 7x7x5.5, white. 8/£1.00

X3880 (700) Sub min PCB mntg 7x7x5.5, black. 8/£1.00

X3916 (200) Momentary push to make, sp make contact. Needs 11.5mm dia hole. 3/£1.00; 100+ 0.20

X6763 (250) Momentary sealed black push switch 'flexibutton'. Needs 22mm dia hole, 1 pr each no and nc contacts rated 5A 250v ac. List 6.89. Our Price £2.00; 100+ 1.20

X6800 (140) Std illuminated rect latching switch by RS Components Ltd. 1 no and 1 no contacts rated 5A 250V ac. (No lamp or bezel) Their price 12.09 Our Price £3.00; 100+ 1.80

X6793 (364) Very sim to above but diff man'r £3.00; 100+ 1.80

A couple of push button banks:

X6799 (120) 3 independent DPCO switches with knobs 60p; X3877 (45) 3 independent DPCO switches without knobs. 40p;

Microswitches

X3789 (80) Licon V4 microswitch 13A 20x9.5x6mm 2/£1.00

X3770 (100) Lever microswitch 20.6x10.5x6.5mm 1M. 1B contact rated 5A 2/£1.00

X3771 (80) Heavy duty microswitch 46x28.5x16.3mm by Burgess, model E19 15A 250V ac. 2 SP make contacts. £1.00

RELAYS

X6766 (230) Coil for contactor, 42-48V 50Hz. Probably more useful for the wire - 36swg ecw. 3/£1.00; 100+ 0.20

X3848 (143) National sealed relay 20x10x10 with SPCO contacts 24V coil £1.00; 100+ 0.60

X6804 (525) 'Continental' relay, PCB mntg DPCO 1A contacts 48V coil £1.00; 100+ 0.60

X6802 (300) ITT flat pack relay 42.5x17x10 DPCO contacts. 48V coil £1.00; 100+ 0.60

X3861 (25) ITT flat pack relay 42.5x31x10. 4PCO contacts. 24V coil £2.00; 100+ 1.20

FUSES

X3856 (3500) 20x5mm 250mA quickblow. 100/£2.00; 1000+ 0.012

X3853 (1200) Belling Lee ceramic wire ended 15x5mm 50mA 5/£1.00; 100+ 0.10

X3954 (480) Littlefuse SAFE-T-PLUS fuses. Radial lead, body 13.2x8 dia 62mA Pack of 10 £2.00

X3741 (1200) 20x5mm quickblow ceramic sand filled rated 10A PCB 10 £1.00

X3755 (160) PCB mntg ultra fast fuse by Buss 0.5A 9x9x5mm List 0.96 Our Price 3 for £1.00

X3754 (1000) Sub min PCB mntg 5A 0B fuse. 6x3mm dia List 0.48. Our Price 6/£1; 100+ 0.09

Some wire ended 20x5mm antir surge fuses

X3756 (800) 500mA

X3757 (300) 1A

X3758 (1000) 15A

All at 10 for £1.00

K931 SLEEVING PACK

Back in stock after some time, this extremely popular pack contains a great many sizes of sleeving. Lengths vary from 10 to 77mm with diameters from 1 to 40mm. Big variety of types and colours, too - PVC, silicone, neoprene, rubber in clear, pink, yellow, red, green, grey, black and white. Pack of 200 £3.50

K865 Electrolytics. 100 each of 28 different PC mntg caps from 0.1 to 1000µF. (Full listing of values on request) 2800 for £50.00

K7000 Resistors. 100 each of 30 different values from 5R6 to 680k. Sub min 1/8th watt 5% bandiered. Body size 3.2x1.9 (maybe one or two values larger) 3000 for £10

K540 Resistors. Assorted values and sizes from 1/4W to 2W, all with full length leads 500 for £3.00

K637 Integrated Circuits. Big range of linear and logic chips, all brand new and marked, 6 pin to 40 pin 100 for £5.00

K538 Diodes. Full spec small signal diodes like 1N4148. 1000 for £4.00

K898 Terminal Strips. Screw and 0.25" tab type, mostly PCB mntg from 3 to 12 way. A total of 40 ways for £1.00

K896 Jumper Leads. A total of 50 ribbon leads from 4 to 10 way, up to 170mm long, terminated one or both ends with PCB headers. 50 for £3.00

K905 Ceramic Plate Caps. A pack of physically small devices in a wide range of values up to 1000pF. 200 for £2.00

K549 Trimmer Caps. A small assortment of compression and film trimmers. 20 for £1.75

K930 Fuses. 20mm and 1.25" quick blow and anti surge types up to 20A rating. 100 for £4.00

HARDWARE

A selection of metric and self tapping screws, always useful to constructors. Quantities aren't vast, so mixed packs seems the best idea.

K933 M3 - Steel and stainless steel, some black in lengths from 12 to 30mm Panhead, c/sunk, buttonhead all included. All pozi. Pack of 200 £2.00

K934 M4 - Just 3 types - 16mm panhead poz; 16 and 25mm buttonhead black socket screw. Pack of 200 £2.00

K935 Self tappers. All small, No 2 and No 4, 1/4 to 1/2" long. All pozi, some black. Pack of 200 £2.00

X3899 (5000) M2 panhead pozi 8mm long 200/£2.00

A couple of knobs...

X3932 (150) 33.5dia x 18.5 with spun ally insert and black marker line. Screw fix for 6 or 6.35mm spindle. 3/£1; 100+ 0.20

X3940 (75) Ally finish over plastic, nice quality, to fit std spined spindle. 34 dia x 18.5. 3/£1

Connectors

Some 0.1 pitch headers and sockets, all for PCB mntg.

X3850 (450) Gold plated right angle plug, 18 way 4/£1.00; 100+ 0.12

X6801 (2500) Double row right angle plug, 20x2 way, 4/£1.00; 100+ 0.12

X6765 (750) 20 way socket. 4/£1.00; 100+ 0.12

X3952 (3000) Sub min 0.06" 4 way PCB mntg skt 10/£1.00; 100+ 0.06; 1000+ 0.04

X3937 (25) Veropins - double sided 1mm for PCBs. Normally 1.38/100 Pack of 1000 £6.00

X3929 (60) 14 DIL IDC plug, gold plated. 4/£1.00

X3941 (700) Surface mount metal co-ax skt. nice quality. 5/£1.00; 100+ 0.10

X3749 (20) Disk drive connector kit - 17w ds edge conn to 34w socket + power connector. £2.50

X3785 (200) TNC plug, long shank £1; 100+ 0.60

200 WATT INVERTERS Nicely cased units 12v input 240v output 150watt continuous, 200max. £49 ref L0762.

6.8MW HELIUM NEON LASERS New units, £65 ref L033
COINSL0TTOKENS You may have a use for these? mixed bag of 100 tokens £10 ref L020.

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £6/set. Ref F/XP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £4/set Ref F/TK1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set Ref F/EH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means - cause it to levitate. £10/set Ref F/GRA1.

WORLDS SMALLEST TESLA COIL/LIGHTNING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects. 'Plasma In a Jar', St Elmo's fire, Corona, excellent science project or conversation piece. £5/set Ref F/BTC1/LG5.

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £10/set Ref F/CVL1.

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £6/set Ref F/VS9.

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM too! DISCRETION ADVISED. £8/set Ref F/TJ5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £8/set Ref F/BHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £12/set Ref F/LC7.

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Delays gift, amazing gift, conversation piece, magic trick or science project. £6/set Ref F/ANT1K.

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £6/set Ref F/ULB1.

ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/SOUND AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £6/set Ref F/HGA7.

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £6/set Ref F/DOG2.

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £12/set Ref F/LLIST1.

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 Ref F/LLS1.

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £6/set Ref F/PSP4.

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £5/set Ref F/BD1.

ELECTROMAGNETIC GUN PLANS Projects a metal object a considerable distance - requires adult supervision. £5 ref F/EML2.

ELECTRIC MAN PLANS, SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £5/set Ref F/EMA1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £8/set Ref F/PM5.

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 Ref F/HVM7/

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

INFINITY TRANSMITTERS The ultimate 'bug' fits to any phone or line, undetectable, listen to the conversations in the room from anywhere in the world! 24 hours a day 7 days a week! Just call the number and press a button on the mini controller (supplied) and you can hear everything! Monitor conversations for as long as you choose £249 each, complete with leads and mini controller Ref L079. Undetectable with normal RF detectors, fitted in seconds, no batteries required, lasts forever!

SWITCHED MODE PSU'S 244 watt, +5 32A, +12 6A, -5 0.2A, -12 0.2A. There is also an optional 3.3v 25A rail available. 120/240v I/P. Cased, 175x90x145mm. IEC inlet Suitable for PC use (6 d/drive connectors 1 m/board). £10 ref PSU1.

VIDEO PROCESSOR UNITS/76v 10AH BATT/12V 8A TX Not too sure what the function of these units is but they certainly make good strippers! Measures 390X320X120mm, on the front are controls for scan speed, scan delay, scan mode, loads of connections on the rear, inside 2x 6v 10AH sealed lead acid batts, pcb's and a 8A? 12v toroidal transformer (mains in). Condition not known, may have one or two broken knobs due to poor storage. £17.50 ref VP2.

RETRO N I G H T S I G H T Recognition of a standing man at 300m in 1/4 moonlight, hermetically sealed, runs on 2 AA batteries, 80mm F1.5 lens, 20mw Infrared laser included. £325 ref RETRON.

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 Mhz but easily changed to cover 63-130 Mhz. Works with a common 9v (PP3) battery. 0.2W RF. £7 Ref 1001.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric mic. 8-30vdc. At 25-30v you will get nearly 2 watts! £12 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob yourself but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, inc speaker. £15 ref 1013.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w pulse handling, microphone included. £14 Ref 1014.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £20 Ref 1028.

STROBE LIGHT KIT Adjustable from 1-60 Hz (a lot faster than conventional strobes). Mains operated. £16 Ref 1037.

LIQUID LEVEL DETECTOR KIT Useful for tanks, ponds, baths, rain alarm, leak detector etc. Will switch 2A mains. £5 Ref 1081.

COMBINATION LOCK KIT 9 key, programmable, complete with keypad, will switch 2A mains, 9v dc operation. £10 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £6 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £9 ref 1131.

TELEPHONE BUG KIT Small bug powered by the 'phone line, starts transmitting as soon as the phone is picked up! £8 Ref 1135.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction control supplied with 12 LEDs (you can fit tracs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOURESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2A transformer also required. £8 ref 1069.

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc, adjustable sensitivity. £8 ref 1073.



Check out our
WEB SITE

<http://www.pavilion.co.uk/bull-electrical>

PREAMP MIXER KIT 3 input mono mixer, sep bass and treble controls plus individual level controls, 18vdc, input sens 100mA. £15 ref 1052.

METAL DETECTOR KIT Range 15-20cm, complete with case, 9vdc. £8 ref 1022.

SOUNDEFFECTS GENERATOR KIT Produces sounds ranging from bird chips to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

15 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-18vdc, can use ground plane, yaqi or open dipole. £69 ref 1021.

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9 ic design, pcb, lcd display and all components included. £29

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1, 640k, serial

*SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3 P&P PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS WELCOME (ACCESS VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500

FAX 01273 323077

E-mail bull@pavilion.co.uk

port, hard drive with min 100k free. £24.99
DIVING RODS Expensive technology cannot challenge the fool proof art of water diving, passed down from generation to generation. Seeing is believing. Use in the home, garden, countryside or desert, it's divinely simple! £4.99 a pair ref E3.

HUGE BUBBLE MAKING KIT You'll be amazed at the size of the bubbles you can achieve with this bubble making kit. Once you have got the knack it is possible to make bubbles of up to 40 feet long. £11.99 ref E9.

FM CORDLESS MICROPHONE This unit is an FM broadcasting station in miniature. 3 transistor transmitter with electret condenser mic - fet amp design result in maximum sensitivity and broad frequency response. 90-105mhz, 50-1500hz, 500 foot range in open country! PP3 battery required. £15.00 ref 15P42A.

MAGNETIC MARBLES They have been around for a number of years but still give pleasure to curiosity and amazement. A pack of 12 is just £3.99 ref GI/R20

STETHOSCOPES A fully functioning stethoscope for all those intricate projects. Enables you to listen to motors, pipes, heartbeats, walls, insects etc. £6 ref MAR66.

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £39.99 ref NIK39.

Miniature adjustable timers, 4 pole c/o output 3A 240v, HY1230S, 12vDC adjustable from 0-30 secs. £4.99

HY1260M, 12vDC adjustable from 0-60 mins. £4.99

HY2405S, 240v adjustable from 0-5 secs. £4.99

HY24060m, 240v adjustable from 0-60 mins. £6.99

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR29P1.

POWER SUPPLY fully cased with mains and op leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

9v DC POWER SUPPLY Standard plug in type 150ma 9v DC with lead and DC power plug. price for two is £2.99 ref AUG3P4.

COMPOSITE VIDEO KIT Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector. 150watt. 12v fan, iec inlet and on/off switch. £12 Ref EF6.

VENUS FLY TRAP KIT Grow your own carnivorous plant with this simple kit. £3 ref EF34.

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG6P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together! believed to cause rain! £3 a pair Ref EF29.

3' by 1' AMORPHOUS SOLAR PANELS 14.5v, 700mA 10 watts, aluminium frame, screw terminals, £44.95 ref MAG45.

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles! good to experiment with. £7 ref 7P30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £7 ref 7P36.

FLYING PARROTS Easily assembled kit that builds a parrot that actually flaps its wings and flies! 50 m range £6 ref EF2.

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 miles per hour! Range of over 200 metres! £7.99 ref R9.

BALLON MANUFACTURING KIT British made, small blob blows into a large, long lasting balloon. Hours of fun! £3.99 ref GI/E99R

9-0-9V 4A TRANSFORMERS, chassis mount. £7 ref L0T19A.

2.6 KILOWATT INVERTERS, Packed with batteries etc but as they weigh about 100kg CALLERS ONLY! £120.

MEGA LED DISPLAYS Build your self a clock or something with these mega 7 seg displays 55mm high, 38mm wide. 5 on a pcb for just £4.99 ref L0T16 or a bumper pack of 50 displays for just £29 ref L0T17.

CLEARANCE SECTION, MINIMUM ORDER

£15, NO TECHNICAL DETAILS AVAILABLE,

NO RETURNS, TRADE WELCOME.

2000 RESISTORS ON A REEL (SAME VALUE) 99P REF BAR340

AT LEAST 200 CAPACITORS (SAME VALUE) 99P REF BAR342

INFRA RED REMOTE CONTROLS JUST 99P REF BAR333

CIRCUIT BREAKERS, OUR CHOICE TO CLEAR 99P REF BAR335

MICROWAVE CONTROL PANELS TO CLEAR £2 REF BAR 329

2 TUBES OF CHIPS (2 TYPES OUR CHOICE) 90P REF BAR305

LOTTERY PREDICTOR MACHINE! JUST £1.50 REF BAR313

HELLA/ROVER ELECTRIC H/LAMP LEVELLER £2 REF BAR311

SINCLAIR CS 18" TYRES TO CLEAR AT JUST 75P REF BAR318

LARGE MAINS MOTORS (NEW) TO CLEAR AT 75P REF BAR310

MODEMS ETC FOR STRIPPING £2.50 EACH REF BAR324

110V LARGE MOTORS (NEW) TO CLEAR AT 50P REF BAR332

MODULATOR UNITS UNKNOWN SPEC JUST 50P REF BAR323

GX4000 GAMES COLOSSES JUST £4 REF BAR320

SMART CASE MEMORY STORAGE DEVICE, LOADS OF BITS INSIDE, PCB, MOTOR, CASE ETC. BUMPER PACK OF 5 COMPLETE UNITS TO CLEAR AT £2.50 (FOR 5) REF BAR 330.

2 CORE MAINS CABLE 2M LENGTHS PACK OF 4 £1 REF BAR337

PC USER/BASIC MANUALS, LOADS OF INFO. £1 REF BAR304

PCB STRIPPERS TO CLEAR AT 2 FOR 99P REF BAR341

3 M 3CORE MAINS CABLE AND 13A PLUG. 60P REF BAR325

WE BUY SURPLUS STOCK

FOR CASH

BUYERS DIRECT LINE 0860 425692

FREE CATALOGUE

100 PAGE CATALOGUE NOW

AVAILABLE, 45P STAMP OR FREE


ON REQUEST WITH ORDER.

Pico Releases PC Potential


Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.

Hardware and software are supplied together as a package - no more worries about incompatibility or complex set-up procedures. Unlike traditional 'plug in' data acquisition cards, they simply plug into the PC's parallel or serial port, making them ideal for use with portable PC's.

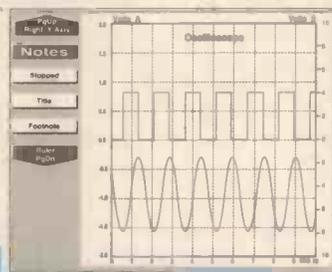Call for your Guide on 'Virtual Instrumentation'.



PicoScope
'Virtual instrument' software.

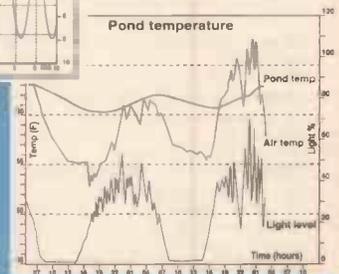

PicoLog
Advanced data logging software.

NEW from Pico TC-08 Thermocouple to PC Converter **8 channel Thermocouple Interface**

- Connects to your serial port - no power supply required.
- Supplied with PicoLog datalogging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs (B,E,J,K,N,R,S and T types)
- Resolution and accuracy dependant on thermocouple type. For type K the resolution is better than 0.1°C.

TC-08 £ 199

TC-08 + Calibration Certificate £ 224

complete with PicoLog, software drivers and connecting cable. A range of thermocouple probes is available.



SLA-16 & SLA-32 Logic Analysers **Pocket sized 16/32 channel Logic Analysers**

- Connects to PC serial port.
- Up to 50MHz sampling.
- Internal and external clock modes.
- 8K Trace Buffer.

SLA-16 £ 219
SLA-32 £ 349
with software, power supply and cables



ADC-10 **1 Channel 8 bit**

- Lowest cost in the Pico range
- Up to 22kHz sampling
- 0 -5V input range

Carriage UK free, Overseas £9 Oscilloscope Probes (x1, x10) £10



ADC-100 Virtual Instrument **Dual Channel 12 bit resolution**

- Digital Storage Scope
- Spectrum Analyser
- Frequency Meter
- Chart Recorder
- Data Logger
- Voltmeter

The ADC-100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field. Flexible input ranges ($\pm 200\text{mV}$ to $\pm 20\text{V}$) allows the unit to connect directly to a wide variety of signals.

ADC-100 with PicoScope £199
with PicoScope & PicoLog £219

The ADC-10 gives your computer a single channel of analog input. Simply plug into the parallel port.

ADC-10 with PicoScope £49
PicoScope & PicoLog £59

PICO TECHNOLOGY





MAIL ORDER ONLY • CALLERS BY APPOINTMENT

EPE MICROCONTROLLER P.I. TREASURE HUNTER

The latest MAGENTA DESIGN - highly stable & sensitive - with μ C control of all timing functions and advanced pulse separation techniques.

- New circuit design 1994
- High stability drift cancelling
- Easy to build & use
- No ground effect, works in seawater
- Detects gold, silver, ferrous & non-ferrous metals
- Efficient quartz controlled microcontroller pulse generation.
- Full kit with headphones & all hardware



KIT 847.....£63.95

DIGITAL LCD THERMOSTAT

A versatile thermostat using a thermistor probe and having an l.c.d. display. MIN/MAX memories, -10 to 110 degrees celsius, or can be set to read in Fahrenheit. Individually settable upper and lower switching temperatures allow close control, or alternatively allow a wide 'dead band' to be set which can result in substantial energy savings when used with domestic hot water systems. Ideal for greenhouse ventilation or heating control, aquaria, home brewing, etc. Mains powered, 10A SPCO relay output. Punched and printed case.

KIT 841.....£29.95

PORTABLE ULTRASONIC PEST SCARER

A powerful 23kHz ultrasound generator in a compact hand-held case. MOSFET output drives a special sealed transducer with intense pulses via a special tuned transformer. Sweeping frequency output is designed to give maximum output without any special setting up.

KIT 842.....£22.56

DIGITAL CAPACITANCE METER

A really professional looking project. Kit is supplied with a punched and printed front panel, case, p.c.b. and all components. Quartz controlled accuracy of 1%. Large clear 5 digit display and high speed operation. Ideal for beginners - as the μ F, nF and pF ranges give clear unambiguous read out of marked and unmarked capacitors from a few pF up to thousands of μ F.

KIT 493.....£39.95

ACOUSTIC PROBE

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches, and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers, and nosy parkers.

KIT 740.....£19.98

WINDICATOR

A novel wind speed indicator with LED read-out. Kit comes complete with sensor cups, and weatherproof sensing head. Mainspower unit £5.99 extra.

KIT 856.....£28.00

BUCCANEER I.B. METAL DETECTOR


An Induction Balance (I.B.) detector with audible output. Providing good sensitivity and easy construction.

COMPLETE KIT - INCLUDES ALL HARDWARE, HANDLE, SEARCH HEAD, PCB etc.

CIRCUIT REJECTS IRON WHILST PICKING UP GOLD, SILVER, COPPER etc.

A SOLID RELIABLE DESIGN.

KIT 719.....£54.99

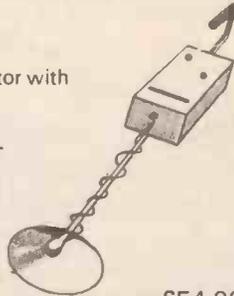

1000V & 500V INSULATION TESTER

Superb new design. Regulated output, efficient circuit. Dual-scale meter, compact case. Reads up to 200 Megohms.

Kit includes wound coil, cut-out case, meter scale, PCB & ALL components.

KIT 848.....£32.95



MOSFET MKII VARIABLE BENCH POWER SUPPLY 0-25V 2.5A.

Based on our MkI design and preserving all the features, but now with switching pre-regulator for much higher efficiency. Panel meters indicate Volts and Amps. Fully variable down to zero. Toroidal mains transformer. Kit includes punched and printed case and all parts. As featured in April 1994 EPE. An essential piece of equipment.

KIT 845.....£64.95



ULTRASONIC PEST SCARER

Keep pets/pests away from newly sown areas, fruit, vegetable and flower beds, children's play areas, patios etc. This project produces intense pulses of ultrasound which deter visiting animals.

- KIT INCLUDES ALL COMPONENTS, PCB & CASE
- EFFICIENT 100V TRANSDUCER OUTPUT
- COMPLETELY INAUDIBLE TO HUMANS

KIT 812.....£14.81



SPACEWRITER

An innovative and exciting project. Wave the wand through the air and your message appears. Programmable to hold any message up to 16 digits long. Comes pre-loaded with "MERRY XMAS". Kit includes PCB, all components & tube + instructions for message loading.

KIT 849.....£16.99

12V EPROM ERASER

A safe low cost eraser for up to 4 EPROMS at a time in less than 20 minutes. Operates from a 12V supply (400mA). Used extensively for mobile work - updating equipment in the field etc. Also in educational situations where mains supplies are not allowed. Safety interlock prevents contact with UV.

KIT 790.....£28.51

MOSFET 25V 2.5A POWER SUPPLY

High performance design has made this one of our classic kits. Two panel meters indicate Volts and Amps. Variable from 0-25 Volts and current limit control from 0-2.5A. Rugged power MOSFET output stage. Toroidal mains transformer.

KIT 769.....£56.82

INSULATION TESTER

A reliable and neat electronic tester which checks insulation resistance of wiring and appliances etc., at 500 Volts. The unit is battery powered, simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. A very popular college project.

KIT 444.....£22.37

DIGITAL COMBINATION LOCK

Digital lock with 12 key keypad. Entering a four digit code operates a 250V 16A relay. A special anti-tamper circuit permits the relay board to be mounted remotely. Ideal car immobiliser, operates from 12V. Drilled case, brushed aluminium keypad.

KIT 840.....£19.86

E.E. TREASURE HUNTER P.I. METAL DETECTOR MKI

Magenta's highly developed & acclaimed design. Quartz crystal controlled circuit MOSFET coil drive. D.C. coupled amplification. Full kit includes PCB, handle, case & search coil.

- KIT INC. HEADPHONES
- EFFICIENT CMOS DESIGN
- POWERFUL COIL DRIVE

- DETECTS FERROUS AND NON-FERROUS METAL - GOLD, SILVER, COPPER ETC.
- 190mm SEARCH COIL
- NO 'GROUND EFFECT'

KIT 815.....£45.95



Comstep PC Computer Interface and Driver board

Drives two motors from PC parallel port. Supplied with comprehensive software. Needs 12Volt 1A supply.

With 2-200 Step Motors

KIT 846.....£67.00

Power Booster for Comstep

Adds to Comstep and allows motors up to 4 Amps to be driven. Two boosters drive two motors from a single Comstep. Uses standard Comstep software.

With MD24 Motors

KIT 850.....£39.95

EDUCATIONAL BOOK & PACK

ADVENTURES WITH ELECTRONICS

The classic book by Tom Duncan used throughout schools. Very well illustrated, ideal first book for age 10 on. No soldering. Uses an S.DEC breadboard.

Book & Components.....£28.95

Book only.....£7.99

Versatile Stepping motor Interface

A Magenta design, gives Half and Full-Wave drive. Up to 1Amp and 24Volts. CMOS inputs - Drive from logic or computer port. Needs power supply.

KIT 816.....£9.82

DC Motor/Gearboxes

Our Popular and Versatile DC motor/Gearbox sets. Ideal for Models, Robots, Buggies etc. 1-5 to 4-5V Multi ratio gearbox gives wide range of speeds.

LARGE TYPE - MGL £6.95

SMALL - MGS - £4.77



Stepping Motors

MD38...Mini 48 step...£8.65

MD35...Std 48 step...£12.98


MD200...200 step...£16.80

MD24...Large 200 step...£22.95

PIC DEVELOPMENT & TRAINING SYSTEM PIC

YOUR KEY TO ANOTHER NEW AGE OF ELECTRONICS

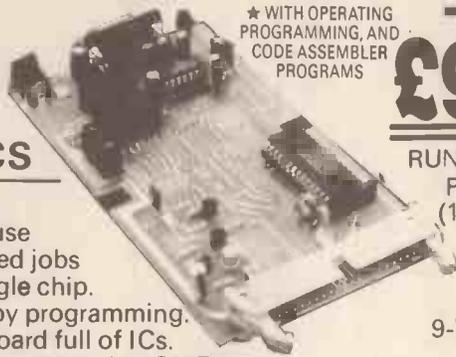PICs are being used more and more because they allow complicated jobs to be done with a single chip. All the work is done by programming. One PIC replaces a board full of ICs. Saving time, space, power, and MONEY.



★ WITH OPERATING PROGRAMMING, AND CODE ASSEMBLER PROGRAMS

£99 INCLUDING VAT

+ £3.00 p&p

RUNS WITH ANY PC POWER SUPPLY (12V at 200mA)

£8.99

PC LEADS

9-WAY **£6.00**

25-WAY **£7.00**

HOW DO I START WITH PICs?

- STEP 1** – Buy the PIC-DATS Development & Training System
STEP 2 – Follow May & June '95 EPE Series – showing how to program for practical applications
STEP 3 – Start writing and testing your own programs

PIC PROJECT – LIGHT CONTROLLER DEVELOPMENT SYSTEM (NO SOFTWARE)

A real-world application for a PIC microchip. This project can be made to do just what you chose by writing your own software. It can be programmed to work as a 4-Channel Light Chaser or a simple controller for domestic lighting. Zero volt crossing signal is provided and there is a 4x3 matrix keypad. (Less case).

Kit 855.....**£35.95**

PIC 16C84 DISPLAY DRIVER

NEW!

USES PIC16C84 to drive a 2 LINE x 16 LCD Display.

Another **NEW** PIC project from Magenta. Supplied with PCB, industry standard 2 line x 16 character display, PIC16C84, components, and software to include in your own programs. Full display data and program service code is applied. Ideal development base for meters, terminals, calculators, counters, timers etc. Just waiting for your application.

KIT Ref. 860.....**£17.99**

SIMPLE PIC16C84 PROGRAMMER

NEW!

Based on the design in February '96 EPE. Magenta have made a proper PCB for this circuit and a full kit of parts. The PCB eliminates the risk of layout errors. Additional contact points are provided to allow connection to RA and unused RB pins when testing programs. Kit includes 1 – PIC16C84 chip, lead, connector and all software.

Programmer Kit – with software disk, lead, connector and PIC16C84 chip, including PCB.
 Kit 857.....**£12.99**

Power Supply Unit 12V-14V.....**£3.99**

Extra PIC16C84 Chips.....**£7.36**

KIT HIGHLIGHT

We have noticed a number of customers buying the PIC 16C84 Programmer and Kit 855. This is an ideal combination. Kit 855 allows Mains Power to be controlled safely using a PIC16C84. Experiment with chaser patterns and dimming using phase control. Special kit with all components and blank PIC16C84 and reprints.
 Kit 855/16C84.....**£39.95**

68000 DEVELOPMENT AND TRAINING SYSTEM

Never before at this price! Our own 68000 board kit. Used all over the world in schools and universities. Double Eurocard PCB with RAM, ROM, and I/O. Full featured MONITOR and LINE BY LINE ASSEMBLER ON BOARD. Just needs power, and a serial link to your PC. Supplied with full data and applications course. Use to learn, or as a stand-alone computer board.

£55.00!

Kit Ref 601



BAT DETECTOR



An excellent circuit which reduces ultrasound frequencies between 20 and 100 kHz to the normal (human) audible range. Operating rather like a radio receiver the circuit allows the listener to tune-in to the ultrasonic frequencies of interest. Listening to Bats is fascinating, and it is possible to identify various different types using this project. Other uses have been found in industry for vibration monitoring etc.

KIT 814.....**£21.44**

Mini-Lab & Micro Lab Electronics Teach-In 7

As featured in EPE and now published as Teach-In 7. All parts are supplied by Magenta. Teach-In 7 is £3.95 from us or EPE Full Mini Lab Kit – £119.95 – Power supply extra – £22.55 Full Micro Lab Kit – £155.95 Built Micro Lab – £189.95

MAGENTA

Tel: 01283 565435 Fax: 01283 546932 All prices include VAT. Add £3.00 p&P.



Tel (0191) 251 4363
 Fax (0191) 252 2296
ELECTRONIC COMPONENTS
 Station Road, Cullercoats,
 Tyne & Wear
 NE30 4PQ
 U.K.

4000 Series		74HC Series		74LS Series	
4000	£0.17	74HC00	£0.20	74LS42	£0.25
4001	£0.20	74HC02	£0.21	74LS47	£0.72
4002	£0.17	74HC03	£0.21	74LS51	£0.24
4006	£0.40	74HC04	£0.18	74LS73	£0.40
4007	£0.18	74HC08	£0.21	74LS74	£0.25
4008	£0.31	74HC10	£0.16	74LS75	£0.25
4009	£0.19	74HC12	£0.20	74LS83	£0.31
4010	£0.23	74HC14	£0.22	74LS85	£0.35
4011	£0.20	74HC20	£0.28	74LS86	£0.20
4012	£0.16	74HC27	£0.16	74LS90	£0.48
4013	£0.19	74HC30	£0.22	74LS92	£0.35
4014	£0.30	74HC32	£0.21	74LS93	£0.42
4015	£0.24	74HC42	£0.25	74LS107	£0.23
4016	£0.30	74HC73	£0.40	74LS109	£0.21
4017	£0.31	74HC74	£0.23	74LS112	£0.21
4018	£0.27	74HC75	£0.40	74LS113	£0.21
4019	£0.48	74HC76	£0.20	74LS114	£0.21
4020	£0.31	74HC85	£0.24	74LS122	£0.31
4021	£0.31	74HC86	£0.22	74LS123	£0.31
4022	£0.32	74HC107	£0.40	74LS125	£0.27
4023	£0.16	74HC123	£0.33	74LS126	£0.25
4024	£0.32	74HC125	£0.24	74LS132	£0.21
4025	£0.15	74HC126	£0.46	74LS133	£0.30
4026	£0.78	74HC132	£0.37	74LS136	£0.16
4027	£0.26	74HC133	£0.29	74LS138	£0.40
4028	£0.34	74HC138	£0.25	74LS139	£0.25
4029	£0.40	74HC139	£0.35	74LS145	£0.26
4030	£0.17	74HC151	£0.33	74LS147	£1.26
4031	£0.70	74HC153	£0.27	74LS148	£0.70
4033	£0.56	74HC154	£0.85	74LS151	£0.25
4034	£1.24	74HC157	£0.40	74LS153	£0.25
4035	£0.31	74HC158	£0.25	74LS154	£0.70
4040	£0.38	74HC160	£0.64	74LS155	£0.25
4041	£0.31	74HC161	£0.28	74LS156	£0.36
4042	£0.22	74HC162	£0.45	74LS157	£0.22
4043	£0.28	74HC163	£0.27	74LS158	£0.21
4044	£0.35	74HC164	£0.35	74LS161	£0.48
4046	£0.32	74HC165	£0.35	74LS161	£0.32
4047	£0.38	74HC173	£0.38	74LS162	£0.44
4048	£0.28	74HC174	£0.27	74LS163	£0.44
4049	£0.22	74HC175	£0.27	74LS164	£0.24
4050	£0.26	74HC192	£0.45	74LS165	£0.48
4051	£0.43	74HC195	£0.32	74LS170	£0.30
4052	£0.32	74HC240	£0.37	74LS173	£0.24
4053	£0.40	74HC241	£0.37	74LS174	£0.24
4054	£0.56	74HC243	£0.48	74LS175	£0.24
4055	£0.34	74HC244	£0.42	74LS190	£0.60
4060	£0.48	74HC245	£0.46	74LS191	£0.60
4063	£0.29	74HC251	£0.25	74LS192	£0.60
4066	£0.22	74HC253	£0.25	74LS193	£0.24
4067	£0.20	74HC257	£0.25	74LS195	£0.24
4068	£0.16	74HC259	£0.57	74LS196	£0.24
4069	£0.20	74HC273	£0.35	74LS197	£0.24
4070	£0.26	74HC299	£0.64	74LS221	£0.40
4071	£0.22	74HC356	£0.45	74LS240	£0.32
4072	£0.17	74HC365	£0.34	74LS241	£0.32
4073	£0.17	74HC367	£0.25	74LS242	£0.32
4075	£0.17	74HC368	£0.25	74LS243	£0.30
4076	£0.30	74HC373	£0.35	74LS244	£0.40
4077	£0.28	74HC374	£0.40	74LS245	£0.60
4078	£0.20	74HC390	£0.52	74LS247	£0.32
4081	£0.23	74HC393	£0.38	74LS251	£0.24
4082	£0.21	74HC423	£0.37	74LS257	£0.24
4085	£0.28	74HC553	£0.42	74LS258	£0.24
4086	£0.26	74HC563	£0.48	74LS266	£0.14
4089	£0.55	74HC564	£0.48	74LS273	£0.32
4093	£0.22	74HC573	£0.43	74LS279	£0.25
4094	£0.31	74HC574	£0.45	74LS365	£0.21
4095	£0.56	74HC640	£0.73	74LS367	£0.21
4097	£1.20	74HC688	£0.64	74LS368	£0.21
4098	£0.48	74HC4002	£0.16	74LS373	£0.33
4099	£0.38	74HC4017	£0.64	74LS374	£0.34
4502	£0.38	74HC4020	£0.36	74LS375	£0.34
4503	£0.40	74HC4040	£0.45	74LS377	£0.32
4508	£1.40	74HC4049	£0.25	74LS378	£0.62
4510	£0.36	74HC4050	£0.24	74LS393	£0.24
4511	£0.36	74HC4060	£0.44	74LS398	£0.24
4512	£0.32	74HC4075	£0.27	74LS395	£0.26
4514	£0.77	74HC4078	£0.32	74LS399	£0.62
4515	£0.99	74HC4511	£0.64	74LS670	£0.69
4516	£0.44	74HC4514	£0.84		
4518	£0.44	74HC4538	£0.41		
4520	£0.43	74HC4543	£0.90		
4521	£0.62	74LS Series			
4522	£0.40	74LS00	£0.20	AD524AD	£23.04
4527	£0.40	74LS01	£0.14	AD548JN	£1.62
4528	£0.40	74LS02	£0.29	AD592AN	£4.52
4529	£0.44	74LS03	£0.29	AD595AC	£14.64
4532	£0.32	74LS04	£0.21	AD620AN	£9.88
4534	£2.48	74LS05	£0.14	AD625JN	£16.20
4536	£1.00	74LS07	£0.32	AD633JN	£8.25
4538	£0.37	74LS08	£0.23	AD648JN	£2.57
4541	£0.33	74LS09	£0.14	AD652AQ	£14.88
4543	£0.49	74LS10	£0.14	AD654JN	£7.25
4555	£0.34	74LS11	£0.17	AD698AP	£23.28
4556	£0.40	74LS12	£0.14	AD707JN	£2.24
4560	£1.18	74LS13	£0.14	AD708JN	£5.69
4566	£1.96	74LS14	£0.21	AD711JN	£1.51
4572	£0.25	74LS15	£0.14	AD712JN	£2.38
4584	£0.24	74LS20	£0.16	AD736JN	£8.75
4585	£0.47	74LS21	£0.14	AD795JN	£5.94
4724	£0.70	74LS22	£0.14	AD797AN	£8.69
40106	£0.37	74LS26	£0.14	AD8112AN	£6.32
40109	£0.58	74LS27	£0.14	AD813AN	£8.81
40163	£0.46	74LS30	£0.20	AD817AN	£3.85
40174	£0.34	74LS32	£0.21	AD708JN	£5.69
40175	£0.36	74LS37	£0.14	AD711JN	£1.51
40193	£0.60	74LS38	£0.19	AD829JN	£6.41
		74LS40	£0.14	AD830AN	£6.14

AD847JN	£6.50	TBA800	£0.70	BY126	£0.13	AC128	£0.40	BC338	£0.10	BDS53C	£0.47
AD896KN	£7.73	TBA810S	£0.64	BY127	£0.18	AC187	£0.48	BC338-25	£0.10	BDS54C	£0.50
ADEL2020AN	£2.06	TB820M	£0.30	CA741CE	£0.39	AC188	£0.18	BC348B	£0.14	BF180	£0.31
ADM222AAH	£3.55	TDA102A	£1.49	CA747CE	£0.39	AC189	£3.84	BC357	£0.75	BF182	£0.31
ADM232AAH	£3.55	TDA1170S	£2.48	CA3046	£0.37	AC197	£1.67	BC393	£0.73	BF185	£0.58
ADM485JN	£2.97	TDA2002	£1.04	CA3059	£1.16	AD149	£0.17	BC411	£0.13	BF194	£0.31
ADM690AN	£5.13	TDA2004	£3.11	CA3080E	£0.73	AD162	£0.92	BC44C	£0.40	BF194B	£0.19
ADM691AN	£6.48	TDA2030	£1.18	CA3130E	£0.98	BC107	£0.16	BC461	£0.40	BF195	£0.19
ADM695AN	£6.48	TDA2050V	£3.98	CA3140E	£0.51	BC107B	£0.17	BC463	£0.29	BF244	£0.35
ADM699AN	£3.58	TEA5115	£3.11	CA3189E	£1.22	BC108	£0.14	BC478	£0.32	BF244B	£0.40
AMP04FP	£10.94	TL061CP	£0.35	CA3240E	£1.12	BC108A	£0.14	BC479	£0.32	BF248	£0.35
BU704GP	£8.56	TL062CP	£0.60	DG121CJ	£1.55	BC108C	£0.16	BC490	£0.24	BF257	£0.33
CA741CE	£0.39	TL064CN	£0.72	DG121CJ	£1.55	BC109	£0.17	BC516	£0.22	BF259	£0.33
CA747CE	£0.39	TL071CP	£0.48	DG141DJ	£4.19	BC109C	£0.18	BC517	£0.20	BF337	£0.40
CA3046	£0.37	TL072CP	£0.50	DG142DJ	£4.19	BC11	£0.41	BC527	£0.20	BF355	£0.38
CA3059	£1.16	TL074CN	£0.58	EL2020CN	£4.99	BC115	£0.41	BC528	£0.20	BF423	£0.10
CA3080E	£0.73	TL081	£0.33	EL2030CN	£5.67	BC116	£0.41	BC537	£0.20	BF451	£0.19
CA3130E	£0.98	TL082CP	£0.54	EL2030CN	£5.67	BC118	£0.41	BC546B	£0.08	BF459	£0.38
CA3140E	£0.51	TL084CN	£0.63	EL2030CN	£5.67	BC12	£0.28	BC546C	£0.08	BF469	£0.36
CA3189E	£1.22	TL094CN	£1.49	EL2030CN	£5.67	BC134	£0.36	BC547B	£0.09	BF492	£0.36
CA3240E	£1.12	TL7705ACP	£1.62	EL2030CN	£5.67	BC135	£0.36	BC547C	£0.09	BF494	£0.31
DG211CJ	£1.55	TL7705ACP	£1.62	EL2030CN	£5.67	BC140	£0.25	BC548C	£0.08	BF498	£0.32
DG212CJ	£1.55	TL7705ACP	£1.62	EL2030CN	£5.67	BC141	£0.27	BC549C	£0.10	BF550	£0.30
DG411DJ	£4.19	TL7705ACP	£1.62	EL2030CN	£5.67	BC142	£0.31	BC550C	£0.10	BF551	£0.25
DG412DJ	£4.19	TL7705ACP	£1.62	EL2030CN	£5.67	BC143	£0.31	BC551C	£0.10	BF552	£0.25
EL2020CN	£4.99	TL7705ACP	£1.62	EL2030CN	£5.67	BC149	£0.21	BC557B	£0.08	BS107	£0.21
EL2030CN	£5.67	TL7705ACP	£1.62	EL2030CN	£5.67	BC154	£0.36	BC557C	£0.08	BS170	£0.23
ICL7106	£2.80	TL7705ACP	£1.62	EL2030CN	£5.67	BC157	£0.12	BC558C	£0.08	BSW66	£1.35
ICL761DCPA	£1.06	TL7705ACP	£1.62	EL2030CN	£5.67	BC159	£0.12	BC559C	£0.08	BU126	£1.35
ICL7621	£1.70	TL7705ACP	£1.62	EL2030CN	£5.67	BC160	£0.28	BC560A	£0.09	BU205	£1.41
ICL8038	£5.25	TL7705ACP	£1.62	EL2030CN	£5.67	BC170	£0.16	BC560B	£0.09	BU208A	£1.24
ICM7555	£0.36	TL7705ACP	£1.62	EL2030CN	£5.67	BC170B	£0.16	BC637	£0.21	BU326A	£1.40
ICM7556	£0.98	TL7705ACP	£1.62	EL2030CN	£5.67	BC171	£0.11	BC638	£0.21	BU500	£1.54
L165V	£2.63	TL7705ACP	£1.62	EL2030CN	£5.67	BC171B	£0.16	BC639	£0.21	BU508A	£1.42
L272M	£1.89	TL7705ACP	£1.62	EL2030CN	£5.67	BC172	£0.13	BC640	£0.21	BU508D	£1.44
L298	£6.99	TL7705ACP	£1.62	EL2030CN	£5.67	BC172B	£0.13	BC641	£0.22	BU508E	£1.74
LF347N	£0.86	TL7705ACP	£1.62	EL2030CN	£5.67	BC177	£0.01	BC642	£0.20	BU506	£1.06
LF351N	£0.43	TL7705ACP	£1.62	EL2030CN	£5.67	BC178	£0.18	BC643	£0.20	BUT11A	£1.30
LF353N	£0.42	TL7705ACP	£1.62	EL2030CN	£5.67	BC179	£0.18	BC644	£0.20	BUT11AF	£1.30
LM301A	£0.84	TL7705ACP	£1.62	EL2030CN	£5.67	BC179A	£0.17	BC645	£0.21	BUX84	£0.78
LM308N	£0.58	TL7705ACP	£1.62	EL2030CN	£5.6						

EVERYDAY PRACTICAL ELECTRONICS

VOL. 25 No. 5

MAY '96

Editorial Offices:
EVERYDAY PRACTICAL ELECTRONICS EDITORIAL
ALLEN HOUSE, EAST BOROUGH, WIMBORNE
DORSET BH21 1PF
Phone: Wimborne (01202) 881749
Fax: (01202) 841692. DX: Wimborne 45314
**Due to the cost we cannot reply to orders or queries
by Fax.**

See notes on Readers' Enquiries below – we regret lengthy technical enquiries cannot be answered over the telephone.

Advertisement Offices:
EVERYDAY PRACTICAL ELECTRONICS
ADVERTISEMENTS
HOLLAND WOOD HOUSE, CHURCH LANE
GREAT HOLLAND, ESSEX CO13 0JS
Phone/Fax: (01255) 850596

TWENTY YEARS ON

Whilst looking at some past issues of *Everyday Electronics*, to see when a particular advertiser first started placing ads, I came to the January 1976 issue. (Incidentally the advertiser is Magenta Electronics who have regularly advertised in our pages since 1976.) What first caught my eye was a picture of yours truly holding a radio control transmitter in a project heading photograph – I must have been very young!

Further inspection of the issue revealed an *Easy to Build Digital Clock* by P. J. Fischer; that clock is still keeping perfect time in my office twenty years later. It even passed the electrical safety check, now required for office equipment, with flying colours. I wonder if any other readers have projects built twenty or more years ago still in daily use; please let me know if you have.


SUBSCRIPTIONS

Two other items in that issue are also of interest; one is the announcement of the closure of the *Everyday Electronics Subscription Service*, "due to the escalating costs on packing and postage". Although I was the Assistant Editor at that time I cannot recall this event, perhaps subscriptions were not significant then. Anyway I'm pleased to say that the service was obviously reintroduced some time later – I don't know when – and today it represents an excellent and economical way of receiving your magazine each month. In fact the subscription rate in the UK is now £5.40 less than the cover price of twelve issues.

SINCLAIR

The final item of interest in the '76 issue is a news report in *Shop Talk* (our longest running column dating from the very first issue in 1971) about the Sinclair Black Watch. Apparently one Mike Kenward, who wrote the column at that time, apologised for not publishing a review of the kit, which had still not turned up from Sinclair – not unusual as I recall.

Unfortunately, I well remember putting the kit together (it finally arrived two months later), not a particularly easy operation. I also remember the watch was bulky to wear, the angular edges of the case caught on everything and the batteries went flat after about a week if you wore the watch in bed. This was because the display would come on if there was any pressure on the watch face. In short it did not match the longevity of our clock project. All things Sinclair are the subject of a recent exhibition and a book – see our news pages for more details.

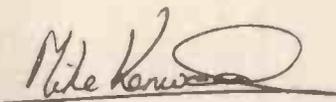

SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £24. Overseas: £30 (£47.50 airmail). Cheques or bank drafts (in £ sterling only) payable to *Everyday Practical Electronics* and sent to EPE Subscriptions Dept., Allen House, East Borough, Wimborne,

Dorset BH21 1PF. Tel: 01202 881749. Subscriptions start with the next available issue. We accept Access (MasterCard) or Visa. (For past issues see the *Back Issues* page).

BINDERS

Binders to hold one volume (12 issues) are available from the above address. These are finished in blue p.v.c., printed with the magazine logo in gold on the spine. Price £5.95 plus £3.50 post and packing (for overseas readers the postage is £6.00 to everywhere except Australia and Papua New Guinea which cost £10.50). *Normally sent within seven days but please allow 28 days for delivery – more for overseas orders.*

Payment in £ sterling only please. Visa and Access (MasterCard) accepted, minimum credit card order £5. Send or phone your card number and card expiry date with your name, address etc.



Editor: MIKE KENWARD
Secretary: PAM BROWN
Deputy Editor: DAVID BARRINGTON
Technical Editor: JOHN BECKER
Business Manager: DAVID J. LEAVER
Subscriptions: MARILYN GOLDBERG
Editorial: Wimborne (01202) 881749
Advertisement Manager:
PETER J. MEW, Frinton (01255) 850596
Advertisement Copy Controller:
DEREK NEW, Wimborne (01202) 882299

READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply *must* be accompanied by a stamped self-addressed envelope or a self-addressed envelope and international reply coupons. **Due to the cost we cannot reply to queries by Fax.**

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it.

COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data, or answer queries, on projects that are more than five years old.


ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY PRACTICAL ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or in inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the UK. Readers should check the law before buying any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use or ownership. The laws vary from country to country; overseas readers should check local laws.

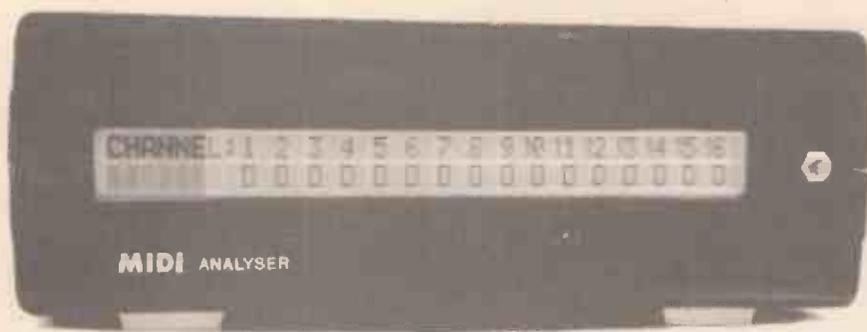

Screen display for 16-Channel monitoring

which for Screen 1 is converted to decimal for presentation on the display. The Analyser's other screens present this data in different ways.

Note On and Note Off data are processed further. Together, they are used to increment and decrement a counter which indicates on the display the number of notes held down simultaneously (polyphony). Note On data is broken down even further to provide an actual note name, C#, for example, as well as the octave number and velocity information.

MIDI VARIATIONS

MIDI data is supposed to conform to a stringent specification. Different manufacturers, however, may interpret the rules in slightly different ways. For example, some synthesisers use *running status*, which uses fewer MIDI bytes by only sending one status byte followed by several data bytes, to play a sequence of notes. This can be preferable to sending a separate status byte with each individual note.

Equipment that receives MIDI data must be capable of understanding these

differences, which, of course, makes their software much more complex. Provided the equipment design does not deviate from the accepted MIDI standard, there should be no problem.

CIRCUIT DESCRIPTION

The complete circuit diagram for the MIDI Analyser is shown in Fig. 4. MIDI data entering the Analyser via the In socket SK1 drives the l.e.d. in the optoisolator, IC2, via resistor R1. Diode D1 protects IC2 against reverse polarity.

Serial MIDI data from the collector, pin 5, of the phototransistor in IC2, is fed directly into the microcontroller IC1 at its RB0 input pin 6. This signal is also buffered by transistors TR1 and TR2, before being fed to the Thru socket SK2.

The values of resistors R2 and R3 have been chosen to ensure that TR1 switches on at the same point that the microcontroller detects a logic low on the RB0 input. Resistor R4 is used to bias the phototransistor in IC2 to equalise its switch-on and switch-off times. Transistor TR2 acts as a current sink for the MIDI current loop.

Crystal X1 and capacitors C1 and C2 set the microcontroller's clock rate at 8MHz. Port B of the microcontroller is connected to the l.c.d. module, using port bits RB1 to RB7. Port A provides the l.c.d. with bit 0, from pin RA0. This arrangement has been used because bit zero of Port B (RB0) is used by the microcontroller as an interrupt source responding to incoming serial data.

Adjustment of the display contrast is provided by preset potentiometer VR1, which is connected across the power supply rails.

Power for the MIDI Analyser is supplied by four AA cells giving about 6V. Diode D2 drops this voltage by about 0.6V, which provides the l.c.d. module and microcontroller with a little over 5V.

CONSTRUCTION

The specified box has two removable plastic rectangular panels which slot into guides at the front and back. The rear panel accommodates the On/Off switch S1 and has two holes for the In and Thru sockets SK1 and SK2.

The front panel accommodates the Screen Select switch S2 and the l.c.d. module X2. The p.c.b. mounting holes should line up with four of the many pre-formed mounting studs in the base of the box.

Component positioning on the panels can be seen in the photographs. Take care cutting out the slot for the l.c.d. and leave room for switch S2 to fit alongside it. Holes for MIDI sockets SK1, SK2 are best left until the assembled p.c.b. can be used to confirm their best position. On the prototype, their centres were 19mm above the base of the panel and 38mm apart.

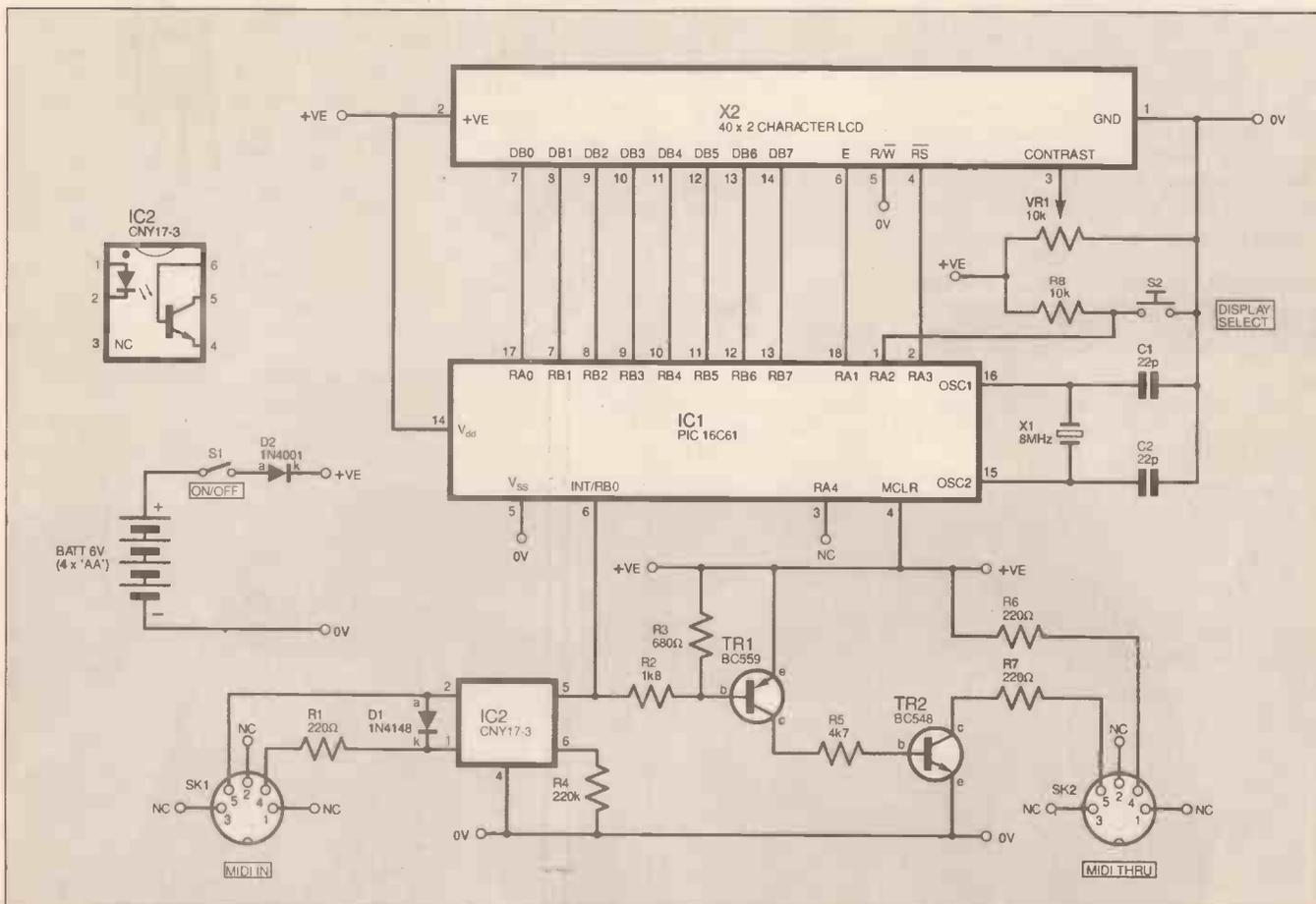


Fig. 4. Complete circuit diagram for the MIDI Analyser. Note that switch S2 is a push-to-make and release-to-break type.

MIDI ANALYSER

COMPONENTS

Resistors

R1, R6,	220Ω (3 off)
R7	1k8
R2	680Ω
R3	220k
R4	4k7
R5	10k

See
**SHOP
TALK**
Page

All 0.25W 5% carbon film

Potentiometers

VR1	10k sub-min. horizontal preset, lin
-----	-------------------------------------

Capacitors

C1, C2	22p ceramic disc (2 off)
--------	--------------------------

Semiconductors

D1	1N4148 signal diode
D2	1N4001 rectifier diode
TR1	BC559 <i>npn</i> transistor
TR2	BC548 <i>nnp</i> transistor
IC1	PIC16C61 microcontroller, pre-programmed (see text)
IC2	CNY17-3 opto-isolator

Miscellaneous

X1	8MHz crystal
X2	LM018L or TLCM4021 40-character x 2-line intelligent l.c.d. module
S1	s.p.s.t. rocker switch
S2	push-to-make switch, sub-min.

SK1, SK2 p.c.b. mounting 5-pin 180° DIN socket (2 off)

Printed circuit board, available from the *EPE PCB Service*, code 992; ABS plastic case, internal dimensions 197mm x 145mm x 55mm, removeable front and rear panels; 18-pin d.i.l. socket; 6-pin d.i.l. socket; battery holder (long type) for 4 x AA cells; battery clip (PP3 type), nuts and bolts to suit; connecting wire; cable ties; solder, etc.

Approx Cost
Guidance Only

£39




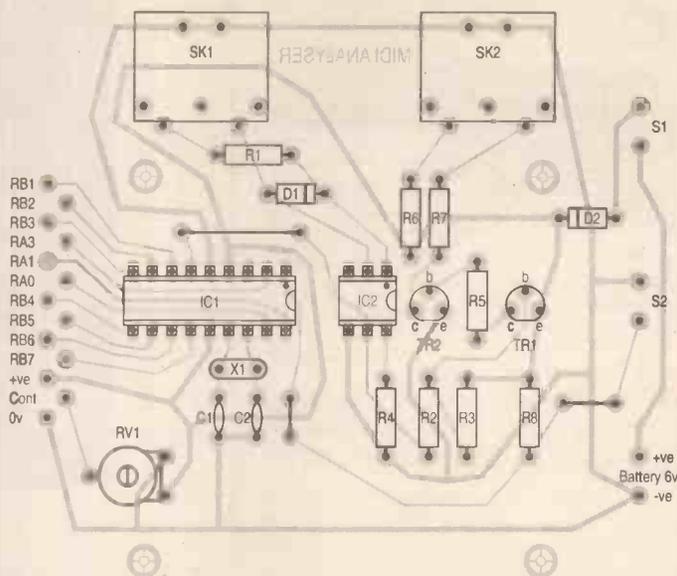


Fig. 5. Printed circuit board component layout and actual size copper foil master for the MIDI Analyser.

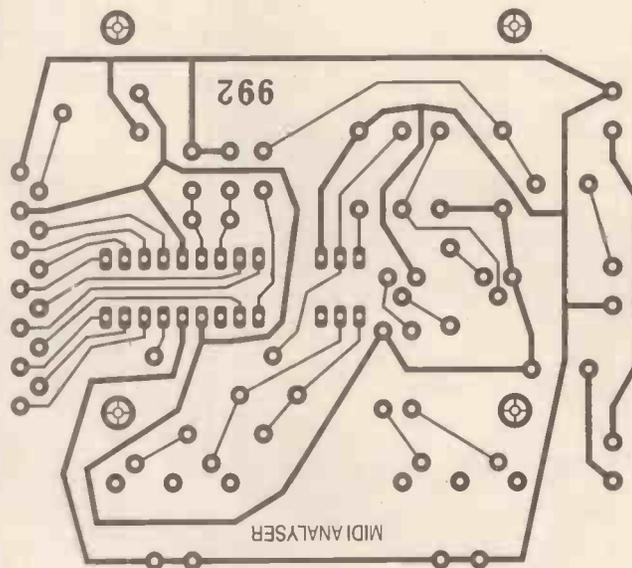

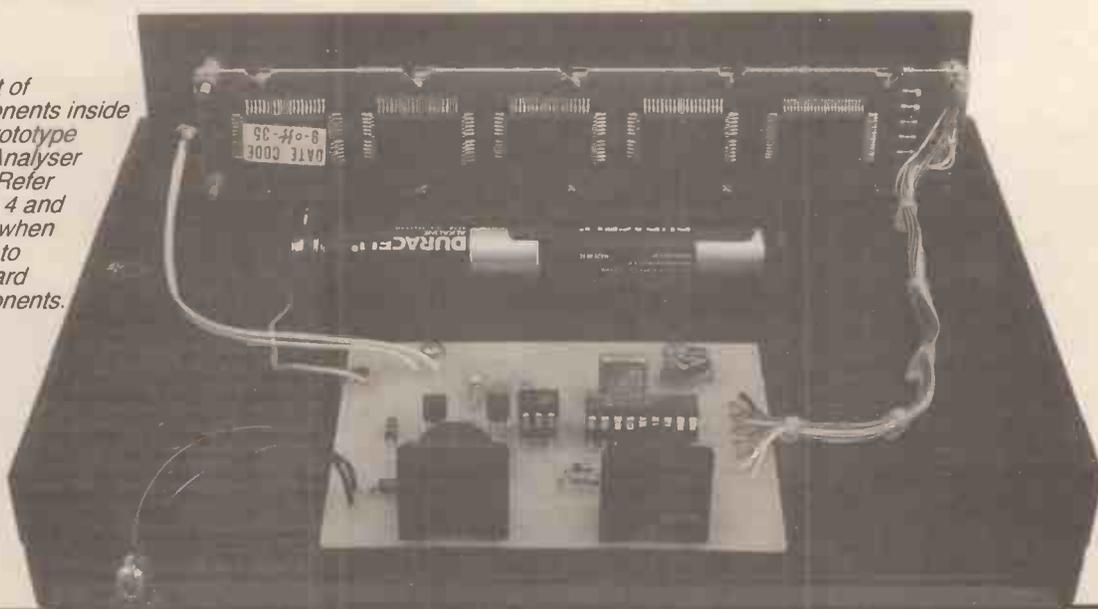Layout of components inside the prototype MIDI Analyser case. Refer to Fig. 4 and Fig. 6 when wiring to off-board components.



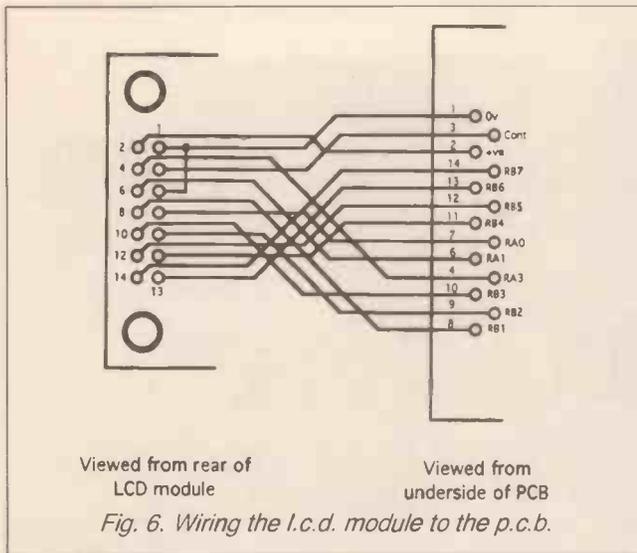

One of the display module mounting bolts glued to the rear of the front panel.

Details of the topside printed circuit board (p.c.b.) component layout and copper foil master track pattern are shown in Fig. 5. This board is available from the *EPE PCB Service*, code 992.

Assemble the board in the usual way – smaller components first, working steadily up through the large ones, paying attention to polarities where marked. Check your work thoroughly!

With the main p.c.b. fully assembled and loosely placed in position, wire the l.c.d. module to it, referring to Fig. 6. Do not forget to link together pin 1 and pin 5 on the l.c.d. module. Next, wire up switches S1 and S2

roughly flush with the front of the module.

Remove the four thin plastic panel guides (two on each half of the box casing) as these will interfere with the finished panels when they are slid into the recesses of the box casing. Dab a spot of glue (e.g. *Araldite*) onto each of the screwheads and place the module onto the rear side of the front panel, making sure that it is evenly aligned with the rectangular cut out. When the glue has dried, more of it can be applied to strengthen the mounting.

Viewing window cutout for the display readout module.



and the battery holder. The latter is stuck down in between the front panel and the p.c.b. with double-sided sticky pads.

Mount the main p.c.b. with four self-tapping screws. It may be necessary to slightly raise the p.c.b. off the mounting studs with washers so that it mounts evenly, otherwise the solder on the underside may foul the other studs.

Fit the display Screen Select switch S2 and check that the l.c.d. module will fit alongside lining up with the front panel rectangular cutout. The right hand side of the l.c.d. module may need to be slightly filed down to accommodate S2 and line up with the cutout.

The l.c.d. module has to be glued onto the rear side of the front panel by four countersunk screws which are first fitted into the module's mounting holes.

Fit these four mounting screws and lock them with nuts either side of the l.c.d. module, making sure that the screw heads are

TESTING

On completion of the assembly, and without connection to any MIDI device, fit batteries and switch on. The l.c.d. should immediately show the Screen-1 display (as at top of Fig. 1) but if not, adjust the contrast of the display with preset VR1.

If the screen message still does not appear, or if only the top line of the l.c.d. goes slightly dark, then remove power and re-check the assembly. Should the top line of the l.c.d. go dark, then this indicates that

the l.c.d. is not being initialised by the microcontroller.

If all is well, connect the MIDI Out socket of one MIDI device (preferably a keyboard) to the MIDI In socket of the Analyser. Connecting with the power already switched on should not cause a problem.

Continuously press and release a key on the keyboard. Data will be shown in place of some of the dashes on the first display screen, such as Note name with its associated Octave and MIDI Channel number. If this is not so, then re-check cabling and connectors to the keyboard and Analyser.


Now try connecting a cable from the MIDI Thru socket on the Analyser to the MIDI In socket on another instrument and check that the same notes are played by both instruments.

If you have access to a two-channel oscilloscope and a MIDI device that outputs real-time data continuously, such as a sequencer or a drum machine, then connect the latter to the input of the Analyser. Then connect Channel 1 of the scope to IC1 pin 3 (line RA4) and Channel 2 to IC1 pin 6 (line RB0) whilst triggering (synchronising) on Channel 2.

For this test, it is also necessary to connect a pull-up resistor between IC1 pin 3, and the positive supply. The value is not critical, but 4k7 is suitable. The resistor is required because the output RA4 on IC1 pin 3 is an open collector type.

Check for the waveforms shown in Fig. 7. If the MIDI device is correctly outputting continuous data (which should be repeated bytes of F8 hex, for "real-time" data), then the scope should trigger easily.

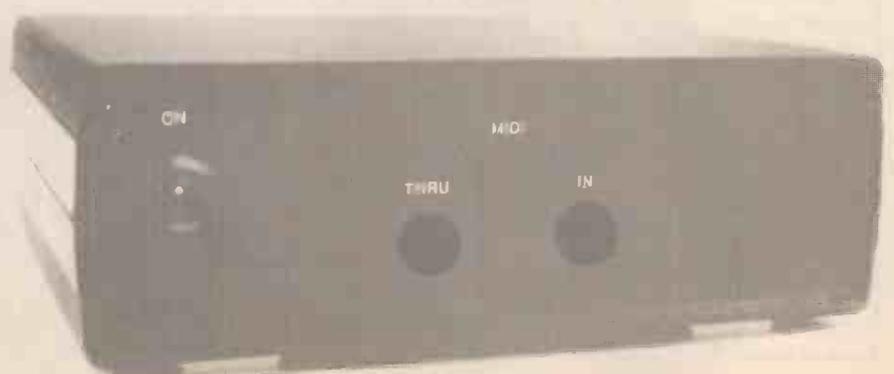The top waveform in Fig. 7 shows ten pulses of very short duration. These are the ten interrupt pulses, and should line up approximately with the centres of the data



HISTORY OF THE MIDI

Long ago, well, somewhat over a quarter of a century ago, thanks to a certain Mr Moog, the Synthesiser was born, a musical instrument in which musical sounds were generated electronically. Nearly every aspect of these sounds could be altered and "shaped", to sound exactly as the owner wanted (well almost!).

However, these synthesisers were generally monophonic and very restricted, allowing only one note to be played at a time. Furthermore, a method of remotely controlling a synthesiser was needed and several analogue methods were proposed.

The most common of these was the Control Voltage Gate, called the CV Gate. If, for instance, a voltage of 4V was applied to the synthesiser's CV input, a middle C would play. A voltage of 5V would cause the C one octave higher to play, and 3V would cause C an octave below middle C to play.

This technique was referred to as the *one volt per octave control system*. Although other systems existed, this was the most popular.

Any intermediate voltage would generate notes, or more importantly, frequencies in between them. However, the system was fraught with problems, as the characteristics of synthesisers varied wildly, and tuning them to

anything like the right values was a real feat! Slight temperature variations also caused immense problems. Even so, the first step to a universal synthesiser control had been taken.

DIGITAL TUNING

In the early 1970s, synthesisers began using digital electronics, and this solved the problems of tuning accuracy and temperature variations. For the first time, *patches* or sets of data representing a particular sound set-up could be saved in the synthesiser's memory. There was no more need to remember all those chunky knob positions to obtain your "fat sax" sound.

The next challenge was to use digital electronics to connect synthesisers together. Commonly, keyboard players in touring bands had several synthesisers in their set-up, and the dream was to be able to control all of them from a "Master" keyboard, so that it was unnecessary to reach over all the other keyboards and press loads of buttons in the middle of a live performance.

This point, along with many others, was noted when the first digital control systems for keyboards were developed. There were several of these systems, but their main drawback was that there was still no compatibility between different instrument manufacturers.

UNIVERSAL INTERFACE

Sequential Circuits, an American synthesiser maker, proposed the first "all manufacturer" digital interface for synthesisers in October 1981. It was called the USI or Universal Synthesizer Interface and used a serial data communications link.

Over the next year, various refinements were introduced to the USI, such as the inclusion of opto-isolation to prevent accidental damage to incorrectly connected instruments, and to prevent mains hum. Also, an increase of serial data speed to 31250 bits per second was implemented. This rate was chosen because it was an easy division (1/32) of the 1MHz clock frequencies of computers at that time.

However, it was to be a further year before the first true MIDI instrument was born, which was Sequential Circuits' *Prophet 600* synthesiser in December 1982. A month later, the first two MIDI synthesisers from different companies were hooked up and demonstrated to an amazed audience at the meeting of the National Association of Music Merchandisers.

The original 1.0 specification for MIDI has remained unchanged since then, although, of course, many subsequent additions have been made, such as the MIDI Sample Dump standard in 1986, and MIDI Time Code messages in 1987.

pitch-wheel down, this value should decrease to zero.

Moving on, the Real-time field (RT) shows a moving chevron (>) if timing data is received from any MIDI device. Plug in a sequencer or drum machine and see if it outputs real-time data. If this field is static, or stays as a dash, then no real-time data is being received.

Similarly, the Sequence field (SQ) shows a moving chevron if a Start or Continue MIDI code is received, and a Stop code should halt the chevron movement.

DISPLAY SCREEN-2

The two rows of the second display screen show a bargraph or analogue representation of key velocity (top row), and after-touch (bottom row). This representation gives a more realistic display of these parameters.

DISPLAY SCREEN-3


The third screen simply shows which MIDI channels are active. The square under the appropriate channel number darkens when MIDI data is received on that particular channel. After a preset time of about a second, the square goes light again if no more data is received on that channel.

With several devices connected in a MIDI chain, it can be useful to see how each is allocated.

DISPLAY SCREEN-4

The final display screen shows a five-octave keyboard. When keys are pressed on a connected MIDI keyboard, the corresponding keys darken and extend (if white), or lighten and extend (if black).

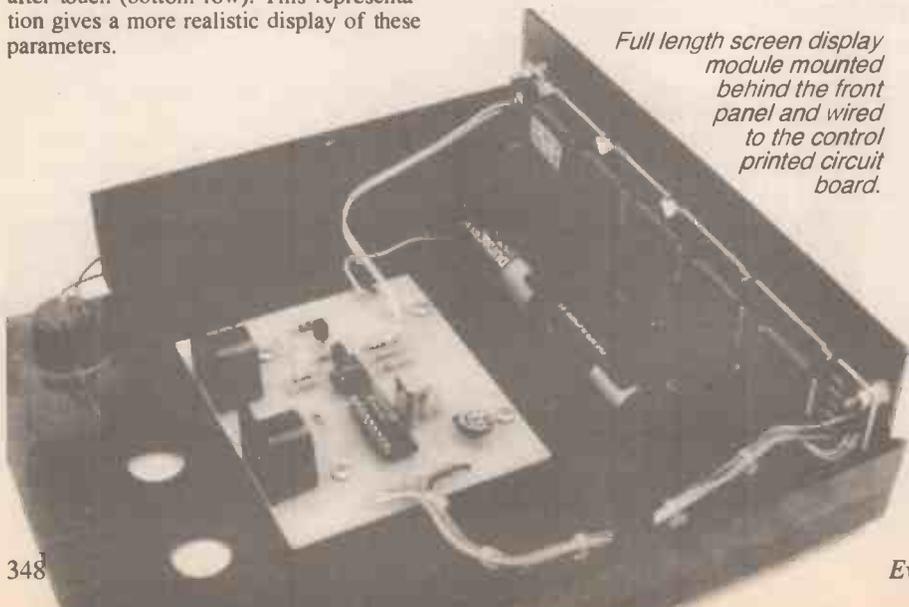Full length screen display module mounted behind the front panel and wired to the control printed circuit board.



This is quite useful for demonstrating the speed and accuracy of MIDI Note On and Note Off data. Keys pressed outside the range of this keyboard display (Octaves 3 to 7 inclusive) are not shown.

PRACTICAL USES

One of the main uses of the MIDI Analyser is to ascertain what MIDI features a particular instrument has. For instance, select the second display screen, then press and release a key several times on a connected synthesiser.

If the top bargraph moves in sympathy with your playing, then that keyboard has velocity sensing, and it is very useful to see how hard you strike each key (volume).

If your synthesiser does not have velocity sensing, then the velocity bargraph will only move to the half-way point denoting a velocity value of 64, which is the default value.

Similarly, if a keyboard responds to After-touch, then the same will occur with the bottom bargraph when the key is pushed into the touch-sensitive cushion underneath it.

The Real-time chevron on the first display screen will immediately show if a Drum Machine or Sequencer is transmitting real-time data. The speed of this moving chevron indicates the rate at which Real-time data is being received.

By selecting the third display screen, it can quickly be found out on which channel a particular piece of MIDI gear is transmitting. In a complicated MIDI setup, the analyser can be an important test tool for finding out why a Synthesiser, Sequencer or Drum Machine remains coldly silent! □

MIXED-MODE SIMULATION. THE POWER OF VERSION 4.


New
Version 4

Analog, Digital & Mixed Circuits

Electronics Workbench® Version 4 is a fully integrated schematic capture, simulator and graphical waveform generator. It is simple to mix analog and digital parts in any combination.

Design and Verify Circuits... Fast!

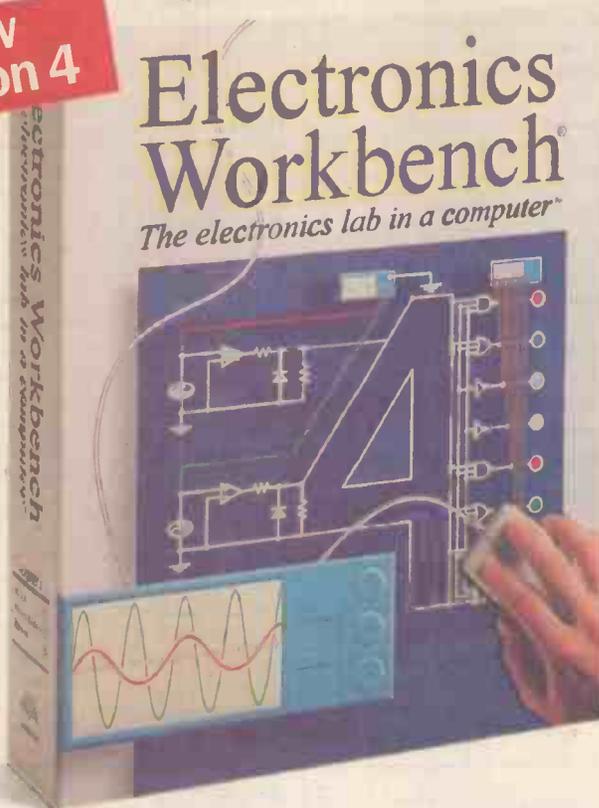Electronics Workbench's simple, direct interface helps you build circuits in a fraction of the time. Try 'what if' scenarios and fine tune your designs painlessly.



More Power

Simulate bigger and more complex circuits. Faster. On average, Electronics Workbench Version 4 is more than 5 times faster than Version 3.

More Parts

Multiple parts bins contain over twice the components of Version 3.

More Models

Over 350 real world analog and digital models are included free with Electronics Workbench. And, if you need more, an additional 2,000 models are available.

Incredibly Powerful. Incredibly Affordable.

If you need mixed-mode power at a price you can afford, take a look at this simulator and graphical waveform generator that mixes analog and digital with ease.

With over 20,000 users world-wide, Electronics Workbench has already been tried, tested and accepted as an invaluable tool to design and verify analog and digital circuits. With Version 4 true mixed-mode simulation is now a reality with incredible simplicity.

Electronics Workbench™

The electronics lab in a computer™


Order Now! Just £199*

44-(0)1203-233-216

RM Robinson Marshall (Europe) Plc

Nadella Building, Progress Close,
Leofric Business Park,
Coventry, Warwickshire CV3 2TF
Fax: 44 (0)1203 233-210
E-mail: rme@cityscape.co.uk

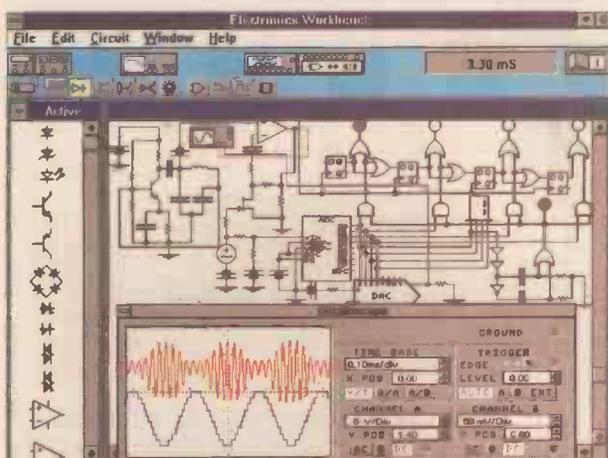Shipping charges UK £5.99. All prices are plus VAT.
All trade marks are the property of their respective owners.
Electronics Workbench is a trademark of Interactive Image Technologies Ltd., Toronto, Canada.
* 30 Day money-back guarantee.



True mixed-mode simulation: Simultaneous AM transmission, digitization and pulse-code modulation of a signal.

Australia: 2-519-3933 • Brazil: 11-453-5588 • Cyprus: 09-641801 • Denmark: 33-25-0109 • Finland: 0-297-5033 • France: 14-908 9000 • Germany: 711-62-7740 • Greece: 1-524-9981
Hungary: 1-215-0082 • India: 11-544-1343 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 603-2937481 • Mexico: 5-396-3075 • Netherlands: 18-031-7666
New Zealand: 9-267-1756 • Norway: 22-16-70-45 • Portugal: 1-814-6609 • Singapore: 462-0006 • Slovenia: 61-317-830 • South Africa: 331-6-8309 • South Korea: 2-2-222-3431
Spain: 1-553 3234 • Sri Lanka: 1-86-5970 • Sweden: 8-740-5500 • Thailand: 66-2-398-6952 • United Kingdom: 203-23-3216

RADIO DATA MODULES MODEM TRANSCIVERS

UK, E.E.C, Scandinavia, Eastern Europe, North & South America, Middle East, South Africa, New Zealand, Far East or Australia. Wherever you are, we have a module on the right frequency for you!

New !: TXR-XXX-DTR100



Only 55 x 23 x 15mm

**20% Discount On Evaluation Pairs
UK, US, EEC or Australian Models**

- Efficient 5V operation *
- 400 to 500MHz Versions *
- Range up to 5Km *
- Compact Size Ideal for Hand Helds *
- UK, North American, Australian *
- MPT, I-ETS & FCC Approval *
- Up or 64 selectable channels *
- 100+ Price Only £115.00 *

Low Voltage Transmitters Simplify Interfacing !

- Reduce Component Count, Cost, Size & Power Drain *
- Twice as fast as the - A version, up to 20,000 bps *
- Drives directly from a PIC output Port III *
- Available UK Approved MPT1340 418MHz *
- Export I-ETS-300-220, 433.92MHz *



TXM-418-F Transmitter



SILRX-418-F Receiver

*** Special UK 40% Off Introductory Offer ***
*** Only £29.95 per pair Inc VAT ***

Exclusive : South African Modules on 403MHz

- TXM-403-A, SILRX-404-A, RXM-403-A *
- High Quality FM system > 120M Range *
- Evaluation Kits Available *
- No Price Surcharge *
- Eg : 1000 + TXM's Only £5.95 Each *



RXM-403-A

VHF Modules for UK, Australia and Beyond !

- UK, 173MHz to MPT1344 & MPT1328 Licence Exempt *
- Miniature Low Cost 1 & 10mW Transmitters *
- 173.500MHz Transmitters & Transceivers for Australia *
- PCB mount or canned, Superhet Receivers *
- Low Cost Meter Reading Transceivers on 183.8875MHz *
- Prices from £20.00 to £340.00 each *



RXM-173/183-4666-60

World Leading BIM Transceiver £84.95 per pair !



BIM-418-F

Approved to MPT1340 & I-ETS-300-220

World leading in price, performance and size the BIM high speed transceiver has already found a home around the World in many wire free products from computer networks, hand held terminals to EPOS. Available on 418 and 433.92MHz

- 5V Operation, PIC Compatible Logic *
- Exclusive RS232 Serial Version £79.95 *
- Packet Controller Parallel I/O Board £79.95 *
- Evaluation Kit with 2 BIM's £149.95 *
- Volume Discounts Prices Available for OEM's



BIM-433-RPC


Check our Prices, Now with Free Postage ! *

Transmitters (1+ Price)

TXM-418-A 0.25mW	£12.50
TXM-433-A 0.25mW	£14.75
TXM-418-F 0.25mW	£14.75
TXM-433-F 0.25mW	£14.75
TXM-403-A 0.25mW	£14.75
TXM-173-4689 1mW	£22.50
TXM-173-4689 10mW	£24.50
TXM-184-4689 10mW	£29.95

Antennas (1+ price)

Helical-173MHz	£4.90
1/4 Wave 418MHz	£4.90
Dipole 418MHz	£23.50
VHF Whip Antenna	£35.00
UHF End Fed Dipole	£35.00

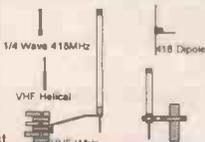

Receivers (1+ price)

SILRX-418-A	£22.50
RXM-418-A	£29.05
SILRX-433-A	£23.95
RXM-403-A	£23.95
RXM-403-A	£29.05
SILRX-418-F	£23.95
SILRX-433-F	£23.95
RXM-173-60	£31.62
RXM-184-60	£31.62

Credit Card Payments Welcome. Exports 2/4 day delivery by DHL, UPS or Air Express Available. All prices in Pounds Sterling

*Prices unless otherwise stated exclude VAT. Damage free on all non-account mainland UK orders. Insurance available at additional cost

Radio - Tech Limited, Overbridge House, Weald Hall Lane
Thornwood Common, Epping, Essex CM16 6NB.
Sales +44 (0) 181 368 8277 Fax +44 (0) 181 361 3434
International +44 (0) 1992 57 6107 Fax +44 (0) 1992 56 1994

SECURITY

ULTRASONIC MOVEMENT DETECTOR
Xtal controlled oscillator, detector circuits & edge mounted transducers on one PCB just 75x40mm. Detection range 4-7m. Adjustable sensitivity. LED indicator. Outputs to drive external relay/circuits. 9V DC operation. 3049-KT. £14.95

MINI CCTV CAMERA



- FEATURES**
- Compact & light camera PCB module 54x38L x30mmH, 33 grams
 - Low power consumption 12V DC, 150mA
 - Low light requirement 0.1Lux (IR LED on)
 - High quality image resolution CCIR image 512x562 pixels
 - Video output 1Vp-p/75Ω
 - Lens 3.6mm, F1.8
 - Field of view 74° x 55°
 - Maintenance free
 - Built-in electronically controlled auto-iris
 - Internal synchronisation

ASSEMBLED UNIT: 3047-AS £89.95

X-FACTOR PUBLICATIONS

THE EXPERTS IN RARE & UNUSUAL INFORMATION!

Full details of all X-FACTOR PUBLICATIONS can be found in our catalogue. N.B. Minimum order charge for reports and plans is £5.00 PLUS normal P.&P.

SUPER-EAR LISTENING DEVICE Complete plans to build your own parabolic dish microphone. Listen to distant voices and sounds through open windows and even walls! Made from readily available parts. R002 £3.50

TELEPHONE BUG PLANS Build you own micro-beetle telephone bug. Suitable for any phone. Transmits over 250 metres - more with good receiver. Made from easy to obtain, cheap components. R006 £3.00

LOCKS - How they work and how to pick them. This fact filled report will teach you more about locks and the art of lock picking than many books we have seen at 4 times the price. Packed with information and illustrations. R008 £3.50

RADIO & TV JOKER PLANS We show you how to build three different circuits for disrupting TV picture and sound plus FM radio! May upset your neighbours & the authorities!! DISCRETION REQUIRED. R017 £3.50

INFINITY TRANSMITTER PLANS Complete plans for building the famous Infinity Transmitter. Once installed on the target phone, device acts like a room bug. Just connect the target phone & activate the unit to hear all room sounds. Great for home/office security! R019 £3.50

THE ETHER BOX CALL INTERCEPTOR PLANS Grabs telephone calls out of thin air! No need to wire-in a phone bug. Simply place this device near the phone lines to hear the conversations taking place! R025 £3.00

GENERAL KITS

3 DIGIT LED COUNTER 2 board basic event counter. Main board has 3 digit counter circuit. 2nd board has Count & Reset switches & debounce circuit. Cascaded with other boards to provide more digits. Box & battery holder provided. 9V battery. 78x50x25mm. 3001-KT. £14.95

OP-AMP FUNCTION GENERATOR Quad Op-Amp connected as oscillator & wave shapers to generate audio range wave-forms. Oscillator generates Square Wave from 6Hz to 4kHz. Other amps produce Triangle & pseudo. Sine outputs. Solder pad outputs. 9V powered. 47x40x22mm. 3023-KT. £4.95

LOGIC PROBE Original, modern design tests both CMOS & TTL circuits as well as detecting fast pulses. Gives visual & audio indication of logic states found. Powered from circuit under test. Its operation is fully explained. 3024-KT. £7.95

ROULETTE LED A great introduction to gambling... er electronics! Watch the ball spin round the roulette wheel, slow down & drop into slot. Uses 10 LEDs, CMOS decade counter & Op-Amp to teach Voltage Controlled Oscillator (VCO) principles. 9V powered. Educational & fun! 3006-KT. £10.95

PELTIER JUNCTION HEAT PUMP Boil or freeze water instantly! Use for regulated cooling of temperature sensitive components and much more. 3066-KT. £21.95

9V XENON TUBE FLASHER This powerful high voltage xenon flasher runs off a simple 9V battery. A transformer is used to step up the 9V supply voltage to the high voltage required to flash the 25mm long tube. Flash rate adjustable between 0.25 to 2 second intervals. 3022-KT. £11.95

LM383 AMPLIFIER MODULE Proven, popular building block for use in any audio project where general amplification required. Power output dependent on supply voltage & load resistance. Typical ratings: Over 10W for 18V supply & 2W speaker; 1W for 9V supply & 8W speaker. 3047-KT. £9.95

SWITCHING POWER SUPPLY Replace expensive 9V batteries with cost-effective 1.5V cells. IC based circuit acts as a step-up switching power supply. Selectable 1.5 or 3V DC output. Gives a fixed output of 9V @ 18mA from a 1.5V "AA" cell. Solder pads for input/output, 1 cell & 2 cell "AA" holders & jumper switches supplied. 40x15x12mm. 3035-KT. £4.95

SINGLE CHIP AM RADIO Complete mini sized AM radio on a PCB. Tuned Radio Frequency front-end, AM Radio IC & 2 stages of audio amplification. All components supplied inc. prewound coil & speaker. 32x102mm. 3063-KT. £9.95

TRAIN SOUNDS 4 selectable sounds - Whistle Blowing, Level Crossing Bell, Chugging & "Clickety-Clack". 2.5-6V. Supplied with all components inc. speaker, 16 x 23mm COB PCB, switches & 2 x "AA" battery holders. S67. £4.95

plus AUDIO • EDUCATIONAL • LASER • SECURITY • TEST GEAR • BOOKS & more

Our high quality product kits are supplied with all components, fibre glass PCB's & comprehensive instructions. FREE CATALOGUE with order or send 2 x 1st Class stamps (refundable) for details of over 100 kits & publications. Mail order only. Please ADD £2.00 P. & P. (Europe £3, Rest of World £5) & make cheques/PO's payable to Quasar Electronics. Goods normally despatch within 5 working days. Please allow 28 days for delivery. Prices include VAT at 17.5%. For safety send cash by recorded delivery.

Quasar Electronics Unit 14 Sunningdale BISHOP'S STORTFORD Herts CM23 2PA
E-mail: 101364.3610 @compuserve.com

COMBINATION LOCK

Versatile electronic lock comprising main circuit & separate 9 key touch-pad for remote opening of lock. 120VAC/10A relay supplied. 9-12V. 3029-KT. £9.95

LIGHT ALARM Protect your valuables with this practical, clever little circuit. Alarm sounds if even the smallest amount of light falls on the circuit. Place in cash box etc. 3008-KT. £4.95

THE SCREAMER! Painful alarm siren gives out a massive 110db of ear piercing noise. Box supplied has two 35mm piezo elements already built into their own resonant cavity. PCB fits inside box to give a neat, compact unit. Use as part of an alarm circuit or just for the fun of it! 6-9V operation. 3015-KT. £9.95

SURVEILLANCE

High performance surveillance kits Room transmitters supplied with sensitive electret microphones & battery holders/clips. All transmitters can be received on an ordinary VHF FM radio.

MTX - Miniature 3V Transmitter
Easy to build & guaranteed to transmit 500 metres (over 1000m possible with higher voltage & better aerial). 3-9V operation. Only 45x18mm. 3007-KT. £4.95

MRTX - Miniature 9V Room Transmitter
Our best selling 'bug'. Super sensitive, high power 1000m range (Up to 1 mile with 15V supply & better aerial). 9V operation. 45x19mm. 3018-KT. £5.95

HPTX - High Power Room Transmitter
High performance, 2 stage transmitter gives greater stability & high quality reception. 1000m range with 9V battery. 6-12V operation. On/off switch. Size 70x15mm. 3032-KT. £8.95

VTX - Voice Activated Transmitter
Powerful 2 stage voice activated transmitter. Only operates when sounds are detected. 1km range. Low standby current - conserves battery power. Adjustable sensitivity & turn-off delay. Only 63x38mm. 3028-KT. £8.95

TRI - Telephone Recording Interface
Connect between phone line & cassette recorder. Automatic-ally switches on tape when phone is used. Records all conversations. Powered from line. 48x32mm. 3033-KT. £6.50

TRVS - Tape Recorder Vox Switch
Very sensitive, voice activated switch - automatically turns on cassette recorder when sounds are detected. Adjustable sensitivity & turn-off delay. 5x19mm inc. mic. 3013-KT. £7.50

MTTX - Miniature Telephone Transmitter
Attaches anywhere to phone line. Transmits info when phone is used! Uses phone line as aerial & power source. 500m range. 45x15mm. 3016-KT. £5.50

Two Station Intercom/Hand Wired Bug
Each has its own speaker, microphone & filter (LM386). Turn into a hard wired bug by using 4 stand ribbon cable supplied to send power from the receiving unit to the remote 'bug' unit. 9V. 3021-KT. £12.95

Telephone Amplifier Kit
Pick-up coil & sensitive amplifier let you hear conversations without even holding the phone! Can be used for surveillance purposes. 3055-KT. £8.95

LED SEQUENCE/RANDOM FLASHER. 5 ultra bright red LED's flash in sequence or random. Ideal for model railways. On/off switch. COB PCB 15x8mm (spare provided). 3V powered. 3003-KT. £3.95

LED DICE The classic electronic project that never loses its popularity. Combines a great game with an easy introduction to electronics & simple circuit analysis. 7 LED's simulate a real dice face. The dice rolls, slows down, stops on a number at random. Uses a 555 timer & counter IC. Box included. 9V operation. 3003-KT. £8.95

STAIRWAY TO HEAVEN GAME This game of skill tests your hand-eye co-ordination. If you press the switch each time the green part of the bi-polar LED lights you climb higher up the stairway - but miss, & you start again! Introduces you to several basic electronic circuits. Box provided. 9V operation. 78x50x19mm. Role's Hairs NOT included! 3005-KT. £8.95

DC MOTOR SPEED CONTROLLER Control the speed of any common DC motor rated up to 100V (5A). Operates on 5-15V. Uses NE555 IC to pulse-width modulate a TIP122 high current switching power transistor. In this way torque of the motor is not lowered. Box mounted. 3067-KT. £19.95

SWITCHING POWER SUPPLY Replace expensive 9V batteries with cost-effective 1.5V cells. IC based circuit acts as a step-up switching power supply. Selectable 1.5 or 3V DC output. Gives a fixed output of 9V @ 18mA from a 1.5V "AA" cell. Solder pads for input/output, 1 cell & 2 cell "AA" holders & jumper switches supplied. 40x15x12mm. 3035-KT. £4.95

SINGLE CHIP AM RADIO Complete mini sized AM radio on a PCB. Tuned Radio Frequency front-end, AM Radio IC & 2 stages of audio amplification. All components supplied inc. prewound coil & speaker. 32x102mm. 3063-KT. £9.95

TRAIN SOUNDS 4 selectable sounds - Whistle Blowing, Level Crossing Bell, Chugging & "Clickety-Clack". 2.5-6V. Supplied with all components inc. speaker, 16 x 23mm COB PCB, switches & 2 x "AA" battery holders. S67. £4.95

plus AUDIO • EDUCATIONAL • LASER • SECURITY • TEST GEAR • BOOKS & more

Our high quality product kits are supplied with all components, fibre glass PCB's & comprehensive instructions. FREE CATALOGUE with order or send 2 x 1st Class stamps (refundable) for details of over 100 kits & publications. Mail order only. Please ADD £2.00 P. & P. (Europe £3, Rest of World £5) & make cheques/PO's payable to Quasar Electronics. Goods normally despatch within 5 working days. Please allow 28 days for delivery. Prices include VAT at 17.5%. For safety send cash by recorded delivery.

Quasar Electronics Unit 14 Sunningdale BISHOP'S STORTFORD Herts CM23 2PA
E-mail: 101364.3610 @compuserve.com

New Technology Update

Ian Poole investigates the latest developments in micro-machines, and discovers there's even a version which runs on steam!

MINUTE machines manufactured using technology more akin to semiconductors, and sizes to suit are now becoming a reality. Even though they are still very much a laboratory phenomenon, ideas for everyday uses are coming thick and fast.

Possible uses in medicine have been suggested. They could be used to give small doses of drugs over a prolonged period of time. Although they are likely to find many good uses in this area, their possibilities stretch well beyond the confines of medicine.

Some researchers are looking to their use in shrinking integrated circuit sizes even smaller. As the limits of the current technologies are being approached, these micro-machines could be used in the manufacture of components up to a hundred times smaller than those which can be made at the moment.

Dopant Levels

To achieve this the machines could be used in a number of ways. For example, they could be used for controlling dopant levels in semiconductor materials very accurately.

One of the major features in semiconductor manufacture is the control of the dopant levels. If these could be controlled locally and accurately this would give much greater flexibility in manufacture, allowing more complicated and dense structures to be made.

In another strategy they could be used after the main high temperature processing in additional stages of manufacture. Here they could be used to actually machine areas of the i.c. structure to include items like optical modulators and other items which cannot be made using the standard techniques.

Diamond Based

Taking their use in semiconductor manufacture a stage further, these machines could be used in the manufacture of semiconductors with new substrates. Diamond is an ideal candidate. Not only is diamond the hardest substance known to man, but it is also a very good semiconductor.

One of its advantages is its high level of heat conductivity. This would enable much more heat to be generated in a small area whilst still being able to remove it so that the circuit did not run too hot.

However, diamond is not particularly easy to use. With the use of micro-machines it would be relatively easy to create substrates and locate impurities

at precise points to give the required structures.

In addition to their use in i.c. manufacture, it is being proposed that the machines themselves could be built into future generations of computers.

Beginnings

Micro-machines were first investigated over 25 years ago. Since then the techniques for constructing them have been refined to a degree where they can be manufactured to give some remarkable results.

A number of micro-electro-mechanical systems or MEMS have been designed. One of the first was a complete gas chromatograph in which the system included micro-machined valves, a gas column, flow detector and finally a detector all on one chip.

In just the same way that standard integrated circuits started in a small way and grew dramatically, so the same could happen to these micro-machines.

A number of techniques are being used to make these machines. In one development researchers at Stanford University are using a reactive ion etching technique. This enables "trenches" as deep as 200 microns and with feature sizes of 20 microns to be made.

Other investigations include looking at alternative materials. Silicon is brittle when etched, and this can reduce the reliability. Furthermore, when placed in real situations these machines are likely to become contaminated and their reliability will fall.

Results

In one development by researchers at Sandia a small motor has been fabricated. Manufactured from machined polysilicon it has been shown to rotate at a speed of 300,000r.p.m.. Although the machine itself has been in existence for some while one problem was in ascertaining whether it was actually rotating at that speed and not a sub-harmonic!

Rotating at such a high speed made many people wonder about the life of the bearings. Although silicon is relatively hard (and brittle) such high speeds can wear bearings out quickly. It has been stated that the bearings are good for at least 800 million revolutions.

To manufacture the gears a number of processes are needed. Sacrificial oxide layers are used to separate the moveable layers from the stationary ones and a layer of silicon nitride placed between the moving surfaces to reduce friction. To

produce the whole structure eight mask levels are required, although if more complicated machines are required it is likely more stages will be needed.

Despite the detailed knowledge of the processes involved, scientists are still baffled by the life of the bearings. Some precautions including the silicon nitride layer have been included in the process but it was never anticipated the bearing life would be so great.

Micro-Steam

One micro-machine actually runs on steam, generating a force per unit area of the machine that is an order of magnitude greater than conventional electrostatic actuators.

It consists of a small cylinder manufactured by depositing silicon onto a substrate. A spring-loaded piston is placed into the cylinder and water dropped onto the surface of the machine.

A small amount of the water is pulled into a heating area by capillary action, and the steam passed into the cylinder where it forces the piston out. When the heat is removed the pressure from the steam rapidly falls and the piston quickly returns into the cylinder.

All-Aboard

The natural extension of these micro-machines is to fabricate them on the same chip as an integrated circuit. This is not particularly easy because of the complex nature of micro-machine manufacture.

It requires the use of high temperatures to enable any stresses in the structures to be relaxed. Unfortunately, these prolonged high temperatures lead to problems in CMOS circuit manufacture.

If the micro-machine is manufactured first then this leaves the substrate unsuitable for laying down the electronic circuitry afterwards. If the CMOS circuitry is constructed first then it can be damaged. In particular, the metallisation layers are not able to withstand the high temperatures.

Currently, methods of constructing the CMOS circuitry first and then laying down the micro-machines are being investigated. In most i.c.s, aluminium is used for the metallisation, but to overcome the problems in this process, titanium is being investigated.

Whilst titanium is able to withstand the high temperatures, it creates some new problems. First, the metal reacts with the silicon to produce titanium silicides, and second, it does not adhere to the silicon surface sufficiently. Research into solving these problems is progressing.

ELECTRONICS DOWN-UNDER

Fresh back from revisiting Australia, Hazel Cavendish looks at how the Aussies are reacting to technology

WHEN I arrived for two months in Australia I thought I had a golden opportunity to collect some innovative stories for *EPE*. My journey took me from Sydney through the bush country of New South Wales to Melbourne, the Mornington Peninsula and far-flung parts of W.A., and I was fortunate in that two of my hosts had electronic interests.

Thirty years absence from the country revealed enormous progress in many spheres, notably in the development of city centres and industrial areas, and a plethora of new high-rise buildings. There was also a different aura of sophistication in the cities, generated by the large influx of European immigrants who have contributed cultural changes and national cuisines to their adopted country, as well as their scientific know-how.

Fired with tedium

Australian newspapers all carry technical articles and publish regular scientific supplements, in which Electronics figure largely and I perused these eagerly – but with a varying degree of disillusion.


Australia must be a paradise for newspaper journalists, who appear able to publish articles of exceptional tedium, consisting largely of technological treatises and commercial hand-outs, sprinkled with over-zealous use of unexplained abbreviations in block capitals, which could only discourage the lay reader. I constantly asked my various hosts whether they read the technology sections, only to be told: “No, but they come in very handy for lighting the fire or wrapping the potato peelings.”

I soon came to realise that although most Australians embrace technology – and indeed welcome it eagerly – they seldom initiate it. Just as there is an amazing absence of home manufacture of essential goods, Australians prefer to import their electronics – and then utilise them – rather than develop them themselves.

One also reads some surprising claims of “discovery” in electronic technology, backed up by statements which claim that Australia was the first to develop this or that, when one was aware that other countries got to that point quite some time ago.

Veering to Europe?

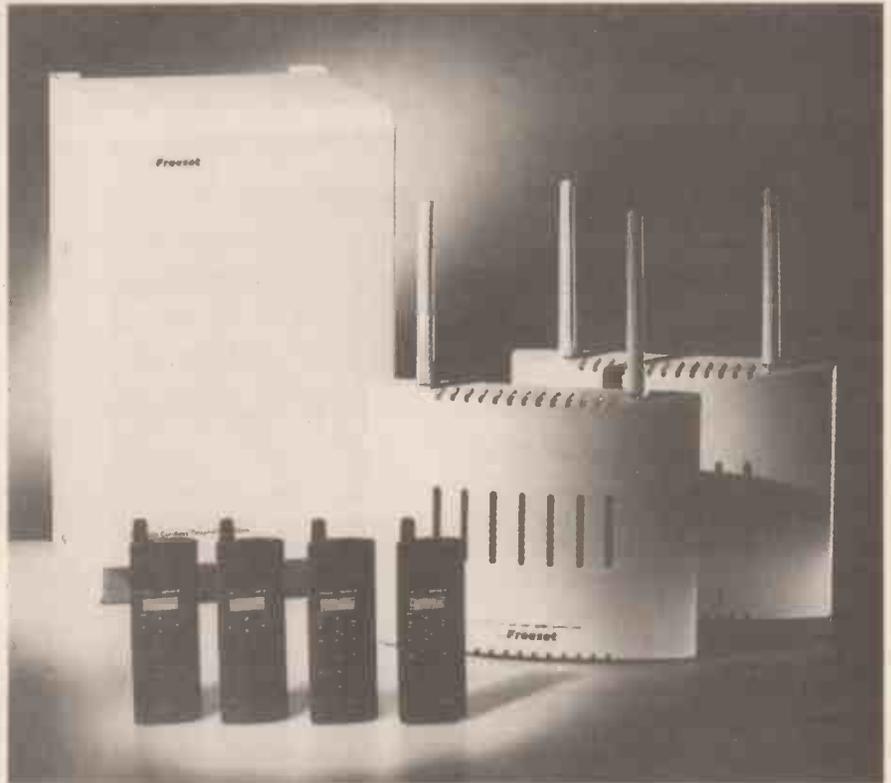Australia has been obsessed for some time now that its future lies with the Pacific basin countries. Now there are signs of a sea-change. A prominent



Freeset is a unique digital cordless phone system comprising a radio exchange, base stations and portable handsets.

Australian has declared that the national obsession with Australia's push into Asia is misguided.

Mr Duncan Campbell, former secretary of the Dept. of Foreign Affairs between 1975 and 1979 and previously an Ambassador for his country in Italy – now described in their newspapers as a leading bureaucrat – has warned Australians against being mesmerised by Asia and argues that the country should appreciate and nurture its substantial ties with Europe. He points out that Australia's latest current account transactions with the European Union totalled more than \$40 billion – 20 per cent of the total.

The *Australian* newspaper covered his recent speech, at a “Business in Europe” lunch, in which he said the Federal Government's foreign affairs were lopsided and bore little resemblance to the statistical reality. Cumulative European investment in Australia was well over \$1 billion and almost 30 per cent of the total. He predicted a new, mature relationship with Europe in a post-republic Australia, bolstered by post-war European migrants.

Encouraging IT in Oz

Australians are keenly interested in every aspect of Information Technology, and would like to appear on the world stage. In January this year a consortium of Australian IT companies invested over half a million Australian dollars in an electronics, hardware and software manufacturing facility in Brisbane, Queensland. Oz Electronics Manufacturing sets out to provide assistance to Australian developers seeking to become internationally competitive.

“For the first time this enables innovative Australian operations with relatively small marketing muscle to compete successfully in the international arena”, said MD Max Rose. “We can offer expertise in the manufacture of componentry that meets the stringent requirements of European and North American markets.”

In an effort to encourage home-bred innovation, the Australian Institute of Engineers in Canberra offers “Excellence Awards” to a range of products submitted by firms every year.

Communicating importance

The importance of every aspect of this technology in a country of vast distances between cities is marked by the amount of space devoted to it in technical supplements. The Swedish firm of Ericsson claims to occupy 70 per cent of the market share in cordless business telephone systems, having introduced their cordless portable telephones to Australia three years ago. The firm quotes a forecast that the world market for these systems could be worth US \$5 billion in 1998.

Ericsson Australia has supported the European movement to DECT (Digital European Cordless Telephony) as a Radio Equipment and Systems Cordless Telecommunications standard.

"Freeset" is their latest system complying to the DECT standard that can be connected to any private automatic exchange, extending the telephone services for every user over the entire premises of a large company.

The system comprises: Radio Exchange, providing radio control and

interfacing to the network; Base Stations, which provide coverage in an area and support eight simultaneous calls; Portable Telephones, which provide a range of services to users.

Speech is encoded into a digital format before transmission. The coding used is the Adaptive Differential Pulse Code Modulation standard. Radio communications between the Base Stations and the Portable Telephones are based on Multiple Carrier, Time Division Multiple Access and Time Division Duplexing which provides full duplex operation.

All system communications are encrypted to ensure complete privacy and protection against eavesdropping techniques and fraud by unauthorised users.

The Freeset system provides transparent service access for up to 600 users without confining them to specific coverage areas.

Long-distance Cordless

The Ericsson company is working on a development for the future which will enable people in widely distant

Australian cities to communicate with homes and businesses via their cordless portables for a local charge – an important step forward for a country in which distances are enormous.

The implementation of the open air interface for DECT, known as Generic Access Profile (GAP), will allow the use of portables of one manufacturer in an infrastructure environment of another.

Another development is known as "Radio in the Local Loop" which is defined as a radio interface into the PSTN (Public Service Telephone Network) from the end point of communication. It is thought that it will be possible to replace the last few kilometres of cable to residential addresses with radio technology (Base Stations).

This scenario would allow for three new business opportunities: Radio interface to homes with fixed handsets; Radio to homes with a repeater and cordless phones in the home; Neighbourhood mobility. The last of these is thought to be an area of great potential.

SINCLAIR ARCHEOLOGY

A legend in his own life-time, Sir Clive Sinclair has repeatedly created immense public interest in his various inventions, even though not all have received the success hoped for.

As readers who live in Sussex may well have discovered, an exhibition about Sir Clive and his products was recently on display at Hove Library. Arranged by one of Sir Clive's greatest fans, Enrico Tedeschi, it drew in not only crowds of visitors, but also Sir Clive himself.

Enrico, who is an historian and writer with an interest in radios and electronics, comments that he has been collecting examples of Sir Clive's work for many years.

Amongst the many memorabilia on display was the ill-fated C5 electric trike plus, of course, greater successes such as the Z80 computer.

Although the exhibition has now finished, Enrico is determined to keep alive the public's interest in the Sinclair Legend and has published a book which thoroughly records it all. Visiting the exhibition, Sir Clive said "I found the book astonishing. It is remarkably complete and will be a great help to me".

The book is called *Sinclair Archeology - the complete photo guide to collectable models* and Enrico not only researched, wrote and illustrated it, but he has also printed, collated and bound it.

To obtain a copy of the book, send a cheque or postal order for £12 (which includes £2 UK postage) to Hove Books, 54 Easthill Drive, Portslade, Brighton, Sussex, BN41 2FD. Orders can also be placed by phone to 01273 410749.



Sir Clive in 1989, proudly displaying the Z88 computer which, at the time, was his latest invention.

FARNELL TAKING OVER

Major British components distributor Farnell Electronics PLC of Leeds has been involved in discussions with a view to taking over the American Premier Group. It is understood that in principle all has been agreed and that only the nitty-gritty of legal arrangements has still to be completed.

Assuming that this take-over goes ahead, Farnell will become what is reckoned to be the largest catalogue-based distributor of electronic components in the world. Premier currently owns major distributors in Newark, USA.

Having realised a 1994-5 turnover of £514 million, Farnell has been disposing of its UK manufacturing operations and buying more distributor bases. It has also opened an American distribution outlet in South Carolina, primarily to service the East Coast.

As we go to press, the latest financial market news is that Farnell has received subscriptions for 94.4 per cent of its £349 million rights issue, launched as part-funding for its £1.9 billion acquisition of Premier.

Farnell are pleased to accept orders for electronic components and equipment from non-account holders and it is well worth while obtaining their catalogue. Their WWW site also contains details of their product ranges and has links to many semiconductor suppliers, the URL is: <http://www.farnell.co.uk>. Farnell's sales telephone number is 0113 263 6311.

CHIDEABLE QUOTES

These astonishing quotes were seen in *Transmission Lines*, the newsletter for the Friends of CHiDE, the Centre for the History of Defence Electronics:

"Everything that can be invented has

been invented", Charles H. Duell, Director, US Patents Office, 1899.


"Radio has no Future", Lord Kelvin, commenting on Marconi's experiments in 1897.

CHiDE was established in 1995 at Bournemouth University and is a UK pioneer in the use of advanced electronics and information technology to promote the public understanding of the history of electronics.

It creates multi-media presentations for schools, museums and libraries, travelling exhibitions and a Virtual Museum on the Internet.

To find out more about CHiDE, contact: Friends of CHiDE, The Centre for the History of Defence Electronics, Bournemouth University, Room 413, Studland House, 12 Christchurch Road, Bournemouth, Dorset BH1 3NA. Tel: 01202 503902.

THERMIONIC VALVES - THE C.R.T.

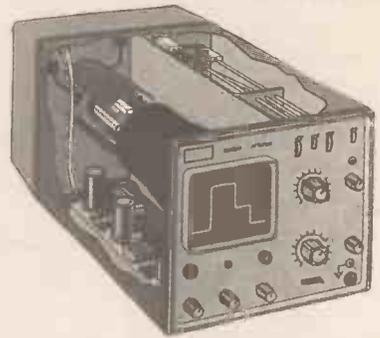

IAN POOLE

Part Two

Valves may be ancient in origin, but they are still much used, especially as cathode ray tubes.

LAST month we looked at the history of the thermionic valve and discussed some of its varieties. These were principally designed for amplification use in various forms. In this concluding article, a very different form of valve technology is examined – that of the cathode ray tube.

The cathode ray tube (c.r.t.) is one of the most extensively used display inventions ever made. It has been in widespread use for over 50 years, and despite the fact that other thermionic devices are now rarely used, the production of c.r.t.s is still increasing.

Even though many companies are spending vast amounts of money developing other forms of display, the c.r.t. still outperforms most of them. It offers high definition, full colour capability, high light output, wide angle of view and, above all, it is relatively cheap to produce.

Against this, the c.r.t. has several disadvantages. It is large and heavy, consumes a large amount of power, and requires high voltages to drive it. These disadvantages make it unsuitable for applications in portable equipment, such as laptop computers, where power consumption, size and weight are prime considerations. But, for domestic televisions and desk-top computers, the c.r.t. is still the only viable option.

ORIGINS

Work which directly led to the development of the c.r.t. can be traced back to the middle of the nineteenth century. At this time a number of people were making investigations into what we now know are electrons.

In his researches in Germany, a researcher named Hittorf discovered that the particles leaving a cathode travelled in straight lines. These emissions became known as cathode rays. During the 1870s, William Crooke established that the rays could cause fluorescence in an evacuated tube.

By the late 1870s, many properties of cathode rays were known, including the fact that they could be deflected by a magnetic field. However, it took until 1897 before J. J. Thomson, an eminent scientist at the Cavendish Laboratory in

Cambridge, verified that they could be deflected by an electric field as well.

Then, in 1907, Boris Rosing in Russia used a c.r.t. to display simple images on a screen. As electronics was still in its infancy, the images were generated mechanically using moving magnets.

GROWTH OF TV

After this, much development of the c.r.t. came about with the introduction of television. Research into TV was undertaken on both sides of the Atlantic, although with surprisingly little cooperation. In the States, RCA were developing their system, first demonstrating a TV receiver which used a c.r.t. in 1932.

Meanwhile, in the UK, the EMI-Marconi system was chosen by the BBC, against fierce competition from John Logie Baird's mechanical method, with the first public TV transmission starting in 1936.

The war put a stop to much of TV development, although the c.r.t. itself was greatly improved for use in military radar systems. After the war, TV transmissions were resumed and interest started to grow


again. In Britain, the Coronation was televised in 1953, and this gave an enormous boost to the acceptance of TV into daily life.

The next major development was to be able to display colour. Many systems were put forward. John Logie Baird with his characteristic inventiveness managed to display two images on one screen and then combine them optically to produce a two-colour picture. However, it was realised that this approach would not be viable for volume manufacture.

The "shadowmask" system in use today was first demonstrated at RCA by a team led by Goldsmith and Schroeder. A great deal of development was required because a large number of coloured phosphor dots were needed and these had to line up exactly with holes in a shadowmask.

Acceptance of the system was slow because of the enormous cost of the tubes. Once colour did start to become accepted, many countries quickly followed suit, the BBC in Britain starting their colour transmissions in 1967.

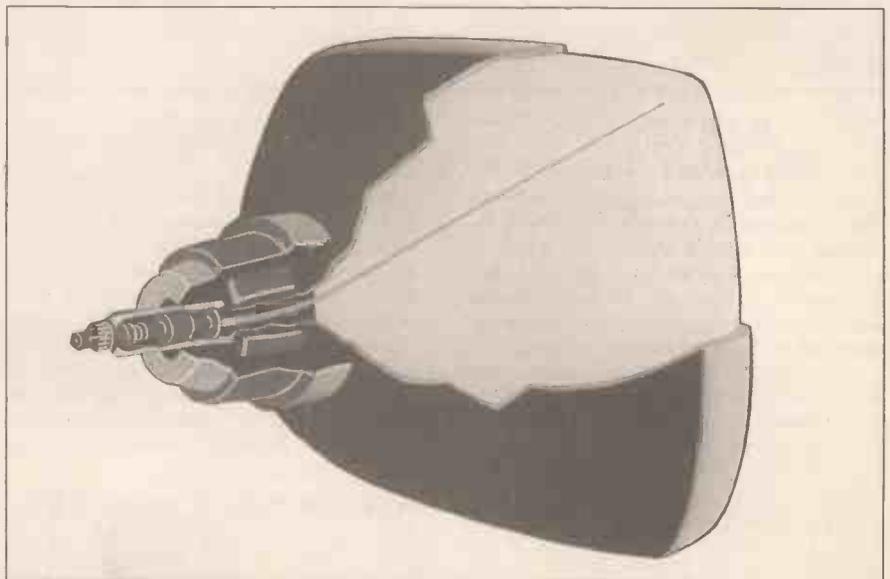Colour TV gave a new lease of life to c.r.t. production around the world. Even so, this was only a forerunner to the impetus given by the introduction of the personal computer. Now sales of c.r.t.s for PC monitors far outstrip those used for TVs.



Cutaway view of a modern c.r.t. This illustration and the title photograph, courtesy of Philips Test and Measuring Instruments.

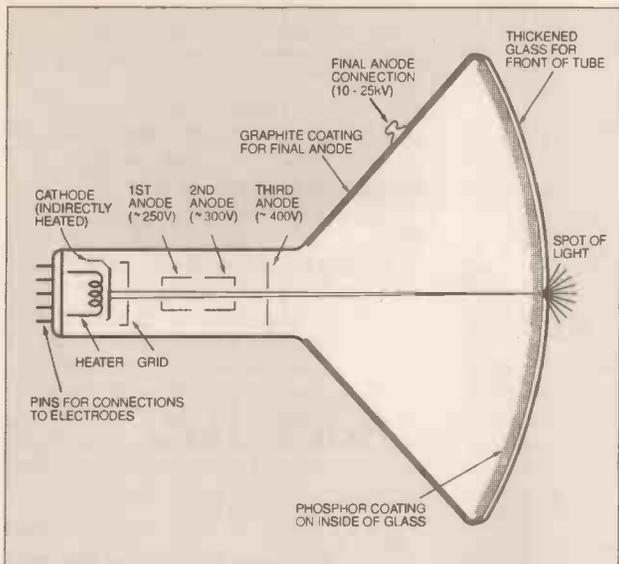


Fig. 18. Simplified diagram of a c.r.t. In essence, only one anode is required.

BASICS

The cathode ray tube, picture tube, or just "tube", is based on the thermionic valve, which was explained in Part 1.

It consists of an electron gun, the deflection circuits and the screen. The electron gun generates the electron beam, which travels towards the screen while being deflected up and down and side to side by magnetic or electrostatic fields. Once the beam hits the screen, the kinetic energy of the electrons is converted into light energy by a phosphor coating on the inside of the glass.

The electron gun consists of an assembly with a cathode, grid and one or more anodes. The cathode is indirectly heated in exactly the same way as in an ordinary valve. When the cathode reaches the operating temperature, electrons are emitted by it and are attracted, past the grid, towards the positive potential of the anodes, as shown in Fig. 18.

The grid is held at a negative potential with respect to the cathode, and by altering the level of bias on it, the number of electrons can be controlled. When a negative voltage is placed on the grid, it tends to repel the electrons moving out from the cathode because like charges repel one another. This reduces the electron flow and hence the intensity of the beam.

When the bias is reduced, i.e. made less negative, the electrons are not repelled back by the same degree and their flow towards the anodes is increased. In this way, the number of electrons reaching the screen can be controlled, allowing the level of light emitted by it to be altered.

Once the electrons pass the grid, they are accelerated by the potential on the anode, their velocity increasing the nearer they get to it. A small hole is present in each anode. Some electrons hit the anode, but others pass straight through the hole, travelling on towards the screen.

To ensure that most electrons are focused towards the anode hole, the grid is specially formed. Unlike the mesh or gauze grids found in ordinary valves, the grids found in c.r.t.s are solid cylinders with a small hole at the end. This enables a relatively narrow beam of electrons to flow out towards the anode, making best use of the total electron emission from the cathode.

A c.r.t. with a single anode cannot produce high quality display results. To achieve such results, further anodes have to be used to accelerate the electrons sufficiently to generate the required light output. They also help focus the beam to the fine point needed to achieve optimum definition, as shown in Fig. 19.

As shown in Fig. 18, the additional anodes are held at increasing voltage levels. Typically, the first anode might be at around 250V, and then the second and third ones might each be 50V to 100V above the previous one.

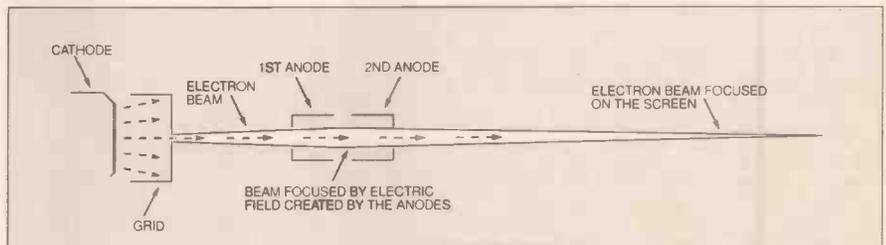


Fig. 19. Anodes in the electron gun.

SCREEN

To enable the electron beam to illuminate the screen, the screen is coated with a phosphor layer. This converts the kinetic energy of the fast moving electrons into light, in other words, it fluoresces.

The phosphor contains a mixture of phosphates, silicates and sulphides. By changing the composition of the phosphor, it is possible to change its fluorescent characteristics, including the colour.

Even though the electron gun already contains a number of anodes, a final anode is also created in the flared part of the tube, as shown in Fig. 18. The final anode is normally made by coating the inside of the glass with a carbon layer. It is usually held at a potential of several kilovolts. A typical figure might be 15kV or more.

The connection to the final anode is easily seen on a c.r.t. It is a thick well-insulated cable connected to the flared section of the tube via a robust connector, part of which is embodied into the tube. The connection has to be placed well away from all other connections to the tube in order to prevent the very high voltage from arcing over.

As the phosphors are conductive, the inner front surface of the tube is at the same potential as the graphite coating forming the final anode. This has the effect of pulling the electrons towards the screen and accelerating them even more. Once they strike the screen, the current is conducted away through the final anode connection.

Warning: Under no circumstances should the back of a television be removed except by experienced persons. Exceedingly high voltages are present

which could be fatal. These can remain in the set even after it is switched off.

BEAM DEFLECTION

Positioning of the beam on the screen can be achieved in two ways. The first method is by the use of a magnetic field.

When a conductor carrying an electric current is placed within a magnetic field, a force will be exerted on it. This fact is used in a variety of applications, such as electric motors, for example. The same is true for a beam of electrons within a cathode ray tube. These behave in exactly the same way, except that they do not have a conductor to confine their flow.

Making use of this fact, coils are placed over the neck of the tube and controllable currents are fed through them, creating variable magnetic fields, as shown in Fig. 20.

There are two sets coils, orientated so that their fields are at right angles to one another. Between them, they control the vertical and horizontal deflections of the beam. In this way the dot of light created by the beam can be moved anywhere on the screen.

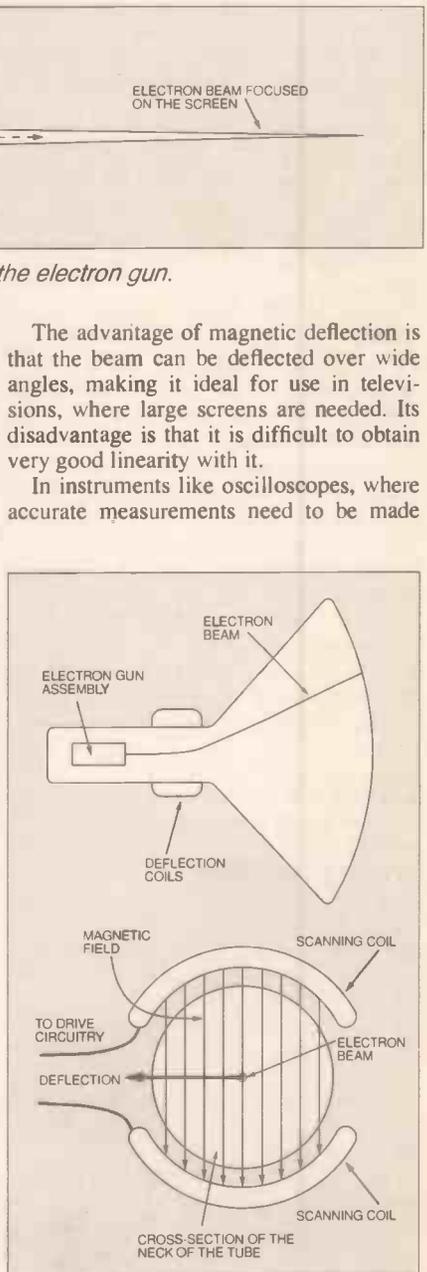


Fig. 20. Magnetic deflection.

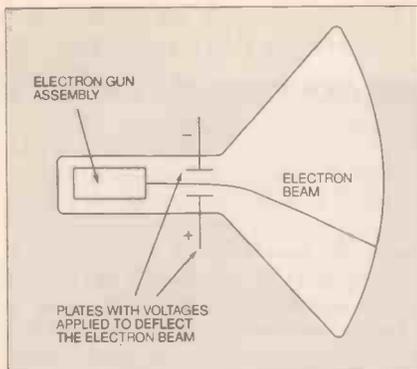


Fig. 21. Electrostatic deflection.

from the screen, electrostatic deflection is used, as shown in Fig. 21. This method is based on the fact that like-charges repel one another and unlike-charges attract.

The tube is fitted with control plates after the focus anode. One pair is required for horizontal deflection, and another for vertical. When voltages are applied to the plates, the beam deflection is proportional to the voltage applied.

The problem with electrostatic deflection is that it does not give as much deflection as magnetic. Consequently, tubes using this method of deflection have to be much longer.

When the electron beam is fired along the tube, it has to be deflected sufficiently to cover almost the entire screen, as shown in Fig. 22. For a given screen size, the shorter the tube, the wider the angle which is required. To achieve a wide deflection angle, much greater levels of drive are required. It is also more difficult to maintain the accuracy and definition over a wide angle. Despite this, most modern tubes have a scanning angle of 110 degrees.

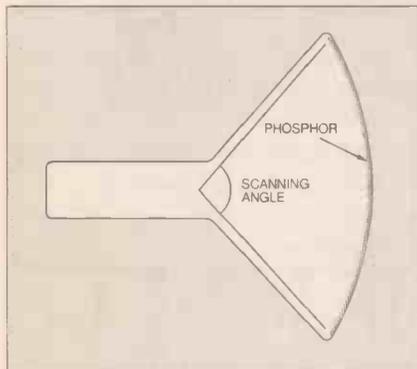


Fig. 22. Scanning angle.

TUBE SIZES

Tube sizes are now usually quoted as a single measurement in centimetres. This is the measurement across the diagonal of the active screen area, as shown in Fig. 23. Obviously, for the size to be meaningful, the ratio of the width to height must be known. For the current 625-line terrestrial transmissions, the ratio is fixed at 4:3. This means that a 51cm (20-inch) tube will have a width of 40.5cm (16 inches) and a height of 30.5cm (12 inches).

It is now accepted that to create better realism, the picture should be wider than that generally used, possibly with an aspect ratio of 2:1. With a wide screen of this ratio, stereo sound adds much more effect than it does with the current 4:3

ratio. It is likely that over the coming years wide-screen TV will become far more universally used.

SCANNING

The ability to see a television picture on a c.r.t. depends on the fact that human eyes have "persistence of vision". This means that an image projected onto the retina of the eye will continue to be perceived ("seen") briefly after the image has been removed. How this can be applied to create a meaningful picture on a TV screen is as follows:

A spot of light can be made to oscillate backwards and forwards. At slow oscillation rates, the spot will be clearly seen as it moves, but as the rate speeds up, the spot will gradually become a blur, and eventually be seen as a continuous line.

The dot can then be made to vary in intensity as it moves backwards and forwards. The eye registers these changes as areas along the line which are light and others which are dark.

Once one line has been scanned, the dot can be moved downwards slightly, rapidly returning to the other side of the screen, and another similar line displayed, and so on until the whole screen has been covered. In this way a whole picture can be displayed.

When the whole picture has been scanned, the spot can return to the beginning and trace out the whole screen again. When this cycle is performed fast enough, the eye does not perceive any flicker.

Ideally, a TV picture would need to be displayed at a scan rate of about 30 times a second for flicker to be unnoticeable. In the UK, TV pictures are refreshed 25 times a second. This is not quite fast enough to remove all the traces of flicker.

To overcome this problem, a technique called "interlacing" is used, in which all the odd-numbered lines are sent first, and then followed by the even-numbered lines, as shown in Fig. 24.

Because the even-numbered lines are interlaced between the odd-numbered lines, then, at distances from which the TV screen is normally viewed, it appears that the picture is refreshed fifty times a second and the eye does not detect any flicker. (Flicker can still be noticed, though, if the transmitted pictures have originally been recorded on film, which typically is photographed at 24 or 25 frames a second.)

COLOUR

The discovery of how to display monochrome (black and white) images on a c.r.t. was a great achievement, but it did not take long before the need arose to be

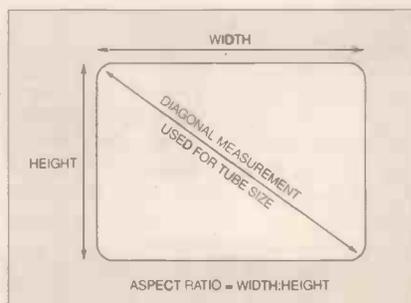


Fig. 23. Aspect ratio and size.

able to display colour pictures. The same basic principles are used to achieve this, although several major additions are needed.

To display colour, c.r.t.s rely on the fact that it is possible to mix together lights of different colours to obtain the others. For example, red, green and blue light, when mixed in the correct proportions, produce white light.

By changing the colour proportions, it is possible to make any colour across the visible spectrum. Blue and red together give magenta, green and red combine to form yellow, blue and green produce cyan.

Colour production in this way is known as an *additive* technique. Note, though, that mixing coloured *lights* produces different colours to those produced when mixing *pigments* such as paint or ink, a technique which is known as *subtractive* colour mixing.

Colour cathode ray tubes use the principle of colour addition to produce all the required colours. They have three types of phosphor on the screen so that the three primary colours can be produced. By controlling the proportion of each colour relative to the others, it is possible to change the overall colour perceived (although close-up examination of the screen will show that the individual primary colours still retain their identity). By controlling the intensity of all three colours together, while still maintaining their required ratios, it is possible to control the perceived brightness.

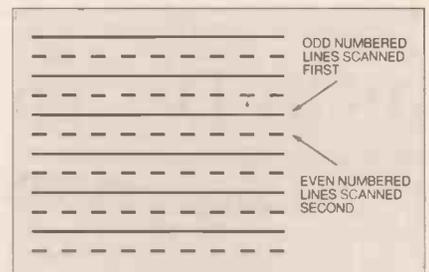


Fig. 24. Interlacing of screen scan.

TUBE CONSTRUCTION

At a first glance, a colour tube looks very similar to an ordinary monochrome one. However, on the inside it contains three separate electron guns, one for each primary colour, as shown in Fig. 25. These are all contained in the neck of the tube as before. The coloured phosphors are placed on the screen in dots or lines. The design of the tube then has to ensure that each gun can only illuminate the correct phosphor. This is achieved mechanically by placing a mask (known as a shadowmask) between the screen and the guns.

As the three guns are not in exactly the same position, it means that the three electron beams hit the screen at slightly different angles. The shadowmask allows each beam to reach its own colour, and prevents it from illuminating any other colour, as shown in Fig. 26.

In theory, it seems very easy to produce a shadowmask that only allows the correct beam to reach each type of phosphor dot. In practice, it is not quite so easy because of the very tight tolerances needed.

The first tubes which were made

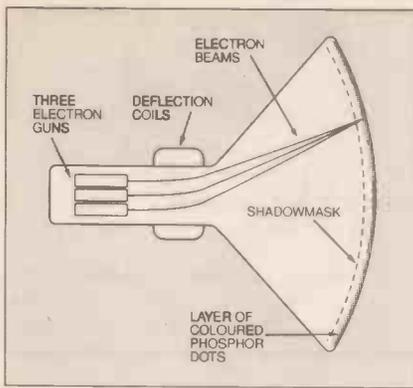


Fig. 25. Construction of a colour tube.

used groupings of three phosphor dots ("triads"), together with electron guns in a triangle or delta shape. These were notoriously difficult to align, and it was often found that the colour in one part of the picture might not be quite right because the electron beam was influenced by an external magnetic field and would hit the wrong colour phosphor. The other problem was that the shadowmask covered up a significant portion of the screen, and this had the effect of reducing the brilliance.

To overcome these problems, most tubes are now manufactured with the scanning coils as part of the main

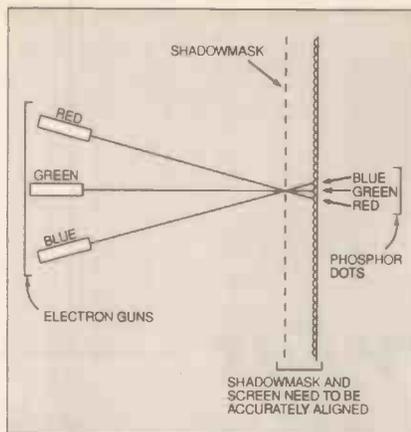


Fig. 26. Operation of the shadowmask.

assembly, allowing very accurate alignment during manufacture. Also, the shadowmask is often modified to have elongated dots or slots. This allows greater illumination of the front of the screen by the electron beam, resulting in greater image brilliance.

The famous Sony Trinitron tube takes this idea even further. Instead of using small phosphor strips, it uses complete strips on the tube which pass from top to bottom. The shadowmask also has similar strips. This technique produces the maximum possible screen illumination.

However, even with the enormous improvements which have been made with tube manufacture, large stray magnetic fields can still cause a problem. This is why high-fidelity loudspeakers, which normally have large magnets inside them, should be kept away from a colour television or monitor.

CONCLUSION

The Cathode Ray Tube is a highly successful invention. Most homes have at least one, and usually more; offices are full of them inside the monitors that go with computers; ships of all sizes use them with their radar systems, as do aircraft; oscilloscopes continue to benefit from their versatility; and numerous other applications exist as well, including such items as cash machines at Banks.

Other technologies have challenged their supremacy, but none have yet succeeded. The cathode ray tube is still dominant in its field. In this respect, thermionic valves continue to flourish.

The hey-day of the "ordinary" valve, though, has passed. Even so, they are not totally outdated by semiconductor technology and are still used in a wide variety of specialised applications.

It seems likely, therefore, that thermionic valves in their various guises will remain in use for many years to come. □

PCB Designer

For Windows 3.1, '95 or NT



Runs on any PC running Windows 3.1, Windows 95 or Windows NT with a minimum 2MB RAM
Will work with any Windows supported printer and monitor



Looking for the price?
It's just £49.00 all inclusive.
...no VAT...no postage...
...no additional charges for overseas orders.
Dealers and distributors wanted.

Internet
Visit our WWW site at www.niche.co.uk for more information and a working demo. The demo is also available via anonymous FTP from [ftp.demon.co.uk](ftp://ftp.demon.co.uk) in the dir /pub/ibmpc/win3/apps/pcbdemo/ as [pcbdemo.zip](ftp://ftp.demon.co.uk). Internet e-mail pcb@niche.demon.co.uk.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer, much higher than the screen shot shown here.

Niche Software (UK)

22 Tavistock Drive, Belmont, Hereford, HR2 7XN.

Phone (01432) 355 414

Available in South Africa from JANCA Enterprises, PO Box 32131, 9317 Fichardtpark at R299,00

FOX REPORT

by Barry Fox



Hotly HiFi

As Ian Poole says (EPE April 1996), thermionic valves are still very much used. Go to any genuine hifi show (as opposed to a home entertainment bash) and the first thing that hits you is the heat. Most of the manufacturers of high end hifi now sell valve amplifiers. The high power models waste the equivalent of a two bar electric fire per channel of sound.

Bell Labs invented the transistor in 1947. Sony started to make transistorised radios in 1955. By the 1970s most home electronics used transistors instead of valves. In 1988 Bell's manufacturing company Western Electric closed its last tube production line in Kansas City. The factory went over to semiconductor manufacture. Most other Western factories had already shut down.

The first transistor amplifiers sounded very nasty. Whereas valves roll off overload signals, transistors slice off the peaks to create square waves. As designers learned to use transistors, the sound got better and there are now some very good solid state amplifiers.

Heavy Metal

A hard core of buffs has always preferred valves ("tubes" in the USA) and are happy to pay tens, even hundreds of thousands of pounds, for units too large and heavy for any shelf or table to support. The smothering capacitors are so huge that they must be pre-charged at the factory. House mains cannot deliver the current.

Factories in China and Russia have continued to make valves. They service backward telecommunications industries and the military who know that valves can withstand the electromagnetic pulse of a nuclear explosion. Hifi designers are wary of these valves as substitutes for the original favourites, notably the Westrex 300B triode amplifier valves. Genuine original 300Bs now change hands for \$1000 each.

Taking the Tube

"Just about every manufacturer of high end hifi now sells a tube amplifier", Charles Whitener of the Westrex Tube Division in the US told me when I heard that the company was offering new 300Bs. "A year ago we decided to start production again. The original staff are using the original tools. We have just produced the first tubes ready for sale".

The new 300Bs will sell for \$350 each. Westrex will make 25,000 this year, purely for the hifi market. Whitener claims the new valves will be indistinguishable from the originals. We must wait for the hifi industry's judgement on that. Particularly interesting, Whitener says Westrex hopes soon to start production

for Europe at a factory in the UK. He won't say who, but Western Electric was once the owner of Standard Telephones and Cables in the UK and of NEC in Japan.

BT on Superhighway

British Telecom denies press reports that it is having second thoughts on building an information superhighway. And for once I sympathise with BT. Business journalists seem to think that the only way to build a highway is to dig a trench down through the UK and lay a brand new optic fibre. In reality, as BT says, the future highway will be a network of networks, some new some existing.

Last October Labour leader Tony Blair struck a deal with BT Director Norman Tebbit. BT would build a broad band superhighway in the UK and provide connections free for educational establishments, in return for the right to start broadcasting entertainment into homes in direct competition with the cable TV companies. The current Conservative government has refused even to consider relaxing the rules on broadcasting until the next century. So you can be sure that BT is not going to let Labour's golden promise slip through its fingers.

Who pays the Highwayman?

This leaves one very important question. How will cash-strapped schools and hospitals be able to afford to use the free connections to the information superhighway which British Telecom will give them. We now know the answer. Other people who use the telephone will pay.

"There will be a levy on consumers", Geoff Hoon, Labour's Shadow Minister

responsible for Information Technology and the Superhighway told the Rights Stuff conference on media rights and payments held in London in early February.

Isn't that just another way of saying there will be a new tax?

"It is not a tax", protests Hoon. "It will be a very modest percentage paid by subscribers to the telephone networks."

Geoff Hoon admits that his wife, a teacher, immediately asked him how schools could afford to use their free connections. They must buy computers and pay experts to make them work and train students to use them. Then they must pay the price of the telephone calls, which will often be lengthy, and the cost of the information received down the line.

Hoon acknowledges that the total cost of using BT's free connections will be "very considerable". He says Labour's plans for a levy flows from an idea put forward last year by Oftel, the UK's telecoms watchdog. Oftel suggested that telecoms operators should charge educational establishments at an artificially low rate and then claim back the difference from a Universal Service Fund. The money for the fund would come from all the operators, and thus indirectly from their other users.

Don Cruickshank, Oftel's Director-General, stressed that the scheme could only go ahead if there was support from the government following full public debate. Hoon says Labour finds the idea "attractive" and takes it a lot further. Labour's fund will also pay for schools' equipment and training and the retrieval of high value information from whoever is selling it down the line.

But, when schools surf Labour's new superhighway, you and I will be picking up the tab.

Are there holes in BT's Net?

British Telecom has a terrible track record on computer services for consumers. Telecom Gold electronic mail, Prestel's messaging service, the Phone Base telephone directory and Electronic Yellow Pages were all good ideas spoiled by silly design faults. They had been developed by engineers, for engineers, but offered for sale to the general public.

BT is moving late into the Internet, and promising that things this time will be different. BT Internet, we are assured, has "ease of use as the first priority". This may prove true. The software may install like a dream, thanks to auto-sensing of the user's modem ports, and auto-setup of the software to match the modem.

On the other hand it may not. I really don't know and neither do any of the

people who have glibly regurgitated BT's publicity claims for "the access service with everything you need to help you on your way".

At the press launch we saw the system working on line, but only saw an edited video of the installation procedure.

I asked the obvious question. Could I please try the installation software myself on my own PC?

"We are trialling it now", admitted Rupert Gavin, BT's Director of Multimedia Services. "We are making final revisions".

There were no copies of the software available for the press to test. Until consumer road-tests there is no way of knowing whether BT Internet really is easy for non-engineers to use, or whether it's another Phone Base and EYP.



Is your PCB design package not quite as "professional" as you thought? Substantial trade-in discounts still available.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395

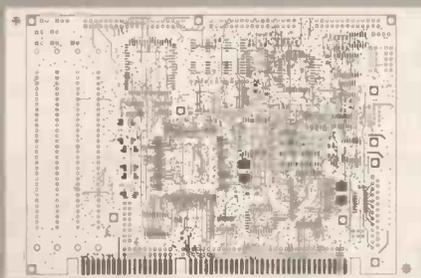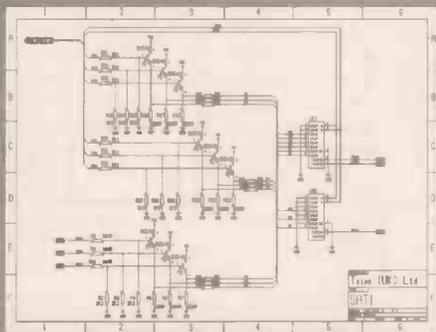

BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1
- Full netlist support- BoardCapture, OrCad, Schema, Tango, CadStar
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator- Database ASCII, BOM
- Thermal power plane support with full DRC

£395

Board Router

Gridless re-entrant autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing


£200

Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)



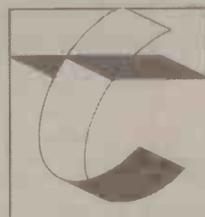For further information contact
 Tsien (UK) Limited
 Aylesby House
 Wenny Road, Chatteris
 Cambridge, PE16 6UT
 Tel 01354 695959
 Fax 01354 695957
 E-mail Sales@tsien.demon.co.uk



tsien

MIND MACHINE MK III TAPE CONTROLLER

ANDY FLIND



Part Three

Build up a library of tapes with this inexpensive tape-based programmer. It will also find many other applications.

WHILST very simple and effective in use, last month's *Program Controller* for the *Mind Machine Mk III* project is a complicated and expensive item to construct. There will undoubtedly be readers who feel their experience is insufficient to tackle such a project, or would like to try programmed operation at a lower cost in terms of both cash and construction time.

A simple and inexpensive method of control will be of interest to these people and this project should fill this need. Although intended primarily for the *Mind Machine Mk III* it can be used for anything that requires a controlling voltage over a period of time, and a stereo tape could be used to give two accurately synchronised simultaneous signals. Like last month's slider potentiometer based unit, it can also be adapted for use with the earlier *Mind Machine* design.

RIGHT RESULT

A previous tape-based *Mind Machine* project used recorded stereo "binaural" sounds, which were then played back through headphones whilst an optional circuit drove the l.e.d. "light" glasses using the two signals. A problem with this was that the recording and playback equipment had to be of excellent quality

since the smallest noise content was very obvious when listening to almost pure sinewave signals.

Even slightly worn tape could cause problems and all recordings had to be "first generation". High speed dubbing and copying was generally unacceptable even with Dolby noise reduction.

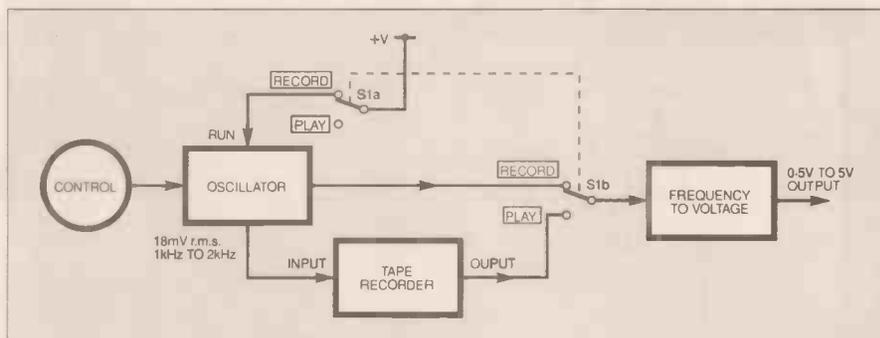


Fig. 1. Block diagram for the Tape Controller System.

This system operates in an entirely different way. A mono tone is recorded and its frequency is used to control an output voltage, which in turn controls the *Mind Machine* signal generator.

The frequency of the recorded tone is restricted to between one kiloHertz (1kHz) and two kiloHertz (2kHz), this narrow

range ensuring good results with cheap monophonic equipment. In fact, results from the prototype are excellent even using a pocket micro-cassette "dictating" machine on a slow tape speed, which gives up to an hour's operation.

HOW IT WORKS

A block diagram of the Tape Controller system is shown in Fig. 1. The switch S1 is shown set to Record, for taping a program.

The oscillator provides a signal of 1kHz to 2kHz with a constant amplitude sinewave output of about 18mV from a low impedance. This is suitable for most tape recorder microphone inputs.

At the same time the signal is connected to a frequency-to-voltage converter, which changes it into a voltage of 0.5V to 5V for controlling the *Mind Machine*. The operator uses the system in "manual" mode, but at the same time the control sequence is recorded on tape.

For subsequent use the switch is set to Play and the tape is replayed from a headphone output to the frequency-to-voltage converter which then delivers exactly the same control sequence automatically. A library of tapes can be built up and copies may be made as needed, even using high-speed dubbing equipment, with no loss of performance.

CIRCUIT DESCRIPTION

The complete circuit diagram for the Tape Controller is shown in Fig. 2. The oscillator, consisting of IC1 and IC2, is of the "integrator and comparator" variety.

The integrator is IC2b, and the output (pin 7) of this goes to the input of the first comparator in IC1. This is a dual

WARNING NOTICE

Photic stimulation at Alpha frequencies can cause seizures in persons suffering from Epilepsy. For this reason such people **MUST NOT** try the *Mind Machine*.

A user who is not a known epileptic, but when using the *Mind Machine* begins to experience an odd smell, sound or other unexplained effects, should **TURN IT OFF IMMEDIATELY** and seek professional medical advice.

Because of the above possibility, the *Mind Machine* should not be used while on your own.

YOU MUST TREAT THIS UNIT WITH DUE RESPECT

timer, but, wired as shown, one of the timer circuits is used as a comparator, with switching points at one-third and two-thirds of the supply voltage, whilst the other is used as an inverter to supply the correct output signal polarity for operation of the integrator.

The amount of output voltage applied to the integrator is adjustable by potentiometer VR1 to control the frequency. Carbon pots have wide manufacturing tolerance, the track resistance between individual specimens varying by as much as 20 per cent.

The arrangement of resistors R2 to R5 together with the buffer IC2a eliminate the lower range setting resistor normally used in such a circuit so that both ends of VR1 are connected to low-impedance voltage sources and variations in its overall value therefore have no effect upon the frequency range. The preset resistor (pot.) VR2 is used for trimming the output to the exact range required.

The triangle-wave output from the integrator IC2b is a.c. coupled through capacitor C2 so that the final output is symmetrical about ground. The two diodes D1 and D2 initially clamp the voltage to around 1.2V peak-to-peak, and with the resistor R9 shape it to something approaching a sine wave.

Attenuation and further shaping by resistors R10, R11 and capacitor C5 give a final output with an almost constant amplitude of 50mV peak-to-peak (about 18mV r.m.s.) and a remarkably sinusoidal shape, ideal for most tape recorder

microphone inputs. Within reason, the circuit is independent of supply voltage change, and it will operate from supplies between 6V and 15V, although really intended for a nominal 9V supply.

INPUT SIGNAL


On the receiving side, the input signal is a.c. coupled through capacitor C6 to the input of comparator IC3. This requires a minimum of about 200mV peak-to-peak (75mV r.m.s.) for reliable operation but happily accepts much higher levels, making it suitable for operation from most tape recorder Headphone outputs.

The positive feedback applied to this stage through resistor R16 ensures clean switching action. Capacitor C8 and resistor R17 differentiate the output from IC3 into brief negative trigger pulses for timer IC4.

The output pulses from IC4 pin 3 have a constant width of about 360µs, so the average d.c. value varies with their frequency. IC5a gives low-pass filtering to separate out this d.c. level whilst IC5b

provides further filtering and a small gain, with a d.c. "offset" introduced by resistor R24 to arrive at the final output range of 0.45V to 5V (for a 9V supply) required. This output varies with supply voltage of course, but this matches the corresponding change in input required by the Mind Machine's signal generator, so where both are run from the same supply regulation is unnecessary.

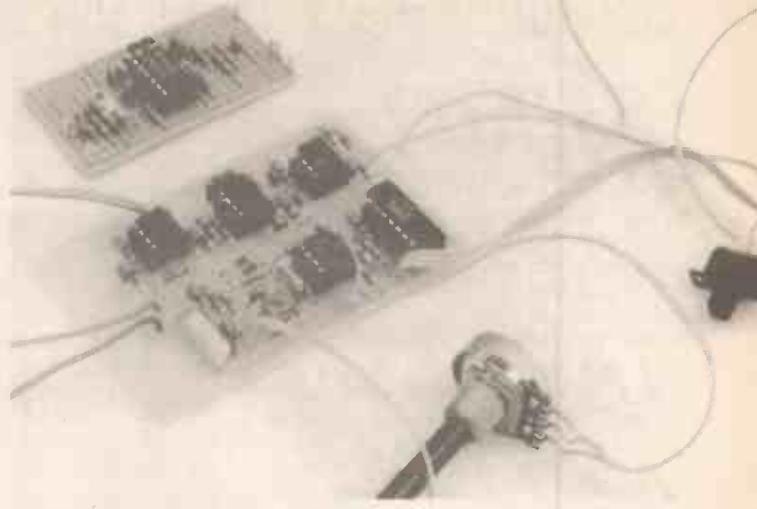The two-pole switch S1 selects Record or Play. Whilst recording, IC1 reset pin 10 is held at positive supply potential to allow the oscillator to run and a signal is taken directly from the oscillator to the input of IC3.



Completed Tape Controller board together with the Signal Level Indicator board.

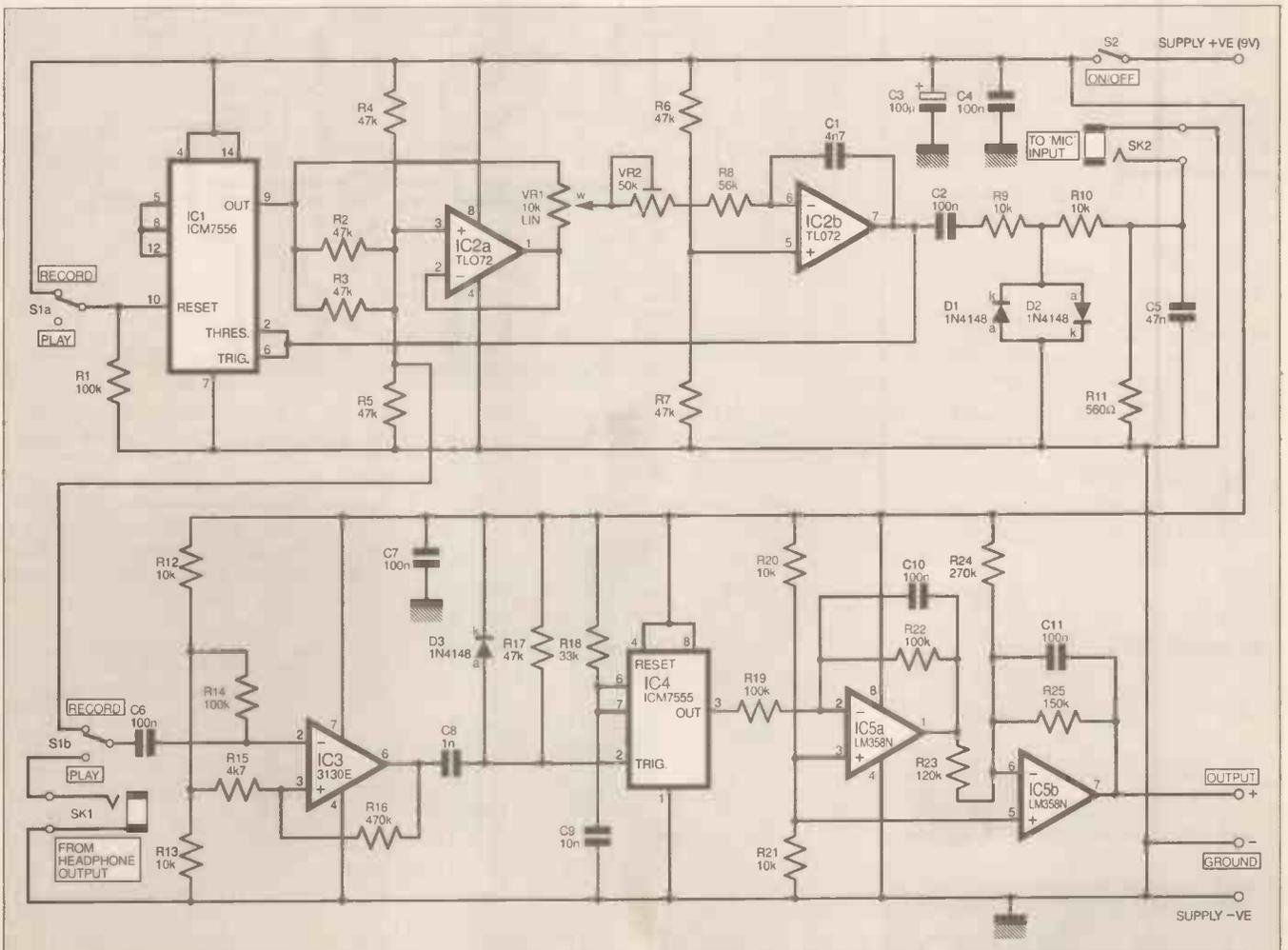


Fig. 2. Complete circuit diagram for the Tape Controller. The Record/Play switch is a double-pole "slider" type.

For playback, IC3 is connected to the Headphone input socket SK1 and resistor R1 is allowed to pull pin 10 of IC1 negative to stop the oscillator. This is not strictly necessary, but prevents any chance of interference from this source.

CONSTRUCTION

Construction of this circuit should prove straightforward. The positions of all the components on the printed circuit board (p.c.b.) are shown in Fig. 3, together with a full size copper foil master. This board is available from the *EPE PCB Service*, code 989.

First, all the small components such as resistors, capacitors and diodes should be fitted, in order of physical height for ease of working. Correct polarity, as marked in the layout diagram, is essential for capacitor C3. Since this is a radial-lead component laid horizontally for a low profile, a drop of glue applied to its body before soldering will help to secure it.

COMPONENTS

CONTROLLER

Resistors

R1, R14,	
R19, R22	100k (4 off)
R2, R3, R4, R5,	
R6, R7, R17	47k (7 off)
R8	56k
R9, R10,	
R12, R13,	
R20, R21	10k (6 off)
R11	560Ω
R15	4k7
R16	470k
R18	33k
R23	120k
R24	270k
R25	150k

All 0.6W 1% metal film

Potentiometers

VR1	10k rotary carbon, lin.
VR2	50k cermet preset, horiz.

Capacitors

C1	4n7 polyester layer
C2, C4, C6,	
C7, C10, C11	100n resin-dipped ceramic (6 off)
C3	100μ radial elect. 25V
C5	47n resin-dipped ceramic
C8	1n ceramic plate
C9	10n polyester layer

Semiconductors

D1, D2,	
D3	1N4148 signal diode (3 off)
IC1	ICM7556 CMOS dual timer
IC2	TL072 dual op.amp
IC3	3130E CMOS op.amp
IC4	ICM7555 CMOS timer
IC5	LM358N dual op.amp

Miscellaneous

SK1	3mm mono jack socket (2 off)
S1	2-pole 2-way slider switch
S2	single-pole slider switch (optional)

Printed circuit board available from *EPE PCB Service*, code 989; case, size to choice – see text; 8-pin d.i.l. socket (4 off); 14-pin d.i.l. socket; control knob; multistrand connecting wire; solder pins; solder etc.

Approx Cost
Guidance Only

£18

excluding case

Solder pins are useful for making external connections but these may be a tight fit in the board, in which case they may have to be fitted first. Sockets are recommended for the five i.c.s as this makes testing much easier.

The board has a couple of holes to allow it to be mounted above the Mind Machine Sound/Lights signal generator board with a pair of spacers, or screws with nuts, for positioning. The case can be as suggested for the original, though it might be made into a more compact unit as this board takes up much less space than last month's slider-pot controller.

FIRST TESTS

Prior to installing the p.c.b. in its case, the completed board should be powered

with 9V before any of the i.c.s are inserted. If it draws around 1.2mA the construction is probably OK so far.

Following this, control potentiometer VR1 should be connected, points A and B shorted together and point C connected to point D to simulate the "record" condition. The points mentioned are also shown in Fig. 4, the external wiring connections diagram.

Next, IC1 and IC2 should be fitted, and when the board is powered it should take a supply current of about 5mA. If checked with a meter for d.c. voltage, pin 9 of IC1 and pin 7 of IC2 should both be within 0.5V of half the supply voltage.

If available, an oscilloscope can be used to check the signals at these points which will be (hopefully!) a rail-to-rail


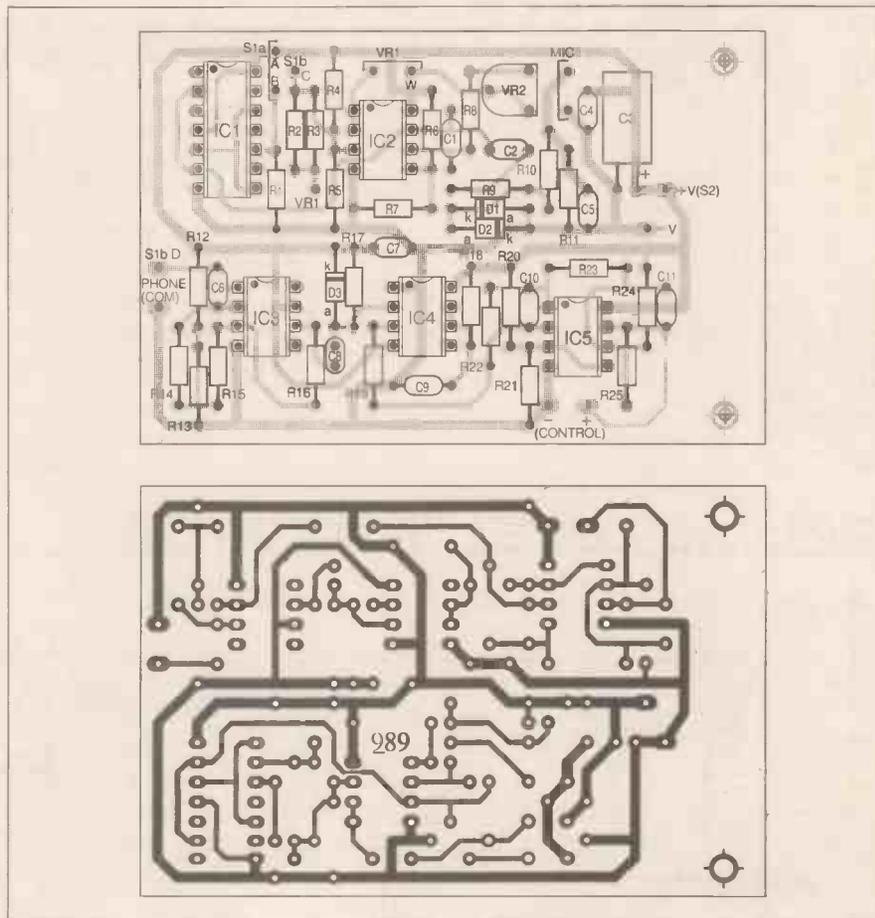


Fig. 3. Tape Controller printed circuit board component layout and full size copper foil master pattern.

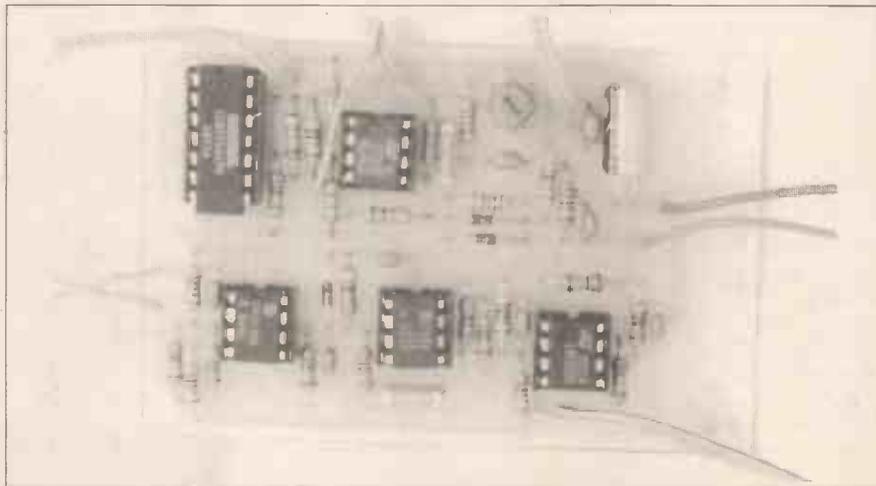

Layout of components on the completed Controller p.c.b. Note the radial electrolytic capacitor is mounted flat on the board.

squarewave from IC1 and a 3V peak-to-peak triangle from IC2. An 18mV signal should be present at the output connection, which should be checkable with most DVMs. This completes the signal generation side.

Fitting IC3 should add about half a milliamp to the supply current. If points C and D are still connected IC3 will have an input, so the average d.c. voltage at its output should be around half the supply and a 'scope should show a rail-to-rail squarewave output.

Inserting IC4 in the board should add another half-milliamp to the supply for a total of about 5.5mA. The average d.c. voltage at pin 3, the output, will be somewhere around 3V to 6V, varying with the setting of VR1's wiper. It also depends on the setting of preset VR2 though, which will be set up shortly. Fitting IC5 should take the supply current to its final value of about 6.5mA and the output voltage should vary with the setting of VR1.

Final adjustment consists of re-checking that the supply is 9V, then setting VR1 to minimum and adjusting preset VR2 for an output of 0.45V. If VR1 is then turned right up the output should be around 5V.

A frequency meter can be used to check the frequency range of about 1kHz to 2kHz, though this is not really necessary. Finally, connections can be made to a tape recorder and a signal sequence recorded and replayed as a complete functional test.

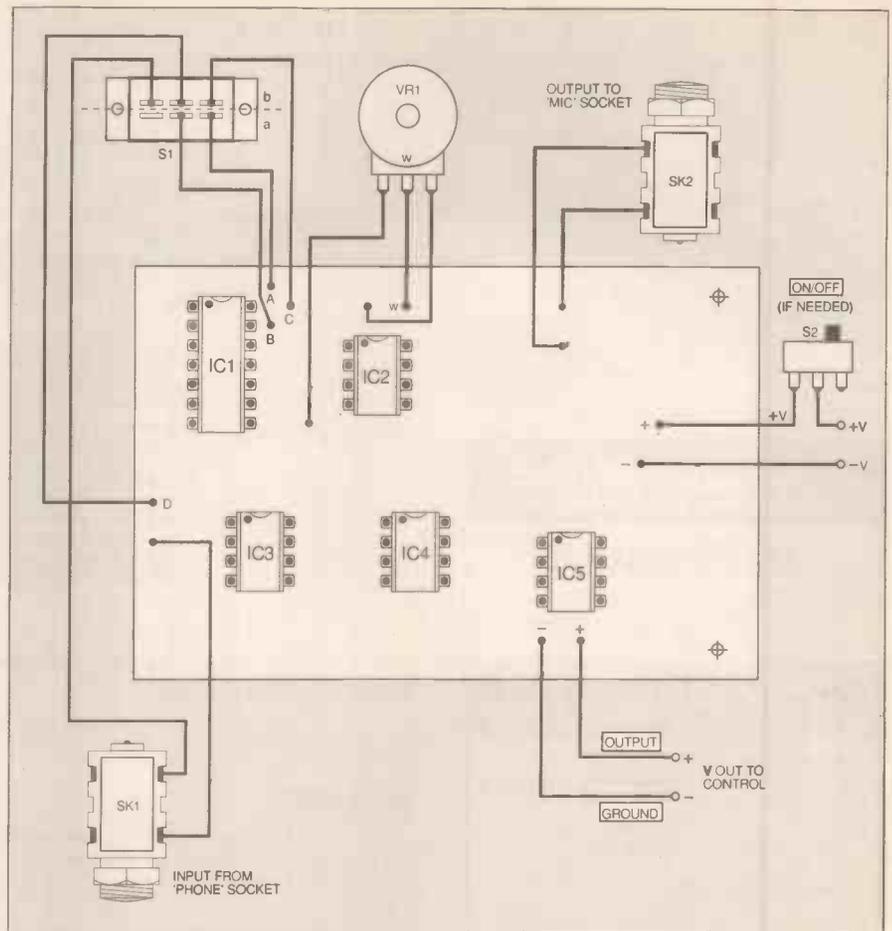


Fig. 4. Interwiring from the printed circuit board to off-board components.

SIGNAL LEVEL INDICATOR

For playback, the level supplied to the p.c.b. must be higher than about 70mV r.m.s. The easiest way to check this is to record brief periods of signal at the high and low ends of the range and play them back whilst monitoring the recorder output with a DVM on an a.c. voltage range.

The tape recorder's volume control can be set for a measured output of around 500mV r.m.s. and its setting noted for future use. With some recorders the level may vary with frequency, which is why both ends of the range should be checked.

For constructors who either don't have a DVM or who prefer a real "Rolls-Royce" job, the circuit of Fig. 5 can be incorporated into the unit to provide a continuous indication of "Input Level". This consists of an "absolute-value" circuit, or perfect full-wave rectifier, built with IC1a and IC1d followed by a voltage-to-current converter IC1c to drive the meter.

An artificial "ground" of half the supply voltage is provided by IC1b. This circuit works with supplies down to 5V, draws only a couple of milliamps and indicates up to one volt r.m.s. with a

frequency coverage of about 300Hz to 10kHz.

A simple and compact stripboard layout for the Level Indicator circuit is shown in Fig. 6, together with an underside view showing breaks in the copper strips and soldered connections. The meter used is a 1mA unit, though others can be used with suitable adjustment of resistors R9 and R10. These should be chosen using the formula $R = 0.44/I$, where I is the full-scale current of the meter used.

Power can be taken from the main supply, and the input should be connected to the headphone connection socket, so that it is disconnected during recording. These connections are also shown in Fig. 6. In


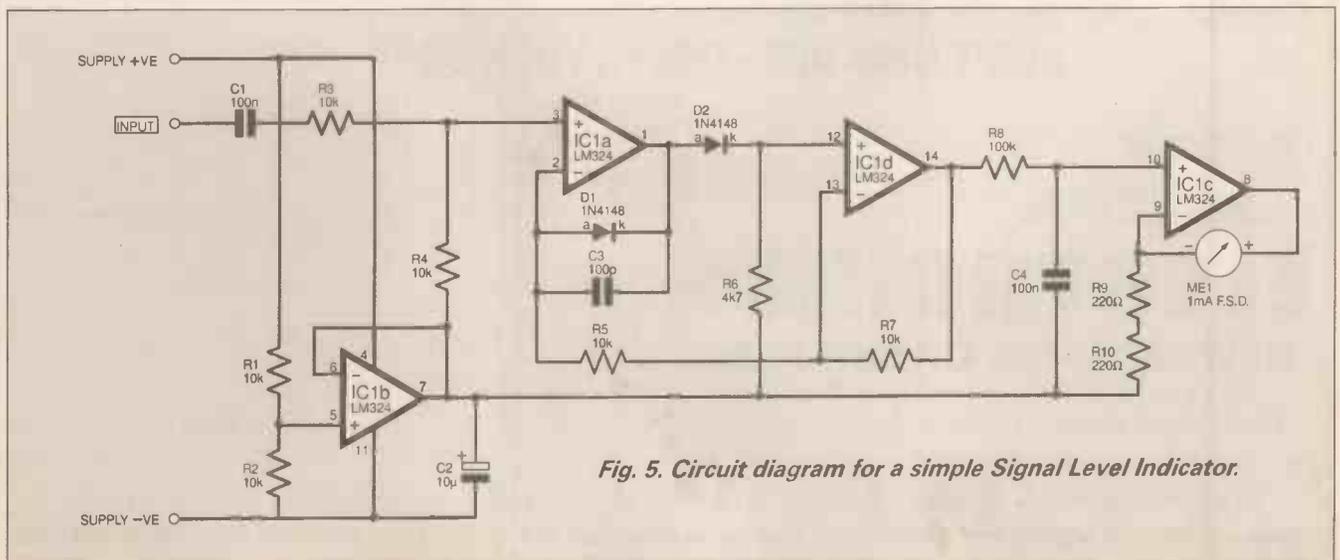


Fig. 5. Circuit diagram for a simple Signal Level Indicator.

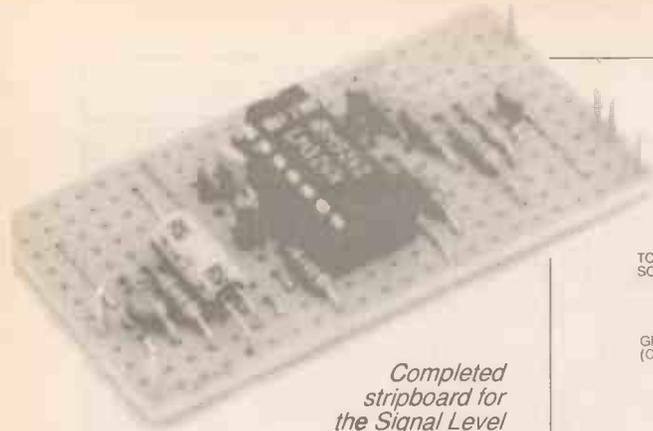

Completed stripboard for the Signal Level Indicator.

COMPONENTS

LEVEL INDICATOR

- Resistors**
 R1, R2, R3, R4, R5, R7 10k (6 off) **See**
 R6 4k7 **SHOP**
 R8 100k **TALK**
 R9, R10 220Ω (2 off) **Page**
 All 0.6W 1% metal film

- Capacitors**
 C1, C4 100n resin-dipped ceramic (2 off)
 C2 10μ radial elect. 50V
 C3 100p ceramic

- Semiconductors**
 D1, D2 1N4148 signal diode (2 off)
 IC1 LM324N quad op.amp

- Miscellaneous**
 ME1 1mA f.s.d. moving coil meter (see text)
 Stripboard, 0.1in. matrix, size 12 strips × 23 holes; 14-pin d.i.l. socket; multistrand connecting wire; solder pins (6 off); solder etc.

Approx Cost **£4**
Guidance Only **excluding meter**

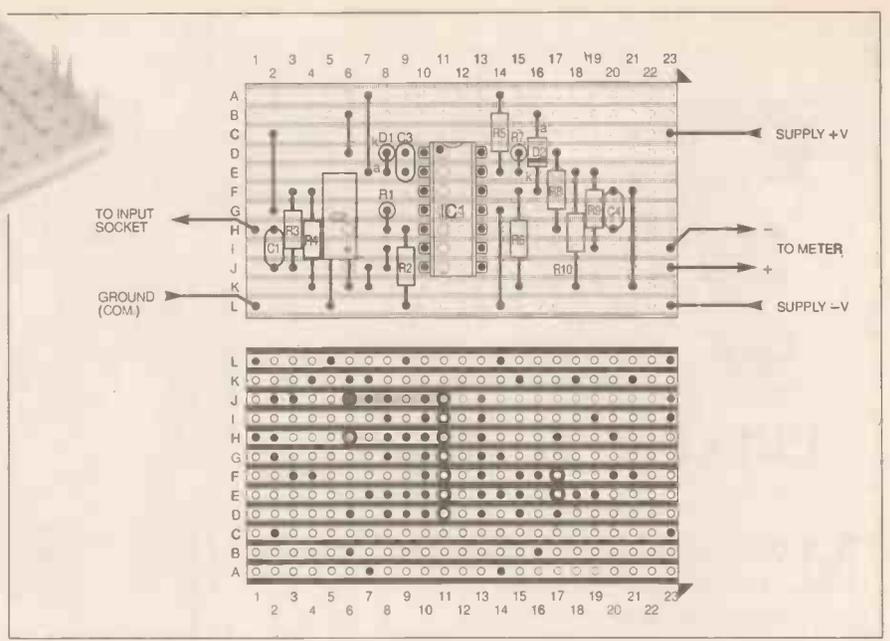


Fig. 6. Signal Level stripboard component layout and details of underside breaks required in copper tracks.

use, the input level should be adjusted for a meter reading of half-scale.

IN USE

The Tape Controller could be used with the original Mind Machine, the only snag being that it would need a regulated supply. Two approaches to this are possible.

The simplest would be to supply the whole circuit from a pack of eight NiCad cells, which would have a sufficiently constant output voltage to power the programmer without regulation. Another method would be to obtain a constant 10V supply from an ICL7660 used as a step-up converter, powering it from the regulated 5V supply of the original signal generator board. In both cases the output would need to be divided by two to match the input range of the old signal generator, using a pair of 10k resistors.

There must be many other applications where a controller of this type could prove useful. Different output voltage ranges and offsets can easily be arranged by altering the values of resistors R24 and R25.

With two controllers and a stereo recorder two signals could be recorded simultaneously onto the two channels. Alternatively, for portable applications, a tiny pocket dictating machine can be used as the controller.

The author has a Sanyo TRC-570M micro cassette recorder which cost only around £30, yet has sockets for external microphone and headphone, voice-activated recording and two tape speeds. The faster speed will give a half-hour recording, and the unit runs for ages on a pair of AA batteries. It works perfectly with the controller board and, needless to say, finds plenty of other uses. □

NEXT MONTH * CHILD'S NIGHTLIGHT * TELEPHONE LINK
*** FREQUENCY GENERATOR & COUNTER ***
PLUS - Special Series - OSCILLOSCOPES
DON'T MISS OUT - ORDER YOUR COPY NOW!

EVERYDAY

PRACTICAL

ELECTRONICS

NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of *Everyday Practical Electronics* for me each month

Signed

Name and Address
 (BLOCK CAPITALS PLEASE)

.....

.....

.....

..... Post Code

Everyday Practical Electronics is published on the first Friday of each month and distributed S.O.R. by Seymour. Make sure of your copy of EPE each month - cut out or photostat this form, fill it in and hand it to your newsagent.



IF AN ADVERT IS IN PRINT, IS IT PROPER?

Most advertisements are legal, decent, honest and truthful. A few are not, and, like you, we want them stopped.

If you would like to know more about how to make complaints, please send for our booklet: 'The Do's and Don'ts of Complaining'. It's free.

The Advertising Standards Authority.

We're here to put it right. ✓

ASA Ltd., Dept. Z., Brook House, Torrington Place, London WC1E 7HN.
This space is donated in the interests of high standards of advertising.

PIC EEZE

This is the easiest way to start using PIC microcontrollers. PIC EEZE is a powerful and versatile development system that allows a cheap entry level into the world of PIC programming. Can be upgraded whenever you're ready.

PIC EEZE-1 £44.95

supports: 16C61/62/63/64/65/71/73/74/84/620/621/622/Serial EEPROMs.

PIC EEZE-2 £52.95

supports: as PIC EEZE-1 plus 16C54/55/56/57/58.

PIC EEZE-3 £72.95

supports: as PIC EEZE-2 plus In Circuit Emulation (even A to D on 71)

All systems have high quality PCB with a quality universal ZIF socket (so you don't have to spend any more money to get an easy to use system), on board regulation, expansion port and when new PIC versions are released the system can be software upgraded. All software is **FREE** so you won't have to keep spending to keep up. Microchips Assembler and simulator along with our own programming software and PIC examples are supplied on disc. Connects to PC via parallel port. A serial version will be available soon (Please ring as it may already be available). A suitable PSU and Lead are required, which we can supply if needed. Interface Lead £4.00. PSU £4.95.

LPAK £28.00

An introduction to PIC programming. The board plugs into any PIC EEZE system expansion port and has on board 7-segment displays, LED's button and switches which can be controlled via software to show simple PIC programming for beginners.

DPAK £28.00

Demonstration boards (2) for 18/28 pin PIC's. The first board is a stand alone PCB c/w ready made oscillator, regulation, etc, and it can be used with breadboards, i.e. sockets, etc, or it can be used with the second board which is a version of LPAK.

Compiler to create your own BASIC PIC's - ring for availability.

SUPPORT

We will give continuing support to users of our systems with their PIC projects/problems. Further expansion of the system is planned which include - a 17CXX Adapter, Smart Card Reader and **FREE** software to allow the system to be used for data logging and PC I/O port control.



Please add £2.00 P&P and make cheques payable to **LENNARD RESEARCH**


29 Lavender Gardens, Jesmond, Newcastle upon Tyne, NE2 3DD.
Telephone (0191) 281 8050.

Summer '96 Circuit Catalogue now in preparation...

The summer 1996 catalogue has 280 pages packed with over 4000 products.

- ▶ New Multimedia CD ROM titles
- ▶ New radio amateur equipment
- ▶ Even further additions to our Computer section
- ▶ PIC Microcontroller projects and modules
- ▶ Hundreds of new products including Books, Computers, Rigs & receivers, Semiconductors and Test Equipment
- ▶ 280 pages, 25 sections and over 4000 products from some of the worlds finest suppliers

£1.95 + P&P

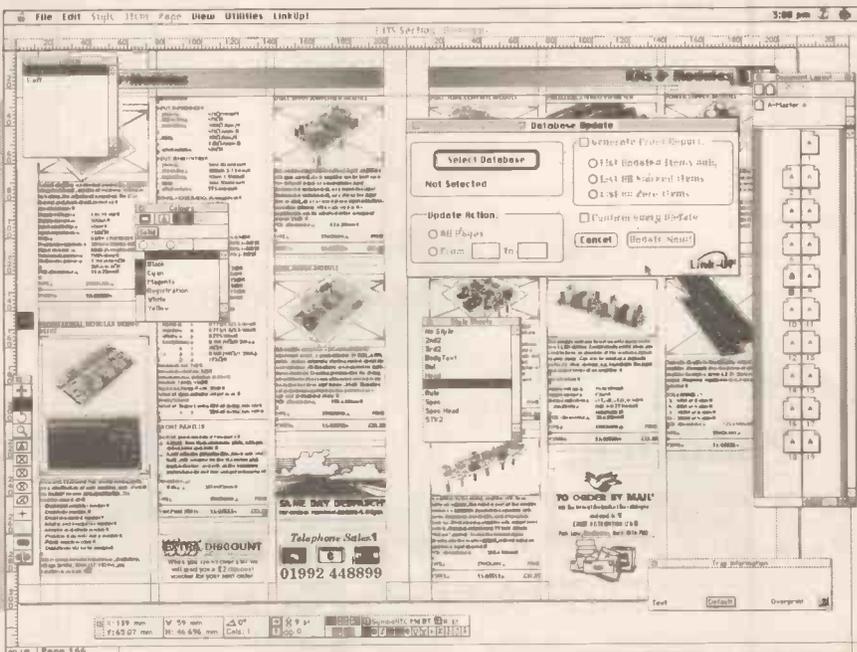

Cirkit

Tel: 01992 448899 Fax: 01992 471314



Cirkit Distribution Ltd ▶ Park Lane ▶ Broxbourne ▶ Herts ▶ EN10 7NQ

VERSATILE PIR DETECTOR ALARM



ANDY FLIND

Will protect places other systems cannot see. Ideal for remote sites.

PASSIVE infra-red (PIR) detectors are currently one of the most reliable ways to detect the presence of the human body, and are widely used in intruder alarm systems, automatic door openers and many other applications.

Despite the many ready-built detectors available, there are still occasions where construction from scratch may be necessary. There could be a need to build one into another piece of equipment, or to disguise it in some way, or it might be helpful to be able to adjust circuit values to alter the basic sensitivity.

"Micropower" operation, which is possible with this project, may be needed for battery operation at a remote site. Even if none of these reasons apply, there is still the fascination of working with very sensitive circuits which appear to be "aware" of their surroundings.

ON GUARD

The prototype for this project was designed to protect the author's garage, following an attempted break-in and several thefts from nearby properties. There was also a need to protect a garden shed some distance from the nearest household mains power supply, so micropower operation was desirable.

The garage door faced onto a secluded alley along which people can walk, so the circuit had to be able to distinguish the brief "blips" caused by passers-by from the more prolonged signals that would be generated by potential felons loitering in front of it. An inconspicuous sensor "eye" was preferred to avoid attracting unnecessary attention to the door, since if it was obviously protected by an alarm this might give the impression that there were articles of value within.

Apparently a burglar, if aware of a PIR detector, is able to disable it by spraying it with aerosol foam. The sensor of this project can easily be concealed, looking out through a small hole drilled in the door at waist height, and the sensitivity can be set with a simple "pulse counting" circuit.

Two types of output are available, and where it is used as part of a system a few additional components allow the detection of any tampering with wiring connecting it to this. The basic circuit can be operated from battery supplies as it has a "standby" drain of just 200 μ A, making it ideal for the protection of remote sheds, garages and other locations where mains power is not readily available.

SENSOR


The sensor in a PIR device is a type of piezo-ceramic element which generates a voltage when exposed to long-wave infra-red radiation of the kind given off by the human body. This voltage is very small and is sourced from a very high capacitive impedance.

Steady signals such as those resulting from the ambient temperature have to be cancelled out, so the sensors usually have an internal discharge resistor of very high value connected across the element and a built-in f.e.t. source follower to buffer its output. A circuit designed to work with one of these sensors needs very high voltage gain at low frequency, usually below two Hertz (2Hz), with a threshold comparator to decide when the signal level corresponds to the presence of a body.

CIRCUIT DESCRIPTION

The full circuit diagram of the PIR Detector project is shown in Fig. 1. Amplification and level sensing is carried out by the upper section of the circuit, which is designed around IC2, an LP324 quad op.amp i.c.

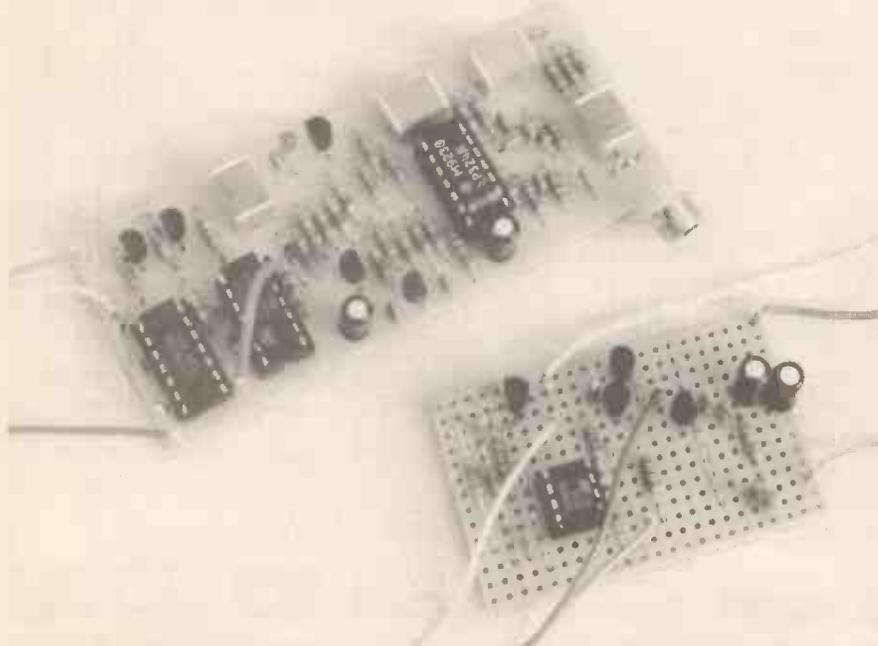This is the "micropower" version of the well-known LM324 and typically draws just 100 μ A of supply current for all four amplifiers. It's slower, but this is not a problem with this application. The LM324 can be used instead if low power consumption is not important.



Complete Sensor p.c.b. and Loop Interface strip board.

Detector IC1 is the PIR sensor, with resistor R1 providing the source load for its internal f.e.t. The output from this is a.c. coupled to the first amplifier stage IC2a by capacitor C1. Resistor R2 and capacitor C2 filter out any local high-frequency interference such as nearby transmitters, mobile phones and the like.

This stage operates as an inverting amplifier with a maximum voltage gain of about 90. The frequency response is tailored by components C4, R7 and C3, R4, which give it a bandpass response centred on 1.3Hz. The half-gain bandwidth is about 0.5 to 3.2Hz, with a fairly rapid roll-off both above and below this.

The second amplifier stage, IC2b, provides further voltage gain of about 22 with more frequency response tailoring, giving a total maximum voltage gain at 1.3Hz of close to 2000. The remaining two amplifiers, IC2c and IC2d, are connected to form a window comparator which detects both positive and negative excursions beyond the preset level.

To alter the basic sensitivity the value of shunt resistor R11 can be changed, higher values will raise the threshold voltages and reduce the sensitivity. With the value shown the thresholds are $\pm 30\text{mV}$, if R11 is omitted altogether they will rise to 95mV .

STABLE SUPPLY

The very high, low-frequency gain of this part of the circuit requires an exceptionally stable supply to ensure stability. Conventional decoupling is not effective at such low frequencies so a regulator has to be relied upon to prevent any voltage fluctuation.

An LP2950 5V voltage regulator, IC3, is used here to ensure supply stability. This offers significant advantages over the more common 78L05 type. Its quiescent drain is less than $100\mu\text{A}$, contributing to the very low overall consumption of this project.

It can operate with less than half a volt between the input and output potentials, allowing a wider range of supply voltages.

Most important, it has better rejection of sudden fluctuations of input voltage.

For design purposes it was assumed that this sensor would be used with systems either using batteries or relying on battery backup from time to time. So, when an alarm is initiated, the battery voltage may take a sudden dive as it is called upon to drive a large siren or bell.

Working on the assumption that the maximum such voltage drop would be 2V, the output stability of the standard 78L05 type of regulator was found to be inadequate, passing enough of the sudden input change through to the output to cause a false alarm. The improved performance of the LP2950 eliminates this problem. Unfortunately it is more expensive but, if cost is a problem, a 317 regulator can be used provided appropriate resistors are inserted to set its output to 5V.

SIGNAL PROCESSING

The lower part of the circuit diagram (Fig. 1) is concerned with processing the

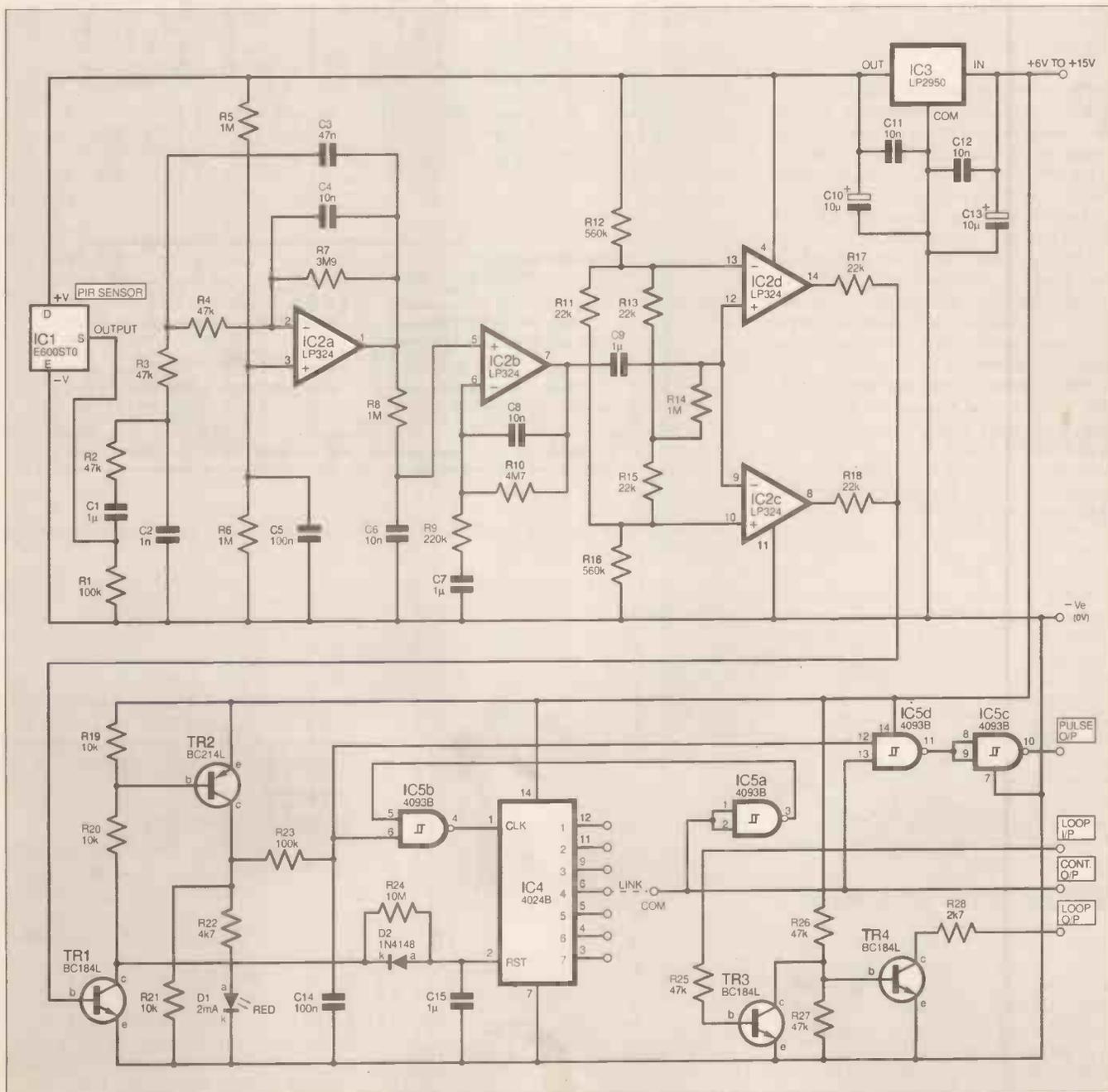


Fig. 1. Complete circuit diagram for the pulse-counting Versatile PIR Detector Alarm.

signal from the comparator and providing outputs suitable for various systems. By its nature, the output from a circuit using a PIR device consists of a series of pulses, so a good way of adjusting sensitivity is by counting a predetermined number of these pulses before initiating the alarm.

This circuit does this as follows: When either of the window comparator outputs (IC2d pin 14 and IC2c pin 8) goes high, transistor TR1 is biased into conduction. This turns on TR2, which lights the l.e.d. D1 to indicate signal detection. Transistor TR1 also discharges capacitor C15 via diode D2, taking the Reset input of the counter IC4 low so this i.c. is able to start counting.

At this point all the outputs from IC4 are "low", so IC5b has a "high" input from IC5a and can pass the output from TR2 to the Clock input of IC4. Resistor R23 and capacitor C14 delay this signal briefly so that C15 can be discharged before it arrives.

When the input from the comparator ends, TR1 turns off and C15 starts charging through R24. It takes about eight seconds to reach a level sufficient to reset IC4 and if the next pulse arrives before this, capacitor C15 is discharged again whilst the counter advances another step.

If enough pulses are received without an eight-second interval, the selected counter output will go high. This prevents further clock impulses by sending a low input to IC5b from IC5a, and the output will remain high until an eight-second break allows C15 to charge and reset IC4.

The Continuous Output is one of the two available to the user. The second is a Pulsed Output, generated by IC5d and IC5c by combining the continuous output with the signal from TR2 collector (c). Both can be used with the "Loop" option to detect any tampering with wiring to the unit, which will be explained later.

SENSITIVITY

Count advance in IC4 takes place on negative edges to the Clock input which correspond to the leading edges of the pulses from the detector IC1; so the first output, from IC4 pin 12, goes high immediately and can be used for instant response when the pulse counting is not required. The second output requires two pulses before it goes high, the third four and so on up to the seventh output from pin 3 which operates after sixty-four pulses.

The prototype is set to sixteen, pin 5, and has not so far operated "in anger" although just ten seconds spent in front of the "eye" is sufficient to trigger it. All seven outputs from the divider are available for sensitivity selection, though it is unlikely the highest will be needed. For low cost and reliability selection is made by a soldered link.

SELECTIVE SYSTEM

This is a relatively simple circuit to construct and test although its compact layout requires careful soldering. However, before commencing the construction, some of the possible options available should be considered and chosen before starting.

If the Pulse Counting feature is not required IC4 and IC5 can be omitted, along with resistors R23 and R24, diode D2 and capacitors C14 and C15. The output can

then be taken from the collector of TR2, a convenient connection point being from where the top of R23 would have been.

Indicator l.e.d. D1 is not essential, it is included to assist when positioning the unit. It could be made externally visible as a warning if required, or it could be disconnected after setting up to save power.

Simple systems will probably not need the Loop components, transistors TR3 and TR4 with their four associated resistors which should be omitted anyway in microworld applications as they increase the supply current.

CONSTRUCTION

The printed circuit board component layout and full size copper foil master pattern for the PIR Sensor is given in Fig. 2. The off-board wiring is shown in Fig. 3. This board is available from the *EPE PCB Service*, code 988.

When the required configuration has been decided, it is suggested that all the resistors and diode D2 (if used) are fitted first. This should be followed by the small ceramic capacitors, sockets for IC2, IC4 and IC5, then the transistors.

Finally, the regulator IC3 and the polyester capacitors C1, C7, C9 and C15 should be soldered in place on the p.c.b. Solder pins are useful to simplify wiring to off-board connections. The circuit board should now be ready for testing.

TESTING

The first test routine is to power up the board with no i.c.s fitted save IC3, using a supply between 9V and 12V. The current drawn should be very small, perhaps a hundred microamps, and the regulated 5V supply from IC3 should be present.

This can be followed by insertion of IC2. The outputs of IC2a and IC2b (pins 1

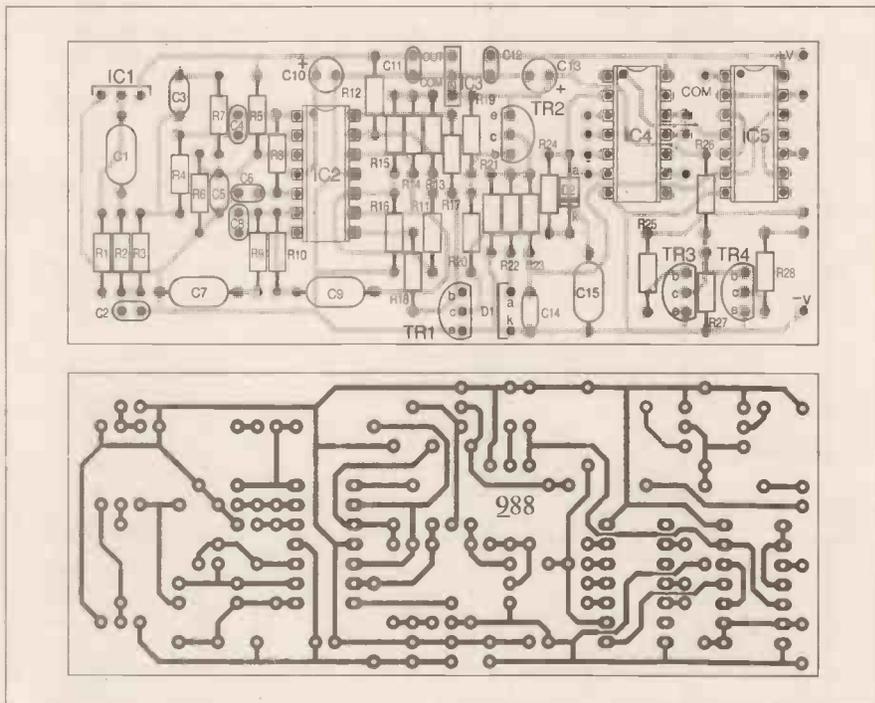


Fig. 2. Sensor printed circuit board component layout and actual size underside copper foil master pattern.


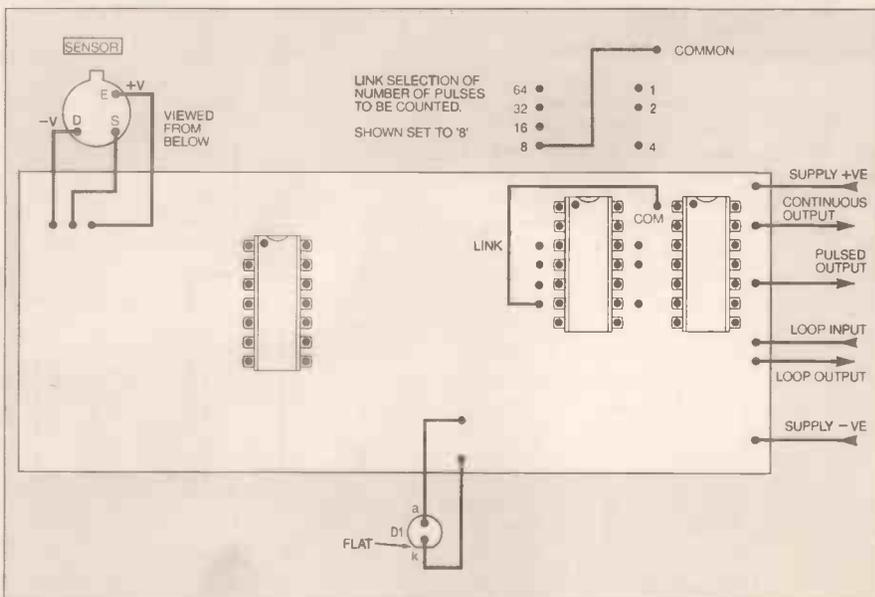


Fig. 3. Interwiring connections to Sensor board and link to select pulse count details.

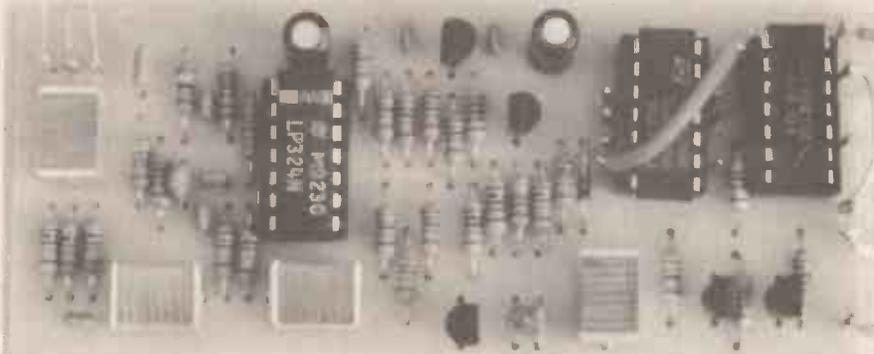

PIR Sensor Board

Resistors

R1, R23	100k (2 off)
R2, R3,	
R4, R25,	
R26, R27	47k (6 off)
R5, R6,	
R8, R14	1M (4 off)
R7	3M9
R9	220k
R10	4M7
R11, R13,	
R15, R17,	
R18	22k (5 off)
R12, R16	560k (2 off)
R19, R20,	
R21	10k (3 off)
R22	4k7
R24	10M
R28	2k7

All 0.6W 1% metal film.

Capacitors

C1, C7,	
C9, C15	1µ polyester layer (4 off)
C2	1n resin-dipped ceramic
C3	47n resin-dipped ceramic
C4, C6,	
C8, C11,	
C12	10n resin-dipped ceramic (5 off)

C5, C14	100n resin-dipped ceramic (2 off)
C10, C13	10µ radial elect. 25V (2 off)

Semiconductors

D1	3mm red low-current (2mA) l.e.d.
D2	1N4148 signal diode
TR1, TR3,	
TR4	BC184L <i>n</i> pn transistor (3 off)
TR2	BC214L <i>p</i> np transistor
IC1	E600STO low-noise, infra-red detector
IC2	LP324 quad op.amp (low power version of LM324N)
IC3	LP2950CZ micropower 5V positive regulator
IC4	4024B CMOS 7-stage ripple counter
IC5	4093B CMOS quad Schmitt NAND gate

Miscellaneous

Printed circuit board available from *EPE PCB Service*, code 988; plastic or metal case, size to choice – see text; 14-pin d.i.l. socket (3 off); p.c.b. stand-off pillar (4 off); multistrand connecting wire; solder pins; solder etc.

See
**SHOP
TALK**
Page

and 7) should both have quiescent d.c. potentials of 2.5V, though it should be noted that this circuit will take several seconds to settle after switch-on. The outputs of IC2c and IC2d (pins 8 and 14) should both be at negative supply potential so the collector (c) of transistor TR1 should be high and that of TR2 low.

The l.e.d. D1 should be connected next, and the proverbial “wet finger” dabbed across the 5V positive supply and the top of C1 should cause it to flash.

If the pulse counting circuit is to be used, IC4 and IC5 should be inserted, and one of the link options connected before power is re-applied. Detail of these are shown in the connection diagram of Fig. 3. The third output, IC4 pin 9, is suggested for testing. If the continuous output is now monitored, it should go positive with the fourth flash of the l.e.d., and return to the low state about eight seconds after the l.e.d. is extinguished.

This completes functional testing, so the PIR sensor IC1 can now be connected up for a full test and any necessary sensitivity adjustments can be made. The unit is extremely sensitive, even without the fresnel lens often used with PIR devices, so it may be necessary for some purposes to increase the value of resistor R11 to reduce range.

If the sensor is mounted off-board, miniature 2-core screened cable is recommended, with the screen connected to the 0V (battery – VE) point. Note that the case of the sensor is connected to its 0V lead. Pinout details for the PIR sensor are shown in Fig. 4, which also shows the direction of maximum detection sensitivity.

Siting the detector behind a surface with a hole will help to generate an infra-red image that moves across the element for a better response, or placing a short tube over it will make it more directional. Experiments indicate that many substances transparent to visible light seem to attenuate longwave infra-red to some extent, so the prototype was protected with polythene cut from an ordinary bag. For more demanding applications special material or a lens could be used.

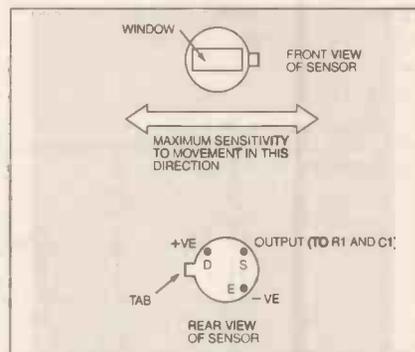


Fig. 4. Sensor pinout and sensitivity details.

Supply voltage for this project can be anywhere between 6V and 15V, making it ideal for use with the 12V supplies of most alarm systems, but also allowing operation from 9V dry battery supplies. PP3 type batteries are not recommended, but a pack of six alkaline “AA” cells should give operation for more than a year, and “C” or “D” cells even longer.


These larger cells will probably be needed in any case for powering an alarm siren in a remote location. One interesting possibility would be to supply the Sensor Board from a rechargeable PP3, using a solar panel to top this up during daylight hours.

LOOP INTERFACE

The “Loop” circuit is intended for use with larger systems, which will normally

ASSEMBLY

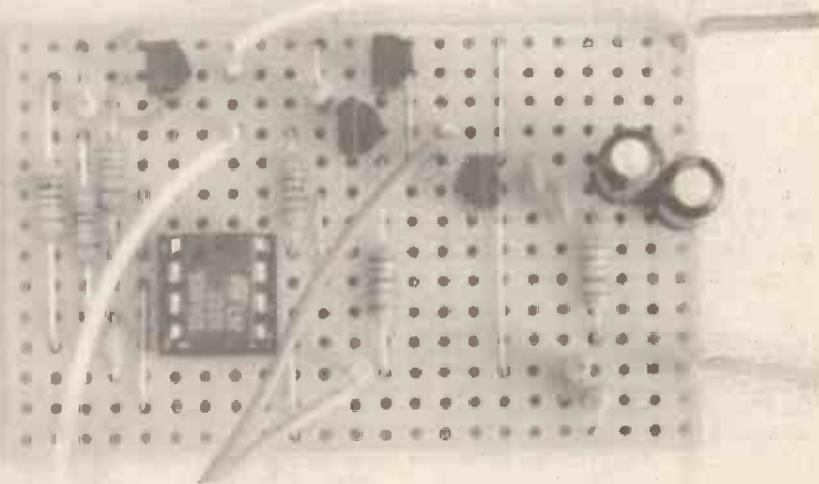The type of case used will depend on the use to which the unit is to be put so the choice is left to the constructor. Connections for the infra-red sensor, l.e.d., supplies and outputs are shown in Fig. 3.



Layout of components on the Loop Interface stripboard.

have a mains power supply, perhaps with a lead-acid backup battery. It works, as the name suggests, by detecting any variation in a small but continuous current passed around the wiring between it and the main sensor system to detect any tampering.

A three-core cable is needed, the positive and negative supplies, and one for the signal. This has 5V supplied at the system end through a 2.7 kilohm (2k7) resistor, and the assumption is that under normal conditions it will be terminated to negative at the Sensor end through another 2k7 resistor so the voltage on the "loop" wire

will always be 2.5 volts. This is monitored at the system end by a window comparator, with more than half a volt of deviation either way being interpreted as an active alarm.

At the sensor end (Fig. 1), transistor TR4 is biased on by the positive supply through resistor R26, and provides the termination through R28. "Loop input" is connected to the selected output, Pulse or Continuous. If this goes high, it will turn on transistor TR3, which then turns off TR4. This, or cutting of any of the three wires, or short-circuiting any or all of them, will result in an alarm

being given at the system end. The supply is also current-limited to prevent damage to the power supply in the event of a wiring short-circuit.

INTERFACE CIRCUIT

The Loop Interface circuit used with the prototype is shown in Fig. 5. The primary supply to this unit is a battery-backed 12V supply, actually 13.8V most of the time as this is the normal lead-acid charging voltage.

A 78L05 regulator, IC2, provides a 5V supply for the interface circuit. This goes out to the loop connection through R3 and the voltage on this wire is monitored by the window comparator IC1. Resistor R2 and capacitor C1 filter any interference from the input to the comparator.

The thresholds are set by resistors R5, R6 and R7. When either threshold is exceeded, the appropriate output sinks current from R9 to turn on transistor TR3 so the output goes positive.

Transistors TR1 and TR2 with resistor R4 limit the supply current to 10mA. For currents below this TR1 is biased on by R1 and the voltage drop across R4 is less than 0.6V. At 10mA, the voltage across the base-emitter of TR2 reaches 0.6V and TR2 turns on, drawing base current away from TR1 to limit its collector current.

The worst-case condition for this part of the circuit would be a short circuited supply, where it would still dissipate only about 120mW which it should be able to withstand indefinitely.

INTERFACE BOARD

A piece of 2.54mm (0.1in.) stripboard, size 14 strips x 23 holes is used for construction of the Loop Interface circuit. The board component layout for this interface, together with underside breaks in copper strips, is shown in Fig. 6. This is fairly

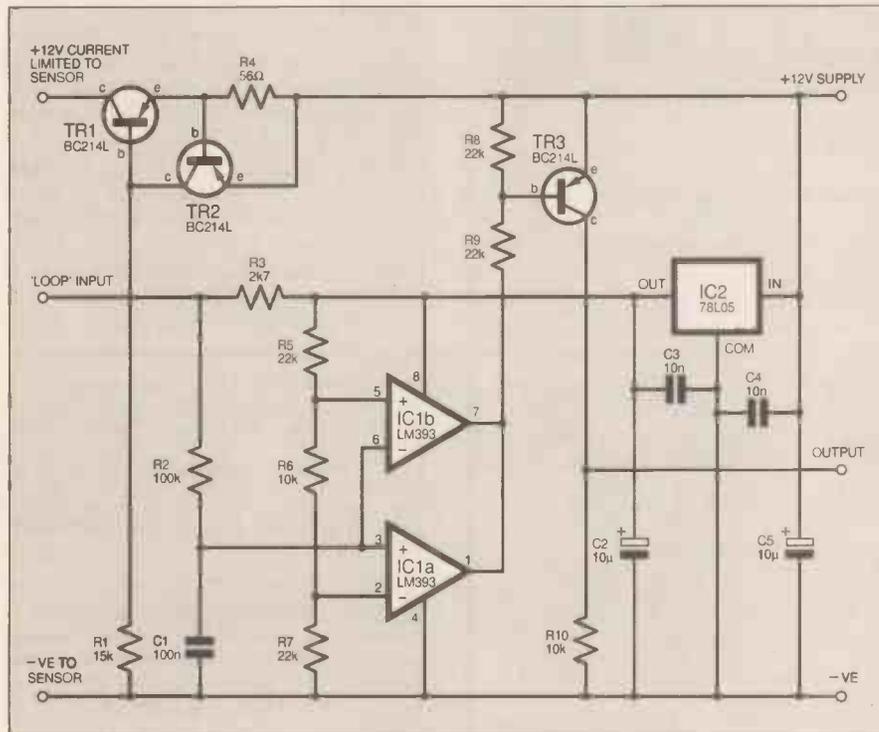


Fig. 5. Circuit diagram for the Loop Interface.

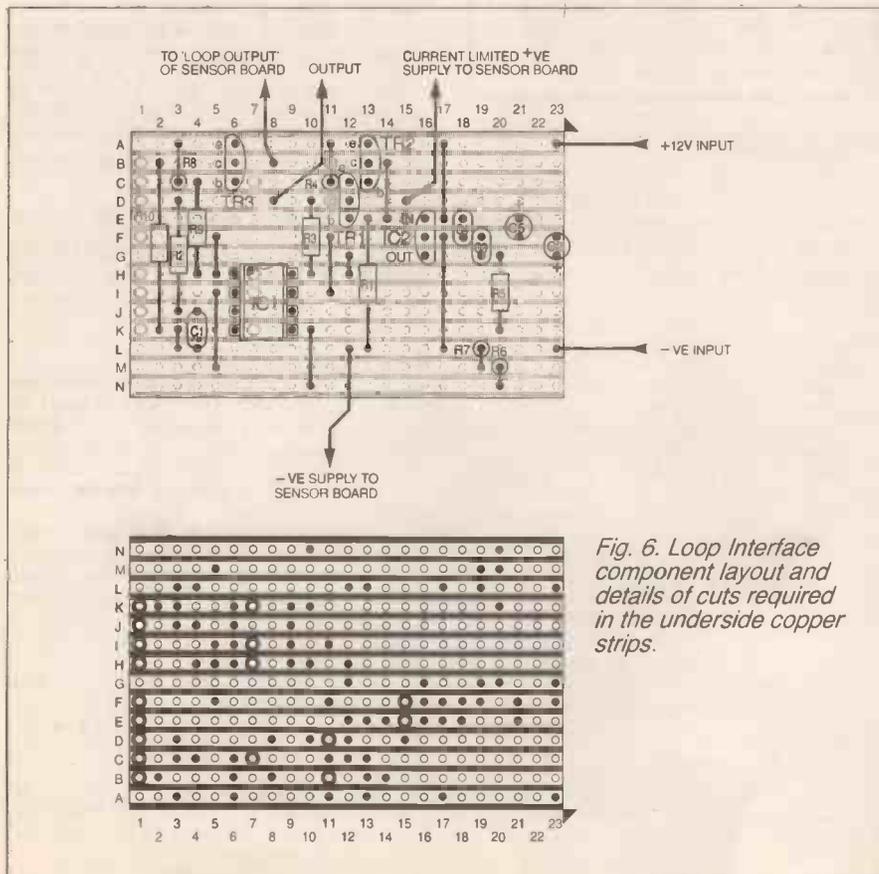


Fig. 6. Loop Interface component layout and details of cuts required in the underside copper strips.

COMPONENTS

LOOP INTERFACE

Resistors

R1	15k	See SHOP TALK Page
R2	100k	
R3	2k7	
R4	.56Ω	
R5, R7,		
R8, R9	22k (4 off)	
R6, R10	10k (2 off)	
All 0.6W 1% metal film		

Capacitors

C1	100n resin-dipped ceramic
C2, C5	10μ radial elect. 25V (2 off)
C3, C4	10n resin-dipped ceramic

Semiconductors

TR1, TR2,	
TR3	BC214L pnp transistor (3 off)
IC1	LM393 dual comparator
IC2	78L05 5V 100mA positive regulator

Miscellaneous

Stripboard, 2.54mm (0.1in.) matrix, size 14 strips x 23 holes; case, see text; 8-pin d.i.l. socket; single-core link wire (component lead off-cuts); multistrand connecting wire; solder pins; solder etc.

Approx Cost
Guidance Only

£4

compact as stripboards go, and to keep the links to a minimum four of the resistors are fitted in a vertical position.

Where more than one interface is required, the resistors R5, R6 and R7 together with the 5V supply and decoupling may be common to all of them. This is reflected in the layout, where the 5V and threshold voltages are generated separately by the section of the circuit to the right of the positive supply output pin, and are carried to the comparator through "bus" strips. If more interfaces are needed, only the section to the left need be duplicated.

Construction of this circuit is straightforward. The breaks in the strips should be made first as shown in Fig. 6, and a careful check of them carried out with a magnifying glass as it's very easy to leave an almost invisible sliver of copper around the edge of a stripboard break. The nine breaks at the left-hand edge will only be necessary if another Interface is added to the left of these.

The components can now be fitted, using a d.i.l. socket for comparator IC1. Solder pins are recommended for wiring to the board as they make this much easier.

With a 12V supply connected, the presence of the 5V from the voltage regulator IC2 should be checked. The action of the 10mA current limit should also be tested, this can initially be done with a 100 ohm resistor which will protect the circuit (and the testmeter!) if the limit fails to operate for some reason. IC1 can now be fitted and tested with a potentiometer connected across the 5V supply, to ensure that the output operates for input deviations of more than about half a volt from 2.5V.

SIREN ALERT

Finally, for those wanting to make a quick and easy connection to a siren, here's a way to do it. Horrendously loud sirens for 12V operation in alarm systems are available from many suppliers, so all that is needed is a power interface.

The simple way to do this is with a power MOSFET as these require virtually no drive current apart from a tiny pulse to charge and discharge the gate capacitance when changing state. The prototype uses an IRF740 power MOSFET in the circuit arrangement shown in Fig. 7.

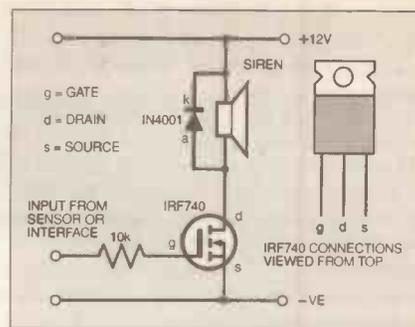


Fig. 7. Simple circuit diagram for interfacing to a warning Siren using a power MOSFET.

This can be driven directly by the Interface Loop of Fig. 5, or by either of the outputs from the Sensor board. The Continuous Output is preferable as this will give a steady output lasting for eight seconds after the intruder has left the area.

Since the MOSFET device has very little resistance in the "on" state it will dissipate very little power, even with a siren drawing an amp or more, so a heat-sink will probably not be necessary. □

SHOP TALK with David Barrington

MIDI Analyser

Several of the components required to make up the *MIDI Analyser* project are special items and are not likely to be available from the usual local dealer. This obviously applies to the ready programmed PIC16C61 microcontroller.

The two-piece ABS plastic case used in the model came from the Maplin range of Union Brothers boxes, code BZ76H. The small pushbutton switch also came from the same source (JM47B).

The diode/transistor 6-pin d.i.l. optoisolator type CNY17-3 is fairly common and should be widely stocked. There seem to be about three versions of this device and it is the one designated with the "-3" that is used here. Some suppliers may offer an alternative which should work but they have not been tested in this set-up. The 8MHz crystal is a general purpose type and should be carried by most of our component advertisers.

Now to the two major items for the Analyser; the PIC microcontroller and the alphanumeric display. Designers, Julian and Brett are able to supply a pre-programmed PIC16C61 microcontroller and the display module for very reasonable sums. A separate program for the PIC is not available for this project because the Analyser may be produced commercially.

The programmed PIC16C61 is obtainable for the sum of £12 and the display module for £12. All prices include postage and packing. (Overseas readers should add £2 to the total order).

All orders should be sent to: **Julian ILETT, 99 Telford Way, Hayes, Middlesex, UB4 9TH.** All cheques should be made payable to **J. ILETT.**

We understand that they have only 28 display modules available and are not likely to have any more. However, any type of 40-character 2-line alphanumeric l.c.d. module should function in this circuit as long as it uses the Hitachi HD44780 controller chip. A similar device is listed by Maplin but is about twice the price.

The Analyser printed circuit board is available from the *EPE PCB Service*, code

992, see page 403. You should find that 6-pin d.i.l. sockets are now stocked by advertisers, but, as suggested, it is a relatively easy task to use an 8-pin socket and lop two pins off one end.

Mind Machine Mk III - Tape Controller

We do not expect any purchasing problems to be encountered by readers tackling the *Mind Machine Mk III Tape Controller* and optional add-on Signal Level Indicator board. All components should be "off-the-shelf" parts.

Some readers have asked for the source of the case, called-up in Part One. This is a Verobox type 202-21035F, obtained from Maplin, code LL06G.

The Tape Controller p.c.b. is available from the *EPE PCB Service*, code 989. Once again, all readers must heed the "warning panel" in the article about possible side effects when using the unit with the Sound and Lights module.

Versatile PIR Detector Alarm

As "micropower" operation (about 200µA on standby) is called for in the *Versatile PIR Detector Alarm*, a couple of the components should only be ones as specified.

The LP324N quad micropower op.amp i.c. is currently listed by **Farnell (Tel: 0113 262 6311)**, code LP324N, and **Electromail (Tel: 01536 204555)**, code 648-646. The N-suffix should be quoted as a surface mount version is also available.

The above i.c. is the low-power version of the popular LM324 and typically draws just 100µA of supply current for all four internal amplifiers. The LM324 version can be used instead if low power consumption is not important, i.e. as part of a larger alarm system.

A minor problem surfaced when trying to source the low-noise, infra-red sensor or "pyroelectric IR detector", as they are sometimes listed in catalogues. The type used in the prototype model is marked E100SV1 and was originally listed by Maplin but is no longer available and no alternative source could be found. How-

ever, the E600STO detector has practically an identical specification and is listed by Maplin, code UR69A and Farnell, code 516-170.

The PIR Alarm printed circuit board is available from the *EPE PCB Service*, code 988. Micropower 5V positive regulator type LP2950CZ is now fairly common and most of our component advertisers should carry supplies.

Countdown Timer (Teach-In '96)

We do not expect any buying problems to be encountered when searching for components to build the *Countdown Timer*, this month's *Teach-In* project.

The binary coded "thumbwheel" rotary switches and 2-digit 7-segment i.e.d. displays are reasonably common devices and are stocked by most of our component advertisers. The switches are the type which can be mated side-by-side.

The plastic case, with sloping front panel, is an ABS Console type 2801. The Timer printed circuit board is available from the *EPE PCB Service*, code 993.

Bat Band Converter B.F.O.

As the *B.F.O.* board is even smaller than last month's one used in the *Bat Band Converter*, and also uses surface mount devices (SMDs), extreme care must be taken when soldering up this board. Components which determine the frequency are critical but the rest of the devices can be changed.

Most f.e.t.s will work in this circuit, but watch the pinouts. The 1,000µH fixed inductor came from **Electromail (Tel: 01536 204555)**, code 235-212. The small plastic box, which also houses the converter, is a "mountable" type from Maplin, code FK73Q.

Although SMDs are now well established, some of the traditional component suppliers may not carry a great variety of devices and you may have to shop around. Also, small orders may cost a premium as devices seem to be sold in numbers of 10 upwards.

We understand that **Gothic Crellon (Tel: 01743 788878)** of Wokingham are willing to supply these on a "one-off" basis, cash with order. Call them first for details.

The small surface mount printed circuit board is available from the *EPE PCB Service*, code 984. This includes the small Bat Band Converter board.

VIDEOS ON ELECTRONICS

A range of videos designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They have proved particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.

VT201 to VT206 is a basic electronics course and is designed to be used as a complete series, if required.

VT201 54 minutes. Part One; D.C. Circuits. This video is an absolute must for the beginner. Series circuits, parallel circuits, Ohms law, how to use the digital multimeter and much more. **Order Code VT201**

VT202 62 minutes. Part Two; A.C. Circuits. This is your next step in understanding the basics of electronics. You will learn about how coils, transformers, capacitors, etc are used in common circuits. **Order Code VT202**

VT203 57 minutes. Part Three; Semiconductors. Gives you an exciting look into the world of semiconductors. With basic semiconductor theory. Plus 15 different semiconductor devices explained. **Order Code VT203**

VT204 56 minutes. Part Four; Power Supplies. Guides you step-by-step through different sections of a power supply. **Order Code VT204**

VT205 57 minutes. Part Five; Amplifiers. Shows you how amplifiers work as you have never seen them before. Class A, class B, class C, op.amps. etc. **Order Code VT205**

VT206 54 minutes. Part Six; Oscillators. Oscillators are found in both linear and digital circuits. Gives a good basic background in oscillator circuits. **Order Code VT206**

By the time you have completed VT206 you have completed the basic electronics course and should have a good understanding of the operation of basic circuit elements.

VCR MAINTENANCE

VT102 84 minutes: Introduction to VCR Repair. Warning, not for the beginner. Through the use of block diagrams this video will take you through the various circuits found in the NTSC VHS system. You will follow the signal from the input to the audio/video heads then from the heads back to the output. **Order Code VT102**

VT103 35 minutes: A step-by-step easy to follow procedure for professionally cleaning the tape path and replacing many of the belts in most VHS VCR's. The viewer will also become familiar with the various parts found in the tape path. **Order Code VT103**

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier.
(All videos are to the UK PAL standard on VHS tapes)

Now for the digital series of six videos. This series is designed to provide a good grounding in digital and computer technology.

VT301 54 minutes. Digital One; Gates begins with the basics as you learn about seven of the most common gates which are used in almost every digital circuit, plus Binary notation. **Order Code VT301**

VT302 55 minutes. Digital Two; Flip Flops will further enhance your knowledge of digital basics. You will learn about Octal and Hexadecimal notation groups, flip-flops, counters, etc. **Order Code VT302**

VT303 54 minutes. Digital Three; Registers and Displays is your next step in obtaining a solid understanding of the basic circuits found in today's digital designs. Gets into multiplexers, registers, display devices, etc. **Order Code VT303**

VT304 59 minutes. Digital Four; DAC and ADC shows you how the computer is able to communicate with the real world. You will learn about digital-to-analogue and analogue-to-digital converter circuits. **Order Code VT304**

VT305 56 minutes. Digital Five; Memory Devices introduces you to the technology used in many of today's memory devices. You will learn all about ROM devices and then proceed into PROM, EPROM, EEPROM, SRAM, DRAM, and MBM devices. **Order Code VT305**

VT306 56 minutes. Digital Six; The CPU gives you a thorough understanding in the basics of the central processing unit and the input/output circuits used to make the system work. **Order Code VT306**

By now you should have a good understanding of computer technology and what makes computers work. This series is also invaluable to the computer technician to understand the basics and thus aid troubleshooting.

VT401 61 minutes. A.M. Radio Theory. The most complete video ever produced on a.m. radio. Begins with the basics of a.m. transmission and proceeds to the five major stages of a.m. reception. Learn how the signal is detected, converted and reproduced. Also covers the Motorola C-QUAM a.m. stereo system. **Order Code VT401**

VT402 58 minutes. F.M. Radio Part 1. F.M. basics including the functional blocks of a receiver. Plus r.f. amplifier, mixer oscillator, i.f. amplifier, limiter and f.m. decoder stages of a typical f.m. receiver. **Order Code VT402**

VT403 58 minutes. F.M. Radio Part 2. A continuation of f.m. technology from Part 1. Begins with the detector stage output, proceeds to the 19kHz amplifier, frequency doubler, stereo demultiplexer and audio amplifier stages. Also covers RDS digital data encoding and decoding. **Order Code VT403**

VT501 58 minutes. Fibre Optics. From the fundamentals of fibre optic technology through cable manufacture to connectors, transmitters and receivers. **Order Code VT501**

ORDERING: Add £1.50 p&p per order for UK orders. **OVERSEAS ORDERS:** Add £3 postage for countries in the EEC. Overseas orders outside the EEC countries add £3 per tape airmail postage (or £6 per order surface mail postage).

All payments in £ sterling only (send cheque or money order drawn on a UK bank).

Visa and Mastercard orders accepted - please give card number, card expiry date and cardholder's address if different from the delivery address.

Orders are normally sent within seven days but please allow a maximum of 28 days - longer for overseas orders.

Send your order to: Direct Book Service, 33 Gravel Hill, Merley, Wimborne, Dorset BH21 1RW (Mail Order Only)


Direct Book Service is a division of

Wimborne Publishing Ltd.,

Tel: 01202 881749. Fax: 01202 841692


£29.95
each inc. VAT

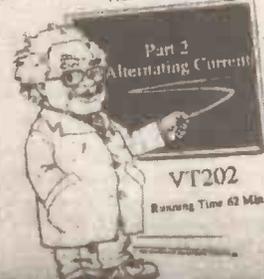UCANDO
VCR EDUCATIONAL PRODUCTS COMPANY
PRESENTS



UCA
VCR EDUCATIONAL
PRODUCTS COMPANY

PHOTOTRANSISTOR

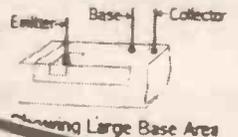

ORDER EIGHT OR MORE TOGETHER - GET ONE FREE (or order 16 together and get TWO FREE)

★★★★ NEW ★★★★★ VT502 LASER TECHNOLOGY

The latest release from UCANDO is a 57 minute video on Laser Technology. The video is divided into five sections each looking at a different type of laser. Following a basic introduction covering some of the common uses of laser devices, the video proceeds to cover the operation of the Ruby Rod laser, HeNe laser, CO₂ gas laser and semiconductor laser devices. It also covers the basics of CD and bar code scanning.


PHOTOTRANSISTOR



PROFESSIONAL CIRCUIT AND PCB DESIGN AIDS FOR WINDOWS

CADPAK for Windows

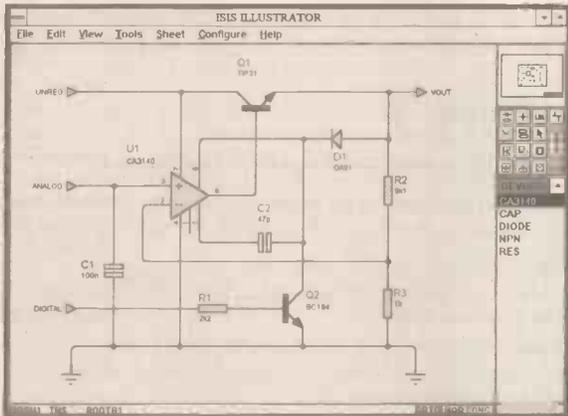CADPAK is especially suited to educational, hobby and small scale schematic and PCB design. CADPAK includes both schematic drawing and 32-bit PCB drafting tools but as an entry level product, there is no netlist link between them.



The schematic drawing module of CADPAK, ISIS ILLUSTRATOR, enables you to create circuit diagrams like the ones in the magazines.


- Runs under Windows 3.1 making full use of Windows features such as on-line help.
- Full control of appearance including line widths, fill styles, fonts, colours.
- Automatic wire routing & dot placement.
- Fully automatic annotator.
- Complete with device and comprehensive package libraries for both through hole and SMT parts.
- Advanced route editing allows deletion or modification of any section of track.
- Gerber, Excellon and DXF outputs as well as output via Windows drivers. Also includes Gerber viewer.
- Exports diagrams to other applications via the clipboard.
- CADPAK is also available for DOS.

CADPAK FOR WINDOWS £ 149

CADPAK FOR DOS £ 79

PROPAK for Windows

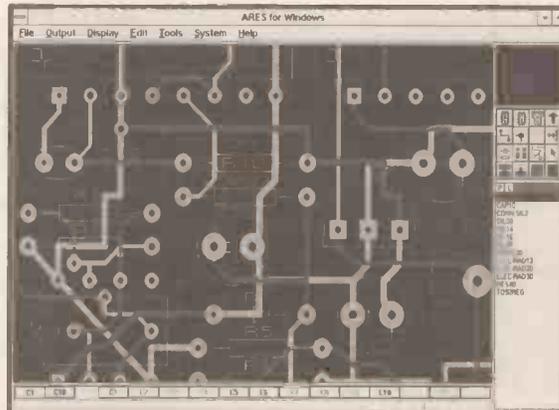PROPAK has all of the features in CADPAK plus netlist based integration, automatic power plane generation and a powerful auto-router. PROPAK includes enough schematic capture and PCB design functionality for all but the most demanding applications.



PROPAK's schematic drawing editor ISIS ILLUSTRATOR+ Includes even more features than ISIS ILLUSTRATOR. PROPAK's 32-bit PCB design tool, ARES for Windows, is our most powerful and easy to use yet.

- Multi-sheet and hierarchical designs.
- Netlist link between modules guarantees consistency between schematic and PCB.
- Netlists are also compatible with SPICE-AGE and most other electronics CAD packages.
- Generates a full bill of materials.
- ASCII data import facility.
- Electrical rules and connectivity checkers.
- Ratsnest display with automatic update during placement and routing.
- Multi-strategy autorouter gives high completion rates.
- Power plane generator creates ground planes with ease.
- PROPAK is also available for DOS.

PROPAK FOR WINDOWS £ 495

PROPAK FOR DOS £ 395

Call or fax us today for a demo pack. Please state whether you would like a DOS or Windows pack.

Prices exclude postage (£5 for UK) and VAT. ISIS ILLUSTRATOR and ARES for Windows are also available separately. All manufacturers trademarks acknowledged.

labcenter

E l e c t r o n i c s

53-55 Main St. Grassington, N. Yorks. BD23 5AA


Tel: 01756 753440 Fax: 01756 752857

TEACH-IN '96

A Guide to Modular Circuit Design

Max Horsey

Part 7

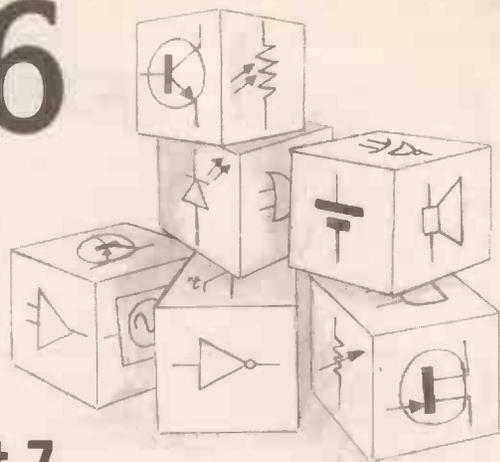

DURING this series of articles, a range of circuit modules is examined, divided into Input, Processor and Output sections. Where possible a choice of module is offered within each section.

Each of the ten Parts of the Series is accompanied by a constructional article explaining how a complete project may be devised by employing the modules described, together with a p.c.b. design. Each project will be one of many possible ideas that could be

implemented and it is hoped that readers will design for themselves a variety of circuits by combining modules provided in the whole series.

The proposed range of modules covered by the Series is detailed in Part 1, Table 1.1. Each module is chosen to link easily with adjacent modules in the same Part, but modules may also be linked with modules in other Parts of the Series.

Max Horsey is Head of Electronics at Radley College.

HERE in this seventh Part of *Teach-In*, the following Input, Processor and Output modules are examined:

INPUT MODULES: Clock pulse generator synchronised to the mains a.c. supply, crystal controlled oscillator

PROCESSOR MODULES: Diode logic gates, divide-by-100 counter, simple 7-segment counter/decoder

OUTPUT MODULE: Decoder/driver for 7-segment displays

The example project based around a selection of these modules is a Countdown Timer which obtains its timing signal from the a.c. mains supply. It provides a continuous digital readout on a bank of four 7-segment light emitting diode (l.e.d.) displays.

Another useful combination which readers could experiment with would be to use the crystal oscillator to provide the timing pulse, feeding the same processing modules as in the example project, but using a liquid crystal display (l.c.d.) instead of the l.e.d. displays to achieve a portable low current timer.

POWER SUPPLY

It is assumed that a power supply of 12V d.c. will be used with the modules, since this is commonly required for relays, sirens, solenoids, etc.

However, the clock pulse generator requires a 50Hz 9V a.c. supply to be derived from the 230V a.c. mains supply via an isolating transformer. This supply can also be converted into 12V d.c. to act as the power supply for the circuits.

Note, if an l.c.d. is used instead of a 7-segment l.e.d. display, then a 9V d.c. supply may be required since some l.c.d.s are not designed for 12V operation.

A.C. CLOCK PULSE GENERATOR

The term "clock pulse" means, in this case, a series of pulses which can be

used to make other circuits respond according to certain fixed timing requirements. As has previously been seen in other Parts of the series, clock pulses can be produced by an astable circuit.

The advantage of using a 50Hz mains derived clock pulse instead of an astable derived one is that, over a 24-hour period, the frequency of the supply can be regarded as constant. This enables multiples or sub-multiples of that frequency to be used for accurate timing purposes. Typically, frequencies of 50Hz, 100Hz, one second and so on can be derived from the mains waveform, depending upon the arrangement used.

This technique can be far more accurate than most free running astables can achieve. The disadvantage is that a mains supply is essential – a battery cannot be used.

Some mains powered equipment, both commercial and published in constructional magazines, uses "direct mains drive". In other words, the mains supply is connected directly (although often via a capacitor) to the electronic circuit without a mains transformer. *This can be*

a very dangerous approach for inexperienced constructors, for whom a mains transformer should be considered essential.

It is possible to buy a mains adaptor (the plug in type) which supplies an a.c. output. This is the safest approach since all the mains parts are housed in a sealed plastic case.

DERIVING 100Hz WAVEFORMS

The circuit diagram in Fig. 7.1 shows how a waveform at a frequency of 100Hz can be derived from the 230V a.c. mains power supply. It also provides a smooth d.c. output suitable for other *Teach-In* modules.

The mains transformer T1 (or adaptor) should be chosen to provide about 9V a.c. if a 12V d.c. supply is required, or 6V a.c. for a 9V d.c. supply, depending upon the requirements of the circuit to be powered.

Note that the full-wave bridge rectifier REC1 and smoothing capacitor C1 will produce a d.c. voltage which is about 1.4 times greater than the original a.c.

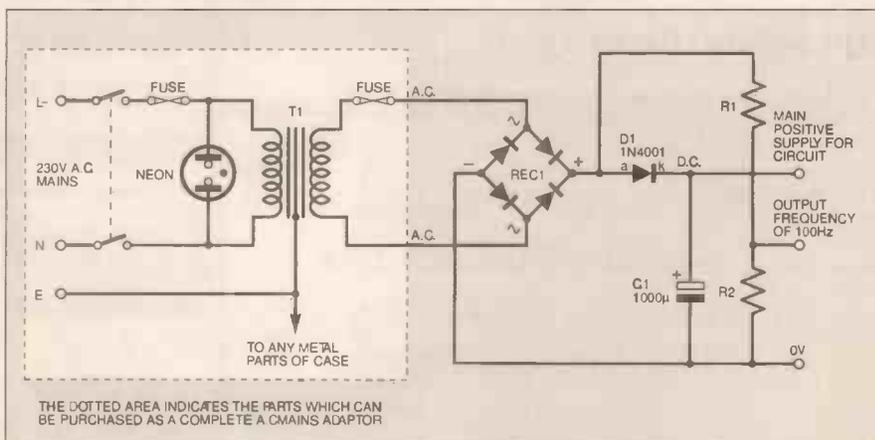


Fig. 7.1. Deriving a 100Hz signal from an a.c. power supply. Typical values for R1 and R2 would be: 10k and 47k respectively.

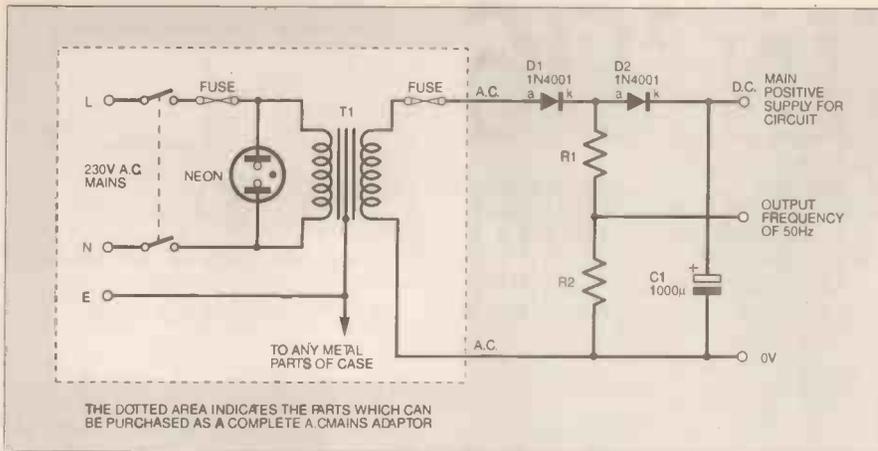


Fig. 7.2. Deriving a 50Hz signal from an a.c. power supply.

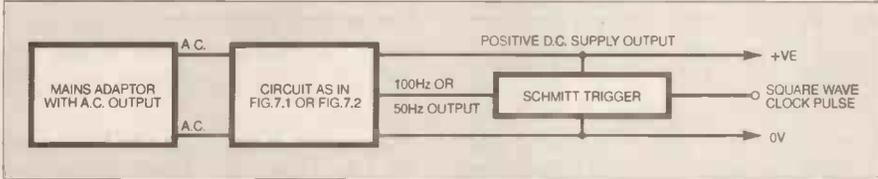


Fig. 7.3. A Schmitt trigger improves the clock waveform shape.

voltage. However, the output current available will be reduced accordingly, i.e.:

$$\text{d.c. output voltage} = \text{a.c. voltage} \times 1.4$$

$$\text{d.c. output current} = \text{a.c. current} \times 0.7$$

It is likely that the peak voltage of the 100Hz signal at the junction of REC1 and diode D1 will be higher than the circuit supply voltage at D1/C1. This is an unsatisfactory situation and is solved by using the potential divider consisting of resistors R1 and R2, for which typical values are: R1 = 10k, R2 = 47k.

It is important for subsequent circuits that the peak voltage at R1/R2 is never allowed to exceed the d.c. voltage at D1/C1.

DERIVING 50Hz WAVEFORMS

The circuit in Fig. 7.2 shows how the same transformer or mains adaptor can be made to produce a 50Hz output. Again it is assumed that the same transformer will supply d.c. power to the circuit. Two diodes, D1 and D2, are connected in series to form a half-wave rectifier. For various reasons beyond discussion here, this type of supply is generally less satisfactory than the circuit in Fig. 7.1, particularly if the circuit requires a substantial current.

Typical values for resistors R1 and R2 are again 10k and 47k respectively.

SQUARING THE OUTPUT

The 100Hz and 50Hz outputs from Fig. 7.1 and Fig. 7.2 are distorted portions of sine waves. As such, they are not always suitable as clock pulses for other parts of a circuit. Some circuits require clock pulses which have a very abrupt change from 0V to positive and back again.

Most counter chips will probably increment their count when a slowly changing clock input voltage crosses a pre-determined threshold level. However, as discussed in other parts of the series, slowly changing voltages can cause erroneous pulses to be generated as the threshold is crossed.

Additionally, there are occasions when a clock signal needs to be capacitively coupled to the next part of the circuit. In such cases, pulses may not be generated

across the coupling capacitor if the input waveform is too slow.

The solution is to use a Schmitt trigger as described in Part 1. The output from the Schmitt trigger will either be at 0V or positive, with no significant intermediate level. (In reality, the change is never truly instantaneous, but is sufficiently fast for it to be disregarded in slower speed circuits.) The block diagram for such an arrangement is shown in Fig. 7.3.

To sum up the circuits of Fig. 7.1 to Fig. 7.3:

ADVANTAGE:

Very accurate long-term timing is possible

DISADVANTAGES:

A mains supply is essential
Battery/portable operation is not possible

CRYSTAL OSCILLATOR

If a very accurate timing signal is required, but a mains a.c. source is not available, then a crystal controlled oscillator offers an excellent solution. Crystals are manufactured to vibrate at a very precise frequency, as determined during manufacture. For example, many digital watches use a crystal oscillator running at a frequency of 32768Hz.

This may seem a rather awkward number, but if divided by two, then by two again,

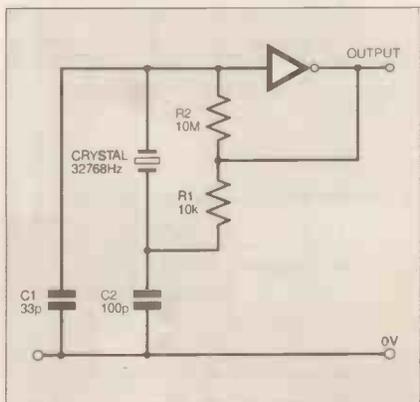


Fig. 7.4. A simple crystal oscillator circuit.

and so on, after a total of 15 divisions the answer will be one. In other words:

$$32768\text{Hz divided by } 2^{15} = 1\text{Hz}$$

So if the output from this crystal oscillator is divided by two, fifteen times, the result is a precise 1Hz signal which can be used to control a timer or clock.

The crystal is normally supplied in a metal can with two leads. It can be connected either way round.

To make the crystal oscillate, an amplifier of some kind is required – ideally a CMOS logic gate, plus one or two resistors and capacitors. A typical circuit using a single CMOS inverter is shown in Fig. 7.4. There are many other circuit configurations which could be used instead.

To divide a frequency by two, a T-type bistable can be used, as shown in Part 5 (Fig. 5.7). By using 15 such bistables, a 1Hz clock pulse can be produced.

If this sounds cumbersome, a study of a components catalogue will reveal a number of i.c.s packed with T-type bistables.

For example, a CMOS 4020B i.c. is available with 14 stages of division. However, for just a few more pence, a CMOS 4060B provides 14 stages *plus* the extra gate required for the crystal oscillator. It can be connected as a complete timing generator which produces a clock signal of 2Hz, as shown in Fig. 7.5.

If a 1Hz clock pulse is required, then the addition of one T-type bistable from Part 5 can be used connecting it to the output of the circuit in Fig. 7.5.

The circuit shown will operate on supplies of up to 12V with the 32768Hz "watch" crystal shown.

OTHER OUTPUTS

The 4060B i.c. has a number of outputs from various points along the chain of T-type bistables. Assuming a crystal with a frequency of 32768Hz, the following frequencies are available:

PIN	Divide by	Frequency (Hz)
3	2^{14}	2
2	2^{13}	4
1	2^{12}	8
15	2^{10}	32
13	2^9	64
14	2^8	128
6	2^7	256
4	2^6	512
5	2^5	1024
7	2^4	2048

Note that an output for 2^{11} (16Hz) is not provided.

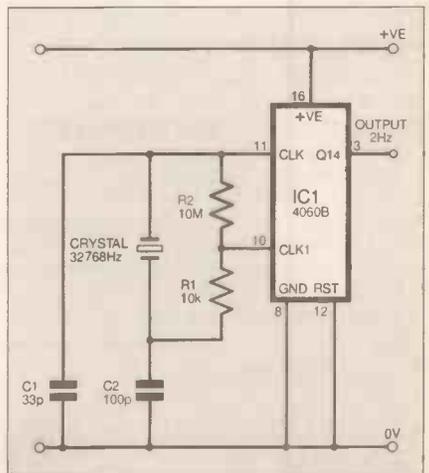


Fig. 7.5. Combined crystal oscillator and counter circuit.

Remember that the frequencies shown in this table assume that the 32768Hz crystal is used. Crystals with other frequencies will produce a different result. The output frequency can be calculated by using the "Divide by" column.

For example, divide by 2^4 means divide by: $(2 \times 2 \times 2 \times 2)$ i.e. divide by 16.

Note the usefulness of the frequency available from pin 15. If a liquid crystal display is used it will require a "back-plane" (BP) frequency of between 30Hz and 100Hz. The 32Hz square wave available from pin 15 is ideal and saves having to construct another astable.

Pin 12 of the 4060B is the Reset input. When connected to 0V as shown in Fig. 7.5 it allows the i.c. to function normally. If pin 12 is made positive, the i.c. is reset and all its outputs go low (to 0V).

DIODE LOGIC GATES

All the logic gates mentioned so far in this series have been based on the CMOS 4000 series of integrated circuits. However, other ranges of i.c.s exist and it is also possible to make gates based on op.amps, transistors or even diodes.

In Fig. 7.6 is shown how an OR gate and an AND gate may be created using a pair of diodes and a resistor. This is often very useful if only one gate is required since it saves purchasing an i.c. which contains four gates.

Of course, such a simple gate has limitations. For a start, there is the voltage drop across each diode which may be undesirable in some cases. The gate also requires a significant current at its inputs and can supply only a very tiny current. In other words, it has a low input impedance and a high output impedance.

Obviously, it cannot be described as a good gate! However, it can be used very effectively if driven from the outputs of normal CMOS logic, and in turn is used to drive the input of another CMOS gate.

With the OR gate, the resistor ensures that the output remains at 0V unless one or other input is positive. If either or both inputs are made positive, the output voltage will rise.

If either or both inputs of the AND gate are connected to 0V then the output will be at 0V. However, if both inputs are made positive the resistor will cause the output to go positive.

If a NOT gate (inverter) is required, a single *npn* transistor may be used, as shown in Fig. 7.7. Any small-signal type will do, such as BC108, BC184L, etc. The output will always be at the opposite logic level to the input. This circuit can be used, therefore, to convert an OR gate into a NOR gate, and an AND gate into a NAND gate.

DIVIDE-BY-100 COUNTER

The processing module shown in Fig. 7.8 is a divide-by-100 counter based

on the CMOS 4518B i.c. The circuit provides one output pulse for every 100 input pulses. The i.c. is a dual BCD (Binary Coded Decimal) counter, which means that the output is in 4-bit binary but resets on each tenth Input pulse (instead of 16 pulses).

Note that the i.c. contains two completely separate counters, A and B, which share a common power supply, pin 8 = 0V, pin 16 = +VE.

Remembering that low = logic 0 (0V) and that high = logic 1 (positive supply voltage) the pins are as follows :

Counter A	Counter B	Function
Pin 1	Pin 9	Clock input
Pin 2	Pin 10	Enable input
Pin 3	Pin 11	Output Q1 (least significant)
Pin 4	Pin 12	Output Q2
Pin 5	Pin 13	Output Q3
Pin 6	Pin 14	Output Q4 (most significant)
Pin 7	Pin 15	Reset

Note that either the Clock input or the Enable input may be used to "clock" the counter, depending upon whether you wish to count at each rising edge of the clock signal, or each falling edge.

Taking the "clock" signal to the Clock input, the count occurs on the rising edges when the Enable input is held high. If the Enable input is taken low, the count stops.

Taking the "clock" signal to the Enable input, the count occurs on the falling edges when the Count input is held low. If the Count input is taken high, the count stops.

In the circuit of Fig. 7.8, the signal to be counted is brought into the Clock input, pin 1, of Counter A. To allow the count to proceed, the Enable input, pin 2, is held high.

The Q1 output from pin 3 will be at half the frequency of the clock signal. The Q2 output from pin 4 will be half that of pin 3, and the Q3 output from pin 5 half again. Since the device is a BCD counter, the Q4 output from pin 6 will change from high to low after the first eight clock pulses, but then switch back to 0V at the tenth pulse. In other words, Counter A will divide the input by 10.

Since the Q4 output from pin 6 switches from high to low at each tenth clock pulse, it is fed to the Enable input of Counter B, pin 10, which counts at each falling edge. Clock input pin 9 is therefore held at 0V to enable the count to proceed.

The division continues through Counter B, ending with another "divide by 10" output at pin 14 (Q4). Therefore the total division between the first clock input, pin 1, and the final output at pin 14 is 100.

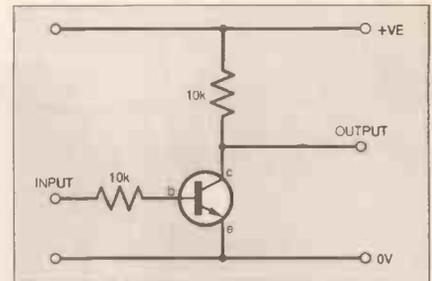


Fig. 7.7. A simple transistor inverter.

The circuit may be used to provide one-second pulses if a 100Hz pulse rate is fed into pin 1. The output pins could be used in other permutations if a another "divide by" number is required.

In the circuit as shown, Reset pins 7 and 15 are connected to 0V so that they have no effect. If a reset facility is required then, as in previous modules in the series (e.g. Part 6, Fig. 6.7), use a "tie-down" resistor connected between the Reset pins (both joined together) and the 0V line. The pins can then be connected to the reset signal source, either a switch or another circuit. (This principle is illustrated again Fig. 7.10.)

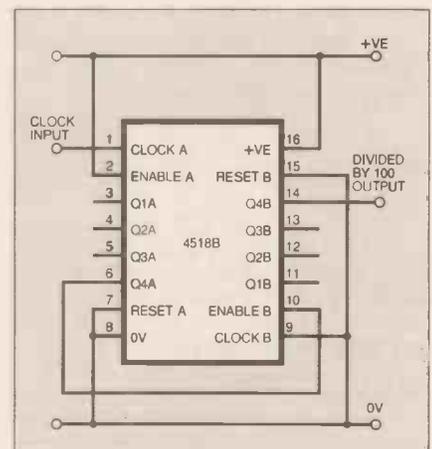


Fig. 7.8. A divide-by-100 circuit.

DISPLAYING COUNTS

If a 7-segment i.e.d. display of BCD counter values is required, the circuit in Fig. 7.9 can be used with each decade counting stage.

A variety of 7-segment (light emitting diodes) displays exists, consisting of seven i.e.d.s arranged in the well known figure-of-eight configuration. As with the i.c.d. modules described in Part 6, the i.e.d. segments are known as a, b, c, d, e, f, g.

Seven-segment i.e.d. displays are available as common anode and common cathode types. The type used here is a common cathode display, in other words, the cathodes of each segment are joined to a common pin connected to 0V.

The pin arrangement on i.e.d. displays can vary between types, and the catalogue from which they are obtained should be consulted to establish the pin identities. Pins not shown should be left unconnected.

Making the correct i.e.d.s light to show the required number is a little complicated, but i.c.s exist which perform this function, such as the CMOS 4511B BCD to 7-segment decoder/driver in Fig. 7.9.

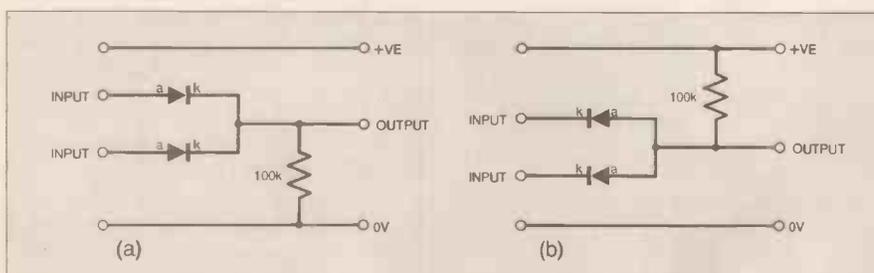


Fig. 7.6. (a) A diode OR gate. (b) A diode AND gate.

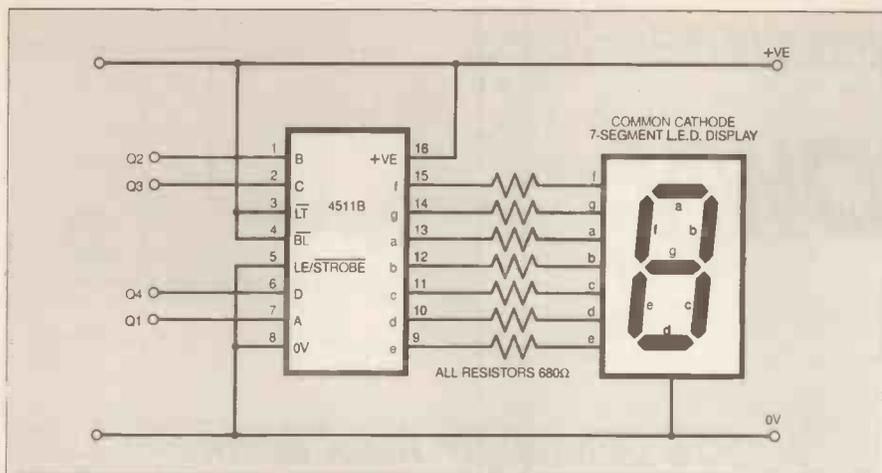


Fig. 7.9. The 4511B i.c. converts a BCD input code into a format suitable for driving a seven-segment l.e.d. display.

The binary input pins are labelled A, B, C, D and they are normally connected in order to the Q1, Q2, Q3, Q4 output pins of the driving BCD counter.

Output pins a to g feed the 7-segment l.e.d. display pins of the same letter. Note that resistors between the outputs and the display are necessary to limit the current flow.

All normal l.e.d.s require a series resistor (as discussed in Part 4, Fig. 4.15), and the values shown will provide a bright display on a 12V supply. With a 5V supply the values could be reduced to, say, 330Ω.

TRICK LIGHTING

The circuit in Fig. 7.9 indicates the most straightforward way of using the 4511B. However, it can perform some extra tricks:

When Lamp Test (LT) input pin 3 is connected to 0V, the seven outputs become positive, making all the l.e.d. segments light up for testing purposes. For normal operation, pin 3 must be connected to the positive supply.

When Blanking (BL) input pin 4 is connected to 0V, all outputs remain low, making the l.e.d. segments switch off. This would be useful in a battery powered device if you wanted the circuit to continue working, but only wished to see the display occasionally in order to prolong the battery life. For normal operation, this pin must be connected to the positive supply.

It is also possible to suppress leading zeros (e.g. 0264 would read 264) by

using pin 4. For example, in the accompanying example Countdown Timer project, if pin 4 of IC11 is disconnected from the positive supply (by cutting away the track joining pin 3 to pin 4), and pin 4 joined instead to pin 7 of IC10, the tens of minutes display would switch off whenever a zero was present.

If Latch Enable (LE/Strobe) input pin 5 is made positive, the outputs latch at whatever state they are in. In other words, the number displayed "freezes", and remains so until pin 5 is returned to 0V, its normal operating condition.

COUNTER WITH DISPLAY

If a simple counter and 7-segment l.e.d. display is required, there are several i.c.s which will count and produce an output for driving a single 7-segment display in one operation. The type described here is the CMOS 4026B which can count upwards (as do most counter chips). A type 4033B is also available with slight differences, and there is also the 40110B device which can count up or down.

Details of the 4026B connections are shown in Fig. 7.10. The 7-segment display used with this i.c. must be a common cathode type.

The pins should be connected as illustrated if a straightforward counter is required. As in Fig. 7.9, pins labelled a to g are connected to the appropriate l.e.d. segments via resistors.

If a pushbutton switch is connected

between the Clock input and positive, the counter will increment by one each time the switch is pressed. Of course, the problem of switch contact bounce may arise, causing the counter to accidentally increment by several counts. Switch contact bounce - and its solution - was discussed in Part 6.

If a switch is connected across the points labelled P, the counter will reset to zero whenever the switch is pressed.

When power is first applied, the counter may display a number other than zero. If a capacitor, say 100nF (0.1μF), is connected between points P, a positive pulse will occur at the Reset pin whenever power is connected, causing an automatic reset.

Both the capacitor and a manual reset switch may be connected if required. Be sure to connect them in parallel. In other words, both the capacitor and the reset switch should be connected directly to points P.

LINKING COUNTERS

As shown, the counter counts to nine and then resets to zero on the tenth pulse. Each time it resets, it provides a positive-going output level change at pin 5, the Carry Out pin. This pin may be linked directly to the Clock input on another 4026B to allow counting to 99.

The Reset pin 15 on the tens counter may be linked directly to pin 15 on the units counter. Further i.c.s may be cascaded in the same way to enable counting to any desired number.

Pin 2 is a Clock Inhibit pin. When it is at 0V, the counter works normally. When pin 2 is positive, the i.c. cannot count.

Pin 3 is the Display Enable pin. When it is positive, the display works normally. If pin 3 is switched to 0V, the display is blanked (turned off), even though the count can continue normally.

For information about pins 4 and 14, manufacturer's data for the 4026B should be consulted. (Ask your component supplier how to get data sheets - for this or any other i.c.) These pins should be left unconnected in this circuit.

To sum up the counter/display circuit in Fig. 7.10:

ADVANTAGE:

A simple inexpensive way of counting

DISADVANTAGE:

A rather inflexible circuit. For example, a timer requires a Carry/Reset operation at the end of each 59 seconds. This would be hard to achieve with the module shown.

If total flexibility is required, then at the expense of a little more circuitry, the counter module based on the 4029B i.c. should be used. This was examined in Part 6, and is used in the project associated with Part 7. The 4029B is also a perfect match for the output module shown in Fig. 7.9.

EXAMPLE PROJECT

The Countdown Timer is the example project (elsewhere in these pages) which shows how the modules in *Teach-In* Part 7 can be combined in a practical application.

PART EIGHT

The modules to be examined in *Teach-In* Part 8 are an Audio Input, Signal Mixer, Position to Voltage Sensor, VU Processor i.c., Direct Driver. The example project is a VU Warning with Alarm.


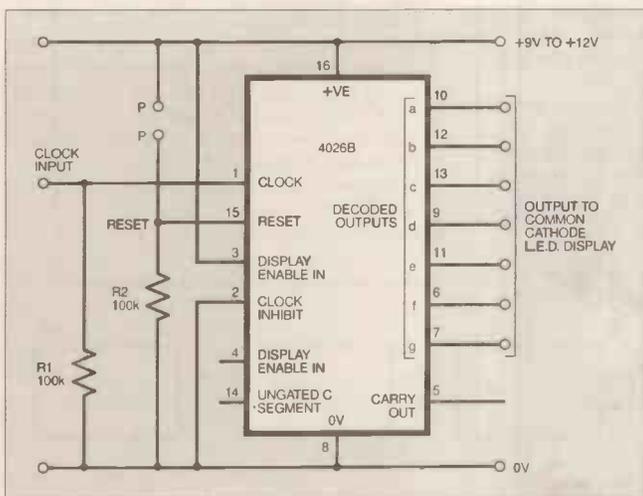


Fig. 7.10. The 4026B i.c. is a combined counter and 7-segment l.e.d. display driver. Points P are for a reset function.

CORRECTION

In *Teach-In* Part 4 (Feb. '96), *Vari-Speed Dice* page 138, Fig. 3, the polarity of capacitor C5 should be reversed.

COUNTDOWN TIMER

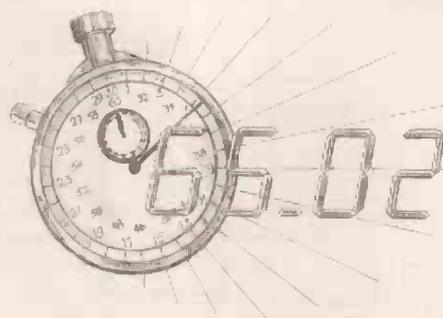

MAX HORSEY PCB DESIGN BY **ALEX SIMM**

It's time to keep it under the counter, but still above board!

BASED on the information provided in *Teach-In* Part 7, this article shows how modules may be selected and combined to produce a working project.

The Countdown Timer described here includes an easy to set rotary switch control, plus an optional relay output to enable automatic control of remote equipment.

SPECIFICATION

- Four-digit 7-segment l.e.d. readout
- Maximum time 99 minutes 59 seconds
- Accurate to within 0.5 seconds
- Relay switches on during timing
- Buzzer sounds for two seconds at end of timed period
- Time set up on four rotary switches
- Pushswitches for Start and Reset
- Mains operated (via a 6V to 10V a.c. output adaptor)

ACCURACY

In theory, an astable could provide the clock pulse which keeps the timer counting at the correct rate. Clearly, though, an accurate signal is necessary and the general purpose astables outlined in *Teach-In* Part 6 would not be constant enough.

Instead, an accurate clock pulse generator was selected from *Teach-In* Part 7, Fig. 7.1. This uses the frequency of the UK a.c. mains supply which, over a 24 hour period, is rigorously controlled for an average of 50Hz. When this is full-wave rectified, a ripple-waveform with a frequency of 100Hz is obtained.

The 100Hz frequency is then shaped, divided, fed to a count-down counter which can be preset, and the results output to a decoder and display module.

MAKING CHOICES

A bewildering array of i.c.s is available which could complete the counting and display process, but it helps at this stage to select the type of display required and work backwards. A liquid crystal display (l.c.d.) consumes very little power, making it suitable for battery driven devices. However, as the project is mains driven, simpler, less expensive 7-segment l.e.d. displays were chosen.

This in turns means that the CMOS 4511B is a good choice for the decoding

and driving i.c., and the CMOS 4029B makes an ideal counting companion, particularly since it can be programmed to start at any number. The 4511B decoder/driver was described in Part 7, and the 4029B counter was described Part 6.

This project also shows how the "parallel load" or "JAM" inputs on the 4029B are used to make the counter jump to a number other than zero or nine.

BLOCK DIAGRAM

The block diagram in Fig. 1 includes the following modules, full details of which may be found in the appropriate *Teach-In* Part stated:

- | | |
|---|--------|
| Mains generated clock pulse | Part 7 |
| Schmitt trigger | Part 1 |
| Counter/divider | Part 7 |
| Bistable (latch) | Part 3 |
| Monostable (buzzer timer) | Part 2 |
| Transistor output driver (for buzzer and relay) | Part 1 |
| CMOS 4029B counter | Part 6 |
| CMOS 4511B decoder/driver | Part 7 |
| 7-segment l.e.d. display | Part 7 |

The block diagram is expanded into two circuit diagrams, the first of which is shown in Fig. 2.

A.C. CONVERSION

It is essential to power the Countdown Timer from a 6V to 10V 50Hz a.c. supply. A normal d.c. supply cannot supply the required clock pulses to allow timing.

Referring to Fig. 2, the a.c. supply is converted into a 100Hz signal by the full-wave rectifier REC1. From here the supply

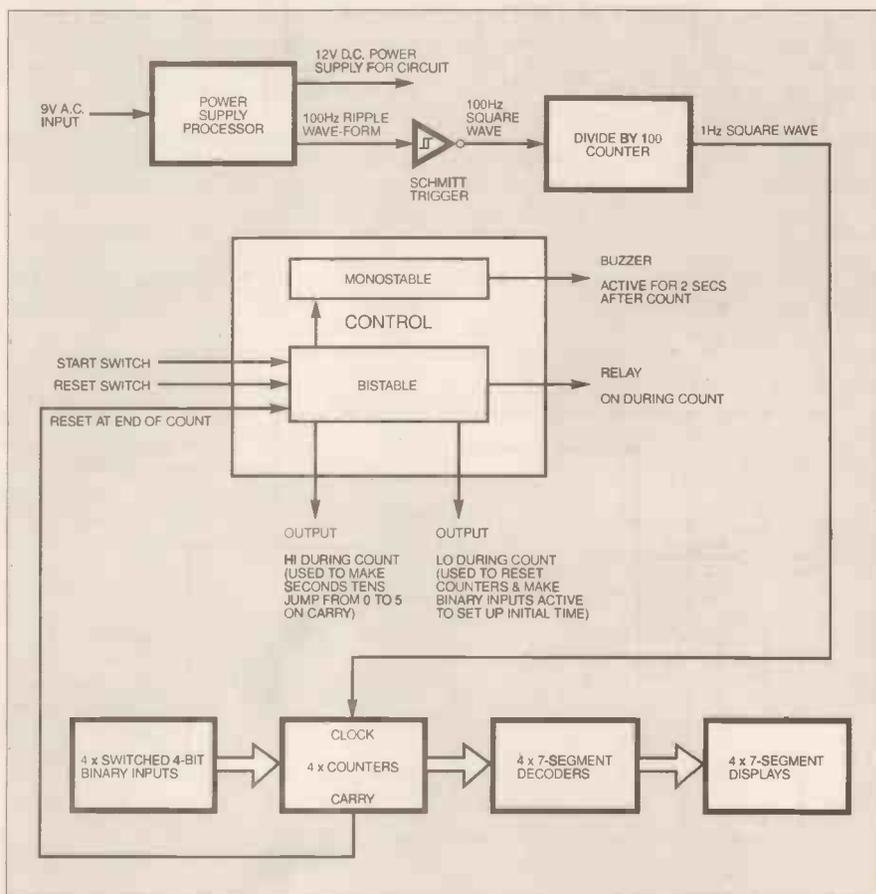


Fig. 1. Block diagram for the Countdown Timer. The relay is optional.

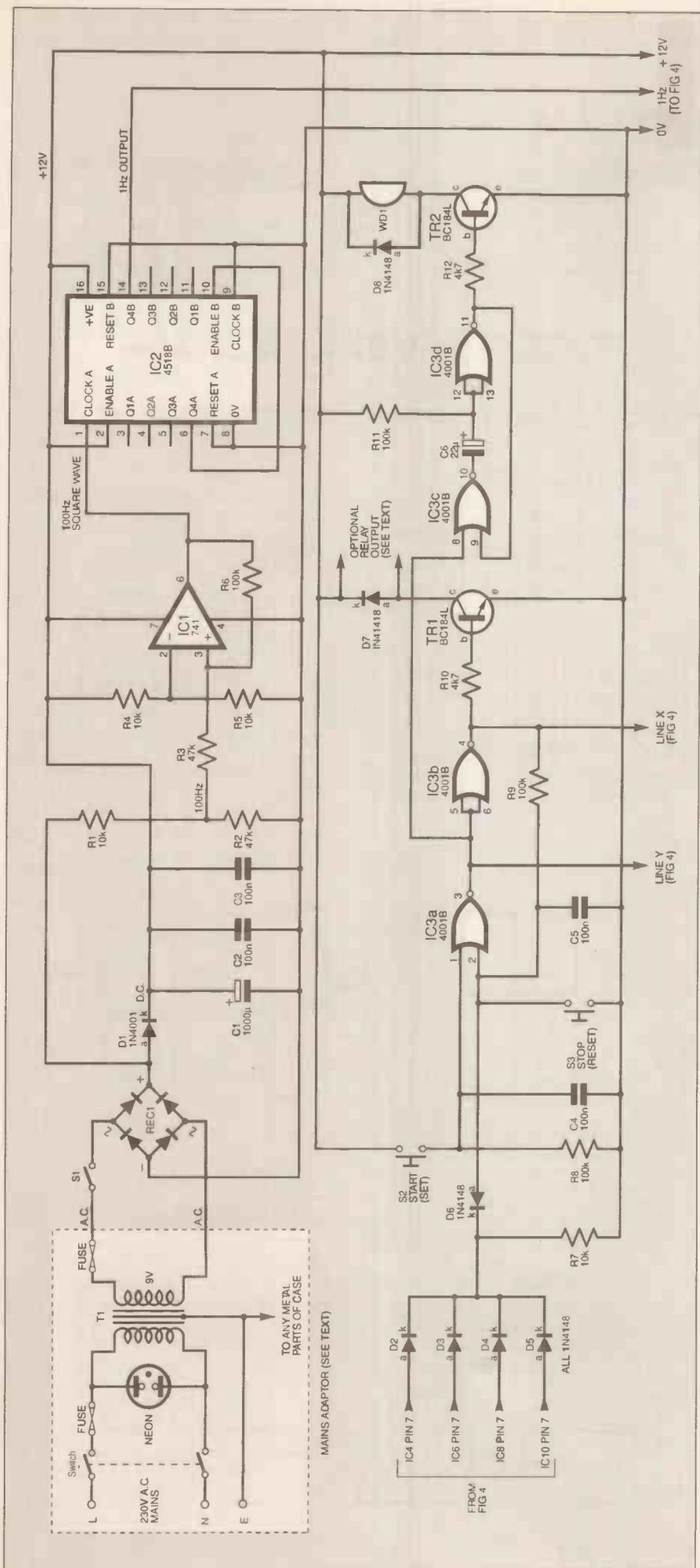


Fig. 2. Details of the power supply, clock pulse generator and basic control circuits.

divides, part of it being routed through resistor R1 to the processing circuit which shapes the 100Hz timing pulses.

Most of the supply, though, is routed via diode D1 to provide power for the circuit. The 100Hz ripple would cause havoc if present on the d.c. supply, consequently capacitor C1 is used to provide overall smoothing, then C2 and C3 remove spikes. The inclusion of diode D1 ensures that these capacitors do not smooth out the required ripple!

Capacitor C3 may appear redundant when shown next to C2. However, in the p.c.b. (printed circuit board) layout, these capacitors are at opposite ends of the board to ensure removal of the high frequency noise which the circuit may generate and impose on the power supply tracks.

When all the segments of the displays are lit (i.e. when displaying 8888) something like 120mA is required by each display, making a total of 480mA. Depending on the actual total current drawn, the value of 1000µF suggested for the smoothing capacitor C1 may be a little low in some instances. This could result in low level ripple on the d.c. supply rails.

In this application, the i.c.s are quite tolerant of a slight ripple voltage and there should be no ill effect apart from the buzzer sounding a little strangled! A larger capacitor may be used if preferred, depending upon the space available in the finished project.

Alternatively, *high efficiency* 7-segment displays could be used (at a price) in which case all the 680Ω resistors which supply each segment of each display could be increased to about 1.2 kilohms (1k2), thus halving the current consumed.

TIMING SIGNAL

The 100Hz timing signal output from the rectifier, REC1, is reduced in voltage by the potential divider formed by resistors R1 and R2. The timing signal is a series of half sine waves and these must be converted into square waves before being applied to the clock input of the first counter stage (IC2).

A Schmitt trigger based on op.amp IC1 achieves this conversion. (Schmitt triggers were discussed in Part 1, pages 869 and 870).

From IC1's output pin 6, the resulting square wave is sent to the clock input pin 1 of IC2, a CMOS 4518B counter/divider. As discussed in Part 7, Fig. 7.8, when connected as shown, the i.c. divides by 100, thus converting the 100Hz square wave into a 1Hz clock pulse.

As detailed in Fig. 4, this is applied to the clock input pin 15 of IC4, which is a 4029B presettable BCD (Binary Coded Decimal) up/down counter. Its pinouts are shown in Fig. 3.

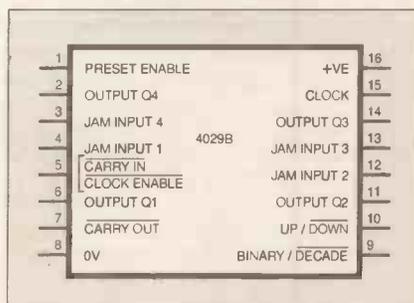


Fig. 3. Pinouts of the 4029B counter i.c.

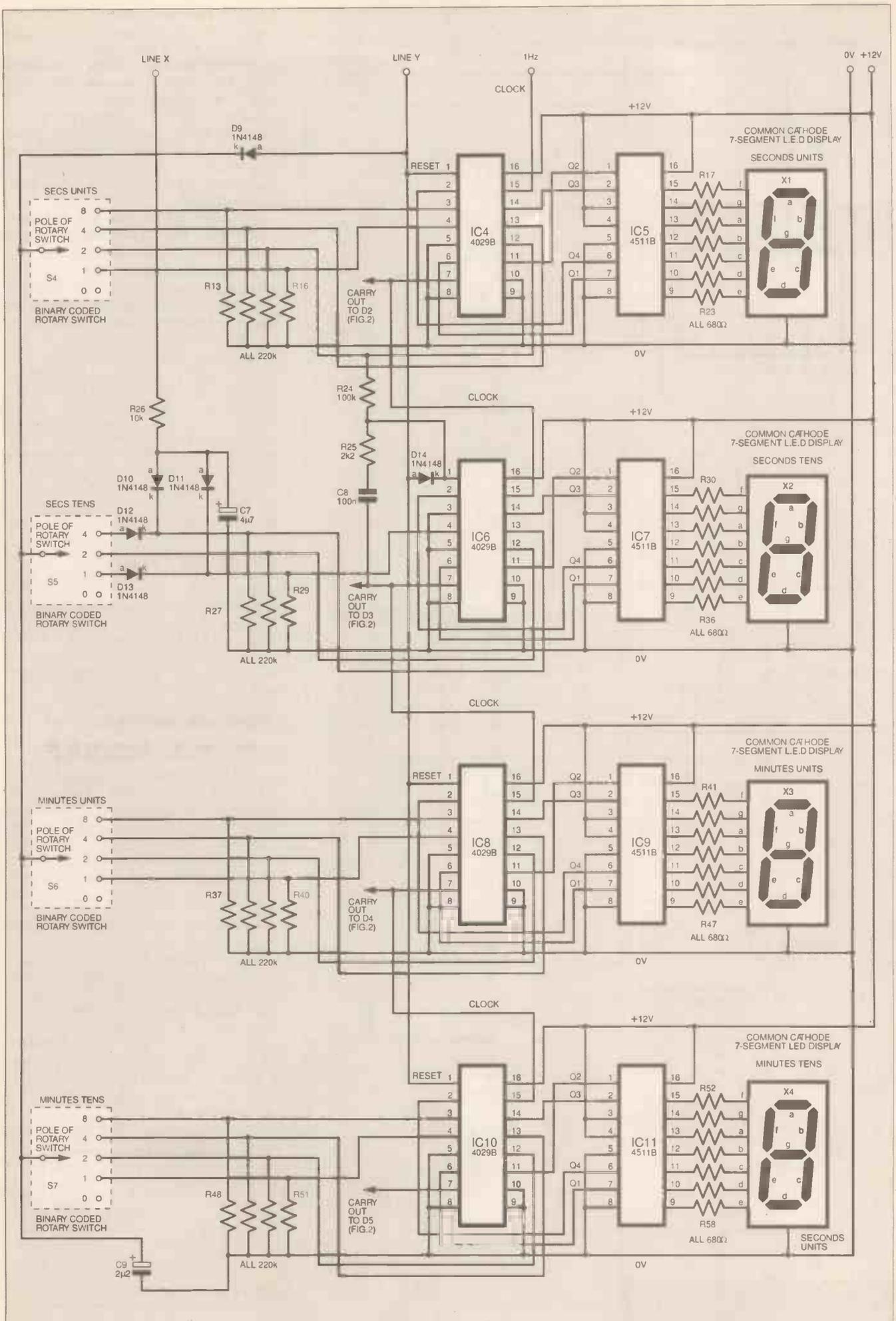


Fig. 4. Circuit diagram for the four counter display stages.

The 4029B counter i.c. can be programmed to count down by connecting pin 10 to 0V (see Part 6). Therefore the "units of seconds" stage must supply a "carry out" pulse when it changes from zero to nine. This pulse is applied to the clock input of IC6.

All four counters are similarly connected in series, the carry out signal from each providing the clock signal for the next.

COMPONENTS

Resistors

R1, R4, R5,	
R7, R26	10k (5 off)
R2, R3	47k (2 off)
R6, R8, R9,	
R11, R24	100k (5 off)
R10, R12	4k7 (2 off)
R13 to R16,	
R27 to R29,	
R37 to R40,	
R48 to R51	220k (15 off)
R17 to R23,	
R30 to R36,	
R41 to R47,	
R52 to R58	680Ω (28 off)
R25	2k2

All 0.25W 5% carbon film

Capacitors

C1	1000μ elect. radial, 16V
C2 to C5,	
C8	100n ceramic disc (5 off)
C6	22μ elect. radial, 16V
C7	4μ7 elect. radial, 16V
C9	2μ2 elect. axial, 16V

All voltage ratings are minimum values

Semiconductors

D1	1N4001 rectifier diode
D2 to D14	1N4148 signal diode (13 off)
REC1	W005 bridge rectifier, or similar
TR1, TR2	BC184L npn transistor (2 off)
IC1	741 op. amp
IC2	4518B dual BCD counter
IC3	4001B quad 2-inputs NOR gate
IC4, IC6,	
IC8, IC10	4029B 4-bit presettable up/down counter (4 off)
IC5, IC7,	
IC9, IC11	4511B BCD to 7-segment decoder/driver (4 off)

Miscellaneous

S1	s.p. min. toggle switch
S2, S3	push-to-make switch (2 off)
S4 to S7	BCD rotary switch (see text) (4 off)
WD1	12V buzzer
X1 to X4	2-digit 7-segment l.e.d. display (2 off)

Printed circuit board, available from the EPE PCB Service, code 993; end cap for rotary switches (2 off); a.c. mains power adaptor with 9V a.c. output (see text) plus cable-mounting power input socket to suit; 12V relay (optional - see text); plastic case with sloped panel, 194mm x 120mm x 60mm (max. height); Speedbloc connectors (2 off) (optional - see text) red filter for display; 8-pin d.i.l. socket; 14-pin d.i.l. socket; 16-pin d.i.l. socket (9 off); 24-pin d.i.l. socket (4 off) (see text); cable ties; 18-way ribbon cable; connecting wire; solder, etc.

Approx Cost
Guidance Only **£39**
excl. case and power supply

The carry out signals are also needed for two other functions:

1. To cause the timer to stop, reset and sound a signal from the buzzer when all the counters have reached zero

2. To ensure that IC6 (the tens of seconds counter) jumps from zero to five instead of zero to nine.

DIODE AND GATE

For the sake of simplicity, the block diagram of Fig. 1 shows the final carry output connected to the Reset input of the control module. This would stop the counter as the tens of minutes count switches from zero to nine. However, it would also cause the timer to count an extra second before switching off the optional relay. Ideally, a signal is needed at the moment when the count reaches 0000 rather than a second after.

Returning to Fig. 2, this is achieved by means of a diode AND gate which creates a signal when all four counters have reached zero. To avoid using yet another i.c., an arrangement of diodes (D2 to D6) is used to simulate a logic gate.

If any of the counters is not at zero, its carry out pin will be high (logic 1) therefore holding the top end of R7 (as seen in Fig. 2) at logic 1. If all the counters are at zero the top end of R7 will fall to logic 0. This is used to cause Stop and Reset conditions as described later.

PARALLEL LOADING

The CMOS 4029B may be "parallel loaded" with a 4-bit binary number at its JAM inputs to cause the outputs to jump to any required number when Reset pin 1 is made high. When counting in decimal mode, these i.c.s happily count down 2, 1, 0, 9, 8 etc. However, in Fig. 4, counter IC6 must instead count down 2, 1, 0, 5, 4 etc.

For example, the counter might have to count down from 32m 01s to 32m 00s to 31m 59s. This is achieved by holding its pins 4 and 13 positive whilst applying a reset pulse to pin 1.

Problems arise because the parallel load inputs may already be set to a number other than five by the rotary switches. Therefore the rotary switches (fed from line Y) have to be disabled during counting, whilst pins

4 and 13 of IC6 are held high during the count via resistor R26 and diodes D10 and D11 (fed from line X).

The timer control module causes line X to be high during the countdown, and line Y to be high before or after the countdown. Capacitor C7 stops the voltage from R26 rising too quickly - to prevent the tens of seconds jumping to a value of five at the start of the countdown.

Capacitor C9 ensures that the number registered by the rotary switches is maintained at the parallel load (JAM) inputs, until the logic level at the reset pins falls to zero.

To summarise:

Before/after countdown:

X = low, Y = high, parallel load inputs cause counters to copy numbers set by switches

During countdown:

X = high, Y = low, tens of seconds counter (IC6) set to jump to five when a pulse is received at pin 1.

The carry out signal from IC6 is reduced to a brief pulse by means of C8, R25 and R24. This method of obtaining pulses by means of a series capacitor was described in Part 2 (see A.C. Coupling). Diode D14 prevents the other three counters from being reset by this pulse.

TIME SETTING


Four binary output rotary switches are used for setting up the time required.

Whenever the timer is not counting, line Y is high and supplying power to the switches via diode D9, making the Reset Enable input (pin 1) of each counter positive. The parallel load system is hence enabled, and the outputs from the counters copy the numbers set up by the switches.

CONTROL MODULE

The control module is built around the four NOR gates housed in IC3. The countdown sequence starts when switch S2 is pressed. NOR gates IC3a and IC3b form a bistable (or latch), which causes output pin 4 (line X) to be high during countdown. Output pin 3 (line Y) is high before and after countdown.

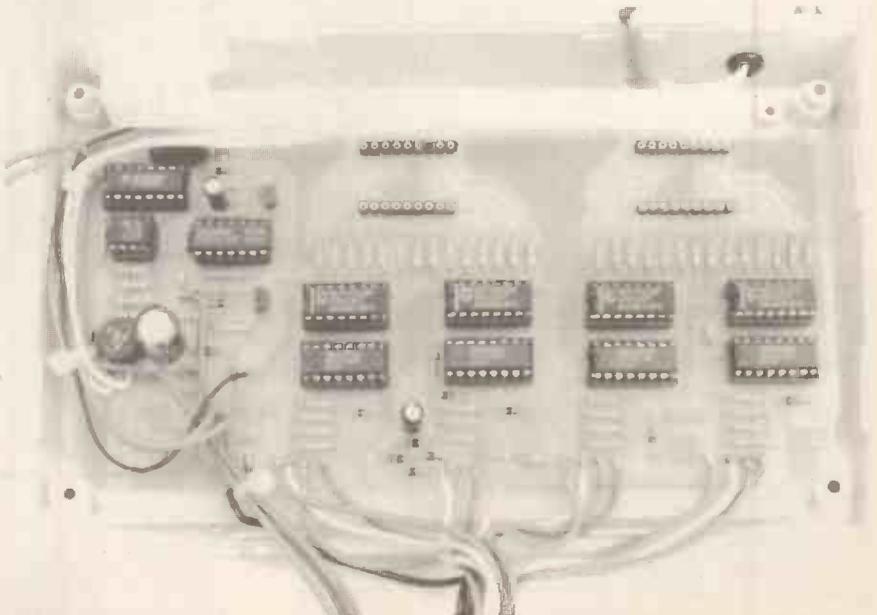Via resistor R10, pin 4 also drives npn transistor TR1, which can be used



to switch on an optional relay during countdown. The bistable is unlatched by pulling down the voltage at pin 2. This is achieved either by pressing the Stop/Reset switch S3, or automatically at the count of 0000 via diode D6, as described earlier.

A monostable formed by IC3c and IC3d is used to make the buzzer WD1 sound, via transistor TR1, for about two seconds whenever output Y switches from low to high. This signals the end of the count. The buzzer-on time may be increased, if preferred, by increasing the value of R11 up to a maximum of 1MΩ, which gives about 20 seconds.

DECODER AND DISPLAY

The l.e.d. decoder/driver i.c.s are CMOS 4511B devices, which were described in Part 7 (Fig. 7.9). For the prototype, four 7-segment displays were purchased as two double displays.

POWER SUPPLY

For the sake of safety, it is assumed that a commercial power adaptor will be used with this counter. However, adaptors which supply an a.c. output are not common. Note that an a.c. (so called) power adaptor plugs into the a.c. mains but normally supplies d.c.

It is also possible to construct a suitable power supply, and a small transformer could be purchased and housed either with the timer, or in a separate box. A suitable transformer would be a 6VA type with 230V a.c. inputs and 9V a.c. outputs. This will supply just enough current if its two 9V secondary coils are connected in parallel.

The 680Ω resistors supplying the displays could be raised to say 820Ω or even 1k2Ω if high efficiency displays are used, in order to reduce the current consumption, or a 6V 6VA transformer could be used.

If a mains adaptor is constructed in this way, observe the need for safety, such as using a double-pole mains on/off switch, plus a neon and fuse as shown in the dotted section of Fig. 2.

Note that if a 12V a.c. adaptor is used, the d.c. supply from diode D1 could rise to over 16V, possibly causing damage to the i.c.s and smoothing capacitor C1. A simple if crude method of dropping the d.c. supply is to add, say, four 1N4001 diodes in series with D1. This should knock out about 2.8V.

These extra diodes should be connected between the positive output of rectifier REC1 and diode D1. Ensure that resistor R1 remains connected directly to the anode (a) side of D1.

CONSTRUCTION

Full details of the printed circuit board are shown in Figs. 5 and 6. This board is available from the *EPE PCB Service*, code 993.

Since the timer will be in use around the home, its general appearance is particularly important. When designing the prototype p.c.b., therefore, the case was selected first and the p.c.b. made to fit. It would be wise to check that the p.c.b. *does* fit into the case before inserting any components. If any trimming is necessary, this is much simpler when performed on an unassembled p.c.b.

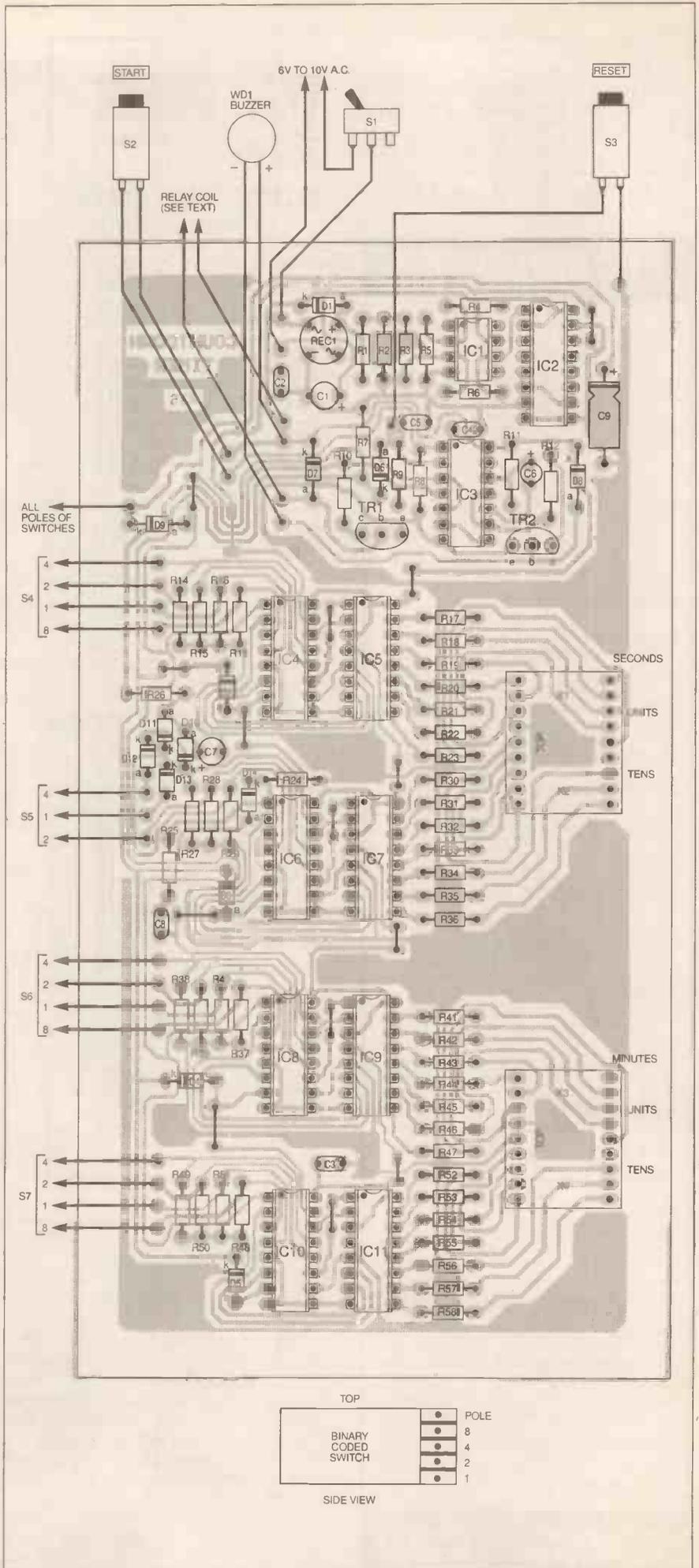


Fig. 5. Component layout on the printed circuit board.

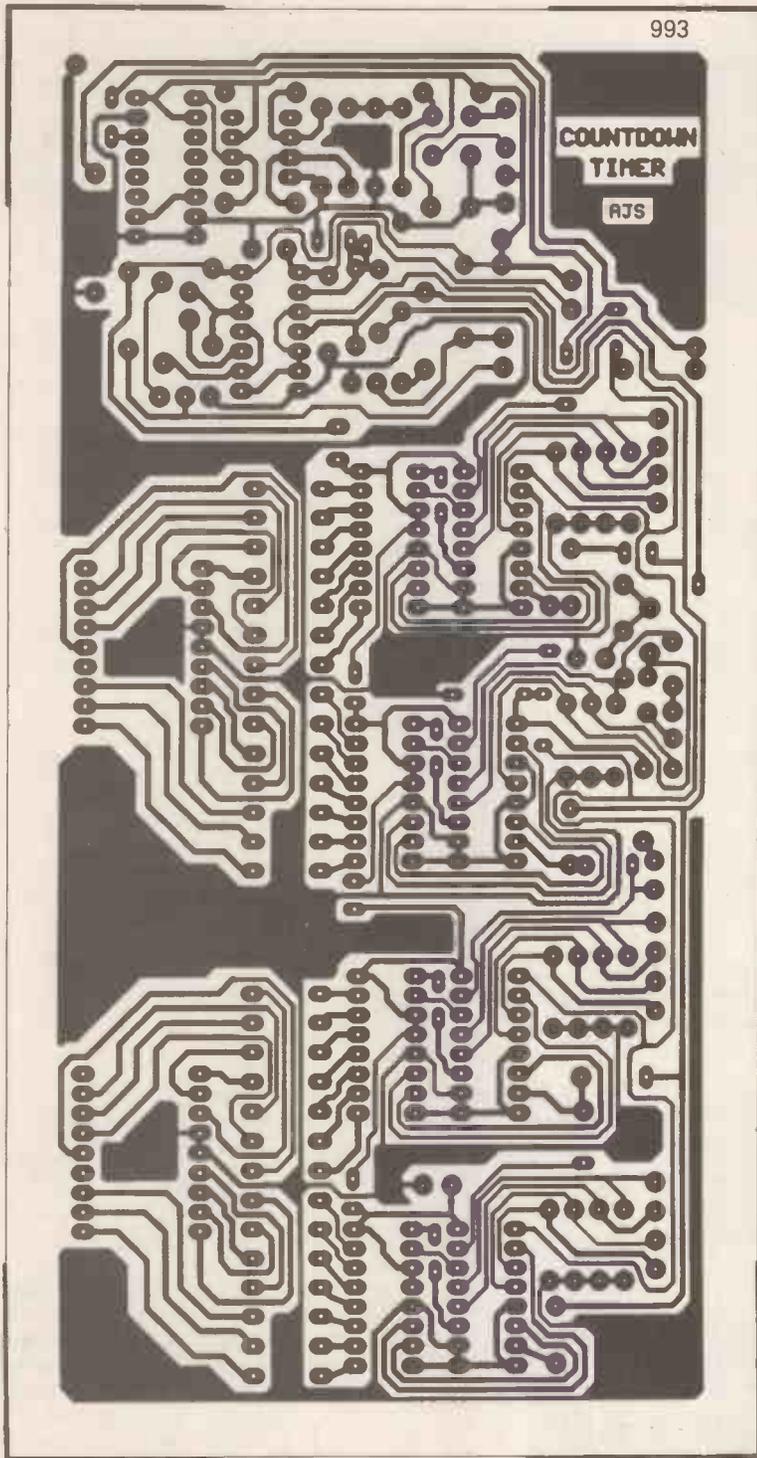


Fig. 6. Full-size underside copper foil track master pattern.

Start p.c.b. assembly by inserting the d.i.l. (dual-in-line) sockets, followed by the on-board wire links (the short bare wires used to link certain p.c.b. pads) and smallest components. As usual, check the polarity of diodes and electrolytic capacitors to ensure that they are fitted the correct way round. The bridge rectifier is labelled to ensure a correct fit.

LINKING THE DISPLAYS

The two pairs of 7-segment displays will eventually be mounted on the front panel of the case. However, provision has

been made on the p.c.b. to allow d.i.l. sockets to be mounted, into which the displays may be plugged for testing.

When installed in a case, the displays can then be linked via a set of colour-coded individual wires, or by ribbon cable. For example, Speedbloc plugs are available which may be clamped onto Speedbloc ribbon cable so avoiding the need for soldering all the connections. Note that a 24-pin Speedbloc plug is likely to be the nearest to the required 18 pins.

These plugs can be inserted into the display sockets, providing a neat finish. Note, though, that Speedbloc connectors for use at the display end of the cable do

not seem to be available. Consequently, the individual ribbon wires must be soldered to a standard d.i.l. socket at the display end.

This is not an easy operation, though a small piece of stripboard could be used to help with the soldering operation. A 20-way ribbon cable may be used, but care must be taken to use the appropriate connections at each end of the cable (Speedbloc ribbon cable is all-grey, i.e. not colour coded).

If all this sounds too cumbersome and costly, wires may be soldered to the p.c.b. instead of fitting sockets. In this instance, note the importance of using a variety of colours to distinguish between the different wires.

SWITCHES

Insert terminal pins for the other external connecting wires. Link the rotary time setting switches as shown, checking that the units of seconds switch is on the right hand side when viewed from the front.

Push the four switches together so that they form a single unit. End pieces are available to make a neat finish at the two sides. The pole of each switch is the top contact and all the poles connect to a single point on the p.c.b.

A quick method of joining the poles together is to push a piece of single-core bare wire straight through the set of holes in one operation. A single insulated wire can then be used to join the set of poles to the p.c.b.

Join the other contacts of the switches to the p.c.b., colour coding the wires to avoid confusion. Ignore any advice about making "a mechanically sound joint before applying the solder" – solder is quite strong enough to hold the wires on its own.

So, tin the contacts of the switches with a layer of solder, strip the insulation from the ends of the wires so that only about 2mm of bare wire shows, then tin the wire.

Now attach each wire to each contact without additional solder. This method is quick, easy, requires only two hands, and above all allows the wires to be easily disconnected when the switch unit is positioned in the case.

RELAY

The use of a relay with the Timer is optional and the choice of relay will depend on the item to be controlled. Although the circuit includes a driver for a relay with a 12V coil, the relay was not implemented in the prototype.

If mains powered equipment is to be switched by a relay, several safety points must be considered.

It is imperative that the relay is securely bolted to the case and that its mains wiring can NEVER come into contact with other parts of the circuit. The relay contacts and their wiring must be adequately rated for the current to be switched. The mains cable must be secured in its case entry hole by a suitable clamping gland.

Mains wiring should NOT be attempted by inexperienced persons. If in any doubt, consult a qualified electrician.

TESTING

Plug in the i.c.s the correct way round taking the usual precautions to avoid

damage and static electricity "zapping". Touch an earthed metal object before handling them. Finally, insert the 7-segment displays directly into the sockets on the p.c.b. for testing.

As with all the projects in this series, it is wise to first test the circuit with a regulated 9V or 12V 100mA d.c. supply. Remember that the timer will only count when fed with an a.c. supply, but much of the initial testing can be accomplished more safely with a 100mA d.c. supply. Remember also that although 12V d.c. is acceptable for testing, a 12V a.c. supply is too high, as explained earlier.

Assuming that a d.c. supply is connected (either way round) to the "a.c. input", some segments of the displays should light. Press switch S3 (Reset) and check that the displays switch to the setting displayed by the rotary switches. Check that if the rotary switches are turned, the change is copied on the 7-segment displays.

So far, counting will not have taken place because the circuit requires an a.c. supply. Assuming that all is well, connect the a.c. supply of about 6V to 9V.

If the circuit behaved properly on the d.c. supply it should now do the same, except that counting down should occur when the Start switch (S2) is pressed. If not, an oscilloscope will confirm whether a 100Hz square wave is present at the output of IC1.

FAULT FINDING

All circuits are tedious when they do not work, and if you have made any errors, this one may be more frustrating than most! A common problem is failure of one or more display segments. This may be caused by a poor connection or a short circuit between two adjacent connections.

An unrecognisable array of lit segments which do not form proper numbers is often caused by a mix up between connections. Check that the display connectors are plugged in the correct way round.

If the rotary switches produce strange results when turned, check their connections carefully. It is particularly important to establish which contact represents the

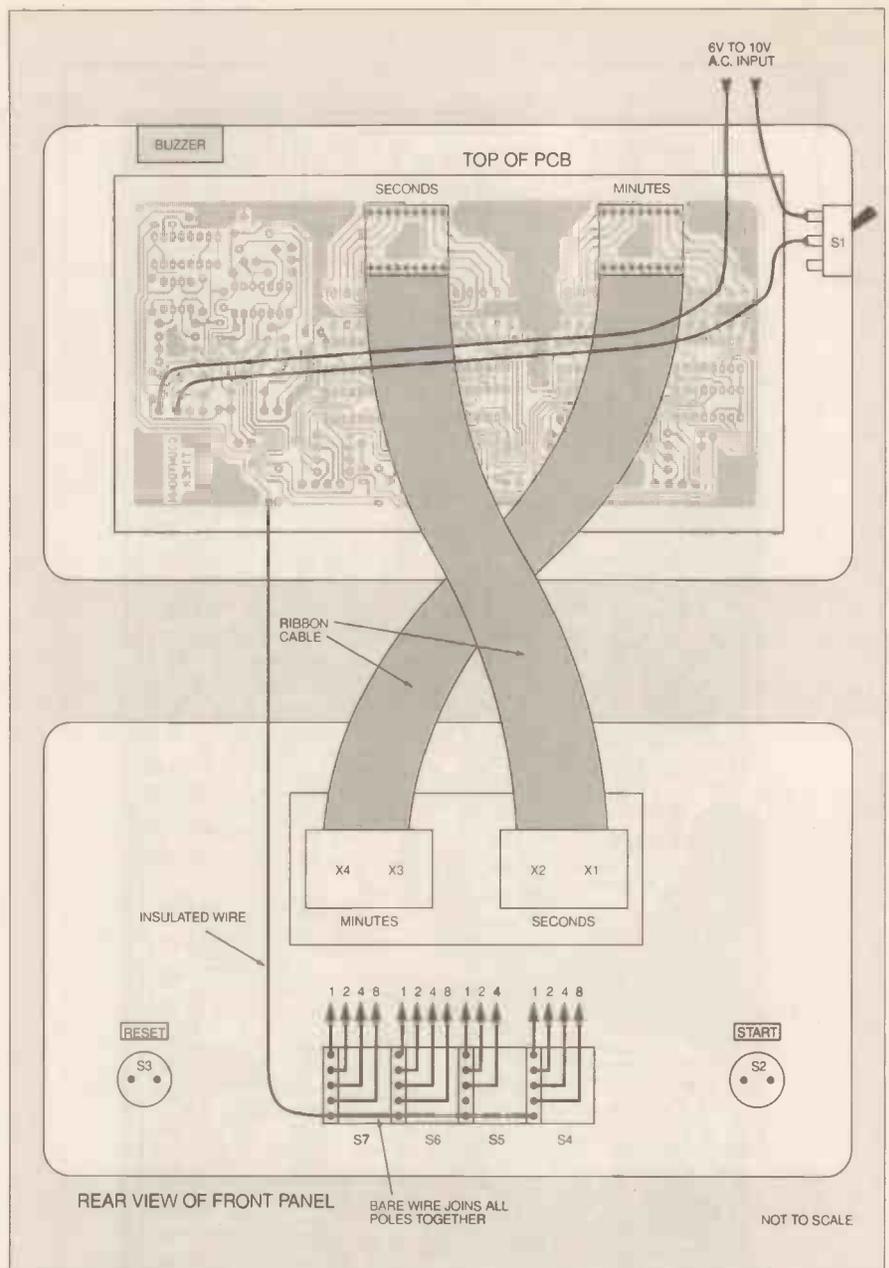


Fig. 7. Interwiring of the p.c.b. to the case-mounted components not shown in Fig. 5.

"common" pole. If in doubt, disconnect one switch and check it with a multimeter (on a low resistance range), noting that the output is in binary. In other words, when the switch is set to 0 the common pole should not connect with any other contact. When set to 1, common should connect with the first contact; when set to 2, common should connect with the second; when set to 4, the third, and when set to 8, the fourth.

Other faults can be located with the multimeter. For example the positive and negative supply voltage for each i.c. can be checked by the meter, set on a suitable d.c. voltage range (e.g. 12V or greater).

If a short circuit exists causing the supply voltage to collapse, try removing all the i.c.s and displays, and use the multimeter set to Ohms to locate the fault. When connected across the positive and negative supply pins of each i.c. socket, the meter will show a reading of an ohm or two. A lower reading indicates that you are closer to the short circuit.

If a fault still persists, see the fault finding guide in Part 1 for further hints, and use the circuit description given earlier to test each module in the circuit.



CASE DETAILS

The p.c.b. is designed to fit in a case with a sloping front panel. There is little room to spare in the specified case and so careful layout is important. Check especially that there is sufficient clearance between the front panel fittings and the p.c.b. Depending on the purchasing source for the rotary switches, they may need to be trimmed slightly. The p.c.b. should be mounted at the very bottom of the case.

The general layout of the case is shown in Fig. 7 and the photographs. Drill and file holes for all the switches, 7-segment displays, low voltage a.c. power input cable or socket, and relay if required.

A red filter for each display provides a significant improvement in readability and may be glued to the inside of the front panel. Each display may now be carefully glued to the filter, ensuring that the number is the correct way up! If the glue is applied around the sides of the displays rather than their fronts it will be hidden from view.

HARD WIRING

The rotary switch set is pushed in from the front. If the connecting wires have been attached by the method described earlier, disconnecting and reconnecting will only be a few minutes task.

Connect the displays to the p.c.b., noting that the connectors must be the correct way round. If this is difficult to work out, experiment, but do not leave the timer switched on if the display fails to

light at all, since this indicates that the polarity may be the wrong way round.

Twist the connector round the opposite way at the display end. If the display lights, but does not indicate proper numbers, then assuming that it worked properly when plugged directly into the p.c.b., the plug at the p.c.b. end may have been accidentally moved sideways by one position.

If this is not the case then – unfortunately – the wires are probably mixed up. This is a difficult and frustrating situation; a

multimeter on its buzzer setting will help identify which wire is which.

Finally, screw the front panel to the body of the case, checking that the wires are neatly folded. Also ensure that if a large version of the rotary switch is used, its connections do not short circuit against the p.c.b.

PART 8

The example project associated with the next part of *Teach-In* is a VU Display with Alarm.

SEETRAX CAE RANGER PCB DESIGN

WITH COOPER & CHYAN AUTOROUTER

RANGER2 + SPECCTRA £400.00

RANGER & SPECCTRA AUTOROUTER
Together giving the most cost effective
PCB design system on the market TODAY!
SEETRAX'S ease of use combined with
COOPER & CHYAN'S renowned gridless
autorouter, at an outstanding price.

R2 Outputs: 8/9 & 24 pin printers, HP
Desk & Laser Jet, Cannon Bubble Jet,
HP-GL, Gerber,
NC Drill, AutoCAD DXF
Demo Disk available at £5.00 +VAT

RANGER2 £150

Upto 8 pages of schematic linked to artwork
Gate & pin swapping - automatic back annotation
Copper flood fill, Power planes, Track necking,
Curved tracks, Clearance checking,
Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SPI)
Gerber-In viewer, AutoCAD DXF in & out

UPGRADE YOUR PCB PACKAGE
TO RANGER2 £60

TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 0SG
Call 01705 591037 or Fax 01705 599036 + VAT & P.P

All Trademarks Acknowledged

INTERFACE

Robert Penfold



THIS month we continue with our look at serial interfacing techniques. In last month's article we considered some aspects of the receiver section of the 6402 UART. In this month's article we look further into the operation of the receiver section, and then progress to the transmitter section.

A practical serial decoder circuit based on the 6402 is then described. For pinout details of the 6402 refer to Fig. 2 in last month's *Interface* article.

Status Symbols

The receiver section of the 6402 provides three status outputs that indicate various types of error. It is not certain that the decoded data is erroneous if one or more of these outputs has been activated, but it is clearly a strong possibility. If one of these "flags" is repeatedly activated, the most likely cause is that the computer is set for the wrong baud rate or word format.

Brief details of these outputs are provided in Table 1. In each case the output is normally low, and it goes high when active. All three outputs are tristate, and are controlled by pin 16. This pin is taken low to enable the status outputs, or high to switch them to the high impedance state.

Table 1: Status Outputs

Pin No.	Function
13	Parity error
14	Framing error (no stop bit detected)
15	Over-run (new byte of data commenced before the previous byte has been dealt with)

There is a further status output at pin 19, and this is an important one in many applications. This output goes high when a complete byte of fresh data has been received. It is reset by pulsing pin 18 low.

In some applications there is no problem if a continuous stream of data appears on the eight data outputs of the receiver. For example, a digital-to-analogue converter circuit normally needs nothing more than a series of data bytes fed to its inputs.

In some applications though, it is essential that the receiving circuit knows when a fresh byte of data has been received. The status output at pin 19 can be used to automatically reset itself via pin 18 and a simple inverter/timer circuit. This process generates a pulse when a new byte of data is available, and the pulse can be used to indicate to the main circuit that fresh data is ready for processing.

Bit-by-Bit

The basic action of the transmitter section is to take eight-bit bytes of data on

its parallel inputs, and to then transmit this data on its serial output, bit by bit, with stop, start, and (where appropriate) parity bits being added. The eight parallel input lines are at pins 26 to 33, and the serial output signal is available at pin 25.

Note that, in common with most serial chips, the 6402 is designed to drive an RS232C input via an inverting buffer stage. In addition to inverting the serial output signal, this stage must convert the 5V logic levels from the UART to normal RS232C drive levels of plus and minus 12V.

Although the transmitter and receiver sections of the 6402 have common control inputs, and must use the same word format, there are separate clock inputs. If required, transmitter and receiver sections can therefore operate at different baud rates. The transmitter clock input is at pin 40, and like the receiver clock input at pin 17, this input requires a clock signal at 16 times the required baud rate.

In order to get the 6402 to transmit a byte of data it is necessary to pulse the transmitter buffer register load input (pin 23) low. On the face of it this pin should not be pulsed at a rate which is higher than that at which the 6402 can transmit bytes of data.

clocked-out from there. Note that this is a tristate output which is controlled via pin 16.

The status output at pin 24 (transmitter register empty) is similar, and it goes high when the transmitter is not actually transmitting any data. This output is not a tristate type, incidentally.

Obviously both of these status outputs are potentially useful for handshaking purposes. Alternatively, the data flow can simply be kept down to a rate that the baud rate in use can comfortably handle.

Acting as the reset input for both the transmitter and receiver sections, pin 21 is the master reset input of the UART. This pin is normally low and is pulsed high in order to reset the device. In normal use a reset pulse is applied to the device at switch-on, and thereafter the master reset input is simply held low.

Receiver Circuit

A simple serial decoder circuit based on a 6402 UART (IC1) is shown in Fig. 1. The RS232C input signal is at signal levels of about plus and minus 12V, and these must be converted to standard 5V logic levels before being applied to the serial input of IC1.

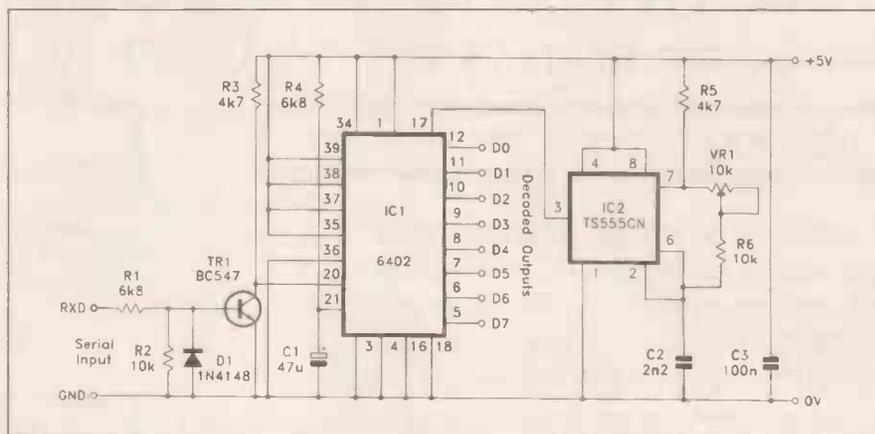


Fig. 1. Circuit diagram for the RS232C to parallel data converter.

In practice this would not result in corruption of the serial data stream, and the transmission of one byte will not be curtailed in order to start the next byte. Pulses on pin 23 are simply ignored if a byte of data is already being transmitted. This could obviously result in "lost" bytes of data in some circumstances, but in others it would be of no real importance.

The transmitter section provides two status outputs. The one at pin 22 goes high if the transmitter buffer register is empty. In other words, this output goes high if the transmitter section is ready to receive a new byte of data.

Serial data is not clocked-out direct from the parallel inputs, but is first loaded into a buffer register, and then

Special RS232C receiver devices are available, but in this application the input signal should be very "clean", and something less than optimum noise handling is acceptable. A simple common emitter switching stage based on transistor TR1 is therefore used to provide the conversion to normal logic levels, and it also gives the necessary inversion of the input signal.

Resistor R4 and capacitor C1 provide IC1 with a positive reset pulse at switch-on. The inputs at pins 35 to 39 program the word format (see last month's *Interface*), and the method of connection shown in Fig. 1 provides a format of one start bit, eight data bits, one stop bit, and no parity. Pin 34 is connected to the +5V rail so that the binary pattern on

pins 35 to 39 is loaded into IC1's control register.

The decoded bytes of parallel data are available at pins 5 to 12, and pin 4 is connected to the 0V rail so that these outputs are permanently enabled. In a stand-alone application the tristate capability of these outputs is not of great value, but if necessary this facility can be utilised by applying a control signal to pin 4 of IC1.

Connecting pin 16 to the 0V rail activates the status outputs. These outputs could be used to drive indicator l.e.d.s., but this is not something that I have found to be particularly useful in practice. If data is not being decoded correctly is usually pretty obvious anyway.

The data register ready input at pin 18 serves no useful purpose in a basic serial interface of this type, so it is simply wired to the 0V rail.

Clocking In

At low to medium baud rates a serial interface does not really require the precision of a crystal controlled clock generator, and a simple C/R oscillator gives quite good results. In this circuit a simple 555 astable circuit based on IC2 is used to provide the clock signal.

A low power CMOS 555 timer was used for IC2, but it should work equally well using a standard 555. The current consumption of the circuit will be increased from around 2mA or 3mA to about 9mA if a standard 555 is used.

The drawback of using a simple C/R oscillator is that it must be adjusted to give the correct output frequency before the interface will function correctly. The specified values give an output frequency that can be adjusted to 19.2kHz, which gives operation at 1200 baud. The output frequency is controlled by preset resistor VR1, which should ideally be a multi-turn "trimpot."

If possible, the output frequency at pin 3 of IC2 should be set to the correct figure with the aid of a Digital Frequency Meter. However, a suitable setting can be found by trial and error, and it is just a matter of trying various settings until you find one that gives properly decoded bytes of data. There should actually be a small range of settings that give good results, and VR1 is adjusted to the middle of this range.

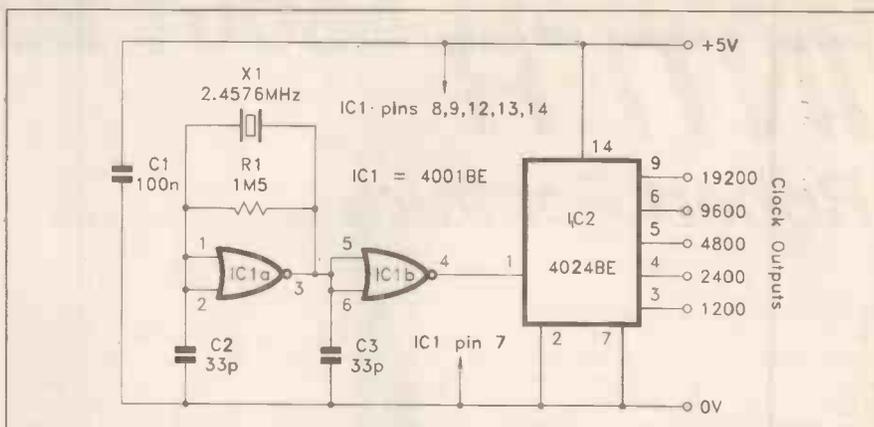


Fig. 2. Circuit diagram for a simple crystal controlled baud rate generator.

This circuit can handle other baud rates if the value of timing capacitor C2 is altered to suit. The output frequency is inversely proportional to the value of C2. A value of 1nF would therefore permit operation at 2400 baud, and a value of 4n7F would provide operation at 600 baud.

Remember that it takes at least ten clock cycles per byte, and that the maximum rate at which data can be received is only about one tenth of the baud rate. A baud rate of 1200 baud therefore supports a data flow of up to about 120 bytes per second.

Crystal Clear

A crystal controlled clock circuit is perhaps a better choice for high baud rates where relatively high clock frequencies are required. A circuit of this type does not have to be particularly complex, but it is inevitably more expensive due to the cost of the crystal.

A 2.4576MHz crystal is the most readily available type for baud rate generation, and Fig. 2 shows the circuit diagram for a baud rate generator based on a crystal having this operating frequency.

A CMOS 4001BE quad 2-input NOR gate is used for IC1, but in this application only two of the gates are actually used, and their inputs are wired together so that they operate as simple inverters. The unused gates have their inputs connected to the +5V rail so that they are not left vulnerable to static charges.

Gate IC1a is used in a conventional crystal oscillator circuit, and IC1b acts as a buffer stage. IC2 is a CMOS 4024BE seven stage binary counter, and its clock input is fed with the 2.4576MHz signal from IC1b.

The first two stages of IC2 are not used, but the other five outputs provide baud rates from 1200 to 19200 baud. Of course, the clock frequency is 16 times the baud rate, and the output frequencies from IC2 range from 19.2kHz to 307.2kHz.

Taking Advantage

If the crystal controlled baud rate generator is used, omit IC2, R5, R6, VR1, and C2 from the main circuit. Pin 17 of the 6402 UART is then driven from the appropriate output of the baud rate generator.

An advantage of the crystal controlled clock circuit is that there is no need for any setting up. With the computer sending at the right baud rate and with the correct word format, properly decoded bytes should always be produced.

However, do make quite sure that the computer's serial interface is set correctly, as many of the problems encountered with serial interfacing seem to be due to an inadvertent mismatch in the baud rate or word format.

Next Month: A circuit for serial transmission will be provided, plus details of how to use these circuits with a PC.

RING BINDERS FOR EPE


This ring binder uses a special system to allow the issues to be easily removed and reinserted without any damage. A nylon strip slips over each issue and this passes over the four rings in the binder, thus holding the magazine in place.

The binders are finished in hard wearing royal blue p.v.c. with the magazine logo in gold on the spine. They will keep your issues neat and tidy but allow you to remove them for use easily.

The price is £5.95 plus £3.50 post and packing. If you order more than one binder add £1 postage for each binder after the initial £3.50 postage charge, (for overseas readers the postage is £6.00 each to everywhere except Australia and Papua New Guinea which costs £10.50 each).

Send your payment in £'s sterling cheque or PO (Overseas readers send £ sterling bank draft, or cheque drawn on a UK bank or pay by credit card), to Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Tel: 01202 881749. Fax: 01202 841692 (We cannot reply to queries or confirm orders by Fax due to the cost).

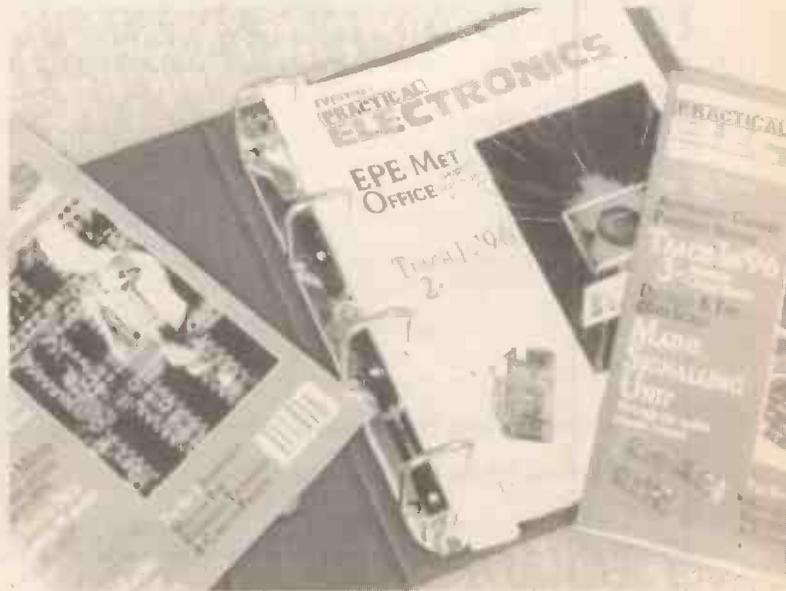We also accept credit card payments. Mastercard (Access) or Visa (minimum credit card order £5). Send your card number and card expiry date plus cardholders address (if different to the delivery address).



LEARN ALL ABOUT ELECTRONICS

The essential reference work

- Easy-to-use format
- Clear and simple layout
- Comprehensive subject range
- Regular Supplements
- Sturdy ring-binder
- Projects to build
- Components checklists
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Detailed assembly instructions
- Professionally written

ORDER NOW
and get a
FREE SUPPLEMENT
plus our
30 DAY MONEY BACK GUARANTEE

The revised edition of **The Modern Electronics Base Manual** contains practical, easy-to-follow information on the following subjects:

BASIC PRINCIPLES: Symbols, components and their characteristics, active and passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, analogue electronics, physics for electronics.

CIRCUITS TO BUILD: From basic principles to circuit-building, The Modern Electronics Manual and its Supplements describe how to assemble radios, loudspeakers, amplifiers, car projects, computer interfaces, measuring instruments, workshop equipment, security systems, etc.

GUARANTEE

Our 30 day money back guarantee gives you complete peace of mind. If you are not entirely happy with the Manual, for whatever reason, simply return it to us in good condition within 30 days and we will make a full refund of your payment – no small print and no questions asked.
(Overseas buyers do have to pay the postage charge)

ESSENTIAL DATA: Extensive tables on diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The Manual also has an extensive **Glossary**, and covers **Safety, Specialist Vocabulary with Abbreviations and Suppliers**. The most comprehensive reference work ever produced at a price you can afford, the revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.

OVER 1,000 A4 loose leaf pages in a sturdy ring binder all for just **£39.95** plus **£6.00** post and packing. Regular Supplements continuously extend the Manual with new material, each Supplement contains approximately 160 pages of information. These are sent about five times a year and cost **£23.50** plus **£2.50** p&p. You can of course return any Supplement (within 10 days) or cancel the Supplements at any time.

Wimborne Publishing Ltd., Dept. Y5
Allen House, East Borough,
Wimborne,
Dorset BH21 1PF
Tel: 01202 881749 Fax: 01202 841692

PLEASE send me **THE MODERN ELECTRONICS MANUAL** plus a **FREE SUPPLEMENT**.

I enclose payment of **£45.95**. I shall also receive the appropriate supplements several times a year. These are billed separately and can be discontinued at any time. Should I decide not to keep the Manual I will return it to you within 30 days for a full refund.

FULL NAME
(PLEASE PRINT)

ADDRESS

..... POSTCODE

SIGNATURE

I enclose cheque/PO payable to Wimborne Publishing Ltd.

Please charge my Visa/Mastercard/Access

Card No. Card Ex. Date

ORDER FORM

Simply complete and return the order form with your payment to the following address:
Wimborne Publishing Ltd, Dept. Y5
Allen House, East Borough, Wimborne,
Dorset BH21 1PF

OVERSEAS ORDERS: All overseas orders must be prepaid and are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the Manual return it within a month for a refund of the purchase price (you do have to pay the overseas postage). **SEND £39.95 PLUS THE POSTAGE SHOWN BELOW:**

EIRE	AIR MAIL ONLY £11
EUROPE (E.E.C. Countries)	AIR MAIL ONLY £20
EUROPE (non E.E.C.)	SURFACE MAIL £20, AIR MAIL £26
U.S.A. & CANADA	SURFACE MAIL £25, AIR MAIL £32
FAR EAST & AUSTRALIA	SURFACE MAIL £31, AIR MAIL £33
REST OF WORLD	SURFACE MAIL £25, AIR MAIL £44


Note surface mail can take over 10 weeks to some parts of the world. Each manual weighs about 4kg including the free supplement when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

INGENUITY UNLIMITED

Our regular round-up of readers' own circuits. We pay between £10 and £50 for all material published, depending on length and technical merit. We're looking for novel applications and circuit tips, not simply mechanical or electrical ideas. Ideas *must be the reader's own work and not have been submitted for publication elsewhere*. The circuits shown have NOT been proven by us. *Ingenuity Unlimited* is open to ALL abilities, but items for consideration in this column should preferably be typed or word-processed, with a brief circuit description showing all relevant component values. Please draw all circuit schematics as clearly as possible.

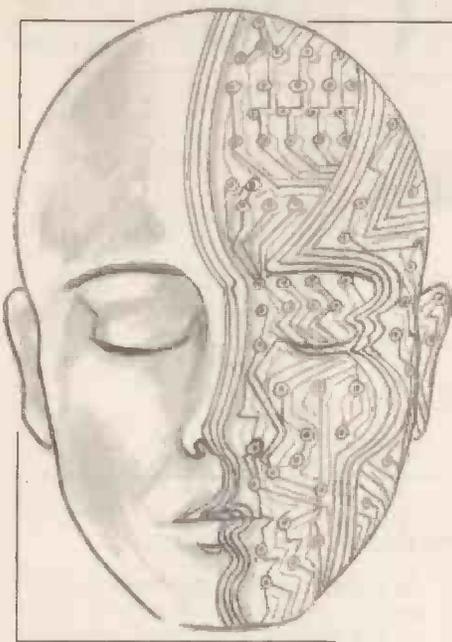Send your circuit ideas to: Alan Winstanley, *Ingenuity Unlimited*, Wimborne Publishing Ltd., Allen House, East Borough, Wimborne, Dorset BH21 1PF. They could earn you some real cash!



D.C. Lamp Dimmer - let there be light

THE D.C. Lamp Dimmer circuit outlined in Fig. 1 will adjust the brightness of a d.c. lamp or the speed of a suitable d.c. motor. An oscillator is formed around the Schmitt inverter IC1a, and is buffered by IC1b. This in turn drives TR1 which is a Darlington power transistor.

The lamp LP1 forms the collector (c) load for the transistor and this is driven at a nominal 330Hz. The duty cycle is, however, fully variable using potentiometer VR1, and consequently the power delivered to the load can be controlled between 5 per cent and 95 per cent, approximately. No flicker will be apparent at this frequency. The circuit consumes little power itself and is ideal for controlling car instrument panel lights.

*Martin Campbell,
Undercliffe,
Bradford, W. Yorks.*

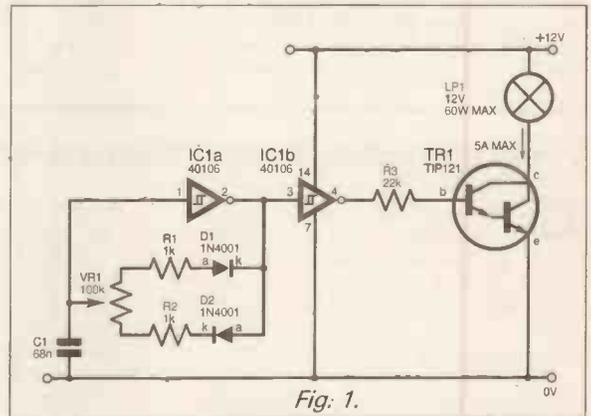


Fig. 1.

Infra-Red Headphone Link - cordless cans

ALTHOUGH not hi-fi, with my simple infra-red circuit it is possible to use headphones with no direct connection to the audio source. Fig. 2(a) illustrates a simple transmitter circuit suitable for connecting to an audio source. Diodes D1 to D3 are three infra-red light-emitting diodes in series, driven by TR2 an n-channel MOSFET transistor with a drain current rating of 500mA maximum. (Listed in the

Cricklewood Catalogue, Tel. 0181 450 0995 - A.W.) The illumination of the l.e.d.s is modulated by the audio signal applied, with TR1 current-limiting and shunting the bias of TR2 to ground when TR2 source current exceeds roughly 100mA.

Potentiometer VR1 should be adjusted for best results. A 9V power supply is best used in this circuit due to the sustained level of current consumption. The transmitter range is

about one to two metres but this can be extended by using reflectors behind the diodes.

A suggested receiver circuit, using an infra-red photodiode, D4, to detect the IR light, is shown in Fig. 2b. The received signal is a.c. coupled to TR3, another MOSFET.

The output is taken from the drain terminal via capacitor C5. Bias can be adjusted with pot. VR2, and this circuit will run from a PP3 size battery. The circuit could be adapted for other applications.

*Upake de Silva, Age 15,
Nugegoda, Sri Lanka.*

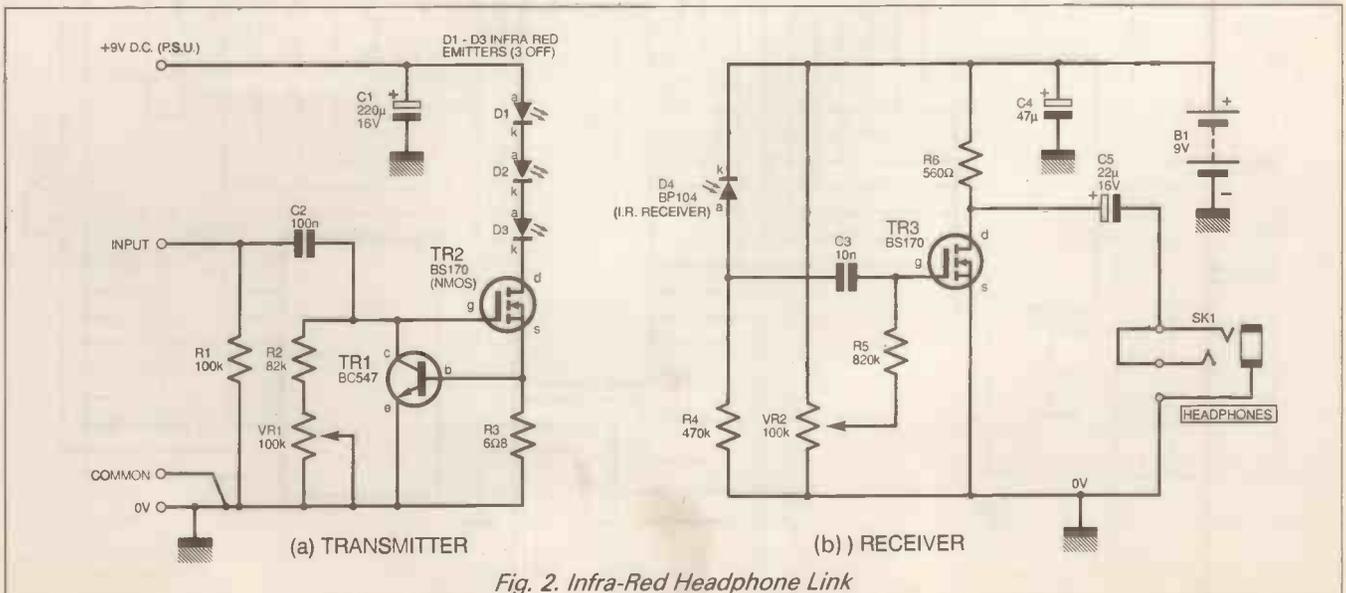


Fig. 2. Infra-Red Headphone Link

Remote Handset Tester

- check it out

THE DEVICE in Fig. 3 arose due to the constant number of requests I receive to help repair infra-red controllers for televisions and VCRs. This Remote Handset Tester is very useful and convenient, and could quickly pay for itself by helping to recover faulty remote handsets.

Pulsed infra-red light generated by the handset falls upon D1 which creates a pulse waveform across R1. This is capacitively coupled to TR1 base and an amplified signal is coupled by C2 to a pulse-stretching circuit based around TR2, C3 and associated components. Hence the driver transistor TR3 conducts and illuminates the l.e.d. D2 whenever infra-red light is received by D1.

A functional remote controller with fresh batteries will operate the tester from approximately 500mm whilst one with near exhausted batteries may only work over a few centimetres. Coincidentally, the design also self-tests its own battery by giving an initial flash of D1 when the switch S1 is first closed. The IR photodiode should be roughly a 940

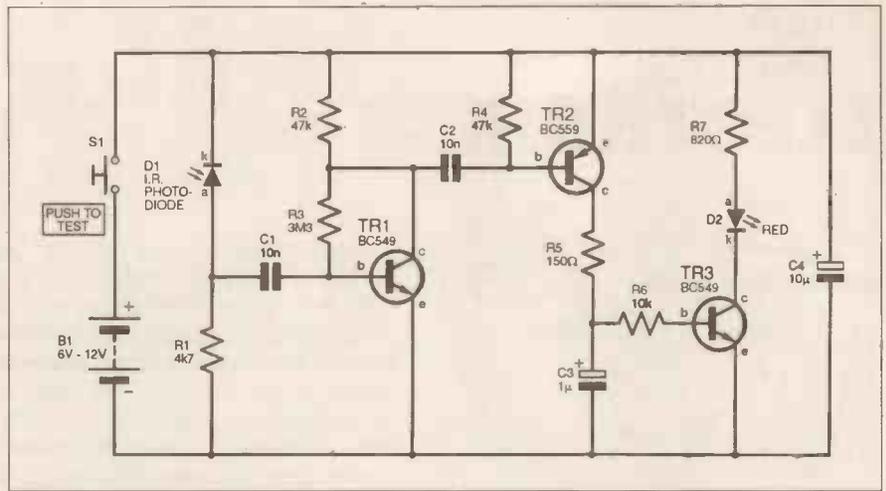


Fig. 3. Circuit diagram for the Remote Handset Tester.

nanometre type, whilst the transistor types themselves are not critical. The circuit will operate from a 6V to 12V rail (e.g. a 12V battery) and C4 decouples the power supply rails.

As a footnote, remote controls which have been dropped very often have a leg broken on

the quartz crystal (usually 455kHz) or breaks between the IR emitter and driver transistor. Remotes contaminated by liquid spillage should be cleaned thoroughly with isopropyl alcohol or similar, using a lint-free cloth.

*Kenneth G. Cargill,
Strathfoyle, Northern Ireland.*

Programmable Timer/Sequencer - done to a turn!

DESIGNED originally to assist with an exercise course for boxing practice, the circuit diagram of the Programmable Sequencer shown in Fig. 4 could be applied in a number of other timing uses. In my own application, the number of rounds and the duration of each round is selectable.

Prior to the start of each round, an audible tone is generated and a seven-segment l.e.d. display shows the round number. Prior to the end of that round, the buzzer sounds again. It could alternatively be used as an egg timer, for example, sounding before the eggs are "done" and the display can indicate soft, medium or hard.

In Fig. 4, IC1 is a 2240 timer/counter device which clocks up to 256 periods, the durations of which are determined by resistor

R1 and capacitor C1. The 2240 has its reset and trigger pins (10 and 11) wired via a pushswitch S1.

The timer is used to operate a memory chip, IC2. I used a 27C64 64K (8K × 8) type which was adequate for boxing practice, but the device can be exchanged for other variants depending on the program required.

The first eight addressed bits are used by the timer/counter to step through the 256 steps available for each program. The other six bits are selected by an external switch network S2 to S7 which permits up to 2⁶ programs, each of 256 steps. The 27C64 has eight outputs which was enough for a single digit l.e.d. display plus a piezo buzzer.

Access to an EPROM programmer is necessary, and working out the code to drive

the display and buzzer can be tricky because each display bit is considered individually: any character possible with 7-bits can be used. I found it easy to set up the individual output codes as "labels" which were then used in the program. To write "1" to display, 00000011 was required so the label "One" was set up as this.

The EPROM requires a 5V rail which was derived from a 7805 voltage regulator running from a 12V battery, making it quite portable. An eight-Darlington buffer, IC3 was utilised to drive the l.e.d. display and sounder (WD1) directly. IC3 has open collectors which can be returned to a higher voltage than the +5V rail used, so it could power other loads.

*David Dawson,
Barlston, Stoke-on-Trent.*

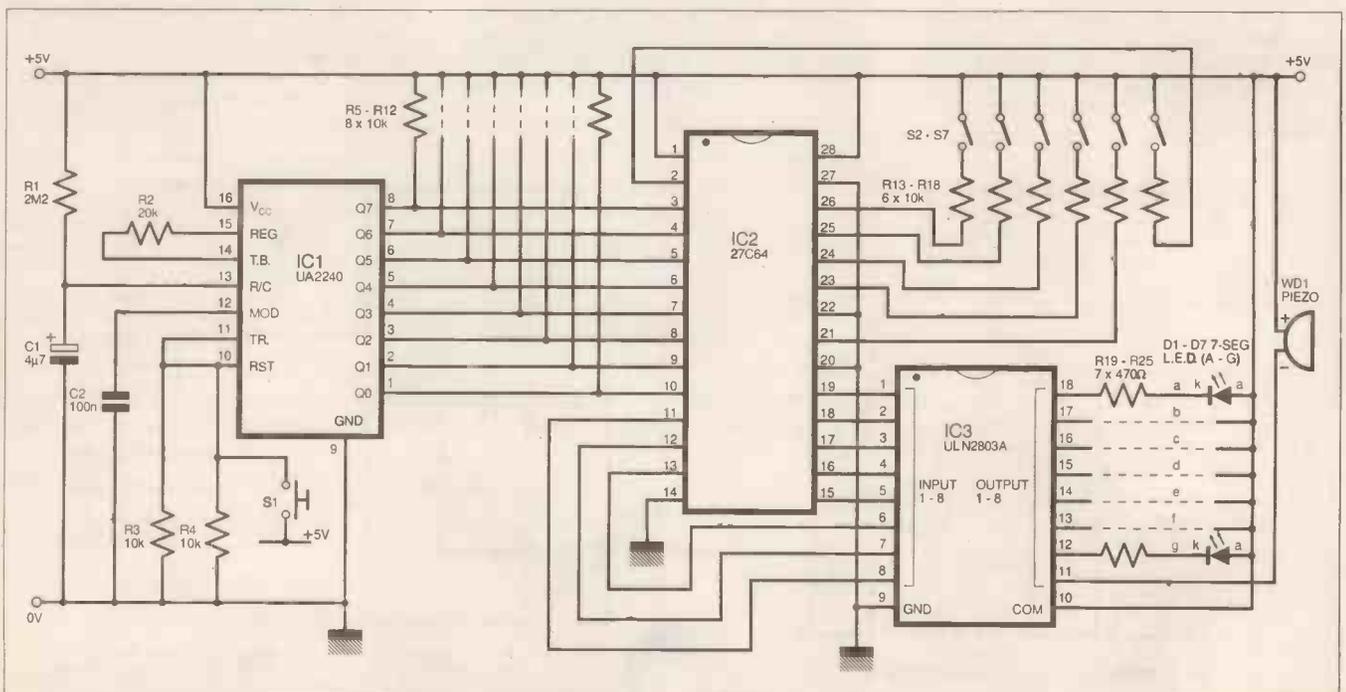


Fig. 4. Circuit diagram for a Programmable Timer/Sequencer.

EVERYDAY

PRACTICAL

ELECTRONICS

BACK ISSUES

We can supply back issues of *EPE* by post, many issues from the past five years are available. An index for each year is also available – see order form. Alternatively, indexes are published in the December issue for that year. Where we are unable to provide a back issue a photostat of any *one article* (or *one part* of a series) can be purchased for the same price.

DID YOU MISS THESE?

NOV '94 Photostats Only (see below)

PROJECTS ● 1000V/500V Insulation Tester ● Video Modules, Part 1 (Simple Fader, Improved Fader, Video Enhancer) ● Active Guitar Tone Control ● Power Controller ● TV Off-er.
FEATURES ● Electronics from the Ground Up, Part 2 ● Consumer Electronics Show.

DEC '94

PROJECTS ● Spacewriter Wand ● *EPE* Fruit Machine ● Universal Digital Code Lock ● Video Modules, Part 2 (Horizontal Wiper, Vertical Wiper, Audio Mixer) ● Rodent Repeller.
FEATURES ● Electronics from the Ground Up, Part 3 ● Embedded Controllers ● Index for Volume 23.

JAN. '95 Photostats Only (see below)

PROJECTS ● Magnetic Field Detector ● Moving Display Metronome ● Model Railway Track Cleaner ● Beating the Christmas Lights ● *EPE* Fruit Machine, Part 2 ● Video Modules, Part 3 (Dynamic Noise Limiter, System Mains Power Supply).
FEATURES ● Electronics from the Ground Up, Part 4 ● Electromagnetic Compatibility ● Checking Transistors.

FEB '95

PROJECTS ● 12V 35W PA Amplifier ● Foot-Operated Drill Controller ● The Ultimate Screen Saver ● MIDI Pedal Board ● Model Railway Signals.
FEATURES ● Electronics from the Ground Up, Part 5 ● Transformerless Power Supplies ● Quickroute 3.0 Review.

MARCH 95

PROJECTS ● Multi-Purpose Thermostat ● Name of the Game-1 Counterspell ● Sound Activated Switch ● Audio Amplifier ● Light Beam Communicator.
FEATURES ● Electronics from the Ground Up, Part 6 ● Understanding PIC Microcontrollers ● Visio Graphics Software Review.
FREE Multi-Project PCB with this issue.



APRIL '95

PROJECTS ● National Lottery Predictor ● Auto-Battery Charger ● Light-Activated Switch ● Switch On/Off Timer ● Continuity Tester ● Name of the Game-2 Counterspin.
FEATURES ● Electronics from the Ground Up, Part 7 ● Circuit Surgery ● The Hard Cell (Mobile Telephones).

MAY '95 Photostats Only (see below)

PROJECTS ● PIC-DATS-1 (PIC Development and Training System) ● R.F. Signal Generator – 1 ● MIDI Pedal ● Club Vote Totaliser ● Name of the Game-3, On Your Marks and Games Timer.
FEATURES ● Electronics from the Ground Up, Part 8 ● Las Vegas Show Report.

JUNE '95 Photostats Only (see below)

PROJECTS ● PIC-DATS-2 (PIC controlled 4-Channel Light Chaser) ● *EPE* HiFi Valve Amplifier – 1 ● R.F. Signal Generator – 2 ● AA to PP3 Converter ● Name of the Game – 4, Star-Struck!, Six-Shot Light Zapper, Wander Wands.
FEATURES ● Electronics from the Ground Up, Part 9 ● Smart Cards.

JULY '95

PROJECTS ● Windicator ● Curtain Winder ● Ramp Generator – 1 ● High Voltage Capacitor Reformer ● *EPE* HiFi Valve Amplifier – 2
FEATURES ● Bridge Rectification Enhanced ● Ingenuity Unlimited.

AUG '95

PROJECTS ● Solar Seeker ● Personal Practice Amplifier ● Infra-Red Remote Control Unit ● Versatile Microcontrolled 3-Digit Timer ● Ramp Generator – 2.
FEATURES ● Static ● Circuit Surgery.

SEPT '95 Photostats Only (see below)

PROJECTS ● Simple Theremin ● Low Range Ohmmeter Adaptor ● Comprehensive Security System ● Vandata ● Hum-Free Battery Eliminator.
FEATURES ● Cave Radio ● Ingenuity Unlimited.



OCT '95

PROJECTS ● Ginormous VU Meter ● Sound Switch ● Audio Sinewave Generator ● Treble Booster ● Infra-Red Controller/Alarm ● Capacitor Check ● Experimenter's Bargraph Test Board.
FEATURES ● Circuit Surgery ● Security Tagging ● Using Bargraph Displays.
FREE ● Multi-Project PCB with this issue.

NOV '95

PROJECTS ● Digital Delay Line ● Video Enhancer ● 50Hz Field Meter ● Temperature Warning Alarm ● Current Tracer ● Distortion Effects Unit.
FEATURES ● Teach-In '96 Part 1 ● Developments in Radio Broadcasting Technology ● Turnpike for Windows Review ● Ingenuity Unlimited.

URGENT?

NEED AN ARTICLE TODAY? TRY OUR NEW FAX ON DEMAND SERVICE
- see page 392 for details

DEC '95

PROJECTS ● Light Operated Switch ● Stereo "Cordless" Headphones ● *EPE* Met Office – 1 ● Modular Alarm System ● Audio Meter and Amplifier.
FEATURES ● Teach-In '96 Part 2 ● Circuit Surgery ● Index for Volume 24.

JAN '96

PROJECTS ● Printer Sharer ● Mains Signalling Unit ● Automatic Camera Panning System ● Audio Signal Generator ● *EPE* Met Office – 2.
FEATURES ● Teach-In '96 Part 3 ● Ingenuity Unlimited ● European Consumer Electronics Show ● Techniques – Actually Doing It ● Maths Plus Review ● Decibels and dBm Scale.

FEB '96

PROJECTS ● Simple PIC16C84 Programmer ● Mains Signalling Unit – 2 ● PIC Electric Meter – 1 ● Vari-Speed Dice ● Analogue Frequency Meter.
FEATURES ● Teach-In '96 Part 4 ● Circuit Surgery ● Making Your Own PC.B.s ● Techniques – Actually Doing It.

MARCH '96

PROJECTS ● Mind Machine Mk III Part 1 ● High Current Stabilized Power Supply ● Multi-Purpose Mini Amplifier ● Infra-Zapper ● PIC-Electric Meter – 2.
FEATURES ● Teach-In '96 Part 5 ● Ingenuity Unlimited ● Flight PAL Trainer Review.
FREE ● Headphones (UK copies only).

APRIL '96

PROJECTS ● Dolby Pro-Logic Decoder (Free Booklet) ● Bat-Band Converter ● Event Counter ● Mind Machine Mk III Part 2 Programmer ● Hearing Tester.
FEATURES ● Teach-In '96 Part 6 ● Circuit Surgery ● Thermionic Valves – The C.R.T.

BACK ISSUES ONLY £2.50 each inc. UK p&p.

Overseas prices £3.10 each surface mail, £4.10 each airmail.

We can also supply issues from earlier years: 1990 (except March), 1991 (except May, June, Aug., Sept. and Nov.), 1992 (except April and Dec.), 1993 (except Jan., Feb., March and April), 1994 (except April, June and Nov.), 1995 (except Jan., May, June and Sept.). Please note we are not able to supply copies (or 'stats of articles) of *Practical Electronics* prior to the merger of the two magazines in November 1992. Where we do not have an issue a photostat of any *one article* or *one part* of a series can be provided at the same price.

ORDER FORM – BACK ISSUES – PHOTOSTATS – INDEXES

Send back issues dated

Send photostats of (article title and issue date)

Send copies of last five years indexes (£2.50 for five inc. p&p – Overseas £3.10 surface, £4.10 airmail)

Name

Address

I enclose cheque/PO./bank draft to the value of £.....

Please charge my Visa/Mastercard £.....

Card No. Card Expiry Date

Note: Minimum order for credit cards £5. Please supply name and address of cardholder if different from that shown above.
SEND TO: **Everyday Practical Electronics, Allen House, East Borough, Wimborne, Dorset BH21 1PF.**
Tel: 01202 881749. Fax: 01202 841692. (Due to the high cost we cannot reply to queries or orders by Fax.)
Payments must be in £ sterling – cheque or bank draft drawn on a UK bank.
Normally supplied within seven days of receipt of order.
Send a copy of this form, or order by letter if you do not wish to cut your issue.

M5/96

FAX ON DEMAND

EVERYDAY

PRACTICAL

ELECTRONICS

ON FAX

WHY WAIT?

We Give You The Fax!

Projects and Series
From the Past Year's
Issues of *EPE*

AVAILABLE INSTANTLY!
24 HOURS A DAY!

WHAT IS EVERYDAY PRACTICAL ELECTRONICS ON FAX?

HAVE you ever wanted to get hold of past project or part of a Teach-In series fast? *EPE ON FAX* is a new service aimed at providing you with the article you need on-demand, seven days a week, 365 days a year, 24 hours a day.

All the projects and major series from the past year have been stored on computer and linked to a sophisticated selection system that uses the latest voice and Fax technology. You can select the article you require from a menu and have it downloaded to your Fax machine on demand.

The service will be constantly updated with new material as each issue is published, thus providing a live, instantly available, resource covering the latest *EPE* articles.

- 1 Call the *EPE ON FAX* system from the handset of your Fax machine. The handset must be switched to "tone".
- 2 Following voice prompts, select either an index of articles, or a specific article by known article number (if you have previously received the index), from the keypad on your Fax machine or connected handset.
- 3 *EPE ON FAX* delivers your choice of article to your Fax machine, complete with cover sheet, while you wait.



HOW TO USE *EPE ON FAX*

- From your Fax machine call 0897 124 125, making sure that your handset is switched to "tone". You will then hear a series of messages, which will help to guide you through the system.
- For one of the available indexes, which contain the document numbers and the number of pages of each article, press "1" when prompted.
- To obtain a particular document, press "2" when prompted and, when requested, enter the document number you want from the keypad on your Fax machine. The system will then confirm your selection.
- When you have selected the document that you require, you will then be prompted to press the Start or Receive button on your Fax machine. Please make sure that you hear a definite Fax squeal before you press Start.

HOW MUCH WILL IT COST?

EPE ON-FAX service is a higher rate premium line phone service. Calls cost £1.50 a minute.

FURTHER INFORMATION

If you would like further information about how this project was put together, ring Starcomm Limited on (0113) 2940600.

TRY IT NOW! CALL 0897 124 125

THE ELECTRONICS SERVICE MANUAL

ESM IS ABOUT ELECTRONICS AND ELECTRONIC EQUIPMENT, EXPLAINING:

- What it is • How it works • How to test it • How to take it apart
- How to find faults • How to fix it

OFFERING:

- Down to earth advice • Vital data • Facts to feast on
- Knowledge at your finger-tips

TOPICS COVERED:


- TV • Audio • Video • Computers • Disk drives • Techniques
- Test gear • Workshops • Addresses • Pinouts • Symbols • Safety
- Logos • Tools • Data • etc

WHO IT'S FOR:

- Across the board appeal!
- Ideal for: Technicians • Engineers • Students • Hobbyists

LITERARY MERIT:

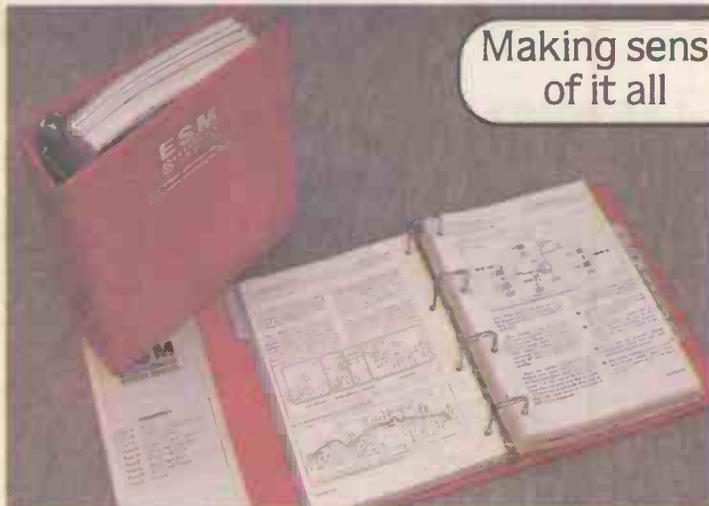- Authoritatively written • Clearly presented • Highly readable
- A living library in words, drawings and photographs



Making sense of it all

SUPPLEMENTS

Detailed technical servicing notes on various types of equipment are covered in the quarterly Supplements, plus additional valuable information for other sections of the Manual

FREE

We will send you the latest Supplement FREE with your Manual

PRICES

Manual only £39.95 plus P&P
Over 850 A4 pages edited by Mike Tooley. Supplied in robust ring binder. Latest Supplement included FREE. 24-hour despatch

Supplements £23.50 plus P&P

Approximately 160 pages of facts and data in each Supplement

GUARANTEE

Our NO-QUIBBLE MONEY-BACK GUARANTEE gives you *complete peace of mind*. If you are not entirely happy with the Manual or its Supplements, for whatever reason, simply return to us in good condition (within 30 days for the Manual, 10 days for Supplements) and we will make a FULL REFUND of your payment. (Overseas buyers do have to pay the postage charge.)

HOW TO OBTAIN ESM

Order now! - just fill in the order form.
Or, to find out more about ESM, ring, fax or write to:

Wimborne Publishing Ltd, Dept. Y5
Allen House, East Borough, Wimborne,
Dorset BH21 1PF

Tel: 01202 881749 Fax: 01202 841692

ELECTRONICS SERVICE MANUAL COVERAGE AND CONTENTS

SAFETY

Safety practices, life-saving techniques, legal requirements

UNDERPINNING KNOWLEDGE

Electronics theory, component theory & functions, circuit techniques, fault diagnosis, detailed equipment principles

PRACTICAL SKILLS

Component identification, avoiding static, soldering & component replacement techniques

TOOLS AND EQUIPMENT

Choosing tools & test gear, workshop practice, optimising test equipment

SERVICING TECHNIQUES

The Supplements include detailed guidelines on how to service specific types of electronic equipment

TECHNICAL NOTES

Detailed examination of how specific types of electronic equipment work

REFERENCE DATA

Detailed tables of specifications for semiconductors, including pinouts

USEFUL ADDRESSES

Manufacturers' & suppliers' addresses, including logos

INDEX

Itemised key subjects in the Manual and individual Supplements

PRIORITY ORDER FORM

Full name:.....
(BLOCK CAPITALS PLEASE)

Address:.....
.....
.....

Post code:.....

Telephone Number:.....

- I enclose cheque/PO payable to WIMBORNE PUBLISHING LTD
 Please charge my Access (Mastercard)/Visa card. Expiry date.....

Card No:.....
(Please advise cardholder's address if different from above)

Please send me each new quarterly Supplement when it is published. I understand that these are billed separately and that they can be returned within 10 days or discontinued at any time.

I understand that should I decide not to keep the Manual I can return it to you within 30 days for a FULL REFUND (overseas customers must pay the postage).

Signature:.....

Please send this form (or copy) to: Wimborne Publishing Ltd, Y5, Allen House, East Borough, Wimborne, Dorset BH21 1PF

PLEASE URGENTLY SEND ME

Item	Cost	Postage	Total
ESM Manual	£39.95	£	£
One Supplement free with Manual	FREE	FREE	£0.00
Payment in £ Sterling only		Total	£

POSTAGE CHARGES

Manual		
Postal Region	Surface	Air
UK	£5.50	-
Eire	-	£11
Europe (EEC)	-	£20
Europe (Non-EEC)	£20	£26
USA & Canada	£25	£32
Far East & Australia	£31	£33
Rest of World	£25	£44

NOTE: Surface mail can take over 10 weeks to some parts of the world.
Each Manual weighs about 4kg when packed.


£1 BARGAIN PACKS

- List 1

1,000 items appear in our Bargain Packs List - request one of these when you next order.

- 1 x 12V Stepper Motor. 7.5 degree. Order Ref: 910.
- 1 x 10 pack Screwdrivers. Order Ref: 909.
- 2 x 5 amp Pull Cord Ceiling Switches. Brown. Order Ref: 921.
- 5 x reels Insulation Tape. Order Ref: 911.
- 2 x 14mm Bull-races. Order Ref: 912.
- 2 x Cord-Grip Switch Lamp Holders. Order Ref: 913.
- 1 x D.C. Voltage Reducer 12V to 6V. Order Ref: 916.
- 1 x 10 amp 40V Bridge Rectifier. Order Ref: 889.
- Lightweight Stereo Headphones. Moving coil so superior sound. Order Ref: 896.
- 2 x 25W Crossovers. For 4ohm loudspeakers. Order Ref: 922.
- 2 x NiCad Constant Current Chargers. Easily adaptable to charge almost any NiCad battery. Order Ref: 910.
- 18V-0V-18V 10VA mains transformer. Order Ref: 83.
- 2 x White Plastic Boxes. With lids, approx. 3" cube. Lid has square hole through the centre so these are ideal for light-operated switch. Order Ref: 132.
- 2 x Reed Relay Kits. You get 8 reed switches and 2 coil sets. Order Ref: 148.
- 12V-0V-12V 6VA mains transformer, p.c.b. mounting. Order Ref: 938.
- 1 x Big Pull Solenoid. Mains operated. Has 1/2" pull. Order Ref: 871.
- 1 x Big Push Solenoid. Mains operated. Has 1/2" push. Order Ref: 872.
- 1 x Mini Mono Amp. 3W into 4 ohm speaker or 1W into 8 ohm. Order Ref: 495.
- 1 x Mini Stereo 1W Amp. Order Ref: 870.
- 15V D.C. 500mA p.s.u., nicely cased. Order Ref: 942.
- 1 x In-Flight Stereo Unit is a stereo amp. Has two most useful mini moving coil speakers. Made for BOAC passengers. Order Ref: 29.
- 1 x 0-1mA Panel Meter. Full vision face 70mm square. Scaled 0-100. Order Ref: 756.
- 2 x Lithium Batteries. 2-5V penlight size. Order Ref: 874.
- 2 x 3m Telephone Leads. With BT flat plug. Ideal for 'phone extensions, fax, etc. Order Ref: 552.
- 1 x 12V Solenoid. Has good 1/2" pull or could push if modified. Order Ref: 232.
- 4 x In-Flex Switches. With neon on/off lights, saves leaving things switched on. Order Ref: 7.
- 2 x 6V 1A Mains Transformers. Upright mounting with fixing clamps. Order Ref: 9.
- 2 x Humidity Switches. As the air becomes damper the membrane stretches and operates a microswitch. Order Ref: 32.
- 5 x 13A Rocker Switch. Three tags so on/off, or changeover with centre off. Order Ref: 42.
- Mini Cassette Motor, 9V. Order Ref: 944.
- 1 x Suck or Blow-Operated Pressure Switch. Or it can be operated by any low pressure variation such as water level in tanks. Order Ref: 67.
- 1 x 6V 750mA Power Supply. Nicely cased with mains input and 6V output lead. Order Ref: 103A.
- 2 x Stripper Boards. Each contains a 400V 2A bridge rectifier and 14 other diodes and rectifiers as well as dozens of capacitors, etc. Order Ref: 120.
- 12 Very Fine Drills. For PCB boards etc. Normal cost about 80p each. Order Ref: 128.
- 5 x Motors for Model Aeroplanes. Spin to start so needs no switch. Order Ref: 134.
- 6 x Microphone Inserts. Magnetic 400 ohm, also act as speakers. Order Ref: 139.
- 6 x Neon Indicators. In panel mounting holders with lens. Order Ref: 180.
- 1 x In-Flex Solderstat. Keeps your soldering iron etc always at the ready. Order Ref: 196.
- 1 x Electric Clock. Mains operated. Put this in a box and you need never be late. Order Ref: 211.
- 4 x 12V Alarms. Makes a noise about as loud as a car horn. All brand new. Order Ref: 221.
- 2 x (6" x 4") Speakers. 16 ohm 5 watts, so can be joined in parallel to make a high wattage column. Order Ref: 243.
- 1 x Panostat. Controls output of boiling ring from simmer up to boil. Order Ref: 252.
- 2 x Oblong Push Switches. For bell or chimes, these can switch mains up to 5A so could be footswitch if fitted in patress. Order Ref: 263.
- 50 x Mixed Silicon Diodes. Order Ref: 293.
- 1 x 6 Digit Mains Operated Counter. Standard size but counts in even numbers. Order Ref: 28.
- 2 x 6V Operated Reed Relays. One normally on, other normally closed. Order Ref: 48.
- 1 x Cabinet Lock. With two keys. Order Ref: 55.
- 6 1/2 80 5 Watt Speaker. Order Ref: 824.
- 1 x Shaded Pole Mains Motor. 3/4" stack, so quite powerful. Order Ref: 85.
- 2 x 5 Aluminium Fan Blades: Could be fitted to the above motor. Order Ref: 86.
- 1 x Case, 3 1/2" x 2 1/4" x 1 3/4" with 13A socket pins. Order Ref: 845.
- 4 x Luminous Rocker Switches. 10A mains. Order Ref: 793.
- 4 x Different Standard V3 Microswitches. Order Ref: 340.
- 4 x Different Sub-Min. Microswitches. Order Ref: 313.

YOU SAVE £40

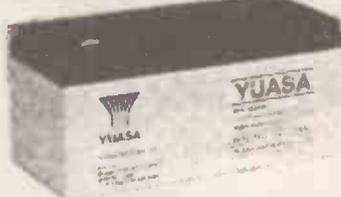

THE JAP MADE 12V 15AH SEALED LEAD ACID BATTERY from regular suppliers costs £50, you can have one from us for only £10 including VAT if you collect or £12.50 if we have to send. Being sealed it can be used in any position and is maintenance free. ALL in tip top condition and fully guaranteed, Order Ref: 12.5P2. Or if you want a smaller one we have 12V 2.3AH, regular price £14, yours for only £5, Order Ref: 5P258.

Infra Red Controller. Made for Thorn TV sets but suitable for other control purposes. Fully built and ready to operate, real bargain, £21, Order Ref: 2P304.

Hall Effect. Give positive or negative pulses when magnet passes over it. Mounted on small PCB, 2 for £1, Order Ref: 1032.

Mains Klaxon Type Alarm. Very loud output but adjustable. Completely encased, shelf or wall mounting, £5, Order Ref: 5P226.

Figure-8 Flex. Figure-8 flat white pvc lead, flexible with .4 sq.mm cores. Ideal for speaker extensions and bell circuits. Also adequately insulated for mains lighting. 50m coil, £2. Order Ref: 2P345. 12m coil, £1. Order Ref: 1014.

Friedland Underdome Bell. Their ref: 792, a loud ringer but very neat, 3" diameter, complete with wall fixing screws, £5. Order Ref: 5P232.

High Current A.C. Mains Relay. This has a 230V coil and changeover switch rated at 15A with PCB mounting with clear plastic cover, £1, Order Ref: 965.

Ultra Thin Drills, actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack. Order Ref: 797B.

You Can Stand On It! Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools in. Internal size approx. 10 1/2" x 4 1/2" x 6" high. Complete with carrying strap, price £2. Order Ref: 2P283B.

Ultrasonic Transducers. Two metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair. Order Ref: 1.5P/4.

Power Supply with Extras. Mains input is fused and filtered and the 12V DC output is voltage regulated. Intended for high class equipment, this is mounted on a PCB and, also mounted on the board, but easily removed, are two 12V relays and Piezo sounder, £3. Order Ref: 3P80B.

Mains 230V Fan. Best make "PAPST", 4 1/2" square, metal blades, £8. Order Ref: 8P8.

BIG BUYER

Please note if you order 10 of an item you may deduct 10%. If you order 25, then deduct 25% but add VAT. If you need 100 or more, you can usually deduct 40% but please ring to confirm.

12V 10A Switch Mode Power Supply. For only £9.50 and a little bit of work because you have to convert our 135W PSU. Modifications are relatively simple - we supply instructions. Simply order PSU Ref: 9.5P2 and request modification details, price still £9.50

Very Powerful Mains Motor. With extra long (2 1/2") shafts extending out each side. Makes it ideal for a reversing arrangement for, as you know, shaded-pole motors are not reversible, £3. Order Ref: 3P157.

45A Double-Pole Mains Switch. Mounted on a 6" x 3 1/2" aluminium plate, beautifully finished in gold, with pilot light. Top quality, made by MEM, £2. Order Ref: 2P316.

Lamp Dimmer. Suitable for up to 250W, on standard plate so fits directly in place of existing switch. Coloured red, blue, yellow or green but will take emulsion paint, £2 each, Order Ref: 2P380.

Philips 9" High Resolution Monitor. Black and white in metal frame for easy mounting. Brand new, still in maker's packing, offered at less than price of tube alone, only £15. Order Ref: 15P1.

12V/24V DC Solenoid. The construction of this is such that it will push or pull. With 24V this is terrifically powerful but is still quite good at 12V, £1. Order Ref: 877.

Don't Stand Out In The Cold. Our 12m telephone extension lead has a flat BT socket one end and flat BT plug other end, £2. Order Ref: 2P338. 20 W 5" 4 Ohm Speaker, £3, Order Ref: 3P145. Matching 4 ohm 20W tweeter, £1.50. Order Ref: 1.5P9.

£3 BARGAIN PACKS

- MAINS SUPPRESSOR/FILTER, 25A, Order Ref: 3P13.
- MAINS TRANSFORMER, 36V 3A, Order Ref: 3P14.
- SIGNAL BOX, 3 pilot lamps in white metal case, Order Ref: 3P16.
- 120W CHOKE, 8ft tube, Order Ref: 3P17.
- 0-5A PANEL METER, ex-W.D. equipment, Order Ref: 3P20.
- KEYBOARD intended for OPD computer, Order Ref: 3P27.
- SOLAR CELL, 750mA, Order Ref: 3P42.
- PROJECT BOX with lid, 165 x 119 x 75mm, Order Ref: 3P49.
- INSTRUMENT TYPE MAINS INPUT SOCKET with built-in filter, Order Ref: 3P50.
- 6-CORE 5A FLEX, 12m, Order Ref: 3P54.
- 20V 3A MAINS TRANSFORMER, Order Ref: 3P59.11.
- 1/2RPM 2W MOTOR, Order Ref: 3P64.
- METAL PROJECT BOX, size 8" x 4 1/2" x 4", made for GPO, Order Ref: 3P74.
- THIN CONNECTING WIRE, 2-cores twisted together, full length 500m, Order Ref: 3P78.
- 12V 1A PSU, filtered and regulated on PCB with relays and Piezo sounder, Order Ref: 3P80.
- HORN SPEAKER, 8 Ohm, size 4 1/4" Order Ref: 3P82.
- 20A TIME SWITCH, ex-electricity board, Order Ref: 3P84.
- ABS PROJECT BOX, 145mm x 95mm x 58mm, Order Ref: 3P85.
- HEAT AND LIGHT LAMP BC 250W, Order Ref: 3P86.
- 16-IN-ONE TOOL KIT, Order Ref: 3P100.
- RAINBOW PIANO with tune chart, Order Ref: 3P101.
- BT INSULATION TESTER, faulty but should be repairable. Supplied with circuit diagram, Order Ref: 3P103.
- MODERN TELEPHONE HANDSET without dial, cream. Order Ref: 3P104.
- 20V 4A MAINS TRANSFORMER, Order Ref: 3P106.
- 40V 2A MAINS TRANSFORMER, Order Ref: 3P107.
- 3-CORE 20A FLEX, 10m, Order Ref: 3P109.
- 2-CORE 20A FLEX, 15m, Order Ref: 3P110.
- QUARTZ CLOCK MOVEMENT with 2 sets of hands, modern and period, Order Ref: 3P111.
- 20W LOUDSPEAKER, 5" 4 Ohm by Goodmans, Order Ref: 3P145.
- 0V-80V PANEL METER, Order Ref: 3P147.
- CUPBOARD DOOR ALARM, Order Ref: 3P155.
- WATER LEVEL ALARM, fully adjustable, Order Ref: 3P156.
- HEAVY DUTY MAINS MOTOR with 2 1/2" spindle each side, Order Ref: 3P157.
- RESETTABLE 6-DIGIT 12V COUNTER, Order Ref: 3P158.
- 0V-10V PANEL METER, Order Ref: 3P159.
- 6FT MINERAL FILLED METAL CLAD 1,000W ELEMENT, Order Ref: 3P161.
- TIME AND SET SWITCH for mains at 30A, Order Ref: 3P164.
- 25A 3-CORE FLEX, 10m, Order Ref: 3P166.
- AMSTRAD 8" 15W WOOFER, Order Ref: 3P167.
- 12V BRUSHLESS FAN mounted in frame with its own drive circuit, Order Ref: 3P168.
- SOLENOID AIR VALVE 110V, Order Ref: 3P178.
- TRANSFORMER AND RECTIFIER for 12V charger, Order Ref: 3P188.
- 12V 3A MAINS TRANSFORMER, Order Ref: 3P181.
- WALL MOUNTING MAINS THERMOSTAT, Order Ref: 3P182.
- 5" 8 OHM SPEAKER IN WOODEN CABINET, Order Ref: 3P183.
- MULTICORE VIDEO LEAD with end plugs, Order Ref: 3P187.
- D.C. PANEL METER, 0V to 20V, Order Ref: 3P188.
- 15uF 440V A.C. CAPACITOR, Order Ref: 3P190.
- 20uF 440V A.C. CAPACITOR, Order Ref: 3P191.
- 25uF 370V A.C. CAPACITOR, Order Ref: 3P192.
- MINI STEPPER MOTOR, 1.5 degree steps, Order Ref: 3P193.
- MAINS OPERATED WATER VALVE, suit high or low pressure, Order Ref: 3P192.
- PANEL METER, 0V-100V D.C., Order Ref: 3P194.
- AMSTRAD AMPLIFIER, ref no. not known, is stereo and has 10 LED's on front panel, Order Ref: 3P195.
- 14uF 400V A.C. CAPACITOR, Order Ref: 3P199.
- HALOGEN LAMP 12V 20W, Order Ref: 3P200.

£4 BARGAIN PACKS

- MOTORISTS LEAD LAMP, hand grip plastic body, glass lamp cover and heavy duty wire shield with hanging bracket Order Ref: 4P31.
- ABS BOX with lid, size 220mm x 150mm x 64mm, Order Ref: 4P8.
- 120W TRANSFORMER 40V at 3A output, Order Ref: 4P15.
- 100W TRANSFORMER, main winding 30V at 3 1/2A, secondary winding 20V-0V-20V at 1A, Order Ref: 4P24.
- PANEL METER 0-100uA, 100mm x 100mm, complete with glass front but less case, Order Ref: 4P32.
- DITTO but 100-0-100uA, Order Ref: 4P32A.
- 80W TRANSFORMER 20V-0V-20V with one winding tape at 18V, Order Ref: 4P36.
- AMSTRAD 8" 15W SPEAKER with matching tweeter, 8 Ohm, Order Ref: 4P57.
- FAN 12V by Jap Nipon, body size 93mm x 93mm, Order Ref: 4P65.
- STRIPPER BOARD with lots of IC's, all plug-in, ex-Sentinal phone control unit, Order Ref: 4P67.
- AM/FM RADIO, nicely cased with clip for attaching to cycle, Order Ref: 4P72.
- VENNER TIME SWITCH, 24hr, day length controller, ex-electricity board, Order Ref: 4P74.
- EMI 2-SPEED MOTOR 100 r.p.m. and 500 r.p.m., reversible, Order Ref: 4P80.
- LARGE PANEL METER, scaled 20-0-40A but needs a shunt Order Ref: 4P91.
- 2-PART METAL CASE, ideal car battery charger, etc, Order Ref: 4P89.
- JAPANESE PRECISION MADE MOTOR, reversible, 1500rpm, Order Ref: 4P94.


Prices include VAT and carriage cost if order over £25 otherwise add £3. Send cash, uncrossed postal orders, cheque or quote credit card number.

J & N FACTORS

Pilgrim Works (Dept. E.E.)
Stairbridge Lane, Bolney,
Sussex RH17 5PA

Telephone: 01444 881965
(Also fax but phone first)

BAT BAND CONVERTER B.F.O.

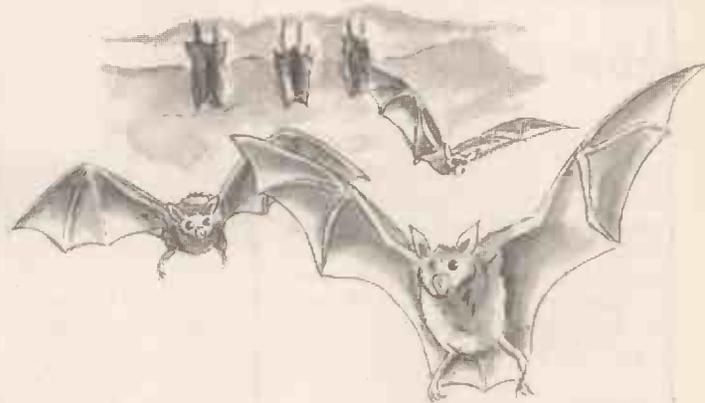

BILL MOONEY

Translate "bat talk" to a more realistic sound by adding this small board to last month's Bat Band Converter.

ENVELOPE detection as used in last month's Bat Band Converter is a very satisfactory method of generating an audible representation of the ultrasound produced by bats.

Faithful translation of the bat pulses to our audio range in a product detector/mixer results in on/off pulse tones. However, the pulse length is so short that we only hear a series of clicks in most cases. The characteristics are nonetheless different to envelope detection.

Adding a Beat Frequency Oscillator (B.F.O.) to the Bat Band Converter/Radio set-up results in a degree of product detection and restores some tonal information to the envelope. The effect is to add colour to the sound and it certainly makes the translation seem more realistic.

If the ultrasound signal is random noise there is little difference in sound quality. But when a pure tone is involved from, say, a watch crystal at 32.768kHz or a combination of simple resonances from the jingle of coins, the effect is quite impressive.

As for bat detection, the sound is certainly more impressive with a B.F.O. and the lower pulse rates in particular are more plausible. As the bat pulse may sweep across the radio pass band and only produces an audible heterodyne when it is close to the B.F.O. frequency, say plus or minus 10kHz, we never get a Morse code-like on/off bleep.

In keeping with the Bat Band Converter, no electrical connection is required to the Radio Receiver and there is plenty of room in the present Converter box lid to take the miniature, printed circuit board – see photograph.

CIRCUIT DESCRIPTION

The full B.F.O. circuit diagram is shown in Fig. 1. It uses a surface mount field effect transistor (f.e.t.) to make up a basic Colpitts oscillator. The high inductance to

capacitance ratio means that it can be tuned from about 400kHz to 500kHz using the trimmer capacitor TC1. This will cover any radio i.f. likely to be encountered.

Total current consumption is about 1.5mA depending on the spread in f.e.t. characteristics. The power supply will normally be the same as that used for last month's Converter and therefore, since the

available from the EPE PCB Service, code 984a/b. (It was combined with last month's Bat Band Converter p.c.b.).

The board component layout and full size copper foil track master pattern are shown in Fig. 2. When it comes to making up this p.c.b. the f.e.t. TR1 should be placed last.

The output capacitor C5 crosses a track and it needs to be placed squarely on its pads. Don't forget to connect the reverse side copper as a "screen", a small loop of Kynar wire snugly fitted around one edge of the p.c.b. will suffice. The supply decoupling capacitor C4 is not at all critical as long as it has a case size "B" to fit on the copper pad sizes given.

The type 3204 sealed trimmer capacitors

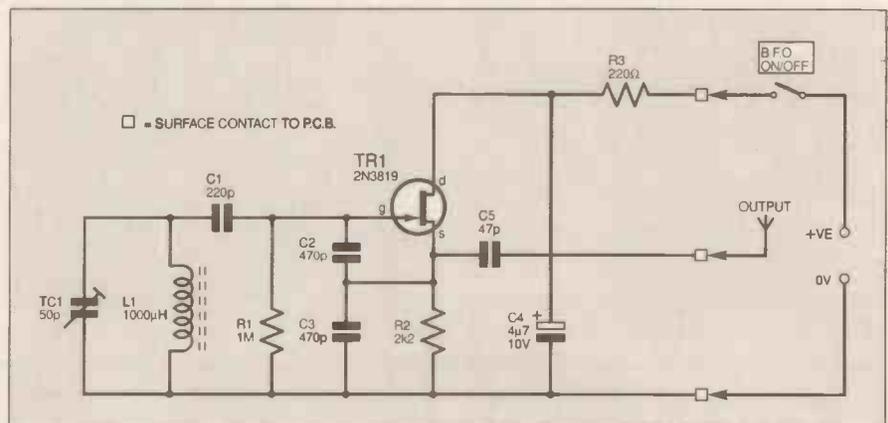


Fig. 1. Complete circuit diagram for the B.F.O.

B.F.O. will go on working down below 4V, a very long life can be expected from a PP3 battery.

The output from the B.F.O. is taken from the source (s) terminal of TR1 through C5. A small aerial may or may not be needed depending on how effectively the radio i.f. amplifier is screened. The r.f. output at C5 is about 2V peak and the aerial should not need to be longer than about 30cm.

CONSTRUCTION

A simple circuit of this type is easily put together, with a little patience, in a compact form using SMDs (Surface Mount Devices). In fact, the B.F.O. is built up on a very small double-sided (only one side etched), surface mount p.c.b. This board is

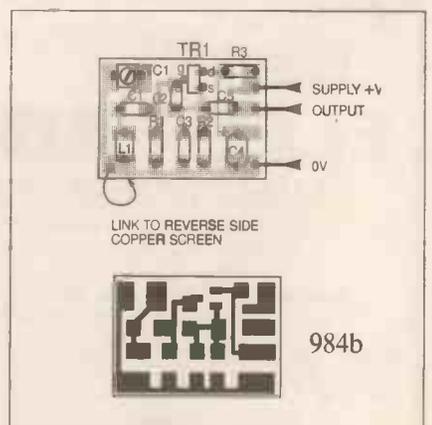


Fig. 2. Printed circuit board component layout and copper foil master pattern.

COMPONENTS

B.F.O.

See
SHOP
TALK
Page

Resistors

- R1 1M
(EIA code 105)
R2 2k2
(EIA code 222)
R3 220Ω (EIA code 222)
All surface mount (SMD), size 1206

Capacitors

- C1 220p COG dielectric, 50V
C2, C3 470p COG dielectric, 50V
(2 off)
C5 47p COG dielectric, 50V
All above SMD size 1206
C4 4μ7 SMD tantalum 10V,
case size B
TC1 50p sealed SMD trimmer,
type 3204

Semiconductor

- TR1 2N3819 j-f.e.t. in SMD
SOT23 package

Miscellaneous

- L1 1000μH fixed (10%), SMD
type CM45 or similar
S1 min. on/off toggle switch
Printed circuit board available from
EPE PCB Service, code 984a/b (com-
bined with Converter p.c.b.); 1mm
socket and plug; Kynar (wirewrapping)
insulated wire; multistrand connecting
wire; solder etc.

Approx Cost
Guidance Only

£12
including p.c.b.

have a small blob of silicone rubber on top to prevent ingress of solder during wave soldering. This is best removed with a pair of tweezers as it tends to cause a little backlash.

Even with the 1206 sized SMD chips, commonly used for hand working, this unit is quite small and in particular it has a very low profile. It could be slotted inside a portable radio where it may have other uses when not bat spotting. This option may be preferred if it is difficult to get enough injection of the carrier with a particular receiver or where it has a short wave band.

However, for this project it will fit neatly in the lid of the Converter box, see photograph. The output is taken to a 1mm socket and it will need its own on/off switch. The full wiring diagram is shown in Fig. 3.

First prototype B.F.O. board installed in the lid of the Bat Band Converter (last month).

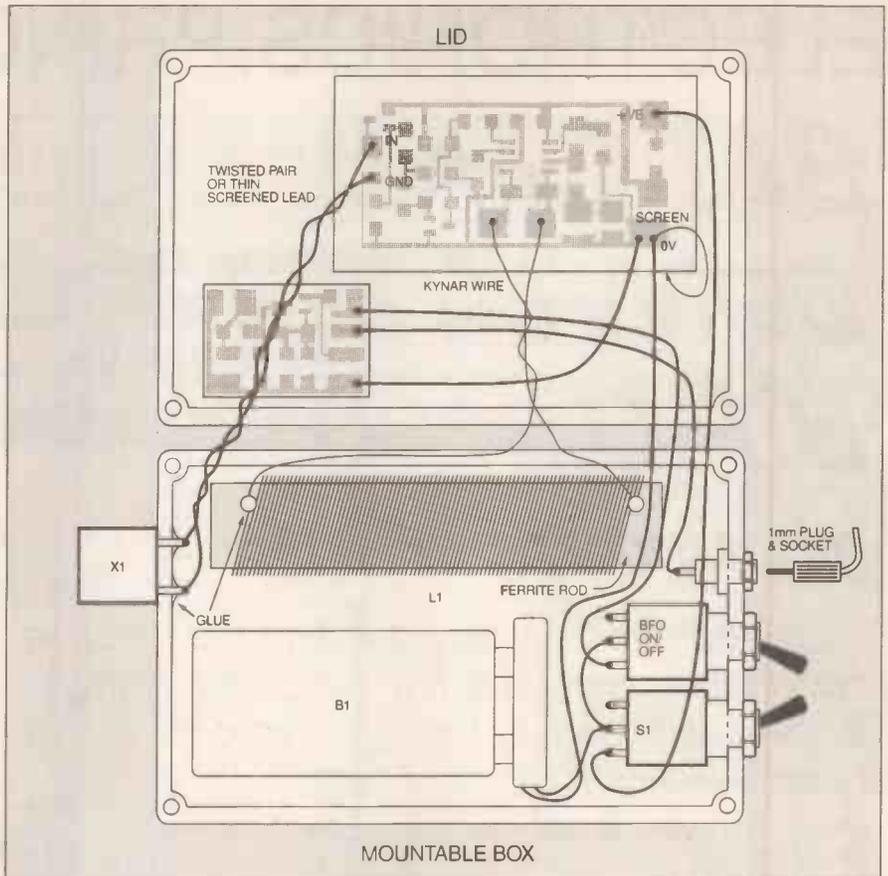


Fig. 3. Wiring the B.F.O. board, additional switch and output socket into last month's small Bat Band Converter case.

TESTING

To get the B.F.O. up and running, first check that the current is around 1.5mA. This can be done by measuring the voltage drop across resistor R3, about 0.35V.

Tune the radio to a weak station at the low frequency end of the medium wave. With the B.F.O. close-by a strong heterodyne should be heard. If the beat frequency is very weak you will need to increase the level of injection by connecting a short length of wire to the B.F.O. output, trailing it over the receiver.

Next, adjust trimmer capacitor TC1 for zero beat. Check that all stations on the band produce a heterodyne. The second harmonic of the B.F.O. will appear between 910kHz and 940kHz.


Finally, switch on the Bat Converter and tune the radio to the maximum sensitivity

position. Whilst rattling some keys or coins, switch on the B.F.O. The sound should become more realistic and metallic.

Excessive B.F.O. injection will begin to operate the radio's a.g.c. (automatic gain control). This will reduce the sensitivity of the system but it may be used as a means of controlling the system gain.

The continuous tone from a quartz watch or clock crystal makes little impression on the envelope detector but you should be able to detect it as a whistle with the B.F.O. switched on. It is not always very strong so that the transducer needs to be placed quite close to the clock mechanism.

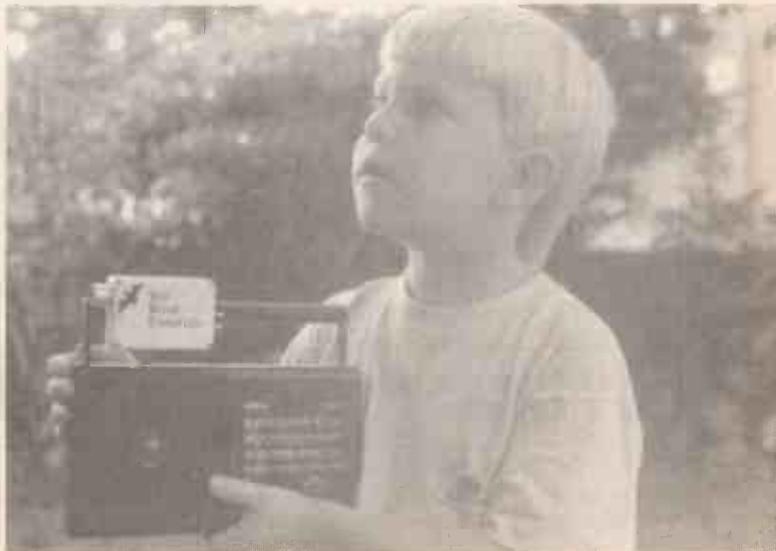The signal should appear just below the high sensitivity peak at 40kHz on the carrier side. There may be one or two heterodynes from distant medium wave stations so that care is required to find the correct signal. □



ELECTRONICS PRINCIPLES 3.0

Electronics Principles 3.0

Basics Dc Theory Ac Theory Transistors Diodes Binary No's Digital Op - Amps

Two's Complement Numbers.

RC Parallel Circuit.

Tri-State Data Latch.

Inverting Operational Amplifier

Resistor 'Rin'

Resistance

Ohms

kOhms

Mohms

Actual Value: 25000

Formatted Value: 25k

Cancel OK

Vin = 200mV

Vout = 2V

Rin = 10k

Rf = 100k

Gain (Av) = 10

Formulae.

$$\text{Gain (Av)} = \frac{R_f}{R_{in}}$$
$$\text{Vout} = \text{Input} * \text{Gain (Av)}$$

OP-Amps

Inverting

Non-Inverting 1

Non-Inverting 2

Dual-Supply

Differential

New Values.

Resistor 'Rin':

10k

Resistor 'Rf':

100k

Input 'V':

200mV

Calculations. Topic Theory. Print.

Cascade up to sixty-four Windows containing an extended range of 284 interactive analogue and digital electronics topics in full colour. For a **demo disk** please send £2.00 cheque/postal order or eight first class stamps.

Complete Package Still Only £49.95

ELECTRONICS TOOLBOX VERSION 3.0

A Windows version of the popular Toolbox Software. Presents over a hundred commonly used formulae in a way that makes calculations easier, thus encouraging experimentation in circuit design. Just select the formula, "pop" in your values and find the result!

Only £19.95

GCSE MATHEMATICS VERSION 2.0

A series of programs covering all the major topics required by the school syllabus. An easy to use package enabling you to study or revise in what we believe is an interesting and enjoyable way. There are over one hundred and fifty mathematics topics with interactive, full colour graphics, enabling a "learning through doing" approach to encourage experimentation. As used in many schools throughout the UK.

Only £49.94

Also available MATHEMATICS PRINCIPLES 2.0 covers all GCSE topics but without reference to the school syllabus. Particularly useful to mature and overseas students.

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex. UK. CM8 2BJ. Tel/Fax 01376 514008.
E-mail Address, Sales@eptsoft.demon.co.uk. WWW Pages. <http://www.octacon.co.uk/ext/ept/software.htm>

Upgrades, Site Licence details or further information: Please telephone.

Add £2 per order for UK post and packing. Make cheques payable to EPT Educational Software.

Switch, Visa and Mastercard orders accepted - Please give card number, expiry date.

OVERSEAS ORDERS: Add £2.50 postage for countries in the EEC. Outside EEC add £3.50 for airmail postage.

DIRECT BOOK SERVICE

ELECTRONICS TEACH-IN 88/89
INTRODUCING MICROPROCESSORS
 Mike Tootley B.A. (published by *Everyday Practical Electronics*)

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc.

Sections cover Microcomputer Systems, Microprocessors, Memories, Input/Output, Interfacing and Programming. There are various practical assignments and eight Data Pages covering popular microprocessors.

And excellent introduction to the subject even for those who do not wish to take the City and Guilds assessment.
 80 pages **Order code TI-88/89** £2.45

ELECTRONICS TEACH-IN No.6
DESIGN YOUR OWN CIRCUITS
 (published by *Everyday Practical Electronics*)
 Mike Tootley B.A.

This book is designed for the beginner and experienced reader alike, and aims to dispel some of the mystique associated with the design of electronic circuits. It shows how even the relative newcomer to electronics can, with the right approach, design and realise quite complex circuits.

Fourteen individual p.c.b. modules are described which, with various detailed modifications, should allow anyone to design and construct a very wide range of different projects. Nine "hands-on" complete DIY projects have also been included so readers can follow the thinking behind design, assembly, construction, testing and evaluation, together with suggested "mods" to meet individual needs.

The subjects covered in each chapter of the book are: Introduction and Power Supplies; Small Signal Amplifiers; Power Amplifiers; Oscillators; Logic Circuits; Timers; Radio; Power Control; Optoelectronics.

The nine complete constructional projects are: Versatile Bench Power Supply; Simple Intercom; Bench Amplifier/Signal Tracer; Waveform Generator; Electronic Die; Pulse Generator; Radio Receiver; Disco Lights Controller; Optical Communications Link.
 136 pages **Order code TI6** £3.45

TEACH-IN No. 7. plus FREE SOFTWARE
ANALOGUE AND DIGITAL ELECTRONICS COURSE
 (published by *Everyday Practical Electronics*)

Alan Winstanley and Keith Dye B.Eng(Tech)AMIEE
 This highly acclaimed *EPE Teach-In series*, which included the construction and use of the Mini Lab and Micro Lab test and development units, has been put together in book form. Additionally, EPT Educational Software have developed a GCSE Electronics software program to complement the course and a FREE DISK covering the first two parts of the course is included with the book.

An interesting and thorough tutorial series aimed specifically at the novice or complete beginner in electronics. The series is designed to support those undertaking either GCSE Electronics or GCE Advanced Levels, and starts with fundamental principles.

If you are taking electronics or technology at school or college, this book is for you. If you just want to learn the basics of electronics or technology you must make sure you see it. *Teach-In No. 7* will be invaluable if you are considering a career in electronics or even if you are already training in one. The Mini Lab and software enable the construction and testing of both demonstration and development circuits. These learning aids bring electronics to life in an enjoyable and interesting way: you will both see and hear the electron in action! The Micro Lab



The books listed have been selected by *Everyday Practical Electronics* editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order to your door. Full ordering details are given on the last book page.

FOR ANOTHER SELECTION OF BOOKS SEE NEXT MONTH'S ISSUE.

Note our UK postage costs just £1.50 no matter how many books you order!

microprocessor add-on system will appeal to higher level students and those developing microprocessor projects.
 160 pages **Order code TI7** £3.95

ELECTRONIC PROJECTS BOOK 1
 (published by *Everyday Practical Electronics* in association with *Magenta Electronics*)
 Contains twenty projects from previous issues of *EE* each backed with a kit of components. The projects are: Seashell Sea Synthesizer, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three-Channel Sound to Light, BBC 16K sideways RAM, Simple Short Wave Radio, Insulation Tester, Stepper Motor Interface, Eprom Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser, Ioniser, Bat Detector, Acoustic Probe, Mainstester and Fuse Finder, Light Rider - (Lapel) Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.
 128 pages **Order code EP1** £2.45

PROJECT CONSTRUCTION

TEST EQUIPMENT CONSTRUCTION

R. A. Penfold
 This book describes in detail how to construct some simple and inexpensive but extremely useful, pieces of test equipment. Stripboard layouts are provided for all designs, together with wiring diagrams where appropriate, plus notes on construction and use.

The following designs are included:-
 AF Generator, Capacitance Meter, Test Bench Amplifier, AF Frequency Meter, Audio Multivoltmeter, Analogue Probe, High Resistance Voltmeter, CMOS Probe, Transistor Tester, TTL Probe.

The designs are suitable for both newcomers and more experienced hobbyists.
 104 pages **Order code BP248** £2.95

A BEGINNER'S GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold
 The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor.
 166 pages **Order code BP285** £3.95

HOW TO DESIGN AND MAKE YOUR OWN P.C.B.S

R. A. Penfold
 Deals with the simple methods of copying printed circuit board designs from magazines and books, and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.
 80 pages **Order code BP121** £2.50

AUDIO AMPLIFIER CONSTRUCTION

R. A. Penfold
 The purpose of this book is to provide the reader with a wide range of preamplifier and power amplifier designs that will, it is hoped, cover most normal requirements. The preamplifier circuits include low noise microphone and RIAA types, a tape head preamplifier, a guitar preamplifier and various tone controls. The power amplifier designs range from low power battery operation to 100W MOSFET types and also include a 12 volt bridge amplifier capable of giving up to 18W output.

All the circuits are relatively easy to construct using the p.c.b. or stripboard designs given. Where necessary any setting-up procedures are described, but in most cases no setting-up or test gear is required in order to successfully complete the project.
 100 pages **Order code BP122** £2.95

DESIGN YOUR OWN CIRCUITS
 See *ELECTRONICS TEACH-IN* No. 6 above left.

RADIO / TV / VIDEO

ELECTRONIC PROJECTS FOR VIDEO ENTHUSIASTS

R. A. Penfold
 This book provides a number of practical designs for video accessories that will help you get the best results from your camcorder and VCR. All the projects use inexpensive components that are readily available, and they are easy to construct. Full construction details are provided, including stripboard layouts and wiring diagrams. Where appropriate, simple setting up procedures are described in detail; no test equipment is needed.

The projects covered in this book include: Four channel audio mixer, Four channel stereo mixer, Dynamic noise limiter (DNL), Automatic audio fader, Video faders, Video wipers, Video crispener, Mains power supply unit.
 109 pages **Order code BP356** £4.95

SETTING UP AN AMATEUR RADIO STATION

I. D. Poole
 The aim of this book is to give guidance on the decisions which have to be made when setting up any amateur radio or short wave listening station. Often the experience which is needed is learned by one's mistakes, however, this can be expensive. To help overcome this, guidance is given on many aspects of setting up and running an efficient station. It then proceeds to the steps that need to be taken in gaining a full transmitting licence.

Topics covered include: The equipment that is needed; Setting up the shack; Which aeriels to use; Methods of construction; Preparing for the licence.

An essential addition to the library of all those taking their first steps in amateur radio.
 86 pages **Order code BP300** £3.95

EXPERIMENTAL ANTENNA TOPICS

H. C. Wright
 Although nearly a century has passed since Marconi's first demonstration or radio communication, there is still research and experiment to be carried out in the field of antenna design and behaviour.

The aim of the experimenter will be to make a measurement or confirm a principle, and this can be done with relatively fragile, short-life apparatus. Because of this, devices described in this book make liberal use of cardboard, cooking foil, plastic bottles, cat food tins, etc. These materials are, in general, cheap to obtain and easily worked with simple tools, encouraging the trial-and-error philosophy which leads to innovation and discovery.

Although primarily a practical book with text closely supported by diagrams, some formulae which can be used by straightforward substitution and some simple graphs have also been included.
 72 pages **Order code BP278** £3.50

25 SIMPLE INDOOR AND WINDOW AERIALS

E. M. Noll
 Many people live in flats and apartments or other types of accommodation where outdoor aeriels are prohibited, or a lack of garden space etc. prevents aeriels from being erected. This does not mean you have to forgo shortwave listening, for even a 20-foot length of wire stretched out along the skirting board of a room can produce acceptable results. However, with some additional effort and experimentation one may well be able to improve performance further.

This concise book tells the story, and shows the reader how to construct and use 25 indoor and window aeriels that the author has proven to be sure performers.

Much information is also given on shortwave bands, aerial directivity, time zones, dimensions etc.
 50 pages **Order code BP136** £1.75

TESTING, THEORY, DATA AND REFERENCE

TRANSISTOR DATA TABLES

Hans-Günther Steidle

The continually growing number and variety of semiconductor components mean ever greater problems for the user. It is difficult to gain an overall picture of the types which may be suitable for a particular application, from those currently available. However, as a starting point, the electrical parameters of a device are usually sufficient.

The tables in this book contain information about the package shape, pin connections and basic electrical data for each of the many thousands of transistors listed. The data includes maximum reverse voltage, forward current and power dissipation, current gain and forward transmittance and resistance, cut-off frequency and details of applications.

A book of this size is of necessity restricted in its scope, and the individual transistor types cannot therefore be described in the sort of detail that may be found in some larger and considerably more expensive data books. However, the list of manufacturers' addresses will make it easier for the prospective user to obtain further information, if necessary.

Lists over 8,000 different transistors, including f.e.t.s.
200 pages **Order code BP401** £5.95



▶ Transistor Data Tables

MORE ADVANCED USES OF THE MULTIMETER

R. A. Penfold

This book is primarily intended as a follow-up to BP239, (see below), and should also be of value to anyone who already understands the basics of voltage testing and simple component testing. By using the techniques described in Chapter 1 you can test and analyse the performance of a range of components with just a multimeter (plus a very few inexpensive components in some cases). Some useful quick check methods are also covered.

While a multimeter is supremely versatile, it does have its limitations. The simple add-ons described in Chapter 2 extended the capabilities of a multimeter to make it even more useful.

84 pages **Order code BP265** £2.95

ELECTRONIC TEST EQUIPMENT HANDBOOK

Steve Money

The principles of operation of the various types of test instrument are explained in simple terms with a minimum of mathematical analysis. The book covers analogue and digital meters, bridges, oscilloscopes, signal generators, counters, timers and frequency measurement. The practical uses of the instruments are also examined.

Everything from Audio Oscillators, through R, C & L measurements (and a whole lot more) to Waveform Generators and testing Zeners.

206 pages **Order code PC109** £8.95

A REFERENCE GUIDE TO BASIC ELECTRONICS TERMS

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

The wonders of electronics multiply unceasingly and electronic devices are creeping relentlessly into all walks of modern life. As with most professions, ours too has a language of its own, ever expanding and now encompassing several thousands of terms. This book picks out and explains some of the more important fundamental terms (over 700), making the explanations as easy to understand as can be expected of a complicated subject and avoiding high-level mathematics.

Through its system of references, each term is backed up by a list of other relevant or more fundamental terms so that a chosen subject can be studied to any depth required.

472 pages **Order code B*286** £5.95

GETTING THE MOST FROM YOUR MULTIMETER

R. A. Penfold

This book is primarily aimed at beginners and those of limited experience of electronics. Chapter 1 covers the basics of analogue and digital multimeters, discussing the relative merits and the limitations of the two types. In Chapter 2 various methods of component checking are described, including tests for transistors, thyristors, resistors, capacitors and diodes. Circuit testing is covered in Chapter 3, with subjects such as voltage, current and continuity checks being discussed.

In the main little or no previous knowledge or experience is assumed. Using these simple component and circuit testing techniques the reader should be able to confidently tackle servicing of most electronic projects.

96 pages **Order code BP239** £2.95

ELECTRONICS-BUILD AND LEARN

R. A. Penfold

The first chapter gives full constructional details of a circuit demonstrator unit that is used in subsequent chapters to introduce common electronic components - resistors, capacitors, transformers, diodes, transistors, thyristors, fets and op.amps. Later chapters go on to describe how these components are built up into useful circuits, oscillators, multivibrators, bistables and logic circuits.

At every stage in the book there are practical tests and experiments that you can carry out on the demonstrator unit to investigate the points described and to help you understand the principles involved. You will soon be able to go on to more complex circuits and tackle fault finding logically in other circuitry you build.

120 pages **Order code PC103** £6.95



LOUDSPEAKERS FOR MUSICIANS

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Bridges the gap between complicated technical theory, and "cut-and-try" methods which may bring success in design but leave the experimenter unfulfilled. A strong practical bias - tedious and higher mathematics have been avoided where possible and many tables have been included.

The book is divided into six basic sections: Units and Constants, Direct-Current Circuits, Passive Components, Alternating-Current Circuits, Networks and Theorems, Measurements.

256 pages **Order code BP53** £3.95

NEWNES ELECTRONICS TOOLKIT

Geoff Phillips

The author has used his 30 years experience in industry to draw together the basic information that is constantly demanded. Facts, formulae, data and charts are presented to help the engineer when designing, developing, evaluating, fault finding and repairing electronic circuits. The result is this handy workmate volume: a memory aid, tutor and reference source which is recommended to all electronics engineers, students and technicians.

Have you ever wished for a concise and comprehensive guide to electronics concepts and rules of thumb? Have you ever been unable to source a component, or choose between two alternatives for a particular application? How much time do you spend searching for basic facts or manufacturer's specifications? This book is the answer, it covers resistors, capacitors, inductors, semiconductors, logic circuits, EMC, audio, electronics and music, telephones, electronics in lighting, thermal considerations, connections, reference data.

158 pages **Order code NE20** £12.95

INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE

A. Michaels

Helps the reader to find possible substitutes for a popular selection of European, American and Japanese transistors. Also shows material type, polarity, manufacturer and use.

320 pages **Order code BP65** £3.95

AUDIO AND MUSIC

INTRODUCTION TO DIGITAL AUDIO

(Second Edition)

Ian Sinclair

Digital recording methods have existed for many years and have become familiar to the professional recording engineer, but the compact disc (CD) was the first device to bring audio methods into the home. The next step is the appearance of digital audio tape (DAT) equipment.

All this development has involved methods and circuits that are totally alien to the technician or keen amateur who has previously worked with audio circuits. The principles and practices of digital audio owe little or nothing to the traditional linear circuits of the past, and are much more comprehensible to today's computer engineer than the older generation of audio engineers.

This book is intended to bridge the gap of understanding for the technician and enthusiast. The principles and methods are explained, but the mathematical background and theory is avoided, other than to state the end product.

128 pages **Order code PC102** £7.95

AUDIO

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Analysis of the sound wave and an explanation of acoustic quantities prepare the way. These are followed by a study of the mechanism of hearing and examination of the various sounds we hear. A look at room acoustics with a subsequent chapter on microphones and loudspeakers then sets the scene for the main chapter on audio systems - amplifiers, oscillators, disc and magnetic recording and electronic music.

320 pages **Order code BP111** £3.95


PROJECTS FOR THE ELECTRIC GUITAR

J. Chatwin

This book is for anyone interested in the electric guitar. It explains how the electronic functions of the instrument work together, and includes information on the various pickups and transducers that can be fitted. There are complete circuit diagrams for the major types of instrument, as well as a selection of wiring modifications and pickup switching circuits. These can be used to help you create your own custom wiring.

Along with the electric guitar, sections are also included relating to acoustic instruments. The function of specialised piezoelectric pickups is explained and there are detailed instructions on how to make your own contact and bridge transducers. The projects range from simple preamps and tone boosters, to complete active controls and equaliser units.

92 pages **Order code BP358** £4.95

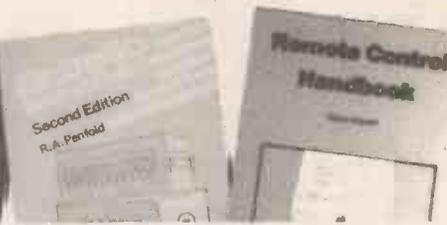

50 CIRCUITS USING GERMANIUM SILICON & ZENER DIODES

AN INTRODUCTION TO LIGHT IN ELECTRONICS

F. A. Wilson

Marconi first bridged the Atlantic with radio waves, then of a mere 200 kilohertz. Since then for communication we have moved up the frequency scale through megahertz and microwaves and are now probing light waves. Accordingly no self-respecting electronics engineer can afford not to be conversant with light and its uses in electronics since development of opto-electronic devices and communication systems is proceeding at a truly explosive rate.

This book is not for the expert but neither is it for the completely uninitiated. It is assumed the reader has some basic knowledge of electronics. After dealing with subjects like Fundamentals, Waves and Particles and The Nature of Light such things as Emitters, Detectors and Displays are discussed. Chapter 7 details four different types of Lasers before concluding with a chapter on Fibre Optics.

161 pages **Order code BP359** £4.95

PRACTICAL ELECTRONIC DESIGN DATA

Owen Bishop

This book is a comprehensive ready-reference manual for electronics enthusiasts of all levels, be they hobbyists, students or professionals. A helpful major section covers the main kinds of component, including surface-mounted devices. For each sort, it lists the most useful and readily available types, complete with details of their electronic characteristics, pin-outs and other essential information.

Basic electronic units are defined, backed up by a compendium of the most often required formulae, fully explained. There are five more extensive sections devoted to circuit design, covering analogue, digital, radio, display, and power supply circuits. Over 150 practical circuit diagrams cover a broad range of functions. The reader is shown how to adapt these basic designs to a variety of applications. Many of the circuit descriptions include step-by-step instructions for using most of the standard types of integrated circuit such as operational amplifiers, comparators, filters, voltage converters and switched-mode power supply devices, as well as the principal logic circuits.

328 pages **Order code BP359** £4.95

Temporarily out of print

MIDI SURVIVAL GUIDE

Vic Lennard

Whether you're a beginner or a seasoned pro, the MIDI Survival Guide shows you the way. No maths, no MIDI theory, just practical advice on starting up, setting up and ending up with a working MIDI system.

Over 40 cabling diagrams. Connect synths, sound modules, sequencers, drum machines and multitracks. How to budget and buy secondhand. Using switch, thru and merger boxes. Transfer songs between different sequencers. Get the best out of General MIDI. Understand MIDI implementation charts. No MIDI theory.

104 pages **Order code PC111** £6.95

PRACTICAL ELECTRONIC MUSICAL EFFECTS UNITS

R. A. Penfold

This book provides practical circuits for a number of electronic musical effects units. All can be built at relatively low cost, and use standard, readily available components. The projects covered include: Waa-Waa Units; Distortion Units; Phaser; Guitar Envelope Shaper; Compressor; Tremolo Unit; Metal Effects Unit; Bass and Treble Boosters; Graphic Equaliser; Parametric Equaliser. The projects cover a range of complexities, but most are well within the capabilities of the average electronics hobbyist. None of them require the use of test equipment and several are suitable for near beginners.

102 pages **Order code BP368** £4.95

LOUDSPEAKERS FOR MUSICIANS

Vivan Capel

This book contains all that a working musician needs to know about loudspeakers; the different types, how they work, the most suitable for different instruments, for cabaret work, and for vocals. It gives tips on constructing cabinets, wiring up, when and where to use wadding, and when not to, what fittings are available, finishing, how to ensure they travel well, how to connect multi-speaker arrays and much more.

Ten practical enclosure designs with plans and comments are given in the last chapter, but by the time you've read that far you should be able to design your own!

164 pages **Order code BP297** £3.95

CIRCUITS AND DESIGN

REMOTE CONTROL HANDBOOK (Revised Edition)

Owen Bishop

Remote control systems lend themselves to a modular approach. This makes it possible for a wide range of systems, from the simplest to the most complex, to be built up from a number of relatively simple modules. The author has tried to ensure that, as far as possible, the circuit modules in this book are compatible with one another. They can be linked together in many different configurations to produce remote control systems tailored to switch a table lamp on and off, or to operate an industrial robot, this book should provide the circuit you require.

240 pages **Order code BP240** £3.95

COIL DESIGN AND CONSTRUCTIONAL MANUAL

B. B. Babani

A complete book for the home constructor on "how to make" RF, IF, audio and power coils, chokes and transformers. Practically every possible type is discussed and calculations necessary are given and explained in detail. Although this book is now twenty years old, with the exception of toroids and pulse transformers little has changed in coil design since it was written.

96 pages **Order code 160** £2.50

PRACTICAL ELECTRONICS HANDBOOK -

Fourth Edition, Ian Sinclair

Contains all of the everyday information that anyone working in electronics will need.

It provides a practical and comprehensive collection of circuits, rules of thumb and design data for professional engineers, students and enthusiasts, and therefore enough background to allow the understanding and development of a range of basic circuits.

Contents: Passive components, Active discrete components, Discrete component circuits, Sensing components, Linear I.C.s, Digital I.C.s, Microprocessors and microprocessor systems, Transferring digital data, Digital-analogue conversions, Computer aids in electronics, Hardware components and practical work, Standard metric wire table, Bibliography, The HEX scale, Index.

440 pages **Order code NE21** £12.99

AUDIO IC CIRCUITS MANUAL

R. M. Marston

A vast range of audio and audio-associated i.c.s are readily available for use by amateur and professional design engineers and technicians. This manual is a guide to the most popular and useful of these devices, with over 240 diagrams. It deals with i.c.s such as low frequency linear amplifiers, dual pre-amplifiers, audio power amplifiers, charge coupled device delay lines, bar-graph display drivers, and power supply regulators, and shows how to use these devices in circuits ranging from simple signal conditioners and filters to complex graphic equalizers, stereo amplifier systems, and echo/reverb delay lines etc.

168 pages **Temporarily out of print**

50 CIRCUITS USING GERMANIUM, SILICON AND ZENER DIODES

R. N. Soar

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most simple and inexpensive of components - the diode. Includes the use of germanium and silicon signal diodes, silicon rectifier diodes and Zener diodes, etc.

64 pages **Order code BP38** £1.95

A BEGINNERS GUIDE TO CMOS DIGITAL ICs

R. A. Penfold

Getting started with logic circuits can be difficult, since many of the fundamental concepts of digital design tend to seem rather abstract, and remote from obviously useful applications. This book covers the basic theory of digital electronics and the use of CMOS integrated circuits, but does not lose sight of the fact that digital electronics has numerous "real world" applications.

The topics covered in this book include: the basic concepts of logic circuits; the functions of gates, inverters and

other logic "building blocks"; CMOS logic i.c. characteristics, and their advantages in practical circuit design; oscillators and monostables (timers); flip/flops, binary dividers and binary counters; decade counters and display drivers.

The emphasis is on a practical treatment of the subject, and all the circuits are based on "real" CMOS devices. A number of the circuits demonstrate the use of CMOS logic i.c.s in practical applications.

119 pages **Order code BP333** £4.95

OPTOELECTRONICS CIRCUITS MANUAL

R. M. Marston

A useful single-volume guide to the optoelectronics device user, specifically aimed at the practical design engineer, technician, and the experimenter, as well as the electronics student and amateur. It deals with the subject in an easy-to-read, down-to-earth, and non-mathematical yet comprehensive manner, explaining the basic principles and characteristics of the best known devices, and presenting the reader with many practical applications and over 200 circuits. Most of the i.c.s and other devices used are inexpensive and readily available types, with universally recognised type numbers.

182 pages **Order code NE14** £13.95

OPERATIONAL AMPLIFIER USER'S HANDBOOK

R. A. Penfold

The first part of this book covers standard operational amplifier based "building blocks" (integrator, precision rectifier, function generator, amplifiers, etc), and considers the ways in which modern devices can be used to give superior performance in each one. The second

part describes a number of practical circuits that exploit modern operational amplifiers, such as high slew-rate, ultra low noise, and low input offset devices. The projects include: Low noise tape preamplifier, low noise RIAA preamplifier, audio power amplifiers, d.c. power controllers, opto-isolator audio link, audio millivolt meter, temperature monitor, low distortion audio signal generator, simple video fader, and many more.

120 pages **Order code BP335** £4.95

TIMER/GENERATOR CIRCUITS MANUAL

R. M. Marston

This manual is concerned mainly with waveform generator techniques and circuits. Waveform generators are used somewhere or other in most types of electronic equipment, and thus form one of the most widely used classes of circuit. They may be designed to produce outputs with sine, square, triangle, ramp, pulse, staircase, or a variety of other forms. The generators may produce modulated or unmodulated outputs, and the outputs may be of single or multiple form.

Waveform generator circuits may be built using transistors, op.amps, standard digital i.c.s, or dedicated waveform or "function" generator i.c.s.

The manual is divided into eleven chapters, and presents over 300 practical circuits, diagrams and tables. The subjects covered include: Basic principles; Sine wave generators; Square wave generators; Pulse generator circuits; "Timer i.c." generator circuits; Triangle and sawtooth generators; Multi-waveform generation; Waveform synthesiser i.c.s; Special waveform generators; Phaselocked loop circuits; Miscellaneous "555" circuits.

267 pages **Order code NE18** £13.95

COMPUTING

WINDOWS 95 EXPLAINED

P. R. M. Oliver and N. Kantaris

If you would like to get up and running, as soon as possible, with the new Windows 95 operating system, then this is the book for you.

The book was written with the non-expert, busy person in mind. It explains the hardware that you need in order to run Windows 95 successfully, and how to install and optimize your system's resources. It presents an overview of the Windows 95 environment.

Later chapters cover how to work with programs, folders and documents; how to control Windows 95 and use the many accessories that come with it; how to use DOS programs and, if necessary, DOS commands and how to communicate with the rest of the electronic world.

170 pages **Order code BP400** £5.95

INTERFACING PCs AND COMPATIBLES

R. A. Penfold

Once you know how, PC interfacing is less involved than interfacing many eight-bit machines, which have tended to use some unusual interfacing methods.

This book gives you: A detailed description of the lines present on the PC expansion bus. A detailed discussion of the physical characteristics of PC expansion cards. The I/O map and details of the areas where your add-on can be fitted. A discussion of address decoding techniques. Practical address decoder circuits. Simple TTL 8-bit input and output ports. Details of using the 8255 parallel interface adaptor. Digital to analogue converter circuits. In fact everything you need to know in order to produce successful PC add-ons.

80 pages **Order code BP277** £3.95

HOW TO CHOOSE A SMALL BUSINESS

COMPUTER SYSTEM

D. Weale

This book is for anyone intending to buy an IBM compatible computer system, whether it is their first system or a replacement. There are sections on hardware, application and systems programs, and how to actually make your choice as well as sections on the law, ergonomics

and a glossary of common terms. The text contains many useful tips and some warnings (which could save much effort and expense). After having read this book you should have a better idea of what is suitable for your needs, how to obtain it and how to ensure that the system is operated with the minimum of difficulty.

144 pages **Order code BP323** £4.95

HOW TO EXPAND, MODERNISE AND REPAIR PCs

AND COMPATIBLES (Revised Edition)

R. A. Penfold

Not only are PC and compatible computers very expandable, but before long most users actually wish to take advantage of that expandability and start upgrading their PC system. Some aspects of PC upgrading can be a bit confusing, but this book provides advice and guidance on the popular forms of internal PC expansion, and should help to make things reasonably straightforward and painless. Little knowledge of computing is assumed. The only assumption is that you can operate a standard PC of some kind (PC, PC XT, PC AT, or an 80386 based PC).

The subjects covered include: PC upgrading; Memory upgrades; Adding a hard disk drive; Adding a floppy disk drive; Display adaptors and monitors; Fitting a maths co-processor; Keyboards; Ports; Mice and digitisers; Maintenance (including preventative maintenance) and Repairs, and the increasingly popular subject of d.i.y. PCs.

156 pages **Order code BP271** £5.95

THE PRE-BASIC BOOK

F. A. Wilson, C.G.I.A., C.ENG., F.I.E.E., F.I.E.R.E., F.B.I.M.

Another book on BASIC but with a difference. This one does not skip through the whole of the subject and thereby leave many would-be programmers floundering but instead concentrates on introducing the technique by looking in depth at the most frequently used and more easily understood computer instructions. For all new and potential micro users.

192 pages **Order code BP146** £2.95

SERVICING PERSONAL COMPUTERS -

3rd EDITION

Mike Tooley BA

The revised and enlarged third edition contains a new chapter on servicing 68000 based microcomputers. It has been updated throughout and includes many new photos and diagrams. It is essential for anyone concerned with the maintenance of personal computer equipment or peripherals, whether professional service technician, student or enthusiast.

240 pages **Order code NE15** £25

A CONCISE USER'S GUIDE TO MS-DOS 5

N. Kantaris

If you are a PC user and want to get the most out of your computer in terms of efficiency and productivity, then you must learn the intricacies of its MS-DOS operating system. With this book you will learn to do just that in the shortest and most effective way.

The book explains: The enhancements to be found in MS-DOS version 5, over previous versions of the operating system. How the DOS operating system is structured so that you can understand what happens when you first switch on your computer. How directories and subdirectories can be employed to structure your hard disk for maximum efficiency. How to use the DOS Shell program (a menu-driven graphical interface) to perform various house-keeping operations on your disk. How to manage disk files, and how to use the MS-DOS Editor to fully configure your system by writing your own CONFIG.SYS and AUTOEXEC.BAT files. How to optimise your system by either increasing its conventional memory or increasing its speed. How to write batch files to automate the operation of your system.

A summary of all DOS commands, illustrated with examples, is given in the penultimate chapter, which turns it into a useful reference guide.

124 pages **Order code BP318** £4.95

DIRECT BOOK SERVICE ORDERING DETAILS

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add £1.50 to your total order for postage and packing (overseas readers add £3 for countries in the EEC, or add £6 for all countries outside the EEC, surface mail postage) and send a PO, cheque, international money order (£ sterling only) made payable to Direct Book Service or credit card details (including card expiry date), Visa or Mastercard (Access) - minimum credit card order is £5 - quoting your name and address, the order code and quantities required to DIRECT BOOK SERVICE, 33 GRAVEL HILL, MERLEY, WIMBORNE, DORSET BH21 1RW (mail order only).

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of *Everyday Practical Electronics*) before ordering from old lists.

For a further selection of books see next month's issue.

DIRECT BOOK SERVICE IS A DIVISION OF WIMBORNE PUBLISHING LTD.

BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or in next month's issue of *Everyday Practical Electronics* (all books with a BP prefix to the order code are Babani books). Many readers have asked us to also supply various other Babani books, which have a reputation for value for money.

Our customers tell us they appreciate our speedy service and low postage charge and they would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (£1.50 for UK p&p no matter how many books you buy). We are pleased to be able to respond; we are now able to meet all your requirements for Babani books.

Code	Title	Price	Code	Title	Price	Code	Title	Price
BP37	50 Projects Using Relays, SCRs and TRIACS	£2.95	BP262	A Concise Introduction to WordPerfect (revised edition)	£3.95	BP334	Magic Electronics Projects	£4.95
BP39	50 (FET) Field Effect Transistor Projects	£2.95	BP264	A Concise Advanced User's Guide to MS-DOS (revised edition - covers version 6.2)	£4.95	BP336	A Concise Users Guide to Lotus 1-2-3 Release 3.4	£5.95
BP44	IC 555 Projects	£2.95	BP273	Practical Electronic Sensors	£4.95	BP337	A Concise Users Guide to Lotus 1-2-3 for Windows	£5.95
BP48	Electronic Projects for Beginners	£1.95	BP274	A Concise Introduction to SuperCalc5	£4.95	BP341	MS-DOS 6 Explained (covers V6.2)	£5.95
BP56	Electronic Security Devices	£2.95	BP276	Short Wave Superhet Receiver Construction	£2.95	BP343	A Concise Introduction to Microsoft Works for Windows	£5.95
BP76	Power Supply Projects	£2.50	BP280	Getting the Most From Your PC's Hard Disk	£3.95	BP345	Getting Started in Practical Electronics	£4.95
BP78	Practical Computer Experiments	£1.75	BP281	An Induction to UHF/VHF for Radio Amateurs	£3.50	BP346	Programming in Visual BASIC for Windows	£5.95
BP84	Digital IC Projects	£1.95	BP284	Programming in QuickBASIC	£4.95	BP349	Practical Opto-Electronic Projects	£4.95
BP90	Audio Projects	£2.50	BP292	Public Address Loudspeaker Systems	£3.95	BP350	Electronic Board Games	£4.95
BP95	Model Railway Projects	£2.95	BP294	A Concise Introduction to Microsoft Works (revised edition)	£4.95	BP351	WordPerfect 6 Explained	£5.95
BP115	The Pre-computer Book	£1.95	BP298	A Concise Introduction to the Mac System & Finder	£3.95	BP352	Excel 5 Explained	£5.95
BP125	25 Simple Amateur Band Aerials	£1.95	BP301	Antennas for VHF and UHF	£4.95	BP353	WordPerfect 6.0 for Windows Explained	£5.95
BP126	BASIC & PASCAL in Parallel	£1.50	BP305	Learning CAD with AutoSketch for Windows	£5.95	BP354	Word 6 for Windows Explained	£5.95
BP132	25 Simple SW Broadcast Band Aerials	£1.95	BP306	A Concise Introduction to AmiPro 3	£4.95	BP357	A Concise Introduction to Pressworks	£5.95
BP136	25 Simple Indoor and Window Aerials	£1.75	BP311	An Introduction to Scanners and Scanning	£4.95	BP367	Electronic Projects for the Garden	£4.95
BP144	Further Practical Electronics Calculations & Formulae	£4.95	BP312	An Introduction to Microwaves	£3.95	BP370	The Superhet Radio Handbook	£4.95
BP145	25 Simple Tropical and MW Band Aerials	£1.75	BP313	A Concise Introduction to Sage	£3.95	BP372	CA-SuperCalc for Windows Explained	£5.95
BP147	An Introduction to 6502 Machine Code	£2.95	BP315	An Introduction to the Electromagnetic Wave	£4.95	BP373	An Introduction to Networks for PC and Mac Users	£5.95
BP148	Computer Terminology Explained	£1.95	BP317	Practical Electronic Timing	£3.95	BP362	Access One Step at a Time	£4.95
BP171	Easy Add-on Projects for Amstrad CPC 464, 664, 6128 and MSX Computers	£2.95	BP320	Electronic Projects for Your PC	£4.95	BP360	A Practical Introduction to Sage Sterling + 2 for Windows	£4.95
BP182	MIDI Projects	£2.95	BP324	The Art of Soldering	£3.95	BP361	Sage Sterling + 2 for Windows Explained	£5.95
BP190	More Advanced Electronic Security Projects	£2.95	BP325	A Concise Users Guide to Windows 3.1	£4.95	BP363	Practical Electronic Music Projects	£4.95
BP192	More Advanced Power Supply Projects	£2.95	BP326	An Introduction to Satellite Communications	£5.95	BP364	A Concise Introduction to Designworks 2	£5.95
BP193	LOGO for Beginners	£2.95	BP327	DOS One Step at a Time (covers Version 6.2)	£3.95	BP385	Easy PC Interfacing	£4.95
BP198	An Introduction to Antenna Theory	O.O.P.	BP328	Sage Explained	£5.95	BP387	Windows One Step at a Time	£4.95
BP245	Digital Audio Projects	£2.95	BP329	Electronic Music Learning Projects	£4.95	BP388	Why Not Personalise Your PC	£4.95
BP246	Musical Applications of the Atari ST's	£5.95	BP330	A Concise User's Guide to Lotus 1-2-3 Release 2.4	£4.95	BP389	Power Point for Windows Explained	£5.95
BP249	More Advanced Test Equipment Construction	£3.50	BP331	A Beginners Guide to MIDI	£4.95	BP400	Windows 95 Explained	£5.95
BP250	Programming in FORTRAN 77	£4.95				BP401	Transistor Data Tables	£5.95
BP251	Computer Hobbyists Handbook	£5.95				BP402	MS Office - One Step at a Time	£5.95
BP258	Learning to Program in C (revised edition)	£4.95						
BP259	A Concise Introduction to UNIX - Revised Edition	£4.95						
BP261	A Concise Introduction to Lotus 1-2-3 (revised edition)	£3.95						

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

PCB SERVICE

Printed circuit boards for certain EPE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to The PCB Service, *Everyday Practical Electronics*, Allen House, East Borough, Wimborne, Dorset BH21 1PF. Cheques should be crossed and made payable to *Everyday Practical Electronics* (Payment in £ sterling only).

NOTE: While 95% of our boards are held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail.

Back numbers or photostats of articles are available if required - see the *Back Issues* page for details.

Please check price and availability in the latest issue.

Boards can only be supplied on a payment with order basis.

Special KNOCK DOWN SALE of PCBs.

We have a few p.c.b.s left from past projects these are being offered at the knock down price of £1.00 each - no matter what size they are (some of these boards are worth over £8.00 each) while stocks last. This price includes VAT and UK post - overseas orders please add 50p postage (or £1 per board for airmail postage).

£1.00
EACH
inc. VAT
and p&p

Doorbell Delay 616; Midi Pedal 639, Midi Merge 640; Audio Lead Tester 641; Power Supply 25V 700mA 656; Hand Tally, main board 699 and display board 700; Automatic Light Control - PSU board 747; Modular Disco Lights - Masterlink 752 - Dimmer Interface 765 - VU Sound Module 767; Knockerbox 775; Auto Nightlight 779; Sonic Continuity Tester, 789; Tie Pulser, 794; Cricket Game, 798; Quick Prom, 799; Emergency Lighting Unit, 816; Car Electric Window Enhancer, 821; Simplify Atari STFM Interface, 822; Personal Stereo Amp. Add-On, 823; Electronic Fire, 820; Mind Machine MkII - Magic Lights, 827; Superhet Radio Control Receiver, 828; Linear Clock - Timing Board 830, Display Board, 831; Universal Alarm Module, 9070; Electronic Snooker Scoreboard, 832; Mind Machine MkII - Computer Interface, 833; Electronic Gong, 835.

Any of the above for just £1 each inc. VAT and p&p.

Back numbers or photostats of articles are available see the *Back Issues* page for details.

PROJECT TITLE	Order Code	Cost
Bike Odometer (pair of boards)	836/7	£7.00
Amstrad PCW A to D Converter (double-sided)	838	£9.85
Experimental Electronic Pipe Descaler	839	£5.50
Sound Activated Camera Trigger	840	£5.34
L.E.D. Sandglass		
Main and Display boards	841/2	£7.30
Kettle Alert	843	£5.19
Linear Power Supply (double-sided)	844	£9.77
Multi-Purpose Audio System		
Six Channel Stereo Mixer	845	£11.98
Multi-Purpose Audio System		
Microphone Pre-Amp module	846	£4.88
RIAA Pre-Amp module	847	£5.11
20 Metre Receiver	848	£6.63
Multi-Purpose Audio System		
Tone Control and 1W Stereo Amplifier	849	£6.09
Tone Control	850	£5.12
1W Stereo Amplifier	851	£4.88
Three-Way Christmas Tree Lights Flasher	853	£5.65
Auto Alarm	854	£5.49
250W/600W Battery to Mains Inverter	855	£13.92
Multi-Purpose Audio System		
10W + 10W Stereo Power Amplifier		
Amplifier	852a	£5.65
Power Supply	852b	£5.49
Pond Heater Thermostat	856	£5.77
Timer/NiCad Capacity Checker	857	£6.30
Multi-Purpose Audio System		
Balanced Microphone Preamplifier	858	£5.30
Balanced Microphone Power Supply	859	£5.14
Whistle Controlled Light Switch	860	£5.19
Battery to Mains Inverter - U.P.S. charger board	862	£7.38
Three Phase Generator		
Visual Doorbell	861	£5.95
CCD TV Camera - Control Board	863	£5.80
(double-sided, plated-through-hole)	865	£15.00
Telephone Ring Detector		
CCD TV Camera	864	£4.72
Combined Video, Test & Ext Plug Boards	866a/e	£11.00
Frame Grab Control (double-sided p.t.h.)	867	£15.00
EPE SoundDAC PC Sound Board	868	£4.77
L.E.D. Matrix Message Display Unit		
Display Board	870	£18.00
CPU Board	871	£7.20
Stereo Noise Gate	873	£6.14
Simple TENS Unit	875	£5.84
Capacitance/Inductance Meter	876	£6.44

PROJECT TITLE	Order Code	Cost
Advanced TENS Unit JUN'94	877	£6.56
Digital Water Meter – Scaler	878	£11.19
Counter/Display	879	pair
L.E.D. Matrix Message Display Unit		
Keypad	872	£5.19
PC Interface	880	£5.82
Microprocessor Smartswitch	881	£5.61
Microcontroller P.I. Treasure Hunter	882	£6.60
Print Timer JULY'94	874	£5.82
Watering Wizard	883	£6.60
Simple NiCad Charger	884	£4.98
Voxbox	885	£6.90
Stereo HiFi Controller – 1 Power Supply	886	£5.66
Stereo HiFi Controller – 2 AUG'94		
Main Board	887	£7.39
Expansion/Display Boards (pair)	888	£9.80
Dancing Fountains – 1 Pre.amp	889	£5.28
Pump Controller	890	£5.41
Filter	891	£5.23
6802 Microprocessor Development Board	894	£9.15
Dancing Fountains – 2 SEPT'94		
PC-Compatible Interface (double-sided)	892	£10.90
Automatic Greenhouse Watering System	895	£5.33
Seismograph – 1 Sensor/Filter	896	£6.23
Clock/Mixer	897	£5.87
3-Channel Lamp Controller	899	£8.17
Seismograph – 2 OCT'94		
PC-Compatible Interface (double-sided)	898	£10.72
Visual/Audio Guitar Tuner	900	£7.55
Digilogue Clock	901	£12.50
Hobby Power Supply	902	£5.00
Audio Auxilexer – Control Board	903	£7.72
Receiver	904	£6.24
Power Controller NOV'94	905	£4.99
1000V/500V Insulation Tester	906	£5.78
Active Guitar Tone Control	907	£4.50
TV Off-er (pair)	908/909	£7.25
Video Modules – 1 Simple Fader	910	£5.12
Improved Fader	911	£6.37
Video Enhancer	912	£5.15
Rodent Repeller DEC'94	913	£6.26
EPE Fruit Machine	914	£8.14
Video Modules – 2 Horizontal Wiper	916	£6.23
Vertical Wiper	917	£6.35
4-Channel Audio Mixer	918	£6.20
Spacewriter Wand	921	£4.00
Universal Digital Code Lock	922	£6.25
Video Modules – 3 JAN'95		
Dynamic Noise Limiter	919	£5.92
System Mains Power Supply	920	£4.98
Magnetic Field Detector	923	£5.77
Model Railway Track Cleaner	924	£5.11
Moving Display Metronome	925	£6.24
The Ultimate Screen Saver FEB'95	927	£5.66
Foot-Operated Drill Controller	928	£5.73
Model Railway Signals	929	£5.96
12V 35W PA Amplifier	930	£12.25
Multi-Purpose Thermostat MAR'95	931	£6.30
Multi-Project PCB	932	£3.00
Sound-Activated Switch		
Audio Amplifier		
Light Beam Communicator (2 boards required)		
Multi-Project PCB APR'95	932	£3.00
Light-Activated Switch		
Switch On/Off Timer		
Continuity Tester		
Auto Battery Charger	934	£5.36
National Lottery Predictor	935	£5.34
R.F. Signal Generator - R.F./Mod. MAY'95	936	£6.48
Coil & Power Supply (pair)	937a/b	£6.10
MIDI Pedal	938	£7.78
Club Vote Totaliser	939	£6.05
PIC-DATS Development System (double-sided p.t.h.)	940	£9.90
EPE HiFi Valve Amplifier – JUNE'95		
Phase splitter	941	£6.71
PIC-DATS 4-channel Light Chaser	942	£7.90
HV Capacitor Reformer JULY'95	943	£5.60
Ramp Generator		
Logic Board (double-sided p.t.h.) & Analogue board (pair)	944/5	£32.00
Automatic Curtain Winder	946	£6.75
Windicator	947	£4.10
Microcontrolled 3-Digit Timer AUG'95	933	£6.61
IR Remote Control – Transmitter	948	£5.76
– Receiver	949	£6.14
Personal Practice Amplifier	950	£6.09

PROJECT TITLE	Order Code	Cost
Low-Range Ohmmeter Adaptor SEPT'95	926	£5.55
Simple Theremin	952	£6.68
Vandata		
Boot Control Unit	953	£10.52
Display Unit	954	£6.61
Sound Switch OCT'95	915	£6.55
Multiple Project PCB	932	£3.00
Audio Sinewave Generator		
Treble Booster		
Infra-Red Controller/Alarm (2 boards required)		
Capacitor Check	955	£5.76
Genomous VU Meter	956	£9.31
Multiple Project PCB NOV'95	932	£3.00
Video Enhancer		
Current Tracer		
Distortion Effects Unit		
Digital Delay Line	958	£8.04
50Hz Field Meter	959	£8.32
Temperature Warning Alarm (Teach-In '96)	960	£6.15
Stereo "Cordless" Headphones DEC'95		
Transmitter	961	£8.04
Receiver	962	£7.66
EPE Met Office – Sensor/Rainfall/Vane	963/965	£11.33
Spiral transparency free with above p.c.b.		
Light-Operated Switch	966	£6.37
Modular Alarm System (Teach-In '96)	967a/b	£7.12
Audio Meter and Amplifier	968	£5.99
EPE Met Office – JAN'96		
Computer Interface (double-sided)	964	£7.69
Audio Signal Generator	969	£6.58
Mains Signalling Unit, Transmitter and Receiver	970/971 (pr)	£9.09
Automatic Camera Panning (Teach-In '96)	972	£6.63
Printer Sharer	973	£9.93
Analogue Frequency Meter FEB'96	957	£6.70
Vari-Speed Dice (Teach-In '96)	974	£5.69
Mains Signalling Unit – 2		
12V Capacitive PSU	975	£6.07
PIC-Electric Meter – Sensor/PSU– Control/Display	977/978 (pr)	£9.90
Multi-Purpose Mini Amplifier MAR'96	976	£6.12
PIC-Electric – Sensor/PSU – Control/Display	977/978 (pr)	£9.90
High Current Stabilised Power Supply	979	£6.62
Mind Machine Mk III – Sound and Lights	980	£7.39
Infra-Zapper Transmitter/Receiver (Teach-In '96)	981/982 (pr)	£8.01
Mind Machine Mk III – Programmer APRIL'96	983	£7.36
Bat Band Converter/B.F.O.	984a/b	£5.80
Hearing Tester	985	£6.87
Event Counter (Teach-In '96)	986	£8.39
B.F.O. and Bat Band Converter MAY'96	984a/b	£5.80
Versatile PIR Detector Alarm	988	£6.76
Mind machine Mk III – Tape Controller	989	£6.70
Midi Analyser	992	£6.74
Countdown Timer (Teach-In '96)	993	£9.44

EPE PRINTED CIRCUIT BOARD SERVICE

Order Code Project Quantity Price

Name.....

Address.....

I enclose payment of £..... (cheque/PO in £ sterling only) to:


 **Everyday Practical Electronics** 
Access (MasterCard) or Visa No.
Minimum order for credit cards £5

Signature..... Card Exp. Date.....

Please supply name and address of cardholder if different from the address shown

REPORTING AMATEUR RADIO

Tony Smith G4FAI

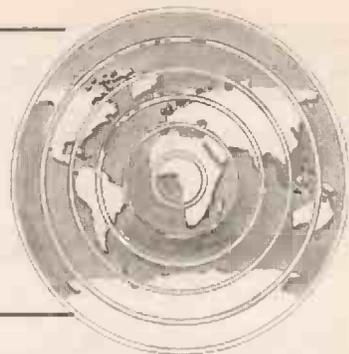

FREQUENCY CLASH

The Radio Society of Great Britain has issued a statement about the possibility of a clash between a number of services sharing the same frequency allocation and radio operated remote controlled car keys, which have been allocated a frequency of 433.92MHz throughout Europe. This frequency lies within a band allocated to UK Government services as primary users, which is also allocated to licensed radio amateurs on a secondary basis.

A clash can occur, says the RSGB, because designers of vehicle security systems do not appear to have taken sufficient account of the fact that the frequency allocated to vehicle radio keys is on a "secondary unprotected" basis. This means that users of such devices may suffer interference from other authorised radio users.

Vehicle immobilisers which set themselves automatically, and can only be turned off by using a radio key, are a recent development and are likely to suffer problems in certain locations where the radio key cannot be used, and the vehicle has to be towed away.

Although such problems may be caused by licensed amateur radio transmitters, they have also been reported to have been caused by non-amateur transmissions in locations such as Portsmouth Harbour, Crystal Palace and Fylingdales.

The RSGB observes that blocking of radio operated keys would be much less likely if designers took the following steps. It has put all of these points to the Radiocommunications Agency:

Use better quality receivers as some types cannot distinguish between the wanted signal from the key and signals from other sources on nearby frequencies.

Use radio keys that transmit higher power. Those currently in use typically only transmit a hundredth of the maximum power they are allowed to use.

Put the receiving aerial inside the car window instead of burying it inside the car's wiring harness. This would allow the driver to hold the key right next to the aerial if necessary.

An alternative frequency allocation for radio operated vehicle keys would be welcomed by the RSGB, but by far the best solution to the problem would be to use infra-red keys instead of radio operated keys.

BAND STATUS

Although amateur bands are allocated on a primary or a secondary basis, amateur stations themselves, apart from beacons and repeaters, have no protection from undue interference from other authorised services.

Additionally, amateur stations using frequencies allocated on a secondary basis must not cause undue interference to other stations of a primary or permitted service to which frequencies have been assigned.

However, the "secondary unprotected" basis of the frequency allocated for vehicle radio keys means that radio amateurs are under no obligation to avoid that frequency. It is the responsibility of manufacturers to ensure that their products cannot be adversely affected by interference from other radio sources.

RSGB SURVEY

By the time this appears in print, the RSGB's planned survey of all radio amateurs and other interested parties, may have been announced. As reported previously, its purpose is to obtain the views of all concerned (not just RSGB members) on the future qualifications and licensing structure of the UK Amateur Service.

At the same time, the International Amateur Radio Union's "Future of the Amateur Service ad-hoc Committee" (FASC), is looking at the international regulations to decide what changes, if any, are needed to take amateur radio into the next century.

The RSGB's survey is being organised by its Licensing Advisory Committee. According to the committee's chairman, Ian Suart GM4AUP, the information obtained will allow the RSGB to be well briefed on UK opinion in time for the IARU Region 1 conference in Tel Aviv later this year.

ONLY OPPORTUNITY

The RSGB survey is vitally important. It could result in fundamental changes, altering the image of amateur radio for ever. After years of controversy, it offers an opportunity to finally establish the views of the UK amateur community on the future structure of the hobby.

Discussions will continue round the world over the next three years, and decisions will finally be taken at the ITU *World Radio Conference* in 1999.

Because of the IARU 3-year regional conference cycle, however, discussion and input from Region 1, which includes the UK, must take place this year.

MILLENNIUM COMMITTEE

Yet another consultative process has been announced by Peter Sheppard G4EJP, RSGB President for 1996, whose presidential theme is "consultation."

Whilst the core activities of the Society will remain unchanged, he feels that new developments such as computers, data, the Internet, novice operation, the trend to use commercial equipment and the imminent *Phase 3D* satellite launch, will all

have a bearing on the everyday activities of the Society and its members.

He has formed a Millennium Committee "with the objective of laying the groundwork for the Society during the period 1996 to 2000 and beyond." RSGB members who feel strongly about any matter relating to amateur radio have been invited to submit their views.

It will be interesting to see the results of both the survey and the conclusions of the Millennium Committee. Much revolves around the use of computers in radio communication. Some amateurs see the future linked more and more with computing, and argue that today's computer enthusiasts represent a vast source of recruitment to amateur radio, particularly if the entrance requirements can be relaxed.

Others see that route as detrimental. They forecast that amateur radio could eventually become just a branch of computing, and that the hobby as they know it today, with its many varied activities, would be lost forever.

ROLE OF THE IARU

In all these discussions, the International Amateur Radio Union has a vital role to play in formulating the future pattern of amateur radio.

The IARU is a worldwide association of national radio societies, with its secretariat located at the ARRL HQ in the United States, and is subdivided into three Regions.

Region 1, of which the UK is a member, covers Europe, Africa, the Middle East and the C.I.S., and has a membership of over 70 countries. *Region 2* covers North and South America, while *Region 3* covers Australasia and most of Asia.

Each Region holds a conference once every three years. The next *Region 1* conference will be later this year, and the other Regions will meet over the following two years. So by 1998 all Regions will have considered and discussed the FASC proposals ready for the *World Radio Conference* in 1999.

The IARU cannot attend WRCs by right, only by invitation. However, the ITU does recognize the interest of the IARU in any proposed change to the regulations affecting amateur radio. That was why *WRC-95* decided to defer until 1999 the proposal by New Zealand to abolish the amateur Morse test.

This delay gives the IARU time to consult all member societies and decide on its position before the proposal is debated. It wants the discussion at *WRC-99* to extend beyond the Morse issue, to cover all regulatory aspects of amateur radio. That is why it is so important for all amateurs to express their views in the forthcoming consultation exercises.

BTEC
Certificated



TUTOR
Supported

NATIONAL
COLLEGE OF
TECHNOLOGY

DISTANCE LEARNING COURSES

The National College of Technology offer a range of packaged learning short courses for study at home or in an industrial training environment which carry modular BTEC awards leading to a higher BTEC certificate. Study can commence at any time and at any level enabling you to create a study routine to fit around existing commitments. Courses on offer include:

- Analogue Electronics
- Digital Electronics
- Fibre/Optoelectronics
- Mechanics & Mechanisms
- Programmable Logic Controllers
- Electronic Testing & Fault Diagnosis

Tutor support and BTEC certification are available as options with no travelling or college attendance required. These very popular courses which are ideal for vocational training contain workbooks, audio cassette lectures, PCB's, instruments, tools, components and leads as necessary to support the theoretical and practical training. Whether you are a newcomer to electronics or have some experience and simply need an update or certification, there is probably a distance learning course ready for you. Write or telephone for details to:

National College of Technology
NCT Ltd., PO Box 11
Wendover, Bucks
Tel: (01296) 624270

JCG ELECTRONIC PROJECTS

PO BOX HP79 WOODHOUSE STREET HEADINGLEY LEEDS LS6 3XN

KITS

RADIO KITS/TRANSMITTERS/ REMOTE CONTROL

- MICRO FM (a). 1km range transmitter, 80-100MHz preset. Received on any FM Radio. 2 x 3cm. £6.95
- MICRO FM (b). Variable mic. sensitivity. Tuneable 80-110MHz. 1km range, 2 x 3-5cm £7.95
- ULTRA MINI FM. 200mtrs range. 80-100MHz, runs off watch battery (inc.), only 1 x 2cm £8.95
- FM TRACKER. Transmits a constant tone for direction finding, tracking etc. 80-110MHz £8.95
- FM RECEIVER (a). Small high quality FM receiver. Covers standard FM broadcast bands. Will drive headphones (not inc.) £10.90
- FM RECEIVER (b). As (a) but with 3 watt audio power amplifier and tuning LED £13.50
- CRYSTAL RADIO. Great introduction to radio electronics. Includes tuner, ferrite aerial and earphone £8.50
- AM RADIO. Single chip radio for use with headphones, (not inc.) or an external amplifier £9.90
- I.R. REMOTE CONTROL. Single channel for lights, garage doors etc. Transmitter - £6.95
Receiver (with mains relay) - £12.20
- 27MHz RADIO CONTROL
Single channel, XTAL controlled Transmitter - £9.50
Receiver (with mains relay) - £15.45

**SEND STAMP
FOR LATEST
CATALOGUE**

- ★ KITS
- ★ SURVEILLANCE
- ★ SECURITY
- ★ AUDIO
- ★ RADIO


MICRO TRANSMITTERS GUIDE

★ Only £3.95

★ Easy to follow guide to building short range F.M.

transmitters and surveillance devices. Packed with useful information and circuits.

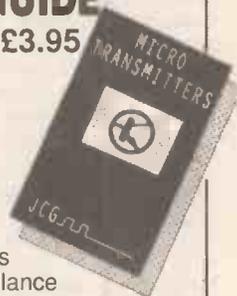(Some of the circuits included cannot be used legally in the UK)



ALL KITS COME COMPLETE WITH PRE-DRILLED P.C.B.'s, HIGH SPEC COMPONENTS AND FULL INSTRUCTIONS - MAIL ORDER ONLY - MAKE CHEQUES/PO'S PAYABLE TO J.C.G. PLEASE ADD 50p POSTAGE AND PACKING.

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX ★ 0131 667 2611

The supplier to use if you're looking for:-

★ A WIDE RANGE OF
COMPONENTS AIMED
AT THE
HOBBYIST

★ COMPETITIVE
VAT INCLUSIVE
PRICES ★

★ MAIL ORDER - generally by
RETURN OF POST ★

★ FRIENDLY SERVICE ★

1995/6 CATALOGUE NOW IN STOCK!
COST: £2.00. Includes vouchers to offset
against future purchases.

OPEN: Monday-Thursday 9.15 - 6.00.

Friday 9.15-5.00

Saturday 9.30-5.00

VISA

FREE CATALOGUE

THINK COMPONENTS - THINK CRICKLEWOOD

- TELEVISION & VIDEO SPARES ● RESISTORS & CAPACITORS ● HI-FI GADGETS & SPEAKERS
- TRANSISTORS & I.C.'s ● AUDIOPHILE CAPACITORS
- IN CAR AUDIO ● COMPUTER BOARDS ● TOOLS & TEST EQUIPMENT ● PLUGS SOCKETS & LEADS



PLEASE SEND ME A COPY OF THE CRICKLEWOOD CATALOGUE.

Name.....

Address.....

EPE

PRICES HELD INTO 1996

Cricklewood Electronics Ltd, 40-42 Cricklewood Broadway,
London NW2 3ET. Tel: 0181-450 0995 Fax: 0181-208 1441

EVERYDAY**CLASSIFIED****PRACTICAL**

ELECTRONICS

Everyday Practical Electronics reaches nearly twice as many UK readers as any other independent monthly hobby electronics magazine, our audited sales figures prove it. We have been the leading independent monthly magazine in this market for the last eleven years.

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Practical Electronics. VAT must be added. Advertisements, together with remittance, should be sent to Everyday Practical Electronics Advertisements, Holland Wood House, Church Lane, Great Holland, Essex CO13 0JS. Phone/Fax (01255) 850596.

For rates and information on display and classified advertising please contact our Advertisement Manager, Peter Mew as above.

RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY
Up to 38 volts d.c. at 6 amps continuous, 10 amps peak, fully variable from 1 to 38 volts. Twin Voltage and Current meters for easy read-out. 240 volt a.c. input. Fully smoothed, size 14½ x 11 x 4½ inches.

£96 inc. VAT
carriage £6

RADIO COMPONENT SPECIALISTS
337 WHITEHORSE ROAD, CROYDON
SURREY, CR0 2HS. Tel: 0181-684 1665

Lots of transformers, high volt caps, valves, speakers, in stock
Phone or send your wants list for quote

SMOKE MACHINES
The World's smallest fog machine takes standard distilled water based smoke fluid - top quality at direct from the manufacturer prices - perfect for mobiles, as it only consumes 200W, and as a backup for larger venues only £138 including VAT, postage and packing, comes with fluid and fitted plug.

We also service and recondition most other makes of smoke machines at very competitive rates, and all service work carries a one years guarantee.

Direct from: Associated Consultant Engineers,
The Blue Bell, Wrangle Bank, Nr. Boston,
Lincs PE22 9DL.

THE BRITISH AMATEUR ELECTRONICS CLUB
exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter.

For membership details, write to the Secretary:
Mr. J. F. Davies, 70 Ash Road, Cuddington,
Northwich, Cheshire CW8 2PB.

Space donated by Everyday Practical Electronics

THE PARALLEL INTERFACE POWER CARD by HANDDI Ltd for complete COMPUTER CONTROL.
This could be your most useful and cheapest computer/PC "add-on" at only £19.95 ... Post FREE!
Drives robotics, motor speeds, stepper motors, lamps, relays etc. using its 8 x 20V/2A outputs.
Many sold already for successful Model Railway Layout control ... FULL INSTRUCTIONS supplied!
Send cheque for £19.95 OR S.A.E. for details to:-
HANDDI Ltd. P.O. 503, Milton Keynes, MK5 6JD.

BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING
THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME
O.N.C., O.N.D. and H.N.C.
Next course commences
Monday 22nd April 1996
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE
(Dept EPE) 20 PENYWERN ROAD
EARLS COURT, LONDON SW5 9SU
TEL: 0171-373 8721

FIRST ON THE WEB
with over 300 kits: lasers, night vision, µC teaching, PIC programmers, CCD cameras, UHF remote control, FM bugs, amplifiers, Peltier modules.
See our web page at:
<http://www.hk.super.net/~diykit>
Use your old PC as a dedicated controller. Plug in our relay board into the parallel port. Eight relays on board. Comes complete with two software packages (DOS & W3.1) and all components. Kit 74. £19.25 airmail post inc. Just send your cheque to:

DIY ELECTRONICS
PO Box 88458, Sham Shui Po, Hong Kong

PC ELECTRONIC AND TECHNICAL PROGRAMS
LOW COST SPECIALIST LIBRARY
GOOD QUALITY PROGRAMS THAT WORK.
Descriptive catalogue available priced at £2.50. Comes with £2.00 off money voucher to place against your first order.

Phone/Fax for your catalogue from
PDSL, Winscombe House, Beacon Road,
Crowborough, East Sussex TN6 1UL
Tel: 01892 663298 Fax: 01892 667473

SAVE OVER £5 - SUBSCRIBE NOW!

EVERYDAY PRACTICAL ELECTRONICS

SUBSCRIPTION ORDER FORM
Annual subscription rates (1996):
UK £24.00.
Overseas £30.00 surface mail, £47.50 airmail.
To:
Everyday Practical Electronics,
Allen House, East Borough,
Wimborne,
Dorset BH21 1PF
Tel: 01202 881749
Fax: 01202 841692

Name

Address

I enclose payment of £.....

(cheque/PO in £ sterling only, payable to Everyday Practical Electronics). Alternatively send Access or Visa number and card expiry date.

Signature

Please supply name and address of cardholder if different from the subscription address shown above. Subscriptions can only start with the next available issue. For back numbers see the Back Issues page.

M5/96

Miscellaneous

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Hove, Sussex BN3 8GR, or phone Brighton 883871.

G.C.S.E. ELECTRONICS KITS, at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT Electronics, 70 Oxford Road, Clacton, CO15 3TE.

PLDs AND EPROMS copied or programmed. We supply logic devices/convert discrete logic to PLDs. Also PCBs designed. Send for details to PO Box 1561 Bath (01225 444467).

VALVE ENTHUSIASTS: Capacitors and other parts in stock. For free advice/lists please ring, Geoff Davies (Radio), Tel: 01788 574774.

PRINTED CIRCUIT BOARDS - QUICK SERVICE. Prototype and Production. Artwork raised from magazines or draft designs at low cost. PCB's also designed from schematics. Production assembly also undertaken. For details send to P. Agar, 36 Woodcot Avenue, Belfast, BT5 5JA or phone 01232 473533 (7 days).

HIGH VOLTAGE DC-DC CONVERTERS, PCB Mounting, 12/24 volt input. Fully encapsulated, ideal for GEIGER, PHOTOMULTIPLIER and ION MOTOR experiments. 2kV Unit £19.00 each or 10kV Unit £49.00 each. Quantity discounts available direct from manufacturer. S.A.E. for further information to:- P.P.S., 33B Rowlands Road, Worthing, W. Sussex, BN11 3JJ. 01903 214100.

100 WATT AMPLIFIER MODULES, £8.95; 3 Heatsinks ± 50V D.C. ex-equip; 12-40V slider P.S.U.'s, £5.00. K.I.A., 1 Regent Road, Ilkely.

WANTED - D.A.T. Digest 1993, 1994 or 1995, E/EPROMs volume. George (0161) 962 7103.

CIRCUIT AND ARTWORK DESIGN SERVICE. Printed Circuit Board manufacture, one offs and quantities. Production assembly and repair service also undertaken. Please contact Darren Smith, S.B. Electronics, 24 Broxton Ave., Orrell, Wigan, Lancs, WN5 8NP or Tel/Fax (01942) 221025.

PCBS AND FOIL TRANSPARENCIES from photocopies or printouts. Low cost. SAE for details: Williams, 29 Albert Road, Mexborough, S. Yorks S64 9BZ.

EPROM PROGRAMMER FOR THE BBC COMPUTER WANTED. American company is looking for new or used memory IC programmer for the BBC computer. Model EPROMER II. Brand TECHNOMATIC preferred or alternative. Contact Anatoly by phone: +1 860 529-8643, fax: +1 860 529-1895, e-mail: anatoly@kahn.com or mail to Kahn Instruments, Inc., 885 Wells Road, Wethersfield, CT 06109 U.S.A.

TRAIN TODAY FOR A BETTER FUTURE

Now you can get the skills and qualifications you need for career success with an ICS Home Study Course. Learn in the comfort of your own home at the pace and times that suit you. ICS is the world's largest, most experienced home study school. Over the past 100 years ICS have helped nearly 10 million people to improve their job prospects. Find out how we can help YOU. Post or phone today for FREE INFORMATION on the course of your choice.

Electrical Contracting
Electrical Engineering
C & G Basic Electronics
C & G Basic Mechanics
TV, Video & Hi-Fi Servicing
Refrigeration & Air Conditioning
PC Repair
Electronic Engineering

Call 0141 306 1195

Please send me my Free Information on your Electronics Courses.

Mr/Mrs/Ms/Miss (BLOCK CAPITALS PLEASE) _____ Date of Birth / / _____
Address _____
Postcode _____
Occupation _____ Tel. No. _____

ICS International Correspondence Schools, Dept ZEEAE. FREEPOST 882, 8 Elliot Place, Clyde Way Centre, Glasgow, G3 8BR. Tel. 0141 306 1195 (9am-7pm) or Tel/Fax: Ireland 01 285 2533. Further offers, which may be of interest, may be sent to you by ICS or other carefully selected companies.

VISA



Cooke International

SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS, GENERATORS, OSCILLOSCOPES, POWER METERS, ETC. ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND FOR LISTS OF EQUIPMENT & MANUALS

ALL PRICES EXCLUDE VAT AND CARRIAGE

DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM-5PM

Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis, West Sussex, PO22 0EB

Tel (+ 44) 01243 545111/2 Fax (+ 44) 01243 542457

EQUIPMENT & ACCESSORIES PURCHASED

SERVICE MANUALS & Technical Books

Available for most equipment, any make, age or model.

Return the coupon for your FREE catalogue

MAURITRON TECHNICAL SERVICES (EPE)

8 Cherry Tree Road, Chinnor, Oxon, OX9 4QY.

Tel:- 01844-351694. Fax:- 01844 352554.

Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps or £4.11 inc VAT for the Service Manuals Index on PC Disc plus catalogue.

NAME _____

ADDRESS _____

POSTCODE _____

Photocopy this coupon if you do not wish to cut the magazine

N. R. BARDWELL LTD (EPE)

200	Signal diodes 1N4148.....	£1.00
75	Rectifier Diodes 1N4001.....	£1.00
50	Rectifier Diodes 1N4007.....	£1.00
10	W02 Bridge Rectifiers.....	£1.00
5	NE555 Timer I.C.s.....	£1.00
50	Assid. Zener Diodes.....	£1.00
30	BC212L Transistors.....	£1.00
30	BC213L Transistors.....	£1.00
30	BC214C Transistors.....	£1.00
30	BC237 Transistors.....	£1.00
20	BC327 Transistors.....	£1.00
30	BC339 Transistors.....	£1.00
30	BC339 Transistors.....	£1.00
30	BC478 Transistors.....	£1.00
30	BC546 Transistors.....	£1.00
30	BC547 Transistors.....	£1.00
30	BC548 Transistors.....	£1.00
30	BC549 Transistors.....	£1.00
25	BC557 Transistors.....	£1.00
30	BC558 Transistors.....	£1.00
30	BC559 Transistors.....	£1.00
25	BC640 Transistors.....	£1.00
30	MPSA42 Transistors.....	£1.00
30	MPSA32 Transistors.....	£1.00
20	2N3702 Transistors.....	£1.00
20	2N3904 Transistors.....	£1.00
5	78L12 12V 100mA Pos Regulators.....	£1.00
10	79M08 8V 500mA Neg Regulators.....	£1.00
25	5mm red l.e.d.s.....	£1.00
25	3mm red l.e.d.s.....	£1.00
25	Assid. high brightness l.e.d.s.....	£1.00
50	Axial l.e.d.s (Diode package).....	£1.00
12	Asstd. 7-segment displays.....	£1.00
2	ORP12 light dependant resistors.....	£1.00
30	Asstd. IF transformers.....	£1.00
48	Asstd. coil formers.....	£1.00
100	Asstd. RF chokes (Inductors).....	£1.00
30	Asstd. connectors edge,d.i.l., sil etc.....	£1.00
30	Asstd. d.i.l. sockets up to 40-pin.....	£1.00
200	Asstd. disc ceramic capacitors.....	£1.00
80	Asstd. capacitors 1nF to 1µF.....	£1.00
80	Asstd electrolytic capacitors.....	£1.00
10	4P3W MBB min. rotary switches.....	£1.00
20	Min. SP/CO slide switches.....	£1.00
20	1" glass reed switches.....	£1.00
200	4N7 mini axial capacitors.....	£1.00
24	24-pin d.i.l. wire wrap i.c. skts.....	£1.00
1	12V motorised volume control 50k.....	£1.00
50	Grommets 6.3mm id, 9.5mm od.....	£1.00
100	of 1/4W 5% resistors any one value, E24, range 1R to 10M.....	£0.45

Prices include VAT, postage £1.25. Stamp for Lists

288 Abbeydale Road, Sheffield S7 1FL

Phone (0114) 2552886 Fax (0114) 2500689

INFOTECH & STREE

76 Church St, Larkhall, Lanarks, ML9 1HE
Phone (01698) 883334/888343 or Fax (01698) 884825

Remember: Not only do we have every sheet ever produced, but we also have

The World's Largest Collection of SERVICE MANUALS & CIRCUITS

We are now successfully running a Library Service which allows you to borrow any manual you want for as long as you want, and when you need another manual, just return the one you have, plus a £4.95 exchange fee and tell us what you want next.

Borrow any Service Manual for £4.95 regardless of its size or normal cost

The cost of this service is a yearly subscription fee of only £59.95. Join now & get a free 'Data Ref Guide'.

3lb mixed component pack.....	£4.95
Jumbo component pack.....	£10
250 off mixed capacitors.....	£4.95
250 off i.c. sockets.....	£3.95
1000 off mixed ceramic caps.....	£7.50
20 off mixed crystals/filters.....	£4.95
25 off mixed relays.....	£3.50
100 off phono plugs.....	£2.95*
10 off mixed displays.....	£3.75*
50 off d.i.l. switches.....	£3.75*
30 off mixed heatsinks.....	£3.75*
30 off mixed switches.....	£3.75*
Brand new 360k 5 1/4" floppy drive.....	£4.50
5 1/4" to 3 1/2" floppy drive converter leads.....	£1.50*
50/1 BNC to BNC lead.....	£1.75
2 phono plug to 2 phono plug lead.....	£1.50*
21-Pin SCART plug to SCART plug lead (all connected).....	£3.50*
As above but plug to socket.....	£3.50*
SCART plug to 4 phone plug lead.....	£2.95
10 off crocodile clip leads.....	£3.50*

Universal Test Lead Kit..... £3.75*

VALVES

QQV0310, £10*; QQV0320A, £10*;
QQV0640A, £20*; ECC82, £3*;
ECH81, £2*; PCL805, £3*;
ORP 11, £3; ORP 40, £3; CV 4004,
4005, 4006, 4007, 4014, 4020,
4024, 4043, 4055, 4064, 5042,
5080, ALL £5 each*

QUANTITY DISCOUNTS AVAILABLE PLEASE RING.

We also buy all forms of electronic components, p.s.u.'s, disk drives etc. Lists to below address.

ALL PRICES INCLUDE V.A.T. PLEASE ADD £2.00 p&p EXCEPT ITEMS MARKED * WHICH ARE 50P. SAE FOR BULK BUYING LIST PAYMENT WITH ORDER TO: Dept EE, COMPELEC, 14 Constable Road, St. Ives, Huntingdon, Cambs PE17 6EQ Tel/Fax: 01480 300819

NEW MINI CAMERA and SPECIAL OFFERS

NEW - Mini Waterproof TV Camera, 40 x 40 x 15mm, requires 10V to 16V at 120mA x 240V AC. (SCART plug) It has a high resolution of 450 TV lines vertical and 380 TV lines horizontal, electronic auto iris for nearly dark (1 LUX) to bright sunlight operation and a pinhole lens with a 92 degree field of view, it focuses down to a few CM. It is fitted with a 3-wire lead (12V in gnd and video out), £93.57 + VAT = £109.95 or 10 + £89.32 + VAT = £124.95

High quality Stepping Motor Kits (all including stepping motors) Complete independent control of two stepping motors by PC (via the Parallel Port) with two motors and software..... Kit £67.00; Built £99.00

Software support and 4-digital inputs kit..... £27.00

Power Interfaces: 4A kit £35.00, 5A kit, £45.00

Stepper kit 4 (manual control) Includes 200 step stepping motor and control circuit..... £23.00

Hand Held Transistor Analyser. It tells you which lead is the base, the collector and emitter and it is NPW or PNP or faulty. £33.45. Spare 6V battery £1.20

LEDs: 3mm or 5mm Red or Green 7p each. Yellow 11p each.

Cable Ties 1p each, £5.95 per 1000, £49.50 per 10,000.

RECHARGEABLE BATTERIES

AA (HP7) 500mAh..... £0.99

AA 700mAh..... £1.75

C 2AH with solder tags..... £3.60

D 4AH with solder tags..... £4.95

1/2AA with solder tags..... £1.55

AAA (HP 16) 180mAh..... £1.75

AA 500mAh with solder tags..... £1.55

C (HP11) 1.2AH..... £2.20

D (HP2) 1.2AH..... £2.60

PP3 8.4V 110mAh..... £4.95

Sub C with solder tags..... £2.50

1/3 AA with tags (Philips CTV)..... £1.95

Standard Charger, charges 4 AA cells in 5 hours or 4 Cs or Ds in 12 to 14 hours, plus 1xPP3 (1, 2, 3 or 4 cells may be charged at a time)..... £5.95

High Power Charger, as above but charges the Cs and Ds in 5 hours; AAs, Cs and Ds must be charged in two or four..... £10.95

Nickel Metal Hydroxide AA cells, high capacity with no memory. If charged at 100mA and discharged at 250mA or less 1100mAh capacity (lower capacity for high discharge rates)..... £3.75

SPECIAL OFFERS - PLEASE CHECK FOR AVAILABILITY

Stick of 4, 42mm x 16mm NiCd batteries, 171mm x 16mm dia., with red and black leads, 4.8V..... £5.95

Five button cell, 6V 280mAh battery with wires (Varta 5 x 250D)..... £2.45

Shaded-pole motor, 240V a.c. 5mm x 20mm shaft, 80mm x 60mm x 35mm, excluding the shaft..... £4.95

115V a.c. 80V d.c. motor, 4mm x 22mm shaft, 50mm dia. x 60mm long body (excluding the shaft) it has a replaceable thermal fuse and brushes..... £4.94 each, £3.95 100 +

7-Segment, common anode, l.e.d. display, 12mm, 45p LM337K, TO3 case, Variable regulator, £1.95, 100 + £1.44 GaAs F.E.T. low leakage current 58873..... £1.95 each, £9.95 10 +, £7.95 100 +

BS250 p-channel MOSFET..... 45p

BC559 transistor..... £3.95 per 100

BC547A transistor..... 20 for £1.00

74LS05 Hex inverter..... £10.00 per 100

Used 8748 Microcontroller..... £3.50

SL952 UHF Limiting amplifier, LC 16 surface mounting package with data sheet..... £1.95

AM27502..... £1.25 each, 90p 100 +

CD4007UB..... 10p 100 +, 6p 1000 +

Sinclair Light Gun, terminated with a jack plug and PP3 clip, gives a signal when pointed at 50Hz flickering light, with output waveform chart..... £3.95

DC-DC Converter, Reliability model V12P5, 12V in, 5V 200mA out, 300V input-to-output isolation, with data sheet..... £4.95 each or pack of 10 £39.50

Hour Counter used 7 digit 240V a.c. 50Hz..... £1.45

QWERTY keyboard, 58-key, good quality switches, new..... £5.00

Airfax AB2003 C large stepping motor 14V 7.5" step, 27 ohm, 6mm dia. body, 6.3mm shaft..... £8.95 or £200 for a box of 30

Polyester capacitors, box type, 22.5mm lead pitch 0.5µF 250V d.c. 18p each, 14p 100 +, 9p 1000 +

1µF 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000 +

0.22µF 250V polyester axial leads, 15p each, 100 + 7.5p each

Polypropylene 1µF 400V d.c. (Wima MKP10) 27.5mm pitch, 32mm x 29mm x 17mm case, 75p each, 60p 100 +

Philips 125 series solid aluminium axial leads, 33µF 10V and 22µF 40V 40p each, 25p 100 +

Philips 10B series, long life, 22µF 63V axial..... 30p each, 15p 1000 +

Multilayer AVX ceramic capacitors, all 5mm pitch, 100V 100pF, 150pF, 220pF, 10,000pF (10n) 10p each, 5p 100 +, 3.5p 1000 +

500pF compression trimmer capacitor..... 50p

40µF 370V a.c. motor start capacitor (dielectric type containing no p.c.b.s.)..... £5.95 or £49.50 for 10

Solid carbon resistors, very low inductance, ideal for r.f. circuits, 27 ohm 2W, 68 ohm 2W 50p each, 15p each 100 +

We have a range of 0.25W, 0.5W, 1W and 2W solid carbon resistors - please send SAE for list

P.C. 400W PSU (Intel part 201035-001) with standard motherboard and five disk drive connectors, fan and mains input/output connectors on back and switch on the side (top for lower case) dims. 212mm x 148mm x 148mm excluding switch, £26.00 each, £138.00 for 6

MX180 Digital Multimeter 17 ranges, 1000V d.c. 750V a.c., 2Megohm 200mA transistor He 9V and 1.5V battery test..... £9.95

AMB 2725-3 EPROMs £2.00 each, £1.25 100 + unless otherwise stated

Inmac deluxe anti-glare static control panel, window size 226mm x 161mm, overall size 264mm x 200mm, held to the monitor with hook and loop tape pads..... £7.95 each

DIP switch 3PCD 12-pin (ERG SDC-3-023) 60p each, 40p 100 +

Disk Drive Boxes for a 5.25 disk drive, with room for a power supply, light-grey plastic 67mm x 268mm x 247mm £7.95 or £49.50 for 10

Handheld Ultrasonic Remote Control..... £3.95

CV2486 Gas Relay 30mA x 10mm dia. with 3-wire terminals, will also work as a neon light..... 20p each, or £7.50 per 100

All products advertised are new and unused unless otherwise stated

Wide range of CMOS TTL 74HC74F Linear, Transistors rechargeable batteries, capacitors, tools etc. always in stock

Please add £1.95 towards P&P, VAT included in all prices

JPG ELECTRONICS

276-278 Chatsworth Road
Chesterfield S40 2BH

Access Visa Orders:

Tel: (01246) 211202 Fax: (01246) 550959

Callers welcome 9.30am to 5.30pm
Monday to Saturday

Mixed metal/carbon film resistors 1/2W E12 series 10 ohms to 1 Megohm	2p
Carbon Film resistors 1/4W 5% E24 series 0.51 R to 10MO	1p
100 off per value - 75p. even hundreds per value totalling 1000	£6.00p
Metal Film resistors 1/4W 10R to 1 MO 5% E12 series - 1/2p. 1% E24 series	2p
Mixed metal/carbon film resistors 1/2W E24 series 1R0 to 10MO	1 1/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 2M2 E6 series	7p
Miniature polyester capacitors 250V working for vertical mounting	
015, .022, .033, .047, .068 - 4p. 0.1 - 5p. 0.12, 0.15, 0.22 - 6p. 0.47 - 8p. 1.0 - 12p	
Mylar (polyester) capacitors 100V working E12 series vertical mounting	
1000p - 3p. .01 to .068 - 4p. 0.1 - 5p. 0.12, 0.15, 0.22 - 6p. 0.47/50V - 8p	
Submin ceramic plate capacitors 100V wkg vertical mountings. E12 series	
2% 1.8pf to 47pf - 3p. 2% 56pf to 330pf - 4p. 10% 39p-4700p	4p
Disc/plate ceramics 50V E12 series 1PC to 1000P, E6 Series 1500P to 47000P	2p
Polystyrene capacitors 63V working E12 series long axial wires	
10pf to 820pf - 5p. 1000pf to 10,000pf - 6p. 12,000pf	7p
741 Op Amp - 20p. 555 Timer - 20p. LM3900	80p
CMOS 4001 - 20p. 4011 - 22p. 4017 - 40p. 4069UB unbuffered	20p
DIL holders, 8-pin 9p. 14-, 16-, 18-pin 12p; 24-pin 18p; 28-pin 20p; 40-pin 25p.	
ALUMINIUM ELECTROLYTICS (Mids/Volts)	
1/50, 2/250, 4/750, 10/25, 10/50	5p
22/16, 22/25, 22/50, 33/16, 47/16, 47/25, 47/50	6p
100/16, 100/25 7p; 100/50	12p
220/16 8p; 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
Subminiature, tantalum bead electrolytics (Mids/Volts)	
0.1, 0.22, 0.47, 1.0, 2.2, 3.3 @ 35V - 4.7/16, 6.8/10, 10/6, 10p; 6.8/35, 12p.	
4.7/25, 6.8/16, 10/6, 11p; 15/16, 22/6, 33/10, 15p; 10/25, 16p; 10/35, 22/16, 20p.	
47/10, 20p; 47/16, 25p; 47/20, 30p; 47/35, 32p; 100/3, 18p; 100/6, 22/6, 20p.	
VOLTAGE REGULATORS	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V - 55p. 100mA. 5.8, 12, 15, V +	30p
DIODES (piv/amps)	
75/25mA 1N4148 2p. 800/1A 1N4006 4 1/2p. 400/3A 1N5404 14p. 115/15mA OA91	8p
100/1A 1N4002 3 1/2p. 1000/1A 1N4007 5p. 60/1.5A SIM1 5p. 100/1A bridge	25p
400/1A 1N4004 4p. 1250/1A BY 127 10p. 30/150mA OA47 gold bonded	18p
Zener diodes E24 series 3V3 to 33V 400mW - 6p. 1 watt	10p
Battery snaps for PP3 - 7p for PP9	12p
L.E.D.s 3mm, & 5mm. Red, Green, Yellow - 10p. Grommets 3mm - 2p. 5mm	2p
Red flashing L.E.D.'s require 9-12V supply only, 5mm	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A. O. blow 6p. A/surge 10p. Holders, chassis, mounting	6p
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0mm - 40p. Machines 12V dc	£15.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£4.50
AA/HP7 Nicad rechargeable cells 90p each. Universal charger unit	£6.50
AA/HP7 zinc/carbon batteries in packs of 4	£1.10 per pack
Glass reed switches with single pole make contacts - 8p. Magnets	20p
0.1" Stripboard 2 1/2" x 1" 9 rows 25 holes - 25p. 3 1/2" x 2 1/2" 24 rows 37 holes	70p
Jack plugs 2.5 & 3.5mm - 14p; Sockets Panel Mtg. 2.5 & 3.5mm	10p
Ear pieces 2.5 & 3.5mm, dynamic - 20p; 3.5mm crystal	£1.50
Multi cored solder, 22G - 8p yard, 18G - 14p yard.	
TRANSISTORS	
BC107/8/9 - 12p. BC547/8/9 - 8p. BC557/8/9 - 8p. BC182, 182L, BC183, 183L, BC184, 184L, BC212, 212L - 10p.	
BC327, 337, 337L - 12p. BC727, 737 - 12p. BD135/6/7/8/9 - 25p. BCY70 - 18p.	
BFY50/51/52 - 20p.	
BFY88 - 15p. 2N3055 - 55p. TIP31, 32 - 30p. TIP41, 42 - 40p. BU208A - £1.50, BF195, 197 - 12p.	
10isers with seven year guarantee, 240V AC, list price £16.95 or more	£16.50
Do not add VAT. Postage 30p (free over £5). Stamp for list.	

THE CR SUPPLY CO

127 Chesterfield Rd., Sheffield S8 0RN Tel: 0114 2557771 Return posting

Millions of quality components at lowest ever prices!

Plus Tools, Watches, Fancy Goods, Toys. Mail order UK only.

All inclusive prices - NO VAT to add on.

Send 43p stamped self addressed label or envelope for catalogue/clearance list.

At least 2,100 offers to amaze you.

Brian J Reed

6 Queensmead Avenue, East Ewell Epsom, Surrey KT17 3EQ Tel: 0181-393 9055

HIGH QUALITY LOW COST C.C.T.V. CAMERA
VERY LOW LIGHT LEVEL.
AUTO ELECTRONIC SHUTTER.
COMPOSITE VIDEO OUT VIA BNC PLUG.
SMALL DISCRETE SIZE.
CAN BE USED WITH PC DIGITISER.



This super quality CCD camera can be connected into your existing TV or video using the AV channel and can be used for discrete surveillance or observing your property externally using a suitable weatherproof housing. Can accommodate lighting levels ranging from daylight to street lighting using its built in electronic shutter. Excellent when using with an infra red source. Built in wide angle fixed focus lens the camera has a resolution of 380 TVL. Can be housed inside an empty floodlight case, (extra).

Special offer price of only: **£79.95 Plus VAT (P&P £3.50)**

For full range of CCTV products send SAE to:
Direct CCTV Ltd., Dept. PE27., Unit 6, Carrick Court, Forrest Grove Business Park, Middlesbrough, TS2 1QE.

SHERWOOD ELECTRONICS

FREE COMPONENTS

Buy 10 x £1 Special Packs and choose another one FREE

SP1 15 x 5mm Red Leds	SP118 2 x Cmos 4047
SP2 12 x 5mm Green Leds	SP119 4 x Cmos 4072
SP3 12 x 5mm Yellow Leds	SP124 20 x Assorted ceramic disc caps.
SP6 15 x 3mm Red Leds	SP125 10 x 1000/16V radial elect caps.
SP7 12 x 3mm Green Leds	SP130 100 x Mixed 0.5W C.F. resistors
SP8 10 x 3mm Yellow Leds	SP131 2 x TL071 Op.amps
SP10 100 x 1N4148 diodes	SP135 6 x Min. slide switches
SP11 30 x 1N4001 diodes	SP137 4 x W005 1.5A rectifiers
SP12 30 x 1N4002 diodes	SP138 20 x 2.2/50V rad. elect. caps.
SP13 20 x Assorted radial elect. caps.	SP142 2 x Cmos 4017
SP18 20 x BC182 transistors	SP144 3 x TIP31A transistors
SP19 20 x BC183 transistors	SP145 6 x ZTX300 transistors
SP20 20 x BC184 transistors	SP147 5 x Stripboard 9 strips/25 holes
SP21 20 x BC212 transistors	SP151 4 x 8mm Red Leds
SP22 20 x BC214 transistors	SP152 4 x 8mm Green Leds
SP23 20 x BC549 transistors	SP153 4 x 8mm Yellow Leds
SP24 4 x Cmos 4001	SP156 3 x Stripboard, 14 strips/27 holes
SP25 4 x 555 timers	SP160 10 x 2N3904 transistors
SP26 4 x 741 Op.amps	SP161 10 x 2N3906 transistors
SP28 4 x Cmos 4011	SP162 10 x 100K hor. trim pots
SP29 4 x Cmos 4013	SP165 2 x LF351 Op.amps
SP33 4 x Cmos 4081	SP167 6 x BC107 transistors
SP36 25 x 10/25V radial elect caps	SP168 6 x BC108 transistors
SP37 15 x 100/35V radial elect caps	SP173 10 x 220/25V rad. elect. caps
SP39 10 x 470/16V radial elect caps	SP175 20 x 1/63V radial elect caps
SP41 20 x Mixed transistors	SP182 20 x 4.7/50V radial elect caps
SP42 200 x Mixed 0.25W C.F. resistors	SP183 20 x BC547 transistors
SP47 5 x Min. pushbutton switches	SP187 15 x BC239 transistors
SP48 12 x Assorted axial elect. caps.	SP192 3 x Cmos 4066
SP102 20 x 8-pin DIL sockets	SP193 20 x BC213 transistors
SP103 15 x 14-pin DIL sockets	SP194 10 x OA90 diodes
SP104 15 x 16-pin DIL sockets	SP195 3 x 10mm Yellow Leds
SP105 5 x 74LS00	
SP106 5 x 74LS02	
SP112 4 x Cmos 4093	
SP115 3 x 10mm Red Leds	
SP116 3 x 10mm Green Leds	
SP117 15 x BC556 transistors	

RESISTOR PACKS - C.Film

RP3 5 each value - total 365 0.25W	£2.40
RP7 10 each value - total 730 0.25W	£3.75
RP10 1000 popular values 0.25W	£6.00
RP4 10 5 each value-total 365 0.5W	£3.40
RP8 10 each value-total 730 0.5W	£6.00

Catalogue £1 inc. P&P or FREE with first order.

P&P £1.25 per order. NO VAT.

Orders to:

Sherwood Electronics, 7 Williamson St., Mansfield, Notts. NG19 6TD.

ADVERTISERS INDEX

N. R. BARDWELL	407
B.K. ELECTRONICS	Cover (iii)
BRIAN J. REED	408
BULL ELECTRICAL	Cover (ii)/336
CHATWIN GUITARS (JCG)	405
CIRKIT DISTRIBUTION	365
COMPELEC	407
COOKE INTERNATIONAL	407
CRICKLEWOOD ELECTRONICS	405
CR SUPPLY CO	408
DIRECT CCTV	408
DISPLAY ELECTRONICS	330
ELECTRONICS SERVICE MANUAL	393
EPT EDUCATIONAL SOFTWARE	398
ESR ELECTRONIC COMPONENTS	340
GREENWELD ELECTRONICS	335
HART ELECTRONIC KITS	333
ICS	407
INFOTECH & STREE	407
J&N FACTORS	394
JPG ELECTRONICS	407
LABCENTER ELECTRONICS	373
LENNARD RESEARCH	365
MAGENTA ELECTRONICS	338/339
MAPLIN ELECTRONICS	Cover (iv)
MAURITRON	407
MODERN ELECTRONICS MANUAL	388
NATIONAL COLLEGE OF TECHNOLOGY	405
NICHE SOFTWARE	357
OMNI ELECTRONICS	405
PICO TECHNOLOGY	337
QUASAR ELECTRONICS	350
QUICKROUTE SYSTEMS	332
RADIO-TECH	350
ROBINSON MARSHALL (EUROPE)	349
SEETRAX CAE	385
SHERWOOD ELECTRONICS	408
SUMA DESIGNS	334
TSIEN (UK)	359

ADVERTISEMENT MANAGER: PETER J. MEW

ADVERTISEMENT OFFICES:

EVERYDAY PRACTICAL ELECTRONICS, ADVERTISEMENTS, HOLLAND WOOD HOUSE, CHURCH LANE, GREAT HOLLAND, ESSEX CO13 0JS. Phone/Fax: (01255) 850596

For Editorial address and phone numbers see page 341.

MP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W)

ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★ Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ Illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
MXF400 W19" x H5 1/4" (3U) x D12"
MXF600 W19" x H5 1/4" (3U) x D13"
MXF900 W19" x H5 1/4" (3U) x D14 3/4"

PRICES:- MXF200 £175.00 MXF400 £233.85
MXF600 £329.00 MXF900 £449.15
SPECIALIST CARRIER DEL. £12.50 EACH

OMP XO3 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass Invert switches in each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS ★

STEREO DISCO MIXER with 2 x 7 band & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

- TYPE 'A'** (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
- TYPE 'B'** (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
- TYPE 'C'** (KSN1016A) 2 x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
- TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
- TYPE 'E'** (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
- LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.



POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

12" iBFC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
12" iBFC 12-200WATTS (100dB) PRICE £175.00 PER PAIR
SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
Delivery £6.00 per pair

IN-CAR STEREO BOOSTER AMPS



PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS

150 WATTS (75 + 75) Stereo, 150W Bridged Mono
250 WATTS (125 + 125) Stereo, 250W Bridged Mono
400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS
Features: ★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection.

OMP MOS-FET POWER AMPLIFIER MODULES

SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P



OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P



OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P



OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £5.00 P&P



OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 150V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 80KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE- INSTRUMENTS, P.A., DISCO, ETC

- ALL EMINENCE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
 - RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
 - 10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
 - RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
 - 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
 - RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
 - 12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.64 + £3.50 P&P
 - RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
 - 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.67 + £3.50 P&P
 - 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P
 - RES. FREQ. 58Hz, FREQ. RESP. TO 5KHz, SENS 98dB.
 - 12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
 - RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB.
 - 15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
 - RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB.
 - 15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
 - RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS** (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.
 - 10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.
 - 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
 - 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
 - RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 - 5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
 - RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
 - 6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
 - RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
 - 8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB.
 - 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.80 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR.
Tel.: 01702-527572 Fax: 01702-420243

POSTAL CHARGES PER ORDER £100 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER. VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



All singing All dancing



That's the CDJ2600 from Soundlab! It's the twin CD for DJ's that does just about everything you could possibly ever need.



It comes as two 2U rack-mount units, finished in black enamel with clear legends and large, user-friendly controls, which are easy to find and use, even in the lowest light conditions.

The green LCD displays both track number and elapsed time to frame accuracy. It even gives a visual reminder should you leave one of the CD trays open.

When you're looking for a cue point, you can choose between two methods offered by a single concentric wheel. The outer ring

gives shuttle search, while the inner portion allows Jog Search. Once found, a cue point can be memorised then used instantly with a single 'cue' button.

An innovative joystick gives you total control over the comprehensive loop facilities: simply pushing the stick upwards memorises the loop start point and pulling it downwards marks the end point, giving a single repeat. Should you then pull the joystick down during the loop, it will repeat continuously.

Left/right movements of the joystick allow pitch bend.

And the CDJ2600 is as tough as it is talented.

The robust twin transport has been designed to survive life on

the road, while damped mechanisms offer a very high degree of mechanical isolation, to maximise playability in any conditions.

High quality sound reproduction is ensured by 16 bit, 8x over-sampling DAC technology, and ease of set-up is guaranteed by the unit's intelligent design.

All these features for only

£499.99

Order Code 51255

For more information call

01702 554161

MAPLIN

MONDO
MAPLIN