

Resistors		Capacitors	Semiconductors		
R1, R2	47R 1W	C1, C4, C31 to 36, C38 to 49	1nF	TR1	BC238, BC239
R3,	3R3	C2	2p2 (for 3W drive)	TR2	BFY51
R4	330k		8p2 (for ½W drive)	TR3, 4	BC327, BC328
R5, 14, 22, 23, 37	1k	C3	10uF/15V tantatalum	TR5	3N204 or 3SK45/51
R6, 38	4k7	C5, 6, 7, 8, 10, 12, 13, 14,		TR6, 10, 11	BSX20, 2N2369
R11, 17, 33	10k	16, 17, 18, 20, 21, 22, 23		TR7	2N3553
R9	56R		10nF	TR8, 9	2N4427
R10	100k	C9, 15, 19, 24	2u2/15V tant	D1, 2, 3, 4, 5, 7, 9, 10,	
R12	22k	C25, C27	220p	11	1N4148 1N914
R24	27R	C26	330p	D6	1N4001
R7, 8, 18, 21, 34	100R	C28, 30	68p	D8	10V1 Zener diode
R15, 29, 30	1k5	C29	150p		
R19	18R	CX	2p2		
R20	150R	TC1, 2	2 to 22p trimmer		
R26, 35,	220R	VC1	250 or 500p variable		
R27, 28	4R7	C37	6p8		
R31	330R				
R32	2k2				
R39, 40	10R				
R13, 36	390R				
RX	22k (mounted underside across L4	RFchokes			
RY (mounted underside L5-see text)	4k7	RFC1	4u7		
VR1	50k preset, vertical mounting	RFC2, 3, 4, 6, 7	Sturns 30swg through ferrite bead		
		RFC5	10u		
				Miscellaneous	
				65MHz · (20m)	HC18/u crystal
				61.5MHz	(15m) HC18/u crystal
				58MHz (10m)	HC18/u crystal
				RLY1 to 6	1150-060-1 9V
				PCB mounting (J Birkett)	
				T1 to 5	10mm block ferrite cores (J Birkett)
				6 off T50-6	Amidon toroids
				TMP Electronics, Ambit	
				SBL-1	balanced mixer
				SW1	2 pole 3 way
				Veronins	

NOTE: L3 and L4 may be replaced with TOKO pre-wound coils type 301-KU-0800. There are extra holes and pads shown in the oscillator board PCB artwork to accomodate them.

The components of one oscillator section only have been included in this parts list. If operation on all three bands is required then the extra components associated with two further oscillator strips will be required.

lator circuits, differing only in the fundamental frequency of the crystals. Taking the 20 metre conversion system as an example; if we have an IF of 144MHz, and wish to tune 14MHz, a local oscillator injection of 130MHz is required at the mixer. Here the sum ($144 + 130 = 274\text{MHz}$) and the difference ($144 - 130 = 14\text{MHz}$) frequencies are generated and suitably filtered by the tuned circuits in the preselector. It will be noted that the conversion crystals are within a few MHz of each other, which greatly simplifies the construction of the injection oscillators. The stabilised overtone circuit around TR10, tuned by L3 produces a signal half that required at the output. The small inductance L4 in series with the crystal allows precise frequency control. Resistor RX mounted underside across L4 reduces any possibility of the stage self-oscillating. This signal is lightly coupled into the next stage TR11 operating in a grounded base mode which acts as a doubler. The resultant frequency appears across L5, tuned by TC1. L6 and TC2 form the second section of the band-pass filter which is sharply tuned at the output frequency. The output from each oscillator is connected to

the same point via diode D9, thus eliminating manual switching at RF. As HT is applied to each oscillator, D9 conducts through R37 and R38, allowing low impedance injection into the mixer. At the same time the other output diodes are reverse biased, and so effectively isolate the signal from the other tuned circuits.

The required mixing product is selected by a twin-section toroidal filter (active both on transmit and receive) tuned by a twin-section 250pF variable capacitor. Low impedance transformation is achieved by the link-windings on the input and output. Originally, inductive coupling between the toroids was used, but later abandoned as the capacitive coupling between the preselector components proved to give very satisfactory performance.

Transmit and receive signals are directed through relay RLY3. On receive the incoming signal passes through the low-pass filter and appears at the receive side of relay RLY4 (point 'A'). This must be connected to RLY3 (point 'A') via a short length of coaxial cable. Depending on the VHF source in use, it is possible to add a wide-band receive pre-amplifier at a later

stage, particularly if the unit is modified for higher output frequencies. In the author's case, signals were so strong that a switched attenuator was envisaged to prevent over-loading the prime-mover! On transmit, the low level signal is amplified by the broad-band class 'A' amplifiers producing an output of around 3 watts into a 50ohm load. No originality whatsoever is claimed for the design. The information is readily available to anyone who has a copy of the 'constructors bible', *Solid State Design for the Radio Amateur*.

It appears that Frank, our illustrious Editor, and myself were thinking along the same lines when he described the broad-band transmit pre-amplifier chain in an earlier edition of this magazine. In fact, I thank him most sincerely for the information on the wide-band transformers which are used at each stage. TR5 acts as an impedance matching device. Any attempt to self-oscillate is halted by R9 across the input. To further reduce the possibilities of self-oscillation, the tantalum capacitors provide the necessary LF decoupling. The high gain VHF devices used for TR6 and TR7 increase the signal sufficiently to drive the push-pull amplifier TR8 and TR9