

current so C1 holds charge for many seconds.


Before C1 can discharge the key will be opened and it will recover charge from the key line of the transceiver via D1. C2 will start to charge slowly through R1 but Q1 will remain on until the voltage on C2 reaches the threshold of the gate's switching action (taking several hundred mSec, depending on the value of R1). During normal transmission the key will close again before this can happen and C2 will be discharged. Thus the PTT line will be grounded steadily during CW transmission.

If the key remains open for more than the time taken for C2 to charge to the gate's switching threshold the gate will change state, Q1 will be turned off, and the PTT line will revert to 'RECEIVE'.

A drawback of this circuit is that as well as powering the gate, C1 is also discharged through R1. Since CMOS schmitt input gates normally come in DIL packages of four (4093) or six (40106) it costs nothing to use a few extra gates to reduce the current drawn from C1. The final circuit, shown in Fig 2, does this.

The final circuit uses two more CMOS gates to isolate the timing circuitry from the key and also requires two diodes and a resistor (D4, D5 & R2) to keep the logic voltages within the permitted range. R1 is connected in parallel with D3 instead of to the "power line" and an extra diode is incorporated to protect Q1 if the system is used with an inductive load (such as a relay) in the PTT line.

 
This circuit uses three gates so that a 4093 quad schmitt NAND which contains four gates is ideal for the application. The pin numbers indicated apply to this part although any other CMOS schmitt input gates (such as the 40106) could equally well be used. The capacitors C1 and C2 should be low-leakage types so it is



Construction of the G4CLF keyer

worthwhile using bead tantalum types rather than aluminium — the extra cost is only pence. The diodes are silicon small-signal types such as the 1N914 or 1N4148 and are quite non-critical, and the VMOS transistor, Q1, is an N-channel type such as the Siliconix VN66AF.

 The circuit may be constructed in any suitable manner — it is very simple and component placing is not at all critical. The author's prototype uses Wainwright Minimount PC breadboarding strip mounted on the base of the morse key itself.



Another variant of the G4CLF keyer.

Connection

Before connecting the keyer to a transceiver several measurements should be made. The voltage and current available at both the PTT and the key connections should be checked by connecting first a high resistance voltmeter and then a milliammeter between these points and ground (note that the connection

of the milliammeter will cause the rig to transmit so a suitable power source and antenna should be connected).

This circuit will work with PTT and key line voltages of between 5 and 18 volts positive and will NOT work with transceivers having negative PTT or key lines. If the PTT line has a voltage above 18 the keyer must be modified by removing D2 (which causes the keyer to be powered from the key line only) and replacing D6 with a higher voltage part. Above 60 volts the VMOS device must also be replaced by one capable of withstanding the necessary voltage. If the key line has a voltage of over 18 volts the keyer cannot take its power from the key line but must be battery powered by a PP3 battery connected in parallel with C1. In addition, D5 must be removed, the grounded end of R2 connected to the battery positive and D4 replaced with a device capable of withstanding the necessary reverse voltage.

Provided the PTT and key currents are more than 100 microamps and less than 250 millamps the circuit should work correctly (PTT currents of over 250 mA may be accommodated by using a higher powered VMOS device).

The keyer is connected to the transceiver by connecting the PTT and key lines to the appropriate sockets of the transceiver — when the key is closed (provided the transceiver is set to 'CW') the rig will switch to 'TRANSMIT' and remain that way until the key has been open continuously for a time set by R1 and C2. In the prototype R1 is 220K and C2 is 0.47 uF and the delay is about half a second but variation in the threshold voltages of the CMOS used may change this quite widely and R1, and even C2, may need to be changed to achieve the correct delay. R1 should never be less than 180K but may be as high as 4.7M.

This keyer has been in use with the author's FT290 for over six months and has proved very useful. It has been widely copied.

COMPONENTS LIST

R1 220K (see text)
R2 1M

C1 100u 25V tant.
C2 0.47u 16V tant.

D1-6 1N914, 1N9148 (see text)

Q1 VN66AF
IC1 4093 CMOS

 


Fig. 2 Final version using 4093.