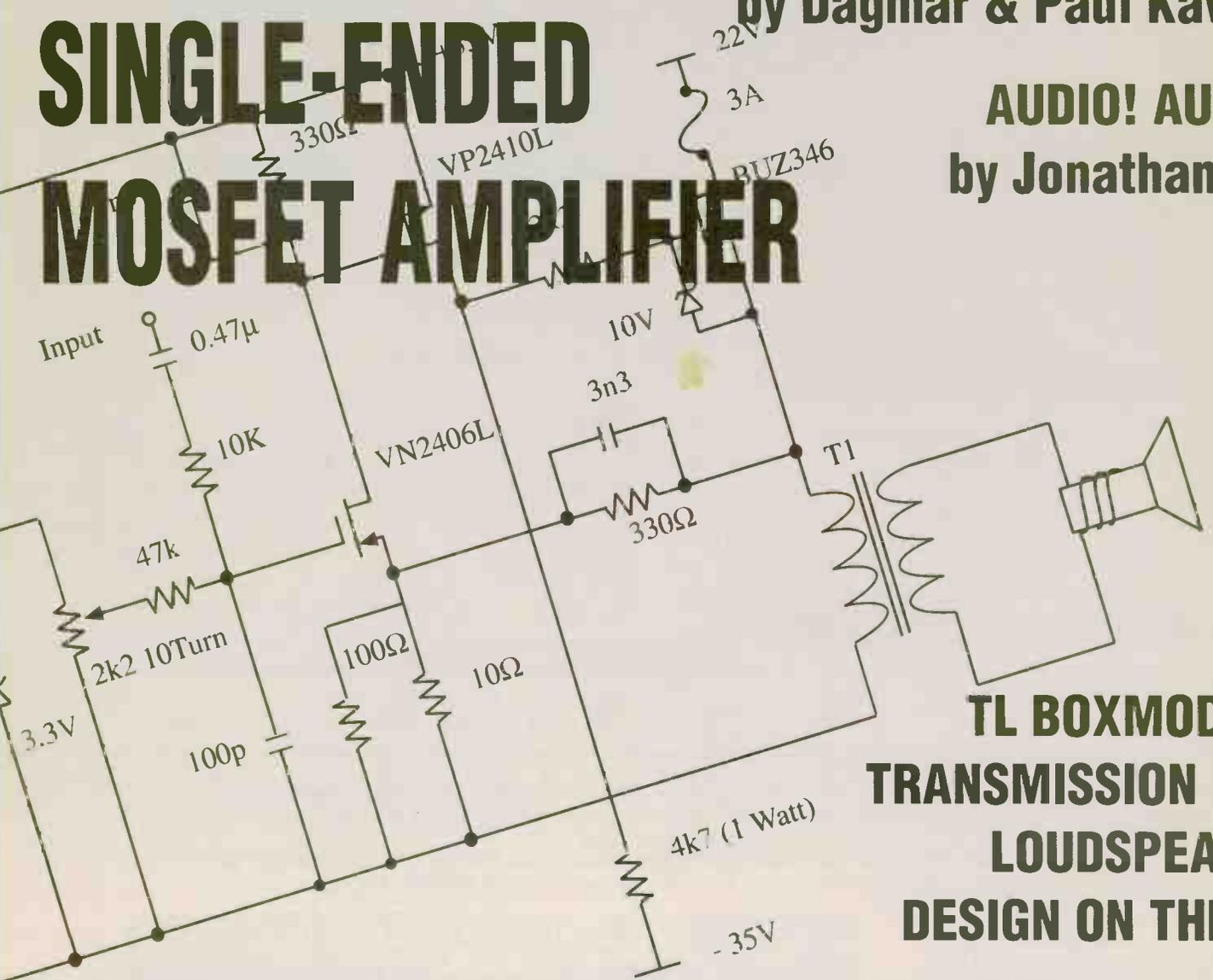



Hi-Fi WORLD SUPPLEMENT

No. 20 FEBRUARY 1996

UNIQUE 15W SINGLE-ENDED MOSFET AMPLIFIER



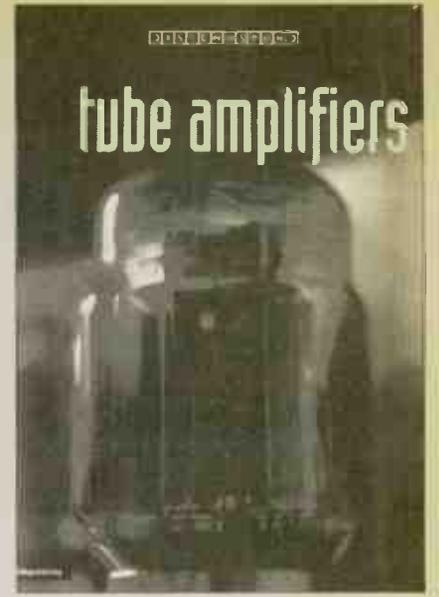**TL BOXMODEL -
TRANSMISSION LINE
LOUDSPEAKER
DESIGN ON THE PC**



BOOK REVIEWS:

TUBE AMPLIFIERS
by Dagmar & Paul Kavsek

AUDIO! AUDIO!
by Jonathan Hill

FREE D.I.Y. SUPPLEMENT No. 20

α**Billington Gold****Ω**

Long known as specialists in rare tube brands, Billington Export provides a line of premium-grade valves to fill the increasing demand for hard-to-find tubes! BILLINGTON GOLD features specially tested valves selected for long life, low microphony and low noise. Versions with gold plated pins are available. BILLINGTON GOLD brand comes from a variety of countries around the world. We have carefully chosen the best manufacturer for each type, with an

emphasis on the highest audio quality and product reliability. We stock one million valves including: BRIMAR, GE USA, GEC UK, MAZDA, MULLARD, RCA, RUSSIAN/SOVTEK/SVETLANA, SYLVANIA, TESLA, THERMIONIC, TUNGSRAM and other rare brands, as well as sockets and CRTs.

BILLINGTON GOLD

2A3	15.50
6L6GC	6.45
12AX7	5.25
300B	60.00
811A	12.00
845	33.00
6550A	11.50
E81CC	5.25
E81CC-01	9.50
E82CC	4.50
E82CC-01	8.50
E83CC-01	8.50
E88CC	7.50
ECC81	5.25
ECC82	4.50
ECC83	5.25
ECC88	6.90
EL34	9.95
EL84	3.60
KT66	9.50
KT88	18.50

RARE BRANDS

3AMP1A Tungstram Hungary	32.40	6550A GE USA	33.00
5C-450A STC UK	259.35	CV4003 Mullard UK	POA
5R4GY USA	POA	CV4004 Brimar UK	POA
5Y3GT RCA	3.90	CV4024 Mullard UK	POA
6BH6 RCA	2.48	DG7-32 Tungstram Hungary	32.48
6L6WGB Sylvania	15.00	ECC81 Mullard UK (CV4024)	POA
6V6GT STC UK	POA	ECC82 Mullard UK (CV4003)	POA
12BH7A GE	11.40	ECC83/ECC803S Tesla	13.13
12E1 STC/ITT UK	POA	EF86 GEC UK (CV4085)	POA
13E1 STC UK	135.00	GZ32 Mazda	8.00
85A2 Mullard	5.93	GZ37/CV378 Mullard UK	POA
807 USA	POA	KT90 Yugoslavian	45.00
5687WA RCA	6.45	PL519 ECG Philips	5.95

YUGOSLAVIAN / ETC

6CG7 Yugoslavian	6.75	ECC83 Yugoslavian	3.09
6X4W Raytheon USA	3.60	ECC85 Tungstram	3.30
5751 (USE ECC83)		ECL86 Tungstram	3.45
6336A Penta USA	58.50	KT90 Yugoslavian	45.00

RUSSIAN/SVETLANA

6AS7G	4.50
6B4G	27.00
ECL82	2.25
SV811-3	22.75
SV811-10	22.75

Try us for ALL Russian/Svetlana valves

SOVTEK

5U4G	3.60	ECC83/12AX7WB	3.50
6L6WGC	6.00	EF86	POA
6SL7GT	2.50	EL34G	6.20
6SN7GT	4.95	EL84	1.99
12AX7WA	3.50	GZ34	5.40
12AX7WB	3.50	GZ34/5Y3GT	2.90
5881/6L6WGC	6.00		

CHINESE

300B Silvertone	60.00
ECC88	3.90
EL34	7.00

SOCKETS

Jumbo 4-Pin for 211, 845, etc.	11.50
Jumbo 4-Pin, Gold Plated, for 211	24.00
UX4 for 2A3, 300B, 811A, etc.	2.25
UX4 Large Locking Type for 300B	6.00
B5 UK	POA
UX5 McMurdo UK for 807	3.60
B7A for 6C33CB	3.23
B7G McMurdo UK, chassis, skirted	0.72
813 Ceramic	15.00
Octal McMurdo UK	1.20
Octal PCB, nylon	2.70
Octal PCB, foreign	1.20
B9A for ECC83, EL34, EF86, etc., suitable for pre-amps: -	
- Ceramic, skirted, chassis, screening can;	
Chinese	1.20
Russian	0.90
- PCB, gold pins	2.40
B9D Magnoval, chassis, for PL519	2.25

We supply sockets for all valves listed in this advertisement

TOPCAPS

For 2C34, 807, etc	1.20
For 12E1, 5B-254M, PL519	3.60

MATCHED TESTING

£2.00 Per Valve
(£4.00 per pair)

All items in stock at time of going to press. Prices in GB Pounds and subject to fluctuation: please check before placing your order. We stock over 3000 valve types and 400 types of CRT. Please ask for our free 50 page catalogue of valves and/or our CRT catalogue.

Payment is accepted by:

ACCESS, AMERICAN EXPRESS, DEBIT CARD, JCB, MASTERCARD, VISA, Bankers Draft, Bank Telex, Eurocheque and Cheque (UK only)
MINIMUM ORDER: UK £50.00 + VAT & Carriage. Export £100.00 (US \$150.00) + Carriage



1E GILLMANS TRADING ESTATE
BILLINGSHURST
WEST SUSSEX RH14 9EZ UK
TEL: (0)1403 784961 FAX: (0)1403 783519
VISITORS STRICTLY BY APPOINTMENT PLEASE

D.I.Y. Supplement

Contents

All rights to the designs are reserved by World Audio Design Ltd. They are published for single use by private individuals. They are not to be used for commercial gain without prior permission from World Audio Design Ltd.
Audio Publishing Ltd and World Audio Design Ltd accept no responsibility for accident or injury arising from the construction or use of any of the designs published.
All of the projects in this supplement have gone through rigorous listening and test procedures. The performance and specification of these projects can only be guaranteed on kits bought directly from World Audio Design Ltd.

KIT NEWS

All that's new in the world of components, drive units and kits for the DIY hi-fi enthusiast.

5

15W SINGLE-ENDED MOSFET AMPLIFIER

Using just three MOSFET transistors per channel, we've come up with a unique design for a 15W Single-Ended amplifier. It's simple to build and gives super results.

6

TL BOXMODEL

Last month we reviewed Robert Bullock's comprehensive BoxModel loudspeaker enclosure design package for reflex and sealed enclosures. This month we take a look at his TL BoxModel, one of the few CAD packages available for Transmission Line design.

16

BOOK REVIEWS

TUBE AMPLIFIERS

A basic introduction to the valve and how it works followed by a focus on the aesthetic design of valve amplifiers.

21

AUDIO AUDIO

An illustrated guide to classic audio amplifiers and control units for the hi-fi enthusiast and collector

23

AUDAX HT240ZO

Audax have just introduced an all new 10" High Definition Aerogel driver. We take a look at this new unit and investigate its potential.

25

DIY LETTERS

A living soap of DIY drama. Write in for advice and help with your designs, or just to tell us how well your project worked.

27

HART

Hart Audio Kits - Your Value for Money Route to Better Sound 2 Penylan Mill, Oswestry, Shropshire, UK. SY 10 9AF Phone 01691 652894 Fax. 01691 662864

Hart Audio Kits and factory assembled units use the very best audiophile components in circuit designs by the renowned John Linsley Hood to give you unbeatable performance and unbeatable value for money.

We have always had the best for easy home construction to professional standards, even in the studios we were making quality assembled printed circuits when HART kits in America were still being regarded as 'hobby' kits. Many years of experience and innovation, going back to the early Grinnell and Henry classics gives us incomparable design expertise in the needs of the home constructor. The current range of Hart kits is designed to give you all the components for a matching ensemble of audio excellence.



K1100 AUDIO DESIGN 80 WATT POWER AMPLIFIER.

This legendary John Linsley Hood designed amplifier is the flagship of our range and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get EK performance at bargain basement prices. Unique design features such as fully FET stabilised power supplies give this amplifier World Class performance with startling clarity and transparency of sound, allied to the famous HART quality of components and ease of construction. Useful options are a stereo LED power meter and a sensitive passive front end giving switched inputs, with ALPS precision Blue Velvet low noise volume and balance controls. Construction is very simple and enjoyable with all the difficult work done for you, even the wiring is pre-terminated, ready for instant use! All versions are available with Standard components or specially selected Super Audiophile components at £29.60 extra per channel, plus £2.40 if you want to include Gold Plated speaker terminals.

K1100G Complete STANDARD Amplifier Kit **£395.21**
A1100B Factory Assembled **£499.21**
K1100SC Complete SLAVE Amplifier Kit, £ **£333.62**
A1100SC Factory Assembled **£422.62**
K1100DM Complete MONOBLOC Amplifier Kit **£261.20**
A1100DM Factory Assembled **£329.20**
RH110 Reprints of latest Amplifier articles **£4.50**
K1100CM Construction Manual with full parts lists **£5.50**

K1400 AUDIOPHILE PREAMPLIFIER. A versatile ultra high quality preamp with no less than seven inputs, all switched by smooth high quality relays. Separate trace output selection. Class 'A' headphone output for low phones. Lo-Z long line drive facility.

Standard Kit **£343.49**
K1400T Kit with Tri-range tone controls **£398.41**



"CHIARA" SINGLE ENDED CLASS "A" HEADPHONE AMPLIFIER.

First Module to appear in our new '2000 Range' of kits. This unit provides a high quality phono output for those many amplifiers that do not have one. Easily installed with special care through the kit, the unit draws its power from our new Andante Ultra High Quality linear toroidal supply. Housed in the neat, black finished, Hart minibox it features the wide frequency response, low distortion and musicality that one associates with designs from the renowned John Linsley Hood. Pre-terminated interconnecting leads and PCB mounted switches provide simple polarity reversal and on-board diagnostics provide visual indication of supply line integrity. Volume and balance controls are Alps 'Blue Velvet' components. Very nicely built into a minibox, since all components fit directly on the single printed circuit board and there is no conventional wiring whatsoever. The kit has very detailed instructions and also comes with a roll of Hart audiograde silver solder. It can also be supplied factory assembled and tested. Selling for less than the total cost of all the components, if they were bought separately, this unit represents incredible value for money and makes an attractive and harmonious addition to any hi-fi system.


K2100 Complete Kit **£109.50**
K2100SA Series Audiophile version with selected audiophile components **£112.46**
A2100SA Factory Assembled and Tested "Chiara" **£149.46**

K3565 "Andante" Audiophile Power Supply Kit to suit **£85.42**
A3565 Factory Assembled and Tested "Andante" **£128.42**
Special Offer, Both Units in Kit Form together with SA version "Chiara" with mains and DC Supply lead **ONLY £184.92**
Factory Assembled and Tested **ONLY £267.88**

K1450 MAGNETIC PICKUP PREAMPLIFIER KIT features a totally discrete component implementation with the superior sound of the Shunt Feedback concept. High quality components fitting to an advanced double sided printed circuit board make this a product at the leading edge of technology that you will be proud to own. Nevertheless with our step by step instructions it is very easy and satisfying to assemble. The higher current consumption of this unit means that it is best powered by our new Andante Audio Power Supply, itself an advanced piece of technology in a matching case. This supplies the superbly smoothed and stabilised supply lines needed by my sensitive preamplifier and features a fully potted Hi-grade toroidal transformer along with a special limited shift earthing system for hum free operation. The K1450 is suitable for all moving coil and moving magnet transducers this unit is especially recommended for, and will extract the very best from the modern generation of low output high quality moving coil transducers. This magnificent kit, comes complete with all parts ready to assemble inside the fully finished 228 x 134 x 63mm case. Comes with full, easy to follow, instructions as well as the Hart Guide to PCB Construction, we then throw in enough Hart Audiograde Silver Solder to construct your kit!

K1450 Complete Kit **£111.58**
K1450SA Audiophile Kit **£133.94**

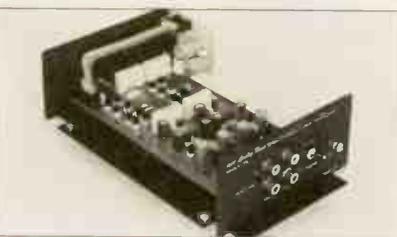Why not buy the reprints and construction manual for the kit you are interested in to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.



ALPS "Blue Velvet" PRECISION AUDIO CONTROLS.

Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability.

MANUAL POTENTIOMETERS

2-Gang 100K Lin **£15.67**
2-Gang 10K, 50K or 100K Log **£16.40**
2-Gang 10K Special Balance, zero crosstalk and zero centre loss **£17.48**

MOTORISED POTENTIOMETERS

2-Gang 20K Log Volume Control **£26.20**
2-Gang 10K RD Spiritual Balance, zero crosstalk and less than 10% loss in centre position **£26.96**

SOLOERING

The size of modern components makes the right soldering equipment essential for good results. Everything we offer we actually use in our own workshops! See our Lists for the full range.

845-820 XS240 ANTEX 240V 2kw Soldering Iron. This is the ideal Multi-purpose iron as the bit is designed to totally surround the element giving the best heat transfer. This excellent design also means that although it is small and handy enough for modern components its heating capacity is better than larger irons of conventional construction. Excellent Value **£9.93**
845-080 S14 Lightweight Soldering Iron Stand. This has provision for the classic clamp sponge for bit wiping. **£9.95**

HART SUPER AUDIOGRADE SILVER SOLDER

Hart Super Audiograde Silver Solder has been specially formulated for the serious audiophile. Not only does it give beautiful easy-to-make joints but it is designed to melt at normal soldering temperatures avoiding the possibility of thermal damage to components or the need for special high temperature irons. A very low residue flux makes perfect joints easy but eliminates the need for board cleaning after assembly.

845-007 3mtrs 22SWG in Hart Mini Tube **£3.90**
845-008 100g Reel Special Valve Grade, 20SWG **£12.90**
845-009 100g Precision PCB Grade, 22SWG **£14.75**
845-110 100g Reel Superfine 24SWG for ultra precise control and easy working **£21.45**

32W VALVE AMP TRANSFORMERS

Special set toroidal transformers, 2 output & 1 mains for the "Hot Audio Power" valve amplifier design described in the Oct. 1995 issue of "Wireless World". Total Wt 4.8kg. Special price for the set **£99**
Post **£8**
Photocopies of Article by Jeff Macaulay **£2**

TECHNICAL BOOKSHELF

"AUDIO ELECTRONICS" J.L. Linsley Hood. Now entirely re-written by the author himself this new book covers the underlying audio techniques and equipment in tape recording, tuners, power output stages, digital audio, test instruments and loudspeaker construction systems. ISBN 0-7506-2181-8 **£19.99** *
"THE ART OF LINEAR ELECTRONICS." J.L. Linsley Hood. The definitive linear electronics and audio book. Learn how to read circuit diagrams and understand amplifiers and how they are designed to give the best sound. The standard reference for all who work, or are interested in this field. 0-7506-0668-4 **£16.95** *
HART Exclusive! FREE amendments sheet with each copy.
"THE ART OF SOLDERING" R. Brewster. Absolutely essential reading for anyone who ever picks up a soldering iron. ISBN 0-85335-324-3 **£3.95** *
"ACTIVE FILTER COOKBOOK" Don Lancaster. All the inside information on the calculation on construction of Low pass, high pass and band-pass filters using Bessel, Chebyshev and Butterworth topologies. BKS14 **£19.95** *
"HOW TO USE OSCILLOSCOPES & OTHER TEST EQUIPMENT" R.A. Penfold. B2P27 **£3.50**
"THE LOUSPEAKER DESIGN COOKBOOK" New 5th Ed. Vance Dickason. All the information you need to build your new super loudspeaker system. ISBN 1-882580-10-9 **£25.95** *
ELECTROSTATIC LOUSPEAKER DESIGN AND CONSTRUCTION Ronald Whitton. This classic describes the important parameters of an electrostatic speaker and indicates how each affects performance. BKT6 **£18.95**
"THE ELECTROSTATIC LOUSPEAKER DESIGN COOKBOOK" Roger P. Sandilands. This new title takes you right through from the theory of electrostatic loudspeakers to hands-on guidance on practical construction, also covering power supply and amplifier suitability. A full chapter also covers transmission line woofers enclosures. ISBN 1-882580-00-1 **£24.95** *
"BULLOCK ON BOXES" R.M. Bullock III with Robert White. Easy to read guide for anyone interested in loudspeaker enclosures, theoretical calculations and practical building and is now considered as one of the classics on the subject. BKA48 **£11.40**
"LOUDSPEAKERS; THE WHY AND HOW OF GOOD REPRODUCTION" G.A. Bragg. The 1949 Classic on the whole subject of high fidelity reproduction. 0-9624-1913-3 **£8.95**

VALVE & EARLY CLASSIC BOOKS

THE VTL BOOK David Manley. Comprehensive modern book on the use of valves. BKVT1 **£17.95**
"VALVE AMPLIFIERS". Morgan Jones. An easy to read medium book on the subject of valve amplifiers which goes through the art with very little theory and a great deal of practical information. If you Macca is where valve amplifiers are then this is your Kom! RRP £25. Our Price **£24.50**
MULLARD TUBE CIRCUITS FOR AUDIO AMPLIFIERS Mullard Ltd. A D.Y. classic, with sheet metal diagrams, parts lists and performance data. BKA27 **£13.95**
"THE WILLIAMSON AMPLIFIER." D. T. M. Williamson. From April 1947, a cult classic power amplifier design reprinted from Wireless World. 0-9624-1918-4 **£6.95**
AN APPROACH TO AUDIO FREQUENCY AMPLIFIER DESIGN. GEC. No less than seventeen valve amplifier circuits from 5 to 1100 Watts. Full of genuine information from the valve era with valve specifications and base connection diagrams. 1-882580-05-2 **£18.95**
AUDIO ANTHOLOGIES, collected articles from Audio Engineering magazine. Six volumes covering the days when audio was young and valves were king! All edited by C.G. McProud. All are £13.95.

VOL 1

The first of the new audio amplifiers, preamps, tuners and speakers after the war. 38 of the best articles from 1947 - 1949. BKA43/1

VOL 2

1950 - 1952. BKA43/2

VOL 3

43 articles 1952-1955, 7 power amplifiers, 18 preamps and 12 loudspeakers. Another novel proposal for an output transformerless 25 Watt valve amplifier. BKA43/3

VOL 4

4 articles from 1955 - 1957. Designs for 12 amps and preamps and 6 loudspeakers. BKA43/4

VOL 5

48 articles from 1958 & 9. BKA43/5

VOL 6

38 articles from 1960 and 1961. BKA43/6

"AUDIO ANTHOLOGIES" Special Offer:

All set for only

"PRINCIPLES OF ELECTRON TUBES" Herbert J. Reich Ph.D. **£79.00**

Reprint of a 1941 textbook on the workings of valves. The use of valves in class A, AB, B, and C operation is covered with sample circuits, topologies and distortion. BKA43/4 **£27.95**

SPECIAL OFFER. With all book orders over £15 we will supply FREE on request, a John Linsley Hood monograph entitled "Digital v. Analogue, Black Disks or Silver?" Postage on books is £2 (£3.50 for heavy books with *) maximum in UK: £4.50 for any number, any size! No waiting! All listed books are normally in stock!

Ordering your HART kit is easy, simply post, telephone or fax your order anytime. Let us know what you require, with your name, address, cheque or credit card number and expiry date. Your daytime phone number is useful in case we need to get back to you. If you need further information on our kits just ask our FREE lists. Overseas order are welcome and we can send anywhere in the World. Post on UK orders up to £20 is £1.50, over £20 - £3.50. Express Courier £10.

QUALITY
AUDIO KITS

24hrs SALES LINE
01691 652894

ALL PRICES
INCLUDE
UK/EU VAT

HART

KIT NEWS


BACK ISSUES FROM FALCON

1995 back issues of Speaker Builder, Audio Amateur and Glass Audio will be available from Falcon Acoustics from early February, 1996.

Besides IMP, Falcon are now also stocking Audiosuite test software, plus UK sourced Mitey Mike and Audiosuite input preamp kit. Also new is AIRR (Acoustic In Room Response) software which gives basic impulse testing with a Soundblaster 16 bit card for the PC.

Falcon are the UK agents for Focal driver units, and are pleased to announce that the full range of Focal loudspeaker kits are now available.

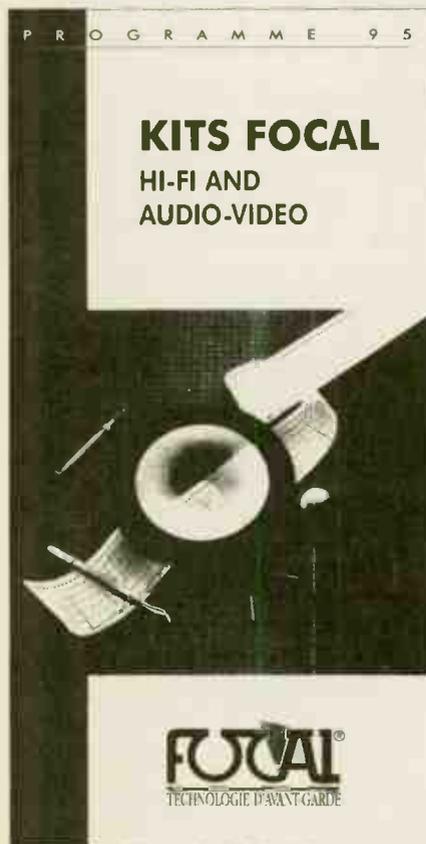Falcon Acoustics
Tabor House,
Norwich Road,
Mulbarton,
Norwich,
Norfolk. NR14 8JT
☎ 01508 578272



SPECIAL TRANSFORMER SET FOR THE NEW "HOT AUDIO" VALVE POWER AMPLIFIER

Hart Electronics are offering special toroidal power supply and output transformers for a new and innovative valve power amplifier design by Jeff Macaulay. They tell us it is a well thought out, modern valve amplifier using EL34 valves to produce a very healthy 32watts of output power. A full power bandwidth of 5Hz to 55kHz is claimed, together with 0.07% distortion at 20W.

The set consists of the three specially wound toroidal transformers, one for the power supply and two output transformers for a complete stereo system. Reprints of the circuit and article describing the amplifier design are available for £2.50 post free.

Price for the complete set of three transformers, including VAT is £99 plus £8 for standard post or £10 courier delivery in the UK.

Also, the Dynamic Range Control Module is a new unit available in kit form from Hart Electronics, offering useful extra facilities that can increase the listening pleasure from your hi-fi system. Quite simply it does exactly what its description implies, compressing or expanding the range of levels present in any signal so that none are louder or softer than you want.

The principles have been known for many years and have been used before, but until this new digital operating principle was devised by John Linsley Hood they have never come up to the standards of low distortion demanded by the serious audiophile, Hart say.

There are three main areas of use for this unit. Curbing the over exuberant range of some CDs, preparing special tapes for use in your car and restoring dynamic range lacking in some compressed signals.

The Hart Dynamic Range Control Module is easily constructed from the kit, all components fitting directly on the printed circuit board. Housed in a matt black casing, 228mm deep, 134mm wide and 63mm high, it makes an unobtrusive addition to your system.

It can be left in circuit permanently, as signals are simply routed through untouched when it is switched off. To preserve signal integrity an external power supply is used. Hart recommend their K2900 'Andante' linear technology audiophile supply.

The Dynamic Range Control Module is Hart Kit number K3550 and will be available in February '96. Price is £99.60. Power Supply K3550 is £89.75. Both prices include VAT. Postage is £3.50. Hart are at:

Penylan Mill
Oswestry,
Shropshire. SY10 9AF
☎ 01691 652894

PV TUBES' NEW CATALOGUE


PV Tubes have a new catalogue available. It features valves, semiconductors, aerials and most other electronic components. For a copy send a large SAE (57p) to:

PV Tubes
104 Abby St.,
Accrington,
Lancs. BB5 1EE
☎ 01245 236521/232611


BILLINGTON VALVE CATALOGUE

As you read this, a new 60 page valve catalogue is being compiled by Billington Export. It contains thousands of different types and comprehensive cross referencing information between different identifications, such as American valves and military CV numbers. Billington's told us they stock the SV81 I power triode from Svetlana but are still awaiting delivery of Western Electric 300Bs. The catalogue is free. For more information contact:

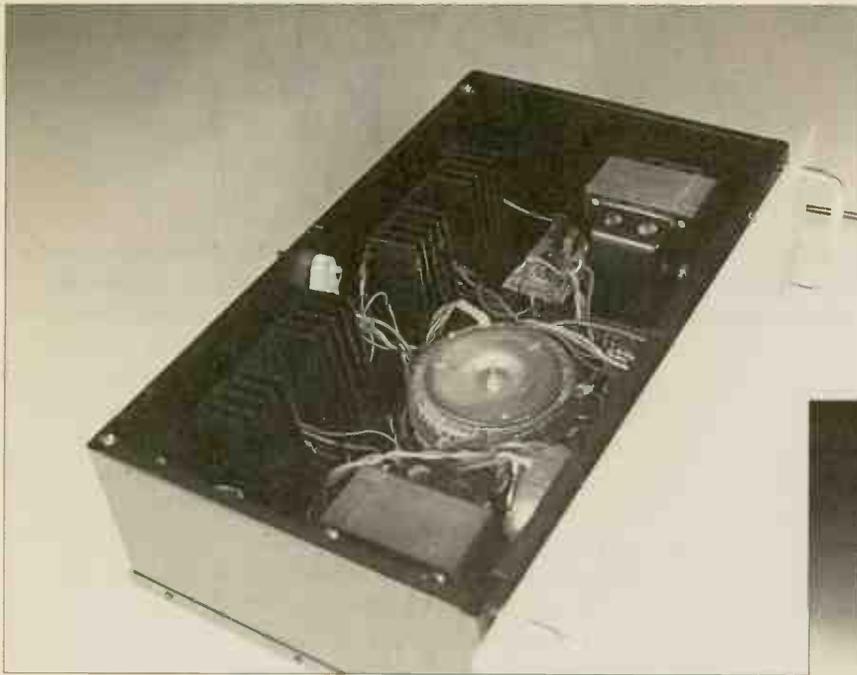Billington Export
IE Gillmans Ind. Est.,
Billinghurst,
West Sussex. RH14 9EZ
☎ 01403 784961



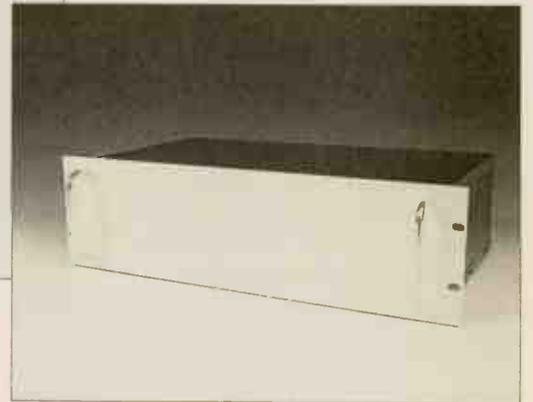Our prototype was built in a Maplin rack mount case. There was plenty of space around the components, making build easy.



A SINGLE-ENDED MOSFET AMPLIFIER

Noel Keyword discusses the merits of Single-Ended working, using MOSFETs.

Many of you have asked us to design a Single-Ended amplifier using solid-state devices, rather than valves - so we have! The low efficiency of such amplifiers causes them to stream heat, which presents a host of problems. Andy Grove, designer of this circuit, has ingeniously produced an amplifier of high efficiency to minimise heat production. Its modestly sized heat sinks run bearably hot for 15watts of Class A power. It isn't a power house, but 15watts per channel is enough to make 90dB sensitive loudspeakers go quite loud. More power can be had from the design with little difficulty; our circuit is, in effect, a useable test bed, a great starting point for experimenters.

So why Single-Ended? Most listeners who have spent time in front of valve

Single Ended amplifiers, myself included, feel they offer a more natural, relaxing and involving sound than push-pull types. There's some magic in S.E. working that yields a subtly richer and more detailed sound than that available from the everyday push-pull amplifier. However, efficiency is low, meaning power output is limited by practical difficulties such as heat dissipation. I should explain that SE working is very simple and has been universally supplanted by push-pull, now used in all modern amplifiers. These days, if you want an SE, you have to build one.

Single Ended output stages also produce more distortion than push-pulls, but this only becomes significant at higher output levels. I believe it's important that SEs, by their very nature, do not distort at the zero crossing

point. As level goes down, so does distortion. In this respect, they are more ideal than push-pulls, which suffer rising distortion at lower levels, alleviated by Class A working and oodles of feedback. Crossover distortion is contrary to music; it rises as musical level declines and its harmonics extend far from the main stimulus, modulating in an unmusical manner. This is only made worse by the application of feedback. I strongly suspect the ear is sensitive to such dissonant signals.

A Single Ended amplifier is quite different. It produces more distortion, but of a type that closely matches the natural harmonic structure of musical instruments. It doesn't clash with them, so it isn't dissonant. I believe the distortion pattern is effectively swamped by music and tends not to clash with it

in a fashion the ear finds jarring and unnatural. I was fascinated to see the way the harmonics of our design fell away smoothly with frequency and collapsed to virtually nothing below a few watts. There was quite obviously none of the modulation of distortion pattern that heavy feedback produces in push-pull amps. either.

I am not trying to say that distortion doesn't matter. On the contrary, you can hear distortion as muddle at high levels. In my experience, using our own sensitive carbon-fibre KLS3 loudspeakers which were designed for such amplifiers,

SE amplifiers sound best when idling along at a few watts output, suggesting the presence of simple, low order harmonic distortion does not explain their unique sound quality. If it did, then they would sound better at high levels, where distortion is at its highest. Delivering a few watts output at 10kHz, this amplifier (Andy's version) produces around 0.2% of purely second harmonic distortion, which is subjectively innocuous.

It is as likely that SE amplifiers sound the way they do because they possess fewer parts and simpler circuits than

push-pull types, so minimising component colourations. I should point out that to capitalise upon this, Andy deliberately kept his circuit simple.

I can't help also feeling that push-pull amplifiers may also cancel low level signals in the way they cancel distortion and supply rail hum. No such cancellation mechanism exists in SE amplifiers. Subjectively, they gain from this. A push-pull can sound "stripped bare", or stark, in comparison to a good SE. All the same, few manufacturers have the nerve to produce SE amplifiers, because they appear so impractical.

HOW THE CIRCUIT WORKS

by Andy grove

The circuit for my MOSFET single-ended amplifier is very simple. ZD1, C1 and Vr1 form an adjustable voltage reference for biasing the amplifier overall. Tr1 is the first stage. The input signal passes through the D.C. blocking capacitor C2 and the gate stopper R2. Tr1 is a simple single-ended common source stage with R4 as its load. C3 is part of the compensation and reduces gain with increasing frequency.

Tr2 is again a common source stage but using a P channel device to allow direct coupling. Tr2's load R6 is connected to a negative rail to give a full bipolar swing to the output FET Tr3.

TR3 is in source follower configuration driving the output transformer T1. DC and AC feedback are taken from the transformer's primary via R5 and C4, C4 being a compensation component to assure a clean square-wave.

The power supplies are very simple. Separate rails are needed to get the low current +/- 35V for the driver stage and +22V at 2A for the output stage.

The resistance of T1's primary winding is used to sense the DC current through Tr3 and this is fed back to Tr1. The downside of this is that as the winding heats the quiescent current changes, although after warm-up everything settles down. This means that the amplifier needs some setting up with a scope to optimise the output power. To do this connect an 8 ohm load of at least 20W capacity, switch the circuit on and adjust Vr1 for approximately 1.5V

across T1's primary and then leave the amplifier for about 1 hour to heat up. Then use a 1kHz signal to make the amplifier clip on the scope, adjust Vr1 for maximum power output with symmetrical clipping, leave and then readjust 15 minutes later. You now have a 15W single-ended amplifier.

There are a few pure Class A, single-ended solid-state power amplifiers around but most use a constant current source as the output device's load. This results in very poor efficiency of 25% maximum, wrongly stated in many textbooks as the maximum theoretical efficiency of any single-ended amplifier. With these designs the transformer in my design is replaced with a current source connected to a negative rail. The minimum negative voltage required is the same as the positive voltage to achieve symmetrical clipping and therefore maximum efficiency.

The quiescent current in such circuits must be sufficient to supply the peak current in the load. Therefore, under ideal conditions, for a given supply voltage Vs and peak current Ipk the idle dissipation will be $2 \times V_s \times I_{pk}$ ($2 \times V_s$ because of the +/- supply rails needed). The power output is $1/2 \times I_{pk} \times V_s$. The efficiency (power out/dissipation) is $(1/2 \times I_{pk} \times V_s) / (2 \times V_s \times I_{pk}) = 0.25$ or 25%. The problem here is a practical one. For any given power output the power dissipation into the heatsink will be very high, equalling $P(W)/0.25$. So a 15W amplifier needs to lose 60W into the heatsink. This will produce a lot of heat,

necessitating very large heatsinks. For example, a modest 30W/channel amplifier will have to lose 240W of heat. This raises some severe difficulties. Heatsinks, complex alloy extrusions anodised black, are very expensive and losing waves of heat from them means using special casework, or a fan.

In my design the transformer, under ideal conditions, has no DC voltage across it (zero DC resistance), therefore it dissipates no power and only one supply rail is needed. The transformer stores energy in its magnetic field and releases it into the load to give the negative voltage swing. By way of contrast, a current source continually burns this energy off as heat. The dissipation with a transformer is now $V_s \times I_{pk}$, the power output is the same as before and the efficiency is $(1/2 \times I_{pk} \times V_s) / (V_s \times I_{pk}) = 0.5$ or 50%.

With this efficiency a 30W stereo amplifier would dissipate 120W of heat in its heatsinks - far less than normal. So whilst transformers are shunned by most engineers nowadays, they offer many benefits, including improved efficiency in a circuit as specialised as this one. There are other benefits, notably loudspeaker isolation. There will be no D.C. output offset voltage and no chance of blowing your loudspeakers if something goes wrong in a DIY circuit like this one. The transformer has a simple 1:1 ratio, meaning it could be bifilar wound.

IMPROVED

STEREO DECODER FOR MONO VALVE TUNERS

Now with revised impedance matching, for wider separation, fuller bass and extended treble.

Experience REAL stereo from your Troughline, Quad, RCA, Rogers, etc. Just connect this great sounding decoder to the multiplex output from your mono tuner. Available as a mains powered boxed unit, or an easily assembled kit of parts, or a fully aligned module only. No special tuner alignment needed.

Complete unit £48.50. Kit £28.50. Assembled module £12.50. (Inc. P&P)

STUDIO 12 Nanjivey Terrace, St Ives, Cornwall, TR26 1BQ. Tel: (01736) 798393




Get on our list - to get closer to this list.

- MIT MultiCap • Wonder Cap • Kimber Kap • Solo • Hovland MusiCap • Solen • Siemens
- Wima • Holco • Rel-Cap • Draloric • IRC • Allen-Bradley • Jensen • Resista • Vishay • Mills
- Caddock • Matsushita • TKD • Noble • Cardas • Kimber Kable • van den Hul • Discovery
- Audioquest • MIT • Alps • Bourns • Shalco • Elma • Electroswitch • Nichicon • Gold Aero
- RAM • Mallory • Panasonic HFQ • Nichicon • Elna • N.O.S. • Ruby Tubes • UltraAnalog
- Burr-Brown • Crystal • Linear Technology • Analog Devices • Edison Price • Motorola • UCC
- International Rectifier • Hitachi • MagneQuest • Sonic Frontiers • Pearl • Tube Sockets
- WBT • Neutrik • Sound Coat • Curcio Audio Engineering • Assemblage and other kits

And it's growing and growing. To order The Parts Connection 1995 Catalog & Resource Guide, send £7 and mailing information. You'll also receive a Discount Coupon worth \$10 off a purchase over \$100 or \$25 off a purchase over \$250* as well as *The Breadboard* bulletin to keep you updated on our latest news, information and growth spurts.

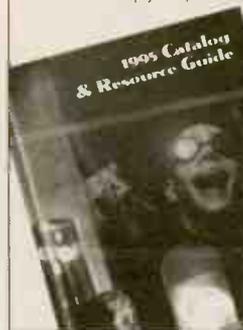*or \$10 US. or credit card information
*catalogue discounts are in US Dollars




THE PARTS CONNECTION

A DIVISION OF SONIC FRONTIERS INC

2790 Brighton Road, Oakville
Ontario, Canada L6H 5T4

Toll Free Order Line 1-800-769-0747
(U.S. & Canada only)

Tel (905) 829-5858 Fax (905) 829-5388

 

Falcon Acoustics Ltd

Incorporating Falcon Electronics Falcon Components

Send for our FREE price list PL24: Just send a large S.A.E. (36p stamp) or \$2 bill (air) overseas. Europe - \$1 bill or 3 International Reply Coupons (IRC)

New and updated FOCAL 'State of the Art' Kits FOCAL 'In-car' & JMLab Speaker Systems.

Increased range of SOLEN 400 & 630v Polypropylene capacitors.

DRIVE UNITS: by FOCAL, and a pick of the best from other manufacturers.

CROSSOVER NETWORKS - Active & Passive Components, Accessories, Large range of Capacitors + Falcon Custom-wound Inductors.

AUDIO AMATEUR PUBLICATIONS

Loudspeaker Design Cookbook, Recipes' Book, Mullard Valve Circuit, and many more - list in P/L. Back year sets of Speaker Builder, Audio Amateur & Glass Audio, plus the Audio Anthology Set.

COMPUTER PROGRAMS

Large selection of Programs available from the very comprehensive Liberty AudioSuite test program via AIRR and LoudSpeaker Ver.6, to the basic Bullock/White Boxresponse.

Also the IMP FFT Test Kit and the Miley Mic Kit

Full details from

(Dept HFV) Tabor House, Norwich Road, Mulbarton, Norwich, Norfolk. NR14 8JT Tel. (01508) 578272

TECHNICAL & GENERAL

Some Necessities - From the Original Classic Turntable Specialists

		P&P	
Connorsseur	BD1/2 Drive Belt	10.25	1.85
	BD1/2 Motor Suspension kit	13.95	2.45
	SAU 2 Headshell	16.75	2.55
	SAU 2 Connecting lead	15.95	3.55
Garrard	<u>Standard Models</u>		
	Wired arm tubes	from 12.75	2.55
	Cartridge carriers (sliders)	10.25	1.85
	Idler Wheels	9.85	2.25
	<u>301/401 Transcription Models</u>		
	Original Thrust pad assembly	10.25	2.25
	Original Idler tension spring	2.95	1.85
	Original Speed control disc - 401	13.75	2.20
	Xeroxcopy Owners Manual 301 incl. full size mounting template	7.85	1.85
	Xeroxcopy Owners Manual 401 incl. full size mounting template	5.70	1.85
	Replacement Intermediate drive wheel	19.95	2.85
	Replacement 301 control knobs On-Off/Speed select	pair 20.25	2.55
	Replacement 301 suppressor unit	5.65	2.25
	Replacement 301 motor pulley (-2%), (-1%), (Std), (+1%)	each 12.65	2.25
Replacement 301 Chrome plated mounting bolts	set 4.70	2.25	
Recommended Lubrication set - early 301 or 301/401 (specify)	5.60	1.85	
Goldring/Lenco	Idler wheel (lock-nut or clip fixing)	19.95	2.85
	Arm Pivot bearings with instructions	8.25	1.85
	Spindle/Main bearing assembly complete	24.85	3.85
	Headshells	from 21.95	2.55
	Instruction books	from 4.20	1.85
Thorens	<u>TD 124 series</u>		
	Idler wheel original	27.50	2.85
	Idler wheel our redesigned replacement	15.35	2.55
	Drive belt	15.25	1.85
	Chassis spring suspension (replaces 'mushrooms')	13.85	2.55
	<u>150/160 series</u>		
	Drive belt	10.25	1.85
	Suspension springs (-1%), (Std), (+1%)	set 11.85	2.55
	Suspension bushes	set 12.50	2.25
	Armboards for most models	from 16.90	2.55
Cecil Watts Dustbugs/Parastats/ (spares incl. Preener wicks)			
Cartridges and styli for 78s & Mono LPs in addition to current Stereo LP			

TECHNICAL & GENERAL PO Box 53. Crowborough, E.Sussex. TN6 2BY Tel:- 01892 654534

AUDIO ENGINEERING

All of us at Audio Engineering wish everyone a very happy xmas and a sonic new year.

And just to prove it, we will include a very high quality 18 range digital voltmeter complete with manual and test leads, FREE!! With every pair of our single-ended output transformers (excluding headphone OTXS), please remember that.

This offer ends on 30th January 1996.

**6 KILO SINGLE- ENDED OUTPUT TRANSFORMERS
ALL BUILT ON A 2 1/2 " STACK OF IMPERIAL E & I 120 LAMINATIONS
TOP SHROUDED, DROP THROUGH, INCORPORATING ANTI- MAGNETIC
INSULATORS COMPLETE WITH FIXING BOLTS AND AMPLIFIER CIRCUITS
WHERE POSSIBLE.**

2200 / 8Ω @ 16.58 TO 1 TURNS RATIO	
2300 / 8Ω @ 17 TO 1	
2500 / 8Ω @ 17.6 TO 1	KT88 TRIODE CONNECTED
2700 / 8Ω @ 18.5 TO 1	
3000 / 8Ω @ 19.36 TO 1	
3200 / 8Ω @ 20 TO 1	
3500 / 8Ω @ 21 TO 1	
4000 / 8Ω @ 22 TO 1	
5000 / 8Ω @ 25 TO 1 PX25	
2200 / 15Ω @ 12 TO 1	
2300 / 15Ω @ 12.4 TO 1	
2500 / 15Ω @ 13 TO 1	
2700 / 15Ω @ 13.4 TO 1	
3000 / 15Ω 14 TO 1	
3200 / 15Ω @ 14.5 TO 1	
3500 / 15Ω @ 15 TO 1	
4000 / 15Ω @ 16 TO 1	
5000 / 15Ω @ 18 TO 1	



PRICE £170 PER PAIR

STOP PRESS!!

By building a ZERO-FEEDBACK, ALL TRIODE, MEDIUM POWERED SINGLE 6V-811-3 AMPLIFIER CIRCUIT DIAGRAMS, CHASSIS LAYOUTS, COMPONENT LISTS ETC FOR THIS PROJECT ARE NOW AVAILABLE. PLEASE SEND £2.50 Cheque/P.O. + S.A.T.

ALL ITEMS INC. P.P. + INS. PLEASE SEND S.A.E.
FOR FURTHER DETAILS, TO P J PERRY
AUDIO ENGINEERING
57 LYNDHURST DRIVE, LEYTON LONDON E10 6JB.
☎ 0181 558 4266

ANDY GROVE'S MOSFET SINGLE-ENDED CIRCUIT

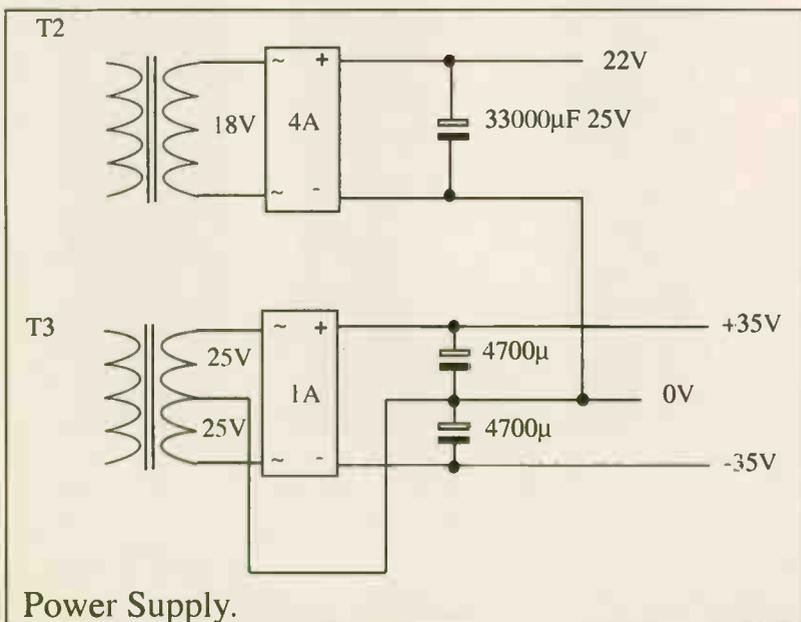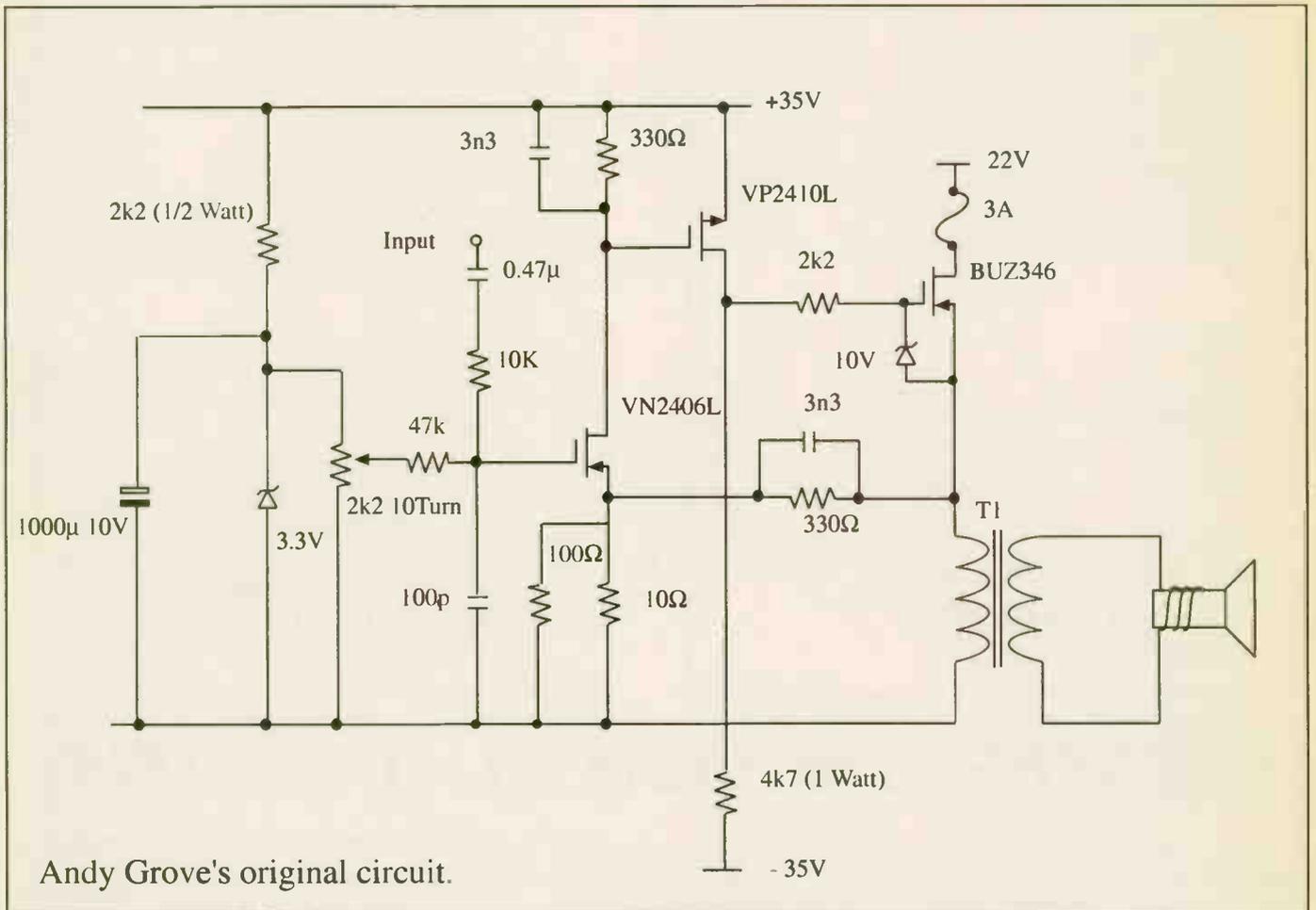

A set of output transformers and circuit boards for the MOSFET single-ended amplifier will shortly be available, please call Tel: 0171 289 3533 for details.

FOXELL & JAMES

*WOOD FINISHES*PAINTS*RESTORATION PRODUCTS*

WE SUPPLY A WIDE RANGE OF DECORATIVE AND PROTECTIVE PRODUCTS.COMBINED WITH A COMPREHENSIVE SELECTION OF WOOD FINISHES INCLUDING STAINS, LACQUERS, VARNISHES, FRENCH POLISHES AND WAXES. OUR STAFF ARE ABLE TO GIVE PRACTICAL ADVICE ON THE USE OF MATERIALS.

FOXELL & JAMES LIMITED
57 FARRINGDON ROAD
LONDON EC1M 3JB

TEL: 0171 405 0152 or 0171 405 2487
FAX: 0171 405 3631

Musical Oasis Co

An Oasis for the home constructor

- > Pair matched valves at low prices.
- > Quality loudspeaker drive units from top manufacturers like:- Morel, Seas & Kar.
- > Exclusive distributor for Keswick Audio magnesium alloy bass, midrange units.
- > Custom wound & standard range of high quality inductors.
- > Passive crossover components.
- > High performance loudspeaker cables & interconnects from major brands.
- > Loudspeaker up-grade components and helpful hints.
- > Treat your system to some real kick ass bass! Now available our new active sub bass kits for Hifi or Home cinema use.

Everything you need to build your own high quality Hifi, A.V, Home Studio or PA loudspeaker system.

Please call to order your 1996 catalogue.
Tel/ Fax (01977) 671823
Mobile (0421) 507842

SPEAKER KITS FROM IPL ACOUSTICS

Over a 9 year period I.P.L. ACOUSTICS have developed a range of high quality speaker kits, using the best units from SEAS, MOREL, AUDAX, and I.P.L. and have produced a comprehensive range of speakers which will compete with the most expensive of commercial designs.


All speakers have biwired crossover kits containing high quality components and terminals.

S5TL
TRANSMISSION LINE



PLUS KIT£373.00
TOTAL KIT£496.00

FIVE
TRANSMISSION
LINE KITS

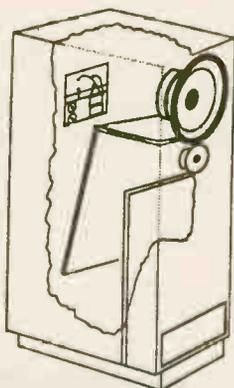

TRANSMISSION LINE
PLUS KITS£166.00 -
.....£373

M3TL
TRANSMISSION LINE



PLUS KITS£166.00
TOTAL KIT£230.00

A2 H.D.A.
AEROGEL KIT



PLUS KIT£185.50
TOTAL KIT£255.00

S3TLM METAL
TRANSMISSION LINE



PLUS KIT£216.50
TOTAL KIT£295.50

PRE-VENEERED CABINET KITS NOW AVAILABLE. Carriage charge extra on all kits.

If you would like further details please send large SAE with 36p stamp for PAGE SPEAKER BUILDING CATALOGUE, comprising VALUABLE ADVICE on DESIGNING, BUILDING, and TESTING speakers and full technical specifications including response curves of eight kits, drive units, and details of SPECIALIST CABLES and ACCESSORIES. KITS FOR A.V. USE NOW AVAILABLE.

I.P.L. Acoustics, 2 Laverton Road, Westbury, Wiltshire, BA13 3RS. Tel: 01373 823333

Connect the dots.



Introducing The Parts Connection's first complete DIY kit: the Assemblage DAC-1 Digital Processor.

It comes in a small package (24cm x 5cm x 18cm chassis), but packs a big punch and a very musical sound. Designed for the rookie or first time kit builder, the only tools required are a pencil tip soldering iron, a screw driver, a wrench, a pair of electronics pliers, and a wire stripper or hobby knife. With only 21 solder joints and a handful of nuts and bolts, this kit goes together in one evening (typically about an hour). It's as easy as connecting the dots.

The parts quality is top notch. The board comes assembled and tested, implementing the Burr Brown 1702 DAC, a Crystal 8412 input receiver, an NPC 5813 digital filter, Analog Device's AD844 and 847 op amps and a custom potted toroidal power transformer.

At \$449 US, the Assemblage DAC-1 offers an outstanding value in digital conversion and comes with a *Satisfaction Guarantee* (return it with-

in 30 days of purchase for a full refund) and an *Assembly Guarantee* (if you can't get it running, we will!). We challenge you to find a DAC anywhere near this price with better measured performance, component quality, and most importantly, sound quality. Call us for more specific information on the performance or construction features.

To order the DAC-1 kit or to order The Parts Connection 1994 Catalog (for £3), full of a lot of other exciting stuff (including a \$10 US discount coupon good on your first order over \$100 US), send us your request and mailing address - or call with credit card information.

2790 Brighton Road, Oakville, Ontario, Canada L6H 5T4
Telephone 0101-905- 829-5858 Facsimile 0101-905-829-5388

ASSEMBLAGE

THE PARTS CONNECTION
A DIVISION OF SONIC FRONTIERS INC.

Toll Free Order Line 1-800-769-0747 (U.S. & Canada only)

F. Langford - Smith Radio Designers Handbook

Langford - Smith Radio designers Handbook is recognised as being the most important reference work ever published.

Vintage Audio are pleased to be able to reprint this important work and bring it to you in its original format. The book contains 1500 pages, in 38 chapters, on every aspect of the design of Valve Amplifier Circuits. Such is the extent of the subjects covered it would be impossible to list them all here. It is best summed up in the Author's preface to the Book

"It has been written as a comprehensive self explanatory reference handbook for the benefit of all who have an interest in the design and application of Audio Amplifiers"

To order your copy at £39 Please call or fax us on:

(011 44) 1239 - 891448

Vintage Audio

BRYNHELYGENEGLWYSWRW, CRYMYCH, DYFED,
WALES.

OVERSEAS DISTRIBUTORS SOUGHT PLEASE CALL (PRINTED TO ORDER ONLY)

UPGRADE YOUR AUDIO

INNOVATIONS AMPLIFIER WITH A VALVE RECTIFIED POWER SUPPLY

For Audio Innovations Series 500/700/800/1000/
1st Audio and 2nd Audio

Replacing the standard Solid-State supply with an off-board Valve Rectified Choke Input Filter Power Supply, will significantly lower Distortion and yield substantial improvements in Dynamics, Bass Control and Resolution. The slow start characteristic of this supply also increases valve life.

Priced at £550.00 inc. VAT and Shipping this unit offers excellent value in terms of performance improvement per pound and will make your amplifier sound like a much more expensive model.

The conversion is reversible, does not devalue your amplifier and is transferable to other models. Comprehensive conversion instructions are provided but some electrical knowledge is essential as potentially lethal voltages are present! Alternatively, definitive audio can do the conversion for an extra £35.00. If you have any doubt about your ability to do this modification safely, please consult us first. VISA and ACCESS welcome.

Please telephone

definitive audio
Brighton 01273 208649

BUILDING THE SINGLE-ENDED, TRANSFORMER COUPLED MOSFET AMPLIFIER, by Haider Bahrani

So you've read the theory, how about the practical? The most important bit with this design is where to put all the chunky bits. By this, I mean the heat sinks, capacitors and transformers. We've tried to put this amplifier together in the cheapest possible way to get the best results.

I've drawn a sketch to show how I put the amplifier together. I've also shown a suggested alternative for those of you who don't mind having an integrated amplifier and hot plate.

The box used is available from Maplin's and the heat sinks came from Electromail. Most of the other components should be available from either of the above, except for the output transformer, which can be ordered directly from us.


As shown, the heat sinks are mounted on brackets directly over the ventilation slots on the floor of the box. The sinks are mounted slightly off the tray itself to reduce the amount of heat transfer, by conduction, to the chassis. There are ventilation slots on the lid too, allowing convection currents to carry the heat away.

The power FETs are best mounted using Silicone Impregnated pads as these eliminate the need for silicone compound which can be a messy business.

The left and right channel amplifiers are on separate boards and positioned as close to the output transistors as possible. This also allows the input signal to take the shortest route to the boards. This does, however, lose some of its appeal if you decide to include a volume control.

The rest of the layout was devised to keep things as symmetrical as possible, low level signal conductors being kept as far as possible from the large signal ones. This includes the output transformer connections to the speaker terminals and boards.

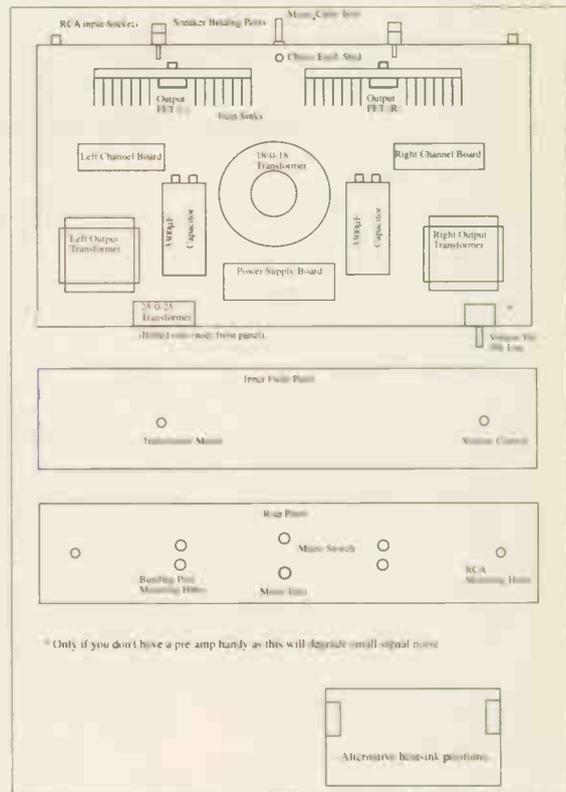Note that the layout shown does not correlate with the PCB layout given.




This is because we initially built the amplifier on Vero Board, seen in the photograph.

15W TRANSISTOR SINGLE-ENDED

Power	16watts
Sensitivity	300mV
Bandwidth	35Hz-40kHz

Distortion

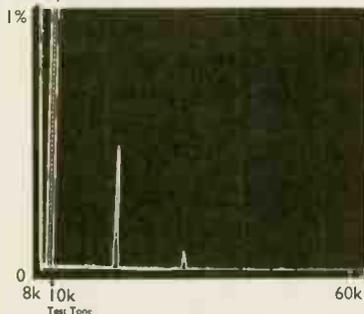

The distortion characteristic for Andy's circuit is identical to Chris's, which is shown above. However, the increased feedback of Andy's yields a figure of 0.05% @10kHz, whereas the lower feedback of Chris's gives 0.5% @ 10kHz, or ten times higher.

SOUND QUALITY

I was struck by the sheer warmth and ease of presentation displayed by this design. It sounded delightfully unforced, which made for very relaxed listening. Strings in particular came over with a richness of tone, but a sense of separation between instruments that was unmatched by today's push-pull designs, most likely due to lack of switching distortion in the crossover region between output devices.

Our prototype had absolutely no glare or hardness in its sound, it was deliciously sweet and easy to listen to, warm and open, rich in its portrayal of tonal colour and impressively able to yield the atmosphere within a recording. There were some defining moments in its audition that I felt summarised its basic character.

A telling old EMI recording of Wagner's Tannhauser, by the Philharmonia, was recorded in 1960.

The string sections of the orchestra usually sound a little shrill and hard. Through this amplifier the effect was audible, but not painful on the ear. There was a sense of the distortion being revealed as parasitic to the music, rather than an intrinsic part of instrument tone. So violins didn't sound thin and screechy, so much as vibrant and real, but with some dissonant harshness creeping in from the recording equipment every now and then. This amplifier also gave the string sections an easy independence from each other that was beguiling; there was space around the musicians.

Its strong but fluid bass was also fascinating. Put these characteristics together and you have a grand, yet easy presentation, with superb reproduction of scale. Orchestras had size and power; there was none of that screechy, pinched sound that characterises mediocre push-pulls. **NK**

AUDIO NOTE AUDIO COMPONENTS PARTS & PRICE LIST

Audio Note

At Audio Note we are committed to providing the highest quality audio components available. Our products are designed and manufactured in Japan, where the finest audio components are made. We have a wide range of products to suit all tastes and budgets, from high-end audiophile components to more affordable consumer products. All our products are guaranteed to be of the highest quality and to provide the best possible sound reproduction. We are proud to be a member of the Audio Note Group, which has been producing high-quality audio components since 1978. Our products are available in a wide range of formats, including CD, cassette, and digital. We also offer a range of accessories, including cables, stands, and speakers. All our products are available at a special price, and we offer free delivery throughout the UK. For more information, please contact us on 01203 251111 or visit our website at www.audiote.com.

AUDIO NOTE OUTPUT TRANSFORMERS

Power Rating	Primary Voltage	Secondary Voltage	Price Ex. UK VAT
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00

COMPLETE KITS

Kit Name	Price Ex. UK VAT
Complete Kit 1	£12.00
Complete Kit 2	£12.00
Complete Kit 3	£12.00
Complete Kit 4	£12.00
Complete Kit 5	£12.00

POSITIVE FEEDBACK

Positive feedback is a key component in many audio systems. It allows for a more accurate reproduction of the original sound, and it can also be used to create a variety of special effects. At Audio Note, we offer a range of positive feedback components, including preamplifiers, amplifiers, and speakers. All our components are designed to provide the best possible sound reproduction, and they are available at a special price. For more information, please contact us on 01203 251111 or visit our website at www.audiote.com.

VACUUM TUBE VALVE

Valve Type	Price Ex. UK VAT
6X4	£12.00
6X5	£12.00
6X6	£12.00
6X7	£12.00
6X8	£12.00

GROUP D

Product Name	Price Ex. UK VAT
Product 1	£12.00
Product 2	£12.00
Product 3	£12.00
Product 4	£12.00
Product 5	£12.00

GROUP B

Product Name	Price Ex. UK VAT
Product 1	£12.00
Product 2	£12.00
Product 3	£12.00
Product 4	£12.00
Product 5	£12.00

GROUP A

Product Name	Price Ex. UK VAT
Product 1	£12.00
Product 2	£12.00
Product 3	£12.00
Product 4	£12.00
Product 5	£12.00

AUDIO NOTE AUDIO QUALITY OUTPUT TRANSFORMERS

Power Rating	Primary Voltage	Secondary Voltage	Price Ex. UK VAT
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00

AUDIO NOTE CHOKE & INDUCTORS

Inductor Value	Price Ex. UK VAT
100µH	£12.00
200µH	£12.00
300µH	£12.00
400µH	£12.00
500µH	£12.00

AUDIO NOTE MAINS TRANSFORMERS

Power Rating	Primary Voltage	Secondary Voltage	Price Ex. UK VAT
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00
100VA	230V	0-230V	£12.00

AUDIO NOTE SILVER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE SILVER FOIL SIGNAL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

At Audio Note we are committed to providing the highest quality audio components available. Our products are designed and manufactured in Japan, where the finest audio components are made. We have a wide range of products to suit all tastes and budgets, from high-end audiophile components to more affordable consumer products. All our products are guaranteed to be of the highest quality and to provide the best possible sound reproduction. We are proud to be a member of the Audio Note Group, which has been producing high-quality audio components since 1978. Our products are available in a wide range of formats, including CD, cassette, and digital. We also offer a range of accessories, including cables, stands, and speakers. All our products are available at a special price, and we offer free delivery throughout the UK. For more information, please contact us on 01203 251111 or visit our website at www.audiote.com.

AUDIO NOTE PAPER IN OIL RESERVOIR CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE PAPER IN OIL SIGNAL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

At Audio Note we are committed to providing the highest quality audio components available. Our products are designed and manufactured in Japan, where the finest audio components are made. We have a wide range of products to suit all tastes and budgets, from high-end audiophile components to more affordable consumer products. All our products are guaranteed to be of the highest quality and to provide the best possible sound reproduction. We are proud to be a member of the Audio Note Group, which has been producing high-quality audio components since 1978. Our products are available in a wide range of formats, including CD, cassette, and digital. We also offer a range of accessories, including cables, stands, and speakers. All our products are available at a special price, and we offer free delivery throughout the UK. For more information, please contact us on 01203 251111 or visit our website at www.audiote.com.

AUDIO NOTE SILVER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE SILVER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE COPPER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE PAPER IN OIL COPPER & SILVER FOIL SIGNAL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE HIGH QUALITY CERAMIC VALVE BASES

Valve Type	Price Ex. UK VAT
6X4	£12.00
6X5	£12.00
6X6	£12.00
6X7	£12.00
6X8	£12.00

AUDIO NOTE HIGH QUALITY STEPPED ATTENUATORS & SWITCHES

Attenuator Value	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE CDEK INTERCONNECT CABLES

Cable Type	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE CABLES & WIRES

Cable Type	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE ACID & CLORIDE FREE SILVER SOLDER

Solder Type	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE PAPER IN OIL RESERVOIR CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE PAPER IN OIL SIGNAL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

At Audio Note we are committed to providing the highest quality audio components available. Our products are designed and manufactured in Japan, where the finest audio components are made. We have a wide range of products to suit all tastes and budgets, from high-end audiophile components to more affordable consumer products. All our products are guaranteed to be of the highest quality and to provide the best possible sound reproduction. We are proud to be a member of the Audio Note Group, which has been producing high-quality audio components since 1978. Our products are available in a wide range of formats, including CD, cassette, and digital. We also offer a range of accessories, including cables, stands, and speakers. All our products are available at a special price, and we offer free delivery throughout the UK. For more information, please contact us on 01203 251111 or visit our website at www.audiote.com.

AUDIO NOTE SILVER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE SILVER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE COPPER FOIL PAPER IN OIL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE PAPER IN OIL COPPER & SILVER FOIL SIGNAL CAPACITORS

Capacitance	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE HIGH QUALITY CERAMIC VALVE BASES

Valve Type	Price Ex. UK VAT
6X4	£12.00
6X5	£12.00
6X6	£12.00
6X7	£12.00
6X8	£12.00

AUDIO NOTE HIGH QUALITY STEPPED ATTENUATORS & SWITCHES

Attenuator Value	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE CDEK INTERCONNECT CABLES


Cable Type	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE CABLES & WIRES

Cable Type	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

AUDIO NOTE ACID & CLORIDE FREE SILVER SOLDER

Solder Type	Price Ex. UK VAT
100µF	£12.00
200µF	£12.00
300µF	£12.00
400µF	£12.00
500µF	£12.00

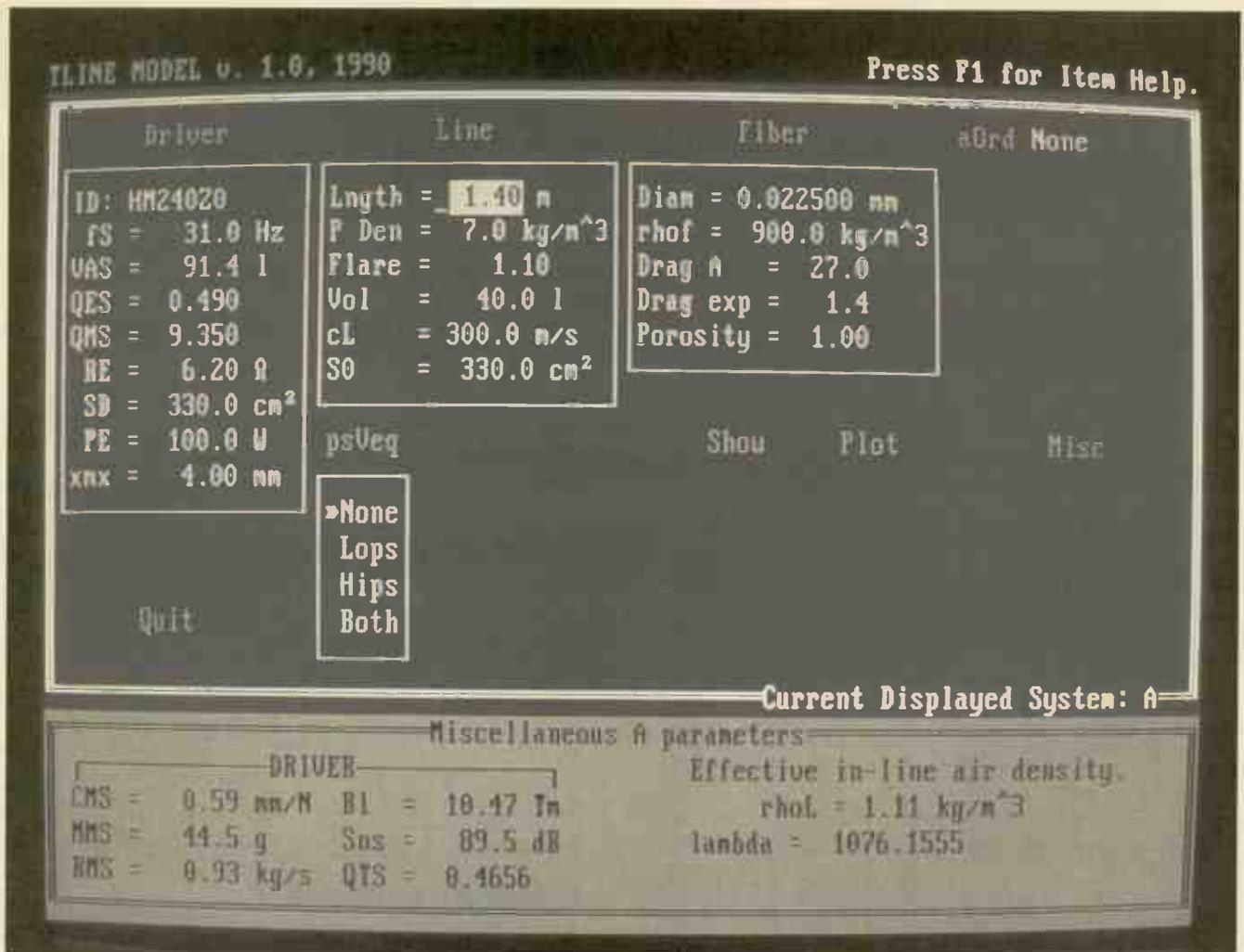

TRANSMISSION LINE LOUDSPEAKERS

Dominic Baker reviews Robert Bullock's TL BoxModel, a transmission line loudspeaker design package for the PC

Transmission line loudspeakers have long been a strong favourite among hobbyists. Their attraction is enhanced by mystique around the basic principle, which is a comparatively recent one. But what seems to compel most constructors is the promise of deep, gut thumping bass.


There are few commercial transmission line loudspeakers. IMF used

to specialise in them and TDL are now the most active in this field. Their loudspeakers are known for extraordinarily deep and powerful bass.

THEORY

In theory, a transmission line should, acoustically, extend to infinity, allowing

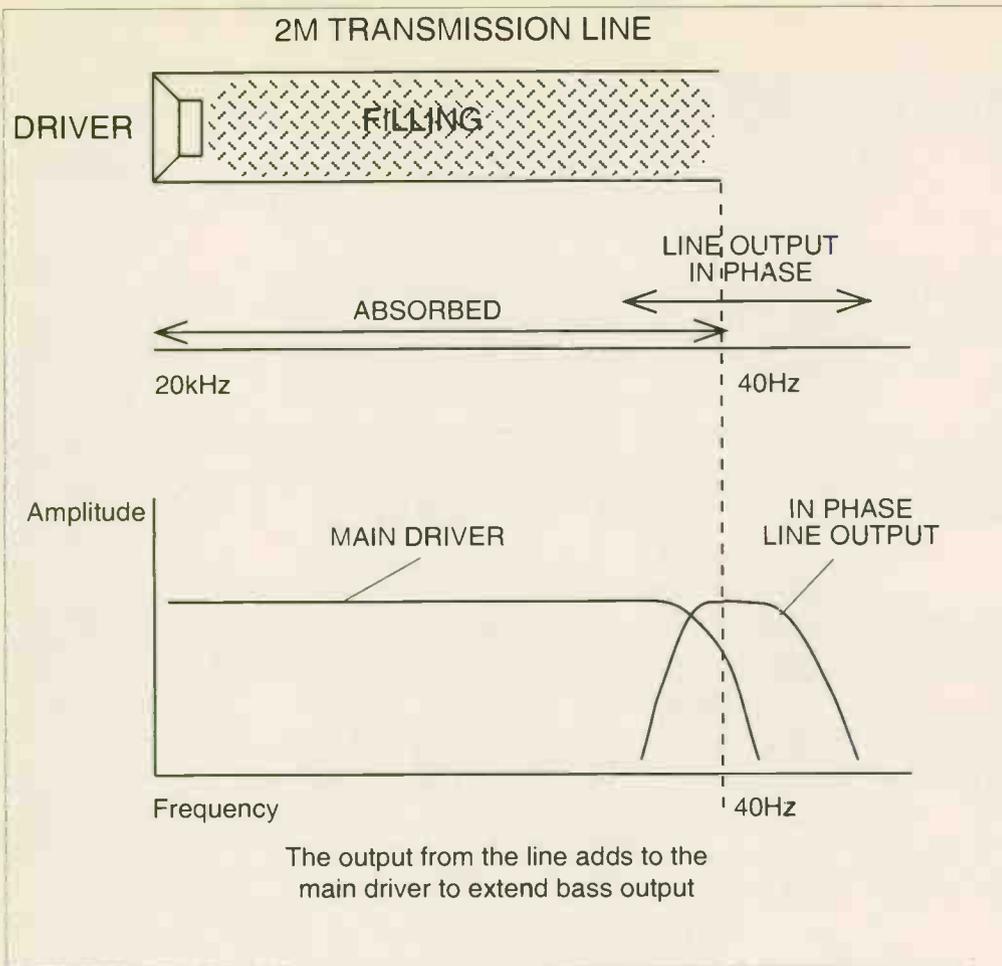it to absorb all of the energy from the rear of the cone. This provides a perfectly resistive termination to the driver. A practical approach to building this kind of transmission line would be to make the line long enough to absorb the rear energy down to the lowest frequency to be reproduced. However, for domestic hi-fi this has its problems, namely size. The line length relates to



In our example, a 2m transmission line is used. The 1/4 wavelength of 2m corresponds to a frequency of 40Hz. At this frequency, the output from the transmission line is in phase with the output of the main driver, adding to its response to extend bass.

the frequency you are trying to absorb, so to reproduce a frequency of 40Hz, which has a wavelength of around 8m, the line will need to be at least this long.

PRACTICE

A practical transmission line loudspeaker is quite different to what theory suggests. The energy that emerges from the end of the transmission line is below the cut off frequency, and will either add to or subtract from the main response, depending on its phase. Frequencies having a 1/2 wavelength corresponding to the length of the line will be in phase with the front radiation of the driver and add to the system response.

A. R. Bailey found that a filling of long hair wool at a density of around 8kg/m³ not only served as an efficient absorber for the line, but at low frequencies appeared to reduce the speed of sound by 50% in the line. This is a very important point. The delay in a line of given length appears to be twice as long when stuffed, so in effect, for the same cut-off frequency the line length

can be halved.

So, in theory the line needs to be comparable to the wavelength of the lowest frequency you wish to reproduce, say 8m for 40Hz. A more practical approach is to allow the rear radiation to add to the forward radiation. Then the line can be 1/2 wavelength long. For a 40Hz lower limit, this line need only be 4m long. The discovery by Bailey that the speed of sound can be slowed by 50% with long hair wool, allows this length to be halved, making it a much more practical 2m long. This last system is what is used in just about all commercial and home-brew TL designs.

TL BOXMODEL

With the cost of high performance PCs coming down by the day, computer aided design packages for designing audio equipment are getting more and more plentiful for the enthusiastic DIYer. We've already seen numerous loudspeaker modelling packages, mainly for simple reflex or sealed types, but

some have branched out as far as isobaric, passive radiator and parallel/series combinations of drivers.

The calculations for these packages are all fairly simple, and can be handled with pen, paper, and calculator if need be. And they should be, initially at least, to gain an understanding of what the parameters mean and how they are derived. This gives invaluable insight into the world of loudspeakers. A good computer package though can open your eyes up to a whole new world in a matter of minutes. Because of the time and complexity involved in manual calculation you are unlikely to get far without computer aided design.

This world of CAD loudspeaker enclosure design allows you to vary the box size, port tuning frequency, ports and their size, ambient temperature, box losses, barometric pressure and more at the click of a button, observing the predicted response - amplitude, phase, impedance, maximum SPL, driver excursion, etc on screen. Powerful stuff, and invaluable to any enthusiast craving knowledge at high speed.

Until now though, I'd never come

The AP ELECTRONICS Route to Musical Happiness EXPERIMENT

With different interconnecting and loudspeaker cables
With SonicLink custom designed mains cables
By changing resistors and capacitors
With large power supplies
By applying simple modifications to improve your circuits
By bypassing high value capacitors with higher quality lower values
Purchased from the AP ELECTRONICS CATALOGUE

LEARN

From your experiments
The features which give the best sound quality.
From knowledge gained through reading AP PERFORMANCE AUDIO

MODIFY

Use the knowledge gained from experimentation
And from tips published in AP PERFORMANCE AUDIO
To rebuild your own amplifiers
To improve the sound quality of your system
To get greater enjoyment from your favourite music.

BUILD

Build your own hifi equipment
From the excellent range of AP ELECTRONIC kits

DESIGN

Design the equipment of your dreams
Make your dream come true
With kits & parts purchased from the AP ELECTRONICS catalogue

A P E L E C T R O N I C S

15 Derwent Business Centre,
Clarke St,
Derby DE1 2BU

Tel: +44-1332-674929 Fax: +44-1332-298836



----- cut out -----

To: AP ELECTRONICS, 15 Derwent Business Centre, Clarke St, Derby DE1 2BU, UK.

Please send me

AP ELECTRONICS CATALOGUE (UK/EC £4.95, Export £6.95) _____

AP PERFORMANCE AUDIO 1996 (Min 3 issues) (UK/EC £5, Export £10) _____

I enclose cheque/P.O. _____ Payable to "AUDIOKITS" or please debit

My Credit Card _____ Exp _/___

FULL NAME _____ SIGNATURE _____

ADDRESS _____

POST CODE & COUNTRY _____

across a similar package capable of modelling a transmission line loudspeaker in the same way.

Transmission lines are a bit of a black art; apart from a few guidelines, like those found in *Quick and Easy Transmission Line Design* by Larry Sharp, there is little real information of any serious weight. Home builders normally have to follow their instincts, pick which advice they feel is most relevant and take the plunge, fine tuning their design perhaps over several years.

this spec. will set you back around £100 second hand, maybe even less with a little searching around.


If you are intending to live your life around TL BoxModel, it is worth using a PC with a maths co-processor, since the program uses calculations involving floating point maths which will otherwise slow things down. Having said this, even a machine with the basic spec. above will turn out four simultaneous graphs in around three minutes - or while you make a cup of tea.

Set the packing density to around 8kg/m³ which, if you are using long hair wool, will slow the speed of sound by around 50% so that a 1/4 wavelength line can be used. Pick a sensible starting point for the line length, around 2m corresponds to a 1/4 wavelength of 40Hz. From experience, Tony has found that with a taper of 1.3, the output from the line will match well with the output from the front of the driver. Reducing the taper to 1.1 will increase bass output, and increasing it to 1.5 reduces it. It is best to use a taper of 1.1 or more to prevent standing waves in the line. The line exit should be set to equal the driver cross sectional area.

Once these parameters are set, you are free to experiment and fine tune the result. A small coupling cavity between the driver and the line, although space consuming, will tend to give a smoother response and deeper bass. As a guideline, for an 8" driver a volume of around 20litres works well.

Tony finds that the default values for Hollofil fibre match long hair wool reasonably well, although he did say that making the stuffing density around 80% of what the package predicts consistently works well in practice. If you intend to use any other type of filling, the exact parameters should be available from the manufacturer concerned.

Other than this, TL BoxModel is relatively straightforward, allowing you to experiment quickly and easily whilst viewing the results on screen. For the TL enthusiast, it is an invaluable tool, giving an insight into how the various parameters affect performance. You'd struggle to ever make sense of this on paper. I have only one criticism. The instructions, which come as text files in the package that you have to print out, are brief to say the least, hence the need for a good book to accompany this package.

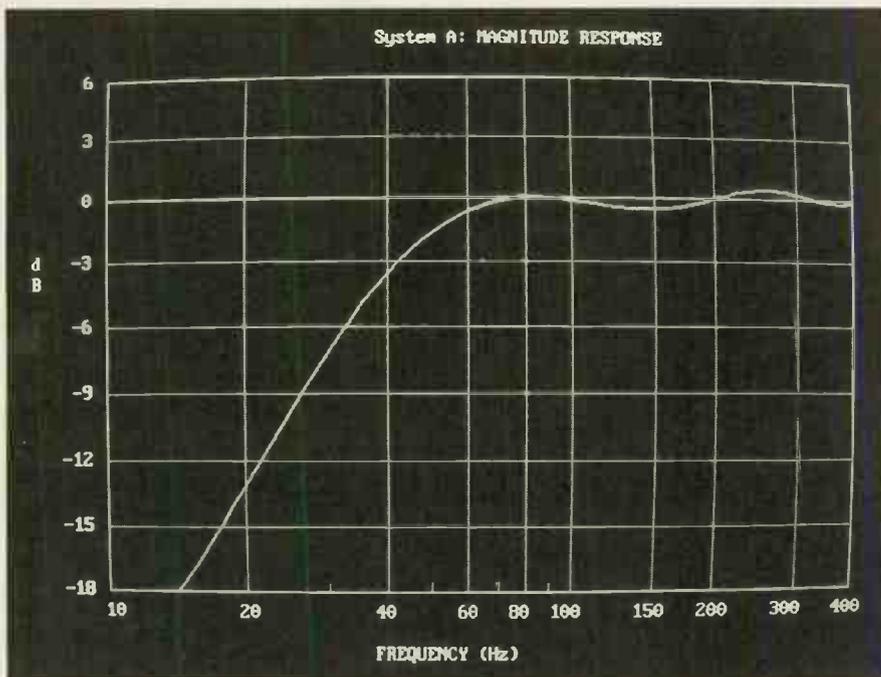

So a computer package that uses the traditional and easy to obtain Thiele-Small parameters to predict the performance of a transmission line loudspeaker is something of a find for the TL enthusiast. TL BoxModel is written by Robert Bullock, a man for whom I am gaining increasing respect as I stumble across more of his work. It is similar to BoxModel (reviewed in *DIY Supplement 19*) in operation, but uses a computer model of a transmission line loudspeaker system that uses the acoustic model proposed by Bradbury (*The Use of Fibrous Materials in Loudspeaker Enclosures*, *JAES*, vol. 24, pp. 162-170, 1976).

TL BoxModel is designed for the IBM PC or a compatible, with at least 256K of memory (RAM) and DOS 2.x or higher. This means just about any PC in working order today, and it also means that if you don't already have a PC there is no need to be disheartened. A PC of

USING TL BOXMODEL

Using TL BoxModel is reasonably simple, but newcomers to transmission line loudspeakers would do well to read as much as possible about the subject. A lot in this package has been left to the operator to make decisions upon, leaving a lot of scope for improving and fine tuning your results. But equally there's room for error and confusion.

Luckily, I had Tony Seaford of Marton Music on line for help. He has experimented with many TL loudspeakers and told me this package accurately predicts results very similar to their measured performance. His first piece of advice, and probably the most valuable, was: make sure you pick the right driver. High Q drivers tend to work best in a TL, so aim for a Qts of around 0.45-0.6.

TL BoxModel £50.00

Marton Music
5 Masterson Ave,
Read,
Burnley,
Lancs. BB12 7PL
Tel: 01282 773198

Valve Data Books

The Vintage Audio Receiving Tube Encyclopedia contains data on 18,000 tubes with 28 schematic diagrams for amplifiers from 3 watts to 250 watts push pull to single ended. 575 pages hardbacked black imitation leather. £39

RCA Receiving Tube Manual A high quality reprint of the much sought after RCA Technical Series RC19. contains Tube characteristics with basing diagrams, & outline drawings 380 pages hardbacked green imitation leather. £27

RCA. Audio & Transmitting Tube Manu. A high quality reprint of the famous RCA. TT-5 Series contains data on TTubes up to 4KW Plate input, with technical data, outlines and typical circuits 316 pages hardbacked red imitation leather. £25

GE Tubes - Essential Characteristics. A reprint of the 1973 edition General Electrics Tube data book contains all characteristics starting OOA & O1A includes Foreign to American Tube interchangability chart, industrial /military cross ref Tube data and basing diagrams. 473 pages in hardback dark blue imitation leather. £29

To order your copy please Call or Fax us on:
(011 44) 1239 - 891448 Tel & Fax

Vintage Audio

BRYNHELYGENEGLWYSWRW, CRYMYCH, DYFED, WALES.

KEF CONSTRUCTOR SERIES

Wilmslow Audio

KEF Uni-Q Technology, the unique KEF driver design that delivers a sharply focused sound stage throughout a room, is now available to the home constructor.

KEF's Constructor Series of loudspeaker drive units and dividing networks, may be used in systems of your own design, or by following the KEF kit plans below:

KEF Kit 60 - A two-way bookshelf/stand-mounted loudspeaker using a single 8" Uni-Q drive unit in a compact 18 litre reflex loaded enclosure. The DN60 dividing network allows bi-wiring/bi-amping.

KEF Kit 80 - An 8" Auxiliary Bass Radiator augments the output of the main 8" Uni-Q driver used with a DN80 bi-wireable dividing network. This is a floorstanding loudspeaker with exceptional bass response.

KEF Kit 90 - An 8" dedicated bass unit, 8" Uni-Q and DN90 bi-wireable dividing network give this three way floorstander extended bass output down to 35 Hz (-6dB).

KEF have designed a range of drive units and dividing networks which, with simple D.I.Y skills, can be transformed into State-of-the-Art loudspeakers capable of giving years of truly high-fidelity performance.

Kit	60	70	80
Boxed	£215	280	370
Total	£290	370	460

Free DIY speaker catalogue export £3.50

Dept. HFV
Wellington Close, Parkgate Industrial Estate,
Knutsford, Cheshire WAI6 8XL
Tel: 01565 650605
Fax: 01565 650080

Open Tuesdays to Saturdays
4 demonstration rooms

ACCESS VISA
AMEX



KEF Kit 60
2-way bookshelf/
stand-mounted



KEF Kit 80
2-way floorstanding



KEF Kit 90
3-way floorstanding

LANGREX SUPPLIES LTD

DISTRIBUTORS OF ELECTRONIC VALVES, TUBES AND SEMI-CONDUCTORS AND I.C.S.

PHONE
0181 684 1166

1 MAYO ROAD • CROYDON • SURREY CR0 2QP
24 HOURS EXPRESS MAIL ORDER SERVICE ON STOCK ITEMS

FAX
0181 684 3056

A selection of our stocks of **New Original Mullard - Brimar** audio types made in UK.
Many other brands available.

STANDARD TYPES			SPECIAL QUALITY TYPES			
ECC81	MULLARD	6.00	A2900/CV 6091 GEC		17.50	
ECC82	MULLARD	6.00	E88CC - GOLD PIN MULLARD		8.50	
ECC88	MULLARD	6.00	E88CC SIEMENS GOLD PIN		8.50	
ECH81	MULLARD	3.00	E88CG01 / CV2493 GOLD PIN MULLARD		10.00	
ECL82	MULLARD	3.50	E188CC - GOLD PIN MULLARD		8.50	
EF86	MULLARD	10.00	ECC81 - M8162 / CV4024 MULLARD		6.50	
EL33	MULLARD	10.00	ECC81 - 6201 / GOLD PIN MULLARD		8.50	
EL84	MULLARD	6.00	ECC82 / CV4003 MULLARD		6.50	
GZ32	MULLARD	8.50	ECC83 / CV4004 BRIMAR		6.50	
GZ33	MULLARD	6.00	EF86 - CV 4085 GEC		12.00	
GZ34	MULLARD	15.00	ECC83 - CV 4004 MULLARD		8.50	
5Z4G	BRIMAR	5.00	AMERICAN TYPES			
6SL7GT	BRIMAR	4.50	5 R4GY RCA	6.00	12B7A GE	7.00
6SN7GT	BRIMAR	4.50	5 Y3WGTA / B SYL / GE	3.50	6146B GE	15.00
6V6GT	BRIMAR	4.25	6 FQ7/6CG7 SYL	7.50	6550A GE	20.00
			6L6GC GE	12.50	7027A GE	20.00
			6L6WGB SYL	10.00	7581A SYL	15.00
			12AX7A GE	7.00		

THESE ARE A SELECTION FROM OUR STOCK OF OVER 6000 TYPES. PLEASE CALL OR FAX FOR AN IMMEDIATE QUOTATION ON ANY TYPES NOT LISTED. WE ARE ONE OF THE LARGEST DISTRIBUTORS OF VALVES IN THE UK. SAME DAY DESPATCH VISA/ACCESS ACCEPTABLE. OBSOLETE TYPE A SPECIALITY. MIN ORDER £10.00.

VISA

OPEN TO CALLERS MON.-FRI. 9AM - 4PM. CLOSED SATURDAY
P&P 1-3 VALVES £2.00, 4-6 VALVES £3.00 ADD 17.5% VAT TO TOTAL INC P&P

Access



These days the valve, or vacuum tube I should perhaps say, is moving firmly into the mainstream of high fidelity. The interest, time and effort being invested in its revival are shown by this book, which is a visual tribute more than a technical treatise. Printed on heavy, high quality white paper, it's a coffee table ode to the tube. The publishers use lavish print quality to reveal, in rich colour and fine detail, the aesthetics of tube amps from around the world.

Introductions by Paul Kavsek and, especially, Ludwig Flich, identify the essence of the tube's attraction, without engaging in polemic. Their sentiments reflect what seems to be a universal appeal, for tube amps are springing up in what must be frightening profusion for anyone whose business is based on little black things that go 'phut'.

In case by now you are wondering, this book is published in Austria. It contains numerous designs alien to UK shores, such as the kitsch Grundig Fine Arts CD preamplifier. When you reflect upon the fact - reflect being the right word because Fine Arts products are smothered in gold plate for the German market - that Grundig are a part of Philips, the fact that even the big boys are starting to take this thing seriously is demonstrated here. Just over the page lies Taiwan's Compass 300B, from Golden Wave, a new one to me. Japan's Ongaku is shown, America's VAC and many, many more glossy, plated and bejewelled behemoths, covering 160 pages, which makes about 80 in all.


There is variety aplenty, but curiously an unusual number of the designs produce 100watts. This is interesting, since in their day only PA amplifiers using GEC DA70s and such

like aimed for such stratospheric powers. At home, in the heyday of the hi-fi valve amplifier, 20watts was considered enough. Many of the amps pictured here are, then, designed for today's world, where disposable incomes can cope with, even demand, items built like a gold plated Forth Road Bridge.

It is here this book's coverage jars a

TUBE AMPLIFIERS

reviewed by Noel Keywood

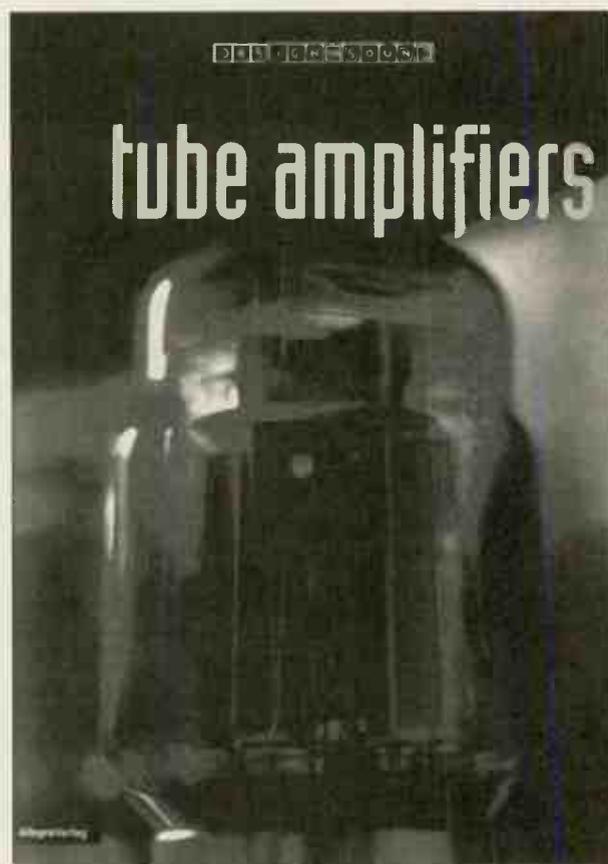

little on my senses. Valve amps that seek to mimic transistor amplifiers generally sound a lot worse in my experience and, irrespective of any conspicuous extravagance, fail to deliver the sonic goods. I suppose my real fear is that if people are sold expensive pups, then the valve revival is likely to fizzle out pretty

quickly, misrepresented by those who understand little about valves and care even less about what they can offer, other than a quick profit (or so they think). Being in a position of designing, testing, reviewing and listening to valve amplifiers, my fears are shaped by experience.

Not included in the book are rarities like Gaku-On and Marantz's latest wonder (they're also a part of Philips!), but rather a selection of what is currently available. Nor are there any prices, which reduces the Wow! factor somewhat. Up front, however, taking pride of position on the first colour spread is a lovely acknowledgement to Harold Leak: a picture

of the workmanlike Leak TL10 Point One, now a classic. Many are still in use of course and their owners usually swear by them. Once a valve man, always a valve man, at least with an amplifier of this nature.

Britain's Graham Tricker has contributed to a technical introduction that aims to provide a simple understanding of the history, construction and technical development of the tube, which in his terminology becomes the valve once again. Many circuit topologies are drawn in outline and even output transformerless configurations are mentioned, although not in detail.

Tube Amplifiers is a colourful compendium of modern valve amplifiers, beautifully pictured, to tempt all those who have just discovered their existence and are curious to learn more. It

brings home forcefully just how much activity there is around the world and how different in style most valve amplifiers are from the modern black box.

Tube Amplifiers is available through the Hi-Fi World library.

Vintage Audio Valves/Tubes

ECC81	(New Boxed Philips or JAN)	£2.50
ECC82	(New Boxed Philips or JAN)	£2.50
ECC82	(New Boxed Mullard)	£3.75
ECC83	(New Boxed Philips or JAN)	£3.75
CV4003	(ECC82 New Boxed)	£1.70
7199	(National USA)	£12.00
6080WA	(New Boxed MULLARD)	£6.58
6336A	(New Boxed USA)	£28.00
300B	(USA)	£135.00
VT4C	(National USA)	£28.00
VA50	(300B Substitute Octal Base)	£32.00
6L6A	(USA)	£11.00
58254A	(807 EQUIV)	£4.50
828	(USA VERY RARE)	£125.00
TT21	(New Boxed GEC KT88 with Top Cap)	£32.00
5U4G	(USA)	£3.50
54GGY	(USA)	£5.75

NOTE! Sold in Matched Pairs or Quads only Minimum order value £20.00 plus VAT carriage at cost

We are always looking to buy the following TUBES 13E1 (New or Ex Equipment), 813, 838, 7241, 6C33, 6146, TBY 350, 613, 6146, PT15, DA100

CALL or
FAX us on
(01239)
891448
TEL & FAX

Vintage Audio
BRYNHLYGEN
EGLWYSWRW, CRYMYCH,
DYFED, WALES
SA41 3SS

Riverside Audio

18, Riverside, Cambridge CB5 8HL. Telephone/Fax: (01223) 512253

Our aim at Riverside Audio is to enable the home constructor to build valve amplifiers which combine superb sound quality with the professional finish of the best high end products - at low price. Our proven designs ensure that you get long and trouble free service from your amplifier. We offer our amplifiers in various forms, from circuit designs through printed circuit boards, to full kits and even fully assembled amplifiers for those who cannot wait to listen to them.

The Riverside 4040 is our integrated amplifier. It features dual mono construction and has five line level inputs and both 4 and 8Ω outputs. The output stage is configured in the classic McIntosh connection, which gives stable, wide-band operation even with difficult loud speaker loads. The stainless steel chassis and transformer cover are hand polished to a mirror finish, and come with semi matt black valve cover. 4xEL34, 4xECC83, 2xECC82. A full description, including circuit diagram, is given in our manual, £6.50. Kit £780, fully assembled £995.

Technical specification: dual mono construction, 40W / channel, 12Hz to 25kHz power bandwidth, distortion 0.1%, five line level inputs, tape output, 230/240V mains input.

Amplifier circuit board: board only £49.50; component pack (including valve bases), add £63; populated board £125; full valve set, add £45. Power supply board: board only £20.50; component pack, add £44; populated board £66. Input board: board only £15.50; component pack, add £16; populated board £33.

The output transformers are configured for McIntosh connection and have excellent low frequency response, and have primary reflected impedance of 3800Ω. Full connection instructions provided. Price £70. The mains transformer is wound for dual mono construction, as this gives superior isolation between channels which sharpens imaging and eliminates inter-channel ground loops in the amplifier. Primary 0-230-240V. Secondaries 2x295V@0.25A (0.4A int.), 2x70V@30mA, 2x70V@5A. Price £60. Other primary voltages can be supplied to special order. Reference book giving connection diagrams, specifications, as well as circuits for using these transformers, £5.

The chassis, comprising main chassis and transformer cover, is hand polished, welded 1/16" stainless steel - NC machine tooled for a perfect fit and clean finish. Each kit also includes a mesh valve cover and baseplate, finished in semi matt black.

Price £310. Also available in mild steel finished in black, £195. For those who wish to use one of these high quality chassis for their own projects, details of the chassis are given in the 4040 manual, £6.50.

Connector kit: 12x gold plated phono connectors, two sets of loudspeaker terminals, an IEC mains socket with integral fuse and switch, and an IEC mains lead with fitted 13A plug, £51.50. Cable kit: all cables required for the 4040, £6.

The Riverside P2 phono preamplifier is designed to partner the Riverside 4040 for those who enjoy the vinyl sound. Equalization is provided for moving magnet output to line level. The P2 features a high accuracy feedback RIAA equalization circuit, ensuring a natural tonality, and a regulated high voltage supply per channel. 3xLCC83, 1xECC81, 2xECC82. Full details and circuit diagram are in the reference manual, £6.50. Kit £225, fully assembled £275.

Technical specifications: 47kΩ input impedance, 1kΩ output impedance for driving long interconnects.

Circuit board: board only £25; component pack, add £37.50; populated board £70; full valve set £20.

The mains transformer is wound for dual mono construction and is toroidal for low leakage flux. Primary 0-230-240V. Secondaries 2x295V@20mA, 2x6.3V@0.45A, 16V@1A. Price £30. Other primary voltages can be supplied to special order. These transformers are also suitable for power supplies in preamplifiers and other line level valve circuits - details in P2 manual, £6.50.

The chassis (main chassis and transformer cover) is made from mild steel. Each kit comes complete with mesh valve cover and base plate, finish in black, Price £110. For those who wish to use high quality chassis for their own projects, details of the chassis are given in the P2 manual, £6.50.

Connector kit: four gold plated phono connectors, IEC mains socket with integral fuse and switch, and IEC mains lead with fitted 13A plug, £15.

We normally ship within three working days. If we do not have the item in stock we will advise you of expected delivery and confirm before dispatch. P&P (in UK): £2 for each part of £40, maximum of £10; manuals free of charge, assembled units despatched by courier free; courier service for £10 on other items.

Write, phone or fax for a catalogue sheet of the full range of Riverside products. Please note our new number.

AUDIO LINKS

AUTUMN 1995 CATALOGUE


SPECIALIST COMPONENTS AT
REALISTIC PRICES

TEL/FAX 01724 870432

DIGITAL STORAGE OSCILLOSCOPE

\$230.

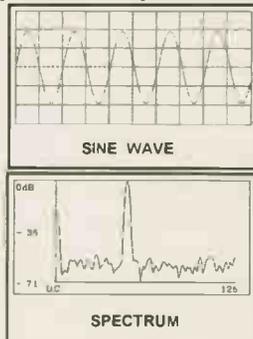The O-SCOPE is a pocket-size module that plugs into a PC's printer port and turns it into a DSO, Spectrum Analyzer, Freq. Counter, DVM and Data Logger. Accepts standard probes.



Operating parameters easily adjustable and continuously displayed. Bandwidths to 22 KHz for the O-Scope I and to 250 KHz for the O-Scope II which also features phase measurement and external trigger capabilities. DOS print screen or log to disk.

O-Scope I, Single Trace \$230.
O-Scope II, Dual Trace 390.
Probe, x1, x10 30.
Sound Level Meter 55.

Prices include software, cables, power supply, instructions and U.S. Airmail shipping cost.

ALLISON TECHNOLOGY CORP.
8343 Carvel Houston, TX, 77036 U.S.A.
Tel: 713-777-0401
Fax: 713-777-4746
BBS: 713-777-4753

Pay by VISA, MasterCard, American Express or Bank Wire Transfer.
Satisfaction Guaranteed.

AUDIO! AUDIO!

JONATHAN HILL

In Jonathan Hill's preface to *Audio!* he marks his position by saying "hi-fi's golden age spanned the 1950s through to the 1960s". This really embraces vintage audio, rather than the full span of audio history stretching from the thirties to the present day. As an organiser of and visitor to vintage audio fairs, including the Audiojumble organised by his Technical Editor John Howes, Jonathan Hill is a vintage buff.

Since John Howes is also a collector of vintage audio, with a fantastic collection of equipment, enough to fill a museum it's rumoured, it is easy to see they're both keen and well grounded in the subject. This enthusiasm lies behind the book.

Audio! Audio! is basically a collectors guide, listing vintage audio amplifiers, valve and transistor, between the period 1945-1972. It is one of the most complete guides available, listing over 150 manufacturers and some 800 products. The listings are headed by the manufacturers name and address, and in some cases a brief note about the company. For example for H. J. Leak & Co. "The trademark, 'Point One', which is widely associated with this company, was originally applied to the first audio power amplifier having a total harmonic distortion as low as point one of one percent. This dates back to June 1945, when, as a result of wartime research in his laboratory, H. J. Leak revolutionised the performance standards of audio

AUDIO! AUDIO!

- the British hi-fi spotter's directory of classic audio amplifiers & control units by Jonathan Hill, Technical Editor, John Howes. Reviewed by Dominic Baker.

amplifiers and designed the original 'Point One' series, beginning with the Point One Type 15".

"At a time when 3 or 4 percent distortion was commonplace in amplifiers, the news of this almost distortionless amplifier was at first greeted with scepticism by the electronics industry. But Leak's figures were subsequently confirmed by the National Physical Laboratory and soon became an accepted world-wide standard. Together with the Williamson circuit and amplifiers produced by Lowther and Quad, Leak amplifiers were at the forefront of a developing British hi-fi industry which by the late 1950s was renowned throughout the world".

The 'Point One' was indeed a landmark product in the evolution of amplifier design, and like a few other innovative and unique products listed in *Audio! Audio!*, I felt it deserved a more detailed description, a circuit diagram maybe, showing the triple loop feedback system Leak used to get such low distortion.

Individual products are listed, together with a couple of lines worth of basic description. This includes an indication of the dates that a particular product was on sale and its original price in pounds, shillings and pence. Younger readers needn't worry though, John Howes includes a conversion table to modern pounds with decimal pence.

There are brief technical details too, where possible giving power output, inputs and their sensitivity, the valve line up and transformer output impedance

taps. In some cases more information is provided, but descriptions are kept short, probably due to the number of amplifiers covered.

The brief introductory paragraph carries two graphs, one showing a comparison between valve and transistor amplifiers available on the market between 1945 and 1970, showing the sudden take-over of transistors around 1966. The second graph covering the same period shows in more detail the break down of valve amplifiers; mono and stereo integrated and power amplifiers shown separately. This is interesting, but little more.

Following on are a couple of pages on record equalisation curves used through the 1950s, and a short history of the valve and how it was developed. I suspect space was at a premium here, because although there is enough of a description to get a feel for how the valve developed through its life, this chapter could certainly have been expanded on further.

It would have been nice to see circuit diagrams for some of the more original or innovative designs, and a description of what they achieved. It would have been even better if each caption could have carried a picture, and a ranking system for their rarity/value would also have been valuable. It must have been a mammoth task just to assemble the information here though, but hopefully Jonathan will expand on this work in future, building it into an invaluable reference guide. As it stands though, it is still the most complete listing of its kind we have come across.

NVA

BLACK BOX RANGE KITS

A range of easy to assemble solid state kit amps, with fully tested and fitted printed circuit boards. If you are competent with a soldering iron these kits should be no problem. A full rebuild and sort out service available.

AP30	Integrated Amplifier	230.00
AP50	Integrated Amplifier	320.00
	Phono Stage Fitted	70.00
A60	Stereo Power Amplifier	300.00
A70	Mono Power Amplifier	570.00 Pair
A80	Mono Power Amplifier	880.00 Pair
P50	4 Input Pre Amp	180.00
P90	6 Input Pre Amp	240.00
	Phono 1 MM or MC Phono Unit	170.00
	Phono 2 MM or MC Phono Unit	240.00
	P.S.U. Power Supply for Phono 2	180.00

EX REVIEW/DEMONSTRATION STOCK BARGAINS, The Emotive Statement (TES) CD Player 1000.00 RRP 2000.00

NVA, 6 Watermill Ind. Est., Aspenden Road, Buntingford, Hertfordshire SG9 9JS

Tel: 01763 272707 Fax: 01763 271594

SOWTER TRANSFORMERS

Sowter Transformers have been used by the Professional Audio Market throughout the world for at least the last twenty - five years.

Using modern technology and Computer Aided Design we are now able to offer a complete design and manufacture service.

Our current lists show a range of over 50 output, 70 power transformers and nearly 30 chokes.

E.A. SOWTER LTD

P.O. BOX 36, Ipswich IP1 2EL

SEND S.A.E. FOR DETAILS

Tel: 0473 252794. Fax: 0473 236188



Vacuum Tubes for Audio Are Back!

Glass Audio brings together yesterday's tube with today's improved components, voltage control, and the exciting new Soviet tubes, to make smooth sound in your livingroom possible again!

YES!

Please send my first issue of *Glass Audio*. I'll pay just \$45.00 for six issues (1 year); \$80.00 for 12 issues (2 years) of the best information on tubes to be found anywhere. I understand that my satisfaction is guaranteed!

Name _____

Street & Number _____

City _____ Postal Code _____

Country _____

REMIT IN US \$ DRAWN ON A US BANK ONLY. PRICE GOOD THROUGH DECEMBER 31, 1995.

We Accept MC/VISA.

Glass Audio

PO Box 176, Dept. HFWS, Peterborough, NH 03458-0176 USA
Phone: (603) 924-9464 or FAX 24 hours a day (603) 924-9467

AUDAX HM240Z0

Dominic Baker takes a look at a brand new 10" High Definition Aerogel bass unit from Audax.

Audax have recently introduced a new drive unit to their range of High Definition Aerogel (HDA) drivers, a 10" bass driver. This is the largest driver in the HDA range, promising deep and powerful bass. We ran a few tests to give DIYers an idea of its potential, which are detailed here along with the driver's Thiele-Small parameters.


EXAMPLE CROSSOVER

I quickly found the HM240Z0 an easy driver to control. A simple 2nd order crossover comprising a 2.6mH series inductor and 150µF capacitor across the driver's terminals gives a very flat and useable response as shown in the plot below. The -3dB point is 450Hz in this example, a sensible point well away from cone break up but high enough to match well with just about any midrange driver.

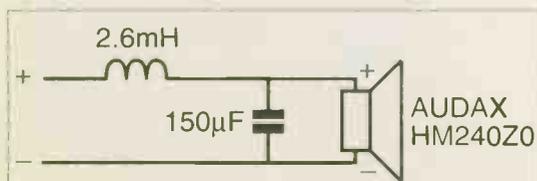EXAMPLE ENCLOSURE

In a 60 litre reflex enclosure tuned to around 30Hz, the HM240Z0 reaches 35Hz (-3dB). This is plenty low enough to play fundamentals well. The HM240Z0 will go a lot lower in a bigger enclosure, but I stuck to a limit of 60

litres because it is a sensible size for a domestic loudspeaker. If you decide to follow this guideline, start with a port of 70mm diameter and 150mm length.



A simple 2nd order filter using the circuit shown to the left gives a very smooth response rolling off at 450Hz, as shown in the plot on the right.


DRIVER PARAMETERS

Nominal Impedance	Z	8Ω
Minimum Impedance	Zmin	6.5Ω
DC Resistance	Re	6.2Ω
Resonance Frequency	Fs	31Hz
Total Q Factor	Qts	0.46
Equivalent Cas air load	Vas	91.4x10 ⁻³ m ³
Effective Piston Area	Sd	3.3x10 ⁻² m ²
BL Product	BL	10.51NA
Power Handling	Pnom	100W
Sensitivity	n	89dB



The HM240Z0 will shortly be available from World Audio Design, please call Tel: 0171 289 3533 for details.

Frequency Response

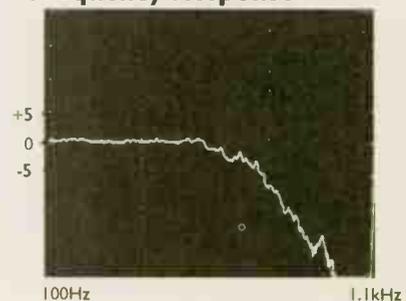

KIT & COMPONENT SUPPLIERS

LOUDSPEAKER KIT SUPPLIERS

Falcon DIY Speakers

Falcon Acoustics Ltd. Tabor House, Norwich Road, Mulbarton, Norfolk NR14 8JT. Tel. 01508 578272
UK distributors of FOCAL drive units, Kits, in Car and JMLab speaker systems plus SOLEN (SCR - Chateauroux) polypropylene capacitors and the largest audio inductor manufacturer in the UK. Stocking Audio Amateur Publications and Computer software. Comprehensive range of D.I.Y Speaker kits, Parts, Accessories and Books.
Please send large SAE (36p) for free price list.
"Everything but the wood"

Audiocab

9 Skew Bridge Close, Wootton Bassett, Swindon, Wilts. SN4 7DW. Tel: 0793 848437.

Loudspeaker cabinet kits are the speciality of "AUDIOCAB". Whether you are prototyping your own loudspeakers or working to a design published in Hi-Fi World, including the KLS3, "AUDIOCAB" will produce a bespoke kit to your specification. "Biscuit jointing" is used to ensure perfect alignment of adjacent panels and cabinets are dry assembled and sanded before dispatch. David Barfield, proprietor, says "no prior experience of woodwork will be required to build our kits and achieve a professional finish". Kits will normally be supplied in 25mm unfinished MDF but any finish is available and designs are usually enhanced by the use of mouldings to escape from the normal "square box". Ready built cabinets can also be specified. Professional, trade and retail enquiries are invited.

Wilmslow Audio

Wellington Close, Parkgate Trading Estate, Knutsford, Cheshire WA16 8DX
Tel. 0565 650605 Fax. 0565 650080

Extensive range of drive units and over 30 different designs of self-assembly kit. Two 'ATC' kits now available. Drive units include those from KEF, Dynaudio, Audax, SEAS, Peerless, Scanspeak and Morel. Everything required for the loudspeaker builder and four dem rooms to listen to the kits in built-up form. Two new kits from Morel - one 3 litre, magnetically shielded, one 11 litre book shelf.

IPL Acoustics

2 Laverton Road, Westbury, Wilts BA13 3RS. Tel. 0373 823333

IPL supply a range of eight speaker kits using drive units from SEAS, Morel, Audax, Visaton etc. including four transmission lines to suit all room sizes. We also supply a full range of drive units, capacitors, and cabinet accessories as well as silver plated P.T.F.E. insulated cables.

UPLIFTING SOUNDS - Tel: 0121 777 4196

Offers assistance in the design and construction of loudspeakers and audio furniture. From innovative to stylistic talk through your ideas with an enthusiast and choose your own level of involvement.

VALVE AND OUTPUT TRANSFORMER SUPPLIERS

P.V. Tubes

104 Abbey Street, Accrington, Lancs. BB5 1EE
Tel. 0254 236521/232611 24 hrs a/p. Fax. 0254395361

For all your electronic components. Valves are new in branded boxes and matched pairs are available. *Pls call for types and prices. We are closed all day Wednesday.

Vintage Valves,

PO Box 147, Station A, Vancouver B.C. Canada, U6C 2M3. Fax (604) 876 5876.
Dynaco, Sherwood, Scott, The Fisher, McIntosh, Eico, Harmon Kardon, Heath, Altec, Stromberg - Carbon. Many vintage parts and equipment available on request.
Wilson Valves
28 Banks Ave., Golcar, Huddersfield, West Yorks HD7 4LZ.
Tel. 0484 654650/420774. Fax. 0484 655699.
Mail order. Call us to find out more about our extensive range of valves. Over 1,000 different types stocked. S.A.E. for list. (Please mark for Dept. HFV).

Langrex Supplies Ltd

1 Mayo Road, Croydon, Surrey CRO 2QP
Tel. 081 684 1166 or fax. 081 684 3056

One of the largest distributors of electronic valves, tubes and semi-conductors in the UK by original UK and USA manufacturers. Obsolete types are a speciality. Telephone or fax for an immediate quotation.

Billington Export Ltd.

1E Gillmans Trading Est., Billingshurst West Sussex RH14 9EZ.

Tel. 01403 784961 or Fax. 01403 783519

Billington Export Ltd. holds large stocks of audio valves including many obsolete brands such as Mullard, GEC, Bnmar etc. as well as Sovtek, Thermionic Gold Brand and the recently introduced Billington Gold range. Also Cathode Ray Tubes (eg. used in Marantz tuner 10B). 50 page catalogue available, tel or fax for a quotation. Minimum order £50.00 UK, £100 export.

PM Components

Springhead Enterprise Park Springhead Road, Gravesend, Kent DA11 3HD. Tel. 0474 560521
P.M. Components Ltd are the specialist component company for High End Audio enthusiasts. We have a design and manufacturing base for audio valves and associated products and have a capability to produce custom tubes for major manufacturers. Our 70 page catalogue is available at £2.50 including U.K. postage. P.M. Components are major stockists for Golden Dragon, Mullard, GEC and Teonex valves and have a vast archive of vintage tubes gathered from every manufacturer in the world.

Chelmer Valve Company

130 New London Road, Chelmsford, Essex CM2 0RG. Tel 0245 265865 Fax. 0245 490064.
Supplier of premium range of audio valves, other valves and components also available. (Please see our ad on outside back cover of this supplement).

RESTORATION

GT Audio 5 Upper Road,

Higher Denham, Bucks UB9 5EJ. Tel. 0895 833099

Professional repair/restoration of all hi-fi including classic and vintage equipment. Supplier of very high quality electronic components, in particular types which are difficult to source. Original valves available, i.e.. Mullard, Bnmar, GEC, GE, RCA, Sylvania etc.

COMPONENT SUPPLIERS

Hart Electronic Kits Ltd Penylan Mill,

Oswestry, Shropshire SY10 9AF

24 Hr sales/enquiries. Tel. 0691 652894

A range of Audiophile kits for 80 watt Power Amplifiers, Tuners, Pre-Amps and Moving Coil/Moving Magnet RIAA Pickup Preamps. All kits are fully engineered, with our thirty years design experience, for easy constructions from circuits by John Lindsey Hood, the most respected designer in the field. Send for lists.

V.R.R.

30 Melbourne Ave, Worthing. BN12 4RT. Tel: 01903 501158

Vintage Radio Restoration

We can provide mains transformers, chokes and single-ended or push/pull output transformers as well as silver cable, paper-in-oil capacitors and other goodies all at reasonable prices. Our 30w monoblock short kit is only £299!

AP Electronics

20 Derwent Centre, Clarke Street, Derby, DE1 2BUT

Check out the AP ELECTRONICS 1994 catalogue. It's free with every order of over £40.00 or can be purchased for a £4.95 cheque payable to 'AUDIOKITS'. Over 80 pages include pre and power amplifier kits, high grade audiophile resistors, capacitors and semiconductors, audio and mains cables, gold and rhodium plated connectors and COMPONENT NOTES on using high grade parts. A quarterly newsletter 'AP PERFORMANCE AUDIO' has been recently launched and your first issue is free.

Cambridge Scientific Supplies

12 Willow Walk, Cambridge CB1 1LA.
Tel: 01223 811 716 Fax: 01223 501 833

Specialist wire products for the knowledgeable audiophile including:- Silver wire (>99.99% purity, stress free) unique quadruple PTFE insulated Silver wire, Silver loaded solder, PTFE sleeving and Nylon braid

sleeving, premium Gold plated connectors and plugs. Custom assembly available. Call Peter Bullock for a catalogue and application note.

RushAudio

126 Station Rd., Tempsford, Sandy SG19 2AY. Tel. 01767 640779 Fax. 01767 640617

RushAudio stock high quality British made polypropylene capacitors (630V dc) ideal for PSU applications. 30uF (100mm x 50mm dia) £22; 40uF (100 x 63) £27; 50uF (100 x 63) £32; 100uF (125 x 76) £55. Cabbage: 1 capacitor £2, 2 - £4, 3 or more - £6. Unfortunately VAT is extra on total of goods plus carriage. Cheque with order appreciated for prompt delivery.

Audio Synthesis have in stock the following audiophile components:

A large selection of Vishay Bulk Foil Resistors, WBT audio connectors for pre and power amplifiers, Teflon insulated high purity SilverWire in various diameters, pure silver interconnects and speaker cables. Kits are available for the original PASSION and ProPASSION passive controllers and attenuators. For 1996 brochures and full details please contact:

Audio Synthesis

PO Box 100, Ilkley, West Yorkshire LS29 9XW
Tel: 01943 600404 Fax: 01943 600383

Audio-Links

7 Fairmont Crescent, Scunthorpe, North Lincolnshire DN16 1EL.
Tel. 01724 870432 / 764804

CUSTOM WOUND TRANSFORMERS & CHOKES

Exceptionally high quality items for valve and solid-state designs at realistic prices.

AUDIO - LINKS, "THE GREEN" INTERCONNECT CABLE

Now available in kit form. All the parts you need to make your own reference interconnects at a fraction of the cost. Vast range of highest quality electronic components and accessories for the D.I.Y. enthusiast. VAT incl. prices, mail order and a friendly service. Open Monday to Saturday 10am - 7pm

Russ Andrews Audiophile Components

Edge Bank House, Skelsmergh, Kendal, Westmorland. LA8 9AS
Tel. 01539 823247 Fax. 01539 823317

World leading supplier of the highest quality premium grade components. If you want the very best sounding resistors, capacitors, inductors, volume controls, wire etc. send for our 1994/95 catalogue. We also have a range of our own design of amplifiers, pre-amps, speakers and CD players built with our components. To receive your copy of our 1994/95 catalogue just mail, phone or fax the address above.

VINTAGE DIY

Loricraft Audio

4 Big Lane, Goose Green, Lambourn, Berks RG16 7SQ. Tel. 0488 72267

Specialist restoration of 301's and 401's using genuine spares and re-manufactured parts to original pristine standards in our newly built workshops designed primarily for these purposes.

CLASSIC TURNTABLES

Technical & General

P.O. Box 53, Crowborough, East Sussex TN6 2BY. Tel. 01892 65 45 34.

The original specialist source of spares, replacements and expertise for the classic turntables. Years of actual experience and comprehensive range of parts (originals and re-manufactures), manuals, ancillaries, No dubious 'improvements' - no harmful 'modifications'. Our specialities: Connoisseur, Garrard, Goldring, Lenco, S.M.E.; Thorens, Watts; Ortofon; Shure; Cartridges and styli for 78s, Mono LPs, Stereo LPs.


YOU CAN ADVERTISE IN THIS SECTION FROM AS LITTLE AS

£30 A MONTH

CALL 0171 289 3533

OR

01245 443555

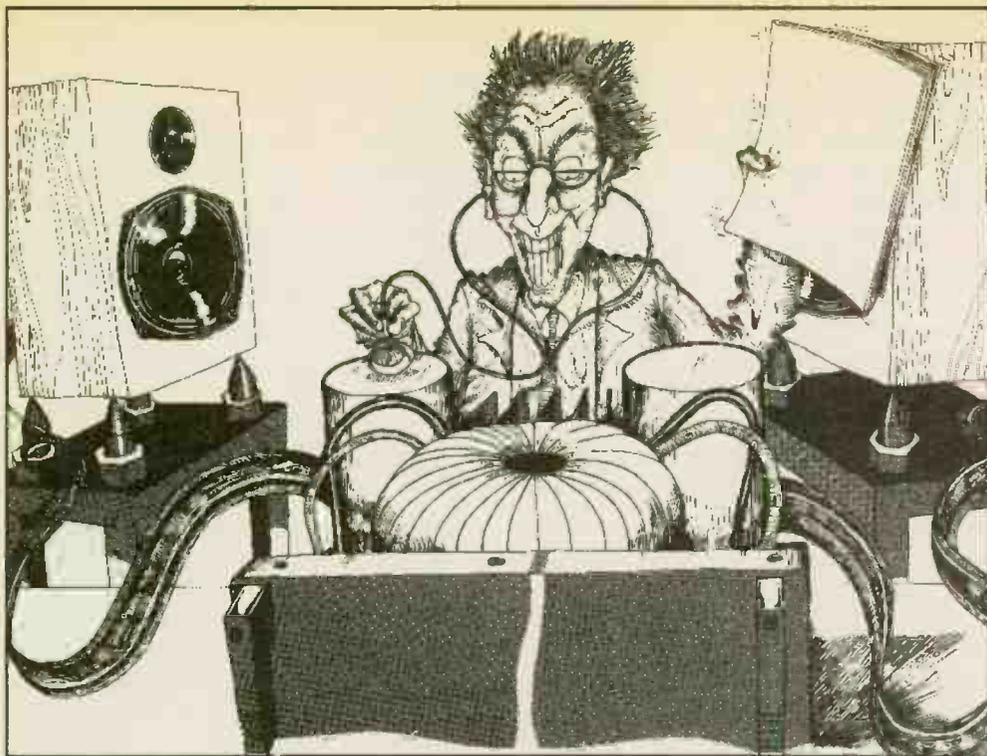

D.I.Y. Letters

ELECTROSTATIC LOVE

I was intrigued to read your article on the Quad/Celestion SL-6000 system in the December edition of Hi-Fi World. I auditioned just such a system about four years ago, but ruled it out on the grounds of cost and domestic unacceptability.

I then had the good fortune to read about the modifications and rebuilds of Quad equipment by Peter Lindley. Not only were his stacked electrostatics a sonic revelation in terms of deep bass, they were also beautiful to look at.

True, these speakers will not deliver cat-scaring, seismic bass but in 99 cases out of 100 they prove more than adequate in the window-rattling department.

For me, stacked Quads are the only answer and involve a lot less sheer heartache than the route to sonic Nirvana you describe in

your article.

**Andrew Mackay
Malvern,
Worcestershire**

Stacked Quads are a legendary arrangement and represent a form of audio purity we could hardly criticise. But they are somewhat intrusive.


Our DIY articles are meant to stimulate ideas and experimentation. They are not offered as definitive solutions, a crazy notion in a field that is so subjective.

In that particular article, the Quad high pass section offers a purist high pass filter with equalisation, based around just one FET, the highly effective VN10KM, that offers around 120dB

of dynamic range.

Experimenters can use this for many purposes.

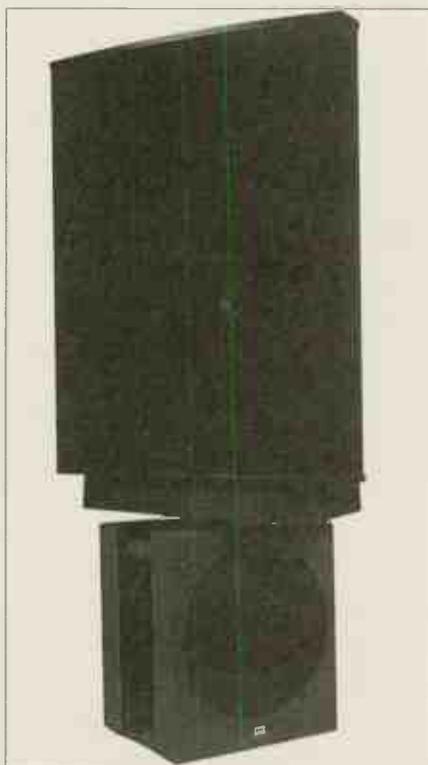The other idea we want to keep alive is the bass dipole. Celestion took this only so far



before deciding it was best abandoned. Our view is that it could have been better developed. We hope to return to the bass dipole to show how this can be done. Behind me lie two massive, high performance Audax bass drivers. Soon they'll find a role in life! NK

REFLEX ACTION

I want to make a new cabinet for my KEF CD7 speakers (B139/B110/T33A) and wish to make them taller with a smaller foot print, i.e. approx. 1000mm high x 300mm x 300mm.

Although the speakers were originally an infinite baffle design and there was a transmission line design, is it worth considering reflex design?

If the bass section in each cabinet is approximately 67 litres, what diameter and length of port should be used and would a front or rear position port be best?

**W J Parish
Bromley,
Kent.**

A drive unit that works well in an infinite baffle is unlikely to give good results in a reflex enclosure. Generally, drivers with a total Q factor (Qts) less than 0.38 favour reflex loading, giving flattest and deepest bass. Drivers with Qts greater than 0.38 tend to work better in a sealed box.

Interestingly the KEF B139 has a Qts of exactly 0.38, so may well perform well in either a sealed or reflex enclosure. However, knowing this driver I would stick with a sealed cabinet, where you should get fastest and best bass quality. The B139 has a heavy cone which, along with the deep bass it is capable of producing, also

We designed our own crossover to match Quad's ESL-63s with Celestion's SL6000 subwoofers. We hope to have our own dipole subwoofer running shortly.

gives it a tendency to sound heavy and slow. The extra damping of the air spring in a sealed box will help minimise this and should give best subjective results. **DB**

VALVE RECTIFICATION

This is, I am afraid, a letter begging some information.

1. I need to specify HT to yield 500V @ 180mA when using bridge connected paralleled EZ81s and π -network filter.
2. The PM6 units for my Lowther Acoustas have shot suspension. However, I do not know, nor can I find out, the address of Lowther Manufacturing Limited. Any idea how much recovering will cost for these units?

I would appreciate it if you could furnish me with the above information, then I can get on with constructing an S.E amplifier (EAR 859 but with valve rectification, hence the question) and finally get the Acoustas back into use. My Castle Richmonds can then be used for a second system.

The main system will consist of Garrard 401, Odyssey RPI, Decca Gold cartridge, home built preamp with valve regulated supply. This is a bit of a hybrid of the above mentioned SE power amp and the Lowthers.

Second system for second hand mono and 78s: Goldring '88', Decca MkI and MkII head, 78 head. Lowther MkIV home built min. tone controls, Lowther LL15s MkI - very nice amp this - and the Castle Richmonds. Also, a cheap Onkyo cassette deck. No CD player for the simple reason that I have no CDs

**David Eggleston
Dundee,
Scotland.**

A simpler approach would be to use a single valve rectifier capable of handling 500V @ 180mA, the GZ37 being one such example. These are cheap and in plentiful supply, so this

would be a good choice. It is impossible to be precise about voltages, because unknowns such as transformer regulation affect final results. You'll have to experiment. We can only give guidelines here.

Firstly, the GZ37, like most Mullard rectifier valves, needs a 5V heater supply, in this case providing 2.8amps.

You will need to use limiting resistors in the anode circuit of the rectifier. The value of these will depend on the mains transformer you use. The total resistance, made up of this resistor and the effective resistance of the mains transformer, must be above 200 Ω or so for the GZ37. The effective resistance of the transformer will be in the region of 100-150 Ω , so a safe value to start with for this series resistor will be around 100 Ω .

The GZ37 itself, like any valve rectifier, will drop volts - expect around 60V or so across it. If you start with a DC line

requirement of 500V, you'll need in AC RMS of 353V. At 0.18A the surge limiting resistor will drop 18V, the valve itself will drop around 60V so the transformer must supply around 430V AC RMS. The exact voltage will depend on the value of the capacitors you use and the DC resistance of the choke in the π -filter. Aim for a 450V-0-450V AC RMS transformer (on-load).

I hope you can see from this that what you propose to do, although it looks straightforward, is a good deal more complex. To get it right, you will probably need to build several prototypes.

Your second question is a little easier to approach, Lowther can be contacted at: PO Box 184, Sidcup, Kent, DA14 4NL
Tel: 0181 300 9166. **DB**

There are some hidden X factors in power supplies that

conspire to defeat accurate calculation. In particular, transformer behaviour under the short term current draw of a capacitor input filter, which a π -filter has, can affect final DC volts, as can the value of the output capacitor used. The text books are surprisingly coy about all this. You'll have to experiment, since we can only give you rough guidance. **NK**

UPGRADE MISSION

I am writing in response to the crossover conversion of Mission 760i 'speaker in the December issue. I've been using this 'speaker for more than a year now, powered by Mr. Jones's 10 watt Class A transistor amplifier (June issue supplement).

In addition to the gold-plated bi-wireable terminals, I've changed the capacitors and also the 'door bell' wires used in it. For the capacitors, instead of using the cheap

Letter of

DUAL VOICE COILS?

I read with great interest your design for the KLS6 loudspeaker in the August '95 Supplement. However, there are still a couple of queries I would appreciate your views on.

Firstly, upon contacting the Australian distributor for Audax I was made aware that in addition to the bass/mid driver you specify for this speaker (HM210Z0), Audax can also supply a dedicated bass driver (HM210Z2).

This driver appears to have better bass extension and an even flatter response up to the crossover point than the HM210Z0, as well as a lower resonance

frequency and higher BL factor. Its sensitivity is rated at 89dB.

Could this unit be substituted into the KLS6 design to give improved bass performance over what is described as the weakest area of the speaker (merely very good) in David Price's review?

If this is the case, could you please outline any changes that would be required to the crossover, port lengths etc. and what effects this would have on the speakers overall specification.

Secondly, on the midrange/treble response plot there appears to be a severe dip at the crossover

point. Is this as severe as it looks and what effect if any does this have on the sound?

Finally, as the drivers are available here, is it possible for you to supply the crossover kit separately?

**Peter Jeffries
Highett Victoria,
Australia.**

The Z2 version of the HM210 is a dual voice coil model. It does 'appear' to have better bass, 'appear' being the operative word. If you look at the impedance curve you will note that this response is for the two 8 Ω voice coils connected in parallel, giving effectively a 4 Ω loudspeaker.

supplied Alcap, I used audio grade polypropylene capacitors available from Maplin Electronics. For the internal wiring, I used silver-plated 'speaker cable' from the same company on the HF unit and QED 79 strand cable on the bass/mid unit.


On the HF unit I found that the treble level is still too high for my hearing. An attenuation with a 3.9Ω 7W wire-wound resistor in series with the tweeter (between the inductor-capacitor

junction and positive tweeter terminal) finally did the trick. For the bass/mid unit, I found that the original capacitor value produces great bass, but with less bass lines. Changing the value to 1.5μF improves bass lines, with satisfactory bass attack. For me, I prefer the latter configuration.

The 1.5μF capacitor is not available at Maplin. However, you can order one (or two) from Cricklewood Electronics Ltd. Changing the

capacitors means that you have to alter the crossover 'board' inside the 'speaker' because of the relatively big size of polypropylene capacitors.

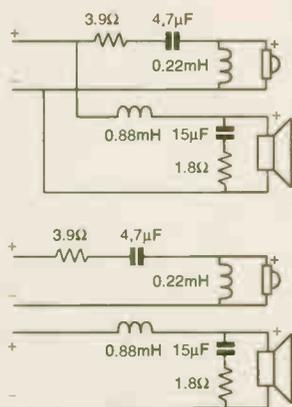Lastly, don't be sad if the 'speaker sounds bright after the conversion. It takes some time for the capacitors to run-in, and be prepared to change its name to 760iSELEMV! (Special Edition Limited Edition Modified Version). Happy D.I.Y.ing, Pok Loh Leeds.



How to bi-wire your Mission 760is. Many of our readers already have, and with good results too.

Adding a second series resistor to the treble arm of the crossover for your Missions will decrease treble level, but it will also effect the response smoothness. Normally the effect this has is to not only drop treble level, but also to roll off high treble. You may well have a shallow dip in the upper midrange/lower treble as a

result, but this will serve to soften the sound which you seem to prefer.

Again, decreasing the 15μF capacitor on the bass driver may well have unbalanced the response. This will mis-tune the filter, probably resulting in a higher -3dB point and slower roll off. This may well reveal more of the upper harmonics of bass lines, but conversely you will be using the driver closer to its break up region, which may be heard as a coarseness.

It is not normally advisable to make such modification 'blind' without test equipment. In this case you may well have achieved a balance which you prefer, but I doubt if it's accurate and is likely to be inconsistent with different forms of music. Obviously, we encourage DIY, but some simple test equipment is necessary in cases like this which will enable you to make a far better job of the modification, and gives even wider scope for improvement. DB

The Month

The Z2 appears to have better bass because it is drawing twice the current.

The lower resonant frequency is almost certainly a result of the extra mass of having two voice coils. The higher BL factor is also explained by the increased current demanded by a 4Ω load. Also worth noting is that although its sensitivity appears to be equivalent at 89dB, it is less efficient. In fact, as far as the amplifier is concerned, it would only produce 86dB for the same power level as an 89dB 8Ω unit.

It is indeed possible to use this Z2 driver in KLS6, but the crossover will have to be re-designed and the impedance curve will dip

lower in the bass, so it won't be such an easy load as far as your amplifier is concerned.

We can supply the crossover components separately, but you should be able to find a supplier of these components locally. As you can see from the final 1/3 octave plot on page 15 of that Supplement, there is no dip in the crossover. The plot you are referring to is a high resolution plot of the tweeter and midrange driver taken individually, and then laid onto the same screen. It does not show how they sum at the crossover point, only the smoothness of the individual responses. DB



WIN A MAPLIN SOLDERING IRON KIT COMPLETE WITH A LENGTH OF SILVER SOLDER

The writer of the most interesting DIY letter each month will receive a superb Maplin soldering iron, stand, booklet on good soldering practice and a length of high quality silver solder. Write in to: Hi-Fi World DIY letters, 64 Castellain Rd, Maida Vale, London W9 1EX.

BASS BINS

Following on from your KLS6 speaker design, I would like to pick your brains. I was thinking of using Audax's new HM210Z0 drive unit, but in a transmission line enclosure. The idea is to make two 15-20 litre enclosures to go beneath my existing speakers in a similar style to Wilson or the Rogers ABI arrangement.

This will provide both a true full-range speaker, for a modest outlay, and an interesting upgrade path in the form of active crossovers and bi-amping etc. At this stage I have only decided on a few of the design considerations. Firstly, the enclosures will be made from 25mm MDF with the base shot filled, and the existing speakers will have a low frequency cut-off in order to prevent them working too close to their lowest Hz output.

My system as it is comprises of a Trichord clocked Technics SLP 777

CD, a Rotel RB/RC870BX pre-power and Celestion 100 speakers which are bi-wired with Audioquest Indigo cables. I like the way the Celestions behave with the Rotel, but the Rotel can be really pushy with them when the music programme calls for some window rattling.

My main question now is: as you have done all the sums with this Audax unit, does it lend itself better to transmission line enclosures or to the reflex design as you have used it for your KLS6?

Colin Parish
Riverside Close,
Bedford.

Your best bet really would be to follow the plans for the bass section of KLS6. This cabinet has been optimised and validated using our test equipment and over many hours of listening. This optimisation process really is where a lot of the effort lies. The original design concept is easy to come up with; fine tuning it to get the result you want is always the lengthy bit. This should ensure that you get good results with the minimum risk and effort, allowing you to sit down and enjoy your music.
DB

TREBLE EXTENSION

I have 99% completed a set of Lowther Acousta 'speakers, a task I would not recommend to anyone except the most enthusiastic of home constructors. The speakers in question have been constructed in M.D.F to specification from original plans, with the addition of baton and gusset type bracing to the large horn panels. In total there are 114 components (including originals).

The PMBA used, although good, was found lacking in frequency range (Brios Feb. '95) as I am still young enough for mine to extend slightly beyond 10kHz. The lack of top end would be a concern, therefore I am

considering the addition of an HF unit run from extra terminals with a series capacitor, so they can bi-wired for extra HF if desired.

If this is a good idea could you recommend a good HF unit that you may have come across on your travels? These units are expensive and an unknown quantity as far as I'm concerned, no more than £100 a pair. As you will appreciate, the fitting of this unit is best done before fitting the front panels (the last panels!)

The units were bought second-hand, boxed and unused. I have been using them in a conventional sealed enclosure for some time. Lowther recommend them not to be boxed for more than 6 months. They were 3 years old when I bought them. They are working fine, but have a slight brown tinge where the voice coil is attached to the cone. Is this just normal heat discoloration?

I'm using Quad IIs for amplification and was thinking of replacing the components for new ones, but do not want to meddle with the original wiring as it's still in good working condition, with the original colours still visible. Is this worth it? If so can you recommend some reasonably priced types.

J.R. MacKay
Hornchurch,
Essex.

Finding a tweeter is not going to be as easy as it sounds. The Lowther drivers are very high quality, and very sensitive. To get a tweeter of similar quality and with the high sensitivity needed you will probably have to look at compression drivers or slot

tweeters. For advice on which would be most suitable contact Kevin Scott at Definitive Audio, Tel: 0115 981 3562. He uses Beyma and Vitavox drivers, both of which should fit the bill nicely.
DB

In your Quad II valve power amplifiers, only replace components that have drifted off value or have failed. You'll need to check all DC voltages to determine this, working from a circuit diagram. Modern components can give quite a different sound, cheap ones often sounding nasty. Aim to use carbon film resistors, not cheap metal films, and only audio grade polypropylene capacitors, like Solens or VITAs. Ideally, for best results, special components, like paper-and-oil dielectric capacitors should ideally be used, available from AudioNote (Tel: 01273 220511). **NK**

CAVITY SICKNESS


For over thirty years I labour with brick house sized reflex cabinets and infinite baffles, folded horns and columns, paralines and tricolumps you needed the kitchen chair to peer into. Concrete pipes, sand filled baffles and chipboard boxes the dog used as a kennel at night.

Then this bloke David Purton writes his little booklet; 'Coupled Cavity Handbook'. Wilmslow Audio put it in the post under plain wrapper for a fiver. The 19" cubes are flat down to 20Hz within excess of 100dB capability and 100 watts power handling and the pair cost less than £200 to build.

Now I only built them to please my wife, because she needed some indoor plant pot holders, but they make noises like a double decker bus and exactly match my Kans for sensitivity on pink noise. Is there a Nobel Prize for services to Hi-Fi?

Chris Bolwell
Gwynedd.

Coupled-cavity working is a topic we covered in our November issue, with regard to the test of Technics' SB-M300 loudspeakers. It was developed by KEF in the early Seventies and is now used in all their Reference Series loudspeakers to give good bass. Shamefully, in my view, Technics offer no acknowledgement of this, trying to disguise its origins by applying their own acronym, DDD (Dual Direct Drive), which means nothing. All the same, Coupled Cavity working is interesting and offers good performance, as Technics have discovered. **NK**

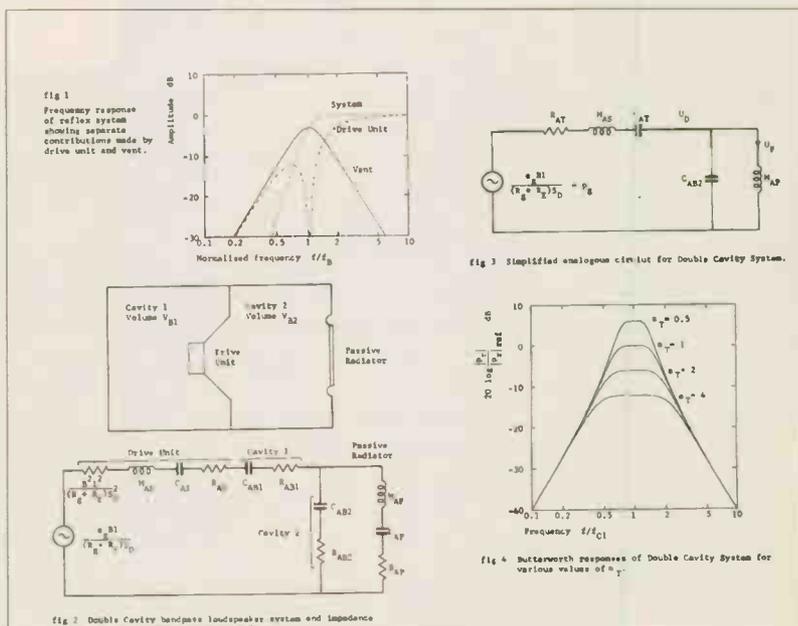

KEF research paper on coupled-cavity loading

THE HI-FI LAW OF DIMINISHING RETURNS

Ask a Hi-Fi dealer to upgrade your system, and he'll sell you ever more expensive bits of hardware, giving you a constantly changing sound, new solutions producing more problems which can only be solved with more expensive equipment. The harder you try, the more it costs and the less satisfying the results. This is the well known Hi-Fi law of diminishing returns. We have an alternative:

THE RATA LAW OF INCREASING RETURNS

Why buy new equipment when it makes more sense to realise the full potential of your existing equipment. Don't replace it, upgrade it; it's cheaper. Most equipment can be transformed by us for the cost of a dozen CDs. Magic? No - logic! To find out how we do it, ask for our 1995/96 Catalogue; it provides discussion, analysis and a definitive resource of audiophile components and advice on the art of recreating music in the home.

Russ Andrews Audiophile Catalogue

Includes :

- CD Players, Preamplifiers, Disc Preamplifiers, Power Amplifiers
- Loudspeakers
- Kimber Kable
- Upgrading Services and Guides
- Audiophile Kits and Components
- Accessories
- Reviews

1995/96 CATALOGUE

Russ Andrews

Edge Bank House, Skelsmergh, Kendal
Westmorland. LA8 9AS
England

Tel: 01539 823247

Fax: 01539 823317

To receive your copy of our 1995/96 catalogue just mail, phone or fax the address above.