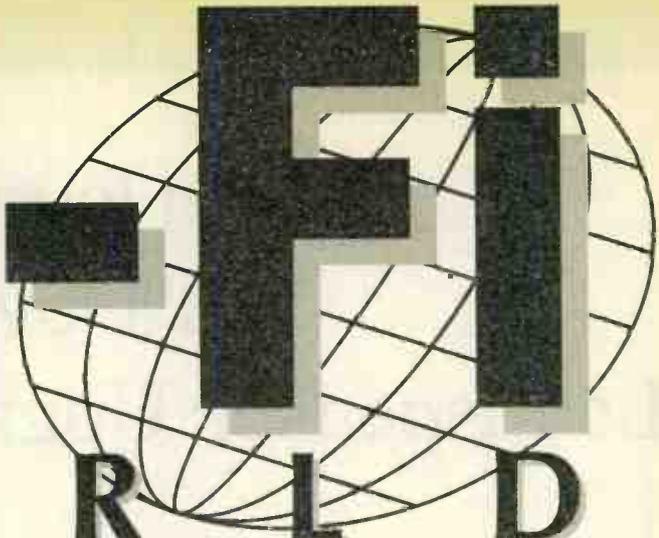


Hi-Fi
WORLD

Hi-Fi

WORLD




NO.40 NOVEMBER 1998

SUPPLEMENT

MESSAGE IN A BOTTLE II

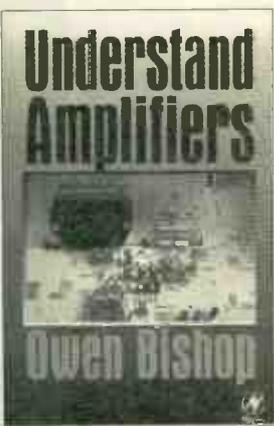
Building the
KEL34 valve
integrated
amplifier



TIPS ON TUBES

Know your valve
technology

PENTODE GRID LAYOUT

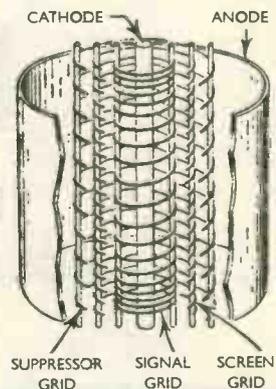

BOOK REVIEWS:
Understand Amplifiers
by Owen Bishop

FREE D.I.Y. SUPPLEMENT No.40

World Radio History

If you love music
you'll love our
Loudspeaker Upgrade Handbook


Order your copy
Russ Andrews Direct 0800 373467

If you really love music
you'll love

TORLYTE

'Phone for our Torlyte Brochure
Russ Andrews Direct 0800 373467

If you really, really love music
you'll love

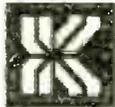 **KIMBER KABLE**

'Phone for our Lifestyle Brochure
Russ Andrews Direct 0800 373467



Russ Andrews Accessories Ltd, Edge Bank House, Skelsmergh, Kendal, Cumbria, LA8 9AS
Tel: 01539 823247 Fax: 01539 823317

Contents

All rights to the designs are reserved by World Audio Design Ltd. They are published for single use by private individuals. They are not to be used for commercial gain without prior permission from World Audio Design Ltd.
 Audio Publishing Ltd and World Audio Design Ltd accept no responsibility for accident or injury arising from the construction or use of any of the designs published.
 All of the projects in this supplement have gone through rigorous listening and test procedures. The performance and specification of these projects can only be guaranteed on kits bought directly from World Audio Design Ltd.

KIT NEWS

Catch up with the latest developments in the cut-throat world of DIY audio.

5

KEL34 PART II

After last month's look at the circuit behind KEL34, we now reveal how the amp shapes up on the test bench and in the listening room.

7

TUBE JOURNEY

Noel Keywood takes us on a technological guided tour of the venerable audio valve and opens up some of its secrets.

14

PARTING COMPANY

Hi-Fi World's DIY boffins spice up the performance of our 300B amplifier with a selection of top-notch components.

17

BOOK REVIEW:**UNDERSTANDING AMPLIFIERS**

by Owen Bishop.

23

DIY Q&A

The World team get you on the stairway to DIY heaven with answers to all your construction conundrums.

25

Watford Valves

7 DAYS A WEEK 9AM - 9PM THE AUDIOPHILES CHOICE

All output valves multi-tested and precisely matched

Full no quibble guarantee. Expert advice on all valve amps

| PRE-AMP VALVES | | | OUTPUT VALVES | | |
|----------------|--------------|-------|---------------|----------|-------|
| | | £ | | | £ |
| ECC81 | Brimar | 4.50 | EL34WXT | Sovtek | 6.00 |
| E81CC | Valvo | 24.00 | EL34 | Svetlana | 8.50 |
| ECC82 | RFT | 3.50 | E34L | Tesla | 8.50 |
| ECC83 | Philips | 6.00 | EL84 | Sovtek | 2.50 |
| ECC83 | Brimar | 10.00 | EL84M | Sovtek | 5.00 |
| ECC84 | RFT | 4.50 | EL84 | Tesla | 6.00 |
| ECC85 | RFT | 4.50 | EL84 | Philips | 12.00 |
| E88CC | Tesla gold | 8.50 | EL84 | Mullard | 15.00 |
| E182CC | Amprex | 12.00 | EL519 | EI | 12.00 |
| E188CC | Phil-SQ-Gold | 16.00 | KT66/7581A | USA | 20.00 |
| ECL85 | Telefunken | 7.00 | KT88 | Tesla | 25.00 |
| ECL86 | Tungstram | 4.00 | PL519 | EI | 12.00 |
| EF86 | Siemens | 7.00 | 300B | Sovtek | 65.00 |
| EL86 | Siemens | 7.00 | 5881 | Sovtek | 4.90 |
| EZ81 | Tesla | 6.00 | 6L6WXT | Sovtek | 8.00 |
| 6SL7GT | Sylvania | 6.00 | 6L6GC | GE | 17.00 |
| 6SN7GTB | UK | 9.00 | 6550A | GE | 24.00 |
| GZ34 | Harma | 6.00 | 6550C | Svetlana | 16.00 |
| GZ37 | Mullard | 9.00 | 6550WE | Sovtek | 16.00 |

SOVTEK KT88

Has received high praise from Audiophiles, Manufactures and Journalists world wide. From the initial tests it has been noted for its clarity and rich tonal balance. An instant upgrade from the Chinese type, and available from us now, fully tested and matched at £20.00 each.

JAN AUDIO SPECIALS 50PCS 100PCS

| | | | |
|--------|----------|------|------|
| 5687WB | Philips | 3.50 | 2.95 |
| 5842WA | Raytheon | 6.00 | 5.75 |
| 6922 | Philips | 2.95 | 2.50 |
| 6080WC | GE | 6.00 | 5.50 |
| 6J5WGT | Philips | 3.50 | 2.95 |

WATFORD VALVES 3 RYALL CLOSE,
BRICKET WOOD, ST ALBANS, HERTS AL2 3TS

Fast mail order/next day delivery/World Wide shipping
1000's more valves stocked. Prices exclude VAT and carriage.



01923 893270

Fax: 01923 679207



TECHNICAL & GENERAL

SOME NECESSITIES - FROM THE ORIGINAL CLASSIC TURNTABLE SPECIALISTS

| CONNOISSEUR | | | P&P |
|-------------------------------------|---|-------------------|-------|
| | BD1/2 Drive Belt | £10.55 | £1.85 |
| | BD1/2 Motor Suspension kit | £13.95 | £2.45 |
| | SAU.2 Headshell | £16.75 | £2.55 |
| | SAU.2 Connecting Lead | £15.95 | £3.55 |
| GARRARD Standard Models | | | |
| | Wired arm tubes | from £12.75 | £2.50 |
| | Cartridge carriers (sliders) | £10.55 | £1.85 |
| | Idler wheels | £9.85 | £2.25 |
| 301/401 Transcription models | | | |
| Original | Thrust pad assembly | £10.85 | £2.25 |
| Original | Idler tension spring | £2.95 | £1.85 |
| Original | Brake pad | £2.20 | £1.85 |
| Xeroxcopy | Owners Manual 301 incl. full size mounting template | £8.85 | £1.85 |
| | " 401 " " " " " | £6.70 | £1.85 |
| Replacement | 301 control knobs On-Off/Speed select | pair £20.25 | £2.55 |
| Replacement | 301 suppressor unit | £5.65 | £2.25 |
| Replacement | 301 motor pulley (-2%), (-1%), (Std), (+1%) | each £15.65 | £2.25 |
| Replacement | 301 Chrome plated mounting bolts | set £6.60 | £2.25 |
| Recommended | Lubrication set - early 301 or 301/401 | (specify) £5.60 | £1.85 |
| GOLDRING/LENCO | | | |
| | Idler wheel (lock-nut or clip fixing) | £19.95 | £2.85 |
| | Arm pivot bearings with instructions | £8.55 | £1.85 |
| | Spindle/Main bearing assembly complete | £24.85 | £3.85 |
| | Headshells | from £21.95 | £2.55 |
| | Instruction books | from £4.20 | £1.85 |
| THORENS | | | |
| TD.124 series | | | |
| | Idler wheel original | £27.50 | £2.85 |
| | Idler wheel our redesigned replacement | £15.35 | £2.55 |
| | Drive belt | £15.25 | £1.85 |
| | Chassis spring suspension (replaces 'mushrooms') | £15.85 | £2.55 |
| TD.150/160 | | | |
| | Drive Belt | £10.55 | £1.85 |
| | Suspension springs (-1%), (Std), (+1%) | set £12.85 | £2.55 |
| | Suspension bushes | (set of 3) £12.50 | £2.55 |
| | Armboards for most models | from £16.90 | £2.55 |
| CECIL WATTS | Dustbugs/Parastats/Spare - incl. Preener wicks | | |

Cartridges and styli for 78s and Mono LPs in addition to current Stereo LPs

TECHNICAL & GENERAL
PO BOX 53, CROWBOROUGH, EAST SUSSEX, TN6 2BY
TELEPHONE: (01892) 654 534

AN ANSWER.....

From the U.K.'s Premier Valve-equipment Repair/Restoration Centre...
to the question we're most-oft asked:

"What exactly do you do?". Well, we.....

Repair, Restore, Re-calibrate, Re-align:-
Tape recorders by Revox, Akai, Tascam, Teac (up to 1");
Valve - amps., pre-amps., tuners, cinema amps.,
theatre-organ amps., industrial/p.a. amps. from Radford, Quad, Leak,
Kalee, Clarke & Smith, Compton, Parmeko, RCA, Altobass etc.;
Valve - Communications Receivers and Transmitters
(to 30MHz/2kW/6" tall) by KW, Marconi, Labgear, Eddystone,
Redifon, RCA, Tiger: and so on.

We will...

Build that Kit for you or

Re-build it if you've had a go but it's gone pear-shaped.

We will...

Custom-build for you a published Classic design.

Design something special (a 250-watt AB2 high-level modulator, Sir?
No problem!!) and build the prototype.

All this,

as well as being an Authorised Service Centre for such respected
names of the Digital Era as Denon, Pioneer, Kenwood, Yamaha.

Overall, some pretty comprehensive facilities....and it will take only
a few minutes of your life plus a few pence from your pocket to call/fax
and discuss your requirements: 0113 244 0378. Or write!

We are:-

AUDIO LABORATORIES (LEEDS)

3 Kildare Terrace Industrial Estate,
Leeds LS12 1DB, England.

▽

KIT NEWS

SILKY SMOOTH SOUND?

AudioCom are now selling Elna's SILMIC series of capacitors. Incorporating silk fibres in their construction, these capacitors sit at the top of Elna's capacitor podium. AudioCom say the new design and materials (such as lead-out wires of Oxygen-Free Copper) result in benefits such as increased signal transfer speed and lower distortion figures. SILMICs come in voltage ratings from 25V to 100V and are priced at £1.44 up to £39.80. AudioCom will also be accepting all major credit cards from late September.

AudioCom
Units 4 and 6,
Trindle Centre,
Warren Street,
Tenby,
Pembrokeshire SA70 7JY
Tel: 01834 842803



TUNNEL VISION

The Svetlana Tube Zone (www.svetlana.com) is the name for the Russian/American valve manufacturer's new web site. Here you'll find a veritable mine of technological information on all things thermionic. Data sheets on Svetlana products are downloadable in Adobe Acrobat, and on-line technical support (including advice on how best to use Svetlana's valves) is available through contacting the company's engineers via e-mail. Finally there's a number of pages called On The Music Scene, which link up musicians and bands who can swap valve anecdotes.

WILMSLOW GET CONNECTED

Wilmslow Audio, famous for their distribution of drive units and 'speaker kits, have announced that the Musitube range of interconnects they distribute are now 'pre-conditioned' to improve performance. Apparently, this process opens the sound out and improves clarity, as well as removing the need to 'burn in' the cable.

As well as interconnects, this technology has also been applied to Wilmslow's mains leads, made of high-quality, silver-plated cable rated at 500V.

Wilmslow Audio
50 Main Street,
Broughton Astley,
Leicester LE9 6RO
Tel: 01455 286603

MONACOR ALL THEY SURVEY

Monacor of Germany are well-known as manufacturers of loudspeaker drivers and related sundries. Now, to assist the tenderfoot 'speaker builder, they have published a new edition of Speaker Building Fascination - Concepts For PA And Hi-Fi', published in both German and


occasionally-amusing Germlish at £6 + £1 P&P.

This 95-page A4 pamphlet gives instructions, drive unit data and plenty of back-up on five PA and no less than 15 hi-fi designs. Project complexity spans beginner's level to moderately difficult, taking in a goodly spread of basic loudspeaker concepts. Unusually for a modest text of this sort, graphs of the impedance and frequency response are given for each loudspeaker.

In case hammered thumbs and glue on the carpet don't strike you as the best way of learning, there is a concise guide to the major 'speaker types at the back with explanatory diagrams and the odd formula.

All of the designs rely on drivers from the Monacor catalogue, which can be bought from their UK importer, Cricklewood Electronics.

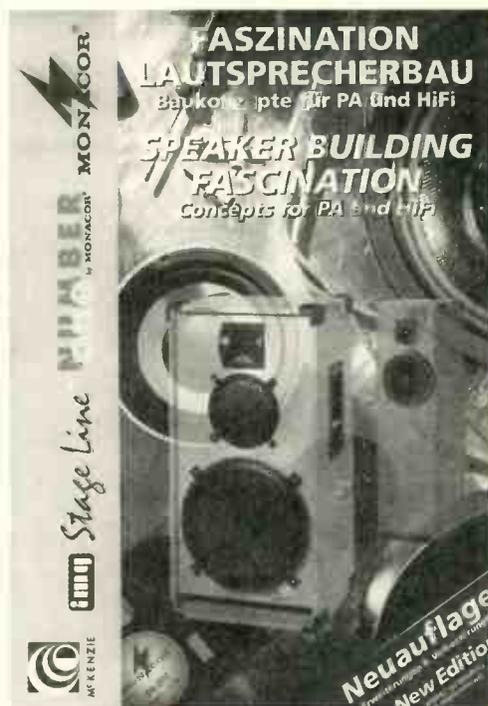
Cricklewood Electronics
40-42 Cricklewood Broadway,
London NW2 3ET
Tel: 0181 452 0161



KEL34 40W VALVE AMPLIFIER

Part II

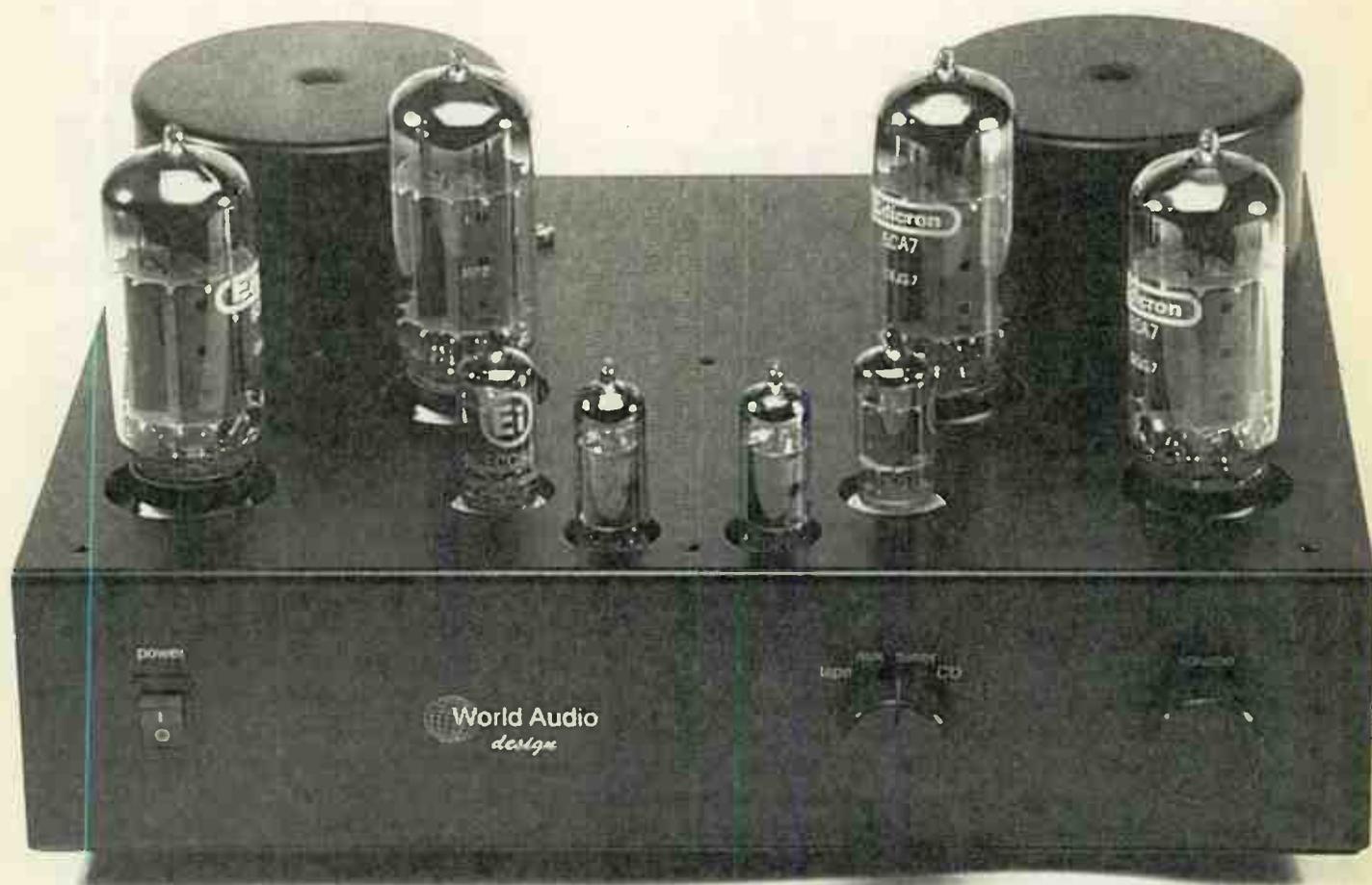In last month's Supplement we introduced KEL34, our brand new 40watt valve integrated. Now, Nick Lucas explains how to build the amp and the World listening team check out its sound.




Our aim with KEL34 was to design an amplifier with the budding DIYer in mind, one which would be both easy to build and easy to maintain. The result is an integrated amplifier, so a pre-amp is unnecessary.

As is common practice, we run all the

inputs directly into the volume control to avoid input overload. Most of the parts sit on a circuit board in the kit, which is marked with component positions to reduce the likelihood of incorrect placement. Making adjustment simple is the fact that bias adjustment isn't required as the amp is self-biasing and

balancing. Finally, KEL34 delivers a good 40watts from a push-pull output stage using a modern, European valve in current production, one that is not too expensive.

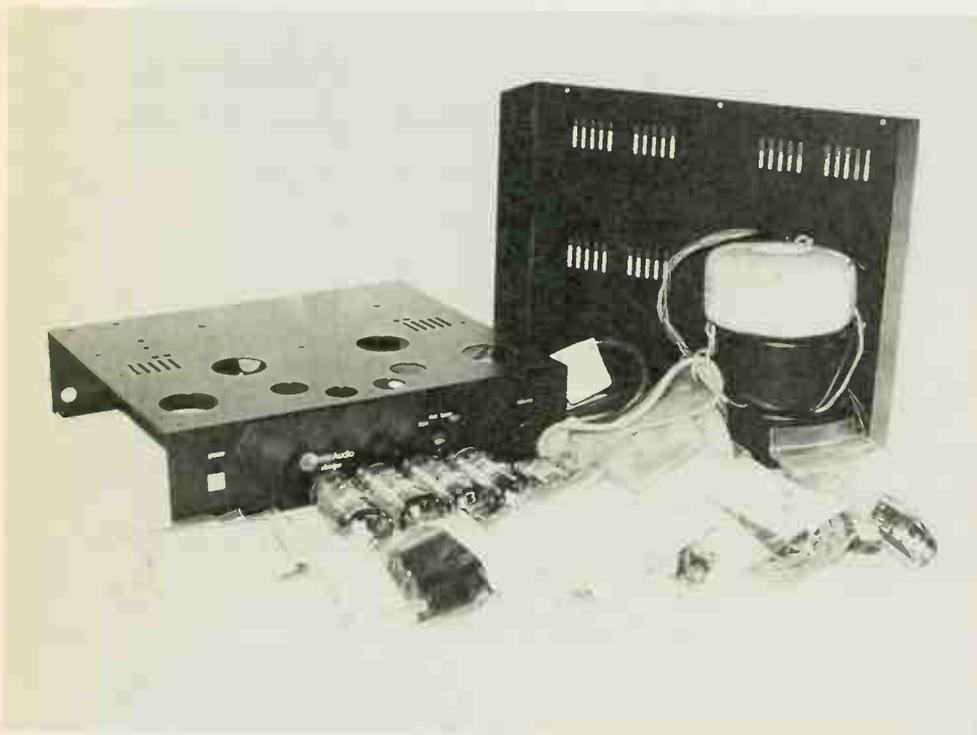Expect to see more of this valve, the 6CA7, because its performance is impressive. A modern version of Philips'




KEL34's chassis comes in two U-shaped sections for easy assembly. The three transformers - mains and output - are all toroidal types.

EL34 power pentode, it has a beefed up anode which accepts higher voltages and dissipates more power than the famous original.

In this second instalment of the KEL34

A double-sided PCB makes the amp far simpler to build than hard-wiring. In the picture below, you can see there's plenty of space on the board which eases soldering.

story, we detail the build sequence and give a break-down of what we are offering. Obviously, those readers who can obtain all the parts can build the amplifier from our published circuit. However, there is always demand for a kit, complete with specialist parts like output transformers, whose quality allows Hi-Fi World valve amps to achieve the same even tonal balance as a solid-state amplifier but with the advantages of valves - namely clean treble free from grit and an open,

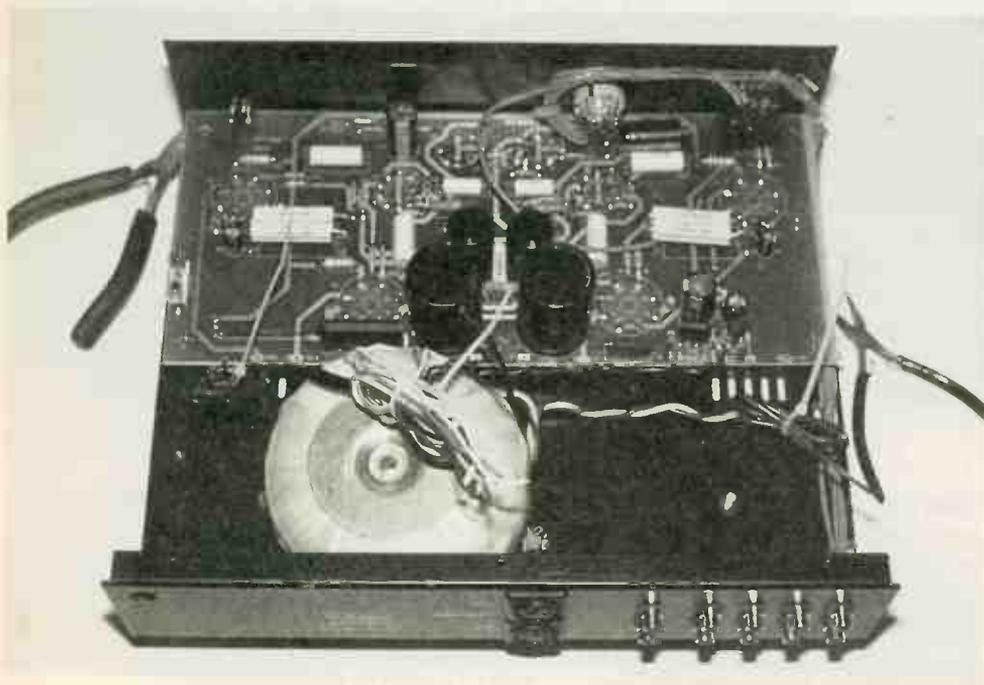

atmospheric sound stage. KEL34 has some serious power too.

Nothing has been left out of the kit; all you need provide are a soldering iron, some solder, a multimeter, a pair of loudspeakers and a musical source.

We have incorporated a couple of features into KEL34 to prevent the sort of errors which usually cause the wrong components in the wrong places. The 30+ parts bags each contain only one value of component and are clearly labelled. The text in the instructions is also backed up with plentiful diagrams and pictures of the kit in various stages of completion. There's a fault-finding section as well, in the unlikely event that constructors run into difficulties. For safety we supply high-voltage protective gloves and, should anyone be unable to complete a kit or make it work, we will sort the problem out.

THE BUILD SEQUENCE

1) Fixing the hardware to the chassis

This straightforward process involves fitting the volume potentiometer, selector, knobs, mains switch, mains lead, output and mains transformers, XLR loudspeaker sockets and the RCA phono inputs.


The latter are supplied with M6 fibre washers to isolate them from the chassis. The chassis earth point is at the volume potentiometer, so it's necessary to scrape the paint away internally where the pot. meets the chassis.

2) Populating the printed circuit board (PCB)

The ease of build of the KEL34 is largely attributable to the fact that all the valves and passive components sit on the PCB. This is clearly labelled and populating it is very straightforward.

The type of PCB we use is double-sided, hence for all joints except the snap-in electrolytic capacitors you will have to solder both sides of the PCB. We could have opted for the PTH type of PCB (where both sides are joined through the hole), but this would have increased costs dramatically.

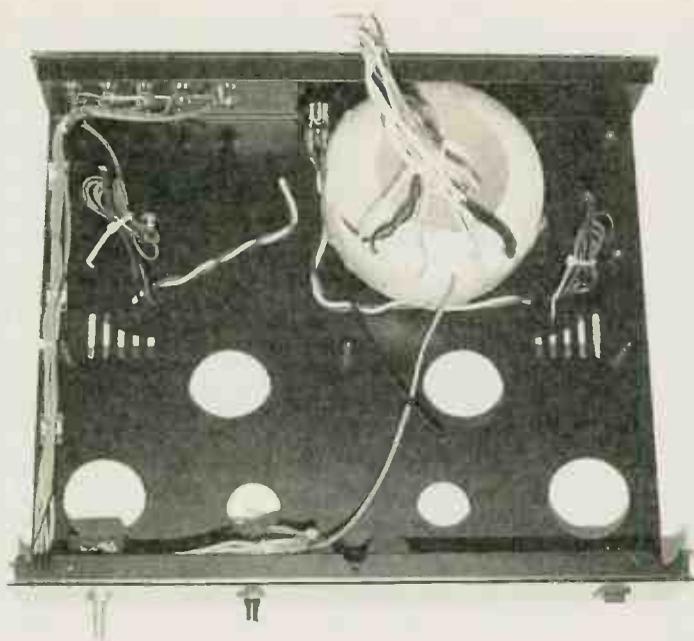The only thing you must double-check while you're populating the PCB is that all the electrolytic capacitors and octal valve bases are correctly orientated. Additionally, some of the resistors in the circuit generate quite a lot of heat, so we recommend raising them above the board to avoid tarnishing its surface.



The input sockets, volume and selector controls should be wired up in the early stages of building.

3) Valve heater connection

Once all the components have been fitted, the heaters can be wired up outside of the chassis with the wire provided. On each valve base the heater pins have their own separate tabs to make life easier.

4) Wiring up the inputs to the selector and volume potentiometer

Using the twin-screen cable provided and following the diagrams, this is soldering by numbers.

5) Mains switch through to output transformer connections

As above, this should pose no problems for competent constructors.

6) Connecting up the PCB

This involves soldering around 25 external connections to the PCB from the mains transformer, output transformer, volume control, mains lead, mains switch and feedback points.

7) Earth wiring

As you may well know, with valve amplifiers it is of the utmost importance that the earth lines are laid along the correct path and in the correct sequence. This is why we have dedicated a diagram in the instructions to this subject to ensure it is done properly. Otherwise hum may infect this otherwise very quiet amplifier.

8) Fixing the PCB inside the chassis

Now that all the various connections

between chassis-mounted components and the PCB have been made, the board itself can be mounted on the underside of the chassis' top-plate.


9) Switch on and hi-fi bliss

Build time is 8hrs-20hrs depending on ability.


If you do encounter any problems, please refer to the fault-finding section of the instructions, or alternatively call the helpline. If the worst comes to the worst, for a nominal fee we will get your KEL34 up and running.

MEASURED PERFORMANCE


Our new amplifier uses Ei 6CA7 pentodes from Yugoslavia, conservatively rated at a 25watt anode dissipation. They are an EL34 variant, a modern update in fact. We bias them to 25watts quiescent dissipation, although the anodes are so large they will take a lot more power. Pushing them heavily into class A will not make the anodes glow, as we have found with cheap valves possessing flimsy anodes, but they are run within Ei's specification to avoid accusations of 'over-running'.

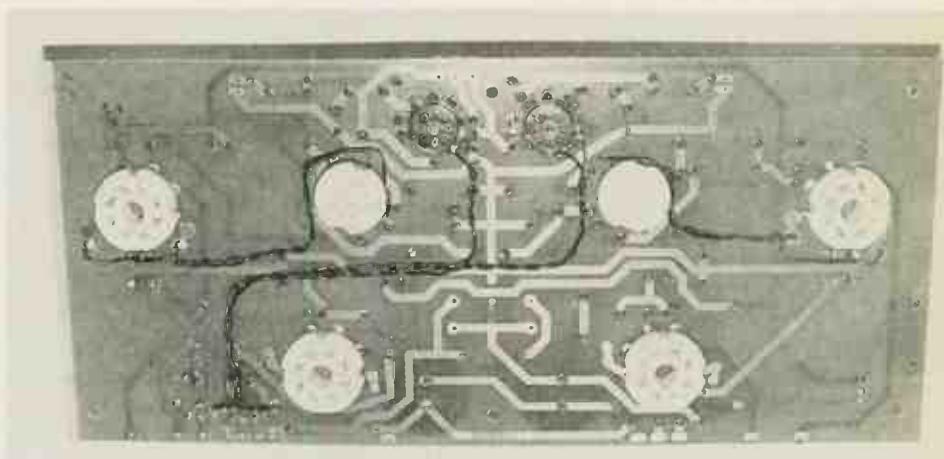

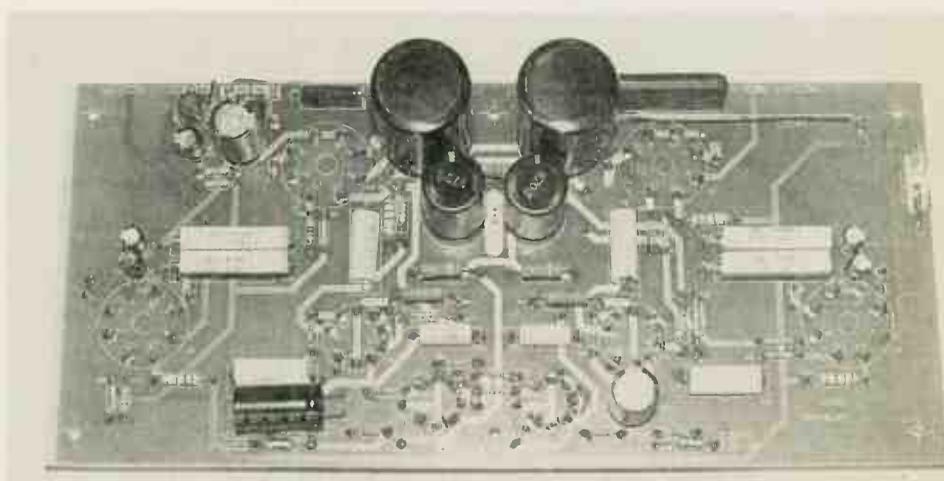On the upper side of the PCB are the valve bases, on the lower all the other components, including the power supply capacitors.



Arcadia Valve Amplifiers

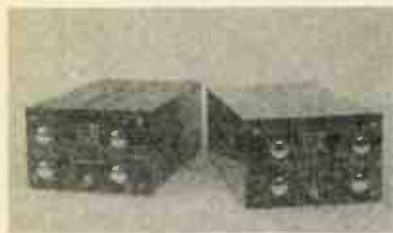

New Line Level Pre-Amplifiers

Two Models Available.

6 line inputs, 10dB of gain, zero feedback
finest quality components, musical results

Model 1 £995, Model 2 £1995

"There's none of the wispy airiness and soft, slow bass that one associates with the breed - just consistently fine tone, edge-of-your-seat dynamics and effortlessness."

Jason Kennedy on the Model 1 in Hi-Fi Choice
Sept '97

OEM, TRADE AND RETAIL ENQUIRIES WELCOME

P.O. Box 21, Bramhall, Cheshire SK7 2FF

Tel/Fax: +44 (0)161 4390727

EMAIL: sjs@audiophile.com

HTTP://WWW.NETFORWARD.COM/AUDIOPHILE/?SJS



SJS Electroacoustics
HAND WOUND INTERSTAGE, OUTPUT AND MAINS TRANSFORMERS FOR VALVE AMPS

Falcon Acoustics Ltd

Falcon Electronics, Basically Sound

NEW:-Big Air Core Inductors - 1.25mm wire

DRIVE UNITS: by FOCAL & Seas, and a pick of the best from other manufacturers.

100+ CROSSOVER NETWORKS: - Active & Passive, Components, Accessories,
COMPONENTS

SOLENE Polypropylene capacitors. 0.1mFd. to 100mFd.

Polyester and Polycarbonate Film Capacitors. 0.1mFd. to 10mFd.

ALCAP Reversible Electrolytic Capacitors (Non-Polar); 50v. 100v & Low Loss. 2mf. to 600mFd.

FALCON Custom-wound Inductors.

FERRITE:- Standard, High Power, Super Power, Super Super Power + AIRCORED 0.56-1.25mm wire

TAPPED INDUCTORS:- 0-10mH in 1mH steps & 0-1mH in 0.1mH steps

AUDIO AMATEUR PUBLICATIONS

NEW- Valves for Audio Frequency Amplifiers from Philips Technical Library plus lots in P/L.

Back year sets of Speaker Builder, Audio Amateur & Glass Audio, plus the Audio Anthology Set.

Altogether 50+ books and 50+ Audio Amateurs magazine year sets. 1997 sets available.

COMPUTER PROGRAMS

Large selection of Programs available from the very comprehensive Liberty AudioSuite test

program via AIRR, LoudSpeaker Ver.6, BassBox 5.1, to the basic Bullock/White Boxresponse.

Also the IMP FFT Test Kit, the Mitey Mic Kit and Mic/Preamp kit for Audiosuite or AIRR

FOCAL®

'State of the Art' Kit Designs

| | | | | |
|------|----------|----------------|----------------------|----------------------|
| B300 | 8.5litre | 2 way Compact, | 88.5 dB/watt system; | -3dB. point of 60Hz. |
| B400 | 18litre | 2 way Compact, | 90.5 dB/watt system; | -3dB. point of 55Hz. |
| C500 | 30litre | 2 way Column, | 89.5 dB/watt system; | -3dB. point of 45Hz. |
| C600 | 52litre | 2 way Column, | 91.0 dB/watt system; | -3dB. point of 42Hz. |
| C700 | 53litre | 3 way Column, | 89.5 dB/watt system; | -3dB. point of 38Hz. |
| C800 | 83litre | 3 way Column, | 90.2 dB/watt system; | -3dB. point of 35Hz. |

A comprehensive range of Focal kits from an even wider range of
High-Tech Loudspeaker units

SUPPLIERS TO THE TRADE SINCE 1972

Send for our FREE price list PL27: Just send a large S.A.E. (38p stamp) or US\$2 bill overseas,
Europe US\$1 bill or 3 International Reply Coupons (IRC) to:- (Dept HFW) Tabor House,
Norwich Road, MULBARTON, Norwich, Norfolk. NR14 8JT Tel (01508) 578272



SERVICE FOR ENTHUSIASTS

High quality Push-Pull or single ended
Output, Mains, Chokes, Interstage, Input and
Cartridge Transformers



Choose from our catalogue or specify a custom design at no extra charge. Range of package options: full or half shrouded or open frame. Encapsulation, as illustrated for our popular size "P+" for output or mains. All transformers built to order by our craftsmen. Usually 3-4 weeks delivery. Free technical support for all our products (Phone, Fax or internet). Free catalogue. Visa, Mastercard, JCB etc.

E A Sower Ltd
PO Box 36 IPSWICH
IP1 2EI England
Tel: (+44) (0) 1473 252794
Fax: (+44) (0) 1473 236188

E-Mail: sales@sowter.co.uk
techsupport@sowter.co.uk
Catalogue and overseas
agents on our Website:
<http://www.sowter.co.uk>

LOUDSPEAKER and ROOM MEASUREMENT PACKAGES

LIBERTY AUDIOSUITE v 3 visit <http://www.libinst.com>

Loudspeaker (and Electronic) Measurement System with

* **HIGHEST CAPABILITY**

Now with Multitone distortion measurements (IMD) using up to
4 simultaneous test stimulus frequencies, plus many new added functions

* **STRAIGHTFORWARD OPERATION**

With built-in, expanded, EASY SCRIPTS

* **DOWN TO EARTH PRICE:**

Plus £15 next day delivery

£696.00 plus VAT

ETF4 (WINDOWS95/NT)

visit <http://www.etfacoustic.com>

Room Measurement and Analysis System

* **ROOM ACOUSTIC MEASUREMENTS**

presented in simple graphical form, easy to understand

* **DESIGN ROUTINES for HELMHOLTZ RESONATORS and QRD
DIFFUSERS** for you to correct room acoustic problems

* uses your existing soundcard, and an omni mic

£125.00 plus VAT

LspCADv3

visit <http://hem1.passagen.se/ljdata>

Combined Room / Loudspeaker Box / Crossover program

* imports data from LAUD, LEAP and MLLSA

£68.00 plus VAT

Tony Seaford at MARTON MUSIC
Phone 01282-773198 or Fax 01282-776413
e-mail 106505.251@compuserve.com

The 6CA7 is robust enough to be able to withstand high HT voltages too, allowing it to deliver oodles of power. It has a massive 800V maximum anode voltage, making it much more robust than Philips' original. Therefore, KEL34 delivers a good 40watts before clipping occurs. In fact, it will swing around 45watts at clip, but a conservative quoted spec is in line with industry practice.

Distortion was low at around 0.15% at ordinary output powers of 1 watt-5watts, even though we do not use too much feedback. This figure comprises second harmonic alone, even at high frequencies.

At high power outputs distortion rises to around 2%, as is common with low-feedback valve amps, as the design moves slowly into soft clipping. Since this only affects short-term musical peaks, it is not a major influence upon sound quality.

Frequency response extends from 20Hz-43kHz (-1dB), channel separation measures 60dB and noise a low -96dB. Input sensitivity with the level of feedback applied measures out at 300mV. NK

| | |
|--------------------|------------|
| Power | 40watts |
| CD/tuner/aux. | |
| Frequency response | 20Hz-43kHz |
| Separat on | 60dB |
| Noise | -96dB |
| Distortion | 0.15% |
| Sensitivity | 300mV |
| DC offset | none |

SITTING IN THE SWEET SPOT

The Ei 6CA7s certainly looked promising on the test bench with their beefy anodes, but how would they deal with the Jamo Concert 8s? After all, these 4ohm stand mounters usually hit valve amps with a double-whammy of heavy current-draw and the transparency to show up ruthlessly the bass problems this creates.

Driving a 3metre set of Cable Talk's Talk 4.1 bi-wire loudspeaker cable, KEL34 and its compound-biased output stage managed a surprising bass control when dealing with Opus 3's Opera Pearls HDCD. The overture to Bizet's Carmen skipped along with real panache, not a hint of looseness or compression at the bottom end spoiling the rendition.

Where KEL34 rejoined the ranks of hot bottles was in the rich tonal colouring and realism valves are so famous for, as it painted strings of all species from a broad palette. A lack of midrange hardness and those 40watts at the loudspeaker terminals lent themselves to raising the volume too. The neighbours might not be too thrilled at the prospect of this unless they happen to share the same musical tastes, but the dynamics and scale which are the end-product make this a highly tempting proposition.

A valve integrated isn't what you'd normally expect to find glowing along to Dance, but KEL34 confirmed its credentials with a spot of DJ Cher. Into

the Jamos, the 6CA7s might not have been able to mimic the downward reach of a megawatt tranny power amp, but they weren't far behind, preferring control and speed to absolute extension. And where some amplifiers with sufficient power to light an oil rig can sound sluggish and blurred, those two pairs of pentodes had a dexterity which guaranteed engagingly musical results even if you're just moshing along to a drum machine.

These two traits suited slower Blues tracks perfectly, the lolloping bass of Joe Beard's Blues Union losing none of its drive or expression. In fact, KEL34 was reminiscent of some of the better classic valve amps working into easy loudspeaker loads - it had crisp lower octaves with a harmonic complexity which the majority of amps, whether solid-state or tube, seem to ignore or miss altogether.

Like all electronics, KEL34 'matures' with time as its constituent parts run in. Vocals, for example, became smoother and more open after a couple of weeks had passed, and the amp delved deeper into recorded ambience to come up with a sound stage any pair of revealing loudspeakers would be happy to relay.

Unlike the majority of its thermionic compatriots, KEL34 doesn't take an idiosyncratic view of tonal balance, preferring to stay neutral in a way that brings to mind transistors more than valves. It is this 'best of both worlds' mix which demonstrates the superiority of valves in a competent design like this.

HOW TO ORDER KEL34

KEL34 is available from Hi-Fi World:

| | UK (inc. VAT & P&P) | Overseas (exc. VAT & P&P) |
|------------------------------|------------------------|------------------------------|
| KEL34 full kit (with valves) | £295 | £260 |
| KEL34 (without valves) | £250 | £220 |
| KEL34 transformer set | £110 | £97 |
| PCB only | £65 | £57 |

All of the above come with a full set of instructions.

Call/fax Nick Lucas on 0171 221 0691 (9am-5pm, Monday to Friday) for more information.

E-mail: wad@hi-fiworld.co.uk

For overseas freight charges, please call, fax or e-mail.

HART

Electronics

Wilmslow Audio have believed for a long time that the **Hart** kit amplifiers were amongst the best sounding amps on the market at any price, so much so that we have bought the company, Hart Electronic kits. We are now able to demonstrate these remarkable amplifiers and welcome you to come along and compare the sound quality with your own equipment.

We feel that these amplifiers sound better than most others irrespective of price !!

'AUDIO DESIGN' 80 WATT POWER AMPLIFIER.



80w Standard Amplifier designed by John Linsley Hood continues to amaze all who listen to it. The delicacy and transparency of sound coupled with its flawless performance and overall reproduction quality, enables it to be compared with amplifiers costing 5 or 6 times as much. This versatile amplifier is offered in three options allowing you to choose which product will suit your own system.

All amplifiers are now produced in **Super Audiophile** versions only.

| | |
|---|---------|
| Standard Amplifier kit..... | £493.81 |
| Standard Amplifier Factory Assembled..... | £593.21 |
| Stereo Power Amplifier kit..... | £432.22 |
| Stereo Power Amp. Factory Assembled..... | £522.22 |
| Monoblock Amplifier kit..... | £306.90 |
| Monoblock Amp. Factory Assembled..... | £386.90 |

1400 Pre Amplifier has been specially designed to offer the added benefit of more inputs than the standard amp. It also offers more comprehensive signal handling with facilities for 2 tape recorders and an in built headphone amplifier. Complete with separate external **Andante** power supply.

| | |
|---|---------|
| 1400 Pre Amplifier kit..... | £343.49 |
| 1400 Pre Amplifier Factory Assembled..... | £443.49 |

"CHIARA" HEADPHONE AMPLIFIER.




Chiara Headphone Amplifier designed by John Linsley Hood is a singled ended class Amplifier for stand alone use or to supplement those power amps that do not have a headphone facility.

A valuable personal listening option and an attractive, harmonious addition to any hi-fi system.

Used in conjunction with Andante power supply.

| | |
|--|---------|
| Chiara Headphone Amplifier kit..... | £115.46 |
| Chiara Headphone Amp. Factory Assembled..... | £152.46 |

SHUNT FEEDBACK PICKUP PREAMPLIFIER

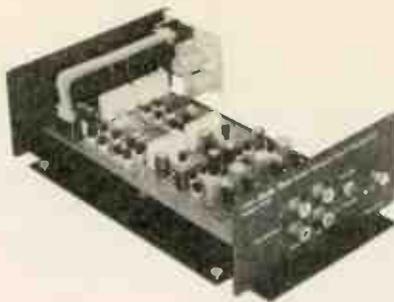

1450 Phono Preamp is able to amplify the minute outputs from moving coil or moving magnet pickups up to a suitable level to feed into any amplifier's standard auxiliary input. The RIAA standard circuitry provides very accurate shunt feedback equalisation. Used in conjunction with Andante power supply.

**Winner of Gramophone audio choice 1997/98
Hi-Fi Buyers Guide**

| | |
|--|---------|
| 1450 Phono Preamp kit..... | £138.94 |
| 1450 Phono Preamp Factory Assembled..... | £188.94 |

"Andante" Linear Technology
AUDIOPHILE POWER SUPPLIES



Andante power supplies are specially designed for exacting audio use requiring absolute minimum noise, low hum field and total freedom from mechanical noise. Available in 2 versions:

The 3550 having 3 - 15v positive and 2 - 15v negative output rails which is ideal for use with our 1400 Preamp, Headphone and Phono Amps.

The 3565 having a single 15v supply for use with any one single item only.

| | |
|-------------------------------------|---------|
| Andante 3550 Power Supply kit..... | £94.75 |
| Andante 3550 Factory Assembled..... | £147.25 |

| | |
|-------------------------------------|---------|
| Andante 3565 Power Supply kit..... | £84.42 |
| Andante 3565 Factory Assembled..... | £133.42 |

400 FM Tuner is a high quality analogue tuner system designed by John Linsley Hood gives the greatest possible sound fidelity from the FM broadcast media. The incorporation of two circuit features around the stereo decoder and IF/demodulator produces results that are staggering, especially in the clarity, transparency and extended frequency response.

| | |
|------------------------------|---------|
| Tuner kit..... | £256.82 |
| Tuner Factory Assembled..... | £336.82 |


Printed Circuit Board Solder Practice Kit

Unsure whether you can construct a Hart kit? - This is your chance to try! Included is a typical PCB, a range of modern components, a roll of the correct grade solder and full set of instructions.

| | |
|--------------------------|-------|
| Solder Practice kit..... | £4.99 |
|--------------------------|-------|

Alps Potentiometers

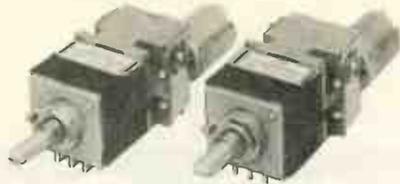ALPS "Blue Velvet" PRECISION AUDIO CONTROLS



Throw out those noisy, ill matched carbon pots and replace them with the exclusive ALPS Blue Velvet range of components. The improvement in track accuracy and matching is incredible giving better tonal balance between channels and rock steady image stability.

Manual Potentiometers

| | |
|---|--------|
| 2 gang 100K Lin..... | £15.67 |
| 2 gang 10K, 50K or 100K Log..... | £16.40 |
| 2 gang 10K Special Balance, zero crosstalk..... | £17.48 |

Motorised Potentiometers

| | |
|--|--------|
| 2 gang 20K Log..... | £26.20 |
| 2 gang 10K RD Special Balance, zero crosstalk..... | £26.98 |

Soldering

| | |
|---|--------|
| Antex 240v 25w Soldering Iron..... | £15.43 |
| ST4 Soldering Iron Stand..... | £4.95 |
| 845-007 22swg Solder -3mtr mini tube..... | £3.90 |
| 845-008 20swg Solder valve grade - 100g reel..... | £12.90 |
| 845-009 22swg Solder PCB grade - 100g reel..... | £14.75 |
| 845-110 24swg Solder - 100g reel..... | £21.45 |

Technical Bookshelf

THE ART OF LINEAR ELECTRONICS

John Linsley Hood..... £19.95

AUDIO ELECTRONICS

John Linsley Hood..... £19.95

HIGH PERFORMANCE AUDIO POWER AMPLIFIERS

Ben Duncan..... £40.00

THE ART OF SOLDERING

R. Brewster..... £3.95

ACTIVE FILTER COOKBOOK

Don Lancaster..... £19.95

HOW TO USE OSCILLOSCOPES & OTHER EQUIPMENT

R. A. Penfold..... £3.50

LOUDSPEAKERS: THE HOW & WHY OF GOOD REPRODUCTION

G. A. Briggs..... £9.95

LOUDSPEAKER DESIGN COOKBOOK

Vance Dickason..... £22.95

AN INTRODUCTION TO LOUDSPEAKER DESIGN

V. Capel..... £3.95

ELECTROSTATIC LOUDSPEAKER DESIGN & CONSTRUCTION

Ronald Wagner..... £15.95

ELECTROSTATIC LOUDSPEAKER DESIGN COOKBOOK

Roger Sanders..... £24.95

BULLOCK ON BOXES

Robert Bullock III..... £11.99

THE COUPLED CAVITY HANDBOOK

David Purton..... £5.00

THEORY & DESIGN OF LOUDSPEAKER ENCLOSURES

J. E. Benson..... £22.95

HIGH PERFORMANCE LOUDSPEAKERS

Martin Colloms..... £24.95

LOUDSPEAKER PROJECTS BOOK #1

Speaker Builder Magazine..... £6.95

A MANUAL OF VENEERING

Paul Villard..... £9.95

LOUDSPEAKERS FOR MUSICIANS

V. Capel..... £3.95

AUDIO ANTHOLOGIES - Volumes 1 - 6

Audio Engineering Magazine..... £13.95

A BEGINNER'S GUIDE TO TUBE AUDIO DESIGN

Bruce Rozenblit..... £15.50

Make your own Audio Interconnects

Using our high quality Audiophile grade double screened signal cable which has linear crystal oxygen free copper covered with foamed polyethylene insulation and a soft blue matt fish pvc.

| | |
|---|-----------------|
| Signal Cable..... | £3.98 per metre |
| T711G Phono Plug..... | £3.25 each |
| T711G Phono Plug (In lots of 10 or more)..... | £2.75 each |

Build your own Loudspeakers and save £££££

Why not build yourself a fantastic sounding pair of loudspeakers at a fraction of the cost of those commercially built and sold by Hi-Fi dealers?

We have an extensive range of kits available to suit all price levels, and we know that they **all sound better than any speakers sold at more than twice the price!!!**

Don't be fooled into buying a lower quality average loudspeaker when for the same money or less you could have a better sounding system, with a higher specification from us, The experts in loudspeaker technology for over 30 years.



New demonstration facilities:
We will soon be opening additional
Demonstration facilities in Wigan, Lancs
Phone to book your appointment


Send for your **FREE** catalogue

Wilmslow Audio & Hart Electronics
50 Main Street
Broughton Astley
Leicester LE9 6RD
Tel: 01455 286603 Fax: 01455 286605
Email: wilmslow.audio@dial.pipex.com

BOTTLE BUILD

Ever wondered just what makes a valve tick?
Noel Keyword reveals the thermionic ingredients.

Watching the anode of a 6L6 valve slowly starting to glow cherry-red surprised me. I was running this sample at its rated maximum, so the maximum rating was exactly that - the very upper limit. A valve cannot be run long-term like this in practice, yet other 6L6 samples had handled power levels above their quoted maximum. The physical structure of a valve and the materials used in it are subjects worth studying in themselves, and useful to anyone running a valve amplifier.

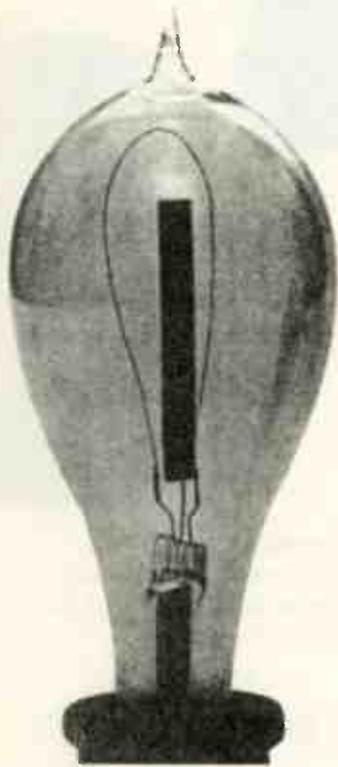

Edison inserted a plate in an electric lamp and observed that a current flowed between this plate and the positive side of the filament supply. He had invented the diode, but at the time (1883) patented it as a galvanometer. This clearly shows how the valve sprang from the electric lamp.

The valve was the world's first electronic amplifying device. It was developed from the light bulb, an ancestry which shows through in its construction. Staying with the triode, let's look at the different issues raised by its physical properties.

ANODE

Area and thickness effect heat dissipation and power rating, so generally speaking greater power handling means a bigger anode and a bigger valve. Hot spots occur if anode thickness is not uniform, a sign of poor-quality materials.

Anodes are made from nickel or nickel-plated iron. The surface is then carbonised to increase heat dissipation. High-power valves use graphite, tantalum or molybdenum instead. For example, an 845 anode (rated at 70watts) is coated with graphite.

The bigger the anode, the more power it can handle, so power valves are always big, unless water-cooled.


The point at which the anode glows determines the power rating of a valve (calculated as the voltage across the valve multiplied by the current passing through it). To cope with anode variability and keep temperature down to avoid gassing, it is common to set power dissipation 10%-25% below this limit. However, where a manufacturer's spec is already conservative, the valve can be run at its maximum rated power.

Overheating drives out occluded gas and degrades the vacuum within the glass envelope. The electrodes and glass of later valves were out-gassed to minimise this.

ELECTRODES

Grids are usually made of molybdenum wire, down to 0.025mm diameter in later valves. Wire grids are commonly wound

PENTODE GRID LAYOUT

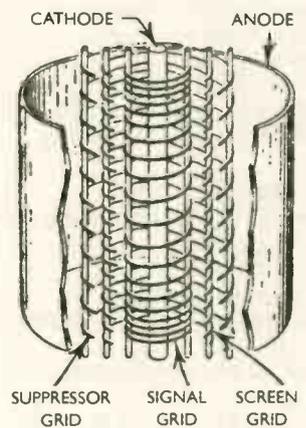

This is a representation of a pentode. At centre lies the emissive cathode. At the periphery lies the anode. Between these electrodes lie the signal grid, screen grid and suppressor grid. The electron stream flows from cathode out to anode, being influenced by the grids on the way.


Source: Sonic Frontiers.

concentrically around nickel supports, as our diagrams show. To improve mutual conductance, spacings were progressively decreased and tolerances improved to prevent electrodes touching. Grid-to-cathode spacings of just 0.1mm were achieved in later valves, at which point heat from the cathode and consequent thermal expansion made further progress difficult.

CATHODE

Electron emission in early valves came from a thoriated-tungsten filament. This is seen most dramatically in the bright emitter of the 211 power valve, where the heater filament is suspended on springs to minimise microphony and cope with expansion.

High emission at lower temperatures

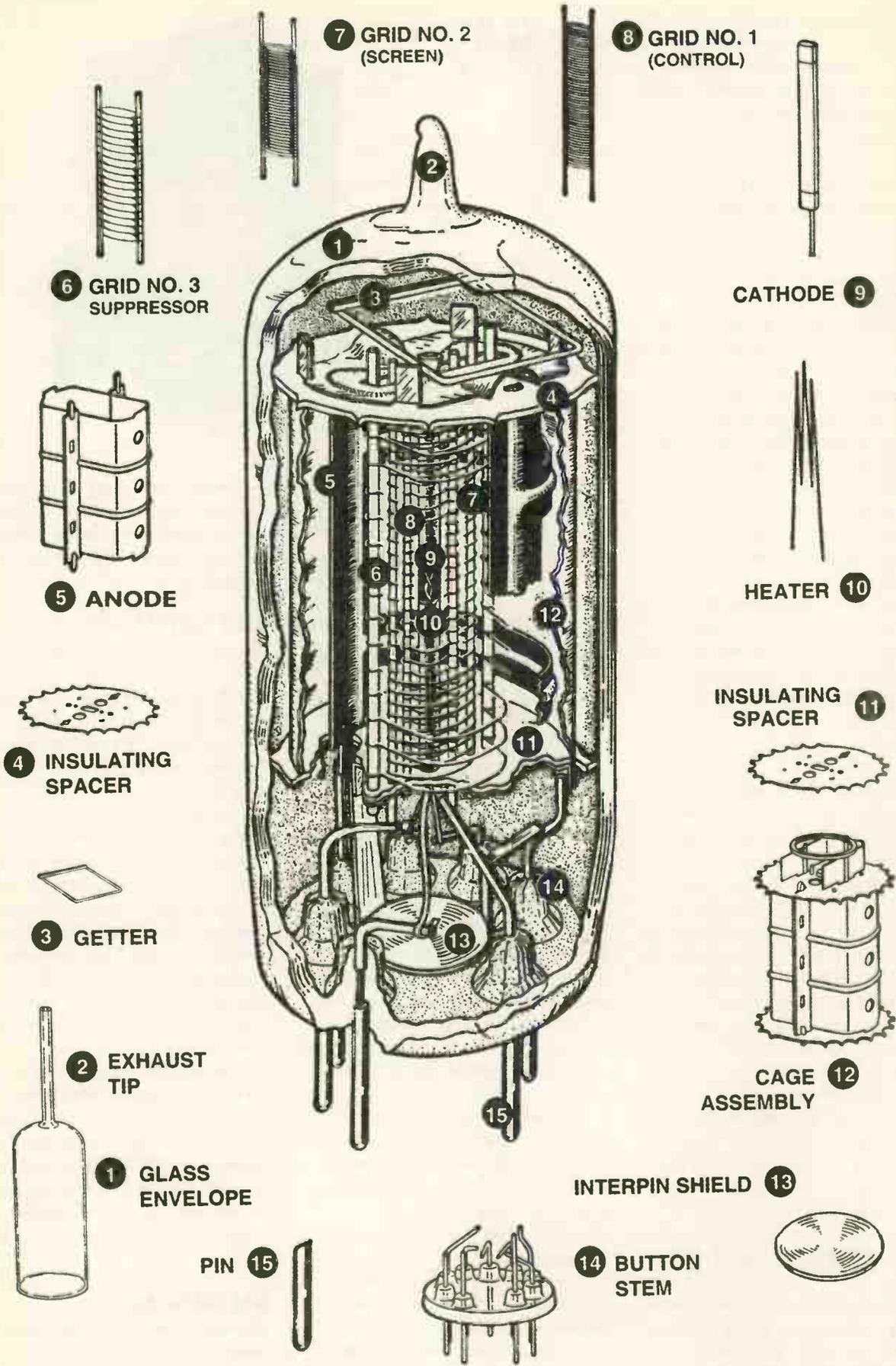

This illustration shows the parts used in the construction of a modern pentode, where the pins are fused into the glass base. At the centre lies the cathode, within which sits the heater. Around the cathode are the grids, arranged concentrically. On the outside lies the anode, which is usually visible. The whole assembly is supported by rigid wires and cushioned against the glass by spacers. Source: Sonic Frontiers.

was the goal achieved with alkaline earth metals such as calcium and barium, or their carbonates. From the late-Twenties on, nickel was coated with these materials to form a cathode, which surrounded the heater, to form an 'indirectly heated' valve.

The lower operating temperature (1000K instead of 1800K) raised filament life from 1500 hours to many thousands of hours.

FILAMENT

It was about 12 years (1903-1915) before tungsten could be made ductile enough to be used as a heater filament. Untreated tungsten filaments glow almost white, running at 2500K. When coated with thorium to improve emission they glow red, running at 1800K. The duller the glow, the longer the life.

The presence of gas in a valve poisoned the filament, shortening life. This problem was overcome by the mid-Twenties.

Most modern valves have cathodes, emissive plates that surround the heater filament. The heater can be seen glowing only where it protrudes from the cathode. Valves for battery operation are directly heated.


VACUUM

The air inside a valve is pumped out (evacuated) to allow unimpeded passage of electrons from cathode to anode, and to give useful heater life.

The first US valves, assembled by Langmuir in 1913, relied on a new form of German pump to get a sufficiently high vacuum: pumping was crucial. Eventually vacuums of one-hundredth to one-thousandth of a millionth of an atmosphere were produced. It was unnecessary to go further. Other matters then had to be considered.

Glass and metal give off occluded gases when heated, and these destroy a vacuum. The seal around the valve's pins must not leak and the glass must not be porous either. The pins and glass are therefore matched to have similar coefficients of expansion. In addition, the electrode assemblies are heated to drive out gas.

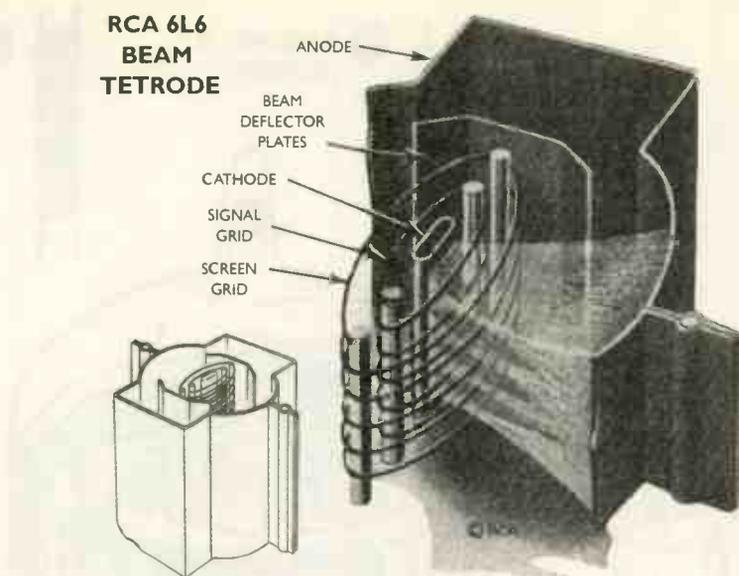Finally, the vacuum is hardened further by firing a 'getter'. Early getters comprised a strip of magnesium, heated by an external coil carrying a Radio-Frequency current until it fired. Carried out after pumping and sealing, this process removes all traces of oxygen by forming



The pentode was developed and patented by Philips in 1926, in order to overcome the distortion produced by standard tetrodes. Faced with this, the Americans developed the more efficient beam tetrode in 1936. Invented by British engineers in 1933, EMI passed the patents to RCA, believing the valve could not be built. To this day US output valves are, by preference, beam tetrodes. Source: History Of The British Radio Valve To 1940.

Diagram: Sonic Frontiers And RCA

magnesium oxide. The silver coating seen on the inner surface of many valve envelopes comes from a magnesium getter.

In the end, alloy getters of barium combined with aluminium or magnesium were used to remove all major gases: oxygen, nitrogen, hydrogen, carbon monoxide and dioxide, plus water vapour.

GLASS BULB

The outer envelopes of most valves are made from soft soda glass. Those with a glass foot (B9G, etc) have soft glass bases through which pass pins of chrome/iron alloy (Philips), or a hard glass base and pins of nickel/iron/cobalt alloy. In both cases, the pins have to match the thermal expansion rates of the glass to maintain a seal.

This technique superseded the use of a glass support stem inside the valve through which passed copper lead-out wires, an idea copied from light-bulb manufacture. These wires were connected to the pins in a moulded, phenolic base.

Long, parallel wires exhibited enough inductance and capacitance to effect high-frequency behaviour, though. For VHF radio and radar use, after 1940 better connection methods were needed. Later RF valves like the EF50 and EF86 benefitted from the layout of the B9A base.

SIZE AND SHAPE

The valve traces its technological roots back to the electric light bulb, so early designs were sized and shaped similarly, with an internal stem carrying the electrode structure fused into the glass envelope and a phenolic base attached after evacuation.

There was a major need to reduce power consumption, weight and size to create valves suitable for high-frequency work. Excessive inter-electrode and lead-out capacitance and inductance also had to be addressed. The natural conclusion of these improvements was the Nuvistor of the early 1960s. It operated at just 135V, and raising the supply voltage above this would cause flashover.

The development of the 6L6 power valve reflects the progress of valves as a whole. Early samples were big, dissipated 23watts on their anodes and could only stand up to 350V HT. Later versions could dissipate 28watts from 550V HT and deliver more power from a smaller envelope.

REFERENCES

History Of The British Radio Valve To 1940
by Keith Thrower.

A Taste of Tubes
by Sonic Frontiers

SONIC SURGERY

Nick Lucas and Richard White warm up their soldering irons and turbo-charge our 300B amplifier with specialist components.



This short introduction is especially for all you DIYers and prospective DIYers out there. It tells the story of Bob.

After 30 hours of toil and serious concentration, Bob is rewarded with a kit amplifier that sounds sweet and involving. He can now relax in his listening chair and wallow in the fruits of his musical labours.

For the first 12 months he is in hi-fi heaven. The second year begins with a slight inkling that he's missing something, but he can't put his finger on what it is. After 18 months he finds this elusive missing link quite by accident, curled up and sleeping. Bob still has his soldering iron from his kit-building hey-day and is ready for some more action. Bob looks up and utters, "It's time for an upgrade." Bob has truly been bitten by the hi-fi bug.

Component upgrading is a reasonably cheap and simple way of improving your sound without going for a trade-in. It is also character building and quite an eye-opening education. The industry has acknowledged the popularity of this process judging by the number of companies specialising in audiophile components, most of whom are mines of information happy to give valuable advice on how a particular component will sound in a specific location.

In past articles we have selected components to uplift World Audio Design kits such as our K5881 push-pull power amplifier,

KLP1 line-level pre-amplifier and KLPP1 phono pre-amplifier.

Now it's the turn of our creme-de-la-creme valve amplifier, the 300B. This push-pull 28watt runs its two pairs of 300B triodes in pure class A with feedback switchable in or out on the back panel. In the kit, we supply components of good quality along with two specially-designed Ansar reservoir capacitors and two Solen signal caps. The resistors are carbon films (which work very well with valve equipment, complementing its warm tones) and wire-wound, ceramic-bodied, high-power resistors.

To make the upgrading easier, we have broken them down into four sections. Our source for components was Paul Morawski of AudioLinks who, upon receipt of a 300B circuit diagram, came up with a list of suitable components.

UPGRADE 1 - THE POWER SUPPLY

The first section up for a revamp was the power supply. Both channels' HT lines are derived from the same secondary winding on the mains transformer before solid-state rectification. This allows the use of a larger electrolytic reservoir cap, giving improved smoothing and lower noise over valve rectifiers (whose partnering caps are limited to a maximum of around 50uF).

This partially smooth voltage then passes through a GZ37

Billington Gold



Long known as specialists in rare tube brands, Billington Export provides a line of premium-grade valves to fill the increasing demand for hard-to-find tubes! BILLINGTON GOLD features specially tested valves selected for long life, low microphony and low noise. Versions with gold plated pins are available. BILLINGTON GOLD brand comes from a variety of countries around the world. We have carefully chosen the best manufacturer for each type, with an emphasis on the highest audio quality and product reliability. We stock one million valves including: BRIMAR, GE USA, GEC UK, MAZDA, MULLARD, RCA, RUSSIAN/SOVTEK/SVETLANA, SYLVANIA, TESLA, THERMIONIC, TUNGSRAM and other rare brands, as well as stockists and CRTs.

BILLINGTON GOLD

| | |
|----------------------|---------------|
| 2A3 | 17.25 |
| 6L6GC | 9.50 |
| 6L6GT | 6.45 |
| 6SL7GT | 4.50 |
| 12AX7 | 5.55 |
| 50CA10 | 22.50 |
| 274B | 12.00 |
| 300B/VA300B | (Pair) 126.00 |
| New improved version | 63.00 |
| 807 | 9.95 |
| 811A | 9.00 |
| 813 | 24.00 |
| 845 | 33.00 |
| 4300B | 66.00 |
| 5881 | 8.00 |
| 6550B/B3 | 12.00 |
| E81CC | 5.70 |
| E81CC-01 | 9.50 |
| E82CC | 5.70 |
| E82CC-01 | 8.50 |
| E83CC-01 | 8.50 |
| E88CC | 8.00 |
| ECC81 | 5.70 |
| ECC82 | 5.70 |
| ECC83 | 5.55 |
| ECC88 | 5.25 |
| EF86 | 9.90 |
| EL34 | 7.50 |
| EL84 | 4.80 |
| GZ34 | 8.40 |
| KT66 | 9.50 |
| KT88 Special | |
| GEC replica | 22.50 |
| KT88 | 18.50 |
| TT21 Chinese | 27.00 |

RARE BRANDS

| | | | | | |
|-----------------------|--------|-------------------------|--------|------------------------|--------|
| 33A-101K | 5.40 | 13E1 STC UK | 120.00 | ECC86 Mullard | 5.93 |
| 300B Tesla | 105.00 | 85A2 Mullard | 4.50 | ECF80/6BL8 | 0.75 |
| 3C24EEV | 27.00 | 350B Chinese | 14.25 | ECL82 Tungstram | 3.30 |
| 3B28 RCA | 14.70 | 807 Ceramic | 30.00 | ECL85/805 | 1.49 |
| 4250A/QB35750 Philips | 72.00 | 807 USA | 6.75 | ECL86 | 2.85 |
| 7591A replacement | 39.00 | 1625 USA | 3.95 | EF39/CV1053 | 1.65 |
| 5Y3GT | 3.90 | 6587WB Philips | 5.93 | EF95/CV4010 Mullard | 1.95 |
| 6AH4GT USA | 7.50 | 5751GE | 6.00 | EF184 RFT | 0.99 |
| 6AS7G Russian | 2.93 | 5814AECG/Philips | 2.70 | EL34 Tesla Blue | 12.00 |
| 6AUSGT GE USA | 3.75 | 6028 | 0.99 | EL34 Tesla JJ | 8.10 |
| 6AU8A USA | 0.75 | 6463 GE USA | 2.40 | EL38 | 13.32 |
| 6BE6/5915 ECG Philips | 0.90 | A2293/CV4079 | 4.43 | EL86 Russian | 1.49 |
| 6BH6 RCA | 2.48 | C3m Siemens | 15.30 | EL90 Brimar | 2.70 |
| 6C33CB Russian | 19.50 | CV4062/E2134 | 5.25 | EZ80 Brimar | 6.00 |
| 6J4/CV5311 | 1.80 | DA42 GEC | 28.50 | F2A Siemens | 120.00 |
| 6Q7G/CV587 STC UK | 3.60 | DG7-32 Mullard | 21.00 | F2A11 Siemens | 120.00 |
| 6SQ7 | 3.00 | E80CC Mullard | 45.00 | KT88 Chinese Unbranded | 12.50 |
| 6U8A RCA | 1.43 | E80F Philips | 18.00 | PCL82 Tungstram | 2.15 |
| 6V6 RCA Black Metal | 15.00 | E80L Philips | 31.50 | PCL86 (ECL86) Russian | 0.53 |
| 6V6GT MWT | 6.00 | E88CC Tesla Gold Pin | 8.85 | PT4D Ferranti | 22.50 |
| 12AU7WA RTC France | 7.88 | EC92 RFT | 2.70 | QQV03/20A GEC | 5.25 |
| 12AU7WA Cifte France | 7.88 | ECC81/CV4024 Mullard UK | 7.50 | S1E12/CV4060 | 43.50 |
| 12E1 STC TTT UK | 16.50 | ECC82 Sylvania | 15.00 | Z2b | 27.00 |
| 12SG7 | 1.65 | ECC83 Yugoslavian | 4.05 | | |

WHOLESALE SECTION

| | |
|--|------------------------------------|
| 6AL5/EB91 Mullard, government box | 100 pieces @ £ 75.00 [£0.75 each]* |
| 9002 RCA USA audio triode | 100 pieces @ £ 60.00 [£0.60 each]* |
| E180CC/7062 Mullard UK box anode GVT | 100 pieces @ £280.00 [£2.80 each]* |
| EF37A Mullard UK Grey | 50 pieces @ £125.00 [£2.50 each]* |
| EF86 Russian, identical to Svetlana EF86 but no logo | 50 pieces @ £210.00 [£4.20 each]* |
| EL34 Chinese tested - guaranteed | 50 pieces @ £175.00 [£3.50 each]* |
| C3M Siemens, government box | 20 pieces @ £150.00 [£7.50 each]* |

RARE SOCKETS

| | | | |
|-------------------|-------|--------------------------------------|-------|
| 47E [for 4212E] | 37.50 | PO5 [for Aa, Ba] | 11.70 |
| 4B4/B5B [for PX4] | .98 | Octal and B9A sockets IN STOCK...POA | |
| 45DA [for DA100] | 15.00 | Side contact for AZ1 [CT8] | 10.43 |

BILLINGTON EXPORT LTD IE GILLMANS INDUSTRIAL ESTATE BILLINGHURST SUSSEX RH14 9EZ

TEL: (0)1403 784961 FAX: (0)1403 783519 email: billingtonexportltd@btinternet.com

VISITORS BY APPOINTMENT ONLY PLEASE


All items in stock at the time of going to press. Prices in GB Pounds. Please ask for our free 50 page catalogue of valves. AMERICAN EXPRESS, MASTER-CARD, VISA, accepted. MINIMUM ORDER: UK £50 + VAT & Carriage. Export £100.00 [US \$150.00] + Carriage. 3,000 OTHER TYPES OF VALVES IN STOCK! PLEASE INQUIRE FOR ANY TYPE NOT LISTED.



CRICKLEWOOD ELECTRONICS

ANSAR SUPERSOUND
Audio Polypropylene 400VDC±5%

The secret's in the metallised film!

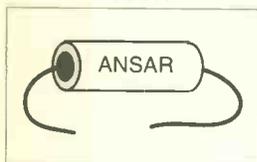

Manufactured specifically for high end audio, these polypropylene capacitors offer exceptional value for money as they use a specially imported high purity metallised polypropylene film, ensuring smooth, detailed and transparent sound quality and extremely low distortion whether they are placed directly in the signal path such as in crossovers or for decoupling etc. Ideal for replacing old, stale and leaky capacitors.

| Part No | Value | Price |
|---------|------------------|--------|
| CW100N | CAP PROPYL 100nf | £1.25 |
| CW150N | CAP PROPYL 150nf | £1.25 |
| CW220N | CAP PROPYL 220nf | £1.25 |
| CW330N | CAP PROPYL 330nf | £1.25 |
| CW470N | CAP PROPYL 470nf | £1.25 |
| CW680N | CAP PROPYL 680nf | £1.25 |
| CW110N | CAP PROPYL 1.1µf | £1.25 |
| CW150N | CAP PROPYL 1.5µf | £1.50 |
| CW220N | CAP PROPYL 2.2µf | £1.85 |
| CW330N | CAP PROPYL 3.3µf | £2.00 |
| CW470N | CAP PROPYL 4.7µf | £2.00 |
| CW680N | CAP PROPYL 6.8µf | £2.50 |
| CW100N | CAP PROPYL 10µf | £3.50 |
| CW150 | CAP PROPYL 15µf | £4.50 |
| CW220 | CAP PROPYL 22µf | £6.50 |
| CW500 | CAP PROPYL 50µf | £9.95 |
| CW1000 | CAP PROPYL 100µf | £20.00 |

Low value capacitors are extensively used in amps & preamps (especially in tone control, bass & treble etc) by changing to polypropylene you can enjoy an enhanced lighter - brighter sound especially in the treble and mid bass range, and a transparent lower bass improvement. Close tolerance & high stability ensure that both channels can be very closely matched.

| Part No | Value | Voltage | Price |
|---------|------------------|---------|-------|
| PP47P | CAP PROPYL 47pF | 250V | £0.35 |
| PP100P | CAP PROPYL 100pF | 250V | £0.35 |
| PP150P | CAP PROPYL 150pF | 250V | £0.35 |
| PP220P | CAP PROPYL 220pF | 250V | £0.35 |
| PP330P | CAP PROPYL 330pF | 250V | £0.35 |
| PP470P | CAP PROPYL 470pF | 250V | £0.35 |

Low Impedance High Temperature (105° C) Radial Electrolytics ± 5%

Superior electrolytics at affordable prices. The low impedance end resistance maximises signal purity, whilst the superior temperature characteristics allow the capacitor to remain very stable under the most varying conditions.


| Part No | Value | Voltage | Price |
|---------|-------------------------|---------|-------|
| 1H50 | LO 2 HI TEMP 1µf | 50V | £0.25 |
| 2U2H50 | LO 2 HI TEMP 2.2µf | 50V | £0.25 |
| 4U7H63 | LO 2 HI TEMP 4.7µf | 63V | £0.25 |
| 10H63 | LO 2 HI TEMP 10µf | 63V | £0.25 |
| 22H63 | LO 2 HI TEMP 22µf | 63V | £0.30 |
| 47H63 | LO 2 HI TEMP 47µf | 63V | £0.35 |
| 100H63 | LO 2 HI TEMP 100µf | 63V | £0.50 |
| 220H50 | LO 2 HI TEMP 220µf | 50V | £0.75 |
| 470H63 | LO 2 HI TEMP 470µf | 63V | £1.25 |
| 1000H35 | LO 2 HI TEMP 1000µf 35V | | £1.50 |
| 2200H50 | LO 2 HI TEMP 2200µf 50V | | £2.25 |
| 4700H25 | LO 2 HI TEMP 4700µf 25V | | £2.50 |

Trobo Solder Lug Reservoir Capacitor 10,000µF 10V

Choosing the right electrolytic for power supply use is very important in keeping down hum whilst allowing maximum current flow for good transient & bass response. Elna capacitors are respected the World over for their exceptional audio attributes.

| Part No | µF/Voltage | Price |
|----------|--------------------|--------|
| 10000C80 | CAL ELNA1000µF/80V | £11.00 |

Monacor Air Cored Inductors.

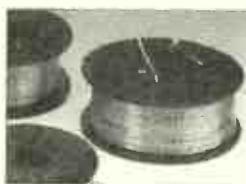

A range of professional air cored inductors for 8Ω or 4Ω crossovers/filters for use up to 3000Hz. 1.2mm enamelled copper wire wound on air spaced plastic bobbins.

| Part No | Specification | Price |
|---------|--------------------|--------|
| P15 | 150µH 0.150 8x19mm | £2.00 |
| P22 | 220µH 0.150 4x19mm | £2.50 |
| P33 | 330µH 0.20 8x19mm | £3.00 |
| P47 | 470µH 0.250 5x19mm | £3.50 |
| P68 | 680µH 0.350 5x19mm | £4.50 |
| P100 | 1mH 0.40 5x19mm | £5.50 |
| P150 | 1.5mH 0.50 70x30mm | £6.50 |
| P220 | 2.2mH 0.60 70x30mm | £8.00 |
| P330 | 3.3mH 0.75 70x30 | £10.00 |

Monacor Ferrite Inductors



A range of professional high efficiency ferrite cored inductors with very low ohmic losses for 8Ω or 4Ω crossovers or filters for use up to 4000Hz. 1.4mm enamelled copper wire (1.3mm on F1000) wound on plastic bobbin.

| Part No | Specification | Price |
|---------|--------------------------|--------|
| F220 | 2.2mH 0.150 400W 55x31mm | £6.50 |
| F330 | 3.3mH 0.20 330W 65x39mm | £9.50 |
| F470 | 4.7mH 0.250 140W 65x30mm | £11.00 |
| F680 | 6.8mH 0.350 140W 65x39mm | £12.00 |
| F1000 | 10mH 0.450 100W 65x39mm | £13.50 |

High Quality Valves

| Part No | Description | Price |
|---------|-------------------|--------|
| 6550C | OUTPUT VALVE | £26.00 |
| 6L6GT | OUTPUT VALVE | £4.50 |
| 65N7GT | OUTPUT VALVE | £4.50 |
| 6V6GT | OUTPUT VALVE | £3.95 |
| ECC81 | TRIODE | £4.50 |
| ECC82 | TRIODE | £4.50 |
| ECC83 | TRIODE | £4.50 |
| EF86 | LOW NOISE PENTODE | £9.90 |
| EL34 | OUTPUT VALVE | £8.50 |
| EL84 | OUTPUT VALVE | £3.50 |
| GZ34 | RECTIFIER | £6.50 |
| KT88 | OUTPUT VALVE | £20.00 |

Valve Holders - High quality valve bases. Chassis mounting with screw fittings.

| Part No | Description | Price |
|---------|----------------------------|-------|
| B9AC | B9A VALVE HOLDER CERAMIC | £1.50 |
| CC | SCREENING CAN | £2.25 |
| OC7C | OCTAL VALVE HOLDER CERAMIC | £2.00 |
| IN | OCTAL VALVE HOLDER PHENOL | £2.50 |

Fully Gold Plated Phono (RCA) Plugs with spring coil cable grip.



| Part No | Description | Price |
|---------|-------------------------------------|------------|
| PPG5A2 | PAIR GOLD PLUGS for up to 5mm CABLE | £1.50 pair |
| PPG8A2 | PAIR GOLD PLUGS for up to 8mm CABLE | £1.50 pair |

Very High Quality Phono (RCA) Plugs



Very high quality satin grey metal with heavy gold plated connections. Top collet cable grip & PTFE insulators. Very low noise.

| Part No | Description | Price |
|---------|-------------------------------------|------------|
| PPG6H2 | GOLD PTFE PLUGS for up to 6mm CABLE | £3.50 pair |
| PPG8H2 | GOLD PTFE PLUGS for up to 8mm CABLE | £3.50 pair |

Extra High Quality Gold Plated Phono Oxygen Free (RCA) Leads (pairs)




Available in 2 colours & 3 lengths. Highly flexible oxy-

gen free cable with extra moulded-in control / grounding wire.

| Part No | Length/Colour | Price |
|---------|-------------------|--------|
| LP10G | 0.8 Metres/Green | £5.50 |
| LP10V | 0.8 Metres/Violet | £5.50 |
| LP20G | 1.5 Metres/Green | £6.50 |
| LP20V | 1.5 Metres/Violet | £6.50 |
| LP35G | 5 Metres/Green | £11.00 |
| LP35V | 5 Metres/Violet | £11.00 |

Bass Reflex Tuning Ports

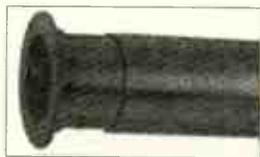

A range of adjustable plastic ports for use in various sizes of loudspeaker cabinets. d=diameter L=adjustable length (mm)

| Part No | Dimensions | Price |
|---------|---|-------|
| R35 | d=35L=110-210 | £2.50 |
| R50 | d=50L=150-280 | £3.00 |
| R70 | d=70L=128-245 | £3.50 |
| R100 | d=110L=160-122 | £5.50 |
| R85 | d=85 angled 45° for narrow cabinets L=210-310 | £6.50 |



High Quality Components at the right price. Please add £2.00 carriage + VAT to all orders. Credit Card phone orders accepted.

rectifier valve, whose anodes are paralleled up, as are its cathodes. In essence, it is behaving like a super-diode, giving the valve touch to the power supply and hence the sound. It also ensures that the 300Bs are not harmed with a surge of current at switch-on since the GZ37 has to warm up for around 30 seconds before current can flow. At this point, the supply splits to separate 3H chokes and 22uF 630V Ansar polypropylene reservoir capacitors.

The first component for replacement was the 1.6A, slow-blow fuse, which was swapped for a miniature circuit breaker. The former is a weak link as you have the fuse wire itself (which is not made of the best audio-grade material) as well as the two touch contacts of the fuse holder. The circuit breaker is an automatic reset device that can be easily soldered straight onto the back of the mains input socket. I used short lengths of 1/1.13mm solid-core wire for rigidity. The breaker's internal contacts are constructed of material superior to fuse wire, yielding a very low internal resistance.

New diodes (D1-4) were called for. These are MUR1400E, which are ultra-fast, soft-recovery types with a very fast switching time of 75ns compared with the 300ns you get with the original BYV96E. They also switch very softly, so they are quiet in operation.

TAKE THE BYPASS

The next three component changes, the bypass caps, are additions to the circuit and warrant an explanation. In audio, an ideal capacitor would have the same characteristics over the entire audio frequency band - its impedance/frequency trace should be a horizontal line. In reality, the trace is more likely to be a parabolic curve with varying angles and depths depending on the value and type of capacitor used. Large value capacitors have a low ESR (Equivalent Series Resistance), troughing at a certain frequency and producing a broad curve. As the frequency increases, so does the resistance, resulting in the curve climbing upwards. Generally, a high-value capacitor gives good bass, smaller ones producing a narrower curve that bottoms out at higher frequencies. Placing the two capacitors together in parallel, the curves bisect to form a 'W' shape, providing an extended impedance/frequency curve which is a lot flatter. This effect can be extended by adding capacitors. As a general rule a bypass capacitor is normally 1/10th minus 1/500th of the previous value. Another bypassing bonus is that smaller capacitors charge and discharge far quicker than their larger companions. The end result is an increase in dynamics and spaciousness.


C9 and C10 were therefore double-bypassed with an Ansar 4.7uF/450V and a 0.1uF/630V M CAPzn™, both of polypropylene. C11 and C12 were bypassed with a 0.22uF/630V

M CAPzn™. These fitted easily around the power supply printed circuit board.

UPGRADE 2 - THE SIGNAL PATH

This time we tried out some resistor changes too, and replaced R1, R2 and R10 with a mix of Vishay and Welwyn Bulk Foil resistors. They are non-magnetic and non-inductive and come terminated with copper lead-outs.

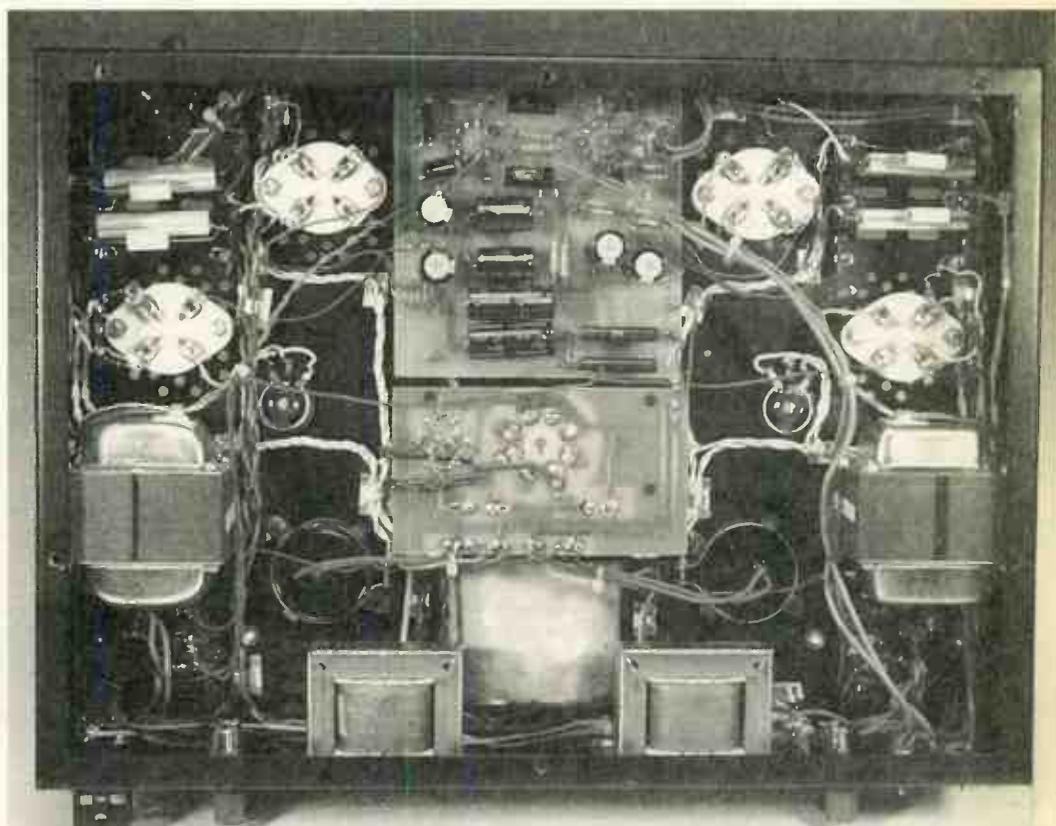For C1 and C4 we used good, old Os-Con SGs. These are



Before the changes - 300B with its complement of standard components which tend to be far smaller than the audiophile parts.

constructed of solid aluminium and black salt to give a series of capacitors which are almost vibration-free and possess very high ripple-current ratings, low ESR and very quick charge/discharge times.

For C3 we returned to an M CAPzn™, while C8 was made up of two Scan-ex polystyrenes in series. All second-section components fit on the driver printed circuit board.

UPGRADE 3 - DECOUPLING


This section entails swapping and bypassing C2 and C3 with a combination of Ansars and M CAPzn™. This was where we started to run into space-management problems. With the larger size of these polypropylene capacitors, along with the replacement and bypass capacitors in the fourth section, make sure you spend some time getting their arrangement within the chassis sorted out - always do a dry-run to make best use of the available space. Then fix the components in firmly with tie-wraps and self-adhesive stickers to avoid vibrational changes.

UPGRADE 4 - THE CATHODES

The fourth section involved replacement and double-bypass of C6 and C7 with Ansars and M CAPzn™ caps. Also, in place of

Rothwell

THE ULTIMATE VOLUME CONTROL

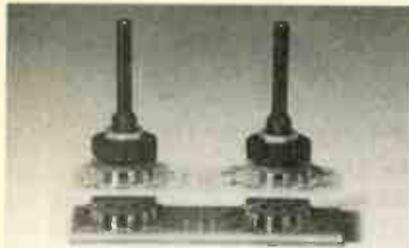

The Rothwell Stepped Attenuator is truly the ultimate volume control. Two 12 way dual gang (stereo) devices are used, one for coarse control, the other for fine. The combination gives 132 volume settings with steps of less than 1dB, and channel balance better than 0.1dB. No pot can come close to the performance of this unit. The sound quality of the attenuator can be staggering when compared to a pot - even the expensive "audiophile" pots using plastic film or cermet tracks pale in comparison. Space, imaging and sheer detail are unsurpassed. This unit may look like an overkill solution to the problem of poor pots, but hearing it proves that it is justified. And using two 12 way devices instead of one 24 or 36 way device not only results in more volume settings - it keeps the price realistic. Instead of the three figure price tag normally associated with stepped attenuators (if you can find one at all), the Rothwell attenuators cost just £79 inc. VAT and postage. Both 10k (ideal for passive pre-amps) and 100k (ideal for valve pre amps) are available, and each unit comes with free application notes giving suggested circuits for various pre amp configurations.

For further details of these attenuators or the other innovative products from Rothwell, (including the only gold interconnects currently available), please contact;

Rothwell Electronics
60 Pennington Road
Great Lever
Bolton
BL3 3BR
Tel/fax 01204 654614

CENTRE ELECTRONICS

'CENTRE HOUSE' 345 STOCKFIELD ROAD YARDLEY
BIRMINGHAM B25 8JP
TELEPHONE 0121 706 0261
Retail Shop Hours Mon-Tues 7-9pm Thurs-Sat 10-4pm

We have pleasure to announce that a range of "Billington" Audio Valves are now available at our retail shop counter. Audio valves of all leading makes and types of vintage and recent manufacture.

A full catalogue of "Billington" Audio Valves and Accessories is also available at only £3.00 inc P+P. Other services offered include Electroplating of Chassis parts small or large items in gold, silver nickel, chrome also special paint finishes including Crackle and Stove Enamel. Complete or part restoration of Vintage Audio, Radio equipment also Kit Builds. Suppliers of rare parts including Transformers (rewinding undertaken) Capacitors Plugs and Sockets, Service data for Vintage Audio and Radio equipment. Valve testing and matching service. Interesting stock of Vintage Audio and Radio equipment always on display.

WANTED - Top prices paid for Valves and Valve Audio equipment and Accessories

Worldwide mail order service available small orders accepted. "Billington valves - no minimum order."

Special Evening opening hours Mon-Tues 7pm-9pm

SPEAKER KITS FROM IPL ACOUSTICS

Over a 9 year period I.P.L. ACOUSTICS have developed a range of high quality speaker kits, using the best units from SEAS, MOREL, AUDAX, and I.P.L. and have produced a comprehensive range of speakers which will compete with the most expensive of commercial designs.


All speakers have biwired crossover kits containing high quality components and terminals.

**S5TL
TRANSMISSION LINE**



PLUS KIT£382.00
TOTAL KIT£506.00

**FIVE TRANS-
MISSION LINE
KITS**

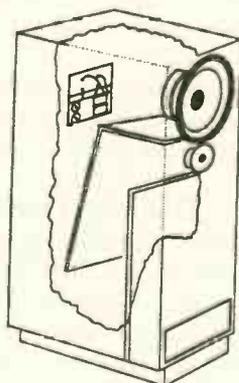

TRANSMISSION LINE
PLUS KITS£177.00 -
.....£382.00

**M3TL
TRANSMISSION LINE**



PLUS KITS£177.00
TOTAL KIT£241.80

**A2 H.D.A.
AEROGEL KIT**



PLUS KIT£187.50
TOTAL KIT£259.00

**S3TLM METAL
TRANSMISSION LINE**




PLUS KIT£233.00
TOTAL KIT£311.50

PRE-VENEERED CABINET KITS NOW AVAILABLE. Carriage charge extra on all kits.

If you would like further details please send large SAE with 36p stamp for PAGE SPEAKER BUILDING CATALOGUE, comprising VALUABLE ADVICE on DESIGNING, BUILDING, and TESTING speakers and full technical specifications including response curves of eight kits, drive units, and details of SPECIALIST CABLES and ACCESSORIES. KITS FOR A.V. USE NOW AVAILABLE.

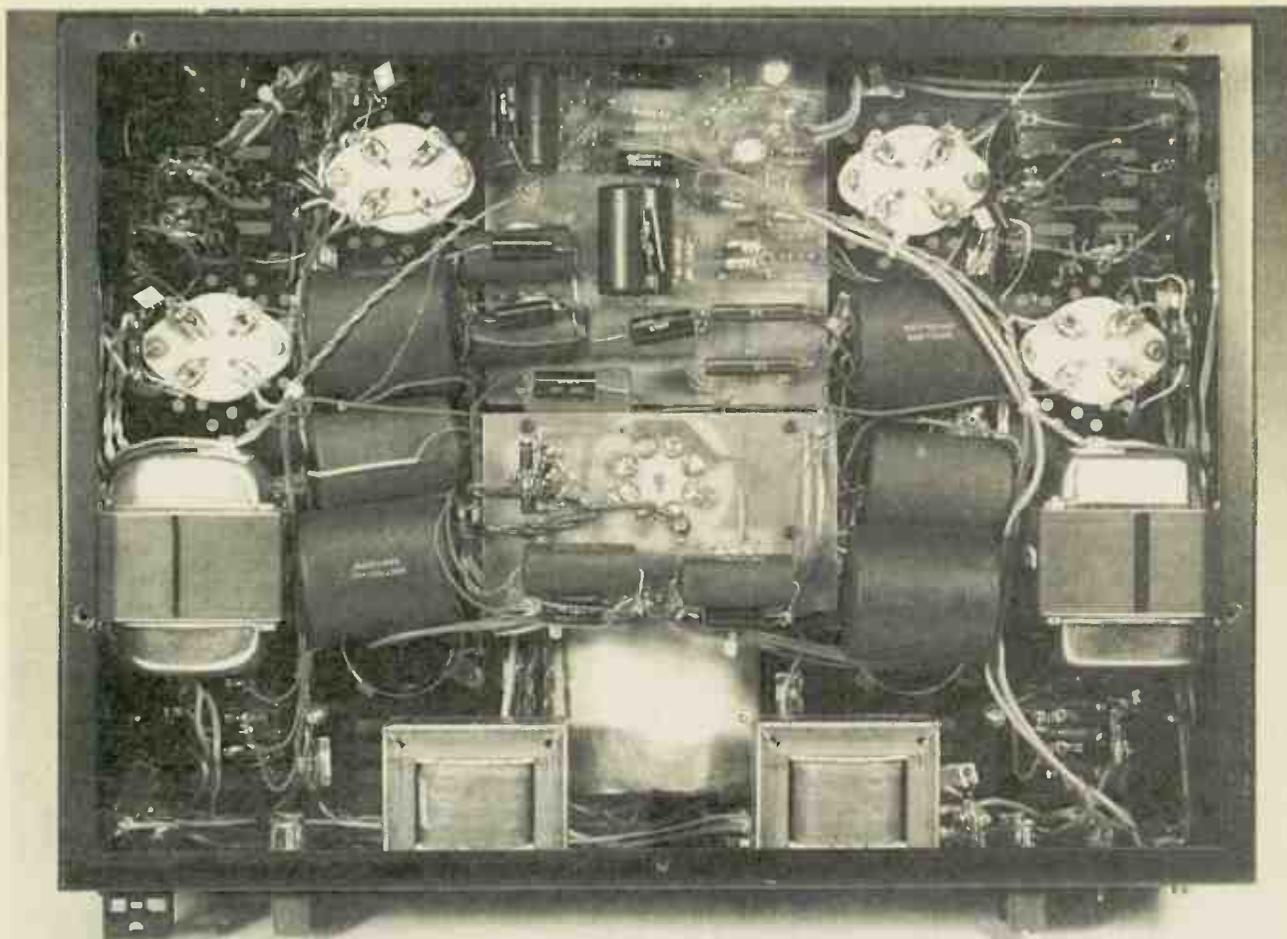I.P.L. Acoustics, 2 Laverton Road, Westbury, Wiltshire, BA13 3RS. Tel: 01373 823333



After the modifications, space is at a premium inside the 300B, especially when the polypropylene reservoir caps have been soldered in.

the standard R12 and R13 we used two Caddock high-power, bulk-foils in series mounted on a heatsink. These fitted easily as the bulk foils come in isolated packages.

All of these modifications are relatively easy to carry out, the only complication being the location of the larger capacitors. The various new parts were then allowed to burn in over the course of a couple of months. We decided to gauge their effectiveness by removing them and soldering back in the original components.

SOUND QUALITY

Undoing an upgrade project like this can be an ear-opening experience. More worryingly of course is the fact that you are removing improvements and trusting that an amplifier will still be worth listening to when you've done.

Removing (with a stifled sob) the Ansar and M CAPzn™ cathode network and replacing the standard ceramic resistors and electrolytics laid a light veil over the sound, particularly vocals. Bass remained coherent but just a smidgen less incisive than the fully-modified version, while the midrange was largely unaltered. Blues Union with Joe Beard had drive to spare and the 300B was not dynamically challenged in the least.

The next stage of deconstruction took out the bypassed de-coupling capacitors and, in the process, left what now seemed to be wide open spaces under the bonnet. Although the choice of de-coupling caps can make or break an amp (or fry it, if they fail!), to the credit of the original design the difference between the two sets of components was not painfully wide.

As demonstrated by the cor anglais in the opening of

Stravinsky's Rite Of Spring, this time there was unquestionably a heavier veil drawn over the proceedings. That said, in spite of the sound lacking a little detail, the amp as a whole sounded more 'at one' with itself and cohesive, the quacking of the bass clarinet possessing a real 'Bronx Cheer' quality which showed that frequency and dynamics were still on board.

Eric Bib and his very acoustic recordings were enjoying a particularly valvesque sound. Bass had become more of a back-seat driver but the performance maintained a real sense of coherence and overall musicality. The reduction of input stage power-supply filtering obviously glossed over some of the finer points of treble insight but, as remarked above, the whole caboodle was still sounding very sweet.

Un-picking the resistor changes and regressing to the standard electrolytics on the input cathode bias gave the amplifier a smoothness which, to some, is identified with the past and names like Peter Walker, Harold Leak et al. Blues Union still packed an addictive punch - in that area the characteristic of the amp had altered little - but the more incisive presentation had softened and bass was tending to slow down.

The last step saw the power supply denuded of its extra capacitance. I had my fingers crossed about the effect this un-smoothing of the current would have; I needn't have worried. Admittedly, for the first time since I began poor recordings could sound slightly grainy but the 300B was far from defeated. Every one of the steps above had made an audible difference, yet the amplifier standing in nothing but its socks still had more than enough to keep a music-lover happy.

Colomor (Electronics) Ltd

Unit 5 Huffwood Trading Estate, Brookers Road, Billingham, West Sussex RH14 9RZ Tel: 0(44)1 403 786 559

Fax: 0(44)1 403 786 560 E MAIL - sales@colomordemon.co.uk

VALVES SPECIAL OFFER

| | £p each | £p each |
|-------------------------------------|---------|--|
| 803 USA | 50.00 | EF91 1.00 |
| 807 CERAMIC BASE | 20.00 | EF95 1.00 |
| 807 USA | 5.00 | PCL86145V, HTR, ECL86 0.50 |
| 808 POA | | £35 / 100; £250 / 1000 |
| 813 RCA | 35.00 | PT15 MARCONI 35.00 |
| 1625 USA | 3.50 | PX4 POA |
| DA100 | 3.50 | PX25 POA |
| DC7-3 MULLARD | 10.00 | VT4C211, GE, USED, TESTED & GUARANTEED 45.00 |
| ESSU8233 AMPREX | 16.00 | B4 BASES 1.00 |
| E80F1 | 5.00 | B5 BASES 1.50 |
| E180CC | 2.50 | |
| EB916 AL5 | 70 | |
| ECC88 MULLARD / FOREIGN | 2.00 | |
| ECC803 TE, EFUNKEN | 18.00 | |
| ECC808 TELLFUNKEN, ORIGINAL WITH <> | 30.00 | |
| EF37A MULLARD, GREY | 2.50 | |
| EF39 CV1053 | 1.25 | |

PLEASE SEND LARGE
1st CLASS STAMPED
SAE FOR OUR
FREE VALVE CATALOGUE.

| TRANSFORMERS, CHOKES & BLOCK CAPACITORS | 75mA 6.3V 5A 6.3V 25A 6.3V 500mA 6.3V 300mA 4V 500mA £40.00 | 5H, 400mA £38.78 ea; 7.5H, 250mA £30.00ea |
|---|---|---|
| Oil filled block capacitors by TTC Dublier 5uf, 1uf, 2uf, 4uf all at 600V £6.00 ea. | Primary 115-250-440V Secondary 640-0-640V 160mA 330-0-330 225mA £50.00 | 10H, 75mA £23.50 ea; 10H, 170mA £33.00ea 20H, 50mA £30.00ea; |
| 8uf, 600V; 5uf, 1KV; 1uf, 1KV; 2uf, 800V; 4uf, 1KV £8.00 ea. | New Mains Isolation Transformers 250V, 50Hz, 1to 13kVA, 13A fused Class F, 13A Skt & Plug £95.00 ea. | 10H, 75mA Varnished £10.00 |
| 8uf, 800V £10.00 ea. | Oil filled Chokes by Parmeko/ Gardeners 2.5H, 220mA; 2.5H, 350mA; 4.5H, 150 mA; 4.5H, 220mA; 4.5H, 280mA; 5H, 110mA; 5H, 200mA; 5H, 250mA; all at £30.00 ea. | .6 H, 300mA A Gardeners, varnished, £8.00 5H 100mA Oil, Parmeko, £15.00 15H, 25mA, Gardeners, varnished, £6.00 ea 20H, 75mA, Oil Parmeko, £30.00 ea. |
| Oil filled Transformer, Gardeners Primary 110-240V; Secondary 250-0-250; 180mA 6.3V, 7A, 5V, 3A £50.00 EA Primary 110 250V Secondary 400-0-400 | | |

| OTHER VALVES | £p each | | £p each |
|-----------------------|---------|--------------------------------------|---------|
| ECC81 | 2.15 | 5R4GA | 6.15 |
| ECC81 CV4024 | 6.00 | 5R4GY | 5.80 |
| ECC82 | 2.50 | 5U4G | 4.95 |
| ECC82 BRIMAR | 7.25 | 5U4G BRIMAR | 6.00 |
| ECC82 MULLARD | 8.00 | 5Z3GT | 3.60 |
| ECC82 CV4003, BRIMAR | 10.00 | 5Z4GT | 1.90 |
| ECC82 CV4003, MULLARD | 12.50 | 5Z4G | 6.00 |
| ECC83 SOVTEK | 3.35 | 6B4G SYLVANIA | 28.95 |
| ECC83 MULLARD | 9.50 | 6B4G SHOULDERED | 35.00 |
| ECC85 | 2.30 | 6BH6 | 2.60 |
| ECC85 MULLARD | 4.00 | 6FQ7 | 9.45 |
| ECC88 TESLA | 2.00 | 6L6G CV1947 | 30.00 |
| ECC88 SIEMANS | 4.95 | 6L6 METAL | 9.80 |
| ECC88 MULLARD | 10.00 | 6L6G Colomor | 6.40 |
| E88CC MULLARD | 10.00 | 6L6GC SYLVANIA | 14.90 |
| E88CC/01 | 10.00 | 6L6GT/C | 2.50 |
| E88CC/01 MULLARD | 16.95 | 6L6WGA SYLVANIA | 12.00 |
| ECH81 | 1.60 | 6L6WGB | 12.00 |
| ECH81 PHILIPS | 3.50 | 6SL7GT | 2.35 |
| ECL82 GERMAN | 4.50 | 6SL7GT BRIMAR | 8.00 |
| EF86 | 4.35 | 6SN7GT | 3.60 |
| EF86 MULLARD | 11.00 | 6SN7GT BRIMAR | 8.00 |
| EL33 CV1438, MULLARD | 12.75 | 6V6GT | 5.10 |
| EL34 SOVTEK | 6.00 | 6X4 | 2.00 |
| EL34B | 6.15 | 6X4WA | 3.30 |
| EL37 MULLARD | 27.45 | 12BY7 RCA | 8.45 |
| EL84 SOVTEK | 2.15 | 12BY7A GE | 8.45 |
| EL84 MAZDA | 5.10 | 13E1 STC, UK | 76.60 |
| EZ80 | 1.90 | 85A2 | 2.20 |
| EZ80 MULLARD | 6.00 | 6072A | 7.45 |
| EZ81 MULLARD | 6.00 | 6146 | 13.85 |
| GZ33 MULLARD | 13.00 | 6336A USA | 49.00 |
| GZ34 | 3.50 | 6550A | 9.55 |
| GZ34 MULLARD | 15.00 | 6550A GE | 24.15 |
| GZ37 MULLARD | 7.00 | 6550A MATCHED PAIRS | 32.00 |
| KT66 MATCHED PAIR | 52.00 | 6550-B2 SVETLANA | 12.75 |
| KT88 | 17.85 | | |
| VT4C GE | 120.00 | AVO CT160 VALVE TESTER £150.00 | |

VAT @ 17.5% TO BE ADDED TO ALL UK & EEC VAILABLE ORDERS
P&P UK 1-3 valves £1.95 4-6 £3.00 7-10 valves £4.55
Other countries please apply for tariff.
Payment by Cheques, P.O.'s, Banker's Draft
sent to address above. Please

WIRE & INSULATION

introduce **DESKADEL** Products

731/733 Ormskirk Road • Pemberton
Wigan • Lancashire • England • WN5 8AT
TEL/FAX: 44 - 1 - 942 887171

The **DESKADEL** range of HI-Fi interconnect, speaker cables, hook-up wires and tone arm wires are precision manufactured featuring **PURE SILVER** conductors insulated with **PTFE** in a variety of designs to suit all applications. Using only the finest materials and the latest manufacturing techniques we aim to provide a selection of quality products for superb natural sound reproduction on a scale previously unheard.

DISTRIBUTORS:

ARBELOS

Tel/Fax: 41-613616466

AUDIO SYNTHESIS

Tel: 44-1-159224138

Fax: 44-1-159229701

ANALOGUE AUDIO PRODUCTS

Tel/Fax: 31-30-6044342

DESKADEL INT BVBA

Tel: 32-3-8892231

Fax: 32-38609181

UNDERSTAND AMPLIFIERS

By Owen Bishop

Reviewed by Haider Bahrani.


When *Understand Amplifiers* dropped onto my desk I was hovering over a prototype amplifier, cursing it for the trouble it was giving me. Our beloved editor had clearly foreseen my difficulties and realised I was in need of help through a therapeutic book review.

Understand Amplifiers is, as the title suggests, a book about amplifiers, the electronic kind that is. When we think of amplifiers, many of us (and especially owners of hi-fi) will picture a box filled with transistors or stacked up with valves ready to pump out music. Amplifiers are, of course, used in many areas of electronics and at frequencies well above and below the audible spectrum. They all, however, stem from the same basic principles, and it is these to which this book is dedicated.

The first chapter basically focuses on the nature of a signal and what is meant by amplifying it. Sine waves play a large part in the explanations, which lead on to more complex periodic signals before moving on into clear and easily comprehensible descriptions of both current and voltage gain.

On the final page of this chapter we meet with one of Owen Bishop's explanatory boxes. The author uses these little asides to add extra detail and depth to the main points. In this case he gives a brief and unambiguous description of noise in electronic circuitry.

The second chapter starts to get a little more technical, but not dauntingly so, as the behaviour of a simple amplifier comes under the spotlight. The circuit in this case is a single-transistor MOSFET amplifier. The reason given for this choice of device is that MOSFETs (Metal Oxide Field Effect Transistors) are the easiest to understand. If truth be told, as a student it took me a great deal longer to understand these devices than other types. However, reading about them here they certainly seem straightforward enough. The chapter then goes on to explain biasing, coupling, input resistance, etc with plenty more explanatory boxes to keep the reader out of the dark.

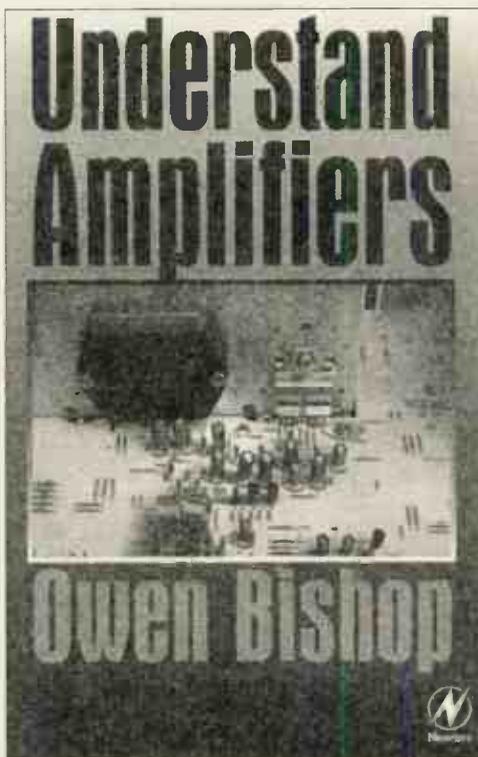

Field Effect Transistors are given more airtime (or should I say page space) with that imaginatively-titled chapter, More FET Amplifiers. This section introduces one or two other types of FET, but concentrates mainly on using MOSFETs in a source-follower configuration, the formation that is common in the output stages of MOSFET power amplifiers.

Chapter Four steers away from solid-state circuitry for a while and looks at the great favourite of the troops at World Towers, the valve amplifier. Although a much older and quite different technology, the basic principles of valve amplifiers are much the same as the ones described in the previous chapters, and the reader is left in no doubt of this fact. The author then goes on to introduce a number of different valves.

From Chapter Five onwards, the device that most electronics dabblers think of when the word "transistor" is used (the Bipolar Junction Transistor, or BJT for short) is examined. Chapter Six gives the BJT and its implementation in basic amplifiers the once over, as per its cousins above.

Things hot up a little when bootstrapping, differential amplifiers and constant-current sources start creeping into the frame. Many of the techniques and circuits are shown using BJTs because this is how they commonly appear in practice although, as before, the principles are much the same and, particularly with FETs, can mostly be duplicated with the other devices.

Power amplifiers are honoured with a chapter of their own and again, most of the formats are described using bipolars. The chapter begins by detailing the class A power amplifier before ascending the efficiency scale via classes B, C and D, with more than a brief mention of their functioning and application. As well as the basic circuits, temperature stabilising techniques are covered as well.


The eighth chapter is dedicated to high-frequency amplifiers, along with all the pitfalls and problems that can cause designers headaches. Amongst these are the evils of stray capacitance, the Miller effect and the results of phase response on a circuit's behaviour. Also discussed are the benefits of different types of devices in the various high-frequency applications.

What follows thereafter is a chapter all about the imperfections that amplifiers (and all electronic circuits) exhibit, including noise, group delay, harmonic distortion, etc. The descriptions are backed up with a well-presented example.

The book is brought to a close with two short chapters on the operational amplifiers which are used in most small-signal circuitry these days. These sections serve as a good general introduction to the subject of op amps.

As an introduction to the topic, or even as a reminder of the vital basics, the *Understand Amplifiers* path is an excellent one to tread. I would also recommend it as an engineer's handbook since I have recently discovered (for the nth time) that nearly all problems have their roots in basic principles.

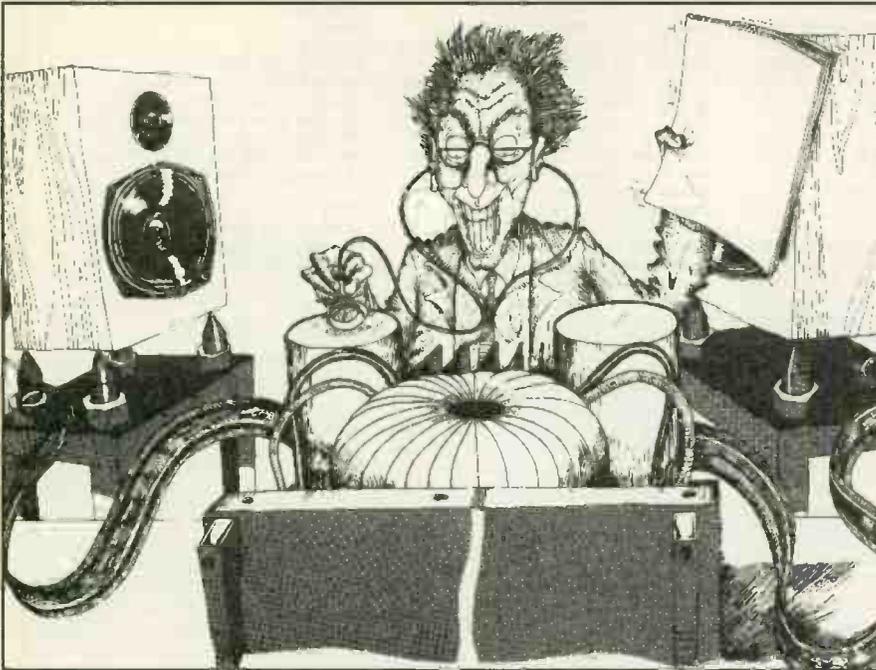Understand Amplifiers
Available from our World Library.
See p50 for order form (book code 1560).
Price: £16.99 plus £2.50 P+P
ISBN: 0750637439



DIY

Letters

HOT SOURCE

If memory does not fail, I think I have read that putting sorbothane on top of capacitors and chipsets can be a good tweak. I am somewhat concerned about heat in digital ICs, though. Do you think this modification will shorten their life, or even damage them?

Joaquín Mejía
quijanoterocio@mx2.redestb.es


A fairly simple gauge of whether or not you can stick sorbothane (or thin patches of Blu-Tack for that matter) to an IC is how hot it feels to the touch when it's powered up. If it's cool, sorbothane away; if it's warm or hot, steer well clear. JM

HI-FI ACTIVITY

Here are some notes on the Maplin DR66 active crossover unit. My initial reactions to the DR66 were similar to K. Foster's (Supplement No36), although prolonged auditioning proved slightly tiring.

I spoke to hi-fi designer John Cheadle, who suggested that what I was hearing may have been due to poor componentry and a cheapo power supply. With his help, I constructed a power supply taken from one of my Arcam A60 amplifiers (now used solely as power amps) which resulted in a considerable improvement.

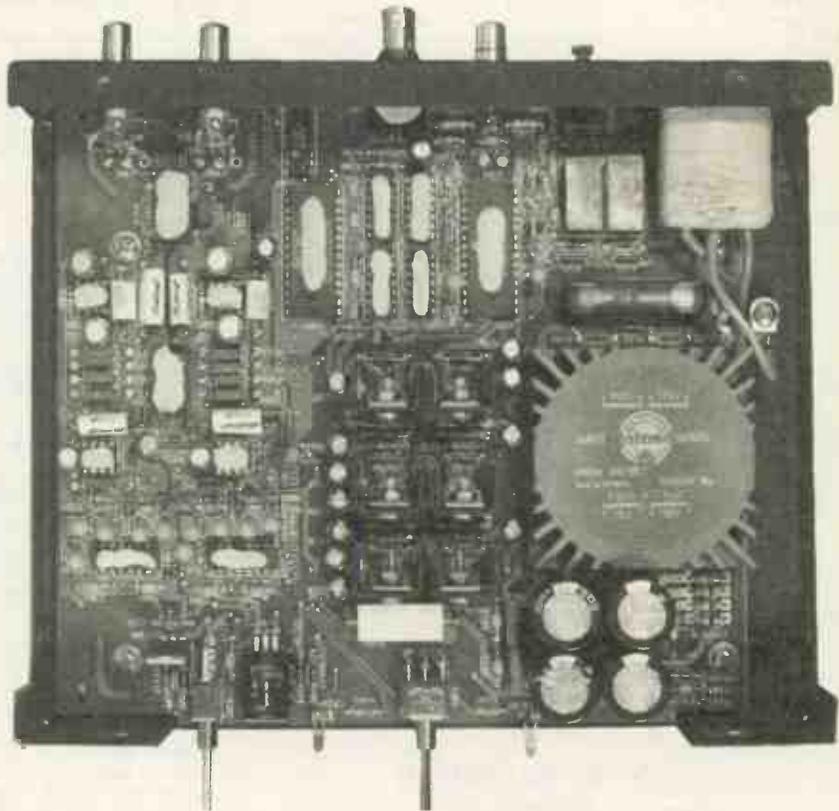John also advised me to change the capacitors, diodes and op amps for better items. These modifications really improved the sound quality in all departments. I have included a separate description of this work. I also lengthened



Another way of cutting out vibration in ICs is a little of the tweaker's best friend, Blu-Tack.

the ports on my 'speakers by about 1 in. to optimise the bass performance with the new crossover characteristics.

Although very pleased with the sound, I am still not sure if it is the optimum arrangement, so I plan to take some measurements when I can get hold of a sound level meter. Falcon Acoustics suggest that a ported 'speaker cabinet will often need to be enlarged after conversion

to active operation. I hope to experiment with larger enclosures soon.

Overall, I thoroughly recommend the DR66. Active crossovers have so many advantages over their passive counterparts. And since many of us now have two amplifiers, the DR66 provides a very cost-effective way of going active.

My system now comprises a Cambridge CD-45E CD player,

KIT & COMPONENT SUPPLIERS

LOUDSPEAKER KIT SUPPLIERS

Wilmslow Audio, 50 Main Street, Broughton Astley, Leicester LE9 6RO
Tel: (01455) 286603
Fax: (01455) 286605

UK distributors of Drive Units from ATC, COLES, DYNAUDIO, KEF, MOREL, PEERLESS, RCL, SEAS, SCANSPEAK AND VOLT.

Comprehensive range of high quality crossover components, acoustic damping products, connectors and veneers. Over 20 different D.I.Y. loudspeaker kits on demonstration, including ATC 50 & 100.

Audio Note (UK Ltd)
Unit C, Peacock Ind. Est.
125-127 Davigdor Road
Have, East Sussex BN13 1SG
Tel: 01273 220511
Fax: 01273 731298

Suppliers of a large amount of components for the Audiophile Kit builder. Valve amplification data and vintage circuits also available. See the double page spread in the back section of the main issue for extra & more detailed information.

Avondale Audio,
The Hollius, Avondale Road
Chesterfield S40 4TF
Tel: 01246 200096
Fax: 01246 207240

Audio Engineers, upgrades, Improvements & servicing to both static and moving parts of the hi-fi chain. (amps as well as turntables). Also bespoke range of own equipment and an extensive range of parts & components available.

European Precision Mouldings Ltd
Highwyh, Sawbridgeworth,
Herts, CM21 0JS
Tel: 01279 600428
Fax: 01279 723846

Manufacturers of the Red Scorpion range of loudspeaker terminals and binding posts.

Falcon DIY Speakers
Falcon Acoustics Ltd., Tabor House,
Norwich Road, Mulbarton,
Norfolk NR14 8JT.

UK distributors of FOCAL drive units & Kits, plus SOLEN (SCR - Chateauroux) polypropylene capacitors and the largest specialist Audio inductor manufacturer in the UK. Stocking Audio Amateur Publications and Audio Computer Software. Comprehensive range of D.I.Y. Speaker kits, Parts, Accessories and Books. Please send large SAE (38p) for free price list. "Everything but the wood"

IPL Acoustics, 2 Laverton Road, Westbury, Wiltshire BA13 3RS.
Tel: 0373 823333

IPL supply a range of eight speaker kits using drive units from SEAS, Morel, Audax, Visaton etc. including four transmission lines to suit all room sizes. We also supply a full range of drive units, capacitors, and cabinet accessories as well as silver plated P.T.F.E. insulated cables.

South Coast Speakers Ltd
326 Portwood Road,
Southampton, Hampshire.
Tel: 01703 559312

UK suppliers for High-Quality Driver Units from: SEAS VOLT VISION SCAN-SPEAK also MOREL RCL & many more. Accessories/Components all of the Highest Quality Inc. ProAudio MKT Capacitors, Inductors wound to order for any values. Many DIY Kits always on demonstration in our comfortable listening area. Custom design services & friendly advice!

VALVE AND OUTPUT TRANSFORMER SUPPLIERS

Wilson Valves, 28 Banks Avenue, Golcar, Huddersfield, West Yorks HD7 4LZ.
Tel: 01484 654650
Fax: 01484 655699

E-mail: wilsonvalves@surfink.co.uk
We stock over 2,500 different types of valves, N.O.S. and New. Please send a S.A.E. for full list. No charge for matching. Most major credit cards accepted.

Chelmer Valve Company
130 New London Road,
Chelmsford, Essex CM2 0RG.
Tel: 01245 265865 Fax: 01245 490064.

Supplier of premium range of audio valves, other valves and components also available. (Please see our main advertisement in this supplement).

Billington Export Ltd.
1E Gillmans Trading Estate,
Billingshurst,
West Sussex RH14 9EZ
Tel: 01403 784961
Fax: 01403 783519

Billington Export Ltd. holds large stocks of audio valves including many obsolete brands such as Mullard, GEC, Brimar etc. as well as Sovtek, Thermionic Gold Brand and the recently introduced Billington Gold range. Also Cathode Ray Tubes (eg. used in Marantz tuner 10B). 50 page catalogue available, tel or fax for a quotation. Minimum order £50.00 UK, £100 export.

Langrex Supplies Ltd
1 Mayo Road, Croydon,
Surrey CRO 2QP
Tel: 0181 684 1166
Fax: 0181 684 3056

One of the largest distributors of electronic valves, tubes and semi-conductors in the UK by original UK and USA manufacturers. Obsolete types are a speciality. Telephone or fax for an immediate quotation.

Watford Valves
3 Ryall Close, Bricket Wood,
St. Albans, Herts AL2 3TS
Tel: 01923 893270
Fax: 01923 679207

Specialist in new old stock and current production valves. Sole UK distributor of the Harma Diamond range selected for their superior performance. Huge range held, stockists of Mullard, GE, Phillips, National, Brimar, Sylvania, Telefunken, RCA, MOV and many more. All valves are new boxed and guaranteed. For free price list and specialist advice call or fax Derek Rocco, Watford Valves.

PM Components
Springhead Enterprise Park,
Springhead Road, Gravesend,
Kent DA11 3HD
Tel: 0474 560521

P.M. Components Ltd are the specialist component company for High End Audio enthusiasts. We have a design and manufacturing base for audio valves and associated products and have a capability to produce custom tubes for major manufacturers. Our 70 page catalogue is available at £2.50 including U.K. postage. P.M. Components are major stockists for Golden Dragon, Mullard, GEC and Teonex valves and have a vast archive of vintage tubes gathered from every manufacturer in the world.

Woodside Sound Engineering,
Arfryn, Llanboidy, Whitland. SA34 0EY
Tel: 01994 448271 Fax: 01994 448665
E-Mail: woodside@arfryn.demon.co.uk

As well as producing transformers for our own products, we can now offer an expanding range of audio transformers for new ventures and Renovations. We can wind transformers for most RADFORD amplifiers to original specification. Contact us with your requirements or a list of standard items is available on request.

CLASSIC TURNTABLES

Technical & General
P.O. Box 53, Crowborough,
East Sussex TN6 2BY.
Tel: 01892 65 45 34.

The original specialist source of spares, replacements and expertise for the classic turntables. Years of actual experience and comprehensive range of parts (originals and re-manufactures), manuals, ancillaries, No dubious 'improvements' - no harmful 'modifications'. Our specialities: Connoisseur; Garrard; Goldring; Lenco; S.M.E.; Thorens; Watts; Ortofon; Shure; Cartridges and stylus for 78s, Mono LPs, Stereo LPs.

COMPONENT SUPPLIERS

PV Tubes, 108 Abbey Street, Accrington, Lancs BB5 1EE. Tel: 01254 872500. Fax: 01254 872166. Large range of electronic and TV components, satellite and aerial equipment. Call today for efficient service.

Audio-Links
7 Fairmont Crescent, Scunthorpe,
North Lincolnshire DN16 1EL.
Tel/Fax: 01724 870432

Large range of specialist electronic components and accessories for solid state and valve enthusiasts. Mail order and a friendly service. Monday to Saturday, 10am - 7pm. Catalogue - £2.00.

AudioCom (UK),
Unit 6, Tindle Enterprise Centre
Warren Street, Tenby
Pembrokeshire, SA70 7JY
Tel: 01834 842803
Fax: 01834 842804

E-Mail: audiocom@connect-wales.co.uk
AudioCom are suppliers of Premium Grade components, including: ALPS, BHC, AEROVOX, Burr Brown, Caddock, Danish Audio Connect, DNM Design, T-Network & Slit Foil electrolytics, Elna, Elma, I.T. Electronics Air Core and Corobar@ 99.99%OFC Inductors, Linear Technology, MIT Multicaps, Nichicon, MUSE premium grade electrolytics, 99.99% Pure Silver Wire, Sanyo OS-CON, Sfernice, Suflex, Vishay... plus many more products at very competitive prices. Our 1998 Audiophile Parts Catalogue available on request.

I.T. Electronics (Germany)
AudioCom (UK),
Unit 6, Tindle Enterprise Centre
Warren Street, Tenby
Pembrokeshire, SA70 7JY
Tel: 01834 842803
Fax: 01834 842804

E-Mail: audoloc@connect-wales.co.uk
I.T. Electronics are manufacturers of audiograde components and accessories. Product range includes polypropylene capacitors, high power resistors, air core, RCA split-pin lockable phono's, interconnects, drive units, over 40 loudspeaker kits. A selection of components are now held in stock, and available by mail order from AudioCom (see our ad for brochure). Alternatively send for I.T. Electronics 245 page handbook, priced £2.50. (German language only)

Hart Electronic Kits Ltd
Penylan Mill, Oswestry,
Shropshire SY10 9AF
24 Hr sales/enquiries Tel: 01691 652894

A range of Audiophile kits for 80 watt Power Amplifiers, Tuners, Pre-Amps and Moving Coil/Moving Magnet RIAA Pickup Preamps. All kits are fully engineered, with our thirty years design experience, for easy constructions from circuits by John Lindsey Hood, the most respected designer in the field. Send for lists.

AP Electronics
20 Derwent Centre, Clarke Street,
Derby, DE1 2BUT

Check out the AP ELECTRONICS catalogue. It's free with every order of over £40.00 or can be purchased for a £4.95 cheque payable to 'AUDIOKITS'. Over 80 pages include pre and power amplifier kits, high grade audiophile resistors, capacitors and semiconductors, audio and mains cables, gold and rhodium plated connectors and COMPONENT NOTES on using high grade parts. A quarterly newsletter 'AP PERFORMANCE AUDIO' has been recently launched and your first issue is free.

Cambridge Scientific Supplies
12 Willow Walk,
Cambridge CB1 1LA.
Tel: 01223 811 716
Fax: 01223 501 833

Specialist wire products for the knowledgeable audiophile including: Silver wire (>99.99% purity, stress free) unique quadruple PTFE insulated Silver wire, Silver loaded solder, PTFE sleeving and Nylon braid sleeving, premium Gold plated connectors and plugs. Custom assembly available. Call Peter Bullock for a catalogue and application note.

Russ Andrews Accessories Ltd
Edge Bank House, Skelsmergh,
Kendal, Cumbria, LA8 9AS
Tel: 01539 823247
Fax: 01539 823317
Orderline: 0800 373467 (UK)

World leading supplier of the highest quality premium grade components. Loudspeaker Upgrade Handbook available. Sole UK distributor of Kimber Kable. NEW Audio Lifestyle Brochure available containing new ranges of accessories. To receive your copy just mail, phone or fax the address above.

Rothwell Electronics
60 Pennington Road
Great Lever
Bolton
BL3 3BR
Tel/Fax 01204 654614

Rothwell Electronics manufactures and supplies stepped attenuators for the DIY audio market, as well as finished valve amplifiers. The attenuators have 132 settings, channel balance better than 0.1dB, and cost just £79 inc. VAT and postage. Call for free brochure.

V.R.R.
30 Melbourne Avenue,
Worthing, BN12 4RT.
Tel: 01903 501158

Vintage Radio Restoration
Bespoke output transformers for most valves, push-pull and single ended. Components and circuits provided to construct high quality valve amplifiers. Mains transformers "C" core ideal for pre-amps. Call for spec.

Kopperae
PO Box 6884, Dundee, DD5 1YB
Tel: 07970 - 654356
Email: wkopp@taynet.co.uk

Kopperae manufacture unique anti-resonance and anti-interference hi-fi accessories that dramatically cut transistor harshness and background noise. These products include the highly effective anti-RF, anti-resonance CD Roof: an attractive medite-copper-damping pad slab that sits on TOP of your CD player. For the DIY enthusiast, we have the Cu Pad, a copper backed self-adhesive damping pad that can be used in a variety of applications, including cutting panel vibrations and lining chassis. We also supply plain 0.6mm sheet copper. Build chip, transformer and DAC shields, or clad casings, and get the significant benefits that RF shielding brings. ALL products are available custom sized. Contact us now for a free brochure

RESTORATION

Audio Laboratories (Leeds)
3, Kildare Terrace, Whitehall Road,
Leeds, LS12 1DB
Tel: 0113 244 0378

Have your pet hi-fi project professionally done. With over 20 years experience in factory-grade kitbuilds and overhauls, to both valve and solidstate equipment, our good reputation stems from meticulous engineering coupled with superb measurement facilities.

VINTAGE DIY

Loricraft Audio
4 Big Lane, Goose Green,
Lambourne, Berks RG16 7SQ.
Tel: 01488 72267

Specialist restoration of 301's and 401's using genuine spares and re-manufactured parts to original pristine standards in our newly built workshops designed primarily for these purposes.

Classique Sounds
Classique House
61 Aylestone Drive
Aylestone, Leicester, LE2 8QE
Tel/Fax: 0116 2835821
Mobile: 0802 213740

Suppliers of quality vintage/valve hifi equipment including Leak, Quad, Radford, Rogers, Lowther, Tannoy, Garrard, Thorens etc. Rebuild service available with 12 months guarantee. Also suppliers of heavy plinths for Garrard 301/401/124, from £175.00. As well as power supplies. Repairs to Quad Electrostatic ESL57 Treble/Base panels. EHT units and dust covers also available. Translucent 99.99% pure silver interconnect cable. Terminated from £59.99 .5m. Guaranteed better than existing cable, regardless of price. Quality modern Hifi also available. Wanted all your vintage hifi equipment.

WELDING

N.Clark Welding & Fabrications
14 Redhills Road
Easton Industrial Estate
Southwoodham Ferrers
Essex CM3 5UP
Tel: 01245 323336

Precision welding and sheet metal work TIG/MIG welding, CNE Punch and Press Milling and Turning Fine Limit and General Engineering Prototype work and batch work undertaken.

a home-built passive pre-amp featuring a Rothwell stepped attenuator (a bargain), the DR66, two upgraded Arcam A60 amps and a pair of kit speakers from IPL; total cost, a little over £1000! I had no previous electronics training and owe many thanks particularly to Rothwell, IPL and AudioLinks for their generous help.

I am now going to build the active crossover unit into the same case as my pre-amp, thus dispensing with the need for interconnects. This will leave a pair of two-metre interconnects per channel (bass/midrange and tweeter). Can you recommend cables which would be particularly suitable for each job? As my equipment is situated adjacent to the TV and video, the cables will need to be screened. I had thought of routing the cables through copper pipe to provide the screening. Does this work, and are there any caveats?

Nick Whetstone
Somerset.

Upgrade Ingredients

If you can use a soldering iron and desolder pump, you should be able to carry out the following work. You will need the following components: Small-value capacitors - polystyrene, polycarbonate or polypropylene - in these values:

2 x 3900pF
3 x 10nF
5 x 8200pF
2 x 39nF
6 x 82nF

Os-Con SG capacitors:
8 x 10uF, 16V
4 x 470uF, 16V (100uF or 150uF would also be fine)

You could bypass the larger caps too, say with 4.7uF Os-cons and 0.1uF box polypropylenes.

Schottky Diodes:
4 x 11DQ10

Burr Brown Op Amps: 2 x OPA4134 PA

You can also fit heatsinks to the op amps (Maplin KU44X) using heatsink compound (Maplin HQ39N).

The above components are available from AudioLinks (tel: 01724 870432), AudioCom (tel: 01834 842803) and Maplin (tel: 01702 554000). The total parts cost is about £50.

THE RECIPE

Remove the four small, black screws around the base of the unit and take off the base-plate. Remove all the small, black screws on the front of the unit as well. Then take off the four control knobs by carefully prising them upwards. Now remove the five black screws from the top of the unit. NB: the screw in the central position is a self-tapper and must be put back in the same location.

Partially remove the main PCB and disconnect the lead from the LED. Now



pull out the main PCB and its smaller companion which carries all the input/output connectors.

The order for changing the components is not too important, but I suggest starting with the smaller capacitors before moving on to the op amps. This process will be considerably easier if you remove the metal plate which is tight against one of the op amps. Undo the nuts on the shafts of the level controls, then unscrew the two bolts holding it onto the PCB (these are on the underside of the PCB). This will enable you to use the special insertion tool (Maplin FR25C), which makes the job far easier.

One word of warning: make sure you

earth yourself while handling and working on the op amps as static electricity can easily damage them. Also remember to insert the new op amps with their indents facing in the same direction as those on the original ICs.

CAPS OFF

Next, replace the six 10uF capacitors with the Os-Cons. Finally, remove the existing 470uF caps; the Os-Cons are placed on the underside. To fit the Os-Con you will need to carefully cut out a 10mm square piece of the smaller PCB, which will allow it to be laid flat. Carefully bend the legs of the Os-Cons to fit through the appropriate holes in the PCB and solder them in place, making sure that they are not in contact with any part of the PCB.

The weight of the Os-Cons will tend to pull the PCB tracks away from the board, so put a blob of solder on the legs where they protrude through the topside to help take the strain. Now trim the legs to equal height leaving

enough to attach the bypass caps if you are fitting them.


Finally, slip some insulating sleeve over the Os-Cons on the underside of the PCB. If you have fitted the 470uF caps, you will find that replacing the base of the case presses them against the PCB.

Before re-assembling the unit, check all the soldered connections

with a multi-meter. Then carefully position the PCB carrying the socketry and secure it in place. Connect the lead from the LED to the PCB. Offer up the main PCB assembly to the top of the case and replace its screws too. All that remains is to push the control knobs back on and replace the base-plate.

MODS FOR ROCKERS. . .

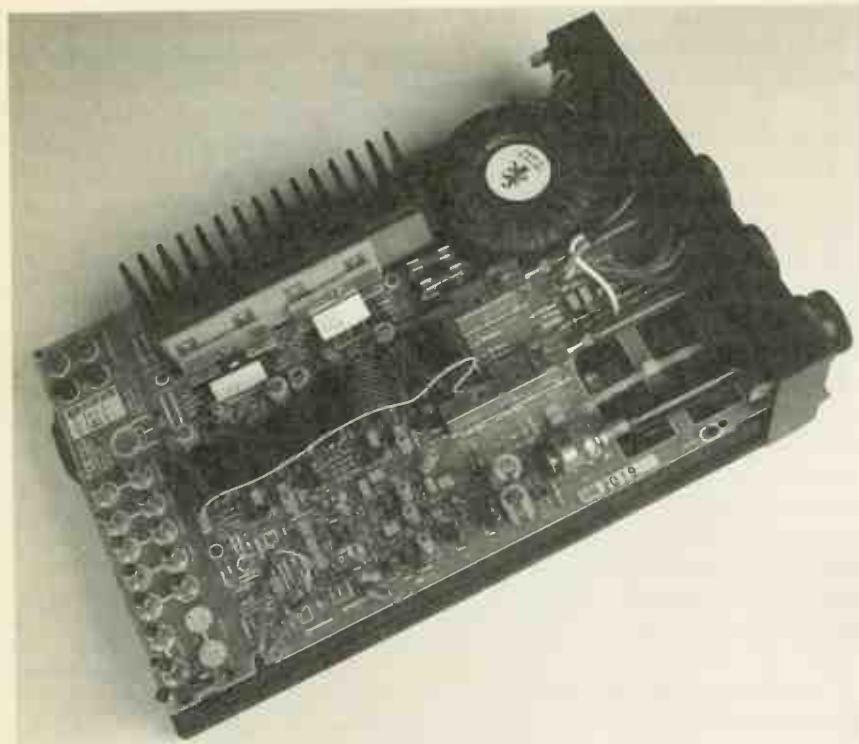I have an original Mission Cyrus I integrated amplifier from 1986. I've owned it since new and it has steadfastly refused to be replaced. It has never gone wrong and, even though I get the upgrade bug about once every two years, I have never found a replacement (much to the consternation of a variety of hi-fi dealers in



Like NAD's 3020, Mission's Cyrus 1 integrated is a classic well worth modifying.

the Thames Valley). Until now that is. The Cyrus is finally being pushed aside in favour of a Yamaha DSP-A1.

As I'll never get rid of the amp, what I'd like to do is modify it without destroying its character. Have you ever published any articles on tweaking this amplifier? If not, do you have any general recommendations?

David Ricketts
ricda06@mail.cai.com

We've yet to publish any Cyrus-specific upgrades, but as a Cyrus I owner myself, I've tried out a few at home. One which works well is to replace the standard 20mm fuses within the amp with 'polyswitch' types of the same rating. These polyswitches look similar to small disc ceramic capacitors and are available from Maplin and RS amongst others. Their advantage is a lower series resistance, which can be heard as faster, harder, deeper bass and a generally cleaner, more sharply-focused sound.

Schottky diodes in the power supply have a similar effect. RS sell some tasty versions which can handle up to 10A at 100V - a little OTT for this application perhaps, but worth tracking down nonetheless.

A change of volume potentiometer brings some of the biggest gains in clarity, speed, detail and involvement. An Alps Blue is one candidate, although if you feel

like pushing the boat out, there's Panasonic's For Audio at £64 from AudioLinks (tel: 01724 870432)

The ribbon cable which connects the sources to the source selector is another prime candidate for replacement. Silver-plated OFC in a PTFE jacket is one option, although it might push the Cyrus' sound to the wrong side of bright. Plain OFC in a PVC jacket might be the answer, if this turns out to be the case.

Although the Cyrus I has a blanking plate on its socket panel to cover it, there is space for connecting a PSX-style power supply. I haven't carried out this mod myself, but I suspect a 500VA external

transformer, Schottky rectifiers and DNM's 10000uF T-Network reservoir capacitors feeding the amp would make a very, very big improvement without drastically altering its character. And don't discount battery power, either (see last month's Supplement for details of how to wire up a split-rail battery PSU). Audiophile resistors (like Holcos) directly in the signal path will help too. JM


... AND EVEN MORE MODS

I was delighted to read your article on the NAD 3020 amplifier in the August edition. I recently dusted off my 3020B with a view to modifying it. I can highly recommend tweaking this amplifier as the removable base-plate and top cover allow easy access to both sides of the PCB for component removal.

I initially replaced the ageing original volume potentiometer with an Alps Blue Velvet, and the electrolytic capacitors in the direct signal path with Sanyo Os-Cons of the same value. This produced a significant improvement in midrange clarity and detail. NAD were very helpful in providing the 3020B/3120 Service Book complete with PCB and circuit layout.

I have since disconnected the power indicator and loudness button, replaced other electrolytics, bypassed the power supply capacitors and replaced the main resistors with Holco H8s (and the internal wiring with silver-plated copper wire). I am still getting improvements in clarity and transparency from this excellent amp, and have been amazed by the effect of simple component changes.

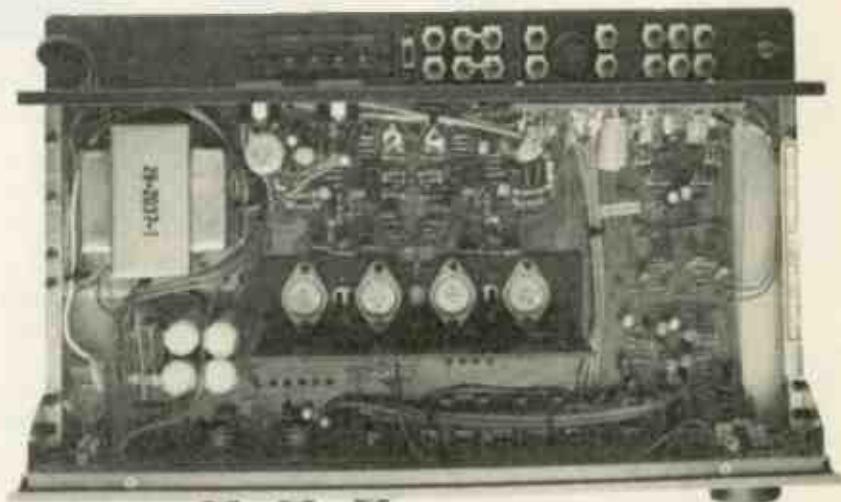Roger McPherson
mcperson@enterprise.net
Continuing the wire theme, there are large



NAD's 3020 amp in its many incarnations handsomely repays tweaking efforts.

gains to be had from point-to-point wiring over PCB tracks which have been cut at both ends (the impact of this on the sound is obviously greater on longer tracks).

Unfortunately, Os-Cons were designed for use as PSU decoupling rather than signal caps, and in my experience don't reveal their full potential when used as such. You'd be better off replacing these Os-Cons with low-voltage Black Gates, which aren't excessively costly. JM

HEGEMAN UP-DATE

Many thanks to Mr Crofts of Nottingham for sending in a sketch plan of the Hegeman horn which featured in June's *Vintage Virtues*.

The floating gherkins in the diagram appear to be anti-resonance dowels; unfortunately there are not too many clues as to the best way of mounting the drivers, but we are sure some intrepid reader will be able to work it out!

Before we are inundated with requests for copies, dimensions and so on, neither we nor Mr Crofts have any further information; we have put a bit of work into cleaning up the pictures below and Haden Boardman has given us the overall size. After that, I'm afraid you're on your own! RMW

FOLLOWING

REGULATIONS

Having cast away some modestly expensive hi-fi equipment due to an upgrade route which resulted in disappointment, my system is now going through a long-term evolution at a pace which is bank-manager friendly.

I first built a World Audio KLPP1, which is more open and neutral sounding and provides more facilities than many pre-amps I tried. This I have plugged into a refurbished Leak Stereo 20 which, just by looking at the tidier design underneath, was a far better quality of product than the Rogers Cadet it replaced.

This leads me on to the next stage of the evolution and raises some questions I hope you can help me with.

There is potential to upgrade the power supply of the Leak Stereo 20 which, from the circuit diagrams I have acquired, looks as though it is rectified through the Mullard GZ34 valve but is otherwise unregulated. I know companies such as Definitive Audio make claims for their power supply which is apparently suited to the Leak Stereo 20, but at £595 I cannot justify in my mind spending that sort of money on an amp which cost me £260. Can you advise me of a method for regulating the power supply, especially if I can build it from a

circuit design to save cost.

Ultimately, I want to play the KLPP1 through a 300B amp which I would like to build from a kit. Whilst I have seen the World Audio 300B, there are two things that have so far caused me to resist.

First, I understand the design to be push-pull rather than single-ended, and I am unsure of the sonic advantages of single-ended over push-pull.

Second, I would prefer to build monobloc single-ended 300Bs if they would be available in kit form. Your October issue highlights the apparently greater choice of valve kits in Japan, but I would like to know if a monobloc kit is available in this country.

Finally, one of my latest acquisitions is an Akai 4000DS open-reel tape deck in almost mint condition. This seems to add a greater sound stage to music, especially lifting vocals above the height of the 'speakers. The pre-pre-amp section from the tape heads, however, is putting out a level of hiss which I feel could be improved on (the KLPP1 when played through anything other than the Leak is absolutely silent) and I would like to know if you are aware of any designs that I could replace this section with. Maplin show an EQ2S circuit but this appears to be for battery-operated units and I am unsure if there would be any improvement.

Adrian Buckmaster
Middlesex.


As you have observed from the circuit diagram, the Stereo 20 has a valve-rectified but unregulated supply. The power supplies of these old amps play a major role in their sound, especially in the bass. Quality can vary from an uncontrolled rumbling to making kickdrums go 'bong' instead of 'thud'. All this bonging is due to a complex interaction between the various inductances and capacitances in the power supply and output transformer, as well as the phase shifts, etc in the feedback loop (if there is one).

Even though the amp may measure relatively flat, there are time-effects at low frequencies. Most transistor amps with their big PSU caps and DC coupled circuitry have that super-damped, dry bass which is quite hard to achieve with a valve amp.

The Definitive Audio power supply is unregulated but uses a choke-input rather than capacitor-input circuit, and the choke and cap are quite large values. This tightens up the bass quality. The

Hegeman Domestic Horn

cut-away view from back

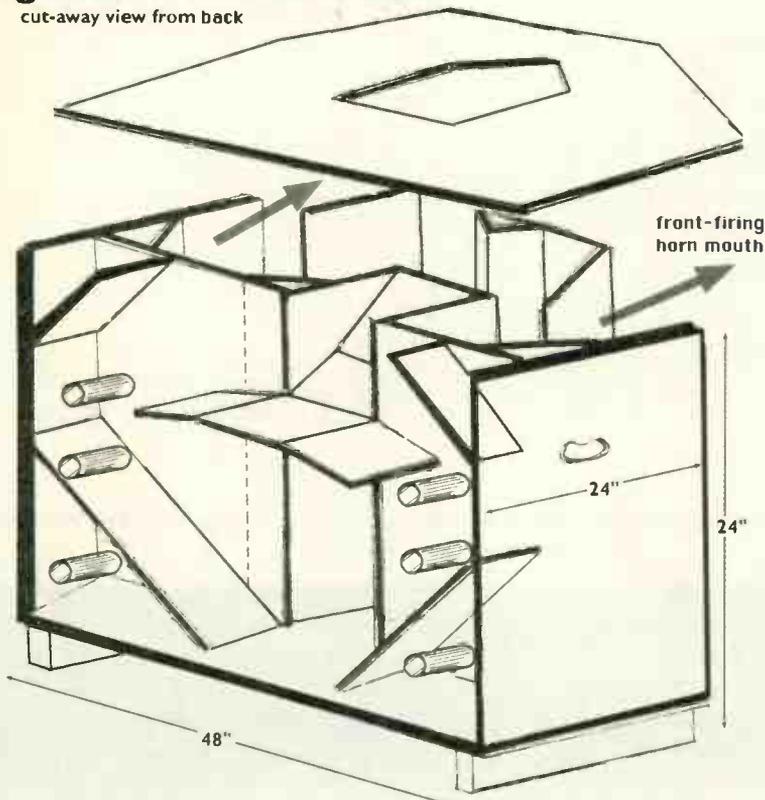

The diagram above shows the immense complexity of the Hegeman's internal cabinet construction.

component quality is good too, so overall there is an improvement in all areas. Modern electrolytic capacitors are way ahead of their vintage counterparts, especially audio-quality types such as Black Gate and Cerafine caps from Japan.

Both the choke input filter and an active regulator require considerably higher voltages from the mains transformer to get the same output as the amp's existing HT voltage, so you couldn't practically use the transformer which is in the amp at present; you would have to get a new mains transformer, new PSU caps and a new choke and build a unit like the Definitive Audio supply. This could turn out just as expensive when the metalwork and so on have been factored in.

I would suggest that there are two easier (and cheaper) options. You could replace the PSU capacitors in your amp with modern, audio-grade parts. Then you

could search around the surplus electronic shops for an old variable-voltage, laboratory power supply such as those made by Solartron. Disconnect the amp's internal supply and connect up the external one. These supplies are very stiffly regulated and really beef up the bass quality. And of course, if you change amps, you just disconnect the supply and use it on your new one after adjusting the voltage.


The original philosophy behind single-ended amplifiers in Japan was very minimalist in that only one output valve per channel is needed for it to work. But there are other advantages to SE working, even when parallel output valves are used.

Sonically, if only one valve per channel is used, there is a beauty and subtlety to the sound which I have never heard anywhere else; imagine the difference between a painting done with a brush with one bristle and one done with an emulsion

roller. To fully appreciate this though, the components used in the amplifier (especially the output transformer) and the circuit topology must be of a very special quality. And if the rest of the equipment in the system paints with a roller, then there's no point bothering.

There are a great many kits available from Japan, from guys like the Audio Professor. Get hold of a copy of MJ Magazine from Japan (which can be ordered from Books Nippon near St Paul's cathedral). Don't rush down the bank to convert your pounds into yen yet though - keep your eyes on our Supplement for a forthcoming SE triode kit.

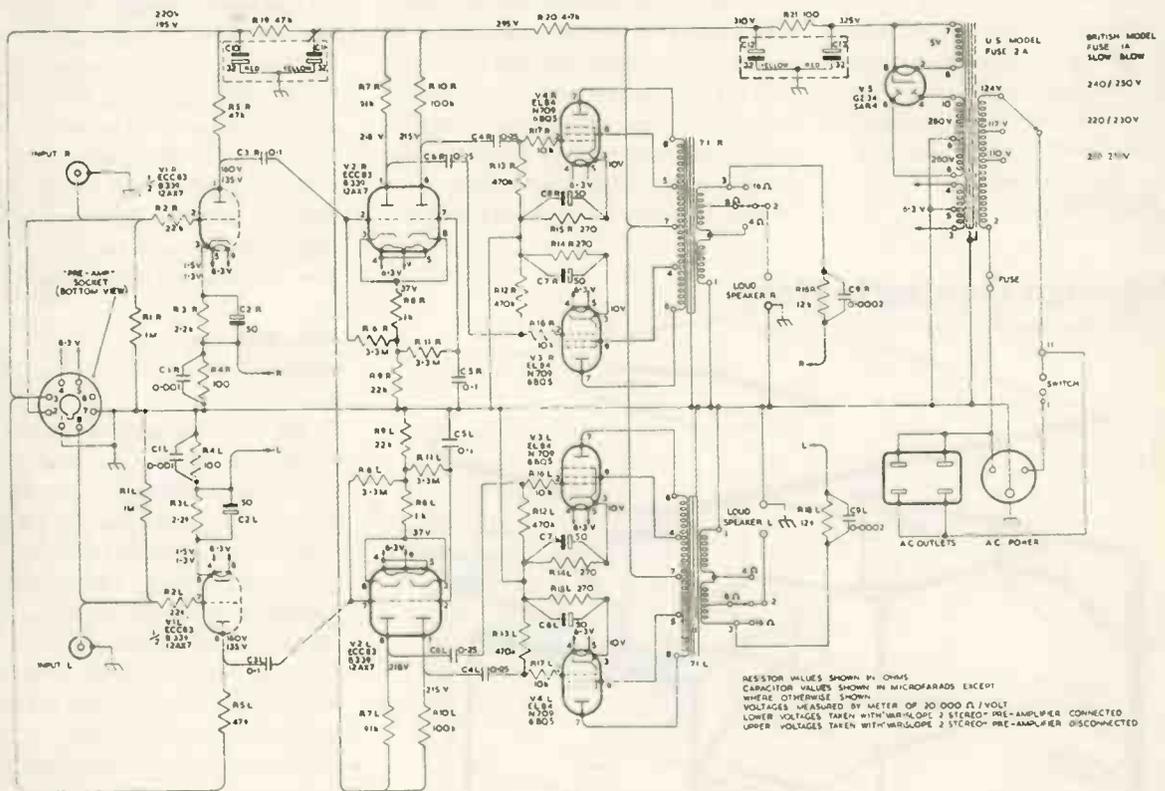As far as your tape deck goes, make sure you are using a good, studio-quality tape from someone like Ampex, and also get it set up by an engineer before doing any modifications. Misalignment will greatly increase noise. GD



As you can see from the Stereo 20's circuit diagram above, the power supply is unregulated. With an old valve-based bench power supply, regulation should be easy to achieve though.

Supplement Advertiser's Index

| | | | | | |
|---------------------|----|----------------------|-------|---------------------|-----|
| Audiolinks | 6 | Glass Audio | 24 | Sowter Transformers | 10 |
| Audiolab Leeds | 4 | Hart Electronics | 12,13 | Technical & General | 4 |
| Billington Export | 18 | IPL Acoustics | 20 | Watford Valves | 4 |
| BK Electronics | 24 | Langrex Supplies | 6 | Wire & Insulation | 22 |
| Centre Electronics | 20 | Marton Music | 10 | | |
| Cricklewood | 18 | Riverside Audio | 24 | Russ Andrews | IFC |
| Colomor Electronics | 22 | Rothwell | 20 | PM Components | IBC |
| Falcon Acoustics | 10 | SJS Electroacoustics | 10 | Chelmer Valves | OBC |



Golden Dragon

Precision Audio Tubes

Please enquire for any tube not listed. We have an inventory of over 2,500 different types in stock.

Golden Dragon High Quality Pre-amplifier Tubes

| | |
|--------------------|--------|
| 12AT7A/E81CC/ECC81 | £ 6.95 |
| 12AU7A/E82CC/ECC82 | £ 6.95 |
| 12AX7A/E83CC/ECC83 | £ 6.95 |
| 12BH7A | £ 9.95 |
| 6DJ8/E88CC/ECC88 | £10.95 |
| 6SN7GT/ECC33 | £ 8.95 |

| | |
|--------|-----------|
| KT66R | £69.95 pr |
| KT88R | £69.95 pr |
| 6550WA | £67.95 pr |

Golden Dragon Special Quality Pre-amplifier Tubes

| | | |
|----------|------------------------------------|------------|
| E81CC-01 | Gold Pins Low Microphony Low Noise | £10.50 |
| E82CC-01 | Gold Pins Low Microphony Low Noise | £10.50 |
| E83CC-01 | Gold Pins Low Microphony Low Noise | NEW £ 9.50 |
| E88CC-01 | Gold Pins Low Microphony Low Noise | £14.50 |

Golden Dragon Triodes

| | Singles | Per matched pair | Per matched quad |
|-----------|---------|------------------|------------------|
| 2A3 4 pin | £22.50 | £50.00 | £100.00 |
| 2A3 Octal | £22.50 | £50.00 | £100.00 |
| 211 | £28.50 | £60.00 | £120.00 |
| 811A | £11.50 | £25.00 | £50.00 |
| 845 | £36.50 | £75.00 | £150.00 |
| 805 | £36.50 | £75.00 | £150.00 |

Golden Dragon T300B Range

| | | | |
|-----------------|---------|---------|---------|
| 300B Super | £79.00 | £160.00 | £320.00 |
| 4.300B | £84.00 | £170.00 | £340.00 |
| 4.300B LX Super | £124.00 | £250.00 | £500.00 |

Golden Dragon Power Tubes

| | Matched Pair | Matched Quad | Matched Octet |
|-----------------------------|--------------|--------------|---------------|
| EL34 Super | £25.00 | £50.00 | £100.00 |
| EL34M | £25.00 | £50.00 | £100.00 |
| E84L (special quality EL84) | £12.50 | £25.00 | £50.00 |
| EL156 Octal | £75.00 | £150.00 | £300.00 |
| 6L6WGB | £25.00 | £50.00 | £100.00 |
| KT66 | £25.95 | £52.00 | £104.00 |
| KT66 Super | £65.00 | £130.00 | £300.00 |
| KT88 | £57.95 | £116.00 | £232.00 |
| KT88 Special (Gold plated) | £67.95 | £136.00 | £272.00 |
| KT90 | £65.00 | £130.00 | £260.00 |
| KT90LX | £75.00 | £150.00 | £300.00 |
| 350B | £29.95 | £60.00 | £120.00 |
| 6L6GC | £19.95 | £40.00 | £80.00 |
| 6550A | £42.95 | £86.00 | £172.00 |
| 6550A Special (Gold plated) | £64.95 | £130.00 | £260.00 |
| 50CA10 | £84.95 | £170.00 | £340.00 |
| 807 | £25.00 | £50.00 | £100.00 |

We have a vast range of tubes available from manufactures all over the world including rare and vintage types. an 80 page booklet of valves available is updated monthly and can be provided at a cost of £2.50 per copy U.K. £4.00/\$7.00 rest of world or you may telephone our Sales Desk for a prompt quotation.

Prices exclude VAT and Carriage. Please add carriage charge of £2.50 for UK orders and VAT at 17.5%

P.M. COMPONENTS LTD., Springhead Enterprise park, Springhead Road, Gravesend, Kent DA11 8HD
Sales Desk 01474 560521 Fax 01474 333762

The Valve. Golden Dragon



Simply, The Best.

For more information contact:

PM Components, Unit B3, Springhead Enterprise Park
Gravesend, Kent. DA11 8HD

01474 560521, fax 333762, e-mail: 101650,2424@Compuserve.com

PRICE VALIDITY TO END NOV 1998 - ASK ABOUT ANY TYPES NOT ON THIS LIST



CHELMER VALVE COMPANY

for High Quality Audio Tubes

Everybody in the tube business knows that the justly famous Brand names of yesteryear like BRIMAR, GEC, MULLARD, RCA & TELEFUNKEN Etc. Etc. are scarce and often very expensive.

Although we supply all major brands when available (and have many in stock) our policy is to offer a range of tubes, mostly of current manufacture, the best we can find from factories around the world, which we process specially to suit audio applications. The result - CVC PREMIUM BRAND.

Our special processing includes selection for LOW NOISE, HUM & MICROPHONY and controlled BURN-IN on all power tubes to improve STABILITY and select out tubes with weaknesses Etc.

A selection of CVC PREMIUM Audio Tubes

| PRE-AMP TUBES | POWER TUBES | POWER TUBES | SOCKETS ETC. |
|----------------|-------------|--|--------------|
| ECC81 | 5.00 | EL34G | 7.50 |
| ECC82 | 5.00 | EL34 (TESLA) | 8.00 |
| ECC83 | 5.00 | EL34 (Large Dia.) | 8.50 |
| ECC85 | 6.00 | EL84/6BQ5 | 4.70 |
| ECC88 | 5.00 | EL509/519 | 13.00 |
| ECF82 | 5.00 | E84L/7189A | 6.50 |
| ECL82 | 5.00 | KT66 | 9.50 |
| ECL86 | 5.00 | KT77 | 12.00 |
| EF86 | 5.50 | KT88 (Standard) | 12.50 |
| E80F Gold Pin | 10.00 | KT88 (Gold Special) | 21.00 |
| E81CC Gold Pin | 6.80 | KT88 (GL Type) | 30.00 |
| E82CC Gold Pin | 8.00 | PL509/519 | 9.00 |
| E83CC Gold Pin | 7.50 | 2A3 (4 or 8 Pin) | 14.50 |
| E88CC Gold Pin | 8.00 | 211 | 22.00 |
| 6EU7 | 6.00 | 300B | 50.00 |
| 6SL7GT | 4.50 | 6C33C-B | 27.00 |
| 5SN7GT | 4.50 | 6L6GC | 6.50 |
| 6922 | 5.20 | 6L6WGC/5881 | 8.00 |
| 7025 | 6.50 | 6V6GT | 5.00 |
| | | 6080 | 11.50 |
| | | 6146B | 10.50 |
| | | (continued) | |
| | | 6336A | 46.00 |
| | | 6550A | 11.00 |
| | | 6550WA or WB | 13.50 |
| | | 7581A | 11.00 |
| | | 807 | 9.00 |
| | | 811A | 11.00 |
| | | 812A | 34.00 |
| | | 845 | 30.00 |
| | | RECTIFIER TUBES | |
| | | EZ80 | 4.00 |
| | | EZ81 | 4.50 |
| | | GZ32 | 11.00 |
| | | GZ33 | 9.50 |
| | | GZ34 | 6.50 |
| | | GZ37 | 7.50 |
| | | 5U4G | 5.00 |
| | | 5V4GT | 4.50 |
| | | 5Y3GT | 4.00 |
| | | 5Z4GT | 4.50 |
| | | B9A (Chassis or PCB) | 1.60 |
| | | B9A (Ch or PCB) G/Plated | 3.00 |
| | | Octal (Ch. or PCB) | 1.80 |
| | | Octal (Ch. or PCB) G/Plated | 4.20 |
| | | 4 Pin (For 2A3, 300B etc.) | 3.30 |
| | | 4 Pin (For 2A3, 300B etc) G/Plated | 5.00 |
| | | 4 Pin Jumbo (For 211 etc.) | 11.00 |
| | | 4 Pin Jumbo (For 211 etc.) Gold Plated | 15.00 |
| | | 5 Pin (For 807) | 3.00 |
| | | 7 Pin (For 6C33C-B) | 4.50 |
| | | 9 Pin (For EL, PL509, Ch. or PCB) | 5.00 |
| | | Screening Can (For ECC83 etc.) | 2.00 |
| | | Anode Connector (For 807 etc.) | 1.50 |
| | | Anode Connector (For EL509 etc.) | 1.70 |
| | | Retainer (For 6L6WGC etc.) | 2.00 |

and a few "Other Brands" (inc. Scarce types).

| | | | | | | | |
|----------------------|-------|--------------------|-------|-------------------|-------|----------------|--------|
| 5R4GY FIVRE | 7.00 | 6B4G / SYLVANIA | 7.00 | 6SN7GT BRIMAR | 10.00 | 13E1 STC | 110.00 |
| 5R4WGY CHATHAM USA | 10.00 | 6BW6 BRIMAR | 5.00 | 12AT7WA MULLARD | 5.00 | 805 CETRON | 50.00 |
| 5U4GB RCA or GE | 12.00 | 6BX7 GT SYLVANIA | 8.50 | 12AY7 GE-SYLVANIA | 7.75 | 5842A GEC | 15.00 |
| 5Y3WGT SYLVANIA | 5.00 | 6CG7/6FQ7 SYLVANIA | 7.50 | 12AZ7 GE | 7.50 | 6080W TUNGSTOL | 12.50 |
| 6AS7G RCA or SEIMENS | 12.00 | 6CL6 RCA or GE | 5.00 | 12BH7A GE or RCA | 13.00 | 6550A GE | 22.00 |
| 6AU6WC SYLVANIA | 3.50 | 6CW4 RCA | 11.00 | 12BY7A GE | 9.00 | 6146B GE | 17.00 |
| | | 6SL7GT STC | 8.50 | 12E1 STC | 12.50 | | |

ALL PRICES IN U.K. POUNDS £

Please note carriage charge extra + VAT (EEC Only) - When ordering state if matching required (add £1.00 per tube).

Payment by CREDIT CARD (ACCESS, VISA, MASTERCARD) or BANKERS DRAFT, TRANSFER or CHEQUE (UK ONLY).

FAX or POST your ORDER - We shall send PROFORMA INVOICE if necessary.

Valve Amplifiers sound better still fitted with CVC PREMIUM Valves!

Chelmer Valve Company, 130 New London Road,
Chelmsford, Essex CM2 0RG. England.

☎ 44 (0)1245 355296 Fax: 44 (0)1245 490064