

# Hobby

December 78  
40p

# Electronics



## LIGHT BEAM TELEPHONE PROJECT

**Audio Mixer Project**  
*Choose your own arrangement*

**Electronic Metronome**  
*Beat out the time*

**Dice Project**  
*Roll your own*

**Calculator Specs**  
*What they mean*

**DIY Printed Circuits**  
*Simple — using Hobbyprints*

**Radio Servicing**  
*Ten quick tips*

**TV Programagame Reviewed**  
*10 games in one kit*

**Soldering Iron Offer**  
*£2.35 all inclusive*

# OSTS <sup>®</sup> now from ambit international

"One Stop Technology Shopping"

Ambit stoppress...news on items available... KV1210: triple AM tuning diode with 2.9v bias only £2.75... DT1200 Digital frequency readout module ..... 911223 ultra low THD/IMD mpX decoder module £9.95.....944378 'Hyperfi' mpX decoder with post decoder muting and pilot cancel £19.95..... VMOS

## COUNTER ATTRACTIONS:

New this month from Intersil, the ICM 7216. This is probably the most significant new IC for frequency counter/timer applications ever devised. It drives a full 8 digit display (LED) and operates on inputs up to 10MHz minimum. The single 28 pin DIL also has:-  
 \*Leading zero blanking \*Frequency ratio \*Period \*Unit counter \*Time Interval \*Overflow  
 The IC cost is £19.82, and the 10MHz HC18U Xtal £2.50 (for timebase functions). The circuit data is free with the IC, or £1 purchased separately. Input preamp board £7.00.  
 New from Ambit is the MC3357. 6v, 2mA standby NBFM IF, detector and squelch with 10.7 - 455 kHz balanced mixer, on-board oscillator device, and 5uV sensitivity. It is ideally suited to our CFM and LFY filter series, and costs £3.12 with full data. Xtal £2.50.

Please note that OSTS prices exclude VAT at 8% throughout this side of the page. Most ambit items are at 12% except those marked \*. Please keep orders separately totalled, although a single combined payment, and 25p postage charge, will be sufficient.

## CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4016	52p	4075	20p	4541	141p
4017	80p	4076	90p	4543	174p
4018	80p	4077	20p	4549	399p
4019	60p	4078	20p	4553	440p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	82p	4557	386p
4023	17p	4086	82p	4558	117p
4024	76p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	90p	4561	65p
4027	58p	4096	105p	4562	610p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	122p	4569	303p
4031	250p	4160	90p	4572	25p
4032	100p	4161	90p	4580	600p
4033	145p	4162	90p	4581	319p
4034	200p	4163	90p	4582	84p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4194	95p	4585	100p
4038	105p	4501	23p		
4039	250p	4502	91p		
4040	83p	4503	69p		
4041	90p	4506	51p		
4042	85p	4507	51p		
4043	85p	4508	248p		
4044	80p	4510	99p		
4045	150p	4511	149p		
4046	130p	4512	98p		
4047	99p	4513	206p		
4048	99p	4514	206p		
4049	58p	4515	300p		
4050	55p	4516	125p		
4051	65p	4517	382p		
4052	65p	4518	103p		
4053	65p	4519	57p		
4054	120p	4520	109p		
4055	135p	4521	236p		

## Micromarket PRICES SLASHED

6800 series	8216	1.95	2114	£10	
6800P	6.50	8224	3.50	2708	£10.55
6820P	6.6	8228	4.78		
6850P	2.75	8251	6.25		
6810P	£4	8255	5.40		
6852	3.65				
8080 series	2102	£1.70			
8080	6.30	2112	£3.40		
8212	2.30	2513	£7.54		
		4027	£5.78		

## Voltage Regs

**NEW LOW PRICES**

7800 series UC TO220 package 1A	all 95p
7900 series UC TO220 package 1A	all £1
78MUC series TO220 package 1/2A	all 90p
78LCP series TO92 100mA	all 35p
L200 up to 3A/adjustable V/A	195p
78MGT2C 1/2amp adjustable volts	175p
79MGT2C 1/2amp adjustable volts	175p
723C precision controller	65p

**MAINS FILTERS FOR NOISE/RFI etc**

1 amp in IEC connector	£4.83
5 amp in 'wire in' case	£3.87
NE550A	73p

## LINEARS non-consumer

81MOS	LM324N	71p
CA3130E	LM339N	65p
CA3130E	LM348N	185p
CA3140E	LM3900-N	60p
CA3140E	709HC to5	64p
CA3160E	709PC diil	36p
CA3160E	710HC to5	65p
CA3160E	710PC diil	59p
Op amps	723CN	65p
LM301AN	741CH to5	65p
LM308H	741CN 8diil	27p
LM308H	747CN	70p
LM318H	748CN	36p
LM318N	NE531T	120p
	NE531N	105p

## OPTO 7 seg displays

**0.43" High Efficiency HP:**

5082-7650	red CA	
5082-7653	red CC	
5082-7660	yellow CA	233p
5082-7663	yellow CC	
5082-7670	green CA	
5082-7673	green CC	

**0.3" Standard HP**

5082-7730	red CA	
5082-7740	red CC	147p

**0.5" Fairchild**

FND500	red CA	150p
FND507	red CC	150p

## TLL-Standard AND LP Schottky

All prices listed in pence \*

N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	N'	LSN'	
7400	13	20	7455	35	24	74126	57	44	74185	134
7401	13	20	7460	17		74128	74		74188	275
7402	14	20	7463			74132	73		74190	115
7403	14	20	7470	28		74133			74191	
7404	14	24	7472	28		74136			74192	105
7405	18	26	7473	32		74138			74193	105
7406	38		7474	27	38	74139			74194	105
7407	38		7475	38	40	74141	56		74195	95
7408	17	24	7476	37		74142	265		74196	99
7409	17	24	7478			74143	312		74197	85
7410	15	24	7480	48		74144	312		74198	150
7411	20	24	7481	86		74145	65		74199	160
7412	17	24	7482	69		74147	175		74248	
7413	30	52	7483A			74148	109		74251	90
7414	51	130	7484	97		74150	99		74253	105
7415	30	24	7485	104	99	74151	64	84	74257	108
7416	30		7486		40	74153	64	54	74279	105
7417	30		7489	205		74154	96		74283	120
7420	16	24	7490	33	90	74155	54	110	74290	90
7421	29	24	7491	76	110	74156	80	110	74295	120
7422	24	24	7492	38	78	74157	67	66	74298	100
7423	27		7493	32	99	74158		60	74299	110
7425	27		7494	78		74159	210		74260	26
7426	36	27	7495A	65	99	74160	82	130	74365	49
7427	27	29	7496	58	120	74161	92	78	74366	49
7428	35	32	7497	185		74162	92	130	74367	43
7430	17	24	74100	119		74163	92	78	74368	49
7432	25	24	74104	63		74164	104		74375	60
7433	40	32	74105			74165	105		74379	130
7437	40	24	74107	32	38	74166			74399	150
7438	33	24	74109	63	38	74167	20		74445	92
7440	17	24	74110	54		74168			74447	90
7441	74		74111	68		74169		200	74490	140
7442	70	99	74112	88		74170	230	200	74668	110
7443	115		74113		38	74172	625			
7444	114		74114		38	74173	170			
7445	94		74116	198		74174	87	120		
7446	94		74118	83		74175	87	110		
7447	82		74119	119		74176	75			
7448	56	99	74120	115		74177	78			
7449	99	74121	25		74180	85				
7450	17		74122	46		74181	165	350		
7451	17		74123	48		74182	160			
7453	17		74124			74183				
7454	17	24	74126	38	44	74184	135			

## From the World's leading radio innovation source:

Apart from the MC3357, mentioned alongside, Ambit has the first easy-to-use low noise, low cost UHF dual gate MOSFET - the BF960 from Siemens. With a gain of 18dB, and a noise figure of only 2.8dB at 800MHz, you will see what we mean. At 200 MHz, the gain is 23dB, and NF only 1.6dB. Combine these figures with the famous ease of use of a dual gate MOSFET, and you have the easiest and most effective front end device yet. £1.60 each

## Moving Coil Meters

Ambit offers a very wide range of low cost meters, together with the unique 'Meter Made' scale system for professional grade scale customizing:

Series	Scale	Area	illumination	cost*
900	14x31mm	internal	12v	250p
920	30x50mm	from behind	275p	
930	30x63mm	internal	12v	375p
940	twin 35x45mm	from behind		350p
950	55x45mm	from behind		300p

Stock movement 200uA/750Ω. The 930 series is 5% linear, others are 77uA at 50% FSD. These and many others available in quantity for OEMs. SAE for full scale details please. (Not in cat.)

## Radio, Audio, Comms ICs:

Only the very best quality - and only types we have used in our own laboratory tests

TD1062	IC to VHF front end system	1.95
TD1083/ULN2204	am/fm/audiio in one IC	1.95
TD1090/ULN2242	am/fm hifi tuner system	3.35
HA1197	LF/30MHz am receiver system	1.40
CA3123E/uA720	LF/30MHz linear system	1.40
TD1651	LF/30MHz linear system	1.81
SD6000	DMOS RF/Mixer pair	3.75

**IF amplifiers**

CA3309E/KB4402	famous FM IF system	1.94
HA1137W/KC	4420 as 3089 + deviation mute	2.20
CA3189E	update with deviation mute	2.75
TBA120a/SN76660M	FM IF and detector	0.75
TBA120S	hi gain version TBA120	1.20
MC1350P	agc IF amp	1.00
MC1330P	synch AM demodulator	1.35
MC1495E	precision 4 quad multiplier	6.86
MC1496P	popular double balanced mixer	1.25

**Communications circuits**

KB4406	differential amplifier	0.50
KB4412	2 bal mixers/agc/gain/doub conv	2.55
KB4413	am/lm/ssh det. AGC, ANL, mute	2.75
KB4417	3mv/mic processor preamp	2.55
KB4423	FM noise blanker system	2.55

**Audio preamps**

LM381	stereo high gain/low THD	1.81
LM1303	stereo audio optimized AO	0.99
TD1054	high quality with alc option	1.95
KB4417	see above	

**Audio Power amps**

TBA810AS	7W RMS overload protected	1.09
TD2002	8W/2Ω in pentawatt package	1.95
TD2020	15W RMS hifi power dc coupled	2.99
TC9A50	10W higher voltage B10	1.80
ULN2283	1W 2.5 to 12V supply capability	1.00
LM3808B	1W power	1.00
LM3801A	2.5W power	1.00
HA1370	HiFi 15w in easy heatsink pack	2.99

## Stereo Decoder Devices

MC1310/KB4400	original pli decoder	2.20
CA3090AQ	RCA's pli decoder	3.25
uA758	Buffered version of 1310	2.20
LM1307/uA707	non pli type	1.55
HA1196	advanced adj. sep pli low thd	3.95
HA11223	new pilot cancel low thd/imd	4.35

All ambit decoders are supplied with the LED beacon of your choice. Please state colour.

## Discrete semiconductors

Some of the biggest stocks of specialist MOS and Fet transistors for radio in the UK.

BF960	80p	40673	55p	40822	43p
40823	51p	MEM680	75p	BF256S	34p
		LED 7107	£20.65		

Most types for most RF circuitry, inc. new UHF T package types etc. See price list.....

<


# Hobby Electronics

Vol. 1. No. 2.

December, 1978

**Monitor** ..... 6  
What's happening in the world of Electronics

**Electronic Metronome** ..... 10

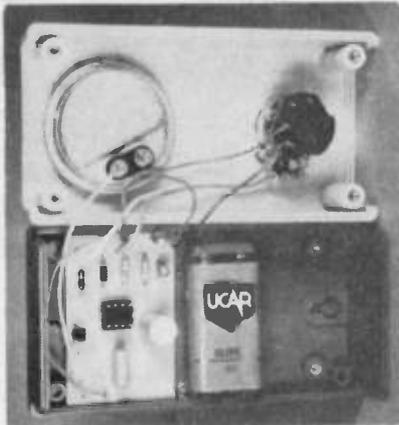


Get rhythm!

**Short Circuits** ..... 12, 17, 25, 50, 52  
Ideas to get you going

**Deep Space Communications** ..... 13  
The ultimate in long distance reception

**Photon Phone** ..... 18

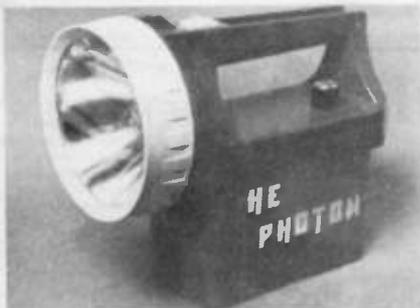

Light beam telephone project

**HE Book Service** ..... 24  
Our recommended reading list

**Special Publications** ..... 25  
Something to read when you've finished this issue

**Into Electronics Part 2** ..... 27  
Introducing passive components

**HE Marketplace** ..... 31, 32  
Two watches, a clock and a soldering iron at true bargain prices

**Understanding Bias** ..... 36  
Getting it all taped


**A look at the next HE** ..... 39  
Sneak preview of the January issue

**Audio Mixer Project** ..... 40



Making 3 + 2 into one

**Lasers** ..... 45

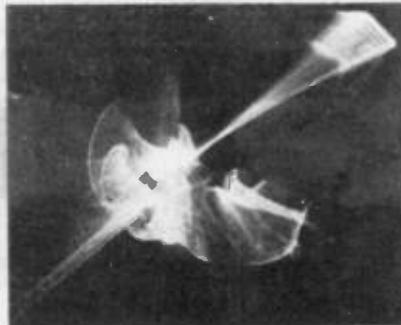

A little light on the subject will make it coherent

**Photocells** ..... 48  
Converting photons to electrons

**Become a HE-Man** ..... 50  
Get one of our Tee-shirts

**Radio Servicing Tips** ..... 51  
Ten logical, easy, get-it-going steps


**Making your own PCBs** ..... 54



A photographic guide

**Hobbyprints** ..... 56  
The easy way to make your own PCBs

**Electronic Dice Project** ..... 57

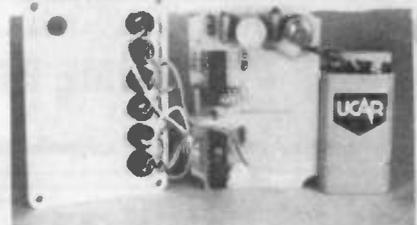

Roll your own!

**Calculators** ..... 60  
Sorting out the buttons

**Teleplay's Programagame Reviewed** 67  
Ten TV games in one kit

**The Tesla Controversy** ..... 70  
Has his work been suppressed?

**Good Evans!** ..... 73  
The world of Gary Evans

**Colour Codes** ..... 75  
How to tell those resistors from each other

**Hobby Electronics**  
25-27 Oxford Street, London W1R 1RF  
01-434 1781  
**Published** by Modmags Ltd,  
**Distributed** by Argus Distribution Ltd,  
**Printed** by Q.B. Ltd, Colchester  
Hobby Electronics is normally published  
on the second Friday of the month prior  
to the cover date

**Editor:** Halvor Moorshead  
**Editorial Staff:** Phil Cohen B.Sc., Ron Harris  
B.Sc., Gary Evans, Steve Ramsahadeo, Paul  
Edwards, Pete Howells  
**Advertising:** Mark Strathern, David Sinfield,  
Joy Cheshire.  
**Admin Staff:** Margaret Hewitt, Bren Goodwin,  
Kim Hamlin, Val Tregidgo, Tim Salmon.

**Copyright.** All material in this publication is  
subject to world-wide copyright protection.  
Permission to reproduce printed circuit board  
patterns commercially or marketing kits of  
the projects must be sought from the Editor.  
All reasonable care is taken in the preparation  
of the magazine to ensure accuracy but  
Modmags cannot be held responsible for it  
legally.

## UNBELIEVABLE WATCH BARGAINS



**VT01**  
5 FUNCTION  
LCD. Hour, Min, Sec.  
Month, Date, 5/S strap.  
Backlight.

ONLY  
£8.95



**VT07**  
12 FUNCTION  
CHRONOGRAPH  
Hour, Min., Sec., DATE,  
Month, 1/100th Sec. Time,  
1 or 2 Event.

ONLY  
£13.95

**VT03**  
SOLAR ALARM  
Hour, Min, Sec. Month,  
Date, Day, alarm any time  
in 24 hour day.

ONLY  
£24.95



**VT04**  
SOLAR  
CHRONOGRAPH

As VT07 but with solar  
panel

ONLY  
£23.95



**VT05**  
CHRONOGRAPHY/  
ALARM  
Dual Time Zone  
Chrono log time  
alarm

ONLY  
£37.95\*



**VT06** ALARM  
Alarm only version of  
VT05

ONLY  
£24.95



**VT06**  
ALARM/STOP WATCH  
CLOCK & Snooze Alarm. Stop  
watch

ONLY  
£15.95


Presentation boxes not included. Please add 65p


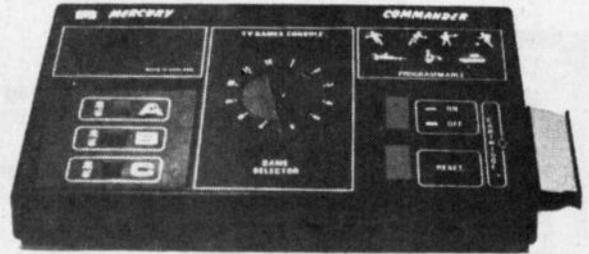
## 'MERCURY COMMANDER' READY BUILT ECONOMY CARTRIDGE SYSTEM (G.I. DEDICATED CHIPS)

Designed and built in Britain by Teleng, one of Europe's largest TV Games manufacturers.

Mercury Commander — Complete with 10 Game Cartridge, 2 joysticks. Mains adaptor — in colour with Videotime TV Sound — No Additional Costs **£39.95\***



Plus additional cartridges

Stunt Rider with hand control, 4 games  
..... **£16.90\***

Road Race 2 games ..... **£10.90\***

Tank Battles with 2 joystick controls  
..... **£21.90\***

More to follow . . . Submarine & Spacewar, Wipeout & Breakthrough, Shooting Gallery.

Game / Aerial Switch Box ..... **£3.95\***

\* Prices include VAT, packing & delivery charges and money back guarantee. Send cheque or P.O. to



**VIDEOTIME PRODUCTS** 56 Queens Road, Basingstoke, Hants RG21 1REA

Tel: (0256) 56417. Telex: 858747.

(Trade & Export Enquiries welcome)



## Dorachime. The 8-Tune Door Chime Kit

at **£12.50 + P&P**

### Sounds Simply Wonderful

(Offer closes 31st January 1979)

If you are the sort of person who delights in novel possessions, this will appeal to you.

Ready to surprise your visitors as their fingers press the bell-push are 8 tunes, stored in Dorachime's micro-circuitry. You can switch between them as you like, merely with a movement to the 'Tune Select' control. Tempo control speeds or slows the music to suit your mood. Ranging from 'Greensleeves' to 'Sailors Hornpipe', the selection has been carefully made to ensure you have something appropriate for every visitor.

The effect on your guests is both stunning and amusing. It is worth the price of the Dorachime, for instance, if just once your bell can play 'O Come All Ye Faithful' to surprise your friends at Christmas. You can see the possibilities.

#### Technologically advanced

You may have read in the prestige national press of the research effort currently devoted to micro computer chips. The Dorachime is a musical revelation of its progress.

It produces, from its powerful little loudspeaker, notes similar in value to a miniature electric organ.



**NOW AVAILABLE**  
8 Chime ready-built  
at £15.50 + p&p  
ALSO 24 Chime version  
Kit - £15.95 + p&p  
Ready-Built - £19.40  
+ p&p.

- A1 Greensleeves
- B1 God Save The Queen
- \*C1 Rule Britannia
- D1 Land of Hope and Glory
- E1 Oh Come All Ye Faithful
- F1 Oranges and Lemons
- \*G1 Westminster Chimes
- H1 Sailor's Hornpipe

\* These tunes play longer if the push button is kept pressed.

MADE IN ENGLAND

You can connect the Chime in seconds to your existing bell circuitry, the only things needed to complete are two standard PP3 (P) batteries, wiring and bell push.

### REMINDER

The DORAM Electronic Hobbies Catalogue is now available. To obtain your FREE copy send 25p contribution to postage and packing.

**Blends with any decor**  
Many ordinary door chimes are bulky, even unsightly. The Dorachime measures a trim 5 1/4" x 3 1/2" x 1 1/2" and its smart white lines will blend sweetly with any colour scheme. Easily assembled in a couple of hours using a soldering iron, small screwdriver, pliers and wire cutters.

**Order now. Guarantee of Satisfaction.**  
Send the coupon immediately. Your Dorachime will be delivered within 21-28 days. If you are not completely satisfied you may return your purchase within 30 days for a full refund.

Doram Electronics Ltd. PO Box TR8  
Leeds LS12 2UF.

An Electrocomponents Group Company

To Doram Electronics Ltd. PO Box TR8 Leeds LS12 2UF

Please send 8-Chime Kit(s) at £12.95 ea (£12.50 + 45p p&p)  
Please send 8-Chime(s) Ready-Built at £15.95 ea (£15.50 + 45p p&p)  
Please send 24-Chime Kit(s) at £16.50 ea (£15.95 + 55p p&p)  
Please send 24-Chime(s) Ready-Built at £19.95 ea (£19.40 + 55p p&p)  
Please send a Hobbies Catalogue I enclose 25p p&p

I enclose cheque/PO for £

I am paying via National Giro Centre Bootle Lancs to your Account

Number 00/643/7257

Please debit my ACCESS Card No.

I expect delivery within 21-28 days

Signature

Name

Address

(BLOCK LETTERS)


Doram Electronics Ltd Reg 1155856

HE 12

# ELECTRONI-KIT

"EDUCATIONAL KITS OF  
EXCEPTIONAL QUALITY"

(AUDIO magazine)

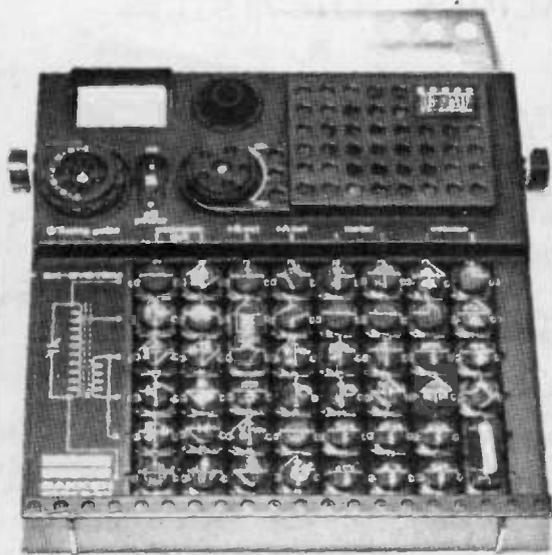

**THIS IS A POWERFUL  
RADIO RECEIVER!**

The same kit is also 150 other different  
actual working projects e.g.:

Computer & Logic Circuits  
Electronic Organ, Timer, Light  
Control, Agility Tester, Lie  
Detector, Siren, Horn, Buzzer,  
Bird, Metronome  
Cds cell light & sound control  
Photogun, Light Oscillator  
Light Switch, Light and Sound  
Morse Code.  
Field Strength Meter  
Hygrometer, Sphygmometer, etc.  
etc.

Radio Receiver, Transmitter,  
Amplifier, Audio Generator, Signal  
Tracer & Injector, Continuity Tester,  
Telegraph, Photoradio Receiver,  
Radio Receiver/Microphone Mixer,  
Illuminometer, Voltmeter, Ammeter,  
Sound Level Meter, Ohmmeter,  
Diode & Transistor Tester,  
Transparency Indicator, etc., etc.

The above is just a *selection* of the circuits available — you  
can also design your own circuits with these superb new  
Denshi-Gakken "EX" construction kits

No previous experience of electronics is required but you  
learn as you construct and have a great deal of fun too. The  
kits are completely safe for *anyone* to use.

Kits are *complete* with very extensive construction  
manuals *PLUS* Hamlyn's "All-Colour" 160 page book  
"Electronics" (free of charge whilst stocks last).

**ALL KITS ARE FULLY GUARANTEED.** Add-on sets (to  
increase the scope of each kit) are available, plus spares  
and accessories as required.

150 PROJECT KIT <b>£39.75</b>	60 PROJECT KIT <b>£25.75</b>
120 PROJECT KIT <b>£33.75</b>	30 PROJECT KIT <b>£18.95</b>
100 PROJECT KIT <b>£29.25</b>	15 PROJECT KIT <b>£16.75</b>

Prices include educational manuals, free book, VAT, p&p (in the U.K.) and  
free introduction to the British Amateur Electronics Club

Callers at 20 Bride Lane will be very welcome. Trade and Educational  
enquiries invited.

See us at **BREADBOARD '78**

**Seymour Hall, 21-25 November.**

Cheque / P.O. Barclaycard / Access No. (or 14p for illustrated literature) to  
DEPT HE

**ELECTRONI-KIT, LTD.  
20 BRIDE LANE, LUDGATE CIRCUS,  
LONDON, EC4Y 8DX (01-353 6430)**

MAINS  
OPERATED

# ELECTRONIC DIGITAL ALARM CLOCK

IMMEDIATE  
DELIVERY

**£8.95**

INCL V.A.T  
POST PAID

THREE FOR £26.00  
POST FREE

HOBBY  
ELECTRONICS  
RECOMMEND  
THIS  
MODEL

BARCLAY  
ACCESS

- Hanimex HC-1100
- Large Bright LED display
- White case with red display  
on black background
- Adjustable dim / bright control
- Silent operation, all electronic
- Space age technology L.S.I. circuitry
- Alarm and 9 minute snooze repeater
- P.M. indicator
- Seconds Display
- Size 100mm x 130mm x 60mm high
- Fully guaranteed



**Henry's**  
RADIO

HENRY'S RADIO  
404 Edgware Rd. London W2  
PHONE (01)723 1008

# ADVENTURES WITH ELECTRONICS

**TOM DUNCAN**

How to make

- a rain detector
- fire and burglar alarms
- an electronic organ
- several sorts of radio
- lots of other electronic devices

To start, nothing has to be known about electronics.  
But by the end of the book the reader will have  
learned a great deal.

The 'bits and pieces' needed for making all these  
models can be bought inexpensively as a complete  
kit, or can be searched for separately at radio hobby  
shops. Full details are given of both methods.


**£2.50**

Available from booksellers

Published by John Murray

# Monitor

## ELECTRONIC DOTTED LINE

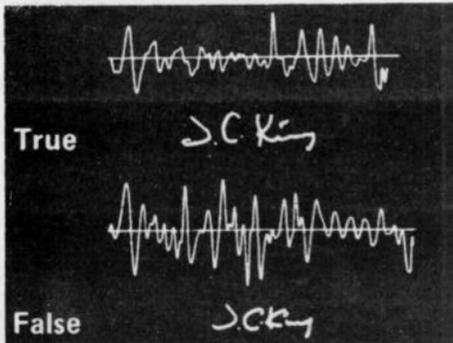

What's the difference between these two signatures? Very little, you may well reply. The computer-produced traces tell a different story, however. They're not based on the signatures as such but on the acceleration of the pen tip and the pressure used while writing.

By using a pen which is wired up to a computer, IBM claim to be able to accept a valid signature of a possible 3,000 with a success rate of 98.3%

Obvious applications are in banks and other places where identification is important.

## GUINNESS GRACIOUS ME

Guinness have installed an automatic weighing system at their St. James' Gate brewery in Dublin. The system, by Avery, uses punched (drunk?) cards to tell it exactly how much barley flake, roast malt or whatever to put in each batch of the brew.

What, we ask ourselves, is the world coming to? Automated Guinness!

The system includes digitising instrumentation, sequencing equipment and a printer.

Lord help Messrs G if the real Guinness affectionados got wind of this. Most people think of the hallowed Guinness brewery as a place where little folk in green linen trip happily around carrying pots of various smelly ferments which they tip into giant wooden vats according to an ancient and mystical procedure. The result of this happy endeavour is the marvellous black stout — and an occasional pea-green river Liffey (which the Dubliners are sometimes heard to refer to as the Whiffey).

Why, if this sort of thing is allowed to go on unchecked, it may enter such hallowed ground as winemaking or even (perish the thought) drinking!

## THE 79 STEPS



Sinclair Radionics have again "broken the cost barrier" with a 79-step programmable calculator for under £25. The 'Enterprise', as well as the normal functions expected of a scientific calculator (trigonometric functions, logs, etc.) has seven independent memories which can be used under program control or manually. Other features include a forward or backward stepping facility for examining the stored program and conditional branching under program control.

Not content with selling just the calculator for under £25, Sinclair have thrown in a case, mains adaptor, alkaline battery and a three volume software library containing, in all, 316 programs as well as an instruction manual.

Sinclair Radionics, London Road, St. Ives, Huntingdon, Cambs. PE17 4HJ.


## OBSOLETE DATA

We have just received a copy of the D.A.T.A. Book of Obsolete Integrated Circuits (8th edition, from London information at £21.25). This invaluable publication lists the electrical and physical characteristics of "every device which has become obsolete since 1965".

The total is nearly 24 000 digital, linear, memory and interface ICs.

It even gives the addresses of the 187 different firms who used to make them!

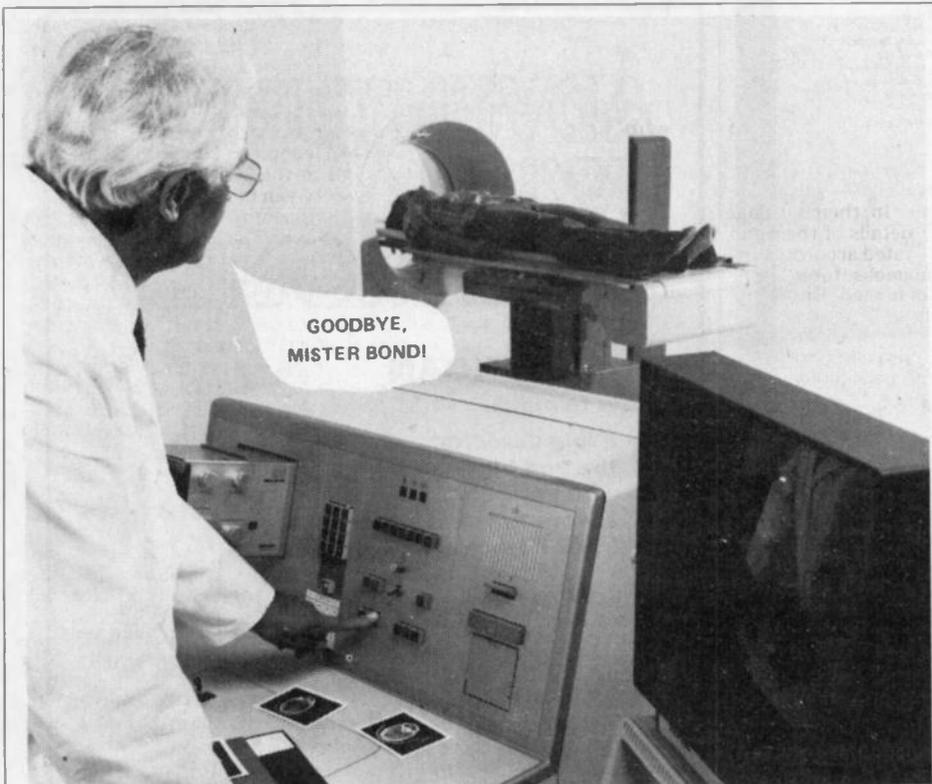London Information (Rowse Muir) Ltd, Index House, Ascot, Berks.



Goldfinger is alive and well and working for Siemens! This gem (minus the baloon) was sent in to publicise the new 'Somaton' head to foot computer tomograph from Siemens and we thought it too good to miss.

# News from the Electronics World

## DIGEST

Pacific Airlines in California are taking delivery of 30 computerised ticket machines. Passengers will be able to insert any one of six credit cards.




The US airforce has placed a contract with a UK company to develop a microprocessor based fire detection system. Hopefully, the system will be able to give a lower rate of false alarms than previous systems. It seems that pilots tend to eject, leaving their sometimes uncombusted F111s to find their own way down!



Researchers at Chelsea College have developed a system which "sucks up" sound. By using two loudspeakers and a microphone as well as some sophisticated electronics, they have succeeded in nullifying the noise from a ventilator.

## SQUEAK, SQUEAK

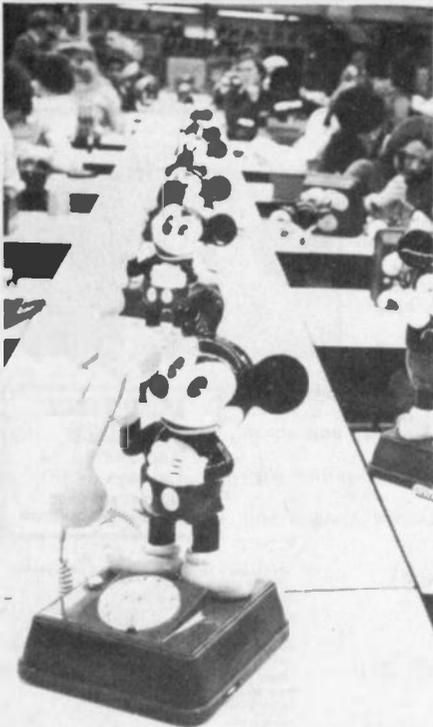

Not content with Buzby, the Post Office has gone and introduced a new telephone that looks very Mickey Mouse indeed. Yes, folks, for a small extra charge (payable in cheese?) you could be the first kid on your block to be the proud (?) keeper of a brand new — latest technology — Mickey Mouse telephone! Available, for the time being, only in the London area (where, you may remember, rats started the great Plague), Mickey is the first of a whole new range of decorative phones that are due early next year.

Racal-Datacom have developed a micro-processor controlled, battery powered teleprinter that fits into a briefcase.



New in the land of the rising Sun, a laser-based video disc system from Matsushita. It can store up to 20 000 still pictures on one 20 cm disc — and you can even record them yourself.



The first chance for the general public to use Prestel, the Post Office's Viewdata service, was at the Motor Show.

## FOUR OF A KIND

'Probably the first thing any aspiring project builder needs (before even the infamous soldering iron) is a fistful of catalogues. The most useful being, in this respect, those from companies making and/or selling electronic components and the various tools, nuts, bolts, boxes, wires, solder etc. etc. etc. that put and hold the components together. Having acquired these, it becomes a great deal easier to make the usual compromise between prices and quality. As most firms publishing catalogues will operate a mail order service, it then becomes possible to gather all the bits for a project in the comfort of your own home (providing someone else is willing to nip round the corner to the post box for you). Four catalogues that we've been sent over the past month came from some quite different companies: Doram who specialise in DIY kits of various sorts; Home Radio and Stevenson who supply components and accessories; and Vero who make boards and boxes.


In their 40 page catalogue, Doram give details of their audio and test gear kits (star rated according to difficulty of construction), books, tools and various other items as well as their range of ready built test gear, available from Doram Electronics Ltd, P.O. Box TR8, Wellington Road Estate, Wellington Bridge, LEEDS LS12 2UF for 25p for P&P.

Home Radio's catalogue shows a large range of components, hardware, tools, test gear and books. Practically every item is clearly illustrated, down to the last nut, bolt or washer, and precisely described, 128 pages, available from Home Radio (Components) Ltd, 240, London Road, Mitcham, Surrey CR4 3HD for £1.25 including P&P.

Stevenson display a good range of components, as well as a stock of hardware bits which should cater for most project builders, 40 pages available from Stevenson, 236, High Street, BROMLEY, Kent, BR1 1PW, free of charge.

The Vero catalogue shows off their range of well known circuit boards and related accessories, as well as their equally well known range of boxes and cases. All the items are clearly illustrated and precisely dimensioned, with instructions for use being given in many instances. 36 pages available from Vero Electronics Ltd, Retail Dept, Industrial Estate, Chandlers Ford, Hampshire, SO5 3ZR, for 25p for P&P.

## WHAT A SPECTACLE!

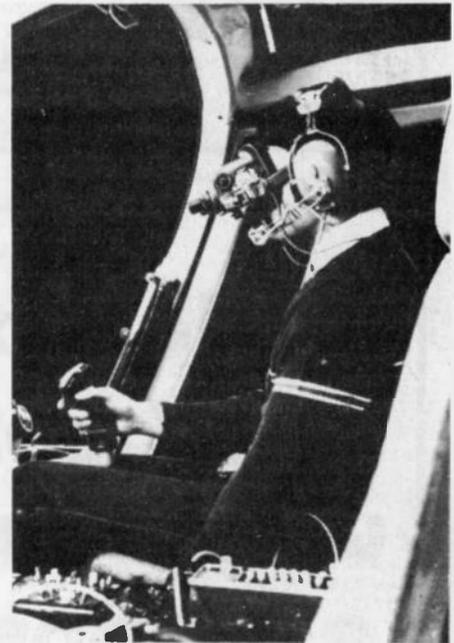

The man in the modern version of the iron mask is a pilot with the Swiss Helicopter Alpine Rescue Service (SHARS) and the contraption on his face is a modified set of ITT night vision glasses. Most of SHARS's work is in the worst of the weather (since that is, when people most need rescuing). With the aid of the glasses the wearer can distinguish between fields, woods and hills — which would appear as complete blackness to the naked eye. Two pilots are essential when the glasses are used, as the wearer cannot see the instruments! Even so, SHARS teams have managed to land in total blackness, with one of the team flying and the other giving directions.

The glasses use electronic vision intensifiers to produce a simulated view, rather like a TV picture, and were originally developed for the military — nice to see them being put to a more humanitarian use.

## ERRATA

Last month we gave the impression that components were available from RS components directly to the amateur. In fact, RS supply only to 'trade'. However, all RS components are available from most major retailers.

The parts list of the amplifier in last month's issue should have included: RV1 100k dual linear; RV2 100k dual linear; RV3 47k linear; RV4 47k dual logarithmic.

In the Waa-Waa circuit diagram, bottom of RV2 should also be connected IC1 pin 3. In the overlay, the input and output connections from C1 and C4 are via SW2.

**SINCLAIR PRODUCTS.** Microvision TV £172  
 PD435 £27.25. Means adaptor £3.24. Cass £3.25.  
 DM235 £48.30. Rechargeable battery units £8.  
 Adaptor/charger £3.70. Cass £8.50. Cambridge  
 Prog. calculator £13.16. Prog. library £3.45. Means  
 adaptor £3.20. Enterprise calculator £20.95.

**COMPONENTS.** Send s.a.e. for full list 1lb. FeC  
 £1.06. Delco Pan 73p. 60 sq. in. pcb 55p. Laminose  
 cutter 75p. Small drill 20p. zn414 £1.05. pcb and  
 extra parts for radio £3.85. Cass £1. 1N4148 14p.  
 AN4002 3.6p. 741 15p. NE555 23p. bc182b.  
 bc183b. bc184b. bc212b. bc213b. bc214e 4.8p.  
 Plastic. equivs bc105. bc109. bcv71. bcv72 4.8p.  
 1/4W 5%. E12. Resistors 10R to 10M 1p. 0.8p for  
 50+ of one value. 16v electrolytics 5/1/2/5/  
 10/22 mf 5p. 100mf 6p. 1000mf 10p. Polyesters  
 250v. 015. 06B. 1mf 11p. Ceramics 50v £6.22pf  
 to 47n 2p. Polystyrenes 63v E12 10pf to 10n 3p.  
 Zeners 400mW £24.2v to 22v 7p.

**TV GAMES.** Send s.a.e. for data. AY-38500 + kit  
 £8.95. AY-38600 + kit £12.50. Tank battles chip  
 £6.90. Kit £7.05. Stunt cycle chip £6.90. Kit 5.60.  
 Rifle kit 4.95.

**TRANSFORMERS** 0-0.6v 100ma 74p. 1 1/2  
 £2.35. 6.3v £1.89 9-0.9v 75ma 74p. 1a £2.2a  
 £2.60. 12-0.12v 100ma 90p. 1a £2.49.

**IC AUDIO AMPS** with pcb JC12 6w £1.60. JC20  
 10W £2.95. JC40 20W £3.95.

**BATTERY ELIMINATORS.** 3-way type 6 7/8v/9v  
 300 ma £2.95. 100ma radio type with press-studs  
 9v £3.35. 9+9v £4.50. Stabilised type 3/6 7/8v/  
 9v 400ma £6.40. 12v car converters 3/4 1/8/  
 7 1/2v/9v 800ma £2.50.

**BATTERY ELIMINATOR KITS.** Send s.a.e. for data  
 100ma radio types with press-studs 4 1/2v £1.80. 9v  
 £1.80. 9v £1.80. 4 1/2 + 4 1/2v £2.80. 6 + 9v  
 £2.50. 9 + 9v £2.50. Stabilised 8-way types  
 3/4 1/8v/6 7/8v/9/12/15/18v 100ma £3.20.  
 1Amp £8.40. Stabilised power kits 2-18v 100ma  
 £3.60. 2-30 1A £6.95. 2-30v 2a £10.95. 12v car  
 converter 6 7/8v/9v 1a £1.95.  
**T-DEC AND CBC BREADBOARDS** s-dec £3.17.  
 t-dec £4.02. u-dec £4.40. u-dec £7.05. 16 di  
 adaptor £2.14. Exp300 £6.21. exp350 £3.40. exp.  
 650 £3.89. esp4b £2.48.

**BI-PAK AUDIO MODULES.** s450 £23.51. AL60  
 £4.85. pa100 £16.71. spm80 £4.47. bmt80  
 £5.95. Stereo 30 £20.12.

**SWANLEY ELECTRONICS**

(DEPT. HE) 32 GOOSEL RD., SWANLEY KENT  
 Post 30p extra. Prices include VAT

Make sure  
 you don't  
 have to turn  
 the  
 newspapers  
 upside down  
 to get your  
 next copy!

To: Subscriptions  
 Hobby Electronics,  
 25-27 Oxford Street,  
 London W1R 1RF.

I would like a postal subscription to HE starting with the  
 issue. I enclose payment (£6.50 for UK and  
 Eire, £7.50 elsewhere, £11.50 air mail).

Name .....

Address .....

**SPECIAL OFFER ONLY TO HOBBY READERS**

**5 FUNCTION LCD**

Hours, mins, secs.  
 month, date, auto calendar,  
 back-light, quality  
 metal bracelet.

**£7.65**

Very slim, only 8mm thick



**THOUSANDS SOLO 11 FUNCTION SLIM CHRONO**

6 digit 11 functions

- \* Hours, mins, secs.
- \* Day, date, day of week.
- \* 1/100, 1/10, secs. 10 x secs, mins.
- \* Split and lap modes.
- \* Back light, auto calendar.
- \* Only 8 mm thick.

This same watch is being sold for £2.00 in newspaper and magazine special offer ads.

Metac Price  
**£12.65**



**HANIMEX Electronic LED Alarm Clock**

**THOUSANDS SOLD**

**Feature and Specification**

- \* Hour/minute display
- \* Large LED display with p.m. and alarm on indicator
- \* 24 Hours alarm with on-off control
- \* Display flashing for power loss indication
- \* Repeatable 9-minute snooze
- \* Display bright/dim modes control

Size 5 1/2 x 3 9/32 x 2 3/16 (131mm x 100mm x 60mm)  
 Weight: 1.43 lbs (D.65 kg)

**£8.65**

**GUARANTEED SAME DAY DISPATCH**

- \* All prices include VAT and carry 12 months written guarantee with our 10-day money-back assurance
- \* All watches sent first class post
- \* Shops open 9.30 a.m. - 6.00 p.m.

Metac electronics have been selling quartz watches probably longer than any other company in the U.K. We carry a very wide range of models and our shops stock most batteries. Fitting is free and the service is open to all.

Please add 30p p&p all orders

Barclay & Access welcome  
 Phone or send Card Number


**METAC Electronics & Time Centre**

67 HIGH STREET Dept. HE OAVENTRY, NORTHANTS  
 Tel: (032 72) 76545

327 EDGWARE ROAD LONDON W2  
 Tel: (01) 723 4783

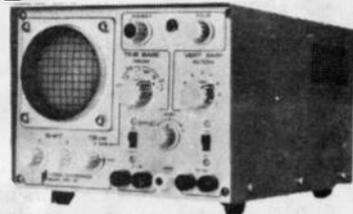**OSCILLOSCOPE FEATURES**

- Response. DC to 5MHz.
- Sensitivity. 100MV to 50V/division.
- Fully calibrated time-base circuit and automatic blanking.
- 100% solid state
- utilising 13 transistors, 1 FET and 1 specially designed time-base module.
- Stabilised power supplies and active sync circuits.
- Rugged construction together with portability.
- Inexpensive - excellent value and performance.



**FROM STOCK**  
**£83.25**  
 Add VAT £7.34  
 Carriage £1.50  
 EXPORT ADD £5.00  
 With full instruction manual

**SPECIFICATIONS**

**ELECTRICAL DATA**  
**VERTICAL AXIS (Y)**  
 Deflection Sensitivity - 100mV/division  
 Bandwidth (between 3dB points) - DC - 5MHz  
 Input Attenuator - (calibrated) - 9 steps 0.1, 0.2, 0.5, 1, 2, 5, 10, 20, 50V/div  
 Input Impedance - 1 Meg/40pF in about Input Voltage - Max - 500V P-P  
**HORIZONTAL AXIS (X)**  
 Deflection Sensitivity - 0.400mV/division  
 Bandwidth (between 3dB points) - 1 Hz - 300KHz  
 Gain Control - Continuous: when time base is EXT position  
 Input Impedance: 1 Meg  
 Input Voltage - Max - 500V P-P  
**TIME BASE**  
 Sweep Range (calibrated) - 100ns/div to 10 sec/div in 5 steps.

Fine Control - Variable between steps - includes time-base calibration position  
 Blanking - Interval - on all ranges

**SYNCHRONISATION**  
 Selection - Internal, external  
 Synchronisation Level - Continuous from positive to negative.

**POWER SUPPLY**  
 Input Voltage - 115/220V AC 10% at 50/60Hz  
 Power Dissipation - 10W

**CAT DATA**  
 - 1/2" read display-angle beam  
 - 1/2" mm high voltage - 750V  
 - Fitted with 10 sections, blue filter graticule

**PHYSICAL DATA**  
 Dimensions - 15cm (h) x 29.5cm (w) x 21cm (d)  
 Weight - 2.0kg (approx.)  
 Stand - 2 position: flat and inclined  
 Case - Steel, epoxy enamelled  
 Colour - Light blue  
 Front Panel - Anodised aluminium, epoxy printing

Also from 248 Tottenham Court Road, London, W.1; 301 Edgware Road, London, W.2.



**HENRY'S RADIO**

All mail to: Henry's Radio  
 404 Edgware Rd. London W2  
 PHONE (01)723 1008 ENGLAND

BUILD THE

# TREASURE TRACER MK III

METAL LOCATOR



AS SEEN ON BBC-1 & BBC-2 TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation (both supplied).
- Britain's best selling metal locator kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including drilled, tinned, fibreglass p.c. board with components sited printed on.
- Complete after sales service.
- Weighs only 22oz.: handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit with pre-built search coil

**£15.95**  
Plus £1.20 P&P  
Plus £1.37 VAT (8%)

Built, tested and Guaranteed

**£20.95**  
Plus £1.20 P&P  
Plus £1.77 VAT (8%)

**MINIKITS ELECTRONICS,**  
6d Cleveland Road, South Woodford,  
LONDON E18 2AN  
(Mail order only)

## BARGAIN PACKS

**TTL**  
7400, 01, 02, 03, 04, 08, 10, 20, 30, 51 ANY MIX 10/£1.00, 100/£9.00.  
7433, 48, 104, 105, 109, 122, ANY MIX 10/£1.90, 100/£18.00  
7445, 46, 92, 95, 151, ANY MIX 4/£1.00  
7443, 83, 96, 156, 160, 162, 163,  
74165, 180, 193, 194, ANY MIX 3/£1.30, 10/  
**£5.20.**  
BC184, 2N711, 12/£1.00, OCP70 5/£1.00  
SIMILAR TO 2N2192 20/£1.00. **MAN 10 1.27"**  
**4/£3.00**  
BAX13, IN4151 100/£1.50, TBA 120A 2/£1.00  
IN5400 10/£0.50, 74S10 20/£1.00  
PANAPLEX 9 DIGIT 7 SEG. DISPLAY 2/£2.50  
THYRISTOR 3A 25V 3/£0.50  
"L/SP 2½ OIA. 40 OHMS 2/£1.00"  
**RESISTORS 10/£0.09, 100/£0.30, ANY MIX**  
E12—10 OHMS TO 1 MEG  
**\*CAPACITORS**  
CERAMIC 27P to 8,700P E12 Series 10/£0.30,  
POLYESTER 0.01 to .1 10/£0.50, ANY MIX 1 MF  
10/£1.00  
ELECTROLYTIC 63V 1MF TO 10MF 10/£0.70. 16V  
10MF TO 100MF 10/£0.70  
**TELEPHONE ORDERS: COV. (0203) 611597 USING**  
ACCESS CARD NO  
V.A.T. add 12½% TO ITEMS MARKED \*. TO ALL  
OTHERS ADD 8%

**IBEK SYSTEMS**

32 OUNSVILLE DRIVE  
COVENTRY  
CV2 2HS

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components. Full range of HE printed circuit boards, normally ex-stock, same day despatch at competitive prices. P.C. Boards to individual designs. Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required).

Alfac range of etch resist transfers, and other drawing materials for p.c. boards.

Send 15p for catalogue.

**RAMAR CONSTRUCTOR SERVICES**  
MASONS ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel. 4879

## PARTS FOR PROJECTS IN HOBBY ELECTRONICS

BC107/8	11p	MC3360	130p
BC109	12p	NE555	27p
BC184	10p	TIL209	13p
BC212	12p	ZN414	100p
CD4017	85p	741	24p

Transformer 240V Pr  
18V 1A Sec 290p (+50p p&p)

## THIS MONTH'S SPECIAL OFFER

2 SN76018	1 SN76131
1 TIL209	2 Heat Sinks
1 1A 100V Br Rect	£5.40.

We carry **LARGE** stocks of **SEMICONDUCTORS/RES/CAPS/ACCESSORIES**. Send 6 x9 Stamped Addressed Envelope for your free list or see our full advert in E.T.I./PW/PE/WW. Add 25p p&p. All above prices inc. VAT.

## TECHNOMATIC LTD.

17 BURNLEY ROAD, LONDON, NW10  
(2 mins from Dollis Hill Tube)  
Hrs Mon-Fri 9.30-5.30  
Sat 10.30-4.30

## HI-PERFORMANCE ELECTRONIC (CAPACITOR DISCHARGE) IGNITION UNIT

... Good for your car and your pocket



Fit one to-day and SAVE, SAVE, SAVE!

Why pay more when you can enjoy the advantages of true capacitor discharge ignition (CDI) at virtually pre-inflation prices? The benefits to your car and your pocket are enormous — easy starting in the coldest of cold weather, an end to burnt contacts and arcing problems, better engine wear and petrol consumption and, of course, easy and secure fitting to your vehicle. **ORDER NOW WHILE WE CAN HOLD TO THESE PRICES** — State if pos. or neg. earth.

INC. V.A.T. AND POST FREE IN U.K.

READY BUILT ONLY

**£14.95**

D.I.Y KIT COMPLETE

**£12.75**

Why be without?

- MADE IN OUR OWN U.K. FACTORY
- SWITCH FOR INSTANT RETURN TO ORDINARY IGNITION
- NEG. OR POS. EARTH MODELS
- HEAVY GAUGE ENCLOSED METAL CASE
- BUILT FOR YEARS OF DEPENDABLE SERVICE
- FULL 12 MONTHS' GUARANTEE

Pay by Access or Barclaycard if you wish

**STIRLING SOUND**  
37 VANGUARD WAY, SHOEBOURNESS, ESSEX  
Tel (03708) 5543

Shop — 222/224 West Road, Westcliff-on-Sea.

To Stirling Sound, 37 Vanguard Way  
Shoebourness, Essex

Please send Mark 5 Ready Built @ £14.95

Kit @ £12.75

NAME

ADDRESS

HE12

**AT BREADBOARD '78** Stand D3

# Metronome

*For those of you with musical aspirations, this project will help you to get into rhythm without beating about the bush.*



TICK, TICK, TICK. Not marks of scholastic approval, but the sound made by our electronic metronome. The metronome is designed to help those learning to play a musical instrument who find that keeping time is one of the first hurdles to be encountered. A sense of natural rhythm is not present in most of us and the metronome, by producing a series of regular beats, is a considerable help in the early days of a potential Andre Previn or Brian May (according to taste).

We would claim that in this case the electronic version is an improvement over the clockwork mechanisms that many of you will have seen. Doing things the electronic way need not be the best method *all* the time but judge for yourselves if our self-contained little box of tricks is not a better proposition than the rather bulky, fragile and often expensive mechanical analogue.

## **TICK IN TIME**

You can see that our metronome was built into a small plastic case with just one control on the front panel. This is the on/off and rate control. The beat can be varied between about 30 and 120 beats per minute, the beat being reproduced by the GPO 'insert' mounted behind the decorative holes on the panel.

## **CONSTRUCTION**

This is largely a matter of choice. We show two alternative component layouts, one using printed circuit board (PCB) specially designed for this project, the other using a general purpose board. Whichever method you care to use, follow the overlay shown with care. It's important to get the IC, transistors, and electrolytic capacitors the right way round if you don't want a 'metronome mort' on your hands.

## **Parts List**

### RESISTORS

R1	2k2
R2	47k
R3	10k

### CAPACITORS

C2	10n	polyester
C1	1u0	35V tantalum
C3	10u	16V electrolytic

### POTENTIOMETER

RV1	1M0 linear with switch
-----	------------------------

### SEMICONDUCTORS

IC1	555 timer IC
Q1	BC184L
D1	1N914



### MISCELLANEOUS

PCB as pattern, GPO insert, PP3 battery, Vero box, wire etc.

Looking through the adverts in this issue should locate most of the components used in the Metronome. If you decide to use the PCB it will be available from people like Ramar, Crofton, and Tamtronix. Vero board should be available from most general component suppliers, Vero also


The GPO insert will be cheapest if bought from a shop dealing in surplus GPO goods but it is also possible to buy this device from the more usual component retailers.

**Approximate cost £5.00.**

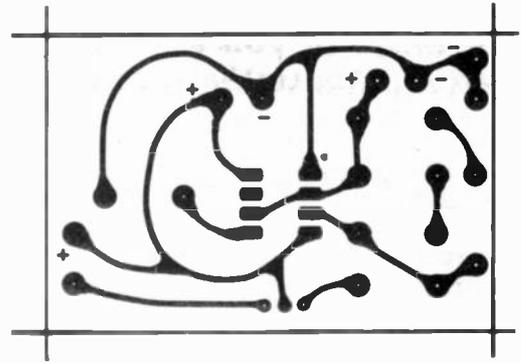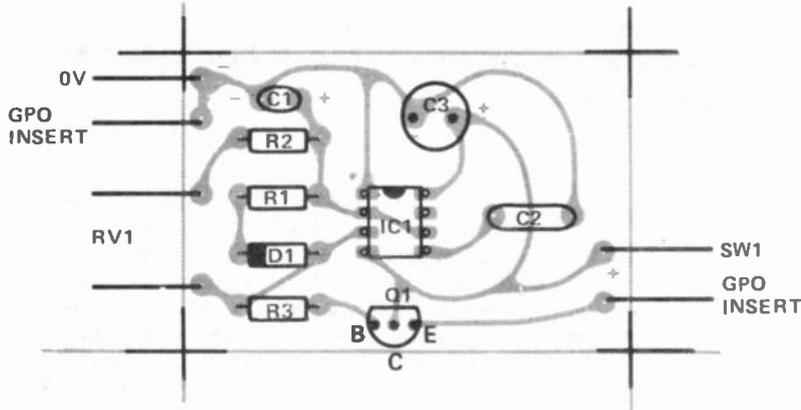



The 'component overlay' above relates the positions of the components on the printed circuit board to their places in the circuit diagram. The metronome is shown opened (below left)

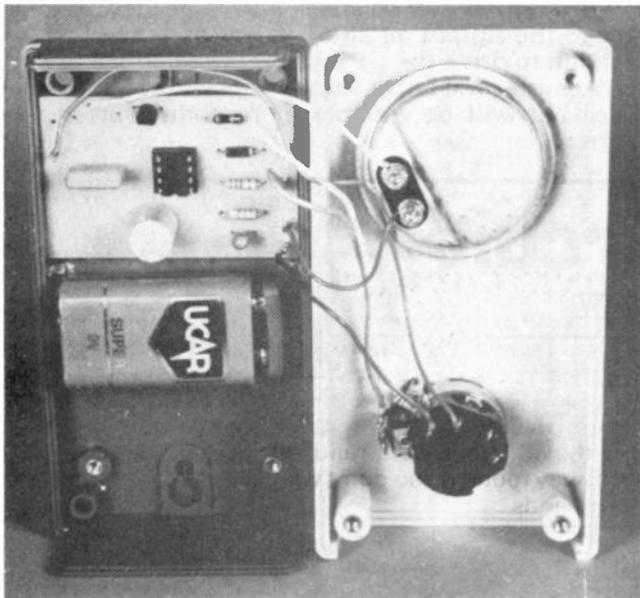to indicate where the major components lie. The printed circuit foil pattern is given (above right).



Drill the front panel with care as any sloppy work here will show up every time you demonstrate your new project. We used Letraset to produce the front panel markings.

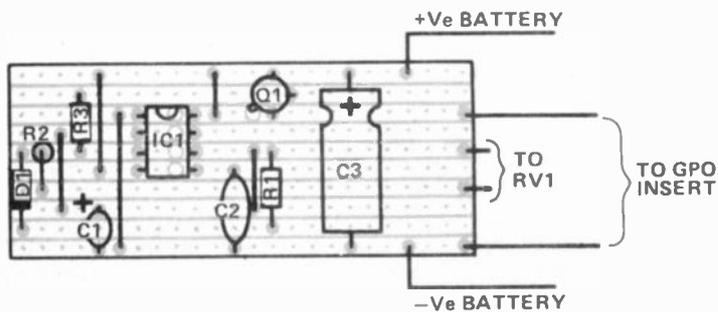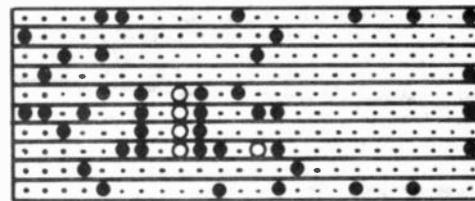When you've finished everything, it's best to put the project to one side for a few hours before carefully checking everything. When this is done, switch on and hopefully you will be rewarded by a series of rhythmic beats.



The Veroboard layout for the construction of the metronome is given here (above and left) as an alternative to the printed circuit board method. In the foil pattern (above), the large black dots represent solder joints while the circles represent breaks in the copper track.

# Metronome


## How it Works

THE beat of the metrome is produced by applying a series of regular electrical pulses to the GPO insert which acts as a loudspeaker.

The pulses used to "drive" the GPO insert are produced by the integrated circuit IC1 called a '555'. This is a very versatile "timer" IC that can be used in a number of different circuit arrangements to produce single timing periods up to many minutes or, as in our case, a series of repetitive pulses.

The 555's internal circuitry consists, in the main, of two comparators and a switch. A comparator compares two voltages and produces an output that depends on the result of the comparison.

The two comparators are connected internally to two of the pins of the IC, one to pin two, the other to pin six. If the voltage on pin two is less than  $\frac{1}{3}$  of the supply voltage then the comparator connected to that pin will turn the output of the 555 on (the voltage at pin three will rise to the supply voltage). This happens when the circuit is first switched on as C1 is discharged. C1 is now charged via D1, R1 and RV1, R2. As the voltage on pin six reaches  $\frac{2}{3}$  of supply, however, the other comparator will turn the output of IC1 off (the voltage at pin three falls to zero). C1 will now discharge only via RV1, R2 as D1 does not allow current to flow now as it is reverse biased.

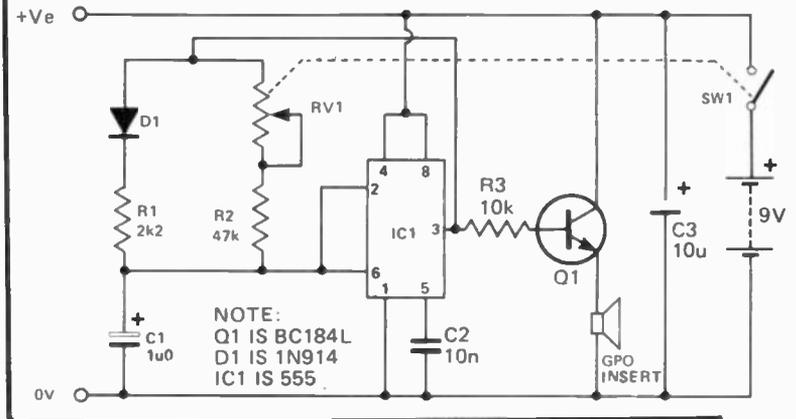

As R1 is of a far lower value than R2 plus RV1, the output of the 555 will be on for a far shorter time than it is off. Thus the timer produces a short, sharp pulse that is just what we want to produce a realistic metronome sound.

By altering the value of RV1 and thus the rate at which C1 is allowed to discharge, we can alter the rate at which the pulses are produced, and thus change the beat of the metronome.

Q1 is an emitter follower and is needed because the output of the 555 is not powerful enough to drive the GPO insert. The voltage at Q1's emitter will be the same as the voltage at its base but will be capable of providing more current.

## Short Circuit

### ONE TRANSISTOR AMPLIFIER

At first glance this may seem a rather complicated circuit — especially for a one transistor amplifier — one of the simplest active circuits in common use, but in fact it is simple enough in its operation. It's just a question of splitting it up into its constituent parts.

Starting with the power supply (from a 9V battery, typically), R7 and C4 provide circuit stability by smoothing the battery voltage. This means that sudden current drain will draw on the current stored in C4, rather than on the battery. Thus these sudden surges will have little effect on the voltage at the tops of R1 and R6 as C4 will be able to handle them.

Resistors R1 and R2 form what is called a divider. This provides a voltage of 3V8 at their junction and this is used to 'bias' the transistor. This means that it is added to the input voltage to the circuit in order to ensure that the average voltage between the base of the transistor and its emitter is about 0V6. This is essential for the correct

operation of the transistor. If this voltage is too high, the transistor will overheat and if it is too low it will not pass enough current to operate.


The bias voltage is added to the alternating input voltage by means of C1. This is called a de-coupling capacitor. Any DC voltage which is present on the input will have no effect on the bias voltage but an alternating voltage will cause the base voltage of the transistor to vary about its bias voltage. This will cause the effective resistance of the

transistor's emitter/collector junction to vary — the higher the base/emitter voltage, the lower the resistance. (This is true of NPN transistor — PNP ones operate in a different direction).

As the base voltage varies then, the current through R6 will vary also. As the top of R6 is fixed at 9V, the voltage on the bottom of it will follow the current variations. This voltage is then de-coupled by C3 (which removes the 6V19 DC and causes the output to vary about 0V).

The network formed by R4, R5 and C2 is necessary to provide stability in the face of two criteria: keeping the base current at the right level and keeping the emitter at a constant voltage so that it doesn't move up and down and disturb the output voltage.

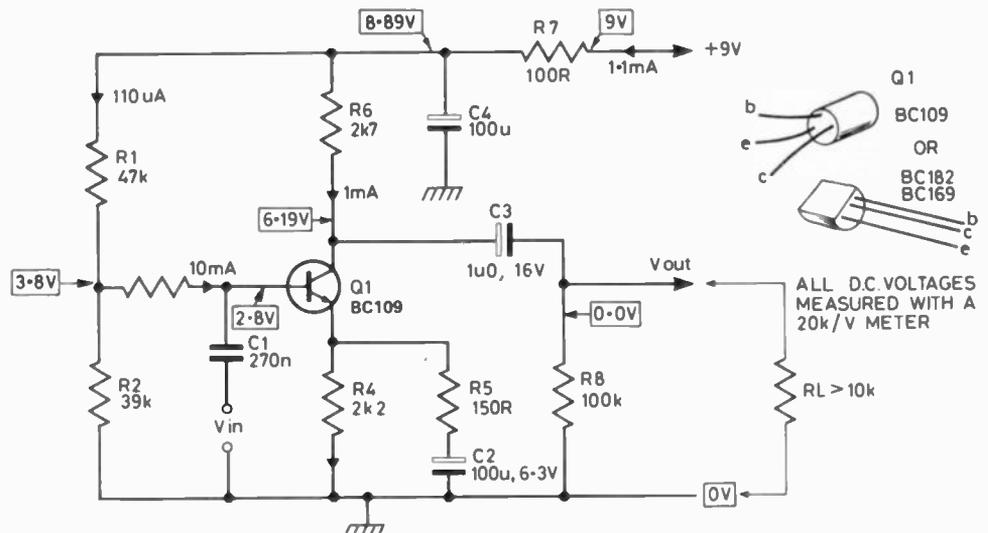The voltage readings on the diagram are what you should expect to find during normal operation. They must be measured with a fairly good meter (about 20 000 ohms per volt) to gain an accurate estimate of their true value.



# Deep Space Communication

**Brian Dance examines the challenges of communications with interplanetary craft.**

IT IS ONE of the triumphs of modern science that we can establish reliable communications with spacecraft at any point in the solar system provided they are not in the radio shadow of some large object as seen from the Earth.

Deep space communications are required for three main purposes

(i) To track spacecraft velocity and distance. This information is required to calculate trajectory and to compute velocity corrections so that the desired trajectory is obtained.

If a pulse is sent to the spacecraft and the on-board transponder immediately sends a pulse in response, the time delay before this pulse is received on earth is a measure of the distance of the craft. The Doppler frequency shift of this signal is a measure of its velocity towards or away from the earth.

(ii) To transmit command signals to the spacecraft. Such a command signal may, for example, switch on a small jet so as to alter the velocity of the craft or it may cause a television camera to point in a certain direction and transmit a picture, or it may switch on a piece of equipment. Many craft have a memory which will store command signals for use at a time when communications are not possible because the craft is behind a planet.

(iii) To send data and television pictures to the earth by telemetry.

During the past twenty years the USA has built up a world-wide network of Deep Space stations for interplanetary communication. This is in almost continuous use and is often receiving signals from quite a number of spacecraft simultaneously.


## **BRIEF HISTORY**

The US Deep Space Communications Network is managed for NASA by the Jet Propulsion Laboratory of the California Institute of Technology (at Pasadena). Pioneering work on liquid and solid rocket propellants was carried out on the Pasadena site of the Guggenheim Aeronautical Laboratory as early as the mid-30's. However, it was the Jet Propulsion Laboratory's work on tracking and data recovery systems for the US army's



guided missiles during the early 1950s which resulted in the development of the present Deep Space Network.

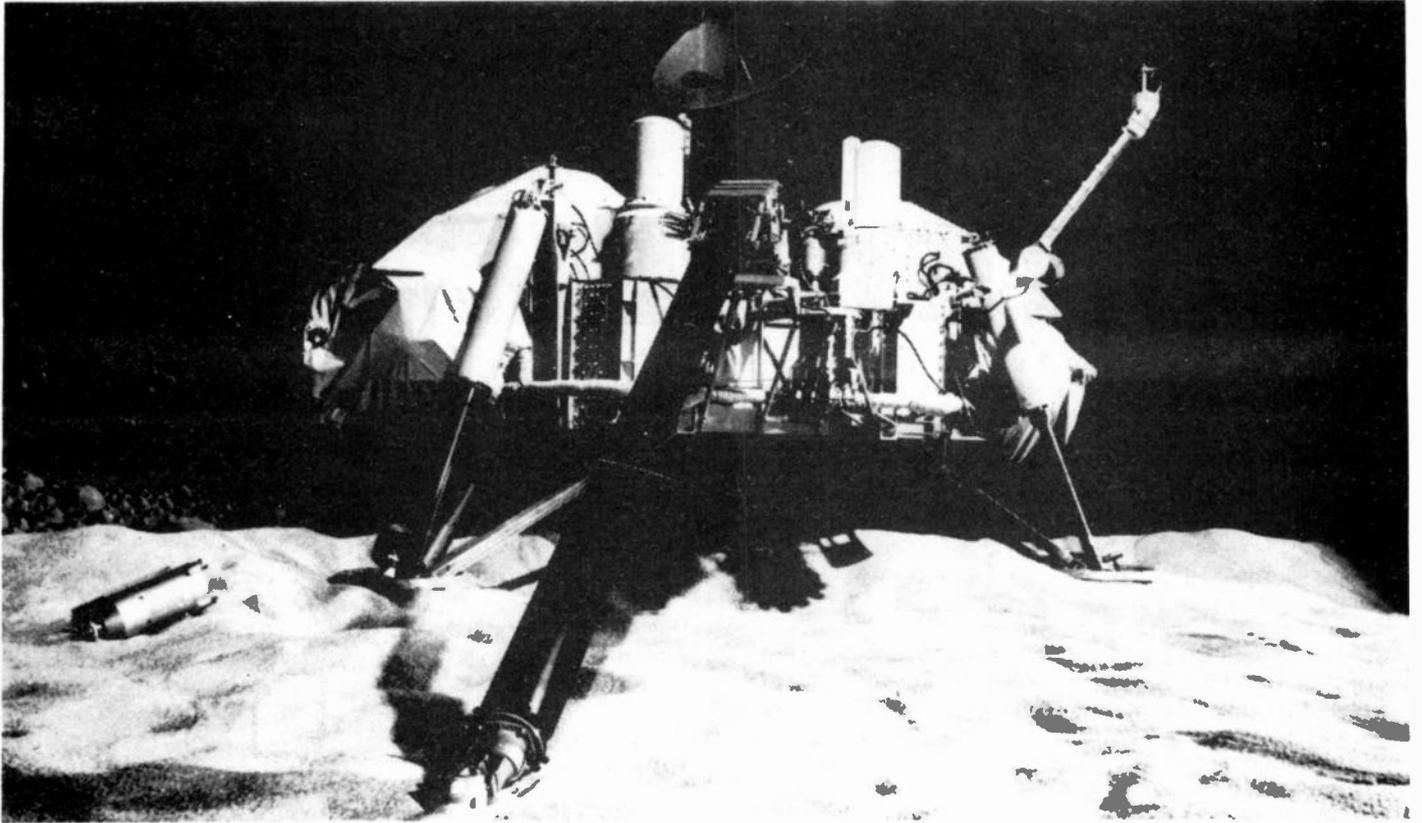The US space programme commenced on 31st January 1958 with the launching of satellite "Explorer 1". This 14 kg spacecraft continued transmitting from Earth orbit until 23rd May 1958; it sent data to a three-station network established by the Jet Propulsion Laboratory incidentally confirming the existence of the Van Allen radiation belts around the Earth.



In September 1958, NASA was created by the US Congress for investigating problems for flight within and outside the earth's atmosphere 'for peaceful purposes to the benefit of mankind'. Two months later the control of the Laboratory was transferred from the US Army to the California Institute of Technology.

The Deep Space Network has provided tracking, command and data acquisition facilities for the Ranger, Surveyor and Lunar Orbiter projects for exploration of the moon, for the Mariner missions to Mars, Venus and Mercury and for the Viking missions for orbiting and landing on Mars. It also supported the Manned Space Flight Network and the Apollo lunar landing programme, apart from collecting data from Pioneers 10 and 11 and the Helios 1 and 2 craft which as the name implies were used to explore space close to the sun.

The Deep Space Network will be involved in even more work during the coming years. The current Pioneer mission to Venus involves receiving signals simultaneously from one large probe, three small probes, a 'bus' carrier vehicle and a Venus orbiting craft. The long duration Voyager 1 and 2 missions to the outer planets (Jupiter in 1979, Saturn in 1980/81 and possibly Uranus in January 1986 and Neptune in 1989) will be carried on simultaneously with work with the Viking craft on Mars and orbiting Mars. In addition, communications must be maintained with Pioneers 10 and 11 outside the orbit of Jupiter, support must be given to the West German space communications facilities working with the two Helios craft, and various other demands made by Deep Space Communications. A Jupiter Orbiter Probe is planned for launching by the Space Shuttle in January 1982 for arrival at Jupiter some two years and eight months later.

## **SEEKING LIFE OUT THERE**

The Deep Space Network is used for many purposes besides deep space including pulsar and quasar studies. The aerials of this network are ideal for radar mapping the surfaces of the planets and the rings of Saturn. It is intended to use two of the aerials for Search for Extra-Terrestrial Intelligence (SETI) — starting about 1979 over a five-year period and covering some 80% of the sky. A search will be made for evidence of radio signals from intelligent extra-terrestrial life — advanced data processing being used to survey the sky over a million different frequency bands. A companion project to be undertaken by the Ames Research Centre will examine 500 selected stars to ascertain if any planets orbiting them are transmitting signals.

## **THE DSN**

The American Deep Space Network employs huge high-gain parabolic dish aerials and very low noise receivers at widely separated places at various longitudes around the globe; this ensures that a spacecraft travelling beyond earth orbit is never out of view of all of the Deep Space Network stations unless it is behind a large object as seen from the Earth. Thus at least one of the stations can communicate with any craft at any time when it is not in radio shadow.

Deep space Network stations are located in groups at three places, Goldstone, California; at Madrid, Spain; and at Tidbinbilla, near Canberra, Australia. Each of these stations is equipped with a huge 64 m diameter dish aerial and two smaller 26 m aerials. Grouping the

# Space Communications

stations together saves money and avoids excessive duplication of equipment. All stations are linked by a special ground communications network which is part of the larger "NASCOM" (No relation! — Ed) network which provides communications between all of NASA's stations.

The ground communications facilities used by the Deep Space Network include INTELSAT communications satellite links and sub-oceanic cables as well as microwave links. Data received from spacecraft are transmitted over high-speed data circuits. Wide bandwidth circuits may carry television pictures of planets and their moons from a Deep Space Network station to the Control Centre at a rate of up to one picture in 48 seconds. In addition, range and velocity information about the spacecraft are transmitted from the receiving station to the Control Centre for navigational purposes. Command signals are sent to the Deep Space Network stations for transmission to the craft. Before transmission they are loaded into a command processing computer which automatically checks them.


The Deep Space Network is not used during the launching phase of a mission. Launches take place from Cape Canaveral, Florida, and use the near-earth facilities of the US Air Force Eastern Test Range in the Atlantic together with the down-range elements of the NASA Spaceflight Tracking and Data Network (STDN) at Merritt Island, Florida. Communications ships and instrumented jet aircraft may also be employed during the launching stage. The STDN system is essentially concerned with manned space flights, earth satellites and lunar probes together with the launching phase of any spacecraft; it consists of 16 stations located throughout the world.

The Goddard Space Flight Centre located in Greenbelt, Maryland, operates the STDN network and the NASCOM network which links all STDN and DSN stations with control centres. The NASCOM network permits the transmission and reception of written messages, facsimile, voice, telemetry and commands by high-speed data lines.

The STDN system provides tracking and communications with the spacecraft during the launching phase, but about the time the launching vehicle is jettisoned and the spacecraft has been put onto its correct trajectory towards the desired planet, the Deep Space Network takes over all communications. It maintains a two-way radio link throughout the remainder of the deep space mission.
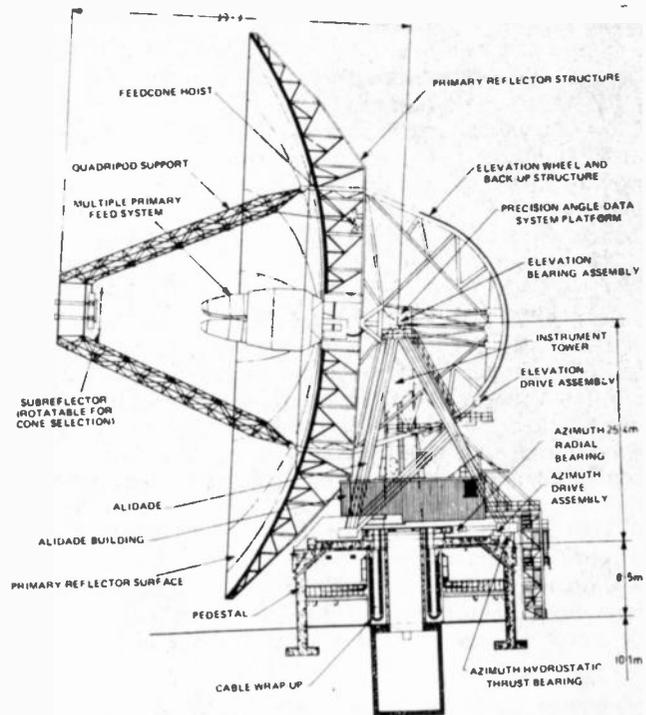
## FREQUENCIES

The standard frequency band used for deep space communications is 2.1 GHz for the up-link from earth to spacecraft and 2.3 GHz for the down-link from spacecraft to earth, these frequencies being in the 'S' band. However, some spacecraft are also equipped with 8.4 GHz (X band) transmitters. Mariner 10 carried a low power X band transmitter not modulated with telemetry, but used with the S band signal for a dual signal for a dual frequency radio experiment. Voyagers 1 and 2 will have both S and X band high power transmitters. The X band down link will be able to send at 115 000 bits/second from Jupiter, but satisfactory reception at distances of  $6.88 \times 10^8$  km at the first encounter with this planet ( $9.27 \times 10^8$  km at the second encounter) may



depend on weather conditions at the Earth receiving station. Rain and other forms of precipitation can seriously degrade reception at X band frequencies, affecting the polarization of the signal, etc.

## POWER LEVELS

The 64 m antenna at Goldstone, California, is equipped for radiating power levels up to 400 kW — the Spanish and Australian 64m aerials have 100 kW transmitters. Each of six 26 m stations is operated at 20 kW. Klystrons are used to generate the radio frequency power.

The Viking Mars craft use transmitters of about 30 W power output, the power being obtained from sunlight by the use of solar panels. The Viking craft which landed on the planet can transmit either directly to earth or to the orbiting craft which can relay the signal to earth.

The Venus Pioneer craft will use solar panels to provide over 200 W of power and will be equipped with a number of aerials. The individual probes from the multi-probe craft will be powered by batteries for a short period after they have separated from the main craft and will transmit directly to earth at levels of 10 W to 40 W. However, the data rates will be relatively low owing to the simple aerials used on these probes. Nevertheless, these data rates should be adequate, since no picture data links are needed.

The Voyager Jupiter craft have to be able to communicate with the earth from enormous distances. The intensity of sunlight is inadequate to provide enough power and therefore plutonium 238 radioisotope thermoelectric generators will be employed. Each craft has three of these generators which are 584 mm in length and 398 mm in diameter and which weigh 12.1 kg. Each of these three generators provides 155 W

initially, about 135 W after five years and about 125 W after 10 years, but only a fraction of this power is available for the transmitter.

The instruments on Voyager require some 99 W. Voyager will be equipped with a 3.7 m diameter dish aerial which will direct the beam towards the earth; this is the largest dish aerial yet built into a spacecraft.

At Jupiter it is expected that the Voyager craft will provide data rates of up to 115 200 bits/second when used with a 64 m earth station and about 640 bits/second when used with a 26 m aerial. When the craft are in the vicinity of Saturn, the data rate will be limited to about 30 000 bits/second when working with a 64 m aerial and 80 bits/second with a 26 m aerial.

The reason for this is that noise introduces errors. A lower rate enables a narrower bandwidth to be employed and this reduces noise. Errors of about one bit in thirty bits are tolerable for TV pictures, however, errors in command signal transmissions *to a craft* must be far smaller to avoid the craft being sent on an incorrect trajectory. Typically the error should be less than one bit in 100 000 bits — command signal errors can be extremely expensive!

Data rates have greatly increased since Mariner 4 transmitted pictures from Mars at 8.3 bits/second — the increase is about 14 000 over a period of ten years.

## SIXTY-FOUR METRE AERIALS

The first of the huge Deep Space Network 64m aerials was constructed at Goldstone, California, part of the design being based on the Australian Radio Telescope aerial at Parkes, NSW; the Goldstone aerial became operational in 1967. Some six years later the Australian 64m aerial at Tidbinbilla (named "Ballima," Aboriginal for "very far away" was brought into regular service, although it assisted with Apollo 17 tracking in 1972.

A 64m antenna collects over six times the signal power compared with the earlier 26m diameter aerials — since the area of a 64m diameter aerial is so much greater. However, other improvements have been made which enable signals of ten times lower intensity to be received than the minimum required by a 26m aerial.

The signal strength from a distant spacecraft is essentially inversely proportional to the square of the distance of the craft from the earth (inverse square law). If a spacecraft at a certain distance produces a signal which is just adequate to be satisfactorily received by a 26m aerial, the same spacecraft will produce a satisfactory signal into a 64m aerial when it is three times farther away. Alternatively a considerably greater data rate can be used with a 64m aerial than with a 26m aerial from the same craft at the same distance.

A 64m diameter aerial is an enormous structure with an overall height of some 73.2m when the aerial is in the horizontal position. The enormous dish must be contoured to an accuracy of  $\pm 1$  mm even at its edges so that the incoming signals of extremely low intensity are concentrated towards the focus of the huge paraboloidal aerial.

Table 1 shows the enormous weight and dimensions of the Tidbinbilla aerial, but the other two aerials of 64m diameter in California and Spain are very similar. These enormous structures must be able to operate in winds of at least 80 km/hour and withstand gales of 190 km/hour when the dish is stowed horizontally.

The antenna must be able to point anywhere above the horizon. Motors with a total power of some 300kW are used to achieve this. The antenna can be directed to any position in space above the horizon with an accuracy of a few thousandths of a degree, yet the huge structure can completely rotate and be moved from horizontal to vertical in about three minutes. The dish must move so that it continues to point at a spacecraft as it moves across our sky despite earth's rotation. Tracking the spacecraft is performed automatically by the station equipment.

Signals can be received as soon as the craft appears above the horizon, since the aerial can be pointed in precisely the required direction beforehand. However, the establishment of two-way communications takes longer if the craft is at any distance; for example, a signal sent to a spacecraft in the vicinity of Jupiter will take about 45 minutes to arrive (depending on the position of Jupiter relative to the earth) — a further 45 minutes will elapse before any responding signal can be received back at the earth.

Apart from the 64m or 26m parabolic aerials, each station must have computers, special receivers, analogue and digital processing equipment, black and white and colour television screens, high speed printers able to read engineering data at 80 000 characters per minute and communications equipment plus engineering laboratories, offices, canteens and dormitories which enable it to be self-sufficient. It must also have its own power plant to supply all of the station requirements — one cannot lose signal through power failure when one is performing such expensive experiments. Each station must also have an atomic time generator so precise that it is accurate to one second in 3 000 years.

## FUTURE IMPROVEMENTS

In order to improve the facilities of the Deep Space Network, it is hoped to increase the diameter of at least one of the 26m diameter aerials to 34 metres by the end of 1978. The construction of a 100m diameter antenna is also being considered, but as one moves to larger diameter aerials, engineering problems become more and more difficult and expensive relative to the increase in signal strength. The possibility of an orbital relay station in deep space is also being considered. The 64m aerials give a gain of well over one million.

Time standards are vital when one is calculating spacecraft trajectories. Very-long-baseline interferometry techniques are being considered for increasing the precision with which the location of each of the Deep Space Network stations is known.

## CONCLUSIONS

The Deep Space Network is a vast engineering project which had to be provided to enable us to obtain information about conditions on other planets and in interplanetary space. Although most of the work of planetary exploration has been carried out by Americans, Australia has provided a very substantial contribution to this work. There will be an increasing demand on the Network during coming years for higher data rates from more distant planets.

HE

**BULK PURCHASE — EXCLUSIVE TO HENRY'S  
ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!**

**QUALITY ITEMS**  
Compare performance and  
specification with units  
costing 3 times as much!

**DIGITAL  
24 HOUR  
CLOCK**

WITH  
BUILT-IN  
ALARM

AS USED IN **BRAUN**  
DIGITAL CLOCKS



- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS ● SIZE 6 1/2" x 2 1/4" x 2 3/4"



MECHANISM ONLY



Assemble  
it in an evening!  
MECHANISM & CASE  
Inc. assembly instructions



Modern  
Styling  
COMPLETE UNIT

**£5.00**

**£6.99**

**£7.99**

THREE FOR £23

THREE FOR £13.50

THREE FOR £20

POST & VAT INCLUSIVE

Send cheque, P.O./M.O. for the correct  
amount which includes VAT and P & P  
or pay by Access/Barclaycard. Send  
name/card number (if applicable) and  
address to:

**HENRY'S RADIO**  
404 EDGWARE ROAD,  
LONDON W2 1ED

AVAILABLE ONLY FROM

**HENRY'S  
Radio**



DELIVERY  
FROM STOCK

# BUILD-IT-YOURSELF NEW! TEST GEAR KIT

BASIC SERVICING  
INSTRUMENTS WITH  
EASY STAGE BY STAGE BUILDING  
INSTRUCTIONS - IDEAL FOR THE AMATEUR

## MULTI RANGE TEST METER

A general purpose meter covering all usual  
ranges of A.C. and D.C. volts current and  
resistance measurements

## AUDIO SIGNAL GENERATOR

New design covering 10Hz to 10KHz  
and variable output. Distortion less than  
0.01% Ideal for HIFI Testing.

## OSCILLOSCOPE

A basic 3" general purpose cathode ray  
oscilloscope for simple testing and  
servicing work. Sensitivity 0.3 volts/cm

**SEND NOW FOR FREE DETAILS**

To LERNAKITS, P.O. Box 156, Jersey.


Name \_\_\_\_\_

Address \_\_\_\_\_

HE 12/78

# Short Circuit

## TWO — TRANSISTOR NOISE SOURCE

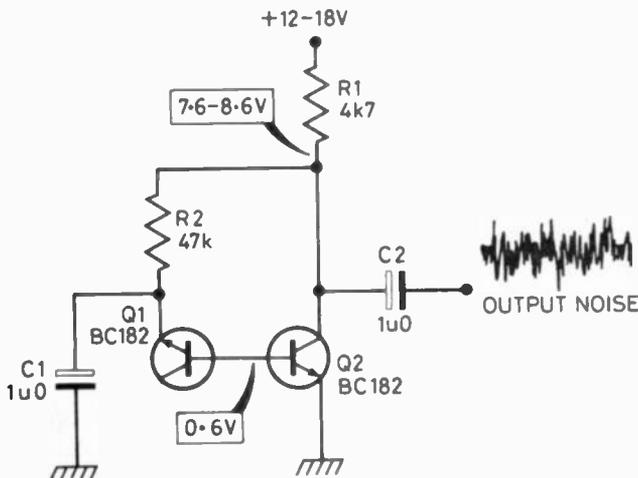

This simple circuit produces electrical noise. This may not seem like a sensible thing to want to produce, but in fact it is very useful. Of course, the sort of noise we mean is not the type neighbours complain about. This circuit produces an

electrical signal which, when suitably amplified, sounds like a hiss of escaping gas. This can be used for sound effect production — with a little additional processing, it can form the basis of sound effects ranging from surf hitting a beach to

a steam train — or for testing loudspeakers by feeding the amplified noise into them and listening to the output.

The operation of the circuit depends on the reverse-bias breakdown of Q1. This occurs when the voltage across the emitter and base of the transistor reaches 7 to 8 volts. At this voltage the semiconductor physics of the transistor cause it to do a very useful thing — produce noise. The rest of the circuit is dedicated to keeping the current through Q1 at just the right level (too little — no noise; too much — dead transistor!) and also to amplifying the result.

Power is supplied to the circuit through R1. This, along with C2 and Q2 form an amplifier which boosts the level of the noise. The bias for Q2 comes through Q1. If Q1 passes a lot of current, Q2 will turn on more and the voltage at the bottom of R1 will drop. This will cause the voltage across Q1 to decrease. In this way the current it passes is kept to a reasonable level. C1 provides a path to earth for the noise which appears on the collector of Q2. This ensures that the fast changes in the amount of current through Q1 (and this is, after all, what we are after) are not 'adjusted' in the same way and lost.

# Photon Phone

***The PHOTON is a light-talker: a communications system which requires no licence.***

THIS IS NOT a morse flasher. This is the equivalent of a two-way radio — but using light instead of radio waves!

All a radio transmitter is, is a source of radio-frequency signals and some means of impressing information onto it. This project uses light, and as a source of light we use — you guessed it — a light bulb!

This project should provide not only an introduction to photoelectronics but also a product which is fun to build and use and (as far as we know) is unavailable commercially in any but a military form.

## **USING IT**

The device is almost as easy to use as a radio — you point your set at the one you want to communicate with; you switch to 'transmit'; with the other set at 'receive', anything you say into the built-in microphone will be heard, via the light beam, at the other set. Reversing the switch positions allows full two-way communication.

The range of the device is limited to about 15 to 20 yards but for many applications (at sea, in a factory, between moving vehicles or just across the street!) this will be sufficient.

The electronics is easy to put together — the only difficult bit is the case.

## **CONSTRUCTION**

The torch body we used can be seen in the various photos in this article. It is made by Ever Ready and should be fairly easy to come across.

The first thing to do is to open it and remove the battery connectors in the inside of the top cover. We need the room and we're using a different type of battery anyway. You will find that these come out with a small amount of force — try not to damage the plastic.

The next thing to do is to take the bulb out and replace it with one of the same size and shape but of a different voltage (see the parts list). You will probably be able to get this at the same place you got the torch body. Now solder the wires onto the OCP71 phototransistor, as shown in the overlay (the diagram which shows you what goes where on the board). Clip the unused (middle) wire short. The diagram shows a view looking onto the end of the wires. Take care not to damage the transistor by excessive heating — it's a good idea to hold the wire you're soldering at a point between the joint and the transistor with a pair of long-nosed pliers while the joint is hot. This will prevent heat from getting into the transistor body. Insulate the wires in some way (Sello-tape will do at a pinch).



Having done that, fit the phototransistor (Q2) onto the bulb as shown in the photo. We used a quick-setting epoxy resin adhesive. You will have to make a small hole in the reflector for the wires to go through. Try to get the transistor as close to the focal point of the reflector as possible. This means mounting it at the very tip of the bulb.

Looking closely at the inside of the torch, you will find that the metal strips which form the normal torch circuit pass from the battery holders (or rather, where the battery holders were until we ripped them out!) up the hand to the switch and then back down to one side of the bulb assembly. Cut the connection between the switch and the bulb. This will probably mean a little minor metalwork with a pair of wire cutters. It should leave you (it is possible to trace the connection path fairly clearly with a little thought) with two connections to the bulb and two to the switch. Solder wires onto all four of these points. Leave the wires fairly long (6 to 8") for future connection to the board.

## **START AT THE BOTTOM**

The speaker fits into the base of the case (poetry, yet! — ED.) at the back. This means that you can either drill an artistic pattern of holes as we have done or just put a few large ones as you think fit. If you don't put any holes at all, the sound won't get in or out.

It's probably a good idea at this stage to solder a couple of wires onto the speaker and glue it into place.

The only thing left to do now is to fit the extension speaker socket (the method should be fairly self-evident from the socket mounting), as the other holes in the case should really be matched with the printed circuit board.

### BOARD MEETING

Having 'acquired' a printed circuit board (see the DIY PCBs article in this issue), fit it into the top of the case (making sure you get it the right way round) and mark out the rest of the holes to be made in the case:

- a) the four PCB mounting holes,
- b) the volume control (RV1) hole and
- c) The SW2 hole (make this big enough for the push-fitting knob).



The construction for the electronics should be fairly straightforward — just follow the diagrams. Watch out that you get C1, the transistors and IC1 the right way round, though. We suggest you use an integrated circuit socket for IC1 — solder it onto the board and then plug the IC into it, making sure all the 'legs' go in. Use a heatsink on Q3. This acts in exactly the same way as a car radiator — it carries the heat into the air, preventing the transistor from overheating.

At the points where wires from the bulb, speaker etc. are to connect to the board, poke stiff wire through and board and solder it, leaving about 1/2in sticking above the board. This will allow you to solder wires on the board *after* it has been bolted down. You will have to use similar bits of wire to connect RV1, as the leads on this will not poke through the holes.

If possible, use a 'lash-up' at this stage — a collection of bits of odd wire connecting the board to the various other bits of the circuit — to check that the board works before you bolt it in.



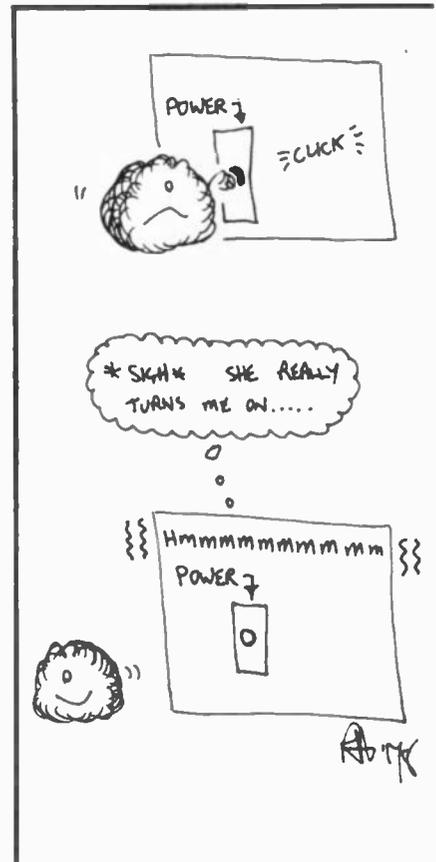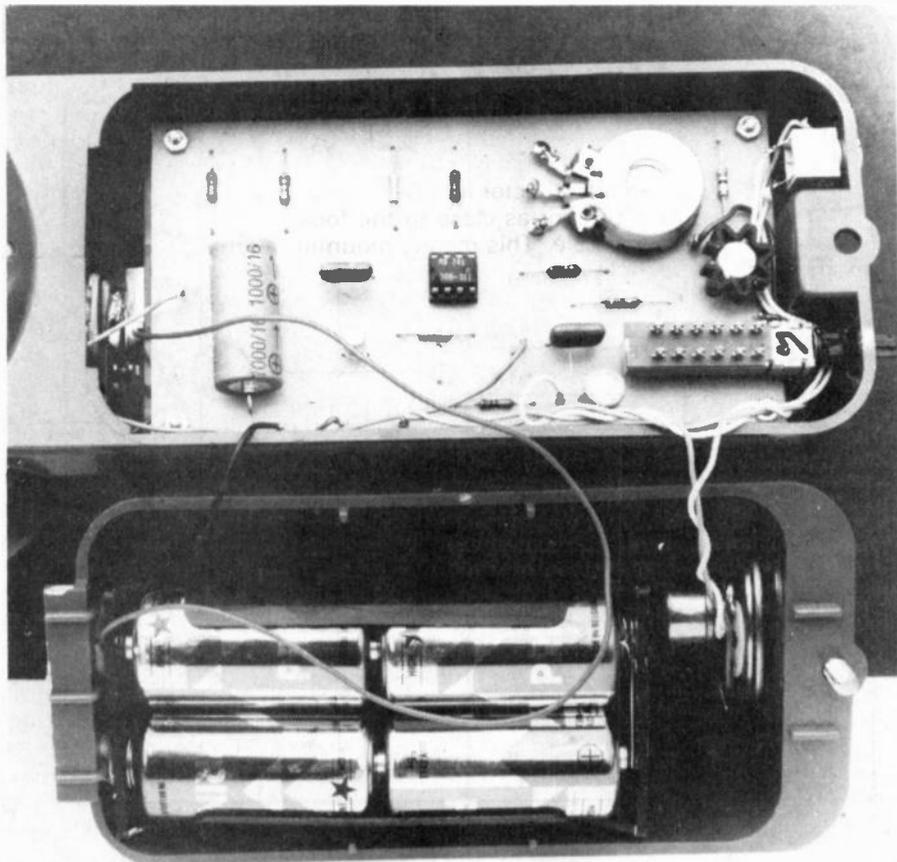*A view of the reflector modifications. The transistor should be placed with the small metal dot (just visible inside the protective gel of its case) towards the rear of the communicator. Some experimentation may be necessary to find the reflector's focal point exactly.*



## BOLT IT DOWN

Use pillars on the four PCB mounting bolts. These are plastic or metal cylinders which slip over the first ¼in or so of the bolts and will hold the board away from the top of the case.

Actually getting the board in is a bit fiddley — but remember that you can always push SW2 in to get it out of the way. It might also be an idea to trim the spindle of RV1 a bit before you mount the board — not too much, though remember you don't know exactly what length it should be until *after* the board is fitted!

Having fitted the board and both of the knobs (SW2 and RV1), you can proceed with the wiring.

The only complicated bit is the wiring of the external speaker socket and the speaker. Connect the 'speaker' point on the board to one side of the speaker and also to the connection on the side of the socket. The 'socket' output of the board goes to the socket connection which is part of the sprung contact of the socket (put a plug into the socket — the bit of the socket that moves is the bit you want). The third socket connection goes to the other side of the speaker. Got all that?

If you're confused, just connect the speaker to the two board outputs mentioned to make sure it all works. You can connect the socket up later.

The battery holders should be connected in series: the "+" connection of one goes to the "-" connection of the other.

The remaining "+" connection goes to the handle switch (SW1 — remember those wires you connected earlier?) and the other side of the switch goes to the board.

*The circuit diagram. SW2 is shown in the 'transmit' position.*

## How it Works


The circuit diagram shows SW2 in the 'transmit' position. The speaker (LS1) acts as a microphone in this mode. C1, R1, Q1 and R2 form a simple single-stage amplifier to boost the signal before it is fed, via C2, to IC1. R4, R6 and C2 set the average voltage at pin 3 of IC1 (the so-called 'bias' voltage).

For a detailed description of what Q2 is and does, see the 'photocells' feature in this issue. Q2 is illuminated by LP1. Suppose LP1 is bright. This will cause more current to pass through Q2 and cause pin 2 of IC1 to go to a higher voltage. IC1 is connected as an inverting amplifier (in much the same way as the op-amps in the 'mixer' project in this issue) and so this will cause the output (pin 6) to fall in voltage. This in turn will turn Q3 down and the current through LP1 will reduce.


All in all, the effect will be to set LP1 at a brightness determined by the pin 3 input of IC1. As this is derived from LS1, speaking into it will cause a brightness fluctuation.

In the 'receive' mode, the light variations at Q2 will cause a voltage variation in the output of IC1. This is used to drive Q3 which is now connected to LS1.

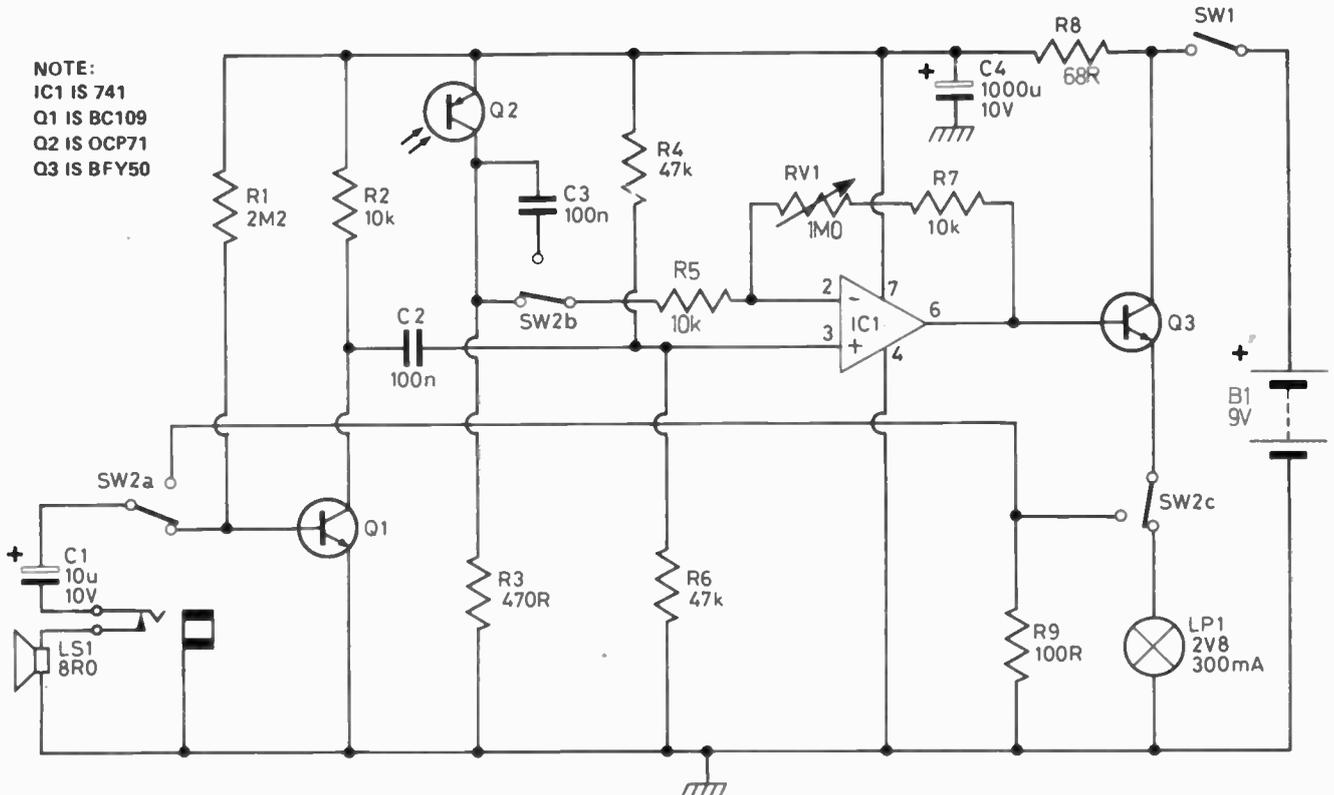
Notice that the rest of the circuit is 'decoupled' from Q3 by R8 and C4. As this device is battery-driven, the current drawn by Q3 will cause major variations in supply voltage. So that these do not interfere with the rest of the circuit's operation, they are filtered out by R8/C4.



# Photon Phone

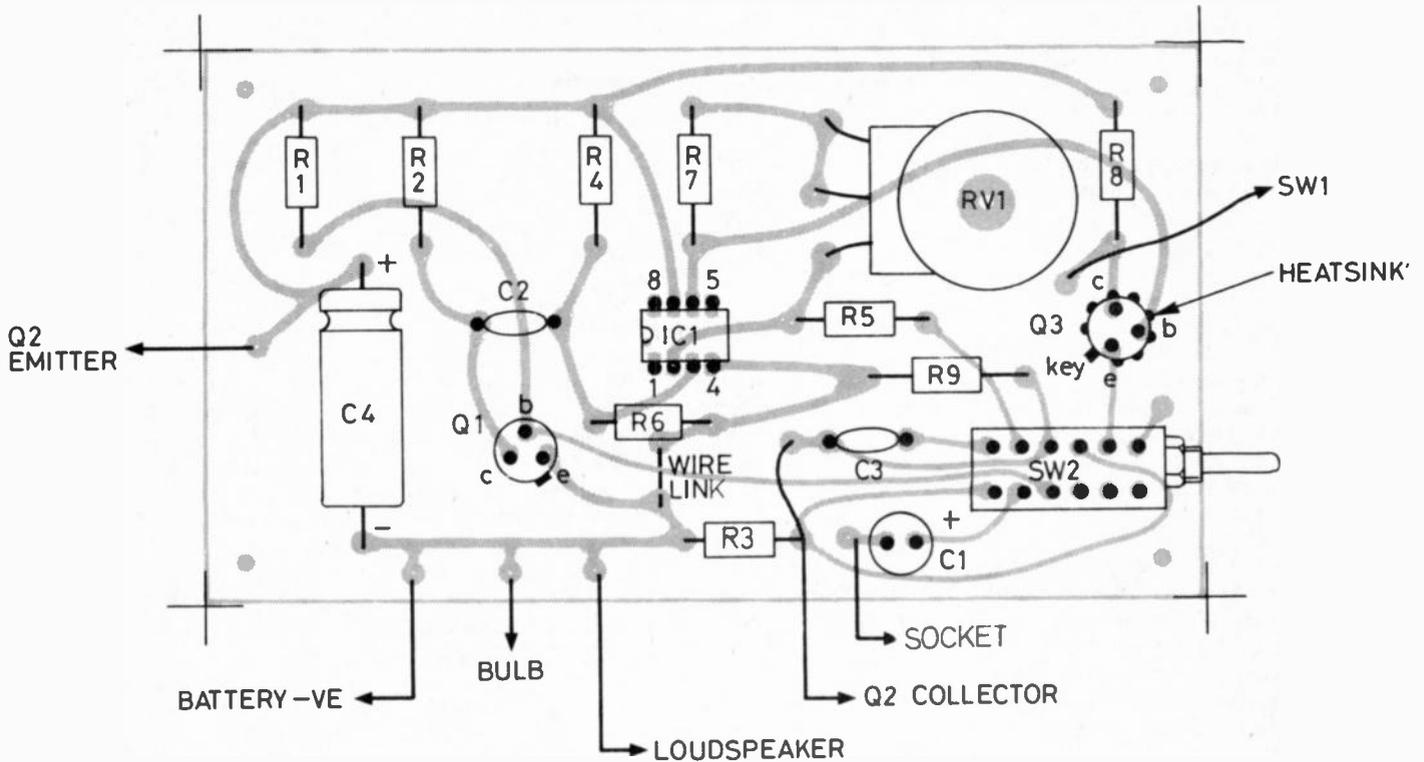

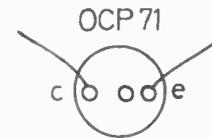**How to position the components on the PCB, make sure the transistors, integrated circuits, diode and electrolytic capacitors are the correct way round before soldering in place.**



## Parts List

### RESISTORS

R1	2M2
R2	10k
R3	470R
R4,6	47k
R5,7	10k
R8	68R
R9	100R

### CAPACITORS

C1	10u 10V electrolytic
C2	100n polyester
C3	100n polyester
C4	1000u 10V electrolytic

### SEMICONDUCTORS

Q1	BC109
Q2	OCP71
Q3	BFY50 + heatsink
IC1	741

### MISCELLANEOUS

RV1	1M logarithmic
LS1	8R, 2 inch
SW2	4 pole 2 way, latching, PCB-mounting switch
LP1	2V8, 300mA

Ever Ready torch; two 4 x HP11 battery holders; 3.5mm earphone socket + matching plug; IC socket.

Most of the components for this project will be available by mail order from advertisements in this issue. The OCP71 is available from Watford Electronics, (33 Cardiff Road, WATFORD, Hertfordshire) for £1.54 inclusive of VAT and P&P.

You should be able to get the torches and bulb from most large department stores.

**Approximate Cost: £9 per unit**

Connect the rest up as per the diagram, and the whole thing should work! If it doesn't, check all the wiring carefully.


## SPOCK TO ENTERPRISE...

With the sets switched on and the SW2s to the relevant positions (one in, one out) point the two devices at each other at a distance of a couple of yards. Speaking into the speaker of the one switched to transmit (SW2 out), you should be able to see the light intensity varying and

a well-placed ear beside the receiving set should be able to hear your voice. (Needless to say, it will not be your ear if it's your voice two yards away!). The volume of the received sound can be adjusted by RV1 to give a pleasant level.

You may find that putting your ear to the speaker while pointing the device is a bit tiresome after a while. This is where SK 1 comes in. A speaker similar to the one already used can be connected across a suitable plug and inserted into the socket. This has the same effect as plugging an earpiece into a radio. The internal speaker is 'disabled' (temporarily!) and the hand-held one is used

# Photon Phone

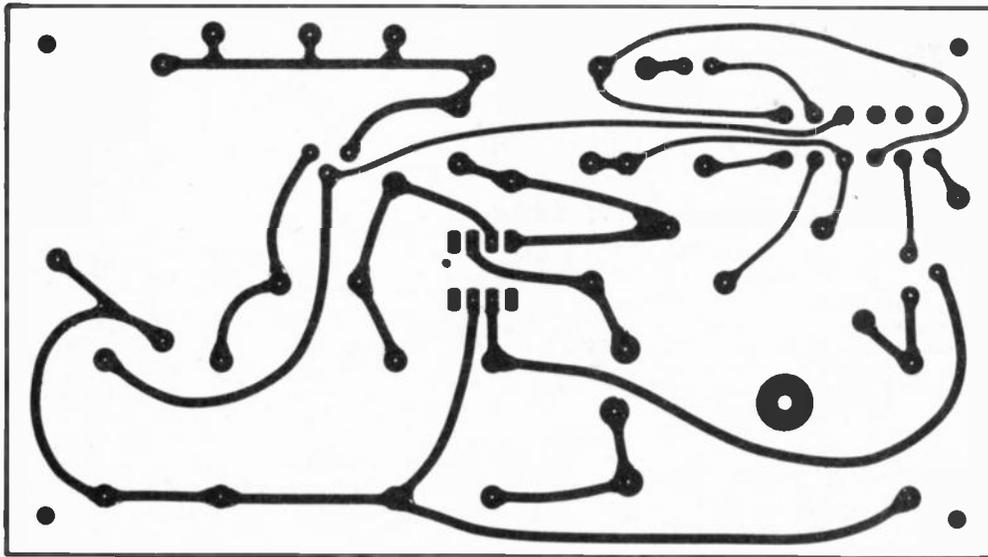

*The printed circuit board pattern shown here is the correct size.*

instead. Putting the external speaker in a small box is a good idea, as is using 'screened' cable for the connecting lead. The centre of the cable goes to the tip connection of the plug.

## **SUMMARY**


This project is difficult to build as a finished product and the fact that two (at least!) are required may seem daunting. However, it can also be built as a 'bread-board' type prototype, or into any type of box you can get your hands on. If you do build it as we suggest, though, you will have a very sturdy product indeed. **HE**



*A rear view of the PHOTON, showing the artistic pattern of holes we drilled to form the speaker grille!*

*The business end. Note how the phototransistor is mounted.*

# Hobby Electronics Book Service

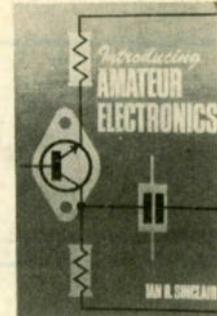

**BUILD-IT BOOK OF OPTOELECTRONIC PROJECTS** by Charles Adams ..... £4.75

A 48 project learn-by-building guide to the super-practical world of optoelectronics with thoroughly readable instructions on how to create everything from an LED circuit monitor to an electronic stopwatch.

**HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS** by Bob Brown and Paul ..... £4.00

This book is for the beginner who wants just enough practical knowledge of electronics to pursue a hobby.

**EASY SPEAKER PROJECTS** by Len Buckwalter ... £3.75

Explains how to make speaker systems ranging from simple shelfboard and ceiling-mounted enclosures to more advanced bass-reflex and omnidirectional ones.

**ELECTRONIC GAMES AND TOYS YOU CAN BUILD** by Len Buckwalter ..... £3.75

A 'just-for-fun' book. No complex electronics theory anywhere — just step-by-step instructions, construction photos, and detailed wiring-construction diagrams for building 15 fascinating electronic games and toys.

**MICROPHONES: HOW THEY WORK & HOW TO USE THEM** by Martin Clifford ..... £4.75

Takes all the mystery out of microphones, shows you how to record almost anything with professional quality, clearly explains how to get different sound effects and better stereo, and fully describes mike positioning techniques.

**BASIC ELECTRONICS COURSE** by Norman H. Crowhurst ..... £5.50

A self-study text for the novice, hobbyist, student — a perfect reference and brush-up guide for technicians and others who want to advance their knowledge of electronics.

**HOW TO TEST ALMOST EVERYTHING ELECTRONIC** by Jack Darr ..... £3.50

Practically every testing technique for almost every kind of electronic equipment is laid out for you in easy, highly readable style.

**ELECTRONICS FOR THE AMATEUR** by Louis M. Dezettel ..... £6.55

Written especially for the radio amateur, discusses radio-wave propagation as it applies to amateur band frequencies, reception and transmission as they pertain to the equipment 'hams' use, and the special field of antennas and how to feed them.

**ELECTRICAL SOLDERING (2nd edition)** by Louis M. Dezettel ..... £4.45

Teaches the hows and whys of electrical soldering. Tells about solder alloys and fluxes. Discusses the various types of soldering devices. Then concentrates on the principles of good soldering and acquiring the needed skill.

**BUILD-IT BOOK OF HOME ELECTRONICS** by Graf and Whalen ..... £3.45

Put electronics to work for you in your home. The authors present thirteen interesting and fun projects that use the latest solid-state devices and ICs.

**BUILD-IT BOOK OF SAFETY ELECTRONICS** by Graf and Whalen ..... £3.45

Contains ideas for building several novel projects to protect toddlers from invading the medicine chest to a motel room from a burglar; and to scare a car thief and more. Thirteen tested safety projects are detailed.

**BUILD-IT BOOK OF FUN AND GAMES** by Graf and Whalen ..... £3.75

All the projects in this book are designed for fun and game applications. The projects include a sight'n'sound metronome, an electronic football game and stereo balance meter, a sound-activated switch and a metal detector.

**IMPROVING YOUR HI-FI** ..... £3.50

This book is aimed at the novice who has just purchased his first audio set-up or is about to do so. It begins with details of how to connect the units together to obtain top performance and explains the meaning and proper use of the many control knobs and switches found on modern hi-fi gear.

**GUIDE TO PRINTED CIRCUITS** by Gordon J. King ..... £3.50

The Text is angled especially at the keen amateur constructor, the experimenter, the service technician and apprentice.

**ELECTRONIC TEST EQUIPMENT** by Harry T. Kitchen £5.00

This book is designed to provide interest for almost everyone involved with electronics. The six chapters explore the more general groups of instruments such as test meters of various types, audio and r.f. signal generators, attenuators and oscilloscopes. Each chapter explains the principles and requirements of particular types of test equipment, including typical circuitry, then discusses the choice, care and use of the equipment.

**FUN WITH ELECTRONICS** by McEntee ..... £3.40

An exciting show-tell-and-build-it book that teaches electronics with plenty of fun in the process.

**AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR** by Ian Sinclair ..... £2.60

Describes in seven chapters the working principles of transistor amplifiers and outlines the steps and circuit design using a modern simplified transistor theory.

**INTRODUCING ELECTRONIC SYSTEMS** by Ian Sinclair ..... £1.80

This book by author-lecturer Ian Sinclair is intended to provide a basic insight into what makes electronics 'tick'.

**INTRODUCING AMATEUR ELECTRONICS** by Ian Sinclair ..... £1.55

This is the book for the complete novice of any age, in which author Ian Sinclair assumes no previous knowledge of the subject by the reader.

**ELECTRONICS FOR THE BEGINNER (2nd edition)** by J. A. Stanley ..... £4.15

A learn-by-doing approach to electronics. Each project is of increasing difficulty, so the beginner also picks up a liberal dose of electronics theory along the way.

**ABC'S OF FET'S** by Rufus P. Turner ..... £3.05

Describes the field effect transistor (FET) in simple language. Deals in detail with the principles of FET operation and stresses the applications of FETs in practical circuits.

**ABC'S OF ELECTRONICS (2nd edition)** by Farl J. Waters ..... £4.15

An introduction to the ever-expanding field of electronics. Covers the principles of electricity, functions of atoms and electrons, magnetic forces and their relationship to electronics.


Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:  
**Hobby Electronics Book Service,  
 P.O. Box 79,  
 Maidenhead, Berks.**

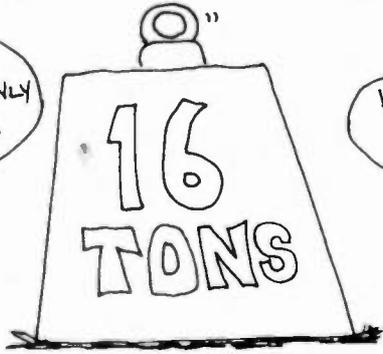**HE-HE!**

D'YOU REALISE THAT IF IT HADN'T BEEN FOR THE DISCOVERY OF ELECTRICITY YOU'D HAVE HAD TO WATCH TELEVISION IN THE DARK !!




OUR PORTABLE ANTI-CRAWTY MACHINE SUDDENLY CUT OUT IN MID-TEST. WHAT D'YOU THINK?




HMMM. LOOKS TO ME AS THOUGH THE BATTERY'S FLAT!!




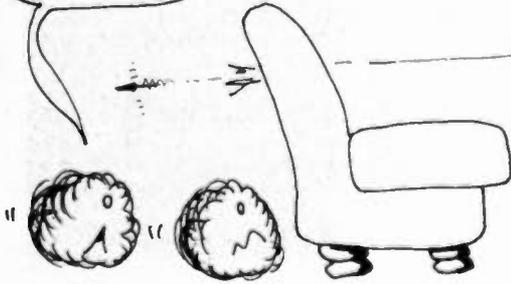
I TOLD YOU T.V. DETECTIVE SHOWS IN 3-D WOULD NEVER CATCH ON !!



CRACK!!  
POW!!  
BLAM!!

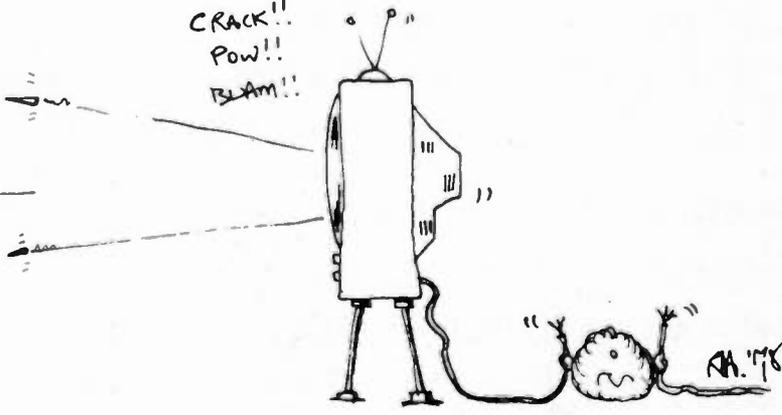

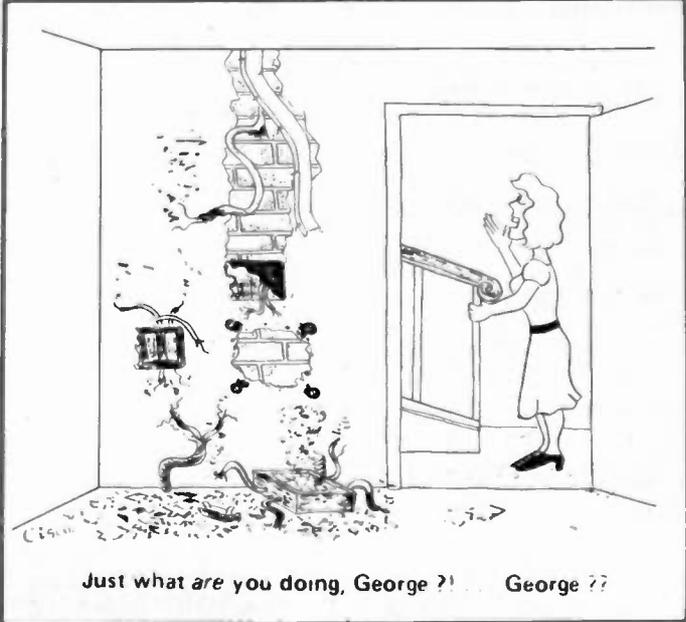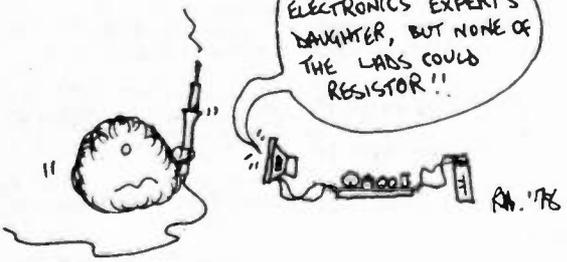SHE WAS ONLY THE ELECTRONICS EXPERT'S DAUGHTER, BUT NONE OF THE LABS COULD RESISTOR !!



Just what are you doing, George ?! ... George ??

# SPECIALS



## TOP PROJECTS

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp, low power laser, printmeter, transistor tester, mixer preamp, logic probe, Ni-Cad charger, loudhailer, scope calibrator, electronic ignition, car theft alarm, turn indicator conveller, brake light warning, LM3900 circuits, temperature alarm, serial matcher, UHF-TV preamp, metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

Book 3: SOLD OUT!

Book 4: £1.00 + 25p P&P.

Sweet sixteen stereo amp, waa-waa, audio level meter, expander/compressor, car theft alarm, headlamp reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit...

Book 5: £1.00 + 25p P&P.

5W stereo amp, stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, general purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter...

Book 6: £1.00 + 25p P&P.

Graphic equaliser, 50/100W amp. modules, active crossover, flash trigger, "Star and Dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show...



## ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.

## electronics tomorrow 75p

A SPECIAL EDITION FROM electronics today



## TRANSDUCERS IN MEASUREMENT AND CONTROL

This book is rather an unusual reprint from the pages of ETI. The series appeared a couple of years ago in the magazine, and was so highly thought of by the University of New England that they have republished the series splendidly for use as a standard textbook. Written by Peter Sydenham, M.E., Ph.D., M.Inst.M.C., F.I.L.C.A., this publication covers practically every type of transducer and deals with equipment and techniques not covered in any other book. Enquiries from educational authorities, universities and colleges for bulk supply of this publication are welcomed: these should be addressed to H. W. Moorshead, Editor.

£3.00 + 25p P&P.

## ETI CIRCUITS

Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.

## ELECTRONICS — IT'S EASY Books 1, 2 & 3.

Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics.



## ORDER FROM

Specials  
Modmags Ltd  
25-27 Oxford Street  
London W1R 1RF

Postage and packing also refers to overseas. Send remittance in Sterling only.

Please mark the back of your cheque pr PO with your name and address.

FROM THE PUBLISHERS OF  
ELECTRONICS TODAY INTERNATIONAL


## ETI CIRCUITS No 2

£1.50

£1.20 + 25p P&P each.

# from ETI

# Short Circuits

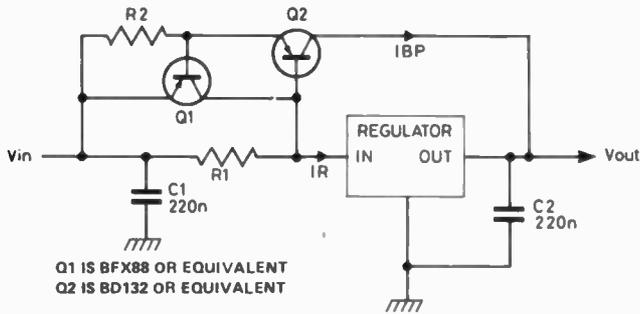

## REGULATOR BOOSTER

diagram) which will limit the current through the power handling one to protect it during a short circuit of the output. During a short circuit, the regulator will presumably look after itself.

The operation of the circuit is fairly simple. As soon as the voltage drop across R1 is greater than the minimum bias voltage for Q2 (0V6), Q2 will turn on. As R1 is a 1 ohm resistor, this will occur when 0.6A is passing into the regulator. Having switched on, Q2 will supply current directly to the load. The regulator will sense its output voltage and if (as is likely, since the current through Q2 will be un-regulated) the output voltage

is now not what it should be it will pass or hold back current as required and so the output will be stable and set at the regulator's output voltage. The two capacitors are necessary to prevent the whole thing from going into a frantic oscillation as the regulator and Q2 try to decide who is doing what.

If the current through R2 rises above that needed to provide a 0V6 drop across it, Q1 will switch on and short out R1, thus removing the bias from Q2. This will prevent Q2 from passing more current than is good for it. Q2 should be mounted on a heat sink to prevent it from glowing red hot.

If you've ever been in the unfortunate position of having a regulator in a piece of equipment which will supply, say, 0.5 A and you find that, for one reason or another, the equipment needs to draw 2A then this little circuit may save the day.

Essentially, it consists of a transistor which will switch on at a certain current flow into the

regulator and bypass it to an extent. In its operation it is similar to a 'current dumping' amplifier. The transistor will pass a large amount of current without regulating it and the regulator will do all the fine tuning to make sure the output is stable. The circuit also includes a second transistor (called Q1 here because it appears at the left of the

## LIGHT SENSITIVE SWITCH

The controlling factor for this whole circuit is the light dependent resistor LDR1 type ORP12. This has the property of having a very high resistance in complete darkness (over 1MO) but in the brightest light this falls to nearly 300R (although individual devices vary greatly).

At first sight it would seem possible to use the ORP12 only, to control the circuit but this has several disadvantages including the fact that the current passed through the device must be kept low.

For simplicity the circuit will be described for 'dark on' using a directly lit LDR.

When daylight is falling on the ORP12 the resistance is fairly low — the actual value is not important but it will probably be in the range of 300R to 3K $\Omega$ . With R1 the two components form a potential divider with the base of Q1 connected to the junction. If the resistance of the ORP12 was high the voltage at the junction would be low but since we are discussing the circuit with the voltage at a reasonable level Q1 is biased on — that is, it is in a conducting state. In this condition the voltage across the transistor is small and since Q2's bias depends upon this voltage, it is therefore held off and

following the chain of R5 and R6 it will be seen that the base of Q3 is connected to the positive supply, and is therefore non-conducting.

As the light level falling on the ORP12 gets less and less, the voltage at Q1 base falls, until it reaches such a level that Q1 tends to conduct less. As the current through Q1 falls, the voltage drop across it increases, and this starts to bias Q2 into conduction.

As Q1 and Q2 share the same emitter resistor there is a regenerative action. Q2, by becoming conductive, raises the voltage on the transistor side of R4 and since the base voltage on Q1 is still at the same level this biases Q1 even more into non-conduction.

The switching action is extremely rapid once it has started and the overall effect is that although the voltage at the base of Q1 is only changing gradually and

slowly, Q2 is switched completely on at a certain point, and Q1 is switched off.

The circuit configuration just described is known as a Schmitt trigger and has a number of applications in several fields of electronic switches.

When Q2 is switched on, the voltage at the collector falls and Q3 is biased into full condition through R6. With Q3 on, current is passed through the buzzer.

A relay can be used in place of the buzzer — its coil resistance hardly matters and does not upset circuit conditions. However, relay coils, when used with transistors, should always be by-passed with a diode. The reason for this is that when the relay is switched off a back voltage of very high level is created which can destroy the controlling transistor. The diode, however, safely shunts this to the


negative line and so protects Q3.

A 'dark off' (or 'light on') circuit can be made by reversing the ORP12 and R1 — which now becomes 33k. In this condition Q1 is on but as the light level increases the voltage at the base of Q1 falls and the same action applies as before.

R1 in both versions of the circuit can be replaced by a variable resistor, and this enables the light level at which the circuit triggers to be varied.

Note that Q1 and Q2 are silicon N-P-N types whereas Q3 is a germanium P-N-P type. Q3 passes quite a large amount of current and can be destroyed unless a heat sink is used — one of the fin types which clip over the body should be adequate.

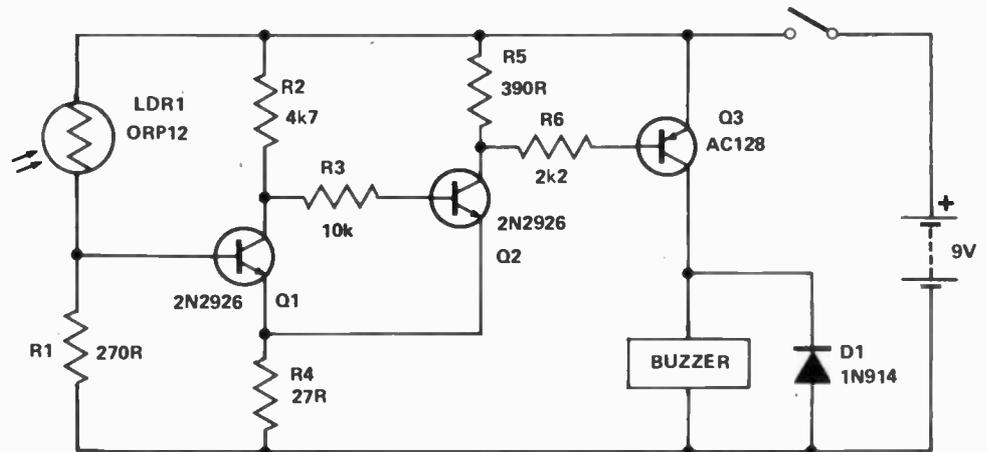When Q3 is off the current consumption is very low — about 4mA and this will be little drain on a battery.



# Into Electronics


by Ian Sinclair

Part 2

***In this second part of our major series which covers electronics along the O/A level syllabus we look at passive components and how they behave in electronics circuits. Block diagrams are also explained.***

IN A COMPLETE circuit, DC current in the form of moving electrons can flow around the circuit, pushed by the EMF (electro-motive force). If the current is AC, the electrons never flow right round the circuit, but only dance to and fro, moving in one direction when one end of the circuit is positive, and in the other direction when the EMF reverses. As we've seen, it doesn't matter to a resistor whether the electrons move steadily or to-and-fro, the power is converted into heat anyway. For some other components though it matters a lot. For example, a moving-coil meter simply cannot cope. The coil and needle cannot reverse direction more than a few times per second, so that for AC of 10Hz or more, the reading is effectively shown as zero.

Other components behave differently think of a circuit with a break in it. Because electrons won't move across the gap, there is no steady current. When the EMF is alternating, there is still some movement of electrons in the rest of the circuit. With the EMF in one direction one end of the gap is positive, the other end negative. When the EMF reverses, the polarity across the gap must also reverse.

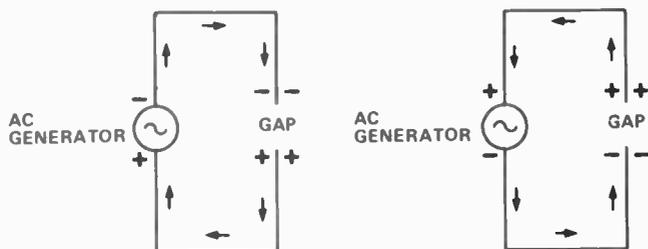

**Fig. 1.** An alternating EMF will cause a to-and-fro movement of electrons even if there is a break in the circuit. Each time the EMF reverses, electrons must move along the wires as far as the break.

Now for this to happen, some electrons have to move. For one end of the gap to be positive and the other end negative, electrons have had to move from the positive end to the negative end (remember that the electron is negatively charged). When the voltage reverses, the electrons have to shuffle around in the

opposite direction. Even with a gap in the circuit, then, there can be some to-and-fro movement of electrons, the type of current we call alternating current.

You could call a capacitor a carefully designed gap in a circuit. Like any other gap in a circuit, a capacitor does not allow steady current to flow, but it will allow electrons to accumulate on one side and drain on the other side of the gap. The first capacitors were made in the shape of jars (because it was thought that electricity was a liquid!) with gold leaf on the inside and also (but not electrically connected) on the outside. Later, metal plates separated by an insulator (known as the **dielectric**) were used. Nowadays, we use paper or plastic insulators coated with metal film each side but we still talk of "plates", and the symbol for a capacitor (Fig. 2) shows two plates separated by a gap.



**Fig. 2.** Symbol for a capacitor. This symbol is used for a fixed capacitor, meaning a capacitor whose value is not deliberately changed (as for tuning a radio). A slightly different symbol is used for an electrolytic capacitor.

It's not so simple as a gap in the circuit, though. The greater the area of these plates, and the closer they are to each other, the greater the number of electrons that have to be shifted from one side to the other to create a voltage across the plates. Even the type of material that lies between the plates can affect this number of electrons. In electronics language (parliamo elettronico?) a lot of charge has to be shifted to get a voltage across the plates. The ratio

$$\frac{\text{amount of charge}}{\text{amount of voltage}}$$


is called **capacitance** and is measured in units called **farads** (abbreviated F). A large amount of capacitance means that a lot of charge has to move to give one volt between the plates, a small capacitance means that only a small amount of charge needs to move to obtain the same one volt between the plates of this device called a capacitor.

We boobed a bit with the unit, though. Using the definition

$$\text{capacitance} = \frac{\text{charge}}{\text{voltage}}$$

and using the units of coulombs for charge (the coulomb is the amount of charge that moves when one ampere flows for one second) and volts for voltage, the unit of capacitance, the farad, is the coulomb per volt, and it's miles too big for practical purposes. We have to make use of the sub-multiples micro-, nano- and pico- when we work with capacitors, so that values such as 10 $\mu$ F, 2.2nF (written as 2n2) and 100pF are the sort of values we are likely to see and use.

The way we make capacitors depends on the sort of values we need. For the smallest pF (picofarad) sizes, we can use small discs or rectangles of insulators, such as silver-mica, coat each side with metal, then make contacts to the two separate metal layers. For larger values, a few nF perhaps, we can pile these plates on top of each other, separated by uncoated plates for insulation, and connect alternate sides together (Fig. 3b).

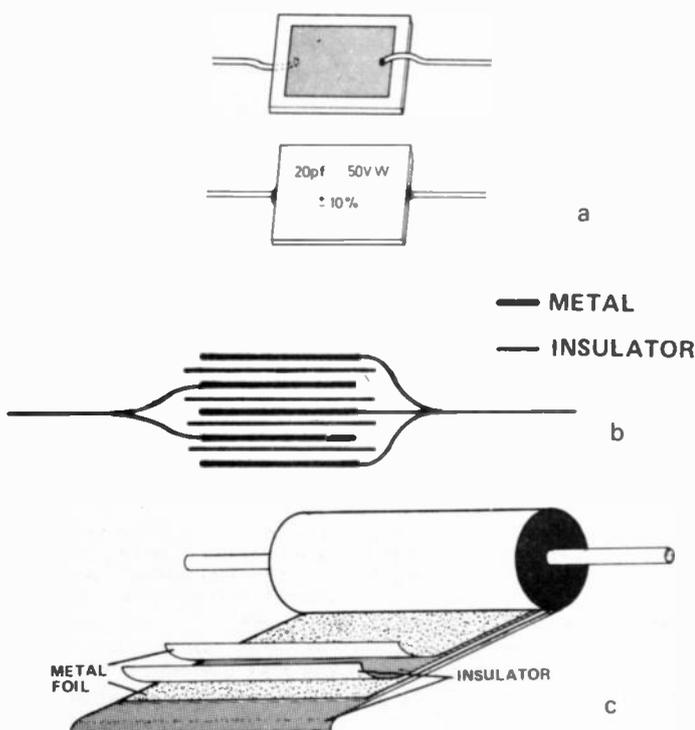


**Fig. 3.** Some practical methods of construction. a) Single metallised plate. b) Multiple plates — showing plates separated, with interconnections, before pressing together and covering with plastic coating. c) Rolled paper or plastic construction.

When we get to values of 10nF or more, an easier construction is to use a ribbon of paper or plastic, metallise each side, then roll the ribbon up along with an unmetallised ribbon to make sure that the metal surfaces do not touch; this gives the tubular capacitor. For values of 1 $\mu$ F upward, even this construction is too bulky, and electrolytic capacitors, constructed like dry cells, are used. The insulator here is a thin film of hydrogen gas, so thin that it will be damaged by having too great a voltage across it. Electrolytic capacitors can have very large capacitance values in a very small size, but work only at comparatively low voltages, and must be polarised.

Polarised? Yes, like a battery there's a + and a — connection to an electrolytic, and the markings must be observed, with the + lead always connected to a higher positive voltage than the — lead. Get these reversed and, at best your circuit will not work, at worst you will have the corrosive paste from inside the capacitor sprayed all over you!

## INDUCTORS AND TRANSFORMERS

If a gap in a circuit can become a circuit component for AC signals, what else is in store? Watch this space for the curly wire trick. Take a length of wire, connect it up in a DC circuit, find its resistance. A few ohms, perhaps? Fine, now coil the wire up, and find the resistance. Just the same, you find. Do all this with an AC circuit, working at high frequency, and you find that coiling the wire up has a very great effect on the current, just as if the resistance had increased.

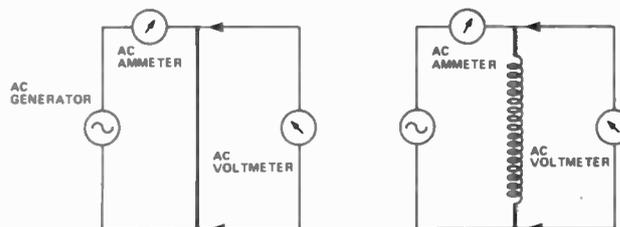

**Fig. 4.** The curly-wire trick a) In an AC circuit a straight wire with low resistance has only a small voltage across it. b) Coiling the wire has the effect of making it behave like a higher resistance, so that the voltage across the wire is greater. This would be noticeable only when the supply frequency was fairly high.

It's no mystery, really. Coiling the wire up makes it an electromagnet when a current flows, and when the current reverses, the direction of the magnetism has to reverse also. It needs a bit of energy to do this though, so that passing an alternating current through such a coil, called an **inductor**, is not so easy as passing the same current through a straight wire or passing DC through the coil. The size of this effect is measured by a quantity called **inductance**, measured in units called **henries** (Mr Henry was an American physicist who died in 1878). As usual, we make use of submultiples like millihenries (mH) and microhenries ( $\mu$ H), though it is possible to make coils of several henries of inductance.


Because inductance is caused by magnetism, winding a coil of wire around a magnetic material, such as soft iron, makes the amount of inductance very much greater than that of the coil alone. Materials like soft iron concentrate magnetism, and it's this effect, called **permeability**, that makes a coil with an iron core have so much more inductance than a similar coil with an air core. For two similar coils, the addition of a magnetic core can make the inductance value many *thousands* of times greater.

Iron cores are less useful, though, when the currents through the wire in a coil are high-frequency signals, because then too much energy is wasted in magnetising and demagnetising the iron. Inductors intended for use with high frequency signals must use air cores or special materials called ferrites.

That's not the end of the tricks we can play with coils, though. Suppose we wind two separate coils, insulated

from each other, on to the same magnetic core. Connect one coil to an AC circuit and pass AC current through the coil. This will magnetise the core, but the magnetism will be alternating, changing direction as the current changes direction. Now for the crunch — the alternating magnetism will generate alternating EMF in the other coil. We can use this other coil as if it were a generator of alternating EMF — which it is. This arrangement is called a **transformer**. The coil which is used to create the alternating magnetism is called the primary coil, and the coil which has the EMF generated in it is called the secondary coil.

The reason for the name, transformer, is that the voltage that comes out of the secondary coil isn't necessarily the same as the voltage across the primary coil. We put an alternating voltage, a sine wave, across the primary winding, and we get an alternating voltage, a sine wave with the same frequency from the secondary winding, but the voltages don't have to be the same. In fact the voltage at the secondary depends on the number of turns in each of the two coils as well as on the primary voltage. The law of the transformer is  $V_s/V_p = n_s/n_p$ ; where  $n_s$  is the number of secondary turns,  $n_p$  is the number of primary turns,  $V_s$  is the secondary voltage,  $V_p$  is the primary voltage.

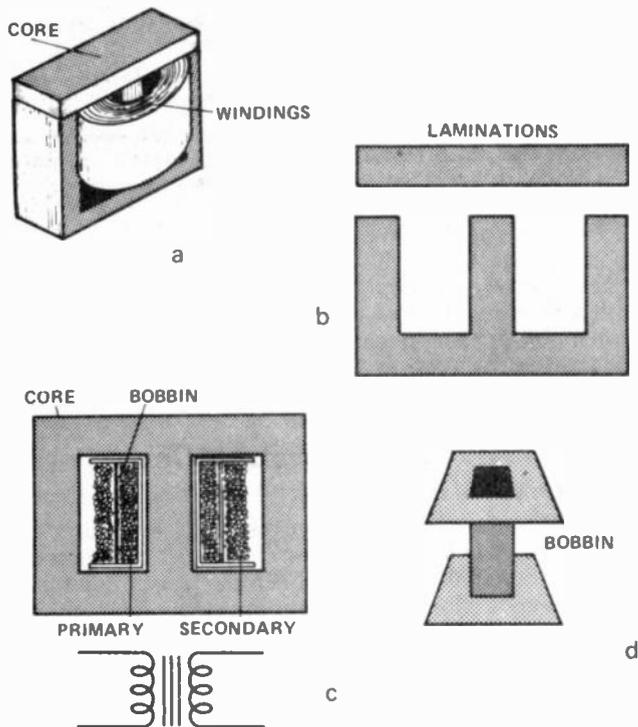

**Fig. 5. The transformer. a) General appearance, b) Core and bobbin, c) Sectioned view, d) Symbol.**


For example, if we have a transformer with 5 000 turns of wire for a primary winding, and a 250V AC supply, what voltage can we expect across a 500 turn secondary winding? The equation is  $V_s/V_p = n_s/n_p$ , and filling in values we get  $V_s/250 = 500/5\ 000$ ; so that  $V_s = 25V$ .

This we would call a **step-down** transformer, because the secondary voltage is less than the primary voltage. We could just as easily make the secondary winding have a greater number of turns, so that the transformer is a **step-up** transformer.

None of this happens when DC is used. Slap some DC through a transformer and all you get is a hot transformer, a smell of burning and a few blown fuses. DC will magnetise the iron core all right, but it won't cause the alternating magnetism that makes the thing work. Worse still, because the resistance of the wire used for transformer windings is low, far too much current will flow through the wire if DC is used. Transformers are strictly AC devices.

## JOINING THEM UP

In a circuit, components like resistors, capacitors and inductors can be connected together. Before we look at what happens in such circuits, let's see what the effect is of joining similar components together. There are two ways of connecting components, in series and in parallel. In a series circuit, the same current flows through the components, one after the other. In a parallel circuit, the same voltage is across each component, though the currents can be different.

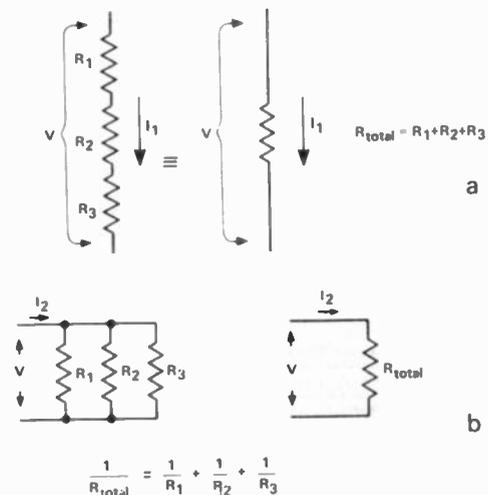

**Fig. 6. Resistor circuit connections. a) In series. Total resistance means the resistance value which would have the same voltage across its terminals for the same amount of current passing through it. b) In parallel. Using the same definition of total resistance leads to the formula shown.**


Connecting resistors in series has the effect of increasing the total resistance, as we might expect. Formula  $R_{total} = R_1 + R_2 + R_3 \dots$  for as many resistors as we have connected in one series circuit with the same current flowing. For example, a 6k8 resistor in series with a 2k2 resistor gives a total of  $6.8 + 2.2 = 9k$ . This is a value we can't obtain in the usual 10% series and this is one use of series connections. A more valuable application is the potential divider shown in Part 1 of this series.

Connecting resistors in parallel makes the flow of current easier because there are several paths for current now. Formally,  $1/R_{total} = 1/R_1 + 1/R_2 + 1/R_3$  for as many resistors as are connected in parallel across the same voltage. For example, a 30R resistor connected in parallel with a 20R will give

$$1/R_{total} = 1/20 + 1/30 = 5/60$$

$$\text{so that } R_{total} = 60/5 = 12R.$$

This is the value of the resistor which could replace the 20R and 30R in parallel. Note that two identical resistors in parallel produce a total resistance equal to half the value of each resistor, three in parallel are equivalent to a resistor of one third of each resistor value and so on; for example, three 3k3 resistors in parallel give 1k1. Parallel connections are very useful for reducing or trimming resistance values down to the size we want. For example, if we want to use 6k and we have 6k8, we must add a resistance R so that  $1/6 = 1/6.8 + 1/R$ . Producing the old calculator and going through the steps we find  $R = 51k$ . (The nearest preferred value is 47k.)

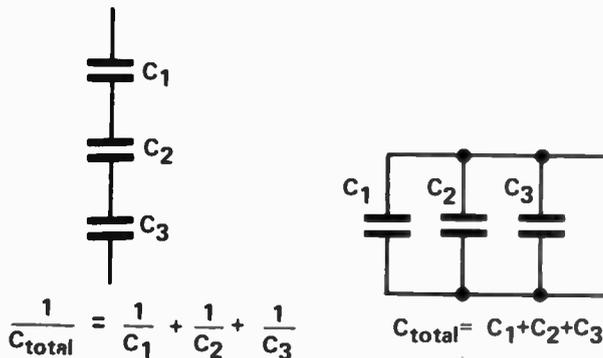

**Fig. 7. Capacitor connections** — the same formulae apply, but they apply to the opposite connections. The simple addition formula applies to parallel capacitors, the inverse formula to the series connection.

Inductors obey the same laws — adding the value for series connections, and using the reciprocal rule for inductors in parallel. Capacitors, just to be awkward combine the other way round. Connecting capacitors in parallel is like adding their plate areas, so creating a larger capacitance. For capacitors in parallel


$$C_{\text{total}} = C_1 + C_2 + C_3 \dots$$

Capacitors in series behave like resistors in parallel, so that

$$1/C_{\text{total}} = 1/C_1 + 1/C_2 + 1/C_3 \dots$$

## TIME CONSTANTS

All a resistor can do is to dissipate power, converting it to heat. Capacitors and inductors can store energy and give the stored energy back again, but both need some time to act. The thing to remember is that we can't *instantly* change either (a) the voltage across a capacitor or (b) the current through an inductor. Take for example, the capacitor and resistor in Fig. 8. Switching on causes the voltage of plate (1) of the capacitor to rise from 0 to +9V. Because of the instant change rule, the voltage of the other plate (2) is also 9V at switch-on. It can't stay at the voltage, though, because current will now flow through the resistor — this is the movement of charge that is needed to charge the capacitor. When the charge has stopped moving, plate (2) voltage is zero and the capacitor is fully charged. The time constant for this arrangement is given by  $C$  (in farads)  $\times R$  (in ohms), result in seconds. Because of the shape of the graph of

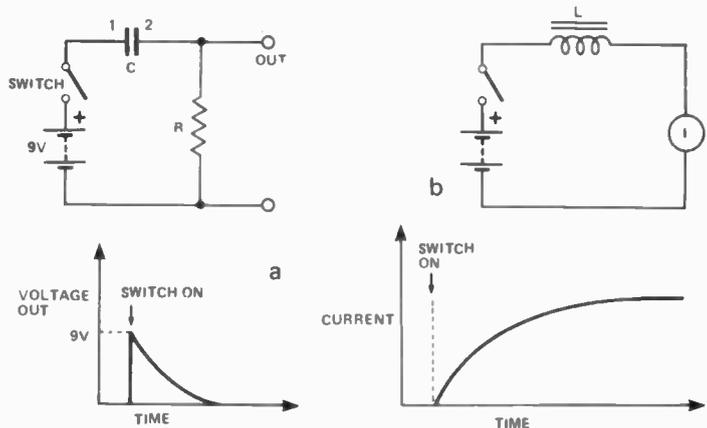

**Fig. 8. Time constants.** a) A capacitor and a resistor connected together have a natural time constant equal to  $CR$  seconds. In the graph of voltage against time that is shown here, the time constant is the time after switch on for the voltage to reach 37% of the battery voltage. b) An inductor has resistance  $R$  (because of the wire it's made from), and its time constant is  $L/R$ . The time constant of an inductor causes a delay in reaching a steady value of current when a voltage is applied across the capacitor. The time constant in this circuit is equal to the time taken, after switch on, to reach 63% of the final current.

voltage plotted against time, the figure of time constant is not the time for the voltage to reach zero but to fall to 37% of its starting value. In this example, the time constant is the time taken for the voltage to reach 37% of 9V, which is 3.3V. The point is that the greater the value of this time constant (great capacitance, greater resistance, or both) the longer it takes for charging to be complete.

The same applies to current in an inductor. Switching on a voltage across a large inductor does not cause instant current. Instead, the current grows gradually with a time constant of  $L/R$  seconds. ( $L$  in henries,  $R$  in ohms). In this case, because current is growing, the time constant is the time to reach 63% of the final current (which is  $V/R$  amps).

## REACTANCE, IMPEDANCE, RESONANCE

In an AC circuit we can have resistors, inductors and capacitors. Any circuit that has capacitors connected in series with the other components must be a circuit for AC only, because capacitors do not pass steady current. Any inductors in a DC circuit will act only as resistors, their inductance has no effect once the current has settled down to its final value. For an AC circuit, however, both capacitors and inductors pass current and will have alternating voltages across them. For a capacitor or inductor, the ratio  $V/I$  meaning the ratio of signal voltage to signal current, is called the **reactance** of the capacitor or inductor, symbol  $X$ , and is measured in ohms. It's measured in ohms because resistance is the ratio of  $V/I$ , using DC values that also result in the unit, ohm.

Why use a different name for these 'AC' ohms? Well, for a start, DC doesn't flow through a capacitor at all, and the resistance of an inductor is only the resistance of the wire it's made from. For an encore, there's another big difference. When an alternating current flows through a resistor, there is, of course, an alternating voltage across the resistor. This voltage is exactly in step with the

# Hobby Electronics

# Marketplace



An example of this watch can be seen and examined at our Oxford Street offices.

## £7.95

(Inclusive of V.A.T. and Postage)

If someone sidled up to you in a pub and offered you a watch like this for eight quid, most people would assume that it was stolen. Well, we can assure you that these are not! This is an LCD watch with style. It has an extra large display and widely-spaced easy-to-use pushbuttons. The case is gilt and comes complete with a matching strap. A very smart watch indeed.

Also, of course, it has the phenomenal accuracy of all truly modern watches — seconds per month. It also keeps track of the date (taking into account long and short months). Naturally, like all high quality LCD watches, it has a backlight. It's guaranteed fully for a year and comes complete with a 12-month battery.

No, this watch isn't stolen — and at seven pounds ninety-five why buy a stolen one?

If you're starting out in electronics — and that is what Hobby Electronics is about — then one of the first things you'll need is a soldering iron. Without one, all you can do is read about it. Having spent £2.35 on this iron, your next one will probably cost you a lot more. The next step up from a good, general purpose soldering iron is an all-singing, all-dancing temperature controlled iron with matching stand. In our experience, there is little in-between — this iron will last you for quite a while.

There's nothing clever about this product — it's made in Britain and offered to HE readers at a low cost. It's guaranteed for three months and comes in two versions — 240V for mains operation and 12V for car battery use.

If you want the 12V version, mark the coupon in some way in its lower right hand corner (an X will be fine). If there is no mark on the coupon, we will send you the 240V version.

Please include with your order a self-addressed label which we can attach to your soldering iron package to ensure that it reaches you quickly.

CBM WATCH

**TO:**  
**CBM Watch Offer**  
**Hobby Electronics**  
**25-27 Oxford Street**  
**LONDON W1R 1RF**

Please find enclosed my cheque/P.O. for £7.95 (payable to Hobby Electronics) for my CBM Giant Display Watch.

Name .....

Address .....

Please allow 14 days for delivery

SOLDERING IRON

**TO:**  
**Hobby Electronics Soldering Iron Offer**  
**86-88 Union Street**  
**Plymouth PL1 3UG**

Please find enclosed my cheque/P.O. for £2.35 (payable to S&R Brewster Ltd.) for my soldering iron

Name .....

Address .....

Please allow 14 days for delivery

MARK HERE FOR 12V VERSION

An example of this soldering iron can be seen and examined at our Oxford Street offices

## £2.35

(Inclusive of V.A.T. and Postage)



# Hobby Electronics

# Marketplace



**Size: 100mm x 130mm x 60mm.**

Over 10% of Electronics Today International's readers have purchased a digital alarm clock from offers in that magazine — the offer is now extended to Hobby Electronics readers. This is a first rate branded product at a price we don't think can be beaten.


The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking switch' is provided under the clock. A 9-minute 'snooze' switch is located at the top.

**An example of this digital alarm clock can be seen and examined at our Oxford Street offices.**

## £8.95

(Inclusive of VAT and Postage)

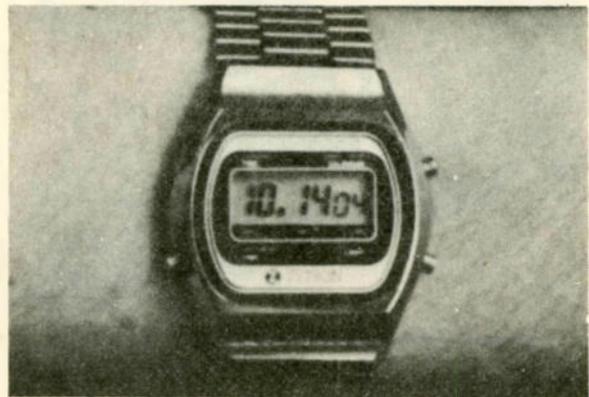

We feel we've got to tell you carefully about this offer which we're introducing for the first time. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The exact same watch is currently being offered by another magazine as a special at £24.95 — some of the discounters are selling it at £29.95 — the price to HE readers for exactly the same watch is £12.95.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

**An example of this LCD Chronograph can be seen and examined at our Oxford Street offices.**

## £12.95

(Inclusive of VAT and Postage)

**To:  
DIGITAL Alarm Offer,  
Hobby Electronics,  
25-27 Oxford Street,  
London W1R 1RF.**

Please find enclosed my cheque/P.O. for £8.95 (payable to Hobby Electronics) for my Digital Alarm Clock.

Name .....

Address .....

Please allow 14 days for delivery.

**DIGITAL ALARM**

**To:  
LCD Chrono Offer,  
Hobby Electronics,  
25-27 Oxford Street, London W1R 1RF.**


Please find enclosed my cheque/P.O. for £12.95 (payable to Hobby Electronics) for my LCD Chronograph.

Name .....

Address .....

Please allow 14 days for delivery.


**LCD CHRONO**

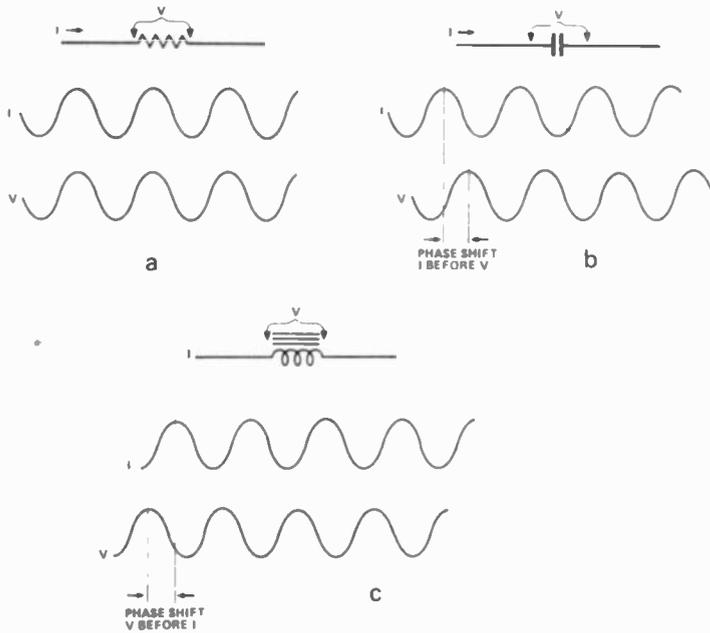

**Fig. 9. Phase shift.** a) When alternating current passes through a resistor, the waves of voltage and of current are in step. b) When AC is applied to a capacitor, the current wave is a quarter cycle (90°) before the voltage wave. c) When AC passes through an inductor, the current wave is a quarter cycle (90°) after the voltage wave.

current — when the current is zero, the voltage is zero, when the current is at its positive peak, the voltage is at its positive peak, and so on. Reactances don't behave like this. Instead, the voltage wave is shifted compared to the current wave, so that we have maximum voltage when the current is zero and zero voltage when the current is maximum. This effect is called a 90° phase shift. The reason for the 90° label is that the shift is one quarter of a cycle, and an alternator generates one cycle of AC by 360° of rotation, hence a quarter cycle is 90°.

Capacitors cause the voltage peak to be a quarter cycle later than the current peak; inductors cause the current peak to be a quarter cycle later than the voltage peak. One simple way to remember which way round it is is the word **C-I-V-I-L** C (for capacitor), I before V; V before I in L (inductor).

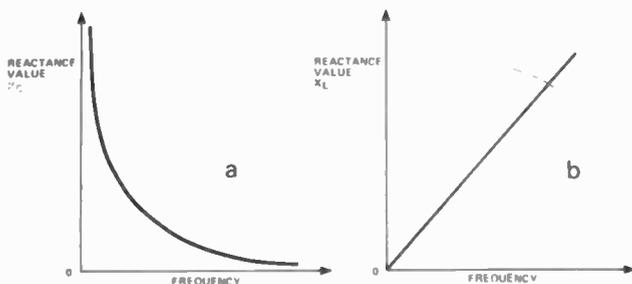

**Fig. 10. Reactance is not constant.** a) The reactance of a capacitor is very high for low-frequency signals, very low for high frequency signals. b) The reactance of an inductor is very low for low-frequency signals, very high for high-frequency signals.

The most noticeable difference between reactance and resistance, though, becomes obvious when we change the frequency of the AC supply. Inductors have more reactance at high frequencies than at low frequencies.

Capacitors have less reactance at high frequencies than at low frequencies. Graphs showing reactance size plotted against frequency look as shown in Fig. 10. For an inductor, the size of reactance is given by  $X_L = 6.3 \times f \times L$ , with  $f$  in hertz,  $L$  in henries.

For exple, a 0.1 H inductor at a frequency of 400 Hz has a reactance of 252 ohms.

For a capacitor, the size of reactance is given by

$$X_c = \frac{1}{6.3 \times f \times C}$$

Now we have to be careful here.  $C$  has to be in units of farads, and we usually use microfarads or smaller units. For example, the reactance of a 0.1  $\mu$ F capacitor at 5 kHz is:


$$X_c = \frac{1}{6.3 \times 5000 \times 0.1 \times 10^{-6}} = 317 \text{ ohms}$$

Because reactance is different in value at each different frequency, we have to calculate the amount of reactance from the fixed values of inductance or capacitance.

When a circuit contains a resistance and a reactance, the whole circuit is neither perfectly resistive nor perfectly reactive, but a mixture of the two is called **impedance**, symbol  $Z$ . The simple laws for adding series or parallel components don't apply to reactances because of the phase shift, and the phase shift of an impedance is somewhere between 0° and 90°.

One type of impedance is rather special. When a circuit contains a resistor, a capacitor and an inductor all in series, or all in parallel, it doesn't behave like any other circuit we have met so far. At low frequencies, this circuit behaves like an inductor, at high frequencies, it behaves like a capacitor. At one frequency in between, called the **resonant frequency**, or frequency of resonance, the circuit behaves like a resistance. At this frequency, the reactances of the capacitor and of the inductor have balanced each other out, leaving only resistance. How much resistance?

If the capacitor and inductor are in series, making this a series resonant circuit, then the resistance at the frequency of resonance is very low, just the resistance of the wire in the inductor unless other resistance has been added. If the inductor and the capacitor have been connected in parallel, making a parallel resonant circuit, then the resistance at resonant frequency is very high,

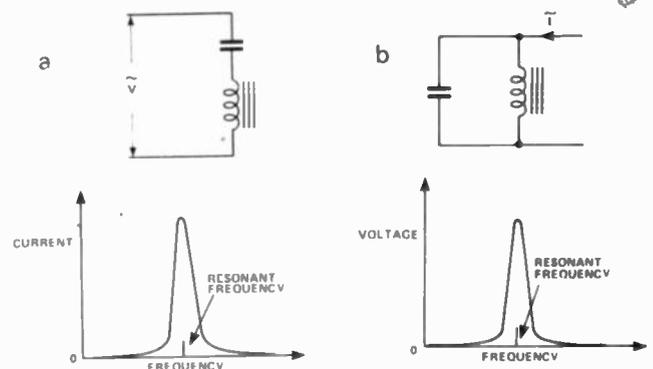


**Fig. 11. Resonance.** a) Series-resonant circuit; the resistance in the circuit is the resistance of the wire of the inductor. The current is maximum at the resonant frequency, when the circuit has only resistance, no reactance. b) Parallel-resonant circuit. The voltage (and the resistance) is a maximum at the resonant frequency.

unless other resistances have been added in parallel. The effect is shown in Fig. 11. We use resonant circuits for tuning a frequency we want. If a parallel resonant circuit is used as a load, then a signal current will produce a large voltage across the load, but only at and around the frequency of resonance. Radio wave tuning, whether of radio, TV or radar signals depends on this resonance effect which lets us select the frequency we want from all the possible frequencies which can be picked up or generated.


## BLOCK DIAGRAMS

A block diagram of an electronic system shows us what is done to a signal, without any detail of how it is done. A block diagram of a car would show an outline of an engine, a gearbox, a clutch and the final drive, but without any details of what happens inside these components. Block diagrams are useful because they show us what to look for in a detailed circuit.

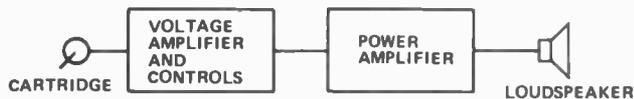

**Fig. 12. Block diagram of a record player. The cartridge converts vibration of the stylus into an electrical signal, which is amplified and used to drive the loudspeaker.**

For example, Fig. 12 shows a block diagram of a simple record player. The cartridge is the transducer that converts the squiggles on the disc into electrical waves. These are then amplified, the amount of amplification is controlled, and the amplified signal used to drive another transducer, the loudspeaker.

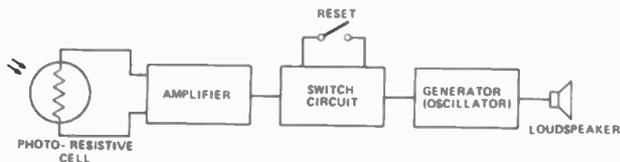

**Fig. 13. Block diagram of a light-operated alarm. Light falling on the photocell causes a signal which is amplified and operates the electronic switch. This in turn switches on the oscillator, and so sounds an alarm from the loudspeaker. The alarm sounds until reset by a switch.**

Taking another example, Fig. 13 shows an alarm which sounds when a light beam hits a photocell. The light falling on the cell causes a signal which is amplified and used to switch on an audio generator, which in turn causes a sound from a loudspeaker. The actual circuit for this would take much longer to understand. Block diagrams are particularly useful for very complex electronic systems such as TV, radar or computers.

## CIRCUIT DIAGRAMS AND SYMBOLS

If we are to be able to build electronics circuits (and that's what we're here for), we need to be able to read and understand circuit diagrams. Why not use photographs and sketches of a finished circuit? Well, it's much more difficult, to start with. Photographs and drawings

are useful only if your components look identical to the ones in the photo, and if you want to copy exactly the layout in the photo. If you can read circuit diagrams, you can use any shape of components, and make your circuits as you want them. It's like the difference between building from a kit and rolling your own.

Circuit diagrams use symbols for each component, and some of the most common symbols are shown in Table 1. Notice the way arrows are used. For components like resistors, capacitors and inductors, arrows are used to mean a variable quantity (a variable resistor or potentiometer, variable capacitors, variable inductors) which can be adjusted. A different symbol is used for preset values that are set to some value and then left alone. An arrowhead used with components such as diodes and transistors shows the normal (+ to -) direction of current flow.

A circuit diagram shows what components are connected together, *not* how they are arranged. A circuit may show a line, representing a connection, joining a battery + pole to one end of a resistor. In the practical layout of the circuit, these components might be near each other or several centimetres apart, but they must be joined by wires or metal strips. The great advantage of a circuit diagram is that it shows the action of each component in a circuit, no matter where it happens to be placed physically. Trying to figure out the action of a circuit by looking at its arrangement on a board is nobody's idea of good clean fun!

In many circuit diagrams the symbol for an earth or ground connection is shown and this sometimes puzzles beginners. It's a hangover from the old days of telegraphs. At first, the electric telegraph used two lines connecting transmitter and receiver. The pioneers then found that they could use one wire line, with the return current flowing through the earth itself, and to do this, the return was taken to a large metal plate buried in the ground. From then on, it's been earth in the U.K. and ground in the U.S.A. and ever shall be.

Nowadays, mains operated circuits use an earth connection for safety, so that any mains voltage fault will cause a large current through the earth connection (rather than through you) so blowing the fuses.

In battery powered equipment, the earth or ground connection may simply be to any metalwork, such as a case. This ensures that the case is at the same voltage as the signal zero voltage line, usually battery negative. The purpose of this is to make sure that the metalwork does not cause interference by radiating signals into or out of the circuit. For many circuits an earth connection is not needed at all, but the earth symbol is sometimes still used on circuit diagrams to show which line of connections is at zero signal voltage.

## PRACTICAL CIRCUIT CONSTRUCTION

Laying out a circuit from a circuit diagram is one of the most satisfying parts of electronics, and yet is seldom taught. In the old days of valves, laying out a circuit used to be a metal bashing exercise which had the constructor pretty cheesed off with the circuit before any wires had been soldered, but modern components and circuit boards have made the whole process so much easier.

Start by looking at the circuit and finding the circuit junctions. A circuit junction is where wires from various

# Into Electronics

	<p>Three types of diode. The first is just a diode, the second is a light emitting diode (which glows when current passes through it). The third is a zener diode, used for creating fixed voltages.</p>		<p>A resistor.</p>		<p>Two wires crossing on a diagram without touching.</p>
	<p>Two types of capacitor. The lower one is of the "electrolytic" or "tantalum" type and can only be used one way round.</p>		<p>A coil. The lines indicate what it was wound on. Two coils which share the same lines represent a transformer.</p>		<p>Earth symbol. Usually means battery negative terminal or chassis.</p>
	<p>Two types of transistor. The first is NPN, the second PNP.</p>		<p>Various forms of variable resistor. The top one is panel mounting, the dot representing the right-hand side when viewed from the front. The other two are pre-set resistors which are used for setting up only. The middle one has its sliding contact connected to one end of the resistive "track."</p>		<p>Two different types of switch. The upper one is only closed while it is held closed.</p>
	<p>Integrated circuits. The box can be of almost any shape, although the top one is usually used to indicate some form of amplifier. The numbers refer to the pin numbers on the IC package.</p>		<p>A loudspeaker.</p>		<p>A fuse.</p>
	<p>Logic gates. Logic ICs usually contain several of these each, and so they are suffixed IC1a, IC14b, et cetera.</p>		<p>A battery. The short terminal is negative (easy to remember it looks like a "—").</p>		<p>A "jack" socket and a "phono" socket.</p>

**Table 1. Commonly-used circuit symbols.**

components are all joined together. For example, Fig. 14 shows a piece of circuit with five junction points. At 1 the battery connects to R1. At junction 2 the input signal (from a socket) connects to C1. At 3, components C1, R1, R2, R3 are all connected together and at 4 the output socket joins to R3 and C2. 5 is the junction at which battery negative connects to C2 and R2. Each of the components in this circuit has two leads, and these two leads must be taken to different junctions. Later we shall be using components with three leads (such as transistors) but the same rules apply, the three different leads on each component must go to three different junctions.


Why should we disfigure our circuit diagrams with these pencilled loops? Well, the reason is that it makes circuit construction simple, electronics by numbers! Practically all circuits nowadays are built on insulating boards which have copper strips laid on them. Each of these copper strips can be used as a junction, with the wire leads of components soldered to the strips. Some types of boards use perforated copper strips, with component lead-out wires fed from the plain side through the holes to the copper side and soldered. Another type of board uses plain undrilled, ready-soldered strips, and the component lead-out wires are soldered directly in place. Whatever type is used one strip represents one circuit junction (the strip can of course be broken to form two or more).

Using our example again we take a circuit board, and make strips with numbers, 1, 2, 3, 4, 5. All we need to do now is to connect the leads of each component across the strips shown in the circuit diagram. For example, R1 is connected between strip 1 and strip 3, R2 is connected between strip 3 and strip 5, C2 is connected between strip 4 and strip 5 and so on. One type of board even has the strips already numbered for you! Couldn't be easier! The only thing to watch is that if you use the drilled type of copper strip board, you must have the strips numbered on *each* side. The reason is that a line of holes looks pretty much the same as any other line of


holes, and it's easy to mistake one for another if they are unmarked. The undrilled type of board is already numbered and needs no other preparation.

Mastered soldering? Make sure the bit of the iron (electric 25W or less) is clean, then switch on and allow it to warm up. Place the component so that its lead is at the correct part of the track of the board. Hold the iron so that its tip touches both track and component leadout wire. Now touch this hot zone with the end of a piece of resin-cored solder and watch the solder run around the wire and onto the track. When it's smooth and before it stops smoking, take the iron away. Let it all cool before disturbing it. That's all! **Do** clean the wire and the track, keep the iron hot and clean. **Don't** snatch the iron away before the solder has flowed freely or keep it on so long that the board starts to burn.

HE

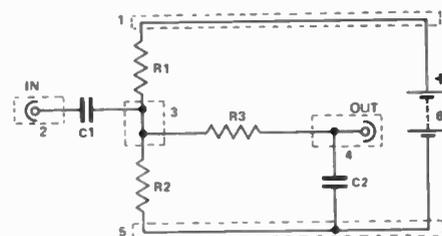

**Fig. 14. Circuit junctions. Marking out a simple circuit diagram so that it can be easily built on strip-board.**

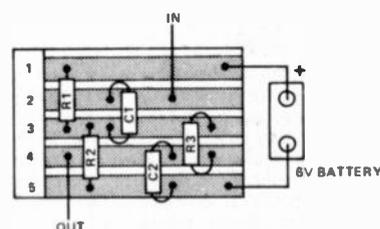


**Fig. 15. Piece of strip-board with the circuit of Fig. 14. assembled.**

# Understanding<sup>®</sup> Bias


**Tape recorder bias is a much misunderstood subject. Ron Harris shares his unbiased views . . .**

MOST USERS of tape machines, be they cassette, Elcaset or open-reel devotees are aware of the presence of the bias oscillator within their machine. In recent times they can also hardly have missed the trend to allow users to alter the bias setting for different types of tape coating.

Many more advanced cassette recorders sport switches which allow for three settings: low noise, chrome and ferrichrome. It may seem strange to have an electrical switch marked up for different materials, and it is all too common for people simply to leave that switch in the position it happened to emerge from the packing case in, and to use whatever tape comes to hand — either from the back of a passing lorry or from 'Shifty Sid's Super Discount Emporium'.

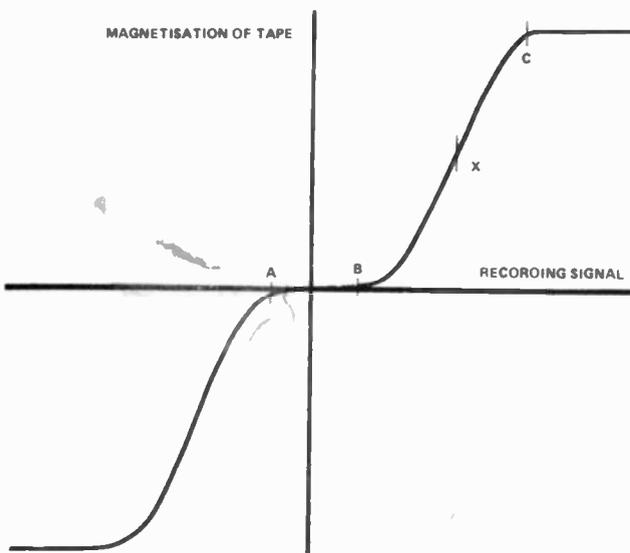

**Fig 1: Graph of tape magnetisation produced against magnetising signal flowing in the tape head. This clearly illustrates the great problem associated with tape recording — the fact that the effect is not a linear one. The section in the centre of the curve between A and B shows that over a range of small signal values, no magnetism at all is imparted to the tape. Beyond C on the curve, 'saturation' occurs — no further increase is possible regardless of changes in the signal.**

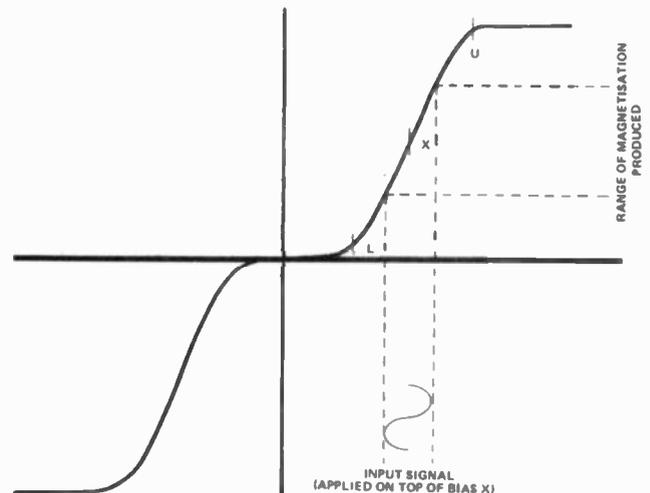

**Fig 2: DC bias. This involves adding a steady voltage to the input signal and recording them both together. As the diagram shows this effectively shifts the signal onto the useful linear section of the curve. L and U are the limits of operation for non-distorted output. Beyond these points the curve is not a straight line, and the transfer of signal to tape is a non-linear one.**

A criminal waste of potential performance, this. Tape bias is there to help the machine overcome the greatest drawback of magnetic tape as a recording medium — non-linearity.


## HEADING FOR TROUBLE

Let's start by considering what happens as the tape passes the recording head, without any thought of bias. If the signal in the record head is very small, no magnetisation at all will occur on the tape.


On the graph of figure 1, any amount of signal between A and B will produce the same effect on the tape — zero. At values of signal greater than B, the tape will retain some magnetism as it moves away — it has been recorded upon. However, if we go on increasing our value of signal up to point C, the tape refuses to

accept any more magnetisation — saturates — and different values of current will now leave the same amount of magnetisation on the tape.

All this means that only between points B and C can we hope to record a varying signal — speech, etc — on the tape: i.e., make the amount of magnetism on it follow the signal flowing in the recording head. Between these points the response is almost a straight line (ie, linear).

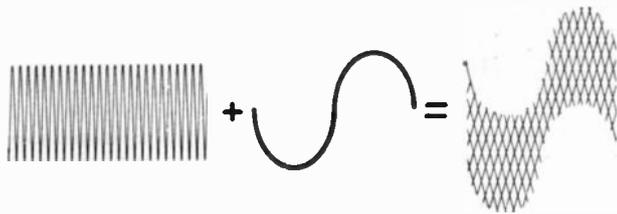

**Fig 3: Addition of the high frequency AC bias signal with the lower frequency signal. The total is used to perform the magnetisation of the tape. For best reproduction the bias frequency should be at least four times the highest frequency to be recorded as a signal. Cassette machines use around 90kHz usually.**

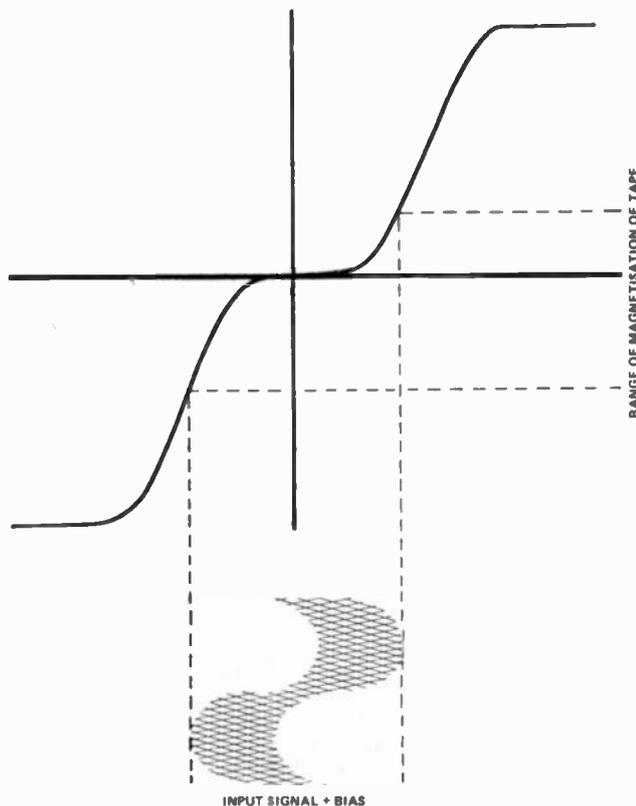

**Fig 4: Recording with AC bias. Since the bias signal used is AC it can effectively 'fill in' the flat portion of the curve, allowing the signal to make use of both linear parts of the curve and doubling the range of magnetisation possible with DC bias.**


## AC OR DC — WHO'S BIAS?

One way around this would be to never let the current in the head fall to zero, so that the portion of the graph between A and B is never used. This means putting a current through it constantly to make the lowest value, say, X on the graph. Doing this is called *biassing*.

An incoming signal would then be added to the constant flow, so that the signal varies about the value X. The disadvantages of this are that the signal is limited to values which produce magnetisation between values L and U on figure 2. This steady DC current — bias current — also raises the amount of noise heard on replay of the tape. This is due to the fact that the bias current does not have an equal effect on all the magnetic particles upon the tape. The differences between the effects will appear as a 'noise' signal.

DC bias is nowadays used only on some low-priced cassette recorders, because of its inherent disadvantages of low signal-to-noise ratio and limited range of signal.

AC bias can overcome these disadvantages of DC bias, and allows a much wider range of signal onto the tape. A high frequency signal is used for the job, and it should be at least four times higher than the highest frequency to be recorded, to make sure it does not interfere with the signal we want to record.

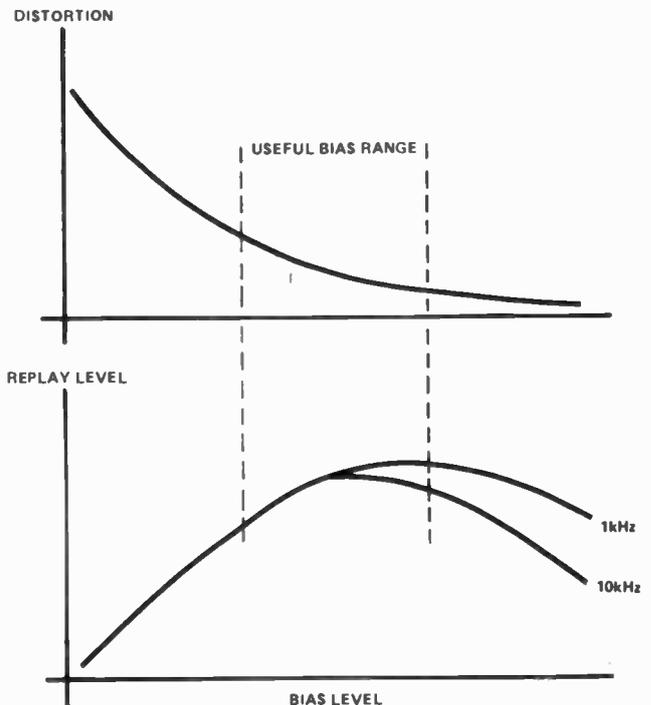

**Fig 5: The effect of amount of bias on both distortion and high frequency response. These graphs are the reason switching is needed on tape machines. For best compromise performance the machine should operate in the centre of the useful bias range. The amount of bias signal required to achieve this will vary from tape to tape — producing whole sets of these curves up and down the graph — and bias level has to be adjusted to correctly position the operation.**

This signal is generated by the bias oscillator within the recorder and is generally around 100kHz in modern machines. This constant value high frequency signal is added to the signal and both are recorded on the tape. The bias current 'fills in' the flat portion of the graph so that the total current in the recording head never falls to zero.


Since the bias is AC the current takes the tape into magnetisation on both sides of the axis, and so an added signal can utilise both sides of the graph such that the peak-to-peak values can be twice the DC value which induces saturation in the tape. Noise is also much less because the bias signal is so weak.

## RESPONSE-IBLE DECISION

Since the frequency of the bias signal is so much higher than the audible spectrum, there is no chance of it being picked up by the heads — witness the fact that Nakimichi machines are famed for their ability to replay 20kHz, never mind 90kHz!

This same bias signal, greatly increased in level, can be also used to clean (erase) the tape — an added bonus.

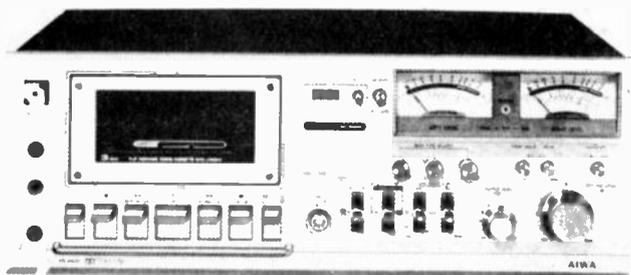Bias, then, reduces distortion as it is increased. However, there comes a point where the high frequency response begins to suffer (see Fig. 5). So optimising the bias means applying the maximum amount that will not degrade response.



*The Aiwa AD6800 cassette machine. Along with its younger brother the 6900, this machine offers the best compromise of bias performance. As well as the usual switches, fine tuning controls are incorporated which allow the user to peak-up performance for any tape.*



*Sony's excellent EL7 recorder. Conceived as a cassette tape machine which would have open-reel performance (by using tape at a higher speed basically) even if it is dependent upon those bias switches to optimise performance.*


This maximum will vary from tape type to tape type, and should ideally be set up for each brand of recording tape. Herein lies the reason for those switches. Each tape type therefore can be (nearly) optimised by changing the switches over. Some machines are now carrying this trend a stage further. For instance, the Aiwa AD 6800 allows the bias to be altered by the user to optimise the high frequency response by 'fine tuning' in addition to the simple switching usually provided.

## SUMMARY

Bias is thus an alternating current signal of high frequency which is added to the audio signal to be recorded. Both are recorded together. This overcomes the non-linearity of the magnetic properties of tape, thus allowing a higher value of signal to be recorded without distortion and aiding signal-to-noise ratio.

To make the best use of your tape machine, set the bias switching to the position marked for the type of tape you intend to use. If you do not, high frequency response and noise may well suffer.


HE

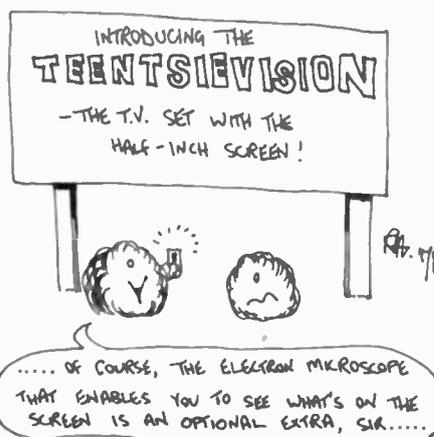

# Hobby Electronics

Next Month

## 4-Channel Equaliser

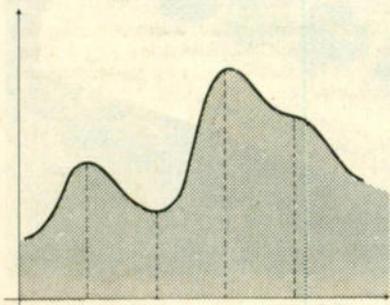


A fully-fledged graphic equaliser with four bands, allowing you to adjust the response of your Hi-Fi to suit the room it's in! Alternatively, this unit can be used as a really sophisticated tone control. This project was designed by a professional audio consultant especially for HE. We think it'll be a winner!

## Viewdata




One of the most exciting developments in modern TV technology is the advent of data transmission and display. Viewdata is Britain's answer to advances which could mean shopping from the home, a computer terminal in every room or even the abolition of commuting!

## Slave Flash

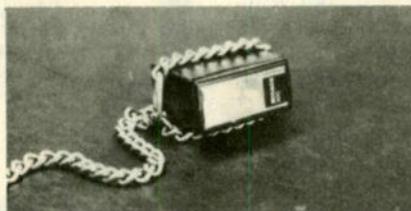

Using one flash gun is fairly straightforward — but how do you use two or more simultaneously?

## Touch Switch

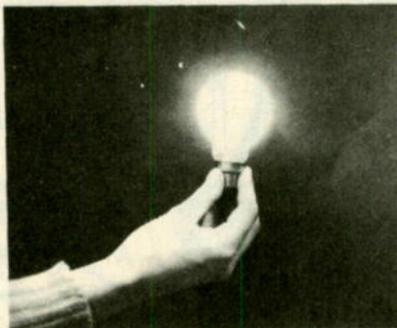


A switch with no moving parts! Just touch it and turn on the lights, motors or whatever turns you on. By the way, the above photo is not an illustration of the switch in action, but one of our staff having a bright idea.

## Holograms

Following on from the LASER article in this issue, we look into (!) holograms — what are they, how are they made and what use are they. This is a fascinating topic and one which is sure to make a big impact on all our lives in the future.

## Project Daedalus

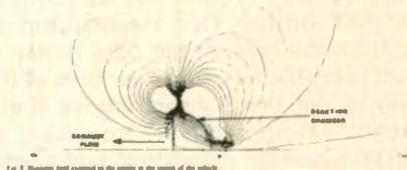


The British Interplanetary Society has just published a report which shows that interstellar flight by an un-manned vehicle is possible with modern technology. The report is nearly 200 pages of detailed drawings, calculations and specifications. We examine it clearly in detail.

## BASIC Programming

If you've ever wondered exactly what's involved in programming a computer, then this is for you. We look at BASIC — one of the most popular computer languages — and see what it's all about. This article will require no previous knowledge and will be much more than an introduction to the subject.

## Variwiper

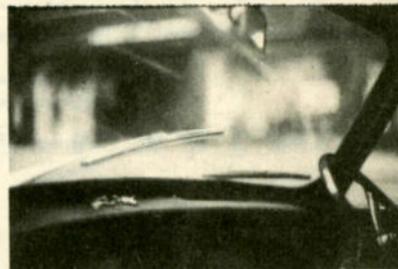

Ever been driving in one of those horrible drizzles which is too fine for the wipers to work properly? This circuit makes them repeat one sweep at pre-set time intervals — ideal for those conditions.

January issue will be on sale on December 8th

The items mentioned here are those planned for the next issue but circumstances may affect the actual content.


# Audio Mixer

***This project should prove invaluable to anyone who is into live music. That is, unless they've just spent five times as much on a commercial one!***

AT FIRST GLANCE this may not seem all that useful an addition to a small band's equipment. It consists basically of input circuitry for handling up to five microphones, guitars or whatever. All it does to these is to mix them together, provide some tone control and send them back out of a single output.

Most small bands which do not own a mixer handle the problem of sound mix by using a PA amplifier with several inputs. This means that the bass guitarist controls the level of the bass guitar, et cetera. This can lead to problems when members of the band decide that they're not being heard above the rest of the instruments! Using a mixer, however, the overall sound balance can be monitored and controlled by someone sitting in the audience.

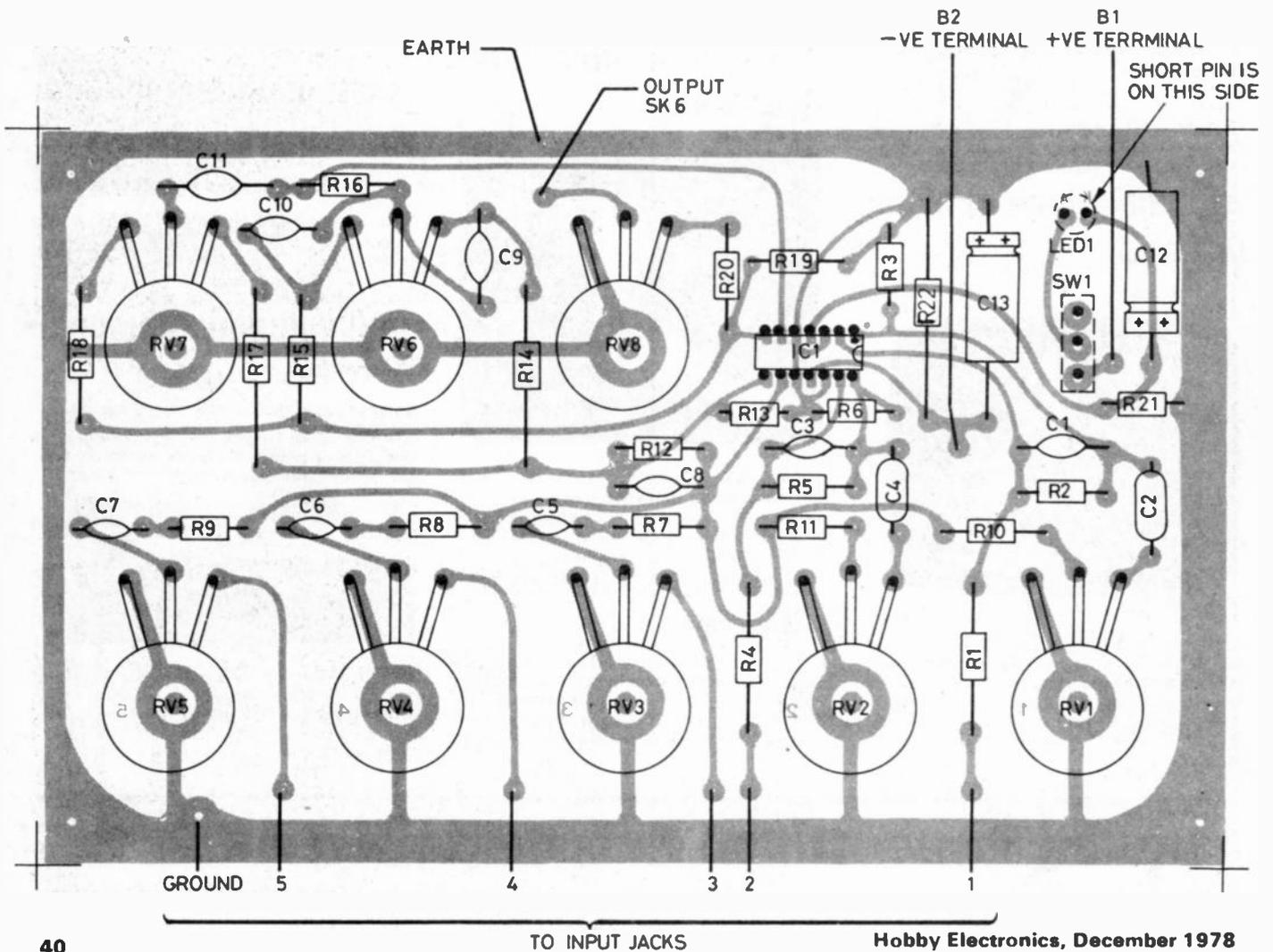This mixer also gives control over the total output level. This means that the band can be faded in or out at the start and finish of a number.



Apart from the facilities offered, what differentiates a good mixer from a mediocre one is the level of 'noise'. This is the amount of 'hiss' you hear with everything turned to full volume and no input. The noise level in this design compares very favourably with commercial mixers in a much higher price range.

Being battery-driven, this unit is particularly suited to 'on the road' applications, but other possible uses include stage sound effects cueing, tape recording, electronic music synthesis, et cetera.

## CONSTRUCTION — THE BOARD

The important thing to watch is the orientation of C12, C13 and IC1. If you follow the 'overlay' carefully you shouldn't have any trouble. Another thing to be wary of if you are using an IC socket for IC1 (an IC socket is usually soldered onto the board — the IC then plugs into it to save the risk of heat damage during soldering), then

be careful that none of the IC pins are bent under the body of the IC.

The LED will only work one way round — one lead will be longer than the other. see the overlay to find out which one.

SW1 is not designed for printed circuit board (PCB) mounting and so the holes for it will be large. The potentiometer spindles will have to cut to length — the final length depending on what type of knobs you buy. Don't cut them until you've constructed the rest of the project. The potentiometer leads will have to be 'lengthened' by soldering stiff wires onto them so that they will reach the board.

## Parts List

### RESISTORS (all 1/4W, 5% tolerance)

R1, 4	10k
R2, 5	100k
R3, 6, 13, 19	4k7
R7, 8, 9, 10, 11	56k
R12	100k
R14, 15, 16	10k
R17, 18	3k9
R20	1k0
R21, 22	4k7

### CAPACITORS

C1, 3	56p	polyester
C2, 4	220n	polyester
C5, 6, 7	100n	polyester
C8	56p	polyester
C9, 10	47n	polyester
C11	4n7	polyester
C12, 13	220u	16V electrolytic

### POTENTIOMETERS

RV1, 2, 3, 4, 5	25k	logarithmic
RV6	100k	linear
RV7	500k	linear
RV8	5k	logarithmic

### SEMICONDUCTORS



IC1	LM324
LED1	any red LED

### MISCELLANEOUS


Printed circuit board, single-pole double-throw switch, 2 off PP3 9V battery (or similar), battery clips to suit, 14-pin integrated circuit socket, VERO sloping-front case, knobs, 6 mono shorting jack sockets.
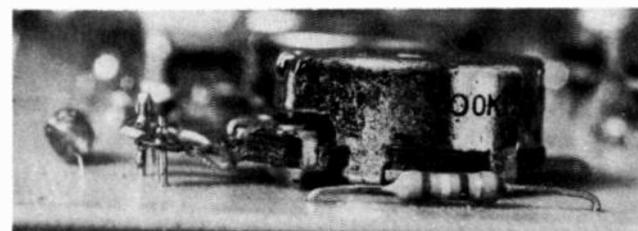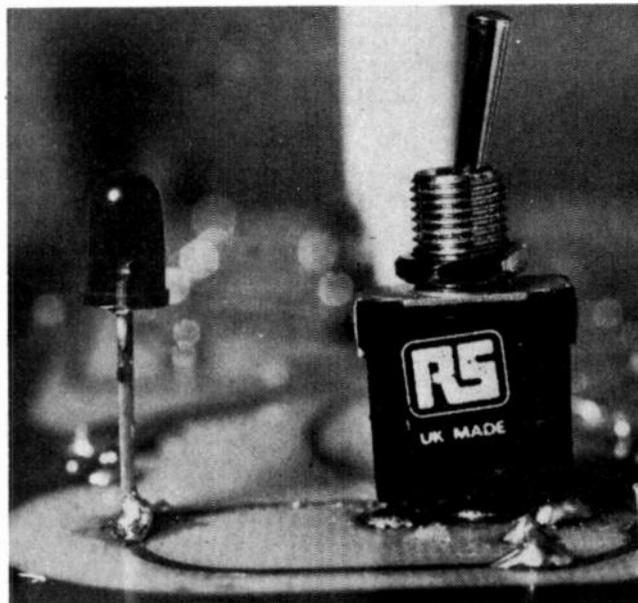
### Approximate Cost: £15




The case for this project is from the VERO range of cases. It should be available from most mail order firms and the same goes for the other components. The switch is an RS single pole, double throw type — any other type may not fit the PCB.



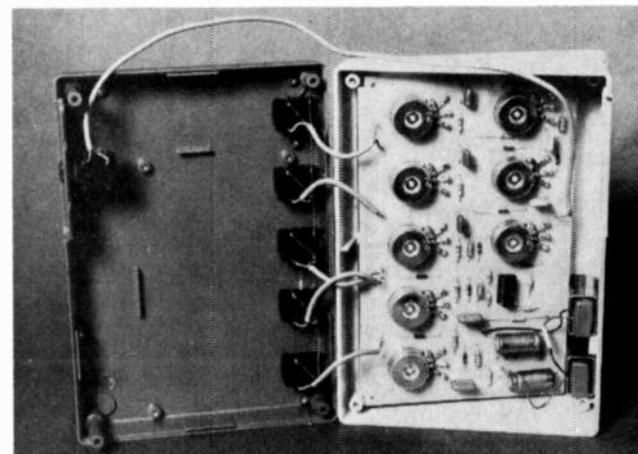*These shots show how the LED, switch and potentiometers are soldered into place. Do not solder the pots until you have bolted them in or you will risk straining the soldered joints.*



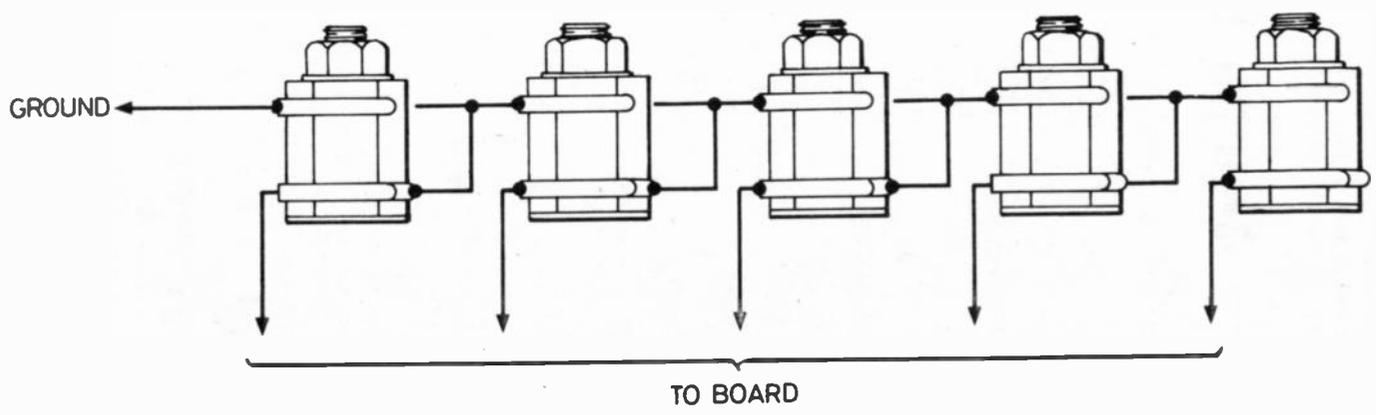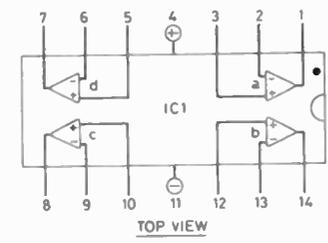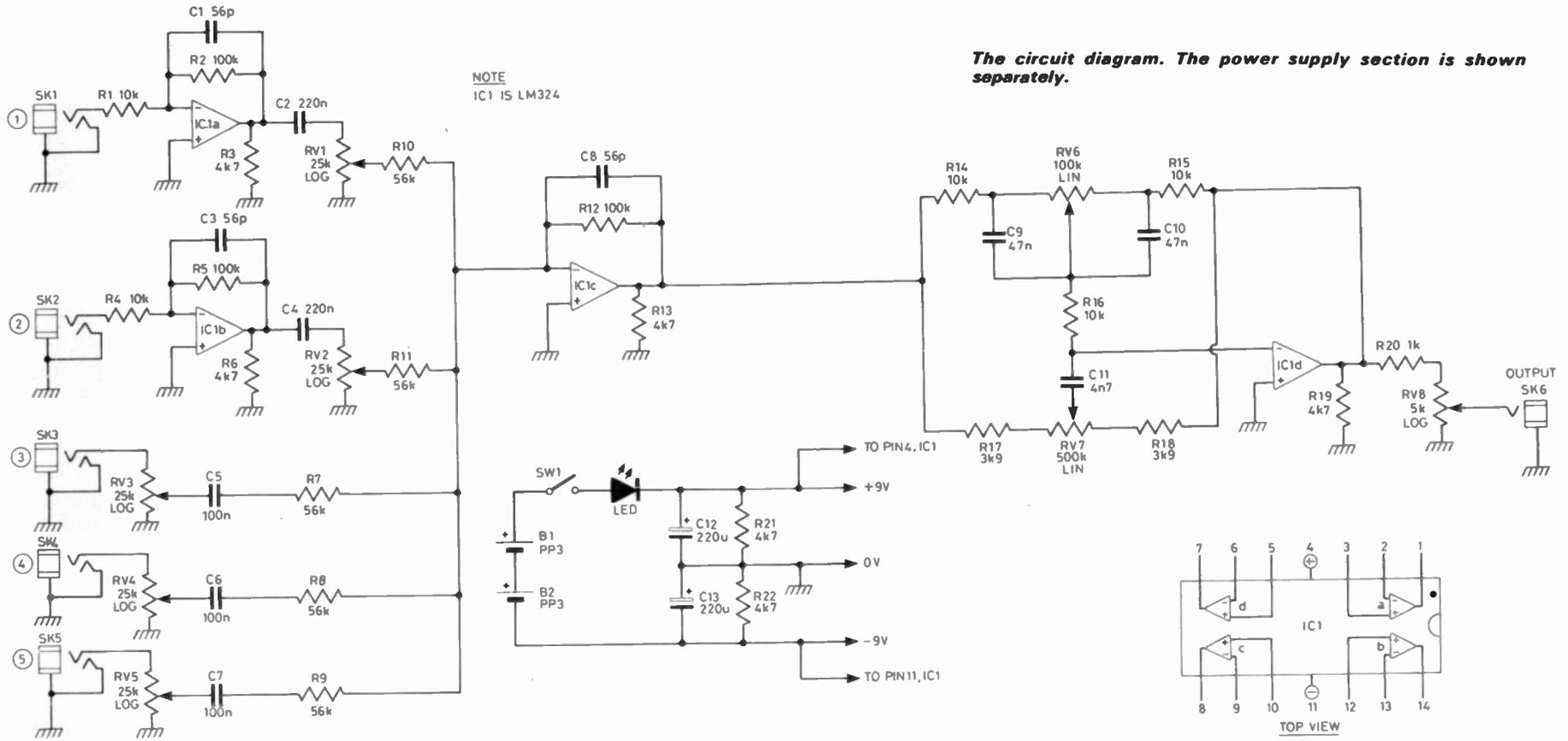
*An internal view. Note the wiring layout.*




**Pinout diagram for IC1. The LM324 IC contains four operational amplifiers with common power supply inputs.**
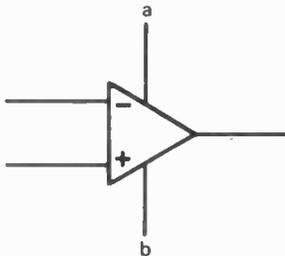
## How it Works

An operational amplifier is shown like this:



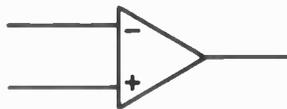Connections a and b are the power supply leads. These are sometimes (as here) omitted for clarity. This leaves:




The leads at the left are inputs and the one at the right is the output. The “-” input is called the inverting input and the “+” input is called — in a burst of ingenuity, no doubt — the non-inverting input.

The operational amplifier is a very simple device in its operation, although each may contain (in a sub-miniature form) dozens of transistors, capacitors, etc.

All it does is to subtract the “-” input voltage from the “+” input voltage, multiply the result by a very large number (called the ‘open-loop gain’ for reasons which we won’t go into at this stage) and output the result. That’s all it does, and yet it’s one of the most flexible active components in use.

Suppose we connect it like this:

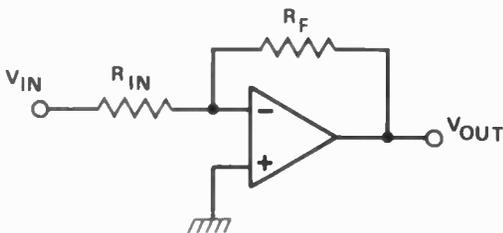


Since the non-inverting input is ‘earthed’, the voltage on it must be zero. Let’s suppose for the moment that the inverting input is above zero — the output will go below zero. In fact, it will go a lot below zero (remember, the open loop gain is a very large number, typically 20 000. This will cause the inverting input to be ‘dragged’ down’ (due to the current through  $R_F$ —the ‘feedback’ resistor). Eventually, the whole thing will settle down with the inverting input at zero volts.

Now, if we put current into the inverting input through the input resistor, the op-amp (operational amplifier) will change the output voltage until the whole thing balances again. The current through the feedback resistor will always be the same as the current through the input resistor and the inverting input will stay at zero volts.

The output voltage will always be a negative number times the input voltage:

$$V_{OUT} = -G \times V_{IN}$$

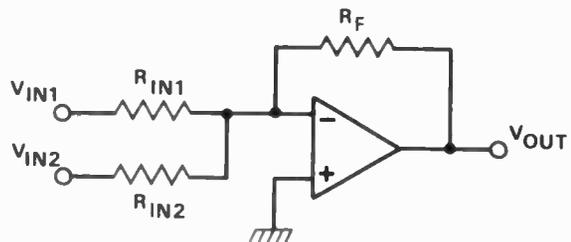The value of  $G$  will be  $R_F/R_{IN}$ .  
If we then add a second input:



The voltage at the inverting input will stay at zero — the circuit will operate exactly as before, except that the output will be  $V_{OUT} = (G_1 \times V_{IN1}) + (G_2 \times V_{IN2})$ . In other words, the output voltage will be the sum of the amplified input voltages. Using this circuit, we can ‘mix’ signals together to form a composite output.


This form of circuit is called a ‘virtual earth mixer’ because the inverting input remains at zero volts (ie earth voltage). Any number of inputs may be mixed in this way by adding more input resistors.

Looking at the circuit diagram, it’s pretty obvious what’s happening (although there are some ‘fiddly bits’ which will require explanation).

IC1a and IC1b are used to boost the low-level inputs from SK1 and SK2. The gain,  $G$ , of each will be  $100k/10k = 10$  times. C1 and C3 are required for the stability of the operational amplifier and R3 and R6 are ‘pull-down’ resistors. These are required because this particular device is good at supplying current but useless at shorting it to earth. These resistors help.

The outputs are AC coupled (to remove any DC bias which may be present) by C2 and C’s 4 thru 7. The inputs to SK3, 4 and 5 should be of a high enough level that they don’t require any extra amplification. Resistors 9 thru 12 and IC1c form the virtual earth mixer itself. Again, C8 and R13 are there to help the device along. IC1d and associated components form a standard ‘Baxendall’ tone control circuit which we won’t go into here.

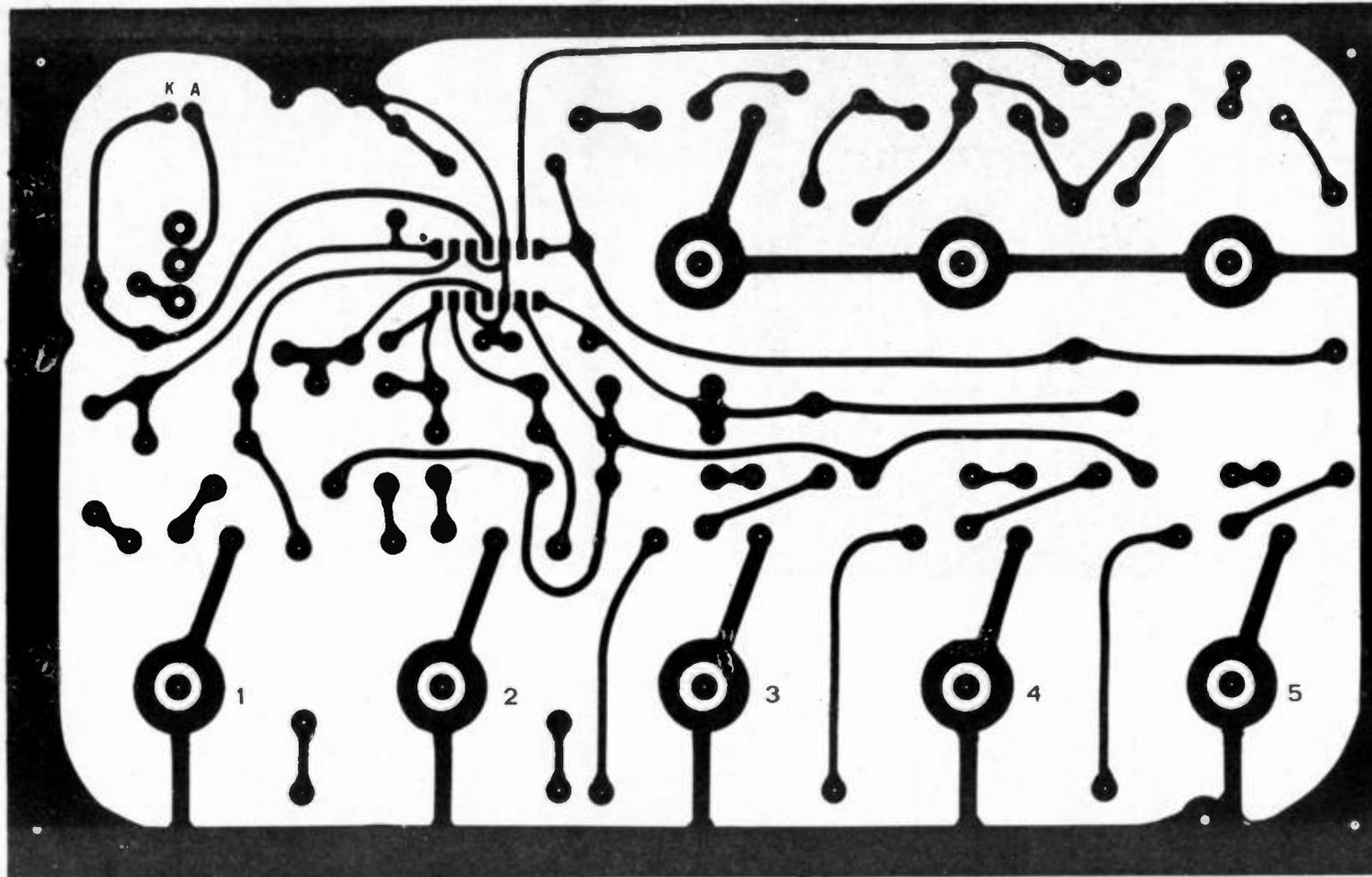The power supply to the IC is through LED1. This means that the effective supply voltage is  $9+9-2=16$  volts (the voltage drop across a LED is about two volts), but this is sufficient.



*The foil pattern. Printed circuit boards can either be made at home (see PCB feature in this issue) or bought from advertisers.*

## CONSTRUCTION — THE REST

The PCB should have holes which match threads on the case but don't screw it down until you've soldered the wires on!

Follow the diagram when it comes to wiring up the sockets and you should have no trouble — but use screened cable or you will run into problems due to 'hum' pickup.

The batteries are connected in series — the negative terminal of one connected to the positive terminal of the other. The other two terminals are connected to the

board. Use battery clips — they're useful when changing batteries!

## USING IT

Inputs 1 and 2 are 'low-level', suitable for microphones, guitars, etc. The other three inputs are for electric piano, synthesiser and the like. A good rule of thumb is that if what you're plugging in has either a) a mains plug or b) a battery, then it can go into one of the high-level inputs (3 to 5). The HE Waa-Waa falls into this category.

Don't leave leads plugged into the unit when there's no input from them — such as guitar leads with no guitars on the end of them. The sockets connect each input to earth if there's no plug inserted as this reduced the amount of 'hum' present.

The tone controls both have a 'neutral' position with the spindle rotated to half way between the end stops.

It is usual to leave the master volume control at full except when fading in or out. This means that the full travel of the control can be utilised, giving a smooth fade.


# Lasers

**Lasers are becoming part of our everyday work and leisure. Jim Perry reviews the state of the art.**

THE FIRST LASER was built by a research scientist called Theodore Maiman, while working for the Hughes Aircraft Corporation, in 1960. At the time the laser was called "The ideal solution to yet unfound problems." The problems have been found by the score in the last 18 years!

The word laser is short for Light Amplification by Stimulated Emission of Radiation, in fact laser devices are oscillators — but who would develop a laser? Radiation from a laser is monochromatic, that is, it occurs as a specific frequency and therefore is a pure source of light. This characteristic enables laser light to be detected in the presence of considerable levels of other optical noise (ie light), with little more than a good optical filter.


Laser light is also coherent. This means that the majority of the waves in the beam are in phase, giving the light the ability to be used to produce interference patterns. Laser light also emerges as a collimated ray, not as a point source radiating in all directions, and only diverges by typically one part in a million. Without modification the beam can act as a weightless line in space, enabling a whole host of alignment measurements to be made. Because the light is gathered into a small aperture, it is of extreme intensity. With further focussing laser beams can be used to produce points of energy capable of reaching millions of degrees in temperature.

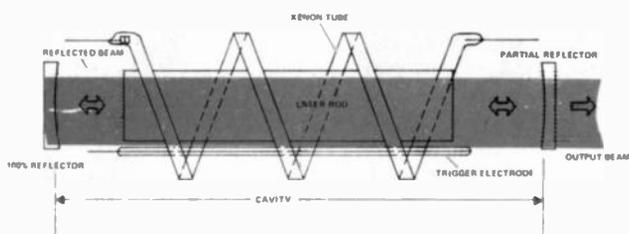

In the ruby laser, as first developed by Theodore Maiman, pump light from a Xenon lamp raised the energy level of chromium atoms in a ruby rod until a pulse of coherent red light emerges from the partial reflector.
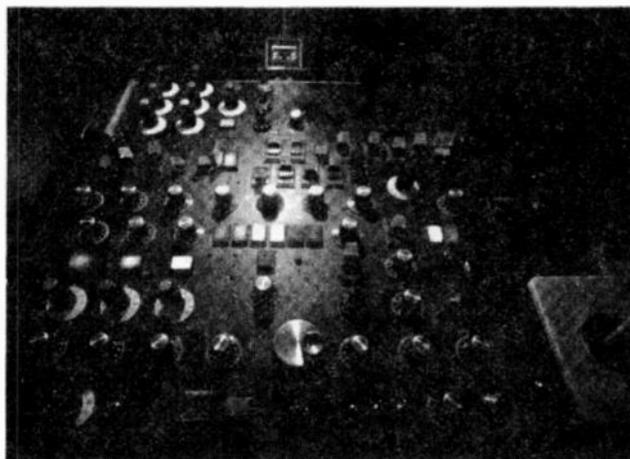
## USE OF LASERS

Possibly the most publicised use is in laser light shows, such as Laserium and Laserock. These two shows are packing audiences into planetariums all over the world. Because of the very pure nature, and power, of laser light it has an almost indescribable 'look' about it — a light so pure is never found in nature. When lasers were only seven years old people started experimenting with the artistic effects made possible, by projecting the beam through cut glass and smoke. Modern laser light




The control panel at Laserium.

shows are extremely sophisticated, using powerful Krypton lasers and thousands of pounds worth of electronics, with dozens of scanners. Scanners are mirrors mounted on galvanometers, signals from the electronics are fed into the coils of the galvanometers — and the laser beam deflected by the mirror. It may sound simple, but the special scanners used cost at least £400! With two scanners at right angles, full X-Y movement of the laser beam is possible — and with upwards of 24 scanners shows like laserium need to be seen, to be believed.
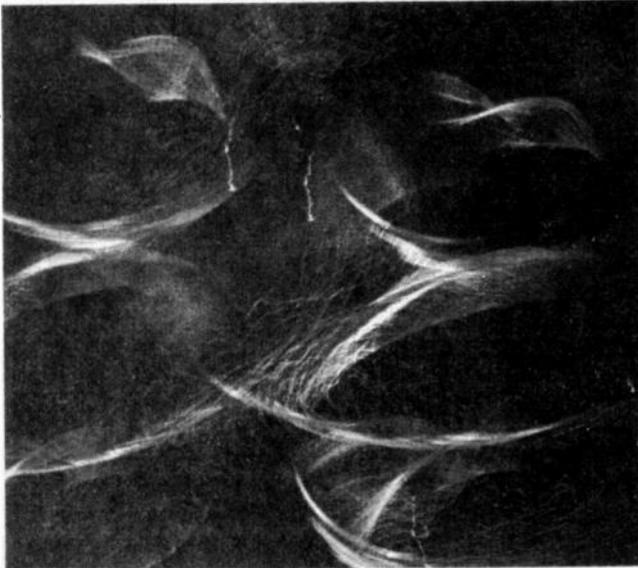
## MEASUREMENTS

Surveyors (and the Military) use lasers in various ways to measure distance (range). A modulated beam of laser light is transmitted out to a possible target, then it is reflected back to the main unit. Knowing the velocity of light (which we do to about one part in a million in air), the distance travelled is easily calculated from the time taken for the laser beam to return. The main design problem is that of 'marking' the beam in some way, so that the returning beam can be detected. This is usually done either by sending out a single pulse, and waiting for its return — or by transmitting a continuously modulated beam, and comparing the phase difference between signals.

Because the times involved are so small, the laser range finding devices are normally only used for quite large distances (hence giving a longer time), and resolution can be within a few centimeters over several kilometres.



An example of a Laserium display (unfortunately we cannot reproduce the vivid colour which is a major characteristic of such displays).

A development of the range finding use is in measuring the profile of land, from a moving plane. If a laser beam is bounced off the ground from a plane in level flight, a readout of the ground profile is possible. When this technique was first used the researchers were puzzled by some obviously wrong results, when flying over lakes. It turned out that the laser beam can even travel through water, and return (at a rather lower intensity) to the aircraft — they were getting a profile of the lake bottom! Further research has now been started into laser depth finders.

## LASER WEAPONS

The death ray laser is not as far away as you might think, but it isn't hand held! As long ago as 1971, tests were made with 60kW lasers capable of igniting wooden targets at up to 4 kilometers. More recently we have heard a story (unconfirmable) about a 3 megawatt laser. It seems this huge beast is mounted in a converted passenger jet — with an extra engine to supply the power needed. The laser is a 192 foot carbon dioxide device, folded in order fit inside the aircraft. Because the beam from a CO<sub>2</sub> laser is infra-red (and can't be seen), a small visible laser is used as a 'tracker' beam — that people can follow the main beam.


One day the tracker laser was out of order, and someone moved the reflector to clean it. Unfortunately someone else switched the monster on — for a few

seconds. The beam burnt a hole through the side of the hangar, two parked aircraft, another hangar wall (on the opposite side of the airfield) and two more aircraft — before finally stopping inside a fifth aircraft. Luckily nobody was in the way, as a three inch hole in your side is not much fun. As said we cannot confirm this story, but can well believe it!

So lasers can do many things, we have only mentioned a few of the many applications. Other uses include medical (eye surgery) engineering (levelling of building sites) and communication (a single laser beam can carry a million TV channels). A further use of lasers, and potentially the most exciting is holography — the subject of a future article in Hobby Electronics. **HE**




A laser rangefinder.

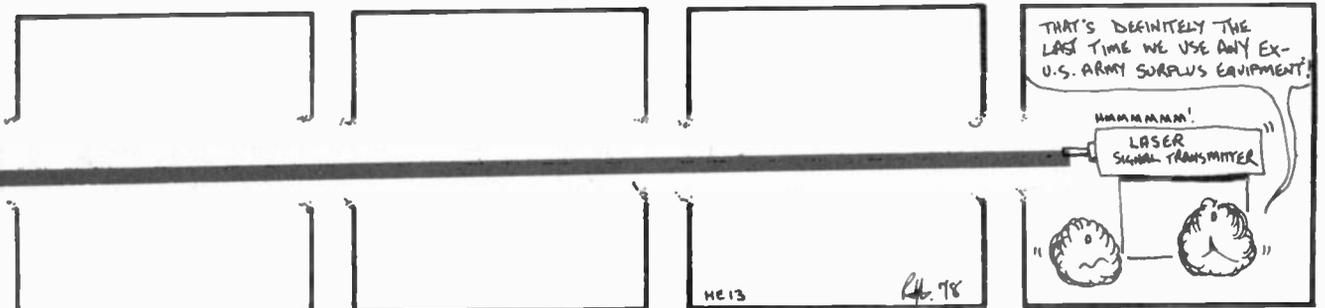
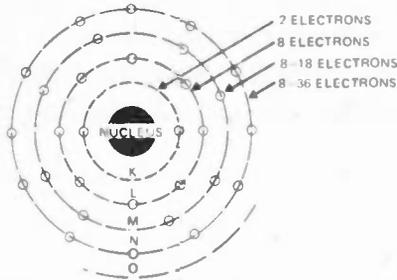
## How it Works

To understand LASER action it is necessary to review atomic theory to some extent. All other electronic systems make use of the energy of free electrons in the atomic system. Lasers, on the other hand, use processes within the atom itself to produce coherent radiation.



*The structure of the atom.*

This diagram shows the now well known structure of the atom. This consists of a central nucleus orbited by one or more electrons. The complexity of the nucleus and the number of orbital electrons is unique to particular elements. The electron orbital paths are confined to discrete levels of shells, each shell corresponding to an energy level. An electron cannot exist in a stable state between shells and if subject to radiation that increases its energy it will jump to the next highest shell. The quantity of electromagnetic radiation necessary to just cause an electron to move to a higher shell is called a photon. Photons can be thought of as minute packets of energy which have the characteristics of both matter and electromagnetic radiation.

### THE PHOTON

The Photon is a fundamental concept in the quantum theory and the relationship of the photon frequency and the energy level to which the atomic system is raised is given by the equation:

$$E = hv$$

where

E = Energy level in ergs

h = Planck's constant ( $6.624 \times 10^{-27}$  erg-sec)

v = Frequency of the photon

A photon of the right frequency is therefore required to raise an electron of a particular atomic system to a higher energy level. When an atom is in its lowest energy state it is said to be in the ground state and when its energy has been increased by a photon it is said to be in an excited state.

From the excited state, a number of possibilities exist for the return to ground state. Firstly the electron may fall to an intermediate level and then to the ground state. A photon will be emitted at each transition having a lower frequency than the incident photon (because each energy level jump is smaller) or alternatively it may jump straight to ground state and emit a photon of the same frequency as the incident radiation. These mechanisms are known as SPONTANEOUS PHO-

TON EMISSION and normally occur very rapidly (less than a microsecond after excitation).

If a photon of the correct frequency is incident upon an atom already in the excited state, it will emit a photon having exactly the same phase as the first photon, and travelling in the same direction. This mechanism is known as STIMULATED EMISSION.

### THE RUBY LASER

The original laser as built by Ted Maiman nowadays appears ridiculously simple. It consists of a ruby rod containing about 0.05% chromium (the chromium component gives the ruby its characteristic pinkish colour). The rod is surrounded by a Xenon flash lamp. The purpose of the flash lamp is to provide excitation, called pumping, at 5 600 angstrom (blue green light) to which the chromium atoms respond.

The chromium atoms, once excited, will spontaneously return to ground state in two steps. They first return to an intermediate level, known as the metastable state, with the emission of red light at 6943 angstrom.

At this point the ruby rod will glow with red light. The flash lamp continues to pump energy to the chromium atoms pushing more of them to upper energy levels until, there are more atoms at the higher energy level than at the lower. This is known as population inversion and at this point the operation suddenly changes. Now photons begin to interact with excited chromium atoms to a significant extent, with a resultant stimulated emission of other identical photons which travel in the same direction as the incident photons.

The ruby rod, which is several centimetres long and half a centimetre in diameter, will have some photons travelling parallel to its axis, and these will be reflected at the ends back into the crystal where they produce still more photons. Those travelling in other directions emerge from the sides and are lost. The build up of photons parallel to the rod continues until, at a critical point, some of the coherent radiation bursts out through the partially reflective end face. Thus, a laser pulse is born. The pumping process continues generating further pulses of coherent red light each having a duration of about one or two milliseconds.

Although such action is possible with a simple ruby rod having both ends polished and perfectly parallel to each other, it is far better to use external mirrors to do the reflection. These are specially constructed multilayer (dichroic) mirrors such that they reflect the frequency of interest with high efficiency. One of them is made partially transmissive to allow the laser pulse to emerge. For the laser to operate at maximum efficiency it is desirable to get as much light as possible into the ruby rod. For this reason the flash lamp is wound around the ruby in a helix.

Since Maiman's first laser began pulsing, some 13 years ago, enormous strides have been taken in the development of laser technology. Many new lasing techniques have been developed and both peak and average power have been increased to staggering levels.

# Photocells

**Photocells are the devices we use to detect light by making use of the energy that is carried by the light to generate an electrical signal. There's a remarkable number of different varieties of photocells, due to the fact that there's an equally remarkable number of substances which are affected by light. K. T. Wilson explains . . .**

LET'S START with any solid-looking chunk of material. All these materials are made up of atoms which, in a solid material, are packed tightly together. These atoms, though, are hollow, mainly empty space, containing a positively-charged core called the nucleus and a lot of incredibly small negatively-charged particles called electrons. These electrons are involved in everything electrical or electronic (and a lot more besides).

Now we can get hold of electrons in comparatively small numbers, just a few millions at a time, and make measurements on them. We're pretty sure, as a result, that all electrons are identical. The electrons inside an atom don't behave as if they are identical, though, because some can be removed much more easily than others. We explain this by saying that the electrons have different energy levels, meaning that some are much more tightly held by the attraction of the nucleus than others. This idea of energy levels is probably one of the most important ideas of modern physics, and it's practically impossible to discuss why electronic components behave as they do without bringing in energy levels somewhere.

## LIGHT READING

What about the light, then? Light, like radio, is an electromagnetic wave. That, translated a bit, means that where you have a light ray there's a voltage oscillation and a magnetic oscillation as well. It's the voltage oscillation that we're interested in — that's the one we pick up in an aerial when we receive a radio broadcast. What happens in an aerial is that the electrons in the metal follow the oscillations of the voltage wave, so that an alternating voltage is created in the wire. That's the radio signal that we detect and amplify.

Now we come across one of these horses-for-courses choices. We find electromagnetic waves at all sorts of frequencies, from a few hundred kHz (long waves), through the UHF band of several hundred MHz, past the much higher frequencies of light waves and beyond. These waves all have two things in common — they travel at the same speed in space — about 300 million metres per second — and they are all emitted in bunches, not continuously. Each bunch of waves carries a definite amount of energy, an amount that depends on the frequency of the waves in the bunch. A bunch of light waves at a frequency of 6 hundred-million-MHz therefore carries a lot more energy than a bunch of medium-wave radio waves at 1 MHz, and it's this bunch energy called the quantum energy (the word quantum

just means bunch) that has an effect on materials.

Measured in this way, radio waves are rather feeble things, just about able to carry out the easy job of moving electrons in wires. Light waves carry a lot more quantum energy, and the energy of one of these bunches of light waves *can* be enough to shift an electron from its own energy level to the next higher one. Can? Yes, because the gap between energy levels is not the same for all substances and only some of the millions of substances we know have just the right arrangement of electrons for packets of light waves to shift one.

The first substance discovered behaving in this way was the element selenium. Selenium is photovoltaic, meaning that the effect of light is to free electrons completely from their atoms. If a piece of selenium is part of a circuit, then the action of light on the selenium is to make it behave like a battery, causing current to flow in the circuit. Selenium is still used for light-measuring meters, but more modern photovoltaic cells, based on another semiconductor, silicon, have been developed. It's these silicon cells which are our main hope for generating electricity direct from sunlight, incidentally, so that there's a lot of research going on at the moment.

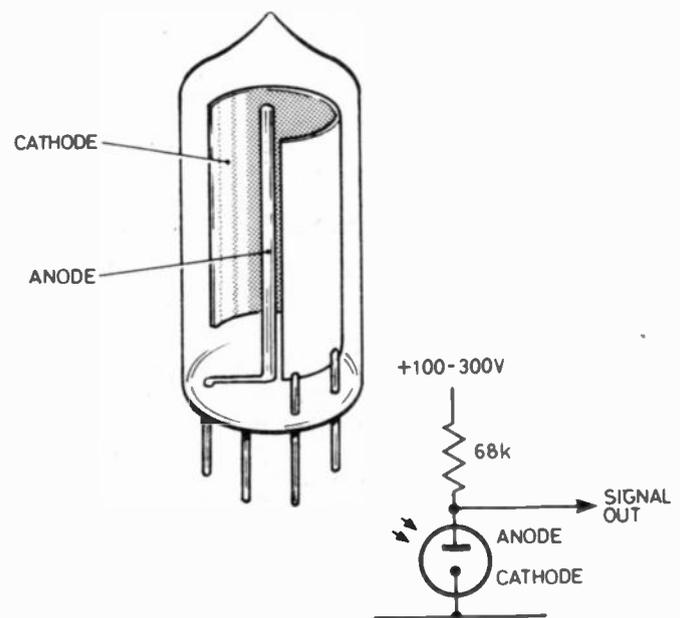


Fig. 1. A vacuum photocell, and typical circuit.

## PHOTO EMISSION

A few substances have electrons with such low energy levels that electrons can be shot out at high speeds when a light beam strikes the material. Materials like this are called photoemissive, but they can be used only in a vacuum. There are two reasons for this. One is that the materials themselves are chemically attacked (oxidised) by air; the other is that the electrons that are released can't get very far if the material is surrounded by air. A vacuum photocell contains a photocathode — a nickel plate coated with the electron-releasing material such as the metal caesium — and an uncoated anode, both inside a bulb from which the air has been removed. To use the cell, a voltage of 90 to 200 V is connected across the terminals (anode positive). When light strikes the photocathode, electrons are released and are attracted to the anode by the positive voltage. The current that flows in the circuit can be detected by a microammeter; it's small but it's there. This type of vacuum photocell was once the main method of detecting light, particularly of rapidly-changing pulses of light such as those from the sound track of a movie film. What made the vacuum photocell particularly suitable was its quick response — there was very little time between starting or stopping the light and starting or stopping the current. Very little time means less than a microsecond, in contrast to the selenium cell which takes about a quarter of a second to respond either way.



Fig. 2. The Cadmium Sulphide LDR, and symbol.

For many years, the selenium cell and various forms of vacuum photocell were the only types of photocells we knew — then the semiconductor age began. We've learned so much about energy levels and how to play with them that a whole new set of photosensitive materials has been invented. Semiconductor materials have their energy levels arranged so that only a small amount of energy is needed to release an electron, allowing the material to conduct better. This process is called electron-hole pair production, because each electron that is released leaves a space, called a hole, in the crystal structure of the semiconductor. The holes behave like conducting particles, assisting the material to conduct. Let's see how this process is used in modern semiconductor materials.

## HARD CELL

One of the most familiar cells is the cadmium sulphide photoconductive cell. Cadmium sulphide is a material that can be evaporated onto any smooth surface, so that it's easy to make into a thin film; cadmium sulphide photocells (often called LDRs — light dependent resistors) use tracks of film of the shape shown in Fig. 2. We

can make electrical connections to each end of such a track, so that the cell can be wired into a circuit as if it were a resistor. In darkness, the cadmium sulphide is practically an insulator, and a cell will have a resistance of 1M or more. Light falling on the material causes electrons and holes to separate, so that the material conducts, and the resistance falls very greatly, to 1k or less depending on the width and length of the track.

Cadmium sulphide cells have some peculiar advantages and disadvantages compared to other types of cells. They can be used in circuits where quite high voltages exist, 300 V for some types of cells, so that these cells can be connected directly across the mains supply. They can also pass quite large currents, so that relays can often be driven directly with no need for transistors.

Photodiodes and phototransistors are the other important classes of modern photocells. Unlike the cadmium sulphide photocell, which consists of a single material, a photodiode has a PN junction. P-type semiconductor material conducts mainly by hole movement, N-type mainly by electron movement, and we can form thin films which are P-type on one side and N-type on the other, with an electrical contact to each. This is, of course, the familiar junction diode, and a diode like this which is reverse biased does not normally conduct because the voltages that are applied have the effect of pulling the holes and electrons away from the place where the two types meet, the junction.

If light hits the junction, though, electron-hole pairs are generated and the junction becomes conducting. With a steady voltage across the junction, a current will flow when the junction is illuminated. The current is small, only a few microamps, but the response speed is very fast, measured in nanoseconds. ( $1 \text{ ns} = 10^{-9}\text{s}$ ). Photodiodes of this type, plus fast pulse amplifiers are the natural choice for detecting very short flashes of light.

## PHOTOTRANSISTORS

The phototransistor is the type of light detector which is chosen for most applications that don't need ultra-high speed or very large currents. A phototransistor is constructed in the same way as any other transistor, with the sandwich of PNP and NPN semiconductor materials. In the dark, it'll work away like any other transistor, with

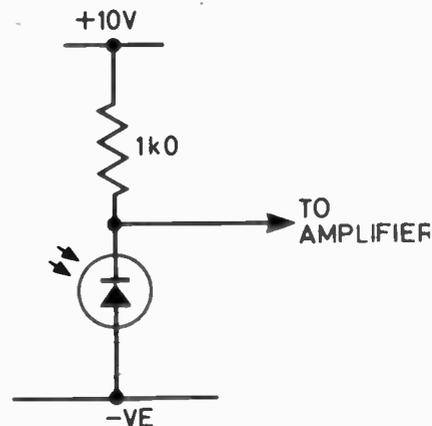


Fig. 3. The photodiode symbol and typical circuit. Though the action of the cell is fast, the maximum frequency of operation is limited by the capacitance of the diode, typically 1 nf (1 000 pF).

the current between the base and emitter layers controlling much larger currents between the collector and emitter layers. In the light, though, interesting things happen — as the advert says! A phototransistor is operated with no connection made to the base — some phototransistor types have no base connection terminal. Now if you operate an ordinary transistor in this way, nothing happens, because it's the current into the base terminal which fills up the base-to-emitter junction with electrons or holes and so makes the lot conduct. A phototransistor is constructed so that light can reach this base-emitter junction, and the light will have the usual action of separating electrons from holes at the junction. Now neither of these can flow to the base contact, because it's disconnected, so that the only possible direction is towards the emitter or the collector.

Suppose the phototransistor is an NPN type, with the collector voltage positive and the emitter voltage negative. When an electron is separated from a hole at the base-emitter junction, the electron will head towards the collector, but the hole isn't so lucky. At the start, there's practically no voltage between the base and the emitter, so there's no reason for the hole to move. The result is that the base gets more and more positive as it

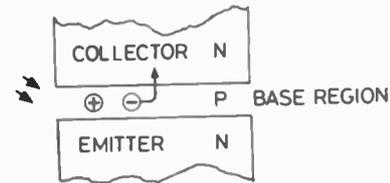


Fig. 4. The phototransistor — symbol and arrangement of junction.

loses electrons and hoards holes. Pretty soon, this positive voltage does exactly what positive bias does to an ordinary transistor — it attracts electrons from the emitter. Most of these electrons go straight to the collector, though, because the base layer is so thin, and the phototransistor then passes several milliamps of current between collector and emitter just to make sure that a few microamps flow to the base. The result is a photocell which can pass much higher currents than a photodiode, though with a slower switching speed.

HE

## Short Circuit

### CMOS MONOSTABLE


A monostable is an electronic circuit that generates an output pulse of defined duration, when triggered by an input signal transition. The monostable action can be used for many different functions, for example: When a cheap push button is used to trigger digital circuitry, spurious pulses often find their way into the circuitry. This is due to the contacts inside the button bouncing, when it is pressed and released — digital circuitry will regard all of the bounces as valid input signals, and act accordingly — this can be disastrous in counting applications. A monostable can be used to 'debounce' the push button. By setting the output pulse duration for a period longer than the longest expected bounce time, all the bounces will have no effect on the main circuitry. So with a simple monostable between each push button and the input circuitry, the digital devices are protected from the horrors of untamed push buttons. There are hundreds of other uses for the monostable, this circuit is one of the cheapest ways of constructing them.

Only two inverters are needed for a monostable circuit. Here, we have used a 4011B quad NAND package, as they are even cheaper than a CMOS inverter package and work just as well.


The monostable period is initiated by the transition of point A

from positive to zero volts. This is called a negative-going edge. Transition of point A in the opposite direction (a positive-going edge) will have no effect.

A negative edge at A causes point B to go to zero volts momentarily. This will then drive point E to zero and this will hold point B at zero volts, even when the pulse at A is finished. The circuit will stay in this state while C2 charges. When C2 is fully charged, there will no longer be a current through R2 and point D will fall to zero again. E will go positive and so will B, after a time determined by the values of C1 and R1. Point C will fall to zero and C2 is fully charged, there will no longer be a current through R2 and point D will fall to zero again. E will go positive and so will B, after a time determined by the values of C1 and R1. Point C will fall to zero and C2 will be discharged, ready for the next pulse from A.

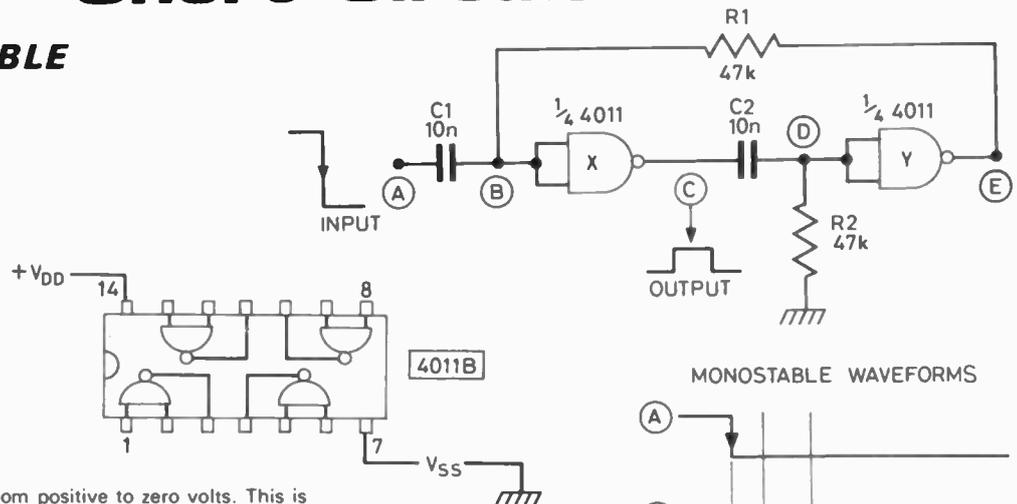

#### MONOSTABLE WAVEFORMS

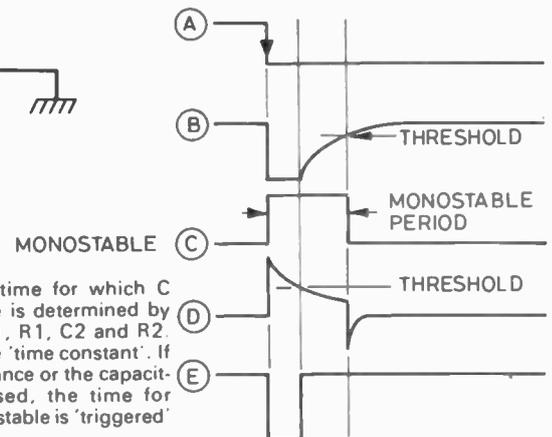

A length of time for which C remains positive is determined by the values of C1, R1, C2 and R2. This is called the 'time constant'. If either the resistance or the capacitance is increased, the time for which the monostable is 'triggered' will increase.

The equations for calculating the monostable period are given on the circuit diagram. Polarised capacitors should not be used, and the resistance value of R should be kept within the range 10k to 10M.

If R1 = R2 and C1 = C2 then typical values are 10mS 100k, 68p: 10mS 1MO, 6n8.

$$\text{MONOSTABLE PERIOD } \tau$$

$$\tau = 0.69(R1 \times C1 + R2 \times C2)$$

IF R1 = R2 AND C1 = C2 THEN

$$\tau = 1.38(R1 \times C1)$$

IF R = 47k, C = 10n THEN  $\tau = 0.7 \text{ mS}$ .

# Radio Servicing Tips

**Here are ten effective ways to help you locate radio faults faster. They are usually obvious (though often unremembered) ideas that have been used and proved profitable. By Terry L. O'Connor.**

## **1. Check Battery Voltage and Current**

Make this a regular procedure. Test receiver battery voltage with it turned ON. Check the current drain with the volume control turned down. The current drain may be checked by placing a milliammeter (most multimeters have a milliamp range) across the receiver's on/off switch terminals (set off). The average transistor radio may draw some 5 to 15 mA if it uses Class B output stages and somewhat more if the output stage is Class A.

Excessive current drain may be caused by shorted or leaky bypass capacitors, incorrect biasing of one or more transistors or by a defective transistor.

## **2. Find the Obvious Faults**

Possibly more than anything else, transistor radios suffer from broken wires and terminals usually caused by the owner dropping the radio. Broken wiring may be quite difficult to analyse, either by signal tracing or voltage readings. A lot of time can be saved by visual checking. The use of an illuminated magnifier can help find broken conductors.

Try slightly flexing the printed circuit board to find tracks that are broken or intermittent. Small resistors are easily cracked and often go open circuit.

Heavy components, such as transformers, often pull away from the printed board and break their connecting leads in the process. Try moving each part from side to side gently and listen for a pop in the speaker. Use a jumper wire with needle point probes at each end to check if the printed track is open.

## **3. Don't worry about transistors or ICs.**

Not at first anyway. It is just an advertising agency's dream — bad transistors or IC's *do* account for only 2 to 3% of all transistor radio defects — check other things first.

Also check earphone sockets — the type which switch off the speaker sometimes leave it off!

## **4. Don't rely on transistor gain checks**

Unless there is laboratory equipment available, your chances of learning anything from a gain check are nil. The DC gain has almost nothing to do with the manner in which a transistor will perform in a practical RF circuit. There are too many other factors involved, such as input and output impedance or biasing.

## **5. Check transistors with an in-circuit transistor**

As the transistors used in portables usually are not plugged in, we must have some exploratory method for checking that does not mean unsoldering the transistor. The quickest way is to use an in-circuit transistor tester, available from many radio components retailers. However, if you do not own a transistor tester (in-circuit variety) you can use a multimeter instead.

With the radio off, place an ohm-meter (20 000 ohms per volt or better) across the Base and Collector of the transistor; and reverse the test leads. There should be more resistance in one direction than in the other. Do the same from Base to Emitter. Typical readings may be 3,000 ohms in one direction and 20 ohms in the other. This usually indicates that the transistor is good, as there is evidence of diode action.

A transistor can also short circuit from Collector to Emitter, without affecting the apparent diode action of the Base-Collector, Base-Emitter paths.

## **6. Signal Trace or Signal Substitute**

You can use a signal generator for signal tracing. Start with the audio and successively trace backwards towards the front end. Never be tricked, though, by the low-impedance base circuit of a transistor. It will greatly attenuate the signal generator's output. Always inject the signal into the higher impedance collector circuit, if possible.

## **7. Never Be Tricked by Gain of Receiver**

A transistor radio may appear to be operating normally especially on strong local stations, but refuse to work when taken to a fringe area. If you work quite a lot on the same kind of radio, you may set up tests with an output meter and your signal generator to determine if the gain is up to scratch. If it is not, check the tuning and tracking (as detailed in TIP 10). Use a substitute capacitor and *shunt* each and every bypass and coupling capacitor in the radio.

Capacitors and IF transformers can cause more weak radio faults than anything else. Transistors can short or open. Try to check IF's by re-tuning them. If they cannot be peaked, they are faulty. If the tuning has to be changed drastically (unless the radio has been tampered with by someone), it is likely the IF transformer is defective and will have low gain, even though it may appear to peak at some position of the slug.

## **8. Check the Oscillator With Another Radio**

Position a working radio, tuned to a station at the high end of the band, near the radio with a suspected oscillator stage. Sweep the defective radio through its tuning range. At some point a whistle or squeal should be heard in the good radio if the defective radio's oscillator is operating. This whistle or squeal should be heard at approximately 455 kHz below the station tuned in on the good radio, if the good radio uses a 455 kHz IF (most do). This allows you to know that the oscillator tuning circuit on the defective radio is operating.

It is also possible to use a peak-to-peak meter or a



# STEVENSON

## Electronic Components

### PLUGS AND SOCKETS

1mm plugs and sockets suitable for low voltage circuits. Available in red or black, Plugs 6p each. Sockets 7p each.

4mm plugs and sockets. Available in black, blue green, brown, red, white and yellow. Plugs 11p each. Sockets 12p each.




Jack plugs and sockets

	unscreened plug	screened plug	socket
2.5mm	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

Din plugs and sockets

	plug	socket
2 pin speaker	7p	7p
3 pin	11p	9p
5 pin 180°	11p	10p
5 pin 240°	13p	10p

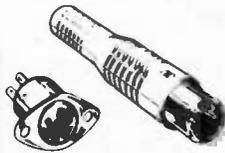

### CABLES

Connecting wire  
Available in packs of eight metres (one metre of each colour) or packs of forty metres (five metres of each colour).

	single	standard
Eight metre pack	16p	16p
Forty metre pack	76p	70p

Screened Cable	Ribbon cable	
Single screened	8p	10 way 58p metre
twin individually screened	11p	20 way 100p metre

### VEROBOARD

Size in.	0.1in.	0.15in.	Veropins - single sided per 100
2.5 x 1	14p	13p	
2.5 x 3.75	42p	40p	
2.5 x 5	52p	50p	0.1in 35p
3.75 x 5	60p	60p	0.15in 40p
3.75 x 17	195p	180p	

### ALUMINIUM BOXES

Boxes complete with lid and screws.



Model	Length	width	height	Price
AL1	3	2	1	48p
AL2	4	3	1½	58p
AL3	4	3	2	65p
AL4	6	4	2	70p
AL5	6	4	3	85p
AL6	8	6	2	116p

We now have an express telephone order service. We guarantee that all orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Telephone: 01-464 2951/5770.

**ORDERS  
DESPATCHED  
BY RETURN  
POST**

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 25+ 10%. 100+ 15%. Prices VAT inc. Please add 30p for carriage. All prices valid to 30th April 1979. Official orders welcome.

BARCLAYCARD AND  
ACCESS WELCOME.



Mail orders to: STEVENSON (Dept HE)

**236 High St, Bromley, Kent, BR1 1PQ, England**

### TRANSISTORS

AC127	17p	BCY71	14p	ZT x 109	14p
AC128	16p	BCY72	14p	ZT x 300	16p
AC176	18p	BD131	35p	2N697	12p
AD161	38p	BD132	35p	3N1302	38p
AD162	38p	BD135	38p	2N2905	22p
8C107	8p	BD139	35p	2N2907	22p
BC108	8p	BD140	35p	2N3053	18p
BC109	8p	BF244B	36p	2N3055	50p
BC147	7p	8FY50	15p	2N3442	135p
BC148	7p	BFY51	15p	2N3702	8p
BC149	8p	BFY52	15p	2N3704	8p
BC158	9p	MJ2955	98p	2N3705	9p
BC177	14p	MPSA06	20p	2N3706	9p
BC178	14p	MPSA56	20p	2N3707	9p
BC179	14p	TIP29C	60p	2N3708	8p
BC182	10p	TIP30C	70p	2N3819	22p
BC182L	10p	TIP31C	65p	2N3904	8p
BC184	10p	TIP32C	80p	2N3905	8p
BC184L	10p	ZTX107	14p	2N3906	8p
BC212	10p	ZTX108	14p	2N4058	12p
BC212L	10p			2N5457	32p
BC214	10p			2N5458	30p
BC277	19p	1N914	4p	2N5459	32p
BC478	19p	1N4001	4p	2N5777	50p
BC479	19p	1N4002	4p		
BC548	10p	1N4004	5p		
BCY70	14p	1N4006	6p		

### DIODES

1N4148	3p
1N5401	13p
1N5402	15p
1N5404	16p
1N5406	18p

BZY88 series 2V7 to 33V 8p each.

### LINEAR

A SELECTION ONLY!  
DETAILS IN CATALOGUE.

709	25p	LM324	50p	NE556	60p
741	22p	LM339	50p	NE565	120p
747	50p	LM380	75p	NE567	170p
748	30p	LM382	120p	SN76003	200p
CA3046	55p	LM1830	150p	SN76013	140p
CA3080	70p	LM3900	50p	SN76023	140p
CA3130	90p	LM3909	60p	SN76033	200p
CA3140	70p	MC1496	60p	TBA800	70p
LM301AN	28p	MC1458	35p	TDA1022	650p
LM318N	125p	NE555	25p	ZN414	75p

### OPTO

LEDs	0.125in.	0.2in.	
Red	TIL209	TIL220	9p
Green	TIL211	TIL221	13p
Yellow	TIL213	TIL223	13p
Clips	3p	3p	

### DISPLAYS

DL704	0.3 in CC	130p
DL707	0.3 in CA	130p
FND500	0.5 in CC	100p



### RESISTORS

Carbon film resistors.  
High stability, low noise 5%.

E12 series. 4.7ohms to 10M. Any mix:

	each	100+	1000+
0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Megohm (650 res.)  
0.5W £7.50. 0.25W £5.70

### CAPACITORS

HERE ARE JUST  
A FEW OF THE  
CAPACITORS STOCKED

TANTALUM BEAD	each
0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V	9p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

### MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047	3p
0.068, 0.1	4p

### RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
			22	33	47	7p
						13p
			220			20p
25V	10	22	33	47		5p
	100					8p
		220				10p
			470			15p
	1000					23p
10V		220				5p
			470			9p
	1000					13p
		2200				23p

### 74LS

LS95	65p
LS123	56p
LS125	40p
LS126	40p
LS132	60p
LS136	36p
LS138	54p
LS139	50p
LS151	50p
LS153	50p
LS155	80p
LS156	80p
LS157	45p
LS164	90p
LS174	60p
LS175	60p
LS190	80p
LS192	70p
LS193	70p
LS196	80p
LS251	60p
LS257	55p
LS258	55p
LS266	40p
LS283	60p
LS290	55p
LS365	45p
LS367	45p
LS368	45p
LS386	35p
LS670	180p

### TTL


7493	34p
7494	52p
7495	52p
7496	50p
74121	25p
74122	33p
74123	40p
74125	35p
74126	35p
74132	50p
74141	56p
74148	90p
74150	70p
74151	50p
74156	52p
74157	52p
74164	70p
74165	70p
74170	125p
74174	68p
74177	58p
74190	72p
74191	72p
74192	64p
74193	64p
74196	55p
74197	55p

### CMOS

FULL DETAILS  
IN CATALOGUE

4001	15p	4029	60p
4002	15p	4040	68p
4007	15p	4042	54p
4011	15p	4046	100p
4013	35p	4049	28p
4015	60p	4050	28p
4016	35p	4066	40p
4017	55p	4068	20p
4018	65p	4069	16p
4023	15p	4071	16p
4024	45p	4075	16p
4026	95p	4093	48p
4027	35p	4510	70p
4028	52p	4511	70p
		4518	70p
		4520	65p

### SKTS

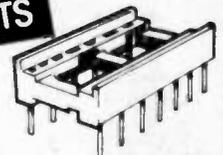


Low profile by Texas

8 pin	10p	24 pin	24p
14 pin	12p	28 pin	28p
16 pin	13p	40 pin	40p

Soldercon pins: 100: 50p  
1000: 370p

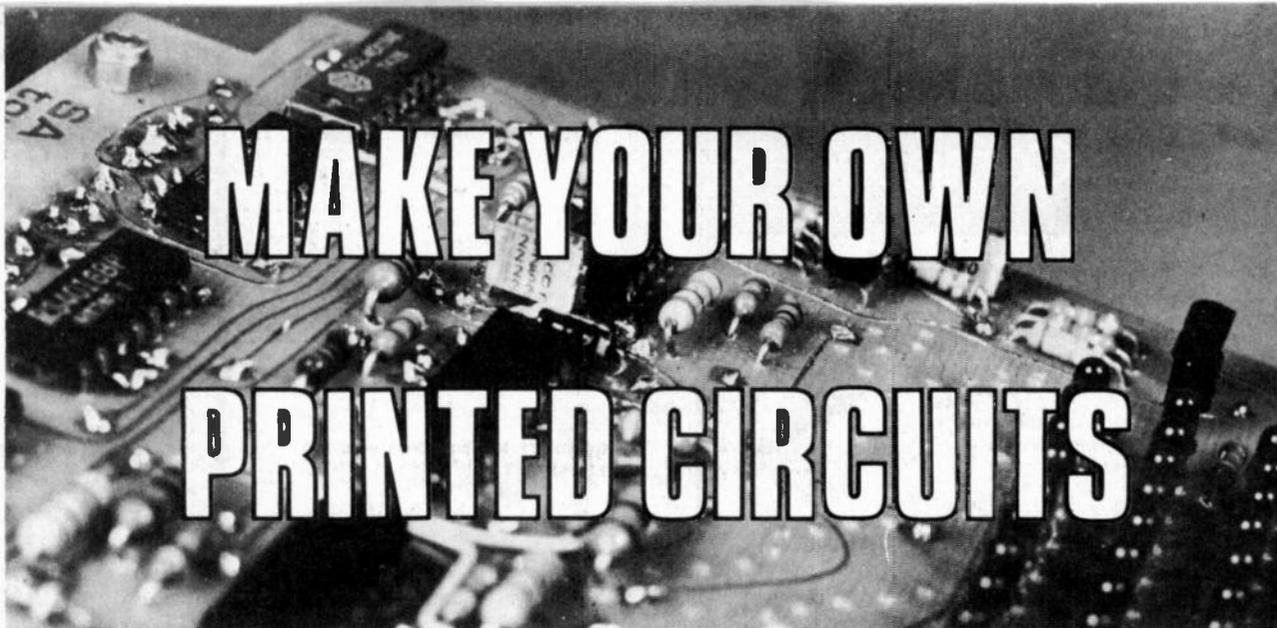AT LAST! OUR  
NEW 40 PAGE  
CATALOGUE  
OF COMPONENTS  
IS AVAILABLE.  
SEND S.A.E.





# MAKE YOUR OWN PRINTED CIRCUITS

**Making printed circuit boards is simple and makes project-building easier and the projects more reliable. Phil Cohen shows how it's done.**

IN ORDER TO AVOID using large numbers of wires to connect components together — which is a very costly, time-consuming and error-prone method — manufacturers of electronic equipment almost invariably use printed circuit boards (PCBs). These consist of a sheet of "synthetic resin bonded paper" (usually referred to as SRBP, for obvious reasons) on which there are copper tracks to connect the components electrically. The component wires are pushed through holes in the PCB and soldered onto the copper tracks on the other side (see facing page). This means that the components are connected together (with little possibility of error) and supported mechanically at the same time. This technique is not confined to industrial use, however, and many electronics enthusiasts use it to great advantage.

## WHAT YOU NEED

Although ready-made printed circuit boards are available for many Hobby Electronics projects (see advertisers in this issue), they tend to be rather expensive — although otherwise excellent — and many people may prefer to make their own. This can be done very cheaply with only a small outlay, the most expensive




**Clean the copper side of the board with sandpaper — be careful not to touch the cleaned surface, as this will cause trouble in later stages.**




item being a miniature drill. The other items required are a blank copper-clad board, an etching tray (must be plastic) and a quantity of ferric chloride etchant. These are all obtainable from electronic component stockists. The appropriate "HOBBY-PRINT" (as advertised in this issue) is also required, although those of you intent on doing things the hard way *could* use a PCB marking pen.



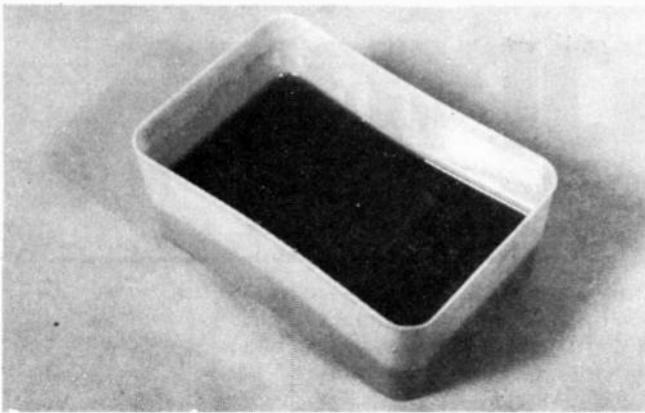
**Rub down the HOBBY-PRINT: This is done using a soft pencil. The parts of the HOBBY-PRINT which stick to the board will protect the copper from the etchant. A PCB marking pen *could* be used at this stage, but the pattern would have to be copied by hand (the pen is of the felt-tipped variety, filled with a substance which will resist the action of the ferric chloride when dry).**



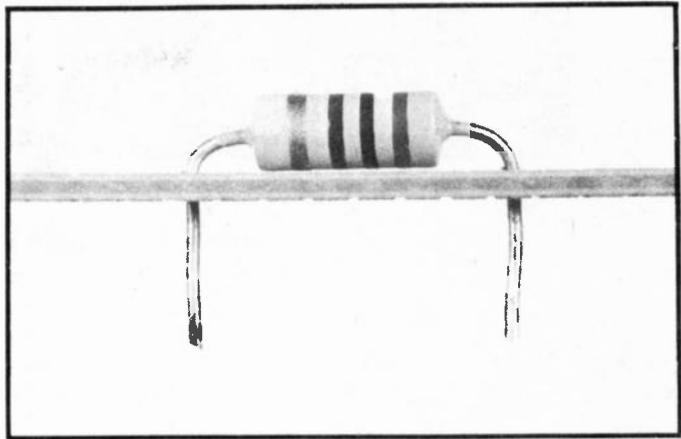
**Etch the board:** Following the instructions on the etchant bottle, dilute enough of the etchant to half-fill the tray. Put the board in the liquid *copper side down* and prop up one end of it with something non-metallic. Leave it for about 15 mins. The copper reacts to form a black powder which floats to the bottom of the tray.



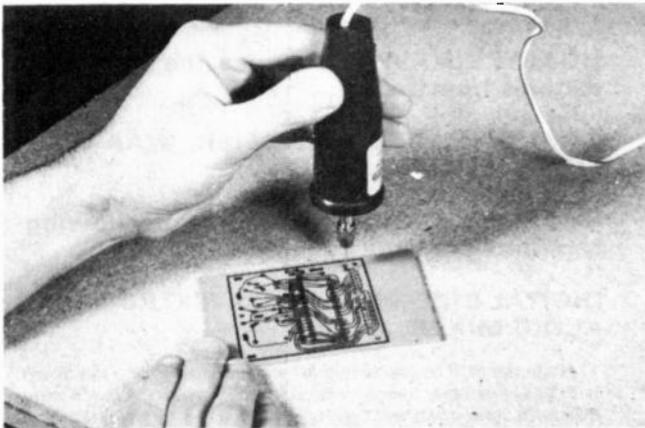**Insert the components one by one and solder them in.** Be careful not to bend the wires too close to the component body as this may damage it.



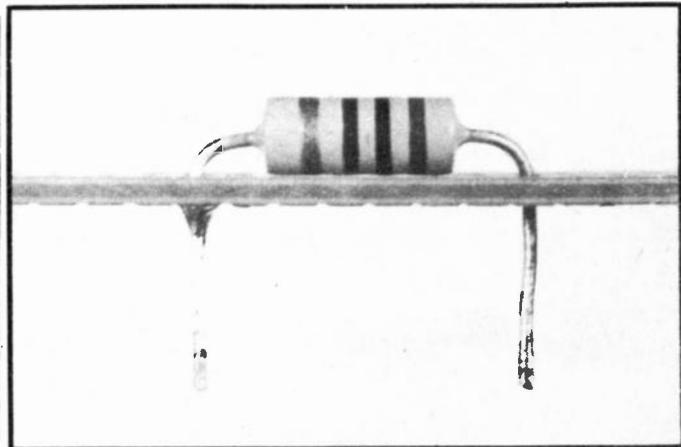
**Wash the board thoroughly** (the etchant will stain clothes and may be harmful to the eyes) and then drill the holes for the component wires. Small battery-driven drills can be bought which are ideal for this purpose.



**Solder the wire onto the copper strip** — apply the solder and the soldering iron at the same time. The solder should flow evenly over both the wire and copper track. Allow the solder time to solidify (about 5 seconds) before moving the board.



**Clean the resist from the board, again using sandpaper.** It is worth doing this thoroughly, as the board may otherwise be difficult to solder. Inspect the board carefully — there may be small breaks in the copper "tracks" due to scratches in the HOBBY-PRINT after it has been applied, or "bridges" from track to track due to fingerprints on the board before etching. Solder across any gaps and scrape away bridges.

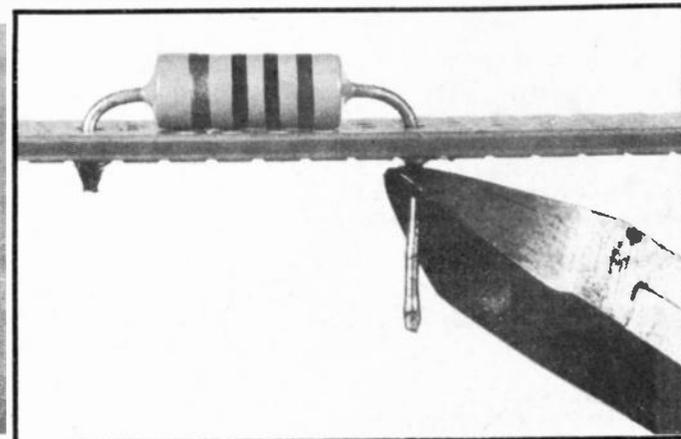

**Trim the wires to length.** This can be done using a pair of "side-cutters" as shown. Be sure to trim down to where the solder begins, to prevent the wire ends from touching each other when they are positioned closely on the board.

HE

# Hobbyprints

An easy, patented method of making PCBs for HE projects.

For some time it has been possible to buy acid resist rub-down pads and track — in fact we use them in the HE workshops and they work very well. HOBBYPRINTS take this idea a stage further — the complete PCB pattern is already on the sheet and can be rubbed down in seconds — and the patterns are nice and crisp, made from the original artwork, used for the prototype.

If you have the facilities for ultraviolet exposure, HOBBYPRINTS make excellent masters — being solid black on a translucent film. With this method you can use the HOBBYPRINTS time and time again!

HOBBYPRINTS are produced exclusively for HE, and the whole system is protected by patents 1445171 and 1445172. Each month we will be bringing out a new HOBBYPRINT, containing the patterns for each issue's projects.



**HOBBYPRINT A — contains the following patterns from issue 1:**

**5 WATT STEREO AMPLIFIER, WAA-WAA PEDAL. BEDSIDE RADIO.**

**HOBBYPRINT B — contains the following patterns from issue 2:**

**DIGITAL DICE. PHOTON (2). METRONOME. AUDIO MIXER.**

1. Clean the PCB as you would for any work giving it a rub down with fine sandpaper (we even supply this in the kit). A quick wipe over with lighter fuel will help to remove any grease marks.
2. Lay down the HOBBYPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a 'repair kit' on the sheet to correct any breaks!
3. Cut the board to size and put it in the Ferric Chloride.
4. When etching is completed, wash the board and use the sandpaper or a scouring powder to remove the resist. The resist pattern is pretty hardy but is easily removed at the final stage.
5. All you've got to do now is drill the board. Time? Only about ten minutes from beginning to end plus etching time (15 minutes usually with a good acid).

## ORDER TODAY

Send cheque or postal order (payable to Hobby Electronics) to:

**HOBBYPRINTS,  
HOBBY ELECTRONICS,  
25-27, OXFORD STREET,  
LONDON W1R 1RF.**

**75p INCLUSIVE OF VAT AND POSTAGE.**

Please mark the letter(s) of the HOBBYPRINTS on the outside of the envelope.



# Push-Button Dice



*We think this project will be a winner...*

GENERATORS OF RANDOM NUMBERS in the range one to six (dice to most of us), are essential items in games ranging from Ludo to Backgammon. This is fortunate for those of us who count electronics amongst our hobbies. Why? you ask, well the answer's simple. When asked what your hobby is, if in reply you answer electronics, as often as not this will be greeted with a yawn, pictures of boring theory and mountains of test gear being conjured up by the questioner. Bring out an electronic game, however, and all this changes. Electronics can be fun.

## NEVER SAY DIE

Unfortunately, most games, in order to be interesting, involve a lot of different factors that our electronics must keep track of. This, in terms of 'hardware' means lots of lamps, switches, and wire — complications. Happily, to build a dice, if our plans are followed, is an easy task, and will impress your friends as it is a distinct improvement over the traditional spotty blocks of wood.

## STRAIGHT AS A DIE

Our photographs show that our die is built into a small box that has a line of Light Emitting Diodes (LEDs) to represent the six numbers plus a push button. Operating the button will activate the circuit and when the button is released one of the six LEDs will be lit, the particular one being impossible to predict. The LED will stay on for about five to ten seconds before going out. The dice is now ready to be "rolled" again.

The dice does not have an on/off switch, as with the LEDs off the circuit draws such a small amount of current from the battery that such a switch is not necessary.

## CONSTRUCTION

As with any project, the exact method of construction is largely a matter of personal choice. The photographs clearly show how our dice went together, but there is no reason why you should not put your project in a different type of case. At any rate the first thing to do is to assemble the PCB according to our overlay.

The dice uses a type of IC known as CMOS and this reason we suggest that you use IC sockets when building the project as CMOS ICs are more electrically 'fragile' than other types of IC.

When mounting the components, make sure that the ICs and the electrolytic and tantalum capacitors are fitted

## Parts List

### RESISTORS (all ¼w 5%)

R1, 3, 5	100k
R2	10k
R4	56k
R6	470R

### CAPACITORS

C1	100n	polyester
C2	100u	16V electrolytic
C3, 5	10n	polyester
C4	100u	35V tantalum

### SEMICONDUCTORS

IC1	CD4011B
IC2	CD4017B
LEDS 1-6	TIL209

### SWITCH

PB1	Miniature push to make
-----	------------------------


### MISCELLANEOUS

PCB as pattern, PP3 battery plus clip, Vero box, wire, etc.


The ICs used in the LED dice are digital CMOS devices, the letter B after the number referring to the fact that the IC features protection devices at its input. Do not worry if the letter B does not appear in the adverts for these ICs as most CMOS devices on sale today are of the B series.

Careful scanning of the adverts in this issue of Hobby Electronics should locate suppliers for all of the components used in the LED dice.


**Approximate cost £4.50.**

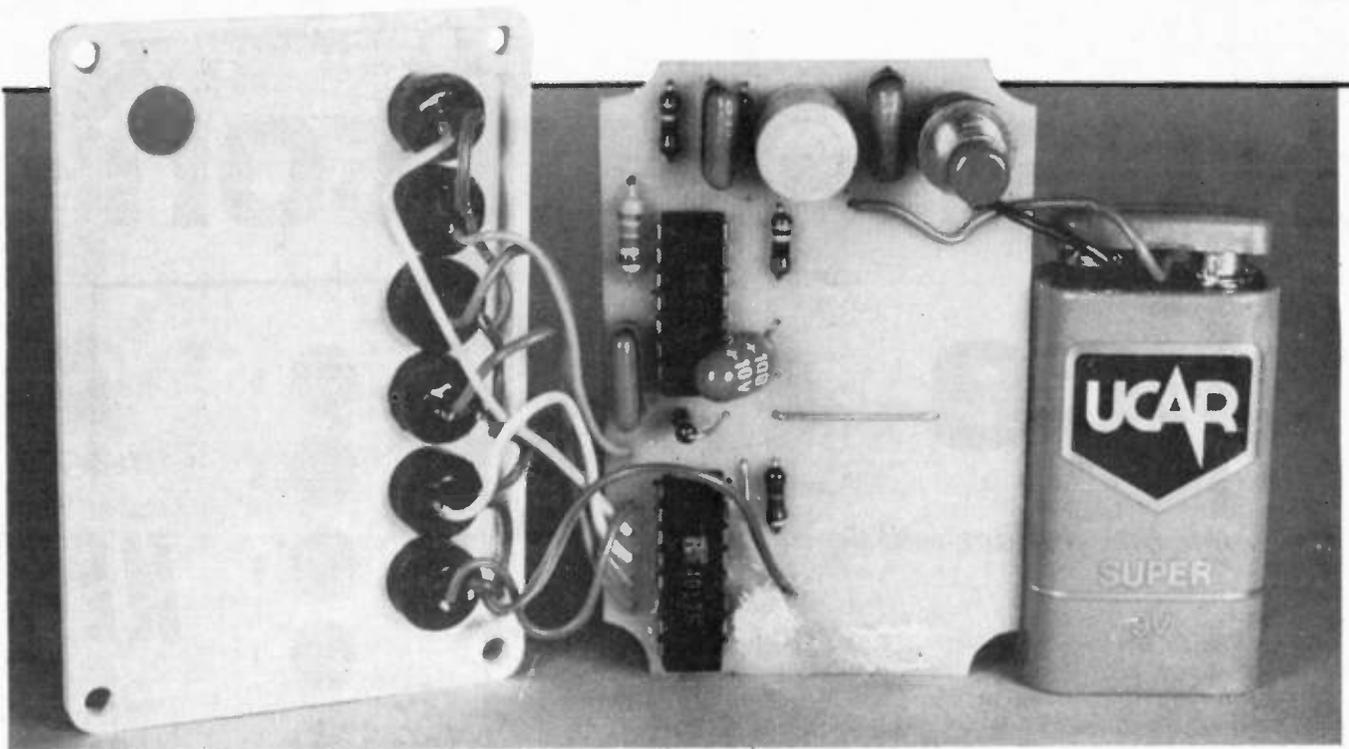

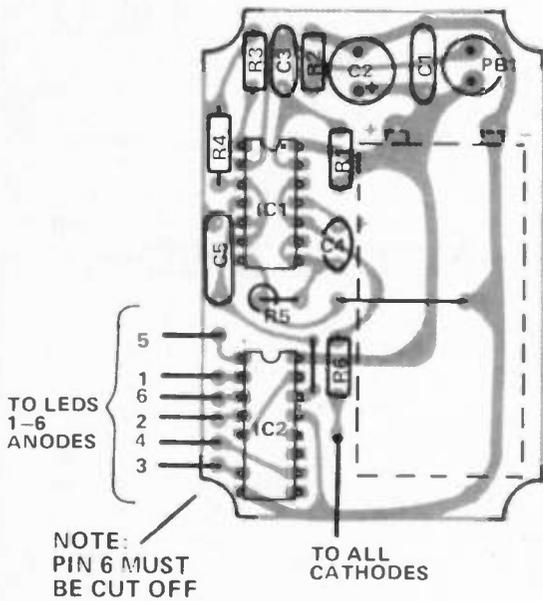
ABOVE: the case opened to show what makes the dice tick. LEFT: the 'component overlay' which links the circuit diagram with the above photo. BELOW: the pattern for the copper foil side of the printed circuit board.



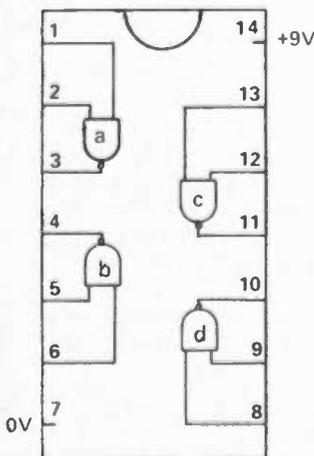Below: Pin out data for IC1 and LEDs 1-6.



a = ANODE  
k = CATHODE

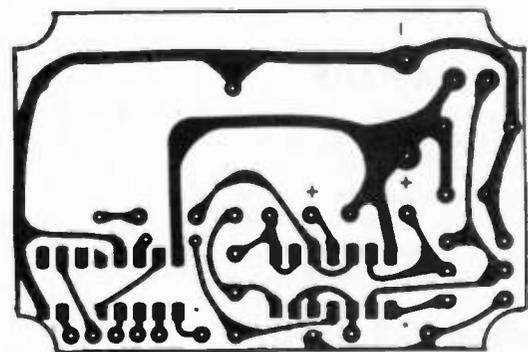

the right way round. Failure to do so will result in a dead LED dice.

When marking out the front panel take care that the LEDs are in a straight line. The LEDs are mounted with special mounting clips that should be available from the people who supply the LEDs themselves.

There is a fair bit of wiring to do so take care when doing this job. It's easy to make a mistake here, and any error can take a long time to find.

When all construction is complete, fit the battery and get ready to roll your first electronic die.


HE

Note: for tantalum capacitors



LEFT: Some tantalum capacitors are not marked with a '+' as in the photo. They instead have a dot on one side only.

# Push-Button Dice

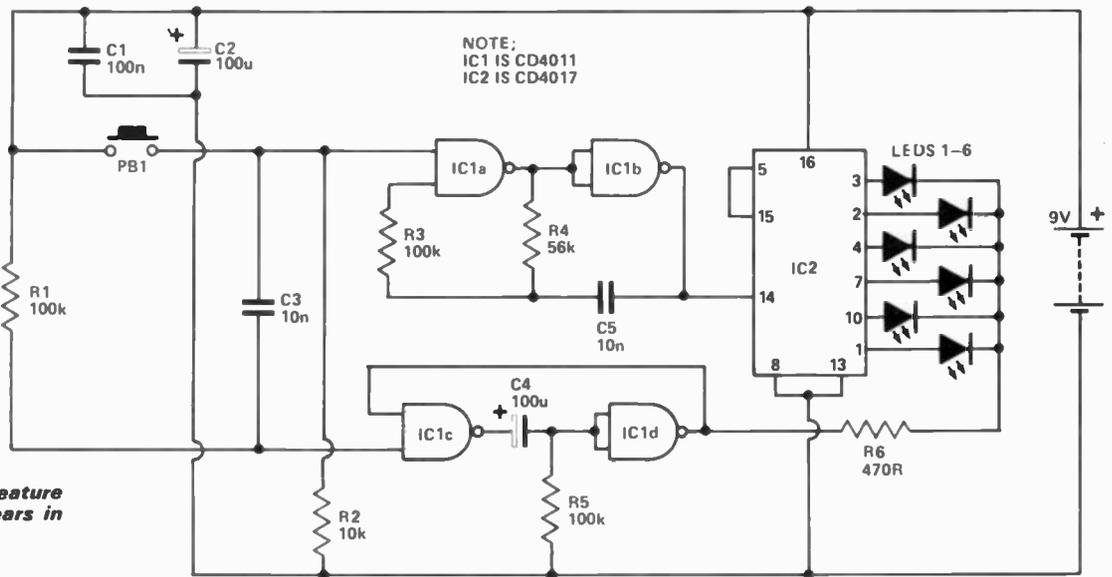

The circuit diagram. A feature on circuit symbols appears in this issue.

## How it Works

THE digital dice, in order to simulate the action of a real die, is required to "stop" with one of the circuit's six light-emitting diodes (LEDs) lit, each LED corresponding to one of the six numbers on the faces of the real die. To do this, it quickly turns each LED on in sequence when the start button is pressed, stopping with one LED on when the button is released. Because the circuit cycles through the sequence very quickly it is not possible to cheat by waiting for a particular LED to light and release the button at this point!

The circuit can be broken down into two sections, one dealing with the display and the other with timing and control signals. The latter are provided by two 'classic' circuit building blocks, namely the 'astable' formed by IC1a and IC1b and the 'monostable' configuration of IC1c and IC1d.

Each circuit is formed from two out of the four logic gates of IC1. The inputs of the logic gate can be in one of two conditions. They can either be 'low' (that is, near 0V), or 'high' (near to the supply voltage, 9V in this case). The output of the gate can also adopt only these two values, the choice being determined by the state of the inputs. In this case as the gates are 'NAND' gates the output will be high at all times except when both the inputs are high at which point the output will go low. 'NAND' stands for 'not-and', the output being low whenever both one input 'and' the other are high.

The astable will not function until the start button takes one of IC1a's inputs high. At this point the output of IC1b will oscillate between 0V and 9V. The circuit is referred to as an astable meaning 'not stable' because the output can assume these two conditions but is stable in neither.

A detailed description of the circuit would take up too much room but briefly the oscillator works like this: Suppose the output of IC1a is low and that as one of this gates' inputs is 'tied' high the other, connected to R3, must also be high. The junction of R3, R4 and C5 is thus high,

but as R4 goes to the output of IC1a, which is low, the charge on C5 will leak away. At some point the voltage at this junction, having fallen to near the 0V rail, will cause the output of IC1a to go high and that of IC1b to go low. C5 will now charge up via R4 which will in turn cause the circuit to assume its original state.


The series of pulses generated by the astable is fed to IC2. This is a counter IC, having ten outputs. As the pulses are fed to its input, each of the ten outputs will be turned on in sequence. For this circuit, however, we only want the IC to count up to six. To achieve this we connect the seventh output of IC2 to another of the IC's inputs called the 'reset' pin. When this pin is taken high it resets the counter back to the start. We now have our count of six.

The outputs of IC2 are taken to LEDs 1-6. LEDs are like ordinary diodes in that they will only pass current in one direction, but in addition when they are passing current will emit light. When an output of IC2 is high the associated LED will emit light if the common point to which the LEDs are taken, R6, is low.

R6 is taken to the output of IC1d. This point is normally high and thus the LEDs are all off. When the start button is released, however, the input of IC1c, junction of C3 and R1, goes low for a brief period of time and causes the output of this gate to go high. C4 'couples' this change to the input of IC1d and causes the output this gate to go low, activating the display and, by virtue of the fact that the output is also connected to IC1c, maintaining the high on the output of this gate. The charge of C4 will leak away, however, via R5 - and cause the circuit to assume the previous state after several seconds. This circuit is termed a monostable because it has two possible states, only one of which is stable (mono = one). It is necessary to include R6 in the circuit because the current passed by the LEDs must be limited to a safe value.

C2 and C1 are included to 'decouple' the supply that is, remove any fluctuations in the supply voltage that might upset circuit action.

# Choosing a Calculator

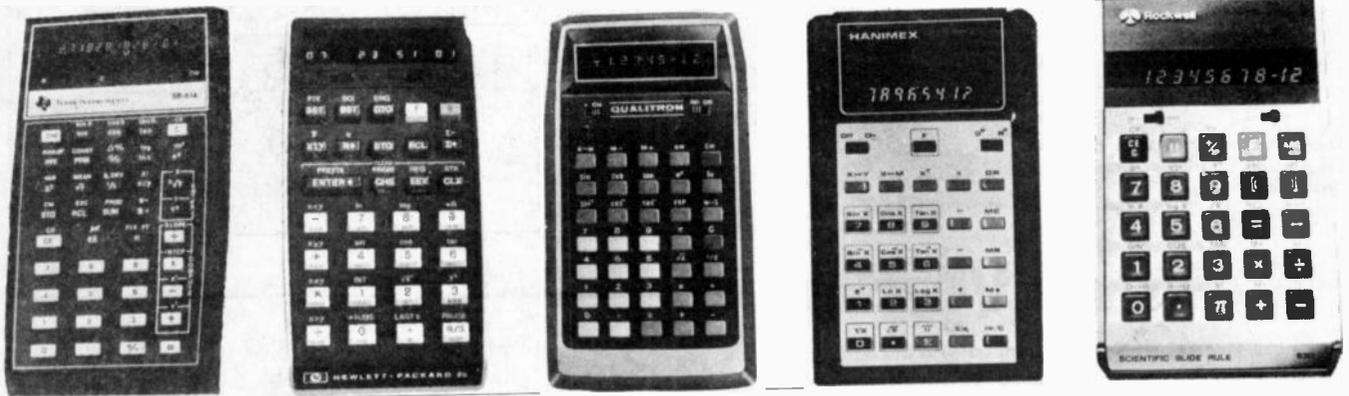

*A few years ago the pocket calculator would have been considered a miracle. Then it became a novelty and now it has become an everyday object. This rapid growth has brought with it a vast range of different calculator types and variants. Phil Cohen explains some of the more common jargon to help the prospective buyer choose.*

## FOUR-FUNCTION



### WHAT IS IT?

This means that the calculator can add, subtract, multiply and divide.

### WHO NEEDS IT?

These facilities are common to almost all calculators — even the cheapest.

For the majority of calculator applications these will be sufficient for adding columns of figures, calculating VAT and checking wage slips. On the other hand, while more advanced calculator functions are not essential, they are sometimes useful and always fun to play with!

## 8-DIGIT ACCURACY

12345678

### WHAT IS IT?

This refers to the fact that the calculator can work with numbers up to 8 digits long (such as 1.2345678 or 12345678).

### WHO NEEDS IT?

Calculator accuracy is, in general,

much better than is required. Eight-digit calculators have become standard (although some run to 12 digits) and it is very seldom, if ever, that their full accuracy is required for any application.

## OVERFLOW INDICATOR

Error.

### WHAT IS IT?

'Overflow' occurs when the calculator is asked to perform a calculation which will give a result too large to display (such as  $1 \div 0 = ?$ ). The calculator will then display some appro-

priate message or symbol.

### WHO NEEDS IT?

This is common to *all* calculators and advertisements sometimes mention it as a facility on cheap calculators which have few other facilities.

## CONSTANT



### WHAT IS IT?

Say, for instance, that you have a column of figures and want to find out what 8% of each of them is. If the calculator does not have a constant facility, you will have to enter each number and then  $\times .08 =$  after each one. Using the constant, all you have to do is to put in  $.08 \times K$  at the start and then enter each number in

turn and press the "=" key to find the answers. The calculator has remembered the ".08X" and saves you the trouble of re-entering it each time (See 'Programmable').

### WHO NEEDS IT?

This allows a repetitive calculation to be performed easily.



**FULLY-FLOATING**

1.23

**WHAT IS IT?**

A 'fully-floating' calculator can work in fractions. Calculators which are not fully-floating can only work in whole numbers. Calculators which can work in fractions have a decimal point key.

**WHO NEEDS IT?**

Very few calculators are not fully-floating and the ones which are not are usually the very cheapest. It is well worth the extra expense to be able to work in fractions of a pound rather than to have to work in pence.

**PERCENTAGE KEY**



**WHAT IS IT?**

The percentage key is a convenience function, used to reduce the number of keystrokes in calculations.

**WHO NEEDS IT?**

If you want to find out what 12.2% of

43 is, you could use: " $12.2 \times 43 =$ " or " $12.2 \div 100 \times 43 =$ " or, if your calculator has a percentage key: " $12.2\% \times 43 =$ ". Each will give the same answer, but the third is easiest to understand.

**SCIENTIFIC NOTATION**

1.23 04

**WHAT IS IT?**

When working with very large or very small numbers, an 8-digit calculator cannot display any number greater than 99 999 999 or smaller than 0.000 000 1. One way of getting round this is to move the decimal point around in the number and display the number and the number of places the point has been moved.

$$\begin{array}{r} 1234.5 \\ \underbrace{\hspace{1.5cm}}_{=3} \\ 1.2345 \quad 3 \end{array}$$

Notice that you can get the original number back again by multiplying the value shown by 10 a number of times. The number of times is the number shown to the right.

$$\begin{aligned} 1.2345 \quad 3 &= 1.2345 \times 10 \times 10 \times 10 \\ &= 1234.5 \end{aligned}$$

3 times

With very small numbers the number-of-times-to-multiply-by-10 (also called the *exponent*) is negative, this means *divide* by 10 three times.

$$\begin{aligned} 1.23 \quad -3 &= 1.23 \div 10 \div 10 \div 10 \\ &= 0.00123 \end{aligned}$$

3 times

**WHO NEEDS IT?**

Most 'scientific' applications will require this facility (including school work after the age of about 16). ↗

---

## ALGEBRAIC LOGIC

$$(1+2) \times 3 =$$

### WHAT IS IT?

This refers to the organisation of the machine — a problem entered on an algebraic logic calculator is entered as it is written. The alternative to this type of organisation is 'Reverse Polish Notation' (see inset).

### WHO NEEDS IT?

In general, algebraic logic is the easier to use but RPN has its advantages — it is faster (once learned), does away with the need for brackets and is used in the more advanced scientific calculators.

---

## MEMORY

M

### WHAT IS IT?

By using a calculator's memory, any number which has been worked out on the calculator can be stored for future use while the calculator is being used to work with other numbers. Many calculators have several memories which can be used independently.

writing down the number for future use (although if the calculator is switched off it will suffer a sort of electronic amnesia and forget everything). In the example given in 'Parenthesis' the following key sequence could have been used: (M = 'store in memory' key, MR = 'recall from memory' key)

"2 × 5 = M 3 × 4 = + MR ="

The number 10 would have been temporarily stored in memory.

### WHO NEEDS IT?

The use of memory is equivalent to

---

## SUMMING MEMORY

M+ M-

### WHAT IS IT?

The M+ button adds whatever is being displayed to the memory. The M- button subtracts the display from the memory.

2 9  
6 14  
4 3

and you want to find out what  $(2 \times 9) + (6 \times 14) + (4 \times 3)$  is, the easy way to do it on a calculator with memory would be "2 × 9 = M+ 6 × 14 = M+ 4 × 3 = M+ MR"

This does away with the need for brackets in this example.

### WHO NEEDS IT?

If you have two columns of figures

---

## FOUR-FUNCTION MEMORY

M+ M- MR MC

### WHAT IS IT?

This means usually that the memory can be added to, subtracted from, recalled or cancelled (set to zero). Some calculators also have Mx, which allows  $(2 + 9) \times (6 + 14) \times (4 + 13)$  to be worked out in a similar way to the example above.

### WHO NEEDS IT?

Memories in a calculator are useful only occasionally and even then require more effort than at first seems to be the case. The use of Reverse Polish Notation renders memories to a certain extent unnecessary.

---

## PARENTHESIS

( )

### WHAT IS IT?

Brackets. Parenthesis keys on a calculator are used in the same way that they are used when a problem is written down  $(2 \times 5) + (3 \times 4) = ?$  tells the calculator to work out  $2 \times 5$  and then add  $3 \times 4$ .

alternative is to do the following:

"2 × 5 = " answer. 10 — write it down.

"3 × 4 = " answer. 12 "+ 10 = " answer 22

Parenthesis is useful for evaluating formulae, but RPN is better (see inset on Reverse Polish Notation).

### WHO NEEDS IT?

This is useful, but not essential. The

---

## PROGRAMMABLE

lrrn run

### WHAT IS IT?

This facility allows the storage of a sequence of keys which can be 'played back' any number of times on request.


ture results from an experiment, say, and it is required to convert them from C to F, the key sequence for the conversion  $(\div 5 \times 9 + 32)$  can be put into the calculator and called up for each value in turn. This feature is very useful for engineering and science students.

### WHO NEEDS IT?

If you have a column of tempera-

# Choosing a Calculator

## CARD-PROGRAMMABLE

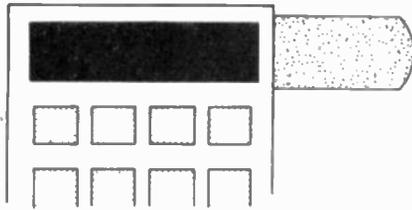

### WHAT IS IT?

This type allows you to store the keys which you programmed it with on a card about the size of a stick of chewing gum. The card is coated with a magnetic material similar to recording tape. A small motor in the machine draws the card through the calculator.

### WHO NEEDS IT?

This type of machine is so expensive that it is really only cost-effective for engineering consultants and astronauts. However, if you *can* afford one (at a couple of hundred pounds), they're probably great fun to play with.

## FULLY SCIENTIFIC



### WHAT IS IT?

This means that the calculator can work out square roots, logs, sines, cosines and other 'scientific' functions.

### WHO NEEDS IT?

These functions are in use from the age of about 13 upwards in the educational system and in any case are fun to play with.

## FUNCTION KEY



### WHAT IS IT?

This enables each key to be used for more than one thing. It works like this: there are two sets of markings on each key (usually one on the key and one above it). There is also a key set aside from the rest, usually marked with an F. After this key has been pressed, the next key will have the effect which is written above it.


### WHO NEEDS IT?

A function key allows more functions to be built into a machine of a given size. Unfortunately, it also makes it more difficult to use. Some machines have two function keys — each of the rest of the keys have three sets of markings on them in different colours. This makes the calculator almost impossible to use quickly. ↵

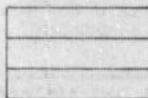
## REVERSE POLISH NOTATION (RPN)

There is a rumour that Reverse Polish Notation (or RPN) was so called because the most difficult European language to learn is Polish (or so the story goes) and people considered RPN to be about as easy to learn as Polish backwards. This in fact not the case. RPN is named after its inventor. RPN is also easy to use (once you get the hang of it) and very quick to work with.


What is RPN? In order to explain, let's look at a simple problem  $3 \times 2 + 1 = ?$ . Most calculators will give you the answer if you key in the problem as it is written. On an RPN calculator the problem would have to be entered as  $3, 2 \times 1 +$  (the comma represents the 'enter' key). This is not terribly easy to follow at first. An RPN calculator has what is usually referred to as a 'stack'. This is a pile of memories, one 'on top of' the other



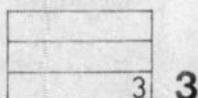
When the number 3 is entered in the example above, it goes into the lowest level of the stack. This is the memory which is shown on the display and so the display will show a '3'



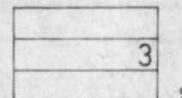
The 'enter' key (or comma as it is shown in the example) moves all the memories up one




The 2 now goes into the bottom memory

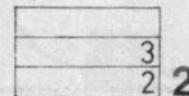

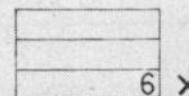
and the  $\times$  multiplies the bottom two and puts the result in the bottom memory



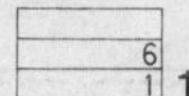The 1 goes into the bottom memory and pushes the results back up



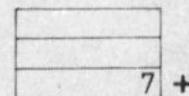and the  $+$  adds the two bottom memories and puts the result in the bottom. The display now reads 7.



RPN is not easy to learn — the easiest way to do it is to get hold of an RPN calculator and play with it. Once it has been learned, however, it does away with the need for brackets and makes calculations much easier.

## LED DISPLAY



### WHAT IS IT?

This is the type of display which is common on the cheapest and the most expensive calculators — not on the medium-priced ones! The display is made up of dozens of tiny light-emitting diodes (LEDs) which glow red when energised.

### WHO NEEDS IT?

The disadvantage of LED displays is that they consume a lot of current — that is, they wear out batteries quickly. The advantage is that they change very quickly, giving an instant indication of whether a key has been pressed.

## LCD DISPLAY



### WHAT IS IT?


This type of display changes colour, parts of it going from clear to opaque to form numbers.

### WHO NEEDS IT?

LCD stands for liquid crystal display. This consists of a fluid between transparent conductive plates. When a voltage is supplied to the plates the

fluid becomes opaque. As this process is essentially chemical, it is very much slower than the LED type of display and this, especially if coupled with an absence of key-click (see, above), makes it difficult to tell whether a key has been pressed hard enough. LCD displays take about  $\frac{1}{10}$ s to change (typically). The major advantage of LCDs is that they use very little power, extending battery life.

## RECHARGEABLE

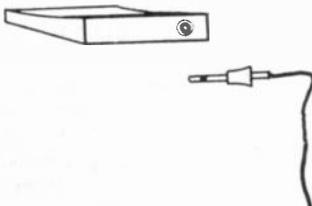

### WHAT IS IT?


Rather than having to change batteries every so often, it is very useful to be able to recharge the existing ones. Unfortunately, this requires special batteries.

### WHO NEEDS IT?

There are two disadvantages to rechargeable batteries. One is that they are expensive (in the short term).

The other is that the amount of charge they hold is limited to a few hours continuous usage (for LED calculators), which is less than it seems. This means that the calculator has to be recharged (which usually takes about 12 hours) every couple of weeks, depending on how often the machine is used. Normal batteries will last several times as long and buying a new set is a lot less trouble than recharging.

## MAINS ADAPTOR

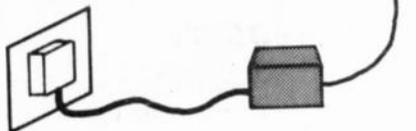

### WHAT IS IT?


This is a device which provides power in a form suitable for:

- recharging a calculator's batteries or
- running the calculator without its batteries or
- both a and b at the same time.

### WHO NEEDS IT?

When buying a rechargeable calculator, be careful that you take into account the price of the mains adaptor — the calculator is virtually useless without it. Most dealers include the price of the adaptor in the price of the machine.

## GUARANTEE

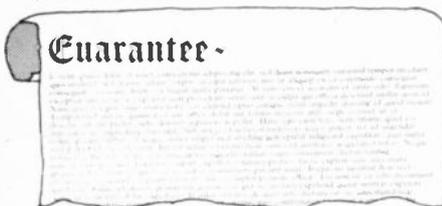

### WHAT IS IT?

Calculator guarantees are of the standard sort usually found with small electronic equipment — ranging from 90 days to 1 year.

### WHO NEEDS IT?

Calculators (especially the medium to expensive ones) are extremely reliable. As long as the machine works when it is bought and is not maltreated subsequently, it should last until the keys wear out — which is not covered by the guarantee in any case.

## KEY SIZE



### WHAT IS IT?


The major advantage of large calculators is that the keys are easier to hit. The disadvantage is loss of portability.

### WHO NEEDS IT?

People with large fingers shouldn't buy calculators with small keys. Don't be blinded by the compactness of a small machine — it is more difficult to use.

# Choosing a Calculator

## KEY-CLICK

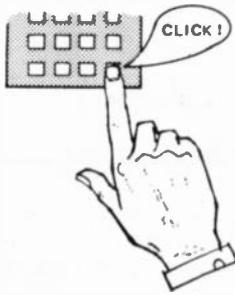


## WHAT IS IT?

This is exactly what it says. When you press a key in, it goes "click". On some calculators the keys are silent, but a small loudspeaker in the device goes "beep" every time a key is pressed.

## WHO NEEDS IT?

This is essential if the calculator is going to be used as anything except a toy. It is surprisingly difficult to tell whether a key has been pressed hard enough if this facility is not present. On the other hand, some manufacturers go too far and make keys which have to be pressed down very hard. The optimum depends on the individual.

## ULTRA-SLIM

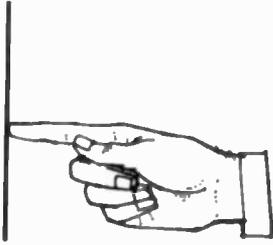


## WHAT IS IT?

LCD technology (see above) has made it possible to produce calculators which run off hearing-aid batteries. This means that they can be made very thin indeed (less than  $\frac{1}{4}$ " thick).

## WHO NEEDS IT?

The major advantage of ultra slim calculators seems to be that they will not produce an 'unsightly bulge' in the breast pocket. The disadvantage is that the key depression distance is limited, making the keyboard more difficult to use.

## ULTRA-SMALL

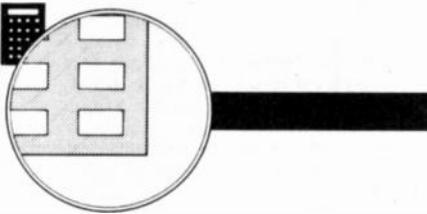


## WHAT IS IT?

The same advances which make ultra-slim calculators possible also make it feasible to produce calculators which are so small that a pencil has to be used to press the keys!

## WHO NEEDS IT?

This is all very well if you have pencil-shaped fingers, but not so good if you don't. To be fair, this sort of device is not much use for the 'serious' user (i.e. someone who wants to use the machine for arithmetic) but makes a good birthday present.

## WRIST

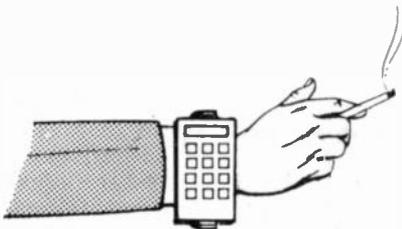


## WHAT IS IT?

For those who feel they may be smitten by the urge to calculate at a moment's notice, there are some calculators available which come complete with a watch-strap and are of a size comparable to a watch.

## WHO NEEDS IT?

Personally, I think this sort of thing is very silly indeed, although I suppose there must be *someone* who finds them invaluable.

## STOPWATCH

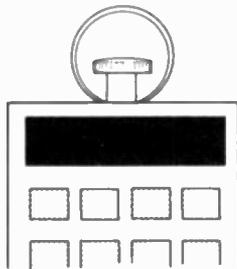

## WHAT IS IT?

One notable exception in the novelty calculator market is the calculator-plus-alarm-clock-plus-stopwatch. These are usually small enough to be carried in a pocket and consist of a display (LCD) capable of showing either the results of a calculation or the time of day, date, et cetera.

## WHO NEEDS IT?

These machines are very useful —

especially for reminding the user about parking meters, appointments, and so on (they're not loud enough to wake the user — well, not loud enough to wake me, anyway). In this combination of calculator-plus-clock the calculator is the tail which wags the dog — these devices are advertised as calculators although a miniature clock would probably be just as useful. The advantage of having the calculator in the same device is that it saves you carrying two devices.

# electronics today

international

What to look for in the January issue: On sale Dec 1st

## CLICK! ELIMINATOR

Fed up with low quality records? Had a hard day and dropped your favourite LP? Kiddies used Bach for target practice?

We can help — do not despair.

Next month we present a design to remove the clicks and scratches from records. The system works in a novel manner, and the system can be built at a fraction of the cost of commercial units.



## DIGITAL TACHO

Compact, easy to build, 10 rev resolution, fast response due to PLL technique and a range to 9999 rpm. With all that going for it how can you afford to miss it? Suitable for standard, CDI, and transistor assisted ignition systems.

## LOG/EXP CONVERTER

This design can be set up for either log or exponential conversion, and incorporates a neat heater for temperature stability. Has an eight octave range.

Articles mentioned here are in an advanced state of preparation but circumstances may affect the final contents.

## LOUDSPEAKERS PRINCIPLES



An article to explain what goes on behind the grilles on those large wooden boxes dominating the living room. All the major types will be covered, moving coil electrostatic piezo-electric etc, as well as explanations of the different methods of 'loading' the units to do their job better.

## computing today no 3

NEWBEAR'S BEARGAGS are an economical way of adding extra power to any small system. Next month we take a look at a typical bag — the petitevid VDU II kit.



### BASIC II

Tandy's level two BASIC upgrade for TRS-80 machines is now available in this country — what extra power does this conversion provide?

COMPUTERS IN BUSINESS. A look at how one small businessman uses a microcomputer at work.

# Kit Review

## —PROGRAMAGAME

***With some TV games costing about a tenner, why should anyone buy a kit costing three times as much? However when the kit gives ten times as much enjoyment it should be taken seriously. We got our hands on this unit from Teleplay and put it through its paces . . . . .***


WHEN TELEVISION GAMES were first introduced to the mass market they were all very simple — to play rather than make. The early versions used hundreds of separate logic devices, to produce two bats and bouncing ball — all the sound effects and scoring were performed by the players! These early units were produced by an American company by the name of Magnavox. It was up to another company, General Instruments, to produce a 'dedicated' circuit that was capable of generating display, score and sound effects. This pioneering device was the AY-3-8500, which had a

repertoire of six games. Two of these games needed an external 'rifle', with built in light sensor and trigger, needless to say most game sets using the 8500 came without the 'rifle' — limiting the games to tennis, football, squash and solo squash.

Since the early days of the now obsolete AY-3-8500, General Instruments have developed several new games. Now you can emulate James Hunt, Evil Knevil or Rommel on your TV set, and the basic games now include basketball and target games that do not need a special 'rifle'.

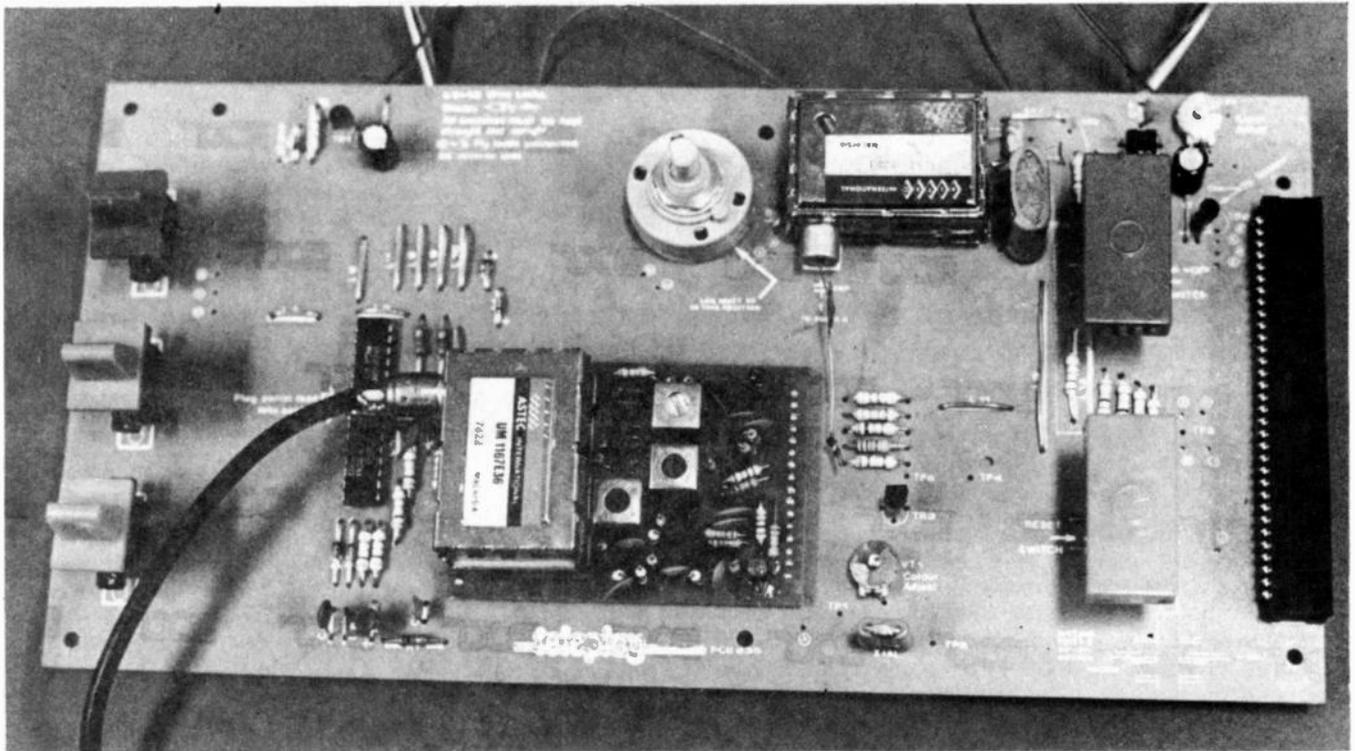***The assembled programagame with game cartridge in place and hand controls connected***





The programagame PCB.

## HOW IT CAME

The kit was packed in several plastic bags, inside an expanded polystyrene container. The resistors, capacitors, transistors, etc were all in the same package. After sifting through all the parts and packs, to check them against the parts list, it became apparent that a rogue joystick pack had been included — and no mains adaptor at all!

There are different types of hand controller for different cartridges, the pack that had been included was meant for the stunt rider cartridge. A phone call to Teleplay produced apologies, the correct joystick pack and a mains adaptor by the next post. While waiting for them to arrive the main unit and cartridge were assembled.

## ASSEMBLY

Construction is simplified by only having a single printed circuit board (PCB) and virtually everything fits directly on to it. First step was to fit all the wire links, resistors, diodes and capacitors — followed by the integrated circuits, crystals and transistors. As all the component reference numbers are clearly silk screened, on the board, the assembly was very straightforward.

The colour modulation circuitry is supplied pre-assembled on a small PCB, which fits on top of the main board, and is fitted like a large integrated circuit. All six switches were mounted on the PCB and the 32 way edge connector (for the plug-in cartridge) soldered in place at this point. After the switches were installed the board was mounted in the upper half of the console box. Both the DIN connectors (for the hand controllers) were supplied with leads fitted and the loose ends were

remaining part of the console were the loudspeaker and power socket, which is a 3.5mm mini jack. From start to finish, the console took about two hours to construct.

Compared to the console, the cartridge was a doddle, with less than a dozen parts on the PCB — it took only ten minutes to assemble. With the console and cartridge assembled it only needed power, the hand controllers, and a colour TV to try the system out. Each hand controller took a further ten minutes to assemble, then came the moment of truth!


## TRYING IT OUT

After a final check to see if everything looked correct a TV was connected to the Programagame and the system switched on. Hey presto! Nothing, apart from a plip plop out of the loudspeaker. Of course, I'd forgotten to tune in the TV to the channel that the game was transmitting on. A quick turn of the dial soon found a game of basketball in full colour, but the bats wouldn't move.

A bit of detective work soon uncovered the culprit — me. I'd missed out a couple of the pins on the 32 way edge connector when soldering it, when soldered the bats worked. All the games worked as expected, and the three handicap switches also functioned correctly — changing bat size, ball size and speed.

Overall the Teleplay Programagame kit is well thought out, the 12 pages of instructions contain enough information for most people to build it. With the availability of different game cartridges it is an economical way of having fun with your TV, and not getting completely bored with the same game selection, over and over again.

## SLOT IT IN

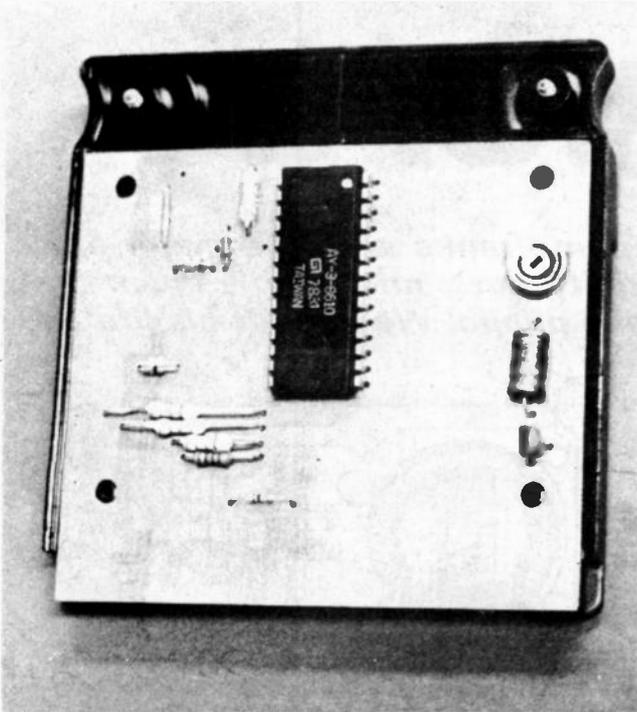

Inside the game cartridge.

The main drawback for the home constructor to all the games has been cost. Each time a new game is released the design of a complete system is published, but you have to purchase a case, power supply and hand controllers. As well as the hardware duplication, you also end up building identical blocks of electronics, to produce oscillators, colour encoders and VHF modulators for each separate game.

The Teleplay Programagame is designed as a main console, with all the common electronics inside — the actual game circuit is fitted inside a plastic cartridge, which slots into the console. In this way it becomes a simple matter to update the unit, as new games become available, you just plug in a new cartridge.

With the basic kit you receive a ten game cartridge that enables you to play football, basketball, tennis, gridball, hockey, target, squash and solo basketball, squash, target. All the games use the joystick hand controllers, which give bat movement across as well as up and down.


All in all, the kit, at about £30 is enjoyable to build, well thought out and, with the variety of games, is far more enjoyable to play than most of the offerings in this field.

HE

The programagame kit in this article was supplied by Teleplay (at 14 Station Road, New Barnet, Herts EN5 1QW).

## TEE-HE!

### HOBBY ELECTRONICS TEE-SHIRTS

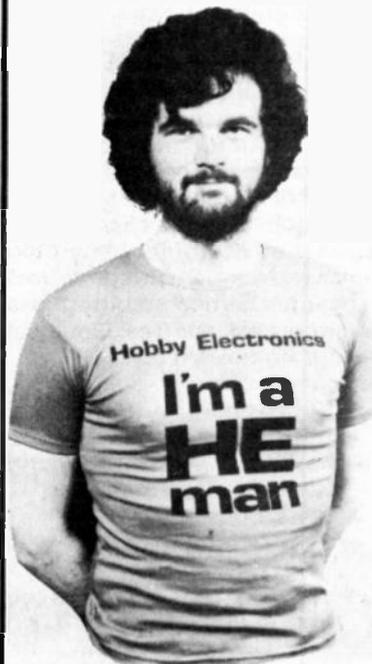

Join the He-men by sporting our cotton Tee-shirts. The photo shows Project Editor Gary Evans wearing a medium-size version — they're also available in Large and Small, please specify which when ordering. All inclusive price is £2.00 from:

HE Tee-Shirts,  
Hobby Electronics,  
25-27 Oxford Street,  
London W1R 1RF.

## HELP!

*If you have any trouble with HE project and you think that:*

- a) We've made a mistake in printing it,*
- b) You've made a mistake in building it and we can help or*
- c) Both,*

*then either send us a letter (with enclosed stamped addressed envelope) marked "TECHNICAL ENQUIRY" at the top or ring us between 3.00 and 5.00 on Tuesday afternoons. Corrections (if any!) will be published in Monitor.*


# The Tesla Controversy

*It is not doubted today that Tesla's name ranks with the major early researchers into the nature of electricity but some people claim that much of his work has never been made public. We look at his life and career . . .*

BY THE BEGINNING of the 1880s, electrical machines were finding their way into both the commercial and domestic fields. Although the nature of AC was understood, practically all motors and generators were DC. Electricity was becoming accepted and arc-lamps, electric lifts, photo-flood lamps and a wide variety of other devices were appearing.

In 1882 however, a young man Nikola Tesla who had been born in Smijan in what is now Yugoslavia, started to devote his undoubted talents to investigating AC. Tesla had the unusual flair for mental visualisation of highly complex ideas, a virtue shared by Faraday who was also working at that time.

At the end of 1883, Tesla exhibited a working model

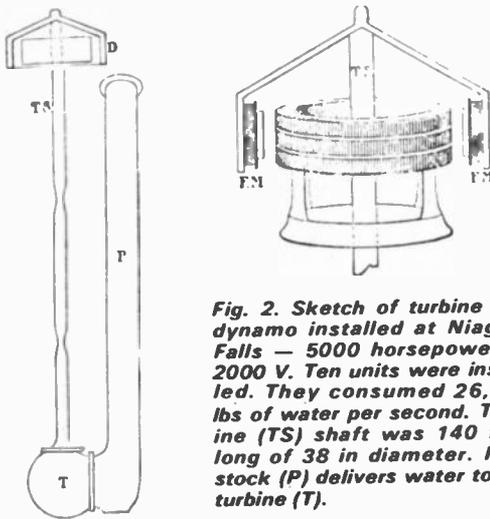


**Fig. 2. Sketch of turbine and dynamo installed at Niagara Falls — 5000 horsepower at 2000 V. Ten units were installed. They consumed 26,000 lbs of water per second. Turbine (TS) shaft was 140 feet long of 38 in diameter. Penstock (P) delivers water to the turbine (T).**

of an AC machine in Paris. (Figure 1 is one of Tesla's own pictures.) He then began a campaign hopefully to persuade the emerging electrical giants, such as the Continental Edison Company, that AC transmission was more efficient than DC and this resulted in a job offer to work with Edison in America. A chance soon came, the repair of DC generators in the ocean-going steamer "Oregon," for him to show his skills.

His work must have been good as he soon became Edison's chief assistant.

A few years later Tesla set up his own laboratory from which he finally reported (in 1888) the electromagnetic rotary field which enabled three-phase power transmission to be implemented. Shortly after this, George Westinghouse, of Westinghouse Electric Co., bought into Tesla's interests and built a hydro-electric system

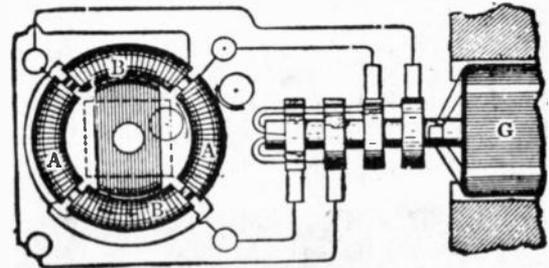

**Fig. 1. Diagram used by Tesla in "The Electrician" to explain how a rotating field may be produced by a poly-phase system.**


(see Fig. 2) of enormous proportion at Niagara Falls.

Tesla was a man of great generosity. It is said he tore up a contract binding Westinghouse to pay him \$12 million — saying that it was more important for the Niagara plant to keep the home-lights burning than for Westinghouse to become bankrupt because of a debt to him.

## TESLA AND RADIO

Notwithstanding his already significant work in power electrical engineering Tesla turned to thoughts of higher frequency (RF) currents — higher by far than the typical 100 Hz limit of power generators of that time.

The pioneers of radio had shown how a spark discharge, produced with an inductor and capacitor (Leyden jars to begin with) was finally proven to be an oscillatory process lying typically in the radio frequency band. Rigs that produced such discharges continued to be developed. The addition of a vibrating bell-like contact or spark-gap discharge arrangements produced a continuous train of discharges. When step-up transformer action was also incorporated, the Tesla coil was formed. (Another name is the Ruhmkorff coil.) Figure 3 is a 1910 Tesla apparatus.

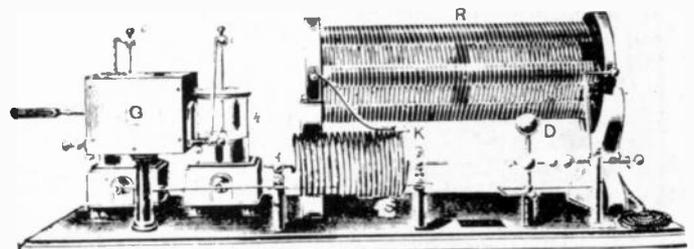

**Fig. 3. Modern (at least in 1910) Tesla coil apparatus.**

It was the spectacular things Tesla did with his radio frequency extremely high voltage generators that gained him so much fame. At a lecture to the American Institution of Electrical Engineers, given around 1891, he made a memorable impression being reported at the time as


*"his work places Tesla among the greatest of our present-day scientists and inventors, such as Edison, Graham Bell and Thomson."*

## MADE HIS MARK WITH SPARKS

Invitations poured in for his spectacular displays with man-made lightning and RF discharges. His equipment used two kinds of generator.

The first was a 384 pole AC dynamo running at 50 revolutions per minute to give 19.2 kHz. The other was a Ruhmkorff-type induction coil used with a condenser (capacitor) and a spark gap. This produced the then amazing half a million volts at "scores of thousands of cycles per second". It was the latter that impressed his audiences, for Tesla "brandished flaming swords like an archangel" — see Fig. 4 (or should it be arc-angel! — Ed).

Fortunately for everybody these RF discharges were

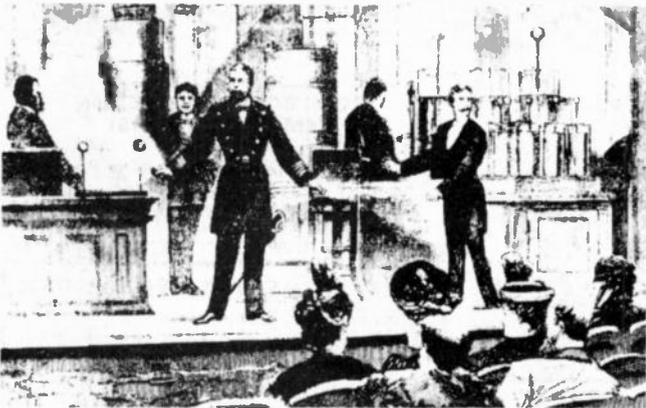


**Fig. 5.** A contemporary print of Tesla's experiments conducted in Berlin in 1894.

not lethal but Tesla said when about to try them out for the first time (experimenters were naive to say the least), "it was as if I were poised to jump from Brooklyn Bridge".

Demonstrations included drawing arcs between a string of people, as recorded, Fig. 5, in a contemporary magazine. Another was to make Geissler tubes (glass tubes filled with rarified air but having no electrical contact with external circuits) glow whilst suspended between, but well free of, the poles of high high-voltage transformer.

In his 1899 he built a huge experimental barn at Colorado Springs in Colorado — 30 metres long and 7½ metres wide on top of which was a 25 metre tower supporting a 60 metre mast. At the top was a 1 metre diameter copper ball.

He subsequently proved the earth is electrically charged at a high potential. The Los Angeles Free Press reported visionary ideas not yet exploited — use of the earth's resonance energy and the launching of waves of electrical energy to transmit power to places remote from generators. There was talk of charging the earth to produce tremendous voltages and of terminals to extract it. Tesla is said to have 'lit 200 incandescent lamps at a

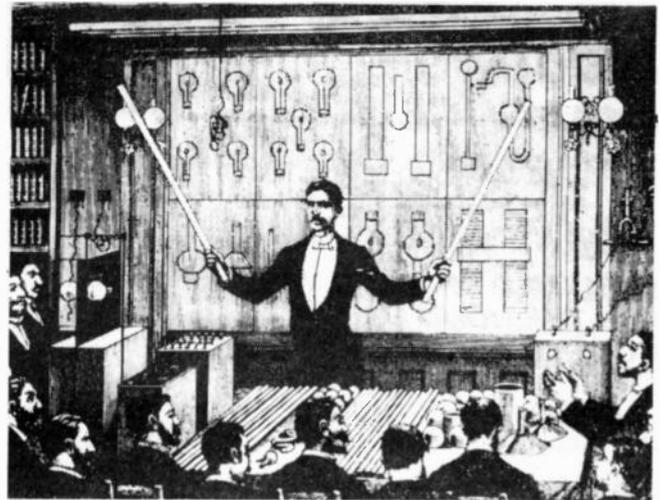

**Fig. 4.** Tesla amazed the scientific world in 1893 by holding glowing tubes aloft without any electrical connections being made to the tubes.

distance of 26 miles'. It is said his ideas failed to be exploited by commerce because the transmitted electricity could not be charged for.


## POWERFUL SECRET?

Tesla died in 1943, his last work being on the use of cosmic rays as energy sources. The Free Press report claimed that the FBI seized his papers and confiscated all of his reports.

Did Tesla have a unique and powerful secret? He certainly was a visionary, perhaps he did discover something great that is being withheld.

It has been suggested that the Russians have recently found out how his way-out experiments were done and in doing so have tapped some new form of energy. Frankly we doubt if there is any truth in the suppression — or rediscovery — of his work but a lot of people do not agree.

Today he is truly acknowledged. His name is used as the now adopted unit of magnetic field intensity and most laboratories possess Tesla-coils for ionising gas in evacuated tubes.

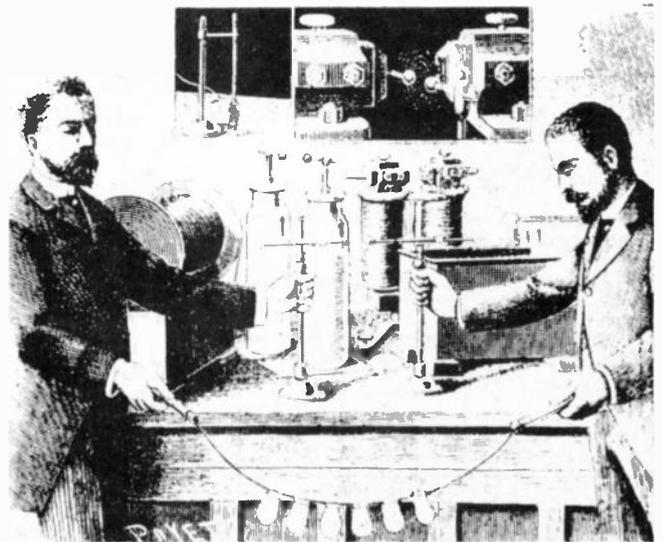

**Fig. 6.** This print of 1894 shows the laboratory equipment used in Tesla's experiments.

# SECOND GENERATION INDUCTION BALANCE METAL DETECTOR

DESIGNED SPECIALLY  
FOR THE HOME  
CONSTRUCTOR

**EASY  
TO  
BUILD**



**EASY  
TO  
USE**

- A second generation Induction Balance, system with improved Variable-Tone detection.
  - Designed by professionals for easy assembly by amateurs but with very good performance.
  - The search coils are fully assembled and adjusted for you.
  - Coils pre-assembled and tested wedge shaped search field
- Uses include:
- ★ Treasure hunting — it's amazing what you can find in the garden or on the beach.
  - ★ Finding lost metallic items.
  - ★ Locating waterpipes and cables under floorboards on in walls.
  - ★ Checking old timber for nails before cutting, etc., etc., etc.

**KIT - COMPLETE WITH PRE-ASSEMBLED SEARCH COILS**

**£16.50**

Plus £1-00p&p Plus £1-32 VAT

**ASSEMBLED & TESTED**

**£22.50**

Plus £1-00p&p Plus £1-80 VAT

Send sae for free components stocklist

**Communication Measurement Ltd**  
15 MALLINSON OVAL, HARROGATE, YORKS.

## TAMTRONIK LTD. (Dept. HE)

217 Toll End Road, Tipton  
West Midlands DY4 0HW. Tel. 021-557 9144

TELEPHONE  
OR LETTER



### ONE-STOP SHOPPING

PCB's, Components, Hardware, Cases, Part Kits and full Kits. A comprehensive service to the H.E. Constructor. Over 110 kits now available for projects from Electronics Today International, Hobby Electronics & Everyday Electronics. Prices include VAT. P&P 30p per order.

Mag. Issue	Project	Ref.	PCB	Component Pack	Hardware Pack	Case	Total
Nov. '78	Bedside Radio	H001	95	7.11	2.88	3.15	13.09
Nov. '78	Stereo Amplifier	H002	3.45	17.65	14.01	3.15	38.26
Nov. '78	Was Was (excl. pedal)	H003	80	1.31	3.59	—	5.70
Nov. '78	Digital Clock	H004	—	11.99	6.81	—	19.80
Dec. '78	Pushbutton Dice	H005	79	3.35	32	45	4.91
Dec. '78	Metronome	H006	61	1.24	1.26	1.65	4.76
Dec. '78	Photon Phone	H007	TBA	TBA	TBA	TBA	TBA
Dec. '78	HE Mixer	H008	TBA	TBA	TBA	TBA	TBA

#### A SPECIAL INTRODUCTORY OFFER

A voucher worth 10% of the advertised prices will be issued to purchasers of full or part kits of H.E. Projects. This offer is valid until 31st December, 1978. The vouchers may be redeemed against future purchases of ANY items offered for sale by Tamtronik Ltd. Send s.a.e. for free catalogue and any kit list, naming kit and kit reference.

TRADE AND EDUCATIONAL ENQUIRIES WELCOME

#### BARGAIN CORNER

100 x 1/2w 1k Carbon Resistors **30p**  
'Plug-In' mains PSU 3v/6v/9v/  
12v DC 300mA. Suitable for cal-  
culators and T.V. Games **£2.99**

Visit our shop at  
32 Market Place  
Great Bridge, Tipton  
West Midlands

# CLASSIFIED

#### MICROPROCESSORS AND COMPUTING

A book to give you a start  
Contents Binary Arithmetic, Principle of  
Operation, Programming, Glossary of Terms.  
50 pages of explanation and diagrams. Price  
£2.30 plus 45p p&p (cheques, crossed P.O.  
only).

Educational Data and Technical Services  
59 Station Road, Cogenhoe, Northampton  
NN7 1LU

#### ROCK BOTTOM PRICES ON SEMICONDUCTORS!

555 24p, 741 19p, JFET 741 35p,  
2N3819 14p, SCR 3A 400v 40p, P&P 20p.  
Lots more in the new mail order lists. S.a.e. to  
J. W. Rimmer, 367 Green Lanes, Harringay,  
London N4 1DY

#### ETCH RESIST TRANSFER KIT SIZE 1:1

Complete kit 13 sheets 6in x 4 1/2in  
£2.50 with all symbols for direct  
application to P.C. board. Individual  
sheets 25p each. (1) Mixed Symbols (2)  
Lines 0.05 (3) Pads (4) Fish Plates and  
Connectors (5) 4 Lead and 3 Lead and  
Pads (6) DILS (7) BENDS 90 and 130  
(8) 8-10-12 T.O.5. Cans (9) Edge  
Connectors 0.15 (10) Edge Connectors  
0.1 (11) Lines 0.02 (12) Bends 0.02 (13)  
Quad in Line.

#### FRONT AND REAR PANEL TRANSFER SIGNS

All standard symbols and wording. Over  
250 symbols, signs and words. Also  
available in reverse for perspex, etc.  
Choice of colours, red, blue, black, or  
white. Size of sheet 12in x 9in. Price £1.

#### GRAPHIC TRANSFERS WITH SPACER ACCESSORIES

Available also in reverse lettering, colours  
red, blue, black or white. Each sheet  
12in. x 9in contains capitals, lower case  
and numerals 1/4in kit or 1/8in kit. £1  
complete. State size.

All orders dispatched promptly.  
All post and VAT paid

Ex U.K. add 50p for air mail  
Shop and Trade enquiries welcome  
Special Transfers made to order

**E. R. NICHOLLS  
P.C.B. TRANSFERS  
Dept. HE/2**

**46 LOWFIELD ROAD  
STOCKPORT, CHES.061-480 2179**

## AD INDEX

AMBIT .....	2
BNRS .....	17
COMMUNICATIONS MEAS	72
DORAM .....	4
ELEKTRONIKIT .....	5
HENRYS .....	5, 8 & 17
IBEK SYSTEMS .....	9
MAPLIN .....	76
METAC .....	8
MINIKITS .....	9
JOHN MURRAY PUBLISHERS	
.....	5
NICHOLLS .....	72
RAMAR .....	9
STIRLING SOUND .....	9
STEVENSON .....	53
SWANLEY .....	8
TECHNOMATIC .....	9
TELEPLAY .....	74
TAMTRONIK .....	4
VIDEOTIME .....	4

# Good Evans

## Gary Evans shows us another peek at the latest developments

WHICH CAME FIRST — The customer or the chip? I ask because I remember the days when it was fairly obvious what any new IC from a semiconductor manufacturer was meant to do. Market research had been carried out, a "need" identified and the device to suit designed and manufactured, with its release accompanied by comprehensive application information. A clear example of this sort of process are the early days of Transistor Transistor Logic (TTL).

The first series of TTL was designated Small Scale Integration (SSI), this referring to the number of logic gates on one chip. As manufacturers got better at producing the ICs so the number of gates it was possible to put in a single chip rose — what to do with the extra power? Field surveys showed that the simple logic functions of SSI were being combined in certain ways (to, form shift registers, JK flip flops etc.) by many end users — it was obvious what to provide within MSI packages.

The manufacturers, being very clever, kept on packing more and more into less and less until we reach the situation today when it is possible to implement the equivalent of a whole army of TTL circuitry onto a single chip of silicon. This is the situation that prompted my initial question.

With so much "Power" available and so much money invested in the development of any particular device, it is impossible for the semiconductor manufacturer to dedicate an IC to one specific function (unless he can predict vast sales of this one product i.e. the AY-8500 TV games chip). Instead he must try and go for an all-singing, all-dancing device that will try to appeal to as many users as possible. The danger is, of course, that it will appeal to nobody.

An example of this latest breed of devices that I had to deal with the other day is the ICM 7217/7227 series from Intersil.

If I say that the ICs are four digit, presettable up/down counters with an onboard presettable register continuously compared to the counter, intended for use in hardwired or process control situations, capable of driving common anode or common cathode displays,

and providing either a decade count (9999) or timing count (5959)—you'll have some idea of an all-singing, all-dancing product.

People are undoubtedly going to use these ICs but one feels the device has no particular user in mind — It's rather a blitz approach.

### RISE AND CHIME

One of the most difficult things I find about doing my job is getting up in the morning. Enjoying my daily toil as I do, it's still an enormous task to convince my sleeping body that the time has once again come to report for work.

A few years ago I was woken up by the most effective of alarm clocks, organic based, it never failed to wake me and made the whole process of returning to the land of labour all the more pleasant by providing various foods to set me up for the day. The device was, needless to say unique and usually referred to as Mum.

My first digital clock met most of my requirements. It never stopped, didn't keep me awake by ticking and had an alarm that bleated for an hour — more than enough to overcome any early morning reluctance on my behalf.





Going back to my fondly-remembered organic system, though, I still missed some sustenance at waking up time. The solution was to build my own tailor made system based on the "STAC" timer from National.

This is a programmable timer that has four outputs each of which can be connected to various items of apparatus and can be switched on or off at four selectable times.

Connect one output to a kettle, one to the bedside lamp, another to the radio and the last to a loud buzzer and you have the perfect alarm system that can be adjusted to your own needs.

Radio first, followed by light and kettle with alarm timed to coincide with the boiling of the kettle, or perhaps kettle first with the rest going off in one go as the kettle boils — it's up to you.

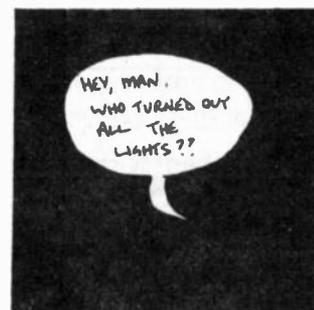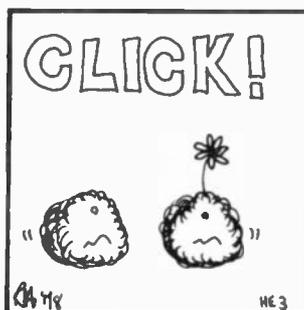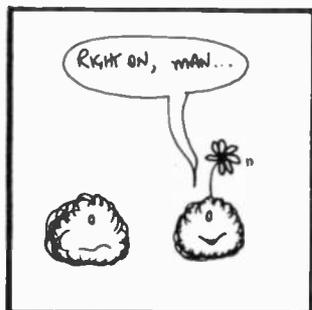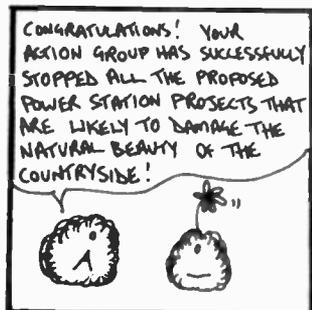It works for me — not only do I get to work on time but I'm able to get on with it when I arrive having been fortified with the vital early morning cuppa.






# Teleplay presents the PROGRAMAGAME of all time!

TELEPLAY have produced a new product of easy to assemble cartridge games, for you and all your family, that will not go out of date. Just ADD each new cartridge, as it becomes available, and your colour video centre will be up to date the Teleplay way. You will save pounds in the long run. Works OK on Black and White TV.


EX-STOCK IMMEDIATE DELIVERY

Money back if not satisfied

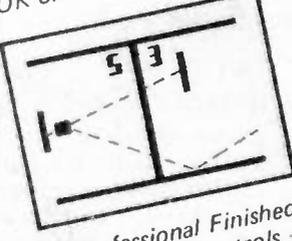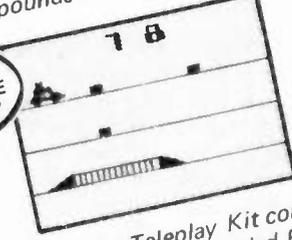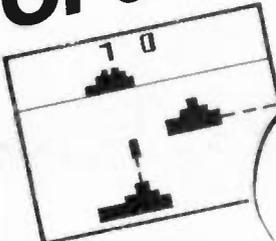We offer all this to you for ONLY **£28.95** + £2.36 VAT Fully Assembled **£35.95**




The Teleplay Kit consists of a Professional Finished Inject Moulded Box - Joystick Hand Controls - one cartridge which consists of 10 games - Football, Tennis, Solo Squash (1 & 2 players), Hockey, Basketball (1 & 2 players), Shoot etc. Mains Adaptor. All holes are pre-drilled - No Special equipment required. You'll be surprised how easy it is to assemble this professional kit! Instruction Manual supplied separately at 0.45p. TELEPLAY GIVES YOU TWICE THE FUN BUILDING AND PLAYING THE MOST PROFESSIONAL TV GAME KIT EVER OFFERED.

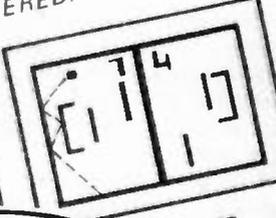

Main Console has 3 Facility Handicapping Switches.

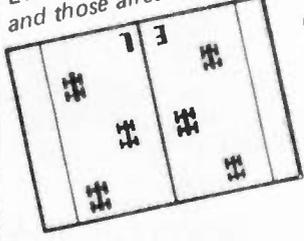Every 3 months a NEW game will become available to you and those already under production include Submarines, Space War, Wipe Out and many more. The price of these will vary from £12 to £19 depending upon the complexity of the game.



Additional cartridges NOW available include:

- Stunt Cycle - 4 games - Cartridges and Hand Controls - £14.95 + £1.14 VAT
  - Tank Battle - Cartridge and Hand Controls - £18.95 + £1.56 VAT
  - Road Race - 2 games - Cartridge - Controls already with basic kit - £12.95 + £1.08 VAT
- Fully assembled add £3.05

REALISTIC SOUND EFFECTS

All parts fully guaranteed.

Electrical knowledge is not a necessity to assemble this project - just simple soldering.

Cheques and Postal Orders to be made payable to TELEPLAY; send your order (No Stamp Needed) to Teleplay, Freepost, Barnet, EN5 2BR or telephone your order quoting your Barclaycard or Access number. Queries and Technical Advice offered either by phone or by calling at our shop.



**SHOP OPEN - 10am to 7pm - Monday to Saturday**  
CLOSE TO NEW BARNET BR STATION - MOORGATE LINE




Watch this page each month for new cartridges, as they become available. All prices include Postage. Compare our prices with similar products in the big stores, which cost well over £100. EUROPE'S LARGEST STOCKIST OF TV GAME COMPONENTS.



14 Station Road, New Barnet, Herts EN5 1QW Tel: 01-440 7033/01-441 2922

# Hobby Electronics


## RESISTOR COLOUR CODE

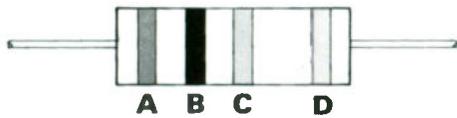

	A and B	C
BLACK	0	-- ohms
BROWN	1	-- 0 ohms
RED	2	- k -
ORANGE	3	-- k
YELLOW	4	-- 0 k
GREEN	5	- M -
BLUE	6	-- M
VIOLET	7	
GREY	8	
WHITE	9	

	D (tolerance)
NONE	20%
SILVER	10%
GOLD	5%
RED	2%
BROWN	1%

## CAPACITOR COLOUR CODE

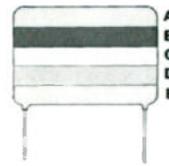


	C	D (tolerance)
BLACK	-- p	20%
WHITE	-- 0 p	10%
GREEN	- n -	5%
	-- n	
	-- 0 n	
	- u -	


	E (voltage)
RED	250 V

A and B: As for resistors.

## EXAMPLES:

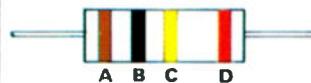

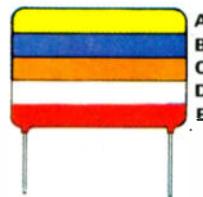A = 1, B = 0, C = -- 0 k, so value is 100 k; D = accuracy = 2%



A = 4, B = 7, C = -- n, so value is 47 n; D = accuracy = 10%; E = voltage = 250 V

## BRITISH STANDARD COMPONENT MARKINGS

M (pronounced mega) means multiply by 1 000 000,  
 k (pronounced kilo) means multiply by 1 000,  
 m (pronounced milli) means divide by 1 000,  
 u (pronounced micro) means divide by 1 000 000,  
 n (pronounced nano) means divide by 1 000 000 000 and  
 p (pronounced pico) means divide by 1 000 000 000 000.

So when we write 10 mV, we mean (10 / 1000) V, or 0.01 V. Note: it is usual to leave the "F" and "ohm" out altogether when writing, but as we rarely talk about resistances less than one ohm or capacitances greater than one farad, this does not cause too much confusion.

Examples: 10 uV = (10 / 1 000 000) V = 0.000 001 V; 330 R = 330 ohms (R is used for ohms when no multiplier is needed); 10 k = 10 000 ohms; 3.9 mV = 0.003 9 volts; 3.9 u = 0.000 003 9 farads.

Now, at some stage, someone decided to jazz up the system by putting the suffix in place of the decimal point, so that: 4k3 is 4 300 ohms and 4u9 is 0.000 004 9 farads.

Also, in case one of the digits got lost, it was decided that there should always be at least three numbers or letters in the value, so: 5k is written 5k0, et cetera.

Examples: 3M0 = 3 M ohms = 3 000 000 ohms; 4n5 = 4.5 nF = 0.000 000 004 5 farads.


## INTEGRATED CIRCUIT NUMBERS

TTL:



Example: DM 74121

CMOS:

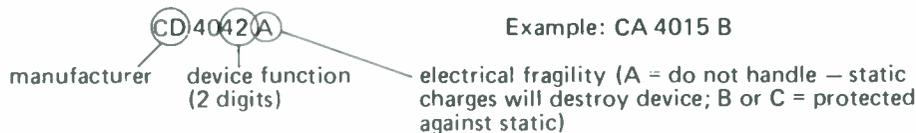

Example: CA 4015 B

OTHER TYPES:



Examples: LM 309, CA 3011, NE 555


# MAPLIN

everything for the modern D.I.Y. electronics enthusiast and more.



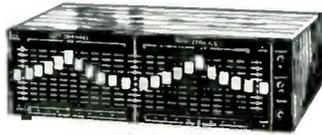
## 100W RMS STEREO DISCO

A genuine 100W RMS per channel (both channels driven) stereo disco with auto fade on microphone, VU meters, full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41 price 25p. Cabinet comes complete with lid and carrying handles.


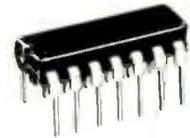
## 10 CHANNEL STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top flight hi-fi class. All this for around £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 25p. (All prices include V.A.T. and p.&p.).



## INTEGRATED CIRCUITS

Over 35 pages in our catalogue devoted to hundreds of useful I.C.s. All with data, pin connections and many with applications circuits and projects to build. Post the coupon now!




## VERY LOW-DISTORTION AUDIO OSCILLATOR

The very low distortion sine wave (0.01% output) is suitable for testing very high quality hi-fi audio equipment. Also includes square wave output. Range 20Hz to 20kHz. Output 0V to 1V in three continuously variable steps. Total cost around £21. Full construction details in our catalogue. Send the coupon below now! (All prices include V.A.T. and p.&p.).


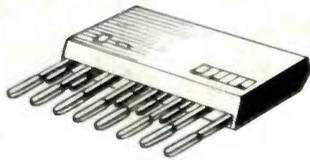
## TOUCH-SENSITIVE PIANO

The revolutionary new IC AY-1-1320 first seen on 'Tomorrow's World' now available. Complete kit of ICs to build a 60-note piano (18 x ICs) order as HQ53H price £36.86. Preliminary circuit details in our October newsletter. Complete design, pcb's attractive veneered wooden cabinet available soon. It's the most realistic-sounding electronic piano we've ever heard and includes simulated damping, loud and soft pedals. Full details in our newsletters. (All prices include V.A.T. and p.&p.).



## PEDAL UNIT

A completely self-contained pedal unit, 13-note, 2-Octave range, 4 organ stops. It can be added to any organ. A really unusual extra is the bass guitar stop which uses four envelope shapers to give a real bass guitar sound. A must for the solo guitarist. Full construction details in our catalogue — post the coupon below, now!



## SWITCHES

We stock a wide range of switches including a really low-priced high quality interlocking push-button switch system which is extremely versatile. We've got toggle switches, slide switches, push switches, rotary switches — there are dozens to choose from, but it's only a tiny part of our fantastic range.



## SYNTHESISER

The International 4600 Synthesiser. A very comprehensive unit. Over 400 sold. We stock all the parts costing less than £500 including fully punched and printed metalwork and a smart leak cabinet. Far less than half what you'd pay for a ready made synthesiser of equal quality. Specification on request. Full construction details in our construction book £1.50. (All prices include V.A.T. and p.&p.).



## 'PE' STRING ENSEMBLE

Unbeatable prices and finest quality components only when you buy from Maplin. All parts available to build this fascinating project. Component schedule available shortly (sae appreciated). Demonstration model in our shop soon. Phone now and compare our prices.



Our bi-monthly newsletter keeps you up to date with latest guaranteed prices — our latest special offers — details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).



## POST THIS COUPON NOW FOR YOUR COPY OF OUR 1979-80 CATALOGUE PRICE 75p

Please rush me a copy of your 280-page catalogue as soon as it is published (8th January 1979)

I enclose 75p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

## IT'S A FANTASTIC BESTSELLER!

216 big (11" x 8") pages! Over a thousand illustrations! Over 30 pages of complete projects to build! Thousands and thousands of useful components described and illustrated! No wonder it's a bestseller!

**DON'T MISS OUT! SEND 60p NOW!**

## MAPLIN ELECTRONIC SUPPLIES

P.O. BOX 3 RAYLEIGH ESSEX SS6 8LR  
Telephone: Southend (0702) 715155  
Shop: 284, London Road, Westcliff-on-Sea, Essex  
(Closed on Monday) Telephone: Southend (0702) 715157