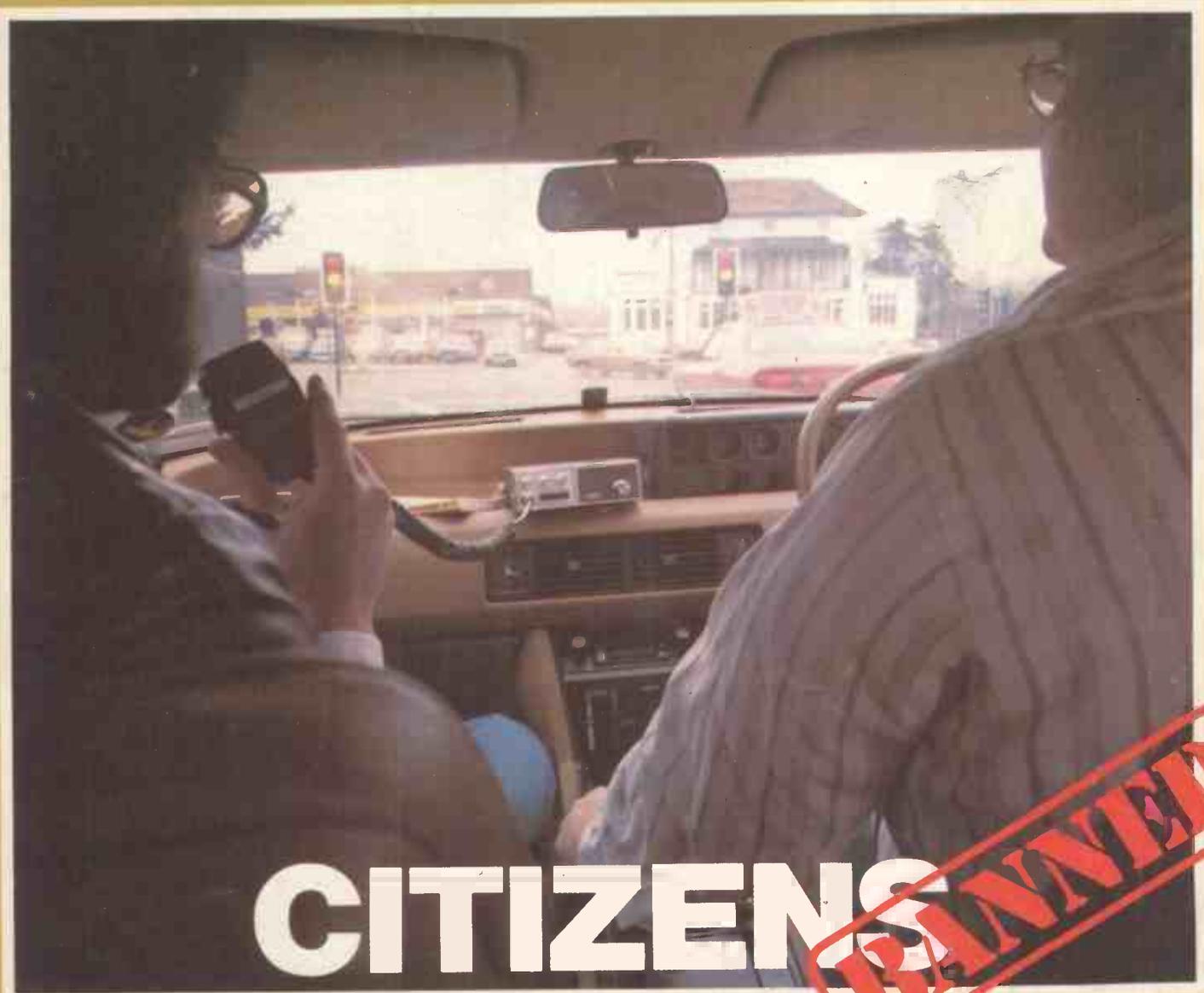


June '79
40p

Hobby Electronics



CITIZENS

BANKRUPT

Moving Coil Multimeters
The most useful piece of test equipment

ASDR Envelope Generator
Novel sound effects unit

GSR Monitor
Galvanic Skin Resistance

Display Techniques
A minor revolution

Drill Speed Controller
One for the handyman

Internal Resistance
Critical design factors in electronics

ambit international

The PW Sandbanks Metal Locator: a kit based on this recently published design for this uniquely effective type of metal locator is available for only £35.00 + 8% VAT. The kit closely resembles the appearance as published, except that a close fitting injection molded housing replaces the vacuum molded electronics box - to improve the environmental suitability of the construction. Carriage for complete kits £1.

The New Catalogue - "Tecknowledgey Part 2"

Part 2 of the catalogue: by the time this advert reaches the press, part 2 should be on sale. Sorry it's late, but it contains so many new and interesting things that we felt we had to hold up production to include them. Part three by the autumn and already there are many new items to go in! Part one 45p, part 2 50p. (inc PP etc).

Radio ICs

TDA1062	HF/VHF tunerhead	1.95
TDA1083	One chip AM/FM rx	1.95
TDA1090	One chip HiFi am/fx	3.35
TDA1220	One chip am/fm rx	1.75
HA1197W	HiFi AM tuner IC	1.40
CA3123E	AM tuner IC	1.40
TBA651	AM tuner IC	1.81
CA3089E	Famous FM IF system	1.94
CA3189E	As 3089+ deviation mute	
	AF preamp, adj, agc	2.75
HA1137W	Improved S/N 3089	2.20
TBA120	limiting amp+detector	0.75
TBA120S	high gain	1.00
MC1350P	agc'd IF preamp	1.20
MC1330P	synch AM/video detector	1.35
KB4406	Cascade IF preamp	0.65
ua753	limiting FM preamp	1.95

Communications circuits

SD6000	DMOS RF/Mixer pair	3.75
KB4412	Bal mixers, IF-agc	2.55
KB4413	AM/SSB det, squelch, agc	2.75
KB4417	mic processor	2.55
MC3355	best thing in NBFM yet	3.12
MC1496P	popular double bal mixer	1.25

Multiplex decoders + noise blanker

MC1310P	popular PLL decoder	2.20
ua758	buffered 1310	2.20
CA3090AO	RCA PLL decoder	3.25
HA1196	improved PLL decoder with stereo preamps	3.95
HA11223	19kHz pilot cancel, low distortion, high S/N	4.35
KB4437	as HA11223 with remote VCO kill facility	4.55
KB4438	stereo MUTING preamp for post decoder mute	2.22
KB4423	impulse noise blanker	2.53

Discrete devices: more than ever:

BF960	800MHz/2.8dB nF mosfet	1.60*
BF961	200MHz/2.0dB nF	0.80*
40822	FM RF amp	0.43*
40823	FM mixer	0.51*
40673	Famous MOSFET	0.55*
2S149/2sK133	120v/100W MOSPOWER output devices	10.50*

LEDS: the best value today

	3mm	5mm	2.5x5mm
Red	0.14	0.14	0.17
Green	0.18	0.16	0.20
Yellow	0.18	0.15	0.20
Orange	0.22	0.29	0.24

100 off mix, 25% discount. All are AEG first grade types - absolutely no junk. 5mm clips for panel mounting 0.03 each

Misc. ICs for radio/audio applications

U237B	5 LED bargraph driver	0.80*
SAS6610	4 station touch tune IC	1.48*
SAS6710	adds 4 stations to 6610	1.48
MSM5523/4	LW, MW, SW and FM digital frequency readout plus clock, timers, stopwatch	£14*
MSM5526	LW/MW/FM DFM with direct drive for LCD	£11*
TCA730	DC volume control	3.50
TCA740	DC tone control	3.50
TDA1028	DC input switch	3.50
TDA1029	DC mode switch	3.50

Radio and Tuner modules

We cannot really list all the details we would like to here - but with advent of the new mark 3 tuner system, the Dorchester and matching AF units, Ambit offers you the widest choice ever, plus hardware and styling that matches the very high standards we have set in this new range.

At last, DIY HiFi which looks as if it isn't.

That's not to say it doesn't look like HiFi - just that it doesn't look like the usual sort of thing you have come to associate with DIY HiFi. The Mk3 outstrips and outperforms all British made HiFi tuners, and most imported ones too. Certainly at the price, there isn't one near it. But more than that, it looks superb - A small pic here would be an insult, so send an SAE for details on the kit that looks as if isn't. It's something else.....


- * Exceptionally high performance - exceptionally straightforward assembly
- * Baseboard and plug-in construction. Future circuit developments will readily plug in, to keep the MkIII at the forefront of technical achievement
- * Various options and module line ups possible to enable an installation approach to the system

and now previewing the matching 60W/channel VMOS amplifier:

- * Matching both the style and design concepts of the MkIII HiFi FM tuner
- * Hitachi VMOS power fets - characterized especially for HiFi applications
- * Power output readily multiplied by the addition of further MOSFETs
- * VU meters on the preamp - not simply dancing according to val level
- * Backed with the usual Ambit expertise and technical capacity in audio

The PW Dorchester-LW, MW, SW, & FM stereo tuner

THE DIGITAL DORCHESTER ALL BAND TUNER

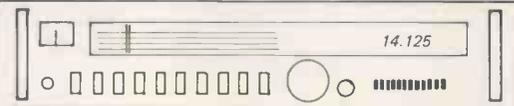

With styling and dimensions to fit in with the rest of AMBIT's new range of tuner & audio equipment.

When the new range of OKI digital frequency display ICs was announced, the original prototype of the Dorchester had been made - but since so many of you wanted to use the OKI frequency counterdisplay system with the Dorchester, we quickly designed a unit to incorporate the necessary facilities. The Digital Dorchester is designed in 19 inch form, and forms a perfect match for the other units in the range. If you don't want to go to the expense of the full Ambit DFM1 module, with AM/FM/Time/Timers, then the MA1023 clock module can be used instead.

The Dorchester has been described in PW Dec., Jan. and Feb. issues - but for those of you who may have missed it - it is an All Band broadcast tuner, covering LW/MW/SW and FM stereo in 6 switched ranges. Construction is very straightforward, with all the switching being PCB mounted - and the revolutionary TDA1090 IC used for AM/FM.

The electronics for the radio section of the Dorchester remain unchanged at £33.00, with 12.5% VAT. The hardware package, of case, meter, PSU now costs £33.00 + 8% with the MA1023 available for an extra £5 only.

For the fully digital version, with Ambit DFM1, the price is £56.50 + 8% VAT.

TERMS etc: CWO please, VAT on Ambit items is generally 12%, except where marked '*'. Catalogue part 1 45p, part 2 50p all inclusive. Postage 25p per order, carriage on tuner kits £3. Phone Brentwood (0277) 216029/227050 9am-7pm. Callers welcome inc. Saturdays.

2 Gresham Road, Brentwood, Essex.

Since AMBIT introduced the "One Stop Technology Shop" to our service, we have been pleased to see just how many users of electronic components appreciate our guarantee to supply goods only from BS9000 approved sources. More than ever, professional and amateur electronics engineers cannot afford to waste time on anything less than perfect pedigree products.

OSTS CD4000 CMOS Micromarket TIL: Standard AND LP Schottky

CD4000		CMOS		Micromarket		PRICES SLASHED		TTL: Standard AND LP Schottky		SEE THE AMBIT AD TOO!	
4001	17p	4059	563p	4522	149p	6800 series	8216 1.95	2114	£10		
4001	17p	4060	115p	4527	157p	6800P 6.50	8224 3.50	2708	£10.55		
4002	17p	4063	109p	4528	102p	6820P 6.6	8228 4.78	Development			
4006	109p	4066	53p	4529	141p	6850P 2.75	8251 6.25	MEK6800 £220			
4007	18p	4067	400p	4530	90p	6810P 4.6	8255 5.40	TK80 £306			
4008	80p	4068	25p	4531	141p	6852	£45	AMI, Signos			
4009	58p	4069	20p	4532	125p	8080 series	2102 £1.70	TI, Intersil,			
4010	58p	4070	20p	4534	614p	8080	6.30	FND507 etc			
4011	17p	4071	20p	4536	38p	8212	2.30	4027 £5.78			
4012	17p	4072	20p	4538	150p						
4013	55p	4073	20p	4539	110p						
4016	52p	4075	20p	4541	141p						
4017	80p	4076	90p	4543	174p						
4018	80p	4077	20p	4549	399p						
4019	60p	4078	20p	4553	440p						
4020	80p	4081	20p	4554	71p						
4021	82p	4082	20p	4556	71p						
4022	90p	4085	82p	4557	386p						
4023	17p	4086	82p	4558	117p						
4024	76p	4089	150p	4559	386p						
4025	17p	4093	50p	4560	218p						
4026	180p	4094	190p	4561	65p						
4027	55p	4096	105p	4562	530p						
4028	72p	4097	372p	4566	159p						
4029	100p	4098	110p	4568	281p						
4030	58p	4099	122p	4569	303p						
4031	250p	4160	90p	4572	25p						
4032	100p	4161	90p	4580	600p						
4033	145p	4162	90p	4581	319p						
4034	200p	4163	90p	4582	164p						
4035	120p	4174	104p	4583	84p						
4036	250p	4175	95p	4584	63p						
4037	100p	4194	95p	4585	100p						
4038	105p	4501	23p								
4039	250p	4502	91p								
4040	83p	4503	69p								
4041	90p	4506	51p								
4042	85p	4507	55p								
4043	85p	4508	248p								
4044	80p	4510	99p								
4045	150p	4511	149p								
4046	130p	4512	98p								
4047	99p	4513	206p								
4048	60p	4514	260p								
4049	55p	4515	300p								
4050	55p	4516	122p								
4051	65p	4517	385p								
4052	65p	4518	103p								
4053	65p	4519	57p								
4054	120p	4520	109p								
4055	135p	4521	236p								

TERMS: CWO please, VAT to be added at 8% (inland), pp 25p per order. When ordering from the OSTs and Ambit - a single combined remittance and pp charge is sufficient. Account details OA.

2 Gresham Road, Brentwood, Essex.

Hobby Electronics

Vol. 1. No. 8

June 1979

Monitor 6 Moving Coil Meters 22 Electronics in Music Pt 2 .. 45

-GSR Monitor 8



A heartwarming project

Short Circuit ... 11, 49, 53, 72


Display Techniques 13



Readout on Readouts

Specials 18
They are too

Envelope Generator 19

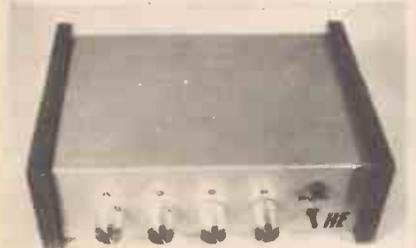

More sound effects



A large scale series

Internal Resistance 31
Batteries, the inside story

Next Month's HE 35

Marketplace 37
Good buys from the good guys

Citizens Banned 38



Conversation piece



A noteworthy series

Kit Review 51



Singing shrubs

Into Electronics 55
Last of the series

HE Book Service 67
Read all about it

Drill Speed Controller 68



A new twist

Hobbyprints 71
Lay 'em down, rub 'em on

Letters 74
From you to us

Hobby Electronics
25-27 Oxford Street, London W1R 1RF
01-434 1781

Published by Modmags Ltd,
Distributed by Argus Distribution Ltd,
Printed by QB Ltd, Colchester
Hobby Electronics is normally published
on the second Friday of the month prior
to the cover date

Editor: Halvor Moorshead
Editorial Staff: Richard Maybury (H.T.G.)
Project Team: Ray Marston, Steve Ramsa-
hadeo, John Fitzgerald
Production: Diego Rincon, Peter Howells
Technical Artists: Paul Edwards, Tony
Strakas
Advertising: Chris Surgenor, David Sinfield,
Joy Cheshire, Sandie Neville
Admin Staff: Margaret Hewitt, Alan Carlton,
Bren Goodwin, Kim Hamlin, Tim Salmon,
Neville MacDonald.

Copyright. All material in this publication is
subject to world-wide copyright protection.
Permission to reproduce printed circuit board
patterns commercially or marketing kits of the
projects must be sought from the Editor. All
reasonable care is taken in the preparation of
the magazine to ensure accuracy but Mod-
mags cannot be held responsible for it legally.

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Electrolytic Can Type				Miniature Low Value											
Electrolytic Axial Leads -10% to +50% Tol				High Ripple, IEC Grade 1, Low E.S.R. Supplied complete with Vertical Fixing Clip				Polyethylene, Axial, ±1% Tol, > 63V D.C. Wkg											
µF	V d.c.	16	25	40	63	2200 µF	16V	2.5A	3.5A	184	100	16	6	10	25	40	63	629	629
1.0					8	4700 µF	16V	5.8A	8.1A	222	1.2	120	16	8	12	25	40	63	629
1.5					8	10000 µF	16V	9.8A	13.7A	346	1.5	150	16	8	15	25	40	63	629
2.2					8	22000 µF	16V	1.3A	1.8A	175	1.8	180	16	6	18	27	38	43	629
3.3					8	2200 µF	25V	4.6A	6.4A	201	2.2	220	16	6	22	38	43	629	629
4.7					8	4700 µF	25V	8.0A	11.2A	264	2.7	270	16	8	27	38	43	629	629
6.8					8	10000 µF	25V	12.8A	17.9A	438	3.3	330	18	8	33	41	43	629	629
10					9	22000 µF	25V	0.9A	1.2A	168	4.7	470	18	8	47	55	63	629	629
15	7				10	1000 µF	40V	2.4A	3.3A	188	5.6	560	18	8	56	63	629	629	629
22	7	7			12	2200 µF	40V	5.6A	7.8A	231	6.8	680	18	8	68	75	83	629	629
33	7	7			12	4700 µF	40V	9.2A	12.8A	367	8.2	820	18	8	82	90	100	629	629
47	7	7			12	10000 µF	40V	1.8A	2.5A	190	12	1200	16	5	12	15	16	629	629
56					12	2200 µF	70V	4.0A	5.8A	235	15	1500	18	6	15	18	20	629	629
100	8	8			12	4700 µF	70V	7.5A	10.5A	376	22	2200	18	6	22	25	27	629	629
150	8	9			29	10000 µF	70V	4.0A	5.6A	222	33	3300	18	6	33	38	43	629	629
220	12				34	2200 µF	100V	7.8A	10.9A	346	39	3900	18	6	39	45	50	629	629
330					37	4700 µF	100V				47	4700	23	6	47	55	63	629	629
470					44	10000 µF	100V				56	5600	23	6	56	63	70	629	629
680	19	28			50	2200 µF	100V				68	6800	23	6	68	75	83	629	629
1000	23	28			50	4700 µF	100V				82	8200	23	6	82	90	100	629	629
1500	32	36			50	10000 µF	100V												

Tantalum Bead				Electrolytic Radial Leads				Trimmers				Polyester Radial Leads											
-20% Tol				-10% to +50% Tol				250V D.C. Wkg. Film Dielectric, Miniature				Dipped Type, ±20% Tol, > 250V D.C. Wkg. C280/352 Style											
µF	V d.c.	3.15	6.3	10	16	25	35	40	50	63	1.4 - 4.1pF	19	Cap B06 A	8 - 3.8pF	46	µF	352	360	PHE280	µF	352	360	PHE280
0.1											2 - 8pF	19	Cap B08 B	8 - 5.8pF	48	0.001	5	6		0.001	5	6	
0.15											2 - 20pF	21	Cap B08 C	1 - 13pF	61	0.0015	5	6		0.0015	5	6	
0.22											5.5 - 59.5pF	29	Cap B08 D	1.7 - 19.7	62	0.0022	5	6		0.0022	5	6	
0.33																0.0033	5	6		0.0033	5	6	
0.47																0.0047	5	6		0.0047	5	6	
0.68																0.0068	5	6		0.0068	5	6	
1																0.01	5	6		0.01	5	6	
1.5																0.015	5	6		0.015	5	6	
2.2																0.022	5	6		0.022	5	6	
3.3																0.027	5	6		0.027	5	6	
4.7																0.033	5	6		0.033	5	6	
6.8																0.047	5	6		0.047	5	6	
10																0.068	5	6		0.068	5	6	
15																0.1	5	6		0.1	5	6	
22																0.15	5	6		0.15	5	6	
33																0.22	5	6		0.22	5	6	
47																0.27	5	6		0.27	5	6	
68																0.33	5	6		0.33	5	6	
100																0.47	5	6		0.47	5	6	

CASES				VERO ELECTRONICS PRODUCTS				HARDWARE			
Small Desk Console - Boss Industrial Mouldings				2.5" x 5" .1" pitch Veroboard				D.I.L. Sockets			
Slope Front Console, Recessed Top				3.75" x 5" .1" pitch Veroboard				8 Pin Low Profile Socket Tin			
ABS Base, C/W Brass Bushes, In Orange				2.5" x 11" .1" pitch Veroboard (5)				14 Pin Low Profile Socket Tin			
1mm Aluminium Top Panel Finished Grey				5.82" x 2.9" .1" pitch V-Q DIP Board				16 Pin Low Profile Socket Tin			
Order Code	W161, D96, H39 (57)	186	Case BIM1005 DR	Order Code	59	VERO 21069J	Order Code	11	OIL SKT 8		
W215, D130, H47 (73)	268	Case BIM1006 DR	70/Pack	VERO 21072D	66	VERO 21076C	13	OIL SKT 14			
Plastic Boxes - Boss Industrial Mouldings				Soot Face Cutter				24 Pin Low Profile Socket Gold			
Moulded Box and Close Fitting Flanged Lid				Pin Insertion Tool for .040 type pin				28 Pin Low Profile Socket Gold			
ABS Case, C/W Brass Bushes, and Lid In Orange				DS Pin, .040 (100)				40 Pin Low Profile Socket Gold			
Order Code	L112 W62 D31	87	Case BIM2003 DR	Order Code	88 Pin, .040 (100)	38/Pack	VERO 21087G	78	DIL SKT 28		
L150 W80 D50	115	Case BIM2005 DR	47	6mm Board Standoff (100)	181/Pack	VERO 21017B	127	DIL SKT 40			
L190 W110 D60	195	Case BIM2006 DR	215/Pack	15mm Board Standoff (100)	226/Pack	VERO 21321K					
Instrument Case - Boss Industrial Mouldings				Verowire Kit (1 open, 2 wire, 25-comb)				Heatsinks			
Covers Manufactured from 14SWG Aluminium				Verowire Combs (100)				Individual Type for 1 x T05 50°C/W			
Chassis Manufactured from 18SWG Mild Steel				Verowire Wire (4)				Individual Type for 1 x T066 10.5°C/W			
Covers Finished Orange				Flip Top Box, Small, Black				Individual Type for 1 x T03 7.2°C/W			
Covers Finished Matt Black				Flip Top Box, Large, Black				Individual Type for 1 x T0220 17°C/W			
Order Code	W250 D167.5 H 68.5 (Chassis 153mm Deep)	1480	Case BIM3000 DR	Order Code	250	VERO 21319J	Order Code	10	Sink 5F		
All Metal Desk Consoles - Boss Industrial Mouldings				Small Desk Consoles - Boss Industrial Mouldings				P.C.B. Components			
Slope Front Console, Recessed Top				Slope Front Console, Recessed Top				Delta Pen, Blue Ink, Slow Drying			
Two Piece All Aluminium Construction				ABS Base, C/W Brass Bushes, In Orange				Fuselers			
Ventilation Slots in Rear and Front				1mm Aluminium Top Panel Finished Grey				Suit 20mm x 5mm Fuse			
Choice of 15° or 30° Sloping Front				Ventilation Slots in Base				F.C.B. Mounting, Open Type			
Off White Top Panel, Blue Base				Order Code				F.C.B. Mounting, Screwdriver Slot			
Order Code	W105 O143 H32 (56)	206	Case BIM6005 DR	W105 O143 H32 (56)	271	Case BIM6006 DR	Order Code	8	Fuse H20B		
W170 D143 H32 (56)	271	Case BIM6007 DR	375	W170 D214 H32 (82)	375	Case BIM6007 DR	17	Fuse H20C			
All Metal Desk Consoles - Boss Industrial Mouldings				Eurocard Size Desk Console - Boss Industrial Mouldings				Lamp Holders, Panel Mounting			
Slope Front Console, Recessed Top				Slope Front Console				Similar In Style to Fuse/H 20P			
Two Piece All Aluminium Construction				ABS Case, C/W Brass Bushes, In Orange				Low Voltage Type Suits LES and M/F Bulbs.			
Ventilation Slots in Rear and Front				1mm Aluminium Top Panel, Finished Grey				Low Voltage, Red, Amber or Green			
Choice of 15° or 30° Sloping Front				Off White Top Panel, Blue Base				Internal Neon 200/240V Red or Amber			
Order Code				Order Code				Bulbs, Low Voltage, L.E.S.			
W102 D140 H28 (51) 15° slope	1018	Case BIM7154A	1018	W169 D127 H45 (70)	375	Case BIM8006 DR	Order Code	22	Bulb LES		
W185 O211 H33 (76) 15° slope	1350	Case BIM7154A	1350				6V, 0.36W, 6.5V, 1W, 14V, 0.75W.				
W254 D287 H33 (76) 15° slope	1572	Case BIM7156A	1572								
W356 D287 H33 (76) 15° slope	1823	Case BIM7156A	1823								
W102 D140 H28 (51) 30° slope	1018	Case BIM7301A	1018								
W165 D183 H28 (102) 30° slope	1202	Case BIM7303A	1202								
W254 D259 H28 (102) 30° slope	1572	Case BIM7306A	1572								
W356 D259 H28 (102) 30° slope	1823	Case BIM7308A	1823								

RESISTORS				Skeleton Presets, Miniature				Skeleton Presets, Standard			
Carbon Film, Fixed				0.1W, E3 Values, 100R-1M, Lin. Vertical Mounting				0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting			
0.25W, E24 Values IRD-10M, 5% Tol.				0.1W, E3 Values, 100R-1M, Lin. Horizontal Mounting				0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mounting			
0.5W, E12 Values IRD-4M7, 10% Tol.				Order Code				Order Code			
1.5 ea.	90p/100 (Mult 10/Value)	£7.90/1000 (Mult 100/Value)	Res RD's	7	7	10	10	10	10	10	10
2 ea.	1.25p/100 (Mult 10/Value)	£10.10/1000 (Mult 100/Value)	Res RD's	7	7	10	10	10	10	10	10
Metal Film, Fixed				Order Code				Order Code			
0.5W, E24 Values, SR-1M, 2% Tol.				Res MR30				Res PR52			
2.5W, E12 Values 10R-27K, 5% Tol.				Res VR37				+ Value			
6 ea.	3.80/100 (Mult 10/Value)	£32.40/1000 (Mult 100/Value)	Res MR30	34	34	34	34	34	34	34	34
13 ea.	7.90/100 (Mult 10/Value)		Res PR52	34	34	34	34	34	34	34	34
Metal Glaze, Fixed				Order Code				Order Code			
0.5W, E24 Values, IR-33M, 5% Tol.				Pot Lin				Pot Lin			
10 ea.	5.40/100 (Mult 10/Value)		Res VR37	34	34	34	34	34	34	34	34
				+ Value				+ Value			

- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR TELEPHONE ANSWERING SERVICE

GMT ELECTRONICS B

Freepost

Birmingham B19 1BR

TEL ORDERS WELCOME

DIGITAL INTEGRATED CIRCUITS

4000 Buffered CMOS - High Speed

5-15V 'B' Series, Up to 20MHz

HEF4001	14	HEF4046	100	HEF4514	250	N7400N	9	N7444A	83	N74122N	39	N74192N	60	N74LS28N	32	N74LS139N	85	N74LS253N	105
HEF4002	14	HEF4047	87	HEF4515	299	N7401N	11	N7445N	65	N74123N	37	N74194N	80	N74LS30N	16	N74LS139N	85	N74LS257N	104
HEF4003	14	HEF4048	28	HEF4516	90	N7402N	11	N7446A	62	N74125N	32	N74195N	70	N74LS32N	24	N74LS154N	122	N74LS280N	107
HEF4006	95	HEF4050	28	HEF4517	382	N7403N	11	N7447A	51	N74126N	32	N74198N	120	N74LS33N	32	N74LS154N	122	N74LS280N	107
HEF4007	69	HEF4051	69	HEF4518	69	N7404N	12	N7448A	44	N74127N	74	N74199N	139	N74LS37N	24	N74LS155N	80	N74LS281N	106
HEF4008	80	HEF4052	72	HEF4519	55	N7405N	12	N7449N	26	N74128N	46	N74201N	160	N74LS38N	24	N74LS156N	80	N74LS282N	107
HEF4011	14	HEF4053	72	HEF4520	65	N7406N	25	N7451N	13	N74129N	60	N74202N	116	N74LS40N	22	N74LS157N	54	N74LS283N	130
HEF4012	14	HEF4056	37	HEF4521	188	N7407N	27	N7453N	15	N74129N	125	N74203N	200	N74LS42N	53	N74LS158N	60	N74LS283N	130
HEF4013	32	HEF4067	380	HEF4522	99	N7408N	13	N7454N	13	N74129N	83	N74204N	150	N74LS44N	22	N74LS158N	60	N74LS283N	130
HEF4014	84	HEF4068	14	HEF4523	120	N7409N	13	N7456N	13	N74130N	85	N74205N	150	N74LS46N	16	N74LS159N	78	N74LS283N	130
HEF4015	60	HEF4069	14	HEF4524	510	N7410N	11	N7470N	26	N74131N	48	N74206N	120	N74LS48N	22	N74LS160N	100	N74LS283N	130
HEF4016	35	HEF4070	14	HEF4529	110	N7411N	18	N7472N	22	N74132N	55	N74207N	150	N74LS50N	16	N74LS160N	100	N74LS283N	130
HEF4017	55	HEF4071	14	HEF4543	155	N7412N	17	N7473N	23	N74133N	96	N74208N	96	N74LS52N	40	N74LS160N	100	N74LS283N	130
HEF4018	65	HEF4072	16	HEF4555	78	N74133N	23	N7474N	23	N74134N	53	N74209N	53	N74LS54N	33	N74LS160N	100	N74LS283N	130
HEF4019	46	HEF4073	16	HEF4556	78	N74134N	46	N7475N	28	N74135N	48	N74210N	48	N74LS56N	33	N74LS160N	100	N74LS283N	130
HEF4020	88	HEF4075	16	HEF4557	386	N74135N	22	N7476N	26	N74136N	59	N74211N	49	N74LS58N	33	N74LS160N	100	N74LS283N	130
HEF4021	85	HEF4076	85	HEF4585	97	N7417N	23	N7480N	43	N74137N	49	N74212N	49	N74LS60N	33	N74LS160N	100	N74LS283N	130
HEF4022	82	HEF4077	14	HEF4724	171	N7420N	11	N7483N	63	N74138N	74	N74213N	74	N74LS62N	33	N74LS160N	100	N74LS283N	130
HEF4023	14	HEF4078	16	HEF4097	90	N7421N	26	N7485N	65	N74139N	74	N74214N	74	N74LS64N	33	N74LS160N	100	N74LS283N	130
HEF4024	45	HEF4081	18	HEF4098	73	N7425N	27	N7486N	23	N74140N	134	N74215N	74	N74LS66N	33	N74LS160N	100	N74LS283N	130
HEF4025	14	HEF4082	18	HEF40106	62	N7426N	22	N7489N	30	N74141N	74	N74216N	74	N74LS68N	33	N74LS160N	100	N74LS283N	130
HEF4027	32	HEF4085	64	HEF40160	119	N7427N	22	N7491A	60	N74142N	65	N74217N	65	N74LS70N	33	N74LS160N	100	N74LS283N	130
HEF4028	52	HEF4086	64	HEF40161	119	N7428N	30	N7492N	33	N74143N	65	N74218N	65	N74LS72N	33	N74LS160N	100	N74LS283N	130
HEF4029	60	HEF4093	50	HEF40162	119	N7430N	11	N7493N	31	N74144N	93	N74219N	65	N74LS74N	33	N74LS160N	100	N74LS283N	130
HEF4030	40	HEF4094	175	HEF40163	119	N7432N	21	N7494N	74	N74145N	134	N74220N	65	N74LS76N	33	N74LS160N	100	N74LS283N	130
HEF4031	200	HEF4104	166	HEF40174	119	N7433N	30	N7495A	48	N74146N	111	N74221N	65	N74LS78N	33	N74LS160N	100	N74LS283N	130
HEF4035	110	HEF4502	91	HEF40175	119	N7437N	21	N7496N	46	N74147N	63	N74222N	65	N74LS80N	33	N74LS160N	100	N74LS283N	130
HEF4040	68	HEF4505	571	HEF40192	140	N7438N	21	N74100N	88	N74148N	62	N74223N	65	N74LS82N	33	N74LS160N	100	N74LS283N	130
HEF4041	75	HEF4508	51	HEF40193	140	N7439N	60	N74107N	25	N74149N	80	N74224N	65	N74LS84N	33	N74LS160N	100	N74LS283N	130
HEF4042	79	HEF4510	70	HEF40194	119	N7440N	12	N74109N	42	N74150N	82	N74225N	65	N74LS86N	33	N74LS160N	100	N74LS283N	130
HEF4043	79	HEF4511	110	HEF40195	117	N7442N	40	N74116N	148	N74151N	69	N74226N	65	N74LS88N	33	N74LS160N	100	N74LS283N	130
HEF4044	84	HEF4512	98			N7443N	79	N74121N	23	N74152N	65	N74227N	65	N74LS90N	33	N74LS160N	100	N74LS283N	130

7400 T.T.L.

N74153N	46	N74151N	22	N74153N	55	N7436N	150	N74154N	96	N74LS		N74LS50N	15	N74LS51N	16	N74LS52N	16	N74LS53N	16	N74LS54N	16	N74LS55N	16	N74LS56N	16	N74LS57N	16	N74LS58N	16	N74LS59N	16	N74LS60N	16	N74LS61N	16	N74LS62N	16	N74LS63N	16	N74LS64N	16	N74LS65N	16	N74LS66N	16	N74LS67N	16	N74LS68N	16	N74LS69N	16	N74LS70N	16	N74LS71N	16	N74LS72N	16	N74LS73N	16	N74LS74N	16	N74LS75N	16	N74LS76N	16	N74LS77N	16	N74LS78N	16	N74LS79N	16	N74LS80N	16	N74LS81N	16	N74LS82N	16	N74LS83N	16	N74LS84N	16	N74LS85N	16	N74LS86N	16	N74LS87N	16	N74LS88N	16	N74LS89N	16	N74LS90N	16	N74LS91N	16	N74LS92N	16	N74LS93N	16	N74LS94N	16	N74LS95N	16	N74LS96N	16	N74LS97N	16	N74LS98N	16	N74LS99N	16
---------	----	---------	----	---------	----	--------	-----	---------	----	-------	--	----------	----	----------	----	----------	----	----------	----	----------	----

LINEAR INTEGRATED CIRCUITS

CA3011	92	NE592K	182
CA3018	75	RC4136	130
CA3020	191	TBA1205	79
CA3028A	86	TCA580	346
CA3046	76	TCA730	450
CA3048	245	TCA740	450
CA3080E	70	TDA100B	326
CA3098E	64	TDAL022	326
CA3100E	90	TDAL028	338
CA3140E	38	TDAL029	338
CA3189E	266	TDAL034B	217
LM301AN	30	TLA2581	266
LM309N	10	TLA2640	292
LM318N	200	TL81CP	75
LM319N	216	TL84CN	140
LM324N	-10	UA709CT	46
LM339N	71	UA709CN	40
LM338N	110	UA710CN	41
LM381AN	180	UA711CN	65
LM382	120	UA711CT	42
		UA711CN	18
		UA717CN	50
		UA748CN	35
MC1458N	35		
MC1496N	97		
NE531	119		
NE536T	216		
NE540	225		
NE555N	25		
NE556N	60		
NE560N	351		
NE561N	423		
NE562N	461		
NE565N	155		
NE566N	170		
NE570N	405		
NE571N	459		

OPTO ELECTRONICS

Light Emitting Diodes, Individual			
.125" (3mm)	Red	14	COY54
	Green	17	COY95
	Yellow	19	COY97
Panel Mounting Clip to suit.	3	LE03 Clip	
2" (51mm) Red			
	Green	15	COY24A
	Yellow	19	COY96
Panel Mounting Clip to suit.	5	LE05 Clip	
Light Emitting Diodes - 7 Segment Display			
3" (7.6mm) C. Anode R.H. Decimal Pt.	Red	160	XAN3061
	C. Anode R.H. Decimal Pt. Green	199	XAN3051
	C. Cathode R.H. Decimal Pt. Red, Low current drain	160	XAN3074
6" (15.2mm) C. Anode L.H. Decimal Pt. Red		230	XAN6620
	C. Anode L.H. Decimal Pt. Green	230	XAN6520
	C. Cathode L.H. Decimal Pt. Red	230	XAN6640
Photoresistors			
ORP12	90	ORP12	
ORP61	90	ORP61	
Phototransistors			
OCPT1	180	OCPT1	
BPX25	275	BPX25	
BPX29	175	BPX29	
Photocoupler			
FC0820	150	FC0820	


SWITCHES

Miniature Toggle - Honeywell				
SPDT	C/O/H	2A/250V A.C., 5A/276V D.C.	58	SW 8A1011
SPDT	Double Bias To Centre		67	SW 8A1021
SPDT	Single Bias To Centre		75	SW 8A1051
SPDT	Bias		70	SW 8A1061
DPDT			86	SW 8A2011
DPDT	C/O/H		92	SW 8A2021
DPDT	Double Bias To Centre		102	SW 8A2041
DPDT	Single Bias To Centre		102	SW 8A2051
DPDT	Bias		96	SW 8A2061
Miniature Push - C & K				
SP	Push To Make, Momentary	0.5A/250V A.C., 1A/28V D.C.	54	SW 8531
SP	Push To Break, Momentary		54	SW 8533
Slide - Switchcraft				
DPDT	Standard Actuator		36	SW 45206
DPDT	Slot Actuator, Voltage Change, Marked 110/240		43	SW 45206F

SEMICONDUCTORS

Diodes							
IN827	193	IN4006	7	8B110G	61	OA202	9
IN514	4	IN4007	8	BY127	15		
IN518	5	IN4148	3	BY206	34		
IN4001	4	IN5402	15	BYX10	19	Microwave	
IN4002	4	IN5404	16	OA47	10		
IN4003	6	BA134	5	OA90	7	BAW95D	1091
IN4004	6	BA136	27	OA91	7	CL980	252
IN4005	7	8B106A1	122	OA200	9	CX111C	1280
Zener Diodes							
400mW C&V7-C33		1.3W C7V5-C75					
BZVBB/82 X79 + Voltage	8	BZK61 + Voltage	16				
Transistors							
2N929	37	2N4427	206	BC478	24	BSX88	18
2N1893	30	2N4856	158	BC547	12	MJE340	48
2N2218A	28	2N4858	134	BC548	10	MPF102	32
2N2222	21	2N4860	122	BC548B	15	OC28	107
2N2369	19	2N5294	43	BC549	12	OC35	95
2N2389A	20	2N5416	108	BC549B	20	OC45	82
2N2646	42	2N5457	35	BC557	14	OCPT1	180
2N2894	49	2N5468	30	BC558	14	TIP29A	41
2N2895	28	2N5469	32	BC559	17	TIP29C	53
2N2904	24	2N6258	432	BCY24	97	TIP30A	44
2N2905A	24	40673	80	BCY70	14	TIP30C	57
2N2905	22	AC188	22	BCY71	14	TIP31A	43
2N2905A	24	AD161	38	BCY72	15	TIP31C	

Monitor

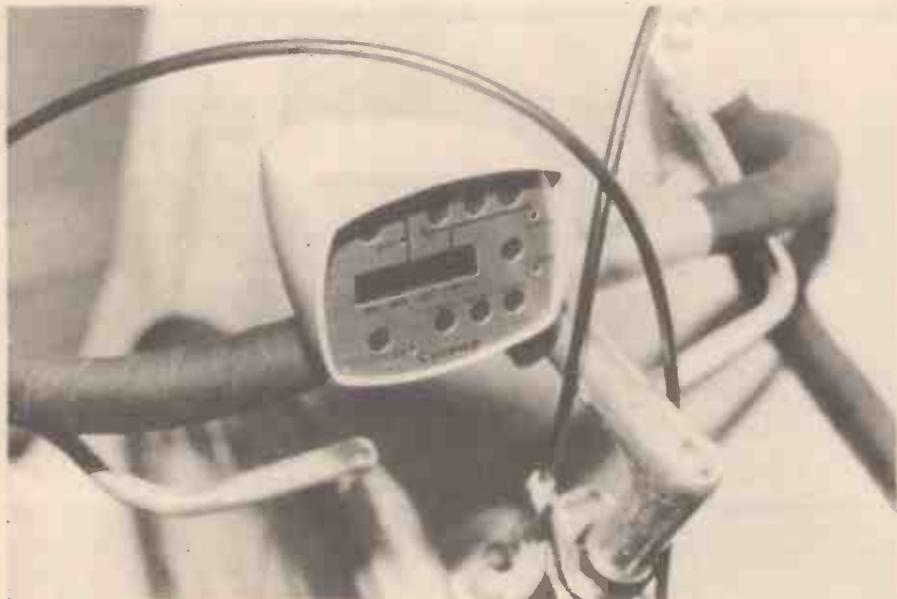

MEGA-CYCLE?

It's good to see young engineers being encouraged to develop their ideas. We've just received the results of the 'Bike of the Future Design Competition', organised by the British Cycling Bureau.

In the Accessories and Components category John Colesby took a joint first prize (£250) for his 'Cyclometer'. A magnetic sensor on the front wheel is connected to the

meter body on the handlebar. A readout of speed (MPH or KPH) is constantly available, along with maximum speed achieved, average speed and distance covered. In addition it can be used as a stopwatch and a 24 hour clock as an option.

Already plans are afoot to market the device commercially and it is hoped it will be generally available in the autumn for around £20-25.

RICH MAN'S TURNTABLE

If your bank balance is sufficiently fluid and you're really into Hi-Fi then this has got to be for you. We don't know if it sounds any better for costing £350.00 but just think how impressed the neighbours will be when they hear how much you paid for it. Seriously though, the turntable is an extremely well made device. It is destined for the professional user (they're the only ones who could afford it).

It features an electronic speed control with direct speed readout on an LED display. The turntable which is instant starting, provides for slip cueing, without a loss in speed and it has back cueing with no drag. Lee Engineering Ltd will be marketing the 'QRK Electronics Galxy', you can find them at: Napier House, Bridge Street, Walton-on-Thames, Surrey.



IRON TAMER

If you've ever suffered from Nylo-sock solderitus (a large blob of solder stubbornly clinging to your skin). The infamous Solder Moth (known for eating large holes in poly-cotton material) or long mysterious scars all over your hands and body, then you're a victim of a wild soldering iron attack.


Soldering irons have been known to leap up without warning at an unsuspecting hobbyist, inflicting grievous wounds. A simple way to control these unruly beasts is to invest in a cage. Adcola, the soldering iron people have introduced such a device, called the L686S Safety Stand. It currently retails for £3.06. If you have any difficulty write to:- Adcola, Adcola House, Gauden Road, London SW4 6LH.



CALCULATOR OF THE MONTH

This month's calculator offering hails from Ingersol of all people, (believe it or not Casio have **not** sent us anything this month!). This machine is very much in the 'credit-card' size range, weight is around 1.25 oz and measures 53 x 85 x 5 mm (approx.)

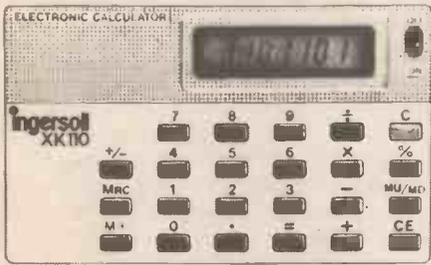Features include the now mandatory 8 digit LCD display with fully floating decimal. In close attendance lurks a 4 function memory, percentage/square root and several other indispensable features. You can expect a 2 000 hour battery life (how could we survive with anything less?) Price? Around the £18.95 mark at your local calc. emporium now.



MICRO-TAPE

The micro-cassette system was first introduced by Phillips several years ago. It has, over the past couple of years enjoyed a great deal of popularity. Several new micro-recorders using the Phillips format have appeared, finding many applications in dictation etc.

The model featured here is claimed to be the smallest yet. The machine is of American origin and measures only 4.1 x 2.5 x 1 inches and weighs just 8.5 ounces, real spy stuff. The recorder has a single slide control to operate record, stop, rewind and playback functions. Up to 1 hours playing time is available from each cassette, (30 mins per side).

The built-in electret microphone is capable of picking up whispered conversations from over 30 ft away. An LED indicator shows when a recording is in progress, and an audible end-of-tape alarm is included.



SOLID STATE CAMERA

Well it had to happen, a really small solid-state camera has been launched upon the unwary British market. The heart of the camera is a 100 x 100 photodiode matrix on a 6mm² silicon chip. The uses are obviously very wide ranging, surveillance and military weapon guidance for instance.

The camera gives a fully line-interlaced TV output, compatible with most systems. The camera was developed in America by the Reticon Corporation. UK distribution is being handled by Herbert Sigma Ltd, Spring Road, Letchworth, Herts.

Obviously all this not going to be cheap an incredible £120 in fact. But as we've seen so many times in the past, prices have a habit of tumbling, very rapidly. If you've got the money (and inclination) contact: Lanier Business products Inc, 100 New Kings Road, London, SW6.



TINY TELLY

Latest news from Japan hints that the long awaited LCD pocket television will be available early next year. We've got some rather vague details, screen size is 2.4 inches, the set consumes only 1.5 watts (only!) and weighs in at 200 grammes. The LCD matrix has 57 600 picture elements (240x240 array). Judging from the rather poor picture we have, it looks rather like a cross between a powder compact and an Starship Enterprise communicator. We just wish they would hurry up we're dying to get our hands on one.

TECHNICAL ENQUIRY SERVICE

As you probably know we offer a Technical Query service for our readers (HE projects only please). If you've written to us and not received a reply it's because you didn't enclose a SAE. Sorry to all those who have called us every name under the sun but we really can't afford the postage. PS please mark your envelopes 'Technical Enquiry'.

ERRATA

If you find that your Digi-Bell project doesn't work very well we're sorry to say there was a little omission on the PCB, a link between pin 1 of IC2 and the junction of C1 (-ve) and R2 was left out.

PARKING METER TIMER

Components for this project should be readily available from most suppliers.

The three position slide switch is available from Stevenson Electronics, or Watford Electronics.

The audible warning device (9v-15mA) can be obtained from Progressive Radio, 31 Cheapside, LIVERPOOL L2 2JD.

We're sorry that some information was omitted from last month's project and hope this will answer any queries.

We apologise to readers of HE for the lateness of recent issues. This has been due to printing problems outside our control; we hope that these will be short-lived.

GSR Monitor

Get into the biofeedback scene and learn to relax scientifically with our Galvanic Skin Response Monitor

THE HE Galvanic Skin Response monitor is a sensitive resistance-monitoring instrument that produces an audible output that changes frequency in response to small changes in the 'victims' skin resistance. The instrument is intended for use in biofeedback experiments, as an aid to reducing or relaxing nervous tension.

The basic theory behind biofeedback is quite simple. Human beings, like most other animals, have the ability to exert a high degree of muscular control in response to visual, aural, thermal, tactile, and other 'sensed' feedback mechanisms. They can control virtually any physical or biological activity that they are able to sense or monitor.

Humans can't normally control functions like heart rate, blood pressure, body temperature, mental activity, emotional stress, etc, because they have no innate way of sensing these so-called 'automatic' actions. The biofeedback theory says that if you provide a person with an artificial means of sensing or monitoring any one of these functions, that person can soon learn to bring that function under conscious control.

MIND OVER MATTER

The biofeedback theory works out pretty well in practice, and biofeedback machines are now widely used in medical and scientific research establishments. One of the most interesting aspects of biofeedback applies to the control of functions of the mind such as nervous tension and anxiety. That's where the GSR monitor comes in.

ALL IN THE MIND?

The human body reacts in several ways when its owner is subjected to mental stress or strain. Extra adrenaline is released, the heart rate increases, and sweat gland activity and pore sizes increase. These last-mentioned, two reactions are reflected in a change in the resistance of the skin. The resistance falls as tension increases, and vice versa.

The GSR monitor gives a practical readout of the skin resistance by monitoring the resistance between the fleshy parts of two adjacent fingers of one hand via a pair of probes and conductive electrodes (steel wool held in place with sticky tape or a metal strap is OK), and presents this data to the user in the form of an audible signal that varies in frequency with the skin resistance and state of mental tension. The tone rises as tension increases, and vice versa.


GSR monitors are easy instruments to build. They normally cover the resistance range 5k Ω to 1M Ω , and incorporate sensitivity and balance or level controls as a means of changing resistance ranges.

In use, the operator hooks himself up to the machine, adjusts it's controls to give a fairly low tone signal, and then patiently tries to reduce the tone frequency by relaxing his mind and body. A fair degree of practice may be needed to get the hang of things, just as a good deal of practice is needed to get the hang of riding a bicycle, but after a few half-hour sessions the user should find that he can exercise a reasonable degree of control over his mental state when using the machine.

CONSTRUCTION AND USE

Take care during assembly on the PCB to ensure that all semiconductor devices and electrolytic capacitors are fitted in the correct polarity. We built our prototype unit in a small (3 x 4 1/2 x 1 1/2 inch) plastic case, and fixed the PCB in place with sticky pads after completing the interwiring. We used a crystal insert as the audio output device, as shown in the circuit diagram. This device

The HE GSR Monitor, the case used in the prototype was made by Vero Electronics.

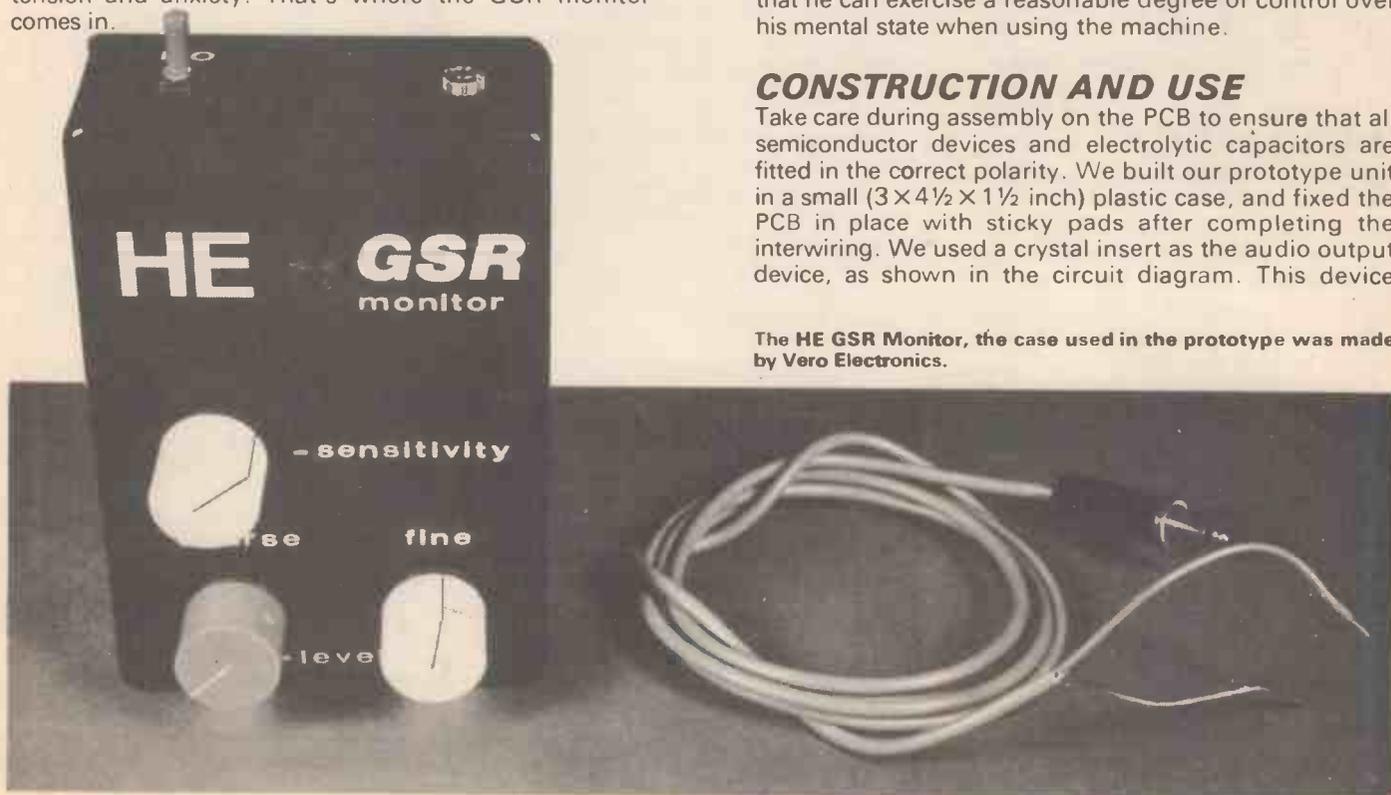

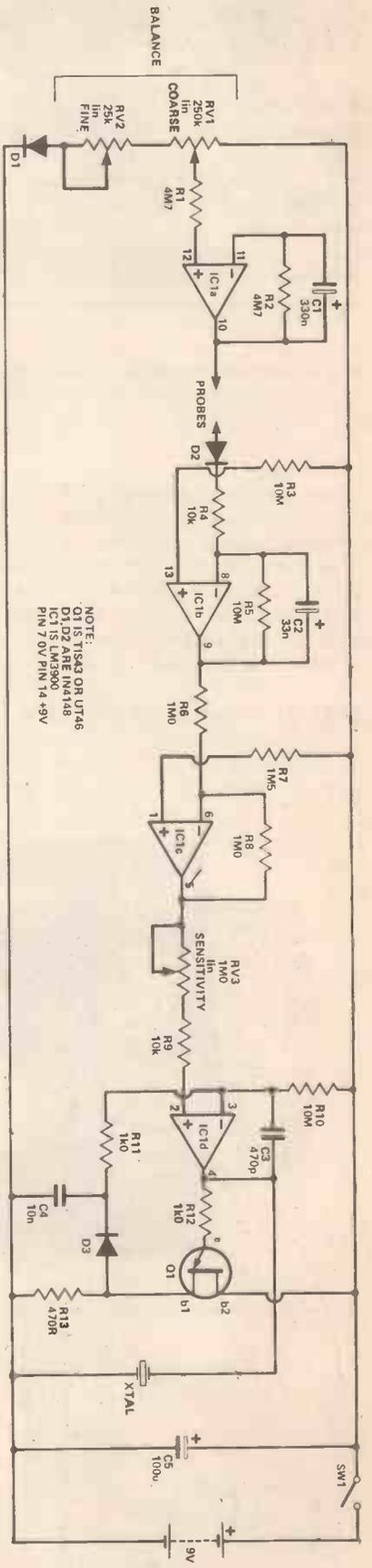


Fig. 1. Circuit diagram of the GSR Monitor, note that the xtal is either a crystal earpiece or microphone insert.

How It Works

The LM3900 used in this project contains four current-differentiating op-amps. More conventional op-amps like the 741 compare voltages presented to their inputs. With the LM3900, voltages are presented to the inputs via resistors to provide input currents. A voltage will be produced at the output sufficient to drive a current through the feedback resistor and into the inverting input which is equal to the difference between the input currents. The voltage appearing at the input pins will always be one diode-drop above ground; about 0.5 volts.

Nine volts from the battery is applied across RV1, RV2 and D1. IC1a acts as a voltage follower and the 0.5 to 9 V from the slider of RV1 appears at the output of IC1a. This provides a low impedance voltage source. Any noise is smoothed out by C1. A current, proportional to the applied voltage and the skin resistance plus R4 will now flow into the inverting input of IC1b. R4 prevents too large a current from flowing if the probes are inadvertently shorted. A small input current produces a large output voltage from IC1b which is then inverted by IC1c to provide the correct sense; an increase in skin resistance produces a decrease in pitch of the output tone.

IC1d and Q1 form a current controlled oscillator. IC1d is arranged as an integrator where current flowing into the non-inverting input causes the output voltage to rise at a certain rate. This would continue until the amplifier saturated, however, at about 6 volts, Q1 will suddenly turn on producing

an increase in the voltage across R13. This causes a current to flow via D2 and R11 into the inverting input resetting the integrator and turning off Q1. C4 ensures that the pulse lasts long enough to fully reset the integrator. The cycle repeats at a frequency proportional to the input current which is controlled by RV3 producing an audible tone in the crystal insert.

Inside the GSR Monitor, everything fits easily into the case.



Parts List

- RESISTORS** (all 1/4W, 5%)
 R1, R2 4M7
 R3, R5, R10 10M
 R4, R9 10k
 R6, R8 1M0
 R7 1M5
 R11, R12 1k0
 R13 470R
- POTENTIOMETERS**
 RV1 250k lin
 RV2 25k lin
 RV3 1M0 lin
- CAPACITORS**
 C1, C2 .033u 35V tantalum
 C3 470p polystyrene
 C4 10n polyester
 C5 100u electrolytic
- SEMICONDUCTORS**
 D1, D2, D3 IN4148
 Q1 TIS43
 IC1 LM3900
- MISCELLANEOUS**
 Crystal insert, SW1 SPST (on-off toggle switch), PP3 and connector, Vero case to suit.

Buylines

Approximate cost £4.00.
 No special notes here. All components used in the project are standard, readily available types.


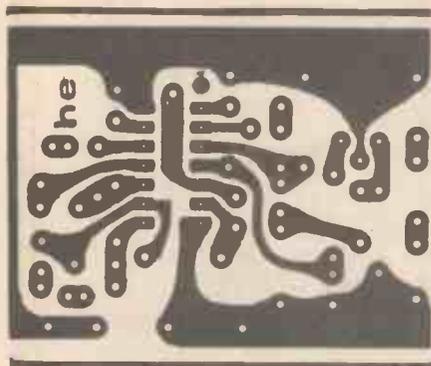


Fig. 3. PCB foil pattern for GSR Monitor, take care when soldering in the IC's to prevent solder blobs.


Fig. 2. Component overlay for GSR Monitor, make sure that all polarised components, ie ICs, diodes etc are inserted the correct way round.

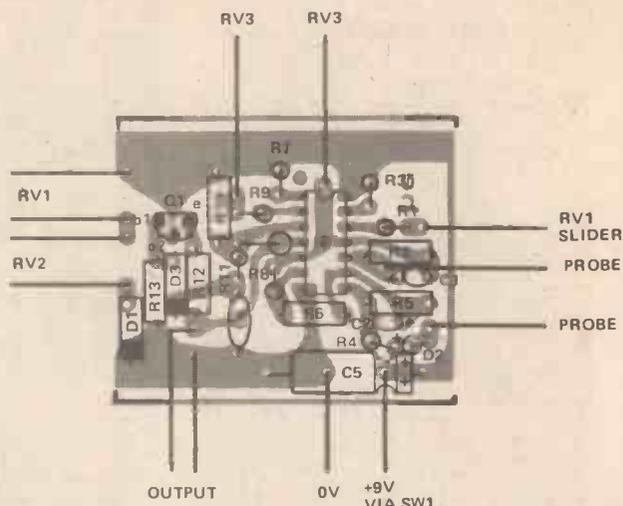

gives a rather low level of audio output, however, and some readers may prefer to use a crystal earpiece output instead, by making a direct substitution of the devices.

When construction is complete, connect a 100k resistor across the probes and switch the unit on. Now adjust the level and sensitivity controls to obtain a fairly low audio tone. Note that the LEVEL controls are very slow acting, and take several seconds to effect the tone signal, and that on most cases the COARSE LEVEL control can be left in the fully anti-clockwise position.

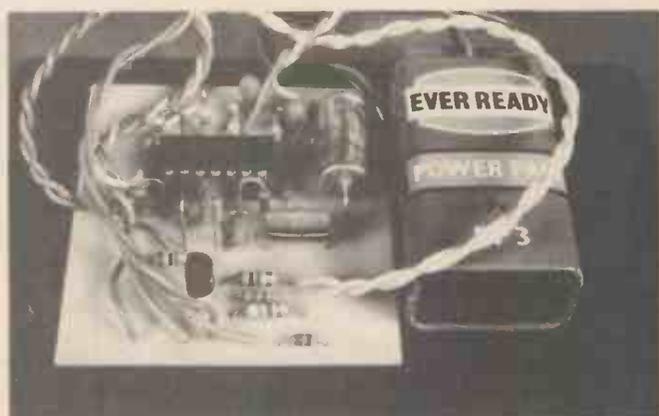Next, reduce the effect value of the 100k probe resistor by shunting it with a 1M Ω resistor, and check that the tone signal rises. Experiment with the LEVEL







Close-up of the PCB and battery, the PCB is mounted on to the case by double-sided sticky pads.



and SENSITIVITY controls to find a setting where the maximum possible frequency shift occurs when a small change is made in the value of the probe resistance. Experiment with different values of resistor, to get the 'feel' of the monitor.

When you are confident that the GSR monitor is ready for use, make up a pair of conductive electrodes from soft steel wool and bond them to the fleshy tips of two adjacent fingers of your non-dominant hand with sticky tape or wire, and connect them to the probes. Now just sit down and relax in a comfortable chair, and try to control the audio tone of the machine with your mind. After a few sessions of practice, you should be able to control the machine's tone, and your own mental state, without difficulty. If you can't, don't ring us, we'll ring you!

HE

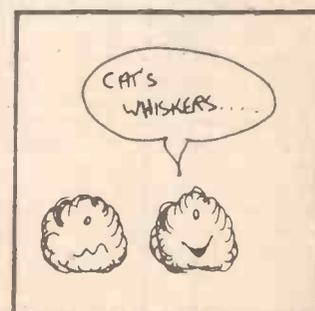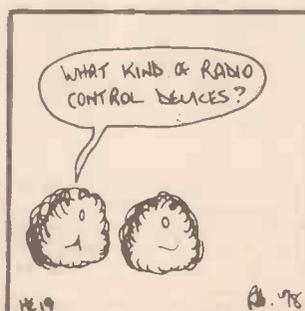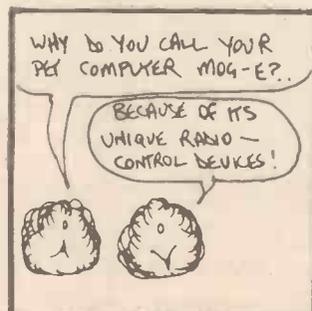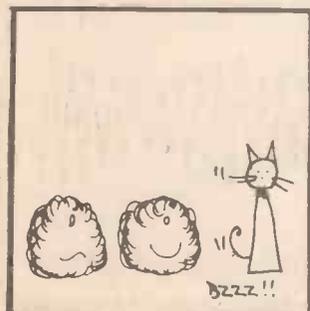



First there was ETI, catering for the middle-range to advanced electronics enthusiast. Then there was HE which was aimed at the newcomer to the field. Now there is Computing Today from the same stable. CT covers the area of small-business and amateur computing and deals with both software and hardware. CT's third issue (cover date of May) is out now — 50p at your newsagent.

Short Circuit

TREMOLO UNIT


This is one of the most popular types of special effect unit for use with guitars, the operation is to amplitude modulate the input signal with a low frequency signal. Thus a constant input as in (a) would emerge from the tremolo unit varying in amplitude at a low frequency as in (b).

In this circuit the input signal is taken to the input of an electronic attenuator (based on IC2) via a common emitter amplifier using Q1. R6 sets the gain of the attenuator (with zero modulating voltage) at about unity, but the amplification provided by Q1 gives an output level of a few hundred millivolts. This can either feed a high level input of the amplifier, or R7 can be adjusted to attenuate the output to a level which is suitable to drive the ordinary guitar input. It is necessary to have the stage of amplification ahead of the IC2 so that this part of the circuit is handling a fairly high signal level, and gives a good signal to noise ratio.



The gain of IC2 can be varied by applying a control voltage to pin 2. This control signal is generated by a conventional CMOS astable circuit which uses two of the gates contained in IC1. The operating frequency of the astable can be varied from about 1 to 10 Hz by means of frequency control RV1. A squarewave signal is produced by the astable, and this must be filtered

to remove the high frequency components in order to give a smooth and pleasant tremolo effect. This filtering is given by R2 and C4. RV2 controls the

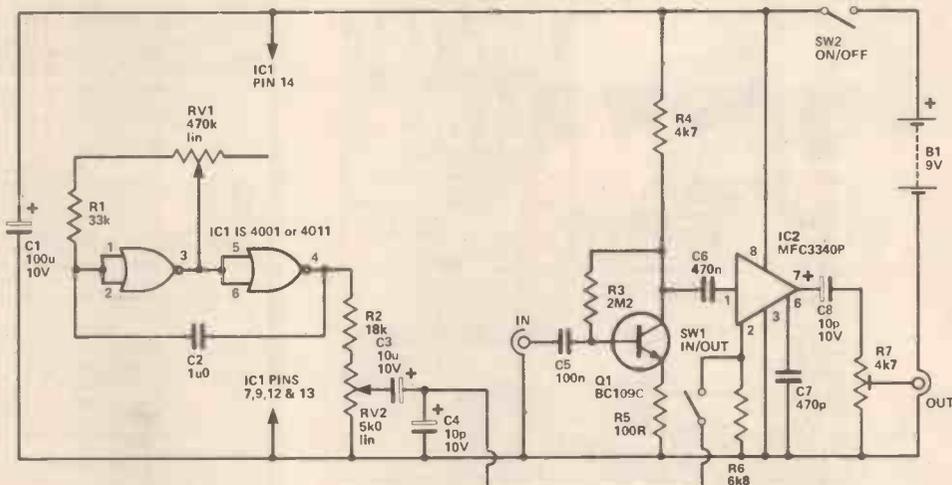amplitude of the modulating signal and acts as the tremolo depth control. SW1 can be used to disconnect the modulation when the tremolo effect is not required.



TOP VIEWS

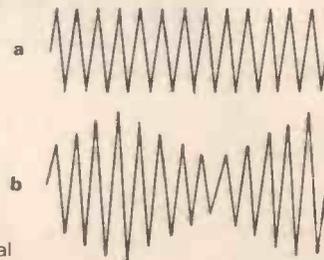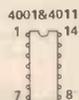

TANTALUM				
BEAD		2200 40V	.64	
1.35V	.10	4700 63	.36	
1.535V	.10	TAG 2200 63V	1.72	
22.35V	.10	TAG 4700 63V	1.90	
33.35V	.10			
47.35V	.10			
68.35V	.10			
1.35V	.10			
1.535V	.11			
2.216V	.10			
2.235V	.12			
3.316V	.11			
3.335V	.12			
4.710V	.11			
4.725V	.12			
4.735V	.13			
6.835V	.15			
10.63V	.12			
10.16V	.13			
10.25V	.15			
10.35V	.16			
15.16V	.15			
15.25V	.16			
22.10V	.15			
22.16V	.16			
22.25V	.18			
33.10V	.18			
33.16V	.24			
33.25V	.26			
47.63V	.16			
47.10V	.18			
47.16V	.25			
68.2V	.15			
100.3V	.16			
100.63V	.24			
100.10V	.28			
220.3V	.24			

RADIAL ELECTROLYTICS			
47.50V	.06	2200 63V	1.72
1.50V	.08	TAG 4700 63V	1.90
2.250/63V	.06		
3.350V	.06		
4.750V	.07		
10.16V	.06		
10.25V	.06		
10.63V	.08		
22.10V	.06		
22.16V	.06		
22.25V	.07		
33.10V	.08		
33.16V	.08		
33.25V	.07		
47.16V	.07		
47.25V	.08		
47.63/50	.15		
100.10V	.06		
100.16V	.08		
100.25V	.09		
100.63V	.22		
220.10V	.04		
220.16V	.10		
220.25V	.19		
330.10V	.18		
330.25V	.19		
470.63	.09		
470.16V	.15		
470.25V	.21		
470.50V	.35		
1000.16V	.18		
1000.25V	.35		
2200.63	.24		
2200.16V	.38		

ADIAL ELECTROLYTICS			
47.63V	.08		
1.63V	.06		
2.63V	.08		
4.75V	.06		
4.75V	.06		
10.25V	.08		
10.25V	.08		
10.63V	.10		
10.450V	.27		
22.25V	.08		
22.450V	.47		
33.25V	.04		
47.10V	.07		
47.25V	.06		
47.63V	.12		
47.450V	.60		
100.16V	.10		
100.25V	.10		
100.63V	.19		
220.16V	.12		
220.25V	.13		
220.63V	.30		
470.25V	.28		
680.16V	.35		
1000.25V	.35		
2200.25V	.70		
2200.40V	.75		
4700.25V	.85		

'MYLAR' Epoxy Dipped Polyester Capacitors.			
Standard values from .001			
mid through .47 mid, 100			
V.O.C. 10%.			
.001: .015: .022: .033: .047:			
.056: .1: .15: .22: .33: .47:			
.00-.0033	.03		
.01-.0022	.03		
.01-.015	.035		
.018	.035		
.022	.04		
.033: .039	.04		
.047: .056	.045		
.068-.082	.045		
.1	.05		
.15	.072		
.18	.075		
.22	.08		
.27	.08		
.33	.085		
.47	.13		

MULTILAYER POLYESTER CAPACITORS 5% Tolerance 7.5mm PCB			
.001	.06		
.0015	.06		
.0022	.06		
.0033	.06		
.0047	.06		
.0056	.06		
.01	.06		
.015	.06		
.022	.07		
.033	.07		
.047	.07		
.068	.08		
.1	.10		
.22 (100V)	.13		
.47 (100V)	.22		
.88 (100V)	.25		
1.0 (100V)	.28		

NOISE SUPPRESSION CAPACITORS 250V AC PCB 10mm 22.25 Radial			
.03			
.035			
.055			
.08			
.04			
.05			
.035			
.06			

5mm FITCH CERAMIC CAPACITORS TUBULAR RADIAL 250V			
Stock Values			
15: 47.56: 100: 1000: 1500: 2200:			
2700: 3300: 4700: 5600: 6800:			
8200: 10,000: 100,000pF			
*New Addition (63V)			

Ceramic Capacitors EDPU 63V Stock Values pF			
1: 2.2: 3.3: 4.7: 5.6: 6.8: 8.2: 10: 12: 15: 18: 22: 27: 33: 39: 47: 56: 68: 82: 100: 150: 180: 220: 270: 330: 390: 470: 560: 680: 820: 1000: 2200: 3300: 4700: 10,000: 22,000:			
1-47pF 2% (Low K)	.03		
56-100pF 2% (Low K)	.035		
100-150pF 2% (Low K)	.055		
180-820pF 10% (Med. K)	.03		
1000-2200pF 10% (Med. K)	.04		
3300-4700pF 10% (Med. K)	.05		
10,000-20 + 80 40V	.035		
22,000-20 + 80 40V	.06		
Alternatives 625/630/632 Series			

GREENWAY ELECTRONIC COMPONENTS

62 MAYPOLE RD
ASHURST WOOD
EAST GRINSTEAD SX RH19 3RB.
Tel: Forest Row (034-282) 3712




DIGITAL 24 HOUR CLOCK

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS

£5.00
£6.99

THREE FOR £13.50 MECHANISMS 10 FOR £39. 100 FOR £300

● AC MAINS
● SIZE 6 3/8 x 2 3/8 x 2 3/8
Your receipt is a 2-year guarantee

HALF PRICE OFFER

HENRY'S Radio

404 EDGWARE ROAD, LONDON W2 1ED 01-723 1008

EXPORT ENQUIRIES INVITED

DELIVERY FROM STOCK

TOPS THE PACK!



COMPONENTS — Now over 1,000 types in stock!

KITS — See the new range of low-cost 'ELEKITS'.

SERVICE QUALITY PRICES — All guaranteed products.

MAGAZINE PROJECTS — Trouble-free!

S.A.E. for list of HE projects

I enclose 30p*, please send catalogue.

Name _____

Address _____

*Refundable with future orders over £5.00.

T.V. GAMES

PROGRAMMABLE - £31.86 inc. VAT COLOUR CARTRIDGE TV GAME

The TV Games can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt The Sub, and Target. The console comes complete with two removable joystick player controls to enable you to move in all four directions [up/down/right/left] and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores, bats and balls. Lifelike sounds transmitted through the TV's speaker, simulating the actual game being played.

Manufactured by Waddingtons Videomaster and guaranteed for 1 year.

6 GAME - COLOURSCORE II - £14.59 inc. VAT

This non-programmable console offers four exciting COLOUR games, Tennis, Squash, Hockey, Solo 1, Football, Basketball, Gridball, Solo 2 and two unique built-in target shooting games. Features include two removable joystick player controls to enable you to move in all four directions [up/down/right/left] and built into these joystick controls are ball serve and target fire buttons. Other features include handicapping switch, ball speed switch, automatic on screen digital scoring and colour coding. Realistic hit sounds are transmitted through the TV's speaker. (Manufactured by Waddingtons Videomaster and guaranteed for 1 year).

10 GAME - COLOUR SPORTSWORLD £24.30 inc. VAT

This non-programmable console offers ten exciting COLOUR games, Tennis, Squash, Hockey, Solo 1, Football, Basketball, Gridball, Solo 2 and two unique built-in target shooting games. Features include two removable joystick player controls to enable you to move in all four directions [up/down/right/left] and built into these joystick controls are ball serve and target fire buttons. Other features include handicapping switch, ball speed switch, automatic on screen digital scoring and colour coding. Realistic hit sounds are transmitted through the TV's speaker. (Manufactured by Waddingtons Videomaster and guaranteed for 1 year).



EXTRA CARTRIDGES:
ROAD RACE — £9.58 inc. VAT.
Grand Prix motor racing with gear changes, crash noises, etc.
SUPER WIPEOUT — £9.90 inc. VAT
10 different games of blasting obstacles off the screen.
STUNT RIDER — £13.13 inc. VAT.
Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses, etc.



CHESS COMPUTERS

THE WADDINGTONS VIDEOMASTER STAR CHESS - £59.50 inc. VAT

PLAY CHESS AGAINST YOUR PARTNER

using your own TV to display the board and pieces

Star Chess is a new absorbing TV game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour (or black and white) on your TV screen. Based on the moves of chess, it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there is a whole new dimension of unpredictability and chance added in the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve month guarantee.

CHESS CHAMPION 6 - £89.50 inc. VAT

PLAY CHESS AGAINST THE COMPUTER - 6 LEVELS

Chess Champion is a newly developed electronic microcomputer, manufactured by WADDINGTONS VIDEOMASTER. The stylish, compact, portable console can be set to play at six different levels of ability from beginner to expert including "Mate in two" and "Chess by Mail". The computer will only make responses which obey international chess rules. Casting, on passant and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazine or newspaper or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button. Chess Champion comes complete with a free 9V mains adaptor, full instructions and a twelve month guarantee.

World chess champion ANATOLY KARPOV says:
"This chess computer is a new and interesting partner with remarkable game variations."

CHESS CHALLENGER 7-£92.50 inc. VAT

Play chess against the computer at 7 different levels. (Similar to Chess Challenger 10 but unit has only 7 levels of play). Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months' guarantee.

CHESS CHALLENGER 10-£154.50 inc. VAT

NEW IMPROVED PROGRAMME - MK 2, APRIL, 1979

Play chess against the computer at 10 different levels. Price includes unit with solid walnut case, deluxe simulated leather & brushed gold foil playing surface & Staunton designed magnetised chess pieces. Comes complete with a mains adaptor and 12 months guarantee.

BORIS - £178.50 inc. VAT

Boris is an advanced chess computer that's programmed for all classic chess moves. He will play Black or White, even himself. He'll even teach you how to play chess and suggests the moves for you when you're unsure of what to do next. Boris can talk to his opponent through his alphanumeric display and will flash different messages during each game to keep you on your toes. Boris will not allow illegal moves, and will allow you to enter problems or set up your own board positions. Boris comes in hand crafted, solid walnut case with chess pieces and board. Comes complete with a mains adaptor and 12 months guarantee.






FOR FREE BROCHURES - SEND S.A.E.

For free illustrated brochures and reviews on TV, and chess games please send a stamped, addressed envelope and state which particular games you require information on.
Callers welcome at our shop in Woking — demonstrations daily — Open from 9am-5.30pm Mon.-Sat. (9am-1pm Wed.).
To order by telephone please quote your name, address and Access/Barcode number VAT is included in all prices above — Postage & Packing FREE

AJD DIRECT SUPPLIES LIMITED, Dept. HE3
102 Bellegrave Road, Welling, Kent DA16 3QD
Telephone: 01-303 9145 (Day). 01-850 8652 (Evenings)

Display Techniques

As digital electronics spreads from the lab. to everyday life, we are becoming more familiar with LED and LCD displays. Tim Orr goes into the pros and cons of a variety of display techniques.

A LOT OF ELECTRONIC equipment needs some sort of a display mechanism. A digital watch needs a number display that consumes almost zero power and which can be seen in daylight and in the dark. Pocket calculators need numerical displays. Digital multimeters and frequency meters need numerical displays. Pocket language translators (English to French for example) need an alphabetic display. Hand held audio spectrum analysers need an array of LED bar displays. In fact there is an enormous present and future requirement for all sorts of displays.

One of the oldest types of display is the light bulb, the incandescent lamp. This, however, requires a lot of power, which usually ends up as heat. It isn't very easy to build into products and it breaks too easily. The modern equivalent is the Light Emitting Diode (LED), the all electronic light source. It can be built in several colours — red, orange, yellow, green and even infra-red. It is basically a diode that emits light when the current passing through it is in the region of 4 to 40 mA. It is possible to construct the diode in a variety of shapes, a common one being the seven segment display (Fig. 1). The seven segments are seven diodes which can be turned off or on. In doing so it is possible to generate a variety of displays. Numbers from nought to nine and sometimes the letters A to F (a mixture of upper and lower case) are produced. The most common use of the seven segment display is to display numbers from some digital system, for example a counter.

COUNT ON THIS

However, the output from a binary decade counter is in an unsuitable form to drive the display. It is in a code called BCD (Binary Coded Decimal), which consists of four signals. These have to be decoded so that the seven segments are turned on in the correct sequence as the count proceeds. The piece of electronics that does this is called a 'BCD to seven segment decoder driver'. Fig. 1c shows the truth table for one of these devices. Most decoders only work from 0 to 9, but a few will also give an A to F display as well. There are two types of seven segment LED displays. One is called 'common anode' because all the anodes are connected together, the other is called 'common cathode' because all the cathodes are common.

Each seven segment display has eight wires connected to it. Thus a ten digit calculator display could

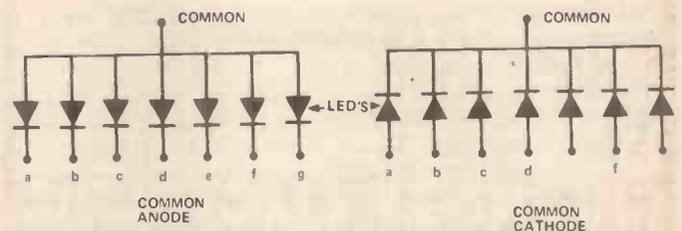


Fig. 1a. Schematic diagram of 7 segment displays

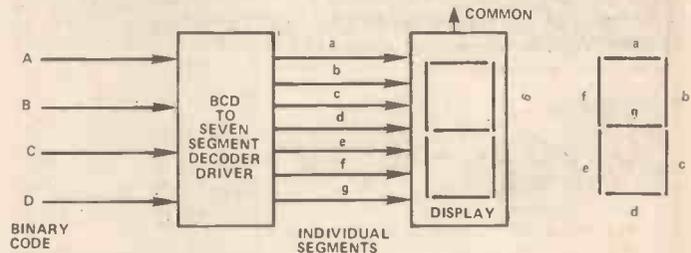


Fig. 1b. 4 bit binary input to 7 segment decoder

BCD	BINARY CODE				SEGMENTS							DISPLAY
	D	C	B	A	a	b	c	d	e	f	g	
0	0	0	0	0	ON	ON	ON	ON	ON	ON	ON	0
0	0	0	0	1	—	ON	ON	—	—	—	—	1
0	0	0	1	0	ON	ON	—	ON	ON	—	ON	2
0	0	1	0	0	ON	ON	ON	ON	—	—	ON	3
0	0	1	0	1	—	ON	ON	—	—	ON	ON	4
0	1	0	0	0	—	ON	ON	—	—	ON	ON	5
0	1	0	1	0	ON	—	ON	ON	—	ON	ON	6
0	1	1	0	0	—	ON	ON	ON	ON	ON	—	7
0	1	1	1	0	ON	ON	ON	—	—	—	—	8
1	0	0	0	0	ON	ON	ON	ON	ON	ON	ON	9
1	0	0	0	1	ON	ON	ON	—	—	ON	ON	A
1	0	0	1	0	ON	ON	ON	ON	—	ON	ON	B
1	0	1	0	0	ON	ON	ON	ON	ON	ON	ON	C
1	0	1	0	1	—	ON	ON	ON	ON	ON	ON	D
1	0	1	1	0	—	ON	ON	ON	ON	ON	ON	E
1	1	0	0	0	ON	—	—	ON	ON	ON	—	F
1	1	0	0	1	—	ON	ON	ON	ON	ON	—	G
1	1	0	1	0	ON	—	—	ON	ON	ON	ON	H
1	1	1	0	0	ON	—	—	ON	ON	ON	ON	I
1	1	1	0	1	ON	—	—	ON	ON	ON	ON	J
1	1	1	1	0	ON	—	—	ON	ON	ON	ON	K
1	1	1	1	1	ON	—	—	ON	ON	ON	ON	L

MOST DECODERS ONLY WORK FROM 0 TO 9

0 = LOGIC LOW
1 = LOGIC HIGH
ON = SEGMENT ON
— = SEGMENT OFF

Fig. 1c. Truth table for BCD to 7 segment decoder/driver

have 80 wires connected to it, which is clearly not a very good idea. It would also mean that the calculator integrated circuit would have to have something like 100 legs on it! The way in which large and even small

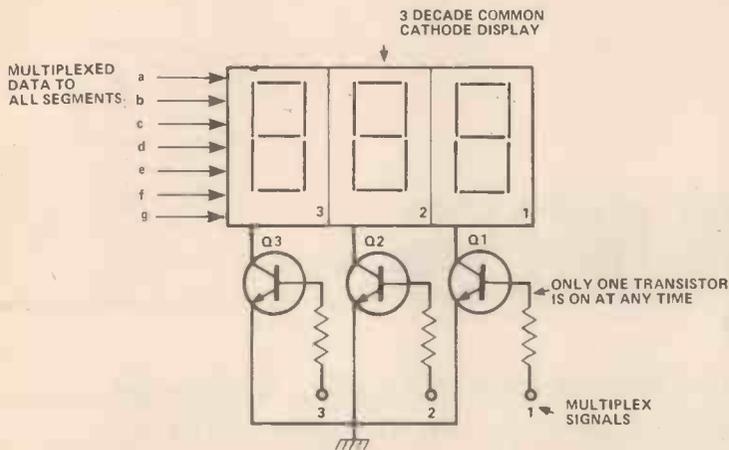


Fig. 2. Multiplexing arrangements to reduce the amount of interwiring

displays overcome this problem is to use a process called multiplexing (Fig. 2). This reduces the number of wires from 80 for a ten digit display to 17 by time sharing the data. What happens is relatively simple. The 'a' segments in the display are connected together and so are all the other segments. However, each common cathode (or anode in the case of common anode), is separately turned on by a transistor. The sequence of operation is as follows. Transistor Q1 is turned on, the seven segment data for display 1 is selected and so display one lights up. Next Q2 is turned on, the data for display two is selected and so display two lights up. Then Q3 is turned on and then the process repeats itself.

SPEED

In a ten digit system each digit will only be on for 10% of the time. If the multiplex speed is fast enough the eye will not see the LED's being turned on and off

and will see a continuous display. Take a LED display pocket calculator. Light up a few digits. They will not appear to flicker. Move the calculator rapidly in a circle and you will see the multiplexing process in operation as a string of flashing digits.

Most multiple seven segment displays are structured so as to be multiplexable. Also many of the integrated circuits that generate the display data output their information in a multiplexed format. Large scale integration (LSI) has produced many useful systems in a single pack. You can buy a Digital Voltmeter (DVM) and a multi-decade counter-decoder integrated circuit (Fig. 3). A few years ago if you wanted to build a four decade counter display system you would have needed four decade counters which generate the BCD codes. Also, four latches (four bits) to store the count. Also four BCD to seven segment decoder drivers and four seven segment displays. This totalled up to 16 IC's and over a hundred wires. However, using the new method, a four decade counter/latch/decoder/driver with multiplexed data output and a four figure display, the system is incredibly simple. This is because all those IC's have been stuck into one LSI chip. This trend towards LSI makes system design so much simpler. For instance a frequency meter can be constructed out of four or five IC's (Fig. 4), or a digital voltmeter can be made from only two IC's (Fig. 5). There are also many other LED displays and drivers. There is a dot matrix which can produce all the letters of the alphabet as well as numbers, (alpha-numeric display). There are also some IC's that can light up a string of LED's for bar displays, the light of the bar being controlled by an analogue voltage. This is particularly useful for making LED audio level meters or a large SY matrix LED display.

HEAVY LED

There are some disadvantages in using LED's. They can consume a considerable amount of current and you

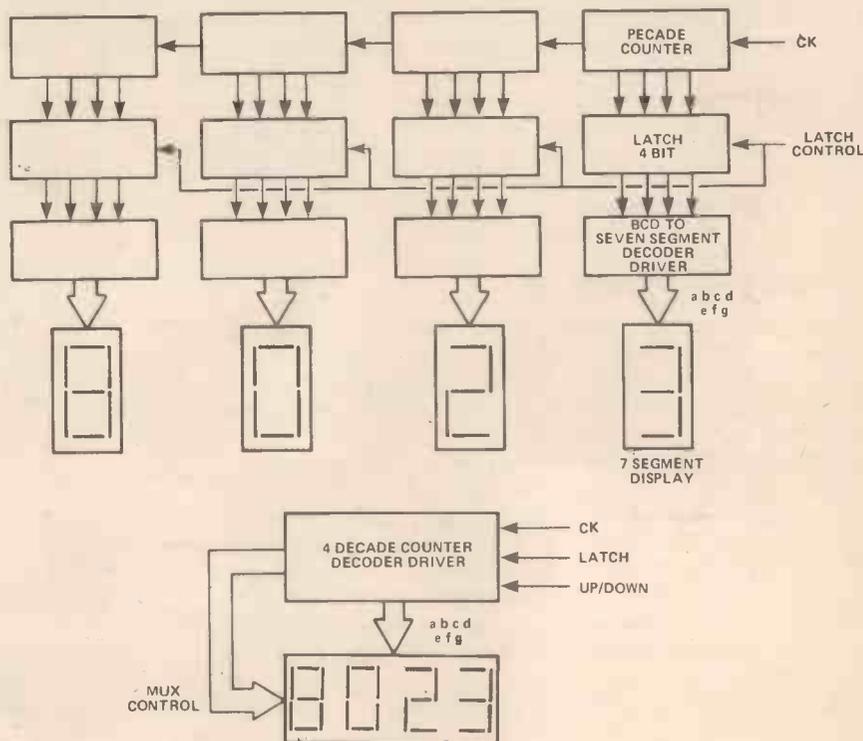


Fig. 3. Two methods of display driving, the older method (upper) uses quite a large number of individual IC's. Using LSI Technology all of this (lower) can be reduced to one chip

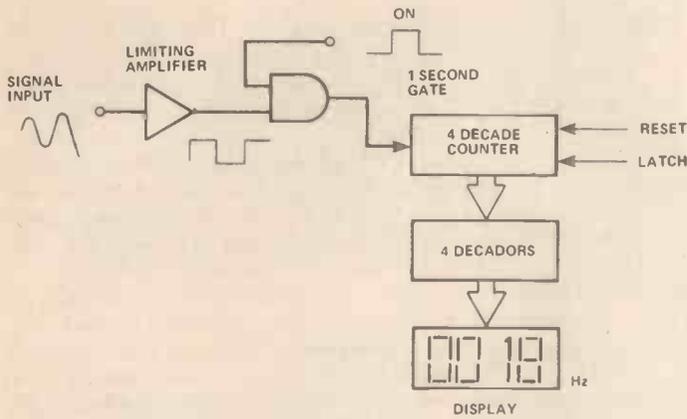


Fig. 4. Using LSI chips a frequency meter can be built using only a few chips

can't see them at all well in strong lighting conditions. This is where the liquid crystal display (LCD) is very useful. It consumes virtually zero power and it usually works on reflected light, so the brighter the better. The display is constructed by sandwiching a liquid crystal in-between two glass plates. The seven segment pattern is deposited on the glass in a thin transparent metal layer. These segments are connected to pins at the side of the display unit. The rear glass plate is one continuous electrode. When an electric field is applied between a front and rear electrode, there is a 'twist effect' that stops any light being transmitted. This makes the electrode appear black. Otherwise, with no field present, all the

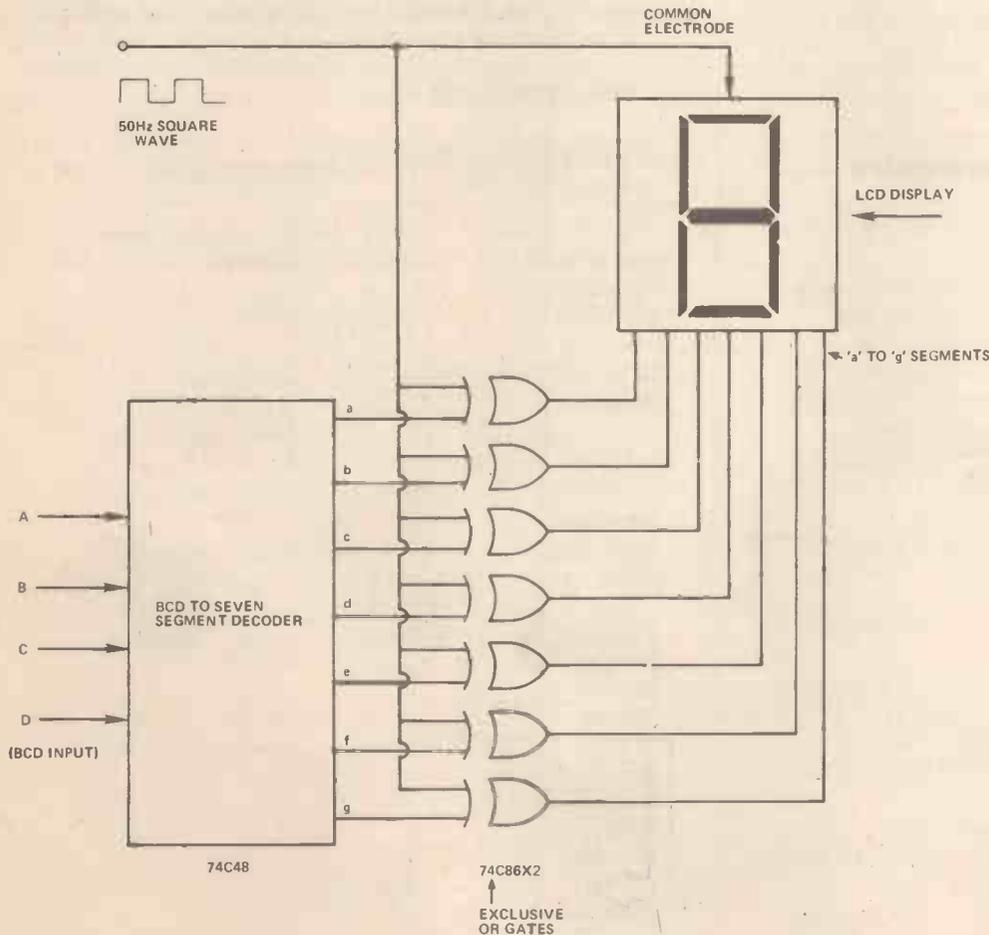


Fig. 6. A method of driving an LCD display using exclusive OR gates

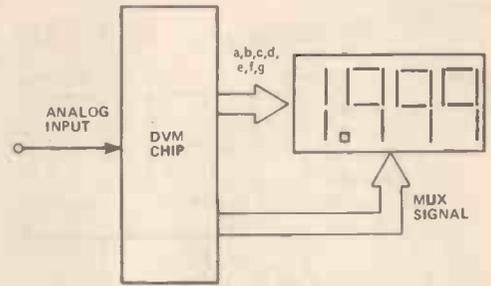


Fig. 5. Again LSI technology produces a simple DVM (Digital Volt Meter) from only a couple of chips

light can pass through the liquid crystal and so it appears transparent.

Liquid crystals can be constructed so that they have a reflective back electrode or they can be transmissive so that they can be illuminated from the rear. There are chemical light sources that can be used for rear lighting. These are small tubes of radioactive material that glow for ten to twenty years. (Beat that EverReady). However, the liquid crystal is slow in changing from dark to light and so cannot yet be used in a multiplexed system. As the pattern of the electrode determines the shape that you see it is relatively easy to get liquid crystal displays built to produce your own particular graphics. Also they are now becoming available in different colours and it has just been announced that a Japanese company has made a working model of a flat liquid crystal TV display although it is still in its early stages.



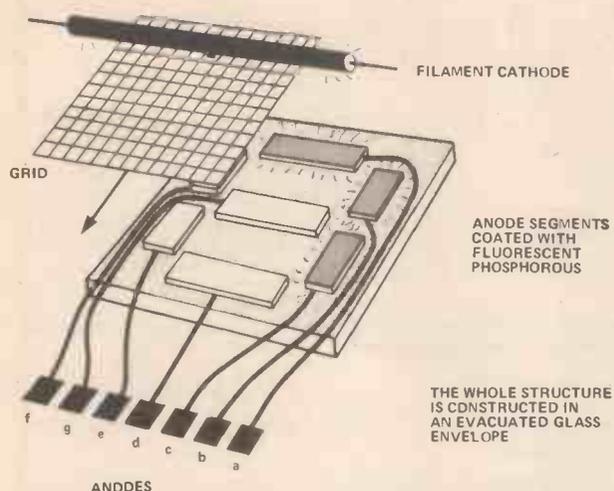


Fig. 7. Construction of a common anode Fluorescent display

LONG LIFE

To ensure an LCD display has a long lifetime, the average DC component of the energising signal should be zero. This is usually obtained with an exclusive OR driving network as shown in Fig. 6. LCD displays do have a few disadvantages. They are rather expensive. They can easily be damaged by mechanical fracture and leakage of their hermetic seal. Also strong sunlight can eventually bleach their polarising filters.

Another very popular display medium is the fluorescent display. This is relatively inexpensive and combines high brightness with moderately low power consumption. The fluorescent display is rather like the old fashioned gas discharge tube. It is constructed inside an evacuated glass envelope and uses three electrodes,

a cathode, which is a low temperature filament, a grid, which is a wire mesh that separates the cathode from the anode (the grid is used to turn the display on and off), and the third electrode is the anode, which can be constructed in any shape, a seven segment being common (Fig. 7). The anode is coated with a fluorescent material that glows a green/blue colour when fast moving electrons (from the cathode) strike it. Thus, by connecting the right voltage to the anode segments (typically 24 V), a seven segment display can be generated.

LIGHT FANTASTIC

Fluorescent displays can be multiplexed and this is where the grid is used. The grid can be biased to collect all the electrons from the filament so that none strike the anodes of that digit and so no light is generated except on the display for which the seven segment data was intended. One company (ITRON) makes an enormous range of display shapes. These include seven segment displays with various characters like AM, PM, kΩ, V, A, analogue bar displays, 14 segment alpha-numeric displays, 5x7 dot matrices. I have also seen fluorescent aircraft altitude displays and enormous XY matrix.

Display technology is making great improvements all the time. Maybe in the next decade we can look forward to developments such as flat tube displays (making pocket TV and oscilloscopes possible) and multi-colour, fast moving multiplexable LCD displays. These could be linked to solid state TV cameras making all electronic cameras possible. The film for these devices could be erasable Read Only Memories. Maybe these will appear in the next decade. However, for those who want to purchase something now, here is a list of a few currently available products. Fig. 8.

HE

Part number & manufacturer	Description	Part number & manufacturer	Description
SN 7447 TEXAS	BCD to seven segment decoder driver	SGS ATES MC14553 Motorola	analogue input into dot display 3 digit BCD counter. Mux output
MM 74C912 National Semiconductors	6 digit BCD display decoder driver. 0→9 A→F outputs. Internal memory	ZN1040 Ferranti	4 decade counter driver. Mux output
MC 14511 Motorola	BCD to seven segment latch/decoder/driver	ICM 7217 Intersil	4 decade counter driver. Mux output
CA 3161E RCA	BCD to seven segment decoder/driver. Designed to go with the CA3162E A to D converter	ICL 7106 Intersil	3½ digit DVM chip with LCD display outputs
TIL 311 Texas	LED dot display + store, decoder, driver. Displays 0→9, A→F (hexadecimal)	ICL 7107 Intersil	3½ digit DVM chip with mux LED output
TIL 307 Texas	LED display + counter decoder driver	CA 3162E RCA	Analog to digital converter. 3 digit BCD outputs. Multiplexed. Designed to go with CA3161E LED seven segment displays
TIL 305 Texas	5x7 alpha numeric dot matrix display. Can display, A to Z, 0 to 9, and other symbols	Fairchild Litronix Monsanto Texas	
DD10R ITT	Bar graph. 10 LEDs in a DIL package	ITT	LCD seven segment displays
LM3914 National Semiconductor	Dot/bar display driver. Converts an analogue input into a dot or bar display	Brown Boveri Swarovski Beckman Hamilins	
UAA 170	Dot display driver. Converts	ITT Futaba	Fluorescent displays



20 x 20 WATT STEREO AMPLIFIER
 Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red rms indicator and stereo jack socket. Functions switch for mic, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watts peak. For use with 8 to 15 ohm speakers.
£29.90
 £2.50 p&p

30x30 WATT AMPLIFIER IN KIT FORM
 For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 4.15 ohms speakers.
£29.00 + p&p £2.50

SPECIAL OFFER
30 x 30 WATT AMPLIFIER KIT with BSR P200 belt drive deck and Shure M75 cartridge.
£55.00 + p&p £5.00

EMI SPEAKER BARGAIN
 Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max 8 ohm impedance.
£14.95
 Per stereo pair + £3.40 p&p

BSR P200
 Belt drive chassis turntable unit semi automatic, cueing device.
£24.95 p&p £2.50
 A.D.C. QLM 30 Mk III Magnetic Cartridge to suit.
£7.75

BSR Manual single play record deck with auto return and cueing lever. Fitted with stereo ceramic cartridge 2 speeds with 15 r.p.m. spindle adaptor ideally suited from home or disco use.
OUR PRICE £10.95 p&p £2.50

GARRARD DECK MODEL CC 10A
 Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.
£7.95 p&p £2.00 Size 12" x 8 1/2"

SANYO Nic/cad battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 3/4" x 1 1/4" x 2" approx.
£7.50 p&p £1.50

BARGAIN FOR PERSONAL SHOPPERS ONLY
Altone UA4 Stereo System
 Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones.
 complete with speakers. **£34.95**

Micro Cassette Recorder
 Pocket size—home or office use or when travelling.
£13.95

Battery operated fluorescent camping lamp.
 Runs off 8 U2 batteries.
£4.50

Mullard

AUDIO MODULES IN BARGAIN PACKS
CURRENT CATALOGUE

PRICE £ AT OVER 25 PER PACK

SEE OUR PRICES


1 PACK 1. 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input.
 OUR PRICE p&p £1.00 **£4.95**

2 PACK 2. 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.
 OUR PRICE p&p £1.00 **£7.45**

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

10 + 10 AMPLIFIER KIT
 An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit.
 Size approximately 9 3/4" x 8 3/4" x 4"
 p&p £2.05 **£11.95**

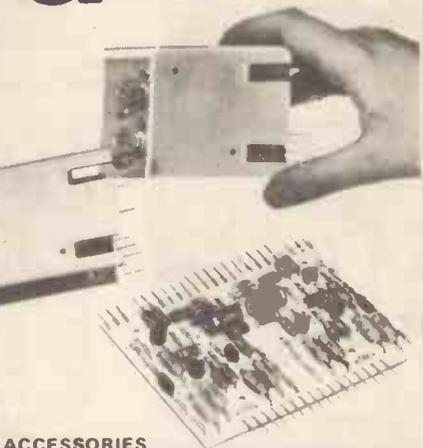ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.



ACCESSORIES
 Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£2.90** plus £1.50 p&p
Two Way Speaker Kit
 Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£3.95** per stereo pair plus £1.50 p&p

BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish **£5.95**

LCD 5 function men's digital watch stainless steel finish **£6.95**

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish **£12.95**

POCKET CALCULATOR. With LED display, memory and percentage key **£2.95**

AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer.
£11.95

125 Watt Power Amp Module **£13.95**

Mains power supply for above unit **£3.50**

MULLARD Built power supply **£1.50**

DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc crossovers **£20.00**

VIDEOMASTER Super Score TV Game with pistol mains operation **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation **£41.95**

VIDEOMASTER COLOUR SHOT TV GAME
 Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED. OPPORTUNITY AT **£9.95 ONLY**

50 WATT MONO DISCO AMP
£29.95
 Size approx: 13 1/4" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches, independent bass and treble controls and master volume.

70 & 100 WATT MONO DISCO AMP
 Size approx 14" x 4" x 10 1/4"
 Brushed aluminium fascia and rotary controls. Five vertical slide controls, master volume, tape level, mic level, deck level. PLUS INTER DECK FADER for perfect graduated change from record deck No 1 to No 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak.
 70 watt **£57**
 140 watt peak p&p £4.00
 100 watt **£65**

For personal shoppers only
DUO II SPEAKERS
 Attractive teak finish, modern design, incorporating 2 speaker units—8" approx woofer and 2 1/2" approx tweeter. 45 to 1800 Hz Impedance 8 ohms. Power 15 watts RMS. 20 watts max. Per stereo pair **£17.00**

FOR PERSONAL SHOPPERS ONLY
STEREO RADIOGRAM CABINET
 Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**
 Size approximately 47" x 15 1/2" x 15"




325 EDGWARE ROAD, LONDON W2 21H HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only. No callers
ALL PRICES INCLUDE VAT AT 12 1/2%
 All items subject to availability. Price correct at 4/4/79 and subject to change without notice

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers **GOODS NOT DESPATCHED OUTSIDE UK**

SPECIALS

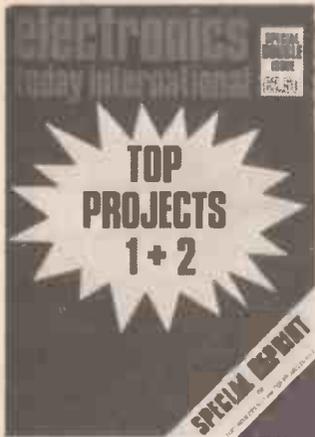

TOP PROJECTS

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp., low power laser, printmeter, transistor tester, mixer preamp., logic probe, Ni-Cad charger, loudhailer, 'scope calibrator, electronic ignition, car theft alarm, turn indicator canceller, brake light warning, LM3590 circuits, temperature alarm, aerial matcher, UHF-TV preamp., metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

Book 3: SOLD OUT!

Book 4: £1.00 + 25p P&P.

Sweet sixteen stereo amp., waa-waa, audio level meter, expander/compressor, car theft alarm, headlamp reminder, dual-tracking power supply, audio millivoltmeter, temperature meter, intruder alarm, touch switch, push-button dimmer, exposure meter, photo timer, electronic dice, high-power beacon, electronic one-armed bandit ...


Book 5: £1.00 + 25p P&P.

5W stereo amp., stage mixer, disco mixer, touch organ, audio limiter, infra-red intruder alarm, model train controller, reaction tester, headphone radio, STD timer, double dice, general purpose power supply, logic tester, power meter, digital voltmeter, universal timer, breakdown beacon, heart rate monitor, IB metal locator, temperature meter ...

Book 6: £1.00 + 25p P&P.

Graphic equaliser, 50/100W amp. modules, active crossover, flash trigger, "Star and Dot" game, burglar alarm, pink noise generator, sweep oscillator, marker generator, audio-visual metronome, LED dice, skeet game, lie detector, disco light show ...

Graphic Equaliser... Marker Generator
Power Amplifier Modules... 62 Sound
CCTV Camera... Headphone Adaptor
LED Dice... Sound-Light Flash Trigger
Expander-Compressor... Skeet
ETI TOP PROJECTS
NO 6 electronics today £1
Burglar Alarm... Digital Thermometer
Stars & Dots Logic Game... Lightshow
Active Crossover... Hear and Tell Unit
Pink Noise Generator... GSR Monitor
Sweep Oscillator... Stereo Simulator

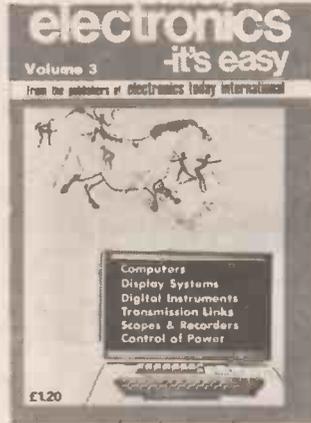

FROM THE PUBLISHERS OF
ELECTRONICS TODAY INTERNATIONAL

ETI CIRCUITS No 2

£1.50

ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and HI-FI! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.

ELECTRONICS — IT'S EASY Books 1, 2 & 3.

Our successful beginners series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail!) and together form an excellent starting point for anyone interested in learning the art of electronics.

£1.20 + 25p P&P each.

ETI CIRCUITS Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.

ORDER FROM

Specials Modmags Ltd 25-27 Oxford Street London W1R 1RF

Postage and packing also refers to overseas. Send remittance in Sterling only.

Please mark the back of your cheque or PO with your name and address.

from ETI

Envelope Generator



Here's a project that you can use to simulate the sound of any musical instrument, or used with the HE White Noise Generator to produce various sci-fi effects.



SO WHAT, YOU MAY ASK, is an ADSR (Attack, Decay, Sustain, Release) envelope generator, and what is it used for? It is a device that is used in electronic sound and music synthesis to mould the output sound envelope of a standard input signal (a tone or white noise signal) to the precise shape desired by the operator. By modifying the envelope, the operator can simulate the sounds of all types of musical instruments, or can simulate man-made sounds such as gun shots, explosions, steam engine 'chuffs', etc., or can create completely new 'science fiction' types of effects at will.

The action of the ADSR generator can be understood more clearly with the aid of the explanatory diagram of Figure 1. The top part of this shows what happens if you pass a steady tone signal through a linear transmission gate (an electronic switch) that is activated by an external control switch. The input signal appears at the output, with virtually zero 'Attack' time, as soon as the control switch is closed, it has a 'Sustain' amplitude identical to that of the input signal for the duration of the switch closure, and disappears with virtually zero 'Release' time as soon as the switch is opened again. The resulting output signal sounds completely artificial and uninteresting.

ATTACK AND DECAY

The lower part of the diagram shows what happens if the same input signal is passed through the ADSR envelope

Fig. 1. The diagram at the top shows the totally artificial waveform that is generated when a simple signal is passed through a transmission gate. The lower diagram shows the more realistic waveform that is produced when the same signal is passed through the ADSR envelope generator.

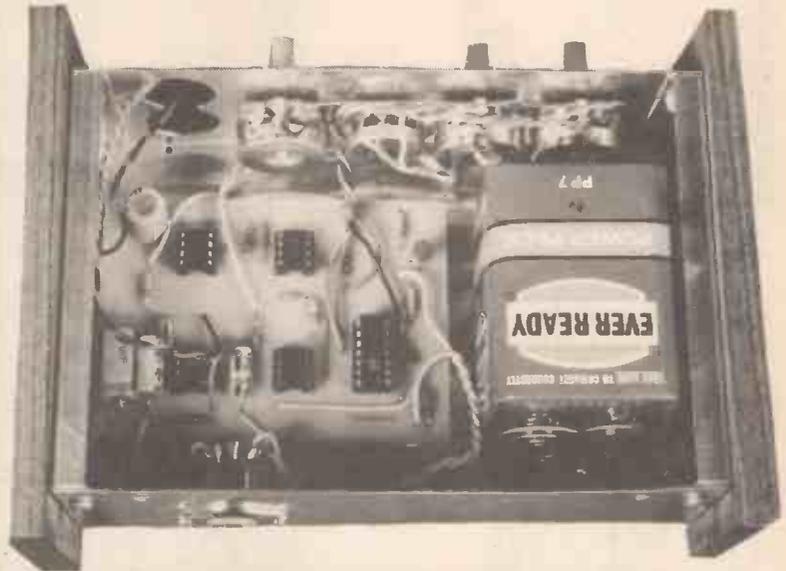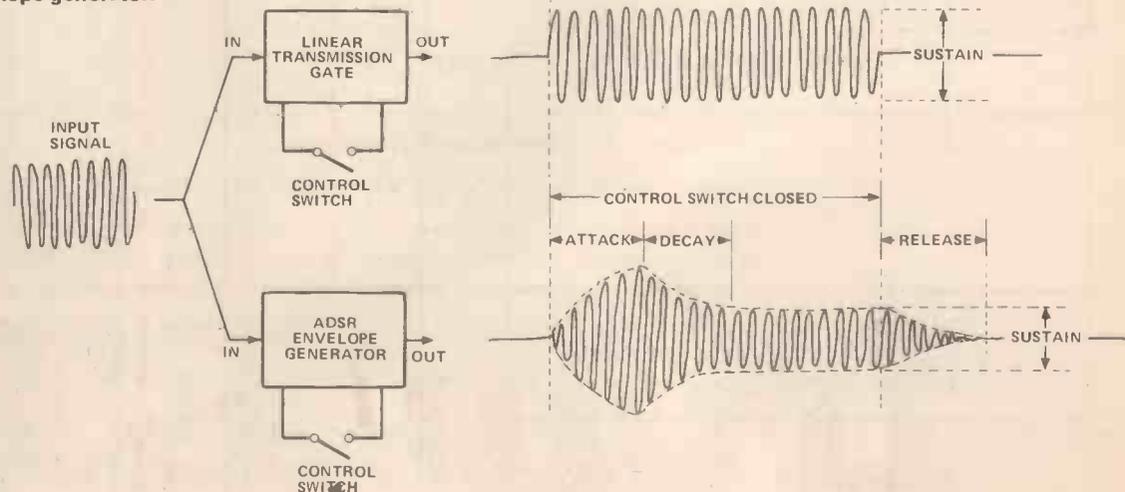

ADSR generator shown with the top removed, using the case specified it looks really professional.

generator. When the control switch is closed, the amplitude of the output signal first rises from zero at a controlled 'Attack' rate to a peak value, at which point it 'Decays' at a controlled rate until it reaches a controlled 'Sustain' amplitude, which it then maintains for the

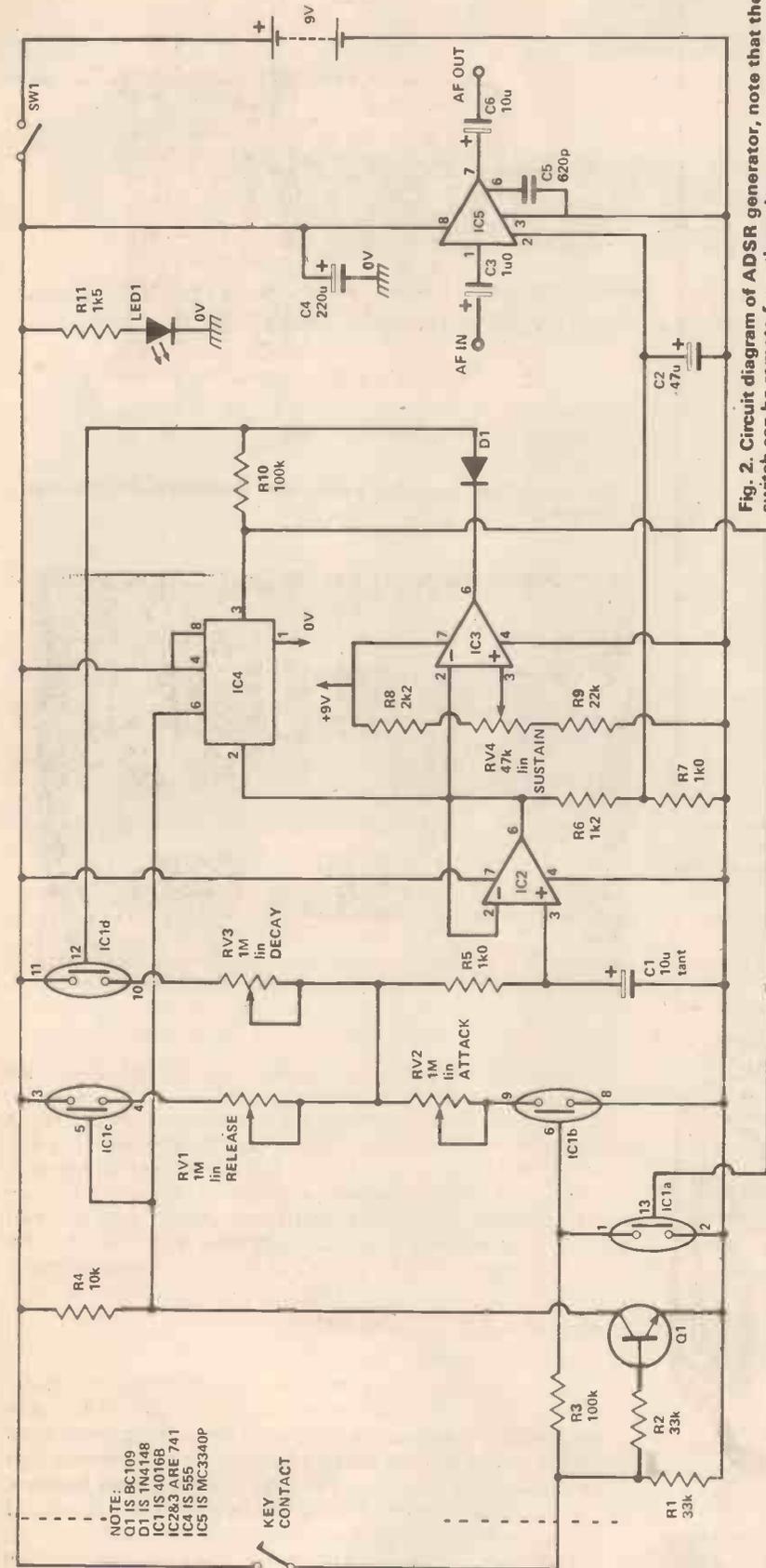


Fig. 2. Circuit diagram of ADSR generator, note that the contact switch can be remote from the unit.

How It Works

The audio signal to be controlled passes through IC5 which attenuates it according to the control voltage on pin 2. This voltage is generated across C1 and fed via voltage follower IC1b, potential divider R6 and R7 and capacitor C2 to the control pin where a voltage of about four volts causes a large attenuation so that no signal appears at the output and a lower voltage about one and a half volts lets the signal pass.

To produce a sound envelope, the control voltage must be somewhere between these two extreme levels and this is achieved by connecting discharging and charging resistors to C1. So that different sound envelopes can be produced, these are made variable and comprise RV1, 2, 3. R5 prevents excessive current flow through the transmission gates of IC1.

When the key contacts are open Q1 is off producing a high voltage (about nine volts) and the control input of transmission gate IC1c. This turns on the gate and RV1 is connected to nine volts via the few hundred ohms resistance of IC1c providing a charging path for C1. IC1b is off and very high resistance of several millions of ohms exists between its input and output. IC1d is also off as the output of IC4 is at a low level.

As the key contacts are closed, IC1c will turn off and IC1b will turn on causing the charge on C1 to leak away via R5, RV2 and IC1b. When the voltage across C1 reaches one third of the supply voltage, the output of IC4 will go high turning on IC1a which turns off IC1b and removes the discharge path. Also, IC1d will turn on and C1 will charge via R5, RV3 and IC1d. The voltage across C1 will

continue to rise until it reaches a level set by RV4. The output of IC3 will go low turning off IC1d causing C1 to become disconnected from any charge or discharge path. The voltage will remain relatively constant thus sustaining whatever level of sound output has been achieved.

In practice the voltage across C1 will drop slightly owing to the leakage of C1 and the input current drawn by IC2. However, these effects are negligible so long as a tantalum capacitor is used for C1.

As the key contacts open, IC1c will turn on. The voltage across C1 will rise and the sound will fade to silence. The output of IC4 will go low again turning off IC1a, b, d, and preparing the system for the next key closure.

Parts List

RESISTORS (All 1/4W, 5%)

R1,2	33k
R3,10	100k
R4	10k
R5,7	1k0
R6	1k2
R8	2k2
R9	22k
R11	1k5

POTENTIOMETERS

RV1,2,3	1M0 Lin
RV4	47k lin

CAPACITORS

C1	10u 16 V Tantalum
C2	47u 16 V Electrolytic
C3	1u 16 V Electrolytic
C4	220u 16 V Electrolytic
C5	620p Polystyrene
C6	10u 16 V Electrolytic

SEMICONDUCTORS

Q1	BC109
D1	IN4148
IC1	4016B
IC2,3	741
IC4	555
IC5	MC3340P
LED 1	TIL220
S1	Sub-min Toggle (on-off)

Case used on prototype is available from Maplin, Type B1. 5 pin. DIN socket (see text).

Approximate cost: £5.00

Buylines

All of the components in the ADSR circuit are commonly used types, and should be available from most suppliers that advertise in this magazine.


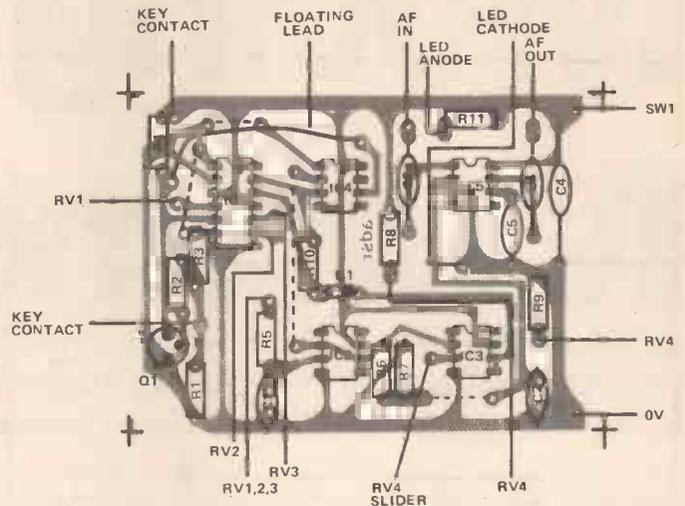


Fig. 3. PCB component overlay, note orientation of polarised components.

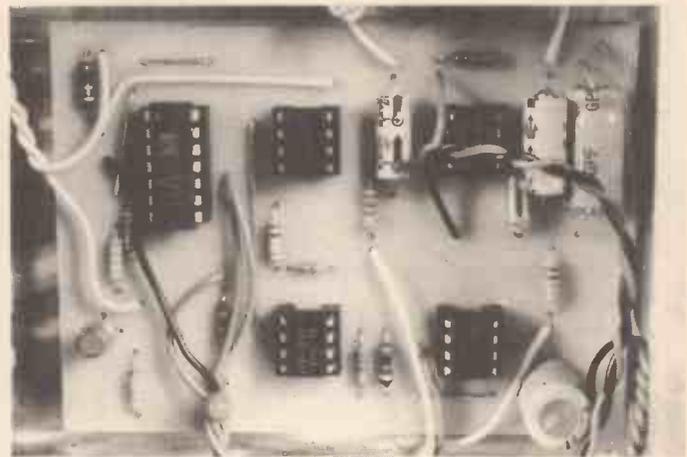

operator, and the resulting output signals can readily be made to sound natural and interesting.

The complete ADSR instrument is intended for use in conjunction with an input signal source (the April '79 HE White Noise Unit, which can also act as an oscillator, is ideal), and an output power amplifier. The instrument can be activated via either a single switch, or via a bank of parallel-connected keyboard switches, which can also be used to control the frequency of the unit's input signal.

CONSTRUCTION

All of the ADSR circuit components other than the pots, switch, and LED, are mounted on a single PCB. Take care when wiring up the PCB to observe the polarities of all semiconductor devices and electrolytic capacitors. On our prototype unit we mounted the PCB and battery, etc., in a metal case measuring approximately 6 x 4 x 2 inches. Interwiring of the PCB and controls, etc., should present no problems. The input, output, and control switch are coupled to our prototype circuit via a 5 pin DIN socket, but alternative connection methods can be used if preferred.

HE

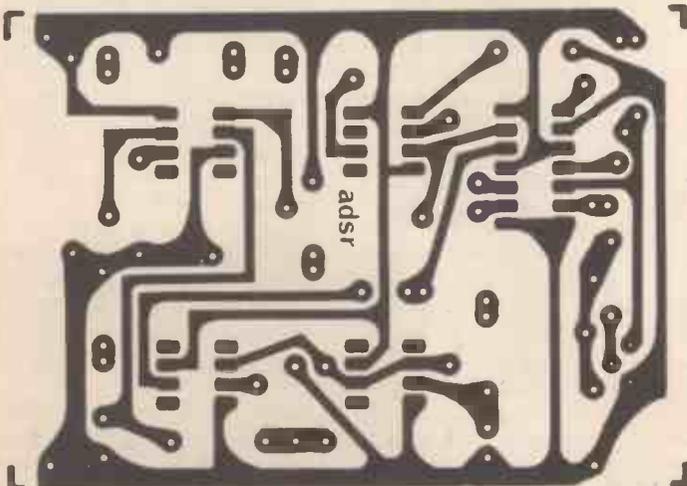


Fig. 4. PCB foil pattern for ADSR generator.

duration of the switch closure. When the switch is eventually opened again, the output signal amplitude falls to zero at a controlled 'Release' rate. The Attack, Decay, Sustain, and Release dimensions of the output sound envelope are all under the full control of the

Moving Coil Multimeters

Moving coil meters are very versatile instruments. Ray Marston explains how they work and how to use them to measure voltage, current and resistance and how to convert them into multimeters.

MOVING COIL or D'Arsonval meters are the most basic and versatile measuring instruments in any electronics laboratory. Essentially, they are sensitive but relatively inexpensive current-measuring electro-mechanical devices that give a visual analogue readout of the magnitude of the current being measured. Individual moving coil meters are designed to measure only single ranges of DC current, but can easily be persuaded to measure a wide range of AC or DC voltages or currents by connecting them to suitable rectifiers, voltage multiplier resistors, or shunts. They can readily be adapted for use as resistance-measuring meters and form the basis of almost all good quality analogue multimeters.

In the next few pages we describe how moving-coil meters work and how to convert any existing meter to read alternative ranges by designing your own shunt and multiplier networks, etc. We also show the full circuit diagrams of two famous high-quality multimeters, the Avo 8 and the Avomitor Mk 5.

HOW MOVING COIL METERS WORK

The operating principle of a moving coil meter is quite simple. The meter incorporates a coil of fine wire wound on an aluminium former or bobbin that is supported by delicate bearings, so that the assembly can move under almost frictionless conditions (hence the title 'moving-coil'). Also mounted on the assembly is a pointer, which projects over a fixed and graduated scale enabling any degree of movement of the coil to be read off the scale. The coil is mounted within the powerful magnetic field of a fixed permanent magnet (see Fig. 1). Current can be fed to the coil via a pair of contra-wound coil springs, which are fitted at opposite ends of the bobbin in such a manner that their tensions balance out when the pointer is in the 'zero' position.

When current is passed through the coil a magnetic field is set up which interacts with that of the permanent magnet and applies a torque to the coil assembly. This rotates until a position is taken up in which the torque is balanced by the force of the two coil springs. The degree of rotation of the assembly, which includes the pointer, is directly proportional to the amount of current passed through the coil. Thus, the scale can be directly and linearly calibrated in terms of current.

All moving coil meters, irrespective of the manner in which their scales are calibrated, work on the basic principle outlined above, and inherently read only mean

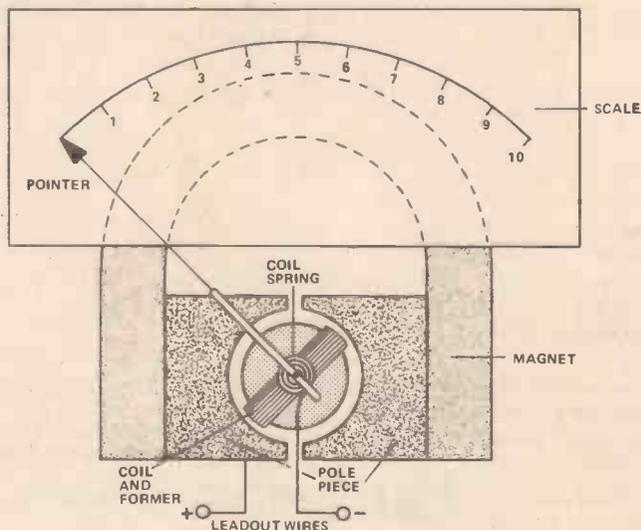


Fig. 1. Basic moving coil meter movement.

DC currents: they do not respond to AC. Most meters are designed with their 'zero' mark on the extreme left of their scales and thus respond only to positive DC currents. A few meters have their zero mark at the centre of their scale and can respond to both positive and negative DC currents. Virtually all moving coil meters are provided with a limited means of external zero adjustment, usually via a small screw-headed device fitted at the front of the meter.

The vast majority of moving coil meters have a basic sensitivity or full-scale current indicating capacity of between a few tens of μA and a few mA. The current indicating range of a meter can be increased above the basic value by wiring the basic meter in parallel with a low-value 'shunt' resistor, as shown in Fig. 2, so that the basic meter reads full-scale when the total current of the circuit is at the prescribed high value.

Alternatively, a meter can be made to give voltage readings by wiring the basic meter in series with a high value 'multiplier' resistor, as shown in Fig. 3, so that the basic meter reads full-scale when the voltage across the complete circuit is at the prescribed value. Similarly, the meter can be made to read AC quantities by feeding the quantities to the basic meter via a suitable rectifier or AC/DC converter network and can be made to read resistance values by connecting the test resistors to the basic meter via a suitable voltage source.

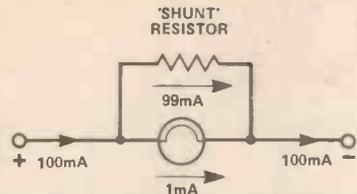


Fig. 2. The current indicating range of a basic meter can be increased by connecting it in parallel with a 'shunt' resistor.

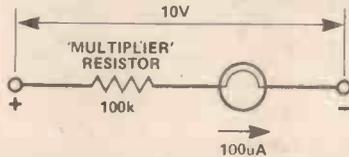


Fig. 3. A basic meter can be made to indicate voltage by wiring it in series with a 'multiplier' resistor.

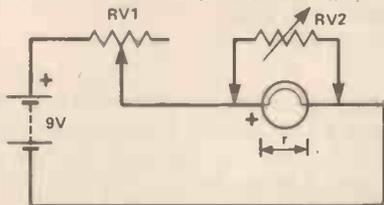


Fig. 4. Set-up for determining the internal resistance, r , of a moving coil meter. Method of use is explained in the text.

COIL SUSPENSION METHODS

All moving coil meters have their movements or coil units suspended on some kind of bearing assembly. Usually the bearings are of the jewelled type. Inevitably, a certain amount of friction occurs between the coil pivots and the bearings, and these meters consequently suffer from a characteristic that is known (in the trade) as 'stiction'.

At best, stiction causes a rising test current to give an indication that is slightly below the true value and a falling test current to give an indication that is slightly above the true value. Whenever an accurate measurement is to be made, these meters should be gently tapped with the finger to overcome stiction and give a true measurement. At its worst, stiction can cause a movement to jam at various points when it is fed with slowly varying currents.

A few moving coil meters have their movements suspended on a taut-band or rod, rather than on bearings. These taut-bands act rather like a torsion bar, with the bar or taut-band doubling as both a frictionless bearing and as a pair of contra-wound coil springs: current is fed to the coil via light-weight fly-leads. Meters of this type are known as moving-coil taut-band suspension meters. They do not suffer from stiction problems, but tend to be rather more expensive than conventional meters.

METER ACCURACY

One of the most important but least understood characteristics of a meter is its accuracy. The accuracy of a moving coil meter is invariably expressed in terms of percentage and may refer to the percentage error inherent in the absolute reading over the 'effective range' of the instrument, or to the 'percentage of

full-scale value' error in an absolute reading over the 'effective range' of the instrument. The 'effective range' is defined as 'from 0.1 of scale range to full-scale value' in DC-indicating meters, and 'from 0.25 of scale range to full-scale value' in AC-indicating meters.

The most misunderstood 'accuracy' term is that relating to 'percentage of full-scale value'. A typical accuracy (possible error) value may be 2%. Take the case of a meter that is calibrated to give a full-scale reading of 100 volts. At full-scale the possible error of indication is 2%, or 2 V, so the true full-scale voltage is in the range 98 V to 102 V. At half-scale the possible error is still 2 V (= 2% of full-scale), so the true value of an indicated 50 volts is 48 V to 52 V and the absolute accuracy is 4%. At quarter-scale the true value of an indicated 25 volts is 23 V to 28 V and the absolute accuracy is 8%. Finally, at one-tenth of full-scale the true value of an indicated 10 volts is 8 V to 12 V and the absolute accuracy is a mere 20%.

The accuracy of most meters is specified in the 'percentage of full-scale value' term and the possible accuracy here is generally restricted by the stiction problem. High-quality jewelled-bearing meters, such as the Avo 8, give typical accuracies in the range 1% to 2% of full-scale. Poorer quality meters have typical accuracies in the range 3% to 5% of full-scale. Meters with taut-band suspension do not suffer from the stiction problem and typically give accuracies of 1% absolute plus or minus 1% of full-scale.

METER SENSITIVITY

The most important characteristic of a meter is its basic full-scale sensitivity or current-indicating capacity. This parameter may be expressed in either of two ways, either in direct terms of its FSD (full-scale deflection) current, or in terms of k/volt (kilohms per volt). The latter figure is of use when converting a milli- or micro-ammeter into a voltmeter and can be deduced by taking the reciprocal of the FSD current figure in milliamps. Thus, a 1 mA FSD meter has a sensitivity of 1 k/volt and a 100 μA FSD meter has a sensitivity of 10 k/volt .

The basic sensitivity of a meter is usually marked on its scale; if not, it can be determined by comparison with a standard meter. Sometimes it's useful to know the voltage that is required to give fsd on the basic meter and this value can be calculated by multiplying the meter fsd current by the meter internal (coil) resistance. The fsd voltage is commonly in the range 50 mV to 150 mV.

METER INTERNAL RESISTANCE

The coil of a meter has a resistance that may vary from a few ohms in low-sensitivity meters to a few thousand ohms in high-sensitivity meters. It is necessary to know the value of this resistance if the indicating ranges of a basic meter are to be changed. In some cases, the basic meter resistance value may be marked on the meter scale; if not, it can be determined by the method described below. Note that **NO ATTEMPT SHOULD EVER BE MADE TO DIRECTLY MEASURE THE COIL RESISTANCE OF A METER WITH AN OHMMETER**, since such an attempt may result in severe damage to the meter movement.

Fig. 4 shows the basic set-up for measuring the meter coil resistance. RV1 must have a value that is between

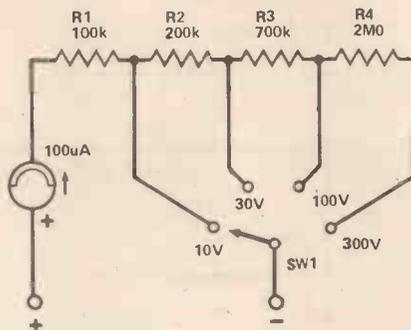
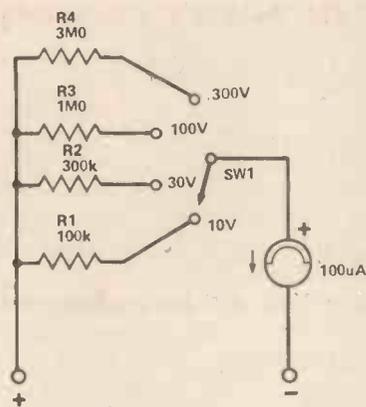


Fig. 5. Two alternative ways of switching multipliers on a 4-range DC voltmeter. Method (a) is sometimes used in low-cost multimeters. Method (b) is used in good-quality multimeters.

10 and 25 times the k/volt value of the meter. Initially, RV1 is set to maximum value, so that the meter draws less than full-scale current when it is first connected. Once the meter is connected, RV1 is adjusted so that the meter reads exactly fsd. A shunt resistor, RV2 (usually a decade resistance box), is then placed across the meter and adjusted until the meter reading falls to exactly half of the fsd value, at which point half of the total circuit current is clearly passing through the meter and half through the shunt, and RV2 has a value equal to the internal resistance of the meter. The measurement can be verified by briefly removing the shunt, at which point the meter indication should return to fsd.

The internal resistance value of the meter can then be established by noting or measuring the value of RV2. Note that RV1 should have a final in-circuit value that is at least 50 times greater than the measured internal resistance of the meter. If not, use a battery with a higher voltage than shown in Fig. 4, and increase RV1 accordingly, as excessive errors may otherwise enter the calibration due to non-constant currents through RV1.

An alternative method of determining the meter resistance using the same set-up as shown in Fig. 4 is to simply connect a precision resistor of known value across the meter in the RV2 position and note the change in meter reading that takes place. The internal meter resistance, r , can then be calculated from:

$$r = R_p(i - I) / I$$

where R_p is the value of the precision resistor in parallel with the meter, i is the fsd rating of the meter, and I is the new reading of the meter.

DC VOLTMETERS

A moving coil (milli- or micro-) ammeter can be made to measure voltages by adding a suitable resistor in series with the meter, as already shown in Fig. 3, the resistor being referred to as a 'voltage multiplier' resistor.

If a meter with a sensitivity of 100 μ A fsd is to be used to measure 10 volts fsd, a multiplier resistor must be found of such a value that, when 10 volts are connected across the 'volt' terminals, a current of 100 μ A must flow. If, for the moment, the internal meter

resistance is ignored, it can be seen from Ohm's Law that the resistance is E/i , where E is the voltage and i is the fsd current of the meter. In this case the answer works out at 100 k, which is ten times the k/volt figure of the 100 μ A meter (= 10 k/volt).

If the voltmeter was required to measure 100 volts fsd, the multiplier would have a value of 1M Ω , or 100×10 k/volt. It can be seen, then, that all that has to be done (ignoring the internal meter resistance) to convert a basic moving coil meter to a voltmeter is to multiply the k/volt figure of the meter by the required fsd voltage in order to arrive at the correct value of series multiplier resistance.

When the internal meter resistance is to be taken into account the formula becomes:

$$R_m = (E/i) - r,$$

where R_m is the multiplier resistance and r is the internal meter resistance.

To take two examples in the use of this simple formula, assume that a meter with a sensitivity of 100 μ A fsd (10 k/volt) and an internal resistance of 1 k Ω is to be used as a voltmeter measuring (a) 3 volts and (b) 30 volts fsd. The following results are obtained:

- (a) $R_m = 30 \text{ k} - 1 \text{ k} = 29 \text{ k}$.
- (b) $R_m = 300 \text{ k} - 1 \text{ k} = 299 \text{ k}$.

Note in case (a) that the exclusion of r from the calculation would have resulted in an error of 3.3% in the final results, but in the case of (b) an error of only 0.33%

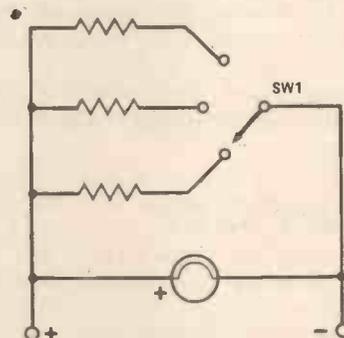


Fig. 6. How NOT to arrange shunt switching on a multi-range current meter. This method is often used in amateur-designed meters: the meter may be destroyed if the switch develops high contact resistance during a measurement.

EXTENDING CURRENT RANGES

To extend the current range of a basic meter a 'shunt' resistor is added across (in parallel with) the basic movement, as already shown in Fig. 2. A known fraction of the current under test passes through the shunt and the remainder passes through the meter, which can thus be calibrated in terms of the total current passed through the circuit. The ratio of the shunt and meter currents is determined by the relative values of the meter internal resistance and the shunt resistance.

The formula giving the required value of a shunt resistor, R_s , is:

$$R_s = n - 1 / r$$

where r is the meter internal resistance and n is the current multiplication factor (the number of times by which the required range is greater than the basic range). Thus, to convert a 1 mA meter to read 50 mA fsd, $n = 50$, and the term $n - 1 = 49$. Assuming the meter internal resistance to be 100 ohms, the shunt will be $100 / 49 = 2.04$ ohms.

An alternative formula, which gives the same result, is:

$$R_s = \frac{I_m \times r}{I_t - I_m}$$

where I_m is the fsd current of the meter, and I_t is the total fsd current of the circuit. Note that this formula finally resolves down to a simple V/I form, in which V is the fsd voltage of the basic meter, and I is the fsd shunt current.

Individual shunt resistors should either be permanently wired across the basic meter, or should be connected to the meter via low-resistance screw terminals. They should **NEVER** be switched into position using the circuit shown in Fig. 6, which is often used in

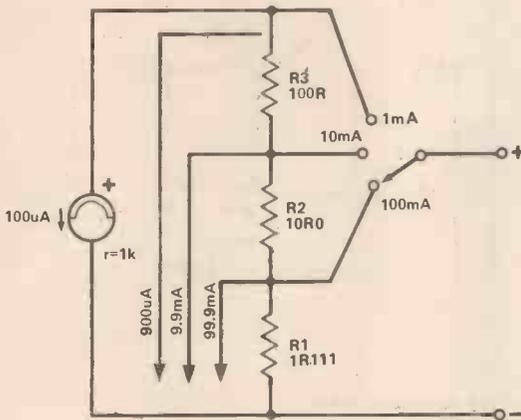


Fig. 7. Worked example of a 3-range universal shunt circuit, complete with range switch connections.

would have resulted from excluding r . It can thus be seen that the internal meter resistance can be ignored in cases other than when low voltages are to be measured.

When a moving coil 'voltmeter' is used it inevitably draws current from the circuit that is being measured, thus altering circuit conditions. The low current taken by the meter, the smaller are the influences that it has on the circuit under test. General-purpose meters that are used for measuring voltages in modern electronics circuits should ideally have sensitivities of at least 10 k/volt, and preferably of 20 k/volt or better.

MULTI-RANGE VOLTMETERS

If several voltage ranges are to be incorporated in a moving coil meter, two methods of range switching are possible. These are shown in Figs. 5a and 5b. To illustrate with an example, assume that a 10 k/volt meter is to give the following ranges: (a) 10 volts, (b) 30 volts, (c) 100 volts, and (d) 300 volts.

The multipliers required (r being ignored in all cases) are (a) 100 k, (b) 300 k, (c) 1MO, and (d) 3MO.

In the case of Fig. 5a the values of R_1 to R_4 are quite straightforward and are as above. In the case of Fig. 5b, however, things are not quite as simple. R_1 measures the 10 V range, and is 100 k. But the 30 V range is made up of R_1 and R_2 in series, so R_2 is $300 \text{ k} - 100 \text{ k} = 200 \text{ k}$. Likewise, (c) is made up of R_1 , R_2 and R_3 in series so $R_3 = 700 \text{ k}$. By the same token, $R_4 = 2\text{MO}$.

The Fig. 5b method of range switching is widely used in good-quality multimeters and sometimes used in low-cost meters.

Resistors used for voltage multipliers should be high accuracy (1% or better) types, with low temperature coefficients. Wire wound or metal film types are best; carbon film resistors are also useable, but metal-oxide types are not, due to their poor temperature coefficients. In high-voltage multipliers, check that the voltage ratings of the multiplier resistors are not exceeded: if necessary, make the resistance up with several resistors in series, so that the applied voltage is distributed across the resistor chain.

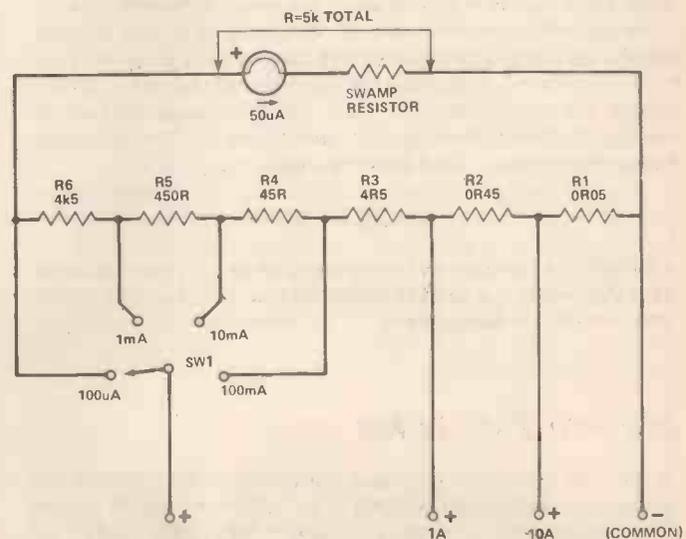


Fig. 8. Practical example of a swamp resistor applied to a 6-range current meter. The 100 uA to 100 mA ranges are switch selected. The 1 A and 10 A ranges are selected via screw terminals.

Fsd voltage sensitivity varies from 250 mV on the 100 uA range to 500 mV on the 10 A range.

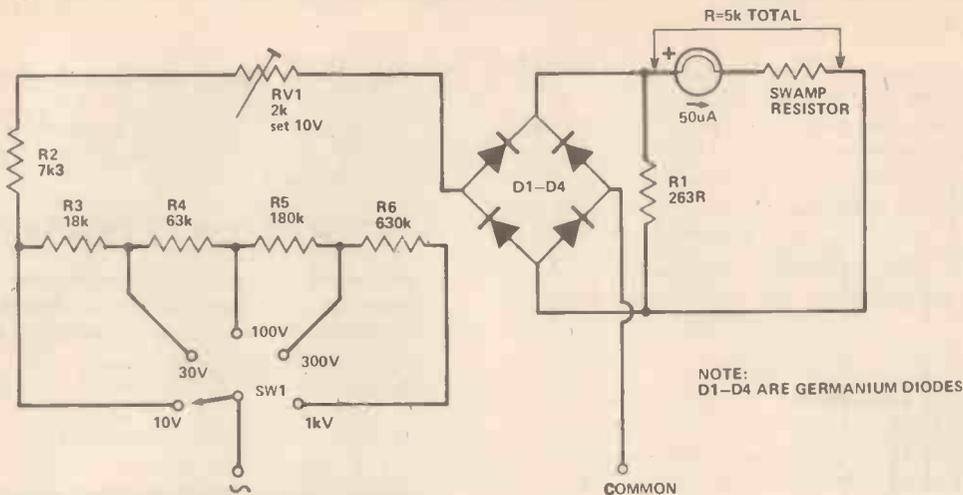


Fig. 9. Practical example of an AC voltmeter covering 10 V to 1 kV in 5 ranges. The meter sensitivity is reduced to 1 k/volt via R1.

amateur-designed multimeters. The switch here is effectively in series with the shunt resistors and inevitably has an unpredictable amount of contact resistance that varies with time and wear, and consequently greatly effects the meter calibration. If the switch contacts go open circuit during a measurement, due to oxidation or a mechanical fault, all of the test current will go through the basic meter, causing possible destruction of the movement.

If a moving coil meter is to be used as a switched multi-range current meter, its circuitry should always be designed around a so-called 'universal' current shunt network.

THE UNIVERSAL SHUNT CIRCUIT

Figure 7 shows the practical circuit of a 3-range (1 mA, 10 mA, and 100 mA) universal shunt, complete with its switch connections. The range resistors are all wired in series and are permanently connected across the meter. The range switch is external to the shunt network, range changing being achieved by tapping into the shunt chain, so the switch contact resistance has no effect on the calibration accuracy of the meter on any of its ranges. Note that, since the basic meter is shunted on all ranges, the lowest effective current range of the circuit is greater than that of the basic meter.

The procedure for designing a universal shunt is very simple and is best illustrated by the practical example of Fig. 7, in which the basic meter has a sensitivity of 100 µA fsd, and an internal resistance of 1 k. The first step in the design is to determine the TOTAL resistance of the R1-R21-R3 chain, which determines the fsd value of the circuit on its LOWEST (1 mA) current range. The total resistance of the chain is given by:

$$R_t = \frac{r}{n-1}$$

where r is the internal resistance of the meter and n is the current multiplication factor. In the case of our example the answer works out at $1000/9 = 111.11$ ohms.

The next step is to calculate the TOTAL value of the HIGHEST current shunt, which in this case is R1 and controls the 100 mA range. The formula for determining the total value of this and all other 'universal' shunts is:

$$R_{st} = r + R_t/n$$

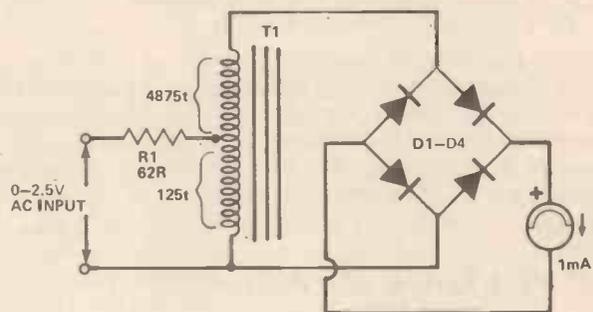


Fig. 10. Example of a low-value (0-2.3 V) AC voltmeter using a step-up autotransformer to give improved meter linearity. This circuit is used in the Avo 8 Mk 2.

and in this case gives a value of $1111.11/1000 = 1.1111$ ohms for R1.

The same formula is used to find the values of all other shunts, and on the 10 mA range gives 11.111 ohms, but since this shunt comprises R1 and R2 in series, the value of $R2 = 11.111 - 1.1111$ ohms = 10 ohms.

Finally, the total shunt value for the 1 mA range is 111.11 ohms, so the value of $R3 = 100$ ohms. The design procedure is then complete.

As a point of general interest it may be noted that, since the total resistance in series with the meter varies with each range of a universal shunt, the fsd voltage sensitivity of the circuit also depends on the current range selected. In our example the fsd sensitivity is 100 mV on the 1 mA range, 110 mV on the 10 mA range, and 111.1 mV on the 100 mA range.

A final point of interest is that it is a common practice in commercial instruments to make all current ranges above 1 amp accessible via screw terminals, rather than via a range switch, thus eliminating the need to use switches with very high current ratings. The terminals are wired directly to the range resistors on the universal shunt.

THE SWAMP RESISTOR

It is a common practice in multi-range commercial current meters to wire a so-called 'swamp' resistor in series with the basic meter, as shown in Fig. 8.c This

Moving Coil Multimeters

resistor has two purposes. On the one hand, it can be used to raise the total series resistance of the meter circuit to a level that precisely matches a previously designed universal shunt network. On the other hand, it can be used to compensate the temperature coefficient of the meter coil, and so give improved accuracy over a wide temperature range. The use of a swamp inevitably increases the fsd voltage value of the meter circuit.

MAKING CURRENT SHUNT RESISTORS

Shunt resistors with values greater than a few ohms can be made by connecting wire wound, metal film or carbon film resistors in parallel to give the desired value: the final resistor should have an accuracy of 1% or better.

Shunt resistors with values below a few ohms can be made up from Eureka or Constantan wire of suitable gauge, cut to suitable length. Most electronics reference books give data tables relating to these wires.

The precise length of wire for a shunt can be found by passing the full test current through the wire via a standard (precision) current meter, and then connecting the test meter across the wire via flexible leads and moving the leads along the wire until the required fsd is obtained, at which point the wire length is correct. One centimetre should be added to each end of the wire, to allow for soldering the shunt to suitable former terminals.

AC VOLTAGE MEASUREMENT

Moving coil meters respond to DC current only. Thus, to measure AC voltage it is necessary to rectify the signal and feed it to the meter via a suitable voltage multiplier resistor. A common means of rectification is via a bridge rectifier, as shown in Fig. 9. Special instrument rectifiers are available for the job, but four ordinary germanium rectifiers connected as a bridge will perform just as well.

All rectifiers have a non-linear action and are most non-linear near the 'zero' end of their characteristics curve. For this reason the rectifiers are usually operated from 0 to 1 mA in moving coil AC voltmeters, rather than from (say) 0 to 50 μ A. Commercial meters thus have a far lower sensitivity on AC voltage ranges than they have on DC voltage ranges.

AC voltmeters are normally calibrated to read RMS values of a sine wave input. In this case the meter passes a current of 1.11 times the pure DC current. The 'multiplier' formula for AC voltage thus becomes:

$$R_m = E/i \times 1.11$$

where i is the pure DC fsd current in amps, remembering that this is normally of the order of 1 mA.

It is important to note on ranges below about 10 volts fsd that the scale readings become distinctly non-linear, particularly at their low ends. Fsd ranges below 2.5 V are rarely provided on commercial instruments, because of the non-linearity problem. It is necessary on low voltage ranges to allow for the rectifier resistance as well as the internal meter resistance when constructing voltage multipliers.

Some high-quality commercial multimeters, such as the Avo 8, use a step-up autotransformer to increase the voltage that is actually fed to the rectifier circuit from a

low-voltage source, as shown in Fig. 10 and thus overcome the non-linearity problem mentioned above. The major disadvantage of this system is that the transformer places severe limitations on the usable frequency range of the instrument.

AC CURRENT MEASUREMENT

Alternating current is a difficult quantity to measure on a moving coil meter and the majority of commercial multimeters make no provision for such measurements. One exception to this is the Avo 8, which provides AC current ranges of 100 mA, 1 A, 2.5 A, and 10 A. The technique used on the Avo 8 is to feed the current through the windings of a step-up autotransformer; the meter and rectifier are connected to the output of the transformer, which steps up the voltage but reduces the current to them and thus overcomes non-linearity problems. The set-up is similar to that of the Fig. 10 circuit.

OHMMETERS: THE SERIES-CONNECTED TYPE

Moving coil meters can easily be converted to read resistance. Two basic types of ohmmeter are in common use and are known as the series-connected and the parallel-connected types.

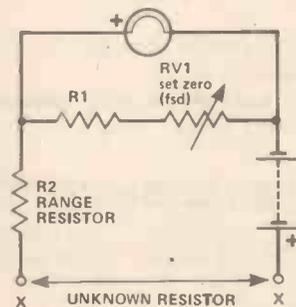


Fig. 11a. Basic circuit of a series-connected ohmmeter. R2 determines the centre-scale resistance value of the meter.

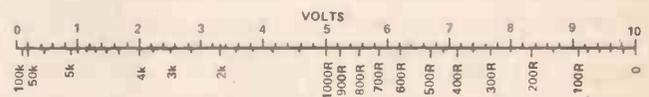


Fig. 11b. Resistance range calibration against a linear volts scale.

The most popular version of the series-connected ohmmeter is shown in Fig. 11a. This circuit has a set-zero variable resistor network wired in parallel with the meter and has a 'range' resistor wired in series with the combination: the value of this resistor is made the same as the required centre-scale resistance reading of the meter. The 'unknown' resistor is wired in series with the meter network, hence the name 'series-connected' ohmmeter.

In use, the X terminals of this ohmmeter are first shorted together and the variable resistor is adjusted to bring the meter pointer to fsd. The unknown resistor is then connected between the X terminals and the new current reading noted. The value of the unknown resistor can then be calculated from:

$$R_x = R(i/i - 1)$$

where i is the fsd current on the basic meter and I is its new current reading.

The meter scale can either be calibrated against a graph made on the basis of a few dozen sets of calculations based on the above formula (see Fig. 11b), or can be directly calibrated against a large number of accurately known resistors.

A major attraction of this circuit is that (a) its calibration accuracy is not influenced by minor changes in battery voltage and (b) once calibrated its scale values can be increased by (say) a factor of ten by simply increasing the value of range resistor R by a factor of ten and either increasing the battery voltage or the effective meter sensitivity by the same amount.

OHMMETERS: THE PARALLEL-CONNECTED TYPE

The parallel- (or shunt-) connected ohmmeter is used for measuring low and very-low values of resistance. The basic circuit is shown in Fig. 12 and the method of use is to first close $SW1$ and adjust the meter to fsd with the X terminals *open-circuit*. The unknown resistor is then connected across the X terminals and the new reading noted. The value of the unknown resistance can be calculated from:

$$R_x = r_i i / I - r$$

where r is the internal resistance of the meter, i is the fsd current of the basic meter, and I is the new current indication.

Note in this circuit that high values of resistance give a high reading on the meter scale, and low values give a low reading: this is the reverse of the reading style given by the series-connected type of ohmmeter.

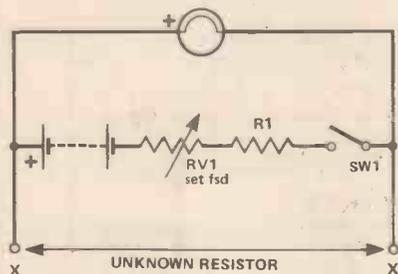


Fig. 12. The parallel-connected type of ohmmeter is used to measure low and very-low values of resistance.

METER OVERLOAD PROTECTION

Moving coil meters are delicate instruments and are easily damaged by overload currents exceeding their fsd values by 50% or more. Ideally, they should be provided with some means of overload protection. A limited degree of protection can be gained by wiring a pair of germanium diodes across the basic movement as shown in Fig. 13. The diodes are non-conductive until the voltage across the meter rises to a couple of hundred millivolts, at which level they start to conduct and shunt further excess current away from the movement.

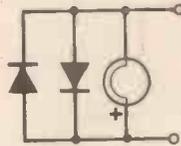


Fig. 13. A moving coil meter can be given a limited degree of overload protection by connecting two germanium diodes as shown.

COMMERCIAL MULTIMETERS: THE AVOMINOR MK 5

A very large range of commercial multimeters are available. They vary from cheap and nasty little things with only a few ranges, to expensive and superbly engineered instruments with thirty or more ranges.

One of the best known and most popular 'middle-of-the-road' multimeters in the U.K. is the Avomator. Figure 14 shows the full circuit diagram of the Mk 5 version of this instrument, and is reproduced by kind permission of Avo Ltd. The instrument has a total of 19 ranges.

The basic movement sensitivity of this multimeter is 60 μ A fsd, but is reduced to 100 μ A by the RV1 and R14 to R18 universal shunt that is permanently wired across the meter. The shunt provides DC current ranges of 100 μ A to 1 amp fsd. No AC current ranges are provided.

Some high quality multimeters use a mechanical or electro-mechanical trip to give overload protection. In the Avo 8, for example, all inputs to the multi-meter terminals are passed to the meter circuitry via a set of contacts that are coupled to a sensitive mechanical trip, which activates and breaks the contacts if the meter pointer exerts appreciable pressure against the scale end stops. This device gives good protection not just to the meter movement, but to all of the meter circuitry as well.

The fsd voltage sensitivity of the Avomator meter movement is set at 100 mV by swamp resistor R19, thus enabling the 100 μ A current range to also function as a 100 mV DC voltage range. Other DC voltage ranges, from 2.5 V to 1000 V, are provided via the R1 to R19 multiplier chain. This same multiplier chain is also used to provide AC voltage ranges from 10 V to 1000 V fsd, but in this case the meter sensitivity is reduced to 1 k/volt by connecting R12 across the meter movement.

The Avometer Mk 5 has two resistance measuring ranges, which span an effective range of 5 ohms to 2M Ω . The multimeter is not provided with overload protection.

COMMERCIAL MULTIMETERS: THE AVO 8 Mk 2

The Avo 8 is reckoned to be a 'Rolls-Royce' amongst multimeters. They are expensive instruments to buy new, but an amateur can occasionally pick up a good second hand one at a reasonable price. A likely choice here is a Mk 2, and the circuit diagram of this particular specimen is reproduced in Fig. 15, by kind permission of Avo Limited.

The Mk 2 has some 31 measurement ranges, running from 50 μ A to 10 amps and 2.5 V to 2500 V on DC, and from 100 mA to 10 amps and 2.5 V to 2500 V on AC, as well as three basic and two special resistance ranges. Sensitivity is 20 k/volt on DC and 1 k/volt on

Moving Coil Multimeters

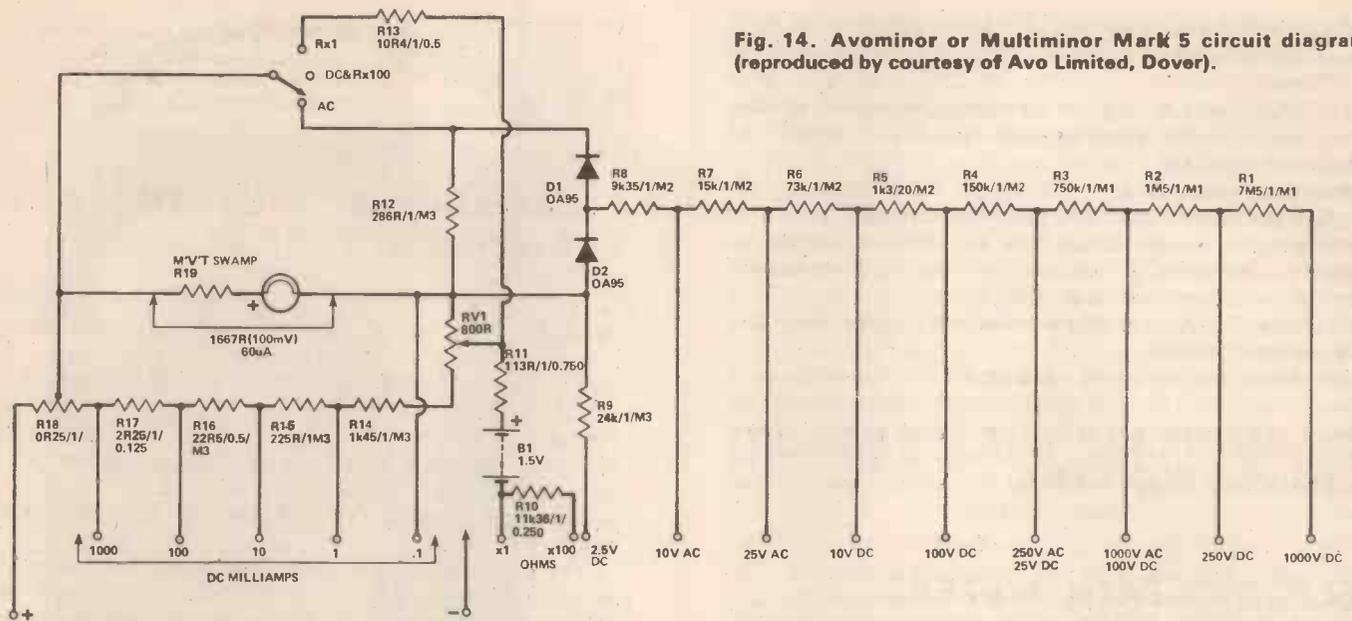


Fig. 14. Avomator or Multiminor Mark 5 circuit diagram (reproduced by courtesy of Avo Limited, Dover).

AC voltage ranges. The instrument is provided with a mechanical cut-out that gives excellent overload protection, as already described.

USING A MULTIMETER

A multimeter is a fairly easy instrument to use if you stick to the following basic rules;

- (1). Most moving coil multimeters are designed to operate accurately only when their faces are in one specific physical orientation, usually horizontal. If you are taking an accurate measurement, never slope the meter at an angle and don't use it vertically if it's meant to be used horizontally.
- (2). When measuring an unknown current or voltage, always set the meter to its highest range and then work down through the ranges until the correct one is found.

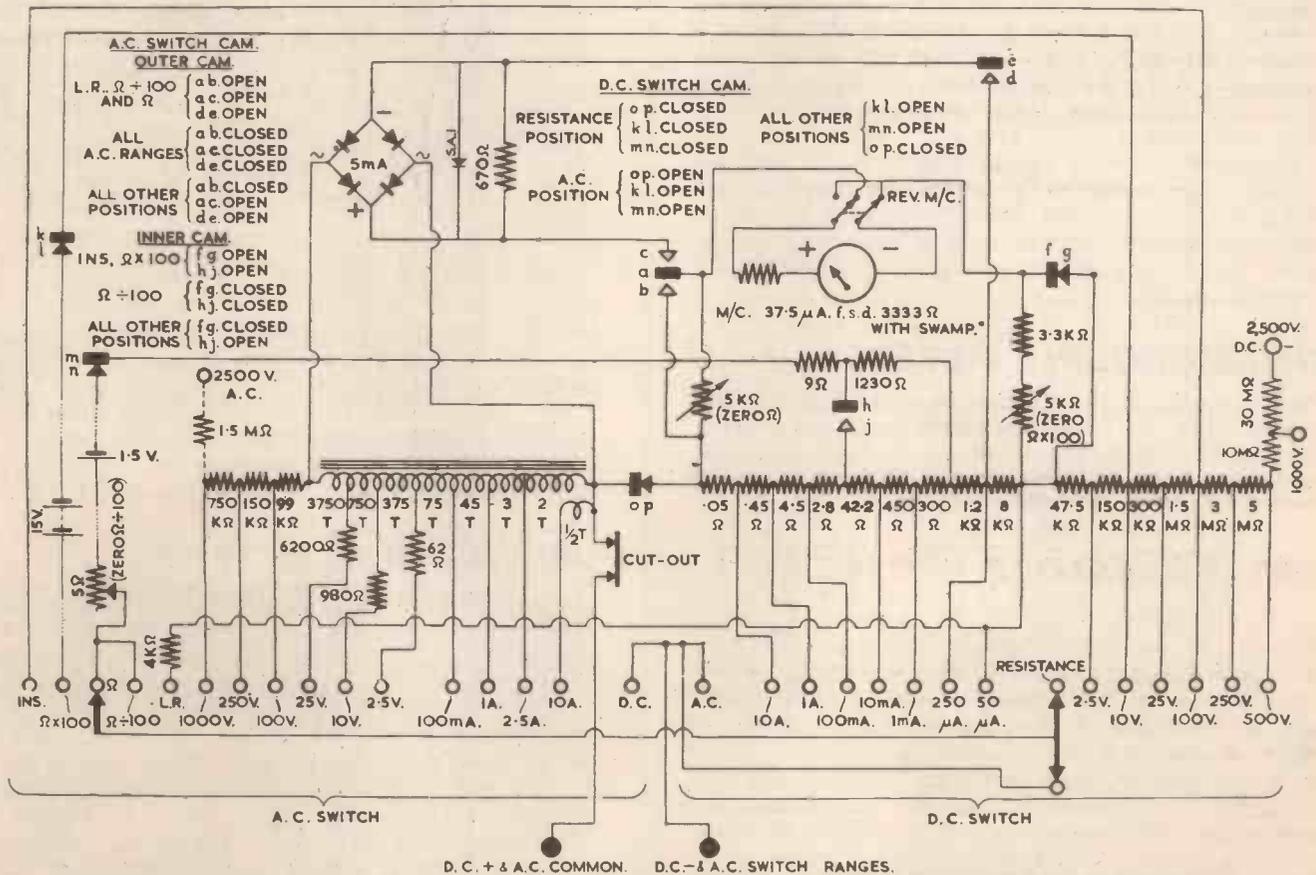


Fig. 15. Circuit diagram of the Model 8 Avometer Mk 2 (reproduced by courtesy of Avo Limited, Dover).

Moving Coil Multimeters

(3). When measuring an in-circuit voltage, always connect the meter across the voltage source, as shown in Fig. 16a.

(4). When measuring an in-circuit current, always connect the meter in series with the current source, as shown in Fig. 16b.

(5). When measuring an in-circuit resistance, always isolate the resistance from all other circuitry and then connect the meter across the resistor, as shown in Fig. 16c. Never try to measure the value of a resistance that has a voltage source applied to it.

(6). Always handle a multimeter with care. They are fragile instruments.

(7). When a multimeter is used on its voltage ranges, its input impedance ($k/\text{volt sensitivity} \times \text{voltage range}$) will shunt any resistance that it is connected to and so will reduce the apparent value of voltage developed across that resistance. Always allow for this 'disturbance' effect when taking voltage measurements.

ELECTROSTATIC METERS

In the preceding pages we have discussed only the moving coil type of analogue meter. There are, however, a number of other types of analogue readout meter that are occasionally encountered in an electronics laboratory. The three most common of these are the electrostatic meter, the thermocouple meter, and the moving iron meter.

Electrostatic meters are true voltmeters, and usually have fixed fsd sensitivities in the range 200 V to 30 kV. They are made up from one fixed and one moving set of vanes, which look and act just like a variable tuning capacitor. A pointer is fixed to the moving vane. When a voltage is applied across the vanes an electrostatic force is set up, and the moving vane rotates by an amount proportional to the force. The meter scales are non-linear and are cramped at the low end.

Electrostatic meters respond to both DC and AC voltages. They appear as capacitors to external signals and draw zero current from DC sources, and a frequency-dependent current from AC sources. They are widely used for high-voltage measurement, particularly in television work.

THERMOCOUPLE METERS

Thermocouple meters are widely used as RF voltage and power indicators at frequencies up to hundreds of MHz, and as wideband AC/DC transfer standards in electrical



The Avo 8 Mk 3.

calibration work. They consist of a thermocouple (a junction of two wires made from dissimilar metals, which generates a voltage in each wire when the junction is heated) that has one set of its wires connected to an ordinary moving coil meter and the other set taken to the outside world via a pair of terminals. When a current is fed through this second set of wires it causes the thermocouple junction to heat up, a voltage in the set of wires connected to the meter, which thus deflects by an amount proportional to the current in the second set of wires.

The major attraction of the thermocouple meter is that its deflection is proportional to the true RMS current in the second set of wires and is not influenced by the shape or frequency of the waveform. The meter can thus be used for measurement from DC to hundreds of MHz and can be used as an AC/DC transfer standard. The two major disadvantages of the thermocouple meter are that its scale follows an approximately square law and that the thermocouple is very fragile (it can be burnt out by quite small overloads).

MOVING IRON METERS

These meters are widely used as AC or DC volt or current meters in low-accuracy applications, such as in battery chargers, etc. They have a fixed coil, through which the measured current is passed, and an iron vane that is mounted on a spindle that is coupled to a pointer. When a current is passed through the coil it sets up a field which repels the vane and causes the pointer to move.

This type of meter is cheap and robust, but has a low sensitivity. It responds equally well to AC and DC, but has a non-linear scale and generally has poor accuracy. It is current operated, and thus can be used in both current and voltage indicating applications.

HE

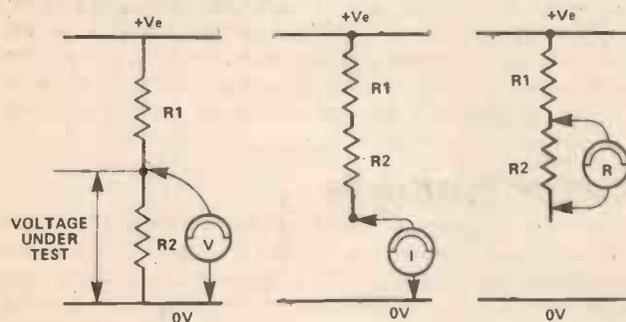


Fig. 16. Correct way to use a multimeter to measure in-circuit (a) voltage, (b) current, and (c) resistance.

Internal Resistance

Resistance is the property which makes it harder for electrons to flow — not hard to understand but what is the effect of resistance within a current generator which is actually causing those electrons to travel? K. T. Wilson examines the internal resistance in batteries.

EVER USE a battery, or a mains supply? Of course you do but do you know what voltage was present. It's not a daft question. You may have a battery labelled 9 V or a power supply labelled 12 V but that's no guarantee that these are the voltages which are given out when you start to take current from the battery or the power supply. You can find, for example, that your 9 V battery gives only 7.2 V when you connect it to a circuit that needs a fair amount of current, or that your mains supply which should be a 12 V gives only 11 V.

TWO PIECE SUPPLY

All this is caused by what is called internal resistance, which is the total resistance of the materials inside the battery or the components and circuits inside the power supply. When we use the phrase 'electrical circuit' we really mean it — electric current goes all the way round, and the flow of current is affected by resistance anywhere in the circuit — including the inside of the battery or the power supply. This internal resistance causes the battery or power supply voltage to drop when we connect a circuit to it. Let's see why. Imagine a battery or a power supply in two pieces (Fig. 1). One piece is a perfect supply giving 9 V no matter what current is taken. The other bit is a resistor of 12 ohms in series. The terminals represent the terminals of the battery.

OHMS'S LAW AND ALL THAT

This is an equivalent circuit, meaning a 'theory' circuit which behaves in exactly the same way as a real one. For any real circuit, we can draw up an equivalent which is a lot easier to work with. Let's see how this one works out. If we don't take any current from this circuit, the voltage at the terminals is just the 9 V of the supply — we sometimes call this quantity the EMF (Electro-motive force) of the supply. When we take some current from the circuit, though, there will be a voltage drop across the 12 ohm resistor. How much voltage drop? Ohm's Law tells us. Suppose we take 100 mA, which is 0.1 A, then the voltage drop is $0.1 \times 12 = 1.2$ V. Now all the voltage which we can get in the circuit comes from the battery action, which converts the chemical reaction, inside the battery into electrical voltage.

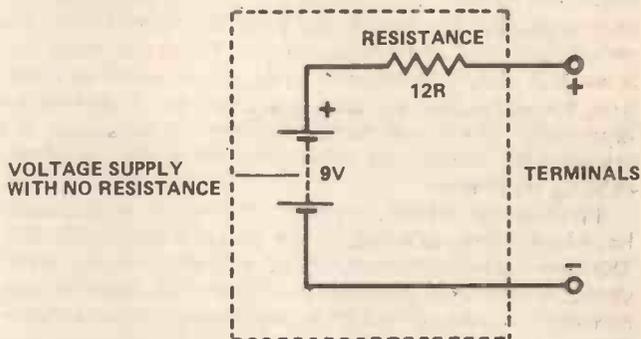


Fig. 1. Equivalent circuit of a battery or power-pack. If we think of the voltage generator part separate from its resistance, the action is much easier to understand.

The voltage at the terminals is therefore less, 1.2 V less, than the voltage which the battery generates. The terminal voltage is 9 V, 1.2 V = 7.8 V. This particular battery will therefore give only 7.8 V at its terminals when a current of 100 mA is drawn.

For a lot of electronic circuits, this change of voltage when current is drawn doesn't matter until the battery voltage starts to drop. This incidentally is what causes owners of multimeters to think they have something wrong with their radio, calculator or flashguns when all that's needed is a fresh battery . . . Why? They take the battery out and measure the voltage. Unless the battery is in a really bad way, the voltage that is measured will be the open circuit voltage, which can easily be quite normal. What you should test is the voltage at the terminals of the battery when the circuit is connected and working. A dud battery gives a very low voltage on this test because the internal resistance increases as the battery gets old and grey.

FUSSY CIRCUITS

There are circuits, though, which definitely dislike having a supply when the current changes. Even stereo amplifier circuits object a bit — it's not at all unusual to find that the maximum power per channel is quite different when both channels are in action than when



only one is driven at a time. Radar and computing circuits are distinctly fussy about changes of voltage too so that the effect of internal resistance on a power supply is a bad thing as far as these circuits are concerned.

The answer to the problem is a voltage stabiliser circuit, which keeps the output terminals of the supply at the same voltage even when the current changes. Don't get too excited by the idea, though. A stabilising circuit isn't magic — it can't increase the voltage of a supply to compensate for the voltage drop of the internal resistance. What a stabiliser circuit does is to let us use a supply whose open-circuit voltage is much higher than we need. The stabiliser then acts as a controller keeping the voltage down to the level we need. For example, if we wanted to replace a 9 V battery supply by a stabilised supply, we would use a 15 V (or higher) supply. The stabiliser would then reduce this 15 V to 9 V. As more current is taken from the circuit, causing the 15 V to reduce to, perhaps, 12 V, the stabiliser adjusts automatically, reducing the 12 V to 9 V. A stabiliser can cope if the amount of current that is taken from the circuit causes the supply voltage (before stabilisation) to fall below or even near the level of the stabilised voltage that is needed.

ALL DOWN TO ZENERS

The simplest form of voltage stabiliser is the Zener Diode. The Zener Diode is a silicon junction diode whose junctions are made by the same process as is used for silicon transistor junctions. We can, in fact, use the base-emitter junction of a silicon transistor as a Zener Diode — for several dozen 2N697's tested, the average Zener voltage was 15 V. The current-voltage graph of the Zener Diode is shown in Fig. 2. As the reverse voltage across the diode is increased, the diode suddenly conducts at a voltage called the reverse breakdown voltage or Zener voltage. Once this voltage is reached, the current through the diode can be varied considerably with no change in the voltage. This makes the Zener Diode a very useful stabiliser. The circuit used is shown in Fig. 3. A voltage supply which must be several volts greater than the Zener Diode voltage is used to feed current to the Zener Diode through a resistor R. The value of R determines how much current can be taken out of the circuit before the Zener stops Zenering. For example — with a 5.6 V Zener Diode and a 9 V supply, the voltage across R is $9 - 5.6 = 3.4$ V. If the value of R is 100 ohms, then the current flowing into the Zener Diode is $I = V/R = 3.4/0.1 = 34$ mA (using $100R = 0.1$ k).

Now if we connect a load resistor across the Zener Diode, it will take some current. If the Zener Diode does its stuff, the voltage across it must stay at 5.6 V, and the current that flows into the load is taken at the expense of the Zener Diode. If, in our example, the load takes 30 mA, then the Zener Diode takes 4 mA. This way, there's still a total of 34 mA flowing and the voltage drop across R is the same. If we tried to draw 34 mA from the Zener Diode circuit, though, we would expect to run into trouble, because that leaves no current passing through the diode and therefore no stabilisation.

A regulator of this type is called a shunt regulator because the device which carries out the regulation — the Zener Diode in this example — is in shunt (or in parallel) with the load.

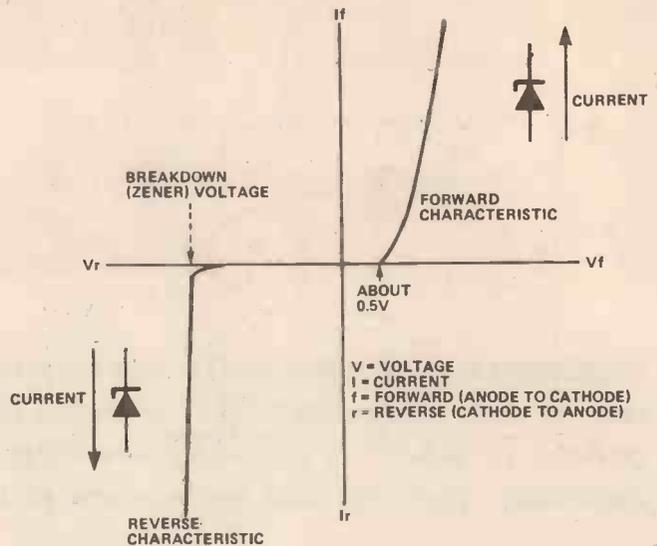


Fig. 2. Current-voltage graph (or characteristic) for a Zener Diode. The part of greatest interest to us is the reverse characteristic.

A shunt regulator works by keeping the current flowing from the supply at a constant value, allowing the load to tap some off as required at the expense of the regulator. The current through R is constant, so that the power rating of this resistor has to be watched. The Zener is dissipating most power when the load is drawing no current, so that this type of regulator is most useful for loads which draw some current all the time.

The device in shunt with the load doesn't have to be a Zener Diode. Fig. 4 shows a circuit sometimes called the amplified Zener which uses a transistor — which can be a high current type — along with a Zener Diode. In this circuit, the Zener Diode is connected between the collector and the base of a transistor, keeping the voltage between the two at the Zener Diode voltage. A low-current, low-power Zener can be used and we usually have to add a load resistor to keep enough current flowing through the Zener Diode for stabilisation. When this combination of transistor and Zener Diode is connected in circuit with a resistor, as if the whole circuit were a Zener Diode, the circuit acts as a shunt stabiliser. When the supply is switched on, current will flow through R1 so that the output voltage rises. When the output voltage rises above the Zener voltage, the voltage at the base of the transistor will also rise until the transistor starts to conduct with about 0.5 V between base and emitter. When the transistor starts to conduct,

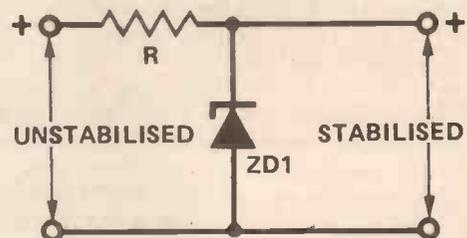


Fig. 3. A simple Zener Diode stabiliser circuit.

Internal Resistance

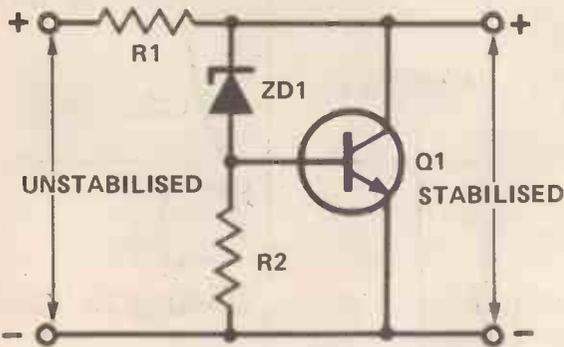


Fig. 4. The Zener-and-transistor shunt regulator, or "amplified-Zener" circuit.

the output voltage is stabilised. Why? Well, for any silicon transistor, a change of base voltage of 0.06 V is enough to cause the collector current to change by a factor of ten. For example, if the transistor passes 1 mA collector current at 0.55 V and the base, then at 0.55 + 0.06 = 0.61 V on the base the collector current will be 10 mA. The base voltage, therefore, stays pretty well fixed, because, even a slight increase in base voltage will cause a large increase of collector current and so a large voltage drop across R1 and that will cause the base voltage to drop!

The result is that the base voltage stabilises at around 0.55 V, and the output voltage at the collector is just the Zener Diode voltage greater. If we use a 5.6 V Zener, for example, the stabilised voltage will be 5.6 V + 0.55 V, about 6.15 V. We can, of course, choose the stabilised output voltage by choosing the Zener Diode voltage.

That's our answer to the internal resistance problem, but it's only part of the answer. There's another type of stabiliser circuit, the series stabiliser which works rather differently, but that will have to wait for another time.

HE

SINCLAIR PRODUCTS microvision tv world model £147.95, UK model £99.95, mains adaptor £6.73, POM35 £28.95, mains adaptor £3.19, case £3.19, DM350 £68.95, DM450 £97.95, DM235 £49.45, rechargeable batts £7.50, mains adaptor £3.70, case £8.45. Enterprise prog. calculator with accessories £22.95. Cambridge prog. calculator £12.13, prog. library £4.48, mains adaptor £3.20. **CSC MAX100** freq meter £75.40. **CALSCOPE** oscilloscopes send sse for data or see the Calscope advert in this magazine. Super 6 £174. Super 10 £236. **COMPUTER GAMES** chess challenger 10 £167. Chess challenger 7 £79. Checker challenger 4 £84. Checker challenger 2 £50. Atari videocomputer £138. Cartridges £13.45. **COMPONENTS** send sse for full list. 1N4148 1.4p, 1N4002 2.9p, 741 15p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 4.5p, resistors 4W 5% £12.10R to 10M 1p, 0.8p for 50+ of one value, 16V electrolytics .5/1.2/5/10/22uf 5p, 100uf 6p, 1000uf 10p, 1 lb FeC1 £1.13, dolo pen 79p, 60sq ins pcb 55p. **TV GAMES** send sse for data AY-3-8500 + kit £8.95, Rifle kit £4.95, AY-3-8600 + kit £15.70. Stunt cycle chip + kit £15.70. Tank battle kit £5.95. **TRANSFORMERS** 6-0-6v 100ma 74p, 1 1/2 £2.35, 6-3v 1 1/2 £1.89, 9-0-9v 75ma 74p, 1a £2, 2a £2.60, 12-0-12v 100ma 90p, 1a £2.49. **IC AUDIO AMPS** with pcb, JC12 6W £1.60, JC20 10W £2.95, send sse for data.

BATTERY ELIMINATORS 3-way type 8 1/2 v/9v 300 ma £2.95, 100ma radio type with press studs 9v £3.35, 9v+9v £4.50, Car converter 12v input, output 4 1/2 v/6 1/2 v/9v 800ma £2.50. **BATTERY ELIMINATOR KITS** send sse for data, 100ma radio types with press-studs 4 1/2 v £1.40, 6v £1.40, 9v £1.40, 4 1/2 v+4 1/2 v £1.80, 6+6v £1.80, 9+9v £1.80. Stabilized 8-way types 3 1/4 v/6 1/2 v/9v/12v/15v/18v 100ma £2.80, 1amp £6.40. Stabilized power kits 2-18v 100ma £2.80, 2-30v 1A £6.95, 2-30v 2a £10.95, 12v car converter 6 1/2 v/9v 1a £1.35. **T-DEC AND CSC BREADBOARDS** 1-dec £4.02, u-deca £4.40, u-decb £6.73, s-dec £3.80, exp300 £6.21, exp350 £3.40, exp325 £1.73, exp 4b £2.48. **BI-PAK AUDIO MOULDS** s450 £23.51, AL60 £4.86, pa100 £16.95, spm80 £4.47, bmt80 £5.95, stereo 30 £20.12, AL30 £3.95, PA12 £7.60, PS12 £1.39, MA60 £35.44.

SWANLEY ELECTRONICS

Dept. HE, 32 Goldsai Rd., Swanley Kent
Post 30p extra. prices include Vat. Official and overseas orders welcome.

Ref.	ELECTRONIC BOOKS	Price
126	Boys Book of Crystal Sets	25p
138	How to Make Aerials for TV (Band 1-2-3)	25p
160	Coil Design and Construction Manual	75p
196	AF - RF Reactance - Frequency Chart for Constructors	15p
200	Handbook of Practical Electronic Musical Novelties	50p
201	Practical Transistorised Novelties for Hi-Fi Enthusiasts	35p
202	Handbook of Integrated Circuits (IC's) Equivalents and Substitutes	100p
203	IC's and Transistor Gadgets Construction Handbook	60p
205	First Book of Hi-Fi Loudspeaker Enclosures	75p
206	Practical Transistor Circuits for Modern Test Equipment	60p
207	Practical Electronic Science Projects	75p
208	Practical Stereo and Quadraphony Handbook	75p
210	The Complete Car Radio Manual	100p
211	First Book of Diode Characteristics Equivalents and Substitutes	95p
213	Electronic Circuits for Model Railways (Reprinting)	100p
214	Audio Enthusiasts Handbook	85p
215	Shortwave Circuits and Gear for Experimenters and Radio Hams	85p
216	Electronic Gadgets and Games	100p
217	Solid State Power Supply Handbook	85p
218	Build Your Own Electronic Experimenters Laboratory	85p
219	Solid State Novelty Projects	85p
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p
221	28 Tested Transistor Projects	95p
222	Solid State Short Wave Receivers for Beginners	95p
223	50 Projects Using IC CA3130	95p
224	50 CMOS IC Projects	95p
225	A Practical Introduction to Digital IC's	95p
226	How to Build Advanced Short Wave Receivers	120p
227	Beginners Guide to Building Electronic Projects	125p
228	Essential Theory for the Electronics Hobbyist	125p
RCC	Resistor Colour Code Disc Calculator	10p
BP1	First Book of Transistor Equivalents and Substitutes	50p
BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p
BP6	Engineers and Machinists Reference Tables	50p
BP7	Radio and Electronic Colour Codes and Data Chart (Reprinting)	25p
BP11	Practical Transistor Novelty Circuits	40p
BP14	Second Book of Transistor Equivalents and Substitutes	110p
BP22	79 Electronic Novelty Circuits	75p
BP23	First Book of Practical Electronic Projects	75p
BP24	52 Projects Using IC741	95p
BP25	How to Build Your Own Electronic and Quartz Controlled Watches & Clocks	85p
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p
BP28	Resistor Selection Handbook (International Edition)	60p
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p
BP30	Two Transistor Electronic Projects	85p
BP31	Practical Electrical Re-Wiring and Repairs	85p
BP32	How to Build Your Own Metal and Treasure Locators	80p
BP33	Electronic Calculator Users Handbook	95p
BP34	Practical Repair and Renovation of Colour TVs (Reprinting)	95p
BP35	Handbook of IC Audio Preamplifier and Power Amplifier Construction (Reprinting)	95p
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	75p
BP37	50 Projects Using Relays, SCR's and TRIACS	110p
BP38	Fun and Games with your Electronic Calculator	75p
BP39	50 (FET) Field Effect Transistor Projects	125p
BP40	Digital IC Equivalents and Pin Connections	250p
BP41	Linear IC Equivalents and Pin Connections	275p
BP42	50 Simple L.E.D. Circuits	75p
BP43	How to Make Walkie-Talkies	125p
BP44	IC555 Projects	145p
BP45	Projects in Opto-Electronics	125p
BP46	Radio Circuits Using IC's	135p
BP47	Mobile Discotheque Handbook	135p
BP48	Electronic Projects for Beginners	135p
BP49	Popular Electronic Projects	145p
BP50	IC LM3900 Projects	135p
BP51	Electronic Music and Creative Tape Recording	125p
BP52	Long Distance Television Reception (TV-DX) For The Enthusiast	145p
BP53	Practical Electronic Calculations and Formulae	225p
BP54	Your Electronic Calculator and Your Money	135p
BP55	Radio Stations Guide	145p
T1	TTL Pin Configuration Guide	175p

Please add 25p p&p

TECHNOMATIC LTD
17 BURNLEY ROAD, LONDON NW10 1ED
(2 minutes from Dollis Hill Tube Station) (Ample parking space)
Telephone: 01-452 1500. Telex: 922800

7400 14p
7404 18p
7408 20p
7410 18p
7413 32p
7420 18p
7430 17p
7447 65p
7473 36p
7490 35p
7493 35p
74121 30p
CA3080 77p
CA3140 75p
ICL8038 370p
LM380 80p
LM741 24p
NE555 24p
T8A800 100p
Z414 100p

DIL SOCKETS
8pin 12p
14pin 13p
16pin 14p

Large range of components available. Send SAE

ANTEX SOLDERING IRONS
C-15W 390p
CX-17W 410p
CCN-15W 410p

COPPERCLAD
X-25W 410p
Spare bit 50p
Stand 170p

VEROBOARDS
01 Copperclad
2 1/2 x 5 62p
3 1/2 x 2 1/2 53p
3 1/2 x 3 1/2 62p
3 1/2 x 5 89p
3 1/2 x 17 240p

POCKET MULTIMETERS
KRT100 580p
(1000 ohms/V)
LT22 1360p
(20kohms/V)
Test Lead Kit 160p
(Prods, Croc clips, bananas, Spades)
10 Test leads with Croc Clip at each end 110p

EXPERIMENTER BOARD
(No soldering, suitable for DIL ICs)
For 1 IC Circuit (up to 22pin)
EXP25 180p
For up to 3x14pin DIL IC
EXP350 360p
For up to 5x14pin DIL ICs
EXP300 641p
IC Test Clips
14pin 285p
16pin 297p
Logic Probe 1900p

Back numbers



**If you find when you look back,
There are gaps in your HEs,
Then we'll send you what you lack,
For a miserly sixty pees.**

Well what do you expect from an electronics magazine — poetry?

However, we at HOBBY ELECTRONICS firmly believe that a complete set of HE will be worth a small fortune in 1990, so why miss out? Getting a set together is easy (at the moment) because we're only five months old. Your sixty pence includes the cost of post, what a bargain, why not start two sets?

**Send to: Back Numbers Dept,
Hobby Electronics,
25-27 Oxford Street,
London W1R 1RF**

Largest range of quality components in the U.K. — over 8,000 types stocked



**Head Office and Mail Order to Dept. HE
A. Marshall (London) Ltd.
Kingsgate House, Kingsgate Place
London NW6 4TK. Tel: 01-634 0805
Telex 21442**

**Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, NW. Tel: 01-723 4242.
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel. 0272 426801/2**

RESISTORS
FIXED
CARBON

0.25 watt ±5% Tol. Available in E12 range 10Ω to 1 meg 2p each
0.5 watt ±5% Tol. Available in E12 range 10Ω to 10 meg 3p each
1.0 watt ±10% Tol. Available in E12 range 10Ω to 10 meg 5p each
2.0 watt ±10% Tol. Available in E12 range 10Ω to 10 meg 9p each

WIRE WOUND
2.5 watt ±5% Tol. Following values only: 10p each
0.5, 1.0, 1.5, 2.0, 2.5, 3.0, 3.3, 3.9, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330

5 watt ±5% Tol. Following values only: 12p each
5.1, 2.2, 3.3, 3.9, 4.7, 6.8, 8.2, 10, 12, 15, 18, 22, 25, 33, 39, 47, 60, 75, 82, 100, 120, 150, 180, 220, 250, 270, 300, 330, 470, 500, 560, 680, 820, 1k, 1k2, 1k5, 2k, 2k2, 2k5, 3k, 4k7, 5k6, 6k8, 7k5, 8k2, 10k, 12k

10 watt ±5% Tol. Following values only: 14p each
1.2, 2.2, 3.3, 4.7, 6.8, 7.5, 8.2, 10, 12, 15, 18, 22, 25, 33, 39, 47, 70, 82, 100, 120, 150, 200, 250, 330, 470, 560, 680, 750, 1k, 1k2, 1k5, 1k8, 2k, 2k2, 2k7, 3k, 3k5, 4k7, 5k, 5k6, 6k8, 10k, 15k, 18k, 20k, 25k

MULLARD MFR25/MFR30 SERIES METAL OXIDE
0.5 watt ±2% Tol. Available in E24 range 10Ω to 1 meg 4p each

Also stocked Non Linear & Light Dependent ranges — see catalogue.

TOOLS
Box joint construction for strength. Small, compact and reliable, insulated handles and smart individual wallet.

GENERAL PURPOSE
100mm (4") Diagonal Cutters £3.40
Round Nose Pliers £3.25
Flat Nose Pliers £3.20
Snake Nose Pliers £3.20
End/Top Cutters £3.60


BOXES AND CASES
See catalogue for full range

ALUMINIUM
BA2 4x4x1 1/2" £0.85
BA3 4x2 1/2 x 1 1/2" £0.80
BA4 4x2 1/2 x 1 1/2" £1.00
BA5 4x2 1/2 x 2" £0.95
BA6 3x1 1/2 x 2" £0.60
BA7 6x4x2" £1.25

REXINE COVERED
RB1 8x4 x 1 1/2" £1.75
RB3 9x5x2 1/2" £2.40
RB5 11x7 1/2 x 3 1/2" £3.55
RB7 15x8x4" £5.00

ABS PLASTIC
3 1/2" x 2 1/2" x 1 1/2" £0.55
3 1/2" x 2 1/2" x 1 1/2" £2.10

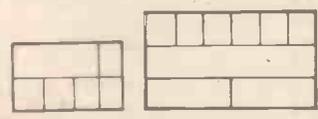RAACO STORAGE BOXES
2 sizes — 4 configurations
96 £0.76 87 £0.76 89 £1.62 818 £1.78



VERO CASES — see catalogue for full range
7 different styles — 18 sizes

PLASTIC CLIP CASES
Anodised Aluminium front panel two 10mm halves clip together
VCC1—85x10x154mm £2.50
VCC2—85x10x154mm £3.15
VCC3—85x80x154mm £3.65

Also — instrument cases — 5 sizes from £2.10
Card frames, flip top boxes, etc. etc

TTL see catalogue for full range

74LS00N	£0.26	74LS83AN	£0.90	74LS168N	£1.45
74LS01N	£0.26	74LS85N	£0.95	74LS169N	£1.45
74LS02N	£0.26	74LS86N	£0.44	74LS170N	£1.90
74LS03N	£0.25	74LS90N	£0.64	74LS173N	£1.10
74LS04N	£0.29	74LS91N	£1.20	74LS174N	£0.75
74LS05N	£0.29	74LS92N	£0.70	74LS175N	£0.75
74LS06N	£0.26	74LS93N	£0.64	74LS181N	£2.75
74LS09N	£0.26	74LS95AN	£0.90	74LS183N	£2.70
74LS10N	£0.26	74LS96N	£1.35	74LS189N	£3.74
74LS11N	£0.26	74LS107N	£0.42	74LS190N	£1.00
74LS12N	£0.26	74LS109N	£0.42	74LS191N	£1.00
74LS13N	£0.58	74LS112N	£0.42	74LS197N	£0.95
74LS14N	£0.75	74LS113N	£0.42	74LS198N	£0.95
74LS15N	£0.26	74LS114N	£0.42	74LS194N	£0.70
74LS20N	£0.26	74LS122N	£0.62	74LS195N	£0.70
74LS21N	£0.26	74LS123N	£0.83	74LS196N	£0.80
74LS22N	£0.26	74LS124N	£1.70	74C00N	£0.24
74LS27N	£0.32	74LS125N	£0.50	74C02N	£0.24
74LS27N	£0.26	74LS126N	£0.50	74C04N	£0.24
74LS29N	£0.29	74LS132N	£0.95	74C06N	£0.24
74LS30N	£0.26	74LS136N	£0.42	74C10N	£0.24
74LS32N	£0.27	74LS138N	£0.65	74C14N	£0.95
74LS33N	£0.29	74LS139N	£0.65	74C20N	£0.24
74LS37N	£0.32	74LS145N	£1.30	74C23N	£0.24
74LS38N	£0.32	74LS147N	£1.65	74C27N	£0.24
74LS40N	£0.26	74LS148N	£1.35	74C29N	£0.92
74LS42N	£0.80	74LS151N	£0.58	74C48N	£1.38
74LS47N	£1.09	74LS153N	£0.58	74C73N	£0.54
74LS48N	£1.00	74LS154N	£1.45	74C74N	£0.56
74LS49N	£1.09	74LS155N	£0.80	74C75N	£0.54
74LS51N	£0.26	74LS156N	£0.80	74C83N	£1.30
74LS54N	£0.26	74LS157N	£0.60	74C85N	£1.30
74LS55N	£0.26	74LS158N	£0.65	74C86N	£0.64
74LS56N	£1.26	74LS160N	£0.80	74C89N	£4.39
74LS73N	£0.42	74LS161N	£0.85	74C90N	£0.85
74LS74N	£0.42	74LS162N	£0.80	74C93N	£0.85
74LS75N	£0.59	74LS163N	£0.85	74C95N	£1.04
74LS76N	£0.42	74LS164N	£1.10	74C107N	£1.22
74LS79N	£0.42	74LS165N	£1.15	74C150N	£4.14

NEW 1979 CATALOGUE
48 pages — largest range of quality components in the UK — over 8,000 line items — 50p post paid. 40p to callers.

MAIL ORDER
Add 40p p/p to all orders.
Tel. credit card orders £10, min ACCESS — BARCLAYCARD.

NEW TELETEXT CHIPS
from Mullard — available from Marshall's — Sole UK distributor to the hobbyist market.

SAA Series, for the reception, display and control of television based text display systems. Suitable for CEE-FAX and 'ORACLE' Remote Control

SAA5000 Infrared/Ultrasonic £3.48
SAA5010 Station selector/DICS £8.13
SAA5012 Binary Input Tuners P.O.A.
TELETEXT (Dedicated I.C.'s)
SAA5020 TIC (Timing Chain) £8.71
SAA5030 VIP (Video Input Processor) £11.81
SAA5040 TAC (Teletext Data Acquisition and Control) £31.82
SAA5050 TROM (Teletext Read Only Memory) £18.86

TIC, TAC & TROM are NMOS — VIP is linear bipolar. We recommend using DIL sockets with these chips.

CAPACITORS Polyester 250VDC — Radial Leads

UF	Price	10c	Price	UF	Price
0.01	£0.06	0.068	£0.07	0.47	£0.14
0.015	£0.06	0.1	£0.08	0.68	£0.20
0.022	£0.06	0.15	£0.08	1	£0.24
0.033	£0.06	0.22	£0.09	1.5	£0.36
impure	£0.06	0.33	£0.13	2.2	£0.37

ELECTROLYTICS — MULLARD

15 Volt	25 Volt	63 Volt
15	£0.10	£0.60
33	£0.10	£0.73
68	£0.13	£0.68
150	£0.16	£0.10
330	£0.42	£0.15
680	£0.50	£0.19
1500	£0.83	£0.42
		£0.33
		£0.30
		£0.78

TANT BEADS
ELECTROLYTIC AXIAL RADIAL METALLISED
POLYESTER EXTENDED FOIL PLASTIC FOIL, MICA, ETC.
ETC. See catalogue.


KNOBES AND SWITCHES
Full range in catalogue

M1 Black plastic with mach. metal insert 25mm dia £0.25
M2 as M1 but with pointer £0.31
M5 — Black plastic with mach. insert and calibrated skirt £0.33
Car Radio knob with chrome top £0.39

Hobby Electronics

Next
Month

BUMPER SHORT CIRCUIT ISSUE

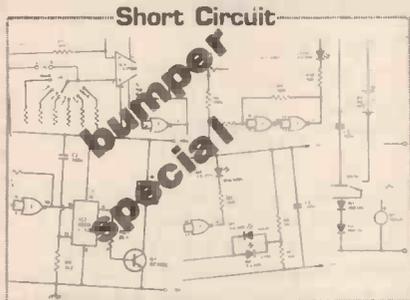


Look out this month for more than your usual share of our very popular, Short Circuit feature. Plenty of circuit designs for you to develop and experiment with.

SHARK



Not a game for the nervous. An LED-based game for two players which involved two swimmers in a race for survival in a shark-infested sea. Which of these two castaways will reach the safety of the island? The unfortunate one is swallowed by the hungry shark, accompanied by a shrill scream. All good family fun!

LINEAR SCALE OHMMETER

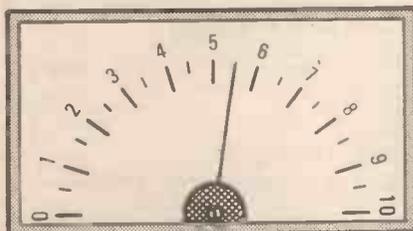


If you ever look at a multimeter on the ohms range you'll notice that most of the numbers are all squashed up one end; this makes accurate readings difficult. The HE Ohmmeter overcomes this difficulty with a linear scale. The range of resistance covered is from 1 k to 1 M ohms in four ranges, a useful addition to any workshop's range of test equipment.

CASSETTE DECKS AND TAPES



Next to the TV and Transistor radio, the Cassette tape recorder is probably the most common piece of domestic electronic equipment. Next month Gordon King takes a close look at what has made the Compact Cassette so popular and one or two of its advantages and drawbacks, warts and all.

RESISTORS

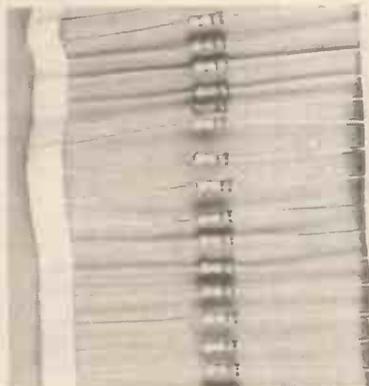


Following the success of our feature on Capacitors (according to our reader questionnaire) we're doing a follow up on the ins-and-outs of Resistors. Like Capacitors it's *not* going to be a formula-strewn study but a rather slanted look into their construction and use. So if you've never heard of Thick Film resistors and Metal Oxide, now's your chance.

HOBBY CHIT CHAT

Ray Marston our Project Editor/Designer starts a new monthly series looking at our fast-moving hobby from the technical point of view. These articles are designed to take a look into the world's largest growth industry, what's new and how it will affect us in our daily lives as well as a more specific look at our own side of the fence in HE.

KIT REVIEW

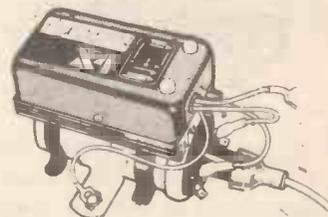


One for the motorist this month, we have built up an Electronic Ignition system from Sparkrite (X4); read all about it next month.

LINEAR ICs

If you've been wondering what's going to happen now Into Electronics has finished, don't worry. Ian Sinclair has begun his follow-up series Linear ICs. Month by month the articles will introduce most aspects of IC use, construction and theory. With the background knowledge gained from Into Electronics your understanding of new technology should increase dramatically.

POINTS CONTROLLER

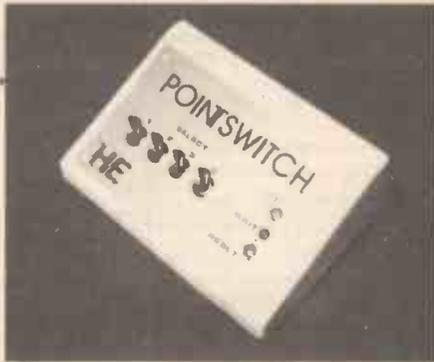

Another project for model railway buffs. This unit gives full control over an unlimited number of electro-mechanical points using a push-button control. This makes an ideal companion to our HE Model Train Controller featured in the April issue.

BABY ALARM

A really simple project to keep one ear on the kids whilst you're building your latest HE project.

The July issue will be on sale June 8th

The items mentioned here are those planned but circumstances may affect the actual contents

LISTEN TO THE SECRET WORLD OF PLANTS

Now in Modular Kit Form, a Biological Amplifier and Sound Synthesiser in one instrument, the *Amazing* See and Hear Yourself at Birmingham Breadboard and at the Festival for Mind, Body and Spirit at Olympia.



Bio Activity Translator™

- ★ Experience the unique Musical Form of Plants
- ★ Hear beautiful patterns of sound created by their natural response
- ★ Compare house plants' reactions to people — with the distinct tunes of those outside
- ★ Easy to operate, internal speaker and batteries
- ★ P.C.B. available as a separate kit, or assembled and tested.

Natural Bio Electric signals, generated within the plant, are monitored by an electrode attached to the leaf. When

amplified and filtered, a VCO, VCA and other exclusive synthesiser circuits are programmed by the control voltage from the plant to produce tracking sequences of notes. These follow in pitch, rhythm and volume the ever changing signal from the plant. A plant reacts as a total living system to many stimuli, with a response above that of the natural biological level. This activity is an indication of their extraordinary sensitivity, which varies from day to day and plant to plant, producing a fascinating insight into the plant kingdom.

Complete Printed Circuit Kit £13.95

Assembled and Tested Printed Circuit £17.35

Case, Speaker and Hardware Kit £12.30

Complete Assembled and Tested unit £33.10

Requires 35Ω speaker, £1.50 extra when ordered with kit. O.P. switch and two 4½ volt batteries.

Includes all screws, wire, punched case and wood end checks.

Requires two 4½ volt batteries. Case size 7¼ x 5¼ x 3¼.

All prices include P. & P. and VAT. Please allow 21 days for delivery

JEREMY LORD SYNTHESISERS (Dept. HE)
52 Becmead Avenue, London SW16 1UQ

OSCILLOSCOPE

FEATURES

- Response: DC to 5MHz.
- Sensitivity: 100mV to 50V/division.
- Fully calibrated time-base circuit and automatic blanking.
- 100% solid state
- utilising 13 transistors, 1 FET and 1 specially designed time-base module.
- Stabilised power supplies and active sync circuits.
- Rugged construction together with portability.
- Inexpensive — excellent value and performance.

FULL INSTRUCTION & OPERATING MANUAL

SPECIFICATIONS

ELECTRICAL DATA

VERTICAL AXIS (Y)
Deflection Sensitivity — 100mV/division
Bandwidth (between 3dB points) — DC — 5MHz
Input Attenuator — (calibrated) — 9 step 0.1, 0.2, 0.5, 1, 2, 5, 10, 20, 50V/div

Input Impedance — 1 Meg/40pF in shunt
Input Voltage — Max — 600V P-P


HORIZONTAL AXIS (X)

Deflection Sensitivity — 0.400mV/division
Bandwidth (between 3dB points) — 1 Hz — 350kHz
Gain Control — Continuous when time base in EXT position
Input Impedance 1Meg
Input Voltage — Max — 600V P-P

TIME BASE

Sweep Range (calibrated) — 100ns/div to 10 sec/div in 5 steps

WITH FULL INSTRUCTION MANUAL

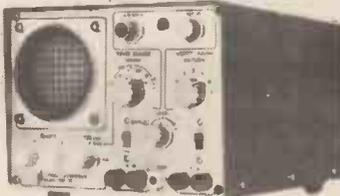

FROM STOCK
£89.95

Add VAT £7.19
Carriage £1.50

EXPORT ADD £5.00

Fine Control — Variable between steps — includes time-base calibration position
Blanking — lateral — on all ranges

SYNCHRONISATION
Selection — internal, external
Synchronisation Level — Continuous from positive to negative

POWER SUPPLY
Input Voltage — 115/220V AC, 10% at 50/60Hz
Power Dissipation — 18W

CRT DATA

— 3" round display—single beam
— Maximum high voltage — 750V
— Fitted with 10 sections, blue filter graticule

PHYSICAL DATA
Dimensions — 15cm (h) x 20.5cm (w) x 28cm (d)
Weight — 3.8kg (approx.)

Stand — 2 position: flat and inclined
Case — Steel, epoxy enamelled
Colour — Light blue
Front Panel — Anodised aluminium, epoxy printing

Also at 248 Tottenham Court Road, London, W.1.
301 Edgware Road, London, W.2



HENRY'S
RADIO

All mail to: Henry's Radio
404 Edgware Rd. London W2
PHONE (01)723 1008 ENGLAND

Hobby Electronics

CLOCK RADIO



Size: 177mm x 90mm x 47mm.

You probably won't believe us as we're selling the goods but we're going to tell you anyway! We have *rejected* eight clock radios for Marketplace, they were all cheap enough but the quality was so poor that we couldn't have lent our name to them. However, we are now able to offer a portable LCD Clock Radio to you which meets our standards.

The clock is a 12-hour one with AM/PM indicated and a back light. The radio is Medium Wave and FM with very nice quality for a small speaker — for FM there's a telescopic aerial. The alarm can be either a 'beep-beep' type or the radio, there's also a snooze facility.

The case is sensibly rugged and is printed on the back with a World Time Zones map, a bit of a cheek really, especially as the time is relative to Japan!

We won't even mention the RRP — but just check on comparable prices — you'll find ours a bargain.

An example of this Clock Radio can be seen and examined at our Oxford Street offices.

£20.50

(Inclusive of VAT and Postage)

To:
CLOCK RADIO Offer,
Hobby Electronics,
25-27 Oxford Street, London W1R 1RF.

Please find enclosed my cheque/P.O. for £20.50 (payable to Hobby Electronics) for my Clock Radio.

Name


Address

Please allow 21 days for delivery UK only

CLOCK RADIO

Marketplace

DIGITAL ALARM CLOCK

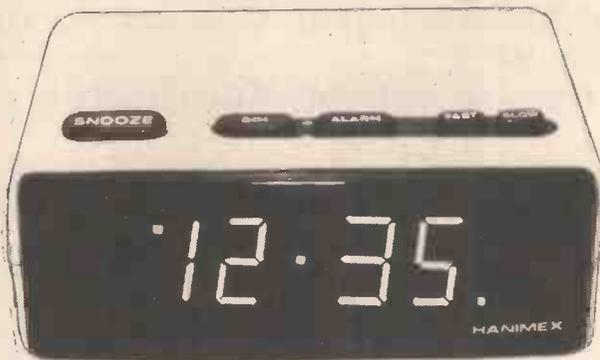

Size: 100mm x 130mm x 60mm.

Over 10% of Electronics Today International's readers have purchased a digital alarm clock from offers in that magazine — the offer is now extended to Hobby Electronics readers. This is a first rate branded product at a price we don't think can be beaten.

The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

An example of this digital alarm clock can be seen and examined at our Oxford Street offices.

£8.95

(Inclusive of VAT and Postage)

LCD CHRONOGRAPH



We feel we've got to tell you carefully about this offer. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The exact same watch is currently being offered by another magazine as a special at £24.95 — some of the discounters are selling it at £29.95 — the price to HE readers for exactly the same watch is £12.95.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

An example of this LCD Chronograph can be seen and examined at our Oxford Street offices.

£12.95

(Inclusive of VAT and Postage)

DIGITAL ALARM

To:
DIGITAL Alarm Offer,
Hobby Electronics,
25-27 Oxford Street,
London W1R 1RF.

Please find enclosed my cheque/P.O. for £8.95 (payable to Hobby Electronics) for my Digital Alarm Clock.

Name

Address

Please allow 21 days for delivery. UK only.

LCD CHRONO

To:
LCD Chrono Offer,
Hobby Electronics,
25-27 Oxford Street, London W1R 1RF.

Please find enclosed my cheque/P.O. for £12.95 (payable to Hobby Electronics) for my LCD Chronograph.

Name

Address

Please allow 21 days for delivery. UK only.

Citizens Banned

We in the British Isles are in a somewhat strange position at the moment, in our midst there are several thousand people breaking the law just by talking to each other, they are using a two-way communications system that is currently illegal. Many of the worlds so-called underdeveloped or politically restrictive countries freely accept CB (Citizens Band) so why not the UK? Richard Maybury and a few CBers (who wish to remain anonymous for obvious reasons) take a look at one of the most contentious subjects in our hobby today.

CHANCES ARE that unless you're a CB'er or have seen the film 'Convoy' all that is pretty meaningless. CB stands for Citizens Band, a short range, two way radio communications system, operating on the Short Wave at around 27 MHz using AM speech modulation.

CB first came into the world in America during the fifties where a Citizens Band was set aside for anyone to use requiring only the formality of a licence. No exams, just a straight fee. The only limitations were the band-spread (for obvious reasons) and output power, limited to 4 watts.

So why are we writing about an American phenomenon? Well it's not anymore, most of Europe, including some 'Iron Curtain' countries have legalised CB, as well as Australia, New Zealand and Canada, nearly everyone except for poor old Britain and Eire. However, although it's illegal it's reckoned by official sources that around 10 000 CB sets are operating in London alone. We would put the figure much higher, there really is a whole subculture out there most of us know nothing about.

CONVOYS AND COPS

Practically all of the 'Rigs' (CB transceivers) in this country are illegally imported, its difficult to say where from but we suspect it's a fair split between the States and Europe.

The craze in Britain really started in earnest about a year ago, inspired probably by the film and record 'Convoy' and the upsurge of interest in America around

the mid seventies (due to the oil crisis and the nationwide 55 mph speed limit). Hardly one American 'cop' show seems to pass without at least one reference to CB.

The current American system, and hence our own British system uses a sophisticated 40 channel arrangement over the 26.9 to 27.4 MHz range. Most rigs use a 'channel synthesizer' a clever device that requires only a couple (sometimes three) crystals to transmit and receive on all 40 channels. As most rigs are either destined for the American or American orientated markets they usually operate with a maximum of 4 watts RF. This is quite sufficient for a 10-15 mile range under normal atmospheric conditions. With the addition of a 'Burner' or 'Boots' (RF power amplifier in CB slang) and an aerial pre-amplifier it's quite possible to hold a Trans-Atlantic conversation utilising 'skip'. This is possible at the moment due to high sunspot activity, but will disappear in a few months. (Skip is where the RF signal 'bounces' around the upper layers of the atmosphere).

Nearly all these rigs are manufactured to strict FCC (Federal Communications Committee) regulations. So (co-channel interference and RF splattering are kept to a minimum. It says a lot for the good design of these rigs, after all when was the last time CB interfered with you? (No, that's not an invitation for 10,000 of you to write in with your tales of woe).

In all fairness though RC (radio control) modellers and certain hospital paging systems operate on two or three of the 40 channels so it can interfere with legitimate users. We are told that quite a strict code of practice exists among CBers and these channels are avoided.



This rather novel CB rig has 80 available channels, by pressing the 'Hi,Lo' switch the set will operate up to 28MHz, we believe this type of rig is now available in the UK.

Below is an example of CB chat, on the left is what you might hear, just for fun we translated it into English, even we were surprised as to how formal it sounds.

"Breaker one four, breaker one four, any breakers got their ears on c'mon."

"Yeah, bring it back the breaker, you've got Moondancer comeback with your handle, break"

"That's a four Moondancer, this the Sewerman, reading you in the nines, break"

"Yeah, Sewerman comeback with your rough twenty, break"

"My rough twenty is the Hackney area, what kinda rig you runnin'? Break"

"Yeah, that's a four, I've got a straight 40 channel digital and I'm running barefoot, is that a four? Break"

"For sure, for sure good buddy, I've got my boots on so my copy's pretty good, break"

"This is Firebird sitting on the side there, have you had any copy from Lucky Lady? Break"

"This is the Sewerman, negatory on that Firebird, it's pretty quiet so far, break"

"Yeah, Sewerman, give me a ten nine on that, the eyeties are treading all over us, break"

"That's a four Firebird, she's not been on channel so far, is that a four? Break"

"That's a four Sewerman, do you fancy an Eyeball? Break"

"Negatory on that Firebird. I'm near my works twenty, so I've got to go down, so I'll wish you all the high numbers and breaker, break"

"Yeah, breaker break Sewerman, all the good numbers. Moondancer, you still on channel, C'mon"?

"That's a four Firebird, what's your rough twenty now? Break"

"Yeah standby Moondancer, I'm in the traffic, Break"

"Yeah standing by, Break"

"Moondancer, you still on channel, C'mon"?

"That's a four Firebird, do you want to move up to two five, two five? Break"

"Yeah Moondancer, see you there, Break"

"Yeah Firebird, you go your wheels moving? Break"

"That's a four, I've got to go down now, cos I need a ten one hundred maybe I'll catch you later, is that a four? Break"

"That's a four, all the high numbers good buddy, and breaker, Break"

"Yeah breaker break"

"Is anyone listening on channel 14, Is anyone listening on channel 14? Please reply. Over"

"Yes, I'm receiving you, my callsign is Moondancer, please reply with your callsign. Over"

"Very good, Moondancer, my callsign is Sewerman, receiving you loud and clear. Over"

"Very good Sewerman, approximately where is your location. Over"

"My approximate location is the Hackney area, what kind of apparatus are you using. Over"

"Yes, that's satisfactory, I'm using an ordinary 40 channel tranceiver with digital display, do you understand? Over"

"Yes I understand, I'm using an RF power amplifier on my apparatus; so you are probably receiving me loud and clear, Over"

"This is another Citizens Band operator listening in. My callsign is Firebird. Have you heard from a CB'er called Lucky Lady. Over"

"This is the Sewerman again, I'm afraid I haven't heard from this lady, it's been very quiet so far. Over"

"Excuse me Sewerman, would you repeat your last message, the Italian gentlemen are rather loud at present. Over"

"Sorry Firebird, I'll repeat my message, as far as I know she has not been using her apparatus, do you understand, Over"

"Yes, thank you Sewerman, would you like to make my acquaintance? Over"

"No, thank you Firebird, I'm nearing my place of work so I'm going to have to switch off, before we part may I wish you the best of luck and may all your future conversations be interference free, Over and out."

"Yes, thank you for all your good wishes, may I wish you the same. Over and out. Moondancer are you still receiving on channel 14, Over"

"Yes, that's correct, where are you now? Over"

"Excuse me for one moment, I'm in a traffic jam, and unable to transmit. Will you bear with me for a few moments? Over"

"Certainly, I'll wait for a while. Over"

"Moondancer are you still there? Over"

"I certainly am, would you like to select another channel, 25, for example. Over"

"Certainly. Moondancer, I will await your call, Over"

"Excuse me Firebird, but are you mobile? Over"

"Yes, I am, but I must switch off now as I need to answer the call of nature rather urgently, possibly we can talk later, is that agreed, Over"

"Yes, certainly, may your reception remain clear my friend, and Over and Out"

"Yes. Over and Out"

Citizens Band Frequencies

Channel No.	Channel Frequency (MHz)	Channel No.	Channel Frequency (MHz)
1	26.965	21	27.215
2	26.975	22	27.225
3	26.985	23	27.255
4	27.005	24	27.235
5	27.015	25	27.245
6	27.025	26	27.265
7	27.035	27	27.275
8	27.055	28	27.285
9	27.065*	29	27.295
10	27.075	30	27.305
11	27.085	31	27.315
12	27.105	32	27.325
13	27.115	33	27.335
14	27.125	34	27.345
15	27.135	35	27.355
16	27.155	36	27.365
17	27.165	37	27.375
18	27.175	38	27.385
19	27.185	39	27.395
20	27.205	40	27.405

* Channel 9 shall be used for emergency.

LIVING IN HARMONY

A lot has been said about Harmonic Interference, the fundamental 27 MHz signal can be propagated on to the 54 and 81 MHz bands, (2nd and 3rd harmonics) but we're sure that very little actual interference occurs with such limited output power.

The recently formed CBA (Citizens Band Association) advocate the legalisation of a CB network on the 230 MHz band (VHF) with frequency modulation. There's a lot to be said for this as many of the technical problems would disappear. We feel however there are no simple solutions but for good or bad CB is here to stay in the UK. Hopefully what happened in Australia can be avoided here. CB users inundated the authorities, catching the so-called pirates proved impossible so the government were forced to legalise it.

We in Britain have a golden opportunity at the moment to start a new system. With the hindsight of all the other countries we could be a world leader in CB personal communications.

During the past few years a lot of UK electronics manufacturers have been bleating about cheap Oriental imports ruining their business. With a new system just think of all those jobs that would be created.


FOREIGN CUSTOMS

The Home Office and Post Office naturally seem to take a pretty dim view of CB, (they're probably thinking of all that lost revenue) with so many CB operators on the air they have a near impossible task trying to catch them. As it is not actually illegal to own a CB rig (it is to use it though), you've virtually got to be caught in the act. As most, if not all Cbers are mobile it is a fair bet that unless they do something very stupid they're not going to get caught.

Of course if the rig was illegally imported (smuggled to you and me) that's another kettle of fish. We've heard of people's houses being searched and CB equipment being confiscated, so beware.



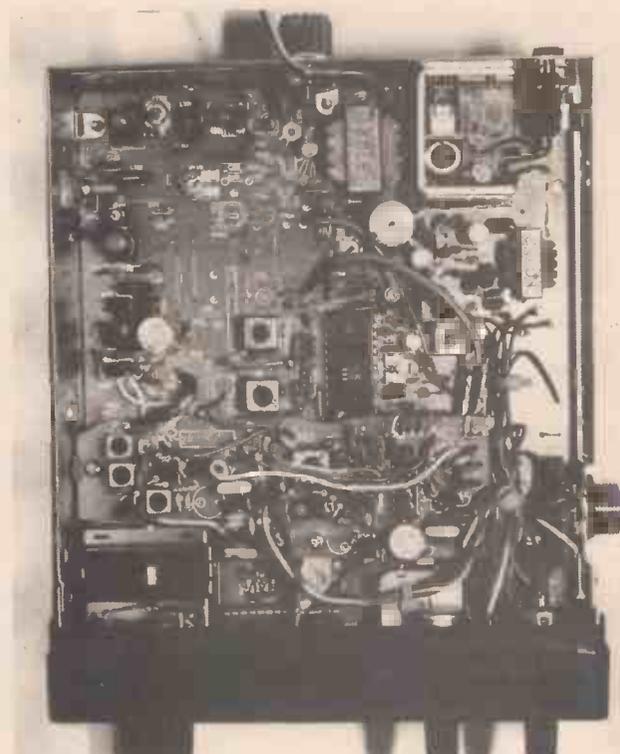A Walkie-Talkie radio working at CB frequencies, these handsets are usually only capable of operating at very limited power, the one shown is an exception using 2 watts RF power.



Inside a typical rig. The RF section can be clearly seen (IF coils). The missing components are, we believe used for a SSB (Single Side Band) option.

Government opposition to CB has always centred around three main arguments. The first is lack of airspace, but as the CBA point out the 230 MHz band is fairly free, much of it unused since World War II.

Number two is use of CB by criminal elements, this

GLOSSARY OF TERMS

ANTENNA The aerial to which the transceiver is connected.

APA Aerial Pre-Amplifier, used in conjunction with a RF power amplifier (see Burner or Boots).

ATU Aerial Tuner Unit, device to give optimum matching between TX/RX and aerial.

BACKDOOR End CB operator in a convoy.

BASE TWENTY The home of a CB operator.

BIG CIRCLE The North Circular Road in London.

BLEEPER BREAKER A coded bleep to signify the end of a transmission.

BOOTS BREAKER See Burner.

BRING IT BACK A CB operator.

BURNER A phrase to indicate that a reply is required.

BUST CHANNEL A RF power amplifier, often with a power output in excess of 100 watts.

CHANNEL Getting caught.

COMEBACK COPY British/American CB utilises 40 separate channels.

C'MON Similar to 'Bring it Back' or 'Break'.

DF Received message.

DX See Bring It Back etc.

EARS Direction Finding.

EARWIG Long Distance.

EYEBALL "Got your EARS On", means are you listening.

EYETIES Listening in to a conversation.

FIVE A meeting between two or more CBers usually arranged with a succession of coded messages denoting place names.

FOUR A somewhat unkind name for the Italians who dominate the CB channels during the early part of the day.

FRONT DOOR "Give me a FIVE", means transmit the numbers one to five for establishing signal strength.

GOING DOWN "That's a FOUR", means simply yes.

HANDLE First CBER in a convoy.

HOLE IN THE WALL Going off the air, switching off.

MEANIES A Breaker's code name.

An area of poor signal strength.

Any anti-CB authorities such as Home Office, Post Office etc.

MIKE Microphone.

MOBILE On the road, moving.

MUSH Noise, masking or interrupting the signal.

NEGATORY NUMBERS No, Negative.

ON CHANNEL "ALL THE HIGH NUMBERS, GOOD BUDDY", is a cordial farewell, referring mainly to the Ten Code.

OPEN READING RIG On the air.

ROGER As On Channel.

ROLLER SKATE Clarity of reception.

RUBBER STATIONARY CB Transceiver.

RUNNING BAREFOOT Yes, OK.

SEAT COVER Production line car.

SMOKEY BEAR Static, not moving.

Stereo Operating without a Burner, or Boots.

SWR Lady friend or wife.

SPAGHETTI The Police.

TEN CODE London.

TEN ONE "Getting you in STEREO", coming through loud and clear.

TEN FOUR Standing Wave Ratio, a method of determining the quality of match between the Rig and aerial.

TEN NINE Italians again, wall to wall spaghetti denotes the Italians are active on the particular channel.

TEN ONE HUNDRED A code devised in America many years ago to convey often repeated messages quickly and clearly. Some examples are given below.

TAKE IT DOWN Signal strength and readability are poor.

TAKE IT UP Yes.

TWENTY Repeat last message.

WALL TO WALL Subtle way of expressing one's desire to answer the call of nature.

WHEELS Move to a (specified) lower channel.

Move to a (specified) higher channel.

A rough twenty is an approximate location.

"Gettin' you WALL TO WALL", receiving you loud and clear. (Or Wall to Wall and Treetop tall.)

A general term for any kind of vehicle.

These are only a few of the currently used phrases and codes. There are obviously many regional variations and dialects, as well as a few rather specific references to locations etc, that we left out deliberately to protect our contacts who are active CB operators.

has got to be self-defeating, only a very stupid villain would discuss his dastardly deeds over the air knowing that hundreds, possibly thousands of people are listening.

Lastly we have administration if CB were ever legalised. This we find very hard to believe, we're sure the PO would find a way of collecting some form of taxation very quickly indeed. The CBA propose that every rig be given a unique identity with a tamper-proof IC module, integral with the system, very simple, very cheap.

PROSECUTION

Actual figures of prosecutions are obviously a little sketchy but we have found out from reliable sources that the number of people taken to court under the Wireless Telegraphy Act, pertaining directly to CB "could be counted on your fingers and toes", to quote an official source. On illegal imports the figures are probably much higher.



A 40 channel rig of the type that are finding their way into this country, as you can see it is not much larger than an ordinary car radio.



TRANSMITTER SPECIFICATION:

- Modulation: 90%
- Frequency tolerance: 0.003%
- Spurious suppression: 60db
- Harmonic suppression: 60db
- Output power: 4W

RECEIVER SPECIFICATION:


- Sensitivity: 0.7 μ v for 10db S+N/N
- Adjustable channel rejection: 70db
- AGC range: 80db
- Squelch range: 0.7 μ v — about 300uv
- Frequency response: 500-2.5KHz
- Audio power: 4W
- Dimension: 174.6mm(W) x 57.2mm(H) x 181.8mm(D)

Fairly typical specifications for a 40 channel CB rig (FCC Specs.).

It seems that every CBer we've spoken to during our research for this article has some tale of someone who knows someone else who's been 'done' but in actuality the figures do not bear these stories out. The CB fraternity seem to have an almost paranoid fear of prosecution, going to extreme lengths to mask their identity with code names and equally furtive enterprises, with some justification we hasten to add.

LIFE SAVER

Those were some of the legal drawbacks and technical problems, so what are the benefits? Judging from the American experience it seems that CB is an astounding success. The US has one channel (channel 9) set aside for emergencies only. All the police and ambulance services constantly monitor channel 9. If for instance a CB operator is present at the scene of a motor accident, (and it's quite likely with over 30 million rigs in operation) help can be summoned swiftly. It's reckoned to have saved countless of lives in the past few years. The police (Smokey Bear, remember Convoy) actually encourage the use of CB as an aid to road safety. If a CBer sees a police speed trap (a radar trap is referred to as Smokey with a camera) a message is sent to all nearby, resulting in an almost instant slow-down of traffic in the vicinity. Even people without CB take notice. It's even rumoured that the police send fake speed trap warnings themselves and can control vast areas of road without actually showing their presence. Now isn't that cunning.

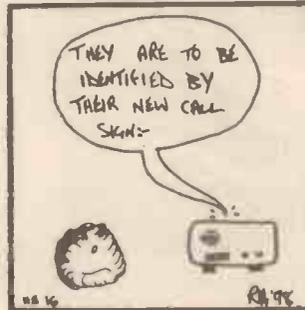

HE'S VIEW

The explosion of interest in Citizens Band Radio, legally in most countries, illegally in Britain, shows there is an enormous interest in it. Since the equipment is manufactured to very rigid technical standards the only sensible argument is that there is not frequency space available.

The authorities (Home Office now, Post Office in the past) are extraordinarily defensive about available frequency space and have used this as a 'trump' card often in the past. The reasons for forcing the pirate radio stations off the air were supposed to be technical when they were really political. There were good political reasons — the pirates were uncontrolled and not answerable to anyone but non-availability of frequencies was used as an argument — yet we've managed to fit about 40 local radio stations on the air since the pirates were silenced.

Other countries with higher densities of population and radio traffic than in Britain have made the frequency space available; this alone should make us discount technical arguments. This leaves the political aspects which are best summed up by 'if practically every democratic nation (and some undemocratic ones) permit it, what is so special about Britain that we must be out of step?'

At the moment it looks like CB will grow and grow in Britain, irrespective of the legal situation; the Home Office may be able to stunt this by devoting enormous resources to tracking down and prosecuting the operators but this publicity would cause a lot of people to ask the fundamental question "why shouldn't we have CB?"

If the authorities had acted earlier, CB could have been allocated onto more suitable frequencies and been properly regulated. It may already be too late.

Anyone who has driven those long miles up the M1 or any long motorway for that matter will testify to the fact that it is all too easy to fall asleep at the wheel. For want of someone to talk to and keep alert many, many lives may have been saved. What a boon it would be to the housebound and lonely.

WHO OWNS THE AIR

The big question of course is will it ever be legalised in the UK? Hopefully the answer must be yes. But not, we

Citizens Banned

hasten to add, by force. It would be unwise to follow in the footsteps of Australia, so what system should we adopt?

There is the established 27 MHz band, plenty of available equipment and well established technology but with inherent interference problems and other channel users, could they co-exist. Then there is the proposed 230 MHz band. By using VHF with frequency modulation most of these problems would disappear. As it is just a proposal there are no manufacturers building suitable equipment in any volume, so there is the potential of job creation. But would the price of such equipment be prohibitive, limiting its usage to the privileged few?

CITIZEN BANNED

The attractions of CB are hard to define. It's possible to make a lot of anonymous friends very quickly. The vast majority of operators follow the unwritten rules — if a "breaker" isn't referred to by his "handle" (call sign) he'll be called a "good buddy" and the whole language is almost elaborately courteous: bad language and swearing is very rare and those who use it are frozen out by other operators.

Most CBers are eager to speak to newcomers and give advice — but anonymously. The security amongst the breakers is very strict.

It's almost impossible to tell who is a CB operator by looking at their "wheels" (transport). The most popular aeriels are those which are very similar to car radio whips or telescopic and those which are clearly not in this category are usually legitimate radio amateurs or two-way radio telephones.

Technically you're not even allowed to listen (your TV licence allows you only to listen to legitimate broadcast stations or recognised amateurs) but many readers will have access to a communications receiver going up to 30MHz and you can hear the CB operators — especially on 27.125 MHz (channel 14) which is used (in London) to establish contact.

A surprising number of women operate CB, our contacts inform us that any night of the week at least half a dozen lady breakers can be heard over the air, and very good they are too we're told, yet another step for women's equality?

AERIALS

A great deal has been said about antennas, much emphasis is placed upon the 'magic' 1 to 1 SWR ratio. The SWR figure denotes the quality of match between the transceiver. The output power will be attenuated by



A CB/Radio/Cassette player combination, a true in-car entertainment centre.



Somewhere in Smokey town, a breaker keys his mike

the presence of Standing Waves in the aerial lead or connections between rig and antenna.

The figure of a 1 to 1 SWR is almost impossible to achieve (despite what people may claim) and a figure of around 2:1 will show only a slight drop in output. Above this figure problems may arise with voltage peaks but as most CB sets are protected against this it's unlikely to cause any trouble.

The positioning of an antenna, however, is very important. For the greatest efficiency it should be as high as possible, this usually means mounting it on the roof of the car. For the greatest omni-directional propagation (All round or symmetrical reception and transmission) it should be mounted in the centre of the roof.

SLANG

The slang used in this country is mainly of American origin. Gradually though English terms are beginning to creep in. (But not we hope the ultra formal language used by Hams, almost totally devoid of humour). As you will see from the glossary there are many phrases that sound quite amusing but we're assured they're all tried and tested, being the easiest way to convey information over what is a potential very noisy communications medium.

POWER OUTPUT

Probably the most controversial side of CB. The American (and most other countries) systems are limited to around 4 watts RF output. People being naturally adventurous are adding Burners (RF power amplifiers) to their rigs. The availability of these burners have been made simple by the Ham fraternity (10 metre power boosters) so power output in excess of 100 watts is quite common. Unfortunately this leads to 'splattering' (co-channel and harmonic interference). This interference can occur over quite a large area. Indeed from our information it seems that most CB prosecutions have involved people using burners. 4 watts would seem to remain fairly inconspicuous.

WHAT DO YOU THINK?

These are the basic arguments for and against CB, a system of one kind or another must be adopted so a decision must be made soon otherwise it will be too late. If you've got any strong views one way or another, why not drop us a line.

You don't have to put your name to it if you are a CB operator, just your 'handle' will do. HE as a magazine would like to follow up this article if response proves sufficient.

If you really do want to get actively involved contact the CBA at 16 Church Road, St Marks, Cheltenham, Glocs GL51 7AN.

HE

STEVENSON

Electronic Components

REGULATORS

78L05 30p	7805 60p	79L05 70p	7912 80p
78L12 30p	7812 60p	79L12 70p	7915 80p
78L15 30p	7815 60p	7905 80p	LM723 35p

HARDWARE


MINIATURE TRANSFORMERS

240 Volt Primary

Secondary rated at 100mA.

Available with secondaries of:

6-0-6, 9-0-9 and	
12-0-12.	92p. each.

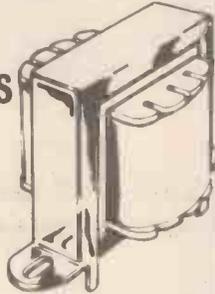

LOUDSPEAKERS

56mm dia. 8 ohms	70p
64mm dia. 8 ohms	75p
64mm dia. 64 ohms	75p
70mm dia. 8 ohms	100p
70mm dia. 80 ohms	110p



TERMINALS

Rated at 10A. Accepts 4mm plug, black, blue, green, brown and red 22p

SWITCHES

Subminiature toggle. Rated at 3A 250V.

SPDT 70p	SPDT centre off 75p
DPDT 80p	DPDT centre off 95p

Standard toggle

SPST 34p	DPDT 48p
----------	----------

Wavechange switches.

1P12W, 2P6W, 3P4W or 4P3W all 43p ea.

Miniature switches (non-locking)

Push to make 15p Push to break 20p

Slide switches (DPDT)

Miniature 14p Standard 15p

CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



TRANSISTORS

AC127 17p	BCY71 14p	ZTX109 14p
AC128 16p	BCY72 14p	ZTX300 16p
AC176 18p	BD131 35p	2N697 12p
AD161 38p	BD132 35p	3N1302 38p
AD162 38p	BD135 38p	2N2905 22p
BC107 8p	BD139 35p	2N2907 22p
BC108 8p	BD140 35p	2N3053 18p
BC109 8p	BF244B 36p	2N3055 50p
BC147 7p	BFY50 15p	2N3442 135p
BC148 7p	BFY51 15p	2N3702 8p
BC149 8p	BFY52 15p	2N3704 8p
BC148 9p	MJ2955 98p	2N3705 9p
BC177 14p	MPSA06 20p	2N3706 9p
BC178 14p	MPSA56 20p	2N3707 9p
BC179 14p	TIP29C 60p	2N3708 8p
BC182 10p	TIP30C 70p	2N3819 22p
BC182L 10p	TIP31C 65p	2N3904 8p
BC184 10p	TIP32C 80p	2N3905 8p
BC184L 10p	ZTX107 14p	2N3906 8p
BC212 10p	ZTX108 14p	2N4058 12p
BC212L 10p		2N5457 32p
BC214 10p		2N5458 30p
BC214L 10p		2N5459 32p
BC477 19p		2N5777 50p
BC478 19p		
BC479 19p		
BC548 10p		
BCY70 14p		

DIODES

1N914 3p	1N5401 13p
1N4001 4p	8ZY88ser 8p
Full spec product.	
1N4148 £1.40/100	£11/1000

LINEAR

THIS IS ONLY A SELECTION!

CA3140 38p	LM301AN 26p	NE555 21p
LM318N 85p	NE566 50p	NE565 85p
LM324 45p	NE567 170p	SN76003 200p
LM339 45p	SN76013 140p	SN76023 140p
709 28p	LM382 120p	SN76033 200p
741 16p	LM1830 150p	SN76477 220p
747 40p	LM3900 50p	TBA800 70p
748 30p	LM3909 65p	TDA1022 650p
CA3046 55p	MC1496 60p	ZN414 75p
CA3080 70p	MC1458 32p	
CA3130 90p		

CAPACITORS

TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68,	each
1 & 2 2uF @ 35V	8p
4.7, 6.8, 10uF @ 25V	13p
22 @ 16V, 47 @ 6V, 100 @ 3V	16p

MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047	3p
0.068, 0.1	4p

POLYESTER

Multigrad C280 series	
0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1	5p
0.15, 0.22	7p
0.33, 0.47	10p
0.68	14p
1.0uF	17p

CERAMIC

Plate type 50V. Available in E12 series from 22pF to 1000pF and E6 series from 1500pF to 0.047uF 2p

RADIAL LEAD ELECTROLYTIC

63v 0.47 1.0 2.2 4.7 10	5p
	7p
	13p
	20p
25v 10 22 33 47	5p
	8p
	10p
	15p
	23p

CONNECTORS

JACK PLUGS AND SOCKETS

2.5mm screened	unscreened	socket
9p	13p	7p
3.5mm 9p	14p	8p
Standard 16p	30p	15p
Stereo 23p	36p	18p

DIN PLUGS AND SOCKETS

plug	chassis socket	line socket
2pin 7p	7p	7p
3pin 11p	9p	14p
5pin 180° 11p	10p	14p
5pin 240° 13p	10p	16p

1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs 6p each Sockets 7p each.

4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs 11p each Sockets 12p each

PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p Double socket 10p

VERO

Size in.	0.1in.	0.15in.	Veropins
2.5 x 1	14p	13p	single sided
2.5 x 3.75	42p	40p	per 100
2.5 x 5	52p	50p	0.1in 35p
3.75 x 5	60p	60p	0.15in 40p
3.75 x 17	195p	180p	

BOXES



Aluminium boxes with lid and screws

	Length	width	height	
AL1	3	2	1	48p
AL2	4	3	1	58p
AL3	4	3	2	65p
AL4	6	4	2	70p
AL5	6	4	3	85p
AL6	8	6	2	116p

THYRISTORS

Plastic cased Thyristors Texas

	4A	8A	12A
100V	36p	45p	62p
200V	42p	53p	68p
400V	51p	66p	86p

TRIACS

Plastic cased Triacs. Texas. All rated at 400V.

4A 70p	12A 90p	20A 185p
8A 80p	16A 95p	25A 215p


CMOS

4001 12p	4026 90p	4069 12p
4002 12p	4027 30p	4071 12p
4007 12p	4028 48p	4081 13p
4011 12p	4029 50p	4093 45p
4013 28p	4040 60p	4510 65p
4015 50p	4042 50p	4511 65p
4016 30p	4046 90p	4518 65p
4017 48p	4049 25p	4520 60p

FULL DETAILS IN CATALOGUE!

SKTS

Low profile by Texas

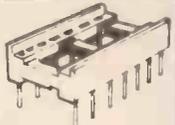

8 pin	8p	16 pin	11p	28 pin	22p
14 pin	10p	24 pin	18p	40 pin	32p

Soldercon pins: 100 50p. 1000 370p

OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	8p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Chips			3p	

DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series: 4.7 ohms to 10M. Any mix	
each	100+
0.25W 1p	0.9p 0.8p
0.5W 1.5p	1.2p 1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

METAL FILM RESISTORS

Very high stability, low noise rated at ¼W 1%. Available from 51ohms to 330k in E24 series. Any mix:

0.25W	each	100+	1000+
	4p	3.5p	3.2p

PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 64 PAGE CATALOGUE OF COMPONENTS. CONTAINS OVER 2500 STOCK ITEMS.




WHY NOT VISIT OUR

NEW SHOP

We welcome callers at our new premises at the address below (5 mins. from High St.) We are open Mon - Sat, 9am - 6pm. Special offers available.

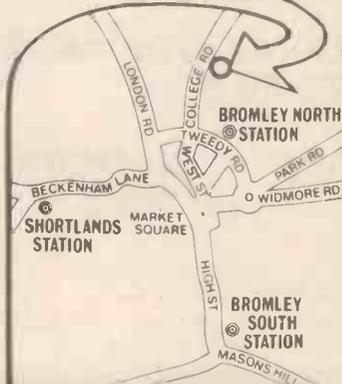Express telephone order service. Orders received before 5pm. are shipped first class on that day. Contact our Sales Office now! Tel: 01-464 2951/5770.



ORDERS DESPATCHED BY RETURN POST

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.

BARCLAYCARD & ACCESS WELCOME.



Mail orders to: STEVENSON (Dept HE)

76 College Road, Bromley, Kent, England

Electronic Music

In this second part of his article, Tim Orr continues to describe how musical notes and other effects are produced from electronic circuits.

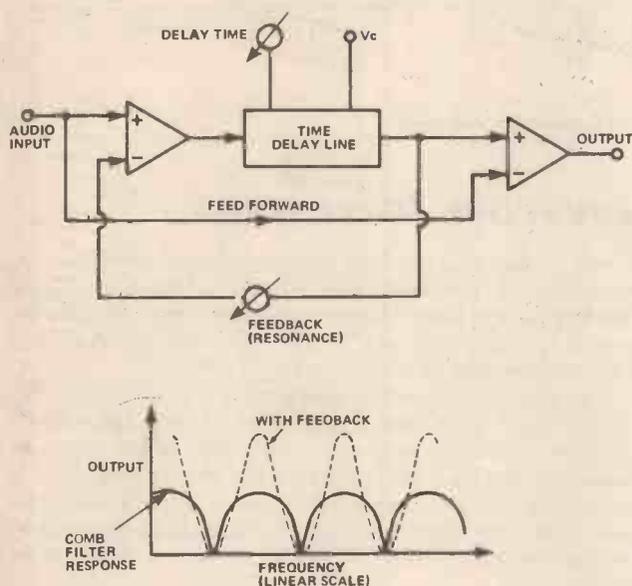


Fig. 9. A COMB filter described in part one

Contour generators produce the VCF sweep and the amplitude envelope of the waveform that comes out of the synthesiser. They are generally initiated and terminated by the gate voltage from the keyboard. Firstly the AD waveform. When the keyboard is pressed, it starts on an exponential charging curve which has an attack time constant determined by the setting of the ATTACK knob. When the keyboard is released the waveform discharges back to where it started from with a time constant set by the DECAY knob. This AD waveform is used to sweep the VCF and sometimes in simpler systems to generate an envelope waveform and even to modulate the VCO.

The ADSR is a similar process to that which occurs in some keyboard instruments. A note is played which then decays away with its natural time constant, but when the note is released the strings are damped and the note is muted. This system has three time constants, an initial attack, a decay and a release. The ADSR is able to synthesise these three time constant parameters, but it also has a sustain level control, thus enabling infinite sustain as long as a note is pressed.

In conventional stringed keyboard instruments time constants are proportional to pitch of the note, low frequency notes have long decay times and vice versa.

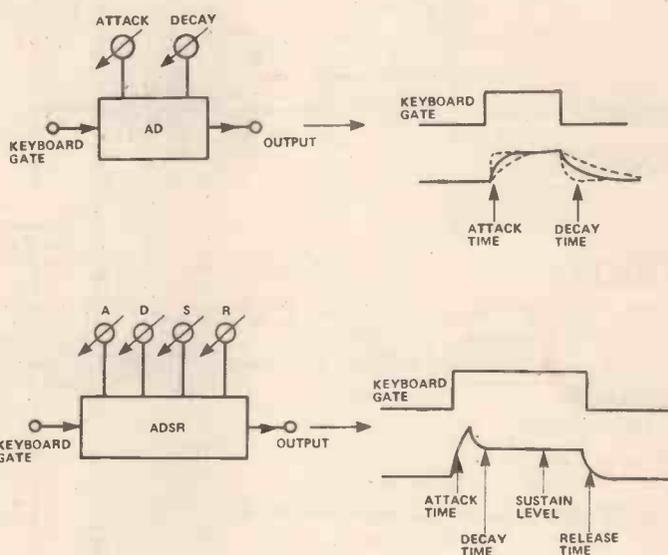


Fig. 10. Contour generators

Also the harder the keyboard is hit the louder the note (keyboard dynamics) and the sharper the harmonic structure. It is possible to synthesise all these effects but with the present state of the art it is still rather complex and expensive. Most synthesisers go for the simple solutions as shown in Fig. 10.

VOLTAGE CONTROLLED AMPLIFIER

The job of the VCA is to produce a signal which is the product of the audio signal times the contour signal. This type of unit is known as an amplitude modulator or a two quadrant multiplier. When the contour voltage returns to zero, the output of the VCA is zero.

Another type of modulator is a four quadrant multiplier some times known as a ring modulator. This has two inputs and produces an output which is the true arithmetic product of the inputs.

Ring modulators are typically used to manipulate natural sounds. If speech is used as one input and a low frequency (50-100 Hz) oscillator as the other, the ring-modulated output sounds rather mechanical, just like a 'Dalek'. What the ring modulator is doing is

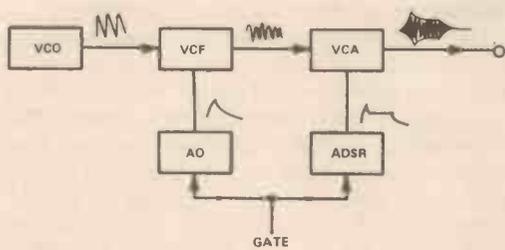


Fig. 11. Typical synthesiser structure

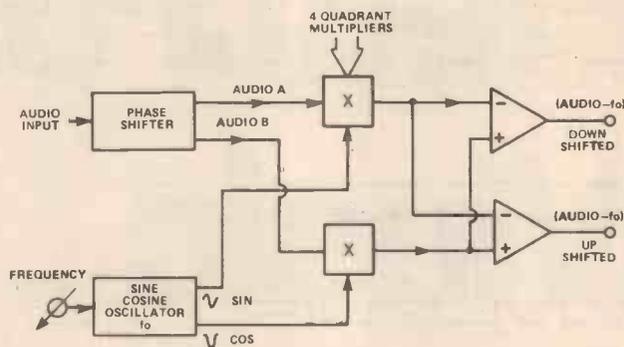


Fig. 13. Arrangement of a frequency shifter

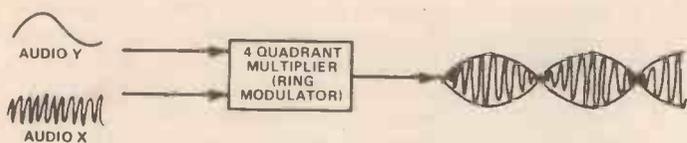
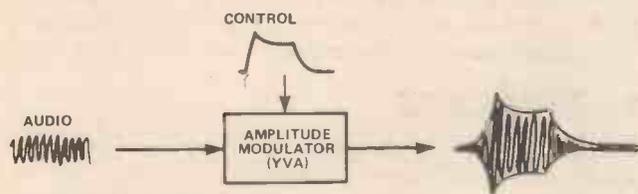


Fig. 12. Voltage controlled amplifiers (VCA)

producing two mixed outputs from the two inputs. If the two inputs were two sinewaves of frequencies f_x and f_y , then the output is made up of two sinewaves mixed together of frequencies $f(x+y)$ and $f(x-y)$. These are known as the upper and lower sidebands respectively.

FREQUENCY SHIFTER

A frequency shifter acts similarly to the ring modulator except that it separates the upper and lower sidebands. This enables a natural sound to be shifted up or down in frequency. The process is known as single sideband modulation in telecommunication jargon. The overall effect is to make a harmonic sound in-harmonic. This is because all the harmonics will be shifted by the same frequency increment and so will lose their integer relationships.

The frequency shifter uses an oscillator that generates sine and cosine waveforms. The audio signal to be processed is passed through a dual phase shifting network such that two outputs in phase quadrature (always 90° apart) are generated. The audio signals and the sinewaves are multiplied together by two ring modulators, the outputs of which are added and subtracted to produce the 'down' and 'up' shifted outputs. The amount of frequency shift is the frequency of the quadrature oscillator.

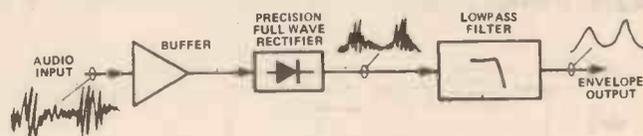


Fig. 14. Envelope follower

ENVELOPE FOLLOWERS

When processing natural signals, from speech or a guitar say, it is sometimes desirable to have a voltage that follows the envelope of the signal. This can then be used to control VCA's or VCF's or other devices. A simple envelope follower is shown in Fig. 14.

The input signal is full wave rectified by a precision rectifier and then lowpass filtered. There are lots of problems with this method. If the filter is set too high then there will be lots of ripple on the envelope output. If it is set too low, the unit will be slow to respond and may even miss short signals. Perhaps the best system would be one that uses a true RMS detector which can now be bought in an IC.

SPRING LINE REVERBERATION

Synthesised sounds can very rapidly become uninteresting. This is partly due to the unchanging quality of their sound. Listen to a sustained note on a flute or a single piano note. There are lots of interesting things going on all the time. The pitch might be wobbling (also the amplitude). The harmonic structure will be changing. There will be, in the case of the piano, sympathetic resonances in the neighbouring strings. One way of reintroducing interest into synthesised sounds is by use of artificial reverberation.

The spring line reverberation unit is a small mechanical device that finds use in electronic organs, practice amplifiers and synthesisers. The unit consists of two long (10 inch) springs connected together at each end. At one end there is an electromagnetic driver, and at the other a magnetic pick up. The input signal is amplified and drives the driver coil. This causes the springs to vibrate and these vibrations propagate down the length of the springs. The pick-up coil receives these vibrations, the signal from which is amplified and mixed with the original. The result is a reverberant quality to the sound output.

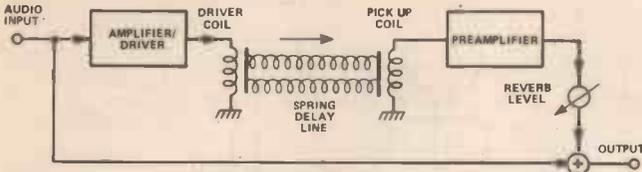


Fig. 15. Spring Line Reverberation

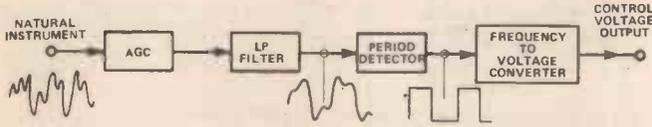


Fig. 16. A pitch extractor (above) and its place in a block diagram (below)

PITCH EXTRACTOR

Several companies have recently introduced guitar synthesisers. These are synthesisers that are controlled by the normal controls of the guitar. In these cases, the guitar has been greatly modified so that its strings and frets act as various forms of electronic contacts. Thus it is possible to control a synthesiser from a guitar. There is, however, another way of doing this and that is by using a pitch extractor. This uses an unmodified guitar and analyses the signal from the pick-up. It performs various electronic processes on the signal so that the fundamental note is extracted, which is then converted into a control voltage that can drive a bank of VCO's say. If an envelope follower and a VCA are used as well then a tracking chord with the amplitude envelope of the guitar signal can be synthesised.

The problems of pitch extraction are numerous and possibly will never be properly solved, but to date there are several devices on the market which work quite well.

SEQUENCERS

Sequencers are used to generate a repetitive rhythm or to memorise a relatively long passage of music. They do this by storing the control voltages necessary to resynthesise it. A digital sequencer memorises a musical melody that is 'played in' via a conventional keyboard. It remembers the pitch voltage and the gate signal as a function of time. Various controls such as 'record, play, stop, recirculate, transpose sequence', are usually available. One such machine, the EMS JKS, is shown below. Note that the keyboard is a 'touch' rather than a mechanical device.

An analogue sequencer is shown in Fig. 18. The sequence is programmed in on a series of pots. The electronics are usually very simple, a counter-decoder or a multiplexer is the usual solution. Also, as there is no keyboard, the parts costs are kept low, but it does suffer the problem of being more complicated to program.

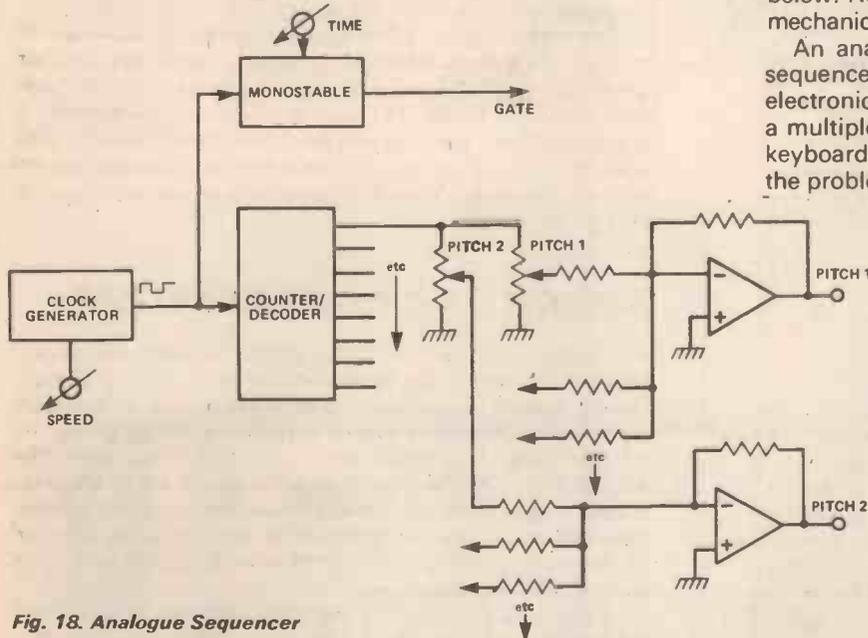


Fig. 18. Analogue Sequencer



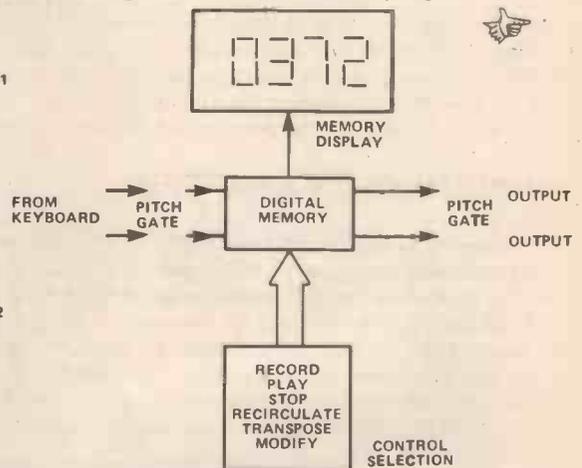


Fig. 17. Digital Sequencer

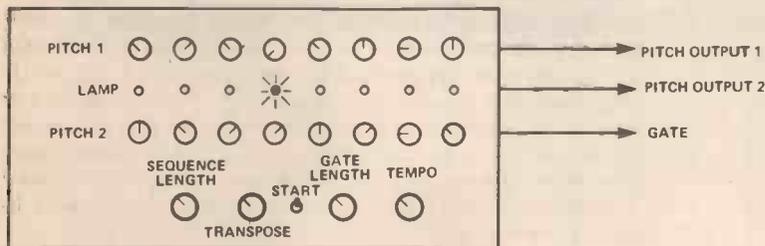

The EMS JKS Sequencer

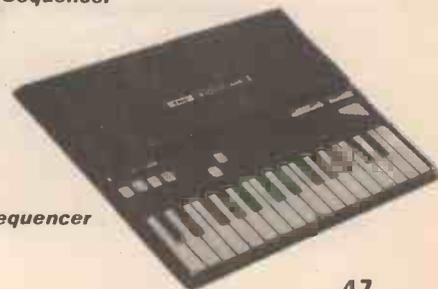

CHANNEL VOCODERS

The Vocoder is a recently introduced piece of EM equipment for processing speech and natural instruments. The concept of vocoders is quite old but it was not originally intended for anything other than telecommunications. The machine has two inputs, one for speech and one for excitation and one output. It analyses both inputs into lots of different frequency bands and then combines them into one output. This output has the articulation of speech and the line spectrum (the harmonic structure) of the excitation. If speech and an electric organ (excitation) are used, then the vocoded output is a 'talking organ'. The organ speaks and yet retains the sound structure and melody of the original organ. The vocoder can do other tricks like time compression and expansion, freezing sounds, changing peoples vocal characteristics. It can also operate on two instruments combining them to produce a new one. Fig. 20 shows a commercial unit.

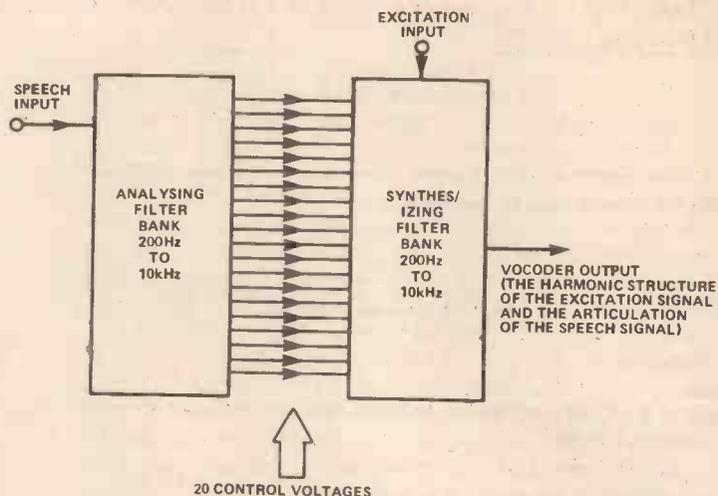


Fig. 19. 20-Channel Music Vocoder, a breakdown of one channel is shown in greater detail


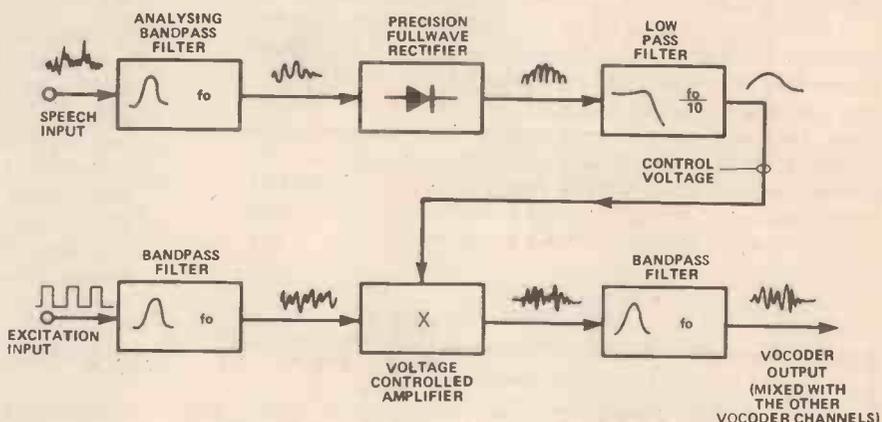


Fig. 20. The EMS Vocoder 2000

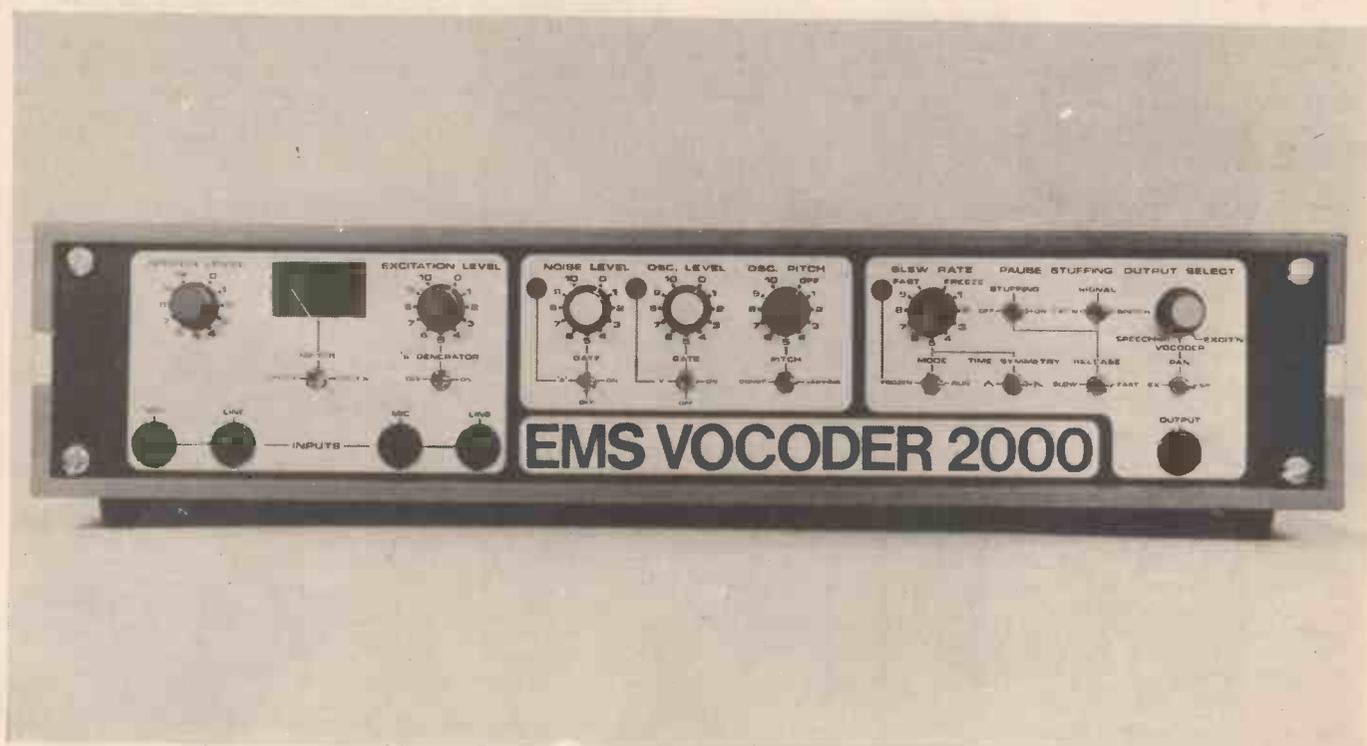

COMPUTER MANIPULATION AND SYNTHESIS

Originally EM was produced in studios and a lot of it was done by tape tricks. Synthesizers now produce most EM and some machines have a very high level of technology in their design. Computers have also produced EM for quite a while, but these have been large expensive installations. Using a computer it is possible to synthesise all the sounds or to use the computer as a sound processor. Apart from the computer there is no real hardware at all. All the processing is done using the computer program (the software). Natural sounds are introduced to the system via an ADC (analogue to digital converter) and sounds produced by the computer leave via a DAC (digital to analogue converter), Fig. 21. By using computer techniques it is possible to manipulate sounds in new and interesting ways. I heard one such manipulation whereby a piece of music performed on a saxophone gradually transmitted itself into a violin.

Perhaps as microprocessors get larger and faster we will see a growth in microprocessor EM peripherals.

Technology has got a firm grip on the music and EM industry, but the sounds generated are still almost totally dependent on the skills of the operator. To bear this out I can cite the following example. In the last few years I have designed seven synthesizers, two vocoders, six guitar effects units, one sequencer, one frequency shifter, two guitar amplifiers, one quadraphonics effects generator, a pair of high quality converters for computer music . . . and I still can't make any music! **HE**


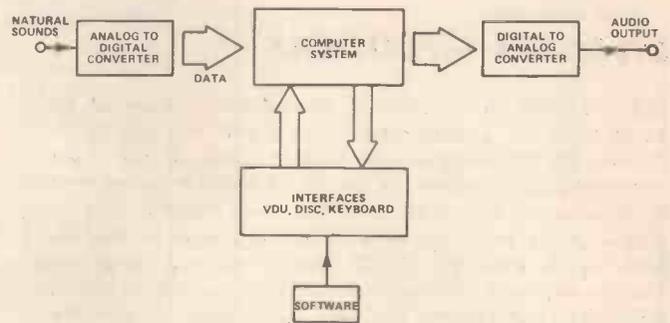


Fig. 21. Computer manipulation and synthesis block diagram with a commercial unit shown below

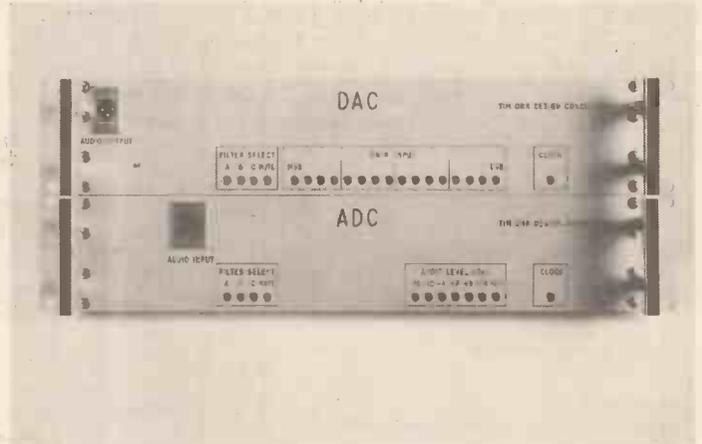

Short Circuit

A. F. MILLIVOLT METER

This simple and inexpensive millivolt meter has three measuring ranges of 10mV., 100mV., and 1 V. RMS full scale sensitivity. The frequency response has -1dB. points at about 20Hz and 75kHz. The instrument is suitable for making audio noise, frequency response, and gain measurements, and would be useful to any beginner interested in the field of audio.

The unit uses a conventional arrangement with a non-inverting op. amp. circuit feeding a meter via a bridge rectifier. The negative feedback loop is taken to the inverting input by way of the rectifier and meter circuit rather than direct from IC1 output. With low voltages applied to the rectifiers they have a high forward resistance, but this results in little feedback and the amplifier having a high level of gain. Thus small input signal amplitudes which would otherwise produce no meter deflection due to the high rectifier resistance are boosted to the point where they give the appropriate meter reading. Therefore, although the rectifier is inherently non-linear, it produces opposing non-linear feedback


which compensates for this and gives the unit linear scaling. RV1 is used to adjust the circuit to the correct sensitivity and D5 protects the meter against severe overloads.

Q1 is used as a low noise source follower buffer amplifier which gives the circuit a high input impedance of about 1 Meg. This ensures that the instrument

imposes little loading on the equipment under test. An attenuator is incorporated at the output of the buffer stage, and this can be used to reduce the basic 10 mV. sensitivity to 100 mV. or 1 V. FSD. The attenuator does not need any low impedance part of the circuit.

To calibrate the unit it is

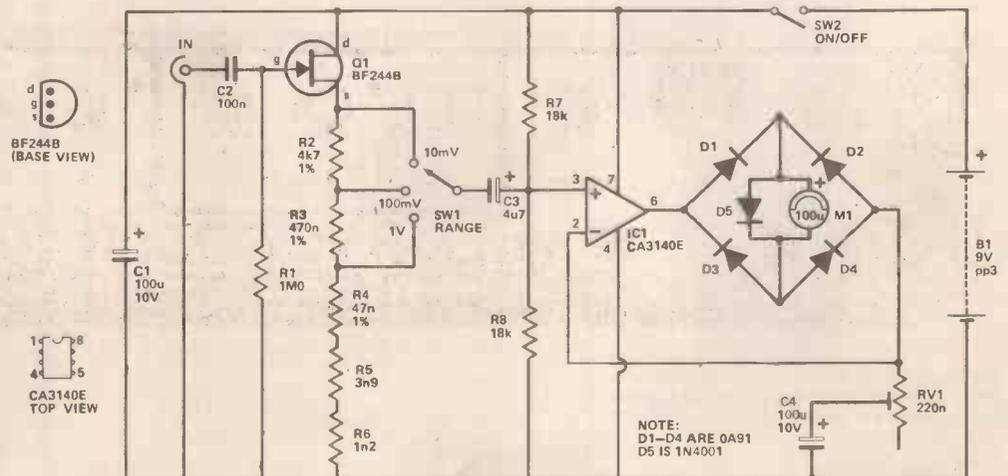switched to the 1 V. range, RV1 is set at maximum resistance, and with a 1 V. RMS audio source connected to the input, RV1 is adjusted for full scale deflection of the meter. The 1 V. audio source can be provided by an AF signal generator set to the correct output level with the aid of a multimeter switched to a low AC volts range.



DIGITAL DEVICES LTD

RETAIL DIVISION (G6GHZ)

TTL	CMOS	LINEARS	
7400 12p	4001 14p	723 43p	
7401 12p	4011 14p	741 27p	
7402 15p	4013 30p	NE555 35p	
7404 13p	4015 55p	TCA940 10w 24v	
7405 13p	4017 53p	Audio IC Normally	
7408 13p	4020 55p	£1.75. While stocks	
7413 23p	4023 14p	last 99p or TWO for	
7432 20p	4025 14p	£1.75	
7440 13p	4026 115p		
7442 40p	4027 33p	ZENERS	
7445 65p	4028 45p	Motorola 1/2 watt in	
7447 50p	4030 33p	2v7, 4v3 & 5v6 only	
7473 23p	4040 60p	7p each, 55p per 10,	
7474 23p	4049 25p	£5 per 100, any mix	
7475 30p	4050 27p	BZY 88's 7p	
7486 23p	4051 55p	Series 2v7, 3v, 3v3,	
7490 30p	4060 95p	3v6, 3v9, 4v3, 4v7,	
7493 37p	4066 35p	5v6, 6v8, 7v5, 9v1,	
7496 55p	4069 15p	10v, 12v, 15v, 16v,	
74121 28p	4093 50p	18v, 20v, 22v, 24v,	
74122 45p		27v, 30v & 33v.	
74123 40p		Zener Development	
74132 45p	DIODES	Packs:	
74151 45p	1N4002 4p	No 1.1 off each of the	
74161 65p	1N4003 5p	above values — 22	
74191 70p		diodes £1.30	
74196 60p		No 2.1 off each of the	
		above plus 4 more of	
		5v6, 9v1, 10v & 12v	
		(Popular values) 38	
		diodes for £2.00.	

Terms of Business: Cash / cheque with order or Access / Barclaycard. If using credit card merely state card number VAT. Please add VAT at 8% to the total of the order. P&P 25p per order up to £5, thereafter post free.

Delivery: Normally by return.

Devices all brand new full spec. by famous manufacturers.

CMOS usually B Series. VAT number 211 2679 92. Remember: Freepost address — NO STAMP REQUIRED ON YOUR ORDER.

FREEPOST
TOWCESTER, NORTHANTS, NN12 7BR

TEE-HE!



Join the He-men by sporting our cotton Tee-shirts. They're available in Large, Medium and Small, please specify which when ordering. All inclusive price is £2.00 from:

HE Tee-Shirts,
Hobby Electronics,
25-27 Oxford Street,
London W1R 1RF.

50

The world's smallest
programmables can be
music to your ears

CASIO FX-501P and FX-502P

POCKET-SIZED PROGRAMMABLE CALCULATORS, WITH MAGNETIC TAPE CASSETTE RECORDING ABILITY, that converts to musical synthesizers!



World's first LCD pocket-sized complete scientific programmable. Both use ALGEBRAIC operating system. The FX-501P offers 128 steps and 11 memories. The FX-502P offers 256 steps with 22 memories. Both have Automatic Power Off after approximately 14 minutes non-use, with the programme stored in the 11 or 22 non-volatile registers. Dimensions of both are: 9.6mmH x 71.1W x 141.2mmD (3/8"H x 2 3/4"W x 5 1/2"D). Supplied with leatherette wallet.

Optional FA-1 Programme Adaptor available for either model — permits programmes to be recorded on standard tape cassette recorders and stored for re-entry later. Also contains a music switch which converts both calculators into musical synthesizers — keys 1 through 8 contain pre-programming for a full musical octave.

FX-501P RRP £59.95 Our price £49.95
FX-502P RRP £79.95 Our price £69.95
FA-1 RRP £25.95 Our price £19.95

Other CASIO LCD scientific from £14.95.

NEW THE AMAZING MELODY 80
Musical calculating diary watch.



ADVANCE SPECIFICATION: Two separate Alarm Tunes, Calculator with keys 1-8, playing individual notes — a mini synthesizer! Complete calendar watch, stopwatch — measuring net and lap times to 1/10 second — alarm timer and calculator with % $\frac{1}{100}$, full memory, date calculations. CASIO RRP £31.95, £25.95.

Other CASIO calculating diary alarm watches
AQ-2000 £24.95, MQ-10 £35.95, MQ-11 £29.95.

★ THIS YEAR'S STAR BUY CASIO 46CS-29B (New model)

Almost certainly the slimmest and most sophisticated ALARM CHRONOGRAPH available today.



- LC Display of hours, minutes, seconds day; And with day, date, month and year.
- Optional 12 hour with am/pm or 24 hour clock display.
- 24 hour alarm setting.
- Optional hourly chimes
- Chrono measures from 1/100 second to 6 hours.
- Net lap, 1st & 2nd place.
- 7.8mm stainless steel case
- Real mineral glass face
- Water resistant to 100 feet.
- Less than ± 10 seconds per month.
- Removable links in bracelet, backlight.

£39.95

Other CASIO multi-functional watches from £19.95.

UNBEATABLE QUALITY AND VALUE FOR MONEY FROM JAPAN — WHY SETTLE FOR LESS?

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of watches or calculators (both on request).

Prices includes VAT, P&P. Send cheque, P.O. or phone your ACCESS or BARCLAYCARD number to:

TIMETRON

Dept. ETI, Beaumont Suite
164-167 East Road
Cambridge CB1 1DB
Telephone 0223 67503

Callers welcome by appointment

Car Audio

Manual
MW/LW



Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

£9.95 + £1.00 Post

Push-Button
MW/LW



One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

£15.60 + £1.00 Post

Stereo FM/
Cassette
+ MW



Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

£38.95 + £1.00 Post

Stereo Speaker Set

Suitable for above stereo unit. Good quality in surface mounted casing. 5W nominal, 8W peak.

£3.95 (pair) + 70p Post

Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

£1.60 + 30p Post

Metal Detectors

Treasure Tracer Mk III

The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive, stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit: £17.50 + £1.00 Post
Built: £22.50 + £1.00 Post



★ **Induction Balance Model**

Built with sensitivity up to 10in on single coin; fitted with speaker and meter; PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

£22.95 + £1.00 Post



All goods guaranteed one year. 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for leaflet.

Minikits Electronics Ltd.

6H Cleveland Road
S. Woodford
London E18 2AN

Hobby Electronics, June 1979

Kit Review

Bio Activity Translator

Do you ever wonder what your plants are thinking? This month's kit review will enable your shrubs to sing, its surprising how melodic they can be.

HAVE YOU EVER wondered what your plants would say if they could talk? If you have a clear conscience (when did you last water them?), then this unit will give them a voice. With the aid of the Bio Activity Translator your plants won't talk to you, but they will *sing*. The Translator combines a biological amplifier and a sound synthesiser in one instrument.

WHY...

The assembly instructions include a brief explanation of the principle of the system. Ionic differences across cell membranes produce a bioelectric potential. Thus, all plants generate small electric potentials naturally, directly related to respiration, photosynthesis, and other chemical reactions which are all part of the plant's metabolism. The Bio Activity Translator produces an audio analogue of the plant's response to its surroundings.

... AND HOW

The natural potential of the plant is amplified and used to increase the gain of a voltage controlled amplifier and turn on a pulse generator. The pulse generator, in turn, triggers a sample and hold circuit. A pulse is also applied



The kit as it comes out of its box, everything is there, only batteries are needed to complete the kit.

to an envelope network to provide extra attack on the sound. The sample and hold network provides a stepped control voltage which follows the biological signal to a voltage controlled oscillator. Thus, the pitch produced is proportional to the level of the biological signal. The rate



The finished product, and very professional it looks too, output sockets are provided in the rear of the case to feed into your hi-fi system.

of change of the biological signal affects the period of the pulse generator and the gain of the voltage controlled amplifier, so that the pitch, speed and volume of the notes produced are all controlled by the biological signal.

CONSTRUCTION

Everything you need to complete the kit (except your trusty soldering iron, solder and screwdriver, of course) is included. Construction is simplified by the clearly marked printed circuit board. Component outlines and numbers are printed on the board, so all you have to do is pick out the right component from the pack and plug it in. We were a little puzzled with where to fix the battery retaining clips. The assembly instructions didn't help us there. However, we found that they screwed directly into the wooden end cheeks of the attractive case.

OPERATION


Calibration couldn't be simpler, involving the adjustment of one preset potentiometer in conjunction with the front panel gain control. The signal is collected by two electrodes with an earth probe to minimise the effects of static electricity. The two electrodes are attached to a clip so that they can be clamped on each side of a leaf or stalk. The earth probe is pushed into the soil.

If you connect your Translator to your favourite Monstera or Rubber Plant and switch on, you will hear a complex pattern of sound, controlled by the plant itself. The sound produced seems to vary from plant to plant and whether the room is light or dark. The system is very sensitive to movement. Shaking the plant produces a dramatic response. We found that outdoor plants made the most satisfactory subjects.


There seems to be unlimited room for experimentation here. The manufacturer has fitted two output sockets on the back of the unit, so that the output can be fed to another amplifier or an analyser of some sort. Try clipping the electrodes to your finger to produce a musical pulse.

The Bio Activity Translator is available from Jeremy Lord Synthesisers, 52 Becmead Avenue, London SW16 and costs from £18.95.

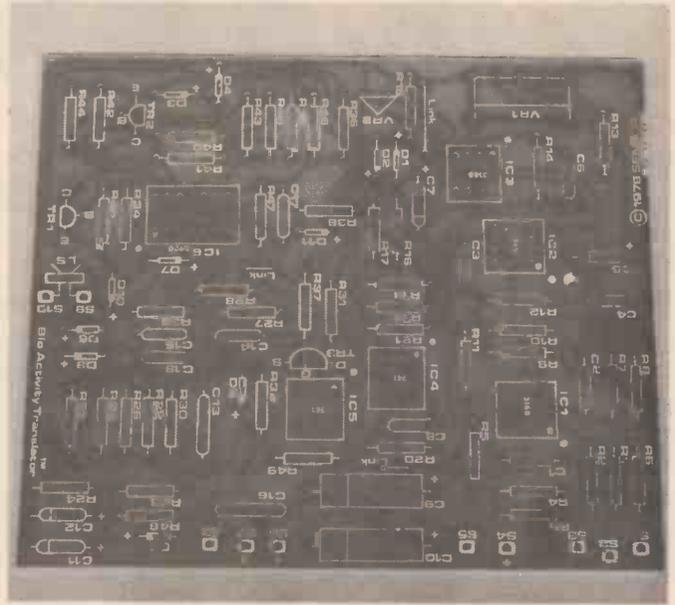The components in their packs, do check for any omissions.



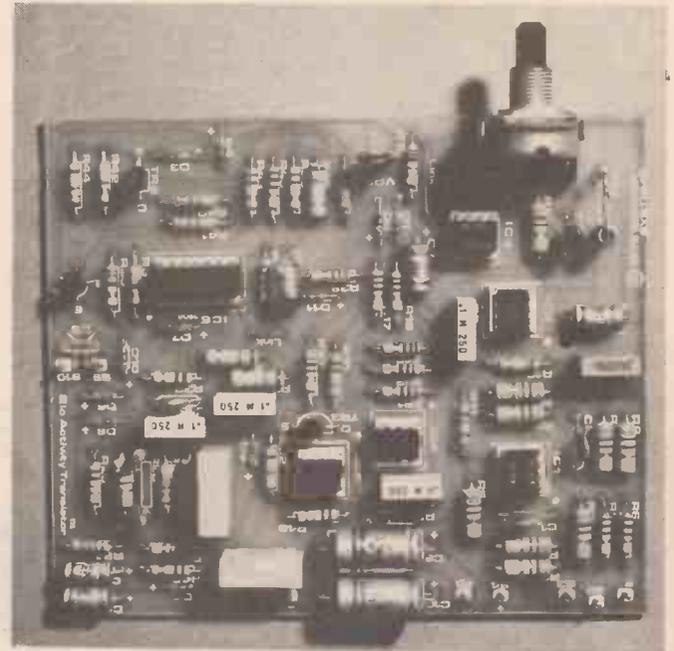The PCB, assembly is simple, just follow the markings.



The PCB assembled awaiting installation.



The front panel of the Bio-Activity Translator.

New Books from the HE Book Service

28 Tested Transistor Project £1.15
Richard Torrens. The projects can be split down into simple building blocks which can be recombined for ideas of your own.

Electronic Projects for Beginners £1.55
F. G. Rayer. Divided into 'No Soldering Projects,' Radio and Audio Frequency, Power Supplies and Miscellaneous.

Solid State Short Wave Receivers for Beginners £1.15
R. A. Penfold. Several modern circuits which give a high level of performance even though only a few inexpensive components are used.

Popular Electronic Projects £1.65
R. A. Penfold. A collection of the most popular types of circuits and projects using modern, inexpensive and freely available components.



Digital IC Equivalents and Pin Connections £2.70
Adrian Michaels. Covers most popular types and gives details of packaging, families, functions, country of origin and manufacturer.

How to Build your own Metal and Treasure Locators £1.20
F. G. Rayer. Gives complete circuit and practical details for a number of simple metal locators using the BFO principle.

Linear IC Equivalents and Pin Connections £2.95
Adrian Michaels. Gives most essential data for popular devices.

Projects in Opto Electronics £1.45
R. A. Penfold. Covers projects using LED's, Infra-red transmitters and detectors, modulated light transmission and also photographic projects.

52 Projects using IC 741 £1.15
Rudi and Uwe Redmet. Translated from an enormously successful German book with copious notes, data and circuitry.

50 FET (Field Effect Transistor) Project £1.45
F. G. Rayer. Contains something of interest for every class of enthusiast. Short Wave Listener, Radio Amateur, Experimenter or audio devotee.

How to Build Advanced Short Wave Receivers £1.40
R. A. Penfold. Full constructional details are given for a number of receivers plus circuits for add-ons such as Q-Multiplier, S-meter etc.

Essential Theory for the Electronics Hobbyist £1.45
G. T. Rubaroe gives the hobbyist a background knowledge tailored to meet his specific needs.

Beginners Guide to Building Electronic Projects . £1.45
R. A. Penfold. Covers component identification, tools, soldering, constructional methods and examples of simple projects are given.

50 Projects using IC CA3130 £1.15
R. A. Penfold. Describes audio projects, RF project, Test Equipment, Household and miscellaneous circuits.

IC 555 Project £1.65
E. A. Parr. Circuits are given for the car, model railways, alarms and noise makers. Also covers the related devices 556, 558 and 559.

50 Projects using Relays, SCR's and TRIAC's £1.30
F. G. Rayer. Gives tried and tested circuits for a whole variety of projects using these devices.

Note that all prices include postage and packing. Please make cheques etc. payable to Hobby Electronics Book Service (in Sterling only please) and send to:

Hobby Electronics Book Service
P.O. Box 79
Maidenhead, Berks.

Short Circuit

BASIC BURGLAR ALARM

A burglar alarm circuit can be very simple if non-essential facilities such as entry and exit delays are omitted, and such a circuit is shown here. It can be used in conjunction with normally open (NO) or normally closed (NC) contacts which can be the usual door and window switches, trigger mats, etc.


SCR 1 is a silicon controlled switch (SCS) which is an NPN/PNP integrated pair of transistors connected to form a highly sensitive thyristor. As the circuit stands, R1 ties the CK terminal to the negative supply and prevents SCR 1 from triggering. The relay will not be energised and the alarm will not sound. If one or more of the NC contacts should open, SCR 1 will be switched on by the gate current it receives through R2, since R1 is then switched out of circuit. Even if the contacts should close again, SCR 1 will remain in the on state because it has a built-in latching action. Thus the relay will be activated and its contacts connect power to the alarm generator. The circuit can also be triggered by one or more of the NO contacts closing, as R3 then provides an adequate gate

bias to switch on SCR 1. Once triggered the circuit can only be reset by switching off using SW1. The current through SCR 1 then falls to zero and the latching action is defeated so that the circuit is ready to commence operation once again when SW1 is closed. Although only two sets of NC contacts are shown, any number of

contacts connected in series can be used. Similarly, any number of NO contacts connected in parallel can be utilized. If no NC contacts are used, R1 should still be included between the GK terminal of SCR 1 and the negative supply rail. C1, C2, and R4 are needed to prevent spurious operation due to stray pick-up of noise spikes or noise

pulses on the supply lines. D1 is a protective diode which suppresses the high back EMF developed across the relay coil as it de-energises.

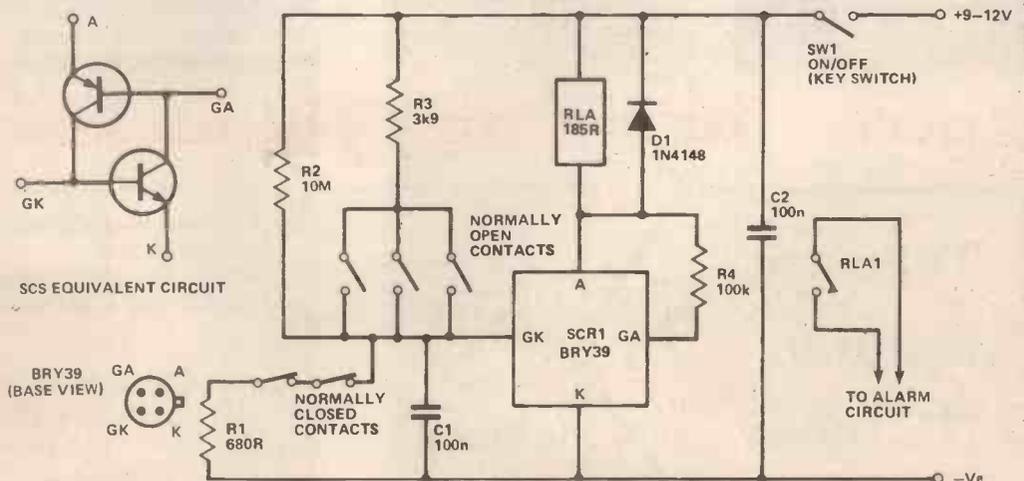The standby current consumption of the unit is only about 1uA and so the unit can be economically run from ordinary dry cell batteries if desired.



Into Electronics Plus


*Ian Sinclair has finished his tale,
So 'Into Electronics Plus' is now on sale,
The cream of Hobby, plus Mr Sinclair,
We modestly believe an unbeatable pair,
The pound you send will be well spent,
(That's apart from paying our rent),
You'll get 'Capacitors', 'Computers', and 'PCBs',
Not at all bad for just one hundred pees.*

The demon HE poet strikes again, he sat up half the night writing this one. (Don't know why he bothered). Seriously though folks Ian Sinclair's series proved such an astounding success we decided to bring it out as a book. Not only that but we've added over twenty more pages of informative features from 'Audio Transducers', and how to make your own PCB's. That's 100 pages for a Pound, a penny a page.

The series was primarily aimed at people taking O/A level courses in electronics but has proved to be just as popular with people starting out in our fascinating hobby.

For your copy just send £1.25 (that includes Post, Packing) to:-

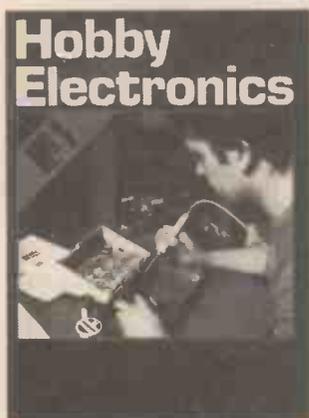'INTO ELECTRONICS PLUS'
HOBBY ELECTRONICS,
25-27 OXFORD STREET,
LONDON, W1R 1RF.



Are you missing out on something?

Take out
a sub to
HE today

To: Subscriptions
Hobby Electronics
P.O. Box 35
Bridge Street,
Hemel Hempstead,
Herts

I would like a postal subscription to HE starting with the issue. I enclose payment (£6.50 for UK and Eire, £7.50 elsewhere, £11.50 air mail).

Name

Address

Into Electronics

by Ian Sinclair

Part 8

Goggle-boxes, fighter-finders and number-crunchers. Ian Sinclair concludes his interesting and instructive guide to the sometimes daunting field of Electronics, and proves it really is easy.

IN THE EARLY days of radio, the problem of transmitters interfering with each other was not serious; there weren't enough of them, and they all had pretty low power outputs. Later on, with many more transmitters in use, the problem seemed to be solved by making each transmitter work at a different frequency — after all, there's a lot of different frequencies to play with. This wasn't enough, though, and here's why.

We can generate a carrier wave of almost any frequency we like, using an oscillator and a set of frequency multipliers. A carrier is a pure sine-wave, which has a single frequency, so that we could have an enormous number of carriers, perhaps one at every 500 Hz all the way from 100 kHz upwards. The trouble is that a carrier by itself is rather useless, and to carry information, audio or otherwise, it must be modulated. Now a modulated carrier is quite another thing, because it no longer has the shape of a simple single sine-wave. If we use a very selective receiver to measure the amplitude of each frequency that is present in a modulated carrier, we find that there are now frequencies present which are neither carrier frequency nor audio frequency — it's the familiar old story of the mixer again. These new frequencies are called *sidebands* and there will be two of them. The upper sideband is at the frequency which is the carrier frequency plus modulation frequency, and the lower sideband is at a frequency which is carrier frequency minus modulation frequency. For example, if we modulate a 1 MHz carrier with a 10 kHz sinewave, we find that the complete modulated signal consists of three frequencies, the carrier at 1 MHz, the lower sideband at 990 kHz, and the upper sideband at 1.010 MHz.

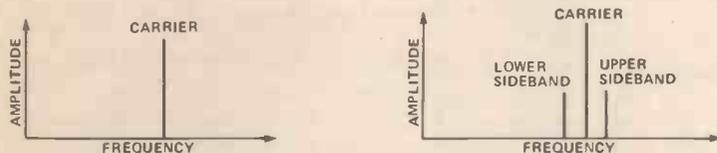


Fig 8.1 An unmodulated carrier is a sinewave. On a graph of amplitude plotted against frequency (a) it appears as a single line. A modulated carrier plotted in the same way (b) shows sidebands.

If the modulating signal is not a single sinewave but a mixture of frequencies such as we get with speech and music, then the sidebands will also consist of a mixture of frequencies on each side of the carrier. It's these sidebands which decide how many transmitters we can use in a given range of frequencies, because transmitters will interfere with each other if their sidebands overlap (Fig. 8.2) even though their carriers are spaced well apart. The bandwidth, which is the range of frequencies from the carrier to the end of one sideband, is the important factor that decides how transmitter frequencies can be allocated.

SIDETRACKED

The problem of these sidebands and the bandwidth that each transmission takes up has occupied many engineers for many years. For various reasons, the range of frequencies that we call the medium waveband has been the most useful for broadcasting — the reasons include transmitter range and ease of reception. The result is that every country in the world wants to transmit on the medium waveband, but the sad fact is that there simply isn't enough room.

Various international conferences have tried to allocate frequencies spaced 10 kHz apart (so that sidebands above 5 kHz cannot be used) fairly among the nations, trying to ensure that transmitters working on closely spaced frequencies were large distances apart. These schemes could have worked but for the rogue — countries which choose to ignore the frequencies allocated to them, and, of course, the pirate radios who find a fair bit of profit in ruining other people's reception. All of this


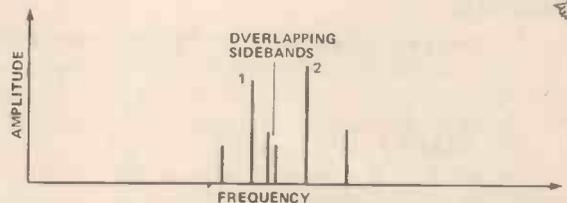


Fig. 8.2 The sidebands of two transmitters can overlap causing interference.

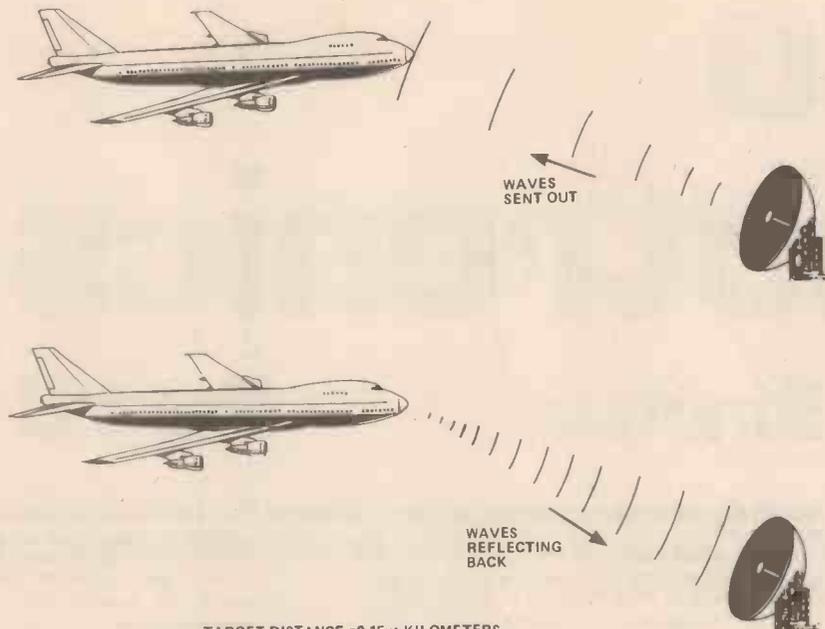

TARGET DISTANCE = 0.15xt KILOMETERS
 t IS THE TIME IN MICROSECONDS BETWEEN
 SENDING OUT A PULSE OF WAVES AND
 RECEIVING THE SAME PULSE BACK AGAIN

Fig 8.3 Principle of radar.

has now made the medium waveband unsuitable for serious broadcasting.

HIGH FREQUENCY

High quality transmission needs the transmission of audio frequencies up to about 14 kHz; radar and TV need much greater bandwidths than this (TV, for example needs about 6 MHz) so that the medium waves are totally unsuitable for such purposes. This is the reason for the extensive use now of the high frequencies, around 90 MHz for high quality sound transmissions, 450 to 800 MHz for colour TV, and 10 000 MHz or more for radar. There's lots more room up there. For example, the bit of the VHF band that we use for stereo broadcasting is ten times the range of frequencies that we have on the whole of the medium waveband.

As a useful bonus, the range of transmitters is not so great, so interference is much less of a problem. Another great advantage of using these frequencies is that we can make use of different methods of modulation, such as frequency modulation, which need greater bandwidth. For example, the FM stereo broadcasts that we transmit in this country need a bandwidth of 220 kHz, even though the audio bandwidth is only 14 kHz; at higher frequencies we can use power-saving methods like pulse modulation.

BOUNCING THE BEAM RADAR

Radar, as anyone will tell you, consists of bouncing radio waves from a target and finding how long it takes for the reflected signal to return. It's like moonwalking — easy if you happen to have all the equipment, but you have to be able to build the equipment first.

The first bit of equipment you need for a radar transmitter is an oscillator which will generate a carrier with a frequency of 1000 MHz or more, preferably up in the 10000 MHz region. Why such a high frequency? One reason, of course, is that there's plenty room for bandwidth, but there are more pressing reasons.

All radio waves travel at the same speed of 3×10^8 m/s (three hundred million metres per second), but the wavelength, the distance from one peak of a wave to the next while in flight is equal to speed divided by frequency. Like all other waves, radio waves will reflect well only from objects which are several times the size of a radio wavelength (ever heard of diffraction?) The wavelength of a 1000 MHz wave (sometimes called 1 GHz, one Gigahertz) is 300 mm, which is just about small enough to bounce from the front of a large aircraft or a medium-sized ship, though we might not get much reflection from a slim fighter. If we want to obtain good reflections from smaller objects, or to be able to distinguish more detail of a larger one (to have better resolution, as we say) then we need to use waves of shorter wavelength, a few centimetres or even millimetres, and that means much higher frequencies.

THE LONG AND SHORT OF IT

Radar requirement number one, therefore, is a generator of high frequency waves, preferably one that can churn out a lot of power, because only a tiny fraction of all the power that is sent out will ever return, even under the most favourable circumstances (Fig. 8.4). The wave generator that's used for all the larger radar transmitters is a device called the magnetron, which spins electrons round at very high speeds past a tuned circuit which consists of a hole in a piece of metal (called a cavity, which sounds uncomfortably like something dental). Magnetrons that are used for most radar purposes do not oscillate continuously, but are turned on and off in short pulses.

The short pulse is the next requirement. If we are to be able to detect the faint reflected wave from a distant object, we will ruin our chances if the transmitter is still belting out thousands of watts. In addition, because we want to measure the time that passes between sending out a pulse and detecting the echo, we need to use a short pulse so that we can measure the time more precisely (Fig. 8.5).

Using a short pulse has another advantage. Magne-

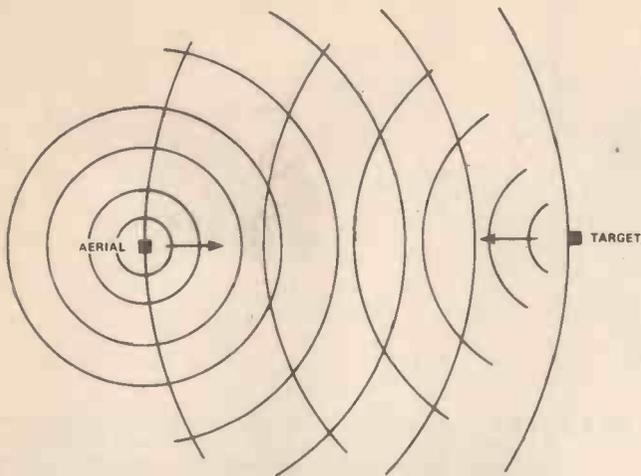


Fig 8.4 The wave sent out by the transmitter spreads out, and only a tiny fraction of it strikes the target. The reflected wave from the target also spreads out, and only a tiny fraction of it strikes the receiver aerial. In practice the ratio is not as bad as it looks, because the transmitted wave can be focused to some extent into a beam.

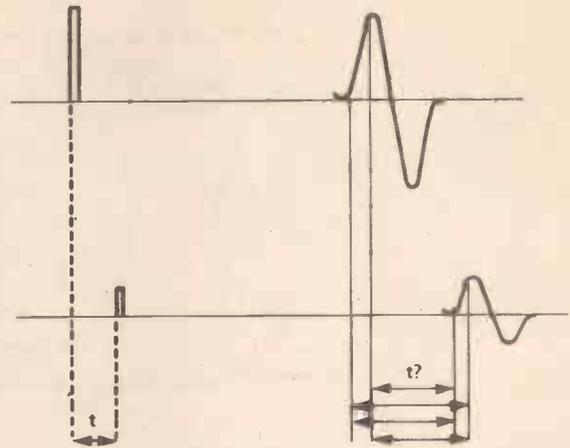


Fig 8.5 The advantage of using a pulse. We can easily measure the time between pulses, counting microseconds between the steep sides. (a) (b) A sine wave is useless for this because we cannot be certain where to start or stop the time measurement.

trons, like all other active devices, have to dissipate heat, using water cooling or forced air cooling. The amount of heat that has to be dissipated depends on the average power that is dissipated and that's the advantage of the short pulse. For example, if we have a magnetron which will dissipate 5 kW continuously, and we switch it on for 10 uS in every millisecond, then the power that can be handled for that 10 uS can be $5 \times \frac{1000}{10} = 500\text{kW}$. Now a short pulse of 500 kW is much more effective from the range point of view than a steady wave at 5 kW, so that the use of pulses enables us to obtain a much greater range than would otherwise be possible.

THE WERE ARE YOU NOW SPOT

Fig. 8.6 shows a block diagram of a radar transmitter. An astable generates synchronising pulses, usually at around 1 kHz. A monostable then generates a short pulse which is used to start off all the action. One piece

of action that is started off is a high voltage pulse generator which, when the trigger pulse arrives, switches the magnetron on and off. During the time of this pulse, the magnetron is oscillating with a very high power output, so that the transmitting aerial is sending out microwaves like mad.

The trigger pulse also starts the timing operation, usually by starting the sweep on a CRT. Some time, a long time in terms of microseconds, after the magnetron has stopped oscillating, the reflected pulse returns. It is then picked up on the aerial, amplified in a superhet receiver (we did say that they had a lot of uses) and used to brighten up the CRT display (what part of the CRT is used for this, do you think?), so that a blob of light appears. Because the sweep voltage has been deflecting the CRT, the blob will appear some distance away from the start of the sweep — and this distance is proportional to the range of the target.

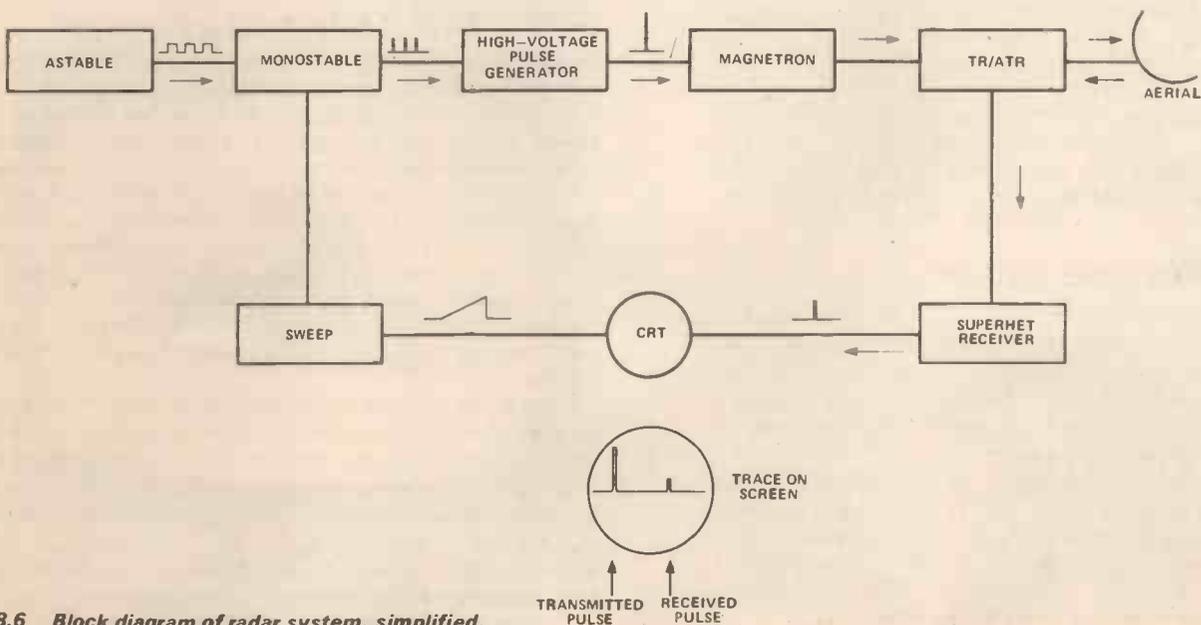


Fig 8.6 Block diagram of radar system, simplified.

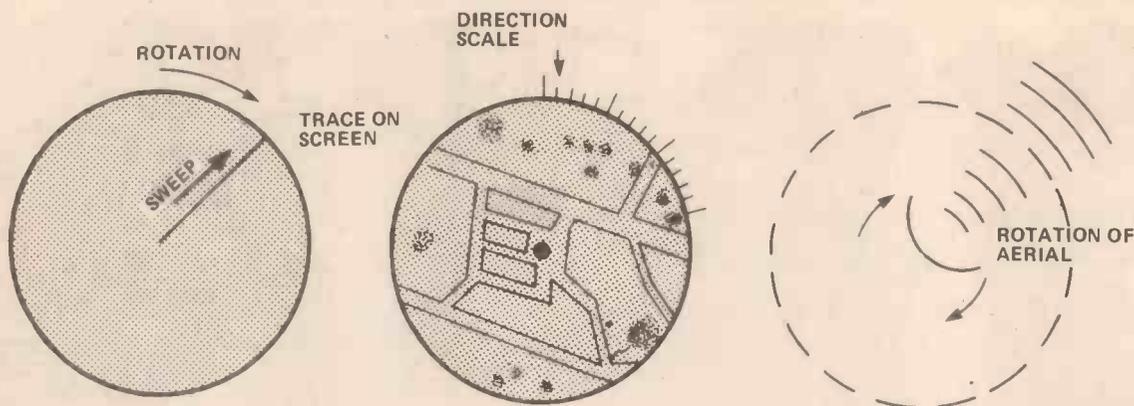


Fig 8.7 PPI Trace (a) direction and rotation of sweep on screen (b) rotation of aerial in step with rotation of sweep (c) typical trace, showing transmitter at centre and the surroundings, with stationary objects and moving targets. A long persistence tube is used, so that the targets leave trails to indicate their movement.

Want a bit more detail? Well, both receiver and transmitter use the same aerial, with protection circuits to ensure that the high power transmitter pulse does not get into the receiver circuits and that the weak returning pulse does not get lost in the transmitter circuits. The devices used for this job are called TR and ATR cells, life's too short right now to deal with how they work.

A PLAN FOR THE FUTURE

The type of display that's used for most radar receivers is the PPI, Plan Position Indicator. In this type of system, the CRT sweep starts from the centre of the screen each time, and moves out to the edge. The aerial rotates, and its rotation is synchronised to the timebase action so that the direction of the sweep is linked to the direction of the aerial. In this way, during one rotation of the aerial, the radar sweeps the skies right around the transmitting station, and the CRT display shows the transmitter as a spot at the centre of the screen, with the targets as blobs of light. The distance from the centre of the CRT to any target measures the range of that target, and the direction is indicated on the scale of degrees around the edge of the CRT (Fig. 8.7). A lot of modern radar sets also use a 'nodding' aerial to measure the height of targets, and the two lots of information are fed into a computer, so that the final display can show figures of height and speed beside each target blob.

Pulse PPI radar is just one widely-used form of radar, and we could fill a book or more on the details of this and others, such as FM rangefinder radar, Doppler speed radar and others. All we can do here is to refer the interested reader to books that specialise in this important branch of electronics. Unfortunately, the books your neighbourhood library may have in stock will probably have been written twenty years ago, or even more.

VISION ON

Let's scratch briefly at the surface of another topic, television. The problem here is how to convert a picture into a waveform. Sound broadcasting is easy by comparison; the transducer simply has to convert the sound waves into electrical waves at the same frequency. Light waves are already electrical, but at a frequency which is too high to be dealt with by electrical circuits; what we need is a signal which shows the position and brightness of everything in the picture for black & white TV, and with colour added for the de luxe version. The problem was tackled nearly a hundred years ago by Nipkov, who invented the idea of scanning.

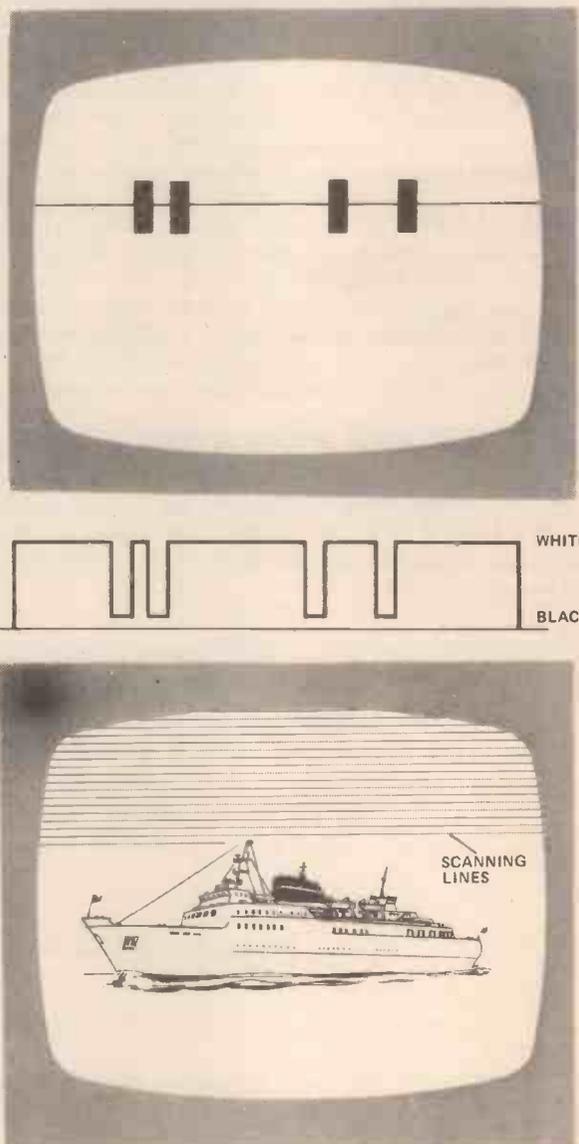


Fig 8.8 Scanning (a) Simple black/white pattern, with a line selected (b) Waveform produced by converting brightness into electrical signal along the line (c) Scanning lines make up a frame of picture.


BUILD TWO FREE PROJECTS ON CSC


ELECTRONICS BY NUMBERS
FREE PROJECTS
NO 1 & NO 2

ELECTRONICS BY NUMBERS FISH'N'CLIKS

Now using **EXPERIMENTOR BREADBOARDS** and following the instructions in "Electronics by Numbers" ANYBODY can build electronic projects. Look at the diagram, this has the same letter/number system as all EXP BOARDS. Look at the "YOU WILL NEED" list and select Q1 this is PNP transistor type HEP-230. This plugs into hole X9, A7 and C9. NOW take C1, a 50 uF capacitor, and put into holes J6 and J14 and do the same with all the components.

NOW YOU HAVE FISH'N'CLIKS

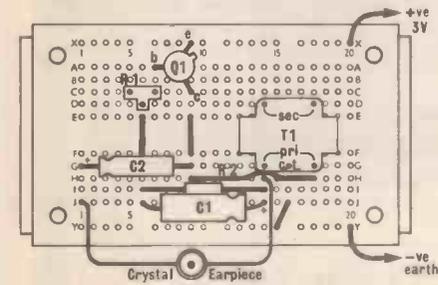

YOU WILL NEED

- B1, B2 - 2x1.5V AAA batteries
- C1, C2 - 50 uF, 12-VDC electrolytic capacitor
- E1 - Crystal earphone
- Q1 - Motorola HEP-230 pnp transistor
- R1 - 5000-ohm pot
- R2 - 27000-ohm, 1/4 watt resistor
- S1 - Spst switch part of R1
- T1 - Mini transistor output transformer; 500-ohm center tapped primary to 8-ohm secondary
- EXP - ANY EXP. BREADBOARD.

The anglers dream come true. This electronic marvel emits a CLIK-CLIK sound that makes fish really hungry. Shove the whole works in a watertight container lower it over the side and wait for the fish to grab the hook.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE A COPY OF THE FULL PROJECT FISH'N'CLIKS, AND A COPY OF PROJECT No 1 "TWO TRANSISTOR RADIO".

PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.

- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.



Europe, Africa, Mid-East: CSC UK LTD.
 Dept 14P, Shire Hill Industrial Estate
 Saffron Walden, Essex CB11 3AQ
 Telephone: SAFFRON WALDEN 21682
 Telex: 817477

EXPERIMENTOR BREADBOARDS.

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.
 All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.


EXP.325. The ideal breadboard for 1 chip circuits. Accepts 8,14,16 and up to 22 pin IC's. **ONLY £1.60.**



EXP.350. £3.15. 270 contact points with two 20-point bus-bars.



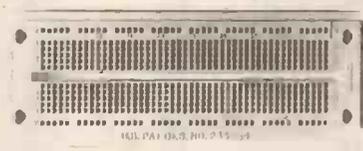EXP. 300. 550 contacts with two 40-point bus-bars. **£5.75.**



EXP. 650 for Micro-processors. **£3.60.**




EXP 4B. More bus-bars. **£2.30.**




ALL EXP.300 Breadboards mix and match with 600 series.

PROTO-BOARDS.

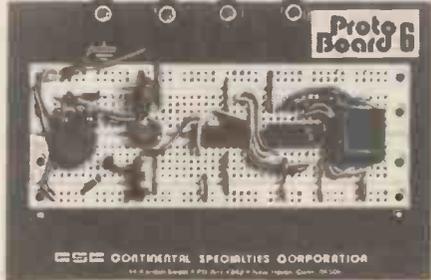THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



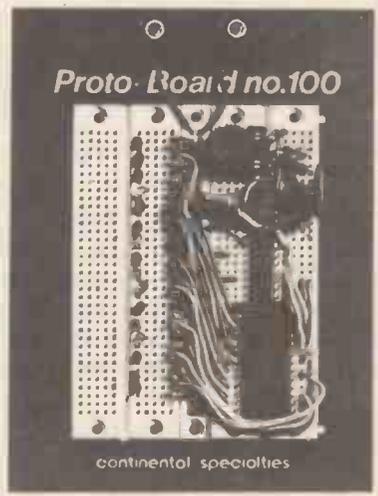PB.6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips. **PROTO-BOARD 6 KIT. £9.20.**



PB.100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy. **PROTO-BOARD 100 KIT £11.80.**

HOW TO ORDER AND RECEIVE FREE COPY OF FISH'N'CLIKS PROJECT WITH BONUS OF FREE TWO TRANSISTOR RADIO PROJECT.

CSC UK LTD. Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0,6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
	PC. 16.		£ 3.78
	PC.16-18.		£ 7.56
	PC. 16-18 Dual Clip.		£12.15
PROTO-BOARDS.			
	PB. 6.	6	£11.01
	PB 100.	10	£13.82

NAME

ADDRESS


FILL IN COUPON & RECEIVE FREE COPY OF ELECTRONICS BY NUMBERS PROJECTS No 1 AND No 2

The latest kit innovation!

from **Sparkrite**

Sparkrite - featured by Shaw Taylor in "DRIVE IN"

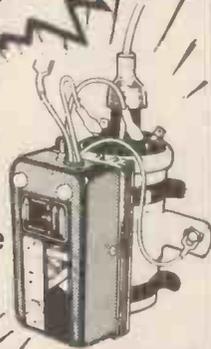the quickest fitting
CLIP ON
capacitive discharge
electronic ignition
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

Electronics Design Associates, Dept. HE 8
82 Bath Street, Walsall WS1 3DE. Phone (0922) 614791

Name

Address

Phone your order with Access or Barclaycard


including postage and packing UK only	QUANTITY REQD.	Send SAE if brochure only required.
X4 KIT £16.65 inc. VAT	<input type="text"/>	I enclose cheque/PO's for
TACHO PULSE SLAVE UNIT £3.85 inc. VAT	<input type="text"/>	£ <input type="text"/>

Access or Barclaycard No.

ELECTRONI-KIT

"EDUCATIONAL KITS OF EXCEPTIONAL QUALITY"

(AUDIO magazine)

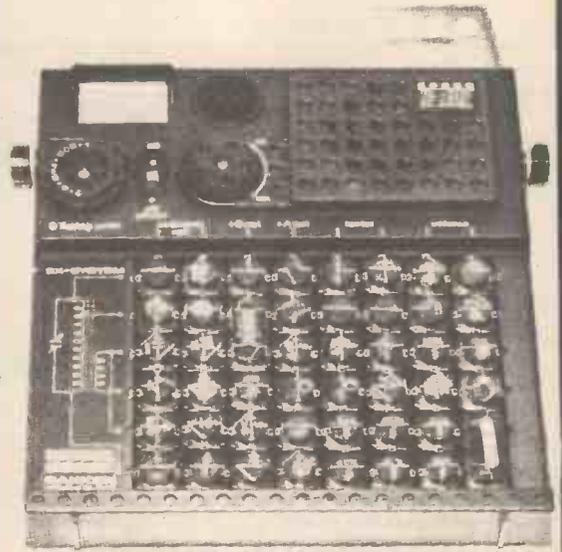

THIS IS A POWERFUL RADIO RECEIVER!

The same kit is also 150 other different actual working projects e.g.:

- Computer & Logic Circuits
- Electronic Organ, Timer, Light Control, Agility Tester, Lie Detector, Siren, Horn, Buzzer, Bird, Metronome.
- Cds cell light & sound control
- Photogun, Light Oscillator
- Light Switch, Light and Sound Morse Code.
- Field Strength Meter
- Hygrometer, Sphygmometer, etc. etc.
- Radio Receiver, Transmitter, Amplifier, Audio Generator, Signal Tracer & Injector, Continuity Tester, Telegraph, Photoradio Receiver, Radio Receiver/Microphone Mixer, Illuminometer, Voltmeter, Ammeter, Sound Level Meter, Ohmmeter, Diode & Transistor Tester, Transparency Indicator, etc., etc.

The above is just a selection of the circuits available — you can also design your own circuits with these superb new Denshi-Gakken "EX" construction kits.

No previous experience of electronics is required but you learn as you construct and have a great deal of fun too. The kits are completely safe for anyone to use.

Kits are complete with very extensive construction manuals PLUS Hamlyn's "All-Colour" 160 page book "Electronics" (free of charge whilst stocks last).

ALL KITS ARE FULLY GUARANTEED. Add-on sets (to increase the scope of each kit) are available, plus spares and accessories as required.

150 PROJECT KIT £39.75	60 PROJECT KIT £25.75
120 PROJECT KIT £33.75	30 PROJECT KIT £18.95
100 PROJECT KIT £29.25	15 PROJECT KIT £16.75

Prices include educational manuals, free book, VAT p&p (in the U.K.) and free introduction to the British Amateur Electronics Club

Callers at 20 Bride Lane will be very welcome. Trade and Educational enquiries invited.

Cheque, P.O. Barclaycard, Access No (or 14p for illustrated literature) to DEPT HE

SEE US AT "BREADBOARD" BINGLEY HALL, BIRMINGHAM 23rd-26th MAY, STAND A7

ELECTRONI-KIT LTD.
20 BRIDE LANE, LUDGATE CIRCUS,
LONDON, EC4Y 8DX (01-353 6430)

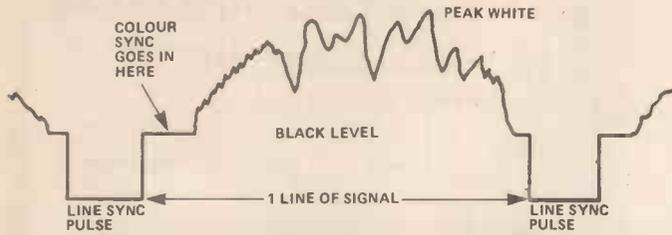


Fig 8.9 Line waveform. The sync pulse causes the receiver timebase to flyback ready to start the next sweep just as the video signal starts. The amplitude of the sync pulses is less than the amplitude of a block signal, so that sync signals cannot appear on the screen.

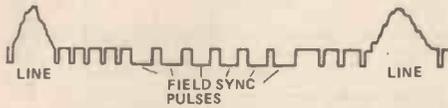


Fig 8.10 Line and field sync pulses. A set of field pulses is transmitted so that the receiver can separate them from the line pulses.

Scanning means selecting a line along the picture, and measuring the brightness of bits of the picture along that line, rather as we are taught to read by making our eye scan the words from left to right (around these parts at least) along each line of print. The result of scanning a line at a steady speed, using something like a photocell, is a waveform whose period is equal to the time taken to scan the line (Fig. 8.8). Now if we select another line slightly below the first one, we can obtain another chunk of wave, and by continuing this process we can analyse the whole picture into a set of waveforms.

IT'S A FRAME-UP

A complete set of lines of picture makes up a frame, a complete picture, and the history of the cinema shows us that if we can show about 20-30 frames per second we can obtain the illusion of movement. For historical reasons, we choose here to make the frame rate half the mains frequency rate, so that our frame rate is 25 Hz; because the mains frequency in the USA is 60 HZ, they use a frame rate of 30 Hz. The idea originally was to synchronise the picture rate to the mains frequency.

Synchronisation is one of the most important features of TV, and the idea appears to have been suggested by the true pioneer of TV as we know it today, Campbell-Swinton who in 1910 took out a patent which was as near as tuppence to a block diagram of a modern TV system, even to the CRT, which at that time was just a laboratory curiosity. The synchronisation problem is something like this. The signal, called the video signal, for each line of transmitted picture, must be used by the receiver to create a line of picture which fits into the same position in a frame. Unless this synchronisation is perfect, the received signal will build up into a scrambled picture — a mass of dots of different brightness which make no sense. The sort of thing, in fact, that we see when the line hold or frame hold controls on the old telly have been thoughtlessly twiddled. We can make sweep circuits which will run at a steady speed for the time of one line, and so what we need is to be able to synchronise the start of each line sweep, so that the sweep of the receiver will start just as the first part of the video signal for that line is starting.

This is done by transmitting a synchronising (sync.) pulse just before the start of each line of video signal.

The waveform of a line of signal looks as shown in Fig. 8.9, with the sync. pulse and the video waveforms. We can arrange things at the receiver so that the CRT of the receiver is cut-off (no electron beam) until the video signal starts, so that the sync. pulse and any unwanted signals during this time have no effect. This cut-off time is also used to transmit the sinewave synchronising signals for colour.

INTERLACING

We need another timebase to sweep the screen vertically, top to bottom, both at the camera and at the receiver, to ensure that each line is equally spaced from its neighbours, and that we have the correct number of lines in each frame. This field sweep as we call it is at a much lower rate than the line sweep, because we don't need anything like as many field sweeps per second as we need line sweeps. This timebase also needs to be synchronised, so that another sync. pulse is needed. In fact, a whole set of pulses is transmitted at the start of each vertical sweep, so that the receiver can sort out which is a line pulse (a single) and which is a field pulse (one with a wife and family).

Now at this point a complication arises. For a bright picture to be free of flicker, we need something like 50 vertical sweeps per second, and this has the advantage of being tied to the mains frequency. If we use the full number of lines per frame, 625 in the UK and most of Europe, 525 in the USA, then the bandwidth that we need to transmit the signal turns out to be a bit on the large side, around 12 MHz. If, on the other hand, we cut down the number of lines in each frame, the picture looks liney, like a five-barred gate. So what do we do?

The answer, folks, is interlacing. Each vertical scan, or field, consists of the alternate lines of the picture, lines 1,3,5,7 and so on. The next field has lines 2,4,6,8, who do we appreciate and all the rest of it. It takes two fields to make up a complete frame of picture; the first field starts with the beginning of line 1, and ends halfway along a line (3 1/2), the second field starts halfway along a line, and ends at the end of a line. How do we arrange this? Well it's quite automatic provided we choose the correct frequencies for the timebases, and there's nothing that has to be done which wouldn't also have to be done if we didn't use interlacing. Not all brilliant inventions need hardware, you know. 

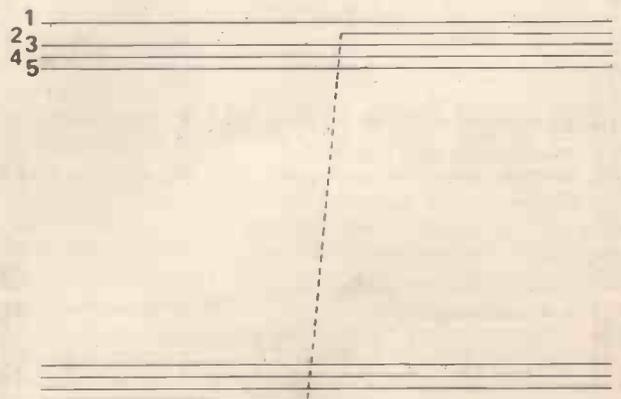


Fig 8.11 Principle of interlacing. Lines, 1, 3, 5 etc. are traced in the first field, lines 2, 4, 6 etc. in the second. The two interlaced fields make up a complete frame of lines.

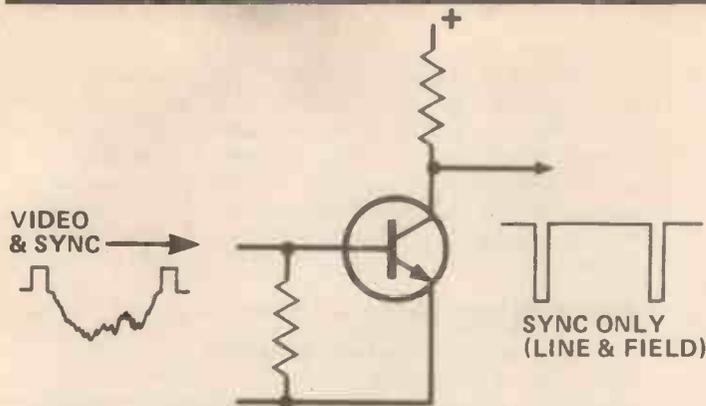


Fig 8.12 Separating sync signals from video.

KEEPING IN STEP

Take a look now at how some of these operations are carried out at the receiver — what does on at the transmitter is a bit more complicated, we'll leave that alone right now. The signals from the aerial are fed into a superhet receiver (what else?) and amplified at an intermediate frequency of around 36 MHz, with a 6 MHz bandwidth. Concentrating on the video signal at the moment, this is obtained by a simple diode demodulator (because the video signal is amplitude modulated) and consists of what is called 'composite video', that is picture signal plus sync. pulses. Now the way the video signal is designed, the actual picture signals start at about 23% of the peak signal amplitude, so that a piece of picture that is black corresponds to a voltage level which is about 23% of peak white. Any voltage less than this 23% does not register on the screen, so that this first 23% of the signal voltage can be used for sync pulses. In the receiver, we need to use these pulses, free of video signal, to synchronise the timebases, so that the first stage of a receiver after the demodulator is a sync separator which, as the name suggests, separates the sync signals from the video signals and also from each other.

Taking these one at a time, the sync. signals are separated from the picture signal by their amplitude difference. The composite signal as it leaves the demodulator is inverted so that the sync. signals are the most positive part of the signal. Now take this waveform to the base of a transistor which has no bias, and only the tips of the sync pulses will cause the transistor to conduct. The waveform at the collector is therefore a set of sync pulses with no video signal at all.

Next problem, to separate a line sync. pulse from the field pulses. The output of the sync separator feeds a differentiating circuit and also an integrating circuit. Each sync. pulse will produce a couple of spikes from the differentiating circuit, and the output of this circuit can be used, though nowadays after a lot of processing, to synchronise the line timebase. Single short pulses produce very little output from the integrating circuit, but a set of longer pulses, all coming in quick succession, causes a slow-rising pulse out of the integrator, and it's this pulse that we use to start the field timebase.

The timebase circuits themselves, are always astables, because they must continue to run even if the sync. pulses do not appear. They are used to drive current through scanning coils slipped over the neck of the CRT. The field timebase is usually fairly straightforward, but the line timebase of the modern telly is a fearsome bit of circuitry. The line deflection coils have a fair bit of inductance, and when the current through

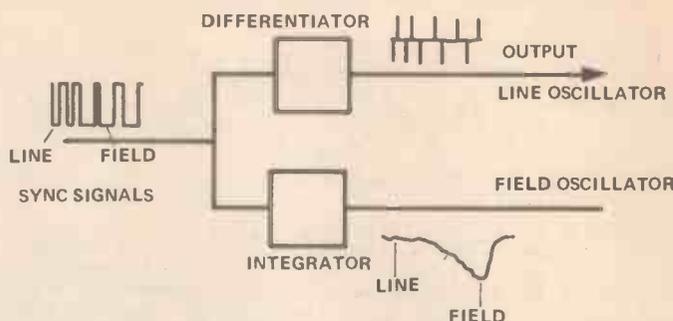


Fig 8.13 Separating the two sync signals from each other.

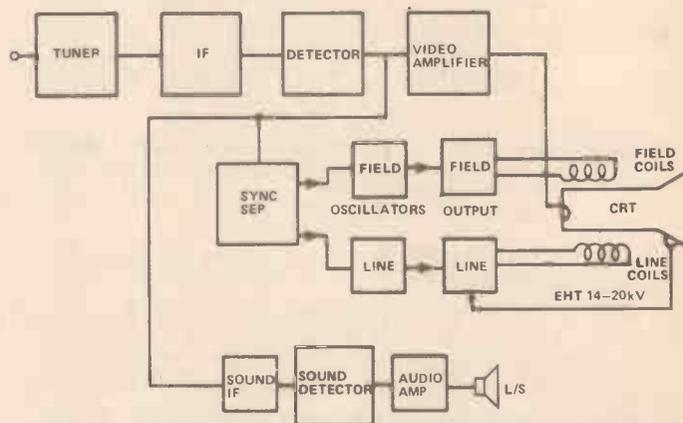


Fig 8.14 Simplified block diagram of B/W TV.

them stops at the end of the line scan, the back-emf is pretty large, several thousand volts. This is stepped up in a line-output transformer, and used to provide the high voltage for the tube.

SOUNDING OUT

Oh, yes, we nearly forgot about the sound signal. It's modulated onto another carrier which is at a frequency 6 MHz higher than the vision carrier frequency. Back in the old days, this used to be separated out at the mixer of the superhet and its different IF amplified separately. Nowadays, a wideband IF amplifier strip amplifies both sound and vision signals in one go, and the separation now takes place at the vision detector. A detector diode will not demodulate an FM signal, so what happens at the diode is signal mixing — the vision carrier beats with the sound carrier to produce a 6 MHz signal, which is still frequency modulated with the sound signal. This only needs a little bit more amplification to be demodulated by an FM detector. After that it's volume control, voltage amplifier, power amplifier and speaker just like any old radio.

We've left out colour. That's because life's too short, but you now should know enough about the basics of TV to pick up a more specialised book on TV and be able to understand it. Some of the books in the Beginner's Guide series are very useful if you want to read further.

NUMBER CRUNCHING

Number crunching is what a computer or calculator does, and we're going to look at how it goes about it. OK, a computer, even a pocket calculator, is a fearsome bit of electronics, and I wouldn't like to start designing one from scratch. Someone once said, though, that Science consists of reaching for the stars with the

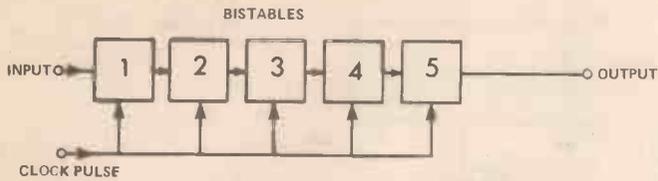


Fig 8.15 Shift register principle. A set of bistables is connected together with a clock pulse used to control each bistable. At a clock pulse, each bistable passes on its output, 0 or 1, to the next bistable in line.

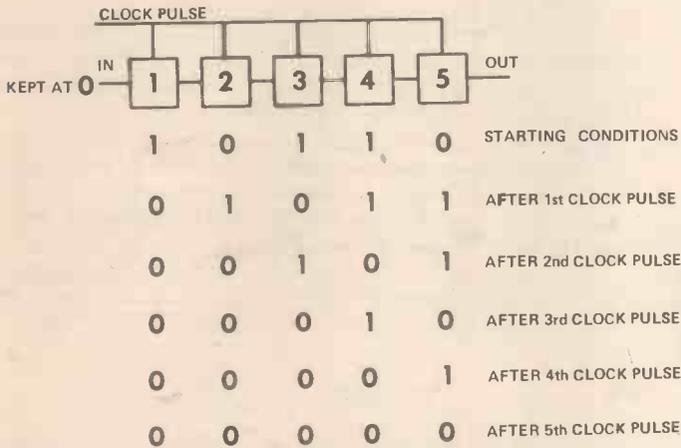


Fig 8.16 Action of a shift register. Five clock pulses will shift out all the signals from this 5-stage register.


advantage that you're standing on the shoulders of everyone who has gone before you. Some of these guys were pretty tall, and we'll make full use of them.

The cleverness of calculators and computers is not in the circuits so much as the way in which they're arranged — they even talk about computer architecture. The circuits are logic gates, bistables, and memories, mainly, types of circuit that we've met before, but in huge quantities, and connected together in a way that makes a lot of difficult calculations very easy to carry out. Every circuit, though, is working in binary code, so that the only digits that are used inside the machine are 0 and 1. The question is how. Fasten your safety belts and we'll take a brief look.

One particularly important use of bistables is in a circuit called a shift register, sometimes just register, which appears in all calculators and computers. We're not going to look at a detailed circuit of a shift register, but we need to know what it does, with the aid of Fig. 8.15. The shift register is a set of bistables, each connected so that the signals at the collector of one bistable are taken to the bases of the next, and so on. The bistables are not the simple bistable type we have looked at, but what are called clocked bistables, in which no action takes place until a clock pulse, a sort of sync. pulse, arrives. Each bistable in the shift register is connected to the same clock pulse oscillator.

CLOCKING-IN

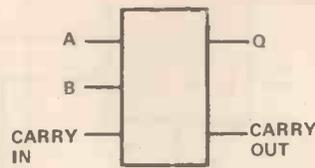Imagine now that this string of bistables is working and the output of each bistable is represented by the voltage of one of the collectors, 0 or 1. Now look at what happens when a clock pulse comes along. Each bistable (Fig. 8.16) hands on the digit that it has at its collector to the next bistable in line (to the right of the diagram). This



A	B	Cin	Q	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Fig 8.17 The full-adder (a) and its truth table (b). The carry terminals are needed from the 1's carried from the previous addition or to the next one.

is where the name shift register comes from, each digit is shifted one stage onwards when the clock pulse arrives. What happens at the first and the last bistables? At the first of the bistables, any number, 0 or 1, that is present will be shifted (or loaded, as we say) into the first bistable when the clock pulse arrives. If the input to the first bistable is 0, then a zero will be shifted into the register at the first clock pulse; if the input is at 1, then a 1 is shifted in. At the output, a 1 or a 0 will be shifted out as each clock pulse comes along. Not terribly difficult really, just a shift of one place on each clock pulse, and yet this is the circuit which above all makes computing possible. Why? Because the action of the shift register is controlled by the clock pulses, and because every operation in computing can be carried out by a combination of logic gates and shifting.

BINARY ADDITION

Let's look at some examples. Adding is carried out with two numbers at a time, as we know from using a calculator. Adding in binary is just as easy as adding in decimal, but how do we do it electronically? We can connect up NAND and NOR gates to form a circuit called a full adder, whose truth table is shown in Fig. 8.17, and this circuit will add two binary digits, plus any carry from a previous stage. The output is a digit, and another carry. The important thing is that this adder can cope with only one digit from each of the numbers being added (plus the carry) so that we have to present the digits of the numbers one step at a time. If, for example, we add 001011 to 101101, then we start with the least significant digits, the 1's in the last place. With these 1's at the inputs, the adder will produce a zero at the output and a 1 at the carry. The next digits are the bits 1 and 0, with the carry 1 from the last step, so the adder once again produces a zero output and a carry 1, and so on. How do we ensure that the adder is presented with a bit from each number at a time? Yes, that's right, we feed the digits from shift registers. One shift register stores 001011, the other stores 101101. The outputs of the shift registers are connected to the inputs of the adders, and another little shift register is used to store the carry. When a clock pulse arrives, the digits stored in the final bistable of each shift register are shifted into the input of the adder — which adds them. The output bit can then be shifted 8.12 into another shift register, and the carry bit stored in its own little shift register. On the next clock pulse, the next pair of digits come tumbling out of their shift register, plus the carry bit from last time round. The output is shifted into the output register, the next carry into its register and so on. There are six bits (digits) in each number, so that six clock pulses are needed to carry out this addition. After these six clock pulses, the output register will store the sum of the two numbers, 111000.



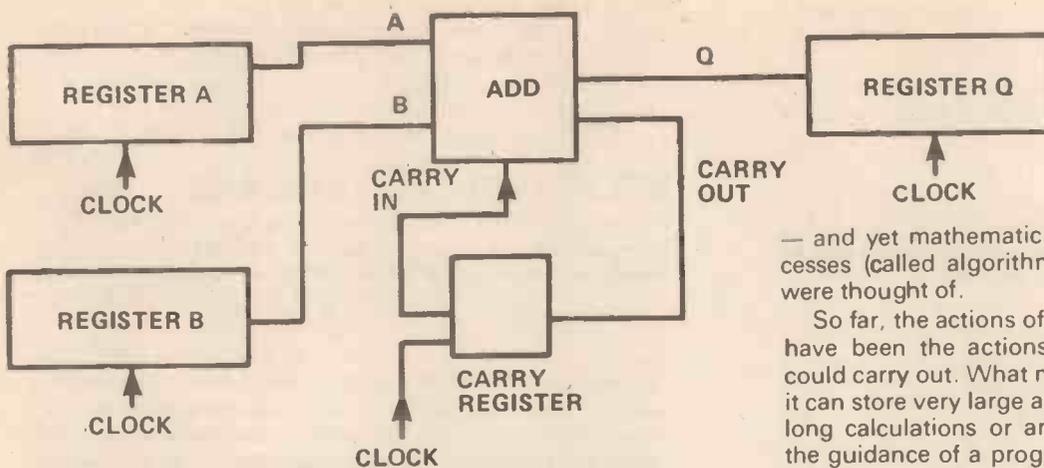


Fig 8.18 An adder used with registers to add two binary numbers.

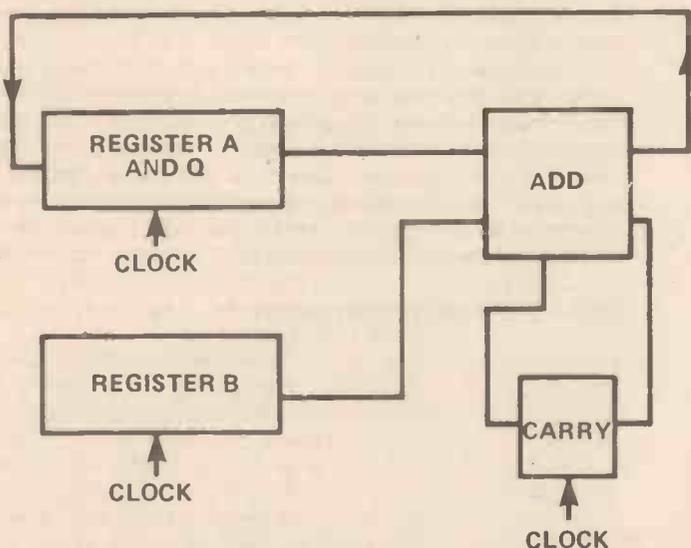


Fig 8.19 A neater arrangement in which the answer is fed into register A at the same time as the number A is clocked out.

REMEMBER THIS

We've described this in terms of three main registers, but most calculators would use only two (they are always referred to as memories). As each set of bits was added, the sum would be fed back to the input of one of the registers which had previously been used to store one of the numbers. That way it is then ready to be added to the next number. One of the main registers in a calculator is always hooked up to the display, and this is always the register into which a number is placed by using the keys. The other register is then used for the output from the adder, until the equals key is pressed, when the second register clocks its contents into the display register.

We've spent a lot of time on addition, and the reason is that all binary arithmetic consists of addition and shifting. Subtracting in binary, for example, consists of inverting each digit (0 for 1, 1 for 0) and adding 1 to one of the numbers, and then adding. Multiplication consists of shifting and adding, and division can be carried out by a similar, but more tedious process. The clever part of most modern calculators is the way in which other functions, such as log, sin, x^y , and so on can be calculated by using only addition and shifting processes

— and yet mathematicians had worked out these processes (called algorithms) centuries before calculators were thought of.

So far, the actions of calculators that we've looked at have been the actions that any old pocket calculator could carry out. What makes a computer different is that it can store very large amounts of numbers and carry out long calculations or arrangements of numbers, under the guidance of a program. Storage of information in a computer will not be confined to the registers, because other forms of storage such as punched cards, magnetic tape, paper tape and magnetic discs ('floppies') can be used to store information and read it in when needed.

Let's think of a simple example to illustrate what goes on. The resonant frequency (remember) of a coil of inductance L and a capacitor C in series is given by

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Now if you were to start working this out on your pocket calculator, you would probably start by entering the value of L, pressing the [X] key and then entering the value of C. Using the [=] key then gives LC, and a quick stab at the [√] key gives the square root. The next lot of key strokes is [X]2[X][π][=], so that the whole denominator has been calculated. Finally, pressing the [1/x] key inverts the number to give the result in Hz.

KEYS FOR GATES

What happens each time a key is pressed? Quite a lot of circuits are switched about, using gates, but the whole process is triggered off by one connection being made, so that some part of the circuit is switched from 0 to 1 or the other way round. Any action like this that can be done by a switch can just as easily be done by the output of a gate, and we can design gates that will close for any combination of inputs we like. Suppose, for example, that we have a set of gates, each with three inputs, and that their normal output is 0. We can design these gates so that one of them switches over for the input 001, another for 010, a third for 011, and so on, with each gate switching only for its own code number. Now if each of these gates activates a set of command circuits like [X], [=], [+], [1/x], and so on, then these operations will be carried out on the numbers in the main registers when the code numbers 001, 010, 011, etc. are presented to the gates.

Programming a computer consists of entering these code numbers, in the correct order, into a set of program registers. We aren't stuck with the instructions + × = and similar functions either. We can use the gates to cause new numbers to be read in from a register or from tape, or to store an output in a memory register, or print it on a printer. Our calculation of resonant frequency might start something like this.

First we load the values of L and C into memory registers. This is done by an instruction to the computer; code numbers which activate the correct gates so that the numbers that follow on the next set of clock pulses are stored in different registers. Each register has a

reference number, so that we know which one is used for each quantity. Assuming that the computer is already programmed, we can now press the start (or execute) key and watch what happens.

The first program register reads out with the first set of clock pulses and it has the effect of activating a set of gates. These gates allow the next bunch of clock pulses to shift the digits that represent the value of L into the main register, called the accumulator. The next clock pulse moves the program (we usually talk about the program counter) one step on, so that the clock pulses that follow set the gates for the instruction 'multiply'. That done, the next clock pulse moves the program on, and the next bunch of clock pulses brings the value of C out of store, and at the same time carry out the multiplication that has been set up ready. The program moves on, with the instruction [=] clocking the result of the multiplication back into the accumulator. Move on again and this time the pulses set up the circuit for finding the square root. We needn't go over it all, because you can see what is happening at the end of each operation, the next clocking activates a program step, which in turn carries out the next instruction.

FAST FIGURES

What makes it all so useful? Well, one thing is speed. The clock pulses in a big computer have a fast rate, 5 MHz or more, so that it doesn't take too long to go through a set of instructions. Even more important is that we can program in decisions. For example, we can include instructions that command the computer to compare the number that is in the accumulator with zero, and to go to another part of the program if the number in the accumulator is equal to zero, or alternatively, less than zero, or greater than zero. This type of instruction, called a conditional transfer, makes a computer much more useful than a simple calculator, because the computer can be made to produce more than one answer, or to work out a whole series of similar steps. We can, for example, program the computer to calculate the reactance of a 470 pF capacitor at 1 kHz, 2 kHz and at every 1 kHz upwards to 1 MHz, and then to stop and print out the answers. This sort of job is very tedious even with a calculator, because there are 1000 calculations needed. The computer can be programmed

to carry out the calculation for 1 kHz, print the answer, add 1 to the number of kHz in the store for L and carry on. Each time round, it can be asked to take the figure of frequency, subtract 1000, place in the accumulator and compare with zero. If the answer's not zero, carry on. If it is zero, stop. That way, when the frequency of 1000 kHz (= 1 MHz) is reached, the computer calls it a day.

WATCH YOUR LANGUAGE

The program as it is stored in the program register of the computer is just a string of figures, called machine code, which will have a different job to do in each different machine. Micro-computer have to be programmed using these machine codes, but large computers use what are called High-Level languages. A high-level language consists of instructions which are represented by letters, such as LDA, JUN, RNA, which can be typed onto an instruction tape. Each of these instructions may need many steps in machine code, and has to be converted into machine code by a circuit called a compiler, which consists of a set of gates. The high-level languages can then be used on any computer whose manufacturers have made a suitable compiler.

Once again, of course, we've only scratched the surface of a very large topic. If you want to take it further, then books alone are not really useful, because you need some practical experience with a computer. Many Technical Colleges run courses in Computer Science, and such courses include programming. On a less ambitious level, you can teach yourself a great deal about programming by learning to use a programmable calculator such as my favourite, the TEXAS T1-57. This is a miniature computer on which the program steps are entered by pressing keys rather than by a tele-type.

We've reached the end of this particular road now, and you've on your own. Along with the practical experience that the projects in HE will supply, plus some good advice at school or college, you now have enough background in electronics to tackle the London OA paper, or even the C & G 224 Part 1 — but remember that both of these require some observed practical work, and the London OA needs an essay of 1000 words as well. All in all, though, it's not a bad achievement for reading your favourite magazine for eight months, is it?

HE

PROGRAM INSTRUCTIONS	MEANING	KEY STEPS	MEANING
LRN	Calculator memories following steps as a program	CLR	Clear the display of any figures
RCL 1	Display contents of memory 1	5.03 STO 3	Stores the number 5.03 in memory 3
x	and multiply by	35 STO 1	Stores the value of inductance in memory 1
RCL 2	Contents of memory 2	.5 STO 2	Stores the value of capacitance in memory 2
=	Display the product	RST	Ensures that program is reset to the start, ready to run
\sqrt{x}	Take the square root	R/S	Runs program — display reads 1.2, which is frequency in MHz
1/x	Invert		
x	Multiply by		
RCL 3	Contents of memory 3		
=	Display product		
R/S	Stop, and leave last result displayed		
LRN	Signals end of program		
RUNNING THE PROGRAM — Finding resonant frequency of 35 μ H and 500 pF		Formula used for this program is $f = \frac{5.03}{\sqrt{L \times C}}$ with f in MHz, L in μ H and C in n	

Fig 8.20 A program for finding resonant frequency, using a TEXAS T1-57.

What to look for in the July issue: On sale June 1st




TELETEXT BOX

ETI goes Teletext next month. A full spec design including full colour and double height characters. Remote control is by ultrasonics, so there is no need to move from your armchair to change the page. The circuit is based upon the Mullard chip set — long awaited that is.

Emphasis has been placed upon ease of construction — the PCBs are plated through and silk screened and everything mounts to the board. With all this offer and with commercial units running at £200 plus you'd expect this kit to cost the earth would you not? Well it will set you back under £160 complete and we don't think that's bad! Don't miss this.

POLYPHONIC KEYBOARD CONTROLLER

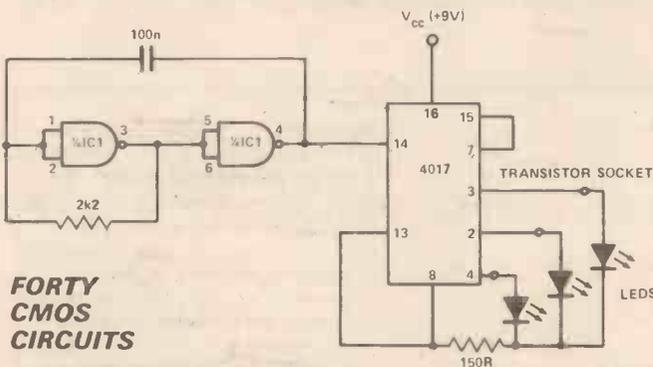We've struck the right chord here. Give up those one note wonders and take up polyphonics — you can't get arrested for it and it'll make your oscillators warble for joy. Play away up to 8 times simultaneously and don't feel guilty about it!



FORTY CMOS CIRCUITS

Another family size, bumper bundle of goodies from our bionic project editor, Ray Marston. In past issues he's covered 555s and 741s. This time it's the turn of CMOS circuits. He's got forty, yes forty, of the little beauties for you. You can't afford to miss them.

SOIL MOISTURE INDICATOR

Don't drown your Dahlias. The most common cause of premature plant death (murder) in the home is over-watering. If you don't want the Sweeney hammering on your door in the middle of the night, we strongly suggest that you build this moisture indicator. Think of it as a happiness guide for your busy Lizzie.



Hobby Electronics Book Service



POPULAR ELECTRONICS BOOKS

Sinclair, I. R., Introducing Electronic Systems	£1.80
Sinclair, I. R., Introducing Amateur Electronics	£1.55
Sinclair, I. R., Electronic Fault Diagnosis	£3.45
Sinclair, I. R., Repairing Pocket Transistor Radios	£2.50
Sinclair, I. R., Oscilloscope In Use	£3.00
Sinclair, I. R., Understanding Electronic Components	£4.00
Sinclair, I. R., Understanding Electronic Circuits	£4.00
Kitchen, H. T., Handtools For Electronic Workshop	£2.75
Kitchen, H. T., Electronic Test Equipment	£5.00
Capel, V., How To Build Electronic Kits	£2.20

AUDIO

Earl, J., Audio Technicians Bench Manual	£3.50
Earl, J., Pickups and Loud Speakers	£3.50
Earl, J., Tuners and Amplifiers	£3.00
Earl, J., Cassette Tape Recorders	£5.25
Earl, J., ABC of Hi-Fi	£4.25
Capel, V., Microphones In Action	£3.00
Capel, V., Improving Your Hi-Fi	£3.50
Capel, V., Creative Tape Recording	£4.00
Hellyer, H. W., Tape Recorders	£4.25
Sinclair, I. R., Audio Amplifiers For Home Construction	£2.75

RADIO CONTROL

Aldridge, D., Transistorised Radio Control For Models	£3.50
Drake, J., Radio Controlled Helicopter Models	£3.95
Jeffries, C. R., Radio Control For Model Yachts	£1.85
Safford, E. L., Radio Control Manual	£2.45
Safford, E. L., Advanced Radio Control	£3.95

COOKBOOKS

Tracton, K., BASIC Cookbook	£4.10
Lancaster, D., TTL Cookbook	£7.00
Lancaster, D., RTL Cookbook	£4.65
Lancaster, D., CMOS Cookbook	£8.20
Jong, W., IC Op Amp Cookbook	£10.00
Lancaster, D., T.V. Typewriter Cookbook	£7.75
Lancaster, D., Cheap Video Cookbook	£7.00
Jong, W., IC Timer Cookbook	£7.50
Lancaster, D., Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business)	£4.95

QUESTIONS AND ANSWERS

SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.

Coker, A. J., Q & A On Electric Motors	£1.50
Hellyer, H., Q & A On Radios and T.V.	£1.50
Hibberd, R., Q & A On Integrated Circuits	£1.50
Jackson, K., Q & A On Electricity	£1.50
Brown, C., Q & A On Hi-Fi	£1.50
Brown, C., Q & A On Transistors	£1.50
Brown, C., Q & A On Electronics	£1.50
Reddihough, J., Q & A On Colour T.V.	£1.50
Miller, H., Q & A On Electric Wiring	£1.50

CONSTRUCTOR GUIDES

Graham, P., Simple Circuit Building	£2.45
Colwell, M., Electronic Diagrams	£2.45
Colwell, M., Electronic Components	£2.45
Colwell, M., Printed Circuit Assembly	£2.45
Ainslie, A., Practical Electronic Project Building	£2.45
Colwell, M., Project Planning and Building	£2.45

BEGINNER'S GUIDE

Sinclair, I. R., Beginner's Guide To Tape Recording	£3.30
Sinclair, I. R., Beginner's Guide To Integrated Circuits	£3.10
Sinclair, I. R., Beginner's Guide To Audio	£3.10
King, G. J., Beginner's Guide To Radio	£3.10
King, G. J., Beginner's Guide To Television	£3.10
King, G. J., Beginner's Guide To Colour T.V.	£3.10
Guilou, F., Beginner's Guide To Electric Wiring	£3.10

PROJECT BOOKS

Marston, R. M., 110 Cosmos Digital IC Projects For The Home Constructor	£3.25
Marston, R. M., 110 Wave Form Projects For The Home Constructor	£3.45
Marston, R. M., 110 Op Amp Projects For The Home Constructor ..	£2.95
Marston, R. M., 110 Semiconductor Projects For The Home Constructor ..	£3.45
Marston, R. M., 110 Thyristor/SCR Projects For The Home Constructor ..	£2.95
Marston, R. M., 110 Electronic Alarm Projects For The Home Constructor ..	£3.45
Marston, R. M., 110 Integrated Circuits Projects For The Home Constructor ..	£3.45
Marston, R. M., 20 Solid State Projects For The Car and Garage ..	£2.50
Marston, R. M., 20 Solid State Projects For The Home	£2.50

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service,
P.O. Box 79,
Maidenhead, Berks.

Drill Speed Controller

An easy-to-build gadget that lets you vary the speed of your power drill, or any other domestic appliance that is powered by a universal electric motor.

THIS PROJECT CAN BE USED to control the speed of virtually any domestic electric drill, power saw, grinder, sander, or other power tool that incorporates a universal electric motor. It enables the motor speed to be smoothly varied from zero to about 75% of maximum via a single control, and incorporates built-in compensation to maintain the motor speed virtually constant at any given speed setting, regardless of changes of load. This latter facility is of great value when tackling low speed jobs like drilling masonry or using fly-cutters on sheet metal, etc.

The drill speed controller is housed in a standard MK surface mounting bakelite box, as used for normal house wiring work. The box plugs into the mains via a cable, and the drill plugs into a standard mains outlet socket that is built into the controller box front cover.

CONSTRUCTION

All components except C1, RV1, and SW1 are mounted on the single PCB, so construction should present few problems provided that care is taken to fit all semicon-

ductors in the correct polarity. It must be emphasised, however, that the controller is connected directly to the mains without the use of an isolating transformer, so care must be taken to ensure that there is no likelihood of any dangerous conditions arising. Under no circumstances touch the wiring when the unit is connected to the live mains.

The SCR used on the prototype circuit is a C106C type, but the design can in fact be used with virtually any 400 volt SCR with a current rating greater than 3 Amps. We didn't bother to fit a heat sink to the SCR on the prototype, but it is probably a good idea to do so in practice. If you do fit a heat sink, make sure it can't come into contact with any other components or wires.

RV1 is mounted on a MK planking plate, suitably drilled, that screws to the right front half of the surface box. C1 is soldered directly across the terminals of RV1, with its positive side going to the R1-side of the pot.

The HE Drill Speed Controller connected up to our workshop drill, already it has found a regular place in our toolkit.



Parts List

RESISTORS (All 1/4W 5% unless stated)

R1	10k 5W
R2	470R
R3,R4	1k0

POTENTIOMETER

RV1	1k0 2W
-----	--------

CAPACITORS


C1	2 μ 2 63V
C2	100n polyester

SEMICONDUCTORS

SCR1	C106D
Q1	BFX88
Q2	BFY50
D1,D2	1N4004


MISCELLANEOUS

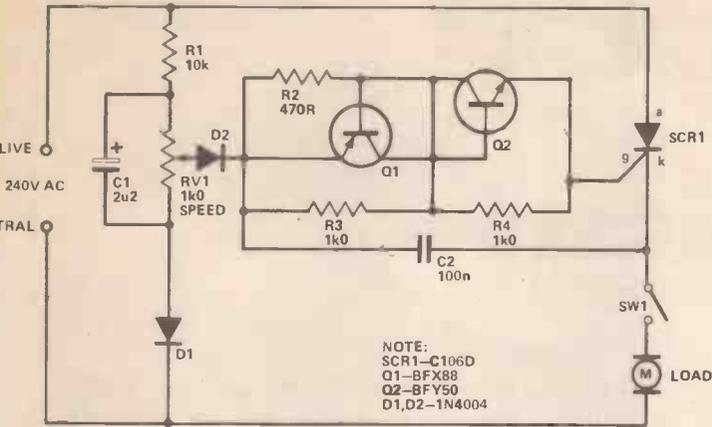MK surface box list no 2025, MK 13A switched socket.
MK 13A plug. MK single blanking plate.



NOTE:
SCR1—C106D
Q1—BFX88
Q2—BFY50
D1,D2—1N4004

Fig 1. Circuit diagram of the HE Drill Speed Controller.

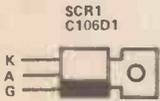

Leadout for TH1. Note the position of the heat-sink mounting hole.

How it Works

A universal motor, when running, generates a voltage that opposes that of the supply. This voltage is called the back EMF, and is proportional to the motor speed. The HE drill speed controller uses this back EMF to sense motor speed, and automatically adjusts the power fed to the motor so that its speed remains reasonably constant under varying load conditions. The speed setting is variable via RV1.

Because of its back EMF characteristics, a universal motor runs at about 75% of its normal maximum speed when it is fed from a half wave rectified power line.

The HE controller uses an SCR (silicon controlled rectifier) to gate half-wave power to the drill motor. The SCR acts like a very fast self-latching power switch. The point at which it turns on during a half cycle depends on the setting of RV1, and on the back EMF of the motor. If the SCR is turned on near the end of each positive half cycle, very little power is fed to the motor; if the SCR is turned on at the start of each positive half cycle, high power is fed to the motor. The SCR turns off automatically at the end of each positive half cycle.

In the initial description of circuit operation, let's assume that SW1 is closed, and let's also ignore the presence of Q1-Q2 and their associated resistors and C2, and assume that D2 is connected directly to the gate of the SCR. In this case R1-RV1 and D1 form a half-wave voltage divider that feeds an adjustable voltage to the gate of the SCR via D2. The SCR turns on when its gate becomes slightly positive to its cathode, and the point at which this occurs depends on the setting of RV1 and on the back EMF, and hence speed, of the motor.

Suppose, for example, that the motor is lightly loaded, and RV1 is set so that the motor runs at

half-speed under this condition. If the load is now removed the motor speed will tend to increase, thus increasing the back EMF and countering the voltage set by RV1, so that the SCR will tend to fire later in each cycle and thus reduce the speed of the motor. The reverse action occurs if the motor load is increased. In either case, a negative feedback effect occurs which tends to cause the motor to operate at a constant speed in spite of load variations.

In extreme cases, when the controller is set for very low speed operation, this negative feedback causes power to be fed to the motor in 'bursts' or 'skip cycles' of half-wave power when the motor is lightly loaded, so that the motor seems to give an erratic form of operation. Capacitor C1 is fitted to reduce this skip cycling effect and give smoother operation.

The action of the Q1-Q2-C2 network, when it is triggered, is such that the SCR has to be supplied with gate current that is derived from RV1 slider. If the SCR is a sensitive type, like the C106D, RV1 can provide this gate current without trouble, but if the SCR is a low sensitivity device, RV1 may not be able to supply adequate gate current. Q1-Q2 and C2 are used to overcome this problem.

Q1-Q2 and their associated resistors act as a voltage-sensitive switch. In each half-cycle, C2 is able to charge up via RV1 slider. As soon as the C1 voltage rises to a suitable value, Q1 and Q2 both switch on and partially discharge C1 into the gate of the SCR, thus delivering a pulse of high current to the SCR gate, quite independently of any current-drive limitations of RV1 slider. The Q1-Q2 and C2 network thus enables virtually any SCR to be used in the SCR1 position, almost irrespective of its gate sensitivity characteristics.

Drill Speed Controller


Note when using the drill (or any other appliance) at low speeds that its motor will run rather hotter than usual, since the motor's cooling fan efficiency is greatly reduced at low speeds. It is wise to occasionally pause and allow the motor to cool down when using it for long periods at low speeds.

Switch SW1 is incorporated in a MK 13 amp switched socket, that screws to the left front half of the surface box.

USING THE CONTROLLER

Plug the controller into the mains, plug the drill into the controller, and switch both units on. The drill speed can be varied from zero to about 75% of full speed via RV1. Note that there may be a 'dead' zone at both the low speed and high speed ends of the control, due to different drill motor characteristics and component tolerances within the controller. This is quite normal.

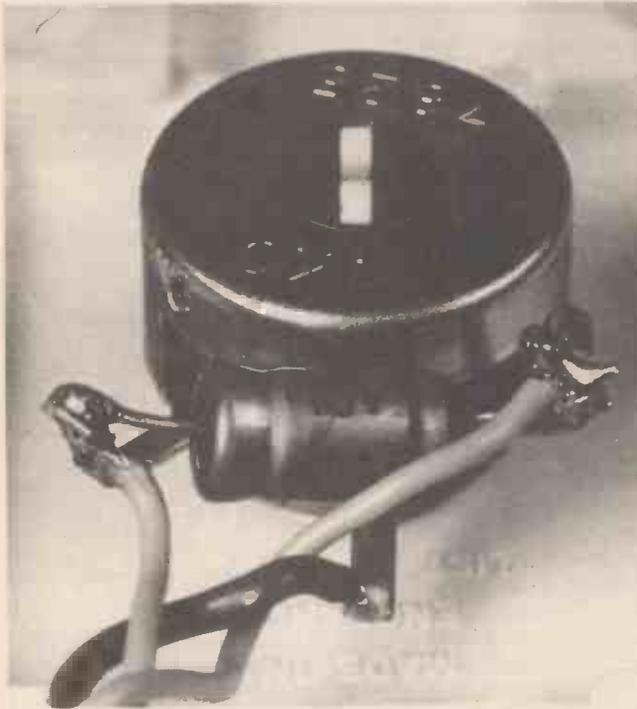At very low speeds the drill runs rather jerkily under low load conditions, due to the 'skip cycling' method of speed regulation that is used in the design. This jerkiness decreases or disappears when the drill is loaded up.




Mounting capacitor C1 on the control potentiometer RV1.

Buylines

All electronic components in this project are readily available types. The SCR can be almost any 400 volt type with a current rating greater than 3 amps.

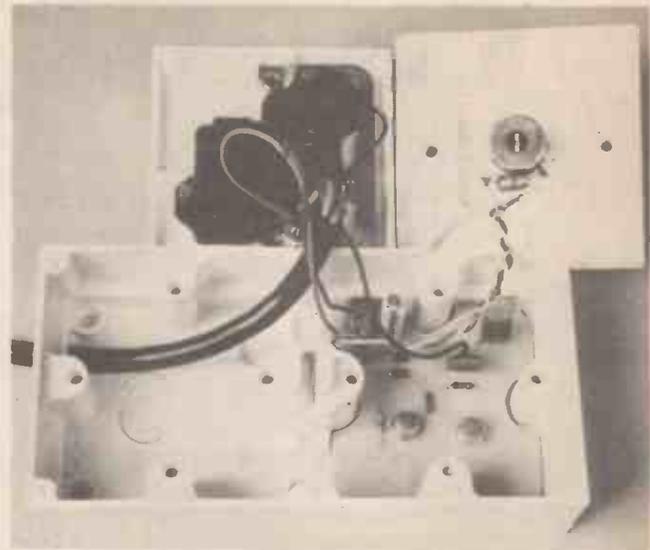The MK products, such as the surface box, etc, are available from most large retailing stores and from D.I.Y. and electrical hardware shops.



Inside the HE Drill Speed Controller, use of a PCB is strongly recommended, especially when using a mains-driven project.

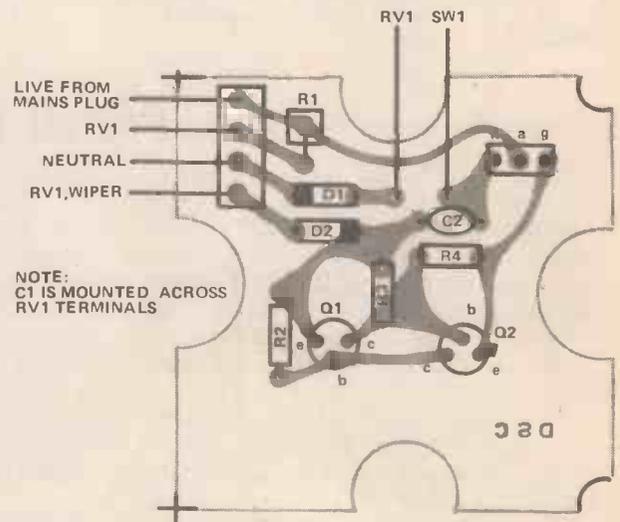


Fig 2. PCB overlay, note position of the thyristor.

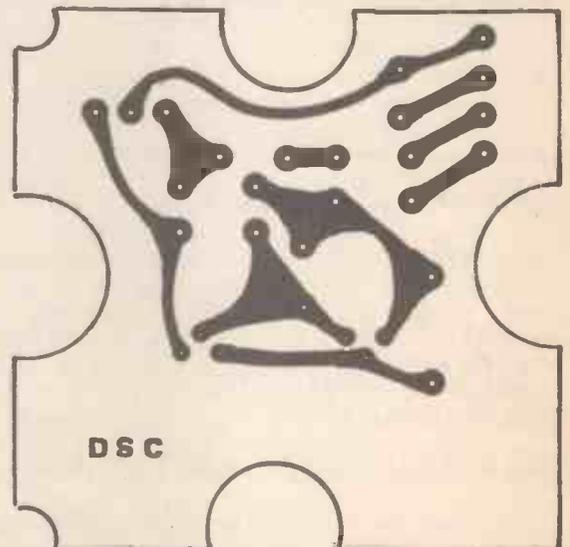


Fig 3. PCB pattern for HE Drill Speed Controller.


Hobbyprints

An easy, patented method of making PCBs for HE projects.

For some time it has been possible to buy acid resist rub-down pads and track — in fact we use them in the HE workshops and they work very well. HOBBYPRINTS take this idea a stage further — the complete PCB pattern is already on the sheet and can be rubbed down in seconds — and the patterns are nice and crisp, made from the original artwork, used for the prototype.

If you have the facilities for ultraviolet exposure, HOBBYPRINTS make excellent masters — being solid black on a translucent film. With this method you can use the HOBBYPRINTS time and time again!

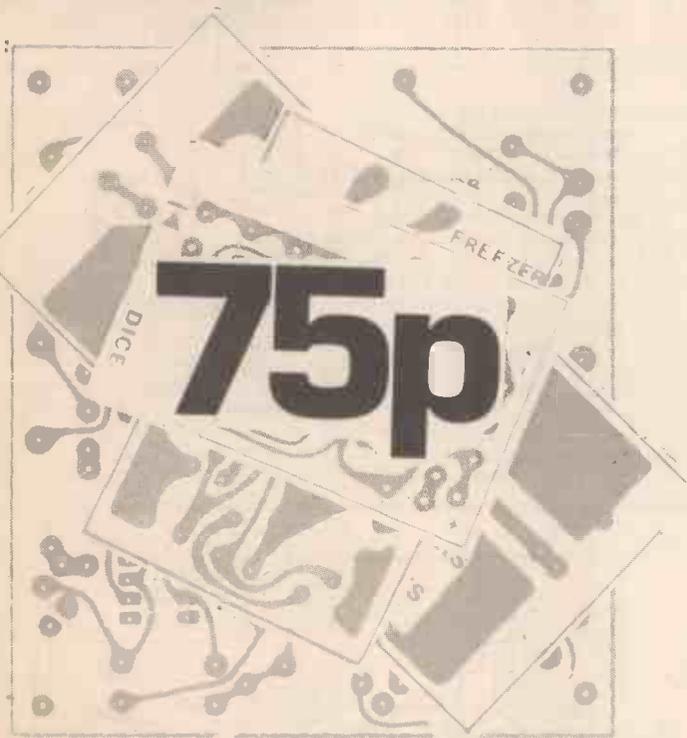HOBBYPRINTS are produced exclusively for HE, and the whole system is protected by patents 1445171 and 1445172. Each month we will be bringing out a new HOBBYPRINT, containing the patterns for each issue's projects.



HOBBYPRINT A (November HE)

5 Watt stereo amplifier, Waa-Waa pedal, Bedside radio.

HOBBYPRINT B (December HE)

Digital dice, Photon (2 copies), Metronome, Audio mixer.

HOBBYPRINTS C (January HE)

Graphic Equiliser, Touch switch, Vari-Wiper, Flash Trigger.

HOBBYPRINT D (February HE)

Short Wave Radio, Sine/Square generator, Scratch/Rumble filter, Car Alarm.

HOBBYPRINT E (March HE)

Light Chaser, Photo Timer, Casanova's Candle, (2 copies), Tone Control (2 copies).

HOBBYPRINT F (April HE)

Train controller, Cistern Alarm, Transistor Tester

HOBBYPRINT G (May HE)

Parking meter timer, Digibell, Power supply, Sound effects unit

How to use HOBBYPRINTS.

1. Clean the PCB as you would for any work giving it a rub down with fine sandpaper (we even supply this in the kit). A quick wipe over with lighter fuel will help to remove any grease marks.
2. Lay down the HOBBYPRINT and rub over with a soft pencil until the pattern is transferred to the board. Peel off the backing sheet carefully making sure that the resist has transferred. If you've been a bit careless there's even a "repair kit" on the sheet to correct any breaks!
3. Cut the board to size and put it in the Ferric Chloride.
4. When etching is completed, wash the board and use the sandpaper or a scouring powder to remove the resist. The resist pattern is pretty hardy but is easily removed at the final stage.
5. All you've got to do now is drill the board. Time? Only about ten minutes from beginning to end plus etching time (15 minutes usually with a good acid).


ORDER TODAY

Send cheque or postal order (payable to Hobby Electronics) to:

**HOBBYPRINTS,
HOBBY ELECTRONICS,
25-27, OXFORD STREET,
LONDON W1R 1RF.**


75p INCLUSIVE OF VAT AND POSTAGE.

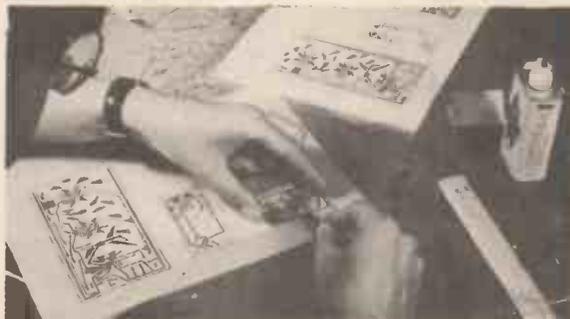Please mark the letter(s) of the HOBBYPRINTS on the outside of the envelope.



Short Circuits

LOGIC LOCK

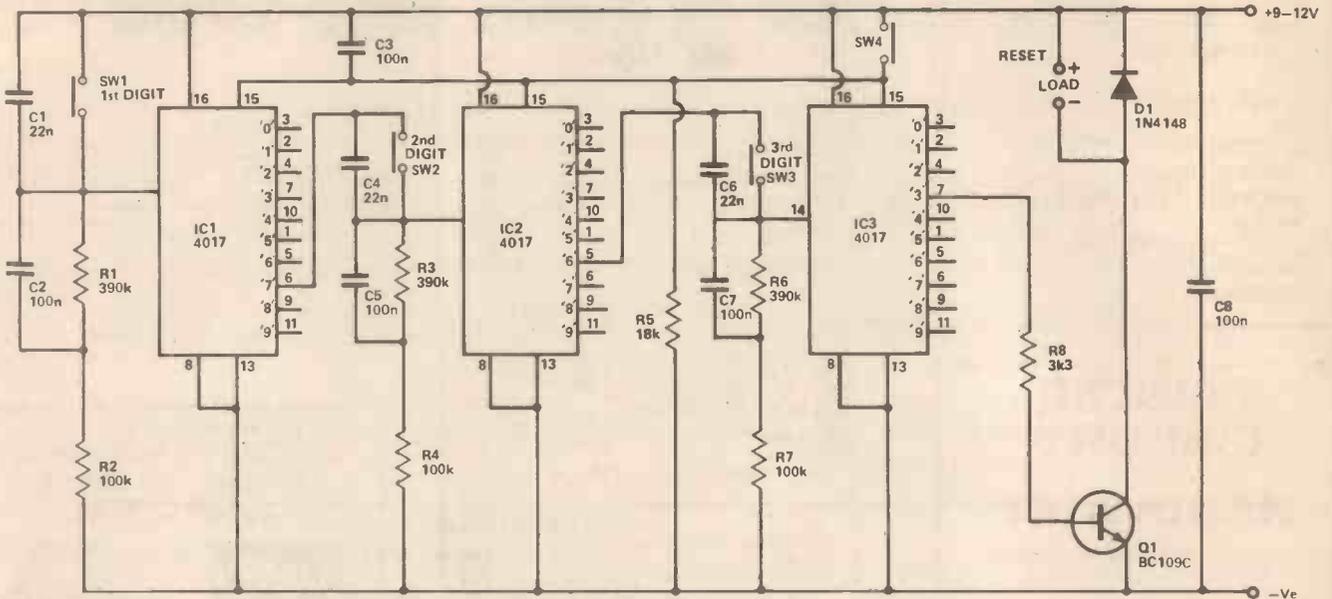


This electronic combination lock can be used instead of a keyswitch as the on/off switch for a burglar alarm or other equipment, or it can be built for its novelty value. It is unusual in that it has three push button switches which are fed with the combination, the number of times each switch has to be pressed corresponding to its combination number. The switches must be operated in the correct order, and in practice they would not be arranged so that they had to be operated starting with the left hand switch and working across to the right hand one. Thus it is possible that someone knowing the

correct combination number would still be unable to "crack" the unit.

SW1 is the first switch, and a clock pulse will be fed to IC1 each time it is operated. C1, C2 and R1 are needed to prevent contact bounce from giving faulty operation (even the cheapest of push button switches will be reliable enough). IC1 is a 1 of 10 decoder, and when power is initially applied to the circuit it is reset to zero by the positive pulse generated by C3 and R5. In other words the '0' output will be high and the other nine will be low. As pulses are fed to IC1 using SW1, outputs '1', '2', '3', etc. will successively be the single

output that assumes the high state.

The next stage is identical to the first, but is driven from the '7' output of IC1, and so seven pulses must be fed to IC2 before IC3 can be clocked using SW2. The third stage is fed from the '6' output of IC2, and so six pulses must be fed to IC3 using SW3. After three clock pulses, IC3 output '3' will go high, switching on Q1 and applying power to the load. This can be a solenoid, a relay, or any DC load requiring 9 to 12 V. at no more than 100mA. If an error is made when entering the combination, the circuit is reset using SW4

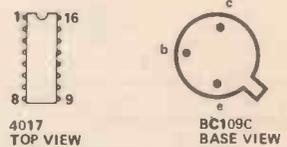


and the combination is entered from the beginning.

Of course, as shown the circuit has a combination of 7-6-3, but by using the appropriate outputs of ICs 1 to 3 any three digit combination can be obtained. The circuit has a standby current consumption of only about 3uA., rising to about 3mA. (plus the load current) when it is switched to the on state.

ELECTRONIC THERMOMETER

This thermometer covers a range of 0 to 50 degrees Centigrade with a linear scale so that the temperature can be read directly from the scale of the 50uA. meter. A range of 0-100 degrees Centigrade can be obtained by substituting a 100uA. meter.

The unit uses silicon diodes D1 and D2 as the temperature sensors, and these would normally be mounted in some form of probe which can be positioned many metres away from the other circuitry if necessary. C1 filters out any noise picked-up in the connecting cable. D1 and D2 are given a small forward bias by R1, and this is made only small so that there is no significant self heating of the diodes. The voltage produced across the diodes is nominally 1.2 V., but it actually varies by about 2mV. per degree C. per diode, or about 4 mV. across both diodes. This voltage is fed to the input of an op. ap. inverting amplifier which

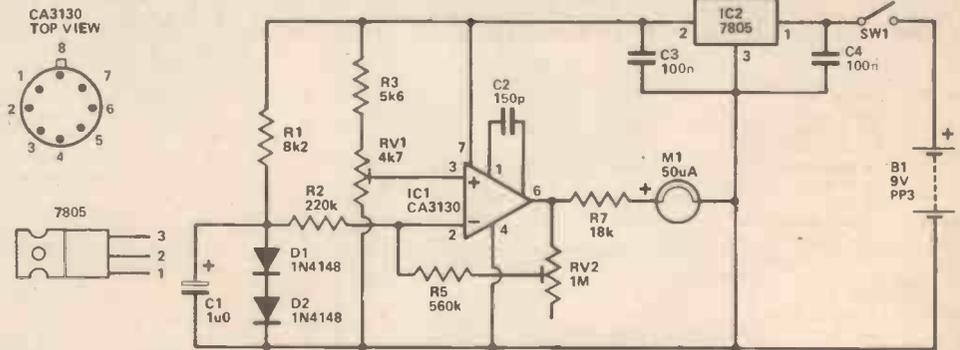

utilizes IC1. With the probe at 0 degrees C. (which can be achieved by immersing the probe in ice) R4 is adjusted for the highest voltage at IC1's non-inverting input that gives zero output voltage. This compensates for the quiescent voltage across the diodes, and gives zero reading on the 1 V. FSD voltmeter circuit which consists of R7 plus M1 and is connected across the output of the amplifier.

If the diodes are now heated to

50 degrees C., the voltage across them will fall by approximately 200 mV. (4 mV. x 50 degrees C. = 200mV.), and this is amplified by a factor of 5 by the amplifier to give about 1 V. at its output and roughly full scale deflection of the meter. In practice R6 is used to adjust the gain of the amplifier so that precisely full scale deflection is produced, and the unit functions as an accurate thermometer. Of course, R6 can be given the correct

setting with the probe at any known temperature which corresponds to a reasonably substantial meter deflection, and the unit does not have to be calibrated at 50 degrees C.

The circuit requires a very stable supply of about 5 V., and this is obtained from a 9 V. battery using a 5 V. monolithic regulator (IC2). C3 and C4 should be mounted close to IC2 in order to prevent instability.

AD INDEX

ACE	12
AMBIT	2
AJD DIRECT SUPPLIES	12
CSC	59
DIGITAL DEVICES	50
EDA	60
ELECTRONIKIT	60
GMT ELECTRONICS	4, 5
GREENWAY ELECTRONICS	12
HENRY'S	12, 36
JEREMY LLOYD SYNTHESISERS	36
MAPLIN	76
MARSHALLS	34

METAC	75
MINIKITS	50
PRESCOTT CLOCK AND WATCH	73
RAMAR	73
RTVC	17
STEVENSON	44
SWANLEY	33
TAMTRONIK	73
TECHNOMATIC	33
TIMETRON	50
VERO	34
V + F SMALLCRAFT	73

SILICON DIODES (1N4148 specification). These high quality components represent remarkable value at 50 for 50p, 150 for £1, 500 for £3, 1,000 for £5. **CARBON FILM RESISTORS** (5%, 1/4, 1/2W), 20 each of 30 different values plus sample 10 of above diodes for £3. Post free from D. Johnston, 12 Balgillo Road, Dundee DD5 3LU.

"RIGHT FROM THE START"

The only really practical Electronics Course available. Instruction manual only £5.95. Manual and Component Kit to cover all projects, including solder boards £21.

QUALITY PRECISION TOOLS

Snipe Nose Pliers £6.40. Flush Side Cutters £5.75. 120mm Box Jointed, Insulated Handles. Similar but Lap Jointed £2.50 and £2.75.

SOLDERING IRONS

Excellent value. Speedyheat 25W 240V inc. 4.4 and 2.2mm Bits £3.15 only.

Any three items deduct 10% add 30p P&P.

C.S.D.

7 Delisome Lane, Hatfield, Herts.

PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices
P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Afford range of etch resist transfers, and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASON'S ROAD
STRATFORD-ON-AVON
WARWICKS. Tel. 4879

1.2V NICADS

Prices include VAT

RECHARGEABLE BATTERIES

BUTTON CELLS

	Dia	Hgt	Price
225mAh	25.0	7.5	0.60
500mAh	34.5	9.5	1.15
4.8v Pack (centre tap available)			
225mAh			2.40
500mAh The original "Deac"			4.60

CYLINDRICAL CELLS

("Vented" for fast charge)

0.5Ah*	HP7 or Size AA	1.10
1.2Ah*	22.5 or 49 O	1.40
1.8Ah* Tagged only	HP11 or Size C	2.05
2.0Ah	HP11 or Size C	£2.20
4.0Ah*	HP2 or Size D	2.75
		7.50

6.0V Pack 5x1.2Ah nicads

Tags available at extra 10p per cell.

Charger — Suitable for any of the above nicads — charges up to twelve cells in series at either 25mA, 50mA, 120mA, 200mA or 400mA rate **£11.95**

Charger for 1 to 4 HP7 or 0.5Ah nicads Only **£5.95**


UK POST AND PACKING

50p PER ORDER

Sizes approx. in mm.

V + F SMALLCRAFT (POPLAR) LTD.
38 Stoneleigh Road, Clayhall
Ilford, Essex
01-550 6642

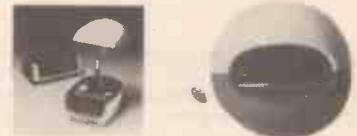BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

(1) With alarm repeat — S.R.S.P. of £17.00 offered at **£3.95 inc. VAT.**

(2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues. S.R.S.P. £31.00 — offered at **£6.95 inc. VAT.**

(3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues. S.R.S.P. of £32.00 — offered at **£6.95 inc. VAT.**

These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases

PRESCOTT CLOCK AND WATCH COMPANY LIMITED
Prescott House, Humber Road, London NW2 6ER

TAMTRONIK LTD. (DEPT. HE)

217 TOLL END ROAD, TIPTON
WEST MIDLANDS DY4 0HW

TEL. 021-557 9144

PRINTED CIRCUIT BOARDS and KITS for HE PROJECTS

Mag Issue	Project	Kit Ref	PCB	Kit	Kit Contents (See key)
Nov 78	Bedside Radio	H001	1.25	15.95	BEHL
	Stereo Amplifier	H002	3.90	43.95	BEHL
	Waa Waa Pedal	H003	.90	6.90	BEH
Dec 78	Push Button Dice	H005	1.10	5.85	BEHL
	H.E. Metronome	H006	.85	6.40	BEHL
	Photon Phone	H007	1.60	—	BEGH
	H.E. Mixer	H008	3.25	23.35	BEGHL
Jan 79	Graphic Equaliser	H009	3.25	24.55	BEGHL
	Flash Trigger	H010	1.10	13.50	BEHL
	Variwiper — Relay	H011R	.90	7.30	BEH
	Variwiper — SCR	H011S	.90	4.10	BEH
	Touch Switch	H012	1.15	4.95	BEH
Feb 79	Short Wave Radio	H013	1.40	11.95	BFH
	Sine/Square Wave Generator	H014	1.95	25.95	BEHL
	Scratch & Rumble Filter (Mono)	H015	1.45	14.40	BEHL
	Scratch & Rumble Filter (Stereo)	H015S	2.90	18.45	BEHL
	HE Car Alarm	H016	1.20	8.35	BEHL
Mar 79	Light Chaser	H017	2.00	14.25	BEH
	Casanova's Candle	H018	1.10	5.95	BEH
	Tone Control	H019	1.00	8.80	BEGHL
	Photographic Timer	H020	1.25	9.95	BEGJL
Apr 79	Model Train Controller	H021	1.40	21.95	BEHL
	Cistern Alarm	H022	.80	2.20	BEHL
	Transistor Gain Tester	H023	.75	5.25	BEGHL
May 79	PSU	H024	1.93	TBA	TBA
	Parking Meter Timer	H025	.92	TBA	TBA
	Digitell	H026	1.35	TBA	TBA
	White Noise Generator	H027	1.67	TBA	TBA

KEY TO KIT CONTENTS

- A. Vero-board(s).
- B. Printed Circuit Board(s).
- C. With Screen printed component layout.
- D. Tag strip.
- E. All Resistors, potentiometers, capacitors, semi-conductors.
- F. As E but with exclusions. Please ask for details.
- G. Di1 and/or transistor sockets and/or soldercon pins.
- H. Hardware includes switches, knobs, lamps and holders, fuses and holders, plugs and sockets, microphones, transformers, speakers, meters, relays, terminal blocks, battery connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, batteries and special miscellaneous items.
- J. As H but with exclusions. Please ask for details.
- K. As H but including connecting wire.
- L. Suitable case(s).
- M. Suitable case with screen printed fascia.
- N. Full kit to magazine specified standards.
- P. Kit with professional finish — incorporating all prime features including screen printed pcb and case where appropriate.

Photocopy of any of listed Projects 30p.

SPECIAL OFFERS

Plug-in mains PSU 3v/6v/9v/12v DC 300MA. Suitable for calculators, TV Games, etc. £2.99
100 x 1/4W 1k resistors 30p
4 x ME 555 £1.00

Pcbs and kits available from TAMTRONIK LTD. for projects from ETI and EVERYDAY ELECTRONICS. Send sae for free catalogue. Please quote project and kit reference number when details of a specific kit are required, sae.

Tamtronik Ltd. reserves the right to change kit content without notice to incorporate current modifications or to make valid substitutions for temporarily unavailable components.

The majority of kits advertised can be supplied from stock, however please allow 21 days delivery since demand on any kit is unpredictable.

SOLDERING IRONS & ACCESSORIES

SRB 18 watt iron, incl. No. 20 bit	£3.78	Spare bits	44p
Stand	£3.25	BIT SIZES	
Solder - Saubit 20ft.	52p	No. 19 (1.5mm), No. 20 (3 mm), No. 21 (4.5mm), No. 21 (6mm).	
L.C. Desoldering bit	£1.00		

"IDEAL FOR THE HOME CONSTRUCTOR"

Visit our shop at Telephone or Letter

32 Market Place
Great Bridge, Tipton
West Midlands



Kits can be supplied excluding pcb and/or case. Send sae for details naming kit and kit reference and free catalogue.

P. & P. 30p

Prices include VAT

Trade and Educational enquiries welcome

Reader's Letters

Please send submissions for the letters page to: Hobby Electronics, 25-27 Oxford Street, London W1. Mark the envelope "Letters Page." Letters which are too long for publication will be suitably edited.

AIR PISTOLS

Dear Sir,

I have brought five editions of HE and have usually found something of interest in it. I made one of the Short Circuits (Power Supply with Transistor Regulation) and it works very well. The thing I like about it, is being able to adjust the voltage to precise limits.

I am not interested in Hi-Fi, Scratch Filters, Metal Locators, Train Controllers, Photo Timers and all this stuff which seem to appear in your rivals from time to time.

What I am interested in however are Air Rifles and Pistols and I would like to make an electronic chronograph to measure the muzzle velocity of a pellet as it is fired from the gun. So how about one, I've never seen such a circuit published before but they are available commercially.

E. Rawstron
Lancashire.

It's good to hear from someone who knows exactly what they want, unfortunately such a circuit is slightly out of our province, we try to aim for less specific projects. A quick word with our workshop confirmed that such a circuit would be extremely complex to build and calibrate but we're passing the idea on to our sister magazine ETI. Anyway keep on sending in your ideas, quite a few similar ideas, have, in the past resulted in actual projects.

INTO ELECTRONICS

Dear Sir,

I have only just discovered your magazine and find it very interesting, especially the article entitled 'Into Electronics' by Ian Sinclair. As I have only brought the April issue, I am wondering whether it is possible to obtain the five parts of this article which have appeared in previous issues.

G. McGowan
Huddersfield.

You must be blessed with second sight, we are trying to make some room in our back numbers department (see backnumbers ad. elsewhere in this issue) and we are bringing out an 'Into Electronics' special. Not only does it contain the whole 'Into Electronics' series but a selection of equally informative articles ranging from 'Audio Transducers' to 'Making your own PCB'. Price will be £1 and we expected it to be on sale within a couple of weeks.

SINE/SQUARE GENERATOR tipped as favourite

Dear Sir,

I assume that the output control labelling shown in the photograph is deliberate, indicating that in the stakes for the best runner in the 'Inexpensive Test Gear Handicap' the 'COURSE' control of HE Test Gear is the winner every time!

G. L. Macmillan
Bahrain (Arabian Gulf)

Glad to see you're on form, it's odds on that any mistake won't go unnoticed furlong. Now we're over that hurdle we hope we will not be saddled with any more unbridled letters of criticism over our spelling.

CAPACITORS

Dear HE

I read and enjoyed your article "Capacitors, The Inside Story", and was wondering whether you could do similar articles on Transistors, Resistors, Diodes and ICs in future editions.

Could you also include something on Oscilloscopes, Synthesizers and Microprocessors.

Jonathon Button
Littleton.

What a lovely man. Your wish is our command. 'Resistors' are scheduled for the July issue. As you will have seen Electronics in Music has been featured (May-June). As for the others they are in the pipeline but no firm date as yet.

PC BORED

Dear Sir,

I enjoy reading your magazine but there is one thing I would like to point out. This is the use of printed circuit boards in nearly all of your projects. These can be quite expensive to buy or make. Several expensive things have to be bought to make these including a small drill and etchants. So, in future it would be easier if you could use strip board for some of your projects.

C. Jackson,
North Yorkshire.

We have had quite a few letters recently on this subject. We really do believe a project looks neater, has a better chance of working and is easier to repair on a PCB but you are the bosses. In the coming issues we will feature at least one or two projects exclusively designed for Vero-Board fans.

QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M1

QUARTZ LCD 7 Function

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

£9.65

Guaranteed same day despatch.
Very slim, only 6mm thick.



M2

QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet.

Metac Price

£12.65 Thousands sold!

Guaranteed same day despatch.



M3

QUARTZ LCD ALARM 6 Function

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

QUARTZ LCD ALARM 7 Function

Hours, mins., secs., day, date, alpha day, back-light, auto calendar.

Adjustable stainless steel bracelet. Only 9mm thick.

£18.65

Guaranteed same day despatch.



M5

QUARTZ LCD Alarm Chronograph with Dual Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£24.65



M6

SOLAR QUARTZ LCD Chronograph with Alarm Time Zone Facility

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£27.65



M7

QUARTZ LCD Alarm Chrono

22 function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

£22.65

Guaranteed same day despatch.

METAC ★ PRICE



M8

SOLAR QUARTZ LCD Chronograph

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins.

Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

£13.65



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass.

List Price £130.00

METAC PRICE

£105.00



M10

SEIKO Chronograph

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap-time. Back light, stainless steel water resistant, HARDLEX glass.

List Price £85.00

METAC PRICE

£68.00



M11

SOLAR QUARTZ LCD 5 Function

Genuine Solar

Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.

£ 9.95

Guaranteed same day despatch.



M12

HANIMEX Electronic LED Alarm Clock



Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).

£8.65 Thousands sold!

Guaranteed same day despatch.

M13

QUARTZ LCD Ladies Slim Bracelet

5 function.

Hours, mins., secs., day, date and back light and auto calendar.

Elegant metal bracelet in silver or gold.

State preference.

£15.95

Guaranteed same day despatch.



M14

QUARTZ LCD Ladies 5 Function

Only 25 x 20mm and 6mm thick.

5 function. Hours, mins., secs., day, date and back light and auto calendar.

Elegant metal bracelet in silver or gold.

State preference.


£9.95

Guaranteed same day despatch.



M15

DIGITAL LED CLOCK

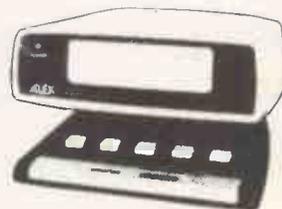

Automatic brightness control. Weekend alarm cancel.

Features and Specification: Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on-off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

£10.95

Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices — minimum order value £100.

Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME
Shops open 9.30 - 6.00.

Metac

ELECTRONICS
& TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753



A quality range of British made electrical accessories plus a 'How to' book. Do your own home electrical work with complete confidence. See cat. pages 129 to 134



This superb organ — build the first working section for just over £100. Full specification in our catalogue



A range of highly attractive knobs is described in our catalogue. Our prices are attractive too!



Mobile amateur radio, TV and FM aeriels plus lots of accessories are described in our catalogue



A pulse width train controller for smooth slow running plus inertia braking and acceleration. Full construction details in our catalogue.




A wide range of disco accessories at marvellous prices. Our catalogue has all the details.



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue



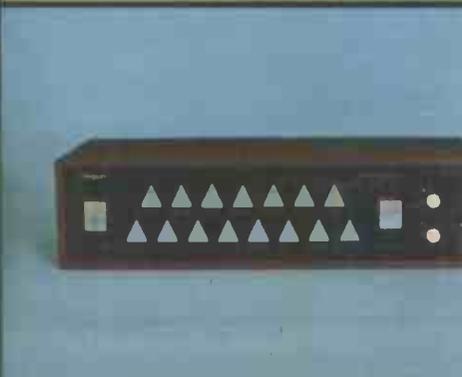The 3800 synthesiser, build it yourself at a fraction of the cost of one ready-made with this specification. Full details in our catalogues



Touch operated rhythm generator, the 'Drumette'. Construction details 25p (incl. VAT). Specification in our catalogue

MAPLIN


ELECTRONIC SUPPLIES LTD
 All mail to:—
 P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155.
 Shop: 284 London Road,
 Westcliff-on-Sea, Essex.
 (Closed on Monday).
 Telephone: Southend (0702) 554155.



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



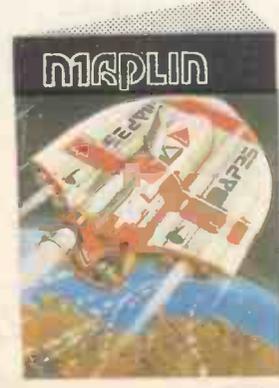An attractive mains alarm clock with radio switching function and battery. Complete kit with case only £13.88 (incl. VAT & p&p) MA1023 module only (incl. VAT)



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages—some in full colour—it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue

Post this coupon now for your copy of our 1979-80 catalogue price 75p.
 Please send me a copy of your 280 page catalogue as soon as it is published (8th Jan. 1979). I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME _____

ADDRESS _____