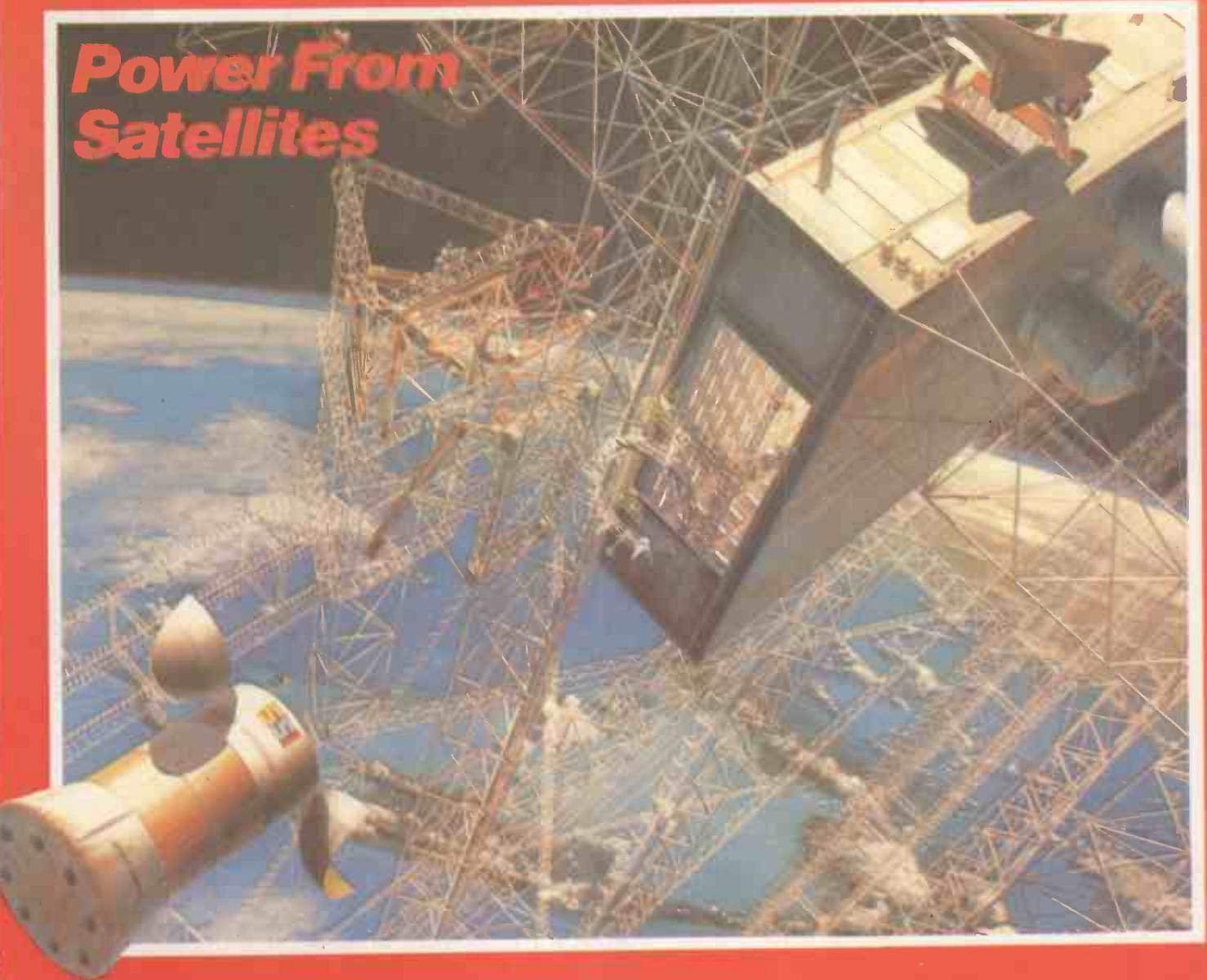


**August '79**  
**45p**

# Hobby Electronics

**Power From  
Satellites**



**Constant Volume Amp**

*Compressed Sound*

**Burglar Alarm**

*Preventive Medicine*

**Tools**

*Starting A Collection*

**Variable Resistors**

*A Potted History*

**Injector/Tracer**

*Simple Test Gear*

**Competition**


*Two Calscopes To Be Won*

# Tecknowledgey for sale.
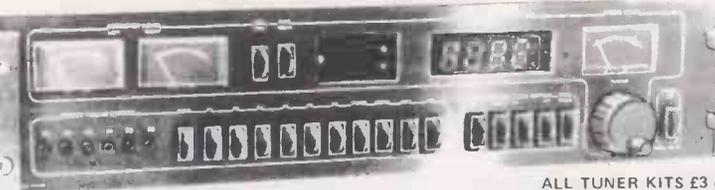
## The Mark III FM Tuner

DIY Hi-Fi will never seem the same again. Ambit's Mark III tuner system is electrically & visually superior to all others. Some options available, but the illustrated version with reference series modules:

£149.00 + £18.62 VAT  
With Hyperfi Series modules £185.00 + £23.12



ALL TUNER KITS £3 carriage

## Features of the system:

- \* Precision construction & design of all parts
- \* Time frequency display
- \* State of the art performance with facilities for updates, using modular plug in systems.
- \* Deviation level calibrator for recording
- \* All usual tuner features

## Digital Dorchester All Band Broadcast Tuner: LW/MW/SW/SW/FM stereo

A multiband superhet tuner, constructed using a single IC for RF/IF processing - but with all features you would expect of designs of far greater complexity. The FM section uses a three section (air gang) tuned FET tunerhead, with ceramic IF filters and interstermination; AM employs a double balanced mixer input stage, with mechanical IF filters - plus a BFO and MOSFET product detector for CW/SSB reception. Styled in a matching unit to the Mark III FM only tuner, employing the same degree of care in mechanical design to enable easy construction. MW/LW reception via a ferrite rod antenna.

Electronics only (PCB and all components thereon) £33.00 + £4.12 VAT  
Complete with digital frequency readout/clock-timer hardware £99.00 + £12.37 VAT  
Complete with MA1023 clock/timer module with dial scale £66.00 + £8.25 VAT

Hardware packages are available separately if you wish to house your own designs in a professional case structure. Please deduct the cost of electronics from complete prices.

## LW/MW/FM LCD Digital Frequency Display - July PW feature

Update your old radio, or build this into a new design. Or use it as a servicing aid - this low power unit with LCD display reads direct frequency in kHz/MHz, or with usual AM/FM IF offsets for received frequency. Low power LCD means no RFI - 15-20mA at 9v even with the divide by 100 prescaler. FM resolution is 100kHz, AM 1kHz. Sensitivities better than 10mV

Complete kit £19.50 + £1.56 VAT. Built and tested version £24.00 + £1.92 VAT  
Various other DFM systems described in our catalogue part 2 - including a one chip solution to providing digital display of FRG7 kHz dial, combined with clock/timers etc.



## PW SANDBANKS PI METAL LOCATOR

Maintaining our professional approach to home constructor kits, we offer the pulse induction 'Sandbanks'. Now with injection molded casing for greatly improved environmental sealing. £37.00 + £2.96vat.

## VHF MONITOR RX WITH PLESSEY IC

4/9 channel version of the PW design - but using standard 3.1k OT crystals, and TOYO 8 pole crystal filter with matching transformers. Coil sets from our standard range to cover bands from 40 to 200MHz. Complete module kit £31.25 + £3.90vat.

## ETI - REMCON RADIO CONTROL

A tried and tested RC system with a full set of supporting hardware from a well known manufacturer. Please send for details - and watch our ads for further news of developments in RC products.

## Radio and Audio Modules : The biggest range/ best specs:

EF5801/3/4 6 stage varicap tunerheads with LO feed and various levels of sophistication. New 5804 include pin AGC loop 'on board'. 5801: £17.45 + £2.18vat - 5803: £19.75 + £2.47vat - 5804: £24.95 + £3.18vat. Frequencies in 40-180MHz on approx.

EF5402 4 stage varicap with TDA1062, compound FET/Bipolar input stage, low noise, balanced mixer, pin agc, osc output. A worthy successor to the 5400. £10.75 + £1.34vat

The 5402 is available centred on a wide range of frequencies from 30MHz to 180MHz. Non standard units £14.75 + £1.84 - 3 weeks.

8319 4 stage varicap tunerhead from Larsholt using MOSFET RF and mixer stages. New temperature compensated oscillator for wide ranges of ambient temperature. £13.45 + £1.68vat

7252 Complete Larsholt FM tuner less stereo decoder. £26.50 + £3.31vat

7253 Stereo FM tuner from Larsholt with FET head. (as 7252) £24.37 + £2.92vat

944378 Hyperfi stereo decoder. The very best. £19.95 + £2.49vat

911223 Pilot cancel stereo decoder, priced to make the MC1310 as obsolete as it now deserves to be. £12.50 + £1.56vat

Inotec 1-A fully DC tuned and switched LW/MW/FM stereo tuner to interface with synthesiser control etc. A first! Details O/A

OSTS: Remember all OSTs stocks are obtained from BS9000 approved sources - your assurance that all devices are very best first quality commercial types. Some LPSN TTL is presently in great demand, so please check by phone before ordering.

## TTL: Standard AND LP Schottky

N'		LSN'		N'		LSN'		N'		LSN'			
7400	13	20	7455	35	24	74126	57	44	74185	134	74377	124	
7401	13	20	7460	17		74128	74		74188	275	74378	130	
7402	14	20	7463		124	74132	73	78	74190	115	92	74379	93
7403	14	20	7470	28		74133		29	74191			74380	37
7404	14	24	7472	28		74136		40	74192	105	180	74390	140
7405	18	26	7473	32	38	74139		60	74194	105	187	74391	140
7406	38		7474	27	38	74139		60	74195	95	137	74395	139
7407	38		7475	38	40	74141	56		74196	99	110	74396	133
7408	17	24	7476	37	38	74142	265		74197	85	110	74398	180
7409	17	24	7478		38	74143	312		74198	150		74445	92
7410	15	24	7480	48		74144	312		74199	160		74447	90
7411	20	24	7481	86		74145	65	97	74200			74490	140
7412	17		7482	69		74147	175		74201			74496	110
7413	30		7483A		110	74148	109	191	74202			74497	249
7414	51		7484	97		74150	93		74203			74670	249
7415	30	24	7485	104	99	74151	64	84	74251	90			
7416	30		7486	104	99	74153	64	54	74253	103			
7417	30		7489	205		74154	96		74257				
7420	16	24	7490	33	90	74155	54	110	74258				
7421	29	24	7491	76	110	74156	80	130	74259				
7422	24	24	7492	38	78	74157	67	55	74260				
7423	27		7493	32	99	74158		60	74261				
7425	27		7494	78		74159	210		74262				
7426	36	27	7495A	65	99	74160	82	130	74263				
7427	27	29	7496	58	120	74161	92	78	74275				
7428	35	32	7497	185		74162	92	130	74278				
7430	17	24	74100	119		74163	92	74	74283				
7432	25	24	74104	63		74164	104	130	74290				
7433	42	32	74105	69		74165	105		74291				
7437	40	24	74107	32	38	74166			74293				
7438	33	24	74109	63	38	74167	20		74295				
7440	17	24	74110	54	54	74168			74296				
7441	74		74111	68		74169			74297				
7442	70	99	74112		38	74170	230	200	74324				
7443	115		74113		38	74172	625	247	74325				
7444	112		74114		38	74173	170		74326				
7445	94		74116	198		74174	87	120	74352				
7446	94		74118	83		74175	87	110	74353				
7447	82	89	74119	119		74176	75		74362				
7448	56	99	74120	115		74177	78		74365				
7449	99		74121	25		74180	85		74366				
7450	17		74122	46	57	74181	165	350	74367				
7451	17	24	74123	48	73	74182	160		74373				
7453	17		74124	32	137	74183			74374				
7454	17	24	74125	38	44	74184	135	210	74375				

IMPORTANT: ALL OSTS PRICES EXCLUDE VAT. CURRENTLY 8% - BUT MAY BE CHANGED BY THE TIME YOU READ THIS. PLEASE REMEMBER TO ADD VAT, and 25p POSTAGE !!

## CD4000 CMOS

4000	17p	4059	563p	4522	149p
4001	17p	4060	115p	4527	157p
4002	17p	4063	109p	4528	102p
4006	109p	4066	53p	4529	141p
4007	18p	4067	400p	4530	90p
4008	80p	4068	25p	4531	141p
4009	58p	4069	20p	4532	125p
4010	58p	4070	20p	4534	614p
4011	17p	4071	20p	4536	380p
4012	17p	4072	20p	4538	150p
4013	55p	4073	20p	4539	110p
4014	95p	4074	20p	4541	141p
4016	52p	4075	20p	4543	174p
4017	80p	4076	90p	4549	399p
4018	80p	4077	20p	4553	440p
4019	60p	4078	20p	4554	153p
4020	93p	4081	20p	4554	153p
4021	82p	4082	20p	4556	77p
4022	90p	4085	87p	4557	386p
4023	17p	4086	117p	4558	117p
4024	75p	4089	150p	4559	388p
4025	17p	4093	50p	4560	218p
4026	180p	4094	190p	4561	65p
4027	55p	4096	105p	4562	530p
4028	72p	4097	372p	4566	159p
4029	100p	4098	110p	4568	281p
4030	58p	4099	125p	4569	303p
4031	250p	4100	90p	4572	25p
4032	100p	4101	90p	4580	600p
4033	145p	4102	90p	4581	319p
4034	200p	4103	90p	4582	164p
4035	120p	4174	104p	4583	84p
4036	250p	4175	95p	4584	63p
4037	100p	4501	23p	4585	100p
4038	105p	4502	91p		
4039	250p	4503	69p		
4040	83p	4506	51p		
4041	90p	4507	55p		
4042	85p	4508	248p		
4043	85p	4510	99p		
4044	80p	4511	149p		
4045	150p	4512	95p		
4046	130p	4513	206p		
4047	99p	4514	260p		
4048	60p	4515	300p		
4049	55p	4516	125p		
4050	55p	4517	382p		
4051	65p	4518	103p		
4052	65p	4519	57p		
4053	65p	4520	109p		
4054	120p	4521	236p		
4055	135p				

## Micromarket

6800 series	8216	1.95	2114	110
	8224	3.50	2708	1
6800P	6.50			
68201	6.0			
6850P	2.75			
6810P	4.4			
6852	3.65			
8080 series	2102	£1.70		
8080	6.30	£3.40		
8212	2.30	£7.54		
	4072	£5.78		

Development  
ME K6800 £220  
TK80 £306  
AMI Signetics  
TI Incelec  
Harris etc. OA

MISC. LSI/Scalars/DVMs  
NE555 30p NE556 75p NE558 180p  
LM3909 72p 95H90UC 120MHz / 80p  
11C90DC 650MHz £14.00  
ICM7166PI 8 decade 10MHz DFM/timer with direct LED drive and all counter features £19.82  
ICM7217A/B 4 decade programmable count £9.50  
ICM7207 clock pulse generator IC £4.95  
ICM7208 7 decade counter/display driver £14.95  
ICM7106CP LCD DVM IC (3 1/2 digit) £9.55  
ICM7106CPK LCD DVM KIT £24.80  
ICM7107CP LED DVM IC £9.55  
ICM7107CPK LED DVM KIT £20.65  
SP629 250p by 100 200MHz scalar £4.20  
M2318 1/2 (divide by 100 to 175MHz) £4.20  
M2318 1/2 (divide by 10 to 45MHz) £4.20

PLEASE REMEMBER TO ADD 8% VAT TO ITEMS LISTED UNDER OSTs

## LINEARS non consumer

BIMOS	LM324N	71p	
CA3130E	84p	LM339N	60p
CA3130T	90p	LM348N	186p
CA3140E		LM3909N	60p
CA3140T	72p	709HC	64p
CA3160E	90p	709PC	65p
CA3160T	99p	710MC	65p
Op amps	710PC	65p	
LM301A	67p	723CN	300p
LM301AN	30p	741CN	60p
LM308H	121p	741CN	80p
LM308H	91p	741CN	70p
LM318H	279p	748CN	36p
LM318N	224p	NE531T	120p
		NE531N	105p

0.43" High Efficiency HP:  
5082 /650 red CA  
5082 /653 red CA  
5082 /650 yellow CA  
5082 /766.3 yellow CC  
5082 /760.3 yellow CA  
5032 /673 green CA  
5032 /673 green CA

0.3" Standard HP  
5082 /730 red CA  
5082 /740 red CA  
5082 /740 red CA  
0.5" Fairchild  
FND500 red CA 150p  
FND507 red CA 150p

Current news: Work continues apace on our HMOS PA kit, and by the time this is published - we expect to be about to launch the product in a style that matches the Mark III system. The unit uses separate transformers and power supplies, and includes a DC offset sensing circuit combined with slow switch-on using a relay. We introduce the HyperFi FM IF with this advert - and a separate leaflet is available on request with an SAE. All new precision revision also available with an SAE. The Mullard DC controlled tone/volume and switch ICs with a 'more than HiFi' specification are in stock at last - together with reams of data (over 50 pages now). Also, RC enthusiasts will be interested to learn that we are supplying parts for various kits now.

Terms: CWO please. Account facilities for commercial customers O/A. Postage 25p per order. Minimum credit invoice for account customers £10.0

# Hobby Electronics

Vol. 1. No. 10

August 1979

**Monitor** ..... 6 **Short Circuits** . 28, 50, 57, 66 **Injector/Tracer** ..... 48  
Experiments and ideas


**Home Security System** .... 8 **Breaker One-Four** ..... 29



Protect your interests




Latest CB news

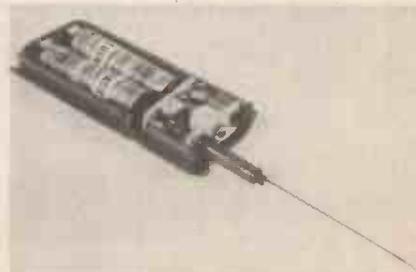

Inexpensive test gear

**Security Installations** ..... 14 **Competition** ..... 30 **Hobby Chit-Chat** ..... 53  
Where the wires go The LM 380 explained

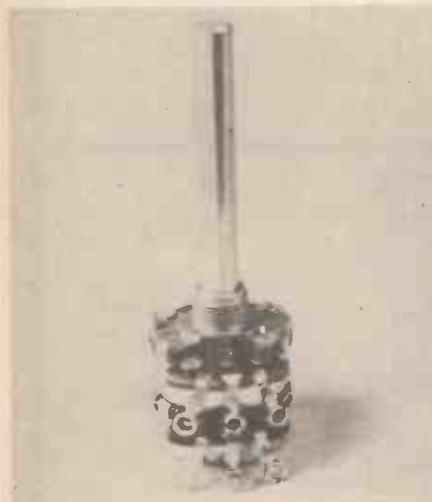**Variable Resistors** ..... 18 **Next Month's HE** ..... 32 **Specials** ..... 58  
Don't miss it Best sellers



Pot slot

**Tools** ..... 33



A beginners guide

**Clever Dick** ..... 59  
Your questions answered

**Backnumbers** ..... 60  
Don't miss out

**Constant Volume Amplifier** 61



Another audio project

**Kit Review** ..... 22 **Next Month's ETI** ..... 45 **Tee-Shirts** ..... 65  
A timely kit Brainy people only Adorn your body

**LED Tachometer** ..... 24 **Market Place** ..... 46 **HE Book Service** ..... 67, 74  
Rev up with this one Sales all year round A voluminous choice

**Into Linear ICs** ..... 74  
Soldering iron time

**Hobby Electronics**  
145 Charing Cross Road,  
London WC2 HOE  
01-437 1002 (4 lines)

**Published** by Modmags Ltd,  
**Distributed** by Argus Distribution Ltd,  
**Printed** by QB Ltd, Colchester  
Hobby Electronics is normally published  
on the second Friday of the month prior  
to the cover date

**Editor:** Halvor Moorshead  
**Editorial Asst:** Richard Maybury  
**Project Team:** Ray Marston, Steve Ramsa-  
hadeo, John Fitzgerald, Keith Brindley  
**Production:** Diego Rincon, Pete Howells.  
**Technical Artists:** Paul Edwards, Tony  
Strakas  
**Advertising:** Chris Surgenor, David Sinfield,  
Joy Cheshire, Sandie Neville  
**Admin Staff:** Margaret Hewitt, Bren Good-  
win, Tim Salmon, Neville MacDonald, Tracey  
Campbell, Loraine Radmore, Marlin Felix.

**Copyright.** All material in this publication is  
subject to world-wide copyright protection.  
Permission to reproduce printed circuit board  
patterns commercially or marketing kits of the  
projects must be sought from the Editor. All  
reasonable care is taken in the preparation of  
the magazine to ensure accuracy but Mod-  
mags cannot be held responsible for it legally.

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

CAPACITORS				Electrolytic Can Type				Miniature Low Value							
Electrolytic Axial Leads -10% to +50% Tol				High Ripple, IEC Grade 1, Low E.S.R. Supplied complete with Vertical Flating Clip				Polyethylene, A, B, 11% Tol., > 63V D.C. Wkg Ceramic Plate, Radial, Low K, 1.8pF - 8.2pF F 25pF Tol, 10-330pF 12% Tol, 100V D.C. Wkg Ceramic Plate, Radial, Med K, 110% Tol, 100V D.C. Wkg Ceramic Plate, Radial, High K, -20% to +80% Tol, 63V D.C. Wkg							
µF	V d.c.	16	25	2200 µF 16V	1.4A @ 85°C	1.4A @ 50°C	166	pF	424	632	630	µF	424	632	630
1.0			40	4700 µF 16V	2.8A	3.6A	184	1.2				100	16	6	10
1.5			8	10000 µF 16V	5.8A	8.1A	222	1.5				120	16	8	12
2.2			8	22000 µF 16V	9.8A	13.7A	346	1.8	5			150	16	8	15
3.3			8	2200 µF 25V	1.3A	1.8A	175	2.2	5			180	16	6	18
4.7			8	4700 µF 25V	4.6A	6.4A	201	2.7	5			220	16	6	22
6.8			8	10000 µF 25V	8.0A	11.2A	264	3.3	5			270	18	8	27
10			9	22000 µF 25V	12.8A	17.9A	438	3.9	5			330	18	8	33
15			10	1000 µF 40V	0.9A	1.2A	168	4.7	5			390	18	5	39
22			12	2200 µF 40V	2.4A	3.3A	188	5.6	5			470	18	5	47
33			12	4700 µF 40V	5.6A	7.8A	231	6.8	5			560	16	5	56
47			12	10000 µF 40V	9.2A	12.8A	367	8.2	5			680	16	5	68
68			12	1000 µF 70V	1.8A	2.5A	190	10	5			820	16	5	82
100			12	2200 µF 70V	4.0A	5.6A	235	12	5			1000	16	5	1000
150			12	4700 µF 70V	7.5A	10.5A	376	15	5			1200	16	5	1200
220			12	10000 µF 70V	10.0A	14.0A	468	18	5			1500	16	5	1500
330			12	2200 µF 100V	4.0A	5.6A	222	22	5			2200	16	5	2200
470			12	4700 µF 100V	7.8A	10.9A	346	27	5			3300	16	6	3300
680			12					33	5			3900	16	6	3900
1000			12					39	5			4700	23	6	4700
1500			12					47	5			5600	23	7	5600
2200			12					56	5			6800	23	7	6800
								68	5			8200	23	7	8200
								82	5						

Tantalum Bead				Order Code			
-20% Tol.				Cap PR ± µF ± Volts			
µF	V d.c.	3.15	6.3	10	16	25	35
0.1				9			
0.15				9			
0.22				9			
0.33				9			
0.47				9			
0.68				9			
1				9			
1.5				10			
2.2				11			
3.3				11			
4.7				11			
6.8				11			
10				14			
15				14			
22				14			
33				16			
47				16			
68				20			
100				20			

Electrolytic Radial Leads				Order Code			
-10% to +50% Tol.				Cap O34 ± µF ± Volts			
µF	V d.c.	6.3	10	16	25	35	40
0.1				6			
0.15				6			
0.22				6			
0.33				6			
0.47				6			
0.68				6			
1				6			
1.5				6			
2.2				6			
3.3				6			
4.7				6			
6.8				6			
10				6			
15				6			
22				6			
33				6			
47				6			
68				6			
100				6			

Polyester Radial Leads				Order Code			
Dipped Type, ±20% Tol., > 250V D.C. Wkg, C280/352 Style				Cap 352			
Moulded Type, ±10% Tol., >100V D.C. Wkg, 10.2mm Pitch Centres				Cap 360			
Moulded Type, ±10% Tol., >100V D.C. Wkg, 7.6mm Pitch Centres				Cap PHE280			
µF	352	360	PHE280	µF	352	360	PHE280
.001	5	6		.1	6	8	9
.0015	5	6		.15	7	9	
.0022	5	6		.22	8	10	
.0033	5	6		.33	10		
.0047	5	6		.47	12		
.0068	5	6		.68	15		
.01	5	6		1.0	19		
.015	5	6		1.5	27		
.022	5	6		2.2	32		
.033	5	6		3.3	38		
.047	5	6		4.7	44		
.068	5	6		6.8	52		

Cases				Order Code			
Small Desk Console - Boss Industrial Mouldings				Slope Front Console, Recessed Top			
ABS Base, C/W Brass Bushes, In Orange				1mm Aluminium Top Panel Finished Grey			
W161, D36, H39	186	Case BIM1005 OR					
W215, D130, H47	268	Case BIM1006 OR					
Plastic Boxes - Boss Industrial Mouldings				Moulded Box and Close Fitting Flanged Lid			
ABS Box, C/W Brass Bushes, and Lid In Orange				Order Code			
L112 W62 D31	87	Case BIM2003 OR					
L150 W60 D50	115	Case BIM2005 OR					
L190 W110 D60	195	Case BIM2006 OR					
Instrument Case - Boss Industrial Mouldings				Covers Manufactured from 14SWG Aluminium			
Chassis Manufactured from 18SWG Mild Steel				Covers Finished Orange			
Chassis Finished Matt Black				Order Code			
W250 D167.5 H 68.5	1480	Case BIM3000 DR					
Plastic Boxes with Metal Lids - Boss Industrial Mouldings				Recessed Top Box			
ABS Base, C/W Brass Bushes, In Orange				1mm Aluminium Top Panel Finished Grey			
L85 W56 D29	97	Case BIM4003 OR					
L111 W71 D42	130	Case BIM4004 OR					
L161 W96 D53	182	Case BIM4005 OR					
Diecast Boxes - Boss Industrial Mouldings				Diecast Box and Flanged Lid			
Aluminium Box and Lid in Natural Finish				Order Code			
L113 W63 D31	104	Case BIM5003 NA					
L152 W82 D50	181	Case BIM5005 NA					
L192 W113 D61	280	Case BIM5006 NA					

VERO ELECTRONICS PRODUCTS				Order Code			
2.5" x 5", .1" pitch Vero-board				59			
3.75" x 5", .1" pitch Vero-board				66			
2.5" x 1", .1" pitch Vero-board (S)				70/Pack			
3.75" x 5", .1" pitch Plain Board				56			
2.5" x 5", .1" pitch V-DIP Board				111			
Spot Face Cutter				89			
Pin Insertion Tool for .040 type pin				122			
OS Pins, .040 (100)				38/Pack			
SS Pins, .040 (100)				38/Pack			
5mm Board Standoff (100)				181/Pack			
15mm Board Standoff (100)				215/Pack			
19mm Board Standoff (100)				226/Pack			
Vero-wire Kit (1 pan, 2-wire, 25-comb)				375/Kit			
Vero-wire Combs (100)				407/Pack			
Vero-wire Wire (4)				226/Pack			
Flip Top Box, Small, Black				192			
Flip Top Box, Large, Black				250			
VERO 21069J				VERO 21069J			
VERO 21072D				VERO 21072D			
VERO 21076C				VERO 21076C			
VERO 21078E				VERO 21078E			
VERO 21084E				VERO 21084E			
VERO 21013A				VERO 21013A			
VERO 21015F				VERO 21015F			
VERO 21087G				VERO 21087G			
VERO 21017B				VERO 21017B			
VERO 21321K				VERO 21321K			
VERO 21322G				VERO 21322G			
VERO 213230				VERO 213230			
VERO 21341D				VERO 21341D			
VERO 21339F				VERO 21339F			
VERO 21340G				VERO 21340G			
VERO 21317D				VERO 21317D			
VERO 21319J				VERO 21319J			
Small Desk Console - Boss Industrial Mouldings				Slope Front Console, Recessed Top			
ABS Base, C/W Brass Bushes, In Orange				1mm Aluminium Top Panel Finished Grey			
Ventilation Slots In Base				Order Code			
W105 D143 H32	156	Case BIM5005 OR					
W170 D143 H32	156	Case BIM6006 OR					
W170 D214 H32	182	Case BIM6007 OR					
All Metal Desk Consoles - Boss Industrial Mouldings				Slope Front Console, Recessed Top			
Two Face All Aluminium Construction				Ventilation Slots In Rear and Base			
Choice of 15° or 30° Sloping Front				Off White Top Panel, Blue Base			
W102 D140 H28	151	15° slope	1018	Case BIM7151A			
W165 D211 H33	176	15° slope	1350	Case BIM7154A			
W254 D287 H33	178	15° slope	1572	Case BIM7156A			
W356 D287 H33	178	15° slope	1823	Case BIM7158A			
W102 D140 H28	178	30° slope	1018	Case BIM7301A			
W165 D183 H28	182	30° slope	1202	Case BIM7303A			
W254 D258 H28	182	30° slope	1572	Case BIM7306A			
W356 D258 H28	182	30° slope	1823	Case BIM7308A			
Eurocard Size Desk Console - Boss Industrial Mouldings				Slope Front Console			
ABS Case, C/W Brass Bushes, In Orange				1mm Aluminium Top Panel, Finished Grey			
W169 D127 H45	170	375	Case BIM8006 OR				

Hardware				Order Code			
O.I.L. Sockets				8 Pin Low Profile Socket Tin			
14 Pin Low Profile Socket Tin				11			
16 Pin Low Profile Socket Tin				13			
24 Pin Low Profile Socket Gold				14			
28 Pin Low Profile Socket Gold				66			
40 Pin Low Profile Socket Gold				78			
Heatsinks				Individual Type for 1 x T05 50°C/W			
Individual Type for 1 x T06 10.5°C/W				10			
Individual Type for 1 x T03 7.2°C/W				26			
Individual Type for 1 x T0126 17°C/W				23			
Individual Type for 1 x T0220 17°C/W				23			
P.C.B. Components				Data Pen, Blue Ink, Slow Drying			
				92			
Fuseholders				Sult 20mm x 5mm Jags			
				8			
F.C.B. Mounting, Open Type				Fuse/H208			
Chassis Mounting, Open Type				Fuse/H20C			
Panel Mounting, Screwdriver Slot				Fuse/H20P			
Panel Mounting, Finger Release				Fuse/H20P			
Fuses				20mm x 5mm Glass			
Quick Blow, Range 100mA-5A				8			
Slow Blow, Range 250mA-5A				22			
				+ Rating			
Lampholders, Panel Mounting				Similar In Style to Fuse/H 20P			
Low Voltage Type Suits LES and M/F Bulbs							
Low Voltage, Red, Amber or Green				75			
Internal Neon 200/240V Red or Amber				95			
				+ Colour			
Bulbs, Low Voltage, L.E.S.				6V, 0.36W; 6.5V, 1W; 14V, 0.75W.			
				22			
				+ Voltage			

RESISTORS				Order Code			
Carbon Film, Fixed				0.25W, E24 Values IRD-10M, 5% Tol.			
0.5W, E12 Values IRD-4M7, 10% Tol.				1.5 ea. 90p/100 (Mult 10/Value)			
				E7.90/1000 (Mult 100/Value)			
				E10.10/1000 (Mult 100/Value)			
				Res RD4			
				+ Value			
Metal Film, Fixed				0.5W, E24 Values SR1-M, 2% Tol.			
2.5W, E12 Values 10R-27K, 5% Tol.				6 ea. 3.80/100 (Mult 10/Value)			

- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES
- ADD 30p P&P
- 24 HR TELEPHONE ANSWERING SERVICE

# GMT ELECTRONICS B

## Freepost Birmingham B19 1BR

TEL ORDERS WELCOME

### DIGITAL INTEGRATED CIRCUITS

4000 Buffered C-MOS - High Speed  
5-15V 'B' Series Up to 20MHz

7400 T.T.L.			
HEF4000	14	HEF4046	100
HEF4001	14	HEF4047	87
HEF4002	14	HEF4048	28
HEF4006	95	HEF4050	88
HEF4007	14	HEF4051	69
HEF4008	80	HEF4052	72
HEF4011	14	HEF4053	72
HEF4012	14	HEF4066	37
HEF4013	32	HEF4067	380
HEF4014	-84	HEF4068	14
HEF4015	60	HEF4069	14
HEF4016	35	HEF4070	14
HEF4017	65	HEF4071	14
HEF4018	65	HEF4072	16
HEF4019	46	HEF4073	16
HEF4020	88	HEF4075	16
HEF4021	85	HEF4076	85
HEF4022	92	HEF4077	14
HEF4023	14	HEF4078	16
HEF4024	45	HEF4081	16
HEF4025	14	HEF4082	16
HEF4027	32	HEF4085	64
HEF4028	52	HEF4086	64
HEF4029	60	HEF4092	60
HEF4030	46	HEF4094	175
HEF4031	200	HEF4104	166
HEF4035	110	HEF4502	91
HEF4040	60	HEF4505	571
HEF4041	75	HEF4508	51
HEF4042	54	HEF4510	70
HEF4043	79	HEF4511	110
HEF4044	84	HEF4512	98
HEF4514	250	HEF4515	299
HEF4516	90	HEF4517	382
HEF4518	69	HEF4519	55
HEF4521	65	HEF4522	99
HEF4523	120	HEF4524	510
HEF4534	110	HEF4539	110
HEF4543	155	HEF4544	171
HEF4555	78	HEF4556	78
HEF4557	386	HEF4558	97
HEF4559	97	HEF4560	171
HEF4562	171	HEF4563	171
HEF4564	119	HEF4565	119
HEF4566	119	HEF4567	119
HEF4568	119	HEF4569	119
HEF4998	119	HEF4999	119
HEF5000	1		

# Monitor




## EDIBLE MEMORIES

There was talk some years ago of making certain parts of space-craft from edible material (seriously) so in the event of an accident the luckless astronauts could survive by eating non-essential equipment until help arrived. Today we have definite proof of this advance in the shape of edible ICs. They're called 'Silly-Con-Chips' and according to the manufacturers 'Hannah's of Johnstone', they are coated with

'pearl of wisdom', the more you eat the wiser you get. We get to hear of most new advances but we must admit defeat over this one, an educated guess from one of our experts assures us that they're a development of bubble (gum?) memories.

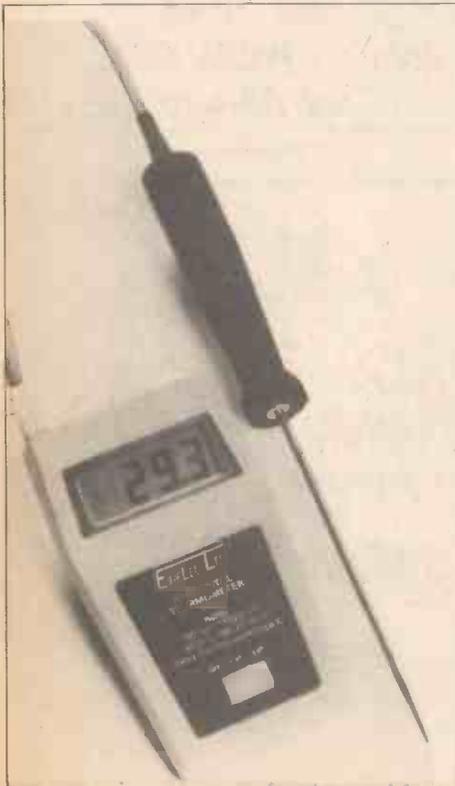Being diligent researchers we decided to put these new devices to the test, we ate the lot, the things we do for HE.



## IRISH THERMOMETER

Have you heard the one about the Irish digital thermometer it had three digits, to be sure, to be sure. Sorry about that, especially to all our Irish readers, it was an old joke after all. Anyway back to business, the Digital thermometer we're featuring really does come from the Emerald Isle its made by EireLec Ltd. They boast an impressive range of features, the range for instance is from  $-150^{\circ}\text{C}$  to  $+1150^{\circ}\text{C}$  to an accuracy of 0.2% of reading.

The instrument is based upon a purpose designed CMOS IC, the IC is responsible for linearisation of the thermocouple input (Vot, no thermistor??), auto zeroing, indication of probe failure (a bit pessimistic) and battery check.

The power department is looked after by our old friend the venerable PP3, it's interesting to see they've made the resolution switchable for either  $0.1^{\circ}\text{C}$  or  $1.0^{\circ}\text{C}$ , the thermometer comes complete with warranty and a choice of either thermocouple (at last!) or platinum resistor probe. Interested? Then EireLec will be only too glad to help, you can find them at: Coe's Road, Dundalk, Co Louth, Ireland.

## CB AGAIN

We actually received a press release from the CBA this month, inside was a copy of a letter sent to the PM, and guess what a reprint of an article from *Cu...om...C.r* magazine. Huh...

## OPEN LETTER TO HE

We are dismayed that you have encouraged an illegal network of CB operators with scant reference to the hazardous effect on the legitimate users of the 27 MHz waveband.

While we recognise the value of CB as a genuine hobby interest and support your claim for legislation of an authorised channel, we condemn any policy which is calculated to seek recognition by swamping the established licensees. Many valuable models have already been lost to interference, some at risk to life and limb. Any encouragement on your part to sustain this intrusion into the established rights of a law abiding community will be seen through the eyes of the modellers as an irresponsible act of aggression. Only by concerted action on the part of recognised Associations and the Government Authority can we possibly hope to recover from this clash of interests, and for our part, the Model Associations and the Trade Federation are already fully engaged in discussions.

The Editors  
Radio Control Models and Electronics

## ACID TEST?

For those of you not familiar with chemistry, it's possible to measure electronically the strength of acids and alkalis. The concentration of these substances are measured in pH units on a scale of 0-14. Semat Ltd have just introduced a new range of digital and analogue pH meters.

Pictured here is the CD 60 LCD meter with a 13mm display. The quoted accuracy is in the order of 0.02 pH units when used with standard electrodes. Other products in their range include a large bench version which also incorporates a millivoltmeter, both instruments are available with either LED or LCD display elements. For further information contact Semat (UK), 89 Lakeside Road, London N13 4PS.



## BUBBLE ETCHER

It's not our fault, really, the price for the Bubble Etcher in last month's Monitor (from Mega Electronics) should have read £55 + Post and Packing + VAT (at 15%).

# News from the Electronics World



## HIGH TECHNOLOGY TEA TRAYS

Following in the success of Du-Ponts coating for frying pans to enable them to withstand the tremendous heat of re-entry from earth orbit, Siemens have developed a range of tea trays that actually generate their own electricity. They claim that in bright sunlight they will develop over 15 watts, most impressive. As with most new technology precise applications are somewhat confused but we're sure it will prove to be another boon to the housewife.

## POSTAL DELAYS

Anyone whose sent us any letters or orders may have experienced delays. We have noticed that even 1st class letters have taken up to four weeks to get in. This is due to the well publicized Post Office problems — and we're in the worst-affected area.

## MASSIVE CALCULATOR SHORTAGE

It looks like the calculator industry has folded at last. For the first time in living memory we haven't received one single calculator. We should have seen it coming, we got nothing from Casio last month, and that's got to be a worlds first (or last). So if any calculator manufacturers are still in business why not drop us a line and tell us about any redundant stock you may have going cheap.

## WE'VE MOVED


By the time you read this we will have moved, along with our sister magazines Electronics Today International and Computing Today to larger offices in Charing Cross Road. The new offices are only about 100 yards from our old Oxford Street offices. Our new address is: 145 Charing Cross Road, London WC2H 0EE. Our new phone number for Technical queries etc is 01-437 1002 (4 lines).

## NEW CATS FOR OLD

Stevenson Ltd, component suppliers of this parish have just sent us their latest catalogue. Good to see it has got considerably fatter due to their increased range. When we reviewed the last catalogue from Stevenson in our April issue it came out as one of the best for value, glad to see that hasn't changed. It's still free on request, send your name and address to: Stevenson, 76 College Road, Bromley, Kent BR1 1DE.
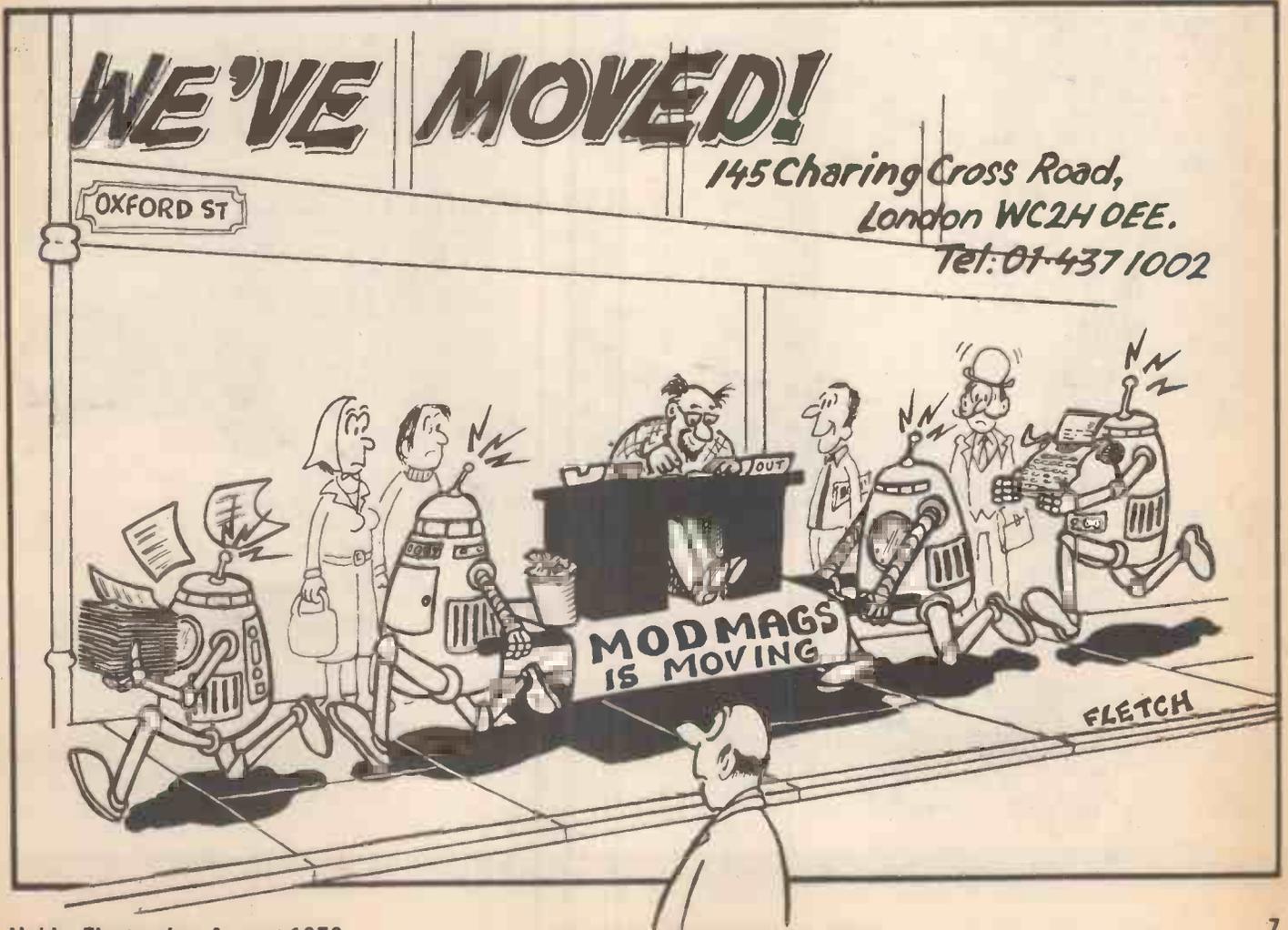
## JAWS IN TIME

We forgot to credit last months cover photo of the Shark to Ardea Ltd and Ron Taylor who took the pic, sorry about that.



# Home Security System

***Protect your private castle against fire, thieves, thugs and thingies with this HE anti-disaster unit.***

THE HE HOME SECURITY UNIT forms the heart of a general-purpose house or office protection system. When it is coupled to suitable input sensors (microswitches, pressure mats, window foil, thermostats, etc) and an output sound generator (a siren or bell) it gives a high degree of protection against burglars and frontdoor thugs, as well as giving fire protection.

The unit is designed around a single low-cost CMOS chip, and draws a very low quiescent current from its HP1 12 volt battery power supply. Particular care has been taken to ensure that the design has good operational reliability, and consequently it has a high degree of immunity against false alarms from lightning strikes, radio interference, etc.



***The HE valuables amassed together, we had to scour the offices for this little lot, burglars please note we've installed the system in our new offices, so beware, it works very well.***

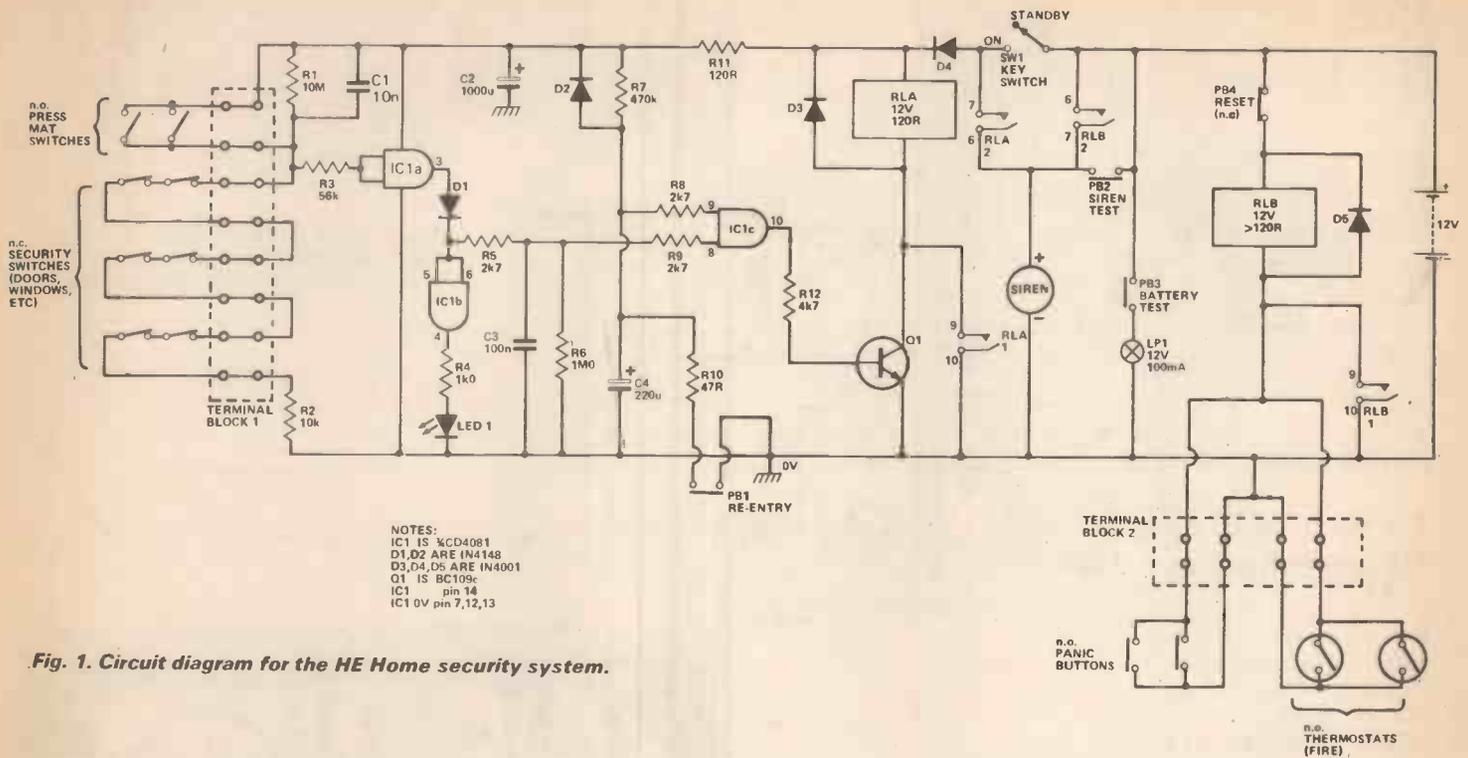


Fig. 1. Circuit diagram for the HE Home security system.

## How It Works

The circuit of the unit can be broken down into two discrete sections, with the PANIC and FIRE alarm circuitry to the right of SW1, and the burglar alarm system to the left. The panic and fire section of the unit is permanently enabled, and basically comprises relay RLB and the parallel-connected normally-open fire and panic 'switches', which are wired in series with the coil of RLB across the power supply. If any of these switches become closed the relay turns on and is self-latched via contacts RLB/1, and activates the siren via contacts RLB/2. Relay RLB can be unlatched and turned off again, provided that all sensor switches are open, by momentarily opening normally-closed RESET switch PB4. The siren can be given a non-latching test at any time by closing PB2, and the battery condition can be roughly checked via LP1 by closing PB3.

The anti-burglar section of the unit is designed around IC1-Q1 and relay RLA, and is supplied with power via the D4-R11-C2 decoupling and smoothing network, which ensures that the circuit is not adversely affected by large supply line transients generated by the siren. IC1 is a CD4081 quad 2-input AND gate CMOS chip. Only three of the available gates of the IC are used in this application.

IC1a is used as a high-impedance non-inverting input buffer. It's input (and output) is normally held at near-zero volts via R1-R2 and the normally-closed security switches, but is pulled

high via R1 if any of the NC switches go open circuit, or is pulled high directly if any NO input switches are closed. The output of IC1a is fed to LED 1 via D1 and IC1b, and is also fed to one of the input terminals of AND connected IC1c via D1 and the R5-R6-R9-C3 network. The other input of IC1c is derived from a simple time constant network formed by C4 and R7, which disables IC1c for the initial 50 seconds after turn-on of the unit. The output of IC1c is fed to the relay via Q1. The complete sequence of operations is as follows.

At the moment of system turn-on IC1c and the relay are disabled via the C4-R7 network, but IC1a and IC1b are enabled. If any of the input sensors are defective at this time, the input and output of IC1a go high and LED 1 is driven on via IC1b. If no sensor faults are present, the owner has 50 seconds in which to pass through 'protected' areas before the alarm will sound. If, at the end of this period, any sensor is activated, the input of IC1a will go high and drive relay RLA on via IC1c and Q1. Once it is activated, RLA self-latches via contacts RLA/1 and activates the siren via contacts RLA/2. The siren then continues to sound until the supply battery runs flat: this mode of operation is considered to have considerable practical advantages over the time-controlled auto-turn-off systems adopted in some commercial alarm units.

Note in the circuit that R1-C1 and R6-C3 are used as simple transient-suppressing networks, and protect the circuit against false-triggering


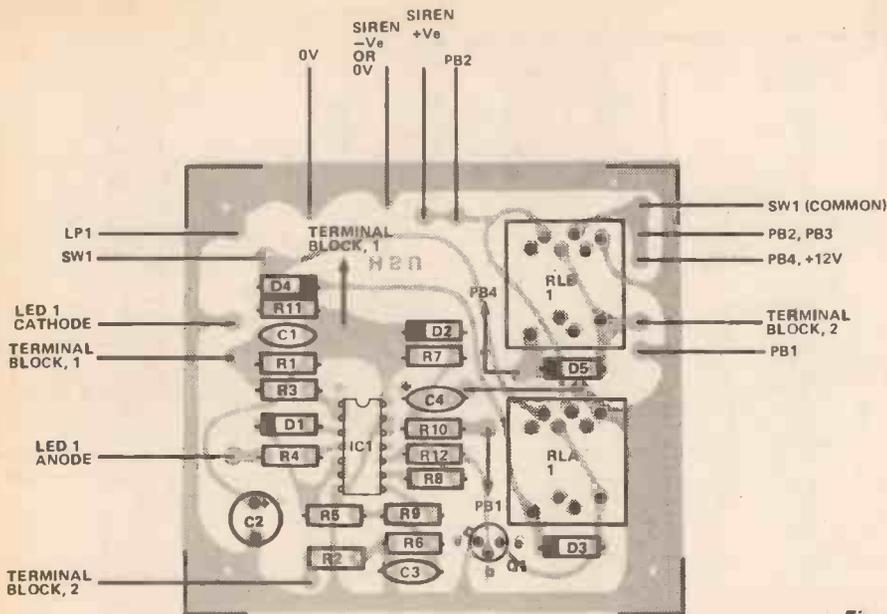


Fig. 2. PCB overlay for the Home Security System, note the position of all polarised components.

Fig. 3. PCB foil pattern for the Home Security system.

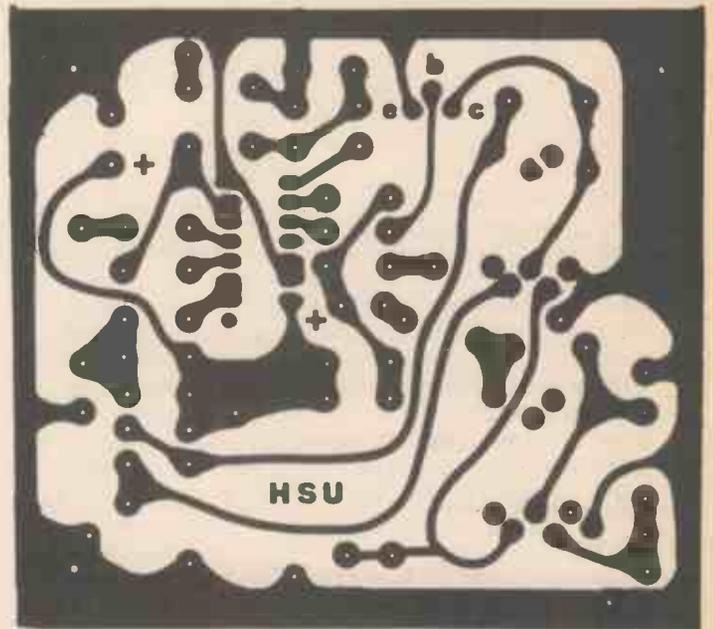

## THE BASIC UNIT

The basic unit incorporates the system's power supply and all the electronic circuitry, including two siren-driving relays, and is intended to be used in conjunction with a number of external sensors and a siren or bell. The unit uses a 12 volt HP1 battery as its power supply, and this battery is capable of powering the system for about one year if the siren is not activated. The unit is designed to give self-latching alarm operation, so once it is activated it continues to sound until it is turned off by the owner or until the supply battery runs flat (which takes about six hours from a fresh battery).

The siren can be activated via either of two relay circuits. One of these is associated with the 'burglar alarm' side of the home security unit, and is only active when the unit is turned to the full ON mode. The other relay is permanently enabled, i.e., when the unit is in either the STANDBY or the ON mode, and can be activated via either thermostat FIRE sensors or via push-button PANIC switches scattered around the house. These panic buttons give a high degree of protection against front door thugs, etc.

Among the many features of the unit are a STANDBY/ON keyswitch on the front panel, a siren test button, a battery test button and lamp, a reset button, and a LED sensor-fault indicator.

Another important feature is a 50 second delay facility, which ensures that the anti-burglar system does not become fully enabled until 50 seconds after initial switch on, thus giving the owner plenty of time to check that there are no sensor faults via the panel-mounted LED, and then walk over pressure mats or through armed doors without sounding the alarm. The system becomes fully enabled at the end of the 50 second period, and the alarm then sounds and self-latches instantly if any sensor is subsequently activated. The system can be temporarily disabled for another 50 second period, to facilitate building re-entry, etc., by momentarily operating a remote RE-ENTRY switch, which can take the form of either a key or a concealed push button

## SENSORS AND SIRENS

The Home security Unit can be used with a variety of types of input sensors, which can be coupled into the system via terminal strips mounted on the rear of the unit. The anti-burglar sensors can take the form of normally-open parallel-connected devices such as pressure mats, and normally-closed series-connected devices such as microswitches, magnetically-activated reed relays, and window foil strip, etc. Fire protection can be obtained by wiring normally-open thermostats in parallel, and thug protection can be obtained by wiring normally-open push-button PANIC switches in parallel.

The system's output sound generator can be any 12 volt electro-mechanical or electronic siren or bell. Figure 2 shows the practical circuit of an electronic siren that produces a warbling sound similar to that of an American ambulance or police car, and which generates about 4 watts into an 8 ohm speaker or 1.2 watts into a 3 ohm speaker.

## Parts List

### RESISTORS (All ¼W 5%)

R1	10M
R2	10k
R3	56k
R4	1kΩ
R5, R8, R9	2k7
R6	1MΩ
R7	470k
R10	47R
R11	120R
R12	4k7

### CAPACITORS

C1	10n polycarbonate
C2	1000µ Electrolytic (PCB mounting)
C3	100n polycarbonate
C4	220µ electrolytic (PCB mounting)

### SEMICONDUCTORS

IC1	CD4081
Q1	BC109C
D1, D2	IN4148
D3, D4, D5	IN4001

### MISCELLANEOUS


Siren (see text)  
2 off — RLA, RLB, 12V 7120R (continental series relays)  
SW1 — Key switch.  
PB1, PB2, PB3, push button switches (momentary action)  
PB4 push button switch (normally closed contacts)  
12V battery HP1.  
8 way + 3 way terminal blocks.  
Case to suit.

## Buylines

Most of the electrical / electronic parts for this project, including the relays, key switch and siren, are available from the larger mail-order advertisers in this magazine: if you haven't got their catalogues, buy them now.

The HPI battery should be available from most large electrical retailers. Anti-burglar sensors and devices such as window foil, microswitches, magnet/reed-relay combinations, pressure mats, alarm bells and enclosures, etc. are available from: — STRATHAND SECURITY, 44 St. ANDREW'S SQ., GLASGOW G1 5PL. Their catalogue, which also gives details of alarm techniques, costs £1, plus P and P.

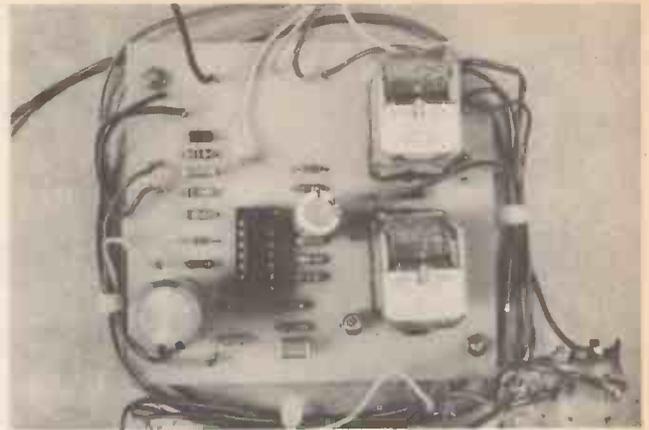The systems siren or bell must be mounted external to the main unit, and can be tested at any time by pressing a non-latching SIREN TEST button mounted on the main unit.



*Close up of the electronics, in circuits of this type always use the best quality components, false alarms are both irritating and embarrassing.*

## CONSTRUCTION

The major part of the electronic circuitry, including the two relays, is assembled on a single PCB, and construction should present few problems so long as care is taken to observe polarities of the electrolytic capacitors and the semiconductor devices. The two relays, which are miniature plug-in 'continental' types, are mounted on the board via 0.1 inch PCB mounting sockets. The relays are 12 volt types with coil resistances greater than 120R (185R on our prototype).

The completed PCB must be mounted in a suitable case, together with the HP1 supply battery that measures 5¼ x 5¼ x 2½ inches. We built our prototype unit into a case with overall dimensions of 6 x 11 x 3 inches. Components SW1, PB2, PB3, PB4, LP1, and LED 1 are mounted on the case front panel, and two screw-type terminal strips or blocks are mounted on the rear to facilitate connections to the systems sensors, etc.

Pay special attention to the circuit interwiring, taking care to relate the component overlay to the circuit diagram. When construction is complete, wire a suitable siren or bell in place, and give the unit a functional check by turning key switch SW1 to the ON position, with no anti-burglar sensors in place. LED 1 should illuminate, but extinguish when a short is placed between R2 and the junction of R1 and R3. The alarm should operate and self-latch approximately 50 seconds after initial switch-off if this short is removed. This timing period is determined by the C4 value.

With the key switch SW1 in the STANDBY position, the alarm should operate and self-latch when a momentary short is placed across the PANIC BUTTON or THERMOSTAT connections of the sensor terminal strip, and turn off again when PB4 is momentarily opened. When the above tests are satisfactory the unit is ready for installation in the home.

If you want to build the electronic siren circuit of Fig 2, do so at this stage. Construction of this circuit should present no problems.

## INSTALLATION AND USE

The installation of a home security system is a fairly major undertaking, with many fine points to consider and individual decisions to be made regarding the degree of protection that is required and the types of sensors that are to be used, etc. An article outlining the



principles of installation is presented after this project and should be read in conjunction with the present story. In short, however, it is up to the individual reader to work out the details of his own sensor and alarm generator networks, and then couple those networks up to the main Home Security Unit.



The HE Home Security System connected up to motorised siren, we can vouch for the units loudness, the ringing is still in our ears.

The anti-burglar sensors must be coupled to the unit via terminal block 1, and the fire and panic sensors must be coupled via terminal block 2. Any number of normally-open (NO) sensors can be wired in parallel, and any number of normally-closed (NC) sensors can be wired in series.

The main unit is best mounted in a central part of the home, such as on a landing or at the foot of the stairs, so that it can be operated with maximum convenience. The alarm sound generator should be mounted fairly close to the unit, to minimise power losses in the connecting leads, and these leads should either be concealed or mounted in armoured sleeving so that they can not be readily cut. Excessive attention does not need to be given to the matter of making the unit and the sound generator super-secure, however, since the system will already have failed in its prime purpose if an unauthorised person is able to get close enough to disable its heart.

If a re-entry switch is mounted on the front door of the house, the wiring between the switch and the main unit should be carefully concealed. If required, a number of re-entry switches can be wired in parallel so that, for example, the system can be temporarily disabled from either the front door or the main bedroom.

The alarm system is very simple to use. The PANIC and FIRE alarm side of the circuit is permanently enabled, and can be operated at any time. The anti-burglar section is enabled only when the main key switch is moved to the ON position. If the panel-mounted LED lights at the moment of turn-on it means that part of the sensor system is either open or closed when it should not be, possibly due to an open door or a chair resting on a pressure mat, etc. The fault must be rectified before the system is put to full use.

If you leave the house or pass through a protected area after turning the system on, remember to use the re-entry facility before returning to the unit, or you'll sound the alarm and annoy the neighbours. HE

## How it Works

IC1, an NE556, contains two so-called 'timer' circuits of the 555 type. One of these timers is available via pins 1 to 6 on the left side of the IC, and the other is available via pins 8 to 13 on the right side of the IC. Pins 7 and 14 are the supply ground and supply positive terminals respectively of the IC.

In the electronic siren circuit, both timers are configured as free-running astable multivibrators. The left hand astable is used as a square wave generator, using timing components R2-R3-C1. It oscillates at a centre frequency of about 950 Hz, and has its output fed to the speaker via R4 and power transistor Q1.

The right hand astable is used as a triangle-wave generator, using timing components R5-R6-C2, and oscillates at about 2.5 Hz. The triangle-wave output is taken from across C2 via emitter follower Q2 and is fed to 'control voltage' pin 3 of the left hand astable and causes its frequency to sweep through the range 800 Hz to 1100 Hz two and a half times per second. The resulting output sound of the speaker resembles that of a modern American ambulance or police siren.

The speaker used in the circuit can have any impedance in the range 3Ω to 8Ω. The circuit output power depends on the speaker impedance, and is about 4 watts on 8Ω or 12 watts on 3Ω. Diode D1 is used to damp the back EMF of the speaker, and protects Q1 against possible damage. D2 and C3 ensure that the main oscillator circuitry is not influenced by the speaker transients.

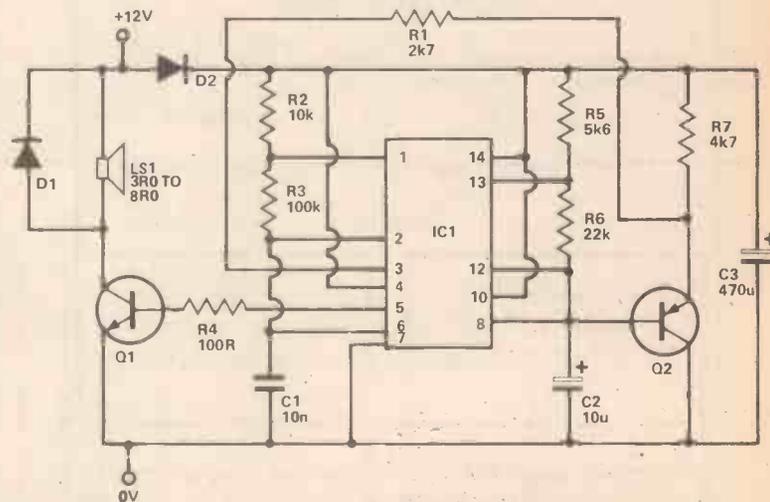
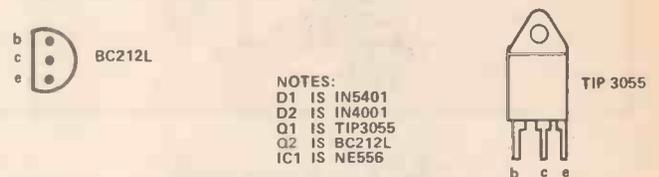


Fig. 4. Circuit diagram for the optional electronic siren.

## Parts List

### RESISTORS (All 1/4W 5%)

R1	2k7
R2	10k
R3	100k
R4	100R
R5	5k6
R6	22k
R7	4k7

### CAPACITORS

C1	10n Polycarbonate
C2	10 $\mu$ Tantalum
C3	470 $\mu$ Electrolytic

### SEMICONDUCTORS

IC1	NE556
Q1	TIP3055
Q2	BC212L
D1	IN5401
D2	IN4001

### MISCELLANEOUS

LS1	3R0-8R0
-----	---------


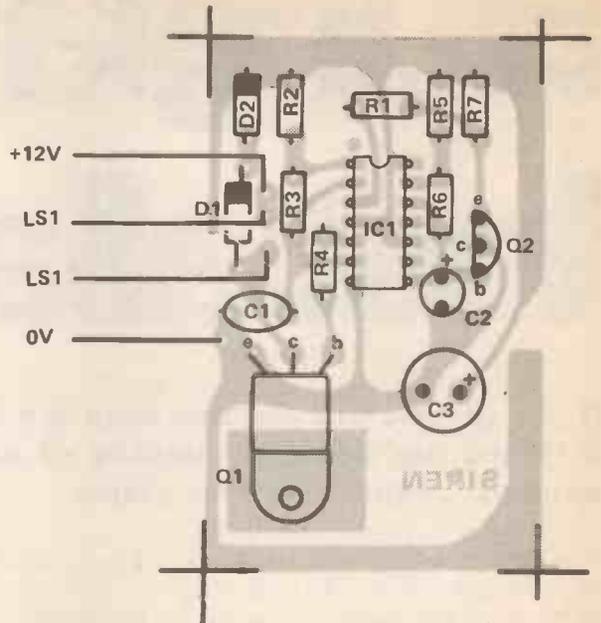





Fig. 5. Overlay diagram for the optional electronic siren.

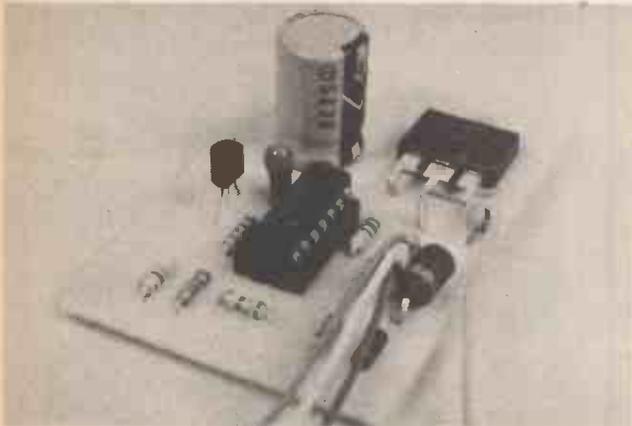

The assembled siren board, it will either fit in the case or in a remote location with the speaker.



Fig. 6. PCB foil pattern for the optional electronic siren.

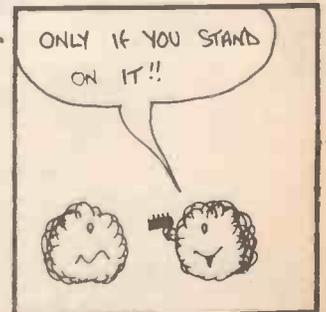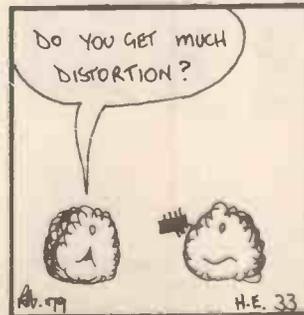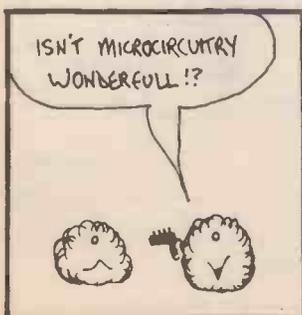

# Burglar Alarm Installation

If you decide to build this month's HE Home Security Unit project, you'll need to learn the basic principles of security system installation. Ray Marston explains in the next few pages.

STATISTICS SHOW THAT the average Englishman has a one-in-four chance of being burgled, beaten up, or burnt in his own home at least once in his lifetime. The chances of such disasters occurring can be greatly reduced by taking a few simple security precautions, such as fitting good locks on all external doors and closing all windows at night and when the house is empty. The chances can be reduced even more by installing a well thought out home security system. With the latter option in mind, let's look at some of the basic principles of home security system installation.

## DON'T GET YOUR FINGERS BURNT.

The disasters most likely to strike you at home are fire, thuggery, and burglary. Most home fires are caused by daft things like lighted cigarettes, pieces of smouldering coal falling onto rugs, overheated electrical appliances, and carelessly placed tea cosies or towels igniting from the heat of gas pilot jets, etc.

The first line of defence against fire is common sense, and the second line is a fire alarm system. The fire alarm system can be a sophisticated affair, including smoke

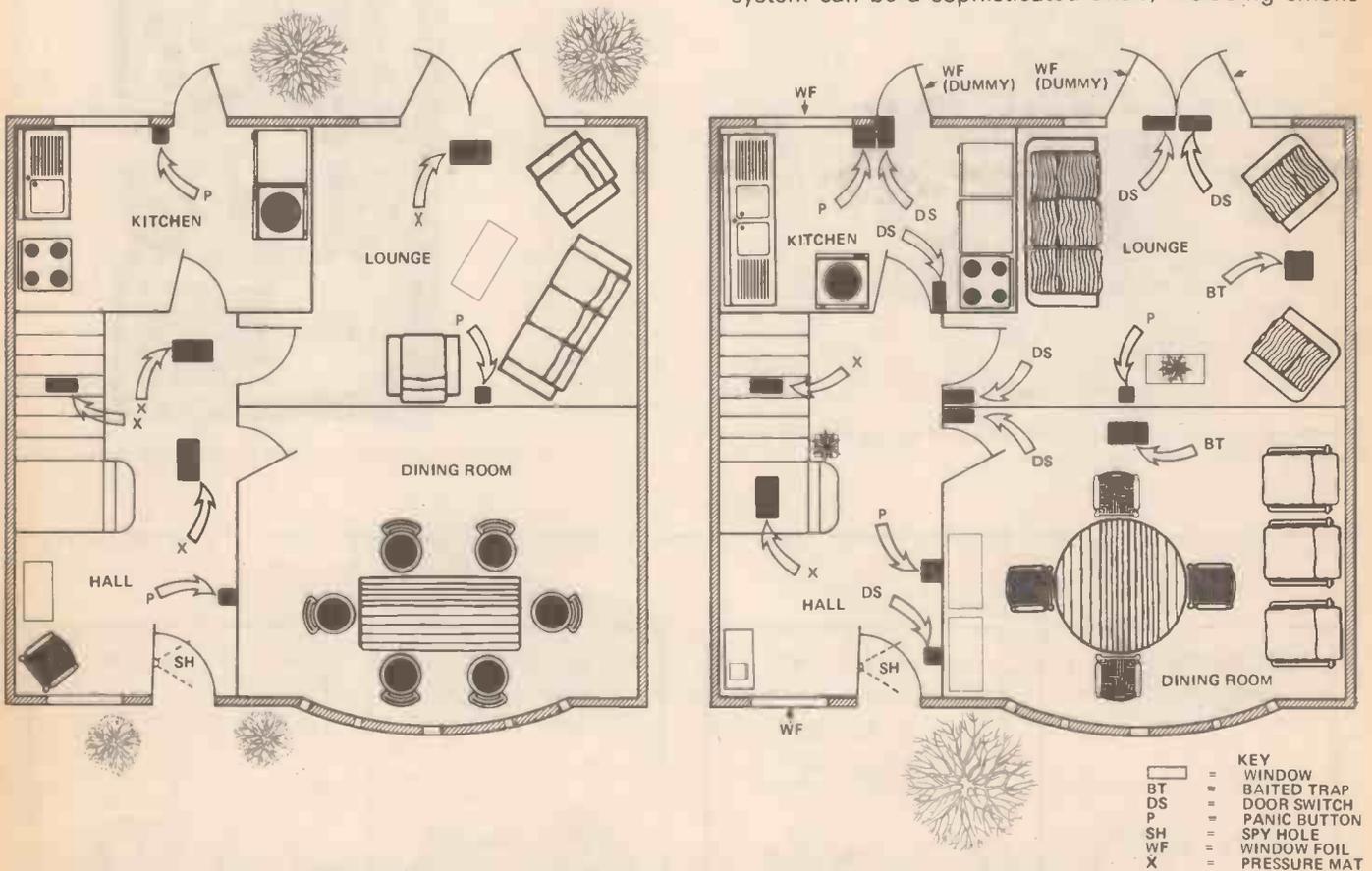


Fig 1. Ground-floor plans of a medium-sized mid-terrace house with two alternative security defence systems.  
 (a) House with minimal 'SPOT' and 'PANIC' defences.  
 (b) House with a high level of 'PERIMETER' and 'SPOT' defences, plus minimal 'PANIC' defences.

and gas detectors, or a simple outfit consisting of a number of normally-open thermostats, all mounted at ceiling height and connected in parallel, and arranged so that they complete an alarm circuit if any of them close. Any type of fire alarm system is better than none at all, provided that the system is reliable. The HE Home Security Unit has a fire alarm facility, and is designed for use with any number of parallel-connected thermostats.

## LOOK OUT, LOOK OUT, THERE'S A THUG ABOUT!

Thuggery is a very real menace to the householder. It normally occurs when one or more males attack the occupier as he (or she) either opens the front door in response to a call, or occurs shortly afterwards when the strangers have gained entry to the house on the pretext of reading a gas meter or selling insurance, etc. Occasionally, the attacks occur late at night following a break-in.

The first line of defence against the thuggery menace is common sense and possibly a 'spy hole' device and a security chain fitted to the front door. An excellent second line of defence is a permanently armed system of PANIC buttons positioned close to likely attack points (front and rear doors, the TV lounge, and the main bedroom) and arranged to activate a self-latching alarm when they are momentarily activated. The HE Home Security Unit is designed for use with any number of parallel-connected normally-open PANIC button switches (ordinary push-button switches).

## SYSTEM RELIABILITY

The most important parameter of any security system is its reliability, or immunity to false alarms. Ninety-nine percent of all burglar alarm soundings are false alarms. Systems that frequently give false alarms tend to be ignored by both the police and their owners.

'Sophisticated' systems, such as radar, ultrasonic, and light-beam types, tend to be significantly less reliable than the 'cruder' types that depend on the activation of microswitches and reed-relays, etc., for their operation. Many alarm systems can be false-triggered by electrical interference from lightning flashes, near-by electric motors, or electric lighters operated close to their sensors. The HE Home Security Unit has been designed to have a high reliability factor.

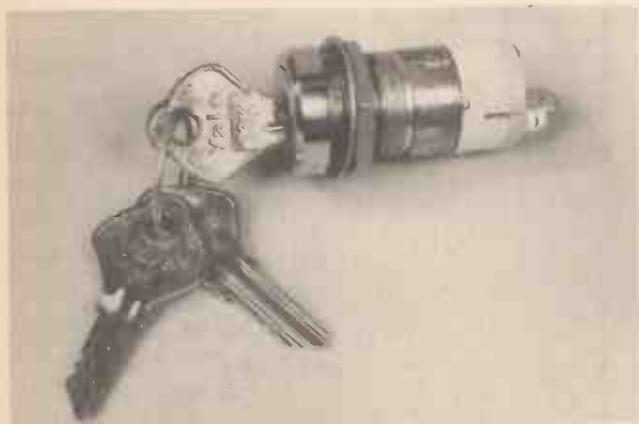


Fig 2. A good quality key switch is an essential item in any home security system.

## PROTECTING YOUR CASTLE.

So let's assume that you've decided to fit the super wonderful reliable HE Security Unit in your home, and have formed some idea of the degree of protection that you need. How do you go about planning the layout of your security switches and sensors?

Any building can, for our present purposes, be regarded as a box that forms an enclosing perimeter around a number of interconnected compartments. This perimeter 'box' is the shell of the building, and contains walls, floors, ceilings, doors and windows. To commit any crime within the building the intruder must break through the perimeter, which thus forms the owners first line of defence.

Once an intruder has entered the building he can move from one room or 'compartment' to the next only along paths that are pre-determined by the layout of internal doors and passages. In moving from one compartment to the next he must inevitably pass over or through certain 'spots' in the building, as is made clear in Figure 1a, which shows the ground-floor plan of a medium-sized mid-terrace house. Thus, to move between the kitchen (a likely break-in area) and the lounge he must pass through three 'spots' comprising the kitchen door, adjacent point 'X', and the lounge door. These typical 'spot' points form the owner's second line of defence.

The house owner can thus obtain protection by using full or partial 'perimeter' defence, or by using 'spot' defence, or by using a combination of these two methods.

'Perimeter' defence sensors include microswitches or reed-relay/magnet combinations which can be fitted to external doors and windows, and window foil which can be fitted to the glazing on external doors, windows, and skylights. 'Spot' defence sensors include pressure mat switches that can be fitted under rugs or carpets, microswitch or reed-relay/magnet door switches, and 'baited traps' comprising an attractive item (such as a clock) placed on top of a concealed microswitch that activates when the item is removed.

When planning the installation, the house owner must try to think like a burglar. Normally, the burglar enters a house from an easy access point that is obscured from the view of the neighbours, ie, a back door or window. Often, he breaks in using tools 'borrowed' from the owner's shed or garage, so these two places should

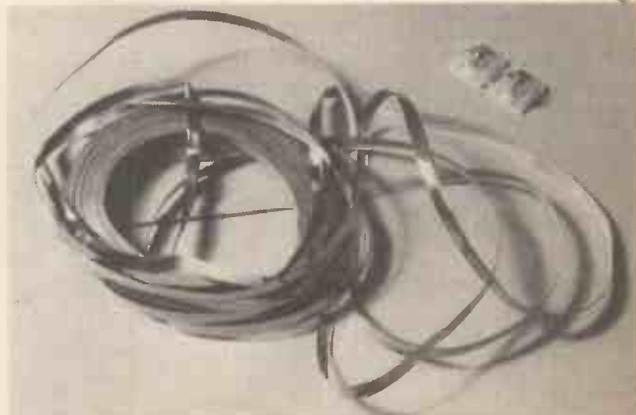


Fig 3. Self-adhesive window foil can be fixed to most types of glazing. It hooks into the security system via special connector blocks.

# Burglar Alarm Installation

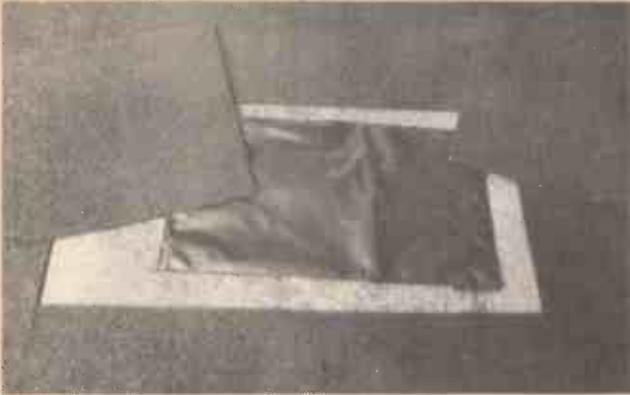


Fig 4. Pressure mats can be hidden under rugs and carpets.

be included in the owner's defence system. Invariably, the burglars first action on entering the property is to secure a rapid escape route, ie, to open the back door. He then starts hunting for stealable goodies.

## TWO EXAMPLES.

Figure 1 shows two alternative ways of installing security defence systems in the ground floor of a medium-sized mid-terrace house. In both cases anti-thuggery protection has been obtained by installing a 'spy hole' device in the front door, and by fixing PANIC buttons at three likely attack points. The houses differ considerably, however, in their methods of burglary protection.

In the case of Fig 1a the owner has reasoned that a burglar is most likely to enter the house via the French windows of the lounge, or via the kitchen door or window. If he enters via the French windows he will be detected via a strategically placed pressure mat, but if he enters via the kitchen he will find nothing worth stealing so will open the kitchen door into the hall, where he will subsequently be detected via another pressure mat. In the unlikely event that the burglar enters the house from the front, he will eventually be detected via a pressure mat located in the hall, adjacent to the dining room door, or via a small pressure mat placed on the stairs. Note that this house owner has made no attempt to keep the burglar out of the house, but has used 'spot' defences to detect him once he has entered. This simple type of installation is highly cost-effective, and gives a reasonably high degree of protection.

By contrast, the house in Fig 1b uses an extensive perimeter and spot defence system. It's owner has



Fig 5. Reed-relay/magnet combinations, or door/window switches, are available in a variety of sizes. The smallest can be used on windows, the largest on garage doors.

decided to try to scare off potential burglars by fixing clearly visible window foil to selected areas of glazing at the front and rear of the house. Some of this foil is genuinely connected into the alarm system, and some is 'dummy'. All external and internal doors are protected by door switches, and two pressure mats are placed on the stairway. Additionally, baited traps are placed in the lounge and dining room. This house has excellent protection.

## HINTS AND TIPS.

Pressure mats are excellent 'spot' defence devices, easily hidden under rugs and carpets. Both standard and stair types are available. Note, however, that they are fairly sensitive, and can easily be set off by large cats and dogs, and by very small elephants. If you own any of these creatures, make sure they are confined to sensible areas when the mats are enabled.

Window foil is an adhesive-backed aluminium strip that bonds to glazing. It couples into the alarm system via special connector blocks. The strip breaks when a window is shattered.

Door/window switches usually come in the form of a reed-relay/magnet combination. The magnet is installed in the door or the opening window, opposite the reed-relay that is installed in the frame. Most commercial units of this type have two sets of output wires in the reed-relay unit, one set giving normally-open operation, and the other giving normally-closed operation.

When you plan your installation, don't forget to make some provision for by-passing the front door protection system, so that you can re-enter the house without sounding the alarm: this facility is provided in the HE unit by the PY-PASS switch.

Don't forget to protect your shed and/or garage.

When you install your system, try to keep all wiring neat and concealed. Thoroughly test each section of the wiring as it is installed.

If possible, fit your system with both internal and external alarm bells or sirens. The external unit should be mounted in a prominent position at the front of the house, where it will act as an excellent burglar deterrent. Special weather-proof housings are available.

Before you proceed with the installation, send off for at least one home-security catalogue. We recommend the one from STRATHAND, 44 St. Andrews Square, Glasgow G1 5PL, who supplied all the bits in the photo's. Their catalogue costs £1 plus P&P, and gives helpful installation notes.

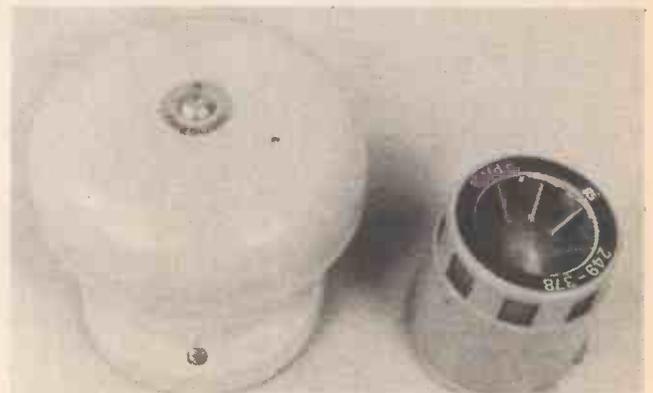


Fig 6. A powerful alarm bell or siren is an essential part of any home security system.

# Codespeed Electronics

P.O. BOX 23, 34 SEAFIELD ROAD, COPNOR  
PORTSMOUTH PO3 5BJ

New, Full Spec. Devices

**MM5314 CLOCK CHIP SNIP.** A bulk purchase allows us to offer these digital clock chips at the unbelievable price of only £1.99 each. With data. Cat. Number 207.

**4-DIGIT LIQUID CRYSTAL DISPLAY.** A super, high contrast 4-digit non-multiplexed display. Digit height is 0.5" and the display is supplied with data and a special, easy to solder, edge connector. £6.95. Cat. Number 206.

**DIGITAL ALARM CLOCK MODULE.** A digital alarm clock module, complete with 0.8" LED display. Just add mini transformer and time setting switches for fully functional clock. With data and instructions, only £6.50. Catalogue number 205.

**9-DIGIT DISPLAY.** A 9-digit, 7 segment gas discharge display. Super, bright 0.25" high digits. With data, only 75p. Cat. Number 310.

**POLARISING FILTER MATERIAL.** A lightly tinted polarising filter material, manufactured by "Polaroid", in 0.006" plastic film. Any size cut, from 1 sq. inch to a maximum size of 19" by 250 feet. Our price — only 2p per square inch. Catalogue Number 701.

**P.U.T.s.** Four MEU21 Programmable Unijunction Transistors (electrically similar to 2N6027). Lots of uses, long delay timers, oscillators, phase controllers and many more. With data and usage sheet. 4 for 50p. Cat. Number 402.

**6-DIGIT LED DISPLAY.** A common cathode 6-digit 7 segment LED display from Texas Instruments Multiplexed with built-in bubble magnifiers. Digit height 0.1". £1.00. Cat. Number 306.

**DIGITAL MULTIMETER CHIP.** This MM5330 d.v.m. chip can be used to build a high accuracy d.v.m. or panel meter. Has auto polarity and over-range indication. Supplied with data and circuit. Requires some additional circuitry. Only £3.95. Cat. Number 404.

**LED CLOCK DISPLAY.** A superb 24-hour LED clock display with 0.8" high digits. Display panel is common cathode and non-multiplexed. A snip at only £3.95. Cat. Number 204.

**25 MINIATURE DIODES.** 25 miniature 1N3470 germanium diodes (600mA, 35v). All brand new. What a bargain (at just 2p each)! 25 diodes for 50p. Catalogue Number 401.

**2102 MEMORIES.** Now at a new low price. These MM2102, 1024 bit static RAMs are offered for only 99p. Supplied with data sheet. Cat. Number 102.

**CALCULATOR CHIP.** An MM5725 calculator chip, offered for only £1.00 (not compatible with calculator keyboards offered as Cat. Number 101). Order Cat. Number 103.

**HIGH-SPEED SWITCHING DIODES.** 10 x 1N4151 high speed diodes. Same as 1N4148 but has higher P.I.V. 10 diodes for 35p. Cat. Number 403.

**10 HYBRID CIRCUITS.** Now miniaturise your home produced PCBs with these 10 hybrid circuits. Each containing 8 resistors and 8 capacitors. Useful values, 10 hybrids for 50p. Cat. Number 801.

### Untested or Used Items

**DEFECTIVE CALCULATORS.** A production line reject calculator with lots of accessible goodies inside. Detachable keyboard, case and PCB with approx. 25 transistors and calculator chip. Not much wrong with some we tested. A bargain at only £2.50. Cat. Number 104.

A full refund guarantee on all items  
Post and Packing please add 25p (Overseas orders add 60p)  
Lots more goodies in our catalogue. Send a medium sized SAE for your free copy.

TANTALUM BEAD	RADIAL ELECTROLYTICS	2200 40V
1.5 35V	.10	4700 6.3
2.2 35V	.10	4700 6.3
3.3 35V	.10	10 3.3 50V
4.7 35V	.10	10 4.7 35V
5.6 35V	.10	10 4.7 50V
1.5 35V	.10	10 10 15V
2.2 35V	.11	10 10 25V
2.2 35V	.11	10 10 50V
2.2 35V	.12	22 10V
3.3 16V	.11	22 16V
3.3 35V	.12	22 35V
4.7 10V	.11	22 50V
4.7 25V	.12	33 10V
4.7 35V	.13	33 25V
8.2 35V	.13	33 50V
10 6.3V	.12	47 16V
10 16V	.13	47 25V
10 25V	.13	47 50V
10 35V	.16	100 10V
15 16V	.15	100 25V
15 25V	.16	100 50V
22 10V	.15	220 10V
22 16V	.16	220 16V
22 35V	.26	220 35V
33 10V	.16	330 10V
33 16V	.24	330 25V
33 25V	.26	470 6.3
47 6.3V	.16	470 16V
47 10V	.18	470 25V
47 16V	.26	470 50V
68 3V	.15	1000 16V
100 3V	.16	1000 25V
100 6.3V	.24	2200 6.3
100 10V	.26	2200 16V

## STAR BARGAINS

3 Amp 100V BRIDGES RECTIFIER 50p ea.

POLYESTER RADIALS  
.01 .025 ea.  
.1 .035 ea.  
.47 .06 ea.  
.68 .08 ea.

## MULTILAYER POLYESTER CAPACITORS 5% Tolerance 7.5mm PCB

1001	.08
10015	.08
10022	.08
10047	.08
10068	.08
101	.08
1015	.08
1022	.07
1033	.07
1047	.07
1068	.06
11	.10
22 (100V)	.13
100 (100V)	.22
100 (100V)	.25
100 (100V)	.28

## NOISE SUPPRESSOR CAPACITORS 250V AC PCB 15mm 2Z 22.5

Radial	.03
0.015 13 0.068	.16
0.022 13 0.1	.18
0.033 14 0.15	.24
0.047 15 0.22	.32

Send SAE for list. Min. order £200. C.W.O. VAT etc. Overleaf 5p

## FITCH CERAMIC CAPACITORS TUBULAR RADIAL 250V

Stock Values	Prices
15-100pf	.03
220-470pf	.04
1000-220pf	.035
2700-10,000pf	.04
1	.04

## Ceramic Capacitors EDPU 63V Stock Values pf

1: 2.2, 3.3, 4.7, 5.6, 6.8, 8.2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1000, 2200, 3300, 4700, 10,000, 22,000	
147pf 2% (Low K)	.03
56-100pf 2% (Low K)	.035
100-150pf 2% (Low K)	.055
100-820pf 10% (Med. K)	.03
1000-2200pf 10% (Med. K)	.04
3300-4700pf 10% (Med. K)	.05
10,000-20 + 80 40V	.035
22,000 20 + 80 40V	.06

# GREENWAY ELECTRONIC COMPONENTS

62 MAYPOLE RD  
ASHURST WOOD  
EAST GRINSTEAD SX RH19 3RB.  
Tel: Forest Row (034-282) 3712

Largest range of quality components in the U.K. — over 8,000 types stocked



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, NW. Tel: 01-723 4242.  
Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel. 0272 426801/2

Head Office and Mail Order to Dept. HE  
A. Marshall (London) Ltd.  
Kingsgate House, Kingsgate Place  
London NW6 4TK. Tel: 01-634 0805  
Telex 21442

## RESISTORS FIXED CARBON

0.25 watt ± 5% Tol. Available in E12 range 10Ω to 1 meg	PRICE
2p each	
0.5 watt ± 5% Tol. Available in E12 range 10Ω to 1 meg	3p each
1.0 watt ± 10% Tol. Available in E12 range 10Ω to 1 meg	5p each
2.0 watt ± 10% Tol. Available in E12 range 10Ω to 1 meg	9p each

**MULLARD MFR25/MR30 SERIES METAL OXIDE**  
0.5 watt ± 2% Tol. Available in E24 range 10Ω to 1 meg  
4p each  
New stocked Resistor & Light Dependent Resistor — see catalogue.

**TOOLS**  
See joint construction for strength. Small, compact and reliable, insulated handles and smart individual wallet.


**GENERAL PURPOSE**  
100mm (4")  
Diagonal Cutters £3.40  
Round Nose Pliers £3.25  
Flat Nose Pliers £3.20  
Snipe Nose Pliers £3.20  
End/Top Cutters £3.80

## BOXES AND CASES

ALUMINIUM	PRICE
842 4x4x1 1/2" £0.85	848 7x5x2 1/2" £1.50
843 4x2x1 1/2" £0.80	849 8x6x3 1/2" £1.90
844 4x5 1/2x1 1/2" £1.00	8410 10x7 1/2" £2.40
845 4x2 1/2x2" £0.95	8411 10x4 1/2x3" £2.25
846 3x1 1/2x2" £0.60	8412 12x5x3" £2.35
847 6x4x2" £1.25	8413 12x8x3" £2.70

**ABS PLASTIC**  
3 1/2x2 1/2x1 1/2" £0.55  
8 1/2x4 1/2x2 1/2" £0.85

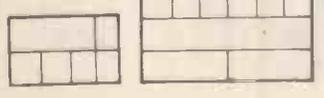**RAACO STORAGE BOXES**  
2 sizes — 4 configurations  
86 £0.76 87 £0.76 89 £1.62 918 £1.78



**VERO CASES** — see catalogue for full range  
7 different styles — 18 sizes

**PLASTIC CLIP CASES**  
Anodised Aluminium front panel two-tone halves, clip together.  
VCC1—85x40x154mm £2.50  
VCC2—85x60x154mm £3.15  
VCC3—85x80x154mm £3.65

Also — instrument cases — 5 sizes from £2.10  
Card frames, flip top boxes etc. etc.

## TTL see catalogue for full range

74LS000	£0.26	74LS83A	£0.90	74LS165M	£1.65
74LS01A	£0.26	74LS85M	£0.95	74LS169M	£1.45
74LS02A	£0.26	74LS86M	£0.64	74LS170M	£1.30
74LS03M	£0.26	74LS90M	£0.64	74LS173M	£1.10
74LS04M	£0.26	74LS92M	£0.74	74LS174M	£0.75
74LS05M	£0.26	74LS95M	£0.64	74LS175M	£0.75
74LS09M	£0.26	74LS95AM	£0.90	74LS181M	£2.75
74LS10M	£0.26	74LS96M	£1.35	74LS182M	£3.70
74LS11M	£0.26	74LS107M	£0.42	74LS183M	£1.00
74LS12M	£0.26	74LS109M	£0.42	74LS184M	£1.00
74LS13M	£0.58	74LS112M	£0.42	74LS185M	£0.95
74LS14M	£0.75	74LS113M	£0.42	74LS186M	£0.95
74LS15M	£0.26	74LS114M	£0.42	74LS189M	£0.70
74LS20M	£0.26	74LS122M	£0.62	74LS195M	£0.70
74LS21M	£0.26	74LS123M	£0.83	74LS196M	£0.80
74LS22M	£0.26	74LS124M	£1.70	74C00M	£0.24
74LS26M	£0.32	74LS125M	£0.50	74C02M	£0.24
74LS27M	£0.26	74LS126M	£0.50	74C04M	£0.24
74LS28M	£0.29	74LS132M	£0.85	74C09M	£0.24
74LS29M	£0.26	74LS136M	£0.42	74C10M	£0.95
74LS32M	£0.27	74LS138M	£0.65	74C14M	£0.24
74LS33M	£0.29	74LS139M	£0.65	74C20M	£0.24
74LS37M	£0.32	74LS145M	£1.30	74C30M	£0.24
74LS38M	£0.32	74LS147M	£1.65	74C32M	£0.24
74LS40M	£0.26	74LS148M	£1.35	74C42M	£0.92
74LS42M	£1.80	74LS151M	£0.58	74C48M	£1.38
74LS47M	£1.09	74LS152M	£0.58	74C57M	£0.56
74LS48M	£1.00	74LS154M	£1.45	74C74M	£0.54
74LS49M	£1.09	74LS155M	£0.80	74C76M	£0.54
74LS51M	£0.26	74LS156M	£0.80	74C83M	£1.30
74LS54M	£0.26	74LS157M	£0.60	74C85M	£1.30
74LS55M	£0.26	74LS159M	£0.65	74C90M	£0.64
74LS56M	£1.26	74LS160M	£0.80	74C98M	£4.39
74LS73M	£0.42	74LS161M	£0.85	74C99M	£0.85
74LS74M	£0.42	74LS162M	£0.80	74C99M	£0.85
74LS75M	£0.58	74LS163M	£0.85	74C95M	£1.04
74LS76M	£0.42	74LS164M	£1.10	74C107M	£1.22
74LS78M	£0.42	74LS165M	£1.15	74C159M	£4.14

**NEW 1979 CATALOGUE**  
48 pages — largest range of quality components in the UK — over 8,000 line items — 50p post paid, 40p to callers.

**MAIL ORDER**  
Add 40p p.p.t. to all orders.  
Tel credit card orders £10 min  
ACCESS — BARCLAYCARD

## NEW TELETEXT CHIPS

from Mullard — available from Marshall's — Sole UK distributor to the hobbyist market.

**SAA Series**, for the reception, display and control of television based text display systems. Suitable for 'CEE-FAX' and 'ORACLE' Remote Control

SAA5000 Infrared/Ultrasonic £3.40  
SAA5010 Station selector/DICS £8.13  
SAA5012 Binary Input Tuners P.O.A.  
TELETEXT (Dedicated I.C.'s)  
SAA5020 TIC (Timing Chain) £8.71  
SAA5030 VIP (Video Input Processor) £11.81  
SAA5040 TIC (Teletext Data Acquisition and Control) £31.82  
SAA5050 TROM (Teletext Read-Only Memory) £18.86  
TIC, TAC & TROM are NMOS — VIP is linear bipolar. We recommend using DIL sockets with these chips.

## CAPACITORS POLYESTER

250VDC — Radial Leads	Price
0.01 £0.06 0.068 £0.07 0.47 £0.14	
0.015 £0.06 0.1 £0.08 0.68 £0.20	
0.022 £0.06 0.15 £0.10 1.0 £0.24	
0.033 £0.06 0.22 £0.09 1.5 £0.26	
pmpr 0.06 0.33 £0.13 2.2 £0.37	

## ELECTROLYTICS — MULLARD

16 Volt	UF	25 Volt	UF	50 Volt	UF	63 Volt	UF
15	10	10	15	10	15	10	15
33	10	10	15	10	15	10	15
68	10	10	15	10	15	10	15
150	10	10	15	10	15	10	15
330	10	10	15	10	15	10	15
680	10	10	15	10	15	10	15
1500	10	10	15	10	15	10	15

## TANT BEADS

ELECTROLYTIC RADIAL POLYESTER METALLISED POLYESTER EXTENDED FILTAL POLYESTER FILM, MICAL ETC. See catalogue.

**KNOBES AND SWITCHES**  
Full range in catalogue

M1 Black plastic with mach metal insert 25mm dia £0.25  
M2 as M1 but with pointer £0.31  
M5 Black plastic with mach insert and calibrated shunt £0.33  
Car Radio knob with chrome top £0.39

# Variable Resistors

## A Potted History


*As promised Rick Maybury peers into the weird and wonderful world of the variable resistor, what they're made of and what they're good for.*

ALL VARIABLE RESISTORS are transducers of one kind or another. The Potentiometer (pot) or Rheostat responds to a mechanical (rotational or linear) movement. The LDR (Light Dependant Resistor) to changes of light, the Thermistor and to a lesser degree the VDR (Voltage Dependent Resistor) to changes in temperature.

Most of us are familiar with the potentiometer, we've all twiddled those knobs that turn up the sound, volume etc but how often do we consider all the things that

variable resistors do without any bidding from us. In many cases variable resistors are quietly going about their business looking after a multitude of electronic devices, controlling, adjusting and measuring, doing things that either we're too slow to do manually or would find impossible to do with our limited and insensitive senses. (Can you accurately measure temperature with your fingers?)

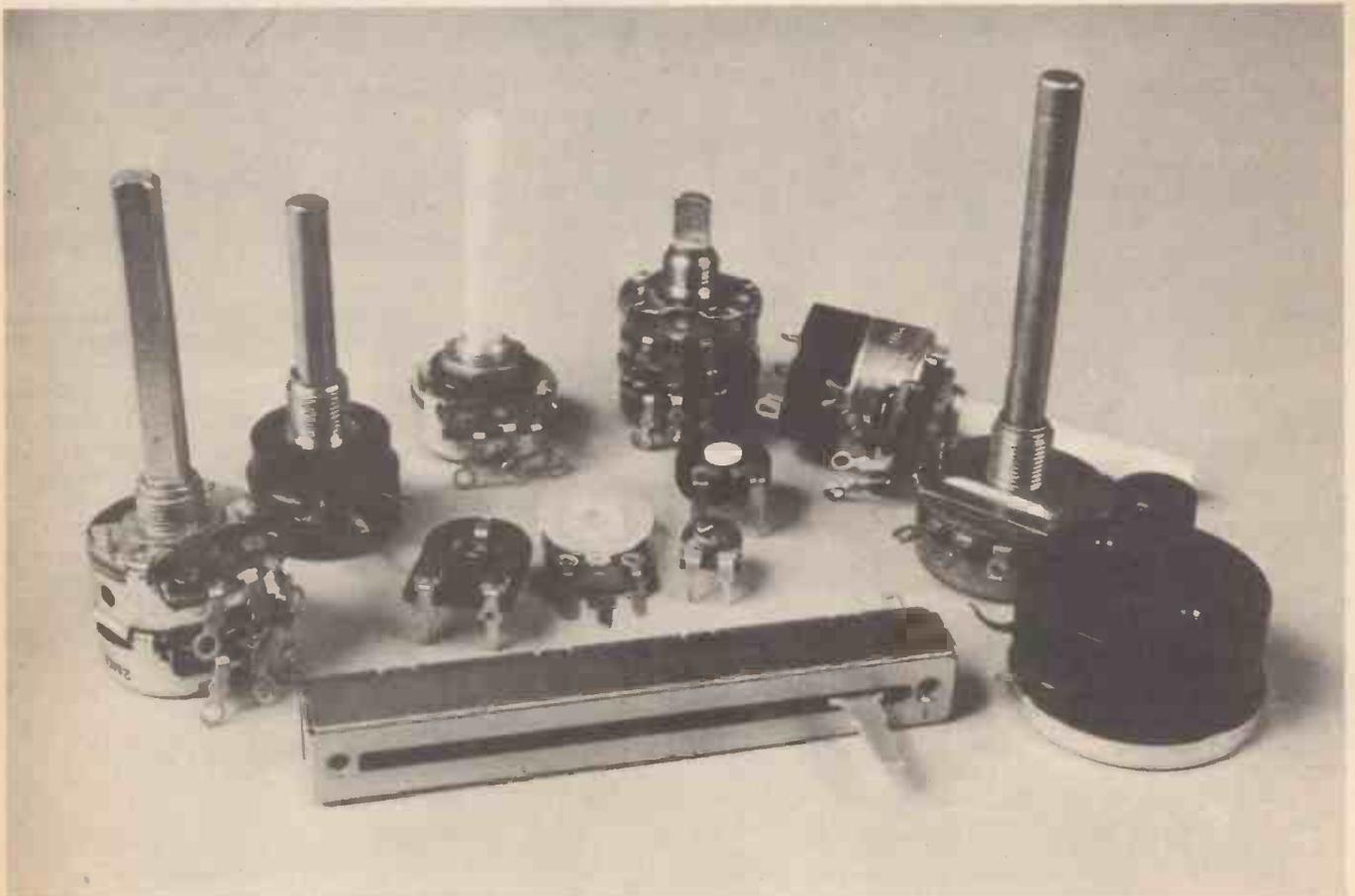Of all the electronic components available to us, the



*A small selection from our workshop, the slider in the foreground has become increasingly popular in recent years with manufacturers of H-Fi equipment.*

# Variable Resistors

amateurs, variable resistors constitute what must be the most diverse family. We will look at the four main types of variable resistor, namely the potentiometer, LDR, VDR and thermistor and consider what lurks beneath the skin of these rather versatile devices.

## POTENTIOMETERS

If you take any kind of fixed resistor, expose the resistive element and move a third contact up and down its length you have a potentiometer or variable potential divider.

Up till only a few years ago many devices we now call 'pots' were called Rheostats, in fact the term rheostat is now only applied to two terminal devices, usually capable of dissipating quite considerable levels of power. These devices are unlikely to cross our paths very much these days so we'll stick to the good old pot found in countless radios, TVs etc. The pots we see on the fronts of most pieces of equipment often represent only a small fraction of pots that may be present in the circuit. The smaller brother of the Continuously Variable (CV) pot is the pre-set, usually considerably smaller and specifically designed to be used only once or twice during its life. Pre-sets are usually adjusted during the initial setting-up of a piece of equipment after manufacture. Design engineers often incorporate several pre-sets in a 'breadboard' design, finally settling upon fixed resistors, decided by the optimum setting of the pre-set in question. Pre-sets are often found in applications where some circuit parameter needs to be calibrated, or to trim the range of a CV pot. If you get the chance take a look into the back of a colour TV set and count how many pre-sets are lurking there, we would be surprised if there's less than forty.



Inside the potentiometer, note the metal wiper pressed on to the shaft, the resistive element (centre) is moulded on to a phenolic former.

## MATERIALS

Most pots we're likely to come across will have their resistive element made from one of five types of material, they are: Carbon Composition, Carbon Film, Hot Moulded Carbon, cermet and Wirewound.

Carbon Composition pots' elements are moulded from a mixture of carbon, ceramic dust and resin. A wiper, usually made from spring steel, constitutes the third contact. Composition pots tend to suffer quite badly from noise, usually after only limited use. As a

consequence they are rarely found in Hi-Fi equipment, although in pre-sets form, where noise and excessive usage are not so much of a problem they are fairly widespread.

Carbon Film pots are manufactured by spraying or screening (you guessed it) a thin film of carbon onto a shaped phenolic former, again a metallic wiper is used. Noise proves to be less of a problem than with composition pots.

Hot Moulded Carbon next, the resistive element is moulded in one integral part containing the insulation and termination as well as the element itself. The wiper is usually made from carbon to minimise wear. Low noise levels and a high degree of conformity (they can make lots of them with identical characteristics) make them popular in so-called 'professional' or 'precision' pieces of equipment.

Cermet pots are a relative newcomer to the variable resistor field, the name cermet derives from ceramic-metal. The resistive element will stand considerable mechanical and electrical abuse and so have become quite popular with our friends the radio control enthusiasts in their servos as feedback pots. Again a metallic wiper is used, low noise levels and power dissipation is directly comparable to Hot Moulded Carbon pots of similar size.



Inside a wire-round potentiometer, the windings are clearly visible inside the outer casing, a small tab of carbon is usually bonded to the underside of the wiper.

The Wirewound pot has got to be the daddy of them all, going back to the days when electronics as a science had not been thought of. The element is wound from resistance wire on an insulating former, a metallic or sometimes graphite wiper is employed in the contact department. Wirewound pots are usually only made in fairly low values, although they do have the advantage of being able to dissipate quite large levels of power. (Up to 200 watts is not an unrealistic figure. Unfortunately wirewounds are somewhat noisy in operation, the resistance also changes in 'steps' giving poor resolution, usually they are bulkier than other pots of equivalent value.

## INS AND OUTS

As with fixed resistors, pots are specified by nominal resistance and power dissipation, unlike fixed resistors we have to state 'Law' and in some cases Resolution.

Law refers to how the resistance changes with respect to the position of the wiper. If the resistance varies in an


equal amount over the whole length of the element we call it Linear or 'Lin' for short. This is not always convenient, we have another law called Logarithmic or 'Log' to accommodate such eventualities. (Just to be awkward we also have B-Law, Anti-log, Semi-log and for the really difficult ones among us, sine and co-sine. As we and you are very unlikely to come across such animals we'll save them for another day.)

If you're still with us, the Log pots change their resistance in a non-linear fashion or to put it another way, tend to be 'all up one end', the resistance changes gradually at first, perhaps over three-quarters of the track's length then suddenly increases (or decreases) in a small part of the track. Normally in any of our projects we will specify a 'Lin or Log' pot. Remember that if you ever replace a pot whether it be CV or pre-set to make sure that the replacement has the same law.

Resolution of pots refers to the amount of resistance change that occurs for any given change of wiper position. Obviously the wirewound pot with its 'stepped' changes has a very poor resolution, the cermet pot however will show a change of resistance no matter how small the change in position might be.

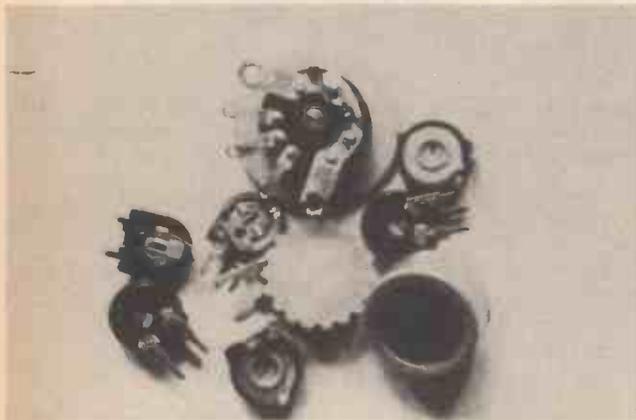
## STYLES

The two main styles of pot, the continuously variable and the pre-set are themselves available in a multitude of different shapes and sizes, appropriate to their function. Most rotary pots have a 270-280 degree limit, both CV and pre-set conform to this standard, with notable exceptions as we will see later. The second largest group of CV pots are the slider pots. Over the past few years they have become very popular with manufacturers of middle-of-the-road Hi-Fi equipment. In most cases they are purely cosmetic, however in certain applications, mixers, graphic equalisers etc, their readability and ease of multi or 'banked' operation are a definite advantage.




*A collection of pre-sets, the upper one is in fact a thumb-wheel pot, with switch, often found in cheap transistor radios, not dissimilar to the genuine pre-set immediately below.*


In certain applications it's necessary to operate two or more pots simultaneously, stereo volume or balance for instance. In these cases the pots are joined together or 'ganged' on a common shaft or slider. The mechanical rotation of pots is carried out in a number of ways, most of the time a simple metallic or plastic shaft is sufficient, but in the case of pre-sets a slotted screwdriver notch is used instead of a shaft. Most oriental transistor radio

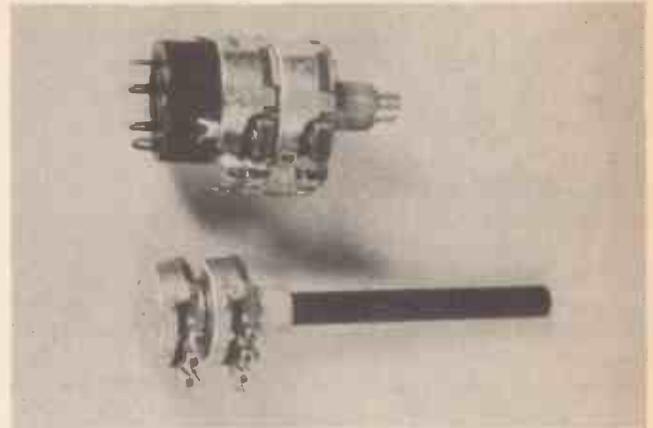

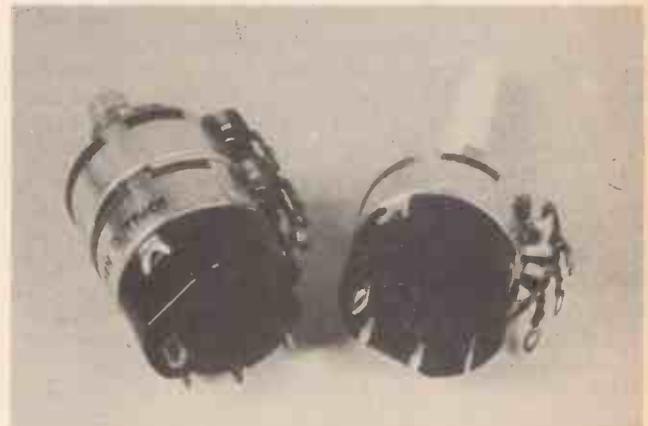*Ganged pots, the two separate pots are joined together by a single shaft, most often seen in stereo systems.*



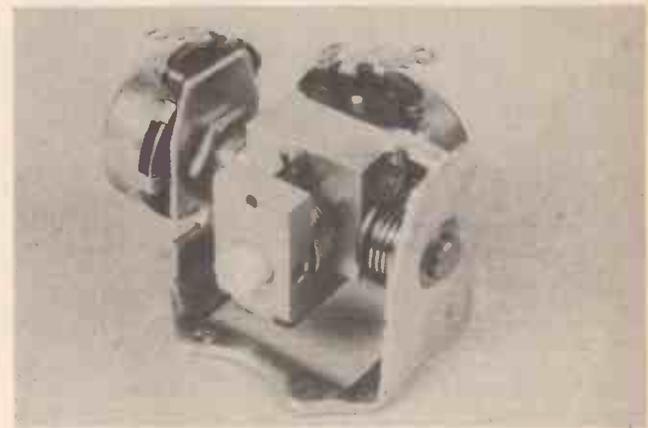*Pots with switches, the switch mechanism is connected to the shaft assembly.*




*An unusual application for pots, this is a joystick (found in radio control systems, synthesisers etc) the mechanical linkage will allow both pots to move in an X Y axis.*

manufacturers seem to favour the 'thumbwheel' pot, usually incorporating an on-off switch on the rear of the pot. Certain types of pre-sets use a hybrid method of construction. The multi-turn pre-sets found in many modern TV and Hi-Fi tuners have a linear track (as opposed to a rotary track) and a threaded screw supporting the wiper. Multi-turn pots have very good resolution factors, ideal for tuner application.

# Variable Resistors
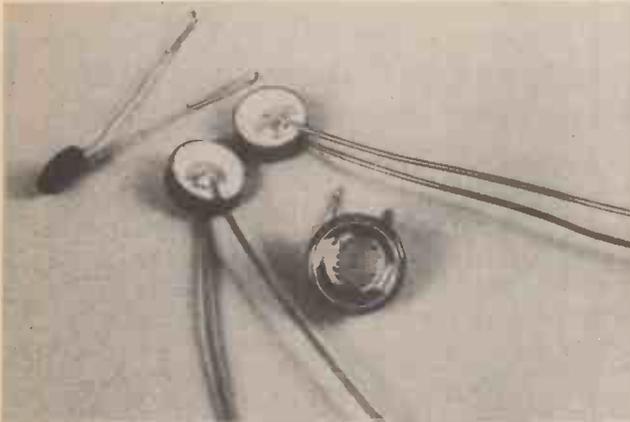
## LDRs, VDRs and THERMISTORS


The last group of variable resistors we shall look at comprise the LDRs, VDRs and Thermistors, in the true sense of the word they are not resistors but semi-conductors but the fact that their resistance does change under external influence makes them worth looking at.



A small selection of thermistors, VDRs and the LDR.
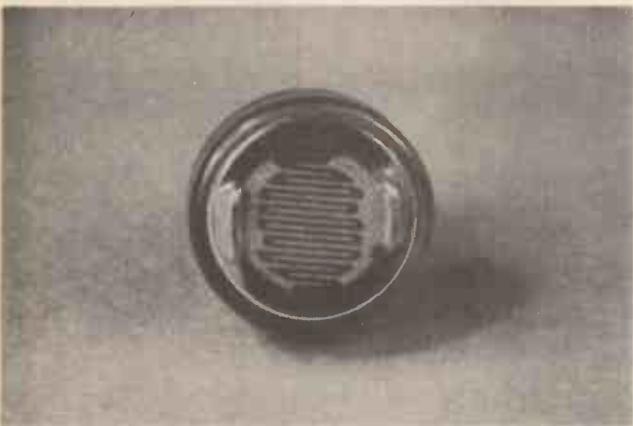
## LDRs

The LDR utilises the photo-conductive properties of many semi-conductor materials such as selenium, cadmium phosphide, silicon and semi-conductor materials generally. As the light energy falling upon these materials increases the number of free electrons also increases, thus the resistance of the material will decrease. (Remember last month?) One of the most common materials used is Cadmium Sulphide (CdS). The resistance of CdS will fall to as little as 5 ohms in bright light and rise to several million ohms in total darkness. These figures are pretty generalised but a fair example is the ORP 12. It has a typical dark resistance of 10 M ohms to around 130 ohms in bright light (1000 Lux). To make the best use of the light available the resistive track of the LDR is 'spiralled' across the body of the cell.



Close up of an LDR, note the track (silver) is cut across the face of the device to expose the maximum amount of resistive element to light.


LDRs are *not* to be confused with Solar Cells, they rely on the photo-voltaic effect, that is, they generate an EMF

in the presence of light. They are most familiar as the 'wings' that protrude from many of the spacecraft that we see and hear about, the wings are made up from thousands of such cells.
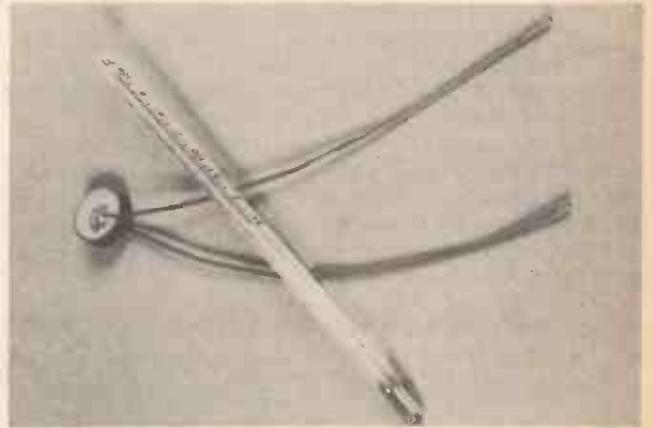
## THERMISTORS AND VDRS

Again we have a bewildering choice of types, styles and applications to look at. Nearly all thermistors (and VDRs, more of that later) have either a Negative Temperature Coefficient (NTC) or a Positive Temperature Coefficient (PTC). In NTC types the resistance of the device will decrease with a rise of temperature, and vice-versa for PTC types.

As the thermistor will decrease (or increase) its resistance with temperature, we can use the self-heating effect of the thermistor to stabilise voltage. If a sufficiently large current is passed through the device it will heat up; if it is strategically placed within the circuit it will respond to any abnormal voltage, or current conditions by varying its resistance accordingly. In these circumstances its called a Voltage Dependant Resistor (VDR).



A thermistor, this style will be mostly found in circuits where a degree of thermal protection is required, note the size next to a medical thermometer.

The degree of resistance change can be tailored to suit the application, some will operate up to several hundred degrees centigrade or many degrees below zero. Many thermistors are specifically designed to be used for temperature measurement, as such they will ideally have as small a mass as possible to allow for measurement of rapid changes of temperature.

The encapsulation of thermistors is extremely important, glass is often favoured in cases where the thermistor is to be immersed in corrosive substances. Sizes of thermistors vary considerably, from almost microscopic bead thermistors to large carbon rod devices several inches long. Obviously for measurement purposes they need to be as small as possible. We've deliberately left the choice of materials to last, that's because it would be impossible to list the materials used, they will vary according to use. Generally though, most are based on one or more types of semi-conductor material or carbon. It's interesting to note that all conductive substances will change their resistances when heated or cooled.

Well that's about it for resistors, coming up soon we will be looking at some of the more exotic and specialised components some of which we have only briefly mentioned in the past.

HE

# Kit Review

## Heathkit Car Clock Timer

***Have you got around £40 and a couple of hours to spare? If so why not have a go at building this excellent car clock/timer from Heathkit, its worth every penny.***

WELL, WHAT CAN WE SAY? We've seen quite a few kits in the past few months, some fair, one or two outstanding, but this one was superb. At £40 it may seem a bit expensive but just ask yourself, how much does a Rolls-Royce cost? This month's offering comes from the kitmakers, Heathkit. If you've been looking for a kit to build you can be sure that Heathkit can supply it. They may not be cheap, but consider how much you can end up spending on a kit that doesn't work.

The kit we received was a car clock/timer, the idea is, that it will give a constant readout of time, as well as providing an elapsed time function ideal for rallies and treasurehunts. We were surprised to see how small the device was, barely six inches across, the electronics however, fit very comfortably inside without any undue cramping. The clock is built on two glass-fibre PCBs, the main one is double sided, both are beautifully made and look strong enough to stand up to even the most cack-handed soldering.

All of the components come in neatly packaged envelopes, we always check the contents against the parts list, this also gets us familiar with some of the more obscure devices. The instruction manuals in many kits often prove to be a bit of a let down, not so with Heathkit, their manual would be better described as a book. Its good to see they've taken the trouble to include a very comprehensive section on faultfinding, not that you'll need it if you follow the instructions.

### CHIPS WITH EVERYTHING

As you would expect the ubiquitous IC rears its many legged body into view. We have three such creatures in this kit. The two 40 pinners carry out the timing functions. It would be interesting to find out why Heathkit didn't use just one purpose-built device. As it turned out our only gripe with the kit arose from the fact that the spacing on the IC sockets was a little tight. Great

***Below, the complete kit spread out for inspection, absolutely nothing is missing or left to chance.***




care should be taken when inserting the ICs. The rest of the parts consisted of a handful of resistors, a couple of capacitors, one transistor, six diodes, a crystal and four push button switches. On the display board two spring metal switches need to be soldered to the board, the contact plates were so small they nearly disappeared down one of the holes without trace.

Actual building time should take no more than a couple of hours or so, providing you follow the very comprehensive, step-by-step instructions. Each stage consisted of about half a dozen parts, after each component has been fitted it can be ticked off in the space provided. (See what we mean, its these little touches that can turn a quite ordinary kit into a real joy to build.)
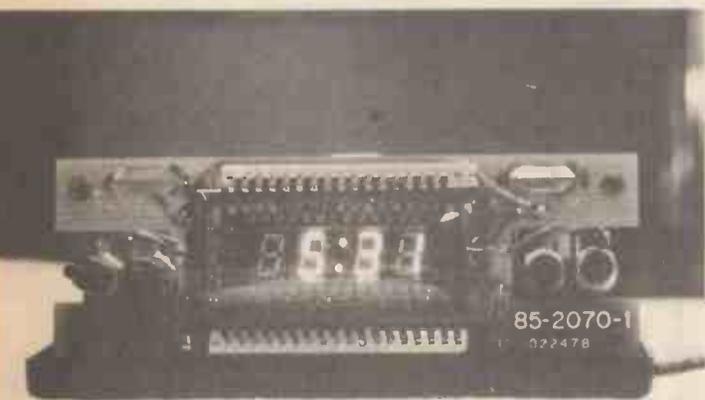
## A TESTING TIME

Providing all is well, nothing is left out, (there's always some strange object that doesn't seem to have a home), Heathkit suggest that before it's fitted into its case some preliminary tests be carried out.


The clock was connected up to a power supply and with bated breath switched on. As usual nothing happened. Nothing wrong with the kit, just our myopic reviewer forgetting to connect up the green wire. The green wire is connected to the ignition side of the cars electrical system. It actually switches on the display so the clock will only appear to be operative when the engine is running. We say appear because it will be working all the time, the display is only blanked out to prevent excess current consumption. Both normal clock and timer functions will continue to operate when the ignition is switched off.



*The completed clock before insertion into the case the two metal strips at the top right and left of the PCB are for time setting.*

Besides ensuring the clocks are working we had to check out the LDR circuit that controls the brightness of the display, and very impressive it is too. The actual display is a four digit flourescent device (green), it has been readable even in bright sunlight, but this will depend to a large extent on where it is mounted.

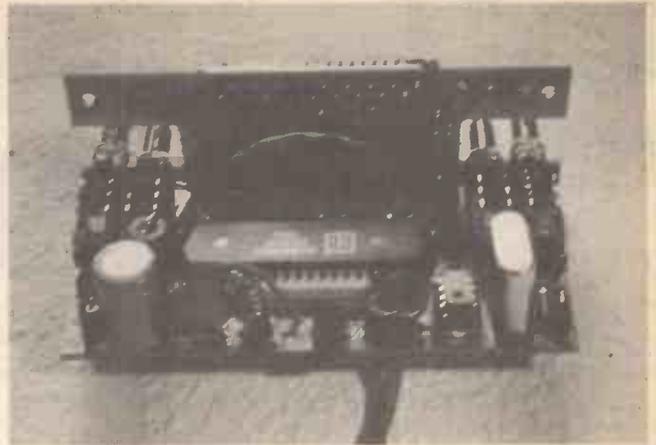All being well the electronics can be put into the rather neat looking two tone grey ABS case. Several options are available, we chose to mount the clock with its bracket on the top of the dash board of the editorial Viva. Apart from looking better it should be easier to read.



*The main timing ICs are mounted top and bottom of the main PCB. The upper one is used for continuous timing functions.*

## ON THE ROAD

With every thing connected up and the clock firmly screwed down on top of the dash (and very good it looks too) we decided to check out its accuracy. The two main clock ICs run independently but from a single timing source. So far under quite variable weather conditions (temperature) and roads, (vibration etc) the main clock has lost five seconds in a week and the timer was accurate to within one second in a twenty four hour period. Both these results are very acceptable considering the adverse conditions and voltage variations of the average car.



*The Heathkit car clock/timer installed on the top of the dashboard.*

## IN CONCLUSION

You may have noticed that this review has said very little about the kit itself. This is simply because the kit went together so easily, and worked first time. It's usually the faults or problems that we write about. As it is, it sounds like one long commercial for Heathkit (it's not actually).

In the past we've commented on a kit's worth as a learning aid, again full marks to Heathkit for their excellent technical explanations, full circuit diagram, soldering instructions, wiring diagrams, component identification etc. etc. We could go on. Let us just say, let all kits be judged by the standard of Heathkit (How about sending us something else Mr Heathkit, those Short Wave radios look rather interesting.)

HE

# LED Tachometer

**The HE Tacho uses 21 LEDs to give a solid-state analogue RPM display. It's an ideal project for the motoring or motor-cycling enthusiast.**

THE HE LED TACHO or 'Rev Counter' is an all solid-state project. It displays engine speed in analogue form (like a conventional tacho) as an illuminated section of a semicircle of 21 LEDs (light-emitting diodes). The length of the illuminated section is proportional to the engine speed, so that half of the semicircle is illuminated at half of full-scale speed, and the full semicircle is illuminated at full speed. In other words, the display is in 'bar' rather than 'dot' form.


The HE Tacho can be used with virtually any type of multi-cylinder petrol engine. It has two speed ranges, each of which can be calibrated via a pre-set pot to give any full-scale speed range required by the individual owner. Our prototype is calibrated to give full scale readings of 10000 RPM and 1000 RPM on a 4-cylinder 4-stroke engine. The lower range is of great value when adjusting the engine's ignition and carburation for recommended tick-over speeds.

The unit is designed for use only on vehicles fitted with 12 volt electrical systems. It can be used with conventional or CD (capacitor-discharge) ignition systems, and is wired into the vehicle via three connecting leads. It can be used on vehicles fitted with either negative or positive earth electrical systems.

## CONSTRUCTION

The complete unit, including the 21-LED display, is wired up on a single PCB. Take extra care over the construction, paying special attention to the following points.

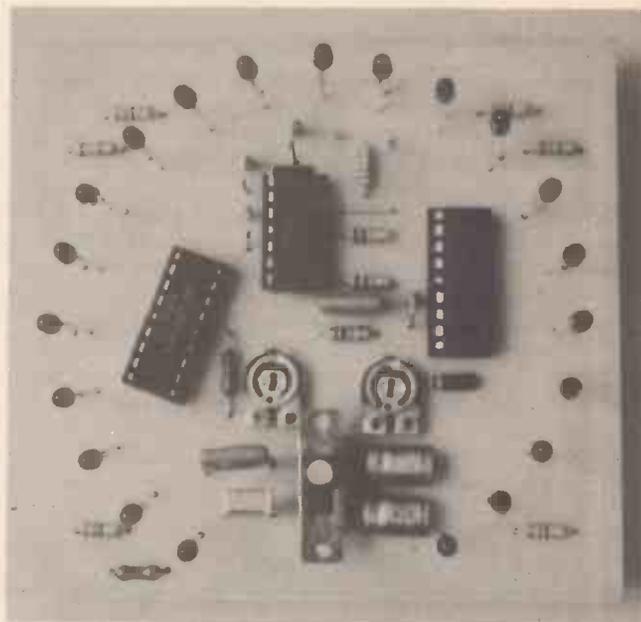- (1). Confirm the polarity of each of the 21 LEDs, by connecting in series with a 1k0 resistor and testing across a 12 volt supply, before wiring into place on the PCB. Note that LED colours can be mixed, if required.
- (2). Take care to connect all semiconductor devices and electrolytic capacitors into circuit as shown on the overlay. Note the orientation of the three ICs.
- (3). Note that four LINK connections (using insulated wire) are used on the underside of the PCB: if in doubt about these connections, cross-check with the circuit diagram. Also note that the external connections to the unit (0 V, + ve, and CB) are made via solder terminals (Veropins).
- (4). Note that the values of C2 and C3 must be chosen to suit the engine type and the full-scale RPM ranges required (see the conversion graph). Our prototype is calibrated to read 10 000 RPM and 1000 RPM on a 4-cylinder 4-stroke engine, and uses C2 and C3 values of 22n and 220n respectively.



**The HE tachometer, make sure all polarised components are inserted the correct way round.**

When the construction is complete, connect the unit to a 12 volt supply and check that only LED 1 illuminates: if all LEDs illuminate, suspect a fault in the IC1 wiring.


## CALIBRATION

The unit can be calibrated against either a precision tachometer or against an accurate (2% or better) audio generator that gives a square wave output of at least 3 volts peak-to-peak. The method of calibration against an audio generator is as follows:

Connect the tacho to a 12 volt supply, and connect the square wave output of the audio generator between the 0V and CB terminals of the unit. Check against the conversion graph to find the frequency needed to give the required HIGH range full-scale RPM reading on the type of engine in question, and feed this frequency into the tacho input. Switch SW1 to it's HIGH range (10 000 RPM on our prototype) and adjust RV1 for full-scale reading.

Repeat the procedure on the LOW range of the tacho (1000 RPM on our prototype), adjusting RV2 for full-scale reading.

# LED Tachometer

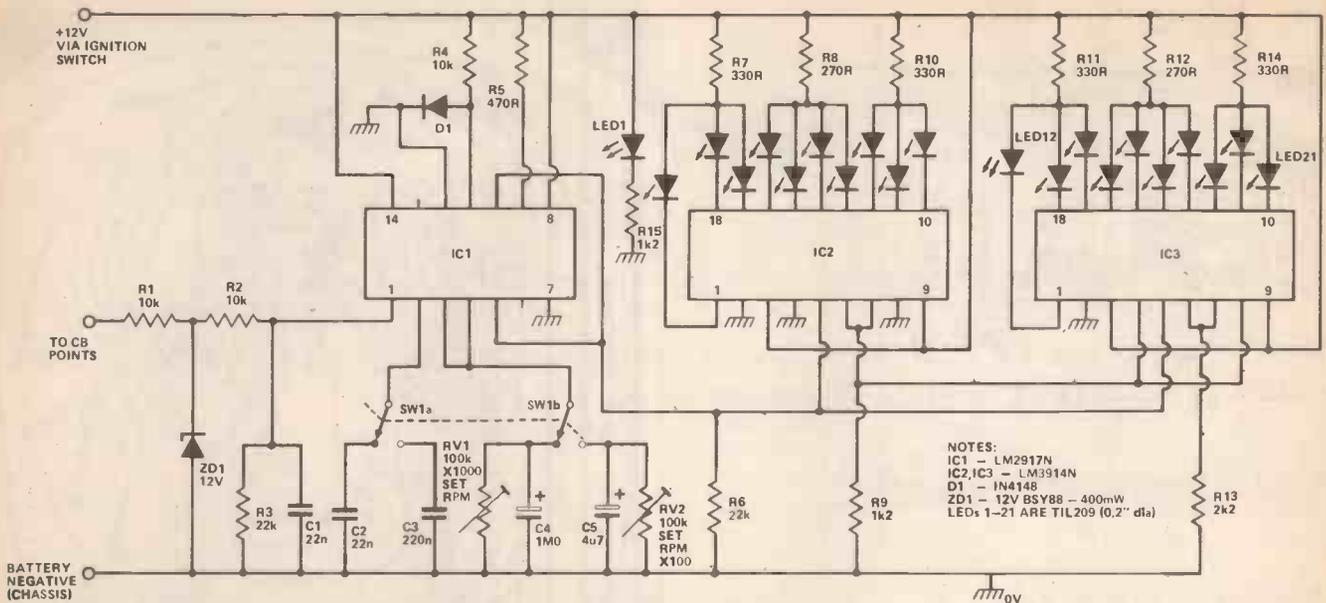

NOTES:  
 IC1 - LM2917N  
 IC2, IC3 - LM3914N  
 D1 - 1N4148  
 ZD1 - 12V BSY88 - 400mW  
 LEDs 1-21 ARE TIL209 (0.2" dia)

Circuit diagram of the LED Tacho, refer to the conversion graph for values of C2, C3.

## How It Works

The ignition signal appearing on a vehicle's contact-breaker (CB) points terminal has a basic frequency that is directly proportional to the RPM of the engine. The HE LED Tacho works by picking up the CB signal, extracting its basic frequency, converting the frequency to a linearly-related D.C. voltage, and displaying an analogue representation of this voltage (and thus the RPM) on a semicircular scale of 21 LED's (light-emitting diodes). The tacho can thus be broken down, for descriptive purposes, into an input signal conditioner section, a frequency-to-voltage converter section, and LED voltmeter display section.

The input signal conditioner section comprises R1-R2-R3-ZD1-C1. The CB signal of a conventional ignition system consists of a basic RPM-related rectangular waveform that switches alternately between zero and 12 volts, onto which various ringing waveforms with typical peak amplitudes of 250 volts and frequencies up to 10 kHz are superimposed. The purpose of the input signal conditioner is to cleanly filter out the basic rectangular waveform and pass it on to the frequency-to-voltage converter. It does this by first limiting the peak amplitude of the signal to 12 volts via R1 and zener diode ZD1, and then filtering out any remaining high frequency components via R2-R3-C1. The resulting 'clean' signal is passed on to input

pin 1 of IC1.

IC1 is a frequency-to-voltage converter chip with a built-in supply-voltage regulator. The operating range of the IC is determined by the value of a capacitor connected to pin 2, and by a timing resistor and smoothing capacitor connected to pins 3-4. In our application, two switch-selected presettable ranges are provided. The D.C. output of the IC is made available across R6, and is passed on to the input terminals of the IC2-IC3- LED voltmeter.

IC2 and IC3 are LED display drivers. Each IC can drive a chain of ten LED's the number of LED's illuminated being proportional to the magnitude of the IC's input signal. Put simply, the IC's act as LED voltmeters. In our application, the two IC's are cascaded in such a way that they perform as a single 20-LED voltmeter with a full scale range of about 2.4 volts: the configuration is such that the voltmeter gives a 'bar' display, in which the first 10 LED's are illuminated at full scale voltage. Resistors R7-R8-R10-R11-R12-R14 are wired in series with the display LED's to reduce the power dissipation of the two IC's. LED1 is permanently illuminated so that the RPM display does not blank out completely when the vehicle's engine is stationary with the ignition turned on.

## INSTALLATION


The completed unit can either be mounted in a special cut out in the vehicles instrument panel, or (preferably) can be assembled in a home-made housing and clipped on top of the instrument panel. In either case, try to fit some kind of light shield to the face of the unit, so that the LEDs are shielded from direct sunlight.

To wire the unit into place, connect the supply leads

to the tacho via the vehicles ignition switch, and connect the unit's CB terminal to the CB terminal in the vehicle's distributor. Note that the unit can be fitted to vehicles using either positive or negative earth systems.


The lower range of the tach (1000 RPM on our prototype) is of great value when adjusting the vehicles engine for correct tick-over: it is thus advantageous to arrange the tacho housing so that it can be easily dismantled from the vehicles instrument panel.

# LED Tachometer

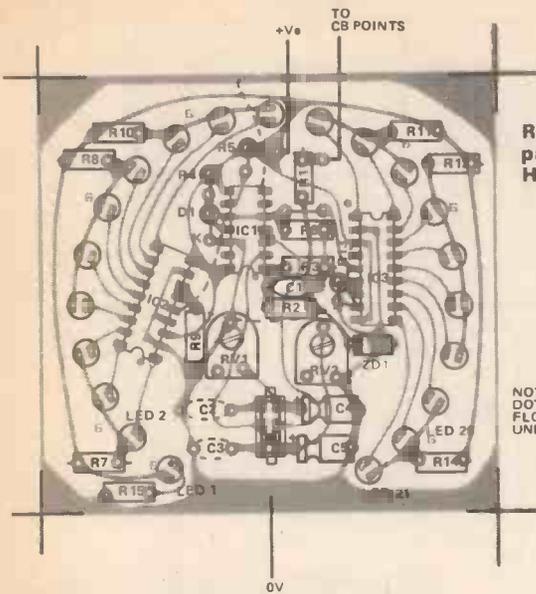

Right, PCB foil pattern for the HE tachometer.

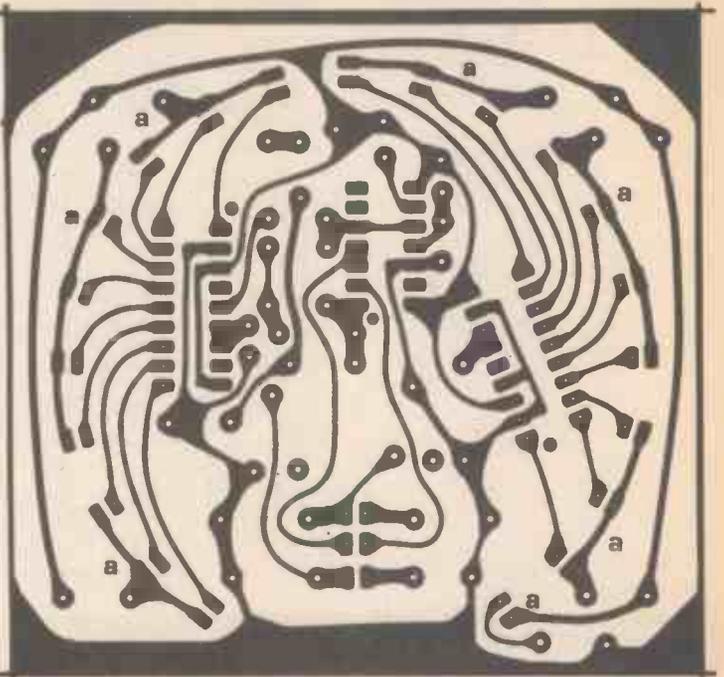NOTE: DOTTED LINES SHOW FLOATING LINKS MADE UNDERSIDE OF PCB



Component overlay for the HE Tacho.

## Parts List

### RESISTORS

R1, R2, R4	10k
R3, R6	22k
R5	470R
R7, R10, R11, R14	330R
R8, R12	270R
R9, R15	1k2
R13	2k2

### POTENTIOMETERS

RV1, RV2	100k Sub. min. preset
----------	-----------------------

### CAPACITORS

C1, C2*	22n polyester
C3*	220n polycarbonate
C4	1µ0 elect. 63V
C5	4µ7 elect. 63V

\* = values used on prototype: see text

### SEMICONDUCTORS


IC1	LM2917N
IC2, IC3	LM3914N
ZD1	12V @ 400mw
D1	IN4148

LEDS 1-21 are TIL209 0.2" dia.


### MISCELLANEOUS

Miniature slide switch (two position double pole). PCB foil pattern.

Approximate cost £10.00.

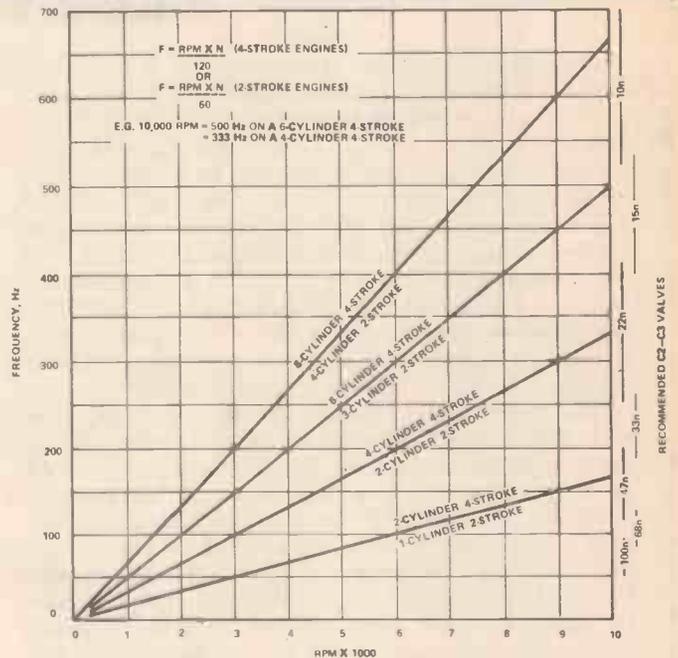

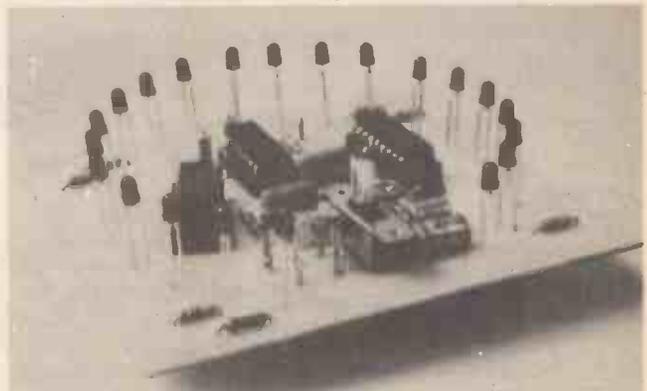Conversion Graph for determining values of C2, C3.



The Tacho prior to installation.

## Buylines


The three ICs used in this project are fairly 'rare' types, particularly IC1. We obtained ours from Maplin, but they may also be available from other large stockists such as Marshalls, etc.

# THREE FOR FREE FROM CSC

ELECTRONICS BY NUMBERS  
FREE PROJECTS  
No 1, No 2,  
& No 3.
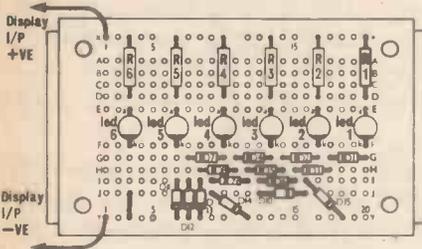
## ELECTRONICS BY NUMBERS LED BAR GRAPH UNIVERSAL INDICATOR

Now using **EXPERIMENTOR BREAD-BOARDS** and following the instructions in "Electronics by numbers" ANYBODY can build electronic projects.  
Look at the diagram and select R1, this is a resistor with a value between 120 to 270 ohm. Plug it into holes X20 and D20, now take LED 1 and plug it into holes E20 and F20. Do the same with the Diodes e.g. plug D7 into holes G7 and G10.



## YOU WILL NEED

- EXP- ANY EXPERIMENTOR BREAD-BOARD
- D1 to D15 - Silicon Diodes (such as 1N914)
- R1 to R6 - From 120-270 ohm resistors ¼ watt.
- LED1 to LED6 - Light emitting diodes.

**LED BAR GRAPHS** are replacing analogue meters as voltage-level indicators in many instances.  
This circuit uses the forward voltage drop of diodes to determine how many LEDs light up. Any type of diode can be used but you must use all the same type. For full working details of this circuit fill in the coupon.  
If you have already built the Two-transistor Radio and the Fish'n'cliks projects you will find that you can reuse the components from these projects to build other projects in the series.

FILL IN THE COUPON AND WE WILL SEND YOU FREE OF CHARGE FULL COPIES OF "ELECTRONICS BY NUMBERS" PROJECTS No 1, No 2 and No 3.

## PROTO-CLIP TEST CLIPS.

Brings IC leads up from crowded PC boards. Available plain or with cable with clips at one or both ends.



- PC - 16 pin. £2.75.
- PC - 16 pin with cable. £6.00.
- PC - 16 with cable and 16 pin clips at both ends. £10.25.



Europe, Africa, Mid-East: CSC UK LTD.  
Dept. 14T2, Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex CB11 3AQ.  
Telephone: SAFFRON WALDEN 21682.  
Telex: 817477.


## EXPERIMENTOR BREADBOARDS.

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build breadboard of any size.  
All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP.4B.

**EXP.325.** The ideal breadboard for 1 chip circuits.  
Accepts 8,14,16 and up to 22 pin IC's.  
**ONLY £1.60.**




**EXP.350.** £3.15.  
270 contact points with two 20-point bus-bars.

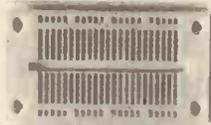

**EXP. 300.**  
550 contacts with two 40-point bus-bars.  
**£5.75.**



**EXP. 650** for Micro-processors. **£3.60.**

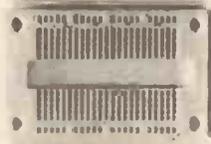


**EXP 4B.**  
More bus-bars.  
**£2.30.**



ALL EXP.300 Breadboards mix and match with 600 series.
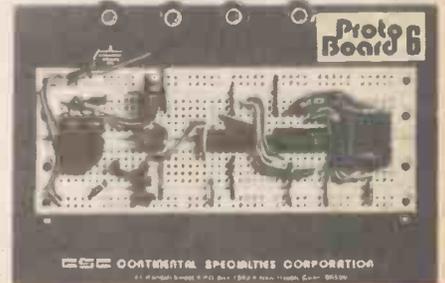
## PROTO-BOARDS.

THE ULTIMATE IN BREADBOARDS FOR THE MINIMUM COST. TWO EASILY ASSEMBLED KITS.



**PB.6 Kit,** 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.  
**PROTO-BOARD 6 KIT. £9.20.**



**PB.100 Kit** complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.  
**PROTO-BOARD 100 KIT £11.80.**

## HOW TO ORDER AND RECEIVE FREE COPY OF TWO-TRANSISTOR RADIO PROJECT, FISH'N'CLIKS AND LED BAR GRAPH.

CSC UK LTD., DEPT. 14T2, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

It's easy. Give us your name and full postal address, in block capitals. Enclose cheque, postal order or credit card number and expiry date. OR telephone 0799 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post that night.

EXPERIMENTOR BREADBOARDS.	CONTACT HOLES.	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INCLUDING POSTAGE AND V.A.T.
EXP. 325	130	1	£ 2.53
EXP. 350	270	3	£ 4.21
EXP. 300	550	6	£ 7.29
EXP. 650	270	use with 0.6 pitch Dip's Bus-Bar Strip	£ 4.69
EXP. 4B.	Four 40 Point Bus-Bars		£ 3.29
TEST CLIPS			
PC. 16.			£ 3.78
PC.16-18.			£ 7.56
PC. 16-18 Dual Clip.			£12.15
PROTO-BOARDS.			
PB. 6.	630	6	£11.01
PB. 100.	760	10	£13.82

NAME .....

ADDRESS .....

FILL IN COUPON & RECEIVE FREE COPY OF  
ELECTRONICS BY NUMBERS PROJECTS Nos 1, 2 AND 3

# CITIZEN'S BAND SPECIAL



Picture from the film *Convoy* courtesy EMI Films Ltd.

No-one could ever accuse HE of being slow to respond to public opinion. Since we carried our major feature 'Citizens Banned' in our June issue the national press, radio and television have all given CB tremendous coverage; obviously we wouldn't claim that HE was responsible but we would like to think we have made some people think about the possibilities of CB.

So for everyone even remotely interested in CB we have produced a 64 page special in record time; it will cover all aspects of CB both at home and abroad, a guide to the law relating to CB, technical information on aerials, the film *Convoy* etc, and views and opinions from the people who know what they're talking about, the R/C modellers the radio amateurs and the major organisations involved in the legislation of CB. PLUS the first English dictionary of CB slang and codes.

The special should be on your newsagents bookshelves by the second week in July, price 75 pence. If you have any difficulty in obtaining a copy write to us at our Charing Cross Road offices, enclosing a PO or cheque for £1.00 (inc P and P) and mark your envelope CB Special.

## Short Circuit

### GUITAR PRACTICE AMPLIFIER

This simple guitar amplifier provides an output that is suitable to drive any normal type of headphones (or earphone), and it permits one to practice without disturbing others, or to practice in a noisy environment where the noise excluding properties of the phones is of considerable benefit.


The circuit is based on an LM389N audio amplifier IC which

contains a small class B power amplifier. The output of the amplifier is coupled to the speaker via DC blocking capacitor C6 and the break contact of headphone socket JK1. Automatic loudspeaker muting is provided by the latter when the headphones are connected to the amplifier. The output voltage swing is considerably in excess of that required by

most phones, and so a degree of attenuation is provided by series resistor R7. R6 and C5 are a Zobel network which aid the stability of the circuit.

As the voltage gain of the amplifier is preset at about 26dB by an internal feedback network, an input level of over 100 mV RMS is required to produce full output. This is far more than the output

level of the majority of guitars. Some form of preamplifier is therefore required. The LM389N has the unusual feature of containing three NPN transistors in addition to the power amplifier circuit. The terminals of these transistors are connected to individual pinouts of the device, and it is two of these devices that are used to form a suitable preamplifier. Q1 is used in the common emitter mode, and unbypassed emitter resistor R3 is used to introduce negative feedback which both boosts the input impedance of this stage to the required level (about 50k) and reduces its voltage gain to the appropriate figure (about 19dB). An input voltage of a little under 10 mV RMS is needed to give maximum output, and this should be sufficiently sensitive to suit any guitar pick-up.

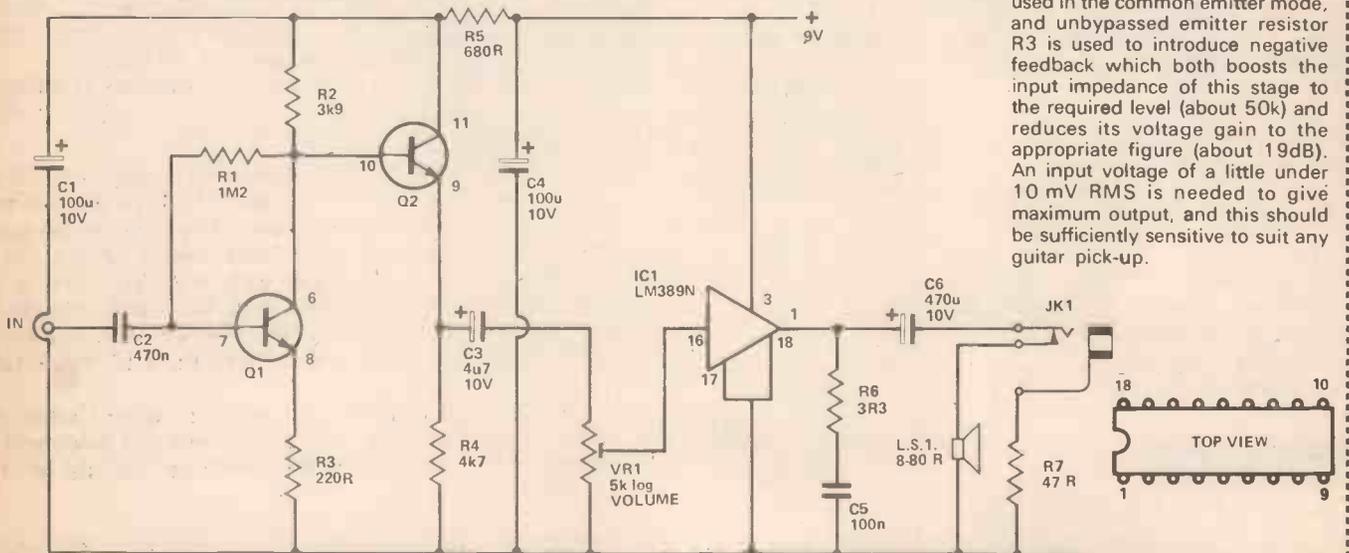

# Breaker One-Four

Send any news, comments, or information you may have to:  
**Breaker One Four,  
Hobby Electronics,  
145 Charing Cross Road,  
London WC2H 0EE.**

***Several hundred letters and quite a few phone calls later we've come to the conclusion that the subject of CB is not going to be swept under the carpet any longer. In view of this we've decided to start a regular column covering as many aspects of CB as we are legally able. We believe we are the first UK magazine to do so, so who knows, we may even change the law.***

THE LETTERS ARE STILL COMING IN concerning our feature 'Citizens Banned', many of them have expressed the wish to be better informed, so for the people who've asked for some kind of column here goes.

We must make a couple of important points first. Firstly we cannot supply any information regarding the availability of CB rigs, circuits etc. Secondly we cannot encourage the use of the 27 MHz system currently in operation, both would be incitement to commit a crime; we've no great desire to run foul of the gentlemen in blue (or any other colour uniform for that matter).

We'll start this month by taking a look back over the past couple of months since the article came out. At least five national dailies have run stories on the recent 'busts' that have been happening in the midlands; isn't it strange that so many articles have started appearing since we ran ours! Of course this is a good thing, the more it is brought to the public's attention, the more people will understand it and hopefully want to experience the delights of 'free speech' for themselves.

## **CLUBS, WHERE ARE YOU?**

We're still waiting to hear from any clubs or organisations that are interested in legalising CB. So far the only club we've heard from is the 10-4 club, their membership is rapidly approaching 200, so keep your letters for them coming. Maybe we will adopt them (if they'll have us) and keep you informed as to their progress. Already they've had a visit from a member of the legal profession to explain the law relating to CB, they are also well in hand with plans to invite a local MP to a meeting to put their points to the people that matter. Meetings are now being held on a regular basis, so if you want to get in touch we'll forward any letters as they are still looking for a permanent address.

## **PETITION**

The petition is doing better than we dared hope. No exact figures yet, but it's into the thousands, so keep them coming. We're having some problems with the post and with moving etc. Send them off as soon as possible and don't worry about not filling them all up. We'll let you know next month when we're handing them over.

## **CBA BANDSTAND**

The CBA have contacted us, it seems someone is using their name to put adverts in the Exchange and Mart, they

would like to point out it has absolutely nothing to do with them, so beware.

News of a newsletter on CB has just reached us, its called 'Bandstand' copies are free, enclose a large skinny SAE and write to: Bandstand, Flagstones, Westheath Lane, Sevenoaks, Kent.

## **LETTERS**

The rest of the column we've set aside for interesting letters, if you think you've got something to say then drop us a line. After all we need to know what you're up to, to make this column as up to date as possible. Meanwhile we're toying with the idea of producing some stickers or badges, more about that next month.

Dear Sir,

I bought my first edition of HE and I have found it extremely interesting. However, concerning the article on CB radio, I must accuse you of writing a very biased article. You almost seemed to be trying to 'sell' the idea to your readers. You actually said, 'Hopefully it will be legalised'.

I have an active interest in amateur radio and can tell you that the amateur service has done a lot for science, in pioneering new ideas in radio telecommunications and electronics. The introduction of Citizens Band radio would bring the amateur service into disrepute.

Jonathon Hallowell  
Manchester

**No one is trying to take anything away from anybody, quite the opposite in fact. Before we get too many 'dog in the manger' type letters consider for a moment a physically disabled driver stuck on a lonely road, late at night and with no means of summoning assistant; the RAE for all its worth is not much use to that person. Have you heard how many lives are saved annually in the US? We could go on.**

**Many people either cannot, or do not want to take the RAE. Why should people be prevented from talking to one another without the aid of the Post Office?**


All the high numbers, stay lucky and BREAKER BREAK.

# COMPETITION


Each month we receive literally dozens of requests for projects, high on the list is an oscilloscope, as we've pointed out in the past its not really practical to build a scope, you simply can't build them as well and as cheaply as a commercial unit. So for all the frustrated scope builders we are giving two away this month as prizes in our first competition.

The first prize is the Calscope Super 10, it's a fine 10 MHz, dual trace instrument, costing £219.00 retail, it features many of the specifications found on instruments costing twice as much. Our second prize is the Calscope Super 6 MHz bandwidth, easy to use controls and perfect for TV servicing applications. It will cost you £162.00 at the moment so as you can see, we're not being mean with the prizes. There will be 20 runners up prizes each receiving a HE Tee Shirt, send in your entry as soon as possible, closing date for entries will be the 20th August 1979.

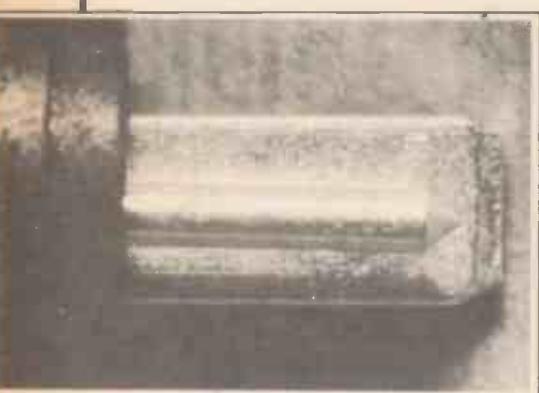The Editors decision will be final. No correspondence will be entered into regarding this competition.




Socket to me? **A**

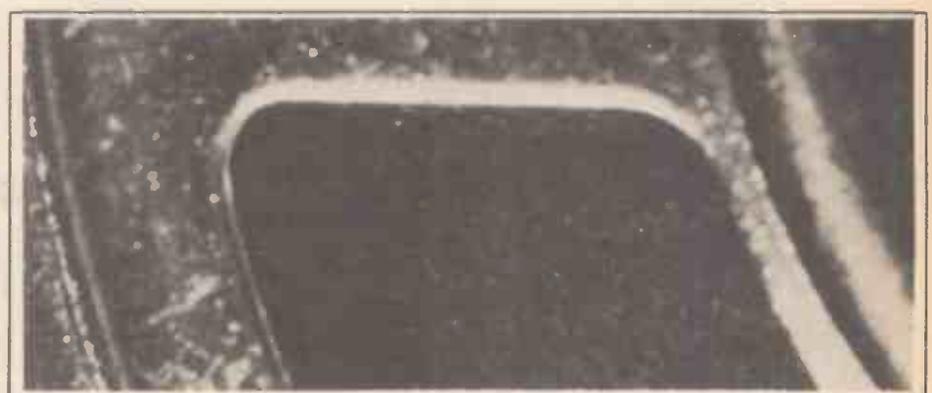


Big talker? **B**




Watch out for this one! **C**

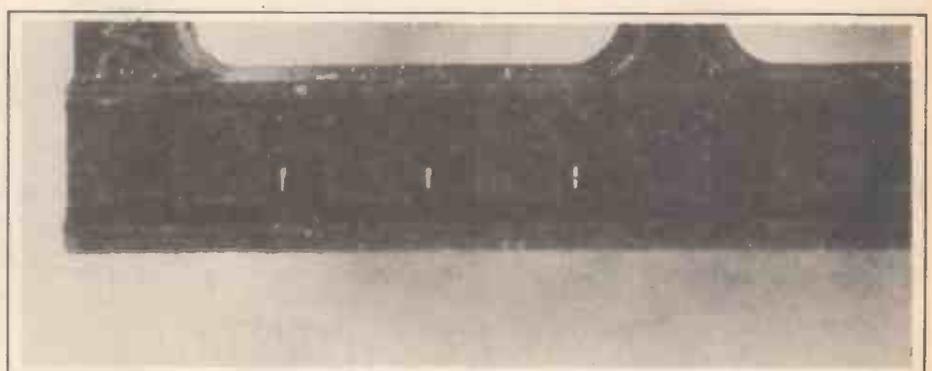


Caterpillar stand? **D**

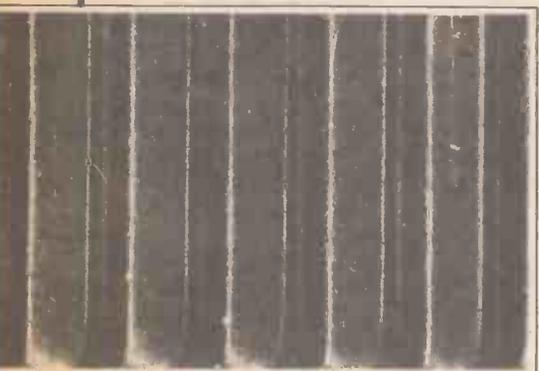




Hot stuff! **E**

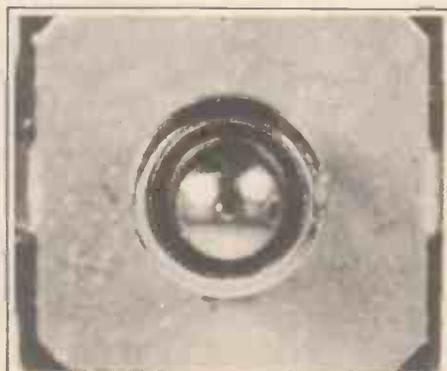

Turned on? **F**

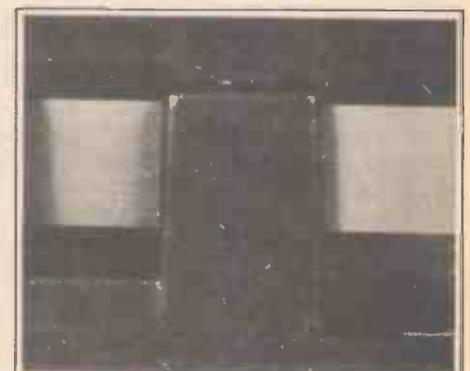

Off the record? **G**

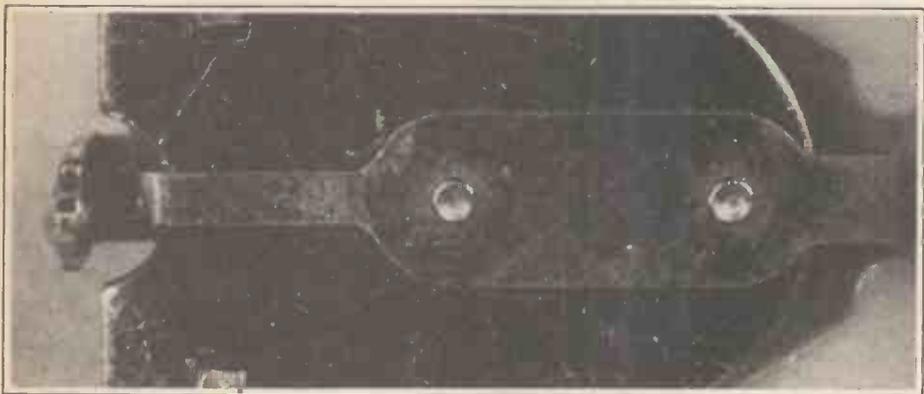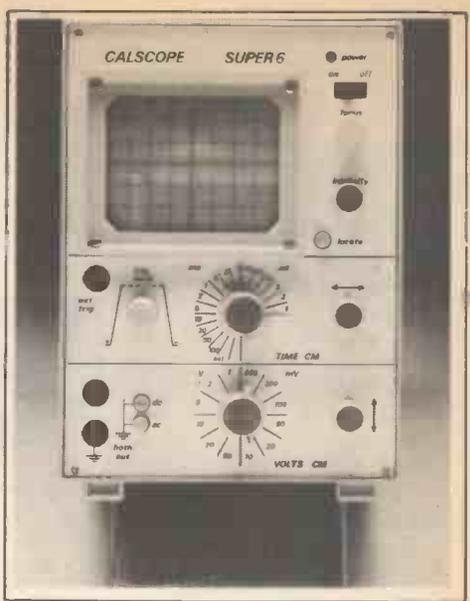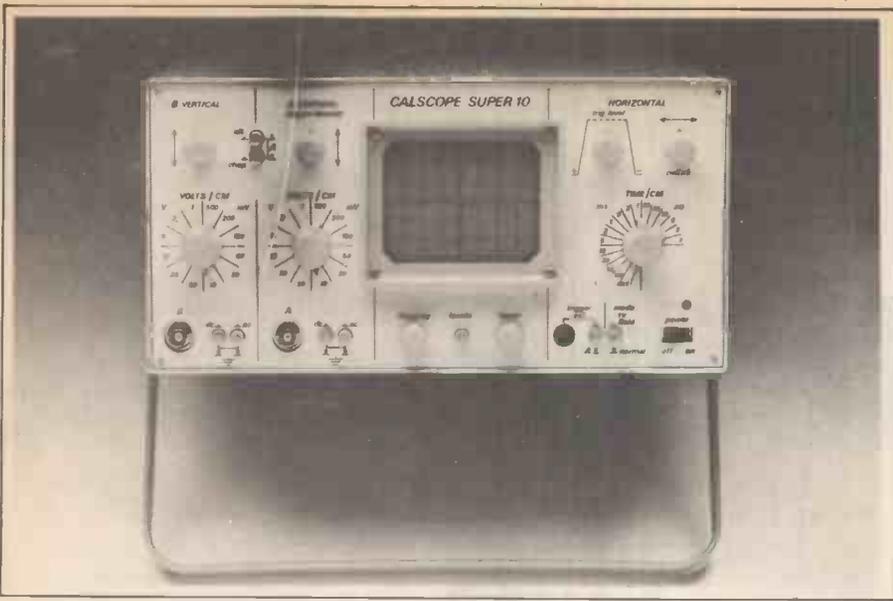


As you can see the competition couldn't be easier. All you have to do is decide what each picture shows, they're all electronic components or hardware and we promise nothing obscure. Send you answers to:

**Hobby Electronics Competiton**  
 145 Charing Cross Road,  
 London WC2H 0EE

- A. ....
- B. ....
- C. ....
- D. ....
- E. ....
- F. ....
- G. ....
- H. ....
- I. ....
- J. ....
- K. ....


... any messages?

H

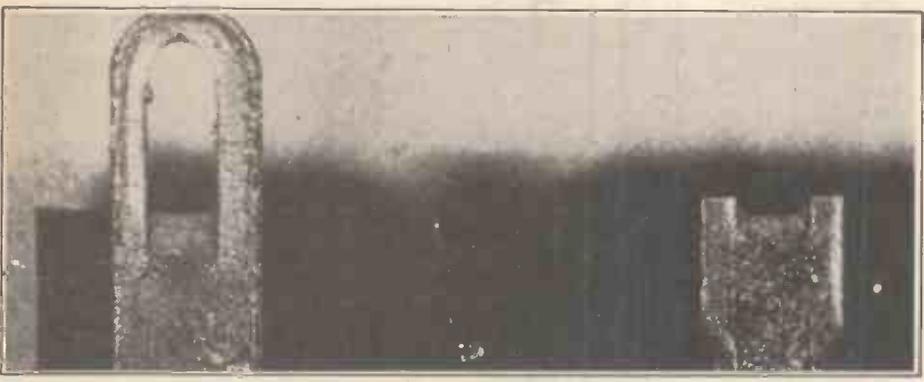

HE ... exposed?

I

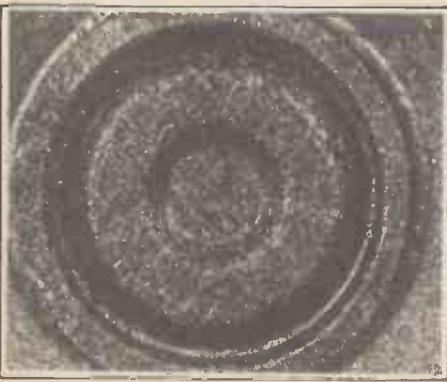

Ice cream?

J



Jaws?

K

Name .....

Address .....

.....

.....

Tee-Shirt size (S, M, L) .....

The winning entry will be drawn from the HE hat, all winners and runners up will be notified by post.

**Next  
Month**

# Hobby Electronics

## ELECTRONIC TIMEKEEPING

Nowadays we take it for granted that a wrist-watch costing little more than £5 will be accurate to within a few seconds a year. Electronic timekeeping as such has been with us for several years now. We have the atomic standard clocks accurate to within one second in a million years (even less in some recently developed machines), or even our own TIM. Look out next month for a detailed investigation into how these clocks (if we can call them that) operate and where future developments may be leading.

## LED CHASER



You may be thinking we've got a thing about flashing light displays, you'd be right too. This month we have a go at a LED Chaser, watch the light appear to move, build several and have your name in lights, annoy the neighbours, it's all here. Easy to build too.

## FET SPECIAL

What do you know about FETs? Next month, rather than bore you with a lot of graphs and theoretical circuits we're doing a large feature on FET projects, there's quite a few RF circuits (no not CB rigs) for you to build and experiment with, we always think it's a lot easier to learn about something by using it rather than reading about it.

## ULTRASONIC REMOTE CONTROL

You can't see it but it's there. Amaze your friends, turn the light on and off, how about switching the telly on or even locking the cat flap? It can all be done with next month's high frequency ultrasonic remote control; popular with the dogs too.

## RADIO CONTROL




We're sorry to say that we upset some of our friends the radio control enthusiasts with our feature 'Citizens Banned' (Hope we're redeemed ourselves now?) So to redress the balance we've persuaded one of the country's leading experts to write a feature on the current R/C scene and what's going to be happening in the future of this fascinating hobby.

## THYRISTORS

Have you ever wondered about Thyristors? These rather interesting semiconductor devices have made considerable inroads into the 'power handling' areas of electronics as well as carving out a whole new field for themselves in control applications. Look out next month for a detailed investigation into the application, characteristics and history of Thyristors.

## HOME COMPUTING

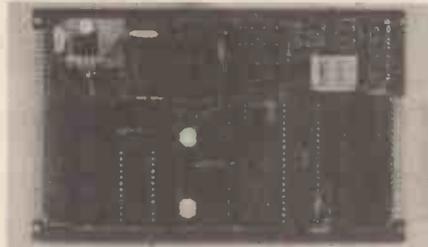

It's been quite a while since we looked at computers, so next month we will be doing an up to the minute investigation into the latest computer happenings, and with a bit of luck a quick peer into the guts of some of the latest machines.

## STEREO AMPLIFIER

At last, a true Hi-Fi, high power stereo amplifier. Not one of your common or garden 5 watt jobs, not even 10 watts per channel, its . . . . . Well, you'll have to wait until next month to find out. What we will say is, that it will hold its head up amongst the many amplifiers that are flooding our high streets, and its British folks, through and through (we think). It uses modular construction so no problems getting all the bits together, we think it's a winner.

## LAMP DIMMER



Lamp Dimmers are always popular, it's good to have a really practical project, one that you'll use every day. And it should save you money too, a good non-nonsense easy to build project, fit to grace any living-room wall.

## BREAKER ONE FOUR



Don't forget to 'eyeball' our new regular feature on CB next month, all the latest news, views and information.

---

## The September issue will be on sale August 10th

---

The items mentioned here are those planned but circumstances may affect the actual contents

# Tools

***What can you never have enough of? The answer is tools, for those of you just starting out in our hobby Rick Maybury takes a look into the wonderful world of tools and points out some of the more obvious things to look out for when parting with your hard earned money.***

IF YOU'RE ANYTHING LIKE US, your entry into the wonderful world of electronics followed a pretty rough transition period. Like us you were probably fascinated by the apparent ease at which examples of high technology could be assembled by even the most dimwitted for just a few shillings. (Still can't get used to this new fangled money). All you needed was a soldering iron (or something that could be persuaded to heat up would do just as well) and a few of those little coloured tubes with a wire at each end and Bobs your uncle.

Your first project was probably far too ambitious and almost certainly didn't work. This is the critical point, most of us did not give up, (you wouldn't be reading this would you?). With luck and hindsight (and plenty of determination too) your second or third project did work, (much to your surprise and delight) and you

proceeded to be 'hooked', probably for life.

## **STARTING OUT**

The point of all this, is that most first-timers can avoid many of these traumas when first embarking on electronics, simply by going into your new hobby well prepared. And this means having the right tools for the right job.

There is a common fallacy that the more you spend the better the quality of tool you will get. To an extent this is true, but there is a breakpoint after which your money will be wasted. A better rule of thumb would be to ask. Ask people who know. Anyone who has worked in the electronics industry will have had all of their unfortunate experiences fairly early on in their careers so



***Basic soldering equipment, don't forget a stand, preferably with a wiper sponge, a solder sucker too will save much heartache and many burnt fingers.***

their toolkit will have evolved into a pretty sophisticated piece of equipment. After all no-one wants to make work for themselves, and every job will have a tool best suited to its speedy completion.

Some of the handiest tools are also the cheapest. Have you ever dropped a screw or nut into an inaccessible part of a radio cabinet? Next time try a small magnet on the end of a piece of string, or magnetise an old screwdriver rather than try to remove it by brute force.

Its obviously difficult to recommend specific makes of tools for your tool box but we can give you the benefit of some of our more disastrous (and rewarding experiences) to start you off. So lets assume you have nothing (not money, however, you'll need plenty of that) and want to start a tool kit.



*A temperature controlled soldering iron, nice to have if you plan to leave it on for prolonged periods.*


## HOT STUFF

Number one tool has got to be the soldering iron. A quick poll around our office and workshop revealed only one thing, every one to their own! Everyone believes their own iron to be the best there is. When you come to think about it this is not altogether a bad thing, soldering irons are perhaps the most used of all tools, and certainly there is no lack of choice. There really are so many good soldering irons around these days there's no excuse whatsoever for not having two or even three, they're not that expensive either.

Your first iron must be a good general purpose 25 watt model, choose one with an iron coated bit, make sure the bit is easily changed, its surprising how much gunge builds up around the bit after only a few hours use. This type of iron will be your main workhorse and will tackle 90% of all your soldering work. The dry joints and solder blobs come when you try to do those jobs a 25 watt iron is not designed for.

Very fine joints, especially those on closely grouped boards containing ICs or sub-miniature stuff need the fine tip and limited heating capacity of a precision 15 watt iron. Again look out for coated bits, easily interchangeable of course.

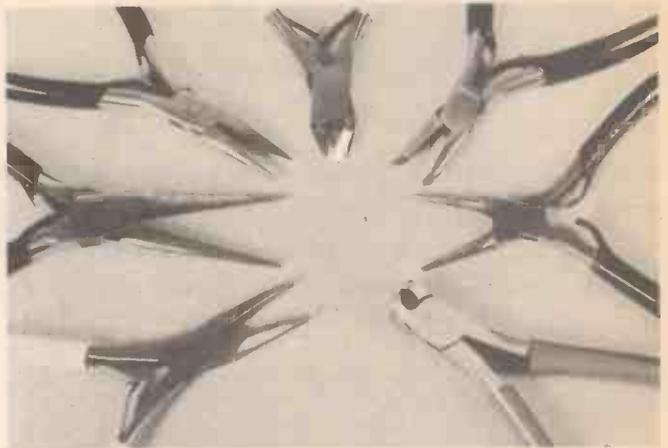The big jobs, soldering chassis earths, tinplate screens etc can only be handled by a 50 or 100 watter. These days we have been blessed with the high capacity soldering guns. They heat up quickly and because of their weight can get a good thermal contact on the workpiece, no messing about.



*Tools that grip, strip and cut, some of the many styles and sizes available.*

As with all tools there are countless variations on the soldering iron theme, everything from rechargeable to variable heat, these types are usually very good for one specific job, so no matter what the literature may say one soldering iron can never be all things to all joints. The right tool for the right job still holds true. Get the feel of one or two, ask around, and whatever you buy, make sure you get a stand with a wiper sponge or you will live to regret, it, and that's a promise.


## A CUTTING REMARK

After you've soldered all your joints on your latest project you'll need to trim off all those surplus bits of wire. No, you don't use the kitchen scissors, you use sidecutters. This is the tool that will wear out most rapidly (apart from the soldering iron bit). You have two options here, buy a cheap pair and discard them when blunt or buy a good pair and hope they last longer, maybe even sharpen them. Whatever you do you will need a couple of sizes, a small one for the miniature work and a hefty pair for the bolt cropping (naughty) etc. It may even be a good idea to have a cheap pair for the rough stuff, see the table at the back for one or two suggestions.

A couple of things to look out for when buying sidecutters, hold them up to the light and make sure the cutting faces mate correctly, check the hinge, is it likely to wear out quickly? Finally look at the handle grips, is the insulation thick enough to prevent you getting a



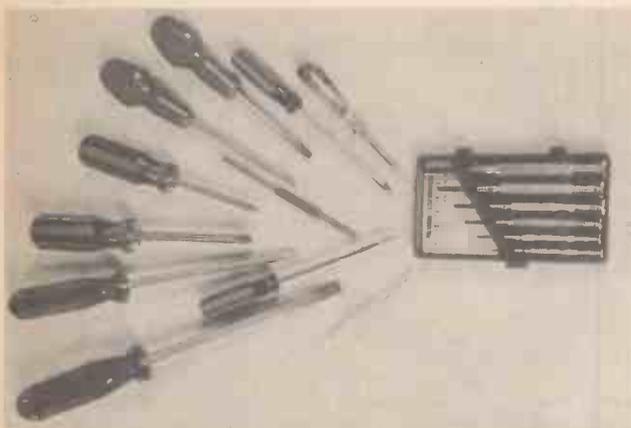*More tools that cut, grip and strip, a good pair of wire strippers could save you a small fortune in dental bills.*



*Screwdrivers, you can never have enough, the jewellers sets are particularly useful when working on sub-miniature equipment.*

shock if they should stray on to voltage carrying wires, you shouldn't be working on live equipment anyway, should you?

## GETTING PINCHED

Pliers now, most of the time a good pair of long-nosed electrical pliers will be quite adequate, look at the tips are they likely to bend or crack?. They probably will if you try to use them for anything they were not designed to do.

A pair of conventional flat faced pliers will also be needed for those large jobs, look out for those handy snippers that are incorporated into some types, both in the jaws and sometimes on the hinge, very useful for cropping thin bolts.

Finally check that they're not going to pinch you if your fingers stray, nasty one that, it hurts for days.

## SCREWDRIVERS

Screwdrivers, you can never have enough screwdrivers, start a collection and get as many different sizes as you can lay your hands on. Avoid at all cost those nasty combination sets of oriental origin that seem to appear from time to time. They are usually all packed neatly in a plastic box with an interchangeable handle or grip. This type is worse than useless. If the blades don't bend, the handles usually crack, one case where you do, get what you pay for, about 50p usually.

Screwdrivers are probably the most used (and



*Box spanners and spanners, again well worth thinking about.*

abused) of all tools so don't be mean, they rarely cost more than £1.00 each, for the larger ones. Don't forget the Phillips and Pozidrive styles, get a couple of sizes of each. Look around for some really miniature ones, they will prove invaluable for some of the imported pieces of equipment. Try to get hold of some plastic screwdrivers (or non-inductive) or trimming tools for variable capacitors coils etc. Finally, going back to the first couple of paragraphs, find a fairly old, long shafted screwdriver and magnetise it. (Strike a permanent magnet along its shaft in one direction only for a couple of minutes — make sure its steel first) this will save many hours of frustration trying to retrieve small screws lost down cracks, or starting off those small cross headed screws that seem to abound in oriental transistor radios.

If you're feeling rich why not invest in a set of box spanners? Stick to about half a dozen BA and metric sizes (2, 4, 6, 8 BA etc) should be enough. They're not tools you'll use a lot but may well get you out of plenty of trouble when you do need them. Its so much easier to do a nut up with one of these than a large pair of pliers, mercilessly thrashing about inside your latest project, decapitating luckless transistors.

## TWISTING THE NIGHT AWAY

Assuming your projects will be housed in cases made from materials other than cardboard, (and they do use cardboard too, we know all about your nasty little habits!), you'll need some twist drills. To make life easy on yourself get hold of a drill to put them in. Two options here, power and hand drills, of course if funds will stretch get both. Whatever you do, you will need a hand drill, they don't cost much, make sure the one you end up with will tightly grip a 1 mm drill, take a pin or needle to the shop with you. Watch out for exposed gears, they bite, nearly as painfully as a large pair of pliers.

The power drill is very much a matter for personal choice, conscience and wallet. A large power drill will come in handy for all those DIY jobs around the house, (that's what you can tell the wife). Variable speed types are worth considering, as much of the time it will be used for drilling pot holes in fairly soft metal, failing that, why not build our HE drill speed controller?

Before we leave drills, if you're going to do a lot of PCB work, it might be worth considering an electric PCB drill, they're small and light, and will slip through SRBP




*Tools for cutting holes, countersinking etc. The purpose-designed PCB drill is well worth thinking about.*

and glass fibre like the proverbial hot knife. As a final thought, when buying drills watch out for the twisted coat-hangers that were masquerading as twist drills a couple of years ago. Don't forget a rack, you'll go cross eyed trying to decipher the miniscule writing on the drill itself.
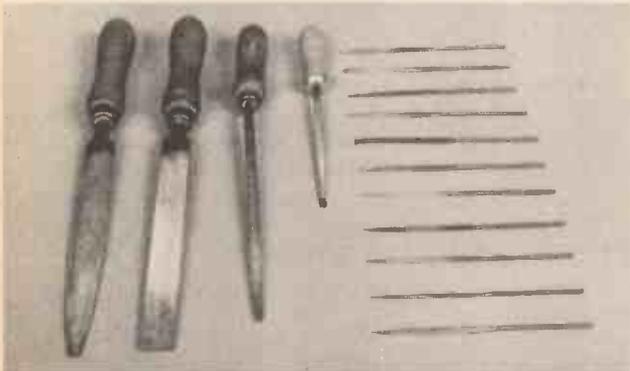
## A HOLE IN ONE

These days making holes is quite a business, some holes you'll need to cut time and time again. A chassis cutter will be well worth having for all those 'pot holes and the larger type of switches. There really is only one type of chassis cutter to have, they're called Q-Max. You'll still need your drill to cut a pilot hole though. The two halves of the cutter are bolted onto either side of the workpiece



*Files, just a small selection, however, sooner or later you'll need most of them.*




*Saws, the large hacksaw is a very worthwhile investment, you'll need the junior version in tight corners. The coping saw will enable you to cut any tricky shapes when housing your projects.*

and with the aid of an Allen key the two halves are screwed together. A shearing action between the two parts leave a neat burr-free hole.
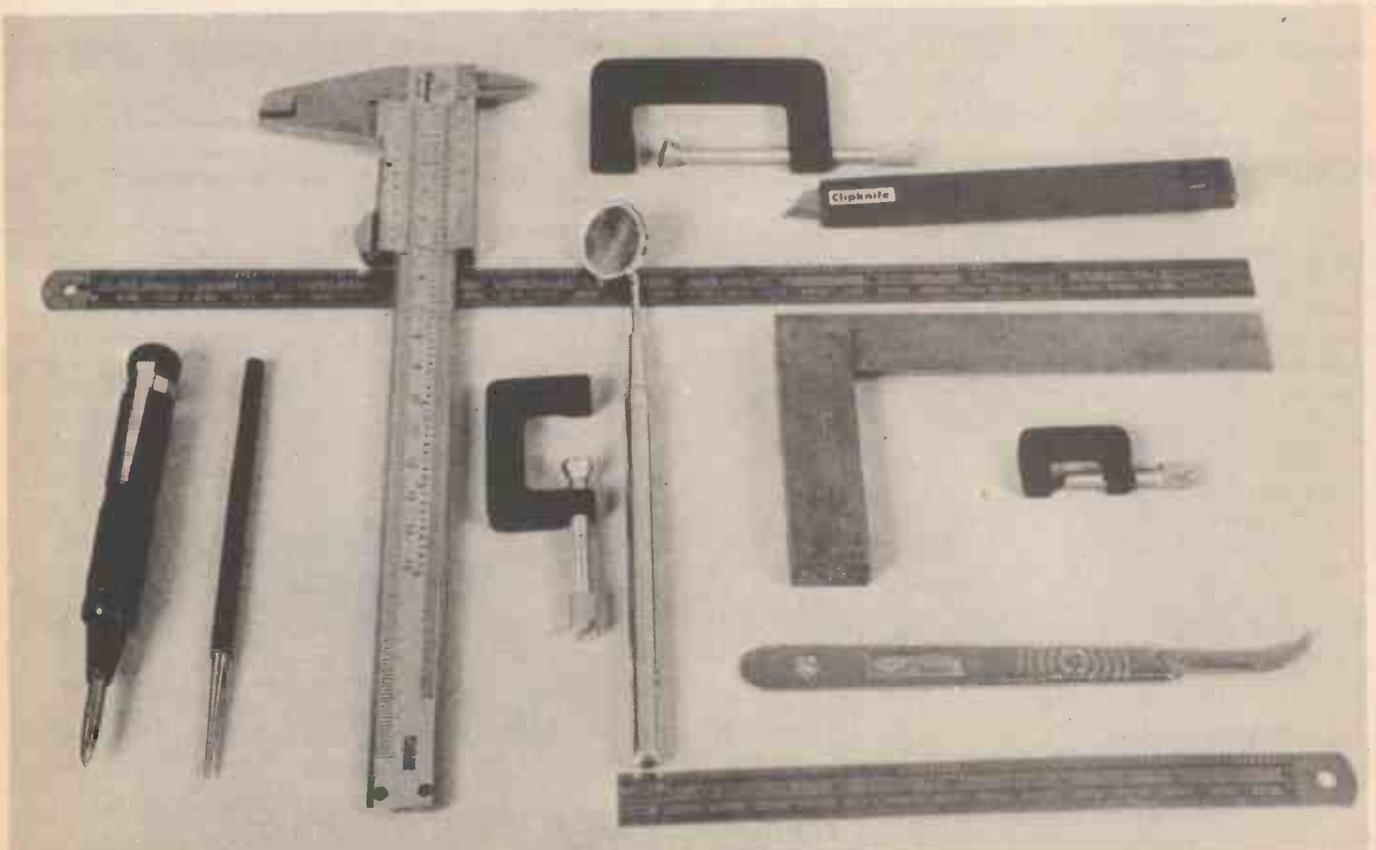
## GETTING IT ON FILE

Just in case all those holes you've drilled aren't quite large enough or not quite the right shape buy a set of files. Only a small selection is needed. Don't forget a reasonably large, coarse one (Bastard) — yes they're really called that. A large and small round, small triangular, and a 'Rats Tail! they're usually about six inches long and taper to a sharp point, ideal for opening up small apertures.



*Essential metal working tools, the automatic centre-punch (far left) will ensure that drills don't go wandering all over your neat front 'panels. The mirror on a stick is handy for seeing into the inaccessible corners. You'll need a sharp scalpel or knife for trimming, slicing etc, it'll also come in handy for cutting the Band-aid when you miss. Remember, it doesn't hurt so much with a sharp knife.*


## CUT IT FINE

So much for holes, how about cutting? The Hack-Saw will be the mainstay for all cutting work. Two types will be most useful. The Junior, about six inches long and a Standard hacksaw. Again don't be mean, lash out a few quid, they'll last a lifetime.

While you're at it get a few spare blades, from our experience blades always break on Sunday afternoons, about an hour after the only shop has closed, and its bank holiday Monday tomorrow. A couple of different grades wouldn't come amiss, you never know when the wife's going to insist you cut back a few branches off the tree.
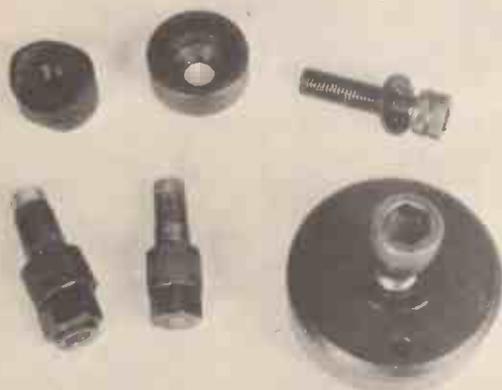
## ODDS AND ENDS

Of course we've only scratched at the surface of what is a vast subject. Let's look at a couple of things worth



Chassis cutters, very useful for large, often cut holes, eg pots and switches.

considering if you've got any money left.

Sooner or later you'll need some kind of de-soldering aid, if money is tight, you may get away with some De-Solder braid, it works by drawing the molten solder into itself by capillary action. A good quality solder pump is the ideal, however, be prepared to pay up to £10 for a decent one.

You may consider buying a PCB jig, they have a lockable action so the board can be moved into virtually any position, again not cheap, around £30-£40 for a pretty average example.

Nuts; don't forget the bolts, you'll need hundreds of them, try looking through the pages of Exchange and Mart for some bulk buys, avoid at all costs those little plastic bags with half a dozen nuts and bolts costing anything up to 50 pence.

Materials; if you're going to make your own PCBs you will need some copper-clad PCB material. We prefer glass fibre to SRBP, it's much stronger and it doesn't cost much more. For the etching get some Ferric Chloride, it's usually cheaper to get it from a chemist than buy those little bottles of acid that are sold for around 60 pence in some component shops.

## TOOLING ALONG

Well, that's about it. As a rule sooner or later most of your tools will end up doing something they were not designed for, so bear that in mind, we're all guilty. Now for those of you that are just starting out, we'll take a look at what might be called an ideal tool box, don't be put off by the cost, you can buy them gradually. In the table we'll mention a few names of manufacturers that we have been pleased with in the past, but don't forget these are personal opinions, your own experience and those around you will be your best guide.

HE

TOOLS	SIZE / MAKE	PRICE (APPROX)
<b>Soldering irons</b> 15 W 25 W 50 + W	Antex, Adcola etc	£2-£5
<b>Screwdrivers</b>	Antex, Adcola, Weller etc Weller etc	£3-£10 £8-£15
<b>Pliers</b>	Broad Blade: large, medium, small	Stanley, Spear etc
<b>Sidecutters</b>	Flat blade: med, small, min.	from 30p to £2.50
<b>Drills (power)</b>	Cross heads: Phillips, large small, PoziDrive	
<b>Drills (hand)</b>	Broad blade, long nosed	Linstrom, CK etc
<b>Drills (twist)</b>	Small, med	from £4-£8
<b>Chassis cutters</b>	Black and Decker, Stanley, Wolf etc	£8-£25
<b>Files</b>	Spear and Jackson, Stanley Dormer, Nos 60, 62, 125, 187, 250, 375	£5-£15
<b>De-soldering aids</b>	Q-Max, 3/8", 1/2", 3/4"	
<b>Miscellaneous</b>	Spear and Jackson, Large coarse, round, large and small, needle file etc	50p-£3
	Erem, Preh etc	£5-£12
	Wire strippers, centre punch, Various, according	
	Steel rule, set square, nuts, bolts (2, 4, 6, BA)	Varies according to supplier

A very brief outline of some of the basic tools you will need to get you started. Of course these are only suggestions, your experience will be your ultimate guide.

# Power From Satellites

*Solar power satellites could provide a real alternative to ground-based solar collector arrays as an infinitely renewable energy source.*

*Brian Dance studies the possibilities.*


WORLD-WIDE DEMAND for energy is growing at around 5% per year. Although conventional power stations using fossil fuels (coal and oil) are now backed-up by nuclear power stations, both fossil fuels and our supplies of fissionable isotopes are being depleted. Some action must be taken to provide for our energy requirements during the next century. Fast breeder reactors have been suggested since they generate fissionable fuel, but some people think the associated environmental hazards are unacceptable.

Controlled nuclear fusion produces little radioactive waste and could use readily available hydrogen from the sea. This method is attractive in principle but despite twenty years' scientific study has not yet produced useful power.
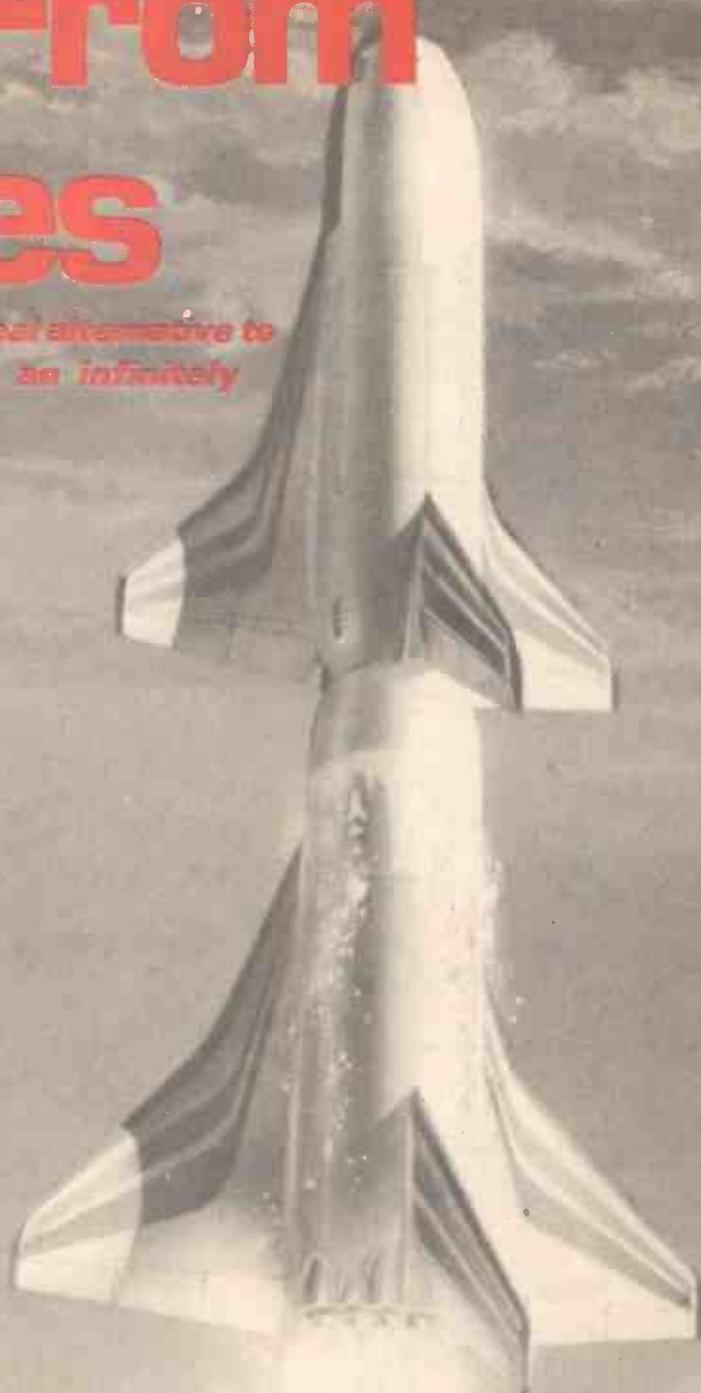
## **SOLAR SATELLITES**

Other sources of power such as the waves of the sea, geothermal sources, photoelectric converters, etc, have been suggested but the most ambitious proposal yet made is for a number of huge satellites (often called 'Powersats' or 'Sunsats') to be assembled in space. They would convert the energy of sunlight into electrical energy which would be sent to the earth as a microwave beam. At the receiving station the energy would be converted into power suitable for feeding to our electricity grid.

This solar power satellite idea is perhaps the most complex and expensive proposal yet made by our civilisation.



# US WORK

Some immediately obvious difficulties include the problem of converting many megawatts of power into a focused microwave beam, the possible effects of the beam on people, animals and plants and its effect on the ionosphere and our weather. But the potential benefits are so great that the United States National Aeronautics and Space Administration (NASA) and the US Department of Energy have provisionally allocated 15.6 million dollars for work on the project up to 1980, at which time it will be compared in detail with other possible energy sources. Now a bill is being considered by Congress which would increase the amount by 25 million dollars for the fiscal year beginning in October 1979.

Bombing Aerospace, Varian Associates, the Jet Propulsion Laboratory of California and the Raytheon Company of Waltham, Massachusetts are some of the companies contracted to work on the project.

Although the US Department of Energy actually manage the funds for the Solar Power Satellite project, NASA is deeply involved with the development of new launch vehicles required for putting huge payloads into orbit. NASA has already established a Solar Power Satellite Office.

The idea of a solar power satellite was first proposed just over ten years ago by Dr Peter E. Glaser. His suggestion was not taken very seriously at first, but NASA investigations in 1971/72 showed that it would be a feasible project. At the present time there is enormous interest in the USA in solar power satellites and campaigns are being organised to encourage the Government to proceed with the work in great haste. Peter Glaser leads a group of industrialists known as the "Sunset Energy Council", this Washington-based



Artist's impression of a 'Solvanna' used to receive and convert the microwave energy from the power satellite, to usable electric power.



Council was formed on solar power satellites. Naturally US electronics manufacturers are well represented on this Council (including General Electric, RCA and Westinghouse), since such a project could bring a vast amount of work to the electronics industry.

## CURRENT IDEAS

The proposals currently being considered are for a number of huge solar power satellites each providing a power level of some 10,000 megawatts and weighing some  $10^8$  kg (100,000 tonnes) with an area of about  $100\text{km}^2$ .

In order to place such an amount of material in orbit, it has been estimated that one would require a few launchings per day of huge Space Shuttle type vehicles over a period of a year or so. Boeing Aerospace are studying the possible effects of such launchings on the environment which will far outweigh the flights of our own Concorde. Launch and recovery problems may be considerable and the choice of rocket fuel may be limited by considerations of the resultant atmospheric pollution.

A solar power satellite would operate in geosynchronous orbit: this means orbiting at a rate calculated to keep the satellite apparently stationary above a point on the earth's surface. The receiving station would always be in a direct line-of-sight from such a satellite which could supply microwave energy for over 99% of its operational life. The other part of the time is spent with the satellite in the shadow of the earth, so it cannot supply power at this time. However, such eclipses of a power satellite would occur only for short periods when it is late at night in the region of the earth being served when electricity demand would normally be quite low.

A satellite in geosynchronous orbit receives at least six times as much solar energy as a similar collector on earth (although a figure of nearly twenty times is more typical). A 10,000 MW (megawatt) solar power satellite could supply all the electricity requirements of New York City or London. About forty-five such satellites would be required to match the present electrical generating capacity of the USA. Smaller satellites providing outputs down to 2500 MW could be economical propositions for some areas.

If it is decided to proceed with the construction of one or more solar power satellites, hundreds or even thousands of people will be working in space on the project.




basic forms seem to be currently in favour. In the photovoltaic type of satellite, an array of perhaps  $14 \times 10^9$  solar cells would be employed with a total area of about  $24.8 \text{ km}$  in length by  $5.2 \text{ km}$  in width ( $129 \text{ km}^2$ ). These cells would convert the energy radiated from the sun into a direct current.

Another possible system is known as the Brayton heat engine satellite; it would employ a series of four huge parabolic-dish reflectors, each about  $5.6 \text{ km}$  in diameter and similar to the reflectors used with conventional microwave aerials. The whole satellite would stretch some  $23.7 \text{ km}$  across space. The parabolic reflectors would collect the energy from the sun and would direct it into a 'solar furnace'. Each reflector would consist of thousands of steerable, extremely thin plastic reflectors which would direct the energy into a dome-like cavity absorber or solar furnace located near each dish.

Helium gas operating in a closed loop could be heated in the solar furnace cavity so that it passes through gas turbines and would then flow through a space radiator where the heat from the gas would be passed to the


## ENERGY CONVERSION SYSTEMS

A number of forms of energy conversion have been studied for possible use in a power satellite, but two

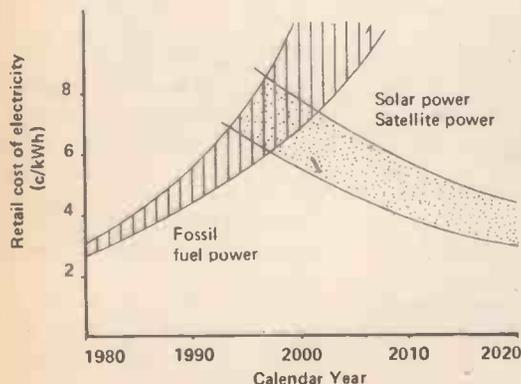

**Fig. 1.** The graph at left shows how the cost of electricity generated from the burning of fossil fuels (coal, oil) will increase over the next two decades. The cost of solar power derived from the proposed satellites is likely to become an economic alternative within 15 years.

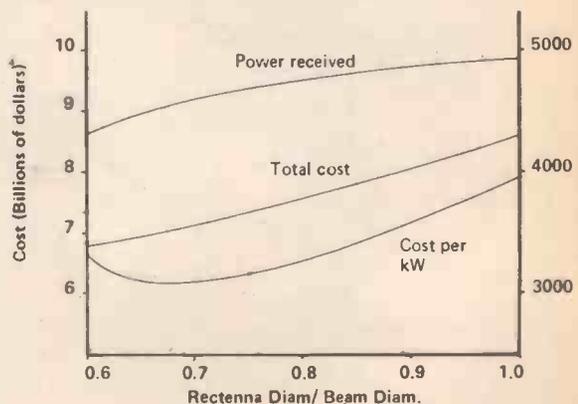
The graph at right indicates how the cost of a solar power satellite system varies depending on the diameter of the receiving antenna (Rectenna) on earth. Optimum cost per kW is obtained from an antenna of about 700 m diameter.


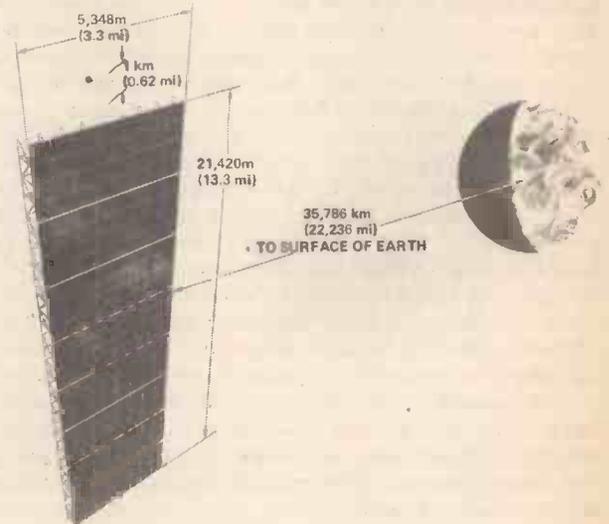
# Power From Satellites



*Space Shuttle type vehicles may be used to ferry materials to a 'factory' in a near earth orbit constructing a power satellite, the completed structure being moved later to a geosynchronous orbit.*



radiator for dispersion into space. The space radiator could employ a liquid metal loop with a helium/liquid metal heat exchanger. A liquid alkali metal such as potassium, would suffer little contamination in space. The gas turbines would drive a dynamo. As there would be no gravitational force in the region, the turbo-generators could be entirely supported by gas bearings.

Power satellites using other types of conversion are possible. The possibility of using thermionic electricity does not seem to be in the running at the moment owing to low efficiency, waste heat rejection and the cost of the materials.

Both the photovoltaic and heat engine systems seem to be possible, although each has its own advantages and disadvantages. In both systems the electricity produced would be beamed to the earth as microwaves. The Boeing study concluded that the weight of either type of satellite would be of the same order, namely 80,000 to 110,000 metric tonnes for a 10,000 MW satellite.

Although the photovoltaic system is less complex, the currently available solar cells are expensive to produce and are believed to be less efficient than thermal cycle engines. In addition, Brayton heat engines have already been operated very successfully on the earth using 7 metre diameter reflectors to generate large amounts of electrical energy.

At the present time it seems that a photovoltaic system using silicon cells is most in favour. Unfortunately they are subject to radiation degradation, but this can be corrected by suitable annealing. It seems likely that silicon solar cells which have spent much time in the region of the Van Allen radiation belt would require re-annealing before use in their geosynchronous orbit.

## MICROWAVE POWER GENERATION

The conversion of some 10,000 MW of power fed in as a direct current into the required 2.45 GHz microwave beam is no easy task. Varian Associates are basing their plans on the use of 70 kW klystrons cooled by heat pipes for microwave power generation in the satellite. It has been estimated that each satellite transmitter would employ some 250,000 70 kW-klystrons in its 1 km diameter transmitting array. However, Raytheon favour the use of 5 kW "amplitron" devices which are crossed field amplifiers of the magnetron type.

The power transmitter design is largely dictated by the fact that it has been decided to limit the maximum power intensity in the ionosphere to 230 W/m<sup>2</sup> (23 mW/cm<sup>2</sup>), since this is the best estimate of the limit below which localised heating of the ionosphere by the power beam can not exceed the heating occasionally produced by natural effects. Incidentally, the fraction of the complete atmosphere heated by the combined power beams of even a large number of solar power satellites will be extremely small.

## THE MICROWAVE BEAM

It is intended that the microwave power beam from the satellite used to convey energy to earth would use a frequency of 2.45 GHz and would be focused on an array of receiving aerials on the earth over an elliptical area of some 12 km by 8 km in size. The receiving area would resemble a chain link fence mounted in stripes high enough above the ground to allow agriculture and animal grazing beneath the aerials.

It has been suggested by Ralph Chernoff of the Jet Propulsion Laboratory that a phased array of aerials on a satellite of a diameter of about 1 km could produce a suitable beam to the earth. Large phased transmitter

arrays are required in order to produce a narrow beam which can be accurately directed. There may be two transmitters per satellite.

At the receiving station the microwave beam would be converted into direct current. A grid interface converter would then change this current into a high voltage alternating current of the mains frequency used in that region. It is probable that part of the power would be used to electrolyse water at the receiver site so as to generate the oxygen and hydrogen required for liquefaction for use as rocket fuel.

Earthbound experiments at the Jet Propulsion Laboratory have used a conventional communications receiver operating at 2.45 GHz as a beam source to direct power on to a tower at a distance of over 1.6km. A receiving antenna was mounted on the tower; it consisted of a phased array of dipoles with each dipole connected to a diode rectifier and smoothing capacitor, the output being connected to a direct current load. An efficiency of 82.5% was obtained at a level of over 30 kW, the efficiency being defined as the direct current power delivered divided by the RF power transmitted. These experiments, which were performed a few years ago, almost abolished any doubts about the feasibility of obtaining high efficiency power transfer through the use of a microwave beam.

A solar power satellite receiving station could also use a suitable array of dipoles and diode rectifiers; such a system is often referred to as a "rectenna" or "rectifying antenna".

Accurate direction of the power beam from the satellite is essential for optimum efficiency. An error of only 1 second of arc in the direction of the beam will produce an error of about 174 m at the ground from a satellite in a geosynchronous orbit at 36,000 km above the earth.

A "retrodirective" technique is employed in which a signal transmitted from the ground station is used to measure and correct for any mechanical inaccuracies in the transmitting antenna. It is desirable that the wavefront emitted from the 1 km diameter transmitting antenna should be planar to within  $\pm 3$  mm ( $\pm 10^\circ$  phase error) for optimum efficiency. It is probably impossible to obtain such mechanical perfection, but the phase front can be electronically controlled by distributing a reference phase synchronisation signal to all of the sub-arrays from a common source on the antenna and comparing this signal with the signal transmitted from the ground.

Rectenna costs have been found to be a major factor in the overall cost of transmitting the power from the satellite to the grid. Owing to the shape of the beam intensity pattern on the ground, one can reduce the size of the antenna array somewhat in order to reduce the



The 'Rectenna' as seen from the air, it would measure 5 miles by 7 1/2 miles. Microwave levels beneath the structure would allow grazing and farming.

cost per kW collected. In other words, the outer parts of the beam contain so relatively little energy that one cannot collect it economically. The graph on the right (Fig. 1) shows a definite minimum in the cost per kW of the collected power for various rectenna dimensions.

## ASSEMBLY LOCATION

Boeing Aerospace have studied the possibility of assembling the parts of the solar power satellite in low earth orbit and then using the power available from the satellite itself to provide electric propulsion into a geosynchronous orbit. The main advantage of an assembly in low earth orbit is the reduction in rocket fuel requirements from 2.1 tons per ton delivered to a geosynchronous orbit to a mere 0.25 tons per ton. This greatly reduces the cost of launching the solar power satellites.

However, there are quite a number of disadvantages of assembly in low earth orbit, some of which are not easy to quantify. Boeing Aerospace feel the main disadvantage of low earth orbit assembly is the relatively long time (about 6 months) required for moving the satellite assembly from low earth orbit into geosynchronous orbit. This delay represents interest chargeable on the cost of the satellite assembly, etc and interest charges on such enormous amounts of money cannot be ignored. Nevertheless Boeing feel that the reduction in the rocket fuel costs make assembly in low earth orbit the best technique.

Other problems associated with assembly in low earth orbit include the radiation damage of the solar power satellite components and solar cells during the relatively long time they remain in the Van Allen radiation belts. The problem of converting the assembled satellite into an electrically propelled unit, the risk of collisions with man-made objects in the low earth orbit and during the relatively slow spiralling passage from low earth to geosynchronous orbit the upper atmosphere drag affecting the construction work.


## HAZARDS

The proposed 10,000 MW beam directed on to the receiving antenna should produce an intensity of some

Rocket type	Time late	Pounds (£s)/kgm	Typical load
Vanguard	1950's	$0.6 \times 10^6$	9 to 14 kg
Thor	1960's	$11 \times 10^3$	450 kg
Saturn	1970's	$0.7 \times 10^3$	110,000 kg
Space Shuttle	1980's	165	
Heavy Lift Vehicle	?	10-15	500,000 kg

Approximate cost of lifting material into earth orbit at various times.

# Power From Satellites

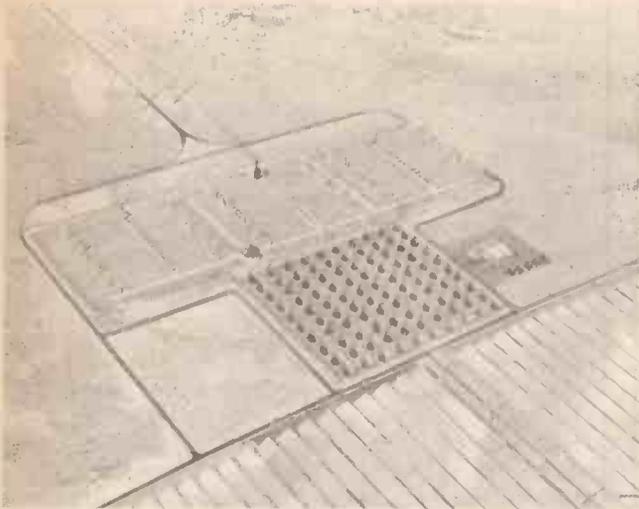

Switchyard which serve as the control point for 5 million kilowatts of electricity produced by the 'powers at' in earth orbit.

230 W/m<sup>2</sup> (23 mW/cm<sup>2</sup>) at the centre of the rectenna and about 10 W/m<sup>2</sup> at the edge of the ellipse. It is rather surprising that the 230 W/m<sup>2</sup> level corresponds to about the level of natural radiation incident upon the ionosphere. Investigations have been made into techniques for reducing the amount of radiation in the side lobes by some 45 dB so that the intensity outside most of the main rectenna area is seldom more than 0.1 W/m<sup>2</sup>. Offshore rectennas have been proposed for use in areas of high population density.

It is claimed that birds and aeroplane passengers would be able to pass directly through the main beam without any harm owing to the low beam intensity. Presumably aeroplane passengers would be fairly well screened from microwave radiation anyway by the metal body of the craft. Peter Glaser has commented: "I have made a standing offer to provide the wine and salad to anyone who promises to eat that duck that flies through the beam — cooked or not!"


Biological tests are to be conducted to ascertain if a microwave beam of 230 W/m<sup>2</sup> produces any effect on birds and flying insects at the 2.45 GHz frequency. Similar tests will be performed at 10 W/m<sup>2</sup> on plants and animals. One wonders whether biological tests at much higher intensities have yet been performed.

Perhaps it is rather remarkable that the rectenna arrays will be suitably elevated to permit frost-free farming or other re-use of the land area. The field strength below the rectenna should be less than the currently recommended maximum US exposure level of 0.1 W/m<sup>2</sup>.

Experiments are planned to test the effect of very high power microwave beams from the huge Arecibo antenna on the ionosphere. These experiments will be carried out with the express purpose of checking that the solar power satellite beam will not produce any detrimental environmental effects.
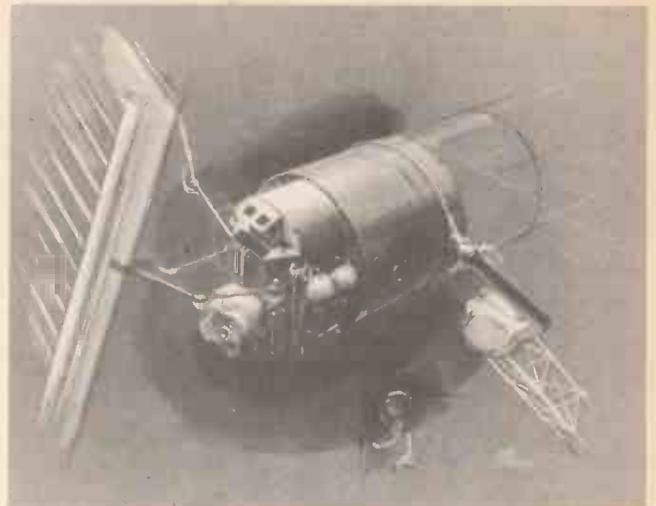
## HEAVY LIFT VEHICLES

The cost of the launch vehicles for placing heavy parts in low earth orbit ready for assembly forms one of the major items of a solar power satellite budget. The Boeing study assumed that a new launcher known as the 'Heavy Lift Vehicle' will be developed which should be able to put



Construction workers would need unique tools to work in the vacuum of space, the drawing shows a one-man capsule manipulating a section of the satellite, below the astronaut in his shirt-sleeve environment.

material into earth orbit for a cost of about 20 dollars per kg. Without such a heavy lift vehicle the whole solar power satellite project would become economically impossible. The enormous fall in the cost of putting material into earth orbit is well illustrated by the table above.

The heavy lift vehicle could either have wings like the shuttle (in which case it could land on the ground like an aeroplane even without using any of its motors) or alternatively it could be a vehicle without wings rather like the Saturn rocket which would return to earth by splashing down in the sea. It seems likely that the type of vehicle without wings will be favoured for heavy loads according to current ideas. The Boeing report shows a Saturn type vehicle 72.98 m in height and 32.68 m in diameter at its base.

## THE EUROPEAN OUTLOOK

The energy requirements of Europe have been studied by the OECD and it is felt that about fifteen 10 000 MW solar power satellites could supply all of Europe's requirements for 1980. (The total number required for the world has been estimated as about sixty-nine.) The total *developmental* cost (not including operation) of a solar power satellite has been estimated as being of the same order as the total investment already made in North Sea oil by European nations.

The problems in Europe associated with a solar power satellite programme are not identical with those in the USA, largely owing to the different population densities. In the highly industrialised regions of Europe (where power consumption and population densities are greatest), there is normally little land to spare for the huge rectenna arrays together with any surrounding safety areas which may be desirable. The low electrical power demand in rural areas and the high cost of conveying power over large distances may render it uneconomic to place rectenna arrays in these rural areas, so some compromise must be sought in choosing the optimum regions for the siting of rectennas.

It is, perhaps, quite amazing that the USA has set a limit of 10 mW/cm<sup>2</sup> as the maximum safe exposure of people to microwave radiation, whereas the upper limit in the USSR is one thousand times smaller, namely 0.01

# Power From Satellites



mW/cm<sup>2</sup>. It is certainly true that exposure to intense, non-ionising radiation at radio frequencies can produce internal heating of biological tissue and this can produce damage if the heat cannot escape rapidly enough for a reasonable equilibrium temperature to be obtained. However, scientists are not yet certain whether other adverse effects than those due to mere heating are also present when personnel are exposed to intense microwave beams. In Western Europe the US standards are applied in radar stations, etc., but it would seem to be highly desirable that the biological effects of microwaves be more intensively investigated so that various countries no longer have a factor of one thousand differences in their safety standards.

## INTERNATIONAL ENTERPRISE

Work on solar power satellites is one of those major technological enterprises which should stimulate international participation and co-operation. The microwave beams can be received in all countries with latitudes between about 65°N and 65°S without any great loss of efficiency. The beam is virtually unaffected by even the heavy rain clouds so often found over many parts of the earth.

One may feel that the use of solar power satellites would not be an economical proposition in countries where the population density is not very high. However, one should remember that once a number of solar power satellites have been placed in geosynchronous orbit, the cost of placing any other such satellites in orbit will be much reduced.

One must not forget the disadvantages of establishing a world-wide solar power satellite system. Such a system would inevitably cause interruption of communications on the 2.45 GHz frequency. However, the enormous power radiated from a power satellite would result in considerable interference not only in the 2.45 GHz band, but also in a relatively wide frequency band around this region and in frequencies which are harmonics of 2.45 GHz. Apart from this problem, increased radio frequency noise is likely to be produced by the microwave energy absorbed by the ionosphere which

results in a raised electron temperature in this region. There would also be interruptions in the radio frequency communications links with aeroplanes or satellites whilst they cross the microwave beams from the power satellites, but doubtless other frequencies or laser beams could be used to overcome this problem.

It seems likely that the equivalent of 1000 or more Saturn V launches would be needed to place one solar power satellite into geosynchronous orbit. The total mass sent into space in a project of this type would easily exceed an astounding 10<sup>6</sup> tonnes/year!

## OTHER REQUIREMENTS

A maintenance vehicle would be needed to maintain and re-supply solar power satellites in geosynchronous orbits — possibly a couple of journeys to each satellite per year. If many solar satellites were in use, a maintenance base in geosynchronous orbit would be justified — especially as it could be used to maintain communications satellites and other non-power craft.

During the construction phase of a solar power satellite (either in low earth orbit or in a geosynchronous orbit) living accommodation must be provided in space for the workers. As the cost of human labour in space will be exceedingly high, intensive studies are in progress to promote the automatic assembly of large structures in space.

## CONCLUSIONS

The need for a non-depletable energy source for the next century is undisputed. Many scientists believe that if the necessary funds are made available quickly, energy could be provided by solar power satellites by about the mid-1990's. The estimated cost of solar satellite produced power is 1700 dollars/kW as against 1400 dollars/kW for power from conventional nuclear power generators. However, the effective cost of satellite generated power will decrease with time, since solar satellites require no fuel and relatively little maintenance. In addition, the cost of fossil fuels will doubtless continue to rise as sources are depleted. The trend of rising fuels costs and falling solar satellite power costs is illustrated in the graph, but obviously all cost estimates are subject to wide variations.

The construction, in space, of equipment the size of a city is quite beyond our present experience. It is not, however, so very far beyond the present state of our art as to be a practical impossibility. No new technological developments are required — only an expansion of current technologies. First of all we must break through the psychological barrier which has convinced us that it is virtually impossible to put a satellite the size of a city and the weight of a battleship into orbit.

If you had perhaps 500,000 million pounds to spend, would you choose to use it on a multi-solar satellite power project, relief for the underdeveloped countries, cancer work or perhaps some other project? Sooner or later decisions of this type must be made about the solar power satellite work. It seems likely that many vital decisions will be made in the USA when the results of the 1980 status report requested by NASA and the US Department of Energy are known.

*The author is indebted to Mr William A. Rice of Boeing Aerospace, Seattle, for the information and photographs which he has kindly provided for this publication.*

# electronics today

international

What to look for In the September Issue: On sale August 3rd



Made your contribution to Confuse-a-Car Week yet? Jog your jalopy's geriatric innards into thinking it's Christmas by giving it one of our car projects.

Now that the Great British Summer's here again, you'll need our heated rear window controller. Hit the button and the wonderful window warmer heats your hindsight for a respectable screen-clearing interval and then switches off again.

Or there's a warning lamp audible repeater. If you're in the habit of driving with your eyes closed (clunk click every trip) you won't see your oil or ignition warning lamps come on. With our repeater you'll hear them.

We're also planning an LED temperature gauge. Watch your radiator blow its top in full technical-our. . . . Next month in motoring ETI.

## SATELLITE SPECIAL

The satellite age dawned in 1957 with Sputnik 1. Since then thousands of tons of hardware have been blasted into orbit around us.

The satellites we have now, a little more sophisticated than Sputnik, monitor our weather, let us look in on a foreign war or the American Open as it happens, take navigation out of the realms of sun and sextant and many more applications, including a few that are distinctly hush-hush.

Next month Ian Graham looks skywards and brings the eye-in-the-sky down to earth.

## LM10? What In The Name Of ETI Is An LM10?

Until last month very few people had even heard of the LM10. In a few more months not having done so will be a bigger disgrace than supporting Chelsea. Ray Marston produces one of his special features to help you out of the second division next month, so don't miss it.

## KEEP IT QUIET, DON'T HISS AND GET IT TAPED PROPERLY

No it's not Dolby. It is based on a brand new chip set from National. It has an amazing low component count. It turns in a very respectable 'sound' and is ideal for home usage. It is inexpensive and a very good reason to buy ETI next month.

# Car Audio

## Manual MW/LW

Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

£1.00  
**£9.95 + Post**

## Push-Button MW/LW

One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

£1.00  
**£15.60 + Post**

## Stereo FM/Cassette

### + MW

Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

£1.00  
**£39.95 + Post**

## Stereo Speaker Set

Suitable for above stereo unit. Good quality in surface mounted casing, 5W nominal, 8W peak.

£3.95 (pair)  
**+ 70p Post**

## Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

**£1.60 + 30p Post**

# Metal Detectors

## Treasure Tracer Mk III

The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive, stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit: £17.50 + £1.00 Post  
Bullt: £22.50 + £1.00 Post

## ★ Induction Balance Model

Built with sensitivity up to 10in on single coin; fitted with speaker and meter; PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

**£22.95 + £1.00 Post**

All goods guaranteed one year. 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for illustrated leaflet.

## Minikits Electronics Ltd.

8H Cleveland Road  
S. Woodford  
London E18 2AN

# ETI MA

## CLOCK RADIO



You probably won't believe us as we're selling the goods but we're going to tell you anyway! We have *rejected* eight clock radios for Marketplace, they were all cheap enough but the quality was so poor that we couldn't have lent our name to them. However, we are now able to offer a portable LCD Clock Radio to you which meets our standards.

The clock is a 12-hour one with AM/PM indicated and a back light. The radio is Medium Wave and FM with very nice quality for a small speaker — for FM there's a telescopic aerial. The alarm can be either a 'beep-beep' type or the radio, there's also a snooze facility.

The case is sensibly rugged and is printed on the back with a World Time Zones map, a bit of a cheek really, especially as the time is relative to Japan!

We won't even mention the RRP — but just check on comparable prices — you'll find ours a bargain.

An example of this Clock Radio can be seen and examined at our Charing Cross Road offices.

**£17.95**

(Inclusive of 15% VAT and Postage).

To:  
**CLOCK RADIO Offer,**  
ETI Magazine,  
145 Charing Cross Road,  
London WC2H 0EE.

Please find enclosed my cheque/PO for £17.95 (payable to ETI Magazine) for my Clock Radio.

Name .....

Address .....

Please allow 28 days for delivery.

## DIGITAL ALARM



THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking' switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

A example of this clock can be seen and examined at our Charing Cross Road offices.

**£10.60**

(Inclusive of 15% VAT and Postage).

To:  
**Hanimex Alarm Offer**  
ETI Magazine  
145 Charing Cross Road,  
London WC2H 0EE

Please find enclosed my cheque/PO for £10.60 (payable to ETI Magazine) for a Hanimex Digital Alarm Clock.

Name .....

Address .....

Please allow 28 days for delivery.

# MARKET PLACE

## LCD CHRONO



We feel we've got to tell you carefully about this offer which we're introducing for the first time. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

### £11.95

(Inclusive of 15% VAT and Postage).

To:  
**LCD Watch Offer**  
 ETI Magazine  
 145 Charing Cross Road,  
 London WC2H 0EE

Please find enclosed my cheque/PO for £11.95 (payable to ETI Magazine) for my LCD Chronograph.

Name .....

Address .....

.....

.....

Please allow 28 days for delivery.

## ALARM-CHRONO LCD



This new addition to our unbeatable selection of bargains is no ordinary LCD watch. It's a slim, multi-function, dual time chronograph alarm watch, no less.

This model will show hours, minutes, seconds, date, day of the week, stop watch, split time, alarm and alternate dual time zone — not all at once, of course. There is also a night light.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The day of the week is indicated by a flag. When used as a stopwatch, the maximum count is 0.1secs. short of thirteen hours.

### £19.95

(Inclusive of 15% VAT and Postage).

To:  
**ALARM/CHRONO LCD WATCH Offer,**  
 ETI Magazine,  
 145 Charing Cross Road,  
 London WC2H 0EE

Please find enclosed my cheque/PO for £19.95 (payable to ETI Magazine) for my Alarm/Chrono LCD watch.

Name .....

Address .....

.....

.....

Please allow up to 28 days for delivery.

# Injector/Tracer


*An ultra-useful piece of low-cost test gear for the DIY electronics enthusiast.*

ONE OF THE MOST USEFUL and inexpensive pieces of test gear that an electronics serviceman or constructor can own is a combined signal injector and signal tracer, or injecto-trace. This amazingly simple yet versatile little device is designed to rapidly and easily locate faults in many types of electronic equipment, including radios, TV's and audio systems.

The HE Injecto-trace generates a 1 kHz 'square' wave which produces harmonics up to 100 MHz or more when used in the INJECT mode, and these signals can be injected into a piece of equipment under test via a simple needle probe and a flying lead. In the TRACE mode the unit will detect AF and RF signals with amplitudes as low as a couple of hundred microvolts and produce the amplified AF or demodulated RF signals in a crystal earpiece. The unit is automatically switched from the INJECT to the TRACE mode when the crystal earpiece is plugged into its jack socket. The HE Injecto-trace measures a mere 3½ x 1¾ x ¾ inches, and is truly pocket sized.
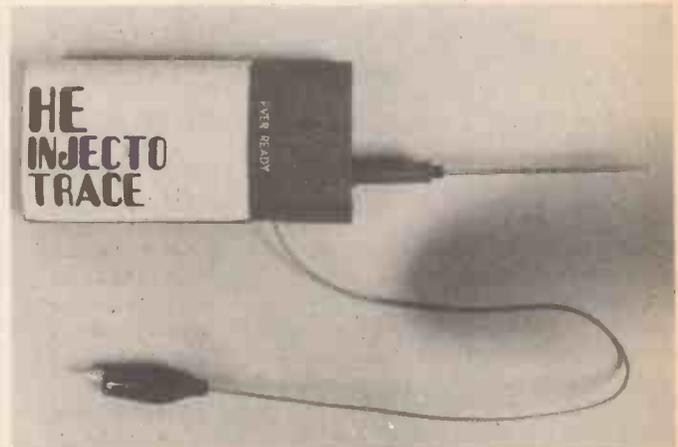
## **USING THE INJECTO-TRACE**

The unit is used in fault-finding applications by systematically working through the defective equipment and



*The HE Injecto Trace in its torch case, note the flying lead and crocodile clip.*

appropriately injecting into, or tracing from, the circuit until the inoperative section of the equipment is located.

Take for example the case of a defective transistor radio in which the battery and the earphone switch (the two most common faults) are known to be good. You can

*The Injecto-Trace being used on a 'dead' radio, by using logical fault finding procedures the faulty component is quickly traced.*



start fault-finding by injecting a signal at the slider of the volume control. If the resulting 1 kHz signal is heard in the set's speaker you'll know that the audio amplifier is OK, and the fault therefore lays further back, in the IF or RF sections of the receiver. If the signal is not heard, you'll know that the audio amplifier is defective. By systematically working either forwards or backwards through the circuit, injecting or tracing as appropriate, the fault area can be easily located.

## CONSTRUCTION


The unit, complete with two HP7 batteries, is built inside a small Ever-Ready pocket torch case and, as can be seen from the photo's, presents a bit of a challenge from the constructional point of view, since the electronics have to be sub-miniaturised.

The PCB is designed specifically to slot into the bulb/reflector compartment of the Ever Ready torch shown in the photo's (it is available from most electrical shops). Note that all components must be mounted vertically on the PCB, with their leads as short as possible. Also note that C2 is mounted with one leg on the PCB and the other on jack socket SK1 (see the circuit diagram), and that the flexible or 'flying' probe lead (a length of lead with a crock clip on one end) passes from the PCB to the outside world via the original on/off switch slot in the side of the torch case. A piece of insulating tape should be fixed to the underside of the assembled PCB, to prevent it shorting against the battery terminals.

A small aluminium panel with the same dimensions as the PCB must be made up to slot into the front of the torch case and hold sub-miniature components SW1 and SK1: our prototype unit also holds a miniature 2 mm socket, into which the metal probe (made from a short length of knitting needle) clips. The interwiring between the PCB and the panel controls must be undertaken with some care, as considerable dexterity is called for in wielding the soldering iron in the limited space of the component assembly area.

HE

Fig. 1. Circuit diagram for the HE Injecto/trace, use only sub-miniature components if the same case as our prototype is to be used.

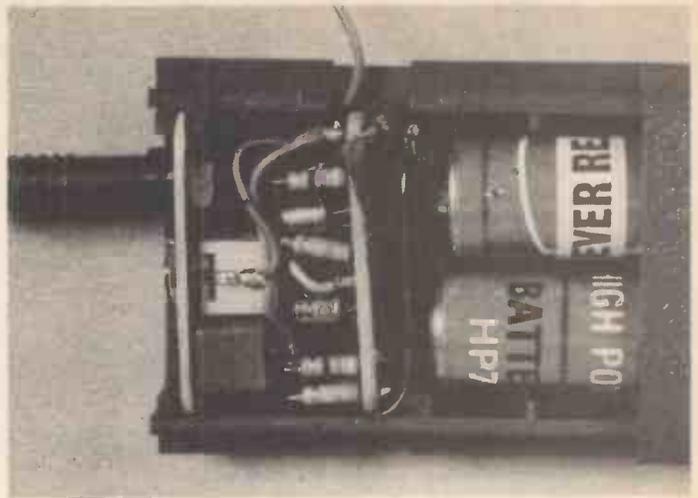


Inside the Injecto-Trace, using the Ever-Ready case results in a really small and compact piece of test gear.
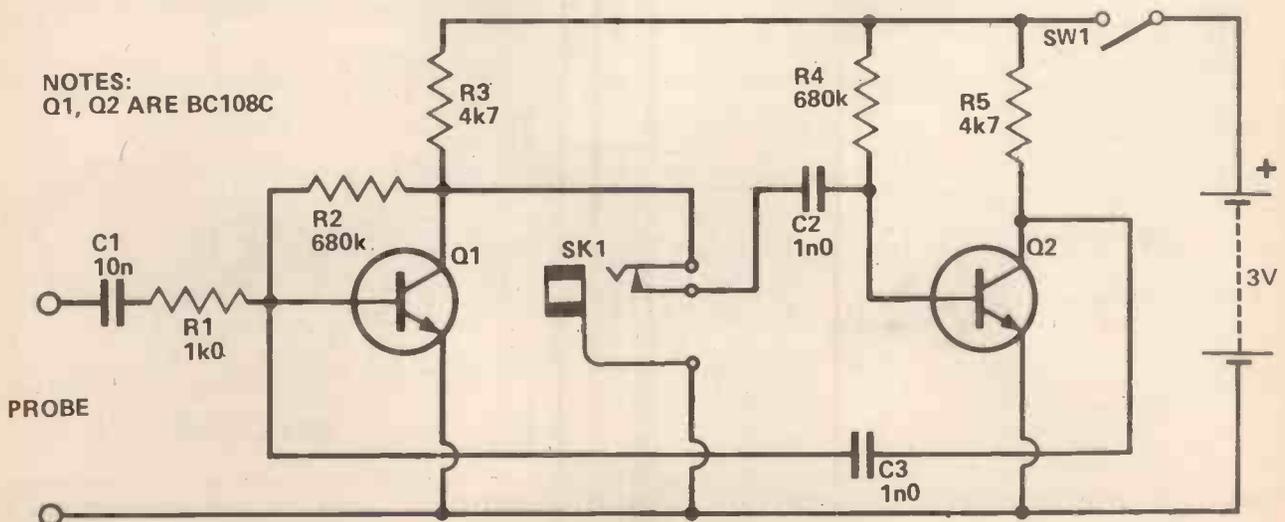
## How it Works

The operating theory of the circuit is very simple. Normally, when the earpiece is not plugged into SK1, C2 is connected directly between the collector of Q1 and the base of Q2, and in this mode Q1 and Q2 act as a modified astable multivibrator that generates an approximately square waveform at about 1 kHz. A distorted and harmonically rich part of this waveform is tapped off at the base of Q1 and can be injected into an external circuit via R1-C1 and the probes.

When the crystal earpiece is plugged into SK1 the earpiece is connected between Q1 collector and emitter, and the connection between Q1 collector and Q2 base is broken. In this case Q1 acts as a high-gain low-level wide-band amplifier, which is driven by signals picked up on the probe, and Q2 is inoperative. The Q1 circuit amplifies AF signals directly, and demodulates RF signals via its base-emitter junction and amplifies the resulting AF components.



## Parts List

### RESISTORS (All 1/4W, 5%)

R1 1k0  
R2, R4 680k  
R3, R5 4k7

### CAPACITORS (All sub-min types)

C1 10n Polycarbonate  
C2, C3 1n0 Ceramic

### SEMICONDUCTORS

Q1, Q2 BC108C

### MISCELLANEOUS

SW1 Sub-min slide switch (PCB type)

SK1 2.5mm Jack Socket

CRYSTAL EARPIECE

PCB

Ever Ready torch case

Approximate cost £3.50

## Buylines

There should be no problems in finding the components for this project. Note, however, that SW1 and SK1 are sub-miniature components. The Ever Ready torch is available from most electrical shops.


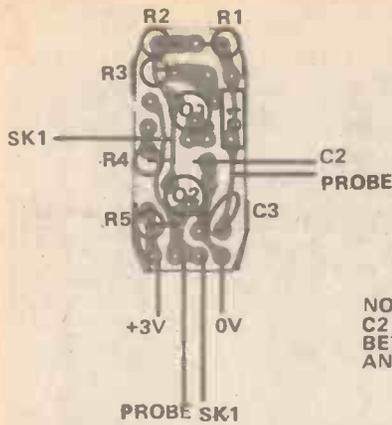


Fig. 2. Component overlay for the Injecto-Trace, keep the leads as short as possible to ensure everything fits in.

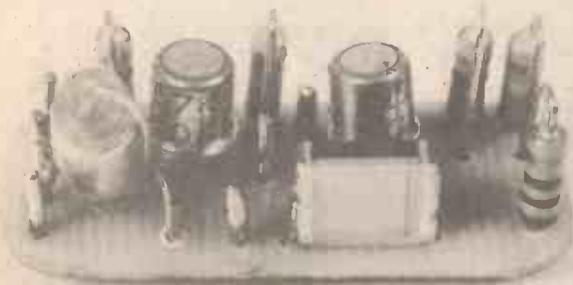

Fig. 3. PCB pattern, this may present some problems to the less experienced, why not try our Hobbyprint service for really first class results.

NOTE:  
C2 IS MOUNTED  
BETWEEN THE PCB  
AND SK1



Close up of the circuit board, you can see how important it is to keep the component leads short.

# Short Circuit

## SCRATCH AND RUMBLE FILTER

Scratch and rumble filtering is a valuable feature in a hi fi amplifier, but is one which is absent from many designs, or if this filtering is present it may well be in the form of a relatively ineffective 6 dB per octave type filter. This circuit is a 12 dB per octave add-on scratch and rumble filter which can be connected into the 'tape monitor' or some similar facility of the amplifier.

This is a conventional second order filter circuit having passive high pass filter formed by the series capacitance C3 and C4, plus the parallel resistance of R2 and R3 (the latter also being used to bias emitter follower transistor Q1). A passive filter of this type gives only a very slow initial roll off, and an ultimate attenuation rate of only 6 dB per octave. A bootstrapping resistor is therefore used to improve performance. Above the cut-off frequency where the gain of the circuit would otherwise fall off somewhat, R1 has the effect of reinforcing the input signal from the output of the buffer amplifier based on Q1. Well below the cut off frequency, losses through C4 result in the signal level at Q1 emitter being well below that at the


junction of C3 and C4. This results in some of the signal at the junction of C3 and C4 being tapped off through R1, with C3 and R1 effectively forming a second high pass filter network. This eliminates the slow initial roll off rate (in fact there is a small and insignificant peak of about 0.5 dB above the cut off frequency) and speeds up the attenuation rate to a nominal 12 dB per octave.

The low pass filter works in

much the same way as the high pass one, except of course, the R and C filter elements have been transposed so as to give the correct filter action.

If only low pass filtering is required, SW1 can be used effectively to bypass the high pass filter components. C2 then maintains DC blocking at the input. SW2 can be used to bypass the low pass filter components when only high pass filtering is required.

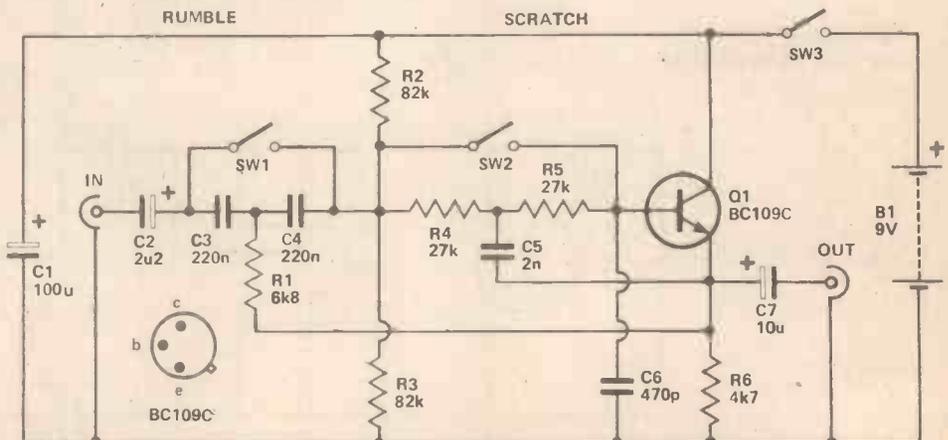With the specified component values the rumble filter response falls below unity at approximately 45 Hz, reaches the -6 dB point just above 30 Hz, and then falls away at a nominal 12 dB per octave. The scratch filter response crosses the unity gain point at about 6.5 kHz, reaches the -6 dB point at approximately 10 kHz, and then falls away at a nominal 12 dB per octave.



# Hobbyprints



We're just etching to tell you about HOBBYPRINTS, we know you won't be able to resist them. There so good we've even patented the idea (1445171 and 1445172). If you're board with all those untidy strip boards or semi-permanent bread boards then read on.

After many months of extensive research we think we've come up with the ideal solution (Ferric Chloride?) to all of those problems people have with making really professional PCBs. (Puns come at no extra charge).

Seriously though, the HOBBYPRINT rub-down transfer, (very similar to the rub-down lettering) is the answer to the project builders prayer. PCBs take up a disproportionate amount of time, using HOBBYPRINTS a typical PCB can be finished in under half an hour. Because HOBBYPRINTS are produced from our original artwork there's no likelihood of making a mistake. They can even be used as photographic masks for ultra-violet PCB production.

Each sheet of HOBBYPRINTS contains all the PCBs for any particular month (an average of four PCBs), so for only 75 pence including VAT and Post and Packing that's not bad value. For a list of projects refer to back numbers ad.

## ORDER TODAY

Send cheque or postal order (payable to Hobby Electronics) to:

**HOBBYPRINTS,  
HOBBY ELECTRONICS,  
145 CHARING CROSS ROAD  
LONDON WC2H 0EE.**

**75p INCLUSIVE OF VAT AND POSTAGE.**

Please mark the letter(s) of the HOBBYPRINTS on the outside of the envelope.

# The latest kit innovation!

## from Sparkrite

*Sparkrite -  
was featured by Shaw Taylor  
in "DRIVE IN"*

the quickest fitting  
**CLIP ON**  
capacitive discharge  
electronic ignition  
in KIT FORM



- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE - Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £3.85 inc. VAT, post & packing.

**Electronics Design Associates, Dept. HE8  
82 Bath Street, Walsall WS1 3DE. Phone (0922)  
614791**

Name .....

Address .....


Phone your order with Access or Barclaycard

Including postage and packing UK only QUANTITY REQ'D. Send SAE if brochure only required.

X4 KIT £16.65 inc. VAT		I enclose cheque/PO's for
TACHO PULSE SLAVE UNIT £3.85 inc. VAT		£

Cheque No. ....

Access or Barclaycard No. ....

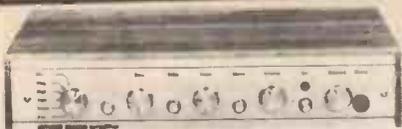

### 20 x 20 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia. red rms indicator and stereo jack socket. Functions switch for mc, magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features two mains outlets DIN speaker and input sockets plus fuse 20x20 watts RMS 40x40 watt/peak. For use with 8 to 15 ohm speakers

£29.90  
£2.50 p&p

### 30x30 WATT AMPLIFIER IN KIT FORM

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output, 60x60 watts peak. For use with 4, 15 ohms speakers.



£29.00  
£2.50

### SPECIAL OFFER

**30 x 30 WATT AMPLIFIER KIT** with BSR P200 belt drive deck and Shure M75 cartridge.

£55.00  
+ p&p £5.00

### EMI SPEAKER BARGAIN

Stereo pair 350 kit. System consists of 13" x 8" approx. woofer with rolled surround. 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max. 8 ohm impedance

£14.95  
Per stereo pair  
+ £3.40 p&p



### BSR P200

Belt drive chassis turntable unit semi automatic, cueing device.

£24.95  
p&p £2.50

A.D.C. QLM 3D Mk III Magnetic Cartridge to suit.

£7.75



**BSR** Manual single play record deck with auto return and cueing lever. Tined with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited from home or disco use

OUR PRICE £10.95  
p&p £2.55

### GARRARD DECK MODEL CC 10A

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth.

£7.95 p&p £2.00 Size 12" x 8 1/2"



**SANYO** Nic/cad. battery, with mains charger equivalent in size and replaces 4 SP11 type batts. Size 3 3/4" x 1 1/4" x 2" approx.

£7.50  
p&p £1.50p



### BARGAIN FOR PERSONAL SHOPPERS ONLY Altone UA4 Stereo System

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones

complete with speakers. £34.95

**Micro Cassette Recorder** Pocket size—home or office use or when travelling.

£13.95

**Battery operated fluorescent camping lamp.** Runs off 8 U2 batteries.

£4.50

# Mullard

## AUDIO MODULES IN BARGAIN PACKS CURRENT CATALOGUE

PRICE & AT OVER **25** PER PACK

### SEE OUR PRICES

**1** PACK 1. 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input  
OUR PRICE p+p £1.00 **£4.95**

**2** PACK 2. 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs.  
illu. OUR PRICE p+p £1.00 **£7.45**

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

### 10 + 10 AMPLIFIER KIT

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit  
Size approximately 9 1/4" x 8 3/4" x 4" p&p £2.05 **£11.95**



### ACCESSORIES

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance.  
£2.90  
plus £1.50 p&p

**Two Way Speaker Kit** Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£3.95** per stereo pair plus £1.50 p&p

### BARGAINS FOR PERSONAL SHOPPERS

LED 5 function men's digital watch stainless steel finish **£5.95**

LED 5 function men's digital watch stainless steel finish **£6.95**

LCD 8 Function CHRONOGRAPH men's digital watch, stainless steel finish **£12.95**

POCKET CALCULATOR. With LED display, memory and percentage key **£2.95**

AM/FM DIGITAL CLOCK RADIO. Accurate 4 Digit Electronic Clock with 1/2" LED display. Buzzer and snooze timer **£11.95**



125 Watt Power Amp Module **£13.95**

Mains power supply for above unit **£3.50**

MULLARD Built power supply **£1.50**

DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc crossovers **£20.00**

VIDEOMASTER Super Store TV Game with pistol mains operation **£14.95**

PORTABLE RADIO/CASSETTE RECORDER, AM/FM with clock LW, MW, SW, VHF mains/battery operation **£41.95**

VIDEOMASTER COLOUR SHOT TV GAME  
Choice of three games—Football, Tennis and Squash. Ready to play—one or two players. MAINS OPERATED OPPORTUNITY AT **£9.95 ONLY**



**323 EDGWARE ROAD, LONDON W2 21 H HIGH STREET, ACTON W3 6NG**

ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 12 1/2%  
All items subject to availability. Price correct at 3/6/79 and subject to change without notice

### 50 WATT MONO DISCO AMP

**£29.95**  
Size approx. 13 3/4" x 5 1/4" x 6 1/4"

50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.



### 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls. Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PEL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak



### For personal shoppers only DUO II SPEAKERS

Attractive teak finish modern design, incorporating 2 speaker units—8" approx. woofer and 2 1/2" approx tweeter. 45 to 1800 Hz impedance 8 ohms. Power 15 watts RMS. 20 WATTS MAX.

Per stereo pair **£17.00**



### FOR PERSONAL SHOPPERS ONLY STEREO RADIOGRAM CABINET

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**  
Size approximately 47" x 15 1/2" x 15"

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432. 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

# Hobby Chit~Chat

**THE DEMISE OF THE  
DISCRETE TRANSISTOR**

**HE project editor and chief designer Ray Marston takes the second of his monthly series of looks at the hobby scene.**

ONE OF THE FRINGE BENEFITS that I have through working for Hobby Electronics is ready access to all of the back issues of HE and its sister magazine Electronics Today International. The British version of ETI was first published in April 1972, a mere seven and a bit years ago. Looking through the back issues of ETI recently I was greatly impressed by the enormous technological changes that have taken place in the hobby electronics scene in that relatively short space of time.

Specifically, I was struck by the fact that most of the projects published in the early, 1970s were based on discrete transistors, whereas most of today's projects are designed around integrated circuits. The discrete transistor has, it seems, become a near-obsolete device in all except the most mundane or the most demanding applications within the past five years.

The transistor itself is, of course, alive and well, since all integrated circuits are based on transistor technology (either bipolar or FET). The reasons for the rise of the IC and the demise of the discrete transistor are primarily economic. An IC containing dozens of transistors usually costs only a fraction of the price, and occupies a fraction of the space, of its discrete transistor equivalent. An IC and its related external components can thus be built on a far smaller and less expensive PCB than an equivalent all-discrete circuit, so the IC user benefits in all ways.

The technological changes that have taken place in our hobby over the past five years have been slow and insidious, rather than sudden and dramatic ones. This process of gradual change will continue throughout the next five years, and beyond. As the years tick by you'll be almost unaware of the changes that are taking place as you effortlessly absorb an apparent trickle of new knowledge. But if, in the year 1984, you look back through your tattered 1979 copies of HE, you will probably be staggered at the total sum of all these gradual technological changes.

## **TOWARDS 1984**

So what changes can you expect to see in the Hobby Electronics scene in the five years between now and 1984? Let's look first at passive components. In the past five years we've seen the demise of the multi-ganged

tuning capacitor as it has gradually been replaced by the Varactor diode, or voltage-tuned solid-state capacitor. We've also seen the demise of the inductor in tuned circuits, as it has been replaced by gyrator circuits in low-frequency applications and by ceramic or crystal networks in high-frequency applications.

In the next five years we can similarly expect to see the demise of the multi-ganged pot or variable resistor as it is replaced by new integrated circuits that are presently under development. We will also see the multi-gang multi-way electro-mechanical switch virtually disappear in all except high-voltage and high-current applications by 1984: these switches are already on the way out, and are expected to be given a final 'heave' within the next two years.

On the digital electronics scene, CMOS ICs will remain strong and healthy over the next five years, but 'conventional' TTL will become obsolete and be replaced by low-power Schottky (LS) TTL: conventional TTL is in fact expected to be 'dead' by 1981.

The much-vaunted microprocessor will continue to become more sophisticated, and the capacities of digital memories will continue to grow. The real explosion in the microprocessor field will, however, come at the low end of the sophistication spectrum as a new generation of 'dedicated' and simplified control oriented processors (COPS) enter our lives. By 1984 the hobbyist will use a COP even more casually than he uses a digital clock chip or a TV games chip today. COPS are already here, but are not set to really take off until 1980-81.

Digital ICs are set to have a big impact on hobby activities such as radio control modelling and model railroading in the next five years. A complete low-cost 4-channel radio control coder/transmitter IC, and a matching receiver/decoder IC, is due to be announced at the end of this year. Hornby are also due to release their microprocessor-based model railway control system this year. Lots of other goodies are in the pipeline.

## **REVAMP OP-AMP**

In the linear IC field, a brand new type of op-amp is due to be announced within the next couple of months, and



could be quite revolutionary. Power ICs will be used increasingly in the output stages of high-power Hi-Fi amplifiers, following new advances in IC technology. Electronic delay lines, based on charge-coupled device (CCD) technology, will achieve vastly increased capacities, and will fall substantially in relative costs, in the next few years.

That, then, is an educated estimate of what is going to happen on our hobby scene over the next five years. If I'm right, we're all in for an interesting time. If I'm wrong, I'll apologise in 1984.

## THE LM380 2-WATT AUDIO AMPLIFIER

If you saw last month's Baby Alarm project you'll have noticed that it was designed around the LM380 integrated circuit. The LM380 is one of those highly popular and useful ICs that every self-respecting electronics enthusiast should get to know about. It is an easy-to-use general-purpose audio power amplifier that can deliver 2 watts into an 8 ohm load with a typical distortion of only 0.2%, and can be used with any single-ended supply voltages in the range 8 V to 22 V. The device has an internally fixed voltage gain of 50 (34 dB), a power bandwidth of 100 kHz, and an output that is well protected with short circuit limiting and thermal shut-down circuitry.

For the benefit of voyeurs, figure 1 shows what the LM380 looks like with its clothes off. Q1 to Q4 form a PNP differential amplifier that has its input signals DC referenced to the ground line via R4 and R5, thus enabling input transducers to be directly connected between the ground and input lines if required. The output of the differential amplifier is coupled directly to the base of common emitter amplifier Q12, which uses Q11 as a constant current (high impedance) collector

load, and the collector signal of Q12 is fed to the output terminals of the IC via the Q7-Q8-Q9 quasi-complementary emitter follower set of output transistors. The output currents of Q7 and Q8 are rated at 1.3 A peak.

The output stages of the IC are provided with biasing, plus a good degree of thermal and overload protection, via D1-D2-R6 and R7. Resistors R1 and R2 automatically set the output of the amplifier at a quiescent value of approximately half supply-line voltage, to enable the IC to provide the maximum possible output power with minimal distortion, and R2 and R3 provide the IC with its internally fixed voltage gain of 34 dB

## HOW TO USE THE LM380

Figure 2 shows the outline and pin connections of the LM380, which is housed in a standard 14-pin dual-in-line plastic package. The package contains a copper lead frame that acts as a heat sink and is internally connected to the three centre pins on either side of the IC (pins 3, 4, 5, 10, 11, and 12). This frame enables the device to support 1.5W at 25°C ambient. The device dissipation can be increased to 3.7W at 25°C ambient by soldering the six heat sink pins into a PCB with 6 square inches (37.5 square cm) of standard copper foil.

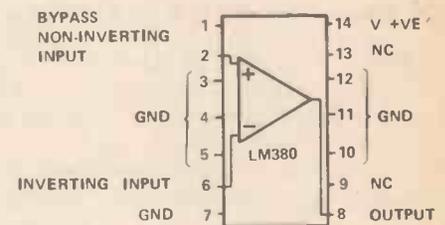


Fig. 2. Outline and pin connections of the standard 14 pin Dual-in-line (DIL) version of the LM380.

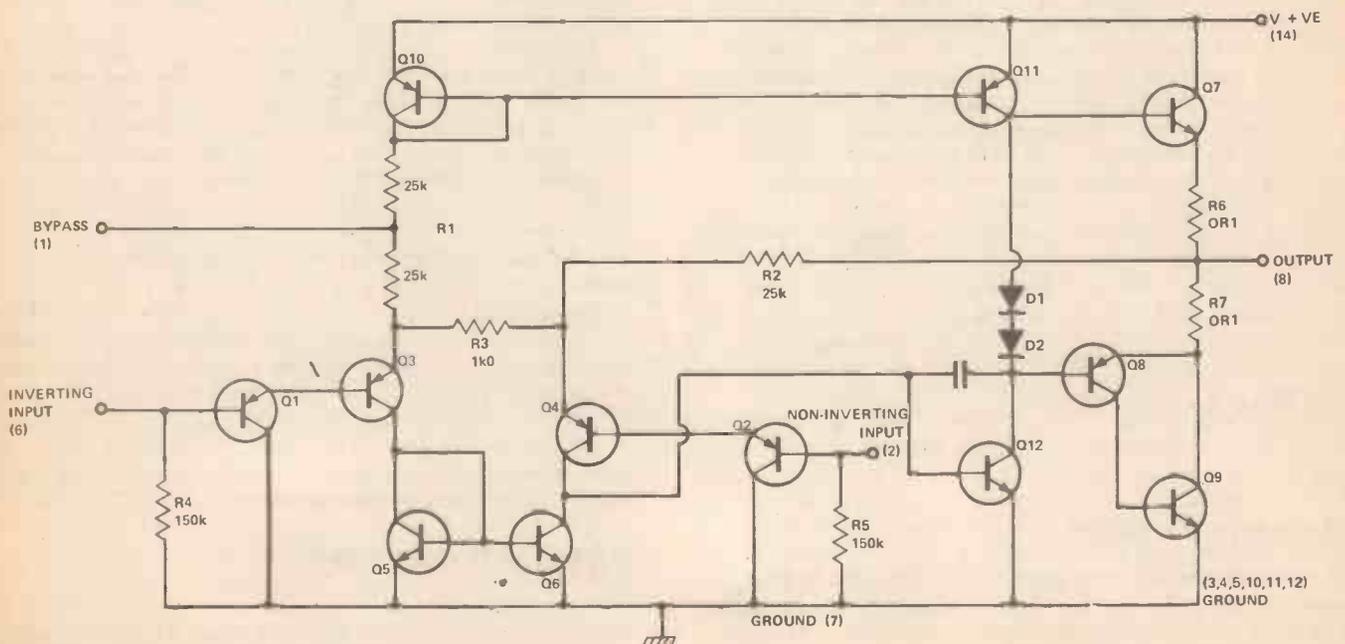


Fig. 1. The internal circuitry of the LM380 IC.

The LM380 is a very easy device to use. Input signals can be direct coupled to either the inverting (pin 6) or non-inverting (pin 2) input terminals, which have input impedances of about 150k. An unused input terminal can either be left floating, or can be shorted directly to ground, or can be tied to ground via a resistance. The output speaker load should be connected between the pin 8 output terminal and ground (pin 7) via a large-value electrolytic capacitor in most applications.

The LM380 can be used with any single-ended supply voltages in the range 8 to 22 volts. In all cases, the supply must be decoupled via a 47uF or larger capacitor located close to the IC, and a 100n ceramic capacitor must be wired as near as possible between pin 14 and the ground terminal of the IC as a precaution against parasitic oscillations. When the IC is used to drive speakers or other inductive loads, a Zobel network (comprising a 2R7 resistor and a 100n capacitor in series) must be wired between the output (pin 8) and ground terminals to protect the IC against high frequency oscillations. If the power supply lines to the IC have high ripple, a 10u or greater capacitor must be wired between the BYPASS (pin 1) and ground terminals to prevent the ripple reaching the speaker. The IC gives greater than 37 dB of ripple rejection at 50 Hz when fitted with this 10u bypass capacitor.

## LM380 APPLICATIONS

The best way to get to know any IC is to put it on your workbench and experiment with it. Figures 3 to 10 show a variety of ways of using the LM380 in audio amplifier applications. Most readers should have little difficulty in wiring these circuits up (on Veroboard or microdeck, etc) straight from the diagrams.

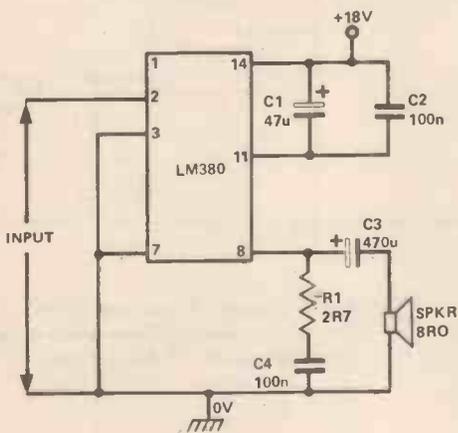


Fig. 3. A simple Non-Inverting 2 watt audio amplifier.

Fig 3 shows how to use the LM380 as a very simple non-inverting 2 W amplifier. The input signal is direct coupled between ground and the pin 2 non-inverting input terminal of the IC, which has an input impedance of about 150k. C1 and C2 are the supply decoupling and anti-parasitic capacitors respectively, and R1 and C4 form the Zobel network across the output of the IC.

Fig 4 shows how the IC can be used in the inverting mode by simply connecting the input signal directly to the pin 6 inverting input terminal and leaving the unused pin 2, non-inverting terminal floating. This diagram also shows how a potential divider volume control (RV1) can be added to the circuit, and how to improve supply-line ripple rejection by wiring C5 between by pass pin 1 and ground.

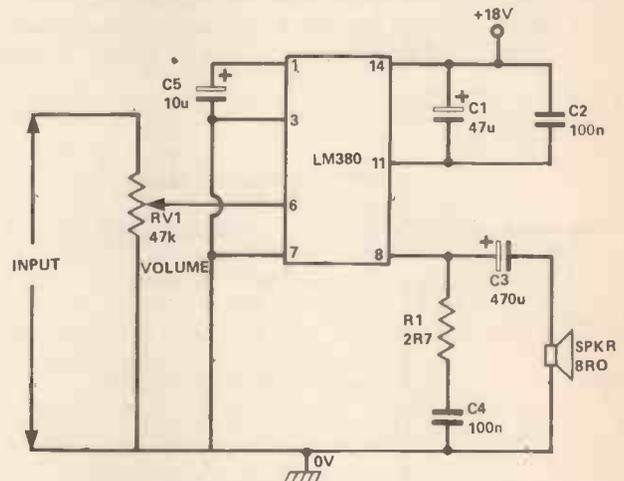


Fig. 4. A the LM380 connected as an inverting 2-watt audio amplifier with volume control and ripple rejection.

Figure 5 shows one way of using the LM380 as a simple non-inverting 2-watt phono amplifier that can be used with any ceramic or crystal pick-up cartridge. Here, RV1 and R2 act as a simple volume control, and C6 and RV2 act as a tone control that gives variable high-frequency roll-off. R2 is wired in series between the pick-up and the slider of RV1 to give the circuit a reasonably high input impedance. A minor disadvantage of the Fig 5 circuit is that, because of the presence of R2, signal attenuation occurs between the pick-up and the input pin of the LM380 at all settings of RV1.

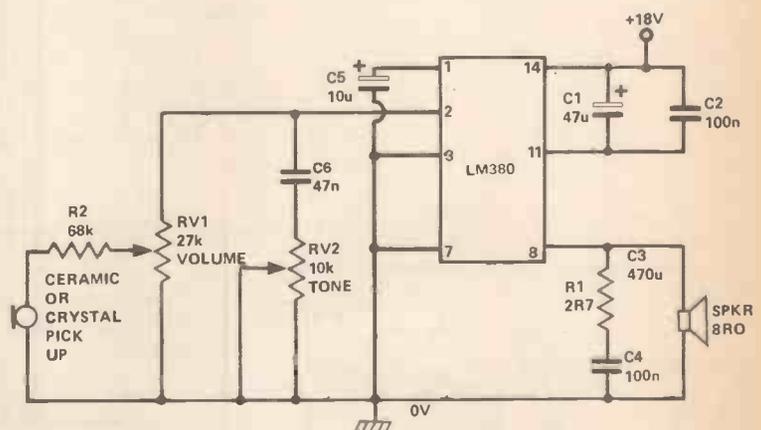


Fig. 5. A simple 2-watt phono amplifier.

Figure 6 shows an alternative, and possibly better, system of volume control that can be used with the LM380. Here, the input signal is fed directly to the pin-2 terminal of the IC's differential input amplifier, and is fed to the pin-6 input terminal via high value variable

resistor RV1. When RV1 is set to zero resistance identical signals are fed to both of the input terminals of the IC, so the amplifier has zero gain and the IC gives zero output: the circuit exhibits an input impedance of about 75k under this condition. When RV1 is set to maximum value, a large signal is applied to pin 2 and a negligible signal is fed to pin 6, so the amplifier has a high gain and the IC gives a large output; the circuit exhibits an input impedance of about 150k under this condition.

The volume control system described above is known as a 'common mode' system, since it relies on the

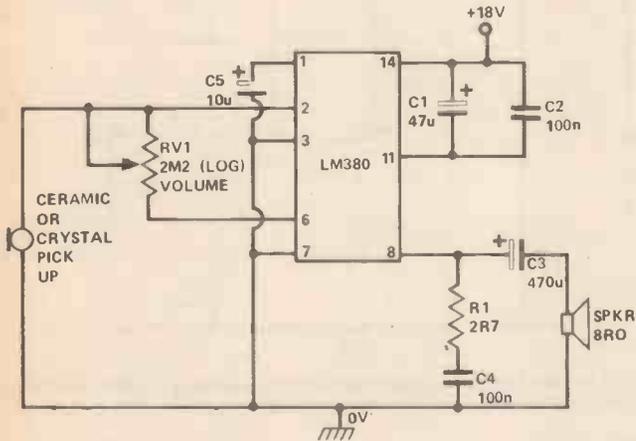


Fig. 6. A 2-watt audio amplifier with 'common mode' volume control.

differential action of the amplifier. It's major advantage is that it provides the circuit with a reasonably high input impedance. Figure 7 shows how a common mode variable tone control can be combined with the common

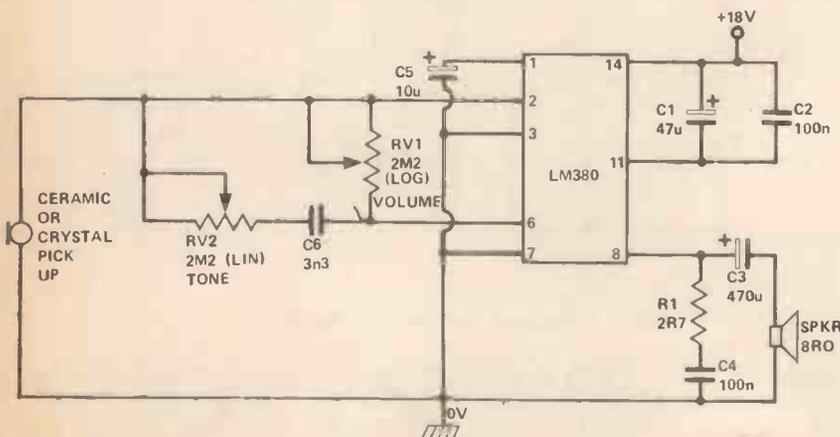


Fig. 7. A practical 2-watt phono amplifier with 'common mode' volume and tone controls.

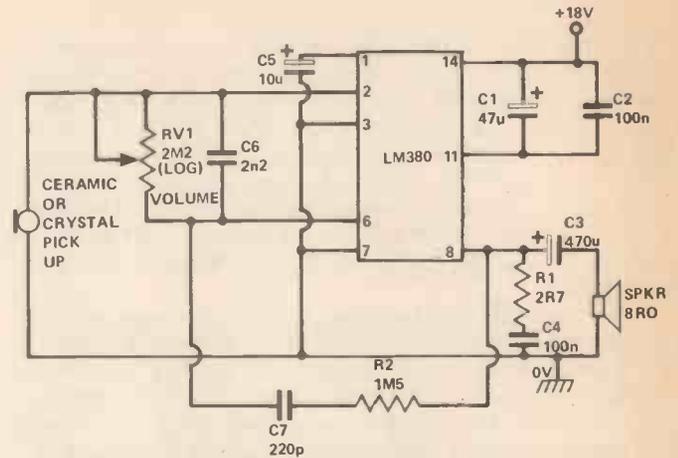


Fig. 8. A phono amplifier with RIAA equalisation.

mode volume control. Alternatively, figure 8 shows how a variable tone control can be dispensed with and replaced with a fixed RIAA equalisation network. Both of the above circuits make excellent low-cost phono amplifiers. They can be used in stereo systems by simply using an identical amplifier, but with ganged controls, in each channel.

The LM380 can be used in a wide variety of audio amplifier applications. Figure 9 shows how it can be used in conjunction with a field-effect transistor (FET) to make a high-input-impedance (10 megohms); 2-watt general-purpose or 'bench' amplifier. Q1 is the FET, and


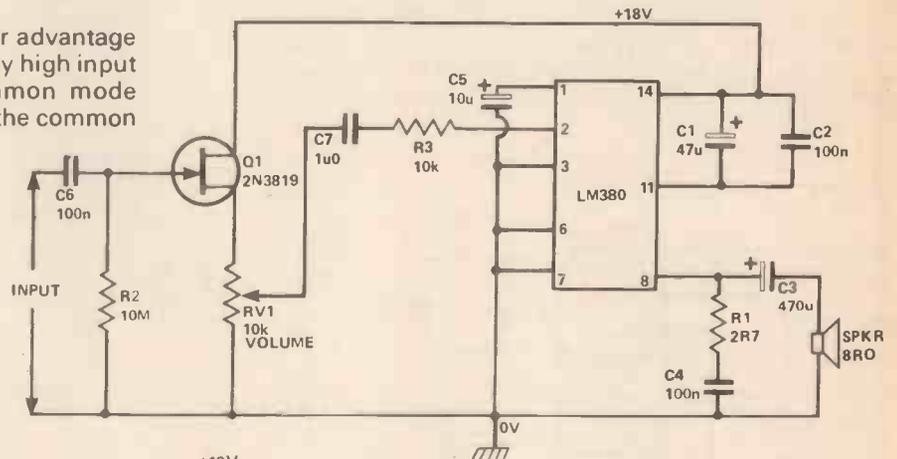


Fig 9. Above: A general purpose 2-watt audio amplifier with an input impedance of 10 Meg ohms.

**Fig. 10. A 4-watt amplifier using two LM380 ICs in a bridge configuration. The circuit uses common mode volume control.**

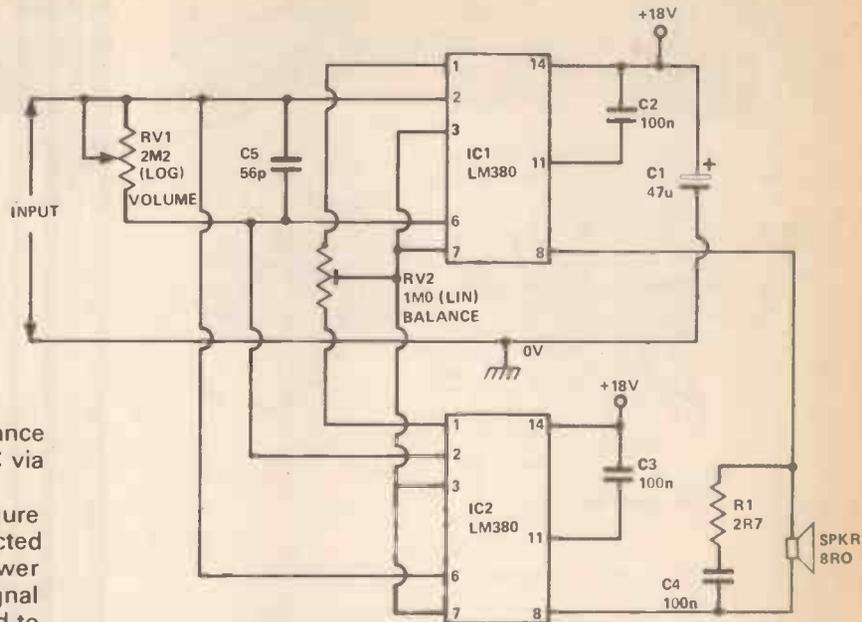

is wired as a source follower, with its input impedance determined by R2, and has its output fed to the IC via volume control RV1 and limiting resistor R3.

Finally, to complete this month's 'Chit Chat', figure 10 shows how a pair of LM380s can be interconnected in a bridge configuration to give an output power roughly double that of a single IC. Here, the input signal is applied to the non-inverting terminal of one IC and to the inverting terminal of the other, thus producing anti-phase output signals from the two ICs and dividing the output power dissipation equally between the two devices. The Fig 10 circuit is shown with a common mode volume control, but the basic bridge configuration can in fact be used with any type of volume control.

Note in the Fig 10 circuit that the speaker is wired directly between the output pins of the two ICs and that BALANCE control RV2 must be pre-set so that negligible

current flows through the speaker under quiescent conditions. To make this adjustment, temporarily connect a DC current meter in series with the positive supply rail of the circuit (both ICs use the same supply rail) and then adjust RV2 for a minimum current reading with zero input signal applied. Once RV2 has been pre-set, it should require no further adjustment throughout the life of the amplifier. **HE**

## Short Circuit

### GAS AND SMOKE DETECTOR

This circuit is primarily intended for use as a gas detector for a boat or caravan, and is designed to run from a 12 V battery supply. It could of course be run from a mains power supply unit if necessary. The quiescent current consumption of the unit is about 130 mA, rising to approximately double this figure when the alarm sounds. Apart from propane, butane, methane, etc., the unit will respond to most smoke, combustible vapours and even carbon monoxide. It will detect these at well below the minimum concentrations required to produce an explosion.

At the heart of the unit is a special sensor device which has a semiconductor section which is heated by a 5 V heating element. The latter is powered from the 12 V supply via a 5 V regulator device, IC1. The semiconductor sensor oxidizes when heated by the element, and exhibits a high resistance between two electrodes which are attached to it. Inflammable gasses, vapours, etc. have a deoxidizing (reducing) effect on the semiconductor material, causing its resistance to fall to only a fraction of its previous level.



The alarm signal is generated by a simple oscillator which uses Q1 as a common emitter amplifier directly driving a common source power FET output stage based on Q2 and having the loudspeaker as its drain load. The positive feedback to produce oscillation (at about 1 kHz) is provided by C3 and R3. However, normally the high resistance of the gas sensor will result in the voltage at RV1 slider being too low to bias on Q1 via R1, and the oscillator will not function. When gas is detected and the gas sensor's resistance falls, the vol-

tage at RV1 slider increases and the oscillator is biased into operation.

For optimum sensitivity RV1 is adjusted for virtually the highest resistance that does not cause the oscillator to switch on (when the sensor is in its high resistance state). If necessary the gas sensor device can be remotely located from the other circuitry. Note that for good stability C1 and C2 should be mounted physically close to IC1.


The type 812 gas sensor has a continuous operating life of

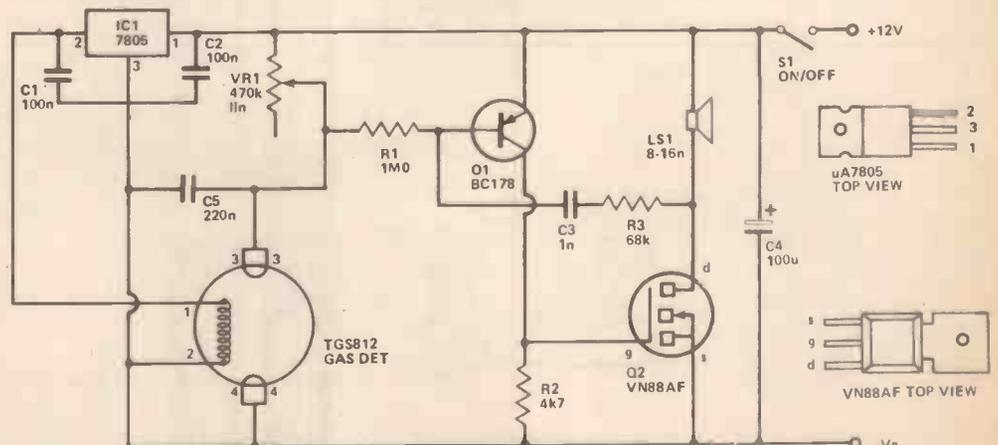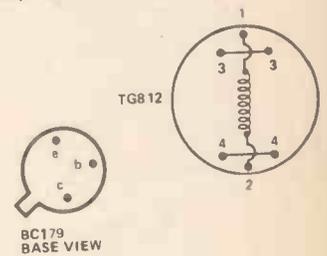approximately two years, after which it will become rather slow in operation and will need to be replaced.



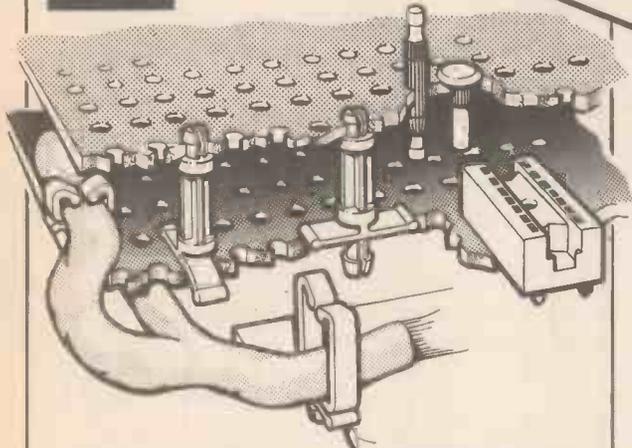**vero**

OUR RANGE OF PRODUCTS ARE NOW INDIVIDUALLY AND ATTRACTIVELY PACKAGED



Our new catalogue lists circuit board accessories for all your projects – DIP sockets, pins, stand-offs, cable clips, hand tools. And we've got circuit boards, module systems, cases and boxes – everything you need to give your equipment the quality you demand. Send 25p to cover postage and packing, and the catalogue's yours.

**VERO ELECTRONICS LTD. RETAIL DEPT.**

Industrial Estate, Chandlers Ford, Hants. SO5 3ZR  
Telephone Chandlers Ford (04215) 2956

**SINCLAIR PRODUCTS.** New 10MHz scope poa. PFM200 £49.48, case £3.19, adaptor £3.19, connector kit £10.58. Microvision TV UK model £89.45, mains adaptor £6.73, POM35 £27.95, mains adaptor £3.19, case £3.19, DM350 £67.46, DM450 £95.95, DM235 £49.95, rechargeable batts. £7.50, mains adaptor £3.70, case £8.45. Enterprise prog. calculator with accessories £2.95.  
**COMPUTER GAMES.** Star chess £59.45, Chess Champion 6 £88.50, Chess Challenger 7 £91, Chess Challenger 10 £152.50, Voice Challenger pos. Checker Challenger 2 £44, Checker Challenger 4 £93, Atari video computer £138, cartridges £13.45.  
**COMPONENTS.** 1N4148 1.4p, 1N4002 2.9p, 741 17p, bc182b, bc183b, bc184b, bc212b, bc213b, bc214c 5p. Resistors 1/4W 5% E12 10R 1p 10M 1p, 0.8p for 50+ of one value, 16V electrolytics 5/1/2/5/10/22µf 5p, 100µf 6p, 1000µf 10p, 1µF FeCl £1.13, Dialo pen 79p, 40 sq ms pcb 80p. Polystyrene capacitors E12 63V 10 to 1000pF 3p, 1n2 to 10n 4p. Ceramic capacitors 50V E6 22pF to 47n 2p, Zeners 400mV £24 2v7 to 33v 7p. Preset pots submin 0.1W 100 to 4M7 8p.  
**TV GAMES.** AY-3-8500 + kit £8.95, Rifle kit £4.95, AY-3-860 10+ kit £15.70, Stunt cycle chip + kit £15.70, AY-3-8603 chip £8.90.  
**TRANSFORMERS.** 6-0.6V 100ma 74p, 1½ £2.35, 6.3V 1½ £1.89, 9-0.9V 75ma 74p, 1a £2, 2a £2.60, 12-0.12V 100ma 90p, 1a £2.49.  
**IC AUDIO AMPS,** with pcb, JC12 8W £1.95, JC20 10W £2.95.

**BATTERY ELIMINATORS.** 3-way type 8/7½/9v 300 ma £2.95, 100ma radio type with press-studs 9V £3.35, 9V+9V £4.50, Car converter 12v input, output 4½/6/7½/9v 800 ma £2.50.  
**BATTERY ELIMINATOR KITS.** 100ma radio types with press-studs 4½v £1.40, 6v £1.40, 9v £1.40, 4½v+4½v £1.80, 6+6v £1.80, 9+9v £1.80, Stabilised 8-way types 3/4W/6/7½/9/12/15/18v 100ma £2.80, 1 Amp £5.40, Stabilised power kits 2-18v 100ma £2.80, 2-30v 1A £6.95, 2-30v 2A £10.95, 12v car converter 6/7½/9v 1A £1.35.

**T-DEC AND CSC BREADBOARDS,** s-dec £3.80, t-dec £4.02, u-deca £4.40, u-decb £6.73, 16 dii adaptor £2.17, exp4b £2.48, exp300 £6.21, exp350 £3.40, exp325 £1.73.

**BI-PAK AUDIO MODULES.** s450 £23.51, AL60 £4.86, PA100 £16.95, spm80 £4.47, bmt80 £5.95, stereo 30 £20.12, AL30 £3.95, PA12 £7.60, PS12 £1.39, MA60 £35.44.

**SWANLEY ELECTRONICS**

Dept. HE, 32 Goldsæl Road, Swanley, Kent  
Post 30p extra. Prices include VAT. Budget add 7% to all prices. Lists 20p post free.

THIS IS A PROJECT FOR ALL THE PEOPLE WHO THINK THAT THE H.E. PROJECTS AREN'T COMPLICATED ENOUGH!!



**SPECIALS FROM MODMAGS**

Mark your envelopes Specials, and send them to: Specials, Modmags Ltd, 145 Charing Cross Road, London, WC2H 0EE.

**ETI CIRCUITS**

Books 1 & 2.

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal – hardly surprising when the circuits cost under 1p each!

£1.50 + 25p P&P each.



**ELECTRONICS TOMORROW**

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone – none of which have appeared in ETI – and a look at the future of MPUs, audio, calculators and video. How can you not read it?

75p + 25p P&P.

**TOP PROJECTS**

Book 1 + 2: £2.50 + 25p P&P.

Master mixer, 100W guitar amp., low power laser, printmeter, transistor tester, mixer preamp., logic probe, Ni-Cad charger, loudhailer, 'scope calibrator, electronic ignition, car theft alarm, turn indicator cancellor, brake light warning, LM3800 circuits, temperature alarm, aerial matcher, UHF-TV preamp., metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

Book 3: SOLD OUT! Book 4: £1.00 + 25p P&P. Book 5: £1.00 + 25p P&P. Book 6: £1.00 + 25p P&P.



**TOP PROJECTS**

Book 7: £1.25 + 25p P&P.

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch filter, light dimmer, IB metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.



**ELECTRONICS – IT'S EASY**

Books 2 & 3.

Our successful beginners' series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail) and together form an excellent starting point for anyone interested in learning the art of electronics.

£1.20 + 25p P&P each.



**INTO ELECTRONICS PLUS**

The complete series of Ian Sinclair's series Into Electronics Plus a selection of some of the most popular and informative articles from HE. Everything from Home Computing to making your own PCBs. £1 + 25p P&P.

## CLEVER DICK



**We start our new feature Clever Dick with a look at some of the more frequently asked questions that arrive each day. Clever Dick will attempt to answer some of them, if you've got a problem why not drop us a line and we'll see what we can do.**

MOST OF THE LETTERS we receive on Hobby Electronics are technical enquiries, providing they're accompanied by a SAE they receive a fairly speedy reply, unfortunately not all of them do have a SAE, so they usually get 'filed'. The purpose of this occasional feature is to answer some of the more frequently asked questions and if space and resources permit, matters not directly connected with HE.

Our first letter comes from Sandra Witter, (good to see the ladies taking an interest), in the past we've had one or two letters from Sandra (haven't we Sandra) as this one concerns the Digi-Bell (June HE)

*Dear Dick*

*I've built the 'Digi-Bell' and have come to the conclusion it would be better described as the 'Relucta-Warble'.*

*The 'thing has been subjected to several 'pullings apart' and 'puttings back together'. I've replaced both ICs and changed a dodgy (wrong value) capacitor, re-soldered every joint on the board, checked it with a multi-meter, even my dad has had it on a 'scope, he reckons that the first stage is working all the time, so when we connect up the battery it keeps sounding. HELP.*

*Sandra Witter  
Coventry.*

Well, we must own up, we did omit a link on the PCB but we did admit to it in the June issue. The second point with the Digi-Bell was the high current consumption experienced by some people, this is easily rectified by connecting all the unused inputs of ICI to 0V. Hope that answers all the questions on the Digi-Bell.

Another common question concerns the availability of PCBs and components, particularly, do we supply them? This letter from A. Atefi is fairly typical.

*Dear Sir,*

*I am enquiring about the GSR Monitor in your June edition. Would you please tell me if it is possible for me to order the PCB and components from you. I would be grateful if you could mention the price so that I can send you a cheque.*

*A. Atefi  
Birmingham*

The answer, sadly is no. It would be very difficult for us to do so. Luckily companies like Tamtronik Ltd (see ad. in this issue) are only too happy to supply all the components, including PCBs and hardware for all our projects.

We've had quite a few enquiries lately on our sound effects projects, the White Noise Effects Generator and the ADSR Envelope Generator. (Yes the PCB for the White Noise Generator was back to front, sorry again). They were developed as a matched pair but there's no reason whatsoever why other inputs cannot be connected to the ADSR, eg guitar organ etc.

Our third main topic this month concerns addresses, people seem to think that we are all-seeing, all-knowing, we must admit that would be nice but we're not. Its no good whatsoever asking us to recommend a decent lawnmower, people do too. If you stick to electronic matters then maybe we can help. M N H Christmas is in luck, he writes:

*Dear Sir,*

*I have been fascinated by computers for many years. Last week I purchased your book Into Electronics Plus to read the feature Home Computers. I find that the cheaper ones, ie £200-£300 are within my price range. I would be grateful if you could supply me with any addresses from where I could obtain further information.*

*Mr N H Christmas  
Middlesex*

Nice easy one this, in London we are particularly fortunate, we have 'Eurocalc' and the 'Byte Shop' both in Tottenham Court Road, along with several other well known shops also in the same road. They can be found displaying some small micro systems, Nascom etc. All the addresses you may need can be found in our sister magazine-Computing Today (plug plug). Look out for the Comp Computer Components Ltd ad there are several low to medium budget machines in their range. They can be found at: 14 Station Road, New Barnet, Herts.

Probably the most frequently asked question is, "Can you supply me with a circuit for . . . . . ?". Most of the time we can find something suitable in our back issues, don't forget ETI goes back seven years. Of course we have to make a small charge for photocopying. The trouble arises when we're asked to design circuits for people. Unfortunately our project team is employed full time in designing our own projects, they just do not have the time or resources to undertake any private work. Sorry to those of you that want everything from multi-bank mixers to a circuit diagram for a BBC colour TV camera. Keep reading HE, you just never know.

Ref.	ELECTRONIC BOOKS	Price
126	Boys Book of Crystal Sets	25p
138	How to Make Aerials for TV (Band 1-2-3)	25p
160	Coil Design and Construction Manual	75p
196	AF — RF Reactance — Frequency Chart for Constructors	15p
200	Handbook of Practical Electronic Musical Novelties	50p
201	Practical Transistorised Novelties for Hi-Fi Enthusiasts	35p
202	Handbook of Integrated Circuits (IC's) Equivalents and Substitutes	100p
203	IC's and Transistor Gadgets Construction Handbook	60p
205	First Book of Hi-Fi Loudspeaker Enclosures	75p
206	Practical Transistor Circuits for Modern Test Equipment	60p
207	Practical Electronic Science Projects	75p
208	Practical Stereo and Quadraphony Handbook	75p
210	The Complete Car Radio Manual	100p
211	First Book of Diode Characteristics Equivalents and Substitutes	95p
213	Electronic Circuits for Model Railways (Reprinting)	100p
214	Audio Enthusiasts Handbook	85p
215	Shortwave Circuits and Gear for Experimenters and Radio Hams	85p
216	Electronic Gadgets and Games	100p
217	Solid State Power Supply Handbook	85p
218	Build Your Own Electronic Experimenters Laboratory	85p
219	Solid State Novelty Projects	85p
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p
221	28 Tested Transistor Projects	95p
222	Solid State Short Wave Receivers for Beginners	95p
223	50 Projects Using IC CA3130	95p
224	50 CMOS IC Projects	95p
225	A Practical Introduction to Digital IC's	95p
226	How to Build Advanced Short Wave Receivers	120p
227	Beginners Guide to Building Electronic Projects	125p
228	Essential Theory for the Electronics Hobbyist	125p
RCC	Resistor Colour Code Disc Calculator	10p
BP1	First Book of Transistor Equivalents and Substitutes	50p
BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p
BP6	Engineers and Machinists Reference Tables	50p
BP7	Radio and Electronic Colour Codes and Data Chart (Reprinting)	25p
BP11	Practical Transistor Novelty Circuits	40p
BP14	Second Book of Transistor Equivalents and Substitutes	110p
BP22	79 Electronic Novelty Circuits	75p
BP23	First Book of Practical Electronic Projects	75p
BP24	52 Projects Using IC741	95p
BP25	How to Build Your Own Electronic and Quartz Controlled Watches & Clocks	85p
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p
BP28	Resistor Selection Handbook (International Edition)	60p
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p
BP30	Two Transistor Electronic Projects	85p
BP31	Practical Electrical Re-Wiring and Repairs	85p
BP32	How to Build Your Own Metal and Treasure Locators	100p
BP33	Electronic Calculator Users Handbook	95p
BP34	Practical Repair and Renovation of Colour TVs (Reprinting)	95p
BP35	Handbook of IC Audio Preamplifier and Power Amplifier Construction (Reprinting)	95p
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	75p
BP37	50 Projects Using Relays, SCR's and TRIACS	110p
BP38	Fun and Games with your Electronic Calculator	75p
BP39	50 (FET) Field Effect Transistor Projects	125p
BP40	Digital IC Equivalents and Pin Connections	250p
BP41	Linear IC Equivalents and Pin Connections	275p
BP42	50 Simple L.E.D. Circuits	75p
BP43	How to Make Walkie-Talkies	125p
BP44	IC555 Projects	145p
BP45	Projects in Opto-Electronics	125p
BP46	Radio Circuits Using IC's	135p
BP47	Mobile Discotheque Handbook	135p
BP48	Electronic Projects for Beginners	135p
BP49	Popular Electronic Projects	145p
BP50	IC LM3900 Projects	135p
BP51	Electronic Music and Creative Tape Recording	125p
BP52	Long Distance Television Reception (TV-DX) For The Enthusiast	145p
BP53	Practical Electronic Calculations and Formulae	225p
BP54	Your Electronic Calculator and Your Money	135p
BP55	Radio Stations Guide	145p
TI	TTL Pin Configuration Guide	175p

Please add 25p p&p

**TECHNOMATIC LTD**  
**17 BURNLEY ROAD, LONDON NW10 1ED**  
 (2 minutes from Dollis Hill Tube Station) (Ample parking space)  
 Telephone: 01-452 1500. Telex: 922800

7400	14p
7404	18p
7408	20p
7410	16p
7413	32p
7420	18p
7430	17p
7447	65p
7473	36p
7490	35p
7493	35p
74121	30p
CA3080	77p
CA3140	75p
ICL8038	370p
LM380	80p
LM741	24p
NE555	24p
TBA800	100p
ZN414	100p

DIL SOCKETS	
8pin	12p
14pin	13p
16pin	14p

Large range of components available. Send SAE

ANTEX SOLDERING IRONS	
C-15W	390p
CX-17W	410p
CCN-15W	410p

COPPERCLAD	
X-25W	410p
Spare bit	50p
Stand	170p

VEROBOARDS	
0.1 Copperclad	
2½x5	62p
3½x2½	53p
3½x3½	62p
3½x5	69p
3½x17	240p

POCKET MULTIMETERS	
KRT100	580p
(1000 ohms/V)	
LT22	1360p
(20kohms/V)	
Test Lead Kit	
(Prods, Croc clips, bananas, Spades)	
10 Test leads with Croc Clip at each end	110p

EXPERIMENTOR BREADBOARDS	
(No soldering, suitable for DIL ICs)	
For 1 IC Circuit up to 22pin	
EXP325	180p
For up to 3x14pin DIL IC	
EXP350	360p
For up to 5x14pin DIL ICs	
EXP300	641p
IC Test Chips	
14pin	285p
18pin	297p
Logic Probe	1800p

# Back Numbers

Shown here is a selection of past issues with their major features and projects. All are available (at the moment) for just 60 pence each, including post and packing. Send your order to:

**Hobby Electronics**  
**Backnumbers Dept.**  
**145 Charing Cross Road**  
**London, WC 2**



## NOVEMBER 78

Projects: Stereo Amplifier, Digital Clock, Wah-Wah Pedal, Bedside Radio.  
 Features: The Edison Effect, Robots, Hi-F Specs, Kit Review, Transducers Metal Locators etc.



## DECEMBER 78

Projects: Metronome, Photon Phone, Audio Mixer, Electronic Dice.  
 Features: Deep Space Communications, Understanding Bias, Lasers, Photocells, Calculators, The Tesla Controversy etc.



## JANUARY 79

Projects: Graphic Equaliser, Touch Switch, Vari-Wiper, Flash Trigger.  
 Features: BASIC programming, Viewdata, Starship Daedalus, Pinball Machines etc.



## FEBRUARY 79

Projects: Short Wave Radio, Sine/Square Generator, Scratch/Rumble Filter, Car Alarm Project.  
 Features: Video Tape Recorders, Radioactivity, CA 3130 Circuits, Computer Glossary etc.



## MARCH 79

Projects: Light Chaser, Tone Controller, Photographic Timer, Cassanova's Candle.  
 Features: TV Signals, Test Gear, SW Aerials, Interfering Waves, Communications Satellites, etc.



## APRIL 79

Projects: Model Train Controller, Cistern Alarm, Transistor Tester.  
 Features: The Telephone System, TV Aerials, Electronics in Warfare, Catalogue Survey etc.



## MAY 79

Projects: Power Supply, Parking Meter Timer, Digibell, White Noise Effects.  
 Features: Feedback, Electronic Music, AB Circuits, 555 Circuits, Aerial Tuners, Varicap Diodes etc.



## JUNE 79

Projects: GSR Monitor, Envelope Generator, Drill Speed Controller.  
 Features: Citizens Banned, Display Techniques, Moving Coil Meter, Electronics in Music Pt 2, etc.



## JULY 79

Projects: Shark, Baby Alarm, Points Controller, Linear Scale Ohmmeter.  
 Features: Cassette Decks and Tapes, Binary Numbers, Fixed Resistors, Short Circuits Special, etc.

# Constant Volume Amplifier

The uses of a Constant Volume Amplifier may at first seem somewhat limited, but any audio enthusiasts will immediately recognise it as a compressor, invaluable in high quality tape recording etc.

ANY ENTHUSIASTIC USER of a tape recorder, cassette or reel to reel, will appreciate that the recording of rapidly fluctuating sound levels such as the human voice or an orchestra for example, can often pose certain difficulties. If the level control is set on the recorder during a loud passage then when a quiet passage comes along, it can be almost inaudible. Likewise if the level is set on a quiet passage then the louder ones will be distorted.

What is needed is a piece of equipment which can strengthen the weak signals and lower the louder. Such a device is the HE Constant Volume Amplifier which attempts to give a relatively unchanging output level for a multitude of inputs.

The key word here, of course, is 'relatively' — we don't really want a *constant* volume level because we might not be able to tell if the orchestra was playing a

crescendo or a quiet passage. The ideal device would simply reduce the volume range. In other words it compresses the volume, in fact equipment of this sort is

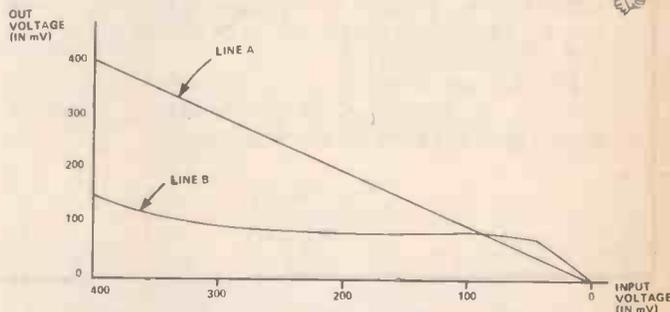


Figure 1. Graph of output vs. input voltage.



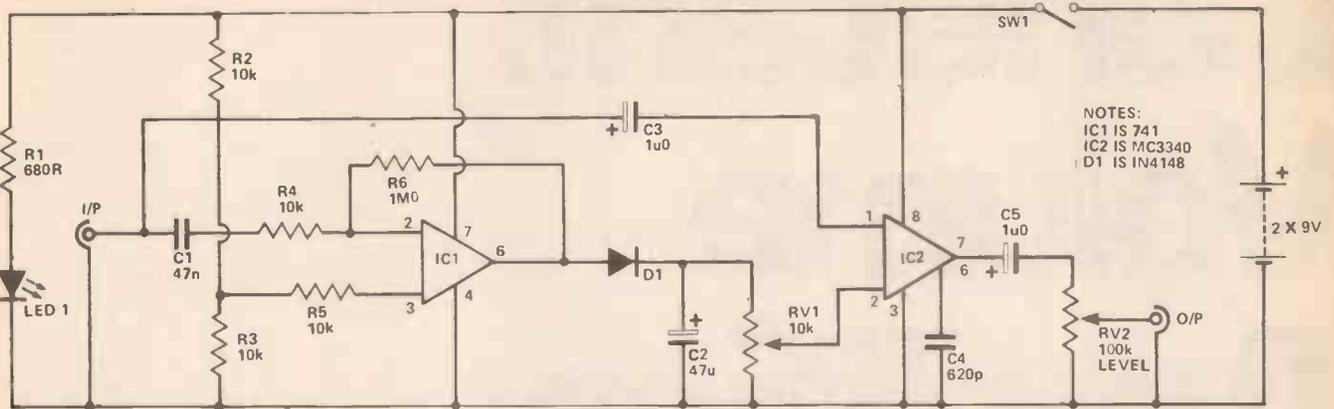


Figure 2. Circuit diagram of the HE Constant Volume Amplifier.

## How It Works

IC 2 is a voltage controlled amplifier. That is, an amplifier whose gain is directly proportional to a DC control voltage present at pin 2. Following the circuit diagram, the signal can be seen to pass through coupling capacitor C3, to pin 1 of IC2, the input. The output from pin 7 is coupled via C5 to the preset RV2 which is set to give the required output amplitude. As the voltage on pin 2 alters, so does the gain of the amplifier. At 3.5 V the gain is at maximum, but at 6 V the output of the amp is virtually zero. At control voltages in between these two limits the o/p amplitude is between maximum and zero. (See figure 4.)

The circuit around IC 1 derives the control voltage. IC 1 is used as an inverting amplifier whose gain is given by the formula

$$\frac{\text{R feedback}}{\text{R input}}$$

according to figure 5. These two resistors correspond to R6 and R4 in the final circuit, giving a gain of  $1\text{M}/10\text{K} = 100$ .

D1 half wave rectifies this amplified AC waveform which is then stored as a DC voltage on C4. The voltage should vary between about 8-14 volts, depending on the amplitude of the input signal. RV1 is used as a variable potential divider to drop this voltage to 3.5 to 6 V DC – used now for the necessary control voltage to pin 2 of IC2.

A compressor should ideally have a fast attack time, in the order of just a few milliseconds, so that any sharp loud note is acted upon quickly, but a relatively slow decay time of say 100 milliseconds – otherwise the effect described previously of a constant CVA would occur. These two times are inherent in the circuit as capacitor C4 charges quickly through D1, when a loud sound is present at the input, but it discharges at a much slower rate through RV1.

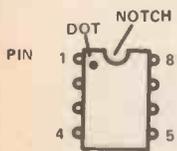


Figure 3. Showing an integrated circuit, viewed from above (with pins pointing away).

locating notch or dot is on the top of the chip (see figure 3).

Some ICs have a dot used as a locator, some a notch and some have both. The printed circuit board has a dot


quite often referred to by people in the know as a compressor.

The graph in figure 1 displays the characteristics of the HE Constant Volume Amplifier showing output voltage vs input voltage. Line A is the graph obtained if the CVA is not used i.e. the output voltage is the same as that of the input (because there is nothing there to alter the input). However, with the CVA in use (line B) the output varies a greatly reduced amount as the input changes.

These results were obtained using the prototype constant volume amplifier and show how effective it functions as an audio compressor.
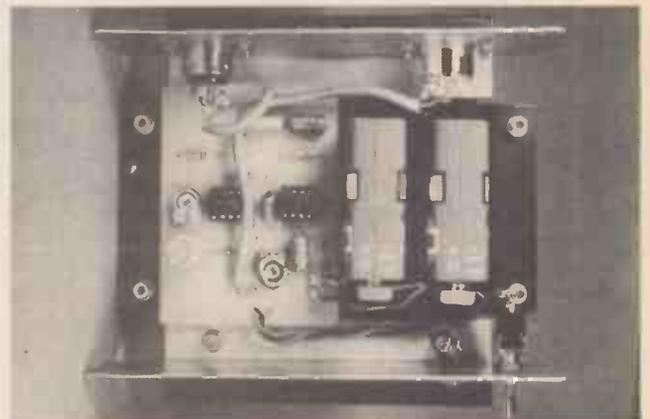
### CONSTRUCTION

Make sure that IC1 and 2 are inserted correctly – note that pin 1 of both ICs is the top left hand pin when the



Note the position of the two nine volt batteries, make sure the metal cases of the batteries don't short against the switch or socket connections.

# Constant Volume Amplifier

etched on it which corresponds to the correct placing of pin 1 for both ICs (see PCB pattern).

Looking at the inside photograph of the case shows the layout of wiring up, which is quite easy. Remember to use screened cable for input and output leads. The case ideally should be metal and earthed, to screen the circuit against mains hum. The earthing can take place at either input or output socket by connecting a short lead from tag 2 of the socket to the tag which is connected to the metal shield. The signal should come from tag 1 of the input socket and go to tag 3 of the output socket. (See figure 4).

The rest of the components should present no difficulties, the circuit being fairly straightforward.

## SETTING UP

The procedure for setting up requires the use of the CVA in situ. Feed an input to the device and the output to an amplifier with the amplifier volume turned down. Set RV2 to mid-position and RV1 fully anti-clockwise then switch everything on. Turn the amplifier volume up till you hear the signal. Now turn RV1 clockwise until distinct distortion of the signal occurs, then turn it back until the distortion just disappears. Finally, adjust RV2 to give the required volume level.

HE

## Buylines

All components bar IC2 should be obtainable at any component stockist as they are common types. If IC2 can't be found locally then any of the larger mail order firms might be able to help. It is also available as an RS Components IC stock number 306-803.

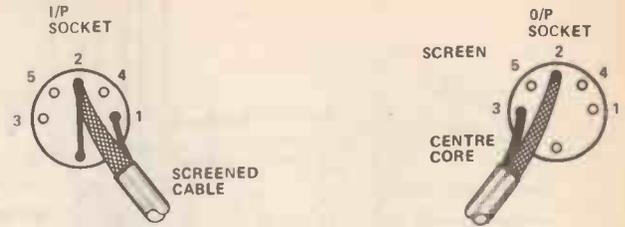


Figure 4. The connections to the input and output sockets.

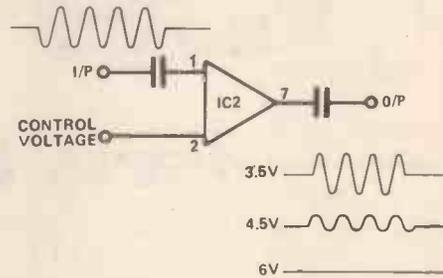


Figure 5. Showing the outputs obtained with various control voltages.



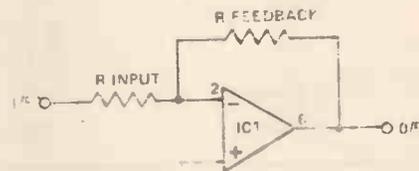


Figure 6. A straightforward operational amplifier circuit.

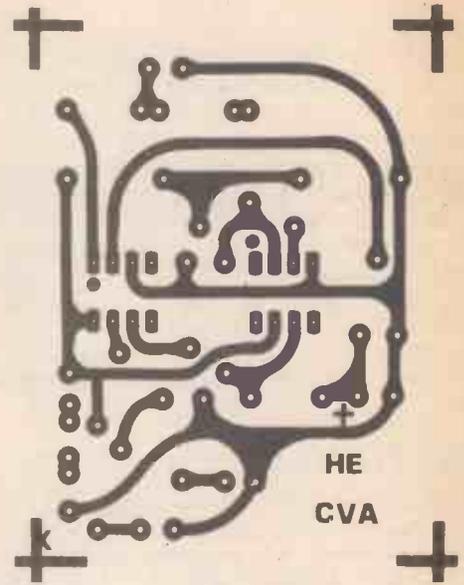

The on-off switch and LED keep the front panel neat and uncluttered.

# Constant Volume Amplifier

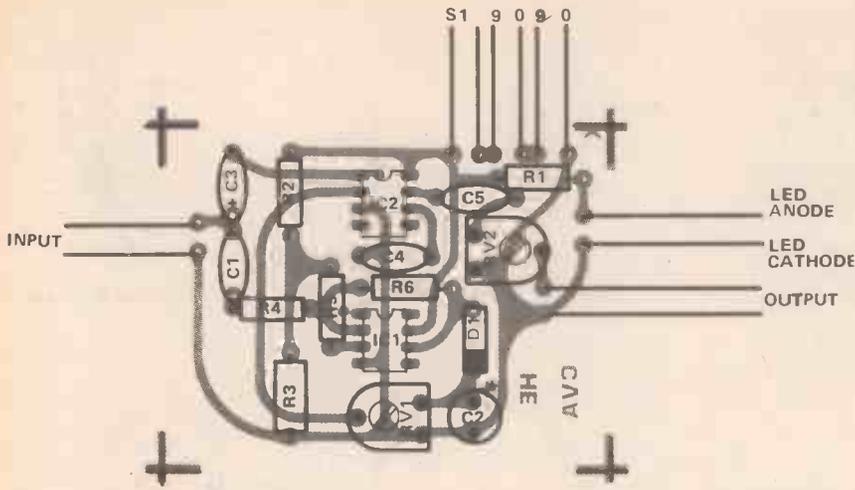

## Parts List

### RESISTORS (All 1/4W, 5%)

R1 680R  
R2,3,4,5 10K  
R6 1M

### POTENTIOMETERS

RV1 10K Preset  
RV2 100K Preset

### CAPACITORS

C1 47nF Polyester  
C2 47uF Elect.

C3,5 1uF Elect  
C4 620pF Polystyrene

### SEMICONDUCTORS



IC1 741  
IC2 MC3340  
D1 1N4148  
LED 1 TIL 220 0.1" LED

### MISCELLANEOUS

Switch 2 x PP3 batteries and clips  
Case to suit 2 x 3-pin Din Sockets

Approximate cost £9.00

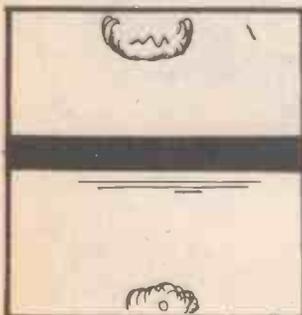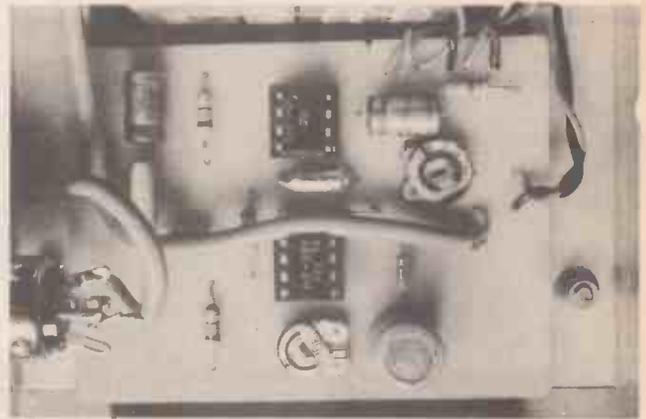Top left. Overlay diagram for the Constant Volume Amplifier.  
Above. PCB foil pattern.  
Below Right. Inside the cabinet, note the use of screened cable for signal wires.



THERE IS A  
FAULT IN THIS  
CARTOON  
PLEASE DO NOT ADJUST  
YOUR MAGAZINE

## 24 TUNE DOOR CHIMES

### DOOR TUNES £16.44 + VAT.

Waddington's Videomaster announce a doorbell that doesn't go Brrringg, Ding-Dong or Bzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES

### PROGRAMMABLE £29.50 + VAT. COLOUR CARTRIDGE T.V. GAME.

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Targit. The console comes complete with two removable joystick player controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



#### EXTRA CARTRIDGES:

- ROAD RACE** - £8.87 + VAT.  
Grand Prix motor racing with gear changes, crash noises
- SUPER WIPEOUT** - £9.17 + VAT.  
10 different games of blasting obstacles off the screen.
- STUNT RIDER** - £12.16 + VAT.  
Motorcycle speed trials, jumping obstacles, leaping various rows of up to 24 buses etc.
- NON-PROGRAMMABLE TV GAMES**
- 6 Game** - COLOURSCORE II - £13.50 + VAT.
- 10 Game** COLOUR SPORTSWORLD £22.50 + VAT.

## CHESS COMPUTERS

### STAR CHESS - £55.09 + VAT. PLAY CHESS AGAINST YOUR PARTNER.

Using your own TV to display the board and pieces Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess. It adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



### CHESS CHALLENGER 7 - £85.65 + VAT. PLAY CHESS AGAINST THE COMPUTER.

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Castling, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.



ELECTRONIC CHESS BOARD TUTOR £19.75 inc. VAT.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.

#### OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:


- CHESS CHAMPION - 6 LEVELS** £82.87 + VAT.
- CHESS CHALLENGER - 10 LEVELS** - £143.06 + VAT.
- BORIS - MULTI-LEVEL TALKING DISPLAY** £165.28 + VAT.

## DRAUGHTS COMPUTERS

### CHECKER CHALLENGER 2 LEVELS £43.98 + VAT. 4 LEVELS £80.09 + VAT.

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.
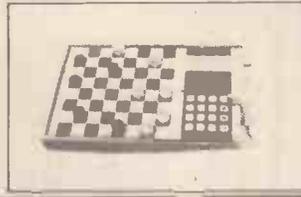
#### PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER






## FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon-Sat 10am-1pm Wed.  
To order by telephone please quote your name, address and Access/Barclaycard number.  
Postage and Packing FREE.

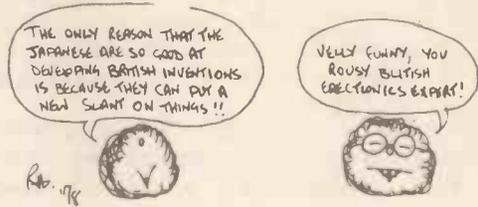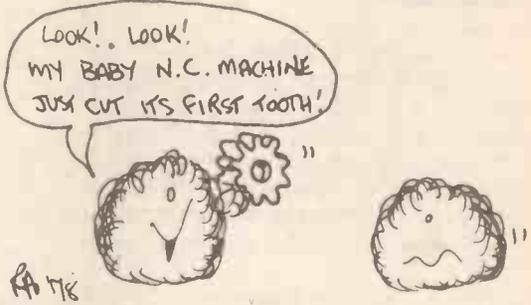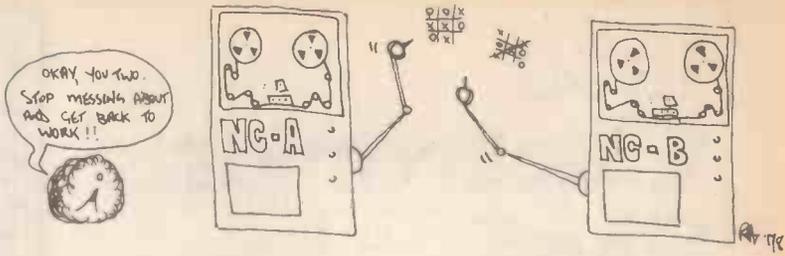**AJD DIRECT SUPPLIES LIMITED, Dept. HE & 102 Bellegrave Road, Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)**



# TEE SHIRTS

We won't guarantee HE Tee-Shirts will make your soldering any better, we won't even claim it will make your projects work first time. What we will say is that it will protect your body from harmful Ultra-Violet radiation from the sun, embarrassing Tomato Ketchup stains on your hairy chest and overweight wallets (if bought as directed in sufficient quantity).

Yes folks, for just £2 all inclusive you can be the first kid on your block to own a brand new HE Tee-Shirt. If you buy more than one your torso need never be left unprotected whilst your other one is in the wash.



Send your cheque, PO or anything negotiable to:  
**HE TEE SHIRTS, 145 Charing Cross Rd, London WC2 4OE.**

# Into Electronics Plus

*Ian Sinclair has finished his tale, So 'Into Electronics Plus' is now on sale, The cream of Hobby, plus Mr Sinclair, We modestly believe an unbeatable pair, The pound you send will be well spent, (That's apart from paying our rent), You'll get 'Capacitors', 'Computers', and 'PCBs', Not at all bad for just one hundred pees.*

The demon HE poet strikes again, he sat up half the night writing this one. (Don't know why he bothered). Seriously though folks Ian Sinclair's series proved such an astounding success we decided to bring it out as a book. Not only that but we've added over twenty more pages of informative features from 'Audio Transducers', and how to make your own PCB's. That's 100 pages for a Pound, a penny a page.


The series was primarily aimed at people taking O/A level courses in electronics but has proved to be just as popular with people starting out in our fascinating hobby.

For your copy just send £1.25 (that includes Post, Packing) to:-

**'INTO ELECTRONICS PLUS'  
HOBBY ELECTRONICS,  
145 CHARING CROSS ROAD  
LONDON, WC2H 0EE.**

From the publishers of  
**Hobby  
Electronics**

**£1**

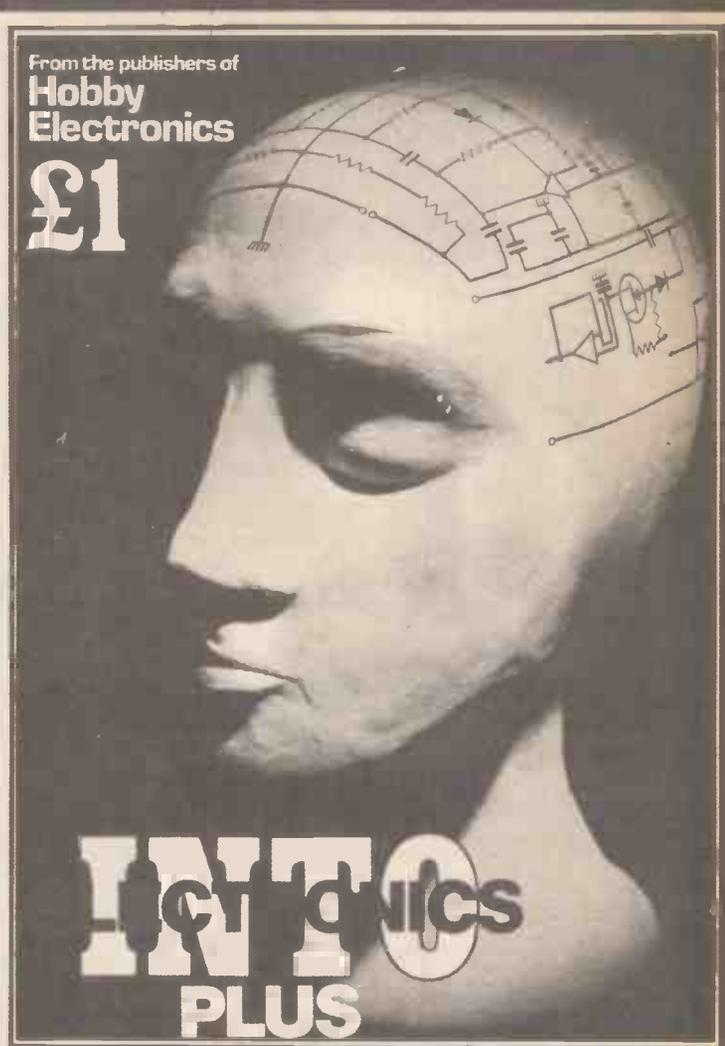

## Short Circuit

### FLASH SLAVE UNIT


The problem of harsh and unnatural shadows that occurs when taking flash photographs using a single flashgun can be overcome by the use of a second flashgun. A flash slave unit is then very useful as it enables the additional flashgun to be triggered by the light from the main gun, thus reducing the amount of interconnecting leads required. The flash slave circuit shown here is extremely sensitive and when used indoors it always seems to trigger reliably regardless of where the main flashgun and the slave unit are positioned. If used out of doors there is likely to be little reflected light to help trigger the slave unit and it may be necessary to have the photocell aimed towards the main flashgun in order to obtain reliable operation (this is common to all flash slave units). The circuit has excellent immunity to saturation by strong ambient lighting. The photocell is a BPX 25 or similar

silicon photo-transistor. The collector to emitter resistance of this component varies over a wide range from darkness to high lighting levels, with the latter giving the lowest resistance. The photo-

cell is connected as part of a potential divider across the supply rails and when the light from the flash unit is received, a negative output pulse is produced by this circuit. This pulse is coupled by

way of C1 to the input of a common emitter amplifier based on Q2. C1 has been given a low value so that it only efficiently couples the fast pulse caused by the flashgun, and slow signals such as those caused by shadows crossing the photocell are blocked.

R2 and R3 forward bias Q2, but by an amount which is too small to produce a significant collector current. However, the negative input from the photocell causes Q2 to conduct heavily and feed a trigger current to SCR 1 gate via current limit resistor R4. SCR 1 then briefly switches on and fires the flash unit. The circuit operates extremely rapidly and there is no significant delay between the firing of the two flashguns. The unit has a current consumption of about 20 to 50uA in normal ambient lighting conditions, falling to less than a microamp if it is stored in darkness and it is therefore quite feasible to omit the on/off switch SW1.

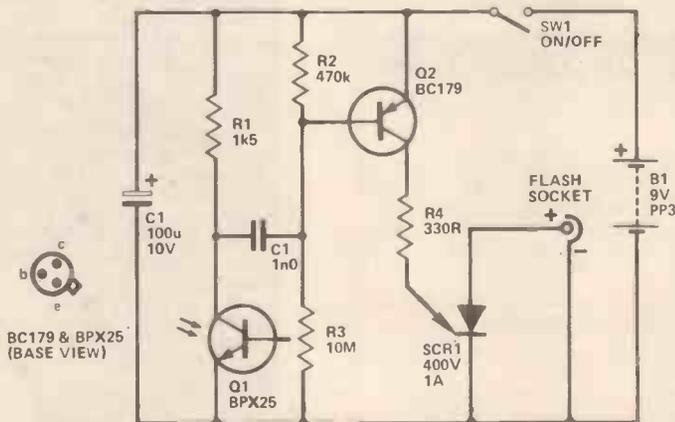



First there was ETI, catering for the middle-range to advanced electronics enthusiast. Then there was HE which was aimed at the newcomer to the field.

Now there is Computing Today from the

same stable. CT covers the area of small-business and amateur computing and deals with both software and hardware.

CT's third issue (cover date of May) is out now — 50p at your newsagent.

## Books from the HE Book Service

### 28 Tested Transistor Project

Richard Torrens. The projects can be split down into simple building blocks which can be recombined for ideas of your own.

### Electronic Projects for Beginners

F. G. Rayer. Divided into 'No Soldering Projects,' Radio and Audio Frequency, Power Supplies and Miscellaneous.

### Solid State Short Wave Receivers for Beginners

R. A. Penfold. Several modern circuits which give a high level of performance even though only a few inexpensive components are used.

### Popular Electronic Projects

R. A. Penfold. A collection of the most popular types of circuits and projects using modern, inexpensive and freely available components.

### Digital IC Equivalents and Pin Connections

Adrian Michaels. Covers most popular types and gives details of packaging, families, functions, country of origin and manufacturer.

### How to Build your own Metal and Treasure Locators

F. G. Rayer. Gives complete circuit and practical details for a number of simple metal locators using the BFO principle.

### Linear IC Equivalents and Pin Connections

Adrian Michaels. Gives most essential data for popular devices.

### Projects in Opto Electronics

R. A. Penfold. Covers projects using LED's, Infra-red transmitters and detectors, modulated light transmission and also photographic projects.

### 52 Projects using IC 741

Rudi and Uwe Redmet. Translated from an enormously successful German book with copious notes, data and circuitry.

### 50 FET (Field Effect Transistor) Project

F. G. Rayer. Contains something of interest for every class of enthusiast. Short Wave Listener, Radio Amateur, Experimenter or audio devotee.

### How to Build Advanced Short Wave Receivers

R. A. Penfold. Full constructional details are given for a number of receivers plus circuits for add-ons such as Q-Multiplier, S-meter etc.

### Essential Theory for the Electronics Hobbyist

G. T. Rubaroe gives the hobbyist a background knowledge tailored to meet his specific needs.

### Beginners Guide to Building Electronic Projects

G. T. Rubaroe. Covers component identification, tools, soldering, constructional methods and examples of simple projects are given.

### 50 Projects using IC CA3130

R. A. Penfold. Describes audio projects, RF project, Test Equipment, Household and miscellaneous circuits.

### IC 555 Project

E. A. Parr. Circuits are given for the car, model railways, alarms and noise makers. Also covers the related devices 556, 558 and 559.

### 50 Projects using Relays, SCR's and TRIAC's

F. G. Rayer. Gives tried and tested circuits for a whole variety of projects using these devices.

Note that all prices include postage and packing. Please make cheques etc. payable to Hobby Electronics Book Service (in Sterling only please) and send to:

**Hobby Electronics Book Service**  
P.O Box 79  
Maidenhead, Berks.

# Into Linear ICs

By Ian Sinclair


## Part 2

*Part two already. This month Ian Sinclair digresses for a moment to take a look at the gentle art of PCB construction, soldering and layout before we get down to the real business of linear ICs.*

IF YOU'VE JUST BECOME accustomed to laying out transistor circuits, then your first look at a circuit diagram for an IC project is a bit off-putting, mainly because so many connections have to be made to one small unit. Don't worry, it's not only easier than it looks, it's even easier than laying out transistor circuits, thanks to the use of DIL packages.

### SPREADING THE BREAD

Any IC circuit can, of course, be soldered onto a specially prepared printed-circuit board (PCB), but for trying out circuits of all sorts, nothing beats a solderless breadboard for speed and ease of handling. The breadboard which is best suited for these circuits is the Euroboard, which has contacts arranged in groups of five, with 25 groups in a column, and four columns. Fig. 1 shows the arrangement — the groups are spaced out 2.5 mm apart on one column — so that the standard IC pin spacing of 2.5 mm can be accepted. The columns are arranged either 7.5 mm apart (A and B; C and D) or 15 mm apart

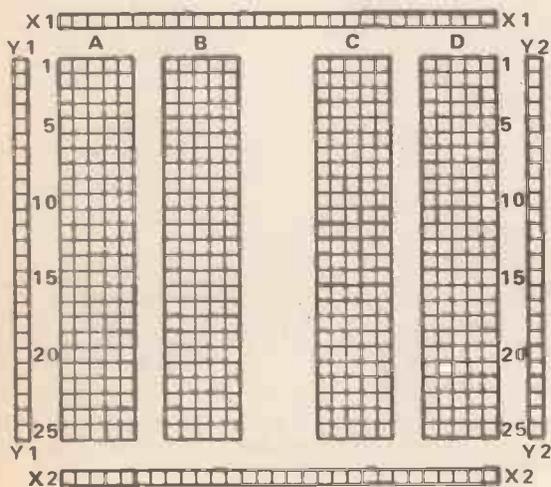

**Fig. 1.** The Eurobreadboard layout. Columns AB or CD are used for small ICs, the larger spacings between B and C can be used for the bigger ICs with 15 mm between lines.


(B and C) so that any of the normal IC's right up to the monster microprocessor can be fitted in. The size of the board is enough to permit assembling any of the circuits we shall use, but the price is as low as several much smaller and less suitable competitors.

The columns are lettered A, B, C, D, and the lines are numbered 1 to 25, so that we can indicate where a connection is made by using a letter and a number. For example A4 means any of the five contacts on the 4th line in column A. Contact is made by inserting a lead into a hole on the correct line, so that if one lead of a resistor is to be connected to A4, the wire end is simply pushed into one of the holes on this line — any one will do.

Now when we plug an IC into this breadboard, each of its pins will be on a different line, one side in one column and the other side in another column. You wouldn't, of course, ever plug an IC into the board so that two pins were on the same line. Each pin will therefore be on a line of its own which can be identified by a letter (for the column) and a number (for the row).

### INSTANT CIRCUIT

This makes construction incredibly easy. Mark on the circuit diagram the letter and number for each pin of the IC. Because most IC's need only a few other components, very few other lines on the board need to be used, and we can use any spare convenient lines. Each circuit diagram (using IC's) in this series will show the Eurobreadboard layout in this way, so that you don't even have to be able to read the circuit diagram particu-

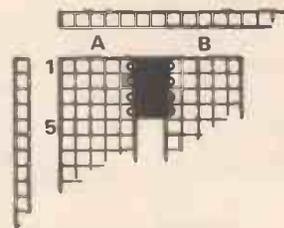

**Fig. 2.** How the small 8-pin IC fits on to the Eurobreadboard. This is the position which will be used in all the circuits in this series using these ICs.

larly well to be able to construct each circuit. At the same time, you'll gain valuable experience in laying out a circuit.

The Eurobreadboard also has four long lines of contacts arranged round the edges, and intended for power supplies.

We'll use these as the power supply points in all the circuits, using X1, for positive supply, X2 for negative (if needed) and Y1 for earth or zero voltage. As always, labelling X1 on a diagram means any contact hole on X1, usually the nearest one. Where a wire link has to be taken from one group of contacts to another, this is indicated on the diagrams by a thickened line.

## SOLDERING IC's

A solderless breadboard is first-rate for testing-out circuits, particularly any circuits which have been modified a bit, but it's not the method we'd use for a permanent circuit — that's a soldering job. Now you've probably used a soldering iron already, but if your experience of soldering is only on transistor circuits, or possibly not at all, then perhaps a little bit of advice might be useful.

One essential point is to have a soldering iron which is suitable for working on ICs. Because of the 2.5 mm spacing between IC pins, an iron with a large bit is definitely out. Most modern soldering irons have replaceable bits, so that it's possible to attach a very fine bit for soldering IC's and then change to a larger one for bigger stuff. A suitable power is around 15-25 watts. Much less than 15, and you find that the solder never readily melts properly, because the copper of the printed circuit board conducts too much heat away. Much more than 25W, and you find that you are overheating the tiny strips on the board, causing them to pull away. Make sure, too, that your iron can be earthed with an earth wire correctly fitted to a three-pin plug. The circuits we're dealing with in this series *don't* need an earthed iron, but if you ever use the type of digital IC's called CMOS, or have to use FET's then you'll need an earthed iron — so why not start now?

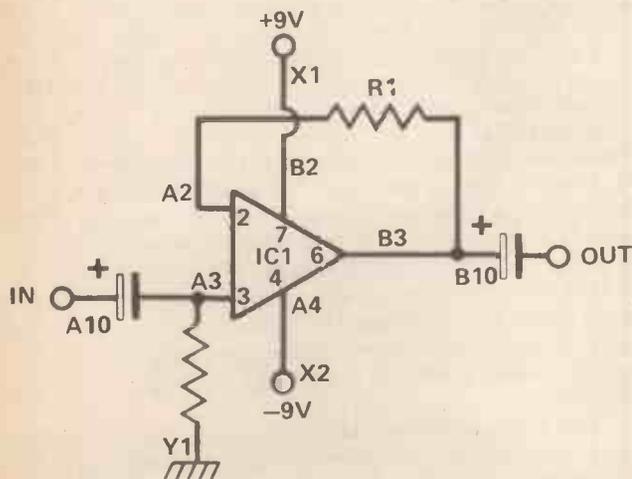


Fig. 3. Instant circuit! When the Eurobreadboard numbers are put on to the circuit, the few extra components that are needed go between these lines and earth or supply lines, or can be accommodated on spare lines.

The technique for soldering an IC goes something like this. First of all, you place the IC on the board, with its pins in the correct places — and then you *check*. Check that it's the correct IC for that part of the board (unless there's only one!), and that it's the correct type of IC — they look pretty much alike. Then locate pin 1 on the IC and check that it's placed in the hole that is intended for pin 1. On a small board, this is easy enough, but checking takes longer if you have a large board which takes twenty or more IC's. Use the small bit on the iron, and fine gauge resin-cored solder — Multicore's size 10 (0.7 mm diameter) is ideal.

## SOLDERING ON

Having checked, solder pin 1 onto its pad. Turn the board over so that it's resting on the IC, hold the tip of the bit of the soldering iron against the track pad just where the IC pin comes through, then touch this point with the end of the solder. When a small drop of solder flows on take the solder away, move the tip of the iron around the pin of the IC so that the solder forms a neat blob around the pin and the pad. At this point take the iron away and blow on the joint to cool it.

Most IC's are fairly heat-resistant, but if you have any doubts about how long it'll take to solder a pin into place, then protect the IC with a heat sink. This doesn't have to be anything elaborate, just a paper clamp of the Bulldog variety clipped onto the IC and touching the pins just where they are bent over at the sides of the casing (Fig. 4). Having soldered in pin 1, check again that you have the right IC, in the right place and the right way up. This may sound unnecessary, but at this point the IC can be removed very easily by heating the solder and pulling the IC out — after you've soldered in a few more pins, removal is a major operation! Having soldered in pin 1, now solder in the pin which is opposite, pin 5 on an 8-pin chip, pin 8 on a 14-pin chip, or pin 9 on a 16-pin chip. Check again — it's your last chance! If it still looks fine, solder in the rest of the pins, let them cool down, and then check that each pin is properly soldered, with no break in the solder around each pin and no little bridges of solder between one track and the next.

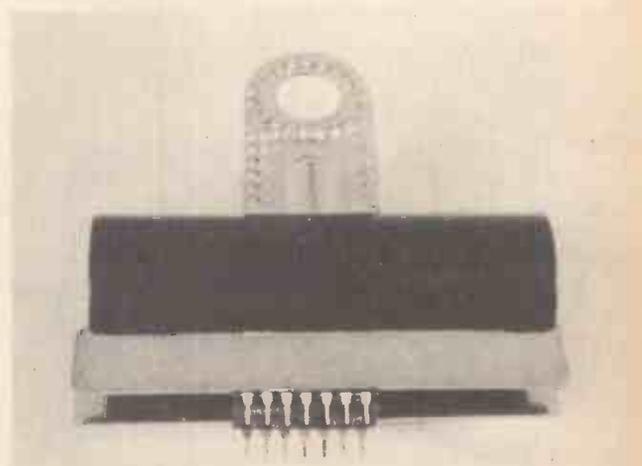


Fig. 4. Using an office paper clamp as a heat-sink. These clamps come in various sizes which are suitable for all the common linear ICs.

## DE METHOD OF DESOLDERING

Even with all the care which you've taken (and you did, didn't you?) inevitably some day you will find that there's one IC in the wrong place, the wrong way up, or of the wrong type, and you have to remove it. If the IC has failed, and you're absolutely sure that it's failed — removal is easy. You simply cut through each pin at the body of the IC, using side-cutters, then take the pins out one by one, holding the remains of the pin in tweezers, and pulling the pin out as you melt the solder with the iron. If, however, there's nothing wrong with the IC and you want to use it again or in another part of the board, then gentler methods are called for.

Various desoldering tools can be bought, but unless you're going to do an awful lot of desoldering (it's cheaper to get the darn thing in the right place first time, folks), the cheapest and simplest method is to make use of copper braid, variously called solderwick or solder-braid. The idea behind this is that solder, like other molten metals, has a large amount of surface tension which pulls it into narrow tubes and small gaps. Copper braid is a mass of small gaps, so that molten solder runs into braid the way oil soaks into lampwick. To use desoldering braid, lay a clean piece of braid over the joint which you want to desolder. It helps if there's a faint coating of flux on the braid — I keep an old tin of Fluxite (which I bought in 1949) handy. Then clean the solder from the bit of the iron by wiping it quickly with a damp cloth, and lay the hot bit on top of the braid so that the braid is sandwiched between the bit of the iron and the joint. Keep the iron in contact until you see the solder on the joint melt and run into the braid — then remove the iron and the braid together. You'll find that it helps to hold the braid with tweezers — it gets mighty hot during this operation. Don't leave the braid soldered to the joint!

This procedure should lap up all the solder from the joint, leaving only a very thin silvery film of solder. If it doesn't take all the solder first time (which means that you're putting too much solder on your joints), then cut off the piece of braid which is now stiff with solder, and try again with a fresh piece of braid. When all the solder has been removed from each pin of the IC, it should be possible to pull the IC away from the board without a struggle. With any reasonable luck, if you check each IC as you go, in the way we've described, you will never have to go through this procedure.



Fig. 5. Examples of Hobbyprints

## BOARD STIFF?

That covers the jobs of soldering and de-soldering, but what about the circuit-boards themselves? What you use as a printed-circuit board (PCB) very much depends on what sort of project you are building. You may, for example, be constructing a project for which a ready-made board is available, in which case your only problem (apart from paying for it and getting it delivered in one piece) is to make sure that each component is soldered in the right place.

You can often save yourself a lot of time and money by etching your own boards — provided that you can get the pattern marked onto the board. For a project from your favourite magazine, you can buy the HOBBYPRINT transfers of instant dry transfer, and every major project in HE has a HOBBYPRINT to match. The laminate board (plastic coated with copper) is cleaned by rubbing the copper surface with fine sandpaper, and finished off by wiping over, using a clean rag moistened with a drop of lighter fuel or white spirit to remove any traces of grease. Once the laminate is completely dry, you then lay the HOBBYPRINT over the copper, with the backing surface of the HOBBYPRINT uppermost. Rub over the back of the HOBBYPRINT with a soft pencil, B, 2B or softer preferably, and make sure that you don't rub so hard that you pierce the paper. Make sure that you have rubbed thoroughly over all the parts where there is printing to be transferred. Then peel the backing-sheet off carefully. If you have been a bit careless, and you've missed a piece of track, or jabbed the pencil-point through, or lifted a piece of track, then panic not, the repair kit which comes with each HOBBYPRINT will attend to it. When the pattern is completely transferred, cover the surface with a piece of stiff paper or cardboard, and cut the laminate to size — I find a fretsaw is the handiest method of doing this. The transfer material is acid-resistant, so that you can now etch away the copper which is not covered by the printed lines.

## COME AND SEE MY ETCHINGS

The etching material is ferric chloride (Iron (III) Chloride to you chemists). It's not very strongly acid, but don't splash it in your eyes (remedy: wash in plenty cold water, then in eyewash, and see a doctor just in case). It will also stain the fingers, so I always play safe and wear rubber gloves and goggles. Make up just what you need. I use a photographic developing tray which I bought from a junk-shop, and I measure out the solid ferric chloride into it, then pour on hot water and stir. When the solid has completely dissolved, put the board in, copper side up, and keep the solution hot from above by shining a desk lamp on to the copper from about six inches above the top — but don't take any risks, and make sure that the desk lamp is properly earthed in case it falls in. If you use a metal tray for etching, it can be kept warm on a hotplate, but I wouldn't be inclined to use the cooker for this job. Move the board around a bit, using tweezers, so that it's always in contact with fresh solution.

You will see the unwanted copper steadily etching away, and when it's all gone, lift out the board and rinse it in warm water. Now use fine sandpaper or Vim to remove the transfer material — you'll have to scrub fairly hard. Dry the board, and drill through each solder-pad so that your components can be mounted. You can, if you like, drill before you scrub off the print.

You'll need a small drill-bit for this job and something suitable to use it in — it's not really suitable for a carpenter's brace. The used ferric chloride solution can be kept in a labelled and well-stoppered bottle until the next time, though it's best made up fresh unless you are etching again in a week's time or so.

Etching is done in exactly the same way, no matter how the board is printed; the important part of the process is cleaning the copper before applying the pattern. Any trace of dirt or grease on the copper (and that includes fingerprints) can cause faulty etching. If you're determined to keep costs low, or if you're building a project for which there is no HOBBYPRINT, you can apply your own pattern. One way is to use readymade shapes of instant transfer, another is to use etch-resist put on with a felt-tip pen. Some of the best PCB's I've seen were done with a drafting pen filled with waterproof Indian-ink; but your draftsmanship has to be good. All of these methods are particularly useful if you have to design a circuit layout for yourself, and if you have stencils for the IC mounting-pads. For HE projects, though, HOBBYPRINTS win every time!

## STRIP-TEASE

There are still a few methods left if you don't want to get involved with etching and marking-out copper laminate. These methods involve the use of stripboards — PC boards which have been machined or etched so as to have parallel strips of copper set at 2.5 mm apart so as to suit the pins of ICs. The original Veroboard consists of long strips made in this pattern and also drilled at 2.5 mm intervals. Other patterns are now available, with short tracks (something like the groups of contacts on the Eurobread-board in arrangement). If you use the long strips, you will have to cut the tracks, as shown in Fig. 6, so that the IC pins do not short to each other.

Stripboards can be used for any IC circuit, providing that they use 2.5 mm pitch strips. The circuits are laid out on the stripboard exactly as you would lay out a circuit on the Eurobreadboard. Unfortunately, most stripboards are not numbered nor lettered (don't ask me why, it can't be for lack of being asked!), so that you will have to do this for yourself unless you can get hold of ready-numbered material. One way is to stick some masking-tape at the end of the strips and write the strip numbers on it. Another method is to make use of the

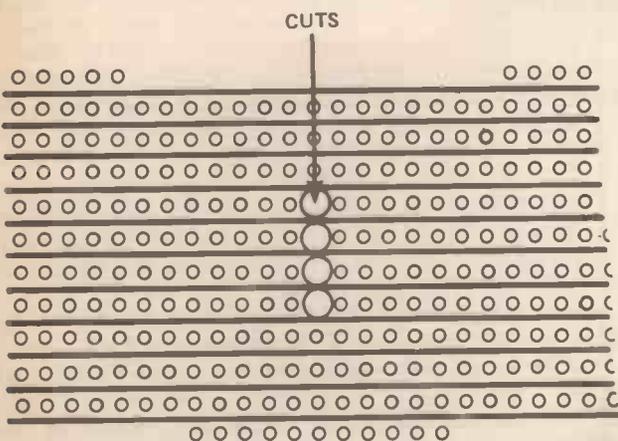


Fig. 6. Cutting 2.5 mm Veroboard to take an 8-pin IC.

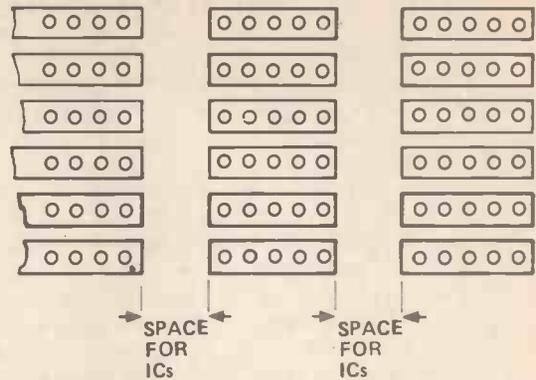


Fig. 7. The track pattern of DIL-board. Using this type of board saves on cutting.

white correcting fluid which is used by typists to cover mistakes (sold as Tippex fluid, Snopaque, etc.) and paint a stripe of this down one edge of the board. Let it dry for a minute (it's fast-drying) and then write the numbers in pen or pencil on it. Remember to number each side of the board, unless you are using single-sided board. Single-sided board is undrilled, so that the components are mounted on the same side as the copper tracks, with each leadout wire butted against the track and then soldered to the track. Circuit layout, circuit tracing, and troubleshooting are all much easier when this type of board is used, because you don't have to keep turning it over.

That's covered the possible constructional methods that you can use; but there's one important point to attend to before we start making linear IC circuits and getting them to work. It concerns power supplies — an important feature of all IC circuits.

## VOLTS WITHOUT FAULTS

The small-scale circuits that we're going to feature can all be battery operated, though a few of the later circuits will take rather a lot of current from the batteries. If you don't have a mains power pack, or if you have a mains power supply which doesn't suit linear ICs, then the use of batteries is an attractive proposition. All of the circuits have been designed to work from either single or twin 9 V batteries, such as the PP3 which seems to power so many small transistor radiqs. If you can spring a bit extra on the larger sizes, such as the PP6 or PP9, you'll find them better value for money, because their life is very much longer than that of the PP3's.

Some circuits specify dual supplies, meaning that

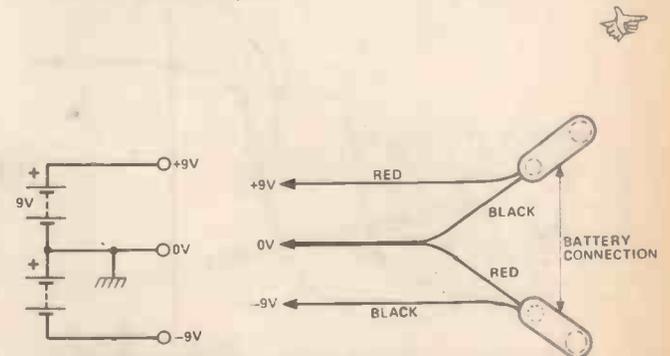


Fig. 8. Using two batteries for a power supply.

there is a positive and a negative supply with a common earth return line. This is particularly easy to arrange when you see batteries, connecting two batteries as shown in Fig 8. A deluxe arrangement consists of the two batteries held in a plastic box, with their connectors wired to a miniature three-pin socket. The leads to the Eurobreadboard can then plug into this socket, which fits the plug one way only. If you don't feel like going to this much trouble, you will have to make sure that you have the supply leads right way round each time — one way is to solder the battery connectors to the leads, which are then plugged into the breadboard. If you see flexible leads, solder the ends lightly, because solderless breadboards don't take kindly to having stranded wire thrust into them — not all of the strands come out again! Generally, there's less of a problem in getting the leads the right way round when only a single 9 V supply is used, and there are only two leads.

## MAINS SUPPLY

A mains-operated supply, is of course, very useful, particularly if you are interested in trying out IC amplifier circuits which operate loudspeakers. These circuits can flatten small batteries pretty quickly, so that extensive work of this kind really calls out for a mains supply. Building such a supply is not difficult (see HE for May, 1979), but you have to remember that the input to such a supply is 240 V mains, and you can't afford to take any risk with the high mains voltage which we use in this country. Building a mains supply is not a job for a beginner, and it demands as much care in mechanical details like shaping metalwork and mounting components as it does in electrical details like correct connections. The construction of a power supply won't

be described here, because there are so many excellent designs and kits around. A kit, incidentally, is a very satisfactory way of building your first mains power supply.

Suppose you don't want to undertake the construction of a mains power pack, but you don't fancy using batteries? There are still a few ways out. One is to buy a power supply — a suitable unit would provide 9-0-9 volts of smooth DC at 0.5 A. This unit could be pricy, but it's certainly quick and safe. Another way is less costly and a bit unusual. Every motorist's accessory shop sells power supply units — called battery chargers. A lot of junk shops also sell them second-hand; there must be millions of them around, and they're only used in the winter. Now the output from these battery-chargers doesn't look much like DC, but if a smoothing capacitor of 5 000  $\mu$ F, 35 V, is added, as shown in Fig. 9, they convert nicely into power supply units with an output of up to 18 V or so. Don't try to put the capacitor inside — there's seldom room, and you may disturb the wiring to the extent of causing a short circuit.

## VARIABLE POWER

Fig. 10 shows how such a supply can be adapted to provide 9-0-9 V for the circuits which need a dual power supply. This circuit is also useful if you happen to have a power-pack which has an 18 V output and no negative output. The circuit consists of a 9V zener diode and a resistor, with the earth line taken from the place where the diode and the resistor connect. Even if the power supply doesn't deliver exactly 18 V, this version of a dual power supply works well enough for all the dual-supply projects in this series. Remember that dual-supply circuits use fewer components.

For circuits that use low currents (like many of the 741 and 555 circuits) the voltage across the zener diode in Fig. 10 can be used as a single supply, leaving the —9 V lead disconnected, but the higher-power circuits can't be operated in this way because the resistor in series with the zener diode won't pass enough current. Another solution will have to wait until Part 7: it's the use of a linear IC which acts as a voltage stabiliser.

The ultimate in power packs, of course, is a variable stabilised mains unit, giving both positive and negative supplies and which can be set to any voltage required. Don't worry if you can't aspire to this, though, every circuit in this series can still be operated by the good old pair of PP3's.

HE

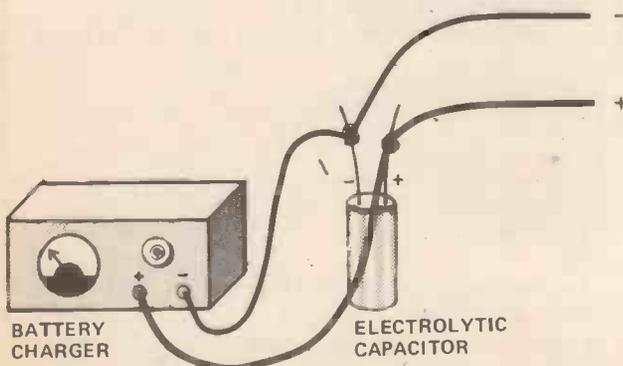
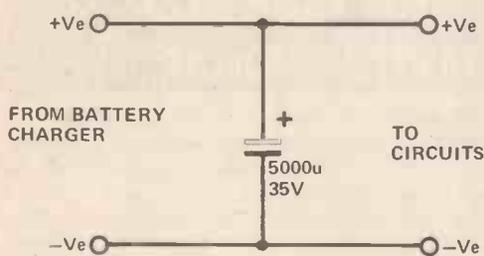


Fig. 9. Adding smoothing to a battery charger — a cheap way to get a single voltage supply suitable for many circuits.

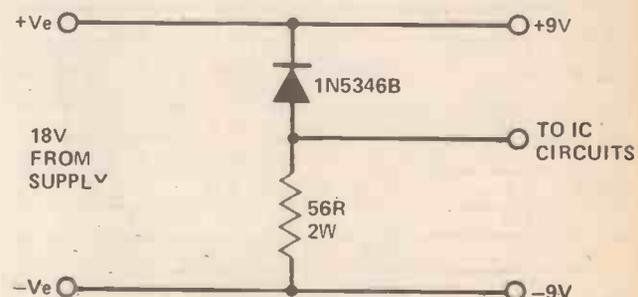


Fig. 10. Obtaining dual supplies from a single 18 V supply. The 1N5346B is a 9.1 V zener diode rated at 5 W and obtainable from RS Components stockists.

## ADVERT INDEX

AJD DIRECT SUPPLIES	65
AMBIT INTERNATIONAL	2
CODESPEED	17
C.S.C	27
E.D.A.	51
GMT ELECTRONICS	4 & 5
GREENWAY ELECTRONICS	17
METAC	75
MAPLIN	76
MARSHALLS	17
MINIKITS	46
PRESCOTT CLOCK & WATCH	73
RAMAR	73
R.T.V.C.	52
SWANLEY	58
TAMTRONIK	73
TECHNOMATIC	60
VERO	58

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components  
Full range of HE printed circuit boards, normally ex-stock, same day despatch at competitive prices.  
P.C. Boards to individual designs  
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Allic range of etch resist transfers, and other drawing materials for p.c. boards.

Send 15p for catalogue.

**RAMAR CONSTRUCTOR  
SERVICES**  
MASON'S ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel. 4879

### BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



(1) (2) (3)  
Returned to Service Department within guarantee period.

- (1) With alarm repeat — S.R.S.P. of £17.00 offered at £3.95 inc. VAT.
- (2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at £7.95 inc. V.A.T.
- (3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues, S.R.S.P. of £32.00—offered at £7.45 inc. V.A.T.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases

**PRESCOTT CLOCK AND  
WATCH COMPANY LIMITED**  
Prescott House, Humber Road, London NW2 6ER

To: Subscriptions  
Hobby Electronics

I would like a postal subscription to HE starting with the issue. I enclose payment (£6.50 for UK and Eire, £7.50 elsewhere, £11.50 air mail).

P.O. Box 35

Bridge Street,

Hemel Hempstead,

Herts

Name

Address

**MICROPROCESSORS AND COMPUTING.** A book to give you a start. Contents: Binary Arithmetic, Principle of Operation, Programming, Glossary of Terms, 50 pages of explanation and diagrams. Price £2.30 plus 45p p&p (cheques, crossed P.O. only). Educational Data and Technical Services, 59 Station Road, Cogenhoe, Northampton NN7 1LU.

## TAMTRONIK LTD. (DEPT. HE)

217 TOLL END ROAD, TIPTON  
WEST MIDLANDS DY4 0HW

TEL. 021-557 9144

## PRINTED CIRCUIT BOARDS and KITS FOR HE PROJECTS

Mag Issue	Project	Kit Ref	PCS	Kit	Kit Contents (See key)
Nov 78	Beehive Radio	HO01	1.25	15.95	BEHL
	Stereo Amplifier	HO02	3.90	43.95	BEHL
	Waa Waa Pedal	HO03	90	6.90	BEH
Dec 78	Push Button Disco	HO05	1.10	5.85	BEHL
	N.E. Meters	HO06	85	6.40	BEHL
	Photo Flash	HO07	1.50	—	BEHL
	N.E. Mixer	HO08	3.25	23.35	BEHL
Jan 79	Graphic Equalizer	HO09	3.25	24.55	BEHL
	Flash Trigger	HO10	1.10	13.15	BEHL
	Varwiper — Relay	HO11A	90	7.30	BEH
	Varwiper — SCR	HO11B	90	4.10	BEH
	Touch Switch	HO12	1.15	4.95	BEH
Feb 79	Short Wave Radio	HO13	1.40	11.95	BEH
	Sine/Square Wave Generator	HO14	1.95	25.95	BEHL
	Scratch & Rumble Filter (Music)	HO15	1.45	14.40	BEHL
	Scratch & Rumble Filter (Stereo)	HO15S	2.90	18.45	BEHL
	HE Car Alarm	HO16	1.20	0.35	BEHL
Mar 79	Light Chaser	HO17	2.00	14.25	BEH
	Cassette's Candle	HO18	1.10	5.95	BEH
	Thru Control	HO19	1.00	8.80	BEHL
	Photographic Timer	HO20	1.25	9.95	BEHL
Apr 79	Model Train Controller	HO21	1.40	21.90	BEHL
	Cassette Alarm	HO22	80	2.95	BEHL
	Transistor GOLF Tester	HO23	.75	5.25	BEHL
May 79	Power Supply Unit	HO24	1.93	21.55	BEJ
	Parking Motor Timer	HO25	82	—	BEH
	Digital	HO26	1.35	4.95	BEHL
	White Noise Generator	HO27	1.67	14.95	BEHL
Jun 79	SSR Monitor	HO28	1.05	10.10	BEHL
	Envelope Generator	HO29	1.50	12.10	BEHL
	Drift Speed Controller	HO30	1.05	6.95	BEH

### KEY TO KIT CONTENTS

- A. Vero-board(s).
- B. Printed Circuit Board(s).
- C. With Screen printed component layout.
- D. Tag strip.
- E. All Resistors, potentiometers, capacitors, semi-conductors.
- F. As E but with exclusions. Please ask for details.
- G. Diode and/or transistor sockets and/or soldercon pins.
- H. Hardware includes switches, knobs, lamps and holders, fuses and holders, plugs and sockets, microphones, transformers, speakers, meters, relays, terminal blocks, battery connectors, etc. BUT excludes nuts, bolts, washers, connecting wire, batteries and special miscellaneous items.
- J. As H but with exclusions. Please ask for details.
- K. As H but including connecting wire.
- L. Suitable case(s).
- M. Suitable case with screen printed fascia.
- N. Full kit to magazine specified standards.
- P. Kit with professional finish — incorporating all prime features including screen printed pcb and case where appropriate.

Photocopy of any of listed Projects 30p.

### SPECIAL OFFERS

Plug-in mains PSU, 3v/5v/9v/12v DC 300MA.  
Suitable for calculators, TV Games, etc. £2.99  
100 x 1/4W 1k resistors 30p  
4 x NE 555 £1.00

Pcbs and kits available from TAMTRONIK LTD. for projects from ET1 and EVERYDAY ELECTRONICS. Send sae for free catalogue. Please quote project and kit reference number when details of a specific kit are required, sae.

Tamtronik Ltd. reserves the right to change kit content without notice to incorporate current modifications or to make valid substitutions for temporarily unavailable components.

The majority of kits advertised can be supplied from stock, however please allow 21 days delivery since demand on any kit is unpredictable.

### JULY PROJECTS

	KIT REF.	PCB	KIT	KIT CONTENTS
HE Shark	HO31	2.00	22.95	BEHL
Points Controller	HO32	1.15	12.35	BEHL
Baby Alarm	HO33	1.45	13.60	BEHL

Kits can be supplied excluding pcb and/or case. Send sae for details naming kit and kit reference and free catalogue.

Trade and Educational enquiries welcome

PRICES INCLUDE  
VAT & P. & P.  
MINIMUM ORDER  
£3.00

Visit our shop at  
**32 Market Place  
Great Bridge, Tipton  
West Midlands**

Telephone or Letter



# Hobby Electronics Book Service



## POPULAR ELECTRONICS BOOKS

Sinclair, I. R., Introducing Electronic Systems .....	£1.80
Sinclair, I. R., Introducing Amateur Electronics .....	£1.55
Sinclair, I. R., Electronic Fault Diagnosis .....	£3.45
Sinclair, I. R., Repairing Pocket Transistor Radios .....	£2.50
Sinclair, I. R., Oscilloscope In Use .....	£3.00
Sinclair, I. R., Understanding Electronic Components .....	£4.00
Sinclair, I. R., Understanding Electronic Circuits .....	£4.00
Kitchen, H. T., Handtools For Electronic Workshop .....	£2.75
Kitchen, H. T., Electronic Test Equipment .....	£5.00
Capel, V., How To Build Electronic Kits .....	£2.20

## AUDIO

Earl, J., Audio Technicians Bench Manual .....	£3.50
Earl, J., Pickups and Loud Speakers .....	£3.50
Earl, J., Tuners and Amplifiers .....	£3.00
Earl, J., Cassette Tape Recorders .....	£5.25
Earl, J., ABC of Hi-Fi .....	£4.25
Capel, V., Microphones In Action .....	£3.00
Capel, V., Improving Your Hi-Fi .....	£3.50
Capel, V., Creative Tape Recording .....	£4.00
Hellyer, H. W., Tape Recorders .....	£4.25
Sinclair, I. R., Audio Amplifiers For Home Construction .....	£2.75

## RADIO CONTROL

Aldridge, D., Transistorised Radio Control For Models .....	£3.50
Orake, J., Radio Controlled Helicopter Models .....	£3.95
Jeffries, C. R., Radio Control For Model Yachts .....	£1.85
Safford, E. L., Radio Control Manual .....	£2.45
Safford, E. L., Advanced Radio Control .....	£3.95

## COOKBOOKS

Tracton, K., BASIC Cookbook .....	£4.10
Lancaster, D., TTL Cookbook .....	£7.00
Lancaster, D., RTL Cookbook .....	£4.65
Lancaster, D., CMOS Cookbook .....	£8.20
Jong, W., IC Op Amp Cookbook .....	£10.00
Lancaster, D., T.V. Typewriter Cookbook .....	£7.75
Lancaster, D., Cheap Video Cookbook .....	£7.00
Jong, W., IC Timer Cookbook .....	£7.50
Lancaster, D., Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business) .....	£4.95

## QUESTIONS AND ANSWERS

SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.	
Coker, A. J., Q & A On Electric Motors .....	£1.50
Hellyer, H., Q & A On Radios and T.V. .....	£1.50
Hibberd, R., Q & A On Integrated Circuits .....	£1.50
Jackson, K., Q & A On Electricity .....	£1.50
Brown, C., Q & A On Hi-Fi .....	£1.50
Brown, C., Q & A On Transistors .....	£1.50
Brown, C., Q & A On Electronics .....	£1.50
Reddihough, J., Q & A On Colour T.V. .....	£1.50
Miller, H., Q & A On Electric Wiring .....	£1.50

## CONSTRUCTOR GUIDES

Graham, P., Simple Circuit Building .....	£2.45
Colwell, M., Electronic Diagrams .....	£2.45
Colwell, M., Electronic Components .....	£2.45
Colwell, M., Printed Circuit Assembly .....	£2.45
Ainslie, A., Practical Electronic Project Building .....	£2.45
Colwell, M., Project Planning and Building .....	£2.45

## BEGINNER'S GUIDE

Sinclair, I. R., Beginner's Guide To Tape Recording .....	£3.30
Sinclair, I. R., Beginner's Guide To Integrated Circuits .....	£3.10
Sinclair, I. R., Beginner's Guide To Audio .....	£3.10
King, G. J., Beginner's Guide To Radio .....	£3.10
King, G. J., Beginner's Guide To Television .....	£3.10
King, G. J., Beginner's Guide To Colour T.V. .....	£3.10
Guilou, F., Beginner's Guide To Electric Wiring .....	£3.10

## PROJECT BOOKS

Marston, R. M., 110 Cosmos Digital IC Projects For The Home Constructor .....	£3.25
Marston, R. M., 110 Wave Form Projects For The Home Constructor .....	£3.45
Marston, R. M., 110 Op Amp Projects For The Home Constructor ..	£2.95
Marston, R. M., 110 Semiconductor Projects For The Home Constructor ..	£3.45
Marston, R. M., 110 Thyristor/SCR Projects For The Home Constructor ..	£2.95
Marston, R. M., 110 Electronic Alarm Projects For The Home Constructor ..	£3.45
Marston, R. M., 110 Integrated Circuits Projects For The Home Constructor ..	£3.45
Marston, R. M., 20 Solid State Projects For The Car and Garage ..	£2.50
Marston, R. M., 20 Solid State Projects For The Home .....	£2.50

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service,  
P.O. Box 79,  
Maidenhead, Berks.

### QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch.

Very slim, only 6mm thick.



M1

### SOLAR QUARTX LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins., secs. Day/date. Fully adjustable bracelet. Back-light. Only 7mm thick.

**£8.65**

Guaranteed same day despatch.



M2

### QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£10.65** Thousands sold!

Guaranteed same day despatch



M3

### QUARTZ LCD ALARM 7 Function

Alarm. Hours, mins., secs. Month, date, day. 6 digits 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick

**£12.65**

Guaranteed same day despatch



M4

### MULTI ALARM 6 Digits 10 Functions

- ★ Hours, mins., secs.
- ★ Month, date, day
- ★ Basic alarm.
- ★ Memory date alarm.
- ★ Timer alarm with dual time and 10 country zone.
- ★ Back light.
- ★ 8mm thick.

**£18.65**



M5

### FRONT-BUTTON ALARM Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins. plus optional seconds or date display. AM/PM indication. Month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light.



Fully adjustable open bracelet. **£22.65** Guaranteed same day despatch

M6

### SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

**£27.95**



M7

### ALARM CHRONO with 9 World Time Zones

- ★ 6 digits, 5 flags.
- ★ 6 basic functions.
- ★ 8 further time zones.
- ★ Count-down alarm.
- ★ Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps.
- ★ Split and lap timing modes.
- ★ Alarm.
- ★ 9mm thick.
- ★ Back-light.
- ★ Fully adjustable bracelet.

**£29.65**



M8

### SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th secs. 10X secs., mins. Split and lap modes. Back-light. Auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£12.65**

Guaranteed same day despatch.



M9

### SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00 METAC PRICE

**£105.00**



M10

### SEIKO MEMORY BANK Calendar Watch M354

Hours, mins., secs., month, day, date in 12 or 24 hour format at all indicated continuously. Monthly calendar display, month, year and all dates for any selected month over 80-year period. Memory bank function. Any desired dates up to 11 can be stored in advance. 2-year battery life.

List Price **£130**  
Metac Price **£105**  
Water resistant. M11



M11

### SEIKO-STYLE Dual Time-Alarm Chronograph

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

**£35.00**



M12

### HANIMEX Electronic LED Alarm Clock



Features and Specification  
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg).

**£9.65** Thousands sold!  
Mains operated.

Guaranteed same day despatch.

M13

### HANIMEX Portable LCD Clock Radio

- ★ Back-light.
- ★ Batteries supplied free.
- ★ Quartz crystal controlled.

**£17.95**



M14

#### HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100.  
Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

### QUARTZ LCD Ladies 5 Function.

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

### PRICE BREAKTHROUGH ONLY

**£18.95**



#### OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, 59.9 seconds.
- On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to any time within a 24-hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch.

M16

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753



Speakers from 1½ inch to 15 inch; megaphone, PA horns, crossovers etc. They're all in our catalogue. Send the coupon now!



A genuine 150W per channel stereo disco to build yourself. Full specification in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



Our catalogue describes a wide range of plugs and sockets, all at marvellous prices. See cat. pages 114 to 129 for details.



61-note touch-sensitive piano to build yourself. Full specification in our catalogue.




A very high quality 40W per channel stereo amplifier with a superb specification and lots of extras. Full construction details in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



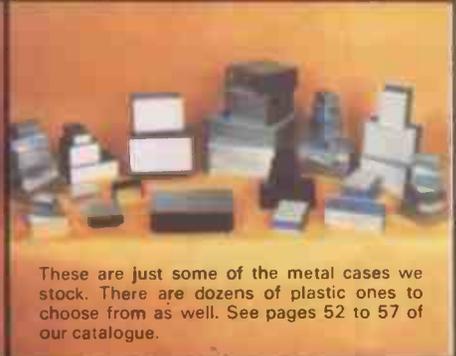A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.

# MAPLIN

**ELECTRONIC SUPPLIES LTD**


All mail to:-  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road,  
 Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554000



Multimeters, analogue and digital, frequency counter, oscilloscopes, and lots, lots more at excellent prices. See cat. pages 106 and 183 to 188 for details.



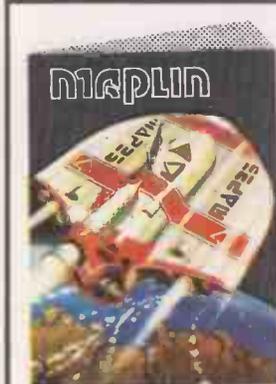A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages - some in full colour - it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin



A superb range of microphones and accessories at really low prices. Take a look in our catalogue—send the coupon now!

**Post this coupon now for your copy of our 1979-80 catalogue price 75p.**

Please send me a copy of your 280-page catalogue. I enclose 75p but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 75p refunded immediately. If you live outside U.K. send £1 or ten International Reply Coupons.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_