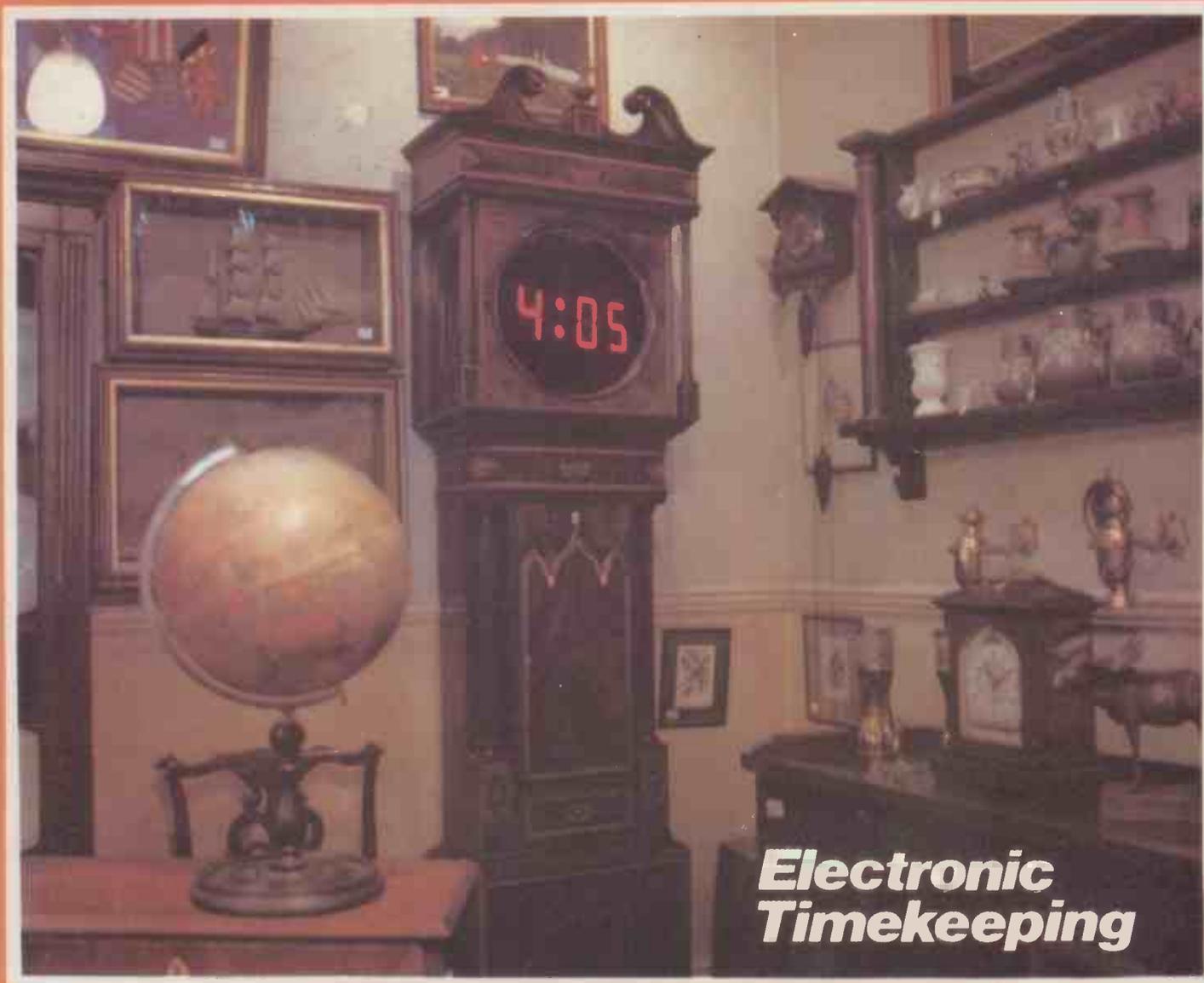


September '79

45p

# Hobby Electronics



**Electronic  
Timekeeping**

## **The HE 'Tantrum'**

*A treat for jaded ears*

## **Ultrasonic Remote Control**

*Do it at a distance*

## **Radio Control World**

*High flyers*

## **Lamp Dimmer**

*Save it*

## **Starburst**

*A treat for jaded eyes*

## **Thyristors**

*Power control*



# Hobby Electronics

Vol. 1. No. 11

September 1979

**Monitor** ..... 6

**Combination lock** ..... 8  
Protect your combinations

**Hobbyprints** ..... 12  
Perfect every time

**Clever Dick** ..... 13  
What energy crisis?


**Thyristors** ..... 14



The state of the gate

**HE Book Service** ..... 22,58  
Read all about it

**Starburst** ..... 23

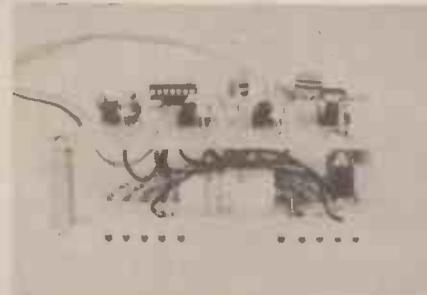

Don't be mis-LED

**Chit-Chat** ..... 27  
The robot story

## TANTRUM

We apologise to readers for the delay in publishing the Tantrum Stereo Amplifier, this was due to production difficulties and will be appearing next month.

**Market Place** ..... 30  
Watch this space

**Lamp Dimmer** ..... 33



Get turned on

**Back Numbers** ..... 36  
Are you missing something?

**Subscriptions** ..... 36  
Why keep missing out?

**Next Month in HE** ..... 37  
Would you believe it?

**Radio Control** ..... 38



Plane and simple

**Ultrasonic Switch** ..... 45



Dog Whistle?

**Short Circuits** ..... 48, 58, 63


**Specials** ..... 49  
Some new additions

**Electronic Time Keeping** .. 50  
How accurate is your watch?

**CB Special** ..... 56  
At long last

**Breaker One-Four** ..... 57  
Get your ears on

**FET Special** ..... 59

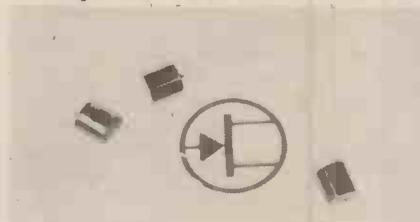

The source of the drain

**Next Month in ETI** ..... 65  
Big Brother

**Into Linear ICs** ..... 66  
Breadboard time

## Hobby Electronics

145 Charing Cross Road,  
London WC2H 0EE  
01-437 1002 (4 lines)

Published by Modmags Ltd,

Distributed by Argus Distribution Ltd,

Printed by QB Ltd, Colchester

Hobby Electronics is normally published on the second Friday of the month prior to the cover date

Editor: Halvor Moorshead

Editorial Asst: Richard Maybury

Project Team: Ray Marston, Steve Ramsahadeo, John FitzGerald, Keith Brindley

Production: Diego Rincon, Pete Howells.

Technical Artists: Paul Edwards, Tony Strakas

Advertising: Chris Surgenor, Steve Rowe, Joy Cheshire, Sandie Neville

Admin Staff: Margaret Hewitt, Bren Goodwin, Tim Salmon, Neville MacDonald, Tracey Campbell, Loraine Radmore, Loraine Stout, Marlin Felix, Halina Di-Lallo.

Copyright. All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing kits of the projects must be sought from the Editor. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally.

**ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED**

<b>CAPACITORS</b> <b>Electrolytic Axial Leads</b> -10% to +50% Tol <table border="1"> <tr> <th>µF</th> <th>V d.c.</th> <th>16</th> <th>25</th> <th>40</th> <th>63</th> </tr> <tr> <td>1.0</td> <td></td> <td></td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>1.5</td> <td></td> <td></td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>2.2</td> <td></td> <td></td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>3.3</td> <td></td> <td></td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>4.7</td> <td></td> <td></td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>5.8</td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>10</td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>15</td> <td>7</td> <td></td> <td></td> <td></td> <td>10</td> </tr> <tr> <td>22</td> <td>7</td> <td>7</td> <td></td> <td></td> <td>12</td> </tr> <tr> <td>33</td> <td>7</td> <td>7</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>47</td> <td>7</td> <td>7</td> <td></td> <td></td> <td>10</td> </tr> <tr> <td>68</td> <td>8</td> <td></td> <td></td> <td></td> <td>12</td> </tr> <tr> <td>100</td> <td>8</td> <td></td> <td></td> <td></td> <td>12</td> </tr> <tr> <td>150</td> <td>8</td> <td>9</td> <td></td> <td></td> <td>29</td> </tr> <tr> <td>220</td> <td>12</td> <td></td> <td></td> <td></td> <td>34</td> </tr> <tr> <td>330</td> <td></td> <td></td> <td></td> <td></td> <td>37</td> </tr> <tr> <td>470</td> <td></td> <td></td> <td></td> <td></td> <td>44</td> </tr> <tr> <td>680</td> <td>19</td> <td>28</td> <td></td> <td></td> <td>50</td> </tr> <tr> <td>1000</td> <td>23</td> <td>28</td> <td></td> <td></td> <td>55</td> </tr> <tr> <td>1500</td> <td>32</td> <td>36</td> <td></td> <td></td> <td></td> </tr> <tr> <td>2200</td> <td>39</td> <td></td> <td></td> <td></td> <td></td> </tr> </table>		µF	V d.c.	16	25	40	63	1.0					8	1.5					8	2.2					8	3.3					8	4.7					8	5.8					9	10					9	15	7				10	22	7	7			12	33	7	7			8	47	7	7			10	68	8				12	100	8				12	150	8	9			29	220	12				34	330					37	470					44	680	19	28			50	1000	23	28			55	1500	32	36				2200	39					<b>Electrolytic Can Type</b> High Ripple, IEC Grade 1, Low E.S.R. Supplied complete with Vertical Fixing Clip <table border="1"> <tr> <th>µF</th> <th>V d.c.</th> <th>16V</th> <th>25V</th> <th>40V</th> <th>50V</th> <th>63V</th> </tr> <tr> <td>2200</td> <td></td> <td>2.6A</td> <td>3.5A</td> <td>4.4A @ 85°C</td> <td>5.8A</td> <td>7.8A</td> </tr> <tr> <td>4700</td> <td></td> <td>2.6A</td> <td>3.5A</td> <td>4.4A @ 85°C</td> <td>5.8A</td> <td>7.8A</td> </tr> <tr> <td>10000</td> <td></td> <td>3.8A</td> <td>5.1A</td> <td>6.4A</td> <td>8.5A</td> <td>11.7A</td> </tr> <tr> <td>22000</td> <td></td> <td>5.8A</td> <td>7.8A</td> <td>9.8A</td> <td>13.7A</td> <td>18.8A</td> </tr> <tr> <td>47000</td> <td></td> <td>8.5A</td> <td>11.7A</td> <td>14.8A</td> <td>20.1A</td> <td>27.4A</td> </tr> <tr> <td>100000</td> <td></td> <td>12.8A</td> <td>17.9A</td> <td>22.8A</td> <td>30.8A</td> <td>41.8A</td> </tr> <tr> <td>220000</td> <td></td> <td>18.8A</td> <td>25.8A</td> <td>32.8A</td> <td>44.8A</td> <td>60.8A</td> </tr> <tr> <td>470000</td> <td></td> <td>27.4A</td> <td>37.4A</td> <td>47.4A</td> <td>64.4A</td> <td>87.4A</td> </tr> <tr> <td>1000000</td> <td></td> <td>40.8A</td> <td>55.8A</td> <td>70.8A</td> <td>95.8A</td> <td>129.8A</td> </tr> <tr> <td>2200000</td> <td></td> <td>59.8A</td> <td>80.8A</td> <td>102.8A</td> <td>138.8A</td> <td>185.8A</td> </tr> <tr> <td>4700000</td> <td></td> <td>87.4A</td> <td>117.4A</td> <td>149.4A</td> <td>201.4A</td> <td>273.4A</td> </tr> <tr> <td>10000000</td> <td></td> <td>129.8A</td> <td>175.8A</td> <td>223.8A</td> <td>300.8A</td> <td>403.8A</td> </tr> <tr> <td>22000000</td> <td></td> <td>185.8A</td> <td>253.8A</td> <td>323.8A</td> <td>433.8A</td> <td>581.8A</td> </tr> </table>		µF	V d.c.	16V	25V	40V	50V	63V	2200		2.6A	3.5A	4.4A @ 85°C	5.8A	7.8A	4700		2.6A	3.5A	4.4A @ 85°C	5.8A	7.8A	10000		3.8A	5.1A	6.4A	8.5A	11.7A	22000		5.8A	7.8A	9.8A	13.7A	18.8A	47000		8.5A	11.7A	14.8A	20.1A	27.4A	100000		12.8A	17.9A	22.8A	30.8A	41.8A	220000		18.8A	25.8A	32.8A	44.8A	60.8A	470000		27.4A	37.4A	47.4A	64.4A	87.4A	1000000		40.8A	55.8A	70.8A	95.8A	129.8A	2200000		59.8A	80.8A	102.8A	138.8A	185.8A	4700000		87.4A	117.4A	149.4A	201.4A	273.4A	10000000		129.8A	175.8A	223.8A	300.8A	403.8A	22000000		185.8A	253.8A	323.8A	433.8A	581.8A	<b>Miniature Low Value</b> Polystyrene, Axial, ±1% Tol, > 63V D.C. Wkg Ceramic Plate, Radial, Low K, 1.8pF - 82pF ±25pF Tol, 10-330pF ±2% Tol, 100V D.C. Wkg Ceramic Plate, Radial, High K, ±10% Tol, 100V D.C. Wkg Ceramic Plate, Radial, High K, -20% to +80% Tol, 63V D.C. Wkg <table border="1"> <tr> <th>µF</th> <th>424</th> <th>632</th> <th>630</th> <th>629</th> <th>µF</th> <th>424</th> <th>632</th> <th>630</th> <th>629</th> <th>nF</th> <th>424</th> <th>632</th> <th>630</th> <th>629</th> </tr> <tr> <td>100</td> <td>16</td> <td>6</td> <td></td> <td></td> <td>1.2</td> <td>120</td> <td>16</td> <td>8</td> <td></td> <td>10</td> <td>25</td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>120</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>1.5</td> <td>150</td> <td>16</td> <td>8</td> <td></td> <td>15</td> <td>26</td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>150</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>1.8</td> <td>180</td> <td>16</td> <td>8</td> <td></td> <td>15</td> <td>26</td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>180</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>2.2</td> <td>220</td> <td>16</td> <td>8</td> <td></td> <td>22</td> <td>28</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>220</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>2.7</td> <td>270</td> <td>16</td> <td>8</td> <td></td> <td>27</td> <td>38</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>330</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>3.3</td> <td>330</td> <td>16</td> <td>8</td> <td></td> <td>33</td> <td>41</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>390</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>3.9</td> <td>390</td> <td>16</td> <td>8</td> <td></td> <td>39</td> <td>43</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>470</td> <td>16</td> <td>8</td> <td></td> <td></td> <td>4.7</td> <td>470</td> <td>16</td> <td>8</td> <td></td> <td>47</td> <td>46</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>5.6</td> <td>5</td> <td></td> <td></td> <td></td> <td>5.6</td> <td>560</td> <td>16</td> <td>5</td> <td></td> <td>56</td> <td>50</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>6.8</td> <td>5</td> <td></td> <td></td> <td></td> <td>6.8</td> <td>680</td> <td>16</td> <td>5</td> <td></td> <td>68</td> <td>55</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>8.2</td> <td>5</td> <td></td> <td></td> <td></td> <td>8.2</td> <td>820</td> <td>16</td> <td>5</td> <td></td> <td>82</td> <td>60</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>10</td> <td>5</td> <td></td> <td></td> <td></td> <td>10</td> <td>1000</td> <td>16</td> <td>5</td> <td></td> <td>1000</td> <td>65</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>12</td> <td>5</td> <td></td> <td></td> <td></td> <td>12</td> <td>1200</td> <td>16</td> <td>5</td> <td></td> <td>1200</td> <td>70</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>15</td> <td>5</td> <td></td> <td></td> <td></td> <td>15</td> <td>1500</td> <td>16</td> <td>5</td> <td></td> <td>1500</td> <td>75</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>18</td> <td>5</td> <td></td> <td></td> <td></td> <td>18</td> <td>1800</td> <td>16</td> <td>5</td> <td></td> <td>1800</td> <td>80</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>22</td> <td>5</td> <td></td> <td></td> <td></td> <td>22</td> <td>2200</td> <td>16</td> <td>5</td> <td></td> <td>2200</td> <td>85</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>27</td> <td>5</td> <td></td> <td></td> <td></td> <td>27</td> <td>2700</td> <td>16</td> <td>5</td> <td></td> <td>2700</td> <td>90</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>33</td> <td>5</td> <td></td> <td></td> <td></td> <td>33</td> <td>3300</td> <td>16</td> <td>5</td> <td></td> <td>3300</td> <td>95</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>39</td> <td>5</td> <td></td> <td></td> <td></td> <td>39</td> <td>3900</td> <td>16</td> <td>5</td> <td></td> <td>3900</td> <td>100</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>47</td> <td>5</td> <td></td> <td></td> <td></td> <td>47</td> <td>4700</td> <td>16</td> <td>5</td> <td></td> <td>4700</td> <td>105</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>56</td> <td>5</td> <td></td> <td></td> <td></td> <td>56</td> <td>5600</td> <td>16</td> <td>5</td> <td></td> <td>5600</td> <td>110</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>68</td> <td>5</td> <td></td> <td></td> <td></td> <td>68</td> <td>6800</td> <td>16</td> <td>5</td> <td></td> <td>6800</td> <td>115</td> <td></td> <td></td> <td>8</td> </tr> <tr> <td>82</td> <td>5</td> <td></td> <td></td> <td></td> <td>82</td> <td>8200</td> <td>16</td> <td>5</td> <td></td> <td>8200</td> <td>120</td> <td></td> <td></td> <td>8</td> </tr> </table>		µF	424	632	630	629	µF	424	632	630	629	nF	424	632	630	629	100	16	6			1.2	120	16	8		10	25			6	120	16	8			1.5	150	16	8		15	26			6	150	16	8			1.8	180	16	8		15	26			6	180	16	8			2.2	220	16	8		22	28			8	220	16	8			2.7	270	16	8		27	38			8	330	16	8			3.3	330	16	8		33	41			8	390	16	8			3.9	390	16	8		39	43			8	470	16	8			4.7	470	16	8		47	46			8	5.6	5				5.6	560	16	5		56	50			8	6.8	5				6.8	680	16	5		68	55			8	8.2	5				8.2	820	16	5		82	60			8	10	5				10	1000	16	5		1000	65			8	12	5				12	1200	16	5		1200	70			8	15	5				15	1500	16	5		1500	75			8	18	5				18	1800	16	5		1800	80			8	22	5				22	2200	16	5		2200	85			8	27	5				27	2700	16	5		2700	90			8	33	5				33	3300	16	5		3300	95			8	39	5				39	3900	16	5		3900	100			8	47	5				47	4700	16	5		4700	105			8	56	5				56	5600	16	5		5600	110			8	68	5				68	6800	16	5		6800	115			8	82	5				82	8200	16	5		8200	120			8
µF	V d.c.	16	25	40	63																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
1.0					8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
1.5					8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
2.2					8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
3.3					8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
4.7					8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
5.8					9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
10					9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
15	7				10																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
22	7	7			12																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
33	7	7			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
47	7	7			10																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
68	8				12																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
100	8				12																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
150	8	9			29																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
220	12				34																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
330					37																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
470					44																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
680	19	28			50																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
1000	23	28			55																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
1500	32	36																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
2200	39																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
µF	V d.c.	16V	25V	40V	50V	63V																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
2200		2.6A	3.5A	4.4A @ 85°C	5.8A	7.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
4700		2.6A	3.5A	4.4A @ 85°C	5.8A	7.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
10000		3.8A	5.1A	6.4A	8.5A	11.7A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
22000		5.8A	7.8A	9.8A	13.7A	18.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
47000		8.5A	11.7A	14.8A	20.1A	27.4A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
100000		12.8A	17.9A	22.8A	30.8A	41.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
220000		18.8A	25.8A	32.8A	44.8A	60.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
470000		27.4A	37.4A	47.4A	64.4A	87.4A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
1000000		40.8A	55.8A	70.8A	95.8A	129.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
2200000		59.8A	80.8A	102.8A	138.8A	185.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
4700000		87.4A	117.4A	149.4A	201.4A	273.4A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
10000000		129.8A	175.8A	223.8A	300.8A	403.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
22000000		185.8A	253.8A	323.8A	433.8A	581.8A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
µF	424	632	630	629	µF	424	632	630	629	nF	424	632	630	629																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
100	16	6			1.2	120	16	8		10	25			6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
120	16	8			1.5	150	16	8		15	26			6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
150	16	8			1.8	180	16	8		15	26			6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
180	16	8			2.2	220	16	8		22	28			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
220	16	8			2.7	270	16	8		27	38			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
330	16	8			3.3	330	16	8		33	41			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
390	16	8			3.9	390	16	8		39	43			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
470	16	8			4.7	470	16	8		47	46			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
5.6	5				5.6	560	16	5		56	50			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
6.8	5				6.8	680	16	5		68	55			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
8.2	5				8.2	820	16	5		82	60			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
10	5				10	1000	16	5		1000	65			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
12	5				12	1200	16	5		1200	70			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
15	5				15	1500	16	5		1500	75			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
18	5				18	1800	16	5		1800	80			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
22	5				22	2200	16	5		2200	85			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
27	5				27	2700	16	5		2700	90			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
33	5				33	3300	16	5		3300	95			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
39	5				39	3900	16	5		3900	100			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
47	5				47	4700	16	5		4700	105			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
56	5				56	5600	16	5		5600	110			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
68	5				68	6800	16	5		6800	115			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
82	5				82	8200	16	5		8200	120			8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					
<b>Tantalum Bead</b> -20% Tol. <table border="1"> <tr> <th>µF</th> <th>V d.c.</th> <th>3.15</th> <th>6.3</th> <th>10</th> <th>16</th> <th>25</th> <th>35</th> </tr> <tr> <td>0.1</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>0.15</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>0.22</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>0.33</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>0.47</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>0.68</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>9</td> </tr> <tr> <td>1</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>10</td> </tr> <tr> <td>1.5</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>11</td> </tr> <tr> <td>2.2</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>11</td> </tr> <tr> <td>3.3</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>14</td> </tr> <tr> <td>4.7</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>15</td> </tr> <tr> <td>6.8</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>16</td> </tr> <tr> <td>10</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>20</td> </tr> <tr> <td>15</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>20</td> </tr> <tr> <td>22</td> <td>11</td> <td>14</td> <td></td> <td></td> <td></td> <td></td> <td>16</td> </tr> <tr> <td>33</td> <td></td> <td></td> <td>15</td> <td>16</td> <td>20</td> <td></td> <td>20</td> </tr> <tr> <td>47</td> <td></td> <td></td> <td>16</td> <td>20</td> <td>20</td> <td></td> <td>20</td> </tr> <tr> <td>68</td> <td>16</td> <td>20</td> <td></td> <td></td> <td></td> <td></td> <td>20</td> </tr> <tr> <td>100</td> <td>20</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>20</td> </tr> </table>		µF	V d.c.	3.15	6.3	10	16	25	35	0.1							9	0.15							9	0.22							9	0.33							9	0.47							9	0.68							9	1							10	1.5							11	2.2							11	3.3							14	4.7							15	6.8							16	10							20	15							20	22	11	14					16	33			15	16	20		20	47			16	20	20		20	68	16	20					20	100	20						20	<b>Electrolytic Radial Leads</b> -10% to +50% Tol. <table border="1"> <tr> <th>µF</th> <th>V d.c.</th> <th>6.3</th> <th>10</th> <th>16</th> <th>25</th> <th>35</th> <th>40</th> <th>50</th> <th>63</th> </tr> <tr> <td>47</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>68</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>1.0</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>1.5</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>2.2</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>3.3</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>4.7</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>5.8</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>10</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>15</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>22</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>33</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>47</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>56</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>68</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> <tr> <td>82</td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td></td> <td>6</td> </tr> </table>		µF	V d.c.	6.3	10	16	25	35	40	50	63	47									6	68									6	1.0									6	1.5									6	2.2									6	3.3									6	4.7									6	5.8									6	10									6	15									6	22									6	33									6	47									6	56									6	68									6	82									6	<b>Polyester Radial Leads</b> Dipped Type, ±20% Tol, > 250V D.C. Wkg. C280/352 Style Moulded Type, ±10% Tol, > 100V D.C. Wkg. 10.2mm Pitch Centres Moulded Type, ±10% Tol, > 100V D.C. Wkg. 7.6mm Pitch Centres <table border="1"> <tr> <th>µF</th> <th>352</th> <th>360</th> <th>PHE280</th> <th>µF</th> <th>352</th> <th>360</th> <th>PHE280</th> </tr> <tr> <td>0.01</td> <td>5</td> <td>6</td> <td></td> <td>1</td> <td>6</td> <td>8</td> <td>9</td> </tr> <tr> <td>0.015</td> <td>5</td> <td>6</td> <td></td> <td>1.5</td> <td>7</td> <td>9</td> <td>9</td> </tr> <tr> <td>0.022</td> <td>5</td> <td>6</td> <td></td> <td>2.2</td> <td>8</td> <td>10</td> <td></td> </tr> <tr> <td>0.033</td> <td>5</td> <td>6</td> <td></td> <td>3.3</td> <td>10</td> <td></td> <td></td> </tr> <tr> <td>0.047</td> <td>5</td> <td>6</td> <td></td> <td>4.7</td> <td>12</td> <td></td> <td></td> </tr> <tr> <td>0.068</td> <td>5</td> <td>6</td> <td></td> <td>6.8</td> <td>15</td> <td></td> <td></td> </tr> <tr> <td>0.1</td> <td>5</td> <td>6</td> <td></td> <td>10</td> <td>19</td> <td></td> <td></td> </tr> <tr> <td>0.15</td> <td>5</td> <td>6</td> <td></td> <td>15</td> <td>27</td> <td></td> <td></td> </tr> <tr> <td>0.22</td> <td>5</td> <td>6</td> <td></td> <td>22</td> <td>32</td> <td></td> <td></td> </tr> <tr> <td>0.33</td> <td>5</td> <td>6</td> <td></td> <td>33</td> <td>38</td> <td></td> <td></td> </tr> <tr> <td>0.47</td> <td>5</td> <td>6</td> <td></td> <td>47</td> <td>45</td> <td></td> <td></td> </tr> <tr> <td>0.68</td> <td>5</td> <td>6</td> <td></td> <td>68</td> <td>55</td> <td></td> <td></td> </tr> <tr> <td>1</td> <td>5</td> <td>6</td> <td></td> <td>100</td> <td>65</td> <td></td> <td></td> </tr> <tr> <td>1.5</td> <td>5</td> <td>6</td> <td></td> <td>150</td> <td>75</td> <td></td> <td></td> </tr> <tr> <td>2.2</td> <td>5</td> <td>6</td> <td></td> <td>220</td> <td>85</td> <td></td> <td></td> </tr> </table>		µF	352	360	PHE280	µF	352	360	PHE280	0.01	5	6		1	6	8	9	0.015	5	6		1.5	7	9	9	0.022	5	6		2.2	8	10		0.033	5	6		3.3	10			0.047	5	6		4.7	12			0.068	5	6		6.8	15			0.1	5	6		10	19			0.15	5	6		15	27			0.22	5	6		22	32			0.33	5	6		33	38			0.47	5	6		47	45			0.68	5	6		68	55			1	5	6		100	65			1.5	5	6		150	75			2.2	5	6		220	85																																																																																																																																						
µF	V d.c.	3.15	6.3	10	16	25	35																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.1							9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.15							9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.22							9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.33							9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.47							9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.68							9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
1							10																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
1.5							11																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
2.2							11																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
3.3							14																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
4.7							15																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
6.8							16																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
10							20																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
15							20																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
22	11	14					16																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
33			15	16	20		20																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
47			16	20	20		20																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
68	16	20					20																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
100	20						20																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
µF	V d.c.	6.3	10	16	25	35	40	50	63																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
47									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
68									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
1.0									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
1.5									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
2.2									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
3.3									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
4.7									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
5.8									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
10									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
15									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
22									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
33									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
47									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
56									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
68									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
82									6																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
µF	352	360	PHE280	µF	352	360	PHE280																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.01	5	6		1	6	8	9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.015	5	6		1.5	7	9	9																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
0.022	5	6		2.2	8	10																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																													
0.033	5	6		3.3	10																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.047	5	6		4.7	12																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.068	5	6		6.8	15																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.1	5	6		10	19																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.15	5	6		15	27																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.22	5	6		22	32																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.33	5	6		33	38																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.47	5	6		47	45																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
0.68	5	6		68	55																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
1	5	6		100	65																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
1.5	5	6		150	75																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
2.2	5	6		220	85																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
<b>Trimmers</b> 250V D.C. Wkg. Film Dielectric, Miniature <table border="1"> <tr> <th>Order Code</th> <th>500V D.C. Wkg. C004 EA Tubular Type</th> </tr> <tr> <td>1.4 - 4.1pF</td> <td>Cap B08 A</td> </tr> <tr> <td>2 - 9pF</td> <td>Cap B08 B</td> </tr> <tr> <td>2 - 20pF</td> <td>Cap B08 C</td> </tr> <tr> <td>5.5 - 59.5pF</td> <td>Cap B08 D</td> </tr> </table>		Order Code	500V D.C. Wkg. C004 EA Tubular Type	1.4 - 4.1pF	Cap B08 A	2 - 9pF	Cap B08 B	2 - 20pF	Cap B08 C	5.5 - 59.5pF	Cap B08 D	<b>Order Code</b> <table border="1"> <tr> <th>Order Code</th> <th>500V D.C. Wkg. C004 EA Tubular Type</th> </tr> <tr> <td>Cap B02 3</td> <td>.8 - 3.8pF</td> </tr> <tr> <td>Cap B02 6</td> <td>.8 - 6.8pF</td> </tr> <tr> <td>Cap B02 12</td> <td>1 - 13pF</td> </tr> <tr> <td>Cap B02 18</td> <td>1.7 - 19.7</td> </tr> </table>		Order Code	500V D.C. Wkg. C004 EA Tubular Type	Cap B02 3	.8 - 3.8pF	Cap B02 6	.8 - 6.8pF	Cap B02 12	1 - 13pF	Cap B02 18	1.7 - 19.7																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																												
Order Code	500V D.C. Wkg. C004 EA Tubular Type																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
1.4 - 4.1pF	Cap B08 A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
2 - 9pF	Cap B08 B																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
2 - 20pF	Cap B08 C																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
5.5 - 59.5pF	Cap B08 D																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Order Code	500V D.C. Wkg. C004 EA Tubular Type																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Cap B02 3	.8 - 3.8pF																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Cap B02 6	.8 - 6.8pF																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Cap B02 12	1 - 13pF																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Cap B02 18	1.7 - 19.7																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
<b>CASES</b> <b>Small Desk Console - Boss Industrial Mouldings</b> Slope Front Console, Recessed Top ABS Base, C/W Brass Bushes, In Orange 1mm Aluminium Top Panel Finished Grey <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>W161 D06 H39 (57)</td> <td>186 Case BIM1005 OR</td> </tr> <tr> <td>W215 D130 H47 (73)</td> <td>268 Case BIM1006 OR</td> </tr> </table>		Order Code	Case	W161 D06 H39 (57)	186 Case BIM1005 OR	W215 D130 H47 (73)	268 Case BIM1006 OR	<b>VERO ELECTRONICS PRODUCTS</b> <table border="1"> <tr> <td>2.5" x 5" 1/2" pitch Veroboard</td> <td>58</td> <td>VERO 21069J</td> </tr> <tr> <td>3.75" x 5" 1/2" pitch Veroboard</td> <td>66</td> <td>VERO 21072D</td> </tr> <tr> <td>2.5" x 11" 1/2" pitch Veroboard (5)</td> <td>70/Pack</td> <td>VERO 21076C</td> </tr> <tr> <td>3.75" x 5" 1/2" pitch Plain Board</td> <td>56</td> <td>VERO 21078E</td> </tr> <tr> <td>5.87" x 2.9" 1/2" pitch V-Q DIP Board</td> <td>111</td> <td>VERO 21084E</td> </tr> <tr> <td>Spot Face Cutter</td> <td>89</td> <td>VERO 21010A</td> </tr> <tr> <td>Pin Insertion Tool for J40 type pin</td> <td>122</td> <td>VERO 21015F</td> </tr> <tr> <td>OS Pins .040 (100)</td> <td>38/Pack</td> <td>VERO 21087G</td> </tr> <tr> <td>SS Pins .040 (100)</td> <td>38/Pack</td> <td>VERO 21017B</td> </tr> <tr> <td>6mm Board Standoff (100)</td> <td>161/Pack</td> <td>VERO 21327K</td> </tr> <tr> <td>15mm Board Standoff (100)</td> <td>215/Pack</td> <td>VERO 21322G</td> </tr> <tr> <td>19mm Board Standoff (100)</td> <td>226/Pack</td> <td>VERO 21323D</td> </tr> <tr> <td>Varowire Kit (1-pen, 2-wire, 25-cmb)</td> <td>375/Kit</td> <td>VERO 21341D</td> </tr> <tr> <td>Varowire Combs (100)</td> <td>407/Pack</td> <td>VERO 21339F</td> </tr> <tr> <td>Varowire Wire (4)</td> <td>228/Pack</td> <td>VERO 21010A</td> </tr> <tr> <td>Flip Top Box, Small, Black</td> <td>192</td> <td>VERO 21340G</td> </tr> <tr> <td>Flip Top Box, Large, Black</td> <td>250</td> <td>VERO 21317D</td> </tr> <tr> <td></td> <td></td> <td>VERO 21319J</td> </tr> </table>		2.5" x 5" 1/2" pitch Veroboard	58	VERO 21069J	3.75" x 5" 1/2" pitch Veroboard	66	VERO 21072D	2.5" x 11" 1/2" pitch Veroboard (5)	70/Pack	VERO 21076C	3.75" x 5" 1/2" pitch Plain Board	56	VERO 21078E	5.87" x 2.9" 1/2" pitch V-Q DIP Board	111	VERO 21084E	Spot Face Cutter	89	VERO 21010A	Pin Insertion Tool for J40 type pin	122	VERO 21015F	OS Pins .040 (100)	38/Pack	VERO 21087G	SS Pins .040 (100)	38/Pack	VERO 21017B	6mm Board Standoff (100)	161/Pack	VERO 21327K	15mm Board Standoff (100)	215/Pack	VERO 21322G	19mm Board Standoff (100)	226/Pack	VERO 21323D	Varowire Kit (1-pen, 2-wire, 25-cmb)	375/Kit	VERO 21341D	Varowire Combs (100)	407/Pack	VERO 21339F	Varowire Wire (4)	228/Pack	VERO 21010A	Flip Top Box, Small, Black	192	VERO 21340G	Flip Top Box, Large, Black	250	VERO 21317D			VERO 21319J																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																				
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
W161 D06 H39 (57)	186 Case BIM1005 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
W215 D130 H47 (73)	268 Case BIM1006 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
2.5" x 5" 1/2" pitch Veroboard	58	VERO 21069J																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
3.75" x 5" 1/2" pitch Veroboard	66	VERO 21072D																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
2.5" x 11" 1/2" pitch Veroboard (5)	70/Pack	VERO 21076C																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
3.75" x 5" 1/2" pitch Plain Board	56	VERO 21078E																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
5.87" x 2.9" 1/2" pitch V-Q DIP Board	111	VERO 21084E																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Spot Face Cutter	89	VERO 21010A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Pin Insertion Tool for J40 type pin	122	VERO 21015F																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
OS Pins .040 (100)	38/Pack	VERO 21087G																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
SS Pins .040 (100)	38/Pack	VERO 21017B																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
6mm Board Standoff (100)	161/Pack	VERO 21327K																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
15mm Board Standoff (100)	215/Pack	VERO 21322G																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
19mm Board Standoff (100)	226/Pack	VERO 21323D																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Varowire Kit (1-pen, 2-wire, 25-cmb)	375/Kit	VERO 21341D																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Varowire Combs (100)	407/Pack	VERO 21339F																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Varowire Wire (4)	228/Pack	VERO 21010A																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Flip Top Box, Small, Black	192	VERO 21340G																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
Flip Top Box, Large, Black	250	VERO 21317D																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
		VERO 21319J																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																	
<b>Plastic Boxes - Boss Industrial Mouldings</b> Moulded Box and Close Fitting Flange Lid ABS Box, C/W Brass Bushes, and Lid in Orange <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>L112 W62 D31</td> <td>87 Case BIM2003 OR</td> </tr> <tr> <td>L150 W80 D50</td> <td>115 Case BIM2005 OR</td> </tr> <tr> <td>L190 W110 D60</td> <td>195 Case BIM2006 OR</td> </tr> </table>		Order Code	Case	L112 W62 D31	87 Case BIM2003 OR	L150 W80 D50	115 Case BIM2005 OR	L190 W110 D60	195 Case BIM2006 OR	<b>HARDWARE</b> <b>D.I.L. Sockets</b> <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>8 Pin Low Profile Socket Tin</td> <td>11 DIL SKT 8</td> </tr> <tr> <td>14 Pin Low Profile Socket Tin</td> <td>13 DIL SKT 14</td> </tr> <tr> <td>16 Pin Low Profile Socket Tin</td> <td>14 DIL SKT 16</td> </tr> <tr> <td>24 Pin Low Profile Socket Gold</td> <td>14 DIL SKT 24</td> </tr> <tr> <td>28 Pin Low Profile Socket Gold</td> <td>78 DIL SKT 28</td> </tr> <tr> <td>40 Pin Low Profile Socket Gold</td> <td>127 DIL SKT 40</td> </tr> </table>		Order Code	Case	8 Pin Low Profile Socket Tin	11 DIL SKT 8	14 Pin Low Profile Socket Tin	13 DIL SKT 14	16 Pin Low Profile Socket Tin	14 DIL SKT 16	24 Pin Low Profile Socket Gold	14 DIL SKT 24	28 Pin Low Profile Socket Gold	78 DIL SKT 28	40 Pin Low Profile Socket Gold	127 DIL SKT 40																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																										
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L112 W62 D31	87 Case BIM2003 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L150 W80 D50	115 Case BIM2005 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L190 W110 D60	195 Case BIM2006 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
8 Pin Low Profile Socket Tin	11 DIL SKT 8																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
14 Pin Low Profile Socket Tin	13 DIL SKT 14																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
16 Pin Low Profile Socket Tin	14 DIL SKT 16																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
24 Pin Low Profile Socket Gold	14 DIL SKT 24																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
28 Pin Low Profile Socket Gold	78 DIL SKT 28																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
40 Pin Low Profile Socket Gold	127 DIL SKT 40																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
<b>Instrument Case - Boss Industrial Mouldings</b> Covers Manufactured from 14SWG Aluminium Chassis Manufactured from 18SWG Mild Steel Covers Finished Orange Chassis Finished Matt Black <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>W250 D167.5 H 68.5 (Chassis 153mm Deep)</td> <td>1480 Case BIM3000 OR</td> </tr> </table>		Order Code	Case	W250 D167.5 H 68.5 (Chassis 153mm Deep)	1480 Case BIM3000 OR	<b>Hardware</b> <b>Hestinks</b> Individual Type for 1 x T05 50°C/W Individual Type for 1 x T06 105°C/W Individual Type for 1 x T03 7.2°C/W Individual Type for 1 x T0126 17°C/W Individual Type for 1 x T0220 17°C/W <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>Sink 5F</td> <td>10 Sink 5F</td> </tr> <tr> <td>Sink TV2</td> <td>26 Sink TV2</td> </tr> <tr> <td>Sink TV3</td> <td>24 Sink TV3</td> </tr> <tr> <td>Sink TV4</td> <td>23 Sink TV4</td> </tr> <tr> <td>Sink TV5</td> <td>23 Sink TV5</td> </tr> </table>		Order Code	Case	Sink 5F	10 Sink 5F	Sink TV2	26 Sink TV2	Sink TV3	24 Sink TV3	Sink TV4	23 Sink TV4	Sink TV5	23 Sink TV5																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
W250 D167.5 H 68.5 (Chassis 153mm Deep)	1480 Case BIM3000 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Sink 5F	10 Sink 5F																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Sink TV2	26 Sink TV2																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Sink TV3	24 Sink TV3																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Sink TV4	23 Sink TV4																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Sink TV5	23 Sink TV5																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
<b>Plastic Boxes with Metal Lids - Boss Industrial Mouldings</b> Recessed Top Box ABS Base, C/W Brass Bushes, In Orange 1mm Aluminium Top Panel Finished Grey <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>L85 W56 D29</td> <td>97 Case BIM4003 OR</td> </tr> <tr> <td>L111 W71 D42</td> <td>130 Case BIM4004 OR</td> </tr> <tr> <td>L161 W96 D53</td> <td>182 Case BIM4005 OR</td> </tr> </table>		Order Code	Case	L85 W56 D29	97 Case BIM4003 OR	L111 W71 D42	130 Case BIM4004 OR	L161 W96 D53	182 Case BIM4005 OR	<b>Hardware</b> <b>P.C.B. Components</b> Data Pen, Blue Ink, Slow Drying <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>Pen 33PC</td> <td>92 Pen 33PC</td> </tr> </table>		Order Code	Case	Pen 33PC	92 Pen 33PC																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																				
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L85 W56 D29	97 Case BIM4003 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L111 W71 D42	130 Case BIM4004 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L161 W96 D53	182 Case BIM4005 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Pen 33PC	92 Pen 33PC																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
<b>Diecast Boxes - Boss Industrial Mouldings</b> Diecast Box and Flanged Lid Aluminium Box and Lid in Natural Finish <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>L113 W63 D31</td> <td>104 Case BIM5003 NA</td> </tr> <tr> <td>L152 W82 D50</td> <td>181 Case BIM5005 NA</td> </tr> <tr> <td>L192 W113 D61</td> <td>280 Case BIM5006 NA</td> </tr> </table>		Order Code	Case	L113 W63 D31	104 Case BIM5003 NA	L152 W82 D50	181 Case BIM5005 NA	L192 W113 D61	280 Case BIM5006 NA	<b>Hardware</b> <b>Fuseholders</b> Suit 20mm x 5mm Fuses <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>Fuse/H20B</td> <td>8 Fuse/H20B</td> </tr> <tr> <td>Fuse/H20C</td> <td>17 Fuse/H20C</td> </tr> <tr> <td>Fuse/H20PT</td> <td>77 Fuse/H20PT</td> </tr> <tr> <td>Fuse/H20P</td> <td>56 Fuse/H20P</td> </tr> </table>		Order Code	Case	Fuse/H20B	8 Fuse/H20B	Fuse/H20C	17 Fuse/H20C	Fuse/H20PT	77 Fuse/H20PT	Fuse/H20P	56 Fuse/H20P																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																														
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L113 W63 D31	104 Case BIM5003 NA																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L152 W82 D50	181 Case BIM5005 NA																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
L192 W113 D61	280 Case BIM5006 NA																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Fuse/H20B	8 Fuse/H20B																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Fuse/H20C	17 Fuse/H20C																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Fuse/H20PT	77 Fuse/H20PT																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
Fuse/H20P	56 Fuse/H20P																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
<b>Small Desk Consoles - Boss Industrial Mouldings</b> Slope Front Console, Recessed Top Two Piece All Aluminium Construction Ventilation Slots in Rear and Base Choice of 15° or 30° Sloping Front Off White Top Panel, Blue Base <table border="1"> <tr> <th>Order Code</th> <th>Case</th> </tr> <tr> <td>W105 O143 H32 (56)</td> <td>206 Case BIM6005 OR</td> </tr> <tr> <td>W170 O143 H32 (56)</td> <td>271 Case BIM6006 OR</td> </tr> <tr> <td>W170 D214 H32 (82)</td> <td>375 Case BIM6007 OR</td> </tr> </table>		Order Code	Case	W105 O143 H32 (56)	206 Case BIM6005 OR	W170 O143 H32 (56)	271 Case BIM6006 OR	W170 D214 H32 (82)	375 Case BIM6007 OR	<b>Hardware</b> <b>Fuses</b>																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																									
Order Code	Case																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
W105 O143 H32 (56)	206 Case BIM6005 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
W170 O143 H32 (56)	271 Case BIM6006 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		
W170 D214 H32 (82)	375 Case BIM6007 OR																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																		

- ACCESS
- BARCLAYCARD
- CASH
- CHEQUE

- FREEPOST ON ORDERS
- VAT INCLUSIVE PRICES \*
- ADD 30p P&P
- 24 HR TELEPHONE ANSWERING SERVICE

# GMT ELECTRONICS B

## Freepost Birmingham B19 1BR

★ DUE TO VAT INCREASE PLEASE ADD 5% TO ORDERS

### DIGITAL INTEGRATED CIRCUITS

4000 Buffered CMOS - High Speed  
5 - 15V 'B' Series, Up to 20MHz

7400 T.T.L.																			
HEF4000	14	HEF4046	100	HEF4514	250	N7400N	9	N7444N	83	N74122N	39	N74182N	60	N74LS28N	32	N74LS138N	85	N74LS253N	105
HEF4001	14	HEF4047	87	HEF4515	298	N7401N	11	N7445N	65	N74123N	37	N74184N	80	N74LS30N	16	N74LS139N	85	N74LS257N	104
HEF4002	14	HEF4048	28	HEF4516	30	N7402N	11	N7446AN	65	N74124N	32	N74185N	79	N74LS32N	24	N74LS153N	76	N74LS258N	107
HEF4006	95	HEF4050	28	HEF4517	382	N7403N	11	N7447AN	51	N74126N	32	N74188N	120	N74LS33N	32	N74LS154N	122	N74LS260N	300
HEF4007	14	HEF4051	69	HEF4518	69	N7404N	12	N7448AN	44	N74128N	74	N74199N	139	N74LS37N	24	N74LS155N	80	N74LS261N	300
HEF4008	80	HEF4052	72	HEF4519	55	N7405N	12	N7449N	12	N74130N	46	N74221N	160	N74LS38N	24	N74LS156N	80	N74LS266N	400
HEF4011	14	HEF4053	72	HEF4520	65	N7406N	25	N7450N	13	N74132N	46	N74222N	160	N74LS39N	24	N74LS157N	54	N74LS273N	130
HEF4012	14	HEF4056	37	HEF4521	188	N7407N	27	N7451N	13	N74134N	60	N74223N	116	N74LS40N	22	N74LS158N	54	N74LS274N	130
HEF4013	32	HEF4057	380	HEF4522	99	N7408N	27	N7452N	13	N74136N	15	N74224N	116	N74LS42N	53	N74LS159N	60	N74LS275N	116
HEF4014	84	HEF4068	14	HEF4523	120	N7409N	13	N7453N	13	N74138N	13	N74225N	116	N74LS44N	22	N74LS160N	120	N74LS280N	100
HEF4015	60	HEF4069	14	HEF4524	510	N7410N	11	N7454N	13	N74140N	26	N74226N	116	N74LS46N	16	N74LS161N	78	N74LS281N	100
HEF4016	35	HEF4070	14	HEF4525	110	N7411N	19	N7455N	15	N74142N	22	N74227N	116	N74LS48N	30	N74LS162N	130	N74LS282N	100
HEF4017	55	HEF4071	14	HEF4526	155	N7412N	17	N7456N	15	N74144N	22	N74228N	116	N74LS50N	45	N74LS163N	98	N74LS283N	100
HEF4018	65	HEF4072	16	HEF4527	78	N7413N	23	N7457N	23	N74146N	22	N74229N	116	N74LS52N	22	N74LS164N	78	N74LS284N	100
HEF4019	46	HEF4073	16	HEF4528	78	N7414N	46	N7458N	26	N74148N	26	N74230N	116	N74LS54N	16	N74LS165N	130	N74LS285N	100
HEF4020	88	HEF4075	16	HEF4529	386	N7415N	22	N7459N	26	N74150N	26	N74231N	116	N74LS56N	22	N74LS166N	78	N74LS286N	100
HEF4021	95	HEF4076	85	HEF4530	97	N7416N	23	N7460N	43	N74152N	54	N74232N	116	N74LS58N	33	N74LS167N	100	N74LS287N	105
HEF4022	82	HEF4077	14	HEF4531	171	N7417N	23	N7461N	63	N74154N	54	N74233N	116	N74LS60N	33	N74LS168N	100	N74LS288N	100
HEF4023	14	HEF4078	16	HEF4532	90	N7418N	26	N7462N	65	N74156N	74	N74234N	116	N74LS62N	45	N74LS169N	91	N74LS289N	100
HEF4024	45	HEF4081	16	HEF4533	73	N7419N	27	N7463N	23	N74158N	54	N74235N	116	N74LS64N	45	N74LS170N	200	N74LS290N	100
HEF4025	14	HEF4082	16	HEF4534	62	N7420N	22	N7464N	30	N74160N	74	N74236N	116	N74LS66N	45	N74LS171N	91	N74LS291N	100
HEF4027	32	HEF4085	64	HEF4535	110	N7421N	22	N7465N	60	N74162N	74	N74237N	116	N74LS68N	65	N74LS172N	128	N74LS292N	100
HEF4028	52	HEF4086	64	HEF4536	119	N7422N	22	N7466N	63	N74164N	74	N74238N	116	N74LS70N	65	N74LS173N	100	N74LS293N	100
HEF4029	60	HEF4093	50	HEF4537	217	N7423N	11	N7467N	63	N74166N	74	N74239N	116	N74LS72N	65	N74LS174N	100	N74LS294N	100
HEF4030	46	HEF4094	175	HEF4538	119	N7424N	21	N7468N	74	N74168N	74	N74240N	116	N74LS74N	65	N74LS175N	100	N74LS295N	100
HEF4031	200	HEF4104	166	HEF4539	119	N7425N	21	N7469AN	48	N74170N	134	N74241N	116	N74LS76N	65	N74LS176N	100	N74LS296N	100
HEF4035	110	HEF4107	45	HEF4540	119	N7426N	21	N7470N	48	N74172N	111	N74242N	116	N74LS78N	65	N74LS177N	100	N74LS297N	100
HEF4040	68	HEF4505	571	HEF4109	140	N7427N	22	N7471N	68	N74174N	63	N74243N	116	N74LS80N	65	N74LS178N	100	N74LS298N	100
HEF4041	75	HEF4508	51	HEF4113	140	N7428N	21	N7472N	88	N74176N	63	N74244N	116	N74LS82N	65	N74LS179N	100	N74LS299N	100
HEF4042	54	HEF4510	70	HEF4115	119	N7429N	12	N7473N	88	N74178N	165	N74245N	116	N74LS84N	65	N74LS180N	100	N74LS300N	100
HEF4043	79	HEF4511	110	HEF4119	117	N7430N	40	N7474N	148	N74180N	69	N74246N	116	N74LS86N	65	N74LS181N	100	N74LS301N	100
HEF4044	84	HEF4512	98	HEF4121	117	N7431N	79	N7475N	23	N74182N	65	N74247N	116	N74LS88N	65	N74LS182N	100	N74LS302N	100

### LINEAR INTEGRATED CIRCUITS

CA3011	92	NE529K	162
CA3018	75	RC4136	130
CA3020	191	TBA1205	79
CA3028A	86	TCA580	346
CA3046	76	TC4730	450
CA3048	245	TC4740	450
CA3080E	70	TDA108	326
CA3089E	253	TDA1022	648
CA3130E	90	TDA1028	338
CA3140E	38	TDA1029	338
CA3189E	26	TDA1038	217
LM301AN	30	TD2581	266
LM308N	95	TD2640	292
LM318N	200	TL081CP	75
LM319N	218	TL084CN	146
LM324AN	110	UA709C1	40
LM339N	71	UA709CN	40
LM381N	110	UA710CN	41
LM381AN	180	UA711CN	65
LM382	120	UA711CT	42
		UA711CN	18
		UA747CN	50
		UA748CN	35

### OPTO ELECTRONICS

Light Emitting Diodes, Individual	Order Code
.125" (3mm) Red	14 COY54
Green	17 COY95
Yellow	19 COY97
Panel Mounting Clip to suit.	3 LED3 Clip
2" (5mm) Red	15 COY24A
Green	17 COY94
Yellow	19 COY96
Panel Mounting Clip to suit.	5 LED5 Clip
Light Emitting Diodes - 7 Segment Display	Order Code
3" (7.6mm) C, Anode R.H. Decimil Pt.	160 XAN3061
Red	33 XAN165N
C. Anode R.H. Decimil Pt.	199 XAN3051
Green	
C. Cathode R.H. Decimil Pt. Red, Low current drain	160 XAN3074
6" (15.2mm) C, Anode L.H. Decimil Pt. Red	230 XAN6620
C. Anode L.H. Decimil Pt. Green	230 XAN6520
C. Cathode L.H. Decimil Pt. Red	230 XAN6640
Decimil Pt. Red	
Photoreistors	Order Code
DRP12	90 DRP12
ORP61	90 ORP61
Phototransistors	Order Code
OCPT1	180 OCP71
BPX25	175 BPX25
BPX29	175 BPX29
Photocoupler	Order Code
FCDB20	150 FCDB20

### SWITCHES

Miniature Toggle - Honeywell	Order Code
SPDT	2A/250V A.C., 5A/28V D.C.
SPDT C/Off	58 SW 8A1011
SPDT Double Bias To Centre	87 SW 8A1021
SPDT Single Bias To Centre	75 SW 8A1041
SPDT Bias	75 SW 8A1051
DPDT	70 SW 8A1061
DPDT C/Off	86 SW 8A2011
DPDT Double Bias To Centre	92 SW 8A2021
DPDT Single Bias To Centre	102 SW 8A2041
DPDT Bias	102 SW 8A2051
	96 SW 8A2061
Miniature Push - C & K	Order Code
SP Push To Make, Momentary	0.5A/250V A.C., 1A/28V D.C.
SP Push To Break, Momentary	54 SW 8531
	54 SW 8533
Slide - Switchcraft	Order Code
DPDT Standard Actuator	36 SW 46206
DPDT Slot Actuator, Voltage Change, Marked 110/240	43 SW 46206F

### SEMICONDUCTORS

Diodes	Order Code
IN827	193
IN814	4
IN916	5
IN4001	4
IN4002	4
IN4003	5
IN4004	6
IN4005	7
IN4006	7
IN4007	8
IN5402	15
IN5404	16
BA138	27
8B1064B	132
8B1127	61
BY127	35
8Y206	34
8YX10	19
DA47	10
DA90	7
DA91	7
DA200	9
OA202	9
MicroWave	
BAV95D	1091
CL895C	2592
CX111C	1280

### SEMICONDUCTORS

Rectifier Bridges	Order Code
1A 400V S.I.L.	93 BY179
1A 60V S.O.L.	84 BY164
1.5A 100V D.I.L.	33 VM18
1.5A 400V D.I.L.	35 VM48
1.5A 100V	45 W01
1.5A 400V	52 W04
2A 100V	89 VS148
2A 400V	109 VS448
6A 100V	143 VH448
6A 400V	183 VH448
10A 100V	172 VJ148
10A 400V	201 VJ448
15A 100V	215 VL148
15A 400V	226 VL448
30A 100V	242 VK148
30A 400V	280 VK448
S.C.R.'s	
4A 400V	54 C106D
12A 400V	108 TIC126D
Triacs	
10A 500V	124 BT138-500
15A 500V	177 BT139-500
23A 500V	492 BTW41-500

### MAINS TRANSFORMERS

Order Code	
Secondaries may be connected in series or parallel to give wide voltage range	
Primaries 0-220, 240V	
6VA - Clamp Type Construction	
Approx. 18% Regulation, F.C. 54, H36, W35	
0-4.5V, 0-4.5V Secondaries	220
0.5V, 0.6V	45
0.12V, 0.12V	120
0.15V, 0.15V	150
0.20V, 0.20V	200
20VA - Clamp Type Construction	
Approx. 16% Regulation, F.C. 70, H48, W46	
0-4.5V, 0-4.5V Secondaries	335
0.6V, 0.6V	60
0.12V, 0.12V	120
0.15V, 0.15V	150
0.17.5V, 0.17.5V	175
0.20V, 0.20V	200
55VA - Clamp Type Construction	
Approx. 10% Regulation, F.C. 92, H64, W57	
0.6V, 0.6V Secondaries	540
0.12V, 0.12V	120
0.15V, 0.15V	150
0.20V, 0.20V	200
0.30V, 0.30V	300


### Zener Diodes

Order Code	
400mW C4V7-C33	
BZY88/BZX79 + Voltage	8
1.3W C7V5-C75	
BZK75 + Voltage	16

### Transistors

2N929	37	2N4427	206	BC478
-------	----	--------	-----	-------

# Monitor

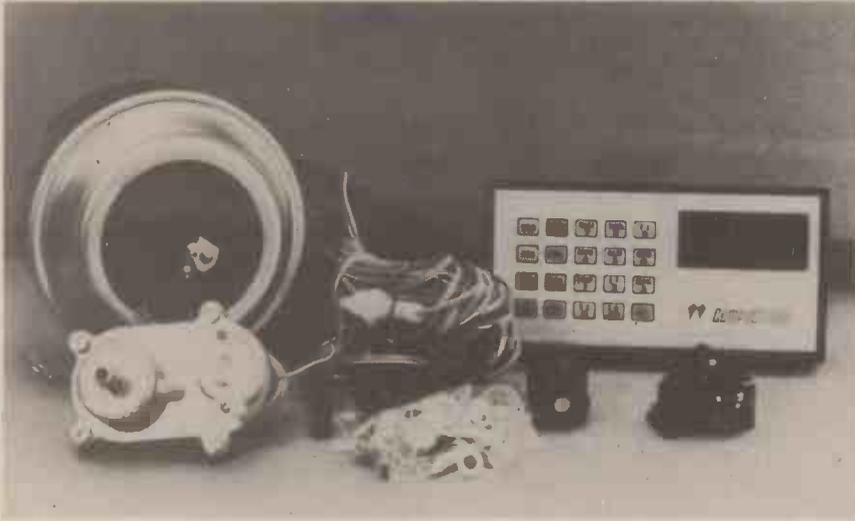

## IT TELLS THE TIME TOO

Without devoting the whole of Monitor to this new device it would be impossible to describe it fully. Anyway we'll have a go at outlining some of its more unusual functions. It's called the "Compucruise—On Board Electronic Computer!" It has 26 different functions, so many in fact that we wonder if things haven't got a little bit out of hand. The main feature is the Cruise control, this will establish and maintain a pre-selected speed, it has a memory that will recall the last setting should the accelerator or brake pedals be used. The next bit comes under the heading Fuel Management, it will inform the driver his or her most efficient driving speed, the best brand of petrol to use and the effects of different types of tyres, pressures etc. would you believe? If that little lot isn't enough it also incorporates a highly accurate Quartz digital clock/stopwatch/alarm/calendar.

Now for the mundane features, temperature

gauge, inside, outside or engine temperature. Battery voltage indicator, generator voltage etc. Time to tank empty, current speed, average speed, it goes on, you'll just have to take our word it does about a million other things too.

All this information is updated once a second from a variety of remote sensors. The "Command Module," measuring 3 inches by 6 inches will sit quite happily on the dashboard of most cars. It can be fitted to nearly any car in about 3 hours (not diesel or fuel injection engines though) requiring the minimum of calibration. Cost, well you wouldn't expect to get much change from a fiver would you? It's actually not as bad as you would think, £173 plus VAT and fitting. Compucruise is currently available from Macpro Ltd, The Coach House, Birdingbury Road, Frankton, Warwickshire CV23 9QR. Who said motoring was getting boring?

## TOOL TIME

Plastic tweezers have never been given the publicity they deserve so we at HE are beginning a campaign to highlight the usefulness of plastic tweezers to the electronic hobbyist. We're starting our campaign by introducing you to the new range of plastic tweezers from Tele-Production Tools Ltd, their range includes three different jaw sizes, coarse, medium and fine serrations. The in-built guides ensure that the faces mate correctly. The tweezers are available in small quantities for about 60 pence, they are particularly useful for handling components that are liable to damage from static discharge.

To obtain your tweezers write to Tele-Production Tools Ltd, Stiron House, Electric Avenue, Westcliff-on-Sea, Essex SSO 9NW.

## COVER STORY

Our thanks to Relcy Antiques of Nelson Road, Greenwich, for being so patient when we took the cover shot. We would also like to point out that they do not sell Grandfather clocks with LED displays. Mind your shop is well worth a visit if you are interested in "scientific" antiques.

## COMMODORE CALCS

New book from Commodore on how to choose your Calculator, one of theirs of course. Nevertheless it makes very interesting reading. Your nearest Commodore stockist should be able to furnish you with a copy. The book covers all of the new range of Commodore machines and there should be something for everyone.

## CASIO'S COMEBACK

We must admit, we were slightly worried about the lack of calculators in the past few months, particularly from our friends Casio, who could be relied to bring out at least two new specimens per month.

We need not have worried, the reason for Casio's disappearance was because they were busily beavering away developing the FX-501P and FX-502P programmables. (Wonder what the bloke who thinks up these names does with the other 23¾ hours of his day?)

Starting with the 501, we have 5 levels of parenthesis, 11 memories and 128 programme steps. The 502 is twice the calc. with 10 parenthesis levels, 22 memories and 256 programme steps. Both live in cases 140x76x16mm, 1300 hours continuous use, auto switch-off, full scientific functions . . . yawn . . . etc., etc.

You guessed it, the cassette recorder connects up to both models via a low cost adaptor. Within the calculators lurks a musical IC that enables a programme to be written and read on to and off of standard cassette tape. Now for the price list. As usual there are recommended retail prices, totally unrealistic as they're always sold cheaper somewhere or other. From the top we have the 501 at £64.95 and the 502 £84.95. The adaptor (FA-1) can be yours for a miserable £24.95. Casio can now be found at 28 Scrutton Street, London, EC2A 4TL and will be only too happy to relieve you of any surplus money you may have.





## SIX DIGIT HAND HELD


Just about everything these days is available in hand-held version, frequency counters are the latest to succumb. This model, called the Max-550, will handle up to 550 MHz on a 6 digit display. The counter is crystal controlled (of course) giving an accuracy of 3 parts in  $10^6$  on signals down to 250 mV. (That means it's very accurate to the likes of you and me.)

Typical applications include audio, video and RF in-circuit testing, checking clock

frequencies in digital systems, ultrasonic equipment in fact anywhere something electrical is happening many times a second. A full range of accessories includes a miniature aerial for direct radio reception, input cable carrying case, AC charger and an adaptor for use with a car battery. The Max-550 can be yours for £93.00 plus VAT. Available from Continental Specialities Corp, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
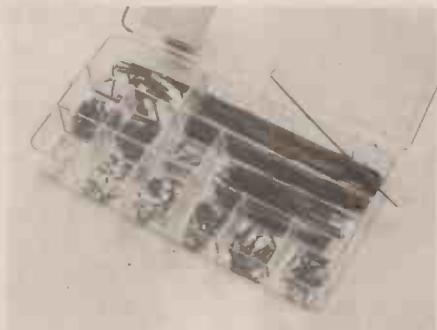
## WIRELESS?

For any of you following Ian Sinclair's new series "Into Linear ICs" you'll have noticed he's using a "Eurobreadboard" to explain much of the theory. This kit of jumper wires might just come in handy. It's intended for use with the Letrokit breadboard. The kit contains 350 wires and comes in a neat plastic box with individual compartments. 14 different lengths are supplied in the kit, the smaller ones conform to the almost standard 0.1 inch matrix. The longer lengths extend up to 5 inches. All the different lengths are colour coded, and each length has stripped ends, bent to 90° for instant insertion. For further details contact: Letrokit Ltd, Sutton Industrial Park, London Road, Earley, Reading, Berks.



## MEETINGS IN MARGATE

Electronics is usually considered to be a solitary pursuit, it needn't be, especially if you happen to live in the Margate area. Dr Ken Smith of the University of Kent has written to tell us about a new club called the Thanet Electronics Club that he's involved with. They meet every Thursday evening at 7.30 pm at the Quarter Deck. Girls are very welcome too he assures us. And so they should be too, just wish a few more would write to us at HE. This sounds like an excellent opportunity for anyone in the Margate area to meet up with a few soulmates, so why not go along one evening? We would like to hear from any other clubs too. How about it?

## FREE RADIO

Supporters of Free Radio, Jackie, Ingrida, Caroline et al might be interested in a convention on either the 13th or 20th (write for confirmation) of October. Both days are Saturdays, the venue will be in Wellington, Telford. The tickets will cost £6.00 and will include food etc. There will be talks, discussions, and slide shows from the people in the know and the possibility of a disco later in the evening. The meeting place will be the Wellington YMCA, we're told it's within respectable distance of the local watering holes so there should be something for everybody. The address to write to is: Caroline News Sheet (CNS) POB, 35 Wellington, Telford, Salop. And please enclose a SAE.

## HOME COMPUTING

We must apologise for the lack of Home Computing this month, believe it or not there just wasn't room. The situation has become quite serious lately, we might just start thinking about a few extra pages soon in order to get everything in. It's interesting to compare HE with the competition, do you realise what good value we are? Just count up how many editorial pages some of the other magazines have, most of them cost an extra 5 pence! We would be very surprised if any of them have as many as us.

## CATALOGUE CORNER

Chromasonics have sent us a supplement to their '79 catalogue, it contains all their updated prices, no they are not all increases you'll be surprised to learn. A quick glance revealed the ZN414 radio chip from Ferranti going at 2 for £1 can't be bad. For your copy contact Chromasonic at: 56 Fortis Green Road, Muswell Hill, London N10 3HN

## COMPETITION


The entries are flooding in now for our picture competition, the closing date for entries is the 20th August so get them to us as soon as possible as we're still having difficulties with the post.

## ERRATA

A gremlin crept into the Injector/Tracer project last month, the overlay diagram Fig 2 was shown 180° out of registration. The shaded PCB foil pattern is in fact the wrong way up. Hope this has not caused too many problems.
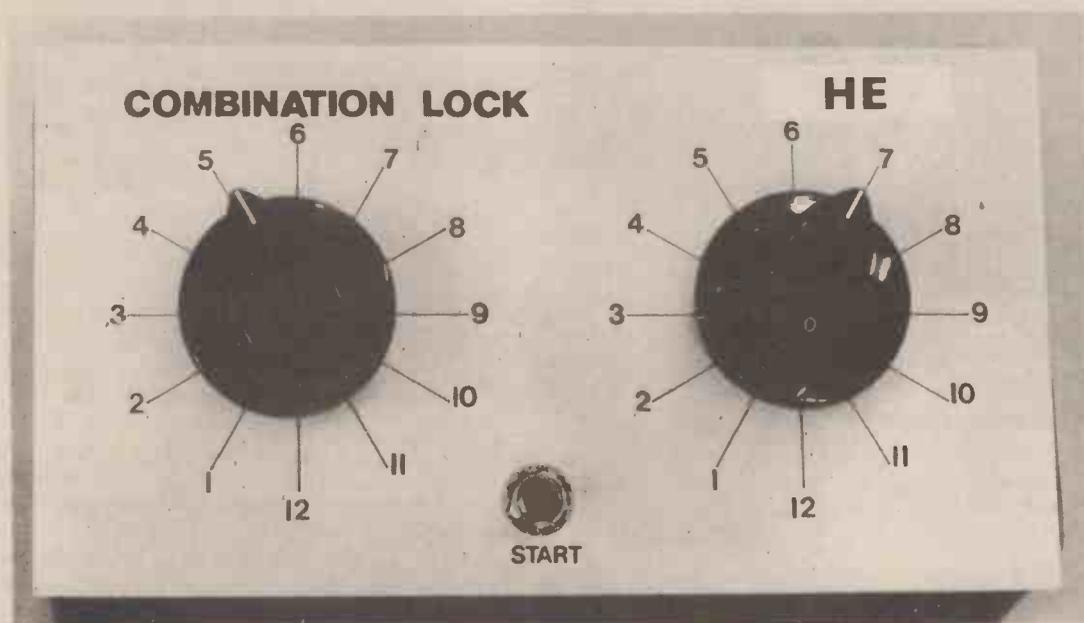
# Combination Lock

*Mechanical combination locks abound — as do ideas for electronic ones. Unfortunately, electronic designs we've seen are either too simple (and of limited use) or too complex — and beyond the average hobbyist. Here's something that's in between these two extremes.*



DIGGING THROUGH THE files produced a wealth of ideas for locks — most of them impractical for the constraints imposed on the project application. Tossing ideas around the office threw up some fascinating techniques . . . . But we had to get a simple project together.

The simplest method is to connect several rotary switches in series to apply power to a solenoid-operated door lock when you dial up the right switch position on each. This has the advantage of extreme simplicity and a reasonable number of possible combinations. Problem is, if you leave that combination set on the switches then security is compromised because somebody, less trustworthy than your good self, may just take notice, Tch, tch.

What was needed was some technique that was self-cancelling or did not reveal the combination once it was 'dialled up.'

It occurred to us that the rotary numerical combination lock, such as on safes (you know — spin the dial, 13 left, 37 right, 21 left), did not reveal the complete combination once the lock was opened.

Having digested that little principle the next thing was to work out how to do it electronically — and in a simple way.

The rotary numerical combination locks operate by successively unlatching a mechanical 'circuit'. When the last combination is dialled the bolt is released. How to do this electronically?

## LATCHING CIRCUITS

A number of 'latches' connected in series and operated in sequence such that power is applied to a solenoid lock when the last latch is selected will be an electronic equivalent to the mechanical combination lock. Next problem — the electronic latch. This can be made up in a number of ways. Relays can be connected to latch on when energised. But they're relatively expensive. Digital logic gates can also be connected to make a latch.

When a silicon controlled rectifier (SCR) has a voltage applied to the gate it will conduct and remain 'on' until the anode-cathode voltage falls to zero. That's a latching operation. SCR's are cheap and readily available and will

handle the current required to operate a solenoid lock and for these reasons were chosen for the latches in this project.

To dial a sequence of numbers, providing the required combination, we first considered a multi-bank, multi-position switch. That turned out to be mechanically awkward and expensive. Suitable switches are also difficult for the average hobbyist to obtain. Two, 12-position, single-pole rotary switches were eventually chosen. They are an 'off-the-shelf' item obtainable from many component outlets.

Dialling three pairs of numbers in sequence on the switches simulates the operation of a rotary numerical combination lock — almost. This provides over 1.7 million combinations!

## RESETTING

That solves the combination problem and the latch problem, but how do you reset the SCRs once you've operated the lock? Simple — turn off the power source. A switch could be used to momentarily disconnect the supply, 'unlatching' the SCRs, resetting the solenoid lock to await its next use.

What if you forget to push the button? Tch, tch, tsc . . .

It seems a peculiarity of human nature that it is easy to memorise a sequence of numbers but very difficult to remember to reset a button or lock.

A simple timer operating a relay can do the job for you. Accordingly, the project has a timer incorporated.

The project is designed to operate from a battery. No current is drawn until the START button is operated. Current will only be drawn from the supply for the 25 seconds duration of the timer.

Mains operation, from a small transformer and rectifier is possible but a battery standby circuit should be included in case of mains power failure.

## SOLENOID LOCKS

There are two basic types: solenoid operated striker plates (i.e.: that are fixed in the door jamb) and solenoid operated bolts (attach to the door itself). We recommend you use a solenoid operated striker plate. Firstly, as they are fixed in the door jamb it is an easy matter to conceal all wiring. Secondly they may be used with existing dead-latching mortice locks. Solenoid operated bolt locks are made to fix on the door itself and require a flexible lead run across the door at the hinged side.

Solenoid operated striker plates or bolt locks are available from specialist locksmiths.


As the project operates from a 12 volt supply, a 12 volt version was used.

For new installations the key barrel of a lock may be dispensed with. In existing locks, the key mechanism may be disabled if you wish.
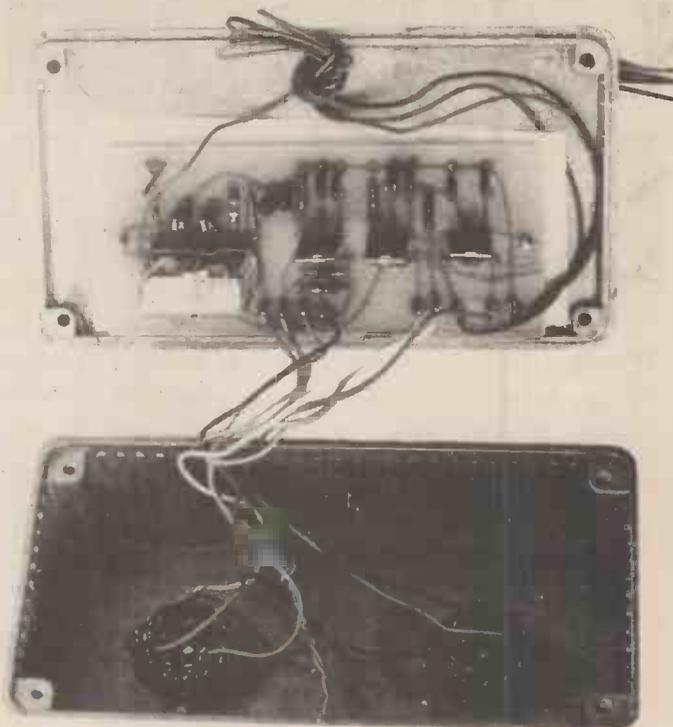
## CONSTRUCTION

The relay and all minor components are mounted on a printed circuit board. For convenience, and to avoid wiring errors, this method of construction is recommended.

Commence by putting all the resistors and capacitors on the board. Take note of the orientation of the tantalum capacitors. Next mount the transistors, diodes



*Interior of the lock. A diecast box provides a rugged and safe housing.*

and SCRs — take note of lead orientation, carefully follow the component overlay diagram. Mount the relay last.

All external connections are made via pc pins inserted in the appropriate holes on the board. To avoid wiring errors, follow a sequence of wiring the connection from each pin, step by step.

Wiring a 'code' on the switches is a fairly simple process. Using the table below, allocate switch position

*This shows how the connection of wires A to C and A' to C' determine the combination of the lock. The above table shows the connection pattern for the combination 4-1, 1-11, 8-4 which can be seen by looking at the switch contact numbers corresponding to A, A', B, B', C and C'.*

SW1 pos no	pc pin	SW2 pos no	pc pin
1	B	1	A'
2		2	
3		3	
4	A	4	C'
5		5	
6		6	
7		7	
8	C	8	
9		9	
10		10	
11		11	B'
12		12	

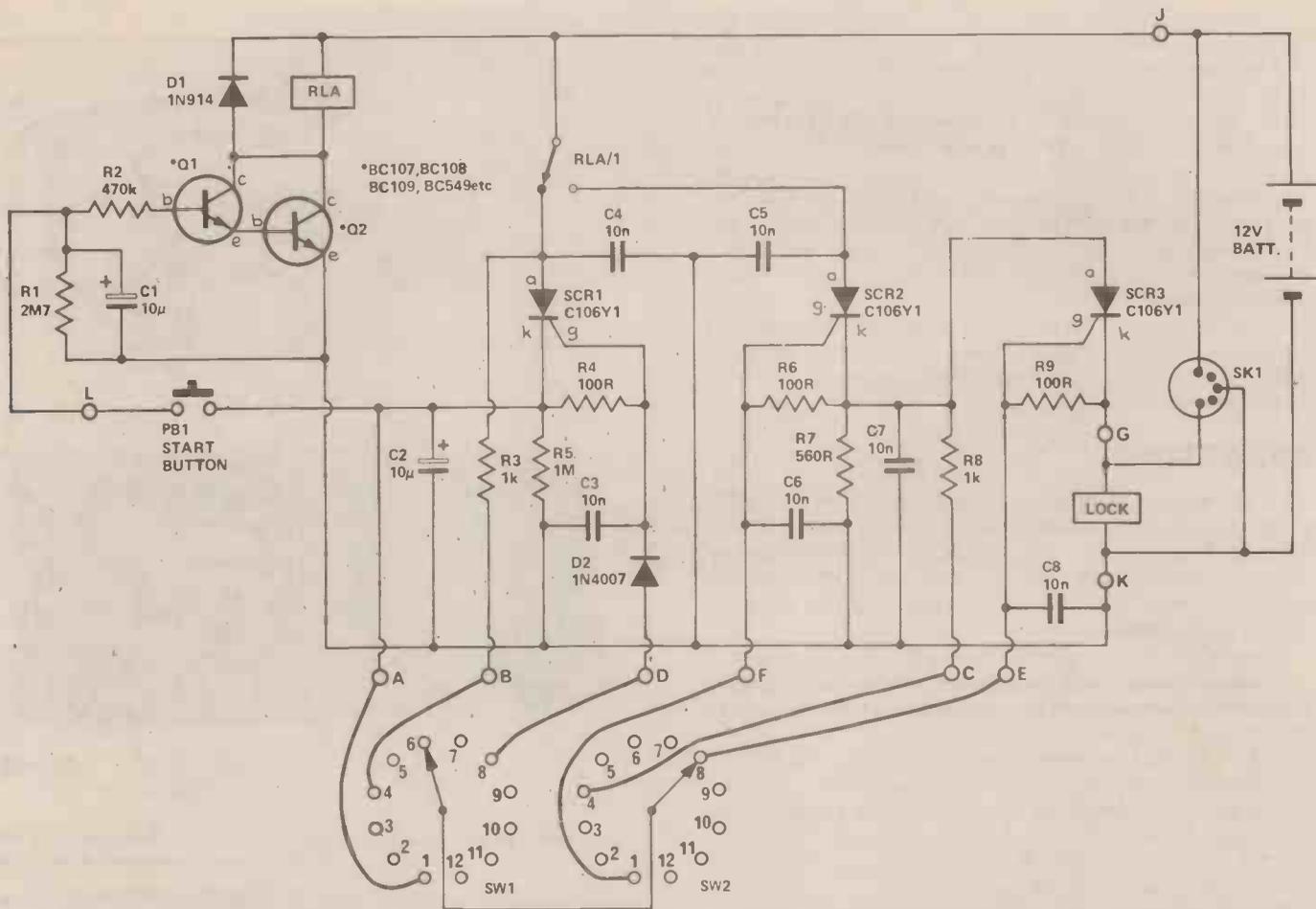


Fig. 1 The circuit diagram, SW1, SW2 and PB1 have to be operated in the correct sequence before the lock will open. Any deviation in sequence will result in the lock remaining secure

## How It Works

An 'initial' code is dialled on SW-1 and SW-2, 4 and 1 in this case. The gate of SCR1 will be forward biased via R5, SW-1, SW-2 and D2, SCR1 turns on, charging C2 to 12 volts.

The push-button PB1 is then pressed. This applies 12 volts from the cathode of SCR1 to the junction of R1/R2. Capacitor C1 will quickly charge to 12 V Q1 and Q2 will turn on, operating the relay RLA. The circuit involving Q1, Q2, R1, R2, C1 and the relay is a 25-second timer. The relay will drop out after about 25 seconds as C1 will slowly discharge via R1, R2 and the input impedance of Q1, Q2, which is very high. The rest of the sequence must be completed within 25 seconds to operate the lock for when RLA drops out, the circuit is 'reset'.

When PB1 is pressed and RLA operates, the relay contacts, RLA1, will then transfer the 12 V supply from the anode of SCR1 to the anode of SCR2. SCR1 will turn off. C2 will then commence to discharge via R7, falling to a volt or so within 10 seconds. The next code sequence must be dialled within this period, otherwise you will have to return to the 'initial' code.

The second code is then dialled on SW-1 and

SW-2, in this case 1 and 11. The gate of SCR-2 will then be forward biased via SW-1 and SW-2, the current it draws will discharge C2. SCR2 will then turn on, applying 12V to the anode of SCR3.

The third code is then dialled on SW-1 and SW-2, in this case 8 and 4. The gate of SCR3 will then be forward biased via R10, turning SCR3 on, energising the solenoid lock. At the end of the 25-second delay, the relay will drop out, resetting the circuit.


An external connection socket, SK1 is provided to enable power to be supplied to the lock should the circuit fail or the batteries run flat.

No current is drawn by the circuit until the operating sequence is commenced.


Diode D1 suppresses operating transients from the coil of the relay and D2 prevents possible spurious triggering of SCR2 and SCR3 via the gate of SCR1 when the latter is turned on.

The circuit is protected from spurious triggering by bypass capacitors C3 and C8 and the SCR gate resistors, R6, R8 and R11.


# Combination Lock

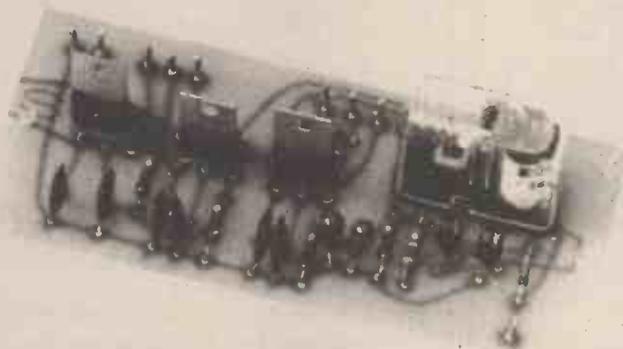

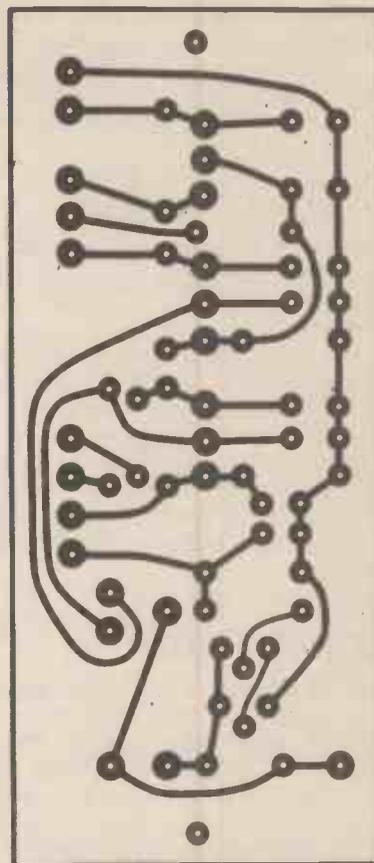The printed circuit board and solenoid striker plate we used. Naturally any type of solenoid lock can be protected using this system.



PCB artwork shown full size.

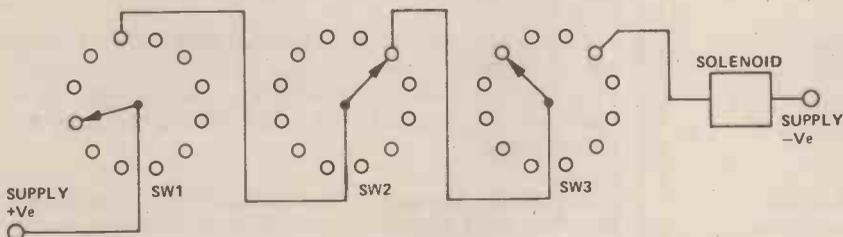

A simple lock using three rotary switches. If you forget to move them off the combination after opening the lock, you'll reveal it.

Fig. 2 The component overlay. See Table 1 and the circuit diagram for an explanation of the lettered AC pins.

## Parts List

### RESISTORS (ALL 1/4 W, 5%)

R1	2M7
R2	470k
R3	1k
R4	100R
R5	1M
R6	100R
R7	560R
R8	1k
R9	100R

### CAPACITORS


C1, 2	10u 25V tantalum
C3-8	10n greencap

### SEMICONDUCTORS

SCR1-3	C106Y1 or C106D1
Q1, 2	BC107, BC108, BC109 or BC549 or equivalent
D1	1N914
D2	1N4007

### MISCELLANEOUS

SW1, 2	1 pole 12 way rotary
PB1	miniature push to make
RLA1	single-pole change-over 12V 180 ohm coil, 240V/5A contacts
SK1	DIN 5-pin or similar
Solenoid-operated lock	(see text), 12V battery, pcb: diecast case.

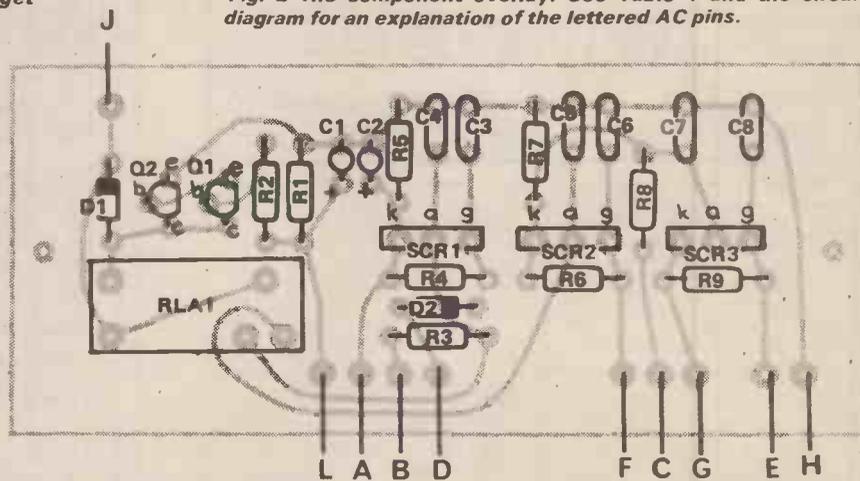

# Combination Lock

pairs for SW1 and SW2 for each code in the three-step sequence necessary to open the lock.

For example, the code sequence of switch position pairs as shown in the diagram is 4-1, 1-11, 8-4. These are respectively shown connected to pc pins A-A', B-B', C-C'.

## INSTALLATION

As this will very much depend on individual circumstances, we can only give you general guidelines.

Firstly, there must be no externally exposed, or visible, wiring. The switches should be mounted such that their shafts protrude from the surface behind which the circuitry is mounted, without the shaft securing nuts being accessible. File a flat on the shafts so that you have a permanent 'location' point for knob grub screws. Better still, use collet knobs.

The external power/connection socket should be placed in a concealed location, known and accessible only to yourself, or those entrusted with the combination.


## OPERATION

1. Dial the 'initial' code. As illustrated in the circuit, turn SW1 to 4 and SW2 to 1.
2. Press the push button, PB1.
3. Dial the second code. As illustrated, turn SW1 to 1 and SW2 to 11. You have less than 10 seconds to do this.
4. Dial the third code. Turn SW1 to 8 and SW2 to 4, as illustrated.
5. The solenoid lock will release.
6. Twenty-five seconds after operating PB1, the circuit will reset and the lock will return to its latched condition.

HE
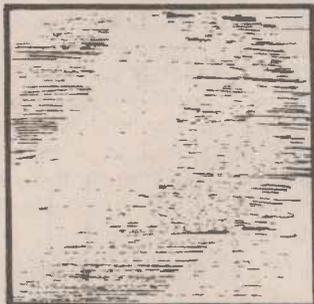
## Buylines


There should be no problems in obtaining any of the components used in the Combination Lock.



BONK!



# Hobbyprints

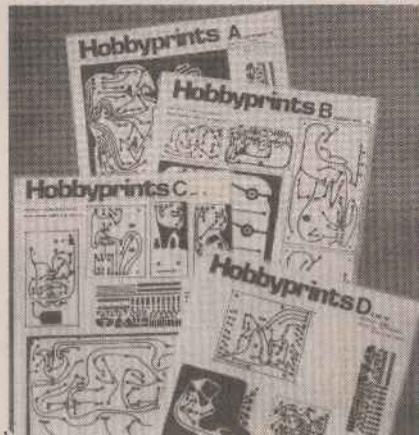

We're just etching to tell you about HOBBYPRINTS, we know you won't be able to resist them. They're so good we've even patented the idea (1445171 and 1445172). If you're board with all those untidy strip boards or semi-permanent bread boards then read on.

After many months of extensive research we think we've come up with the ideal solution (Ferric Chloride?) to all of those problems people have with making really professional PCBs. (Puns come at no extra charge).

Seriously though, the HOBBYPRINT rub-down transfer, (very similar to the rub-down lettering) is the answer to the project builders prayer. PCBs take up a disproportionate amount of time, using HOBBYPRINTS a typical PCB can be finished in under half an hour. Because HOBBYPRINTS are produced from our original artwork there's no likelihood of making a mistake. They can even be used as photographic masks for ultra-violet PCB production.

Each sheet of HOBBYPRINTS contains all the PCBs for any particular month (an average of four PCBs), so for only 75 pence including VAT and Post and Packing that's not bad value. For a list of projects refer to back numbers ad.

## ORDER TODAY


Send cheque or postal order (payable to Hobby Electronics) to:

**HOBBYPRINTS,  
HOBBY ELECTRONICS,  
145 CHARING CROSS ROAD  
LONDON WC2H 0EE.**

**75p INCLUSIVE OF VAT AND POSTAGE.**

Please mark the letter(s) of the HOBBYPRINTS on the outside of the envelope.

# CLEVER DICK

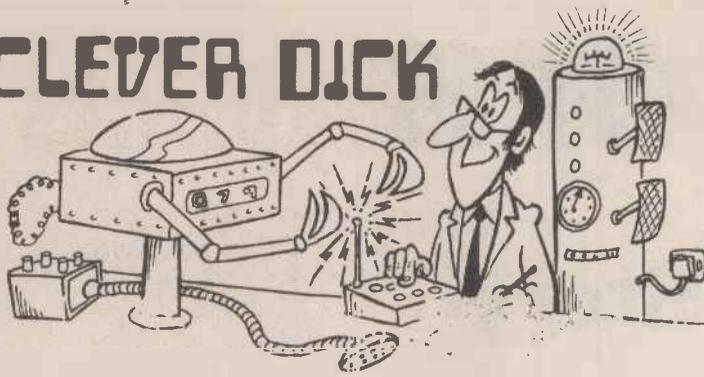

***It's all down to the energy crisis this month, don't worry though, Hobby Electronics is guaranteed energy saving, no batteries, no wires and no connections to be made.***

WHAT WITH ALL THIS energy crisis business it's to be expected that someone would write in with a request for some kind of solar heating circuitry, Congratulations to Mr N. Shapped for being the first.

Dear HE,

*Could I make a suggestion? With the current interest being shown in energy saving, a useful constructional project would be a circuit for the control of a solar energy system.*

N. Shapped  
Anglesea

Well Mr Shapped, we would be only too happy to publish such a circuit but for one thing. We have heard from reliable sources that the gases used as aerosol propellants are breaking down the upper layers of the atmosphere. This will cause what the experts call the 'Greenhouse effect'. In short the temperature of the earth will steadily rise, making solar heating somewhat redundant. With this in mind we were thinking of developing some kind of Greenhouse effect detector, trouble was we had nothing to calibrate it with.

Two letters this month concerning 'Kit Review' (most unusual). They both happen to be about the June review of the Sparkrite Electronic Ignition, though each makes a different point. The first is from Mr N. Allister of Lichfield, Staffs.

Dear HE,

*Having read the Kit review on the Sparkrite Ignition kit an idea sprang to mind. I am keen on motorcycles, unfortunately I can only afford small capacity bikes.*

*Motorcycles are usually fitted as standard with contact breakers. These are not very reliable and can cost quite a bit to replace. Several companies are now coming out with contactless systems for multi-cylinder bikes, rather pointless for a humble one cylinder machine. (Pun intended.) Anyway these systems use an ordinary LED, the light source being interrupted at the appropriate moment during the ignition cycle and triggering the ignition. I would like to see an article on how to make such a circuit. I hope you give this letter some thought and publish such a circuit in the near future.*

N. Allister  
Staffs

The second is from Mr George Tworkowsky (we think) of Gwent, he poses a somewhat different question.

Dear Sir,

*I read your article 'Kit Review' with great interest. It really is a pity that you did not carry out some detailed tests. I have had some experience with electronic ignition. In two years my own specimen failed three times, this I considered dangerous so I disposed of it. I noticed that my fuel consumption had actually increased with the electronic ignition. A friend brought a Sparkrite with similar results, his cold starting did not improve, still needing four or five attempts before his car would start. I think that electronic ignition has still got a long way to go before it can beat a conventional system. To have any advantage a completely new system is required, not an adaptation to a conventional ignition.*

G. Tworkowsky  
Gwent

To Mr Allister we must say we would love to publish such a circuit, the trouble is there are so many different bikes around at the moment it would be literally impossible to come up with a 'universal' fitting to suit everyone. Sorry.

Now to Mr Tworkowsky. Unless, as you suggest extensive and exhaustive laboratory type tests are carried out, results will be purely subjective. Two things, however, must be borne in mind. An electronic ignition system cannot improve a badly tuned car, wrongly adjusted tappets for instance. The second thing to remember is that the contact breakers should not wear at anything like the rate of conventional points. That means the points will retain their optimum (hopefully) setting longer, hence improving fuel consumption, and at nearly £1.30 per gallon every little helps. Don't forget that cold starting should also improve, simply because an electronic ignition system will continue to operate satisfactorily at a much lower voltage.

That's about it for this month. We would just like to say thank you to everyone who took the trouble to write in with suggestions for a new name for the column. We've decided to keep it as 'Clever Dick' simply to avoid confusion. Keep your letters coming in to Clever Dick, we'll try to answer as many as possible, it's good to know that such a column was needed judging by the amount of mail we're receiving.

# Thyristors

## The Great Gate Story

*Thyristors often seem to be the poor relation as far as electronic components go, especially these days with new digital ICs appearing almost daily. We would like to dispell any rumours here and now, the thyristor is alive and well, doing things that only they can do. Ian Sinclair looks at this versatile semi-conductor and a few of its unique features.*

IF YOUR ELECTRONICS interests are in Hi-Fi, or short-wave reception, chances are you'll never have any need to use a thyristor. There's an awful lot of other branches of electronics, though, in which these devices are extremely useful, so let's take a look at how the thyristor works, what it does, and the sort of circuits that are used.

Unlike the ordinary transistor, a thyristor has four layers of semi-conductor material (Fig. 1). Connections are made to the outer layers of this sandwich, and these are called the anode and the cathode connection. One of the middle layers is also connected to a terminal, called the gate.

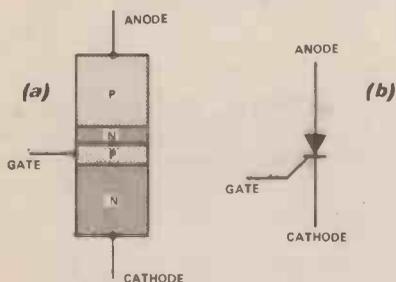


Fig. 1. Four-layer arrangement (a) and the thyristor symbol (b).

How does it work? Imagine the four layers split up as shown in Fig. 2a. This now looks like two transistors (Fig. 2b) connected in series — one a PNP type, and the other NPN. More important, there are connections from

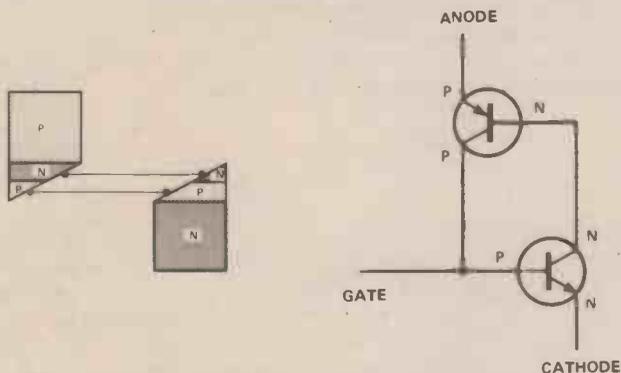


Fig. 2. Two-transistor equivalent (a) as layers, (b) as separate transistors.

the collector of the PNP to the base of the NPN, and from the collector of the NPN to the base of the PNP — that means 100% positive feedback. Using this transistor arrangement as a guide, let's see what we would expect to happen as voltages are applied. One thing has to be added though — the connection to the electrode which behaves like the gate has a bit of resistance in series (Fig. 3), and that makes quite a difference.

With the emitter of the PNP transistor positive and the emitter of the NPN negative, no current will flow when the "gate" voltage is low. Since the "gate" connection is to the base of an NPN transistor, no current will start to flow until the voltage on the box is something like 0.5 V positive to the emitter of the NPN transistor. With the base of this transistor at the same voltage as the emitter, then, there's no conduction in either transistor. Either transistor? Well, you see, the collector of the NPN transistor will be at supply voltage when no current flows, and that keeps the PNP type shut off — a PNP transistor doesn't conduct until its base voltage is **less** than its emitter voltage. Fig. 3 shows a "load" resistor dotted; there's no resistor deliberately placed there but leakage through the semiconductor serves the same purpose.

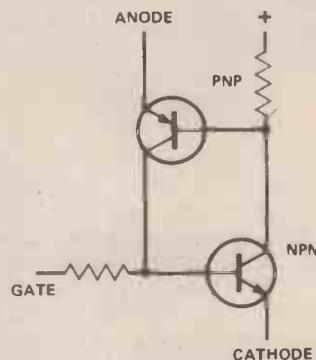


Fig. 3. The equivalent circuit, with gate resistance added.

### GATE RESISTANCE

When the base input voltage rises to around 0.5 V, then, the NPN transistor conducts, its collector voltage drops, making the PNP transistor conduct, and current flows from the emitter of the PNP transistor all the way to the emitter of the NPN one.

This is where the resistance at the "gate" input comes in. When the transistors conduct, the collector voltage of the PNP transistor goes high, keeping the base voltage of the NPN one high. If the input voltage goes low now, some of the current from the PNP transistor will flow through the input resistor, but the base of the NPN transistor will still be kept high enough to ensure that current keeps flowing. This is why the thyristor doesn't shut off. In fact, small thyristors can be shut off if the supply voltage is low by taking the gate voltage negative, so that the voltage at the base of the NPN transistor drops below 0.5 V.

## PEAK CURRENT

There aren't two separate transistors, of course, so what do we look for when we select a thyristor? One obvious factor is the maximum voltage which we can use across the thyristor when it is switched off. This ranges from around 15 V to over 800 V according to the type that is chosen. Note, though, that these voltages are **peak**, so that if you want to use a thyristor with 240 V AC you need a 400 V type to hold off the peak AC voltage.

The next thing to look for is the peak current rating. Many manufacturers quote  $I_{TSM}$  — meaning the peak current flowing for a once-only pulse when the thyristor is triggered on. The repetitive peak current (on every cycle) is symbolised as  $I_{TRM}$ , and is quite a bit less.

The gate trigger current, in milliamps, is labelled  $I_{GT}$  and is usually measured at 25°C — it gets less at higher temperatures. The maximum value for reliable triggering is usually quoted, ranging from about 200  $\mu$ A for a small thyristor to 30 mA or more for a large one. The actual trigger current is often a lot less — I have triggered a small thyristor at 8  $\mu$ A.

$V_{OT}$ , as the letters suggest, means the gate voltage (maximum) which will ensure triggering. This ranges from 0.8 V for a small thyristor to 1.5 V for a large one — once again most samples will trigger at lower values.

Finally, the quantity  $I_N$  is the holding current — at any greater value of current between anode and cathode, the thyristor is guaranteed to keep conducting once triggered. Values range from 5 mA to 40 mA, and, as usual, most samples will stay conducting with quite a bit less.

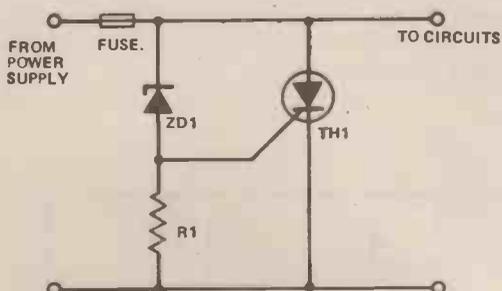


Fig. 4. A crowbar protection circuit.

The thyristor therefore behaves like a diode — but only when the voltage at the gate has set the layers of semiconductor conducting. With the gate connected to the cathode, a thyristor is simply an open circuit, no current can flow in either direction unless, of course, the voltage ratings of the thyristor are exceeded. When the gate voltage is increased sufficiently above the cathode

voltage — about 0.5 V or so — the thyristor will suddenly become conducting, provided the anode is positive relative to the cathode. In this state, the thyristor is said to be triggered. If the anode voltage is zero or negative, or if the gate voltage is too low, no triggering takes place, and the thyristor remains non-conducting. Let's look now at a circuit which makes use of what we know already about the thyristor. Fig. 4 shows what is called a crowbar circuit — it's designed to shut off the power to a circuit very quickly.

This is a thyristor which is normally non-conducting, with its gate connected to zero volts through R1 and to the positive supply through ZD1, a zener diode. You're not too certain about a zener diode? Well, it's a diode which is used reverse biased, but because of its construction it will suddenly conduct at some voltage, usually in the range 2.7 V to 33 V, which is decided when the diode is made. In this circuit, the diode has been selected so that it breaks down at 5.6 V.

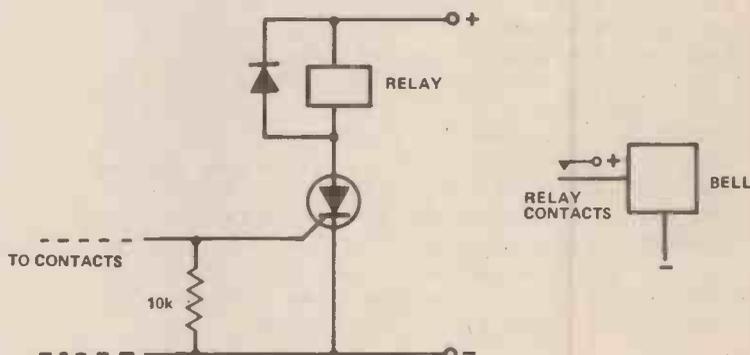


Fig. 5. Burglar alarm basic circuit — the bell cannot be connected directly to the thyristor because each stroke of a bell interrupts the current; this would shut off the thyristor.

## FAST FUSE

Now the normal voltage output of this circuit is 5.0 V, and it's intended to supply a lot of IC's whose supply voltage must not rise much above 5.6 V. What happens if the voltage does get too high? Simple — ZD1 conducts and triggers the thyristor. The thyristor can then conduct, shorting out the power supply and causing the fuse to blow. Once the fuse has blown, there's no voltage in the circuit, and the thyristor instantly resets, ready to resume protection duty when the fault that caused the trouble is sorted out.

Now it may look a bit daft using a thyristor to blow a fuse, but it has two important advantages. The most obvious one is the fuses don't blow just because the voltage rises, so that the fuse doesn't protect the circuit against excessive voltage, it only protects the power supply against excessive current. The other point is that a fuse takes some time to blow, several milliseconds. That may not sound like a long time, but several hundred pounds worth of IC's can be destroyed in only a thousandth of that time. The thyristor operates faster, getting the voltage down as soon as it reaches danger level, and blowing the fuse so that some attention is called for. The name "crowbar" circuit is a good one — the action is pretty much the same as that of putting a crowbar across the supply voltage!

To change output voltage, just switch in another zener diode! The output is not easy to smooth to an acceptable standard for most electronics equipment, but is ideal for battery charging or running lights or motors.

The main application for thyristors, however, is the control of lamps or motors, using the gate to control at what part of the wave the thyristor switches on. Fig. 10 shows how this operates when the supply to the thyristor is a full-wave rectified voltage. If the thyristor is turned on at the start of each wave, the output is at full power — the average value of voltage of such a wave is equal to 63% of peak voltage. If the thyristor is turned on at a later part of the wave, the average value of voltage of the output wave is less, down to nearly zero if the thyristor is switched on very late. This is, incidentally, one of two methods of control, the other will be discussed later.

## TRIGGERING

The problem now is to trigger the thyristor at the correct part of each cycle. One simple method is to use a capacitor and resistor to delay the rise of voltage at the gate. Fig. 11 shows the simplest type of circuit possible, a capacitor connected across the gate, and a resistor feeding the capacitor from the rectifier supply. As the supply voltage rises from zero, following the shape of a half-wave of AC, the voltage across the capacitor will rise much more slowly, so that the gate voltage does not rise high enough to trigger the thyristor until the supply voltage is quite a bit above zero. We can alter the time (after the wave starts from zero) at which the thyristor fires by altering the time constant of the firing circuit. Unless we discharge the capacitor again, however, the thyristor may fire too soon on the next wave, so that D1 is used to ensure that the capacitor discharges when the supply voltage drops at the end of the wave.

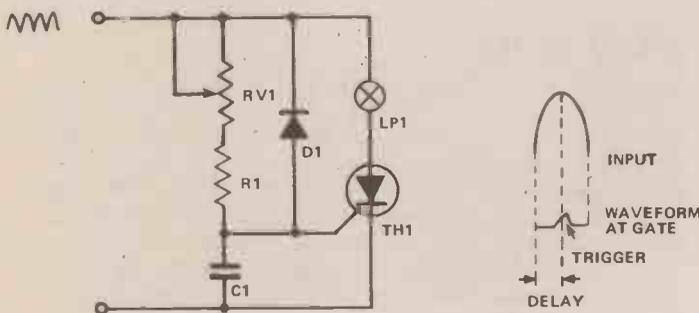


Fig. 11. Simple CR low voltage phase control. Because of the time that C1 takes to charge, the voltage at the gate reaches trigger level some time after the input voltage starts to rise. The delay can be adjusted by altering the setting of RV1. D1 discharge C1 when the input voltage drops to zero again.

One snag of this simple circuit is that the current passing through the charging resistor may not be enough to fire the thyristor, if the resistor is a large value and the thyristor gate needs a large (1 mA or so) current. Most small thyristors will fire with a gate current of a few  $\mu\text{A}$ , but the larger types may need quite a bit more.

A method of overcoming this is the trigger diode — a device which is non-conducting until a few volts are applied between anode and cathode (Fig. 12), and which then becomes fully conducting, with only a small voltage drop. Using such a trigger diode, the voltage across the capacitor (Fig. 11) builds up until the voltage across D2 is enough to breakdown the trigger diode.

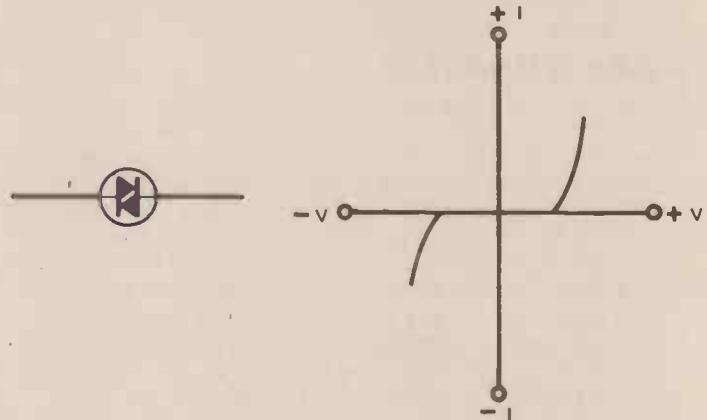


Fig. 12. Trigger diode. (A) symbol (B) characteristic

## LOW VOLTAGE

With the diode fully conducting, the voltage at the gate is more than enough to trigger the thyristor, and gate current is provided by discharging C1 rather than by the small current through R1.

A version of this basic circuit suitable for low voltage supplies is illustrated in Fig. 13. A transistor takes the place of the trigger diode making use of the principle that a transistor will pass a large current from collector to emitter when a small current passes from base to emitter. The capacitor C1 is connected to the base of Q1, so that base current will start to flow when the capacitor has charged to about 0.5 V. The base current causes collector current, so that the emitter voltage rises along with the base voltage. When the emitter voltage rises to about 0.5 V (the base will by this time be at about 1.0 V), the thyristor fires.


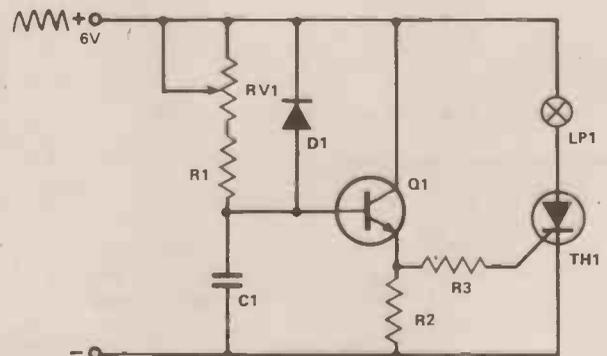


Fig. 13. Using a transistor for triggering a low-voltage circuit.


If the load is AC operated (such as a shaded-pole motor, for example) the circuits used so far do not appear useful because they are based on rectified AC. However, the circuit is still a circuit, whether a rectifier is used or not, and the load can just as easily be connected in the AC part of the circuit (Fig. 14). In this example, the firing of the thyristor completes the circuit, so switching the current on. The change of position of the load from the DC to the AC side of the circuit does not alter the action of the thyristor.

So far, all the circuits we have looked at have been low voltage circuits, for which ordinary low voltage

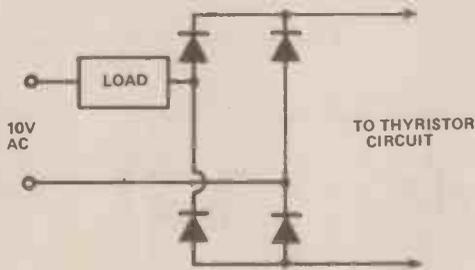

**Fig. 14.** Using an AC load and a bridge rectifier circuit. The thyristor circuits of Figs. 11 or 13 can be used if the voltage is low.

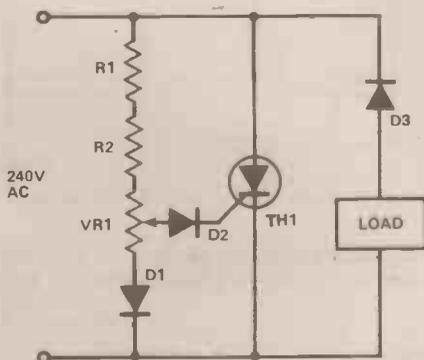components and construction methods are suitable. Many thyristor and triac control circuits, however, make use of AC mains voltages, for which a number of special precautions need to be observed. One essential point is electrical safety. In a mains circuit, the thyristor is connected between the load and one of the mains leads, usually neutral. Since the gate must have a fairly low resistance to the cathode, this means that all the electrodes of the thyristor are connected to mains, and


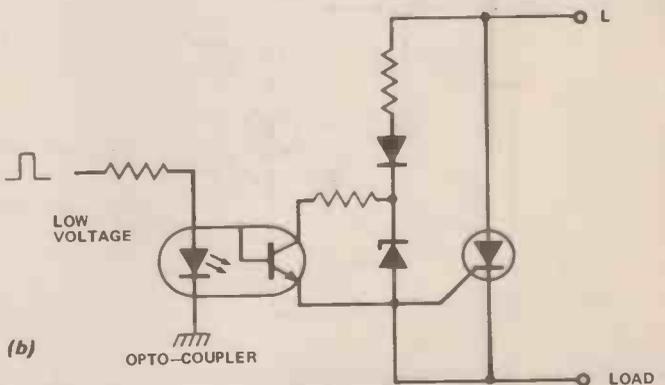


**Fig. 15.** Mains-voltage power control. All parts of the circuit can be at a dangerous voltage.

any firing circuit of the simple type will also be connected to the mains.

Great care must therefore be taken when these mains voltage circuits are isolated from any low voltage circuits and that no mains voltage points can be touched. In the simple power control circuit of Fig. 15, for example, widely used for electric drill or light bulb control, the potentiometer control knob must be well insulated — one useful method is to use a potentiometer with a plastic shaft, with the circuit fitted into a plastic box.

Particular care has to be taken when a heat-sink is needed for the thyristor because the insulators which serve well for mounting power transistors to heat sinks are not good enough for mains voltages. A mains-operated thyristor should never use a metal box as a heat sink — if cooling is needed, the thyristor should be mounted on a finned heatsink mounted on substantial insulators inside a ventilated box.

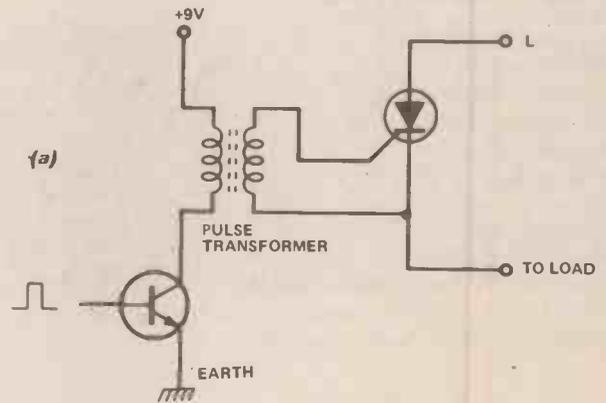

**Fig. 16.** Isolating the firing circuit from the thyristor. (a) Using a pulse transformer. (b) Using an optoisolator. With either device, the insulation between the circuits can be good enough to withstand several thousand volts.

## ISOLATION

Several applications of mains-voltage thyristors and triacs involve driving the gate with signals from low voltage equipment — typical applications include disco lights. There are two safe ways of isolating the thyristors from the low voltage equipment — pulse transformers

Now applications for thyristors such as the crowbar circuit are very useful, but they represent only a fraction of the possible uses. Fig. 5 shows in outline, for example, how a thyristor could be used in a burglar alarm circuit — the point is that the bell will keep on ringing once the thyristor has been triggered, until the power is cut off. Some care is needed, incidentally, in the uses of this circuit. Small thyristors need very little gate current to trigger them, around 1  $\mu$ A, so that a long lead attached to the gate of a thyristor will pick-up any electrical disturbance (next door washing machine, for example) unless a resistor is connected between gate and cathode. Once again, we are making use of the thyristor as a device which can be switched on by a small and brief change of voltage, but which cannot be switched off the same way. Anything that behaves in this way is called a latching device. Now we can connect up relays so that they will latch, but a thyristor is self-latching — this type of behaviour is built in to the thyristor.

## NEGATIVE PULSE

Suppose we **want** the thyristor to stop conducting? it happens, some small thyristors **will** switch off when the gate voltage is pulsed negative, but this is not a reliable way of switching off. Switching off, as far as most thyristors are concerned must be done by reducing the voltage between anode and cathode to a very low value. Once this minimum value, the minimum holding voltage, has been reached, current stops. Unless the gate voltage is kept high, the current will not start to flow again when the anode returns to a positive voltage.

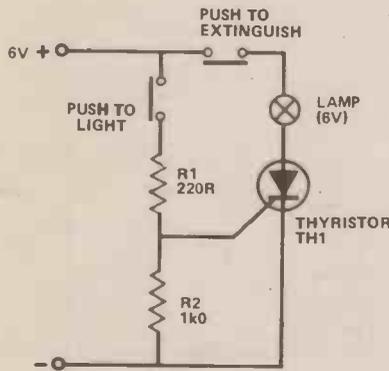


Fig. 6. Simple low-voltage light-switch circuit.

One obvious way to do this, of course, is to interrupt the supply momentarily, as shown in the low voltage lamp circuit of Fig. 6. A less simple method consists of discharging a capacitor at the anode of the thyristor, as shown in Fig. 7. In this circuit, the thyristor is triggered by the action of the push button switch — note the 1k resistor (R2) which prevents the gate from being triggered by stray radiated pulses. Once the thyristor has

been triggered on, there is a low-resistance conducting path between anode and cathode, so that the voltage across the thyristor is low, not much above the minimum holding voltage at which the thyristor switches off.

The switch-off method uses a large-value capacitor C1 which charges up when the thyristor conducts. During the time that the thyristor conducts, the capacitor has one plate at supply voltage and the other at the low voltage of the thyristor anode. When the OFF switch is momentarily depressed, the plate of the capacitor which was at supply voltage is suddenly connected to Zero volts. The other plate will follow it, dropping from about 0.2 V to a negative voltage for a few milliseconds. This is time enough to allow the electrons and holes in the N and P layers of the thyristor to clear and the thyristor becomes non-conducting. By the time the capacitor has re-charged through the load, the thyristor is off.

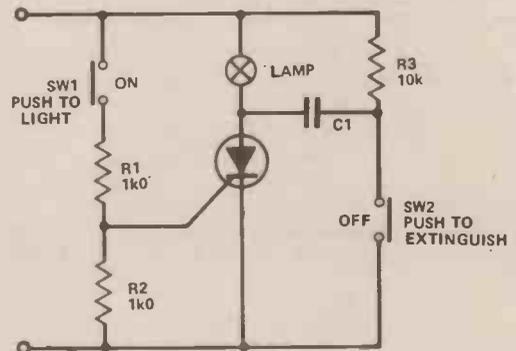


Fig. 7. Using a capacitor to switch off a thyristor.

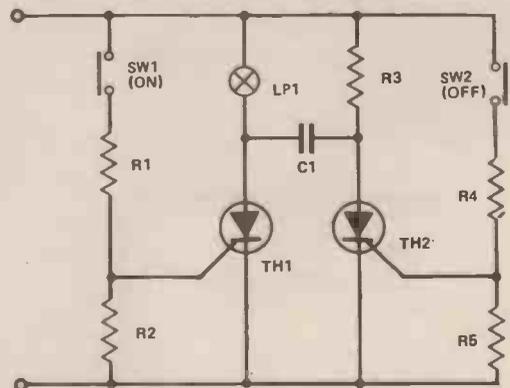


Fig. 8. A two-thyristor switching circuit. The capacitor C1 is connected so that when one thyristor switches on, the other is forced off.

## BACK TO BACK

This method works well when the load has a fairly high resistance (such as a low voltage lamp) and when a large

value capacitance can be used. The capacitor should be a paper or plastic type, because electrolytics do not take too well to having their plates at reverse polarity, which will happen if the OFF switch is kept closed while the capacitor re-charges through the load. A variation of this method uses two thyristors switching each other (Fig. 8).

Thyristors really come into their own, however, when they can be used with a supply which passes through zero volts at regular intervals. An alternating voltage fits this specification nicely, but a rectified unsmoothed supply is even better. The reason is that a thyristor will pass current in one direction only, so that to cope with AC we need two thyristors, or the ready-made two-thyristor device known as the Triac.

Using an unsmoothed rectified supply ensures that the thyristor will turn off each time the voltage reaches zero (or a fraction of a volt above zero). We don't need any special switch-off circuit, but on the other hand we have lost that rather useful latching action. To keep the thyristor conducting we must either keep a current flowing into the gate, or apply a pulse each time the anode voltage starts to rise.

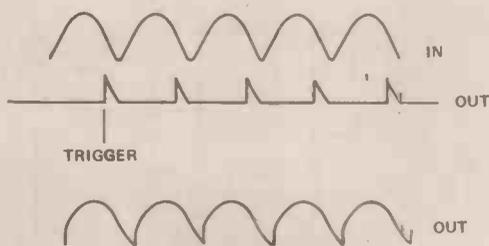
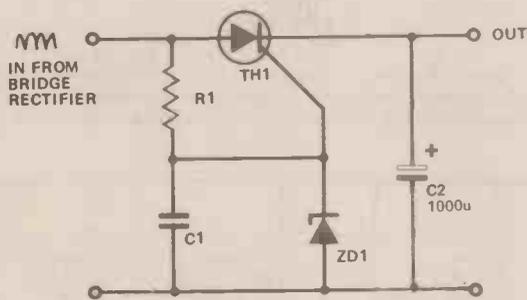


Fig. 9. A simple voltage regulating circuit. If this is used as a better charger (for lead-acid batteries only), C2 can be omitted.

A very simple circuit making use of this principle is shown in Fig. 9. This is a voltage adjuster, which enables you to obtain several switched values of DC voltage from a transformer without using toppings. It's particularly useful for lead-acid (car or motorbike) battery charging, as the voltage is so easy to charge. The

principle is that the zener diode, which may be one of several selected by a switch, applies a steady voltage, equal to the zener diode voltage, to the gate of the thyristor. At the anode of the thyristor, the waveform is a full-wave-rectified wave from the bridge rectifier. The cathode of the thyristor is connected to the reservoir capacitor C2, a large value electrolytic rated at the full peak voltage of the transformer secondary.

To see what happens, imagine that the peak voltage of the rectified wave is 25 V and that we have a 15 V zener diode. When the circuit is first switched on, capacitor C2 is uncharged, so that the cathode voltage of TH1 is zero. When the voltage at the anode starts to rise, the thyristor will not conduct right away, because C1 has to be charged up first. As C1 charges, however, TH1 will switch on, so that current flows, charging C2 to the full peak voltage.

## LOADING

Now if there is no load resistor connected across C2, the thyristor will not conduct again even if it is triggered because the anode voltage will not be any higher than the cathode voltage. Any normal power supply is used with a load, however, so that we can assume that the voltage across C2 will drop quite a bit between the time of the first voltage peak and the next one. If the voltage across C2 is higher than the zener diode voltage, though, the thyristor will not trigger, and the next voltage pulse does not cause the thyristor to conduct.

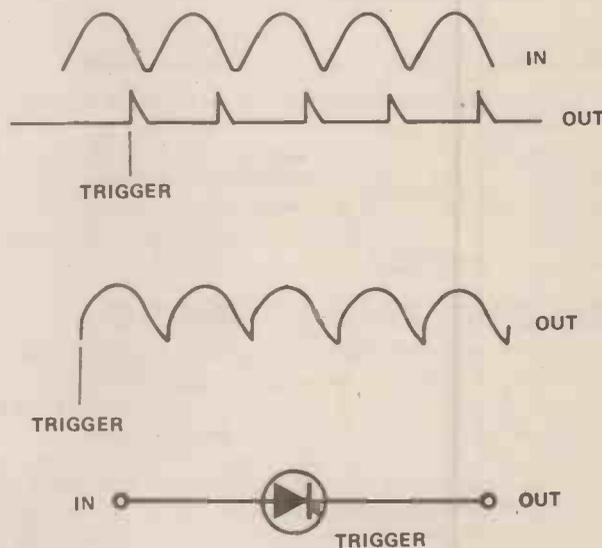


Fig. 10. Phase control of a wave. The average voltage at the output depends on how late in the cycle the thyristor is triggered.

This continues until the output voltage drops to less than the voltage of the zener diode. When this happens, the thyristor will start to conduct whenever the anode voltage is higher than the cathode voltage, and the reservoir capacitor C2 will once again be charged to the full peak voltage. The thyristor will conduct every now and again; enough to keep the average voltage at the output fairly steady at around the zener diode voltage.

# Thyristors

and opto-isolators, illustrated in Fig. 16. Pulse transformers can be obtained which have insulation guaranteed to 4 kV, but which will fire even a large thyristor when a pulse is applied to the primary. Opto-isolation provide smaller output powers, but can be used to trigger a small thyristor which then fires the main thyristor. Great care must always be taken with disco light equipment, because faulty insulation in such equipment is responsible for an increasing yearly total of deaths caused by electrocution.

The other type of problem which is encountered when thyristors are used with mains voltages is that of radio frequency interference (RFI). When a thyristor switches on suddenly at or near the peak of a wave, a large pulse of current flows, and the steep-sided wave is very rich in harmonics. Such a wave is radiated easily from all the wiring around the thyristor, and interferes badly with radio, particularly on the lower frequencies. The long wave radio-4 transmissions, in particular are badly affected by thyristors in TV receivers, in light dimmers, drill speed controllers and other thyristor power circuits.

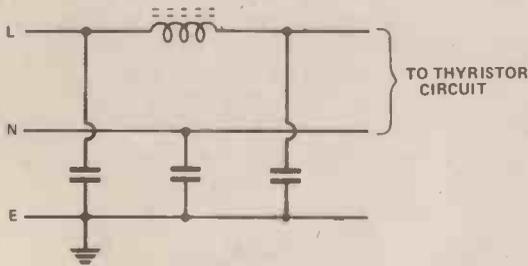


Fig. 17. Reducing radio-frequency interference (RFI).

Complete elimination of RFI is difficult, but a considerable reduction in interference is possible if RF chokes and filter capacitors are fitted into the circuit (Fig. 17). These generally consist of inductors constructed with several turns of insulated wire (typically about 40 turns) on a ferrite rod, with 0.01  $\mu$ F capacitors to earth on each side of the inductor.

## ZERO VOLTAGE CROSSING

A different approach to the problem of interference, and to thyristor control, is the zero voltage crossing control system. This can be used only when the load has a lot of energy storage, such as a large heater, because the idea is to switch the thyristor on when the wave is at zero volts, to keep the thyristor on for several cycles, and then to keep the thyristor off for another few cycles. In this way (Fig. 18) the power can be controlled by varying the ratio of the number of "on" cycles to the number of "off" cycles. Obviously, this is useless for loads such as lights or drill motors, but for loads such as heaters which do not charge noticeably when power is removed for several cycles this method has a number of advantages. For one thing, since there are no sudden switch-on pulses, greater amounts of power can be switched. Because the switching occurs at the zero crossing points of the wave, there is no RFI. The only penalty is a more complex circuit due to the need to generate a pulse when the wave passes through zero, and to time a number of cycles on and another number off. Fortunately, integrated circuit zero-voltage crossing controllers can be obtained from Feranti and from Plessey among other

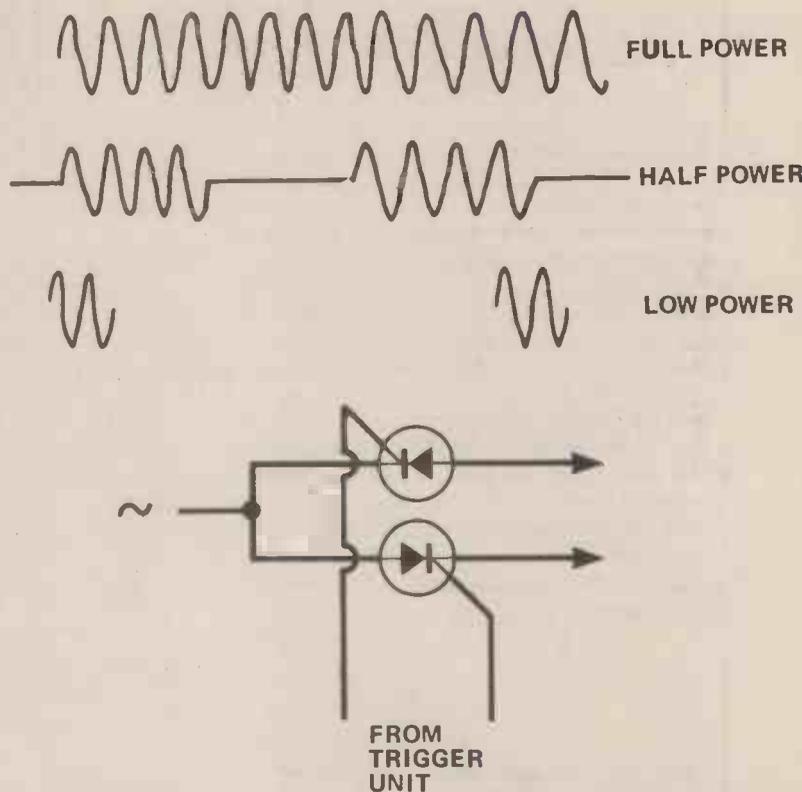


Fig. 18. Zero-crossing control — the thyristor is always switched on just at the zero-voltage level. For full-wave control as shown, two thyristors or a triac would have to be used.

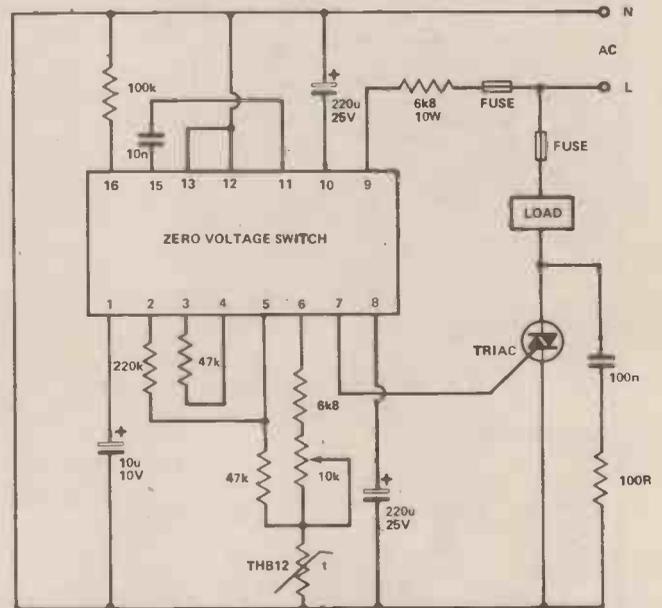


Fig. 19. A zero-crossing switch circuit used for temperature control. Note that all points can be live. (Courtesy of RS Components Ltd).

manufacturers. Fig. 19 shows the circuitry used with a zero-crossing type of circuit controlling a triac. In general, triacs are used on purely AC circuits, with thyristors being used on DC or rectified AC supplies. When very large amounts of power are to be controlled, thyristor bridges can be used when no triac of suitable power rating is available.



**20 x 20 WATT STEREO AMPLIFIER**  
Viscount IV unit in teak simulate cabinet Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input sockets 20 x 20 watts RMS 40 x 40 watts peak for use with 8 to 15 ohm speakers  
Size 14 1/4" x 3" x 10" approx. **NEW feature**—units now includes £31.90  
a built in four channel stereo sound facility. £3.00 p&p

**30x30 WATT AMPLIFIER IN KIT FORM**

For the experienced constructor complete in every detail, same facilities as Viscount IV, but with 30x30 output 60x60 watts peak. For use with 2 15 ohms speakers  
**£31.50** p&p £3.00



**SPECIAL OFFER**

**30 x 30 WATT AMPLIFIER KIT**  
with BSR P200 belt drive deck and Shure M75 cartridge. **£57.00**  
+ p&p £6.00

**EMI SPEAKER BARGAIN**

Stereo pair 350 lit. System consists of 13" x 8" approx. woofer with rolled surround, 2 1/2" approx. Audax tweeter, crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS. 20 watts max 8 ohm impedance.



**£15.25**  
Per stereo pair  
£3.65 p&p

**BSR P200**

Belt drive chassis turntable unit semi automatic, cueing device. **£25.50**  
p&p £2.60


A.D.C. QLM 30 Mk III Magnetic Cartridge to suit. **£7.95**



**BSR** Manual single play record deck with auto return and cueing level, fitted with stereo ceramic cartridge 2 speeds with 45 r.p.m. spindle adaptor ideally suited for home or disco use. **£11.25** p&p  
OUR PRICE £2.75

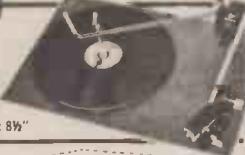**GARRARD DECK MODEL CC 10A**

Record changer with cueing device fitted with stereo ceramic cartridge ready to fit into your own plinth. **£8.15** p&p £2.05 Size 12" x 8 1/2"



**UNIT AUDIO STAND**

Can be used with TV too! Finish in chrome with decorative wood spacer fitted with 4 Kenrick Mini Meteor castors. **£3.95** £1.50 p&p



**BARGAIN FOR PERSONAL SHOPPERS ONLY**  
**Altone UA4 Stereo System**

Features 8 watt total output. Full size BSR manual turntable with cueing and auto return. Socket for tape in and out and stereo headphones complete with speakers. **£35.25**

**Micro Cassette Recorder**

Pocket size—home or office use or when travelling. **£14.25**

**Battery operated fluorescent camping lamp.**

Runs off 8 U2 batteries. **£4.80**

# Mullard

## AUDIO MODULES IN BARGAIN PACKS

CURRENT CATALOGUE  
PRICE &  
AT OVER **25**  
PER PACK

SEE OUR PRICES

- 1** PACK 1 2 x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input. OUR PRICE p&p £1.00 **£5.00**
- 2** PACK 2 2 x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs. OUR PRICE p&p £1.00 **£7.65**



ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS.

**ACCESSORIES**

Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance **£3.00**  
plus £1.50 p&p

**Two Way Speaker Kit**

Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. **£4.05**  
per stereo pair plus £1.55 p&p

AVAILABLE ALSO TO PURCHASERS OF THE 10 + 10 AMPLIFIER KIT

**10 + 10 AMPLIFIER KIT**

An opportunity to buy a 10 watts per channel stereo amplifier kit which is suitable for use with a ceramic cartridge. The amplifier utilises proven Mullard modules and is available at a very competitive price. The amplifier kit comes complete with instructions and includes: a Mullard LP1183 stereo preamplifier module, two LP1173 power amplifiers with integral heatsinks, a power supply, Zobel networks, front and back mounting panels, a finished fascia panel, all control potentiometers (bass, treble, volume and balance), switches, input, output and headphone sockets, wire, and an easily assembled wrap around cabinet to house the finished unit. Size approximately 9 1/4" x 8 3/4" x 4" **£12.25**  
p&p £2.25




**BARGAINS FOR PERSONAL SHOPPERS**

- LCD Solar 5 function with backlite stainless steel finish case and strap **£7.40**
- LCD Solar Chrono 9 function with backlite stainless steel finish case and strap **£9.55**
- Chrono stop watch 9 function with back lite stainless steel finish case and strap **£8.95**
- Solar Alarm LCD stainless steel case and strap. **£21.95**
- AM/FM DIGITAL CLOCK RADIO Accurate 4 Digit Electronic Clock with 1/2" LED display Buzzer and snooze timer **£12.20**
- 125 Watt Power Amp Module **£14.25**
- Mains power supply for above unit **£3.60**
- DECCA 20w Stereo speaker kit comprising 2 8" approx bass units + 2 3 1/2" approx tweeter inc. crossovers **£20.45**
- VIDEOMASTER Super Score TV Game with pistol mains operation **£15.95**
- PORTABLE RADIO/CASSETTE RECORDER. AM/FM with clock LW, MW, SW, VHF mains/battery operation **£42.90**
- ISP Radio Cassette recorder Mains/Battery AM/FM built in mic auto stop. **£24.50**

**50 WATT MONO DISCO AMP**

**£30.60**  
p&p £2.70

Size approx. 13 1/4" x 5 1/4" x 6 1/4"

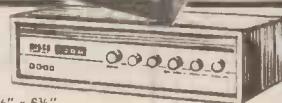

50 watts rms, 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

**100 WATT MONO DISCO AMP**

Size approx. 14" x 4" x 10 1/2"

Brushed aluminium fascia and rotary controls. Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak



P&P £4.05 **£66.45**

**FOR PERSONAL SHOPPERS ONLY**  
**DUO II SPEAKERS**

Attractive teak finish, modern design, incorporating 2 speaker units—8" approx woofer and 2 1/2" approx. tweeter. 45 to 1800 Hz Impedance 8 ohms. Power 15 watts RMS. 18 1/2" x 13 1/2" x 7 1/2" Per stereo pair approx. **£16.50**  
£6.50 p&p



**FOR PERSONAL SHOPPERS ONLY**  
**STEREO RADIOGRAM CABINET**

Finished in a natural teak veneer with opening top. Easily modified to accommodate stereo equipment of your choice. Price **£10.95**  
Size approximately 47" x 15 1/2" x 15"



323 EDGWARE ROAD, LONDON, W.2  
21H STREET, ACTION W3 6NG


ACTON: Mail Order only. No callers  
ALL PRICES INCLUDE VAT AT 15%

All items subject to availability. Price correct at 19.7.79 and subject to change without notice.

NOTE: Persons under 16 years not served without parent's authorisation.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel. 01-723 8432. 9.30a-m-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS NOT DESPATCHED OUTSIDE UK

# Hobby Electronics Book Service

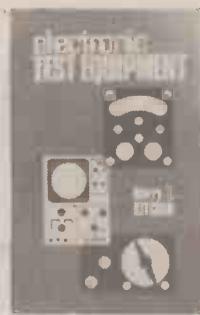

## POPULAR ELECTRONICS BOOKS

Sinclair, I. R., <i>Introducing Electronic Systems</i> .....	£1.80
Sinclair, I. R., <i>Introducing Amateur Electronics</i> .....	£1.55
Sinclair, I. R., <i>Electronic Fault Diagnosis</i> .....	£3.45
Sinclair, I. R., <i>Repairing Pocket Transistor Radios</i> .....	£2.50
Sinclair, I. R., <i>Oscilloscope In Use</i> .....	£3.00
Sinclair, I. R., <i>Understanding Electronic Components</i> .....	£4.00
Sinclair, I. R., <i>Understanding Electronic Circuits</i> .....	£4.00
Kitchen, H. T., <i>Handtools For Electronic Workshop</i> .....	£2.75
Kitchen, H. T., <i>Electronic Test Equipment</i> .....	£5.00
Capel, V., <i>How To Build Electronic Kits</i> .....	£2.20
Darr, J., <i>How to test almost everything electronic</i> .....	£3.50
Brown, R. M., <i>How to read electronic circuit diagrams</i> .....	£4.10

## AUDIO

Earl, J., <i>Audio Technicians Bench Manual</i> .....	£3.50
Earl, J., <i>Pickups and Loud Speakers</i> .....	£3.50
Earl, J., <i>Tuners and Amplifiers</i> .....	£3.00
Earl, J., <i>Cassette Tape Recorders</i> .....	£5.25
Earl, J., <i>ABC of Hi-Fi</i> .....	£4.25
Capel, V., <i>Microphones In Action</i> .....	£3.00
Capel, V., <i>Improving Your Hi-Fi</i> .....	£3.50
Capel, V., <i>Creative Tape Recording</i> .....	£4.00
Hellyer, H. W., <i>Tape Recorders</i> .....	£4.25
Sinclair, I. R., <i>Audio Amplifiers For Home Construction</i> .....	£2.75

## RADIO CONTROL

Aldridge, D., <i>Transistorised Radio Control For Models</i> .....	£3.50
Drake, J., <i>Radio Controlled Helicopter Models</i> .....	£3.95
Jeffries, C. R., <i>Radio Control For Model Yachts</i> .....	£1.85
Safford, E. L., <i>Radio Control Manual</i> .....	£2.45
Safford, E. L., <i>Advanced Radio Control</i> .....	£3.95

## COOKBOOKS

Tracton, K., <i>BASIC Cookbook</i> .....	£4.10
Lancaster, D., <i>TTL Cookbook</i> .....	£7.00
Lancaster, D., <i>RTL Cookbook</i> .....	£4.65
Lancaster, D., <i>CMOS Cookbook</i> .....	£8.20
Jong, W., <i>IC Op Amp Cookbook</i> .....	£10.00
Lancaster, D., <i>T.V. Typewriter Cookbook</i> .....	£7.75
Lancaster, D., <i>Cheap Video Cookbook</i> .....	£7.00
Jong, W., <i>IC Timer Cookbook</i> .....	£7.50
Lancaster, D., <i>Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business)</i> .....	£4.95

## QUESTIONS AND ANSWERS

SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.

Coker, A. J., <i>Q &amp; A On Electric Motors</i> .....	£1.50
Hellyer, H., <i>Q &amp; A On Radios and T.V.</i> .....	£1.50
Hibberd, R., <i>Q &amp; A On Integrated Circuits</i> .....	£1.50
Jackson, K., <i>Q &amp; A On Electricity</i> .....	£1.50
Brown, C., <i>Q &amp; A On Hi-Fi</i> .....	£1.50
Brown, C., <i>Q &amp; A On Transistors</i> .....	£1.50
Brown, C., <i>Q &amp; A On Electronics</i> .....	£1.50
Reddihough, J., <i>Q &amp; A On Colour T.V.</i> .....	£1.50
Miller, H., <i>Q &amp; A On Electric Wiring</i> .....	£1.50

## CONSTRUCTOR GUIDES

Graham, P., <i>Simple Circuit Building</i> .....	£2.45
Colwell, M., <i>Electronic Diagrams</i> .....	£2.45
Colwell, M., <i>Electronic Components</i> .....	£2.45
Colwell, M., <i>Printed Circuit Assembly</i> .....	£2.45
Ainslie, A., <i>Practical Electronic Project Building</i> .....	£2.45
Colwell, M., <i>Project Planning and Building</i> .....	£2.45

## BEGINNER'S GUIDE

Sinclair, I. R., <i>Beginner's Guide To Tape Recording</i> .....	£3.30
Sinclair, I. R., <i>Beginner's Guide To Integrated Circuits</i> .....	£3.10
Sinclair, I. R., <i>Beginner's Guide To Audio</i> .....	£3.10
King, G. J., <i>Beginner's Guide To Radio</i> .....	£3.10
King, G. J., <i>Beginner's Guide To Television</i> .....	£3.10
King, G. J., <i>Beginner's Guide To Colour T.V.</i> .....	£3.10
Guilou, F., <i>Beginner's Guide To Electric Wiring</i> .....	£3.10

## PROJECT BOOKS

Marston, R. M., <i>110 Cosmos Digital IC Projects For The Home Constructor</i> .....	£3.25
Marston, R. M., <i>110 Wave Form Projects For The Home Constructor</i> .....	£3.45
Marston, R. M., <i>110 Op Amp Projects For The Home Constructor</i> ..	£2.95
Marston, R. M., <i>110 Semiconductor Projects For The Home Constructor</i> ..	£3.45
Marston, R. M., <i>110 Thyristor/SCR Projects For The Home Constructor</i> ..	£2.95
Marston, R. M., <i>110 Electronic Alarm Projects For The Home Constructor</i> .	£3.45
Marston, R. M., <i>110 Integrated Circuits Projects For The Home Constructor</i> ..	£3.45
Marston, R. M., <i>20 Solid State Projects For The Car and Garage</i> ..	£2.50
Marston, R. M., <i>20 Solid State Projects For The Home</i> .....	£2.50

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service,  
P.O. Box 79,  
Maidenhead, Berks.

# Starburst

**Expand your universe with HE's pulsating phonoptic display. Ordinary LED chasers beware . . . .**

LOOKING FOR a novel, economical, yet versatile LED display? Here is the answer to your dreams. Featuring an attractive matrix design, audio control input and a choice of three operating modes, the HE Starbursts adds a new dimension to conventional light-chasers.

Assembled on two printed circuit boards, the unit is designed around readily available CMOS chips and uses only a few other discrete components. The display is arranged as five semicircles of ten LEDs each which are illuminated in bands sequentially producing the illusion of either an expanding line of light or a band of light that grows outward and collapses. A novel bonus of the circuit design is the automatic mode where dots and bars are displayed alternately.

The audio signal pre-conditioner, clock oscillator and counter-decoder-driver circuitry is mounted on one board, whilst the other board holds the display and main decoupling capacitor. The circuit is powered by a single PP9 nine volt battery. Choice of a larger battery ensures longer life as currents of up to one hundred milliamps may be drawn when all the LEDs are lit. No provision is made for the battery or power switch on-board enabling the unit to be neatly boxed and mounted in any suitable remote position.


## SEEING THE LIGHT

After applying power to the circuit, the LEDs will illuminate from the centre of the display outwards appearing as a bar or dots of light; or alternately depending on the position of mode switch SW1.

Application of an audio signal will cause the frequency of movement to increase. By adjustment of the input level and control RV1, the display can be made to follow the dynamic range of the audio input; increasing in frequency as the audio input level increases in amplitude. Component values shown make the unit more sensitive to input frequencies above 1 kHz or so and more responsive to melody lines in music and to vocal input.
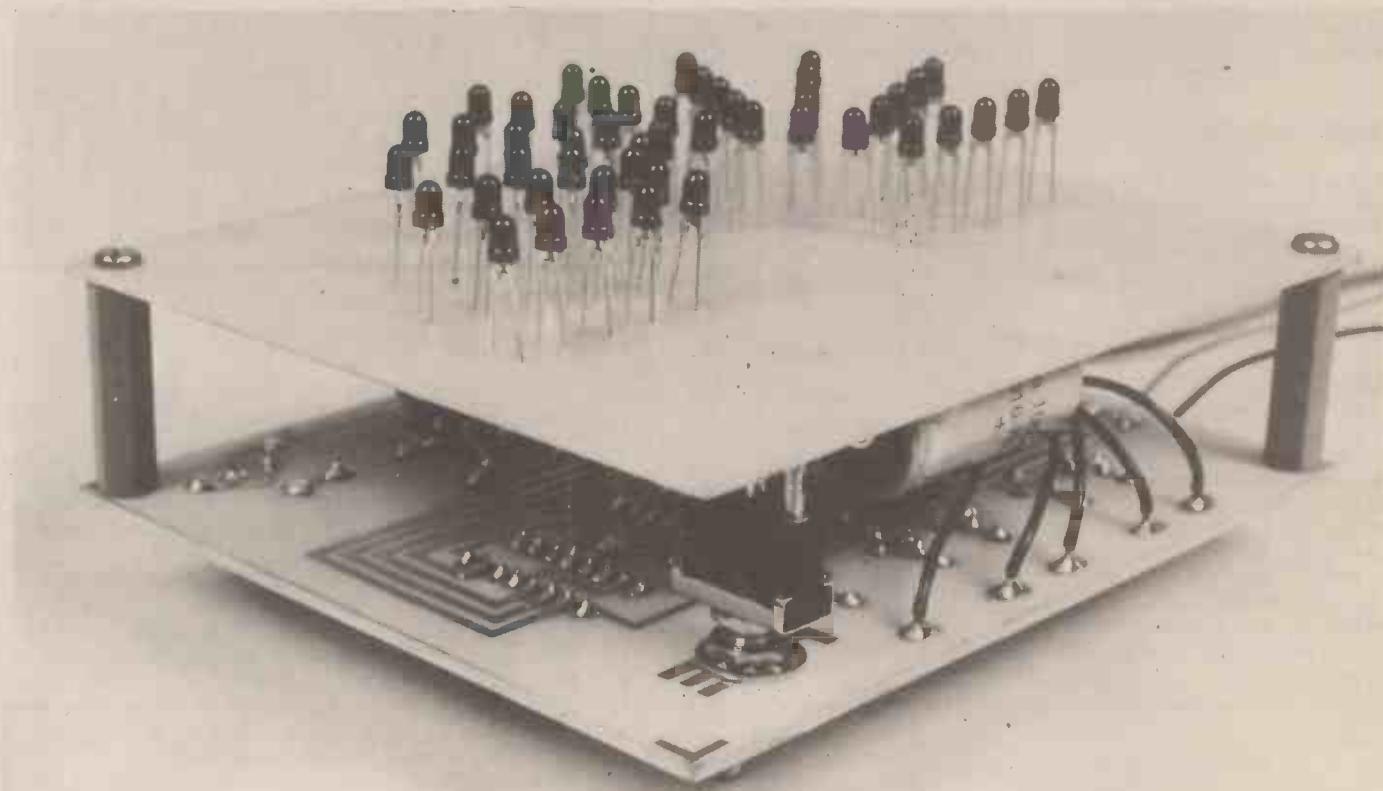
## LUCKY NUMBER

At first glance, it would appear that the way to produce a display such as the one described above might be to use a ' bargraph ' chip driven from a ramp whose frequency would be controlled by the audio signal. However, the CMOS family contains some not so popular but nonetheless versatile chips which enable an economical



*The two boards of the HE "Starburst," the switch in the foreground controls the three modes of display.*

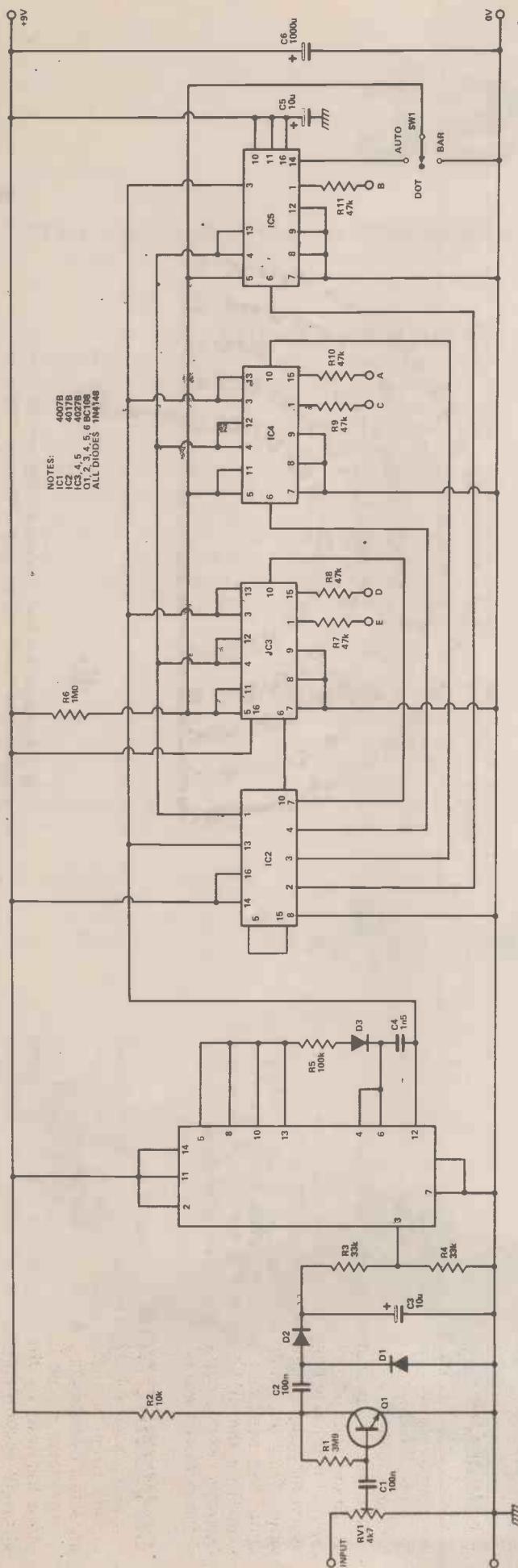


Fig. 1. Circuit diagram for Starburst control circuitry and display. There should be no problem in either obtaining components or assembling the unit.

IC1 is an oscillator whose frequency can be controlled over a limited range by a voltage applied to pin 3. As the voltage rises, the frequency increases. The block diagram does not give much away so the important parts of the circuit have been drawn in simplified form in figure 2.

As can be seen, the chip contains two pairs of complementary transistors which are here connected as inverters and one single transistor (pins 3, 4, 5) which operates as a voltage controlled resistor. It also contains another complementary transistor which is not used here.

Operation of this network is more easily understood by representing it as shown in figure 3. It is the same circuit, though the complementary transistor inverters are now shown in block diagram form. The remaining transistor and the resistor and diode together form the timing resistance Rx and can be considered as a single resistor.



If the circuit is redrawn (fig. 4), it will be familiar as a conventional CMOS oscillator. The resistor and diode are simply there to modify the duty cycle of the oscillator in order to produce a greater control range from the circuit.


## How it Works

well as providing a discharge path for this capacitor. Comparatively high values can be used for these resistors as there is negligible loading by the very high input impedance mosfet in IC1.

The pulses from oscillator IC1 (pin 12) clock five of the flip-flops in IC3, 4, 5 and the decade counter-decoder IC2 which produces a logic 1 high level at its outputs in turn. These signals could be fed to the transistor LED drivers directly but instead are processed by five of the J K flip-flops in IC3, 4, 5. It is this that enables the different modes of operation from the display. The sixth flip-flop is clocked each time a display sequence is completed and its output consists of alternate logic 0s and 1s.

Briefly, these 4027 chips each contain two flip-flops whose outputs following a clock pulse depend on the state of two inputs: J and K. In this design, one input (J) of the five flip-flops is driven by the outputs from the 4017 whilst the other input (K) controls the form the display will take. All the K inputs from these five flip-flops are commoned and brought out to SW1 where a logic '0' or an alternating logic signal is available from the sixth flip-flop. When SW1 is in the 'centre-off position,

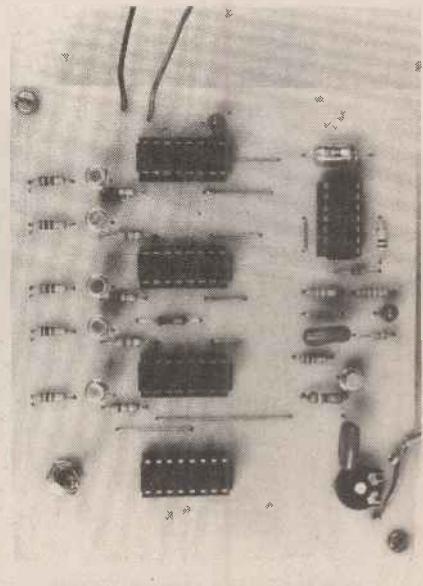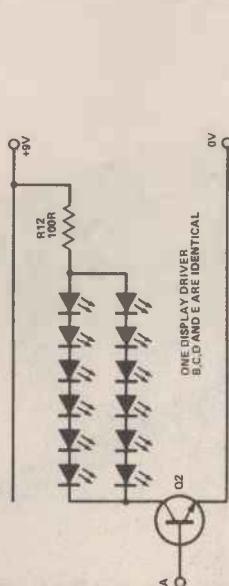

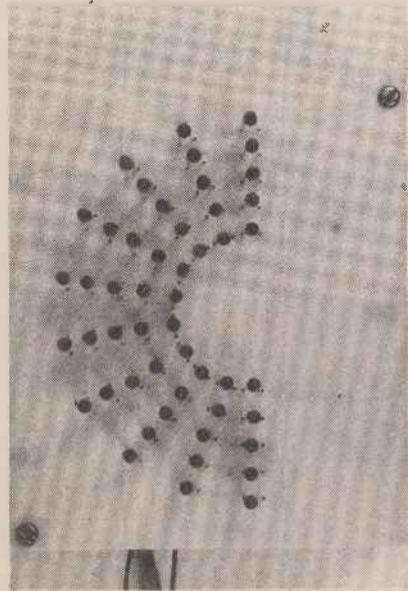

The display board viewed from above, the effects, especially when in the "audio" mode are quite exciting, to say the least.

The control voltage for IC1 is derived from the audio signal input to Q1 via RV1, C1. The amplified signal appearing at the collector of Q1 is coupled via C2 to rectifiers D1, D2 which charge C3. R3 and R4 tap off a proportion of the voltage across C3 as

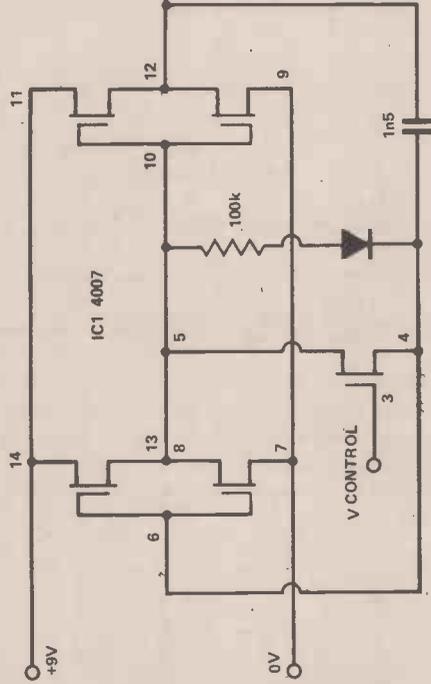


Fig. 2. Simplified view inside the 4007.

yet sophisticated circuit to be produced. By coincidence, all the chips in this project contain the number seven in their device code. They are the 4007, 4017 and 4027.

**SEVEN-UP**

The mainstay of the circuit is the ubiquitous 4017 decade counter-decoder whose outputs are processed by the 4027 chips to produce the logic control signals for the display driver transistors.

The 4007 is probably the least familiar device. It is not strictly speaking a logic chip as it contains only three pairs of complementary metal oxide silicon transistors which may be interconnected in a number of different ways. They are configured here as a novel voltage-controlled oscillator which provides the clock drive signals for the 4017 counter and 4027 JK flip-flops. Operation of this part of the circuit is described in more detail in 'how it works'.

**CONSTRUCTION**

The unit is assembled on two PCBs. Use of our PCBs will greatly simplify construction as well as enabling an attractive free-standing display to be produced.

Wire links should be inserted first and soldered into place followed, by the IC sockets. Use of sockets is strongly recommended. Next, insert the resistors, capacitors and transistors and diodes. Do not insert the

the K inputs are pulled up to a logic '1' by R6 giving a dot display.

The outputs from J K flip-flops control transistors Q2-Q6 which drive the LED display. C5 and C6 are power supply decoupling capacitors.

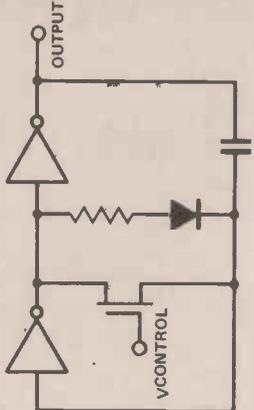


Fig. 3. MOSFET used as a variable resistor.


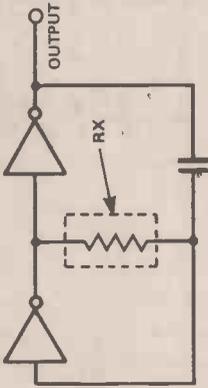


Fig. 4. Conventional CMOS oscillator.

he

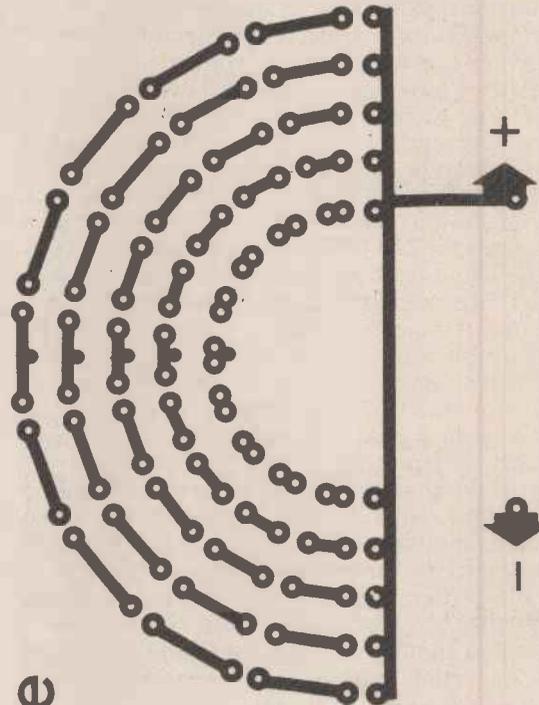

PCB foil pattern for the "Starburst" display board, no problems here, as always take care with your soldering.




CMOS chips at this stage. Note that some of the links pass under the IC sockets. If you do forget to put one in and discover later that it is inaccessible simply use a piece of insulated wire on the underside of the board to complete the connection.

The LEDs are wired in series-parallel and failure of one will cause the other four in an arm to extinguish. The display board can be tested as it is assembled by use of a separate nine volt supply. Insert and solder into place C6 ensuring correct orientation then connect the positive lead of the battery as shown on the overlay and make up a length of wire in series with a 330 ohm resistor. Connect the free end of the resistor to the negative terminal of the battery. Then as assembly of each arm of LEDs is completed, touch the free end of the wire from the resistor to the connector pads on the PCB (shown going to resistors R12 to R16 on the overlay). The LEDs should light. Failure to do so indicates an open circuit or reversed LED. Check for this condition by shorting each LED in turn until the display lights and replace any faulty ones ensuring correct orientation. A short lead, indent or flat on the plastic encapsulation usually indicates the cathode. We used red LEDs. In fact green or yellow LEDs will not work with a nine volt supply as they have a higher forward voltage drop.

Once satisfied that the display board is working correctly, make the remaining interconnections between the boards. We mounted SW1 on the main circuit board, there's plenty of room. Insert the ICs observing the usual CMOS handling precautions and connect a nine volt battery. The display should illuminate. If all is well, connect an audio signal to the input and adjust RV1 for satisfactory operation. Check that operation of SW1 causes the display mode to change.

We used the earphone socket of a transistor radio as an audio source though any signal of around 1 volt peak to peak will do. Finally, disconnect the battery and assemble the boards together using spacing pillars to separate them. That completes construction so switch on, plug in and flash out!

HE

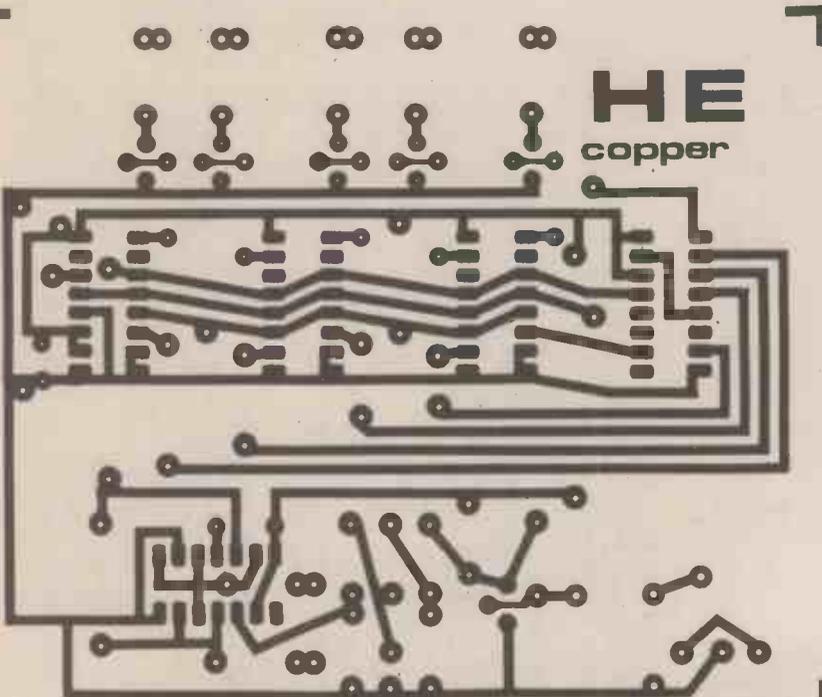


PCB foil pattern for the main control board, take particular care when soldering in the ICs to avoid any solder bridges.

## Parts List

RESISTORS	(all 1/4W, 5%)
R1	3M9
R2	10k
R3, 4	33k
R5	100k
R6	1M
R7,8,9,10,11	47k
R12,13,14,15,16	100R
CAPACITORS	
C1, 2	100n polyester
C3, 5	10µ tantalum
C4	1n5 polystyrene
C6	1,000µ electrolytic
SEMICONDUCTORS	
IC1	4007B
IC2	4017B
IC3,4,5	4027B
Q1,2,3,4,5,6	BC108
D1,2,3	1N4148
LEDs	0.125" red (50 are needed if our display board is used)
MISCELLANEOUS	
SW1	SPDT centre off switch. PCB PP9 battery, connectors. Approximate cost £10.00.
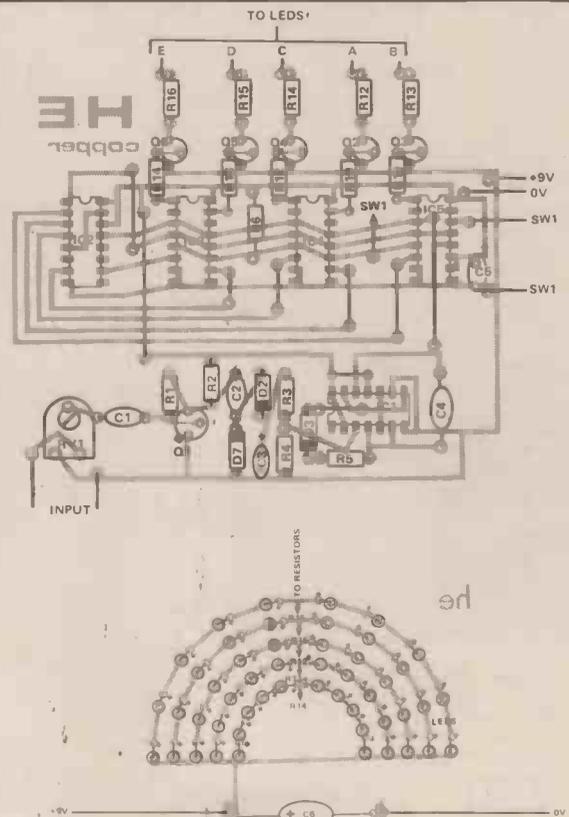
## Buylines

All the components for this project should be readily available from the usual suppliers. It is worth 'shopping around' for the LEDs as these are sometimes offered in quantity at a discount.



# Hobby Chit~Chat

**HE project editor and chief designer Ray Marston takes another look at the hobby scene.**

## **THERE ARE GOOD BOOKS . . .**

EVERY ELECTRONICS HOBBYIST should make a point of building up a decent collection of electronics reference books. Ideally, you should have at least one really good book that explains the basic principles of electronics, another that outlines the principles of 'advanced' electronics, and one more that gives electronics tables, colour codes, IC outlines, and other pure 'reference' data, etc. The following is our recommended short list.

'Foundations of Wireless and Electronics' by M. G. Scroggie, is probably the best introductory text to electronics ever published. It explains the basic principles of electronics in such a clear manner that even a complete layman can understand it. The subject material of the book spans elementary principles of electricity to fairly advanced electronics.

'Foundations —' was first published in 1936, and is now in its ninth edition. The book has sold some 265 000 copies, which shows how good it is. The latest edition runs to 521 pages, and costs £4.45. It is published by Newnes-Butterworth.

Our next recommendation is for 'Electronics — It's Easy'. This is an ETI publication (ETI is the big brother of HE, if you didn't know), and spans the information range of basic principles of electricity to advanced electronics. It makes an excellent companion to 'Foundations —'. 'Electronics — It's Easy' was originally published as a 3-volume ETI 'special'. Volume 1 is now out of print, but the whole three volumes are presently being re-issued as one single book. Release date should be late August, and price about £3.

Our final recommendation is for 'Newnes Radio and Electronics Engineer's Pocket Book', 15th Edition. This is an excellent pocket-sized (you'll need a magnifying glass to read it) reference book of tables, formulae, IC outlines, data, and basic electronic circuits. The book has been compiled by the staff of ETI, is published by Newnes-Butterworth, and is well worth having.

## **AND THERE ARE AWFUL BOOKS**

As a professional book-worm, I'm obliged to read a great many electronics books. Most are pretty mundane, a tiny minority (like those mentioned above) are very good, and a fair number are, frankly, awful. A couple of weeks back, I read what must rate as the most awful electronics book of all. It's called 'Build Your Own Working Robot', is written by an American named D. L. Heiserman, and is

published by Foulsham-Tab. It's well worth looking at, simply because it IS so awful, it must be regarded as a classic of its kind.

The first fourteen chapters of the Robot book describe how to build, for a mere few hundred pounds, a device called BUSTER, which is more or less capable of emulating the actions of one of those cheap (about £5) Hong Kong toy cars that change direction whenever they crash into a wall, which is all very amusing if you like that kind of thing. The book really takes off, however, in chapter 15, which has the title HUNGER INTERFACE.

The HUNGER INTERFACE is, to put it as kindly as possible, interesting. Briefly, what happens is that when 'Buster's' 12 volt battery supply falls below 10 volts a pulsed 3 kHz signal is transmitted from its loud speaker, and this signal activates a kind of giant lighthouse (stop laughing at the back there) that is built into one corner of 'Buster's' private room (apparently, 'Buster' is prone to permanent starvation if he moves out of this room). Buster automatically charges at this lighthouse, like a bull at a red rag, whenever it switches on, and ends up impaling himself on a battery recharging circuit. All very clever.

The lighthouse actually consists of a flashing strobe lamp stuck on top of a five foot pole. At the base of the pole is what is described as a 'nest', which includes (amongst miscellaneous bits of wood and a mirror) a battery charger and a couple of massive metal probes, which get rammed up poor old Buster's charging socket whenever he suffers a slight electron deficiency. In front of the 'nest' are two 8-foot lengths of wooden guide rail, which encompass an area of 32 square feet and, working on the 'pea in a funnel' principle, ensure that Buster gets steered into his nest for a re-charge whenever the need arises. So how's that for American technological know-how?

The final chapter of the book describes how to convert Buster into a white-line follower. Which just about sums up the true value of the project that has cost hundreds of pounds to build and sixteen chapters to describe.

To be fair, whatever this Robot book lacks in sophistication of design of its main project is more than compensated for by its author's originality in the use of strange circuit symbols and notations, his sheer guts in presenting photo's of his constructional efforts, and his (thankfully) utter uniqueness of writing style.

As was said earlier, we thoroughly recommend 'Build

Your Own Working Robot' as THE most awful book. You simply must read it. Our congratulations to its author, and to the staff of the Ohio Institute of Technology in Columbus, who helped engineer, build, and debug the super white-line follower known as Buster.

## RELAY TIMER CIRCUITS

The real 'guts' of Hobby Electronics is the actual building of, rather than reading about, electronic circuits. One of the most useful circuits that the hobbyist can build is the relay timer. It consists of a relay and a few electronic components, configured in such a way that the relay switches on when you press a START button, and then switches off again automatically after a pre-set time delay. The time delay may vary from seconds to days, and the relay contacts can be used to activate such diverse objects as photographic enlarger lamps, porch lights, battery chargers, and tape recorders, etc.

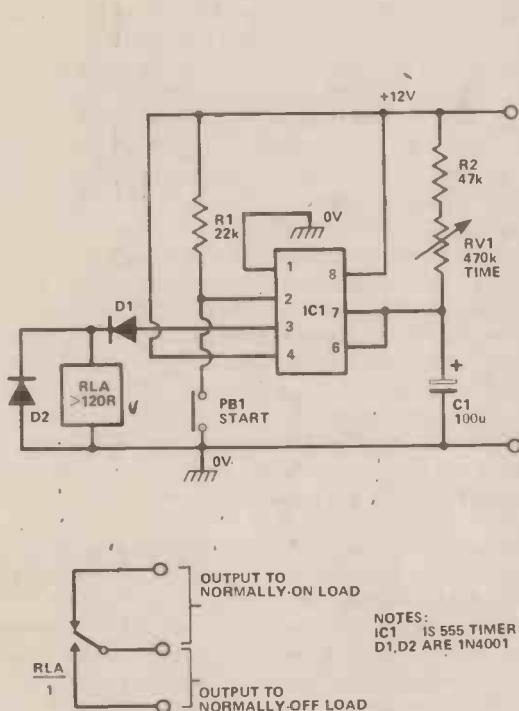


Fig. 1. A simple 6-second to 60-second timer circuit.

Figure 1 shows the practical circuit of a simple 6-second to 60-second timer. The design is based on a type-555 timer IC, wired in the monostable or one-shot mode. The circuit starts a timing cycle when push-button START switch PB1 is momentarily operated. Relay RLA immediately turns on, and C1 starts to charge towards the positive rail via R2 and RV1. Eventually, after a delay determined by the RV1 setting, C1 rises to 2/3rds of the supply rail voltage, at which point the IC changes state, the relay turns off, and the timing cycle is complete. External devices can be turned on or off via the relay contacts.

## WEAKNESSES

A weakness of the basic Figure 1 circuit is that it permanently draws current from the supply rails, even when the relay is off. Figure 2 shows a 2-range timer circuit that does not suffer from this defect, and which covers the timing range of 6-seconds to 10-minutes. The circuit operates as follows:

When START switch PB1 is momentarily closed a START pulse is fed to pin 2 of the IC via R1 and C1, and the relay turns on. Contacts RLA/1 then change over and maintain the power connections to the circuit even when PB1 is released. The circuit then runs through a timing cycle similar to that already described, but with the period determined by either C2 or C3, until eventually the relay turns off, at which point contacts RLA/1 revert to their original state and break the supply connections to the circuit. The timing cycle is then complete. Note that this circuit can be turned off part way through its timing cycle by operating RESET switch PB2.

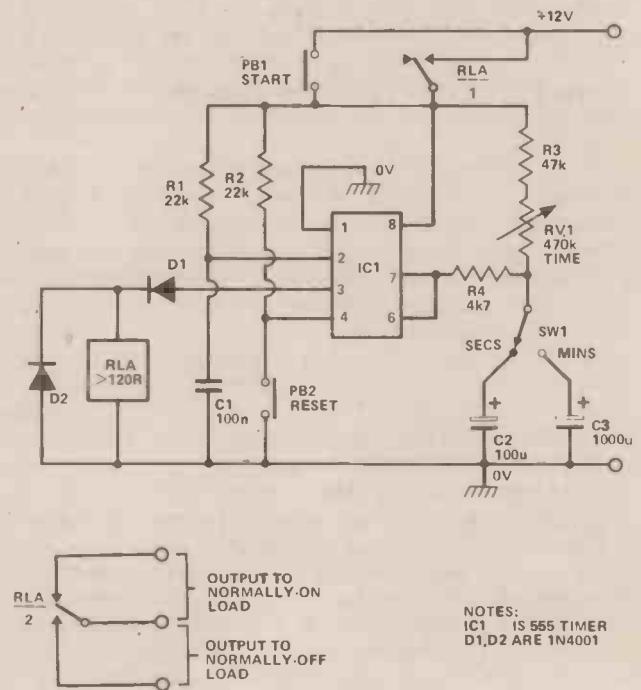


Fig. 2. A 2 range 6-60 second and 1-10 minute timer circuit.

Conventional electrolytic capacitors have very wide tolerances (typically -50% to +100%), and suffer from relatively large and unpredictable leakage currents. Consequently, simple circuits of the types shown in Figs 1 and 2 can not be relied upon to give accurate timing periods, or to give periods that significantly exceed fifteen minutes or so. Figs 3 and 4 show two high-accuracy long-period timer circuits that do not rely on the use of electrolytics for their timing operations.

## FREE RUNNING

In both of these circuits, IC1 is wired as a free-running

astable multivibrator. In the Fig 3 circuit the astable frequency is divided down by IC2, a 14-stage binary counter, so that the relay turns on as soon as PB1 is momentarily closed, and turns off on the arrival of the 8192nd astable pulse, thereby giving total timing periods in the range of 1 to 100 minutes.

The Fig 4 circuit is basically similar to that of Fig 3, except that an additional decade-divider stage is used in position 3 of SW1, thus giving a maximum division ratio

of 81 920, and making maximum timing periods up to 20 hours available from the unit. This circuit is of particular value in giving time-controlled turn-off of battery chargers, etc.

Note in the four timer circuits given that the relay used can be any 12-volt type with a coil resistance greater than about 120 ohms. The relay used in the Fig 2 to Fig 4 circuits should have two or more sets of change-over contacts. **HE**

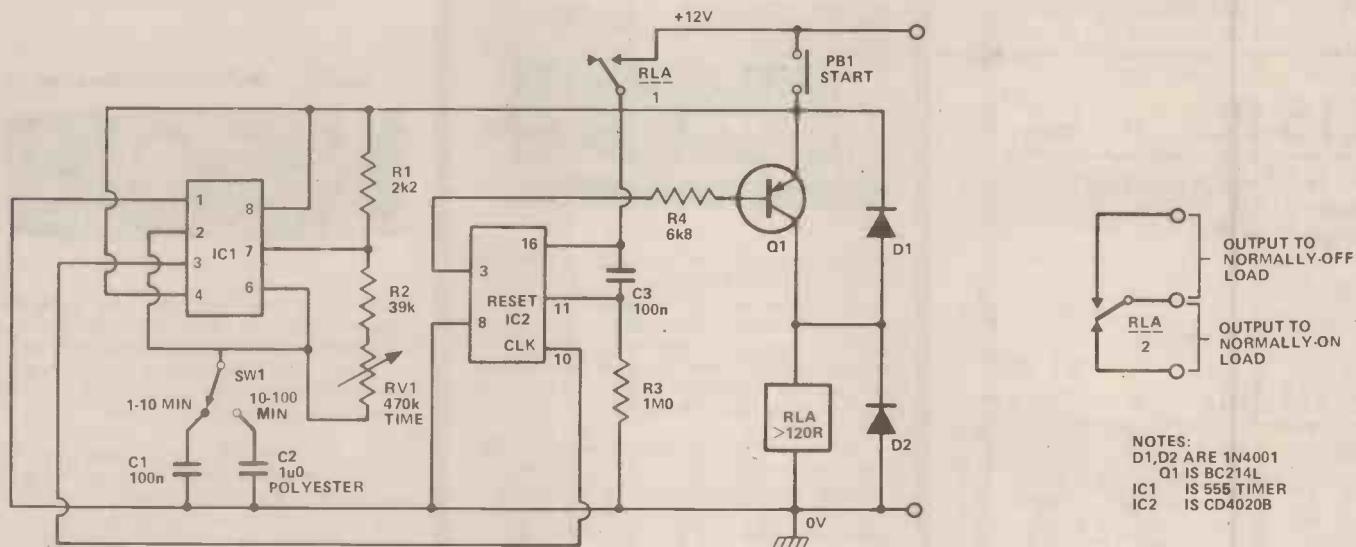


Fig. 3. A 2-range 1-10 minute and 10-100 minute timer circuit.

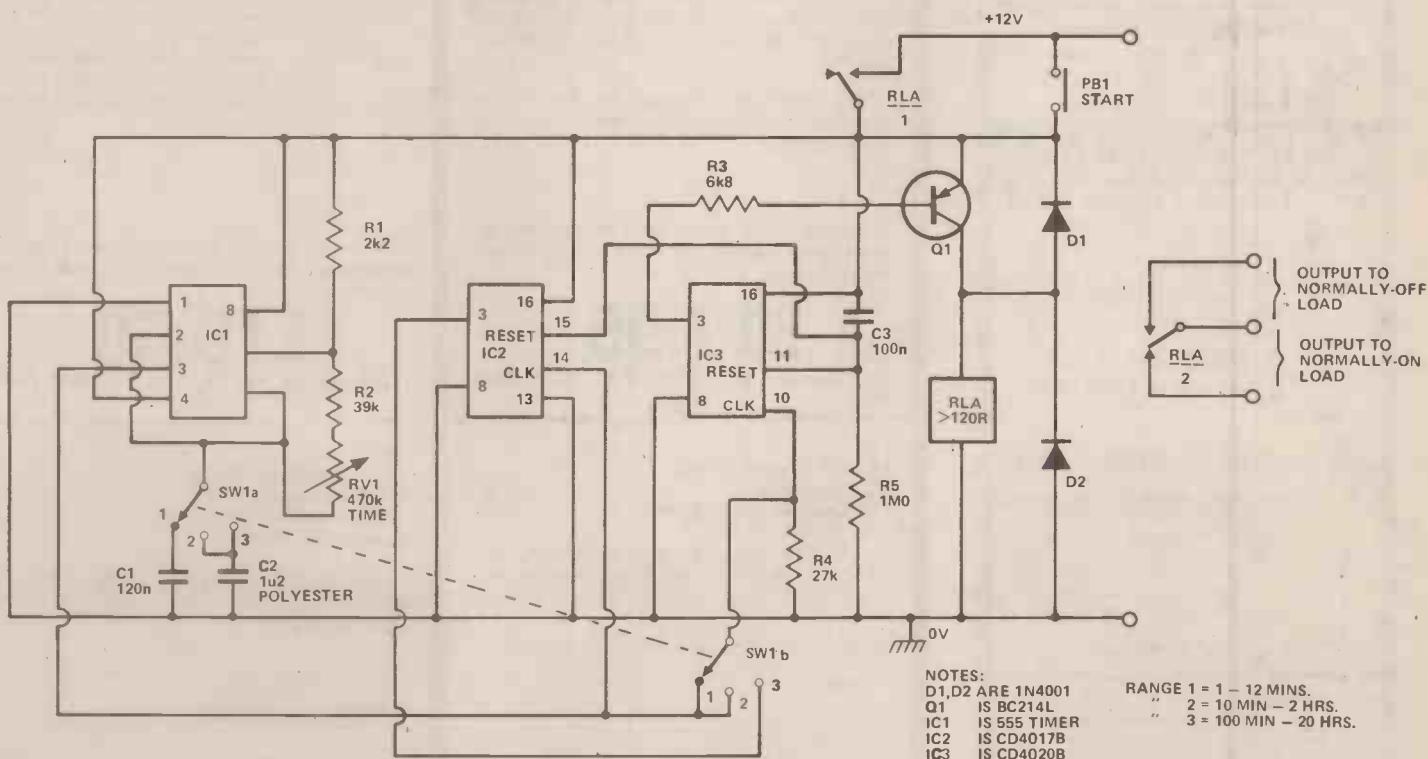


Fig. 4. A wide-range timer covering 1 minute to 20 hours in three ranges.

# Car Audio

Manual  
MW/LW

Full medium and long wave tuning. Complete with speaker and mountings. Suitable for positive or negative chassis. Latest model.

**£10.25 + £1.00 Post**

Push-Button  
MW/LW

One LW, four MW buttons plus manual tuning. Complete with speaker and mountings. Latest model, negative chassis only.

**£15.95 + £1.00 Post**

Stereo FM/  
Cassette

+ MW

Standard cassettes and FM in stereo plus medium wave. Tone and balance controls. Fast forward facility on tape. Adjustable shafts. Suitable for 4 or 8 ohm speakers (not supplied). This model is discounted elsewhere at £50 up.

**£40.95 + £1.00 Post**

Stereo  
Speaker Set

Suitable for above stereo unit. Good quality in surface mounted casing. 5W nominal, 8W peak.

**£4.00 (pair)**

+ 70p Post

Telescopic Car Antenna

Multi-section standard type, suitable for angled mounting with locking key.

**£1.60 + 30p Post**

# Metal Detectors

Treasure Tracer Mk III

The original Treasure Tracer. Sales exceed 7,000. 5-transistor circuit with Varicap tuning. Sensitive, stable BFO design. Built-in speaker and earphone. Fitted with Faraday shield. Kit supplied with pre-built search head.

Kit. **£18.60 + £1.00 Post**

Built **£23.95 + £1.00 Post**

★ Induction Balance Model

Built with sensitivity up to 10in on single coin; fitted with speaker and meter; PP3 battery; 7in dia. search head. Telescopic stem. Excellent pin-pointing, positive reaction to non-ferrous, negative reaction to iron. This model's normal price is £39.95!

**£24.50 + £1.00 Post**

All goods guaranteed one year. 10-day money-back offer. Goods ex-stock at time of going to press. Callers by appointment only please. Send s.a.e. for illustrated leaflet.

**Minikits Electronics Ltd.**

6H Cleveland Road  
S. Woodford  
London E18 2AN

# THE MA

## CLOCK RADIO



You probably won't believe us as we're selling the goods but we're going to tell you anyway! We have *rejected* eight clock radios for Marketplace, they were all cheap enough but the quality was so poor that we couldn't have lent our name to them. However, we are now able to offer a portable LCD Clock Radio to you which meets our standards.

The clock is a 12-hour one with AM/PM indicated and a back light. The radio is Medium Wave with very nice quality for a small speaker. The alarm can be either a beep-beep type or the radio, there's also a snooze facility.

The cylindrical construction is in keeping with the very modern styling. The tuning dial is actually incorporated into one of the end caps!

We won't even mention the RRP — but just check on comparable prices — you'll find ours a bargain.

An example of this Clock Radio can be seen and examined at our Charing Cross Road offices.

**£17.95**

(Inclusive of 15% VAT and Postage).

To:  
**CLOCK RADIO Offer,**  
HE Magazine,  
145 Charing Cross Road,  
London WC2H 0EE.

Please find enclosed my cheque/PO for £17.95 (payable to HE Magazine) for my Clock Radio.

Name .....

Address .....

Please allow 28 days for delivery.

## DIGITAL ALARM



THIS IS THE THIRD digital alarm clock that we are offering (we regret the earlier versions are no longer available). We have sold thousands and thousands of these and our buying power enables us to offer a first rate branded product at a really excellent price.

The Hanimex HC-1100 is designed for mains operation only (240V/50Hz) with a 12 hour display, AM/PM and Alarm Set indicators incorporated in the large display. A switch on the top controls a Dim/Bright display function.

Setting up both the time and alarm is simplicity itself as buttons are provided for both fast and slow setting and there's no problem about knocking these accidentally as a 'locking' switch is provided under the clock. A 9-minute 'snooze' switch is located at the top.

A example of this clock can be seen and examined at our Charing Cross Road offices.

**£10.60**

(Inclusive of 15% VAT and Postage).

To:  
**Hanimex Alarm Offer**  
HE Magazine  
145 Charing Cross Road,  
London WC2H 0EE

Please find enclosed my cheque/PO for £10.60 (payable to HE Magazine) for a Hanimex Digital Alarm Clock.

Name .....

Address .....

Please allow 28 days for delivery.

# MARKETPLACE

## LCD CHRONO



We feel we've got to tell you carefully about this offer which we're introducing for the first time. Why? Because our price is so enormously lower than anywhere else you may suspect the quality.

The display is LCD and shows the seconds as well as the hours — and minutes — press a button and you'll get the date and the day of the week.

Press another button for a couple of seconds and you have a highly accurate stopwatch with hundredths of a second displayed and giving the time up to an hour. There is a lap time facility as well — and of course a back light.

Our Chrono comes complete with a high grade adjustable metal strap and is fully guaranteed.

**£11.95**

(Inclusive of 15% VAT and Postage).

To:  
LCD Watch Offer  
ETI Magazine  
145 Charing Cross Road,  
London WC2H 0EE

Please find enclosed my cheque/PO for £11.95 (payable to HE Magazine) for my LCD Chronograph.

Name .....

Address .....

Please allow 28 days for delivery.

## ALARM-CHRONO LCD



This new addition to our unbeatable selection of bargains is no ordinary LCD watch. It's a slim, multi-function, dual time chronograph alarm watch, no less.

This model will show hours, minutes, seconds, date, day of the week, stop watch, split time, alarm and alternate dual time zone — not all at once, of course. There is also a night light.

Hours, minutes, seconds and day of the week are displayed continuously, while the date will appear at the touch of a button. The day of the week is indicated by a flag. When used as a stopwatch, the maximum count is 0.1secs. short of thirteen hours.

**£19.95**

(Inclusive of 15% VAT and Postage).

To:  
ALARM/CHRONO LCD WATCH Offer,  
HE Magazine,  
145 Charing Cross Road,  
London WC2H 0EE

Please find enclosed my cheque/PO for £19.95 (payable to HE Magazine) for my Alarm/Chrono LCD watch.

Name .....

Address .....

Please allow up to 28 days for delivery.

# STEVENSON

## Electronic Components


ALL PRICES INCLUDE 15% V.A.T.

TTL	7473	20p	74141	55p	
	7474	22p	74145	55p	
	7475	25p	74148	90p	
7400	10p	7476	20p	74150	55p
7401	10p	7476	20p	74150	55p
7402	10p	7485	55p	74151	40p
7404	12p	7486	20p	74154	65p
7406	22p	7489	135p	74157	40p
7408	12p	7490	25p	74164	55p
7410	10p	7492	30p	74165	55p
7413	22p	7493	25p	74170	100p
7414	39p	7494	45p	74174	55p
7420	12p	7495	35p	74177	50p
7427	20p	7496	45p	74190	50p
7430	12p	74121	25p	74191	50p
7432	18p	74122	35p	74192	50p
7442	38p	74123	38p	74193	50p
7447	45p	74125	35p	74196	50p
7448	50p	74126	35p	74197	50p
7454	12p	74132	45p	74199	90p

CMOS	4020	50p	4050	25p	
	4022	50p	4060	80p	
	4023	13p	4066	30p	
	4024	40p	4068	13p	
	4025	13p	4069	13p	
4001	13p	4026	90p	4070	13p
4002	13p	4027	28p	4071	13p
4007	13p	4028	45p	4072	13p
4009	30p	4029	50p	4081	13p
4011	13p	4040	55p	4093	36p
4012	13p	4041	55p	4510	60p
4013	28p	4042	55p	4511	60p
4015	50p	4043	50p	4518	65p
4016	28p	4046	90p	4520	60p
4017	47p	4049	25p	4528	60p
4018	55p				

FULL DETAILS IN CATALOGUE!

### SKTS

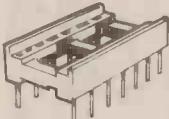

Low profile by Texas

8pin	8p	18pin	14p	24pin	18p
14pin	10p	20pin	16p	28pin	22p
16pin	11p	22pin	17p	40pin	32p

Soldercon pins: 100:50p 1000:370p

### PCBS

Size in.	VEROBOARD	Vero
25 x 1	0.1in. 0.15in.	Cutter 80p.
2.5 x 3.75	14p 14p	
2.5 x 5	45p 45p	
3.75 x 5	54p 54p	Pin insertion tool 108p
3.75 x 17	64p 64p	
	205p 185p	

Single sided pins per 100 40p 40p

Top quality fibre glass copper board. Single sided. Size 203 x 95mm. 60p each.

'Dalo' pens. 75p each.

Five mixed sheets of Alfaco. 145p per pack.

### OPTO

LED's	0.125in.	0.2in	each	100+
Red	TIL209	TIL220	9p	7.5p
Green	TIL211	TIL221	13p	12p
Yellow	TIL213	TIL223	13p	12p
Clips	3p	3p		

### DISPLAYS

DL704	0.3 in CC	130p	120p
DL707	0.3 in CA	130p	120p
FND500	0.5 in CC	100p	80p

### RESISTORS

Carbon film resistors. High stability, low noise 5%.

E12 series. 4.7 ohms to 10M. Any mix:

0.25W	1p	0.9p	0.8p
0.5W	1.5p	1.2p	1p

Special development packs consisting of 10 of each value from 4.7 ohms to 1 Meg-ohm (650 res) 0.5W £7.50. 0.25W £5.70.

### METAL FILM RESISTORS

Very high stability, low noise rated at 1/2W 1%. Available from 51ohms to 330k in E24 series. Any mix:

0.25W	each	100+	1000+
	4p	3.5p	3.2p



PLEASE WRITE FOR YOUR FREE COPY OF OUR NEW 80 PAGE CATALOGUE OF COMPONENTS.

CONTAINS OVER OVER 2500 STOCK ITEMS.

32

### TRANSISTORS

AC127	17p	BCY72	14p	ZTX500	16p
AC128	16p	BD0131	35p	2N697	12p
AC176	18p	BD132	35p	2N3053	18p
AD161	38p	BD139	35p	2N3054	50p
AD162	38p	BD140	35p	2N3055	50p
BC107	8p	BFY50	15p	2N3442	135p
BC108	8p	BFY51	15p	2N3702	8p
BC108C	10p	BFY52	15p	2N3703	8p
BC109	8p	MJ2955	98p	2N3704	8p
BC109C	10p	MPSA06	20p	2N3705	9p
8C147	7p	MPSA56	20p	2N3706	9p
BC148	7p	TIP29C	60p	2N3707	9p
BC177	14p	TIP30C	70p	2N3708	8p
BC178	14p	TIP31C	65p	2N3819	15p
BC179	14p	TIP32C	80p	2N3820	44p
BC182	10p	TIP2955	65p	2N3904	8p
BC182L	10p	TIP3055	55p	2N3905	8p
BC184	10p	ZTX107	14p	2N3906	8p
BC184L	10p	ZTX108	14p	2N4058	12p
BC212	10p	ZTX300	16p	2N5457	32p
BC212L	10p			2N5459	32p
BC214	10p			2N5777	50p
BC214L	10p				

### DIODES

1N914	3p	1N4006	6p
1N4001	4p	1N5401	13p
1N4002	4p	BZY88 ser.	8p
ITT Full spec product.			
1N4148	-£1.40/100.	£11/1000	

### LINEAR

THIS IS ONLY A SELECTION!

709	35p	LM339	45p	SN76477	230p
741	16p	LM378	230p	TBA800	70p
747	45p	LM379S	410p	TBA810S	100p
748	30p	LM380	75p	TD1022	620p
7106	850p	LM3900	50p	TL081	45p
7107	900p	LM3909	65p	TL084	125p
CA3046	55p	LM3911	100p	ZN414	80p
CA3080	70p	MC1458	32p	ZN425E	390p
CA3130	90p	MM57160	590p	ZN1034E	200p

### CAPACITORS

#### TANTALUM BEAD

0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1 & 2.2uF @ 35V 8p

4.7, 6.8, 10uF @ 25V 13p

22 @ 16V, 47 @ 6V, 100 @ 3V 16p

#### MYLAR FILM

0.001, 0.01, 0.022, 0.033, 0.047 3p

0.068, 0.1 4p

#### POLYESTER

Mullard C280 series

0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1. 5p

0.15, 0.22 7p

0.33, 0.47 10p

0.68 14p

1.0uF 17p

### CERAMIC

Plate type 50V. Available in E12 series from 22pF to 100pF and E6 series from 1500pF to 0.047uF 2p

### RADIAL LEAD ELECTROLYTIC

63V	0.47	1.0	2.2	4.7	10	5p
			22	33	47	7p
						13p
						20p
						5p
						8p
						10p
						15p
						23p

### CONNECTORS

#### JACK PLUGS AND SOCKETS

2.5mm	screened	unscreened	socket
	9p	13p	7p
3.5mm	9p	14p	8p
Standard	16p	30p	15p
Stereo	23p	36p	18p

#### DIN PLUGS AND SOCKETS

	plug	chassis socket	line socket
2pin	7p	7p	7p
3pin	11p	9p	14p
5pin 180°	11p	10p	14p
5pin 240°	13p	10p	16p

#### 1mm PLUGS AND SOCKETS

Suitable for low voltage circuits, Red & black. Plugs: 6p each Sockets: 7p each.

#### 4mm PLUGS AND SOCKETS

Available in blue, black, green, brown, red, white and yellow. Plugs: 11p each Sockets: 12p each

#### PHONO PLUGS AND SOCKETS

Insulated plug in red or black	9p
Screened plug	13p
Single socket	7p
Double socket	10p

### LOUDSPEAKERS

56mm dia. 8ohms. 70p 64mm dia. 64ohms. 75p

64mm dia. 8ohms. 75p 70mm dia. 8ohms. 100p

Magnetic earpiece including 2.5 or 3.5mm plug. 15p each

Crystal earpiece including 3.5mm plug. 30p each

### TRANSFORMERS

All 240V Primary.

0 - 6, 0 - 6 @ 0.5A or 0 - 9, 0 - 9 @ 0.4A.	175p
0 - 12, 0 - 12 @ 0.5A or 0 - 15, 0 - 15 @ 0.4A	235p
0 - 9, 0 - 9 @ 1.2A or 0 - 12, 0 - 12 @ 1A.	345p
0 - 12 - 15 - 20 - 24 - 30V @ 1.5A.	455p
0 - 20 - 25 - 33 - 40 - 50V @ 1A.	455p
0 - 20 - 25 - 33 - 40 - 50V @ 2A.	585p
0 - 20 - 25 - 33 - 40 - 50V @ 3A.	715p

Miniature type

6 - 0 - 6, 9 - 0 - 9, 12 - 0 - 12 @ 100mA. 95p

### SOLDERING IRONS

ANTEX X25 (25W) or ANTEX CX (17W) 390p each

Reel of solder (39.6M) 240p each

### POTENTIOMETERS

Single gang Log or Lin 5K - 2M2 28p each

Dual gang Log or Lin 5K - 2M2 80p each

Presets, sub min. type hor. or vert. 100Ω - 2M2 6p each

### CONTROL KNOBS

Ideal for use on mixers etc. Push on type with black base and marked position line. Cap available in red, blue, green, grey, yellow and black. 14p



### SWITCHES

Subminiature toggle. SPDT 70p. DPDT 80p.

Standard toggle. SPST 34p. DPDT 48p.



Slide switches (DPDT) miniature or standard 15p.

Push to make switch. 15p. Push to break switch. 20p.

Wavechange switches: 1P12W, 2P6W, 3P4W, 4P3W. 43p

### BOXES

Folded construction complete with screws.

3 x 2 x 1	52p	4 x 3 x 2	70p	6 x 4 x 3	95p
4 x 3 x 2	64p	6 x 4 x 2	77p	8 x 6 x 2	125p



We now offer one of the widest ranges of components at the most competitive prices in the UK. See catalogue for full details. We welcome callers at our shop in College Road, Bromley, from Mon - Sat, 9am - 6pm (8pm on Weds. and Fridays). Special offers always available.

We also provide an express telephone order service. Orders received before 5pm are shipped same day. Contact our sales office now with your requirements. Goods subject to availability.

**TEL: 01-464 2951/5770**

Quantity discounts on any mix TTL, CMOS, 74LS and Linear circuits: 100+ 10%, 1000+ 15%. Prices VAT inclusive. Please add 30p for carriage. All prices valid to April 1980. Official orders welcome.



Mail orders to: STEVENSON (Dept ET)

**76 College Road, Bromley, Kent BR1 1DE.**

# Lamp Dimmer

## How to Twiddle Your Electricity Bills

*If you're a BRIGHT spark, you will be able to astound your friends with your DIMness simply by building the HE DIMMER.*

THE HE DIMMER IS a self-contained unit, fitting into a standard flush, wall-mounting light switch, which can easily replace your ordinary switch.

The printed circuit board was designed so that it fits into an MK rocker type switch although with modifications it should fit any similar sized switch plate.

Design features of the circuit include preset RV1 to allow for component tolerances and individual preferences of light levels, radio frequency interference suppression and an on board fuse to protect the circuit should anything go wrong (and according to Murphy's Law it normally does). Otherwise the circuit is a fairly standard triac/diac power controller which can be used to dim up to 2 kilowatts of bulb power — a fair amount by any standards.

### CONSTRUCTION

Fit the PCB to the switch plate (with the switch bits removed) first, before any parts are soldered on, as various holes have to be drilled for screws etc. and this is best done without obstruction.

Once this has been done the parts can be inserted. Make extra sure there are no solder bridges across the tracks.

The triac is the only polarised component which, of course, must be inserted correctly. If you obtain the same device as ours, the TRI 400-8, then it can simply be lined up the same way as in the overlay ie with the heat sink tab closest to the coil L1. If you can't obtain the same triac type, then virtually any type can be used as long as you fit the 3 connections G, MT1 and MT2 in the correct places.

Incidentally, the triac is rated at 8 amps, which is about 2 kW of power. At this rating a fair sized heat sink will be necessary, bolted to the triac. However, at bulb ratings up to 200 watts (adequate for house lighting) no heatsink is necessary.

The coil L1 is not critical and therefore easily made by hand. To construct, Scramble, wind 100 turns of 32s.w.g. insulated copper wire around a ½ inch diameter former as in figure 1 (we used the barrel of a pen which was about the right size). Put a spot of glue on the coil of wire and leave it to dry. When dry, slide the coil off the former and fit it to the PCB. Remember to scrape off about half an inch of insulation with wire wool or emery cloth, so that a good soldered connection can be made.



*The HE Dimmer in its wall mounting box. For safety we recommend using a plastic, flush mounting box.*

When the unit is complete it only remains to fit it in the wall and adjust it as described in the section on setting up. Only two connections are necessary — the same two that connect to the back of the existing switch plate and its doesn't matter which way round they are. However, certain safety precautions must be adhered to. If your wall has a metal backing box behind the switch then make sure that nothing on the circuit board touches the box — it may even be necessary to remove it and insert a plastic box in its place.

The PCB has mains voltages on it and for this reason we advise that the board is to be either sprayed or painted with lacquer (nail varnish will do if you have any!???). This will give a degree of protection against shock — which can be fatal.

### SETTING UP

The setting up procedure is simply a matter of adjusting the preset RV1, with RV2 in the low position until the required level of light, in this position, is found. Some people might prefer the main control RV2, to vary from zero to full brightness, but it is probably better to adjust RV1 so that the bulb is just visibly on when the main control is at minimum. This means that it can be visually checked simply by the appearance of the bulb, whether or not the device is off.

Be very careful when adjusting RV1 — do **NOT** use a metal trimmer. Use a plastic one and keep your fingers clear of anything on the PCB whilst connected in circuit.

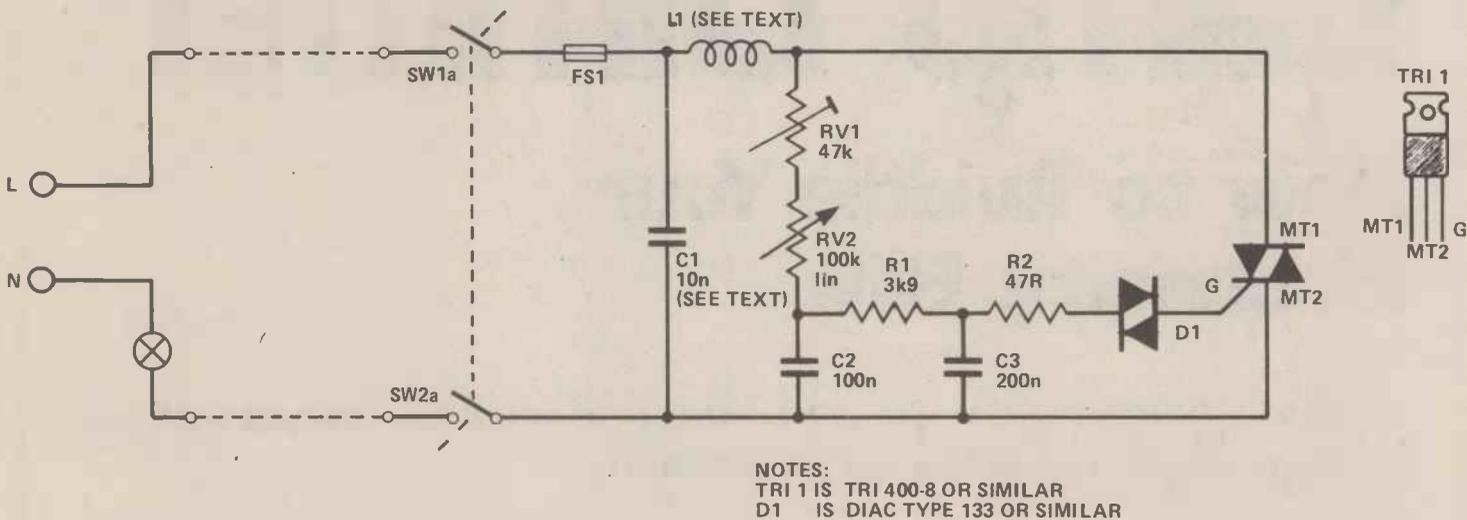


Fig. 1. Circuit diagram of the HE Dimmer, for details of the coil L1 refer to the text and drawing.

## How it Works


The heart of the project is the triac, which is simply an electronic switch which can be turned on by a small pulse of about 5 volts applied to its gate, G. The switch will stay on permanently, until the applied voltage becomes zero, which with mains A.C. occurs at the end of every half cycle, ie 100 times a second.

The triac is switched on every half cycle at a predetermined time during the wave. The trigger or gate pulse can be altered to occur between the beginning and end of each half cycle, the average length of time which the triac is on can be lengthened and shortened, thus altering the average amount of power applied to the bulb, therefore the brightness of the bulb.

The component which produces the trigger is diac D1. A diac only allows current through it when the voltage across it exceeds its triggering voltage (about 32 volts).

All that remains is to vary the position in the cycle when this triggering of the diac at 32 volts occurs. This is done with the RV1, RV2, C2 time delay circuit. Altering RV1 and RV2 alters the time constant of the circuit (ie the time it takes for the capacitor to charge up to the applied voltage) which alters the phase and therefore the point at which the diac triggers, with respect to the voltage applied to the bulb. Varying the potentiometers therefore, alters the average power applied to the bulb.

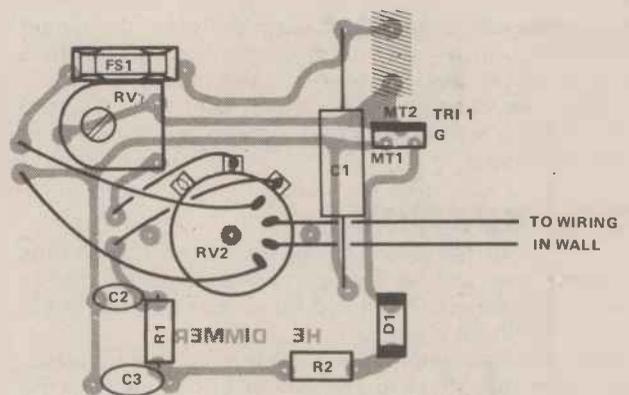Because the voltage applied to the bulb is a bit spiky, radio frequency interference tends to occur and to suppress this, coil L1 and capacitor C1 are included.



NOTE:  
 RV2 IS MOUNTED ON THE P.C.B. WITH ITS SPINDLE PROTRUDING. SOLDER LEADS ONTO THE TAGS OF RV2 AND INTO THE BOARD.

Fig. 2. Overlay diagram for the HE Dimmer, note the position and orientation of the Diac and Triac, especially if using unspecified devices.

## Buylines

The MK rocker type switch plate should be obtainable at any good electrical hardware stockist.

Make sure capacitor C1 is a 300V AC type (or greater), mixed-dielectric capacitors or polypropylene capacitors being normally the only varieties to be so. All components should be readily available.

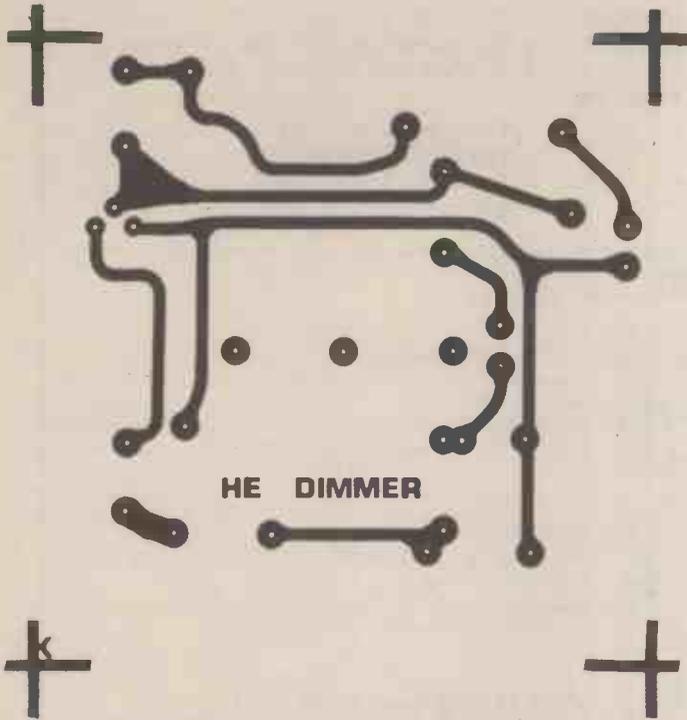


Fig. 3. PCB foil pattern for the Dimmer, take extra care if you make your own PCB to avoid any stray whiskers of copper creating short circuits, mains is dangerous stuff to play around with.



Front panel of the dimmer, experience has shown that a large knob is easier to adjust.



Inside the HE Dimmer, refer to the table for fuse ratings when using high wattage lamps, when adjusting the pot RV1 make sure you use an insulated screwdriver.

## Parts List

### RESISTORS (All 1/4W, 5%)

R1 3K9  
R2 47R

### POTENTIOMETERS

RV1 47K Preset  
RV2 100K LIN with DPST Switch

### CAPACITORS

C1 10n Mixed Dielectric or Polypropylene 300V AC  
C2 100n Polyester  
C3 220n Polyester

### SEMICONDUCTORS

D1 Diac (Type 133 or similar)  
TRI 1 Triac (TRI 400-8 or similar)

### MISCELLANEOUS

L1 Coil, 100 turns (see text)  
FS1 + Holder  
Rocker type switch plate  
P.C.B.  
Knob to suit

FUSE RATING	POWER OF BULBS
60 watts	1/4 amp
100 watts	1/2 amp
180 watts	1 amp
500 watts	2.5 amp
1 kW	5 amp
2 kW	10 amp

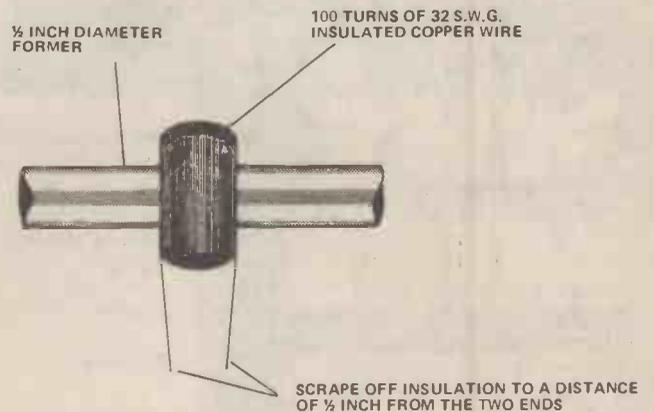


Fig. 4. Details of coil L1, try to keep the coil as neat as possible to avoid any short circuits.

# Hobby Electronics Back Numbers

Shown here are all the past issues with their major features and projects. All are available (at the moment) for just 60 pence each, including post and packing. Send your order to:

**Hobby Electronics  
Backnumbers Dept.  
145 Charing Cross Road  
London, WC2H 0EE**

Shown next to each issue is the relevant code letter to use when ordering Hobbyprints. (See Hobbyprints ad. elsewhere in this issue).



**NOVEMBER 78 (Hobbyprint A)**

**Projects:** Stereo Amplifier, Digital Clock, Wah-Wah Pedal, Bedside Radio.  
**Features:** The Edison Effect, Robots, Hi-Fi Specs, Kit Review, Transducers, Metal Locators etc.



**DECEMBER 78 (Hobbyprint B)**

**Projects:** Metronome, Photon Phone, Audio Mixer, Electronic Dice.  
**Features:** Deep Space Communications, Understanding Bias, Lasers, Photocells, Calculators, The Tesla Controversy etc.



**JANUARY 79 (Hobbyprint C)**

**Projects:** Graphic Equaliser, Touch Switch, Vari-Wiper, Flash Trigger.  
**Features:** BASIC programming, Viewdata, Starship Daedalus, Pinball Machines, etc.



**FEBRUARY 79 (Hobbyprint D)**

**Projects:** Short Wave Radio, Sine/Square Generator, Scratch/Rumble Filter, Car Alarm Project.  
**Features:** Video Tape Recorders, Radioactivity, CA 3130 Circuits, Computer Glossary etc.



**MARCH 79 (Hobbyprint E)**

**Projects:** Light Chaser, Tone Controller, Photographic Timer, Cassanova's Candle.  
**Features:** TV Signals, Test Gear, SW Aerials, Interfering Waves, Communications Satellites, etc.



**APRIL 79 (Hobbyprint F)**

**Projects:** Model Train Controller, Cistern Alarm, Transistor Tester.  
**Features:** The Telephone System, TV Aerials, Electronics in Warfare, Catalogue Survey etc.



**MAY 79 (Hobbyprint G)**

**Projects:** Power Supply, Parking Meter Timer, Digibell, White Noise Effects.  
**Features:** Feedback, Electronic Music, AB Circuits, 555 Circuits, Aerial Tuners, Varicap Diodes etc.



**JUNE 79 (Hobbyprint H)**

**Projects:** GSR Monitor, Envelope Generator, Drill Speed Controller.  
**Features:** Citizen Banned, Display Techniques, Moving Coil Meter, Electronics in Music Pt 2, etc.



**JULY 79 (Hobbyprint I)**

**Projects:** Shark, Baby Alarm, Point Controller, Linear Scale Ohmmeter.  
**Features:** Cassette Decks and Tapes, Binary Numbers, Fixed Resistors, Short Circuits Special, etc.



**AUGUST 79 (Hobbyprint J)**

**Projects:** Home Security System, LED Tachometer, Injector/Tracer, Constant Volume Amplifier.  
**Features:** Security Installation, Variable Resistors, Tools, Satellite Power etc.

# SUBSCRIPTIONS

## WHY MISS OUT?

To: Subscriptions  
Hobby Electronics  
P.O. Box 35  
Bridge Street,  
Hemel Hempstead,  
Herts

I would like a postal subscription to HE starting with the ..... issue. I enclose payment (£6.50 for UK and Ire, £7.50 elsewhere, £11.50 air mail).

Name .....

Address .....

**Next  
Month**


# Hobby Electronics

## ELECTRONIC GAMES



With one eye on Christmas we proudly present the HE review of electronic games. (We enjoy playing with them too). From the humblest hand-held to the most sophisticated video computer, the latest chess playing micros, they're all here next month.

## HOME COMPUTING

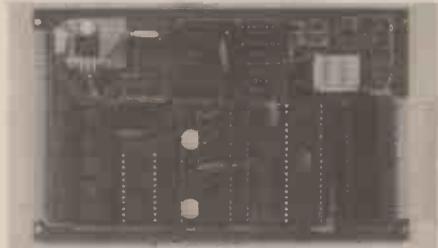

Sorry about the distinct lack of Computing this month, not to worry though, our resident computer expert Pete Howells takes a personal look at the current computer scene, what it's all about, what's happening now and what we can expect in the very near future.

## COMPETITION


We hope we will be able to bring you the results of our August picture competition in next month's HE.

## MICROWAVE COOKING



What's all the fuss about? Chances are it's because most people don't understand Microwave cookers, they've never gained the wide acceptance they deserve in this country. Next month one of the countries leading authorities on microwaves looks at what makes them tick, just how can a Chicken cook in 30 minutes, or a Hamburger in 5? Find out next month.

## AUDIO ANALOGUE FREQUENCY METER

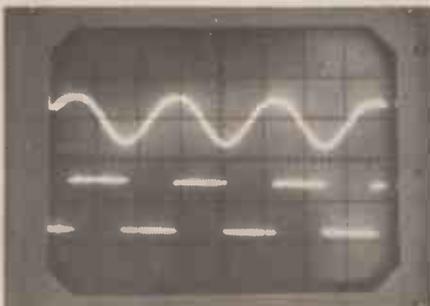

Some people seem to think that unless its got a digital its old-fashioned. We will prove them wrong with this beautifully designed piece of test equipment. The circuit is extremely simple to build yet will give a highly accurate readout of frequencies within the audio range.

If built and calibrated correctly this very useful piece of test equipment should prove to be invaluable for servicing, troubleshooting and experimental purposes. No need to guess anymore.

## HOBBYTUNE

We sat around for ages trying to think of a name for this musical project, nothing seemed to do it justice. See what you think about this stylus operated, miniature organ. We won't promise it'll turn you into a virtuoso overnight but we would be surprised if you're not playing tunes in just a couple of minutes. The HOBBYTUNE has many of the features found on instruments costing three or four times as much to buy, a great project for the kids, it must be better than buying them a drum for Christmas.

## MULTI OPTION SIREN



Yes folks, it's annoy the neighbours time again. Now you can plague them with a variety of different siren noises, yes before you ask, it will sound like an American police siren, but not only that, like a lot of other sirens too. Not recommended for people of a nervous disposition.

## HE TANTRUM



We think the wait will be worthwhile, the Tantrum is a really superb piece of design work. We've incorporated a facility for remote control, (coming up soon) so not only will you be able to enjoy your favourite music from the comfort of your armchair you'll be able to control it as well. Again apologies for its absence this month, they do say it makes the heart grow fonder.

## The October issue will be on sale September 14th

The items mentioned here are those planned but circumstances may affect the actual contents

# Radio Control World

*Just in case the R/C modellers have felt neglected in the past few months we've got Bill Berkinshaw, one of the country's leading experts, to review the current radio control scene and some of the technology behind the latest equipment.*


CONTROL OVER DISTANT EVENTS and activities has always been a source of fascination to mankind, many early weapons such as sling shots, bows and arrows and even the gun were manifestations of this phenomena. Couple this tendency with another natural trait of model making, or image creating and in psychologists terms radio control modelling is an absolute natural.

For many years the Leonardo da Vincis, Stephensons and Cayleys of this world have produced models to prove inventions, only to have to face the problems of operating them without damage and under a degree of control. Many early experiments in the field of aviation attempted to tether and thus control their creations with varying degrees of success. But thanks to modern electronic techniques a degree of precise controllability from a remote situation undreamt of even 20 years ago, is a reality for anyone with the interest, and to be fair, the finance to embrace it. Not that radio control of models or full size cars, aircraft or boats is anything like that new. My father for instance held a licence to operate a spark transmitter for remote control of models in the early 1930's, and full size aircraft such as the D.H. Tiger Moth were flown during WWII under radio control.
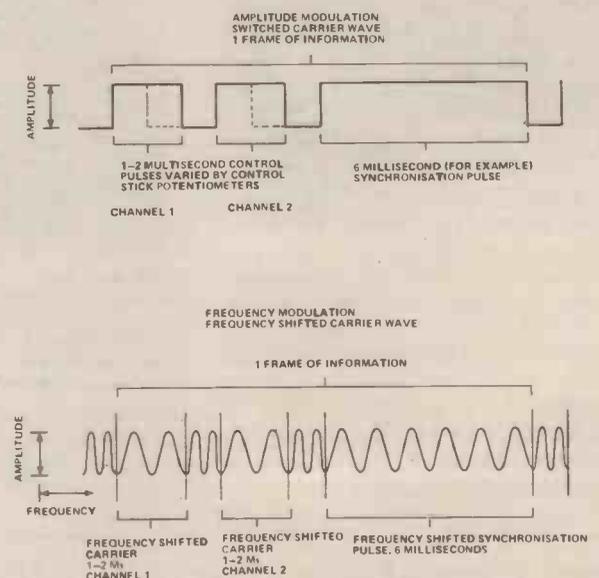
## HOW DOES IT WORK?

A typical radio control system consists of a transmitter, receiver and a number of servos depending on the number of individual items to be operated. Generally the actuation of the controls is by a joystick, either single or dual axis, in the transmitter. Most modern equipment is

*Many modellers now use support trays to operate their transmitters in. This transmitter is a four function type — two dual axis control sticks are fitted.*



described as 'proportional' that is to say a small control stick movement results in a small servo movement — a large control stick movement a large servo movement etc., the servo moving directly in sympathy with the control stick.

The electronics that make it all happen are not very highly sophisticated as modern electronics go, but nonetheless a great deal of careful design work has to go into the system in order that it should work reliably, be light in weight, and of course not cost too much. No electronic knowledge is necessary to operate radio control, only the ability to read instructions and plug in plugs. Most systems are described as Digital Proportional with encoding and de-coding of the signal largely carried out with computer type ICs. A typical transmitter would comprise of an encoding section where a clock generator eg 555 type IC clocks round the various potentiometers coupled to the control sticks. The output from this encoder is then fed, in the form of a chain of pulses of length varying between 1 and 2 mS (milliseconds) plus a larger synchronisation pulse, through a mixer stage and the resulting modulated RF signal fed through various filters to the transmitter aerial.


The RF modulation can be of two basic types, Amplitude or Frequency. Many manufacturers are currently changing over from AM to FM systems for as far as Radio Control is concerned the Frequency Modulation systems tend to exhibit better interference rejection characteristics. This is particularly important at present for the high sunspot activity level, and high illegal CB activity level, are combining to make interference a very real problem for 27 MHz radio control operation. Transmitters are all crystal controlled, most have a plug-in crystal facility, the modellers have an agreed list of 'spot' frequencies within the allocated 27 MHz band. Most modern systems will operate quite happily on 25 KHz channel spacing, many of the latest systems will operate on 10 KHz channel spacing. Normally though 12 spot frequencies only are used ranging from 26.960-27.280 MHz.

## AM OR FM?


The amplitude modulation systems are very simply 'switched carrier wave' transmitters — the carrier-wave being switched on and off in pulses of varying length as dictated by the control stick positions (see Fig. 1) of course for a fair proportion of the time there is no transmission at all and during this time the Automatic Gain Control of the receiver (AGC) tends to open right up and even with correctly damped AGC the receiver is still wide open to any spurious signals around.

An identical means of encoding is used for the Frequency Modulated system but as there is no 'off' time in the data transmission the receiver is at no time 'open' for interference. Modulation is achieved quite simply by employing a capacitatively coupled crystal with a Varicap diode in series, and as the voltage across the varicap is altered the crystal frequency is swung. A deviation of around 1.5 KHz is sufficient and more would not really be desirable as the available bandwidth as specified earlier is only in the order of 10KHz and allowance has to be made for unwanted sideband transmissions when settling on any deviation level as of course sideband deviates just as much as the centre frequency.

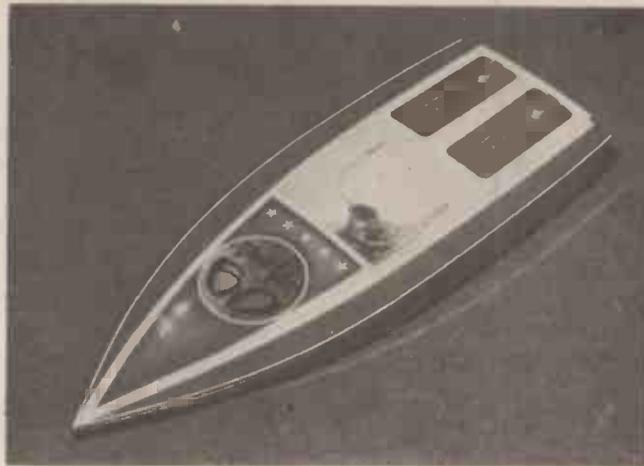Comparatively simple filtering of the RF output is



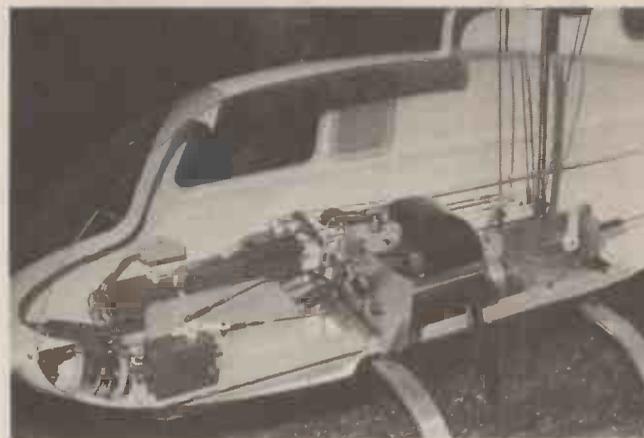*A typical G.R.P. hulled R/C speedboat — this example powered by a 10cc engine. Radio control is limited to throttle and steering. Note the water cooling pipes in the engine compartment.*




*Helicopters are the most complicated of all R/C models. Controls are throttle, collective pitch, main rotor, cyclic pitch (for steering) fore and aft and sideways, and tail rotor pitch. A centrifugal clutch is used between engine and rotors.*




*This superb scale model of the WWII 'Wirraway' was built and flown by twice National Champion David Vaughan. Note the fire extinguisher and detailed instrument panel — and it flies well too!*



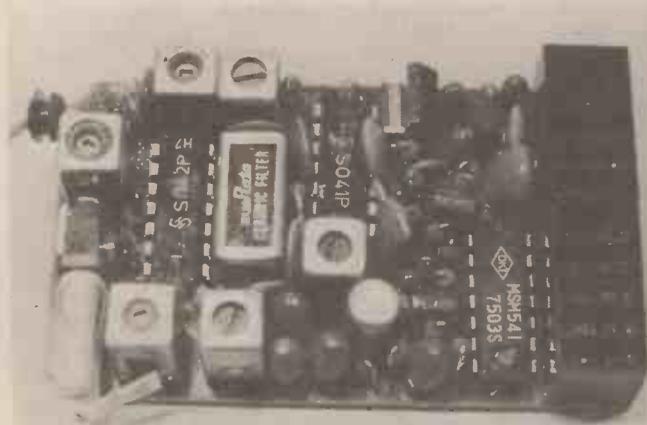Another of David Vaughan's superb models — this one the P51B.



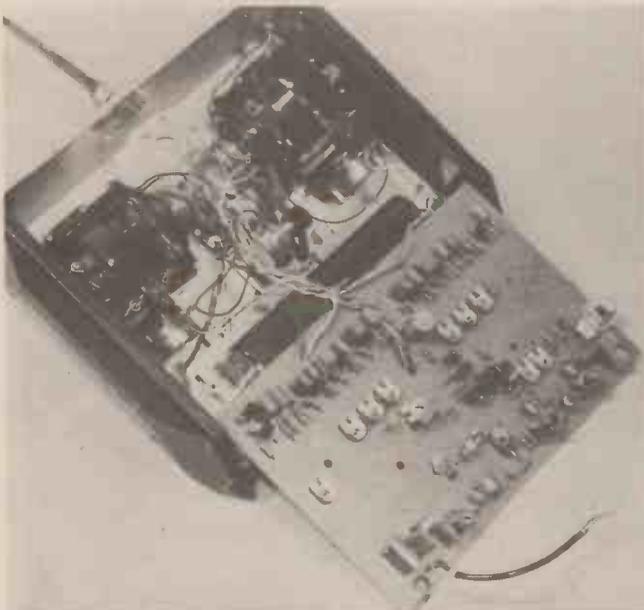Futaba 6 channel FM receiver/decoder. Employs 'transistor radio' type ICs and filter. Decoder chip is the one nearest the output block connector on the right of the photograph. Note the plug-in crystal bottom left of the PC board.



Futaba 6 function FM transmitter. Encoding section is a train of 'half shots' in this case on the section of board nearest the case body. The keen eyed will perhaps spot the varicap diode adjacent to the crystal and the trimmer for adjusting centre frequency. The length of screened cable would normally connect to the aerial and has been removed for photographic purposes.

used, mainly concentrating on removing 13.5 MHz (fundamental frequency of crystal) and 54 MHz (second harmonic) components, but care has to be taken in design for the systems are frequently used with mismatched ie retracted aerials etc. for not all modellers, indeed very few are electronics experts.

## RECEIVERS

Radio control receivers are comparatively simple, not because sophistication is undesirable, but because use of the equipment in models demands that it be light in weight and small in size. Typical radio control receivers weigh in the region of 1.5 ozs and around 2 in square and 5/8in deep. In common with the transmitter, plug-in crystals for easy channel changing are featured. Design follows conventional superhet procedure with double tuned front end, oscillator mixer stage, IF strip, amplification stage then the decoder. Usually this is of CMOS type as any saving in current consumption is worthwhile, and the very low current levels in CMOS ICs represent a very big saving. Discrete component or even TTL logic decoders are now virtually unheard of; 4000 series CMOS types are the norm.

The decoder outputs are fed to a series of servos, these are electro-mechanical devices which receive pulses in turn from the decoder which are images of the pulses encoded by the transmitter. A reference pulse is produced by the servo amplifier which is compared with the pulse received from the decoder. If a difference, either positive or negative is detected then the servo motor is turned on driving the control surface and a feed back potentiometer until the reference pulse, altered by the feedback potentiometer, and the decoded output pulse are equal, whereupon the servo stops. Information updates are fed to the servos from the decoder at the rate of approximately 30 times per second.

Overall accuracy of the system is highly dependent on servo design, not least on the accuracy of the servo feedback potentiometer where much detailed design work has been done to improve upon the resolution and linearity of the servo. Latest of these developments is the use of 'geared-up' feed back potentiometers as use of a larger portion of pot track tends to minimise the effect of minor deviations in resistance from point to point along the track. Of course, similar problems are present right at the very beginning of the chain, at the control stick itself, where potentiometers are also used. It is fair to say that the majority of failures and problems in radio control equipment occur in the electro-mechanical area rather than the electronic.

## POWER

Power for both transmitter and receiver can be either from dry cells (alkaline type preferred) or from rechargeable Nickel Cadmium cells. The latter are by far the most suitable as they are able to cope with occasional high current requirements, have greater capacity and can of course be re-charged indefinitely. From the economic viewpoint alone Ni-Cads are much to be preferred for if any regular use of the equipment is anticipated, continual replacement costs of dry-cells will soon outweigh the cost of Ni-Cads. Transmitter operating voltage varies from make to make but is usually 9.6 volts sometimes 12 V. (either 8 or 10, 12 V Ni Cads). Receiver/servo voltage is almost universally

4.8 volts (4 x 1.2 volt Ni-Cads). Cell capacity is usually 500mAh (milliamp per hour) providing a system operating time of 3-4 hours.

## HOW FAR, HOW HIGH?


IT is fair to say that all modern R/C equipment has more operating range than the normal operator will ever need. The Home Office regulations governing the licensing of R/C transmitters restrict output to a maximum of 1 watt, a level which few transmitters genuinely achieve. This output level is sufficient for the modeller to be able to control his model as far away or as high up as he can see it. It is obvious that if you can't see it, you can't control it, therefore providing the range is sufficient for control of the largest model at the limits of visual range, then all is well; usually about ¾ mile is the maximum needed.

Range is of course not just dependent on transmitter output but also on receiver sensitivity, which despite the incorporation of good AGC is itself a compromise between overloading at close ranges and lack of sensitivity at extreme ranges. A low output transmitter coupled to a very sensitive and selective receiver is perhaps the optimum but receiver electronics come expensive so the reverse situation is more commonplace. FM systems do score in this respect as they do not employ AGC instead a limiting device is employed and the receiver is able to be much more sensitive without fear of swamping when operated close to the transmitter.
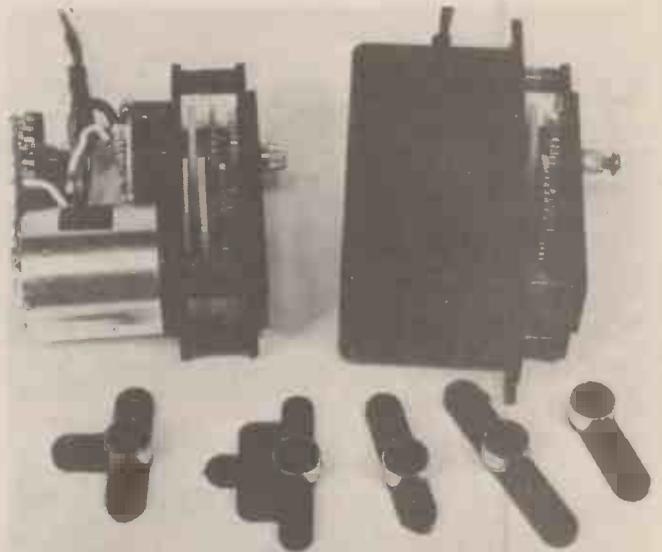
## WHAT CAN BE DONE WITH IT?

Fly, drive, sail or just open your garage door from a distance — there is really no limit to the range of models or devices that can be operated by radio control. Take advantage of the precision and reliability to control superb working replicas of full size aircraft or boats or concentrate on the more sporting side of R/C activities. All over the country every weekend competitions are held for aircraft boats and cars ranging from the concours D'Elegance type to thrilling racing with high speed models. Most users are however purely interested in the dual relaxations of building and operating models. Few are interested in the technical details of the circuitry of their equipment but simply take advantage of the 'plug it together, switch on and use' aspect. Very few ever attempt any sort of servicing and tuning, particularly those who use the equipment in model aircraft, preferring to use the qualified expertise of service agents.

Faults are rare in modern equipment, and if they do occur, are usually as a result of the environment in which the equipment is used. High frequency vibration from high revving two stroke engines, shocks from heavy landings and collisions, moisture from boat use, dirt, are all hazards which the equipment withstands with remarkable reliability. Few uninitiated electronics enthusiasts appreciate the high level of performance that R/C aircraft modellers in particular demand. Most of the models in which the equipment is installed are worth several hundreds of pounds and a momentary malfunction, a click or hiss as heard over a hi-fi loud-speaker can spell total disaster to the R/C aircraft modeller whose model may be flying at less than 10ft above the ground at speeds of up to 150 mph, yet the owner of the equipment will expect 100% reliability for several years of life under the arduous conditions already described.



*Servo internals; motor and amplifier are fairly obvious — the feedback potentiometer is coupled to the amplifier via short flyleads and is integral with the lower gear frame. Typical output levers are arrayed in foreground. Case top is removed in right-hand servo.*




*Radio controlled yachts are a relaxing aspect of R/C modelling, that in the foreground is sailed by Jack Barnard and the other by author Bill Berkinshaw.*



*Typical good quality 6 function system with a comprehensive array of accessories including mains voltage charger for receiver and transmitter batteries, alternative capacity receiver batteries and alternative frequency crystal pairs.*



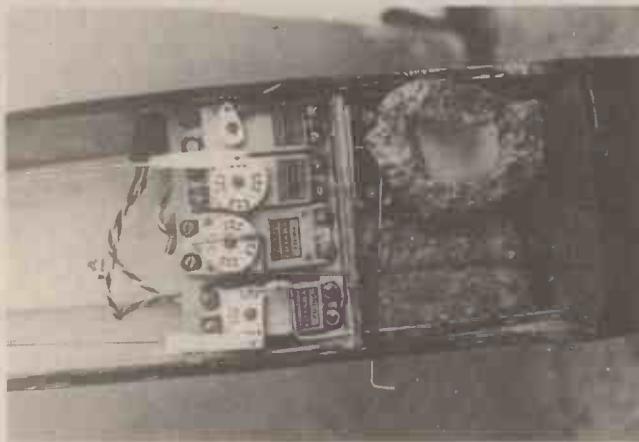*V. Nordigen about to lift the hat from a stake with a Jet Ranger helicopter. Expert pilots can guide models such as this with almost uncanny precision.*



*Installation of servos in a typical R/C aircraft. These operate rudder/steerable nose wheel, retractable nose wheel, elevator, and throttle. The main wheel retract servo and aileron servo are mounted in the detachable wing. Switch and foam packed receiver and battery pack are to the right of the servos.*



*John Ralph, of the North Berks Model Club, launches a thermal soaring glider. The model is towed aloft, as are full size gliders by a line, and then after release float around seeking thermal upcurrents to extend their duration.*

## FUNCTIONS

For model control at its simplest 2 function equipment is the usual. Aircraft can be flown, cars driven or boats floated with only a steering control but few modellers use less than 2 controls. A simple aircraft can be operated by a steering control (either a rudder or ailerons on the wing) and elevators. Some modellers use an engine throttle to control height gain or loss. Cars normally do not need more than two controls, steering and combined throttle and brake (a centrifugal clutch is generally employed). Boats use steering and throttle controls. More complicated aircraft can use a basic four function system, elevators, ailerons, rudder and throttle, plus such items as retractable undercarriage, flaps, brakes, bomb dropping etc. Servos are either of a rotary type output or linear and are coupled up to the various controls by simple wire pushrods and a variety of commercially available plastic horns, cranks etc.

Operating a model by R/C is not anything like as easy as it appears. It is generally fair to say that if the job is difficult to do directly, that is to say 'sitting in it', then to do it remotely by R/C is doubly difficult. The 'Seat of the pants' feel is removed and that otherwise remarkable instrument the human eye is really not very precise at all when it comes to accurately judging distance or altitudes, particularly when the model can be up to half a mile away. It is fairly safe to attempt to drive a car or boat unaided, provided neither are too fast and space is large enough, but to attempt to fly an R/C aircraft without expert help at hand is almost certain to end in disaster. The newcomer to R/C flying will almost certainly not only have his own inexperience to hamper him, but also an untried model and a new engine as well. Most hobby

dealers are able to introduce prospective R/C modellers to like minded enthusiasts in their area.

## **BUILD YOUR OWN**

Home built R/C equipment only accounts for a very small percentage of that in use, largely because the R/C modeller is interested in the flying, driving or boating more than in the building, and also not many have the confidence in their own ability to risk a valuable model to what in their minds might be equipment of dubious reliability. Their fears are to a certain extent unfounded, for there are excellent kits available and just recently excellent designs published. Electronics Today International have recently published details of an AM system whilst Radio Control Models and Electronics have published an FM system. Both publications are experienced in publishing articles of this type and both are almost guaranteed fool-proof provided the instructions are strictly adhered to. Of course the big attraction is the amount of money to be saved which can be quite considerable — possibly up to 50%.

Beware of designing your own equipment, I will accept that most people confident enough to embark on a self design project will probably end up with a system that works but at what cost to fellow modellers'. Badly aligned and poorly designed filter networks on transmitters may not affect your model but what of the other users of the R/C frequency allocations? I would suggest that a minimum of test equipment for the home R/C designer would be a spectrum analyser, digital counter and oscilloscope in order that the transmitter can be adequately checked for sideband emissions.

## **TRY IT YOURSELF**

There are now some 70,000 plus licensed users of Radio Control equipment in the UK all participating in a immensely satisfying and creative hobby. There are a host of model clubs in all areas of the country where any would-be members will receive a warm welcome. If you are interested in seeing R/C models in action either visit your local model shops and enquire (look in the yellow pages) or write to one of the national governing bodies for details of nearest local clubs. Do enclose a SAE to those societies though, and don't forget that a licence is needed. This can be obtained by anyone — no age limits or test, from the Home Office Radio Regulations Department, Waterloo Bridge House, Waterloo Road, London SE1. The cost is £2.80 for 5 years so it cannot be described as expensive.

*SMAE (Society of Model Aeronautical Engineers),  
General Secretary,  
Kimberley House,  
Vaughan Way,  
Leicester.*

*MPBA (Model Power Boat Association),  
The Secretary,  
19 Lea Walk,  
Harpenden, Hert s.*

*BRCA (British Radio Car Association),  
The Secretary,  
7 The Green,  
Werriston,  
Peterborough.*



*Bill Drury adjusts the engine prior to the start of a 10 lap pylon race. Four models similar to the one shown race for 10 laps around a triangular course at speeds approaching 150 m.p.h.*



*A semi-scale VC10 being demonstrated during a model airshow at Woodvale, Lancs. This model is powered by two internal combustion engines in place of the four gas turbines of the original.*



*Past British R/C aerobatic champion and World Champs Team Member Mick Birch starts up the engine in his own design Capricorn model prior to a flight at the British National Champs.*

Ref.	ELECTRONIC BOOKS	Price
126	Boys' Book of Crystal Sets	25p
138	How to Make Aerials for TV (Band 1-2-3)	25p
160	Coil Design and Construction Manual	75p
196	AF - RF Reactance - Frequency Chart for Constructors	15p
200	Handbook of Practical Electronic Musical Novelties	50p
201	Practical Transistorised Novelties for Hi-Fi Enthusiasts	35p
202	Handbook of Integrated Circuits (IC's) Equivalents and Substitutes	100p
203	IC's and Transistor Gadgets Construction Handbook	60p
205	First Book of Hi-Fi Loudspeaker Enclosures	75p
206	Practical Transistor Circuits for Modern Test Equipment	60p
207	Practical Electronic Science Projects	75p
208	Practical Stereo and Quadrophony Handbook	75p
210	The Complete Car Radio Manual	100p
211	First Book of Diode Characteristics Equivalents and Substitutes	95p
213	Electronic Circuits for Model Railways (Reprinting)	100p
214	Audio Enthusiasts Handbook	85p
215	Shortwave Circuits and Gear for Experimenters and Radio Hams	85p
216	Electronic Gadgets and Games	100p
217	Solid State Power Supply Handbook	85p
218	Build Your Own Electronic Experimenters Laboratory	85p
219	Solid State Novelty Projects	85p
220	Build Your Own Solid State Hi-Fi and Audio Accessories	85p
221	28 Tested Transistor Projects	95p
222	Solid State Short Wave Receivers for Beginners	95p
223	50 Projects Using IC CA3130	95p
224	50 CMOS IC Projects	95p
225	A Practical Introduction to Digital IC's	95p
226	How to Build Advanced Short Wave Receivers	120p
227	Beginners Guide to Building Electronic Projects	125p
228	Essential Theory for the Electronics Hobbyist	125p
RCC	Resistor Colour Code Disc Calculator	10p
BP1	First Book of Transistor Equivalents and Substitutes	50p
BP2	Handbook of Radio, TV & Industrial & Transmitting Tube & Valve Equivalents	60p
BP6	Engineers and Machinists Reference Tables	50p
BP7	Radio and Electronic Colour Codes and Data Chart (Reprinting)	25p
BP11	Practical Transistor Novelty Circuits	40p
BP14	Second Book of Transistor Equivalents and Substitutes	110p
BP22	79 Electronic Novelty Circuits	75p
BP23	First Book of Practical Electronic Projects	75p
BP24	52 Projects Using IC741	95p
BP25	How to Build Your Own Electronic and Quartz Controlled Watches & Clocks	85p
BP26	Radio Antenna Handbook for Long Distance Reception and Transmission	85p
BP27	Giant Chart of Radio Electronic Semiconductor and Logic Symbols	60p
BP28	Resistor Selection Handbook (International Edition)	60p
BP29	Major Solid State Audio Hi-Fi Construction Projects	85p
BP30	Two Transistor Electronic Projects	85p
BP31	Practical Electrical Re-Wiring and Repairs	85p
BP32	How to Build Your Own Metal and Treasure Locators	100p
BP33	Electronic Calculator Users Handbook	95p
BP34	Practical Repair and Renovation of Colour TVs (Reprinting)	95p
BP35	Handbook of IC Audio Pre-amplifier and Power Amplifier Construction (Reprinting)	95p
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	75p
BP37	50 Projects Using Relays, SCR's and TRIACS	110p
BP38	Fun and Games with your Electronic Calculator	75p
BP39	50 (FET) Field Effect Transistor Projects	125p
BP40	Digital IC Equivalents and Pin Connections	250p
BP41	Linear IC Equivalents and Pin Connections	275p
BP42	50 Simple L.E.D. Circuits	75p
BP43	How to Make Walkie-Talkies	125p
BP44	IC555 Projects	145p
BP45	Projects in Opto-Electronics	125p
BP46	Radio Circuits Using IC's	135p
BP47	Mobile Discotheque Handbook	135p
BP48	Electronic Projects for Beginners	135p
BP49	Popular Electronic Projects	145p
BP50	IC LM3900 Projects	135p
BP51	Electronic Music and Creative Tape Recording	125p
BP52	Long Distance Television Reception (TV-DX) For The Enthusiast	145p
BP53	Practical Electronic Calculations and Formulae	225p
BP54	Your Electronic Calculator and Your Money	135p
BP55	Radio Stations Guide	145p
TI	TTL Pin Configuration Guide	175p

Please add 25p p&p

**TECHNOMATIC LTD**  
**17 BURNLEY ROAD, LONDON NW10 1ED**  
 (2 minutes from Dollis Hill Tube Station) (Ample parking space)  
 Telephone: 01-452 1500. Telex: 922800

7400	14p
7404	18p
7408	20p
7410	16p
7413	32p
7420	18p
7430	17p
7447	65p
7473	36p
7490	35p
7493	35p
74121	30p
CA3080	77p
CA3140	75p
ICL8038	370p
LM380	80p
LM741	24p
NE555	24p
T8A800	100p
ZN414	100p

DIL SOCKETS	
8pin	12p
14pin	13p
16pin	14p

Large range of components available  
 Send SAE

ANTEX SOLDERING IRONS	
C-15W	390p
CX-17W	410p
CCN-15W	410p

COPPERCLAD	
X-25W	410p
Spare bit	50p
Stand	170p

VEROBOARDS	
0.1 Copperclad	
2 1/2 x 5	62p
3 1/2 x 2 1/2	53p
3 1/2 x 3 1/2	62p
3 1/2 x 5	69p
3 1/2 x 17	240p

POCKET MULTIMETERS	
KRT100	580p (1000 ohms/V)
LT22	1360p (20kohms/V)
Test Lead Kit	160p
(Prods, Croc clips, bananas, Spades)	
10 Test leads with Croc Clip at each end	110p

EXPERIMENTOR BREADBOARDS	
(No soldering, suitable for DIL ICs)	
For 1 IC Circuit (up to 22pin)	
EXP325	180p
For up to 3x14pin DIL ICs	
EXP350	360p
For up to 5x14pin DIL ICs	
EXP300	641p
IC Test Clips	
14pin	285p
16pin	297p
Logic Probe	1900p

# TEE SHIRTS

We won't guarantee HE Tee-Shirts will make your soldering any better, we won't even claim it will make your projects work first time. What we will say is that it will protect your body from harmful Ultra-Violet radiation from the sun, embarrassing Tomato Ketchup stains on your hairy chest and overweight wallets (if bought as directed in sufficient quantity).

Yes folks, for just £2 all inclusive you can be the first kid on your block to own a brand new HE Tee-Shirt. If you buy more than one your torso need never be left unprotected whilst your other one is in the wash.

Send your cheque, PO or anything negotiable to:  
**HE TEE SHIRTS, 145 Charing Cross Rd, London WC2H 0EE.**



**SINCLAIR PRODUCTS:** New 10MHz scope pos. PFM 200 £52.89, case £3.40, adaptor £3.40, connector kit £11.27. Microvision TV UK model £91.44, mains adaptor £6.88, POM35 £29.76, mains adaptor £3.40, case £3.40, DM350 £71.82, DM350 £102.17, DM235 £52.66, rechargeable mats £7.99, mains adaptor £3.94, case £9, recharge prog. calculator with accessories £23.37.

**COMPUTER GAMES:** Star chess £62, chess champion 6 £94, chess challenger 7 £91, chess challenger 10 £152.50, chess challenger pos, checker challenger 2 £46, checker challenger 4 £88, Atari duo computer £147, cartridges £14.32.

**COMPONENTS IN:** 148 1.4p, 1N 4002 3.1p, 741 18p, 1N1129 183p, 1N184p, 1N211h 1N213h, 1N214c 5p, resistors, 1W 5%, 1/4W 1% 10R to 10M 1p, 0.8p for 5%, of one value 16V electronics, 1 1/2 5 10 20uF 5p, 100uF 6p, 1000uF 10p, 1 1/2 1N41C 1.20, diode pen 84p, 40 sq. ins per 64p, polyethylene capacitors E12 E3V 70 to 1000uF 3p, 1 1/2 1 30u4p, ceramic capacitors 50V E6 32p to 100 2p, 200W E24 27 to 33v 7p, 100W 200W 0.1W, 100 0.4M 7.2p.

**TV GAMES:** AY 3-8500 + £69.53, 1N41C £5.27, AY 3-8610 - kit £16.51, stunt even more + kit £16.72, AY 3-8603 1mp £9.48.

**TRANSFORMERS:** 0.46V 100ma 76, 1 1/2 £2.50, 1 1/2 1 1/2 £2.01, 9.9 9V 75ma 76p, 1 1/2 £2.12, 1 1/2 £2.77, 1.2 0.17V 100ma 92p, 1 1/2 £2.65.

**IC AUDIO AMPS:** with prog. JCL12 6W £2.08, JCL20 6W £3.14.


**BATTERY ELIMINATORS:** 3-way type 6 7 8 9v 300ma £3.14, 100ma ratio type with press-studs 9v £3.57, 9v - 3v £4.79, Car converter 12v input output 4 1/2 6 7 7 1/2 9v 800ma £2.66.

**BATTERY ELIMINATOR KITS:** 100ma ratio type with press studs 4 1/2v £1.49, 6v £1.49, 9v £1.49, 4 1/2 - 4 1/2v £1.92, 6+6v £1.92, 9+9v £1.92, 3-wire type 3-way types 3 4 5 6 7 8 9 12 15 18v 100ma £2.98, 1 amp £6.81, stabilised power kits 2 18v 100ma £2.98, 2.30v 1A £7.40, 2.30v 2A £11.66, 12v car converter 6 7 8 9v 1A £1.44.

**T-DEC AND CSC BREADBOARDS:** s.d.c. £4.05, 1 dec £4.28, u-dec £4.69, u-dec £7.16, 16 di adaptor £2.31, exp4b £2.64, exp300 £6.61, exp150 £3.62, exp325 £1.84.

**BI-PAK AUDIO MODULES:** 450 £24.03, AL60 £4.97, PA100 £17.33, sm80 £4.57, sm80 £6.08, Stereo 30 £20.57, AL30 £4.04, PA12 £7.77, PS12 £1.42, MA60 £36.23.

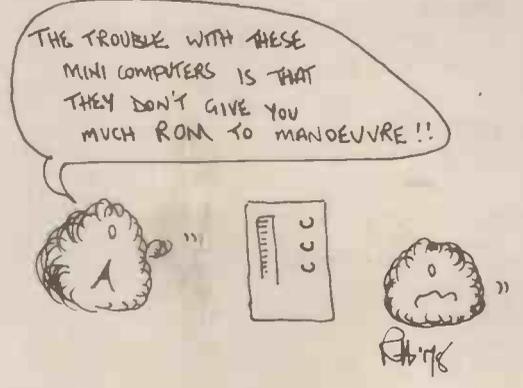**SWANLEY ELECTRONICS**  
 Dept. HE, 32 Goldsai Road, Swanley, Kent  
 Post 30p extra. Prices include VAT. Official and overseas orders welcome. Lists 20p post free.



# Ultrasonic Switch

**Repel insects, upset small furry animals and confuse your cat with HE's Ultrasonic Switch.**

INVISIBLE RAYS have always exerted a considerable fascination on man down the ages. Isaac Newton watched apples falling under their influence and Uri Geller bent spoons with them (or did he?)

This project falls somewhere between these two extremes of the sublime and the ridiculous. It uses ultrasound; a high frequency sound, well above the range of human hearing to control a relay. By selecting a suitable type you can control your TV, Hi-Fi or bedside light at the touch of a button or as you will see later, with a snap of the fingers.

## NOISE ANNOYS

The unit is silent in operation. As the ultrasonic carrier beam consists of very high frequency (40 kHz) waves, special transducers have to be used as ordinary microphones and loudspeakers are very inefficient at this frequency. These transducers are just like crystal microphones and earphones except that they are designed to be resonant, ie very sensitive at a particular frequency. The receiver and transmitter units have different characteristics and best results will be obtained



*Completed units make an attractive and efficient pair.*





ceilings so that greater range will be achieved in a sparsely furnished room or a corridor and satisfactory operation can often be obtained with the transmitter pointing away from the receiver. Our unit gave a maximum effective range of about twenty feet.

### CONSTRUCTION AND USE


Any method of construction may be used although our PCBs are recommended and no special precautions are necessary. However, if you use your unit to control a mains operated device ensure that the mains is kept safely isolated from the control circuitry and use a relay whose contacts are rated for the job.

We mounted our 'Ultraswitch' in an earthed metal case. No special care was taken to protect the transducer from mechanical shock and the unit worked quite reliably.


The transmitter was housed in a small vero-box. Ensure that the transmitter tuning control is easily accessible. It should be adjusted for maximum range. There are no other adjustments to make.

Ultrasonic waves are present in many 'natural' sounds and you will find that the switch will operate at varying range in response to jangling keys, crumpling paper and even, at close range, a snap of the fingers. A novel trick is to operate the unit with a handclap.

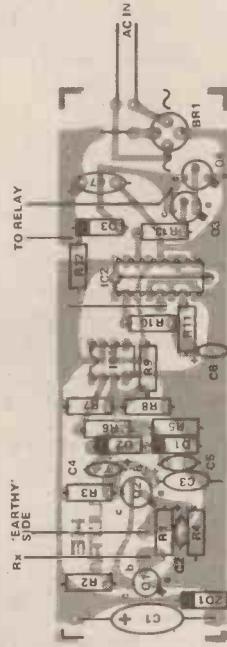Remember to use a suitable relay for your application and make all connections safe. Then press that button and turn on.



# Short Circuits

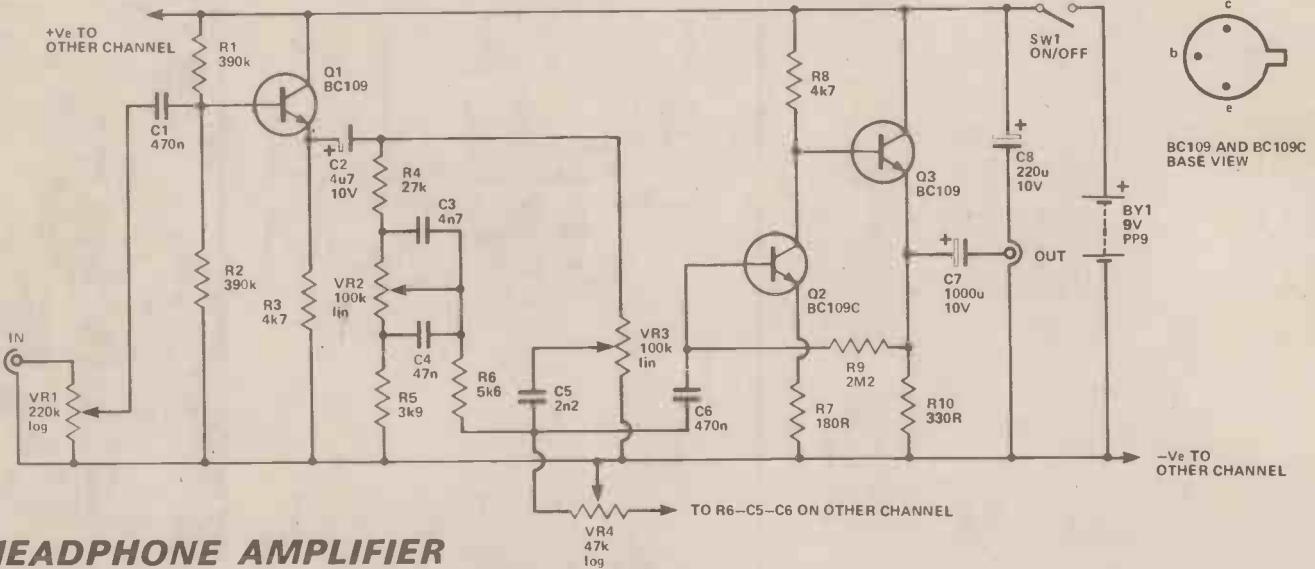

## HEADPHONE AMPLIFIER

This simple stereo amplifier will drive a pair of stereo headphones, and can take its input from either a tuner or cassette deck. It has the advantage over a normal stereo amplifier of being small, completely self contained, and therefore very portable. Of course, many tuners and cassette decks have a headphone output, but this often lacks sufficient drive, and there are usually no tone controls (or volume and balance controls in some cases). This circuit gives the usual

tone, balance, and volume control facilities, and also has plenty of drive. Ideally the unit should be used with phones having an impedance of a few hundred ohms each, and most good quality types fall into this category. It also seems to work perfectly well with inexpensive 8 ohm types.

The circuit shown here is for one channel, all the components being duplicated in the other channel except for S1, BY1, and RV4, which are obviously common to

both channels. The two RV1s are a dual gang component, as are the two RV2s and the two RV3s.

The input signal is applied to volume control VR1, and from here it is coupled to a buffer stage based on Q1. This gives the unit a reasonably high input impedance of at least 100k. Its output feeds a conventional passive tone control circuit that can give bass lift or cut using RV2, and treble lift or cut using RV3. RV4 is used in the standard balance control arrange-

ment. The output from the tone controls is coupled by C6 to a two stage direct coupled amplifier. This uses Q2 in the common emitter mode to give sufficient voltage gain for an output level of up to about 2 V RMS from most sources. Q3 is an emitter follower buffer stage which matches the output from Q2 to the relatively low impedance of the headphones.

The unit has a total current consumption for both channels of about 30mA.

## NICAD CHARGER


This charger is intended for use with the popular AA size NiCad batteries (similar to ordinary HP7 cells). A special charger is needed for NiCad cells because they have a very low internal resistance, leading to an excessive charging current even if the applied voltage is only marginally high. The charger must therefore incorporate a circuit to limit the charge current to the appropriate level.

In this circuit, T1, D1, D2, and C1 form a conventional stepdown, isolation, fullwave rectifier, and smoothing circuit. The other components provide the current regulation. IC1 is used as a comparator with discrete buffer stage Q1 giving a suitably high output current capability for this application. IC1's non-inverting input is fed with a 0.65 V. reference potential provided by R1 and D3. The inverting input is taken to earth by R2 under quiescent conditions, causing the output to go fully positive. With a NiCad cell connected across the output a high current will attempt to flow, causing the voltage across R2 to increase. It can only rise to 0.65V.


however, as a higher voltage here reverses the comparative input levels to IC1, resulting in the output going lower in voltage, and reducing the voltage across R2 back 0.65 V. The maximum output current (and the charge current obtained) is therefore the current produced with 0.65 V. across 10 ohms, or 65 mA. in other words.

Some AA NiCad cells have a maximum recommended charge current of only about 45 or 50 mA, and for these types R2 should be increased to 13 ohms in order to

obtain the appropriate charge current. Some rapid charge types will take 150 mA, and this necessitates reducing R2 to 4.3 ohms (3.3 ohms plus 1 ohm in series if a suitable component cannot be obtained). Also, T1 should be changed to a type having a current rating of 250 mA., and Q1 should be fitted with a small bolt-on finned heatsink. The unit can charge up to four cells (six if T1 is made a 12 V type), and these must be connected in series across the output, not in parallel.

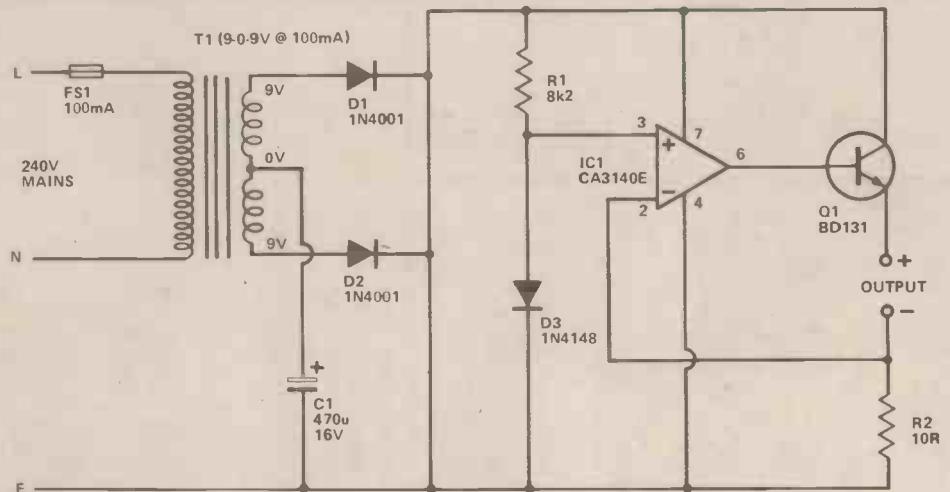

CA3140E TOP VIEW

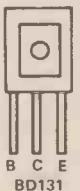

## 24 TUNE DOOR CHIMES

**DOOR TUNES £16.44 + VAT.**

Waddington's Videomaster announce a doorbell that doesn't go Brrringgg, Ding-Dong or Bzzzzz. Instead it plays 24 different classical and popular tunes. It will play the tune you select for your mood, the season or the visitor you are expecting to call. Door tunes is not only great fun and a wonderful ice breaker, but is also very functionally and beautifully designed to enhance your home. There is something for Christmas, something for your continental visitors or your relations from the states, and even something for the Queen. Door tunes is easy to install and has separate controls for volume, tone and tempo.



## T.V. GAMES

**PROGRAMMABLE £29.50 + VAT.  
COLOUR CARTRIDGE T.V. GAME.**

The TV game can be compared to an audio cassette deck and is programmed to play a multitude of different games in COLOUR, using various plug-in cartridges. At long last a TV game is available which will keep pace with improving technology by allowing you to extend your library of games with the purchase of additional cartridges as new games are developed. Each cartridge contains up to ten different action games and the first cartridge containing ten sports games is included free with the console. Other cartridges are currently available to enable you to play such games as Grand Prix Motor Racing, Super Wipeout and Stunt Rider. Further cartridges are to be released later this year, including Tank Battle, Hunt the Sub and Target. The console comes complete with two removable joystick/plug controls to enable you to move in all four directions (up/down/right/left) and built into these joystick controls are ball serve and target fire buttons. Other features include several difficulty option switches, automatic on screen digital scoring and colour coding on scores and balls. Lifelike sounds are transmitted through the TV's speaker, simulating the actual game being played. Manufactured by Waddington's Videomaster and guaranteed for one year.



### EXTRA CARTRIDGES:

**ROAD RACE - £8.87 + VAT.**

Grand Prix motor racing with gear changes, crash noises

**SUPER WIPEOUT - £9.17 + VAT.**

10 different games of blasting obstacles off the screen.

**STUNT RIDER - £12.16 + VAT.**

Motorcycle speed trials, jumping obstacles, leaving various rows of up to 24 buses etc.

**NON PROGRAMMABLE TV GAMES**

**6 Game - COLOURSCORE II - £13.50 + VAT.**

**10 Game COLOUR SPORTSWORLD £22.50 + VAT.**

## CHESS COMPUTERS

**STAR CHESS - £56.09 + VAT.  
PLAY CHESS AGAINST YOUR PARTNER.**

Using your own TV to display the board and pieces, Star Chess is a new absorbing game for two players, which will interest and excite all ages. The unit plugs into the aerial socket of your TV set and displays the board and pieces in full colour for black and white on your TV screen. Based on the moves of chess it adds even more excitement and interest to the game. For those who have never played, Star Chess is a novel introduction to the classic game of chess. For the experienced chess player, there are whole new dimensions of unpredictability and chance added to the strategy of the game. Not only can pieces be taken in conventional chess type moves, but each piece can also exchange rocket fire with its opponents. The unit comes complete with a free 18V mains adaptor, full instructions and twelve months guarantee.



**CHESS CHALLENGER 7 - £86.65 + VAT.  
PLAY CHESS AGAINST THE COMPUTER.**

The stylish, compact, portable console can be set to play at seven different levels of ability from beginner to expert including "Mate in two" and "Chess by mail". The computer will only make responses which obey international chess rules. Casting, on passant, and promoting a pawn are all included as part of the computer's programme. It is possible to enter any given problem from magazines or newspapers or alternatively establish your own board position and watch the computer react. The positions of all pieces can be verified by using the computer memory recall button.



**ELECTRONIC CHESS BOARD TUTOR £19.75 inc. VAT.**

A special bulk purchase of these amazing chess teaching machines enables us to offer them at only £19.75 less than half recommended retail price. The electronic chess tutor is a simple battery operated machine that can actually teach anyone to play chess and improve their game right up to championship level. This machine is not only for total beginners but also for established players wanting to play better chess. Unit contains the electronic chessboard with 32 chess pieces, a 64 page explanatory booklet and a set of 32 progressive programme cards including 8 beginners cards, 16 check mate positions, 9 miniatures, games, 5 openings, 3 end games, 28 chess problems and 2 master games.

Price includes unit with wood grained housing, and Staunton design chess pieces. Computer plays black or white and against itself and comes complete with a mains adaptor and 12 months guarantee.

**OTHER CHESS COMPUTERS IN OUR RANGE INCLUDE:**

**CHESS CHAMPION - 6 LEVELS £82.87 + VAT.**

**CHESS CHALLENGER - 10 LEVELS - £143.06**

**+ VAT.**

**BORIS - MULTI-LEVEL TALKING DISPLAY £165.28**


**+ VAT.**

## DRAUGHTS COMPUTERS

**CHECKER CHALLENGER 2 LEVELS £43.98 + VAT.  
4 LEVELS £80.09 + VAT.**

The draughts computer enables you to sharpen your skills, improve your game, and play whenever you want. The computer incorporates a sophisticated, reliable, decision-making microprocessor as its brain. Its high level of thinking ability enables it to respond with its best counter moves like a skilled human opponent. You can select offence or defence and change playing difficulty levels at any time. Positions can be verified by computer memory recall. Machine does not permit illegal moves and can solve set problems. Computer comes complete with instructions, mains adaptor and twelve months guarantee.

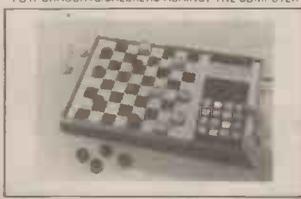**PLAY DRAUGHTS/CHECKERS AGAINST THE COMPUTER**



## FOR FREE BROCHURES - SEND S.A.E

For FREE illustrated brochures and reviews on TV and chess games please send a stamped addressed envelope, and state which particular games you require information on.

Callers welcome at our shop in Welling - demonstrations daily - open from 9am-5.30pm Mon Sat 19am-1pm Wed.

To order by telephone please quote your name, address and Access/Barclaycard number. Postage and Packing FREE.

**AJD DIRECT SUPPLIES LIMITED, Dept. HE9, 102 Bellegrave Road, Welling, Kent DA16 3QD. Tel: 01-303 9145 (Day) 01-850 8652 (Evenings)**

# SPECIALS FROM MODMAGS

Mark your envelopes Specials, and send them to: Specials, Modmags Ltd, 145 Charing Cross Road, London, WC2H 0EE.

### ETI CIRCUITS

**Books 1 & 2.**

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal - hardly surprising when the circuits cost under 1p each!

**£1.50 + 25p P&P each.**



**electronics tomorrow** 75p



### ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone - none of which have appeared in ETI - and a look at the future of MPUs, audio, calculators and video. How can you not read it?

**75p + 25p P&P.**

### TOP PROJECTS

**Book 1 + 2: £2.50 + 25p P&P.**

Master mixer, 100W guitar amp., low power laser, printer, transistor tester, mixer preamp., logic probe, Ni-Cad charger, loudhailer, 'scope callibrator, electronic ignition, car theft alarm, turn indicator cancellor, brake light warning, LM3800 circuits, temperature alarm, aerial matcher, UHF-TV preamp., metal locator, four input mixer, IC power supply, rumble filter, IC tester, ignition timing light, 50W stereo amp. and many more.

**Book 3: SOLD OUT! Book 4: £1.00 + 25p P&P. Book 5: £1.00 + 25p P&P. Book 6: £1.00 + 25p P&P.**



### TOP PROJECTS

**Book 7: £1.25 + 25p P&P.**

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, IB metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.

### ELECTRONICS - IT'S EASY

**Books 2 & 3.**

Our successful beginners' series came to an end some time ago now, and the whole series is available from us in reprint form. The three books between them contain all the information presented in the series (sometimes in more detail) and together form an excellent starting point for anyone interested in learning the art of electronics.

**£1.20 + 25p P&P each.**



### INTO ELECTRONICS PLUS

The complete series of Ian Sinclair's series Into Electronics Plus a selection of some of the most popular and informative articles from HE. Everything from Home Computing to making your own PCBs. £1 + 25p P&P.

# Electronic Timekeeping

## Seconds Out

***If you want to know the time ask a policeman. That may not be such a bad idea these days, especially if his little radio is capable of picking up the time code from Rugby. The ever punctual Rick Maybury looks at atoms that tick phones that tock and watches that don't make any noise at all.***

IT HAS ALWAYS BEEN EASY to tell the time, even if you haven't got a clock or watch you could probably guess to within half an hour. Even before the development of reliable mechanical timepieces, the sundial, sand clock, water clock or even a slow burning candle could indicate the time to the nearest minute. Probably the single most important invention in timekeeping was the pendulum in 1582, it enabled time to be measured to the second.


After that things remained fairly static for the next couple of hundred years. Mechanical escapements improved over the years to such a degree that fractions of a second, as little as 100th of a second, could be accurately measured. Very little new technology came into the field of timekeeping until along came our old friend electricity, then it all began to happen.



***Electronic Timekeeping, Hobby Electronics style, these are just some of the examples of electronic timekeeping available from our Marketplace special offers. The HE Digital Clock was featured as a project in our very first issue in November '78.***
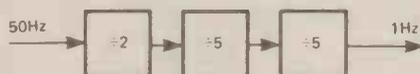
## TIME ON TAP


At first electricity just replaced mechanical energy in electric clocks, until some bright spark in 1918 discovered that an AC electric motor could be synchronised (synchronous motor) to the frequency of the mains. It didn't take long for the electricity board to latch on to this and ensure that over a 24-hour period their generators maintained an average frequency. A clock locked to mains frequency could be compared with a known standard and any losses or gains by the mains-linked clock could be compensated for by slowing down or speeding up the generators. This system of using a central oscillator was the forerunner of today's central standard clock operated by the National Physical Laboratory.



*Divider chain for decoding the mains 50 Hz into a 1 Hz output, the 1 Hz is then used to drive a further chain (see page 54) which will generate the various hours, minutes, seconds and calendar outputs.*
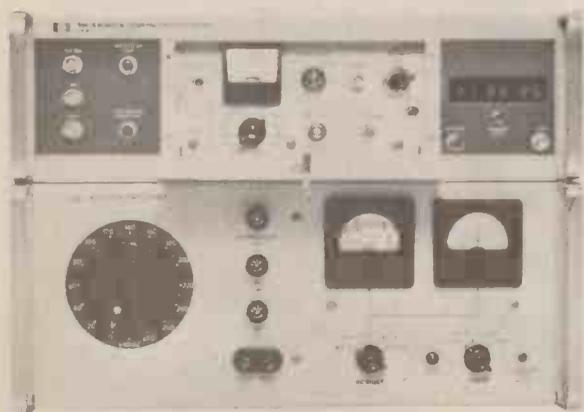
## ATOMIC TICK TOCK

The NPL clock and all standard clocks around the world are based on Atomic Time (AT). There are two main methods of deriving atomic time, they are both based on the natural vibrations of certain materials. These vibrations or Atomic Resonance happens to be one of nature's invariables, rather like the speed of light, it is a fixed constant.




*Atomic clocks. The upper one is a laboratory standard Cesium Beam Frequency Reference, a time output is displayed on the right. The lower one is a portable version of the Cesium Beam clock intended for experimental use, the freedom from mains electricity enables the clock to operate safely even during power cuts.*

The oldest and most accurate type of atomic clock is the Cesium Atomic Beam Controlled Oscillator, quite a mouthful for a really quite simple device. (No we won't be featuring one as a project in HE, it's not *that* simple). The 'clock' is based upon a quartz oscillator, usually running at 5 MHz. This is multiplied up, to the resonant frequency of Cesium. This is a good point to do a bit of defining:

*A second is defined as: The duration of 9,192,631,771 periods of transition within the Cesium atom.*

So to put it crudely the 5 MHz is bumped up to around 9192 MHz and fed to a microwave cavity full of Cesium vapour. The Cesium will of course resonate at only that frequency. Any disparity between the quartz oscillator and the resonating Cesium will generate a difference signal that can be 'feedback' to the crystal oscillator. A frequency lock circuit keeps the crystal oscillator running at the same frequency as the vibrating cesium atoms. In practice the output from this now very stable oscillator is divided down to a usable frequency, usually 1 MHz and 100 kHz so further manipulation will provide an output suitable for timekeeping.

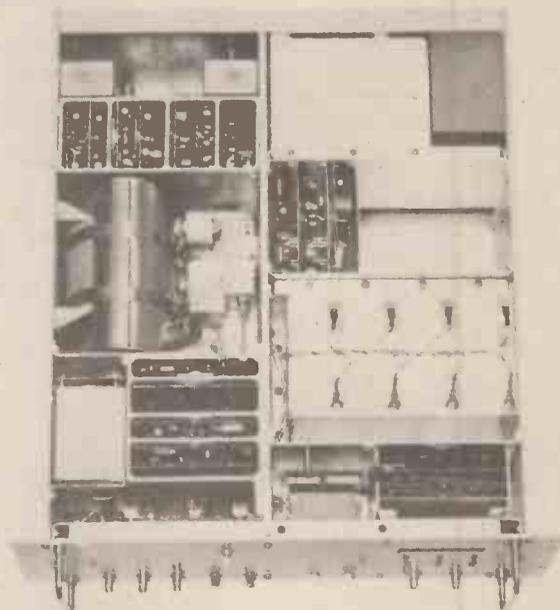

*Inside an Atomic Clock, the cylinder in the middle, on the left-hand side is the actual gas cell, the control circuitry and quartz oscillators can be seen at the top, again on the left.*

The second main type of Atomic clock is the Rubidium Gas Cell Controlled Oscillator. To cut a very long story short, the Rubidium clock operates in a very similar manner to the Cesium clock. Suffice it to say that it is not quite as accurate in the long term as the Cesium clock, variables like the pressure of the Rubidium vapour and the 'buffer gas' that has to be mixed with the Rubidium vapour can affect its overall stability. (We are still talking about a second in a thousand years, but who's quibbling, its doubtful if anyone is going to be around that long to complain).

Of the two main types of Atomic Clock the Cesium clock is referred to as a 'Primary Standard,' that simply means they cannot be calibrated because other than other Cesium clocks there's nothing accurate enough! The Rubidium clock because of its slight deficiencies is relegated to the Secondary Standard league.




It's interesting to note that the United States national standard clock consists of no less than a dozen Cesium clocks all checking one another. Our own British Standard clock is operated by the National Physical Laboratory and a comprehensive time signal is transmitted via radio from their Rugby laboratories.
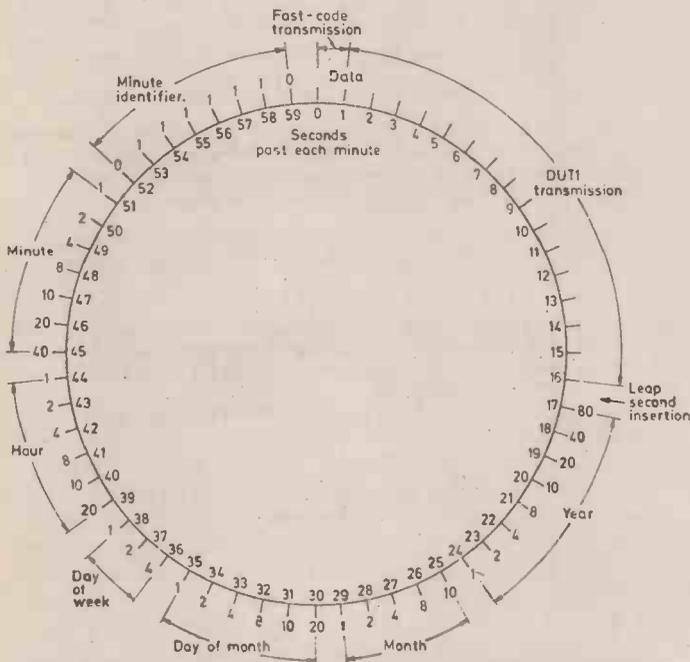
## IT'S NOT CRICKET

The Rugby clock is designated the call sign MSF and is transmitted on 60 KHz at around 50 kW RF power. It can be heard on a specialised receiver throughout most of western Europe. The actual signal transmitted consists of three 'codes', the first two are designated; Fast Code and DUTI. The third code is a Slow Code using UTC or Co-ordinated Universal Time, (probably French if its back to front). The difference between the two can be about one second. UTC is based on the solar cycle, (the same as GMT and BST), as the earth does not rotate on its axis or around the Sun at constant speed its necessary to introduce a 'leap second' every now and again. Strangely enough this was only noticed when the Atomic Clock was developed. The first two codes are based on Atomic Time, the code DUTI stands for Difference between Universal Time and is a slow version of the Fast Code. (Confusing isn't it?)


The Fast Code is transmitted during the first second of each minute and consists of about 30 bits of BCD (Binary Coded Decimal) information giving the Hour, Minute, and Day and Date. The DUTI signal is transmitted between the first and 16th second (Hence Slow Code) and contains all the information of the Fast Code, except at a slower rate. The 17th second is set aside for a control bit to indicate whether or not a 'Leap Second' need be inserted. The final segment from the 17th to the 59th second is full of BCD information for the UTC time.



*The Rugby MSF clock, this diagram represents one minute in the clock's cycle. The fast code lasts from the zero mark to the first second. The two fast codes are from the second second (oh dear, oh dear) to the 16th second and the 17th to the 59th.*

Special receivers can decode this information directly into a time readout. In practice though a receiver will only decode one of the three codes. Being a radio signal

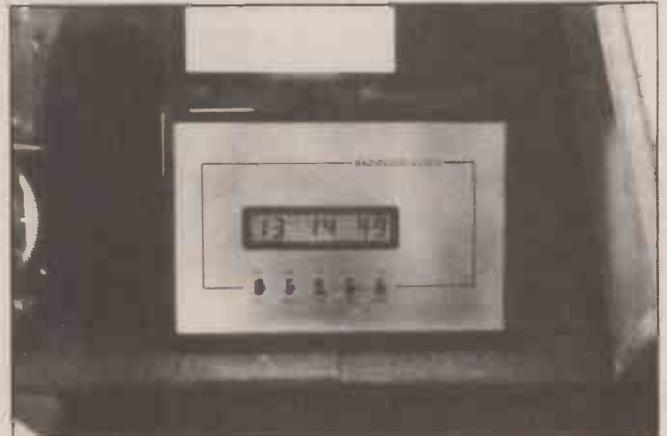it is freely available to anyone wanting to know the right time, and we mean the right time. Recent Cesium clocks are quoted as having an accuracy of not less than one second in 5,000 years.



*A typical MSF receiver, this one operates on one of the 'slow codes', as you can see the controls are kept to a minimum. We wonder how long it will be before a domestic version is on sale.*

## TIM AND TELETEXT

Both TIM (the Post Office speaking clock) and the BBC (Ceefax) and IBA (Oracle) Teletext services are linked to the Rugby MSF time signal.

TIM is a pre-recorded (in 1963 would you believe) on to a rubber tape (mixed with Iron Oxide particles you fool). The rubber tape or 'tyre' is fitted over a spinning brass drum. The 'tape' is split into 79 tracks containing all the well known phrases. Track number one has the 'At the third stroke it will be . . . ' phrase. Tracks 2 to 12 have the hour phrases, ' . . . o'clock'. The next 60 tracks have the minutes, 'one to fifty nine', and the final six tracks have the ten second intervals and the famous 'precisely'. In all there are 12 replay heads scanning the 'tape, they are not actually in physical contact with the tape to avoid wear.



*Mr and Miss TIM, the lady is Miss Pat Simmons who gets something like 430 million phone calls a year; we're told she even phones herself every morning to check the time. Pat retired in 1976 but her original recording made in 1963 will continue for many years to come. The recording actually took over two weeks to record, we're not surprised.*

# Electronic Timekeeping

There are four main speaking clocks in the British Isles, one in constant use (plus one for backup and checking) in London and a further two in Liverpool.

The accuracy of TIM is checked against MSF Rugby and any variation is compensated for by 'advance and Retard' circuits that regulate the speed of the spinning drum. TIM is accurate to within 2 mS (milliseconds) in any one second and an average of 6 mS in any 24-hour period, not bad for 2 pence.

## TELLY TIME

Both the major Teletext services, Ceefax and Oracle are now linked to MSF via their computers. The Ceefax clock (transmitted on the top of every teletext page) is accurate to within 1/50th of a second. The Oracle (also on the top of every page), clock has at the time of writing only just been connected to MSF so figures are not available but we would suspect its accuracy to be similar to Ceefax.




CEEFAX, the clock can be seen on the 'header' on the left-hand side. CEEFAX and ORACLE are both linked to the MSF clock at Rugby so should be accurate to within one-fiftieth of a second.
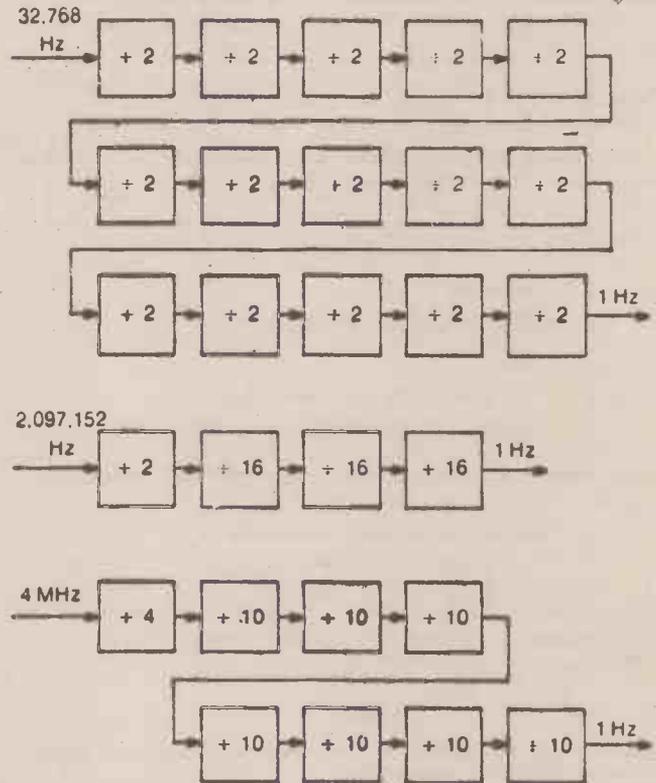
## PERSONAL TIME

All the timepieces discussed so far rely upon a central source of reference, either the Atomic Standard, the mains frequency or even the Sun in the case of a sundial. When time keeping gets to a portable level, ie a wristwatch it becomes necessary to carry around your own reference. At the moment its a little impractical to carry a Cesium beam oscillator on your wrist so our old friend the Quartz crystal oscillator has to suffice. A few years ago, 1960 to be precise (pun intended), the first electronic wristwatch from Bulova actually contained an electronically driven tuning fork. This was mechanically connected via a ratchet wheel to the hands. In its day it was as good if not better than most mechanical chronometers, the manufacturers even gave a written guarantee confirming it to be accurate to within a second per month. Many so-called electronic 'chronographs' of today are hard pressed to better that. Unfortunately, the watch for all its ingenuity still relied on moving parts to operate, and eventually they would wear out.

Back to the present. Today's LCD, LED and now Lithium digital watches all have one thing in common, a quartz oscillator. Up until quite recently they all worked at 32.768 kHz, this strange figure is actually deliberate because it is easily divided with modern digital ICs to a usable 1 Hz. Lately though, higher frequencies of 2.09 and 4 MHz have begun to gain wider acceptance because a higher frequency leads ultimately to greater accuracy.




Divider chain found most modern digital watches, the three frequencies are the most common ones in use today. The actual frequency is governed by a quartz crystal oscillator, this is fed to the chain inside the IC. (See page 54.)



Inside one of our own digital alarm watches, we were surprised to discover the actual bleeper consists of a thin slice of piezo electric crystal on a metal diaphragm inside the back cover. The little grill on the front is in fact a dummy, nonetheless it's loud enough to wake most people. The electronics are sited on the small PCB top left. The display, beneath the PCB is a liquid crystal device, it displays a stopwatch, calendar and of course the time at the expense of only one or two microwatts.

# Electronic Timekeeping

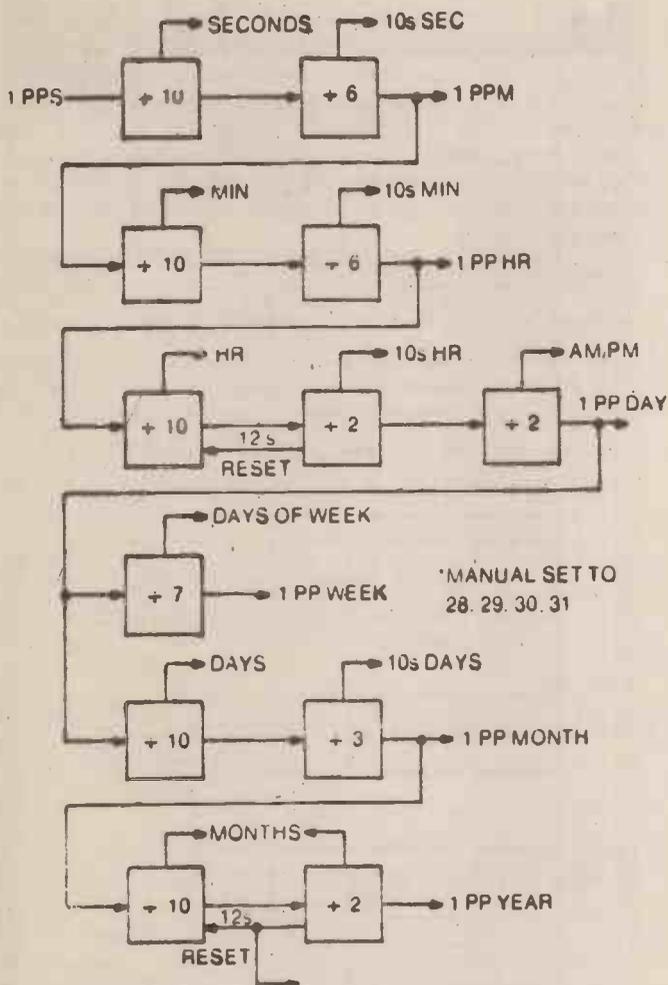

Divider chain for turning a 1 Hz pulse into hours, minutes, seconds, days, months, etc, etc.

By using modern CMOS and I<sup>2</sup>L technology, coupled to an LCD or Lithium display (LEDs tend to be a bit juicy) current consumptions of around 2-5  $\mu$ A are the order of the day. Indeed a typical LCD watch battery should last in excess of one year. One final point with LCD displays, they are a chemical display and as such have a limited life. Even with modern processes a life expectancy of around five years is to be expected. Remember that next time you see one for £100, check how long its guarantee lasts for. With so many LCD watches around the £20 mark its just not necessary to spend that much. Wonder how long it'll be before someone comes up with a disposable watch. If the battery life expectancy of these watches is extended much more they'll start to outlive the displays.

## THE FUTURE

An obvious development has got to be a domestic MSF receiver, (who knows they may even make a wrist-watch version) already there are commercially available receivers but they tend to be a little too expensive for us mere mortals.

The current flood of cheap mains-locked LED, and Fluorescent bedside, alarm, and mantelpiece clocks will continue to grow, after all who wants to keep winding an old clockwork clock that doesn't tell the time

to the second. (Funny thing though, they always did seem to keep going during power cuts.)

The way modern society seems to be going, time, (and we mean accurate time) will continue to play a more important role. Clocks and watches will get more and more accurate, cheaper and cheaper and doubtless sprout more and more semi-useless functions. Look out for the Lithium displays, they rely upon a minute piece of radio-active material to illuminate a small screen. This type of display does have a long life and is readable in the dark, something the LCD watch has never been very good at, even with a backlight.

Well, that's about it, we've literally only just scratched at the surface of electronic timekeeping, one thing you can expect though, is its a subject that is going to get even more involved in the next few years, so keep your eyes peeled for an update in the near future. **HE**



This is where it all began, man's quest for accurate timekeeping relied upon logging regular events. The sundial kept track of the apparent motion of the sun. The more sophisticated sundials were accurate to within 10 minutes at any time of year, quite an achievement. Today we measure much shorter events, the 50 Hz of the mains, the oscillations of the quartz crystal, and if you're really fussy you can count the vibrations of the Cesium atom and you can't get much more accurate than that!

We would like to thank Hewlett Packard Ltd, the BBC the Post Office and the National Physical Laboratory for their help in preparing this article.

# Master Electronics

The **practical** way

No maths needed~  
No dull theory~

Step by step we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- 1) BUILD AN OSCILLOSCOPE
- 2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS
- 3) CARRY OUT OVER 2) EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK

Also

We provide practical tuition for:- 3) Digital Electronics

1) Radio amateurs licence.  4) Computer Technology

2) City and Guilds certificates.  5) Test instrument kits

Mark your interest(s) with an x in box provided.

British National Radio & Electronics School,  
NAME \_\_\_\_\_ P.O. Box 156, Jersey, Channel Islands

ADDRESS \_\_\_\_\_

HE01/9 \_\_\_\_\_

(block caps please).

NOW THIS IS  
SOMETHING  
*and so simple*  
**NEW!** *to construct*

**CONTROL UNIT  
CONSTRUCTION KIT  
for DISCO LIGHTS,  
GROUPS, HOME  
DISPLAYS etc.**

A new world in lighting effects is opened to the amateur interested in miniature electronics evolved for the space and computer programmes. This comes to you NOW, in kit form, an easy to construct 4-Channel 'Chaser' Unit, which when connected to a light display of your own design, will supply an on/off sequence giving the effect of chasing or moving lights. It has a speed control and has the ability to automatically make the lights appear to move forwards, backwards or alternate between the two. The unit is designed to fit into your equipment or into a box of its own. Size of completed unit 180x95x30mm. Price £15.95 including VAT, P & P 30p extra. The 4-Channel 'Chaser' Unit can also be purchased assembled, tested and guaranteed by qualified staff. Special price £21.95 including VAT, P & P 30p extra.

KIT  
**£15.95**  
inc. VAT

**CE**

Send today cheque/postal order to —

**COOK ELECTRONICS**

304A HIGH STREET, WATFORD, HERTS. WD1 2JE

# The latest kit innovation!

## from Sparkrite

*Sparkrite -  
has featured by Shaw Taylor  
in "DRIVE IN"*



the quickest fitting

**CLIP ON**

capacitive discharge

electronic ignition

in KIT FORM

- Smoother running
- Instant all-weather starting
- Continual peak performance
- Longer coil/battery/plug life
- Improved acceleration/top speeds
- Optimum fuel consumption

Sparkrite X4 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in, 1/3 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). The circuit incorporates a voltage regulated output for greatly improved cold starting. The circuit includes built in static timing light, systems function light, and security changeover switch. All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

**THE KIT COMPRISES EVERYTHING NEEDED**

Die pressed epoxy coated case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips, and accessories. Top quality 5 year guaranteed transformer and components, cables, connectors, P.C.B., nuts, bolts and silicon grease. Full instructions to assemble kit neg. or pos. earth and fully illustrated installation instructions.

NOTE— Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. Price £4.25 inc. VAT, post & packing.

Electronics Design Associates, Dept. HE9  
82 Bath Street, Walsall WS1 3DE. Phone: (9) 614791.

Name \_\_\_\_\_

Address \_\_\_\_\_

Phone your order with Access or Barclaycard

\*including postage and packing UK only

QUANTITY REQ'D.

Send SAE if brochure only required.

X4 KIT £17.95 inc. VAT

TACHO PULSE SLAVE UNIT  
£4.25 inc. VAT

I enclose cheque/PO's for

£

Cheque No. \_\_\_\_\_

Access or Barclaycard No. \_\_\_\_\_

# CITIZENS

SUMMER '79

# CB AND

# 75p

A Special from the Publishers of

# Hobby Electronics



Yes, it's here at last, the first British book on CB. The 72 page special from the staff of Hobby Electronics contains a massive technical section, dealing with aeriels, accessories, How to SWR, even a review of a microprocessor controlled 'rig from the States. We have given all the major organisations involved with CB a chance to put their case, everyone from the CBA to the radio control modellers. The legal side of CB in the UK. CB around the world, cartoons, scenes from the film 'Convoy', and a comprehensive dictionary of CB slang, codes etc. Plus much much more. We're sure this will become a much sought after 'standard' work so why miss out. It should be on your newsagents shelves now. If you have any difficulty in obtaining your copy write to us at HE enclosing 75 pence plus 25 pence postage and packing.

The address to write to is.  
**Citizens Band Special.**  
**Hobby Electronics,**  
**145 Charing Cross Road,**  
**London WC2H 0EE.**

# Breaker One-Four

Send any news, comments, or information you may have to:  
**Breaker One Four,**  
Hobby Electronics,  
145 Charing Cross Road,  
London WC2H 0EE.

*This is more like it, we've had a very large postbag for Breaker One-Four over the past four weeks, several clubs contacted us, alas one or two were a touch too late to get in this month but we'll be devoting quite a bit of space to them next month. As you can see the CB scene is really hotting up so keep those letters coming.*

## **CB SPECIAL**

Sorry about the delays and confusion over the special but we had some legal problems. Happily they're all sorted out and it should be on your newsagents shelves now. We have included everything from the legal side to a massive technical section, easily the largest outside the States. Look out for scenes from the film "Convoy," cartoons, a comprehensive CB dictionary of slang and codes, CB around the world and a whole lot more. See the Ad elsewhere in this issue for further details.

## **CB STICKER**

As promised we've produced a "Legalise CB" sticker for your car, the good news is that it is FREE. All you have to do is write to us, mark your envelope CB Sticker and enclose a SAE. Sorry, only one sticker per envelope.

## **SLANG COMPETITION**

Whilst we were compiling the CB dictionary in our "special" it occurred to us just how American it all was. There's nothing wrong with that, except we're British (and proud of it). So each month we'll be holding a CB slang competition, we'll print the best each month, and the winners will each receive a HE Tee-Shirt as well as a place in our all new British CB dictionary that we will be compiling over the next few months.

The only conditions are: it must be new, it must be as British as possible and of course as clean as possible. Remember the purpose of slang is to convey an often repeated message as simply and as quickly as possible over what is potentially a very noisy medium. Send your entries to: CB Slang, Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE.

## **CB ON TAPE**

Even if you can't operate CB in this country (yet, we're working on it) you can listen to, and learn all about "stateside" CB. A cassette tape now on sale over here contains plenty of examples of yankee CB and has a very comprehensive commentary from some (unnamed) American gentleman. The tape is a full length C60 and costs £2.50 from Dave Mills. Every aspect of CB is covered, from how to choose a "handle" to how to check out your rig. With the tape comes an explanatory

leaflet containing all the 10 codes, glossaries etc, and even a mention for HE (thanks Dave). For your copy send your £2.50 (Inc P&P) to: Dave Mills, 267 Charminster Road, Bournemouth, Dorset.

## **CB BAR-BE-Q**

The men from the UKCBC have been telling us about a open day they're planning, Bar-B-Q drinks etc, no firm date as yet but you can be sure we'll let you know, we might even get along ourselves. Venue as far as we can make out is somewhere in Wales.

## **PETITION**

We've settled on the closing date for the Petition, it's the 30th August, unfortunately Parliament are on holiday then so we'll let you know next month of the actual date we will be handing it over.

## **RUMOUR TIME**

If we were to believe all the rumours we hear during the month it would seem that CB will be legalised on just about every day until the middle of 1980. Those sorts of rumours we expect, what we would like help in dispelling are one or two of the more serious rumours that seem to be flying about lately.

Both are of a medical nature, so if there are any doctors out there perhaps they could get in touch with us. The first concerns interference to heart pacemakers, obviously we are most interested in finding out whether the illegal 27 MHz system does any harm in that respect but does RF generally interfere and at what power, any comments?

The second is the problem of paging systems, can someone tell us what kind of power they work at and more specifically, what frequency and what type of coding system they use, particularly hospital pagers. Do they suffer from interference or is it the other way round? Perhaps someone from the R/C modellers would like to comment on that, are you affected by paging systems?

## **CLUB CB**

In by the skin of their teeth are a new club in the Weymouth area. The news comes from Ray Howes who tells us that they have twice monthly meetings on Sundays at around 8 pm at 39 St Thomas Street, Flat 1, Weymouth, Dorset. Sorry it's a bit brief but we only heard the day before we went to press. More details next month.

BREAKER BREAK.

# Short Circuit

## ZENER DIODE TESTER


This circuit is an add-on unit for a multimeter having a sensitivity of 20k/V or better, and it enables a rough check to be made on zener diodes having operating voltages of up to about 33 volts. The unit operates from a standard 9 volt battery (PP6, PP7, or PP9 size), no mains supply or special, high voltage battery being required.

In order to obtain a suitably high voltage for this application from an ordinary 9 volt DC supply it is necessary to have a voltage step-up circuit of some kind. In this case an audio oscillator using IC1 is used to drive the primary winding of step-up transformer T1, giving about 50 V AC from the secondary winding. T1 is actually intended for use as a step-down transformer in transistor amplifier output stages, but it provides satisfactory results when employed in reverse

to give a voltage step-up. The output from T1 is halfwave rectified and smoothed by D1 and C3 to give to give an unloaded DC supply of about 75 to 80 volts (about 40 to 50 V when loaded).

With SW1 at the 'low' position, a current of about 1 to 2 mA. (depending upon the voltage of the zener under test) is fed to the test device through current limiting resistor R4, when W2 is operated and power is applied to the circuit. The multimeter, which is switched

to an appropriate DC voltage range, is connected in parallel with the test device and registers its zener voltage. Switching SW1 to the 'high' position causes about double the previous current to flow through the zener under test, as a lower value current limiting resistor (R3) is then switched into circuit. If the test device is fully functional this should cause only a very small increase in the meter reading, and there may well be no noticeable change in the meter reading at all.

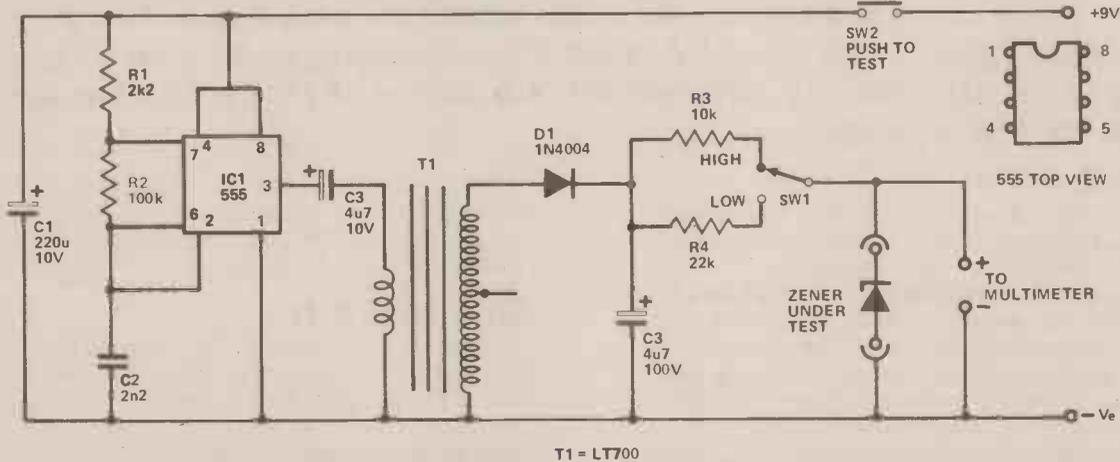

## Books from the HE Book Service

**28 Tested Transistor Projects** . . . £1.15  
Richard Torrens. The projects can be split down into simple building blocks which can be recombined for ideas of your own.

**Electronic Projects for Beginners** . . . £1.55  
F. G. Rayer. Divided into 'No Soldering Projects,' Radio and Audio Frequency, Power Supplies and Miscellaneous.

**Practical Electronic Calculations and Formulae** . . . £2.25  
F. A. Wilson. A valuable reference for the home and laboratory, containing all the most frequently used, and some of the less well known electronic formulae and calculations.

**Popular Electronic Projects** . . . £1.65  
R. A. Penfold. A collection of the most popular types of circuits and projects using modern, inexpensive and freely available components.

**Digital IC Equivalents and Pin Connections** . . . £2.70  
Adrian Michaels. Covers most popular types and gives details of packaging, families, functions, country of origin and manufacturer.

**Radio Stations Guide** £1.45  
B. Babani and M. Jay. An invaluable aid to everyone with a radio receiver helping them to obtain maximum entertainment, value and enjoyment from their set.

**Linear IC Equivalents and Pin Connections** . . . £2.95  
Adrian Michaels. Gives most essential data for popular devices.

**Electronic Security Devices** . . . £1.45  
R. A. Penfold. Full of constructional circuits covering the most basic security systems to the Ultrasonic and Doppler Shift systems.

**How To Build Your Own Solid State Oscilloscope** . . . £1.50  
F. G. Rayer. The book contains concise practical instructions so that even an inexperienced hobbyist can construct a fairly sophisticated instrument with the minimum of difficulty and expense.

**50 FET (Field Effect Transistor) Project** . . . £1.45  
F. G. Rayer. Contains something of interest for every class of enthusiast. Short Wave Listener, Radio Amateur, Experimenter or audio devotee.

**50 Circuits Using 7400 Series ICs** . . . £1.35  
R. N. Soar. The author has managed to compile no less than 50 interesting and useful circuits using this range of devices, covering many different aspects of electronics.

Note that all prices include postage and packing. Please make cheques etc. payable to Hobby Electronics Book Service (in Sterling only please) and send to:

**Hobby Electronics Book Service, P.O. Box 79 Maidenhead, Berks.**

**Essential Theory for the Electronics Hobbyist** £1.45  
G. T. Rubaroe gives the hobbyist a background knowledge tailored to meet his specific needs.

**Beginners Guide to Building Electronic Projects** . . . £1.45  
R. A. Penfold. Covers component identification, tools, soldering, constructional methods and examples of simple projects are given.

**50 Projects using IC CA3130** . . . £1.15  
R. A. Penfold. Describes audio projects, RF project, Test Equipment, Household and miscellaneous circuits.

**IC 555 Project** . . . £1.65  
E. A. Parr. Circuits are given for the car, model railways, alarms and noise makers. Also covers the related devices 556, 558 and 559.

**Second Book of CMOS IC Projects** . . . £1.50  
R. A. Penfold. Following in the success of the original CMOS projects book we present the second volume covering all aspects of CMOS technology from multivibrators to triggering devices.

# FET Special

## Down the Gain Drain

This feature was prepared from '50 FET Projects' by F. G. Rayer, published by Bernard Babani at £1.25. It contains many practical constructional projects using readily available FET devices.

*As our project editor is always saying, the best way to get to know something is to get it on the work bench in front of you. This month we get hold of the FET and show you just what you can do with it (no that's not meant to be rude).*

### INTRODUCTION

FIELD EFFECT TRANSISTORS find application in a wide variety of circuits. The projects described here include radio frequency amplifiers and converters, test equipment and receivers, as well as various miscellaneous devices which are useful in the home.

It will be found that in general the actual FET used is not critical, and many suitable types will perform satisfactorily. The FET is a low noise, high gain device with many uses, and the dual gate FET is of particular utility for mixer and other applications.

This article should be found to contain something of particular interest for every class of enthusiast — short wave listener, radio amateur, experimenter, or audio devotee.

### FET OPERATION

Figure 1 will help clarify the working of the field effect transistor. (a) represents the essential elements of the device, which has Source lead S, Gate lead G, and Drain connection D. The path for current is from Source to Drain through the semi-conductor material, this path being termed the channel. With the N-channel FET, the carriers are electrons. The Source is connected to negative of the supply, and Drain to positive.

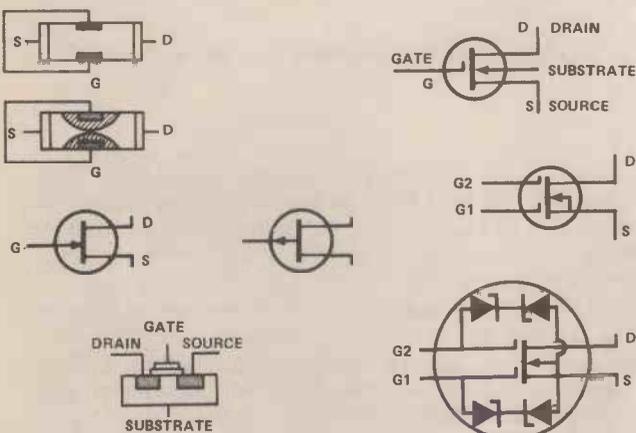


Fig. 1. Construction and symbols used for field effect transistors.

P-type gates are formed on the N-type channel, providing PN junctions. When these junctions receive reverse bias, areas surrounding them are emptied of electron carriers. These "depletion areas" reduce the width of the carrier channel, as at (b). As a result there is a drop in the passage of current carriers from Source to Drain. Increasing the bias causes the depleted regions to extend, and the channel grows smaller, reducing current even further. Eventually the gate can be made so negative that the channel is virtually closed. This is the pinch off region, and current is practically zero. The current from source to drain, and through external circuit items, can therefore be controlled by adjusting the gate voltage. Since the gate to channel junction area is reverse biased gate current is extremely small, and thus the gate input impedance is very high. Generally, the gate current is negligible.

(c) is the symbol for this FET, with S indicating Source (negative), G for Gate, and D for Drain (positive). Such N-channel FETs are conveniently operated with a negative ground or source line. "D" is the symbol for a P-channel FET. Typical types and lead outs are shown later.

(e) represents an insulated gate FET. The gate is insulated from the channel by an extremely thin dielectric so that there is no junction in the way described for (a). The substrate is P-type material with positive hole carriers. When the gate is made negative, positive charges move from the substrate towards the gate, so that the width of the conducting channel is reduced, and thus also the current from drain to source.

### MEDIUM FREQUENCY AMPLIFIER

This circuit, Figure 2, is primarily intended for use over the 1.7MHz to 30MHz range, and will be found to provide considerable gain. RF amplifiers of this kind are generally used to improve long distance short wave reception, to increase volume, and to reduce second channel interference on the higher frequencies.

To avoid winding coils and permit easy band changing, Denco (Clacton) miniature plug in coils may be used. These are the "Blue" (Aerial) ranges, valve type. The most useful coils will be Range 3, 1.67-5.3MHz, or 580 to 194 metres; Range 4, 5-15MHz, or 60 to 20 metres; and Range 5, 10.5-31.5MHz, or 28 to 9.5 metres. Exact coverage depends on the setting of



the adjustable cores, and will also be modified if VC1 is of different value. The coils are inserted in a B9A type holder. If only a single range is wanted, the coil can be mounted by its threaded end, and leads are then soldered directly to the pins.

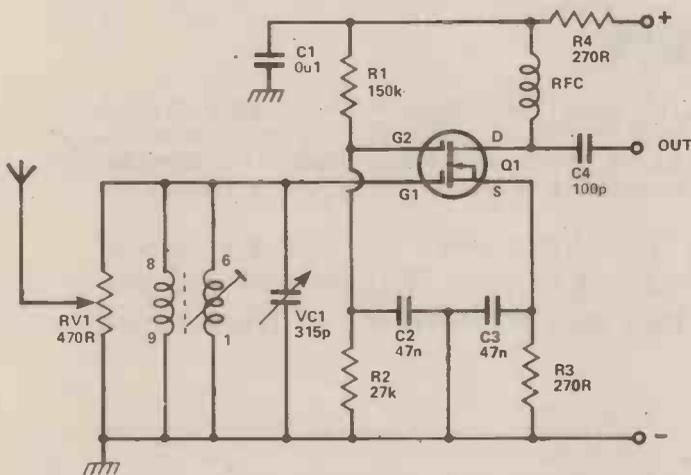


Fig. 2. Circuit diagram for a Medium Frequency RF amplifier.

RV1 is an adjustable aerial input control, as overloading may easily arise with strong signals. R1 and R2 provide the voltage for gate 2, and R3 is for source bias.

The drain circuit is arranged for capacitor coupling by C4 to the aerial socket of the receiver. This lead should not be unnecessarily long, as this may cause losses, as well as picking up signals which cause second channel interference. If the lead is screened, it must be no longer than necessary. A 2.6mH short wave sectionalised radio frequency choke will be satisfactory for the frequencies mentioned.

Construction is best in a metal case, which can have a hinged lid if plug-in coils are to be fitted. No ganging difficulties can arise with VC1, which is adjusted for best volume.

Second channel interference is caused by signals which are  $2 \times 1F$  frequency from the wanted signals. With a 470kHz intermediate frequency, these offending signals will be 940kHz from the wanted transmission. As a result, interference from this cause is unlikely at low frequencies, but very probable at high frequencies. Such second channel interference is considerably reduced, or completely avoided, by using a tuned RF stage of this kind, actual results in this direction depending on the receiver IF, and frequencies tuned.

A 9V supply is adequate, and current may be drawn from the receiver if convenient. Only about 2mA to 3mA or will be wanted. The MEM618, 40602, and 40673 will be found satisfactory here.

### 144MHz CONVERTER

The reception of 2 metre signals is generally with a converter and short wave receiver, preferably of communications type. The latter will have sensitivity and selectivity better than average. With such an arrangement of equipment, the 144MHz or other VHF signal is changed in frequency so that the converter output falls within the tuning range of the receiver.

A converter of this type often has its own RF amplifier, and a relatively low frequency crystal controlled oscilla-

tor, followed by frequency multipliers. This allows high sensitivity and excellent frequency stability, but is a relatively complicated and expensive item. Bearing in mind that at this frequency the RF amplifier will not contribute very much gain, and that tunable VHF oscillators are used in many domestic VHF receivers, it is possible to use the much simpler circuit in Figure 3.

L1 is broadly tuned to the wanted frequency band by T1, and signal input is to gate 1 of Q1. Q2 is the local oscillator, and the operating frequency here is determined by L2 and T2. Oscillator injection is via C3 to gate 2 of Q1. The frequency of the output from the drain of the mixer Q1 is the difference between G1 and G2 frequencies. Thus if the signal at G1 is 144MHz, and Q2 is tuned to oscillate at 116MHz, output will be at 144 minus 116MHz, or 28MHz. Similarly, with the oscillator set at 116MHz, an input at 146MHz to G1 will give an output of 30MHz. Therefore 144-146MHz can be covered by tuning the receiver from 28MHz to 30MHz. L3 is broadly tuned to this band, and L4 couples the signal to the short wave receiver.

The oscillator can actually be tuned above or below the aerial circuit frequency of the converter, as it is the difference between converter signal input and oscillator frequencies which determines the converter output frequency. It is also possible to choose other reception and output frequencies, provided L1, L2 and L3 are chosen to suit.

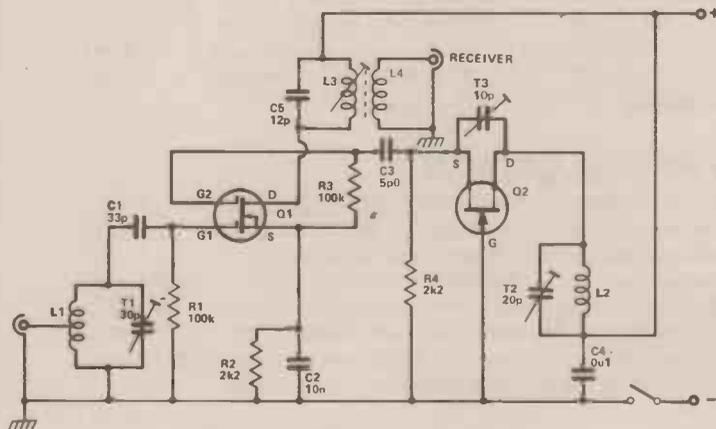


Fig. 3. Circuit for a 144 MHz converter for short wave receivers.

L1 and L2 are wound in the same way, except that L1 is tapped one turn from its grounded end. Each coil has five turns of 18 swg wire, self supporting, formed by winding the turns on an object 7mm in diameter. Space turns so that each coil is  $\frac{1}{2}$ in or about 12mm long.

L3 is fifteen turns of 26swg enamelled wire, side by side on a 7mm former with adjustable core. L4 is four turns, overwound on the earthed (positive line) end of L3. Layout should allow very short connections in the VHF circuits. A co-axial aerial socket is fitted near L1. A screened co-axial lead is preferred from L4 to the receiver, to avoid unnecessary pick-up of signals in the

28-30MHz range. The converter will operate from a 9 V to 12 V supply.

L3 should first be peaked at about 29MHz. If a signal generator is available couple this to Q1 drain by placing the output lead near the drain circuit. Tune generator and receiver to 29MHz, and adjust the core of L3 for best results. Otherwise, couple an aerial by means of a small capacitor to the drain circuit, and tune in some signal in the 28-30MHz range, to allow adjustment of the core of L3.

It is now necessary to tune L1 to about 145MHz, and L2 to 116MHz, or 174MHz. If an absorption frequency indicator is available, this will permit an approximate setting of T2. A dip oscillator will also allow T1 to be adjusted. Subsequently adjust T2 to bring the wanted signals in at the required frequencies on the receiver, and peak these for best volume with T1, and check the setting of L3 core.

The converter is best assembled in a small aluminium box, completely closed, which can be placed behind the receiver. Note that if Q2 is not oscillating, no reception is possible through the converter. Q2 should be a VHF FET, such as the BF244, MPF102, and similar types, and if necessary T3 may be adjusted to secure oscillation here. The 40602, 40673, and similar VHF types will be satisfactory for Q1. If needed, frequencies can be brought within the swing of T1 and T2 by stretching or compressing L1 or L2.

The aerial may be about 38½in long, constructed as a simple self-supporting or wire dipole, with a feeder descending to the converter. Amateur activity is most likely to be greatest at weekends, and in many areas a whip or very short wire aerial will provide local reception.

## FIELD STRENGTH METER

The device in Figure 8 will operate at any frequency up to 250MHz or even higher if necessary. A short whip, rod, telescopic or other aerial picks up radio frequency energy, and rectification by diode D1 provides a positive voltage for the FET gate, across R1. This FET is only operating as a DC amplifier, and the 2N3819 and other general purpose transistors will be satisfactory.

The "Set Zero" potentiometer may be 1k to 10k. With no RF signal present, it allows gate/source potential to be adjusted, so that the meter shows only a small current, which rises in accordance with the strength of the RF present. For high sensitivity, a 100 uA meter can

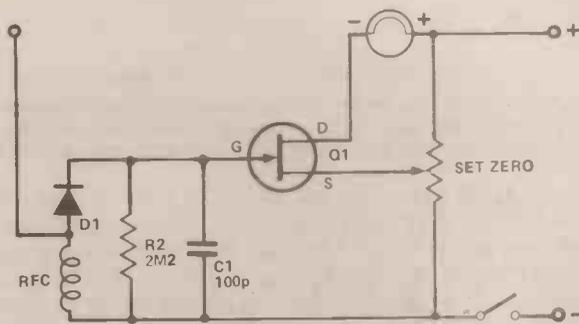


Fig. 4. Field strength meter, useful for determining the efficiency of RF equipment.

be fitted. Alternatively, a meter of lower sensitivity, such as 25 uA, 500 uA or 1 mA can be used, and will provide enough indication in most circumstances.

Should the field strength meter be wanted for VHF only, a VHF choke can be used, but for general usage over lower frequencies, a short wave choke is necessary. An inductance of about 2.5mH is satisfactory for 1.8MHz and higher frequencies.

The device can be constructed in a small insulated or metal box, with the aerial projecting vertically. In use, it allows tuning up a transmitter final amplifier and aerial circuits, or the adjustment of bias, drive and other factors, to secure maximum radiated output. The effect of adjustments will be shown by the rise or fall of the reading of the field strength meter.

## FET TRF RECEIVER

Figure 9 is a circuit giving good headphone reception for persons listening, and it can if wished be constructed as a miniature receiver with a short throw-out aerial. Alternatively, it can be used with reduced range by relying on the ferrite rod alone for signal pick-up.

Q1 is the detector, and regeneration is obtained by tapping the source up the tuning coil. The use of regeneration greatly improves selectivity, and also sensitivity to weak signals. The potentiometer RV1 allows manual adjustment of the drain potential of Q1, and so acts as a regeneration control.

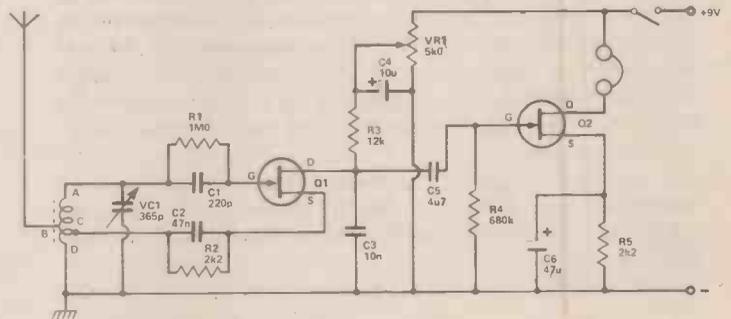


Fig. 5. FET TRF receiver.

Audio output from Q1 is coupled to Q2 by C5. This FET is an audio amplifier, operating the headphones. A complete headset is preferable for general listening, and phones of about 500 ohms DC resistance, or about 2k impedance, will give very good results here. If a miniature earpiece is wanted, this should be a medium or high impedance magnetic unit. A crystal earpiece will require resistance capacity coupling.

The tuning inductor is fifty turns of 26swg wire, on a ferrite rod about 5in × 3/8in. If the turns are wound on a thin card sleeve which can be moved on the rod, this will allow adjustment of band coverage. The winding begins at A, and aerial tapping B is at about twenty-five turns. D is the grounded end of the coil. The best position of the tapping C depends somewhat on the actual FET, on the battery voltage, and on whether the receiver is to be used with an external aerial wire or not. Should the tapping C be too near to end D, no regeneration will be obtained, or regeneration will be weak, even with RV1 rotated for maximum voltage. On the other hand, with too many turns between C and D,



oscillation will begin with RV1 only slightly advanced, and signals will be weak. Best results are expected when regeneration begins smoothly, with RV1 about halfway through its rotation. It was found that only one to two turns were required between C and D. As changing the whole coil by a turn or so has little practical effect on frequency coverage, the best method is to make C two turns from D. Then if necessary unwind half a turn or more at D.

When regeneration is obtained, a heterodyne will be heard if the receiver is tuned through a transmission. RV1 should then be turned back very slightly. Maximum possible sensitivity is achieved when Q1 is almost in the oscillating condition. RV1 has to be set to suit the frequency tuned by VC1, so that final critical adjustment can be made. It is useless to regard RV1 as a gain control, and set it at maximum.

A metal case is suitable where an external aerial wire will be used. Where the ferrite rod only will be employed, for local signals, the box or case must be of plastic or other insulating material.

## TIMER

An adjustable timer, giving a delay of about 10 seconds to 1 minute, can be used for photographic and other purposes; or with various games where each competitor must make his move within the agreed period.

The circuit in Figure 11 can be employed in various ways, as will be explained. When the switch is moved to the "On" position timing begins, and C1 commences to charge through R1 and RV1. The two resistors R4 and R5 hold the source of Q1 at approximately a fixed potential. When the voltage across C1 has reached a high enough level Q1 gate is positive, so that drain current flows through R3. This causes a voltage drop in R3, so that the base of Q2 moves negative. Q2 is a PNP transistor, so conducts, and collector current flows in the relay coil, closing the relay contacts. When the switch is returned to the "Off" position, C1 is discharged through R2, so that the interval can be repeated.

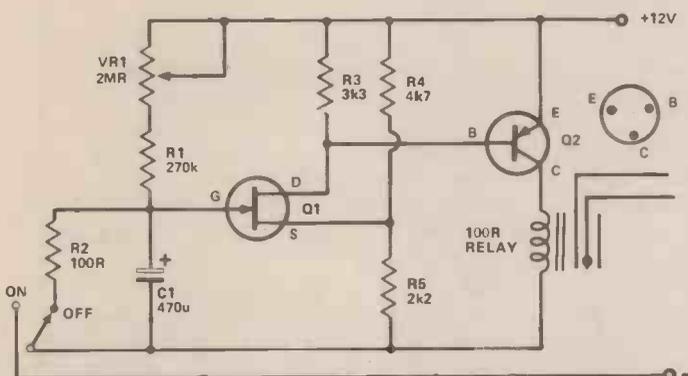


Fig. 6. A timer using a FET, the delay can be varied from about 10 seconds to 1 minute.

A 2N3819 is suggested for Q1, and AC128 for Q2. With C1 as shown (470uF) the interval was found to lie between 10 seconds with a total of 250k in the R1 / RV1 position, up to 1 minute with 2 megohm. So the values in Figure 42 can be expected to allow any interval to be

set from approximately 10 seconds to 60 seconds. Increasing C1, R1 or RV1 will lengthen the interval. Smaller values here will reduce it. This was with current rising to 40mA, with a 100 ohm relay.

It is not of course essential that these values or transistor types be followed exactly, and other relays would also be practicable, provided the circuit and Q2 allows a satisfactory current and voltage to suit the winding. Generally, a relay with a coil resistance of about 100 to 250 ohms will be most satisfactory.

The relay contacts can be so wired, that when the relay coil is energised, the circuit is completed, or interrupted. The former will most usually be wanted. Closure of the contacts can then light an indicator lamp, or sound a buzzer or bell. The use of opening contacts will be convenient for repeating a set interval when enlarging. A 2-pole 2-way switch is then required, so that switching the timer on lights the lamp to begin the exposure, which continues until the relay contacts open.

For games and similar purposes, a 12 volt 3 watt indicator lamp can be operated from the same 12 V supply. Should any kind of mains-voltage circuit be controlled, the relay must be a type intended for this purpose, and care must be taken to arrange mains circuit so that no danger can arise for the user. **HE**

Type No.	Base	Maximum Ratings	Other Information
2N3819	1	200mW 25v	General purpose AF and RF. N-channel.
2N5457/ MPF103	2	310mW 25v	General purpose AF. N-channel.
2N5458/ MPF104	2		
2N5459/ MPF105	2	200mW 25v	General purpose AF and RF. N-channel.
BF244	1	200mW 25v	VHF. N-channel.
7644/ BF244	5	200mW 25v	VHF. N-channel. (Sub. lead omitted)
MPF102	2	200mW 25v	VHF. N-channel.
2N5450/5	3	310mW 25v	General purpose AF. P-channel.
40602/ MEM618	4	330mW 20v	Dual-gate VHF amp and mixer.
40673	4	330mW 20v	Dual-gate VHF amp and mixer.
2N3823	5	300mW 30v	VHF amp/mixer. N-channel.
2N2497/ 500	6	500mW —	Low noise. P-channel.
80111	7	100mW 20v	RF amp. N-channel.

Table showing all the important parameters for the various FETs used in the circuits, the types used are all freely available and with only one or two exceptions are not very specialised.

This article is reproduced by kind permission of Bernard Babani (Publishing) Ltd, The Grampians, Shepherds Bush Road, London W6 7NF, and taken from the book 50 (FET) Field Effect Transistor Projects by F. G. Rayer. The book (Bernard Babani No. BP 39) is available from most component shops price £1.25. It is also available from the HE Book Service, see ad in this issue

# Short Circuits

## SUSTAIN UNIT

Normally each note from a guitar has a high initial volume that rapidly decays to a much lower level, and the gradually fades out. A sustain unit provides a relatively constant output level when used with an electric guitar, despite the wide range of input levels. The most simple form of sustain unit is a clipping amplifier, but these inevitably introduce quite large amounts of distortion. A better method, and the one used in this unit, is to use a compression circuit having fast attack and decay times. This type of circuit is basically a

voltage controlled amplifier, the gain of the circuit being controlled by an output level sensing circuit which varies the gain to produce a fairly consistent output level. Little distortion is produced using this method.



Q1 is used as a low noise pre-amplifier having a voltage gain of about 20dB. Its output is fed by C3 to the input of IC1, the voltage controlled amplifier device. This has a quiescent voltage gain of about 13dB, but this can be reduced to an attenuation of over 70 dB by taking pin 2 of the device several volts positive. C6 couples

some of the output from IC1 to the output socket, and C5 couples the remaining output to a common emitter amplifier based on Q2. The amplified signal at Q2 collector couples via C9 and R7 to a conventional smoothing and rectifier network. The positive bias produced by this network is fed to the control input of IC1 via a low gain amplifier and buffer stage based on IC2.

With low input levels (below about 1mV) the control signal is too small to affect the gain of IC1. Higher level signals produce a proportionately larger control voltage

and lower gain through IC1, preventing the output level from rising much above about 30mV RMS, and giving the required virtually constant output level. The attack and decay times of the circuit are both quite short so that the unit responds suitably rapidly to changes in input level, but neither of these time constants are so short as to cause serious distortion.

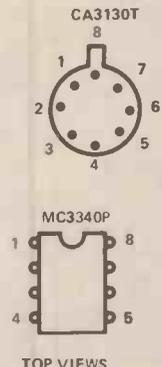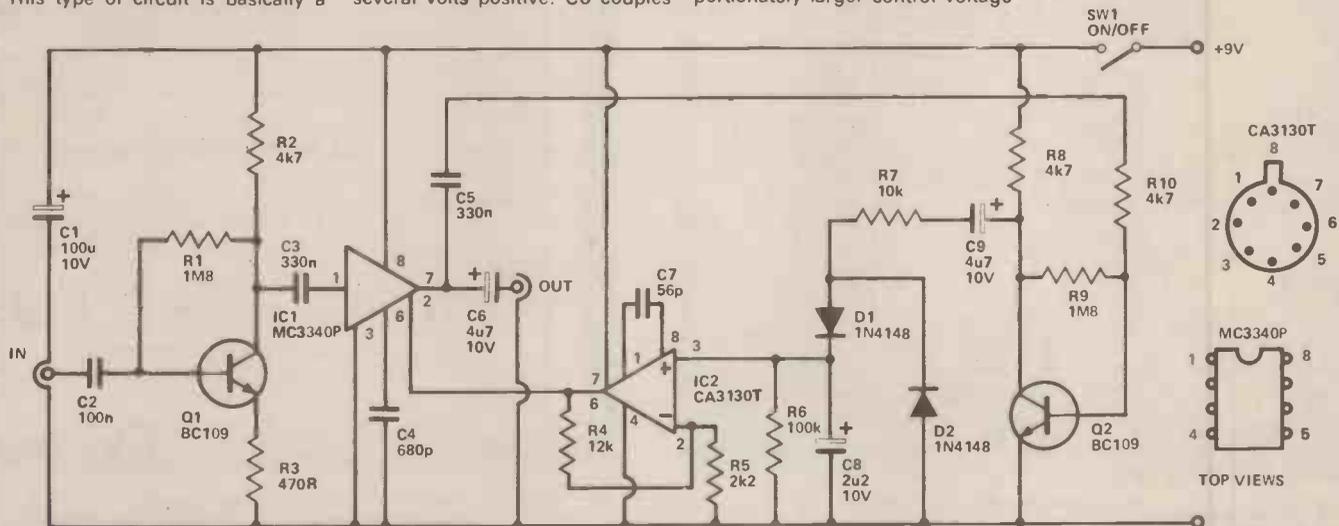The unit will be most effective with the volume control on the guitar set at maximum, unless the output should then be so high as to overload the unit and cause distortion.



## AC METER BOOSTER

Measuring small audio frequency signals is often impossible using an ordinary multimeter because most of these have a lowest AC range of about 1 to 5 V FSD. A simple and inexpensive solution to the problem is to add an amplifier, such as the one shown here, ahead of the multimeter. The amplifier has a switched voltage gain of 10 or 100, and would therefore boost the sensitivity of (say) a multimeter switched to the 2.5 V AC range to 250 mV and 25 mV FSD respectively. Measurements down to just



a few mV RMS can then be made with reasonable accuracy.

The circuit uses a CA3130T operational amplifier in the non-inverting mode. The non-inverting input is biased to about half the supply voltage by R1 and R2, and the input signal is coupled to this point by C1. The input impedance of the circuit is set at over 1M by R1 and R2, so that the unit places little loading on the circuit under test. R3 biases the inverting input and gives a quiescent output voltage of about half the supply potential. Although IC1 has an extremely high (open loop) voltage gain, the voltage gain of the amplifier as a whole (closed loop) is

much lower, and is set by the ratio of two resistances. With SW1 in the 'X 10' position the two resistances are R7, and R3 plus R4. The voltage gain is equal to the sum of the two resistances divided by the shunt resistance (R3 + R4) in this negative feedback network. This gives almost exactly the required figure of 10 with the specified values. With SW1 in the 'X 100' position the lower shunt resistance of R5 and R6 is switched into circuit, boosting the voltage gain to almost exactly 100.

DC blocking at the output is provided by C4. C5 is a supply decoupling capacitor and should be mounted physically close to IC1. C3 is the compensation

capacitor for IC1, and prevents the device from becoming unstable. Note that a carefully designed layout having the input and output well isolated from one another is required, or the circuit as a whole may become unstable. Screened input and output cables should be used to drive the primary winding maximum output of about 3 V RMS. It should therefore be used with the multimeter set to a range of 3 V or less, or if a higher range must be used, the part of the scale above 3 V is ignored. The amplifier has a flat response up to about 30kHz in the 'X 100' mode, and up to about 300kHz in the 'X 10' mode.

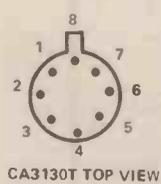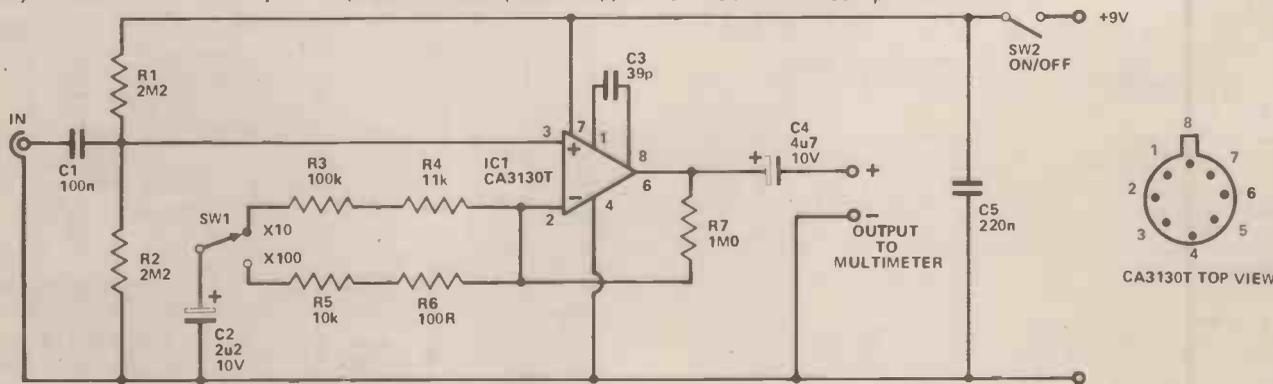

R3, R4, R5 AND R7 ARE 2% OR BETTER



# electronics today

international

What to look for in the Oct issue: On sale Sept 7th

## SPEECH COMPRESSOR

For anyone out there using the airwaves, this ingenious circuit will enable you to increase your average power to peak power ratio considerably — thereby "upping" your talk power! And it doesn't use RF compression either.

---

## REACTION TESTER

Single PCB construction with auto-start and random interval times built in. Readout is in 1/100 secs on two "jumbo" LED displays. All adds up to a pretty nifty little game does it not? Don't be slow picking up ETI next month!

---

## LM 10 APPLIED

Next month Ray Marston attempts to fill the issue with applications — some of which you couldn't ever have dreamed of — for his new champion chip, the amazing LM 10. See how close he gets to making it in the October issue of ETI.

---

## CABLE TESTER

No it is not as simple as it sounds. You should know us better than that by now. This little unit will test any type of audio hook-up wiring — or indeed any conceivable cable.

Each wire is tested, in sequence, for open-circuit or short to earth (or other wires), and then visual indication of the state of each is provided. OK?

## Audiophile amp

Now you've all seen magazine projects for hi-fi amplifiers before. We've done several ourselves! However, we believe that NO-ONE — not even ETI — has produced a design anywhere near this quality before. Specifications include a noise figure of 83dB for the phono input, and a pre-amp distortion of 0.015%.

The power amp produces over 60W at 0.04% THD with particular attention having been paid to "open-loop" performance such that TID is negligible. Hum and noise — 110dB for the power amp. Listening tests played a huge part in settling the final design too.

The system is modular such that either the pre-amp or power amps can be utilised separately. Put them together and you have the best sounding magazine amplifier ever! Full details next month.

---

## Analog delay

Since the advent of CCD (charge coupled devices) you could be forgiven for believing that all other methods of obtaining a time delay on a signal have curled up and died.

This is simply not so, and next month Tim Orr takes time off from String Thing to explain this largely unknown flourishing field.

---

## RADIO CONTROLLED

Of course you've all built our radio control project out there haven't you? No? . . . Oh.

Well the reason why not could simply be that you haven't seen this article yet. Written by Geoff Chapman — one of the few real experts in the field, it illustrates the different types of model that can be operated by R/C and how to get them operational!

Full of the kind of detail you'd spend years of lost patience gathering.

# Into Linear ICs

## By Ian Sinclair

## Part 3

*Deep breath, this month Ian Sinclair (with the help of twenty practical circuits) describes how the 741 op amp can be used to make anything from a 'boing' generator to 'pepping' up the output of your cassette recorder.*

THE 741 IS GOING TO BE our introduction to linear ICs. It would be difficult to choose any other chip, because the 741 is probably the most frequently used of all linear ICs. It can come with a variety of letter codings (LM, MC, CA, NE and others), but as long as these letters are followed by the number 741, it's the same chip. It's also found in a variety of packages, but the one we shall use is the DIL 8-pin one, which is the most convenient one for our purposes.

The 741 is classed as an operational amplifier, meaning that it's a direct-coupled amplifier with a very large voltage gain — 100 000 times or more — and the usual two inputs to which signals or feedback can be connected.

The pinout for the 8-pin package is shown in Fig. 3.1. Note that not all of the pins are connected internally, and two of the pins that are connected are seldom used — we'll show later how and when they are used. Like most operational amplifiers, the 741 is intended for dual +ve and -ve power supplies, but the circuit designs can nearly always be adapted for a normal +ve and 0V type of supply as we shall see.

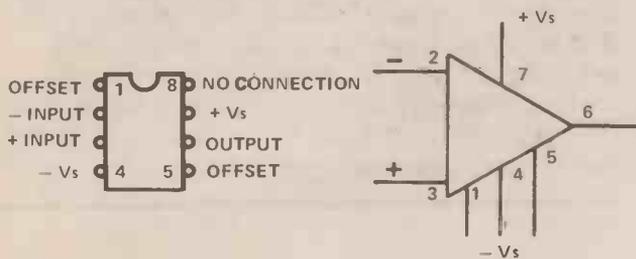


Fig. 3.1 The pin-out diagram of the 741 showing the chip appearance and the circuit symbol.

### CIRCUITS AND MORE CIRCUITS

Now for some circuits. Fig. 3.2 shows what is called a voltage follower. The - (minus) input of the 741 is connected directly to the output through a resistor R1, with no other components in the way, so that there is 100% feedback of bias and signal voltages. The + (plus) input is earthed through another resistor R2, and is used as the signal input.

What does this do? There's no voltage gain, to start with. The signal voltage out is exactly equal, as far as we can measure, to the signal voltage in, which at first sight

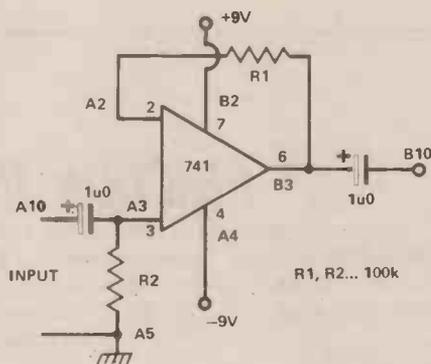


Fig. 3.2 The voltage follower circuit using dual power supplies. The dotted lines indicate where capacitors can be used connected to isolate the 741 from bias voltages in any circuits it's connected to. The letter/number references are to the line positions of the Eurobreadboard.

doesn't seem too encouraging. There is, however, a huge difference between the input and the output resistances. Remember what that's about? Any electronic device behaves as if it had a resistance at its input and another resistance at its output. When we connect these devices (transistors, ICs or whatever) together, these resistances form potential dividers, reducing the amount of signal which can be passed from one device to the next, as illustrated in Fig. 3.3. An ideal amplifier would have a very high input resistance and a very low output resistance. This way we could connect any source

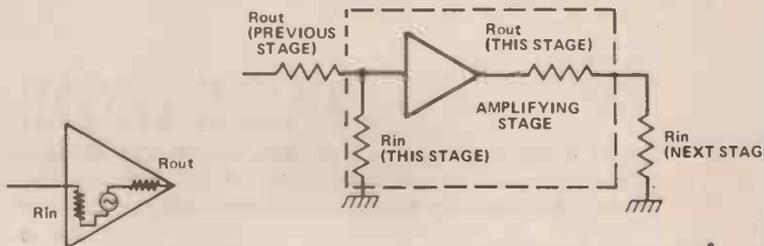


Fig. 3.3 Internal resistances (a) and how they act as potential dividers (b) for the signal.

of signal (tape, disc, microphone, radio . . .) to the input with no loss of signal, and in the same way have no loss of signal at the output even if we connected a very low resistance (such as a loudspeaker) to the output. Sometimes we prefer a lower input resistance for other reasons, but these are the rules for ensuring the greatest possible transfer of signal from one stage to the next.

The circuit of Fig. 3.2 certainly has the correct resistance values, very high at the input and very low at the output, so that the lack of gain isn't always a disadvantage. We can, for example, connect a very high resistance crystal pickup to the input and a low-resistance magnetic earpiece to the output and get a detectable signal at the output. If we connected the pickup directly to the earpiece, we don't hear a thing. This isn't because of a low signal from the pickup — crystal pickups can produce a volt or more of signal — but because of mis-match. The very high resistance of the crystal pickup is connected to the very low resistance of the magnetic earpiece, and the signal is simply divided out of existence! The 741 circuit of Fig. 3.2 is called a voltage follower, and it's a useful headphone amplifier. You can connect its input almost anywhere in an amplifier circuit without affecting the signal voltage (why? Because of the high resistance) and that's not something you can risk with headphones. If you're going to use the voltage follower in this way, though, it's advisable to use a  $0.1\mu\text{F}$  coupling capacitor at the input so that the 741 is not affected by any bias voltage at the place where it's connected. In addition, stick to battery-operated equipment until you have a lot of experience in servicing — you don't get a second chance where there are mains voltages around.

## BIASSED TOWARDS COMPONENTS

Fig. 3.4 shows another version of this circuit, re-drawn this time so that a single supply of 18 V can be used. You can see that this needs more components because the bias on the + input has to be set at a voltage midway between the positive and the zero supply lines. In this circuit, equal value resistors R3 and R4 set the midway voltage to which the + input is returned. The - input is biased by feedback as before, but the input and output have to be capacitor coupled because of the bias voltages.

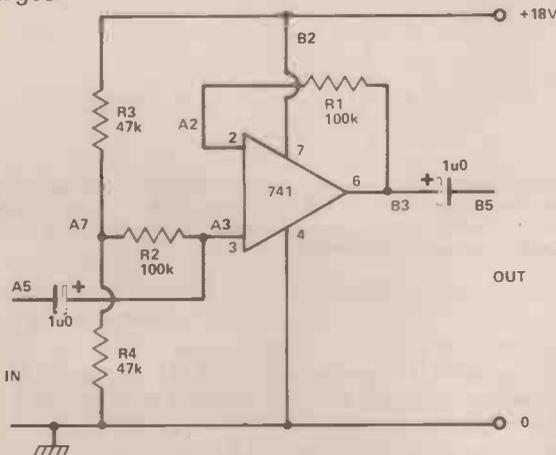


Fig. 3.4 The single-supply version of the circuit of Fig. 3.2. Eurobreadboard line A7 is used for the additional resistors R3, R4 junction with R2.

Both circuits are shown with the letter-and-number locations for a suggested Eurobreadboard layout, with pin 1 of the IC on line A1 of the breadboard. A simple way to demonstrate the high input resistance goes like this. Connect an LED and a 2K2 resistor in series to the board as shown in Fig. 3.5: note the two possible

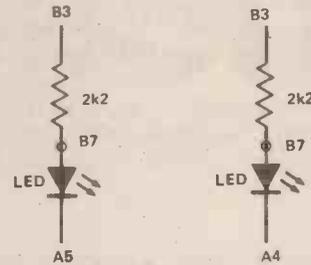


Fig. 3.5 Using an LED voltage detector (a) for the circuit of Fig. 3.2, (b) for the circuit of Fig. 3.4 R2 should be 1M in this circuit when the LED is being used as a detector.

connections according to whether you've built the dual or the single power supply version. Now, with no signal of any sort into the 741, the LED should not light, because the output voltage of the 741 is the same as the voltage at the cathode of the LED. Now touch the input of the 741 circuit with one finger and the +9 V supply with another finger — what happens? Could the resistance between your fingers possibly supply the LED directly (Fig. 3.6)? This 741 circuit is the basis for countless circuits which detect small voltages; circuits such as moisture detectors, 'lie' detectors, continuity testers and so on.

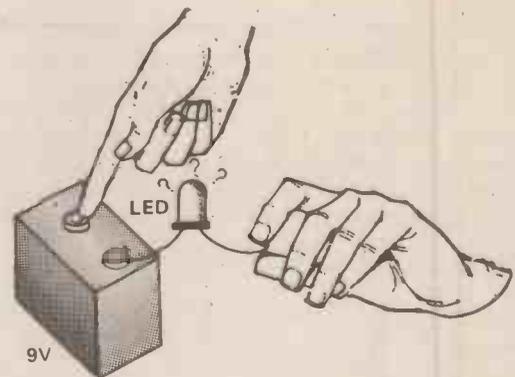


Fig. 3.6 Can enough current pass through your fingers to light an LED?


We needn't, of course, use 100% feedback for our voltage amplifier. Fig. 3.7 shows a circuit which feeds back only a fraction of the output signal. Using a dual voltage supply, this is easily arranged by connecting a potential divider from the output to earth, and taking the - input to the output of the potential divider. This kind of circuit is called a follower-with-gain. It has the same high input resistance as the simple voltage follower, but a voltage gain which is greater than one. The value of voltage gain is given by the ratio:

$$\frac{R1 + R2}{R2}$$


so that if, for example,  $R1 = 47K$  and  $R2 = 15K$ , then the gain is

$$\frac{47 + 15}{15}$$

which is 4.13, as near 4 as makes no difference. The single voltage version of this circuit isn't nearly so simple. The resistor  $R2$  can't be connected directly to earth without disturbing the bias on the + input, so that an isolating capacitor is needed. The usual pair of resistors to set half-supply-voltage, and the coupling capacitors to avoid shorting out the bias will also be needed.

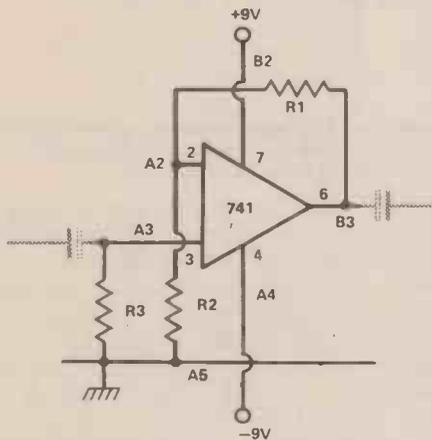


**Fig. 3.7** The follower-with-gain. The (dotted) capacitors will be needed if the circuit is to be connected to any points which are not at earth voltage.

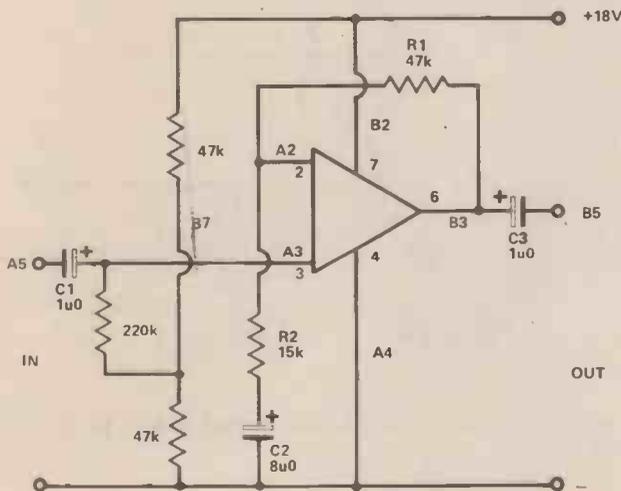

**Fig. 3.8** Single-supply version of the follower-with-gain.  $C2$  is needed to prevent the voltage at  $A2$  from being reduced by the potential divider circuit,  $R1, R2$ .

## GAIN


The gain which this circuit can have makes it much more useful. It can, for example, be used to amplify the signal at a detector diode to form a modern version of the old-fashioned crystal set, as shown in Fig. 3.9. It's also an excellent pre-amplifier circuit, giving a moderate gain along with high input resistance and low output resistance. The output will drive magnetic earpieces quite happily, though the low-resistance earphones which are

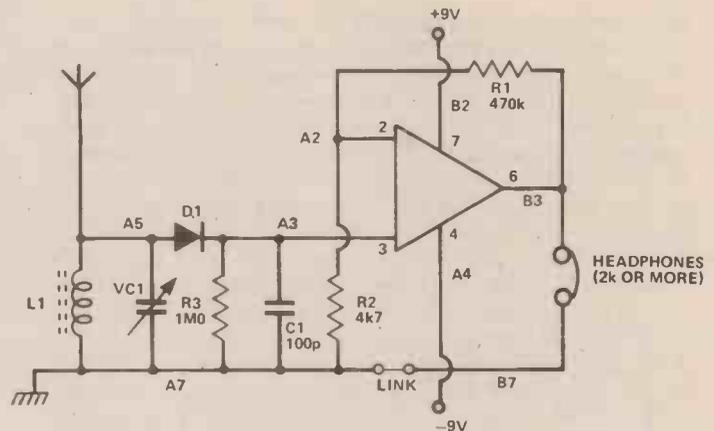

**Fig. 3.9** A simple radio circuit, using the high gain of the 741 to amplify the feeble signals from the diode detector.  $D1$  must be a germanium diode such as OA91. Note the link (wire) between  $A7$  and  $B7$  to ensure enough plug-in points on the earth line.

used along with stereo receivers usually need a bit of resistance connected in series if they are not to overload the 741. For the same reason, low resistance loudspeakers (4R to 15R) should not be used, though the old "transistor radio" 80R loudspeakers will work quite nicely.

Now for the next trick. This time, instead of using the + input for signals, we'll use the - input. Yes, I know that we take the feedback to this input as well, but we can get around that, as we'll see. The circuit of an inverting amplifier, as this type is called, which uses dual power supplies is shown in Fig. 3.10. As usual, the use of two separate supplies makes the circuitry simple, with the + input connected through a resistor to earth.

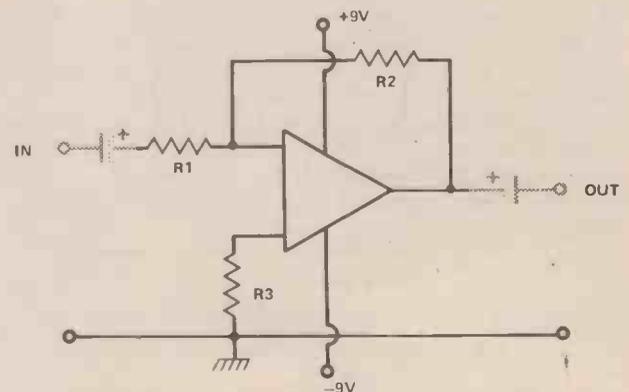


**Fig. 3.10** The basic inverter-amplifier circuit. The value of  $R3$  should be chosen so as to equal  $R1$ . Capacitors, shown dotted, should be used if the input or output is connected to points which are not at earth voltage.

This circuit is different in a number of ways. For one thing, we find that if we connect our signal directly to the - input, the input resistance is as near as we can measure, zero! It's so near zero in fact that the - input is often called a virtual earth — there's zero resistance to earth for signals at this point. We can add some resistance, however, in the shape of  $R1$ , and when we do the voltage gain of the circuit is easy to calculate — it's just  $R2/R1$ . The output resistance is low, the input resistance is  $R1$ , and the output signals are inverted


compared to the input signals.

How can we try this one out? One way is to use it with a signal source which has a low resistance. We can, for example, use a small loudspeaker as a microphone. Fig. 3.11 shows a suitable circuit, with a magnetic earpiece used at the output, which can be used as a remote listening device — not everyone knows that a loudspeaker can double as a microphone.

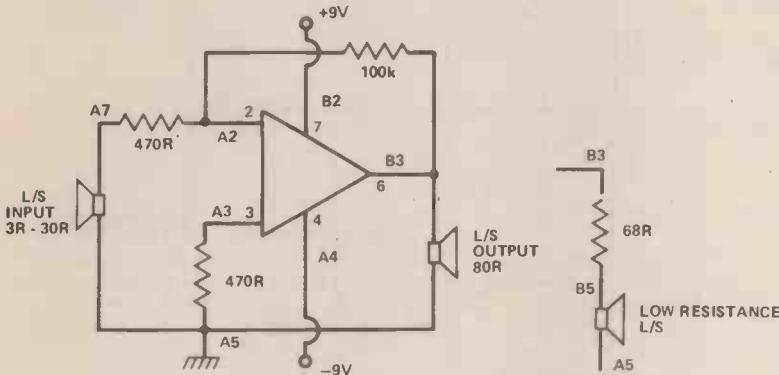

**Fig. 3.11** An eavesdropper circuit. (a) The loudspeaker at the input can be of high or low resistance, but the loudspeaker at the output can be a high resistance type. (b) shows how a lower resistance loudspeaker can be used at the output.

As usual, the circuit is a bit more complicated when a single power supply is used, and coupling capacitors have to be connected to prevent the bias from being shorted out. Fig. 3.12 shows the single-supply version of the circuit of Fig. 3.11.

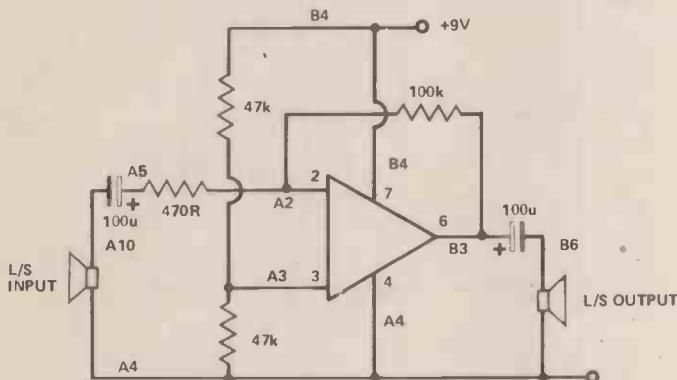


**Fig. 3.12** A single-voltage supply version of the circuit of Fig. 3.11.

## FOR OUR NEXT TRICK . . . .

These circuits are basic circuits — they illustrate with only a few components what a 741 can do. By adding more components we can end up with a lot of useful project ideas, and that's the next step. As always, we've shown the suggested Eurobreadboard layouts along with each circuit diagram. One such circuit is illustrated in Fig. 3.13. This one is an overload compressing amplifier; a boon if you use a microphone live or for tape recording. All microphones give a much greater output when you're close to them than when you're a few feet away, so if you set the gain of an amplifier to be just right when you're three feet from the mike, it's horribly overloaded and distorted when you come closer. The

compressor circuit has a variable gain which corrects this situation — when the signals are small, the circuit has a large gain; when the signals are large the gain drops. It's like having a very smart operator at the volume control, but with the additional advantage of being automatic.

How does it work? The circuit (Fig. 3.13) is basically an inverting amplifier but the feedback is through a pair of diodes, D1 and D2. Now, as you'll recall, diodes conduct one way only, so that to ensure that both halves of a signal voltage will be fed back, we have to use two diodes connected back-to-back. Even when the anode of a diode is positive to the cathode, however, a diode does not conduct until there's enough voltage across it, about 0.15 V for a germanium diode, and 0.5 V for a silicon diode. Once the diode starts to conduct, what's more, it doesn't obey Ohm's law, or anything like it. There's no fixed single value of resistance for a diode, the value of resistance changes as the current through the diodes changes, becoming smaller when there's a lot of current through the diodes, and large when the diodes are almost cut off.

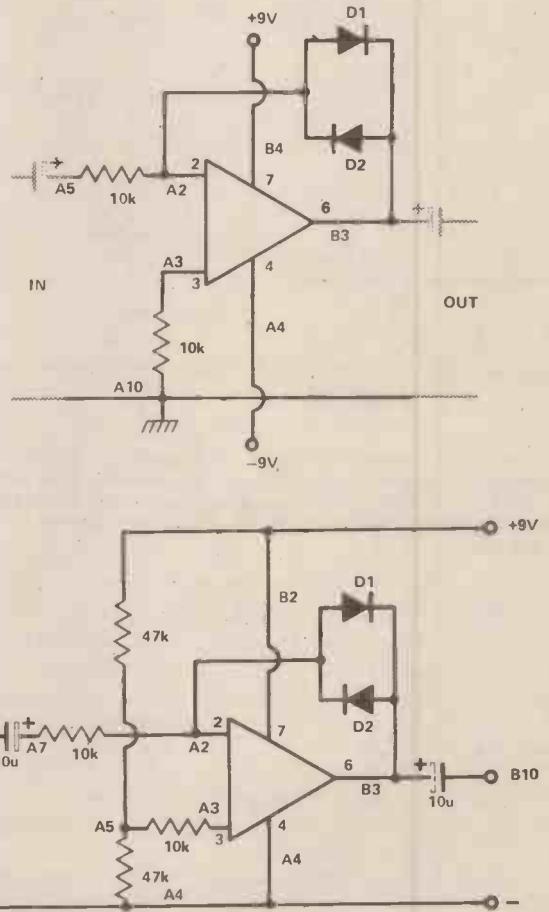

**Fig. 3.13** The diode compressor circuit (a) dual voltage supply version, (b) single voltage supply version.


## COMPRESSION

How does this achieve compression? Well, if the input signal is very small, the amplified signal at the output may be too small to make the diodes conduct, in which case there's no feedback and the circuit operates at full gain. When a larger input signal happens along, the diodes start to conduct, and their resistances act as a

negative feedback resistor, reducing the gain of the amplifier. Still larger input signals make the diode resistance lower, causing more feedback and less gain. In the circuit which is shown, the gain for a 1 mV signal is about 20 times (output 20 mV), but the gain for a 1 V signal is about 0.5 (output 500 mV). One thousand times the original input signal has caused only 25 times the output signal — that's compression!

If you want to use this in a microphone circuit, you'll have to experiment with the best place to connect the compressor — either between the mike and the pre-amp, or between the first stage of the pre-amp and the second. Remember to use coupling capacitors if you're connecting to anywhere which has a bias voltage, and don't take risks with mains-operated equipment.

Something different now, in the circuit of Fig. 3.14. This one is called the 'Buzby-cheeper' because it can be inserted between two stages in an amplifier to make the output sound as if it had come from a telephone. It's a circuit which is very useful in radio and taped plays, and

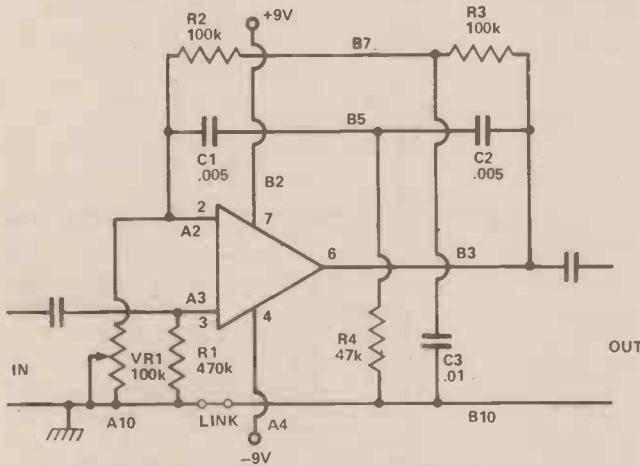


**Fig. 3.14** The 'Buzby-cheeper', dual voltage supply version. Input and output capacitors are shown dotted; they will not be needed if the input is a microphone and the output is to an amplifier or tape recorder. RV1 controls the amount of 'cheep' in the sound.

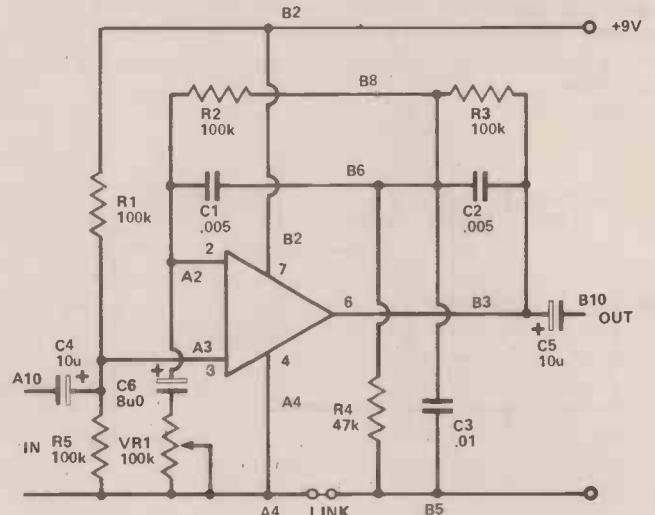I sometimes wonder if it's not used in 'phone-in' programs. The circuit needs a lot more components than any of the circuits we've used up to now, but it's not going to clutter up the wide open spaces of your Eurobreadboard. As usual, the dual-supply version is simpler, but Fig. 3.15 shows an alternative single-supply circuit. The signal input in each case is to the + input of the 741, with feedback of DC bias and of signal through the resistors and capacitors which are connected between input and output — an arrangement which is called a 'network'.



These resistors and capacitors aren't just any old values, they've been chosen so that they control the feedback of signals. At one particular frequency, around 400 Hz, there's less feedback of signal than there is at other frequencies. The result is that we get more gain at that particular frequency range, around 400 Hz, than at other frequencies. It's this feature which makes the Buzby sound, because a telephone acts also to emphasise these same frequencies. The telephone does it unintentionally — it's the construction of the telephone microphone and earpiece which filters out all the other frequencies, but our circuit does this deliberately and with some control because of the use of the 100K

potentiometer. With this control at its maximum resistance setting, the sound isn't terribly 'Buzbied', but decreasing the resistance of RV1 will increase the effect, even to the extent of letting the whole circuit oscillate, generating a tone.



**Fig. 3.15** Single-voltage supply version of the Buzby-cheeper.

Try this one out between a microphone and a tape recorder or between a tape recorder and an amplifier — but if you use a small cassette recorder, the sound may be pretty well Buzbied even without this circuit!

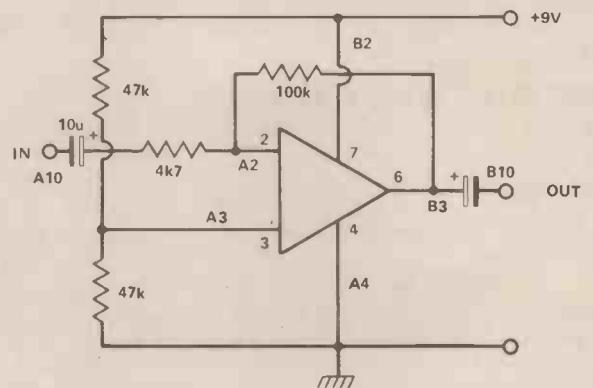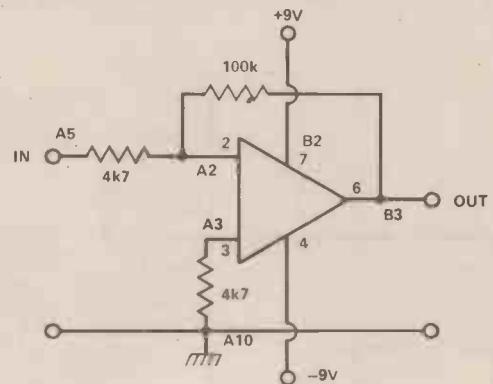

**Fig. 3.16** Microphone booster circuits (a) dual supply, (b) single supply.

## TALK ABOUT TAPE

Talking about recorders, is your cassette recorder sensitive enough when you use it with a microphone? If it isn't, then the circuit of Fig. 3.16 could prove useful. This is a booster preamp which uses the microphone as its input and delivers a boosted signal to the recorder. It can't be used with the built-in microphones which some cassette recorders have, of course, but most recorders have a separate microphone which is seldom very sensitive.

The circuit is straightforward, particularly when dual supplies can be used. The gain is fixed at about 25 times, because there's not much point in having a variable-gain pre-amplifier when the recorder itself has a gain control or has automatic gain-control circuits.

Connections can be a bit awkward when you're trying out the circuit. For testing the breadboarded circuit, I used crocodile clips to connect to the jack plug which was on the end of the microphone cable, with short lengths of wire plugging into the board. The recorder which I used also had a 5-pin socket input, and wires from the board could be inserted (once I found the correct holes) to make contact. A better method would be to solder wires to a jack socket for the input and connect a jack-plug to the board (Fig. 3.17) for the output. Remember that stranded wire must NEVER be plugged into the Eurobreadboard — not all the strands will come out again, and the lost strands will create short circuits inside the board until you peel the backing off and remove them.

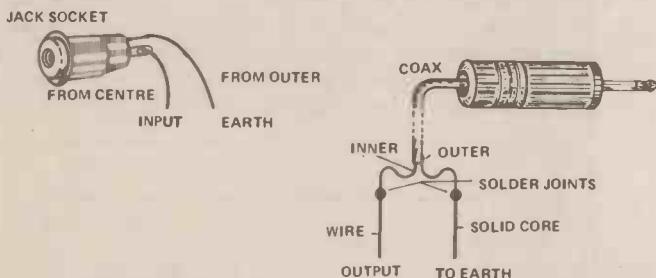


Fig. 3.17 Making connections to and from the booster.

Has that lot whetted your appetite for 741 circuits? If it has, the next one will also be of interest, because it allows you to get a fair amount of audio power to a loudspeaker by adding a couple of cheap transistors to the IC circuit. At the same time, it's not too hard on batteries because the current which the circuit takes is fairly low unless you turn the volume right up.

## SOUNDING OFF

The 741 is a voltage amplifier, and its output resistance is not low enough to drive much current into a low-resistance speaker. In addition, to prevent overheating, the 741 is fitted with circuits which limit the amount of current which can be passed. The transistors which we've added in Fig. 3.18 can pass rather more current to the loudspeaker than a 741, and are completely controlled by the 741. One of these transistors, Q1 is a PNP type, and the other is NPN, but you can't tell them apart by looking at the cans, so be careful not to rub the labels off. An alternative is to use a waterproof marker pen, the kind that's used for marking PCB tracks is ideal, to mark P on top of the PNP can, and N on top of the NPN can. With a dual 9 V supply, this circuit can pass rather a lot

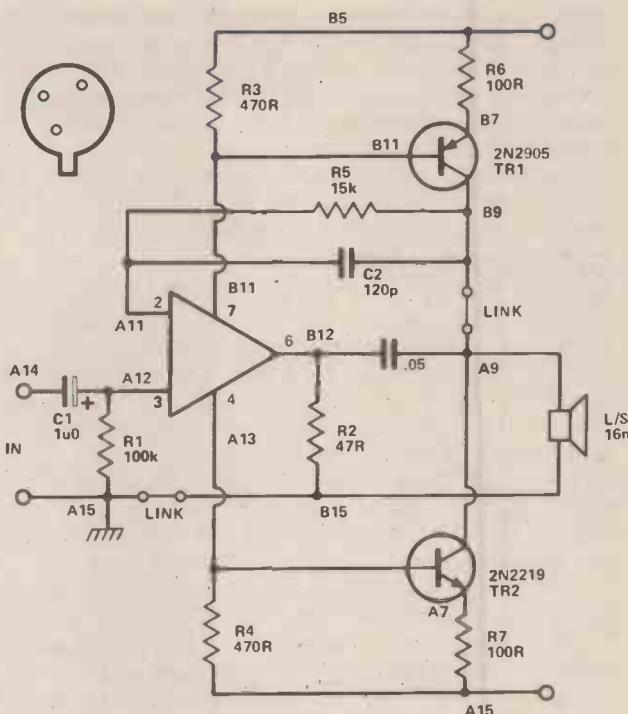


Fig. 3.18 A medium-power output stage using a 741 with two transistors.

of signal current into an 8R loudspeaker, so that emitter resistors R6 and R7 have been added for safety. These resistors also control the bias in the output pair of transistors, so don't be tempted to omit them!

The circuit is a bit unusual, because it doesn't use the output of the 741 directly. The output is simply connected to earth through a resistor, and the output transistors are driven from the power supply terminals! It certainly looks unusual, but it's quite a reasonable way if using the 741, because most of the current flowing in the power supply terminals goes to the output terminal.

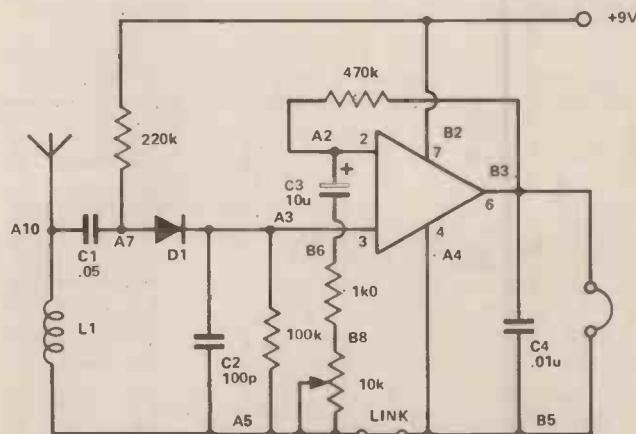


Fig. 3.19 A simple radio circuit using a single voltage supply.

On one half of the signal sinewave current flows mainly through R3 into the 741, and to earth through the output and R2. On the other half of the sinewave, current flows through R2, the output, and so through the 741 to the — supply terminal then through R4. On the positive half of the wave, the voltage across R3 biases Q1 on (it's PNP, remember, so that it turns on

when its base voltage is more negative than its emitter voltage. Q1 then passes current to the loudspeaker. On the other half of the cycle, Q1 is biased off, and the voltage across R4 turns Q2 on, so that current flows through the loudspeaker in the opposite direction and through Q2.

Because of the difference between this and the other circuits we've looked at so far, the constructional methods for this one should be rather different.

## DC COUPLING

Because the circuit is completely DC coupled, the bias/feedback connection is very important. Any fault in this line can cause one of the output transistors to pass a lot of DC through the loudspeaker, and this can happen also if the input line is biased above or below earth voltage. For safety, then, it's a good idea to use an old loudspeaker when the circuit is first tried out, and to couple to the input through a capacitor. Since this is a power amplifier, there isn't much voltage gain, and a preamplifier will be needed if very small signals are to produce an output which can be clearly heard.

The high gain which can be obtained from a 741 can be used for simple radio circuits. The circuit of Fig. 3.19 is just another up-to-date version of the old crystal set, but it's a useful way of using the gain of the 741 to display the principles of radio reception, and quite acceptable results can be obtained if a long-wire aerial is used.

In the circuit of Fig. 3.19 L1 is a tuning coil which consists of 50 turns of enamelled copper wire wound on to a ferrite core. This is connected in parallel to a 500 pF tuning capacitor, so forming a resonant circuit which can be tuned to various frequencies by altering the setting of the variable capacitor. The radio frequency which is selected by the tuned circuit is detected by diode D1, and the resulting audio frequencies are amplified by the 741.

The audio output can be heard if a pair of high-resistance (2K or more) headphones are connected to the output, alternatively a high resistance (80R) loudspeaker can be used.

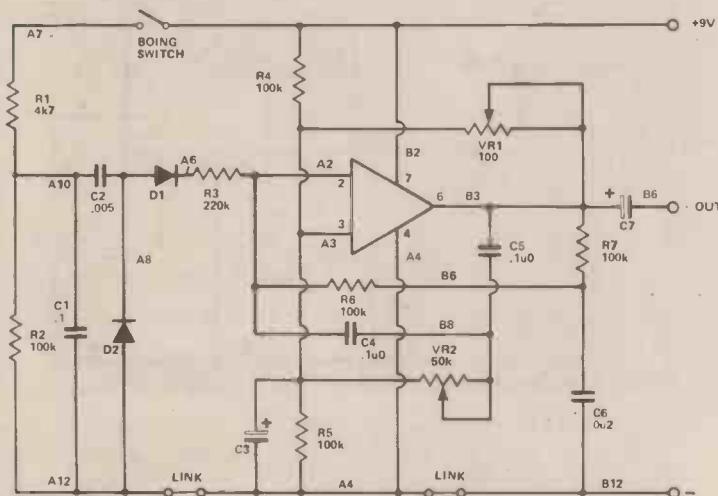


Fig. 3.20 The 'Boing' circuit.

## 'BOING' 'BOING'

How about something different? Fig. 3.20 is a 'boing' circuit — if the signal at its output is taken to an amplifier and loudspeaker, then a drum-like 'boing' sound will be produced each time the push-button is pressed. The pitch of the note can be varied by adjusting RV2, and the amount of 'boing' by adjusting RV1.

It works like this. The 741 has two feedback circuits. One of them uses capacitors and resistors, like the circuit of Fig. 3.14, to ensure that the gain of the 741 is greatest at one selected frequency. There's a variable resistor included in this bit of the circuit to control the pitch (frequency) of the note that we get when the 'boing' occurs. The other bit of the feedback circuit is just a variable resistor, RV1. This, along with resistor R3 decides what the gain of the 741 is for a signal which comes in through D1. When the push-button is pressed, C1 is quickly charged to +9 V, and the rise of voltage is passed through C2 and D1 to the 741 input. This disturbance causes the 741 to give an output, and the feedback network of C4 to C6 and R6 to R7 turns this into a continuous signal. As the charge on C2 leaks away through R3, the — input is slowly biased off, so that the signal produced by the feedback network dies away — end of boing.

## MILLIVOLTMETER

Finally, Fig. 3.21 shows a circuit for an AC millivoltmeter, which allows you to measure the size of small AC signals which are at audio frequencies. The 741 is connected as an inverting amplifier so as to amplify the audio signals at the input. At the output of the 741, the signals are forced by diodes (it's the familiar bridge rectifier circuit) to pass through the meter M, a 1 mA meter, before being fed back through resistor R5 to the

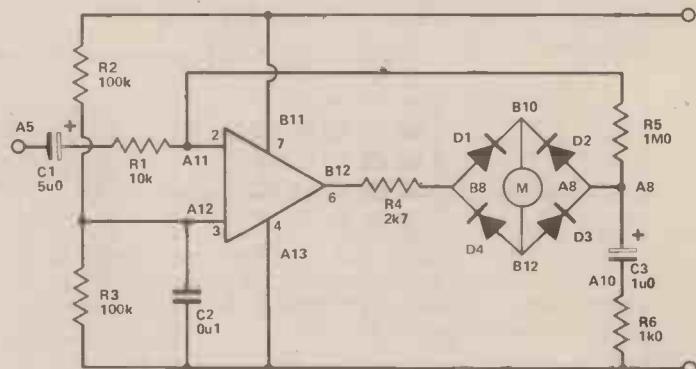


Fig. 3.21 The AC millivoltmeter circuit.

— input of the 741. Because of the way the diodes are connected, signal current always passes through the meter in one direction, so that the meter reads average current. The resistors in the circuit are there to ensure that the meter readings correspond to RMS values of a sine-wave input; their values must not be altered.

The sensitivity of the circuit is selected by the value that is chosen for R1. With the value shown, 10K, the meter reads full-scale for an input of an input of 10 mV RMS; other ranges can be selected by using switched valves for R1. A value of 100 K gives a sensitivity of 100 mV, and a value of 1M gives a sensitivity of 1 V for full-scale meter deflection. For a lot of applications a cheap edge-type meter is adequate, so that the AC millivoltmeter needn't be an expensive project. HE

# THE NEW CASIO CHRONOGRAPHS

Put most solar watches in the shade!

## CASIO 95QS-31B

4 year battery.  
1/100 sec. chrono to six hours.  
Dual time.  
12 or 24 hour.  
Stainless steel encased.  
Lightweight.  
Water resistant to 66 feet (2 at.)  
RRP £29.95

**£25.95**



## CASIO 95 CS-31B

(De-luxe model).  
5 year battery.  
1/100 sec. chrono to six hours.  
Dual time.  
12 or 24 hour.  
Solid stainless steel case.  
Water resistant to 100ft. (3 at.)  
RRP £44.95

**£34.95**

Both have new Lithium batteries which outlast most SOLAR watches. Constant LCD display of hours, minutes, seconds, a.m./p.m. and day. (12 or 24 hour). Dual time (12 or 24 hr.). Automatic day, date, month and year calendar. Mineral glass face. Backlight. High quality s/s bracelets with easily removable links.

**SEIKO—new digitals—lower prices 20% off!**

## LATEST SCIENTIFICS

### CASIO FX-68

LC Display. 37 scientific functions. Trigs, logs, exponentiations, etc. Standard deviations. Polar to Rectangular, R-P and sexagesimal to decimal conversions. Pi, cube root, six levels of brackets. Full memory. 500 hrs. battery. RRP £22.95.

**£19.95**



A very convenient 3/16 x 2 1/4 x 3 3/8" Wallet.

### COLLEGE FX-80 POWERSAVER!

Specification as above plus ENG key. 4,000 hour battery life from two AA size batteries. 3/4 x 3 x 5 1/2". RRP £17.95.

**£15.95**

**PROGRAMMABLES.** FX-501P (£64.95) £54.95. FX-502P (£84.95) £74.95. FA-1 (£24.95) £19.95.

**MELODY 80.** Now only £23.95 (£25.95).

**ISN'T IT WORTH PAYING A LITTLE MORE FOR QUALITY AND RELIABILITY?**

Fully guaranteed for 12 months.

Most CASIO products available from stock. Send 25p for illustrated brochures of this superb range of watches or calculators (both on request).

Prices include VAT, P&P. Send cheque/P.O. or phone your ACCESS or BARCLAYCARD number to:

# TEMPUS

Dept. HE, Beaumont Suite, 164-167 East Road  
Cambridge CB1 10DB. Tel: 0223 312866

## AD INDEX

AJD DIRECT SUPPLIES	49
AMBIT INTERNATIONAL	2
B.N.R.S.	55
COOK ELECTRONICS	55
E.D.A.	55
GMT ELECTRONICS	48&5
GREENWAY ELECTRONICS	64
MAGNUM AUDIO	64
MAPLIN	76
MARSHALLS	64
METAC	75
MINIKITS	30
PRESCOTT CLOCK & WATCH CO.	73
RAMAR	73
R.T.V.C.	21
STEVENSON	32
SWANLEY	44
TECHNOMATIC	44
TEMPUS	73

## BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



(1)



(2)



(3)

Returned to Service Department within guarantee period.

(1) With alarm repeat — S.R.S.P. of £17.00 offered at **£3.95 inc. VAT.**

(2) With luxury lamp and repeat alarm as featured in most major U.K. Mail Order catalogues, S.R.S.P. £31.00—offered at **£7.95 inc. V.A.T.**

(3) With integral luxury light and repeat alarm also as featured in most major U.K. Mail Order catalogues, S.R.S.P. of £32.00—offered at **£7.45 inc. V.A.T.**

These will be sold as received from our customers with the existing fault(s) and without guarantee.

Discounts available on large bulk purchases

**PRESCOTT CLOCK AND WATCH COMPANY LIMITED**

Prescott House, Humber Road, London NW2 6ER

**INTRODUCTION TO MICROPROCESSORS AND COMPUTING.** 50 pages of diagrams and explanation to get you started. Price £2.30 + 45p postage. EDUCATIONAL DATA AND TECHNICAL SERVICES  
59 Station Road, Cogenhoe, Northampton NN7 1LU

**PLEASE MENTION HOBBY ELECTRONICS WHEN REPLYING TO ADVERTISEMENTS**

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors' Hardware and accessories.

Selected range of popular components  
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices.

P.C. Boards to individual designs  
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Alfarc range of etch resist transfers, and other drawing materials for p.c. boards.

Send 15p for catalogue.

**RAMAR CONSTRUCTOR SERVICES**  
MASONS ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel 4879



First there was ETI, catering for the middle-range to advanced electronics enthusiast. Then there was HE which was aimed at the newcomer to the field. Now there is Computing Today from the same stable. CT covers the area of



small-business and amateur computing and deals with both software and hardware.

CT's sixth issue (cover date of August) is out now — 50p at your newsagent.



### QUARTZ LCD 5 Function

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

**£6.65**

Guaranteed same day despatch.

Very slim, only 6mm thick.



M1

### SOLAR QUARTZ LCD 5 Function

Genuine solar panel with battery back-up. Hours, mins., secs. Day/date. Fully adjustable bracelet. Back-light. Only 7mm thick.

**£8.65**

Guaranteed same day dispatch.



M2

### QUARTZ LCD 11 Function SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£10.65** Thousands sold!

Guaranteed same day dispatch



M3

### QUARTZ LCD ALARM 7 Function

Alarm. Hours, mins., secs. Month, date, day. 6 digits. 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick

**£12.65**

Guaranteed same day dispatch



M4

### MULTI ALARM 6 Digits 10 Functions

- ★ Hours, mins., secs.
- ★ Month, date, day
- ★ Basic alarm.
- ★ Memory date alarm.
- ★ Timer alarm with dual time and 5 country zone.
- ★ Back light.
- ★ 8mm thick.

**£18.65**



M5

### FRONT-BUTTON ALARM Chrono Dual Time

6 digits, 5 flags, 22 functions. Constant display of hours and mins. plus optional seconds or date display. AM/PM indication. Month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs. in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light.

**£22.65**

Guaranteed same day dispatch.



M6

### SOLAR QUARTZ LCD Chronograph with Alarm Dual Time Zone Facility

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

**£27.95**



M7

### ALARM CHRONO with 9 World Time Zones

- ★ 6 digits, 5 flags.
- ★ 6 basic functions.
- ★ 8 further time zones
- ★ Count-down alarm
- ★ Stop-watch to 12 hours 59.9 secs. in 1/10 sec. steps
- ★ Split and lap timing modes
- ★ Alarm
- ★ 9mm thick
- ★ Back-light
- ★ Fully adjustable bracelet

**£29.65**



M8

### SOLAR QUARTZ LCD Chronograph

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day date, day of week. 1/100th, 1/10th secs. 10X secs., mins. Split and lap modes. Back-light. Auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

**£12.65**

Guaranteed same day dispatch.



M9

### SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDEX glass.

List Price £130.00

METAC PRICE

**£105.00**



M10

### SEIKO MEMORY BANK Calendar Watch M354

Hours, mins., secs., month, day, date in 12 or 24 hour format all indicated continuously. Monthly calendar display, month, year and all dates for any selected month over 80-year period. Memory bank function. Any desired dates up to 11 can be stored in advance. 2-year battery life. Water resistant.



List Price **£130**

Metac Price **£105**

M11

### SEIKO-STYLE Dual Time-Alarm Chronograph

Mineral glass face. Battery hatch for DIY battery replacement. Top quality finish with fully adjustable bracelet.

**£35.00**


Spec same as M6

**£35.00**



M12

### HANIMEX Electronic LED Alarm Clock

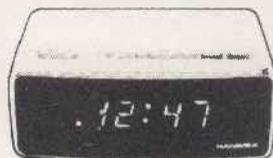

Features and Specification  
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9 minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm) Weight: 1.43 lbs (0.65 kg)

**£9.65** Thousands sold!  
Mains operated.

Guaranteed same day despatch.

M13

### HANIMEX Portable LCD Clock Radio

- ★ Back-light.
- ★ Batteries supplied free.
- ★ Quartz crystal controlled.

**£17.95**



M14

### QUARTZ LCD Ladies 5 Function.

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

**£9.95**

Guaranteed same day despatch.



M15

### PRICE BREAKTHROUGH ONLY

**£18.95**



#### OUTSTANDING FEATURES

- **DUAL TIME:** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing
- **CALENDAR FUNCTIONS** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, 59.9 seconds
- On command stopwatch display freezes to show **intermediate (split/lap) time** while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to any time within a 24-hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day dispatch. **M16**

#### HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. Also Electronic Calibration Service. All prices include VAT.

#### Metac Wholesale:

Trade enquiries: Send for a complete list of trade prices and minimum order details.

Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.



CALLERS WELCOME  
Shops open 9.30 - 6.00.

# Metac

ELECTRONICS  
& TIME CENTRES

North & Midlands  
67 High Street, DAVENTRY  
Northamptonshire  
Telephone: 03272 76545

South of England  
327 Edgware Road  
LONDON W.2  
Telephone: (01) 723 4753

# MAPLIN



A 63-key ASCII keyboard with 625-line TV interface, 4-page memory and microprocessor interface. Details in our catalogue.



Our catalogue even includes some popular car accessories at marvellous prices.



A 10-channel stereo graphic equaliser with a quality specification at an unbeatable price when you build it yourself. Full specification in our catalogue.



These are just some of the metal cases we stock. There are dozens of plastic ones to choose from as well. See pages 52 to 57 of our catalogue.



A massive new catalogue from Maplin that's even bigger and better than before. If you ever buy electronic components, this is the one catalogue you must not be without. Over 280 pages – some in full colour – it's a comprehensive guide to electronic components with hundreds of photographs and illustrations and page after page of invaluable data.

Our bi-monthly newsletter contains guaranteed prices, special offers and all the latest news from Maplin.



Mobile amateur radio, TV and FM aerials plus lots of accessories are described in our catalogue.



A digitally controlled stereo synthesiser the 5600S with more facilities than almost anything up to £3,000. Build it yourself for less than £700. Full specification in our catalogue.



A superb range of microphones and accessories at really low prices. Take a look in our catalogue – send the coupon now!



An attractive mains alarm clock with radio switching function and battery back up! Complete kit with case only £15.92 (incl. VAT & p & p) MA1023 module only £8.42 (incl. VAT).

## MAPLIN

**ELECTRONIC SUPPLIES LTD**

Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 37p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons.

I enclose £1.07. HE979

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_



A superb technical bookshop in your home! All you need is our catalogue. Post the coupon now!



A hi-fi stereo tuner with medium and long wave, FM stereo and UHF TV sound! Full construction details in our catalogue.



Add-on bass pedal unit for organs. Has excellent bass guitar stop for guitarists accompaniment. Specification in our catalogue.

All mail to:-  
 P.O. Box 3, Rayleigh, Essex SS6 8LR.  
 Telephone: Southend (0702) 554155.  
 Shop: 284 London Road, Westcliff-on-Sea, Essex.  
 (Closed on Monday).  
 Telephone: Southend (0702) 554000.