


Hobby Electronics

June '80 50p


ISSN 0142-6192



**Model
Fog Horn**

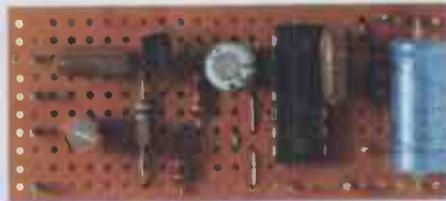

2W Amplifier

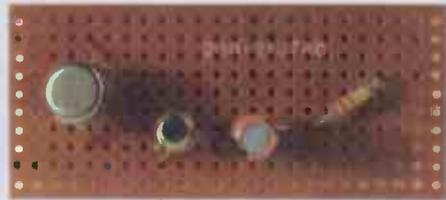

**Metronome
Egg Timer**



CB RADIO: Citizens Still Banned


**Special Reports
On The Last Year**



**Model Car
Two Channel
Proportional**

RADIO CONTROL

Complete Audio/Tuner Kits

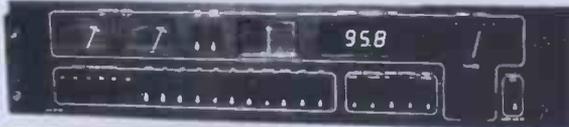

Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules£171.35 inc.
Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching HMOSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit£178.25 inc. Carr. £5.

Preamplifier

More features and facilities, thanks to DC switching and control design


Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/outs. 2 low pass, 2 high pass active filters, genuine volume 'stepped loudness', 1dB channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remotes control, tape dubbing, switched monitor etc. 80dB S/N+, THD 75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit £149 ex VAT.

Semiconductors

Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST


| | | | | | |
|---------|------|---------|------|---------|------|
| CA3089E | 2.11 | HA1197 | 1.61 | SD6000 | 4.31 |
| CA3189E | 2.53 | CA3123E | 1.61 | TDA4420 | 2.59 |
| HA1137W | 1.95 | TDA1072 | 3.09 | MC1330P | 1.38 |
| HA11225 | 2.47 | TBA651 | 2.53 | MC1350P | 1.38 |
| HA12412 | 2.81 | TDA1090 | 3.51 | KB4412 | 2.24 |
| KB4420 | 1.95 | TDA1220 | 1.61 | KB4413 | 2.24 |
| TBA120S | 1.15 | TDA1083 | 2.24 | KB4417 | 2.53 |
| KB4406 | 0.80 | TDA1062 | 2.24 | MC3357P | 3.16 |

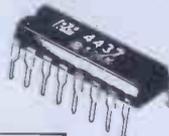

VARICAP DIODES.....

A section from our PL:

| | | | |
|--------|------|----------------------|------|
| BA102 | 0.35 | 16:1 ratio AM tuning | |
| BB204 | 0.41 | KV1215 9v triple | 2.93 |
| BB105 | 0.41 | KV1211 9v dual | 2.01 |
| BB109 | 0.31 | KV1225 25v triple | 3.16 |
| MVAM12 | 1.93 | BB212 9v dual | 2.25 |

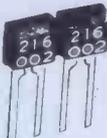

POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).

| | | | | | |
|--------|------------------------|---------------|--------|------------------------|-------|
| 2SK133 | 120v N-ch | 100W MOSFET | £6.33 | 2SJ48 Pch complement | £6.33 |
| 2SK135 | 160v N-ch | 100W MOSFET | £7.29 | 2SJ50 Pch complement | £7.39 |
| PA101B | Kit for 100W MOSFET PA | less Heatsink | £16.10 | (£23 inc heatsink/bkt) | |

ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OK!

| | | |
|---------------|--|---|
| KB4445 | 4 channel dig.prop. FM TX IC. 30mW out (amplifiable) | £2.30 inc |
| KB4446 | 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. | £2.65 |
| KB4445/6 pair | | £4.75. New 8 page data-sheet 35p + SAE. More RC ICs in list |

CMOS, LPSNTTL, TTL, MPU: Listings in the new pricelist.

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

Coming Soon.....

Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here:

SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX OP. 0.2uV basic sensitivity in HF. Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

CATALOGUES 60p ea., all three for £1.60
PRICES SHOWN HERE INCLUDE VAT
POST/PACKAGE CHARGE NOW 35p

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5. Callers welcome

ambit
INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

Radio/Audio/Communications Modules

LW-MW-SW-SW DC tuned and switched

91072 - All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands
MW/LW: £15.58 +1SW £16.73



VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output

944378-2
£26.45



Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

Various digital frequency displays

The World's largest range of receiver DFM's is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility. 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



Components

Crystal Filters

Most popular types are available ex-stock, and in quantity.

| | | |
|----------|--------------------------------|----------|
| 10.7MHz | 25kHz Channel spacing 8pole | £16.67 |
| | 12½kHz | £17.82 |
| | 2.4kHz SSB | £19.78 |
| | Monolithic dual roofing filter | £2.30 |
| 34.5MHz | 1.3dB loss, 80dB stopband HF | |
| | first filter in synth. RX | £36.80 |
| RC XTALS | FM pairs (no splits) | £3.74 |
| | AM pairs | £3.57 |
| USB/LSB | Xtals for 10.7SSB filter | £2.88 ea |



Piezo Sounders


The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz) The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)



Keyboard switches and caps

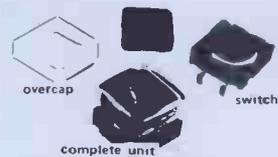From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCM81101 is shown here, with the K75 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCM81101: 17p, K75: 16p - or 29p/pair



LCD CLOCKS

Clocks use 1.5v at 15uA only. DVM 9v/1mA

LCD DVM

| | | |
|----------|-------------------------------|-------------|
| CM161: | 7mm LCD 12/24hr, alarms etc | £11.44 each |
| CM172: | 13mm, 12hr, alarms, timer etc | £14.32 each |
| CM174: | 13mm, 12hr, min/sec stopwatch | £14.32 ea |
| DVM 176: | ICM7106 based LCD 3½digit | £22.36 each |



WHAT'S NEW at AMBIT

NEW PRICELIST/SHORTFORM:- 28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :

£1.50 each - or free with pairs of HMOS and the PA101B

Everything you should know about HMOSFET devices theory and applications.

CWO PLEASE Commercial MA items an application Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt

Parts 1-3 AMBIT catalogues 60p ea, or £1.60 the lot.

Hobby Electronics

JUNE 1980 Vol.2 No.8

Editor: Steve Braidwood, G3WKE.

Assistant Editor: Rick Maybury.

Art Director: Diego Rincon



See page 58



See page 23



See page 43

Project Team: Ray Marston (Manager), Steve Ramsahadeo, John FitzGerald, Keith Brindley.

Technical Artists: Paul Edwards, Tony Strakas.

Advertisement Department: Group

Advertisement Manager: Christopher Surgenor;

Advertisement Manager: Steve Rowe;

Advertisement Representative: Roy Perryment;

Advertisement Production Controller: Sandie Neville.

Editorial Secretary: Halina Di-Lallo.

Managing Director: T. J. Connell.

PROJECTS

- MICROBE R/C SYSTEM** 11
Two-Channel Proportional System For Under £20.
- METRONOME** 32
An Easy-Build Project For The Musician
- EGG TIMER** 43
With 'Soft' or 'Hard' Settings and No External Controls
- TWO-WATT AMPLIFIER** 54
A Versatile Project For the Experimenter.
- FOG HORN** 64
Simple Circuit For The Model Maker
- SHORT CIRCUITS** 34, 36, 46, 56, 62, 72
Heads or Tails, Radio 4 Tuner, Light Change Detector, Crystal Calibrator, Transistor Checker, Cassette Radio Booster

FEATURES

- CITIZENS BANNED II** 23
News from The Front Line: Demos, Petitions, Clubs
- RF BREAKTHROUGH** 37
If The Police Come Through Your Electronic Organ, Or If You Get Tony Blackburn on Your False Teeth, This Is For You
- CHIT-CHAT** 49
LEDs and LED Displays Discussed by Ray Marston
- CATALOGUE SURVEY** 58
A Good Set Of Catalogues Is Essential To The Serious Hobbyist. Take Your Pick.
- INTO ELECTRONICS** 67
Ian Sinclair Tells All About Soldering

NEWS & INFO

- MONITOR, Keep In Touch** 6
- WIN A TEE-SHIRT, Send Us The Name Of Your Component Supplier** 10
- NEXT MONTH'S HE, Car Booster Amp, Sound-Operated Flash, Push-Button Volume Control, Electronic Espionage, Electronics In Photography, Car Hazard Flasher** 17
- BOOKS FOR HE READERS, Learn About Electronics** 18, 74
- CLEVER DICK, Radio Astronomy, Old HE Projects** 19
- HE MARKETPLACE, Seiko Watches For Less Than Fifty Quid** 40
- HOBBYPRINTS/SUBS/BACK NUMBERS, Be A Better HE Reader** 47
- ETI's JULY ISSUE, Spacecraft History, Image Coordinator, Active Filters, Quantum Review** 63

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.

Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002.

Published by Modmags Ltd.

Distributed by Argus Distribution Ltd, 12-18 Paul St., London EC2A 4JS.

Printed by QB Ltd, Colchester.

Copyright: All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing kits of the projects must be sought from the Publisher. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally.

© Copyright 1980
 Modmags Ltd



Simply ahead . .

I.L.P.'s PROVEN RANGE OF HIGH

Chosen in more countries throughout the world than any other U.K. make

I.L.P. constructional modules are different. Whereas most others come with components neatly arranged on open P.C.B.s with little else, I.L.P. modules are encapsulated within totally adequate heatsinks and need no extra components to complete them. As a result, I.L.P. power amplifiers, pre-amp and matching power supply units are infinitely more rugged, impervious to working in extremes of temperature and can be easily positioned to requirement. No additional metal work is needed to take away heat, connections are minimal and utterly simple. Circuitry, workmanship and performance are of the highest standards, equal to the demands of loudspeakers, pick-ups, tuners, digital signals, etc., even more exacting than those of today, making amplifier systems less than the best completely inadequate. Now study the tested and guaranteed specs. for I.L.P. That is why more people in more countries prefer these British designed and made modules.

- FIVE POWER AMPLIFIERS EACH ENCAPSULATED WITHIN LARGE HEATSINK.
- PRE-AMP/ACTIVE TONE CONTROL MODULE COMPATIBLE WITH ALL I.L.P. AMPS AND POWER SUPPLIES.
- SEVEN MATCHING POWER SUPPLY UNITS (FOUR WITH TOROIDAL TRANSFORMERS).
- EASY ASSEMBLY DESIGNS WITH WELL PRESENTED INSTRUCTIONS.

Why toroidal?

Toroidally wound transformers are more compact than their conventionally laminated equivalents, being only half as high and heavy. Their circular profile ensures greater operating efficiency and as such are particularly valuable in heavy duty applications. We have our own production section for winding and making toroidal transformers enabling us to offer this much sought-after type at competitive prices. Four of the larger models in our range of power supply units are now supplied with this type.



**PRODUCTS OF THE WORLD'S FOREMOST SPECIALISTS
IN ELECTRONIC MODULAR DESIGN**

AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS

and staying there

PERFORMANCE MODULAR UNITS

HY5 PRE-AMPLIFIER

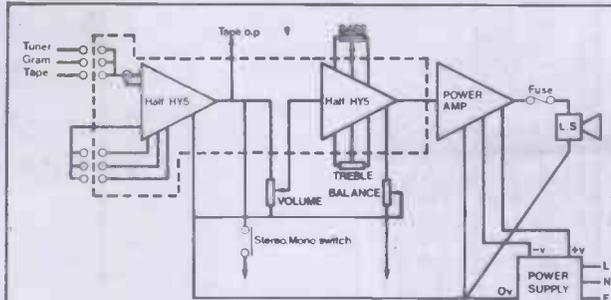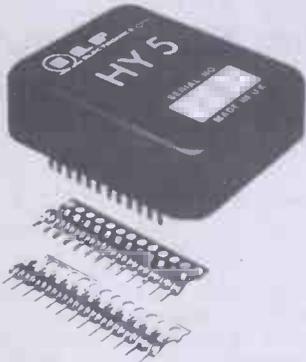


VALUES OF COMPONENTS FOR CONNECTING TO HY5
 Volume - $10K\Omega$ log.
 Bass/Treble - $100K\Omega$ linear. Balance - $5K\Omega$ linear.

The HY5 pre-amp is compatible with all I.L.P. amplifiers and P.S.U.'s. It is contained within a single pack 50 x 40 x 15 mm. and provides multi-function equalisation for Magnetic/Ceramic/Tuner/Mic and Aux (Tape) inputs, all with high overload margins. Active tone control circuits; 500 mV out. Distortion at 1KHz - 0.01%. Special strips are provided for connecting external pots and switching systems as required. Two HY5's connect easily in stereo. With easy to follow instructions.

£4.64 + 74p VAT


THE POWER AMPLIFIERS

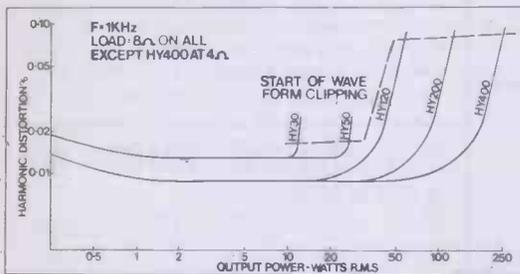

| Model | Output Power R.M.S. | Distortion Typical at 1KHz | Minimum Signal/Noise Ratio | Power Supply Voltage | Size in mm | Weight in gms | Price + V.A.T. |
|-------|----------------------|----------------------------|----------------------------|----------------------|------------|---------------|----------------|
| HY30 | 15 W into 8Ω | 0.02% | 80dB | -20 -0 +20 | 105x50x25 | 155 | £6.34 + 95p |
| HY50 | 30 W into 8Ω | 0.02% | 90dB | -25 -0 +25 | 105x50x25 | 155 | £7.24 + £1.09 |
| HY120 | 60 W into 8Ω | 0.01% | 100dB | -35 -0 +35 | 114x50x85 | 575 | £15.20 + £2.28 |
| HY200 | 120 W into 8Ω | 0.01% | 100dB | -45 -0 +45 | 114x50x85 | 575 | £18.44 + £2.77 |
| HY400 | 240 W into 4Ω | 0.01% | 100dB | -45 -0 +45 | 114x100x85 | 1.15Kg | £27.68 + £4.15 |

Load impedance - all models 4 - 16Ω
 Input sensitivity - all models 500 mV
 Input impedance - all models $100K\Omega$
 Frequency response - all models 10Hz - 45KHz - 3dB

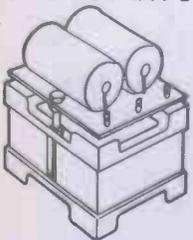THE POWER SUPPLY UNITS (Laminated and Toroidal)



I.L.P. Power Supply Units are designed specifically for use with our power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled transformer, the other with toroidal transformer, having half the weight and height of conventional laminated types.

| | | |
|---------|---|--------------------|
| PSU 30 | $\pm 15V$ at 100ma to drive up to five HY5 pre-amps | £4.50 + £0.68 VAT |
| PSU 36 | for 1 or 2 HY30's | £8.10 + £1.22 VAT |
| PSU 50 | for 1 or 2 HY50's | £8.10 + £1.22 VAT |
| PSU 70 | with toroidal transformer for 1 or 2 HY120's | £13.61 + £2.04 VAT |
| PSU 90 | with toroidal transformer for 1 HY200 | £13.61 + £2.04 VAT |
| PSU 180 | with toroidal transformer for 1 HY400 or 2 x HY200 | £23.02 + £3.45 VAT |

**NO QUIBBLE
 5 YEAR GUARANTEE**
7-DAY DESPATCH ON ALL ORDERS
INTEGRAL HEATSINKS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE
 -see below

★ ALL U.K. ORDERS DESPATCHED POST PAID HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope - we pay postage on all letters sent to us by readers of this journal.



L.P. ELECTRONICS LTD.
 FREEPOST 6, Graham Bell House, Roper Close
 Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778

Telex 965780

Please supply
 Total purchase price £.
 I enclose Cheque Postal Orders International Money Order
 Please debit my Account/Barclaycard Account No.
 NAME
 ADDRESS
 Signature

Monitor

PUSSY PINCHER



This has got to be one of the best publicity photos we've ever received. The gentleman wearing the stocking over his head is apparently trying to steal the telly. In doing so he has unplugged the set so setting off an ingenious alarm that emits a noise 'not unlike that of a scalded cat' according to the makers Ardente.

As Ardente point out, most burglars these days seem to be more interested in pinching Hi-Fis, Colour Tellys and Video Recorders, after all, who's got any money? To protect your investment this little device called the 'Cat Burglar' (at least they haven't given it a boring number) can be fitted inside virtually any piece of domestic mains powered equipment by nearly anyone. In normal use with the mains plug in socket the alarm is dis-armed, if a thief tries to steal your telly he obviously has to unplug it first at which point the alarm is activated. From the publicity blurb, it would seem that the alarm is activated by some kind of 'trembler', once installed this can be adjusted for maximum effect.

Ardente expect the Cat Burglar to retail for around £30, if you want to get in touch with them, they can be found at: Thames Avenue, Windsor, Berkshire.

CLEVER CLOCK



At around £115 this digital clock may seem a trifle expensive but just ask yourself how many other digital car clocks will tell you (now wait for it) your speed, average fuel consumption, distance travelled, how much fuel left, estimated time of arrival, time to empty tank, distance to empty tank and stopwatch functions (to name but a few)?

Installing the device will certainly keep you busy for a couple of weeks. If the prospect of fitting it yourself is a bit daunting then the importers, Station Garage, Shepperton, Middlesex will gladly put it in for you. For another £70 they can supply the Compucruise driving computer which has several more features including a cruise control for motorway driving.

GAMES AND MORE GAMES



Two new games from NIC this month (we've got more of his stock in our office than he's got in his shop). Both come from Mattel and quite frankly, are not the best we've seen. Number one is called Sub Chase, you have to locate a submerged submarine by means of sonar, when you have manoeuvred your destroyer over the sub you launch your depth charges. You have to avoid torpedos and destroy as many subs as possible in the time allotted. This game is ultimately beatable but should keep you amused for a couple of hours.

Second game is called Armour Battle, it has a similar type of display to the Sub game and has totally confused us for the past week. If we can ever decipher the instructions we'll tell you how good (or bad) it is.

Both games have an impressive repertoire of noises and tunes, the sub chase in particular is quite musical.

If you want to try it out for yourself then nip round to NIC in Broad Lane Tottenham.

ROBOTS AGAIN AND AGAIN

It seems Britain is again burying its head in the sand on the subject of Robots. Sir Keith Joseph, writing in a letter to Dr Alfred Spinks of the Advisory Council for Applied Research (ACARD), a government advisory body said, "it is up to individual companies to grasp the opportunities offered by new technology."

This effectively means that the Government will not offer any substantial help to companies wishing to get involved with Robots.

TECHNICAL ENQUIRY SERVICE

We're streamlining our project Technical Enquiry Service so in order to make it ultra-efficient could you ensure that you include an SAE and write the name of the project you're having difficulty with on the outside of the envelope. Please make sure you write Hobby Electronics on the envelope as some letters have been getting mixed up with mail for our sister magazine ETI.

THE PRICE OF ICE



ICE or In Car Entertainment is rapidly becoming the big boom market for Hi-Fi manufacturers. In the next couple of months we will be presenting a very comprehensive review of the current offerings, so, by way of a foretaste how about this extraordinarily cheap stereo radio, cassette combo from our old friends at Minikits.

It is called the HL Autosport and will deliver 8 watts RMS per channel into the speakers that accompany the machine. The interesting thing about this particular device is that the guts are to be found inside a very well known machine

costing almost twice the £45 Minikits are charging. Apart from the speakers it comes complete with a mounting kit and full instructions for installation into negative earth cars. The FM stereo radio section works very well indeed and the cassette, whilst not the best one we've heard, is more than adequate. Our only gripe is the omission of a lockable, rewind facility, but for only £45 you can't complain, now can you?

Minikits can now be found at 88 Hainault Road, Leytonstone, London E11 1EH.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9


ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 30p to ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.
We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

POLYESTER CAPACITORS: Axial lead type.
400V: 1nF, 1.5n, 2.2n, 3.3n, 4.7n, 6.8n, 10n, 15n 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 52p; 1µF 22p; 2µF 32p; 4µF 47p; 10µF 75p; 22µF 110p; 47µF 150p; 100µF 220p; 220µF 330p; 470µF 470p; 1mF 680p; 2mF 1k; 4mF 1.5k; 10mF 2.2k; 22mF 3.3k; 47mF 4.7k; 100mF 6.8k; 220mF 10k; 470mF 15k; 1mF 20k; 2mF 22k; 4mF 25k; 10mF 30k; 22mF 33k; 47mF 36k; 100mF 40k; 220mF 45k; 470mF 50k; 1mF 55k; 2mF 60k; 4mF 65k; 10mF 70k; 22mF 75k; 47mF 80k; 100mF 85k; 220mF 90k; 470mF 95k; 1mF 100k; 2mF 110k; 4mF 120k; 10mF 130k; 22mF 140k; 47mF 150k; 100mF 160k; 220mF 170k; 470mF 180k; 1mF 190k; 2mF 200k; 4mF 210k; 10mF 220k; 22mF 230k; 47mF 240k; 100mF 250k; 220mF 260k; 470mF 270k; 1mF 280k; 2mF 290k; 4mF 300k; 10mF 310k; 22mF 320k; 47mF 330k; 100mF 340k; 220mF 350k; 470mF 360k; 1mF 370k; 2mF 380k; 4mF 390k; 10mF 400k; 22mF 410k; 47mF 420k; 100mF 430k; 220mF 440k; 470mF 450k; 1mF 460k; 2mF 470k; 4mF 480k; 10mF 490k; 22mF 500k; 47mF 510k; 100mF 520k; 220mF 530k; 470mF 540k; 1mF 550k; 2mF 560k; 4mF 570k; 10mF 580k; 22mF 590k; 47mF 600k; 100mF 610k; 220mF 620k; 470mF 630k; 1mF 640k; 2mF 650k; 4mF 660k; 10mF 670k; 22mF 680k; 47mF 690k; 100mF 700k; 220mF 710k; 470mF 720k; 1mF 730k; 2mF 740k; 4mF 750k; 10mF 760k; 22mF 770k; 47mF 780k; 100mF 790k; 220mF 800k; 470mF 810k; 1mF 820k; 2mF 830k; 4mF 840k; 10mF 850k; 22mF 860k; 47mF 870k; 100mF 880k; 220mF 890k; 470mF 900k; 1mF 910k; 2mF 920k; 4mF 930k; 10mF 940k; 22mF 950k; 47mF 960k; 100mF 970k; 220mF 980k; 470mF 990k; 1mF 1000k; 2mF 1100k; 4mF 1200k; 10mF 1300k; 22mF 1400k; 47mF 1500k; 100mF 1600k; 220mF 1700k; 470mF 1800k; 1mF 1900k; 2mF 2000k; 4mF 2100k; 10mF 2200k; 22mF 2300k; 47mF 2400k; 100mF 2500k; 220mF 2600k; 470mF 2700k; 1mF 2800k; 2mF 2900k; 4mF 3000k; 10mF 3100k; 22mF 3200k; 47mF 3300k; 100mF 3400k; 220mF 3500k; 470mF 3600k; 1mF 3700k; 2mF 3800k; 4mF 3900k; 10mF 4000k; 22mF 4100k; 47mF 4200k; 100mF 4300k; 220mF 4400k; 470mF 4500k; 1mF 4600k; 2mF 4700k; 4mF 4800k; 10mF 4900k; 22mF 5000k; 47mF 5100k; 100mF 5200k; 220mF 5300k; 470mF 5400k; 1mF 5500k; 2mF 5600k; 4mF 5700k; 10mF 5800k; 22mF 5900k; 47mF 6000k; 100mF 6100k; 220mF 6200k; 470mF 6300k; 1mF 6400k; 2mF 6500k; 4mF 6600k; 10mF 6700k; 22mF 6800k; 47mF 6900k; 100mF 7000k; 220mF 7100k; 470mF 7200k; 1mF 7300k; 2mF 7400k; 4mF 7500k; 10mF 7600k; 22mF 7700k; 47mF 7800k; 100mF 7900k; 220mF 8000k; 470mF 8100k; 1mF 8200k; 2mF 8300k; 4mF 8400k; 10mF 8500k; 22mF 8600k; 47mF 8700k; 100mF 8800k; 220mF 8900k; 470mF 9000k; 1mF 9100k; 2mF 9200k; 4mF 9300k; 10mF 9400k; 22mF 9500k; 47mF 9600k; 100mF 9700k; 220mF 9800k; 470mF 9900k; 1mF 10000k; 2mF 11000k; 4mF 12000k; 10mF 13000k; 22mF 14000k; 47mF 15000k; 100mF 16000k; 220mF 17000k; 470mF 18000k; 1mF 19000k; 2mF 20000k; 4mF 21000k; 10mF 22000k; 22mF 23000k; 47mF 24000k; 100mF 25000k; 220mF 26000k; 470mF 27000k; 1mF 28000k; 2mF 29000k; 4mF 30000k; 10mF 31000k; 22mF 32000k; 47mF 33000k; 100mF 34000k; 220mF 35000k; 470mF 36000k; 1mF 37000k; 2mF 38000k; 4mF 39000k; 10mF 40000k; 22mF 41000k; 47mF 42000k; 100mF 43000k; 220mF 44000k; 470mF 45000k; 1mF 46000k; 2mF 47000k; 4mF 48000k; 10mF 49000k; 22mF 50000k; 47mF 51000k; 100mF 52000k; 220mF 53000k; 470mF 54000k; 1mF 55000k; 2mF 56000k; 4mF 57000k; 10mF 58000k; 22mF 59000k; 47mF 60000k; 100mF 61000k; 220mF 62000k; 470mF 63000k; 1mF 64000k; 2mF 65000k; 4mF 66000k; 10mF 67000k; 22mF 68000k; 47mF 69000k; 100mF 70000k; 220mF 71000k; 470mF 72000k; 1mF 73000k; 2mF 74000k; 4mF 75000k; 10mF 76000k; 22mF 77000k; 47mF 78000k; 100mF 79000k; 220mF 80000k; 470mF 81000k; 1mF 82000k; 2mF 83000k; 4mF 84000k; 10mF 85000k; 22mF 86000k; 47mF 87000k; 100mF 88000k; 220mF 89000k; 470mF 90000k; 1mF 91000k; 2mF 92000k; 4mF 93000k; 10mF 94000k; 22mF 95000k; 47mF 96000k; 100mF 97000k; 220mF 98000k; 470mF 99000k; 1mF 100000k; 2mF 110000k; 4mF 120000k; 10mF 130000k; 22mF 140000k; 47mF 150000k; 100mF 160000k; 220mF 170000k; 470mF 180000k; 1mF 190000k; 2mF 200000k; 4mF 210000k; 10mF 220000k; 22mF 230000k; 47mF 240000k; 100mF 250000k; 220mF 260000k; 470mF 270000k; 1mF 280000k; 2mF 290000k; 4mF 300000k; 10mF 310000k; 22mF 320000k; 47mF 330000k; 100mF 340000k; 220mF 350000k; 470mF 360000k; 1mF 370000k; 2mF 380000k; 4mF 390000k; 10mF 400000k; 22mF 410000k; 47mF 420000k; 100mF 430000k; 220mF 440000k; 470mF 450000k; 1mF 460000k; 2mF 470000k; 4mF 480000k; 10mF 490000k; 22mF 500000k; 47mF 510000k; 100mF 520000k; 220mF 530000k; 470mF 540000k; 1mF 550000k; 2mF 560000k; 4mF 570000k; 10mF 580000k; 22mF 590000k; 47mF 600000k; 100mF 610000k; 220mF 620000k; 470mF 630000k; 1mF 640000k; 2mF 650000k; 4mF 660000k; 10mF 670000k; 22mF 680000k; 47mF 690000k; 100mF 700000k; 220mF 710000k; 470mF 720000k; 1mF 730000k; 2mF 740000k; 4mF 750000k; 10mF 760000k; 22mF 770000k; 47mF 780000k; 100mF 790000k; 220mF 800000k; 470mF 810000k; 1mF 820000k; 2mF 830000k; 4mF 840000k; 10mF 850000k; 22mF 860000k; 47mF 870000k; 100mF 880000k; 220mF 890000k; 470mF 900000k; 1mF 910000k; 2mF 920000k; 4mF 930000k; 10mF 940000k; 22mF 950000k; 47mF 960000k; 100mF 970000k; 220mF 980000k; 470mF 990000k; 1mF 1000000k; 2mF 1100000k; 4mF 1200000k; 10mF 1300000k; 22mF 1400000k; 47mF 1500000k; 100mF 1600000k; 220mF 1700000k; 470mF 1800000k; 1mF 1900000k; 2mF 2000000k; 4mF 2100000k; 10mF 2200000k; 22mF 2300000k; 47mF 2400000k; 100mF 2500000k; 220mF 2600000k; 470mF 2700000k; 1mF 2800000k; 2mF 2900000k; 4mF 3000000k; 10mF 3100000k; 22mF 3200000k; 47mF 3300000k; 100mF 3400000k; 220mF 3500000k; 470mF 3600000k; 1mF 3700000k; 2mF 3800000k; 4mF 3900000k; 10mF 4000000k; 22mF 4100000k; 47mF 4200000k; 100mF 4300000k; 220mF 4400000k; 470mF 4500000k; 1mF 4600000k; 2mF 4700000k; 4mF 4800000k; 10mF 4900000k; 22mF 5000000k; 47mF 5100000k; 100mF 5200000k; 220mF 5300000k; 470mF 5400000k; 1mF 5500000k; 2mF 5600000k; 4mF 5700000k; 10mF 5800000k; 22mF 5900000k; 47mF 6000000k; 100mF 6100000k; 220mF 6200000k; 470mF 6300000k; 1mF 6400000k; 2mF 6500000k; 4mF 6600000k; 10mF 6700000k; 22mF 6800000k; 47mF 6900000k; 100mF 7000000k; 220mF 7100000k; 470mF 7200000k; 1mF 7300000k; 2mF 7400000k; 4mF 7500000k; 10mF 7600000k; 22mF 7700000k; 47mF 7800000k; 100mF 7900000k; 220mF 8000000k; 470mF 8100000k; 1mF 8200000k; 2mF 8300000k; 4mF 8400000k; 10mF 8500000k; 22mF 8600000k; 47mF 8700000k; 100mF 8800000k; 220mF 8900000k; 470mF 9000000k; 1mF 9100000k; 2mF 9200000k; 4mF 9300000k; 10mF 9400000k; 22mF 9500000k; 47mF 9600000k; 100mF 9700000k; 220mF 9800000k; 470mF 9900000k; 1mF 10000000k; 2mF 11000000k; 4mF 12000000k; 10mF 13000000k; 22mF 14000000k; 47mF 15000000k; 100mF 16000000k; 220mF 17000000k; 470mF 18000000k; 1mF 19000000k; 2mF 20000000k; 4mF 21000000k; 10mF 22000000k; 22mF 23000000k; 47mF 24000000k; 100mF 25000000k; 220mF 26000000k; 470mF 27000000k; 1mF 28000000k; 2mF 29000000k; 4mF 30000000k; 10mF 31000000k; 22mF 32000000k; 47mF 33000000k; 100mF 34000000k; 220mF 35000000k; 470mF 36000000k; 1mF 37000000k; 2mF 38000000k; 4mF 39000000k; 10mF 40000000k; 22mF 41000000k; 47mF 42000000k; 100mF 43000000k; 220mF 44000000k; 470mF 45000000k; 1mF 46000000k; 2mF 47000000k; 4mF 48000000k; 10mF 49000000k; 22mF 50000000k; 47mF 51000000k; 100mF 52000000k; 220mF 53000000k; 470mF 54000000k; 1mF 55000000k; 2mF 56000000k; 4mF 57000000k; 10mF 58000000k; 22mF 59000000k; 47mF 60000000k; 100mF 61000000k; 220mF 62000000k; 470mF 63000000k; 1mF 64000000k; 2mF 65000000k; 4mF 66000000k; 10mF 67000000k; 22mF 68000000k; 47mF 69000000k; 100mF 70000000k; 220mF 71000000k; 470mF 72000000k; 1mF 73000000k; 2mF 74000000k; 4mF 75000000k; 10mF 76000000k; 22mF 77000000k; 47mF 78000000k; 100mF 79000000k; 220mF 80000000k; 470mF 81000000k; 1mF 82000000k; 2mF 83000000k; 4mF 84000000k; 10mF 85000000k; 22mF 86000000k; 47mF 87000000k; 100mF 88000000k; 220mF 89000000k; 470mF 90000000k; 1mF 91000000k; 2mF 92000000k; 4mF 93000000k; 10mF 94000000k; 22mF 95000000k; 47mF 96000000k; 100mF 97000000k; 220mF 98000000k; 470mF 99000000k; 1mF 100000000k; 2mF 110000000k; 4mF 120000000k; 10mF 130000000k; 22mF 140000000k; 47mF 150000000k; 100mF 160000000k; 220mF 170000000k; 470mF 180000000k; 1mF 190000000k; 2mF 200000000k; 4mF 210000000k; 10mF 220000000k; 22mF 230000000k; 47mF 240000000k; 100mF 250000000k; 220mF 260000000k; 470mF 270000000k; 1mF 280000000k; 2mF 290000000k; 4mF 300000000k; 10mF 310000000k; 22mF 320000000k; 47mF 330000000k; 100mF 340000000k; 220mF 350000000k; 470mF 360000000k; 1mF 370000000k; 2mF 380000000k; 4mF 390000000k; 10mF 400000000k; 22mF 410000000k; 47mF 420000000k; 100mF 430000000k; 220mF 440000000k; 470mF 450000000k; 1mF 460000000k; 2mF 470000000k; 4mF 480000000k; 10mF 490000000k; 22mF 500000000k; 47mF 510000000k; 100mF 520000000k; 220mF 530000000k; 470mF 540000000k; 1mF 550000000k; 2mF 560000000k; 4mF 570000000k; 10mF 580000000k; 22mF 590000000k; 47mF 600000000k; 100mF 610000000k; 220mF 620000000k; 470mF 630000000k; 1mF 640000000k; 2mF 650000000k; 4mF 660000000k; 10mF 670000000k; 22mF 680000000k; 47mF 690000000k; 100mF 700000000k; 220mF 710000000k; 470mF 720000000k; 1mF 730000000k; 2mF 740000000k; 4mF 750000000k; 10mF 760000000k; 22mF 770000000k; 47mF 780000000k; 100mF 790000000k; 220mF 800000000k; 470mF 810000000k; 1mF 820000000k; 2mF 830000000k; 4mF 840000000k; 10mF 850000000k; 22mF 860000000k; 47mF 870000000k; 100mF 880000000k; 220mF 890000000k; 470mF 900000000k; 1mF 910000000k; 2mF 920000000k; 4mF 930000000k; 10mF 940000000k; 22mF 950000000k; 47mF 960000000k; 100mF 970000000k; 220mF 980000000k; 470mF 990000000k; 1mF 1000000000k; 2mF 1100000000k; 4mF 1200000000k; 10mF 1300000000k; 22mF 1400000000k; 47mF 1500000000k; 100mF 1600000000k; 220mF 1700000000k; 470mF 1800000000k; 1mF 1900000000k; 2mF 2000000000k; 4mF 2100000000k; 10mF 2200000000k; 22mF 2300000000k; 47mF 2400000000k; 100mF 2500000000k; 220mF 2600000000k; 470mF 2700000000k; 1mF 2800000000k; 2mF 2900000000k; 4mF 3000000000k; 10mF 3100000000k; 22mF 3200000000k; 47mF 3300000000k; 100mF 3400000000k; 220mF 3500000000k; 470mF 3600000000k; 1mF 3700000000k; 2mF 3800000000k; 4mF 3900000000k; 10mF 4000000000k; 22mF 4100000000k; 47mF 4200000000k; 100mF 4300000000k; 220mF 4400000000k; 470mF 4500000000k; 1mF 4600000000k; 2mF 4700000000k; 4mF 4800000000k; 10mF 4900000000k; 22mF 5000000000k; 47mF 5100000000k; 100mF 5200000000k; 220mF 5300000000k; 470mF 5400000000k; 1mF 5500000000k; 2mF 5600000000k; 4mF 5700000000k; 10mF 5800000000k; 22mF 5900000000k; 47mF 6000000000k; 100mF 6100000000k; 220mF 6200000000k; 470mF 6300000000k; 1mF 6400000000k; 2mF 6500000000k; 4mF 6600000000k; 10mF 6700000000k; 22mF 6800000000k; 47mF 6900000000k; 100mF 7000000000k; 220mF 7100000000k; 470mF 7200000000k; 1mF 7300000000k; 2mF 7400000000k; 4mF 7500000000k; 10mF 7600000000k; 22mF 7700000000k; 47mF 7800000000k; 100mF 7900000000k; 220mF 8000000000k; 470mF 8100000000k; 1mF 8200000000k; 2mF 8300000000k; 4mF 8400000000k; 10mF 8500000000k; 22mF 8600000000k; 47mF 8700000000k; 100mF 8800000000k; 220mF 8900000000k; 470mF 9000000000k; 1mF 9100000000k; 2mF 9200000000k; 4mF 9300000000k; 10mF 9400000000k; 22mF 9500000000k; 47mF 9600000000k; 100mF 9700000000k; 220mF 9800000000k; 470mF 9900000000k; 1mF 10000000000k; 2mF 11000000000k; 4mF 12000000000k; 10mF 13000000000k; 22mF 14000000000k; 47mF 15000000000k; 100mF 16000000000k; 220mF 17000000000k; 470mF 18000000000k; 1mF 19000000000k; 2mF 20000000000k; 4mF 21000000000k; 10mF 22000000000k; 22mF 23000000000k; 47mF 24000000000k; 100mF 25000000000k; 220mF 26000000000k; 470mF 27000000000k; 1mF 28000000000k; 2mF 29000000000k; 4mF 30000000000k; 10mF 31000000000k; 22mF 32000000000k; 47mF 33000000000k; 100mF 34000000000k; 220mF 35000000000k; 470mF 36000000000k; 1mF 37000000000k; 2mF 38000000000k; 4mF 39000000000k; 10mF 40000000000k; 22mF 41000000000k; 47mF 42000000000k; 100mF 43000000000k; 220mF 44000000000k; 470mF 45000000000k; 1mF 46000000000k; 2mF 47000000000k; 4mF 48000000000k; 10mF 49000000000k; 22mF 50000000000k; 47mF 51000000000k; 100mF 52000000000k; 220mF 53000000000k; 470mF 54000000000k; 1mF 55000000000k; 2mF 56000000000k; 4mF 57000000000k; 10mF 58000000000k; 22mF 59000000000k; 47mF 60000000000k; 100mF 61000000000k

News from the Electronics World

PHILIPS — SIMPLY POUNDS AHEAD

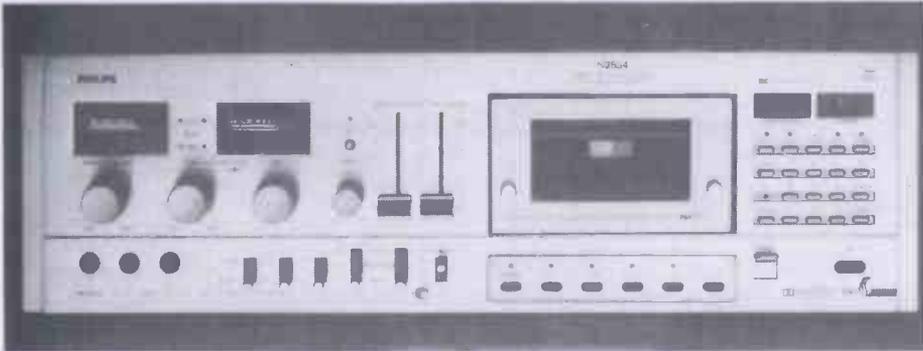

Everyone with £547 to spare pay attention now. Philips would like you to know all about the N2554 Micro-processor controlled cassette deck. The N2554 is part of the new Black Tulip range of Hi-Fi separates and offers a unique degree of versatility to both the home and semi-professional user.

Those of you with sharp eyes may have noticed the rather unusual number of little buttons on the right hand side of the unit. This keyboard controls the coded search system which allows the user to find individual recordings on a cassette tape, play them and repeat them in any chosen sequence.


The system works by recording inaudible

pulses onto the tape. The Computer Coded Search (CCS) is capable of programming up to 50 individually identifiable codes onto each side of a cassette tape, this, Philips assure us, is sufficiently flexible for professional use.

As you would expect the performance figures are pretty good, the N2554 is quite happy to use the latest metal tapes and has separate bias and equalisation switches for Chrome and Ferro tapes.

If you're still with us, the N2554 should be just reaching the shops about now. If you can afford one then why not invite us round one night to hear it. Make sure you've got plenty of custard creams too!

SMALL STUFF

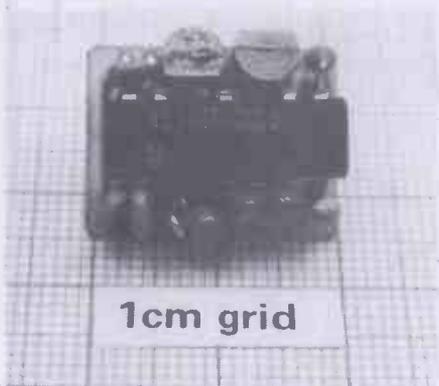

Building an R/C system? If you are then you may be interested in this new subminiature Servo Amplifier from Ambit. The circuit (called the SD1) can be used to drive servo motors rated up to 500mA quite happily and Ambit assure us that it can be equally well employed at the front end of high power systems. As you can see it couldn't be much smaller, maybe we'll try it out in the Microbe it looks ideal. If you want to know more then write to Ambit at: 200 North Service Road, Brentwood, Essex CM14 4SG.


LATE HE

We would like to apologise to everyone for the delay in getting the last two issues onto the newsstands, this was due to circumstances beyond our control.

TRANSFORMERS

Remember the transformer offer in the March and April HE's. Well, that's all they are now — a memory. Sorry, we've sold out.

TOOL TIME

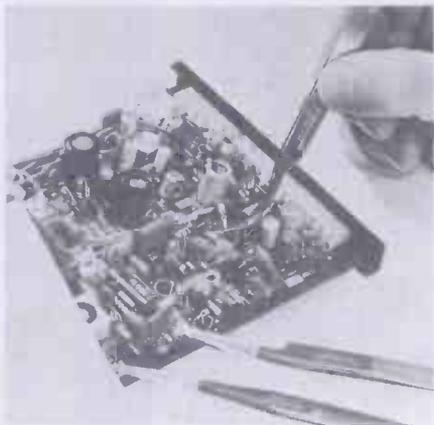

Do you poke about in confined spaces? You do, then take a look at these natty (doubtless state-of-the-art too) metal precision tweezers. They come from a company called Bacho. By the look of them you would be well advised to use them on equipment that has been previously switched off (you would soon discover that anyway). For more information contact Bacho at Bacho Tools Ltd, Beaumont Road, Banbury, Oxon OX16 7TB.

BOOK REVIEW

Ask any electronics engineers which is the best reference book for transistor and sorting out substitutes for foreign semiconductors and chances are he'll say 'Towers'. The Towers International Transistor Selector has been around for some years now. We have just received the latest version called Update 2. It's not cheap at £9.50 but then quality never is. It contains over 20,000 entries (6,500 new ones in this edition alone) and the chances of not being able to find a particular device are pretty slim. This is probably one of the most useful books you'll ever have in your workshop. It is published by W Foulsham & Co ISBN 0-572-00955-0.

CD IGNITION

Some people have been experiencing difficulty in obtaining the high voltage capacitors used in this design. Two types are suggested, they are the B32562 0µ47 and B32563 1µ0. Both are obtainable from Marshalls for 28 and 48 pence respectively.

SINCLAIR ZX80

Many of you have written to us asking for a review on the Sinclair ZX80 micro. Ever eager to please we contacted Sinclair a while ago (about the time of its launch). Even then we were informed that we couldn't have one till May. A couple of weeks ago we tried again, it seems they have so many orders that they cannot even supply review models. Worry not though, our sister magazine, Computing Today, got hold of an early preview model and we took the opportunity to play with it. Suffice it to say we were impressed enough to redouble our efforts and with a bit of luck a review will be coming in the next couple of months.

CATALOGUES

One catalogue that isn't in this month's survey is the new offering from Heathkit. The new catalogue is understandably choc full of the new range of computer goodies that Heath are now offering under the name Zenith Data Systems. For your copy write to Heath at Heath Electronics (UK) Ltd, Gloucester, GL2 6EE.

TRANSLATOR TALKING POINT

Remember the talking translator we mentioned last month? Well, it is now on sale over here, price is about £170 and is currently being imported by those well known purveyors of washing machines, Tempo Ltd. Full report coming soon.

ERRATA

Thanks to Mr Corbett for spotting a couple of errors on the Hobbycom in the March HE. The labels for C2 and C3 on the Overlay diagram (fig. 3) have been transposed. A link is missing both on Figs 3 and 4. It is between the positive side of C6 and the junction of C5 and R5.

Miniclock now, the transistor Q2 in Fig. 5 is PNP and the emitter is connected to the +ve line. The collector goes to the junction of R7 and IC1d. The base connection is correct.

NEW

CONSTRUCTORS PACK 7

ALL THE PARTS TO BUILD THE PRACTICAL ELECTRONICS TRAVELLER CAR RADIO

- * EASY TO BUILD * 5 PUSH BUTTON TUNING * MODERN STYLING DESIGN * ALL NEW UNUSED COMPONENTS
- * 6 WATT OUTPUT * READY ETCHED & PUNCHED P.C.B.
- * INCORPORATES SUPPRESSION CIRCUITS



The pack contains all the electronic components to build the radio, you supply only the wire and solder as featured in the Practical Electronics March issue. The P.E. Traveller features pre-set tuning with five push button options, black illuminated tuning scale, with matching rotary control knobs, one, combining on/off volume and tone-control, the other for manual tuning, each set on wood simulated fascia. The P.E. Traveller has a 6 watts output, negative ground and incorporates an integrated circuit output stage, a Mullard IF module LP1181 ceramic filter type, pre-aligned and assembled and a Bird pre-aligned push button tuning unit. The P.E. Traveller fits easily in or under dashboards. Complete with instructions.

£10.50 p&p £1.75

CONSTRUCTORS PACK 7A
Suitable stainless steel fully retractable locking aerial and speaker (approx 6" x 4") is available as a kit complete.
£1.95 Per Pack, p & p £1.00.
Pack 7A may only be purchased at the same time as Pack 7.
NOTE: Constructor's pack 7A sold complete with radio kit **£15.20** including p&p.

A FEATURED PROJECT IN PRACTICAL ELECTRONICS



323 EDGWARE ROAD, LONDON W2. For Personal Shoppers Only. Mon-Sat 9.30am-5.30pm Closed Thursday
21 HIGH STREET, ACTON W3 6NG. Mail Order Only. No Callers.

NEW 12+12 AMPLIFIER KIT



An opportunity to build your own 12 watts per channel stereo amplifier with up-to-the-minute features. To complete you just supply screws, connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs—tape, speakers and headphones. By the press of a button it transforms into a 24 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus 2 power amplifier assembly kits. Also featured 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia panel with matching knobs. Easy to assemble teak simulate cabinet and ready made metal work. For further information instructions are available price 50p. Free Size 8 1/2" x 8 1/2" x 4" approx. **£13.95** with kit. NOTE for use with 4 to 8 ohms speakers. p&p £2.55

TWO WAY SPEAKER KIT To suit above amp. Comprising 2, 8" approx Philips base unit, and 2, 3 1/2" approx tweeters with 2 crossover capacitors **£4.95** p&p £1.65. Available only to first time purchasers of the 12 + 12 kit.

Mullard AUDIO MODULES IN BARGAIN PACKS

ACCESSORIES ARE ONLY AVAILABLE TO THOSE CUSTOMERS WHEN BUYING OUR BARGAIN PACKS



CURRENT CATALOGUE PRICE AT OVER
£25 PER PACK


SEE OUR PRICES

- 1 PACK 1 2x LP1173 10w RMS output power audio amp modules, + 1 LP1182/2 Stereo pre amp for ceramic and auxiliary input OUR PRICE **£5.00** p&p £1.10
- 2 PACK 2 2x LP1173 10w RMS output power audio amp modules + 1 LP1184/2 Stereo pre amp for magnetic, ceramic and auxiliary inputs illus. OUR PRICE **£7.65** p&p £1.15

ACCESSORIES Suitable mains power supply parts, consisting of mains transformer, bridge rectifier, smoothing capacitor and set of rotary stereo controls for treble, bass, volume and balance. **£3.00** plus p&p £1.60

Two Way Speaker Kit Comprising of two 8" x 5" approx. 4 ohm bass and two 3 1/2" 15 ohm mid-range tweeter with two cross-over capacitors. Per stereo pair plus p&p **£4.05**

£76.00 DISCO AMP

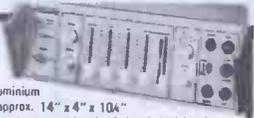

Brushed aluminium fascia and rotary controls. Size approx. 14" x 4" x 10 1/2". Five vertical slide controls, master volume, tape level, mic level, deck level, PLUS INTER DECK FADER for perfect graduated change from record deck No. 1 to No. 2 or vice versa. Pre fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level. Output 100 watts RMS 200 watts peak

EMI SPEAKER BARGAIN

Stereo pair 350 lit. System consists of 13" x 8" approx woofer with rolled surround, 3 1/2" Goodman tweeter crossover components and circuit diagram. Frequency response 20 Hz to 20 KHz. Power handling 15 watts RMS 20 watts max 8 ohm impedance. **£18.25** Per stereo pair p&p £4.20

BSR P200

Belt drive chassis turntable unit semi-automatic, cueing device. p&p £3.00 Shure M75 6 Magnetic Cartridge to suit. **£7.95**



BSR Manual single play record deck with auto return and cueing lever, fitted with stereo ceramic cartridge 2 speeds with 45 rpm spindle adaptor ideally suited for home or disco use. **£12.25** p&p £2.75 OUR PRICE

PHILLIPS RECORD PLAYER DECK GC037 HiFi record player deck, belt drive complete with GP401 magnetic cartridge—LIMITED STOCK. **£27.50** complete. UNBEATABLE OFFER AT BUYER COLLECT ONLY



BARGAIN OFFER Ariston pick-up arm manufactured in Japan. Complete with headshell. Listed price over £30.00. **OUR PRICE £11.95** p&p £2.50

50WATT MONO DISCO AMP

£30.60 p&p £3.20
Size approx 13 1/2" x 5 1/2" x 8 1/2"
50 watts rms. 100 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with infernal push-pull switches. Independent bass and treble controls and master volume.

NOW AVAILABLE



30 + 30 WATT STEREO AMPLIFIER
Viscount IV unit in teak simulate cabinet. Silver finish rotary controls and pushbuttons with matching fascia, red mains indicator and stereo jack socket. Functions switch for mic magnetic and crystal pickups, tape tuner and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30 + 30 watts RMS 60 + 60 watts peak for use with 4 to 8 ohm speakers. Size 14 1/2" x 3" x 10" approx. **£32.90** p&p £3.30 BUILT AND READY TO PLAY



323 EDGWARE ROAD, LONDON W2
21 HIGH STREET, ACTON W3 6NG

ACTON: Mail Order only, No callers
ALL PRICES INCLUDE VAT AT 15%
All items subject to availability. Price correct at 27.3.80 and subject to change without notice.
All enquires Stamped Addressed Envelope.
NOTE: Persons under 16 years not served without parent's authorisation.

Personal Shoppers EDGWARE ROAD LONDON W2 Tel: 01-723 8432, 9.30am-5.30pm. Closed all day Thursday ACTON: Mail Order only. No callers GOODS DESPATCHED TO MAINLAND AND N. IRELAND ONLY

BARGAIN CORNER

Show us that you could have purchased for less within one month of your purchase and we will refund the difference!

MULTIMETERS:



● **DT 1314 A** superb 38 range meter. Special features include 50KΩ / VDC movement, 10 amp DC Scale, resistance up to 100 MΩ, 2 ranges for testing batteries, long extraflex leads, batteries included. Usually sold for £35. **FOR LIMITED PERIOD £25 + 70p post.**



● **DT1004 20** KΩ/VDC movement, 16 ranges and off position, mirror scale, protected movement, battery included. Usually sold for £16, our price £12 + 70p post.



CAR AUDIO:



● **New Model Stereo Cassette/Radio** M.W., stereo FM and stereo cassette player. 8 Watts per channel, fast forward and autostop, includes fitting kit and **FREE SPEAKERS**. Sold elsewhere for up to £85 (believe it or not). Our price £45 + £1.40 post. (For negative earth cars only).

● **End of line clearance** LW/MW stereo cassette players. 8 watts per channel. Fast forward and autostop, usually sold for between £45 and £65. Limited number at £34 + £1.20 post. (For negative earth only). Manual car radios 5 watts, includes fitting kit and speaker. Neg. or pos. earth. £9 + £1.20 post.



METAL DETECTORS:

● **Induction Balance Model.** Highly sensitive model with speaker and meter, 7-inch search head and telescopic stem. Usually sold for £39.95. Our price £24.50 + £1.20 post.

● **BFO Model** Due to importer clearing stocks we can offer this standard model for the incredible price of £11.50 + £1.20 post.

All goods guaranteed one year. 10 day money back offer on all undamaged goods. Goods ex-stock at time of going to press. Send S.A.E. for details.

MINIKITS ELECTRONICS LTD

HOBBY
884 HAINAULT ROAD
LEYTONSTONE
LONDON E11 1EH

TELL US ABOUT YOUR LOCAL COMPONENT SUPPLIERS

We want to know who you go to to buy components, equipment, etc.

PLEASE FILL IN THE COUPON BELOW AND SEND IT TO "THE DEALER LIST", HOBBY ELECTRONICS, 145 CHARING CROSS ROAD, LONDON WC2H 0EE.

SUPPLIER ONE: Name

Address

Supplies: Components/CB/Other

SUPPLIER TWO: Name

Supplies: Components/CB/Other

SUPPLIER THREE: Name:

Supplies: Components/CB/Other


SENDER:

REGION:

Tee-shirt size

WIN A FREE TEE-SHIRT!

IDENTIFY YOUR REGION BELOW:

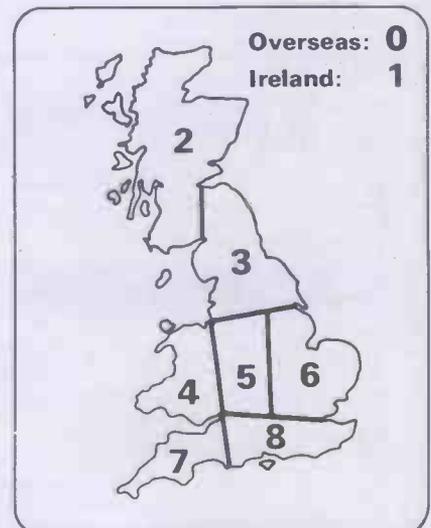

On July 15th we will sort senders by region and send a free HE tee-shirt to a randomly-selected winner in each area (provided you've given us three names of dealers in your area). Please use extra sheets if you know lots of local suppliers. Use a photocopy or facsimile if you don't want to cut up your magazine.

HE Microbe

TWO CHANNEL DIGITAL R/C SYSTEM

At last, the great day has arrived. Hobby Electronics now present what must be the last word in simple, well designed and cheap to build digital proportional R/C systems. The Microbe offers two fully proportional channels and a further two 'switched' channels — all for under £20.

FIRST THE BAD NEWS, the Microbe two channel digital proportional R/C system is not suitable for airborne models. Now for the good news, the complete system excluding servos should cost less than £20 to build!

From the beginning it was decided that the Microbe should be designed for either boats or cars, a full blown 2 + 2 system will be appearing later in the year. With this in mind the Microbe has two fully proportional channels (with provision for two 'switched channels' but more of that later) and is possibly the simplest system ever published. The Rx, Tx combination is based on a pair of purpose-built ICs from National, the LM1871 in the transmitter and LM1872 in the receiver. Because most of the clever stuff, ie encoding and decoding, is done in the ICs external components are kept to an absolute minimum. Setting the system up should present few problems and providing you follow our constructional notes will be rewarded with a really first-class system.

CONSTRUCTION

The only thing to bear in mind when building the Microbe is the design of the PCB. If you try to design your own or use the otherwise excellent Veroboard you will come to grief — take it from us because we know, we've got the 'dud' prototypes to prove it. Still on the subject of PCBs, take extra care when drilling the holes for the coils, they are slightly delicate and do not take kindly to being forced into holes that are too small.

Actual assembly is very straightforward, we chose to use sockets for the Rx IC because we are careful drivers, if your model is going to continuously bounce off brick walls then solder the IC directly onto the PCB. Similarly it's a good idea to seal up the transmitter coil with wax.

The wiring up of the servo output leads depend upon the type of servo used. If you're only using one servo and a R/C motor speed controller (the one in April HE is ideal) then try to adopt some kind of uniformity in the plugs and sockets so that the system can be moved from



The complete Microbe system alongside our 'Letricar' test bed. See last month's R/C review for details.

Parts List

RESISTORS (all 1/4 W 5%)
 R1 22R
 R2 100k
 R3 220R

CAPACITORS
 C1,5,7,8 10n
 C2,6 100n
 C3 100u Tantalum 16 V
 C4 50n
 C9 1n

Note. All capacitors except C3 should be miniature disc ceramic or polycarbonate, for best results use high stability types.
 Working voltages should not be less than 9 V

INDUCTORS
 L1, T3 MKXCSK3464BM
 T1 YRCS12374AC2
 T2 YMCS17104GO
 (See Buylines)

SEMICONDUCTORS
 IC2 LM1872
 D1 IN4148
 XTAL 27MHz min R/C type
 Rx XTAL is 455 kHz below Tx XTAL

MISCELLANEOUS
 Servos — conventional 3-wire type.
 Fleet, Sanwa etc etc.
 Case — Vero type 301
 PCB socket for XTAL
 Plugs and sockets for servos.

Buylines

The coils and ICs used in the Microbe are the only components likely to cause problems.

The coils come from TOKO Ltd and are available from Ambit International Ltd. The ICs are available from NIC (see below).

A complete kit of parts for the Microbe for under £20 is available from NIC, 61 Broad Lane, Tottenham (see ad in this issue).

one model to another without changing all the plugs.

If you are likely to be using the Microbe alongside other R/C systems then it is a good idea to use an interchangeable crystal system, we used crystal sockets on both the transmitter and receiver.

Choice of a box and control surface is up to the individual, we opted for a rotary control for the steering and a linear slider for the forward/reverse function, in either case see the section on alignment for hints on selecting the correct values for the control and trim pots.

ALIGNMENT

Assuming you've now got an assembled Microbe in front of you we can now proceed to the dreaded alignment procedure. First the transmitter must be tweaked

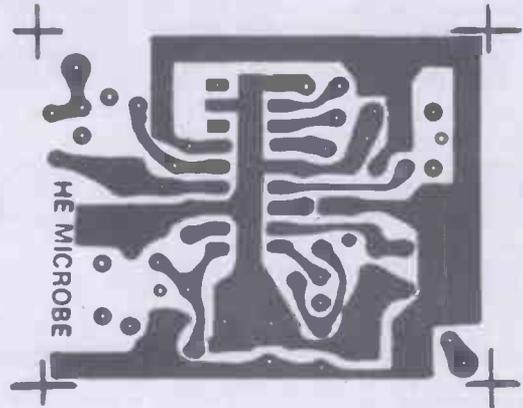


Fig. 6. PCB layout for the Microbe receiver. As with the transmitter, this layout MUST be strictly followed.


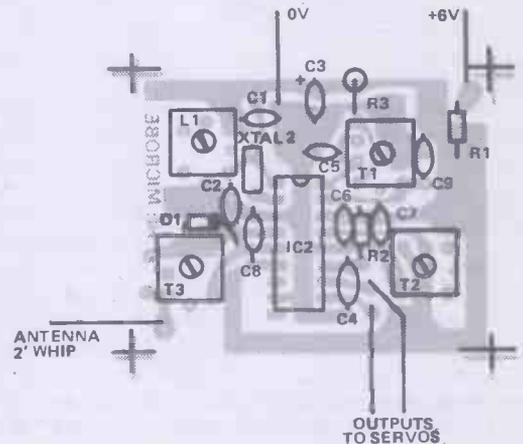


Fig. 7. Overlay diagram for the Microbe receiver. If the system is to take a lot of knocks we suggest you dispense with the IC sockets.

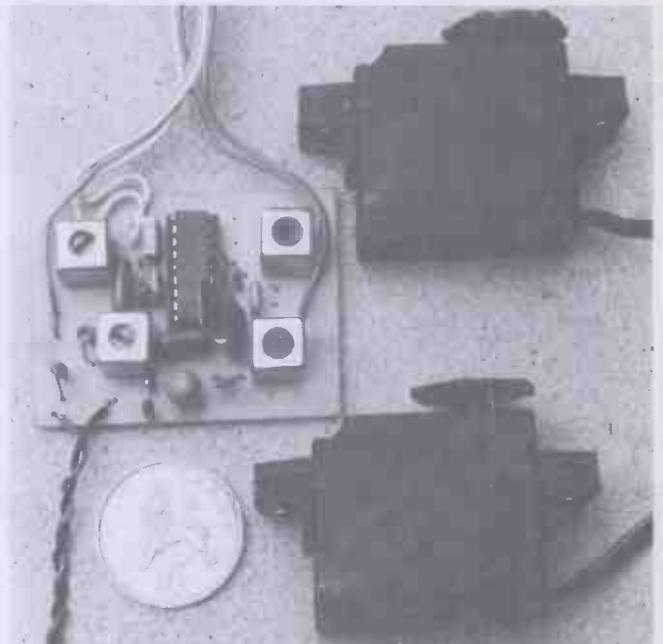


The Microbe receiver next to a couple of standard 3-wire servos. Note the size of the board next to a 10 pence coin!

up for maximum range. Easiest way to do this is with a field strength meter (members of the CB fraternity have at their disposal excellent SWR/FSM meters) otherwise you'll just have to find a receiver capable of receiving on 27 megs and site the TX about six feet away. By twiddling L2 you'll hear a loud buzz of around 100 Hz get progressively louder and softer. Adjust the slug for greatest output then drop some candle wax down the core to seal the slug in place (for the purposes of setting up the transmitter use the values we recommend in the parts list). Make sure all is well by twiddling the pots on the transmitter, the note should change very slightly when either pot is turned.

Now for the receiver. The best way to set up the receiver is with a scope. Monitor pin 2 of IC2, you should see a broad band of noise, this is the oscillator, if this isn't working nothing else will. Adjust the core in L1 for maximum amplitude. With the transmitter switched on and the servos disconnected (place the Tx about 3 feet away from the Rx aerial) monitor the output from pin 15 IC2. With your non-metallic screwdriver adjust the core in T1 for maximum amplitude, still on pin 15 tweak up T2 and T3, now go through T1, 2 and 3 again just for luck.

If you're particularly unfortunate not to have access to an oscilloscope all is not lost. The Microbe can be set up by ear but be prepared for a drop in range. To set the system up by ear you need to connect up one servo. Adjust L1 until the servo just starts to quiver, you'll find this happens over about one turn of the slugs travel set it midway. With all the transmitter pots set midway slowly turn T1. At one distinct point the servo should start to turn and come to rest. If it doesn't then move the transmitter pot slowly whilst turning the T1 slug. Now you should have some kind of response, move the transmitter about two feet further away and with a friend turning the control pot on the Tx adjust T2 and T3 for smooth operation. Repeat this sequence at two or three feet intervals, with each successive move the adjustment should become more critical, continue this until you are satisfied it cannot be improved.

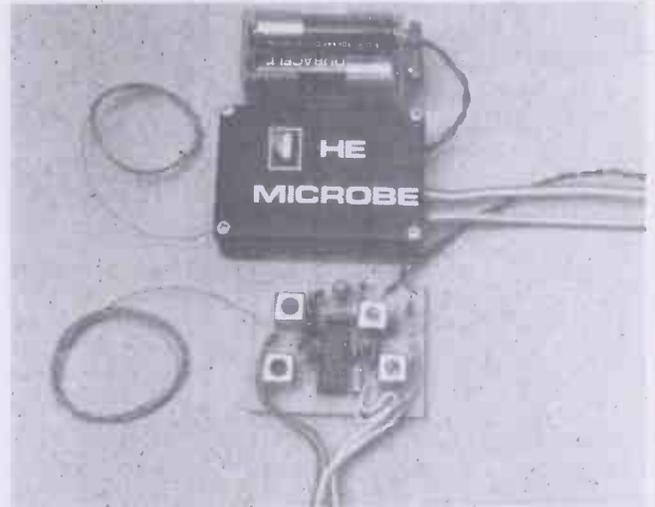The degree of servo rotation is governed by the resistance of RV1 and Rt and RV2 and Rt. (you can use two separate Rts, one for each channel. We found that the best results were obtained by using an 82k resistor for Rt. The servo would move through nearly 180 degrees, as you only use a portion of the rotation of the



Two Microbe prototype receivers. Our four-battery power source will last approximately 2 hours.

pot anyway it made the control very responsive. If for any reason you wish to tailor your system then we suggest that you substitute a 500k pre-set pot for Rt and adjust that until you get the rotation you require. Measure the resistance of the preset and substitute a fixed resistor. The values of RV1 and RV2 are similarly flexible, different degrees of servo rotation can be achieved with pots down to about 10k (don't use anything lower or the servo will hardly move at all)

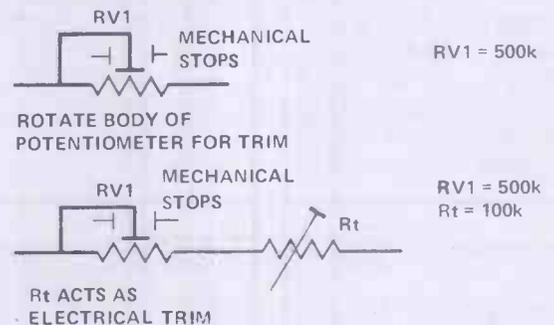


Fig. 8. Two methods of adding 'trim' to the transmitter control pots. Unless you have access to a scope, the 'suck it and see' method is probably best.


INSTALLATION

That just about covers the Microbe system, installation within a box is essential to protect the receiver, (use a waterproof one if your model floats!). It is always a good idea to wrap the receiver up in a piece of foam rubber to protect it against knocks. One final word of warning the Microbe is NOT intended for model aircraft, range on a good day with the wind in the right direction will never be much more than 100 yards, but then that is more than enough for a model car or boat. Don't complain to us if your model runs away from you and we certainly don't want any technical enquiries from people that have built it on anything other than our PCBs. Good luck. **HE**

You will need a licence to operate the Microbe. It costs £2.80 for five years. An application form is available from: The Home Office, Radio Regulatory Department, Waterloo Bridge House, Waterloo Road, London SE1 8UA



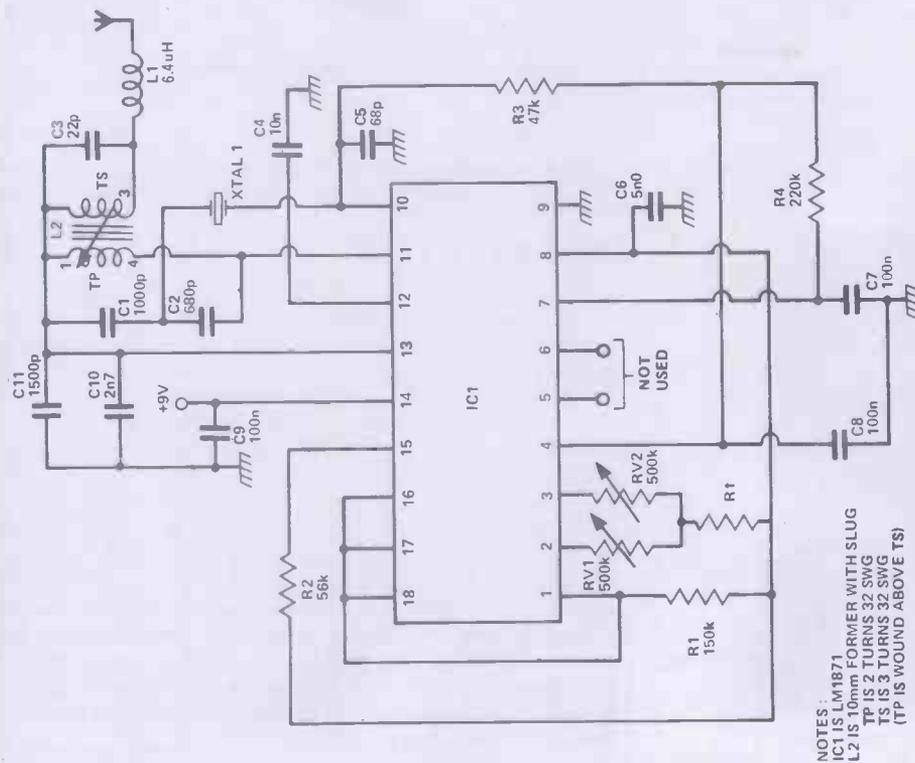The Microbe receiver in its box. As you can see we cut a slot in the box to allow for easy changing of crystals.



NOTES:
 IC1 IS LM1871
 L2 IS 10mm FORMER WITH SLUG
 TP IS 2 TURNS 32 SWG
 TS IS 3 TURNS 32 SWG
 (TP IS WOUND ABOVE TS)


Fig. 1. Circuit diagram of the Microbe Transmitter.

How it Works

TRANSMITTER

Just about all the clever stuff is done by the IC, the external crystal oscillator is controlled by the network comprising L2, C1, 2 and 3, the encoder is controlled by the pots RV1 RV2 and R1. The unused pins 5 and 6 when grounded will make the unused pins on IC2 (6&7) go high, this can be used for simple switching functions.

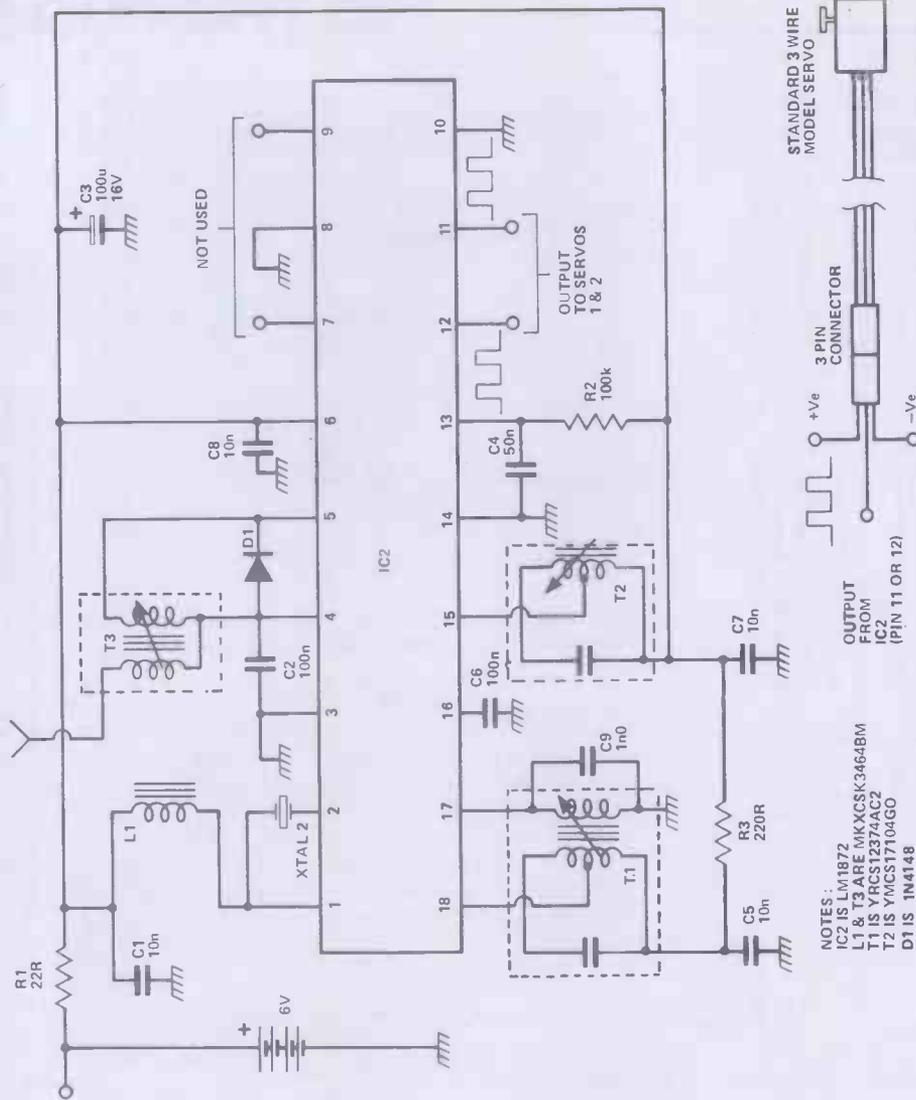For details of adjusting and setting up the control Trims see 'Alignment'. R1 can be two separate resistors for each control pot.



NOTES:
 IC2 IS LM1872
 L1 & T3 ARE MKXCS3464BM
 T1 IS YRCS12374AC2
 T2 IS YMCS17104GO
 D1 IS 1N4148

Fig. 2. Circuit diagram of the Microbe receiver.

How it Works

RECEIVER

As with the transmitter all the hard work, decoding etc is done by the IC. The oscillator comprising XTAL L1 and C1 runs at 455 kHz below the transmitter frequency. T1 controls the mixer section, T2 adjusts the IF response and T3 optimises the aerial input sensitivity. The diode D1 protects the IC against static discharge. C8 provides compensation for the AGC loop which spans a 70dB range.

The receiver section is a simple single conversation design with AGC which mixes down the 455kHz and provides 56dB of gain with the transformers suggested.

The digital decoder section within the IC provides another 30dB of gain resulting in an overall system gain of 88dB.

For best results the aerial should not be less than 24 inches long.

Parts List

RESISTORS (all 1/4 W 5%)

- R1 150k
- R2 56k
- R3 47k
- R4 220k
- Rt1 } Rt
- Rt2 }

(see text)

POTENTIOMETERS

- RV1,2 500k Lin slider (see text)

CAPACITORS

- C1 1000p
- C2 680p
- C3 22p
- C4 10n
- C5 68p
- C6 5n0
- C7, 8, 9 100n
- C10 2n7
- C11 1n5

Note. All capacitors should be disc ceramic or polycarbonate high stability for best results. Working voltages should be not less than 9 V

SEMICONDUCTOR

- IC1 LM1871 (see Rx Buylines)
- XTAL 27MHz min R/C type — see text

INDUCTORS

- L1 6.4uH min choke
- L2 — See text

MISCELLANEOUS

- Case to suite (Vero Box on prototype type 101)
- PCB socket for XTAL
- Aerial, 3ft telescopic with base
- Switch — min toggle
- 10mm coil former with slug.

Buylines

None of the transmitter components should be difficult to obtain. See text for coil winding details. See the receiver 'Buylines' for details of a kit.



HE Microbe


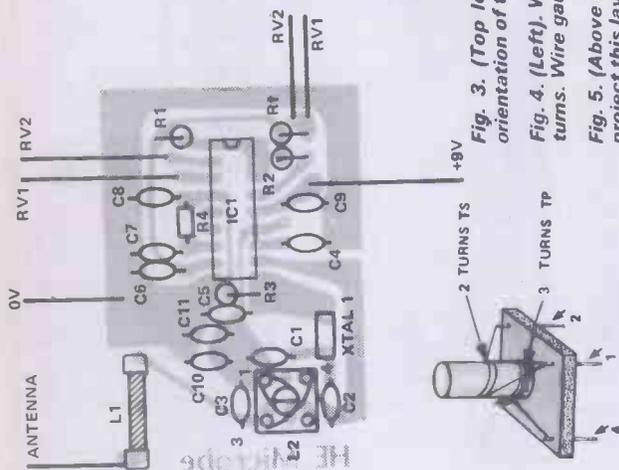


Fig. 3. (Top left). Overlay diagram for the Microbe transmitter, note the orientation of the coil L2, for winding details see Fig. 4.

Fig. 4. (Left). Winding details of L2. The coil comprises two windings of 2 and 3 turns. Wire gauge is not critical, we used 32 SWG.

Fig. 5. (Above right). PCB layout for the Microbe transmitter. For a successful project this layout MUST be used.

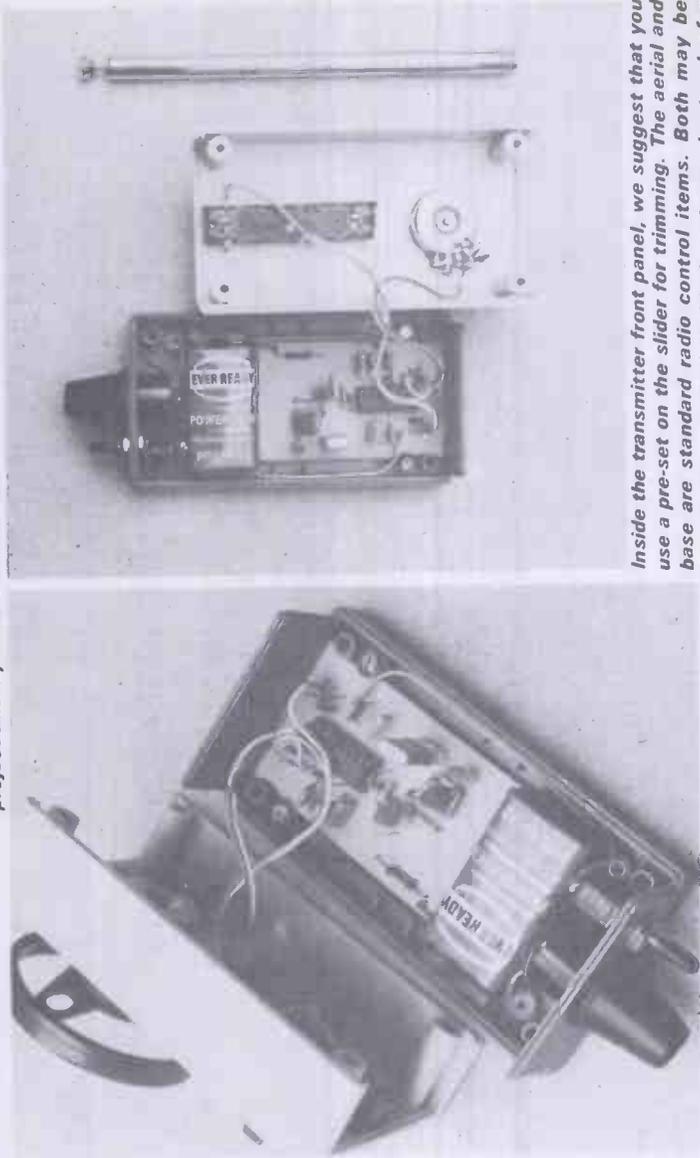

Inside the transmitter front panel, we suggest that you use a pre-set on the slider for trimming. The aerial and base are standard radio control items. Both may be obtained from R/C hobbyist shops. Instead of a telescopic aerial a length of piano wire (24 inches) may be used but be prepared for a drop in range.

Close up of the PCB inside the transmitter case. Try to obtain the transmitter case. Try to obtain ceramic or polycarbonate capacitors as far as possible.

| TTLs by TEXAS | | 74259 | 250p | 4019 | 45p |
|---------------|------|-------------|------|-----------|------|
| 7400 | 11p | 74278 | 290p | 4020 | 100p |
| 74500 | 80p | 74279 | 110p | 4021 | 100p |
| 7401 | 12p | 74280 | 100p | 4022 | 100p |
| 7402 | 12p | 74290 | 150p | 4023 | 25p |
| 7403 | 14p | 74293 | 150p | 4024 | 25p |
| 7404 | 14p | 74298 | 200p | 4025 | 27p |
| 74504 | 90p | 74365 | 100p | 4026 | 130p |
| 7406 | 32p | 74366 | 100p | 4027 | 50p |
| 7407 | 32p | 74368 | 100p | 4028 | 84p |
| 7408 | 17p | 74390 | 200p | 4029 | 100p |
| 7409 | 19p | 74393 | 200p | 4030 | 55p |
| 7410 | 15p | 74490 | 225p | 4031 | 200p |
| 7411 | 24p | 74495 | 200p | 4032 | 180p |
| 7412 | 29p | 74500 | 14p | 4033 | 180p |
| 7413 | 30p | 74502 | 16p | 4034 | 110p |
| 7414 | 50p | 74503 | 18p | 4035 | 110p |
| 7414 | 50p | 74504 | 16p | 4036 | 110p |
| 7416 | 27p | 74505 | 25p | 4037 | 110p |
| 7417 | 27p | 74506 | 22p | 4038 | 100p |
| 7420 | 17p | 74510 | 20p | 4041 | 80p |
| 7421 | 40p | 74511 | 40p | 4042 | 80p |
| 7422 | 22p | 74513 | 40p | 4043 | 90p |
| 7423 | 34p | 74514 | 72p | 4044 | 90p |
| 7425 | 30p | 74515 | 45p | 4045 | 90p |
| 7426 | 34p | 74516 | 40p | 4046 | 100p |
| 7427 | 34p | 74521 | 40p | 4048 | 120p |
| 7428 | 17p | 74527 | 38p | 4049 | 50p |
| 7430 | 17p | 74530 | 20p | 4050 | 48p |
| 7432 | 30p | 74532 | 27p | 4051 | 80p |
| 7433 | 40p | 74542 | 70p | 4052 | 70p |
| 7437 | 35p | 74547 | 90p | 4053 | 80p |
| 7438 | 35p | 74551 | 24p | 4054 | 150p |
| 7440 | 17p | 74555 | 30p | 4055 | 125p |
| 7441 | 70p | 74573 | 50p | 4056 | 135p |
| 7442 | 60p | 74574 | 36p | 4059 | 60p |
| 7443 | 11p | 74575 | 40p | 4060 | 140p |
| 7444 | 11p | 74576 | 45p | 4063 | 120p |
| 7445 | 100p | 74583 | 110p | 4066 | 55p |
| 7446A | 93p | 74585 | 100p | 4067 | 45p |
| 7447A | 50p | 74586 | 40p | 4068 | 27p |
| 7448 | 80p | 74590 | 40p | 4069 | 27p |
| 7450 | 17p | 74592 | 70p | 4070 | 30p |
| 7451 | 17p | 74593 | 80p | 4071 | 25p |
| 7453 | 17p | 74596 | 110p | 4072 | 25p |
| 7454 | 17p | 745107 | 45p | 4073 | 25p |
| 7460 | 17p | 745109 | 80p | 4075 | 25p |
| 7470 | 30p | 745112 | 100p | 4076 | 107p |
| 7472 | 30p | 745113 | 90p | 4081 | 27p |
| 7473 | 34p | 745114 | 45p | 4082 | 27p |
| 7474 | 30p | 745122 | 80p | 4086 | 72p |
| 7475 | 30p | 745123 | 70p | 4089 | 138p |
| 7476 | 35p | 745124 | 180p | 4094 | 250p |
| 7480 | 50p | 745126 | 60p | 4095 | 95p |
| 7481 | 100p | 745126 | 60p | 4095 | 95p |
| 7482 | 84p | 745132 | 95p | 4096 | 95p |
| 7483a | 90p | 745133 | 30p | 4097 | 340p |
| 7484 | 100p | 745136 | 55p | 4098 | 120p |
| 7485 | 110p | 745138 | 75p | 4099 | 200p |
| 7486 | 34p | 745139 | 40p | 4100 | 220p |
| 7489A | 17p | 745145 | 120p | 4101 | 132p |
| 7490 | 30p | 745147 | 220p | 4102 | 180p |
| 7491 | 80p | 745148 | 175p | 4103 | 180p |
| 7492A | 46p | 745151 | 100p | 4104 | 90p |
| 7493A | 30p | 745152 | 60p | 4105 | 95p |
| 7494 | 84p | 745154 | 200p | 4106 | 90p |
| 7495A | 80p | 745155 | 90p | 4107 | 60p |
| 7496 | 65p | 745156 | 90p | 4108 | 470p |
| 7497 | 180p | 745157 | 80p | 4109 | 100p |
| 74100 | 130p | 745158 | 90p | 4110 | 100p |
| 74104 | 60p | 745160 | 100p | 4114 | 250p |
| 74105 | 65p | 745161 | 100p | 4102 | 120p |
| 74107 | 34p | 745162 | 140p | 4103 | 70p |
| 74109 | 55p | 745163 | 100p | 4105 | 55p |
| 74110 | 55p | 745164 | 120p | 4106 | 290p |
| 74111 | 70p | 745165 | 160p | 4110 | 95p |
| 74116 | 200p | 745166 | 160p | 4111 | 95p |
| 74118 | 130p | 745173 | 110p | 4112 | 80p |
| 74119 | 210p | 745174 | 110p | 4114 | 265p |
| 74120 | 110p | 745175 | 110p | 4115 | 300p |
| 74121 | 28p | 745181 | 320p | 4116 | 300p |
| 74122 | 48p | 745182 | 100p | 4118 | 100p |
| 74123 | 48p | 745183 | 100p | 4120 | 100p |
| 74125 | 60p | 745192 | 100p | 4121 | 250p |
| 74126 | 60p | 745193 | 100p | 4126 | 100p |
| 74128 | 75p | 745195 | 140p | 4127 | 150p |
| 74132 | 75p | 745196 | 120p | 4128 | 100p |
| 74135 | 50p | 745201 | 140p | 4132 | 180p |
| 74136 | 75p | 745221 | 140p | 4133 | 180p |
| 74141 | 50p | 745240 | 175p | 4153 | 450p |
| 74142 | 200p | 745241 | 175p | 4156 | 72p |
| 74145 | 90p | 745242 | 170p | 4156 | 72p |
| 74147 | 80p | 745243 | 170p | 4159 | 250p |
| 74148 | 150p | 745244 | 170p | 4159 | 250p |
| 74150 | 100p | 745245 | 350p | 4159 | 250p |
| 74151A | 70p | 745247 | 140p | 4159 | 250p |
| 74153 | 70p | 745248 | 140p | 4159 | 250p |
| 74154 | 70p | 745249 | 140p | 4159 | 250p |
| 74155 | 90p | 745250 | 140p | 4097 | 90p |
| 74156 | 90p | 745253 | 140p | 14411 | 110p |
| 74157 | 70p | 745257 | 120p | 14412 | 110p |
| 74159 | 190p | 745258 | 160p | 14433 | 110p |
| 74180 | 100p | 745259 | 160p | 14500 | 700p |
| 74181 | 100p | 745261 | 160p | 14599 | 290p |
| 74182 | 100p | 745273 | 195p | CD22101 | 350p |
| 74183 | 100p | 745279 | 90p | CD22101 | 350p |
| 74184 | 120p | 745298 | 240p | CD22102 | 700p |
| 74185 | 130p | 745324 | 200p | INTERFACE | |
| 74186 | 120p | 745348 | 200p | IC2 | |
| 74187 | 200p | 745365 | 100p | 0M8123 | 175p |
| 74170 | 240p | 745367 | 100p | DP8304 | 450p |
| 74172 | 450p | 745368 | 100p | DM8835 | 250p |
| 74173 | 120p | 745373 | 180p | DM8836 | 250p |
| 74174 | 90p | 745374 | 180p | MC1489 | 100p |
| 74175 | 85p | 745378 | 200p | MC1489 | 100p |
| 74176 | 90p | 745390 | 160p | 25510 | 350p |
| 74177 | 90p | 745393 | 160p | 75107 | 160p |
| 74178 | 160p | 745445 | 160p | 75150 | 175p |
| 74180 | 93p | 745668 | 100p | 75154 | 175p |
| 74181 | 160p | 745669 | 100p | 75152 | 210p |
| 74182 | 90p | 745870 | 400p | 75232 | 300p |
| 74184A | 150p | 4000 SERIES | | 75234 | 375p |
| 74185 | 150p | 4000 | 15p | 75235 | 375p |
| 74186 | 500p | 4001 | 27p | 75361 | 300p |
| 74188 | 325p | 4002 | 25p | 75363 | 400p |
| 74190 | 90p | 4003 | 25p | 75365 | 90p |
| 74191 | 90p | 4007 | 27p | 75451 | 72p |
| 74192 | 90p | 4008 | 80p | 75491/2 | 96p |
| 74193 | 90p | 4009 | 40p | 8726 | 250p |
| 74194 | 90p | 4010 | 50p | 8728 | 300p |
| 74195 | 95p | 4011 | 27p | 8795 | 200p |
| 74197 | 95p | 4013 | 27p | 8797 | 200p |
| 74198 | 150p | 4014 | 84p | 81S95 | 140p |
| 74199 | 150p | 4015 | 84p | 81S97 | 140p |
| 74200 | 100p | 4016 | 45p | 81S98 | 140p |
| 74221 | 160p | 4017 | 80p | 9601 | 110p |
| 74251 | 140p | 4018 | 89p | 9602 | 220p |

| 93 SERIES | VEROBOARDS | TRANSISTORS | MEMORIES | UART | LOW PROFILE DIL SOCKETS BY TEXAS |
|-----------|------------|-------------|----------|------------|----------------------------------|
| 9301 | 160p | AC126 | 2102-2L | AV-3-1015P | 8 pin 10p |
| 9302 | 175p | AC127/8 | 2107 | AV-5-1013P | 14 pin 11p |
| 9308 | 215p | AC128 | 2111-2 | IM6402 | 18 pin 20p |
| 9310 | 275p | AC129 | 2112-2 | TMS6011NC | 24 pin 28p |
| 9311 | 275p | AC130 | 2114-2L | | 28 pin 32p |
| 9312 | 275p | AC131 | 4027 | | 40 pin 44p |
| 9314 | 285p | AC132 | 4044 | | |
| 9315 | 285p | AC133 | 4049 | | |
| 9316 | 285p | AC134 | 4116 | | |
| 9317 | 285p | AC135 | 4150 | | |
| 9318 | 285p | AC136 | 6810 | | |
| 9319 | 285p | AC137 | 74S201 | | |
| 9320 | 285p | AC138 | 74S202 | | |
| 9321 | 285p | AC139 | 74S203 | | |
| 9322 | 285p | AC140 | 74S204 | | |
| 9323 | 285p | AC141 | 74S205 | | |
| 9324 | 285p | AC142 | 74S206 | | |
| 9325 | 285p | AC143 | 74S207 | | |
| 9326 | 285p | AC144 | 74S208 | | |
| 9327 | 285p | AC145 | 74S209 | | |
| 9328 | 285p | AC146 | 74S210 | | |
| 9329 | 285p | AC147 | 74S211 | | |
| 9330 | 285p | AC148 | 74S212 | | |
| 9331 | 285p | AC149 | 74S213 | | |
| 9332 | 285p | AC150 | 74S214 | | |
| 9333 | 285p | AC151 | 74S215 | | |
| 9334 | 285p | AC152 | 74S216 | | |
| 9335 | 285p | AC153 | 74S217 | | |
| 9336 | 285p | AC154 | 74S218 | | |
| 9337 | 285p | AC155 | 74S219 | | |
| 9338 | 285p | AC156 | 74S220 | | |
| 9339 | 285p | AC157 | 74S221 | | |
| 9340 | 285p | AC158 | 74S222 | | |
| 9341 | 285p | AC159 | 74S223 | | |
| 9342 | 285p | AC160 | 74S224 | | |
| 9343 | 285p | AC161 | 74S225 | | |
| 9344 | 285p | AC162 | 74S226 | | |
| 9345 | 285p | AC163 | 74S227 | | |
| 9346 | 285p | AC164 | 74S228 | | |
| 9347 | 285p | AC165 | 74S229 | | |
| 9348 | 285p | AC166 | 74S230 | | |
| 9349 | 285p | AC167 | 74S231 | | |
| 9350 | 285p | AC168 | 74S232 | | |
| 9351 | 285p | AC169 | 74S233 | | |
| 9352 | 285p | AC170 | 74S234 | | |
| 9353 | 285p | AC171 | 74S235 | | |
| 9354 | 285p | AC172 | 74S236 | | |
| 9355 | 285p | AC173 | 74S237 | | |
| 9356 | 285p | AC174 | 74S238 | | |
| 9357 | 285p | AC175 | 74S239 | | |
| 9358 | 285p | AC176 | 74S240 | | |
| 9359 | 285p | AC177 | 74S241 | | |
| 9360 | 285p | AC178 | 74S242 | | |
| 9361 | 285p | AC179 | 74S243 | | |
| 9362 | 285p | AC180 | 74S244 | | |
| 9363 | 285p | AC181 | 74S245 | | |
| 9364 | 285p | AC182 | 74S246 | | |
| 9365 | 285p | AC183 | 74S247 | | |
| 9366 | 285p | AC184 | 74S248 | | |
| 9367 | 285p | AC185 | 74S249 | | |
| 9368 | 285p | AC186 | 74S250 | | |
| 9369 | 285p | AC187 | 74S251 | | |
| 9370 | 285p | AC188 | 74S252 | | |
| 9371 | 285p | AC189 | 74S253 | | |
| 9372 | 285p | AC190 | 74S254 | | |
| 9373 | 285p | AC191 | 74S255 | | |
| 9374 | 285p | AC192 | 74S256 | | |
| 9375 | 285p | AC193 | 74S257 | | |
| 9376 | 285p | AC194 | 74S258 | | |
| 9377 | 285p | AC195 | 74S259 | | |
| 9378 | 285p | AC196 | 74S260 | | |
| 9379 | 285p | AC197 | 74S261 | | |
| 9380 | 285p | AC198 | 74S262 | | |
| 9381 | 285p | AC199 | 74S263 | | |
| 9382 | 285p | AC200 | 74S264 | | |
| 9383 | 285p | AC201 | 74S265 | | |
| 9384 | 285p | AC202 | 74S266 | | |
| 9385 | 285p | AC203 | 74S267 | | |
| | | | | | |

**Next
Month**


Hobby Electronics

CAR BOOSTER



Having trouble hearing your car stereo? Not any more, with the HE car stereo booster pumping out 18 watts RMS per channel. Not only will you be able to hear the music over the road noise, so will half the street. This simple to build little circuit will connect up neatly to your existing equipment and will give results comparable to, and in most cases better, than commercial units costing many times more. You can't afford to miss it.

PUSH BUTTON VOLUME CONTROL

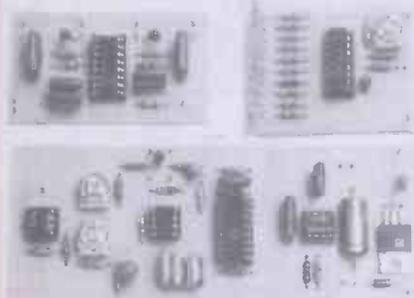

Tired of twiddling pots? Weary of winding volume controls? Sit back in your armchair and adjust the volume of your stereo system electronically. This gadget is actually three projects in one and is guaranteed not to go noisy (as most pots do eventually) or wear out. The system even has a 'memory' so you can instantly mute the sound (if the phone rings) and return it back to where it was. Would we lie to you? Find out next month. (Of course we wouldn't).

SOUND OPERATED FLASH TRIGGER


Have you ever wondered how those amazing pictures of bursting balloons and smashing light bulbs are taken, then worry no more. This nifty gadget will connect up to virtually any electronic flash gun. In a darkened room with the shutter open it will 'fire' the flash gun in response to a sharp noise. Now you can take pictures of milk splashes and unsuspecting burglars, let your imagination go wild next month.

ELECTRONICS IN PHOTOGRAPHY



Next month we take an in-depth look at how the sciences of photography and electronics are coming together. We have persuaded a professional photographer to review the latest equipment on the market and take a candid look at what we can expect to see in the not-too-distant future. Gone are the days when cameras sprouted knobs and buttons, these days a modern camera will even operate the shutter (electronically of course), focus, set the aperture and even develop the film for you.

ELECTRONIC ESPIONAGE

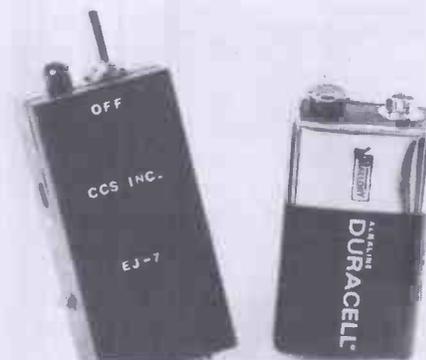

Have you got a secret? If you have, and it's interesting enough then there's a good chance someone is trying their damndest to find out all about it. Next month Rick Maybury dons his cloak and dagger to find out how electronics is helping the spy industry to become even more devious. A few years ago we could all laugh at the gadgets in James Bond films, now it's not so funny. We look at bugs no larger than the head of a match, how tapping the telephone has progressed and a couple of other devices some people would rather you didn't know about. All this plus some pictures of equipment that has never been published before, the HE guide to de-bugging your home and office and look round one of the world's foremost surveillance and anti-bugging equipment shops, right here in Britain.

HAZARD FLASHER

Many older cars lack this now essential (and in some countries compulsory) feature. If you have broken down you can alert motorists and maybe even summon help. This simple little circuit will flash both sets of indicators simultaneously and give an audible warning that the system is functioning. It could save your life one foggy day!!!

PLUS PLUS PLUS

The results of the Heath PMM competition and news of a new series from Ian Sinclair

The July issue will be on sale June 13th

The items mentioned here are those planned but unforeseen circumstances may affect the actual contents.

Books from the HE Book Service

28 Tested Transistor Project £1.55
Richard Torrens. The projects can be split down into simple building blocks which can be recombined for ideas of your own.

Electronic Projects for Beginners £1.65
F. G. Rayer. Divided into 'No Soldering Projects,' Radio and Audio Frequency, Power Supplies and Miscellaneous.

Practical Electronic Calculations and Formulae £2.55
F. A. Wilson. A valuable reference for the home and laboratory, containing all the most frequently used, and some of the less well known electronic formulae and calculations.

Popular Electronic Projects £1.75
R. A. Penfold. A collection of the most popular types of circuits and projects using modern, inexpensive and freely available components.



Digital IC Equivalents and Pin Connections £2.85
Adrian Michaels. Covers most popular types and gives details of packaging, families, functions, country of origin and manufacturer.

Radio Stations Guide £1.75
B. Babani and M. Jay. An invaluable aid to everyone with a radio receiver helping them to obtain maximum entertainment, value and enjoyment from their set.

Linear IC Equivalents and Pin Connections £3.10
Adrian Michaels. Gives most essential data for popular devices.

Electronic Security Devices £1.75
R. A. Penfold. Full of constructional circuits covering the most basic security systems to the Ultrasonic and Doppler Shift systems.

How To Build Your Own Solid State Oscilloscope £1.80
F. G. Rayer. The book contains concise practical instructions so that even an inexperienced hobbyist can construct a fairly sophisticated instrument with the minimum of difficulty and expense.

50 FET (Field Effect Transistor) Project £1.55
F. G. Rayer. Contains something of interest for every class of enthusiast. Short Wave Listener, Radio Amateur, Experimenter or audio devotee.

50 Circuits Using 7400 Series ICs £1.65
R. N. Soar. The author has managed to compile no less than 50 interesting and useful circuits using this range of devices, covering many different aspects of electronics.

Essential Theory for the Electronics Hobbyist £1.55
G. T. Rubarow gives the hobbyist a background knowledge tailored to meet his specific needs.

Beginners Guide to Building Electronic Projects £1.55
R. A. Penfold. Covers component identification, tools, soldering, constructional methods and examples of simple projects are given.

50 Projects using IC CA3130 £1.25
R. A. Penfold. Describes audio projects, RF project, Test Equipment, Household and miscellaneous circuits.

IC 555 Project £2.05
E. A. Parr. Circuits are given for the car, model railways, alarms and noise makers. Also covers the related devices 556, 558 and 559.

Second Book of CMOS IC Projects £1.80
R. A. Penfold. Following in the success of the original CMOS projects book we present the second volume covering all aspects of CMOS technology from multivibrators to triggering devices.


Note that all prices include postage and packing. Please make cheques etc. payable to Hobby Electronics Book Service (in Sterling only please) and send to:

Hobby Electronics Book Service, Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE.

EDUKIT

BUILD AND PROGRAM YOUR OWN MICROCOMPUTER

NO PREVIOUS EXPERIENCE NECESSARY

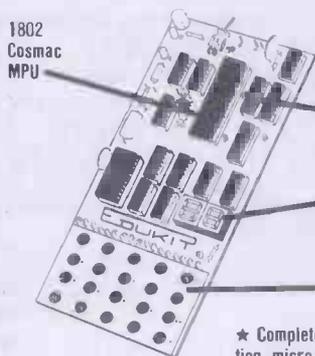

**£29.95 + VAT + 80p P&P
(= £35.24)**

★ Complete with detailed 38-page manual on construction, micro-theory and machine code programming.

Dr. A. A. Berk's extensive experience of microcomputer education is packed into this budget-price machine. Get to grips with silicon-chip technology — theory and hands-on experience — from the basics up — with a real microcomputer!


Manual only £1.49 (deductable against kit order)
S.a.e. for details, or cheques/POs with orders to:

MODUS SYSTEMS LTD. DEPT. HE6
29a EASTCHEAP, LETCHWORTH, HERTS SG6 3DA
TEL: LETCHWORTH (04626) 74468

| <p>Multitesters 100,000 opv AC volts 0-5-10-50-250-1000 DC volts 0-0.5-2.5-10-50-250-1000 DC current 0-10ua-25ua-50ua-10 amp AC current 10 amp Resistance 0-20 ohms-200 ohms-5K ohms-20K ohms-50 K ohms-200 K Ohms-5 meg ohms-50 meg ohms As a transistor tester NFE 0-500 (NPN-PNP) ICD 0-5E ua (NPN-PNP) Dims 178 x 140 x 70mm</p> <p>Please add 30p PP per unit order as NT 20</p> | <p>Multitester 20,000 opv AC volts 0-10-50-100-250-500-1000 DC volts 0-0.5-5-25-125-250-500-1000 DC current 0-50 ua (5ma 250 ua) Resistance 0-3K ohms-300K ohms-3 meg ohms Decibels -20 to +63db Dims 127 x 90 x 35mm</p> <p>Please add 30p PP per unit order as NT 7</p> | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
|---|--|--------|-------------|-------------|-------|-------|----|---|----|------|-------|--|----|---|-----|----------|-------|--|----|---|----|----------|-------|--|----|---|-----|--|--|--|---|
| <p>Multitester 1,000 opv AC volts 0-15-150-500-1000 DC volts 0-15-150-500-1000 DC current 0 1 ma - 150 ma Resistance 0-25K ohms-100K ohms Dims 90 x 61 x 30mm</p> <p>Please add 30p PP per unit order as NT 2</p> | <p>Headphones High velocity mylar diaphragms Coiled lead Finished in a combination of bright aluminium Impedance 15-22000 Hz Frequency response 15-22000 Hz Weight 350 gms</p> <p>Please add 30p PP per unit order as PH 12</p> | | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| <p>Chassis Speakers Fane and McKenzie 12" and 15" Round</p> <table border="1"> <tr><th>Size</th><th>amp</th><th>rating</th><th>description</th><th>Fane</th><th>17.80</th></tr> <tr><td>12</td><td>8</td><td>50</td><td>Fane</td><td>27.90</td><td></td></tr> <tr><td>12</td><td>8</td><td>100</td><td>McKenzie</td><td>25.75</td><td></td></tr> <tr><td>12</td><td>8</td><td>85</td><td>McKenzie</td><td>57.75</td><td></td></tr> <tr><td>15</td><td>8</td><td>150</td><td></td><td></td><td></td></tr> </table> <p>Order as above</p> <p>All prices include VAT Please add 50p PP per unit</p> | Size | amp | rating | description | Fane | 17.80 | 12 | 8 | 50 | Fane | 27.90 | | 12 | 8 | 100 | McKenzie | 25.75 | | 12 | 8 | 85 | McKenzie | 57.75 | | 15 | 8 | 150 | | | | <p>Motorola Piezo Ceramic Tweeters For use on 100W Disco System — And needs no X-over Please add 30p PP per unit order as PZ</p> <p>Please add 30p PP per unit order as PZ</p> |
| Size | amp | rating | description | Fane | 17.80 | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 12 | 8 | 50 | Fane | 27.90 | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 12 | 8 | 100 | McKenzie | 25.75 | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 12 | 8 | 85 | McKenzie | 57.75 | | | | | | | | | | | | | | | | | | | | | | | | | | | |
| 15 | 8 | 150 | | | | | | | | | | | | | | | | | | | | | | | | | | | | | |

ARROW AUDIO CENTRE (MAIL ORDER DEPT.)
20 NORTH BAR, BANBURY, OXON. OX160TF
TELEPHONE BANBURY (0295) 3677
TERMS: CHEQUE/PO WITH ORDER. CALLERS WELCOME

Clever Dick

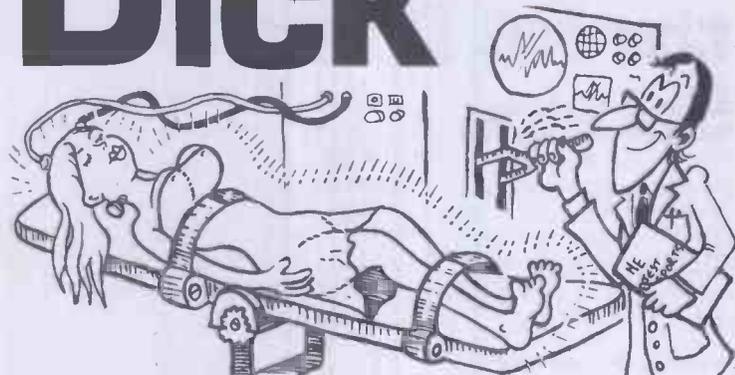

This month we help out an amateur astronomer 'get his ears on' and the mystery of the old HE projects is solved.

OKAY, pay attention now, it's CD time again. Frank Pressdee wins this month's HE Binder for possibly the worst collection of puns ever to elicit a groan, here goes.

Dear CD,

On a musical note, how about featuring a constructional project for a Chorus Generator in a future issue of HE. In the shops these units sound expensive, to the tune of £100.

Surely your technical boys can band together to compose a circuit for such an instrument. This, I'm sure generate a chorus of applause from us electronic music enthusiasts.

Frank Pressdee
Wednesbury

Circuits on that scale are enough to make most designers quaver in their boots. Luckily our sister magazine ETI is not afraid of such enterprises. They have managed to get that Baron of the Breadboard, Mr Tim Orr, to design a Chorus Machine for them. Part one was in last months (May) ETI. You'll need plenty of dough (Do ray me, oh forget it), you may have to sell your car (Allegro?) to pay for it though.

The silly season is here again. Mr R Robots peculiar reading habits are matched only by his dubious name and place of residence.

Dear Clever Dick,

Re. your interesting comments on Negative Ions, may I bring your attention to a most informative article by Adrian Hope in the March edition of Ev'ry'ay E*ec*ro'i's.

Reg Robot
Electroville

No you may not!

Dear Dick,

As the Government is going to abandon we lowly folk in a nuclear war (except for a few pistol-packing guys in command posts) I ask that you publish a circuit for a Geiger Counter for the few that emerge from holes. It would be a good idea so that we can know exactly what will be safe to eat and drink, not being contaminated by fallout.

One last suggestion, how about a circuit I saw some years ago, when a steady, low heat was applied to this device it produced a low voltage, enough to work a

pocket radio. I believe it was made from two different metals.

F G Wagstaff
Somerset

Yes, we have got plans for a pocket radiation monitor, for the October issue in fact. Hopefully we can get it into print before it is too late. Superpowers please note, don't do anything until October.

Your second enquiry refers to the Thermocouple, it is a very simple device, composed, as your suggest, from two dissimilar metals. According to the HE reference books the simplest type of thermocouple consists of a junction of two metals (Platinum and Rhodium are supposedly quite good) connected in series to another junction, one should be hot, the other cold. Under these conditions a small (around 6-10 uV at 0° and 100°C) voltage will flow. The low voltage and expensive materials may explain why we don't hear too much about them.

Mr J F Button has a few questions concerning our projects, like the flies in winter, where do they go?

Dear Dick,

I have several queries:

- (1) Please tell me where you buy the transfers that you use for decorating the projects since you have so many different types?
- (2) What happens to the projects which have no practical use in the office, eg; Dice, LED Displays etc?
- (3) Who pays for the components used in projects?
- (4) Where did you buy the 2% tolerance resistors used in the DFM project (April HE)?

Congratulations on the excellent magazines — HE & ETI — keep up the good work.
Winchester

J F Button

There is nothing mysterious about our panel lettering, we use either Letraset, Mecanorma or Chartpak rub-down transfers. There are something like 2000 different typefaces to choose from and most, if not all are available from artists supply shops, many are to be found near universities or colleges. The only problem from your point of view is expense, because we buy (and use) in quantity it doesn't cost us as much, maybe you could get a few mates together and buy a selection.

Despite what many people think we keep all our projects in working order, this is simply because we like to put them on our stands at exhibitions etc for people, like yourself, who want to play with them, or simply see

how we did it. By the way, just to dispel another rumour, 99% of all our projects are designed and built by our own workshop team and they all work (the projects that is), errors usually creep in when we publish them, although our record for mistakes isn't as bad as some magazines we could mention.

Your third question is easy to answer, you the readers pay for our projects, by buying HE you pay for our wages, offices etc, it's just like any other business, thanks from all of us. If a few more of you buy HE then we can put in for a wage rise, how about it?

Your last question is also easy, because many of you do not live near a components shop we try to ensure that all of the components we specify are obtainable by mail order. The 2% tolerance resistors you mention are readily available from Maplin, Watford, etc.

Mr R H. Durn from West Yorkshire wants to go star gazing, electronically of course.

Dear Dick,

Several years ago I took up astronomy as a hobby and now I am a very keen amateur. Anyhow, a few months ago I came up with the idea of building a small radio telescope. Since I hardly know anything about electronics I was wondering if you could give me any information on the subject.

*R H Durn
W. Yorkshire*

This is not a subject we know too much about either, however, our resident sky watcher Peter Green has dug down into his library and come up with a couple of titles that may be of use to you.

Radio Astronomy For The Amateur by David Heiserman. Published by W Fousham & Co, price £4.35.

Introduction To Radio Astronomy by John Potter Shields.

Both these books have details, circuits etc for constructing Radio Telescopes, the first one by David Heiserman is probably better for the beginner.

Martyn Daniels has been having some problems with his right foot, faster than a traffic warden booking a Rolls Royce-HE to the rescue (well, almost).

Dear Dick

I have two endorsements on my driving licence and would loose my job if I lost my licence. So; how about a circuit for a Radar Speed trap detector. If you can't supply constructional details, who can?

*Martyn Daniels
Worcester*

Unfortunately Martyn Radar detectors bring us into the nether-world of the 1949 Wireless Telegraphy Act. It appears that the equipment you desire can be brought and sold quite legally but may not be used because it receives on a restricted band of frequencies. The circuit itself is a bit out of our scope anyway because it operates in the radio spectrum where frequency is measured in Gigo Hertz (10⁹) Hz. Not only that we have heard that many so-called detectors do respond to Police radar but only when you've been through the beam making their worth somewhat suspect. If you still want to get involved we suggest you look at a commercial unit but remember do not switch it on otherwise you'll be breaking the law. (Luckily it's not endorsable though.) NIC at 61 Broad Lane, Tottenham has one for £21.95. **HE**

MITRAD

COMPLETE PRICE BREAKTHROUGH

GENTS DIGITAL ANALOGUE CHRONOGRAPH

ONLY £29.95 + P/P

Just look at this outstanding watch:

i) 6 functions (hours, mins, secs, month, date, week-day); ii) chronograph resolution; iii) automatic 4-year guarantee; iv) five buttons control all functions; v) back-light available.



The above watch is a new style digital analogue featuring complete up-to-date modern technology. The watch basically constitutes a traditional hand watch plus a modern digital watch, both battery powered.

Hours, mins and seconds are on constant display and with the press of a button, month, date and weekday is displayed.

This unique timepiece also has a chronograph built in which runs to a 1/100th sec, and has a 12-hour capacity. Features include: i) the chronograph can be frozen; ii) two people can be timed simultaneously, and iii) split and lap mode facilities are available.

The watch is finished off with an elegant infinite adjustable stainless steel strap.

**ORDER NOW TO AVOID
DISAPPOINTMENT !!!**

! MITRAD !

THE UNRIVALLED RANGE

! MITRAD !

MITRAD (MIDLAND TRADING COMPANY)

ZETRON

BRITAIN'S FINEST SELLING RANGE

ZETRON

GENTS MEMORY CALENDAR ALARM CHRONO



A really successful watch incorporating all the latest technology.

Hours, mins, secs, weekday and snooze alarm indication on constant display.

A further two optional display modes are available, one being the calendar and month, which can be increased or decreased to give the appropriate month of the year.

A 1/106th second chronograph with split and lap mode facilities are built into the watch with a 12-hour capacity.

A 21-hour alarm with a 10-minute snooze function is also standard to this watch. A further feature is the backlight and fully adjustable stainless steel bracelet.

★
STAR VALUE
£19.95

GENTS QUARTZ ANALOGUE

A truly superb timepiece with extreme accuracy. A choice of two colours on this outstanding watch are available, blue or white.

The calendar in the watch can be set to give a readout in either French or English with date indication being automatic.

An infinitely adjustable stainless steel strap is built in as part of the watch.

The watch is fitted with a long-life battery and comes with luminous markings to aid night-time vision.



YES ONLY £19.95

NEW ZETRON L.C.D. CALCULATOR

Superb value in the economy range of LCD calculators. What more could you ask for? This marvel of the silicon chip era boasts the following:

Four basic functions, chain and mixed operations, constants for four functions, % calculations including discounts and mark-ups. Automatic accumulation in four functions.

★PLUS★

Square Root facility

★PLUS★

Memory facility

★PLUS★

Auto Power Off

(7 minutes)

ALL THIS FOR A

MODEST £4.95



GENTS MELODY ALARM CHRONO DUAL TIME

Brand new Melody Alarm, Chrono. Constant display of hours, mins, secs, weekday, am/pm and mode square flag indication.

The chrono runs to a 1/10th sec (running horse style) split and lap mode facilities are standard. Dual timing facilities. The alarm system is unique in the fact that it plays the tune "Yellow Rose Of Texas" for 20 seconds.

The tune can be actuated at any instance by the press of a button. Backlight, infinitely adjustable stainless steel strap.

VERY LOWLY PRICED

£17.75



NEW QUARTZ L.C.D. TIMER

A new style timer incorporating split second accuracy. The timer is finished in a strong black plastic case with large L.C.D. readout of hours, mins and secs. A further optional display mode of month, date and weekday is available. The timer incorporates a 1/100th sec chronograph with numerous facilities.

(i) The timer can be frozen.

(ii) Two people can be timed simultaneously.

(iii) Split and lap mode facilities are available. A strong black cord is attached to the timer which aids movement at sporting events.



Battery replacement is made easy with a screw back.

OFFERED AT ONLY £19.95

ZETRON

WHERE RELIABILITY, STYLE AND ELEGANCE REALLY COUNT

ZETRON

We are able yet again to offer you the above watches plus a complete quartz watch range. All at unrivalled prices. Just look at the following points:

- (i) 48-hour despatch guaranteed on both retail and trade orders.
- (ii) Full instructions and 12 month manufacturers guarantee.
- (iii) Our own free back-up service.
- (iv) 10-day full money refund if not completely satisfied.
- (v) Free felt presentation case with each watch.

**M
I
T
R
A
D**

Phone or write for free full comprehensive catalogue on the complete range of watches we offer. Large discounts available for bulk buyers. Trade lists on application. Agents wanted everywhere. P/P per item 85p which includes insurance. Cheques or PO's made payable to **MITRAD** and sent to **(Dept. HE), 58 Windmill Ave, Kettering, Northants NN16 8PA. (0536) 522024.**

CB ANTENNAS AND ACCESSORIES

HAPPY ANNIVERSARY TO THE BREAKER ONE FOUR COLUMN AND ALL THE STAFF AT 'HOBBY ELECTRONICS' FROM THE STAFF AT WINTJOY, OUR RETAIL OUTLETS IN THE UK AND FROM OUR SUPPLIERS, SOME OF WHOM ARE LISTED BELOW.



Citizen Band Fibreglass Antennas and Accessories for Marine, RV, Truck, Auto, Van and Motorcycle.

Watch for the new film
"SMOKEY AND THE BANDIT II"
starring **BURT REYNOLDS** and
'Firestik' ANTENNAS!

Shakespeare [®] **CB MOBILE ANTENNA SERIES**
and the Shakespeare fibreglass Super
Big Stick™ base station antenna



SWR METERS, NOISE SUPPRESSION FILTERS, T.V.I. FILTERS, CO-PHASORS, ANTENNAS, LEADS AND NUMEROUS OTHER ACCESSORIES.



Microphones, Power Supplies, SWR Meters, Linear Amplifiers, Preamplifiers, Antennas, Frequency Counters etc., etc.

TELEX [®] **MICROPHONES AND HEADSETS**

TURNER [®] **ANTENNAS AND MICROPHONES**

hy-gain [®] **CB MOBILE AND BASE STATION ANTENNAS**

K40 **SPEECH PROCESSORS AND BASE LOAD ANTENNAS**

WE ARE UK DISTRIBUTORS FOR THE MANUFACTURERS LISTED ABOVE AS WELL AS MANY OTHER COMPANIES. WE BUY DIRECT FROM THEM WITHOUT ANY MIDDLEMEN SO THE PRICES WE CAN OFFER ON THEIR PRODUCTS ARE SOME OF THE BEST IN THE COUNTRY AND THEIR RANGE IS VAST. COME AND SEE US IT MAKES SENSE!

★★ SEND £1 FOR A COMPREHENSIVE CATALOGUE ★★

WINTJOY
Ltd.

*103 High Street, Shepperton,
Middlesex TW17 9BL, England.*


*Tel:
Walton-on-Thames (STD 09322) 48145*

COMMUNICATIONS EQUIPMENT DISTRIBUTORS

UK RETAIL OUTLETS IN SELECTED
AREAS STILL BEING SOUGHT

★★ UNTIL RIGS BECOME LEGAL
WE ARE UNABLE TO SUPPLY
THEM ★★

Citizens Banned II

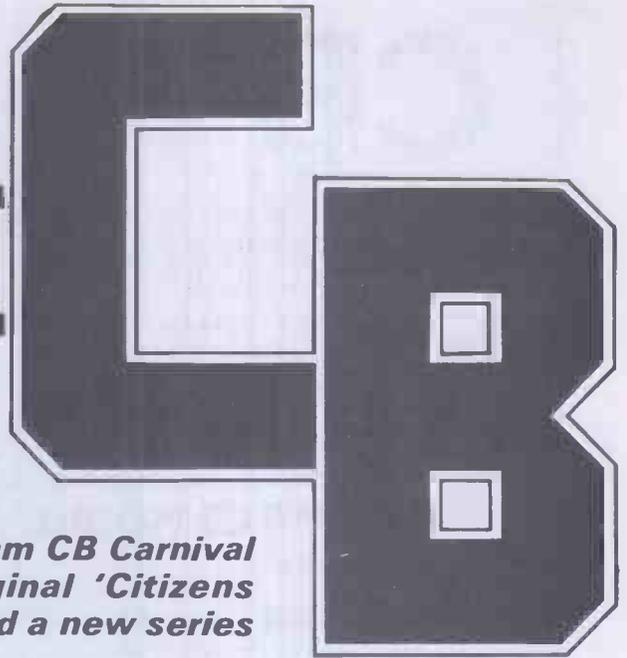

HE's CB Editor Rick Maybury was invited along to the NATCOLCIBAR Technical Committee. We have a picture report on the latest demonstration, news of the Birmingham CB Carnival and another petition. In place of the original 'Citizens Banned' article we have a Club Directory and a new series about CB personalities.

ORIGINALLY I intended that this month's episode of Breaker One Four would have been a backward glance of the year's events since HE first became involved with CB. Fate, in the shape of events beyond our control deemed it necessary that this issue goes to press one week later than scheduled. That one week was probably the most important week in the history of British CB, three major events and at least six regional demonstrations over the weekend of the 26th 27th April made a golden opportunity we couldn't afford to miss.

So, instead of the intended feature Citizens Banned II we now present an extended version of BOF to cover these events. However, the latest Club Directory and a new feature, CBVIP, are included this month, but now to the first of these events.

NATCOLCIBAR

Or, to everyone else, the National Committee for the Legalisation of Citizens Band Radio. On the 25th April I was invited to attend the Technical Sub-Committee of NATCOLCIBAR at County Hall London.

The Committee was chaired most decisively by Richard Town and ably assisted by James Bryant and Bernie Murray, representatives from VERY large UK electronics companies and a couple of not so English companies were also to be seen. Not so obvious were the members of one or two monthly magazines also with an interest in CB. I am sworn to secrecy over specific details but I'm pretty sure they'll be sick when they discover what they missed. Suffice it to say that the proposals NATCOLCIBAR will ultimately present to the Home Office may contain some interesting reading.

The second outcome of this meeting can be seen on page 30. In conjunction with NATCOLCIBAR we are publishing this petition. As you can see it is short and to the point, you will have no excuse if you ignore this one because TANDY have offered to accept these forms in any of their shops on NATCOLCIBAR's behalf. You can if

you wish return them to us at our usual address. In either case they must be returned by the 30th June to be handed over at the next major CB demo on the 6th July in Trafalgar Square. More forms are available either from the GLC or TANDY shops nationwide.

LONDON DEMO AND BIRMINGHAM CARNIVAL

The other main events of the CB Weekend were the series of regional demonstrations and the first ever CB Carnival in Perry Park Birmingham.

As we are somewhat limited, in that we can only be in one place at a time we covered the London Demo and the Carnival.

In terms of numbers both were slightly disappointing, conservative estimates in London put the figure at the London Demo at around the 500 mark. That wasn't really as many as we had hoped for but not bad considering the distinct lack of coverage given to the event by the press. Please take note now that the Demo for the 6th of July will be held in Trafalgar Square, London. Please turn up if you want CB because it's no good the same old faces turning up time after time. If you want CB then do something about it.

CB CARNIVAL


Again, the turnout was lower than we had hoped for but this could have been due to the lack of publicity. We got the location wrong in last month's BOF but that was due to circumstances beyond our control. Even so, around 1 000 of you thought it worthwhile, we were there dishing out balloons and mags, so were a sizeable selection of local Hot Rods and by all accounts a good day was had by all. Keith Townsend assures us that the next Carnival to be held in the Summer will get much more advance publicity, news of that, hopefully next month.



Bernie Murray proudly displays his UKCBC Tee-Shirt.



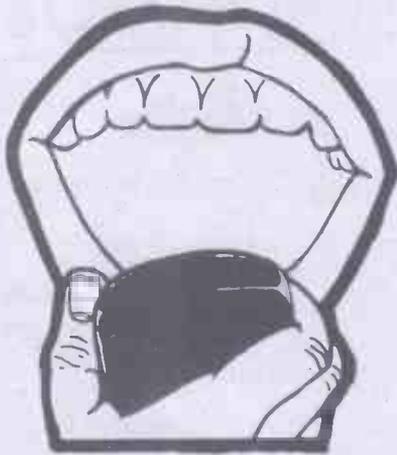Councillor Theo Yard addressing the crowd just before the march commenced.



CB Equipment Specialists

the U.K's leading CB equipment supplier..!

All types of antennae — disguise, tri-band, DV27, DX27, B27, T27, dipoles, twins — every possible type/position of mount. We're approved distributors for antenna specialists. We also sell burners (50-1000 watts), pre-amps, SWR meters, mikes, test equipment, suppression gear, plus, connectors, books, etc. In fact, anything to do with CB EXCEPT RIGS. Special pledge — we will match or beat any genuine price anywhere in the UK.

Mail order expressed by Red Star, all goods returnable if not satisfied.

Phone your requirements, quoting your Access or Barclaycard number for immediate despatch. We'll help with any problems, by phone if at all possible.

SCOTTISH AGENTS:
Victor Morris (Audio Visual) Ltd.
340 Argyle Street, Glasgow
Tel: 041-221 8958

10-21 breakers

Woking(04862) 67944 Mon-Sat.



The procession leaving Speakers' Corner



UBA members 'pushing' for 27MHz



The procession in Trafalgar Square. How about an aerial up there lads?

'Firestik' ANTENNAS

REBEL 500 £10.95

MODEL KW2 £14.40
2' 5/8 + wave 3dB gain. Fire-power rating — 100AM watts, 200 SSB.

MODEL KW3 £15.55
3' 5/8 + wave 6dB gain. Fire-power rating — 300AM watts, 600 SSB.

MODEL KW4 £16.70
4' 5/8 + wave 6dB gain. Fire-power rating — 400AM watts, 800 SSB.

MODEL KW5 £17.55
5' 5/8 + wave 6dB gain. Fire-power rating — 500AM watts, 1000 SSB.

MODEL KW7 £20.15
7' 3/4 + wave 6dB gain. Fire-power rating — 700AM watts, 1400 SSB. + Base/Cable.

● 27MHz = 120 Channel Plus Tunable to 10 Meters.

UNTIL C.B. IS LEGALISED WE DO NOT SUPPLY RIGS.


Shakespeare

We stock a very large selection of CB Accessories. If what you require is not in stock we will gladly order.

- DV27
- DX27
- 5/8 HELICAL WHIPS
- FULLY DISGUISED ANTENNAE
- BASE STATION ANTENNAE
- STARDUSTER ETC.
- SWR METERS
- POWER METERS
- POWER SUPPLIES
- SLIDE MOUNTS
- SUPPRESSION KITS
- MAGIC MIKES
- POWER MIKES
- ANTENNAE MATCHERS
- SPLITTER BOXES

● C.B. Books
Big Dummy's Guide
CB Lingo Bible
In Fact You Name It!!

SRU AUTOS

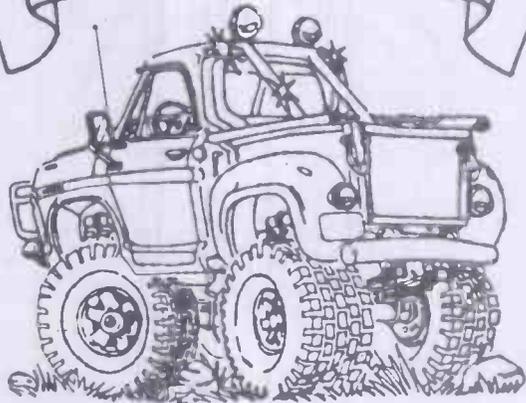

Citizen Band, Antennas and Accessories for Marine, RV, Truck, Auto, Van Motorcycles . . . Mobile and Indoor / Outdoor Base Applications
10-4 Good Buddies

**Come to us for your
Car Spares — Accessories — Customizing Equipment**

**TEL: CHERTSEY (STD 09328) 62556
229 CHERTSEY ROAD
ADDLESTONE, SURREY**

NEWS FROM THE STATES

Now back to business, we have received an unusually large post bag this month, first away is Jim Roths from Hy Gain Electronics over there in Nebraska (that's America dummy). He would like to point out that we had prematurely reported the demise of Hy-Gain in the February BOF. In fact Hy-Gain are alive and well and although they no longer produce rigs they are producing an immense range of antenna systems for just about anybody that wants one. Jim was good enough to send us their latest catalogue, take it from us that should you need wide band VHF log periodic Antenna for 30 to 76 MHz, a 50-foot crank up tower and a trailer to move it round on then they can help you. Wonder how long it would take the HO to figure that one out!

Still in the 'States Mr S. C. Rimple of the Transworld Trading Corp, Dallas, Texas, writes to us to thank us for the mention of Magic Mike. If you can remember back to February (again) we said that Big Glynn Hall at Wintjoy had them in stock. Well, Mr Rimple would like to draw your attention to his latest model which will enable you to get prosecuted twice over for illegal transmissions. (27MHz and 49MHz, the operating frequency of this cordless mike). Oh well, thanks anyway Mr Rimpel.

Last but not least comes a press release from the famous Firestik antenna company of Phoenix Arizona who have also seen HE. (See, even American CBers read HE), they would like you to see the film 'Smokey And The Bandit' which although we haven't seen yet (how about some tickets whoever made it?) has a lot of CB action in it and makes good use of Firestik antennas particularly on Mr Burt Reynolds car.

BACK HOME

Back to good old CBless Britain now. As you may have noticed last month's HE was a little late due to industrial action. This meant that we could not get cracking with our National Directory of Handles. Fear not though, already we have something like 4,500 names and because of the immense popularity we are holding publications over one more month. There is still time to register your handle and get yourself a genuine callsign but hurry.

The C-Beastie this month is dedicated to David Carman who phoned us up a couple of weeks ago sounding most disturbed over their absence during the past couple of months, hope we've made up for it now Dave.

CB CELLARS

So many companies seem to be selling CB equipment these days that we've decided to give them their own column. With a little luck BOF will be getting out and about a bit more now so we can report on how things are going.

Last month we went along to Mura Electronics to meet Elliot Kahan, David Gross and Ged Crow. This villainous trio have a very good range of bits and pieces on offer and have something like 40 different antennas in stock. Best of the bunch was a really professional looking device called the GP227. This "living room" aerial slotted together to make an eighth wave aerial with tri-lobal ground planes, it looks a little like a hat stand. Although they usually stock a range of "Tweety Boxes" they had an interesting little device called the "Lazar" which made a fair impression of Star Wars

sound effects for only £19.95. Mura have offered to give a 10% discount on any of their wares if you take the ad in this issue along to their shop, it's well worth a look round.

Incidentally, Mura are planning to open the first CB shop in the West End of London, just down the road from our offices in Tottenham Court Road at the end of May.



A corner in 'Mura's' shop, some of the items in the show case are very interesting indeed!

If you want to get CB accessories on a Sunday then you could do worse than pay SRU Autos down in Addlestone (near Chertsey) a visit. Besides a very complete range of CB odds and ends, antennas (Firestiks a speciality) you can drool over the customising goodies that they can sell you for your wheels. They can be found at 229 Chertsey Road, Addlestone in Surrey.

CBVIP

Starting this month BOF has a new feature, CBVIP. For the next few issues we will give 'carte blanche' to people, who, have over the last year or so made some contribution to legalisation.

We start straight away with two personalities, both of whom you should know very well. Firstly the 'daddy of them all', James Bryant, President of the CBA and CB Campaigner for more years than we care to remember. Sorry we couldn't get a picture of James in time.

Our second contribution comes from someone, who, whilst extremely active in campaigning for CB has preferred to avoid the limelight, for obvious reasons.



'Mack The Hack' has again put pen to paper in his own unique style. For those curious to know what Mack looks like we have a picture taken a few years ago to protect his anonymity.

THE NEWS

"Ayotollah bites dog", "Mad Pope slays seven", "Mr. Carter kicks ambassador", "Mrs Thatcher and ministers continue to discuss Citizen's Band". Given the media's fondness for the sensational which of the above headlines are we least likely to see? Right — but it's the only one that's true.

"No news is good news" is not the proverb to quote to the breaker. Members of the National Committee are contacted several dozen times per week by frustrated breakers and clubs who have heard nothing of CB in the media but news of the occasional bust (not page 3 of the Sun, idiot, the other sort). These people, understandably, are often extremely frustrated by the apparent lack of any progress towards legal CB and sometimes even want us to take drastic, if not violent, action to promote the course.

In fact there has been a great deal of progress. It's just that the press prefer to report strikes, slayings and sex rather than steady democratic progress towards a worthwhile objective. The first three sell more newspapers!

As you will know there has been progress. It is likely that the Government will legalise CB — but not on 27MHz — before the end of the year. This will only happen if the pressure is kept up. If we sit back and wait for it to happen — it won't.

So it is even more important than ever to write letters and postcards and keep the petitions coming in. Every CB supporter should write to Mr. T. Raison at least once a month, whether he answers or not, and should also write frequently to Mr. W. Whitelaw and Mrs. Thatcher. These letters should be sent to the House of Commons, London SW1A 0AA — the campaign to send postcards to Mr. Raison's home is now over as the postman, the dustmen, and Mrs. Raison were beginning to complain.

I cannot emphasise too strongly that although we are near to success continued pressure is essential. The best methods are not dramatic but tedious — keep writing. Demonstrations are important to keep CB in the public mind but the steady "plop-plop-plop" of letters falling on Tim Raison's doormat (in the House of Commons please) is what will win us the day. Many people will not write for fear of being busted or appearing on some Government list of "troublemakers". This is not Moscow — writing to the Government is what wins here — and the NCLCB have NEVER heard of anyone being busted because he wrote to an MP. So write-write-write.

James M. Bryant,
National Committee for the Legalisation of CB Radio,
President, Citizen's Band Association.



Mack The Hack with his 'Ears On' at a very early age. **Actually he hasn't changed much!**

Many happy returns of the birthday of BOF. So what has happened on the CB scene since Hobby Electronics gave birth to BOF 12 months ago?

Well, we all know that we do not have legalisation — yet. But each morning I scan my newspapers hoping that I can read some item that reports a date for legalisation. Although I feel sure I would know before the press as I constantly have my ears glued to the box, and what better

way to hear what's happening in our CB world.

A year ago it was as difficult to purchase a CB antenna as was a rig, but nowadays... Well, just look at the adverts in HE. Is it so difficult to obtain rigs now? Of course not. I'm not allowed to say how one can obtain them but read on, Nudge nudge, wink wink.

A few months ago, rigs that were obtainable were mostly excess and, secondhand equipment from the U.S.A. There were plenty of 23 channel rigs and the 40 channel ones were rather bulky but still expensive. If one was to poke one's nose into the works you would find that the technology was a few years old.

Now, I have seen rigs with autoscan, memory, and they use the latest IC's. As for size, I recently saw a 40 channel 4 watt mobile rig that will fit into your pocket. Even antennas have changed. 12 months ago a DV 27 was thought to be the 'non sus' or disguise type. I am sorry if I am insulting anyone, but you must be loony if you use one today. Some current antennas are very difficult to discriminate between CB or normal mobile radio types. I used to enjoy a little game, spotting the CB antenna and shouting at the buddy "What's your handle".

Eyeball 20s a year ago were close-kept secrets. They were mostly drinking 20s where breakers would congregate for a natter, conduct deals for gear, and of course a drink or two. If ever the 20 got mentioned over the channels then they were changed instantly. Nowadays the eyeball 20s, clubs, call them what you will, are openly published. Again just read the pages of BOF. The activities of the breakers at these 20s are the same. I recall that last year (and earlier) if you wanted an eyeball with a breaker for a deal or whatever, it would be a question of what other breakers you knew. "Do you know Billy the Kid's landline?" The other breaker would come back with "That's a 4." "Well Billy the Kid will give you my landline" and that was how it was done. Then there was the phone box trick. If you were confident that the other breaker was safe you would both find a phone box that worked of course. Then over a channel one would give the number of the phone box and the first breaker would ring the number and give either your base 20 or base landline and then just in case, a prompt departure was made.

So what have I been up to in the last year? I want to see legal CB in this country, and because of this, I've sipped brandy and tea with MPs, written letters and sent postcards to others. I have managed to have my say on radio 'phone-ins'. I have signed, and collected other signatures for petitions. I have also attended demos and meetings. Some of my good buddies and I were persuaded to study for the RAE. I took the exam in December but I failed, so I shall try again in May. One reason why I started this may have been something to do with waiting for the legalisation of CB. Don't let anyone kid you that the study and exam is easy.

One day the Breaker Takers might get me and snatch my rig. It may cost me a few Green Shield stamps for a fine, but I know they can never take the friendship of the good buddies that I have made whilst involved in the CB scene.

By the time of BOF's next birthday we should have legalisation. If for some silly reason we have not, I believe that this country will have a very successful illegal system. We already have in 'Smoky Town' 'News on Ten' (on channel 10). Many breakers have their ears glued to the box listening for 10-33s. I have heard a rumour (here we go again) that the authorities intend to put a carrier over on 27MHz. I don't know how they can do this without causing interference to other so called users of 27. Can they? What could or would we do then? 2 metres perhaps?

As my 10-10 I would like to quote a sticker I saw on a mobile recently. 'After sex I love my CB radio best' Now that's a big 10-4.

Mack the Hack
London.

C-Beasties



CLUB DIRECTORY

ANGLIA BREAKERS CLUB

c/o Great White Horse Hotel,
Tavern Street,
Ipswich,
Suffolk.

BREAKER ONE FOUR CLUB

Secretary: O K Corral
Napier Barracks, BFPO 20

CBA SCOTTISH REGION

Ron Warbrick,
10, Manse Road,
Stone House,
Lanarkshire.

THE CITIZENS BAND ASSOCIATION (CBA)

President: James Bryant.
16 Church Road, St Marks Road,
Cheltenham, Glos G151.

CBA SW,

Chairman: D. J. Bennet,
7, Wookey Hole Road,
Wells,
Somerset.

CBCB CLUB

Chairman: A. Scott Foster,
103, Southwood Road,
Downside,
Dunstable,
Beds.

CB-NE

Chairman: Ian Morrison
PO Box 61, Sunderland,
Tyne and Wear, SR3 1EZ

CITIZENS BAND RADIO ACTION GROUP

Chairman: Steve James
55 Dartmouth Road, Forest Hill SE23

DON VALLEY BREAKERS

282, Eccleshall Road,
Sheffield S11 8PE.

GBA

Chairman: Bob,
Coronation Service Station,
Middleton Road,
Heywood,
Lancs.

GLASGOW CB CLUB. (CBA)

Chairman: Normund Cram
3 Erskine Road, Whitecraigs,
Glasgow G46 6TQ

HARROW AND WEMBLEY CITIZENS BAND GROUP

Secretary: Bill Ridgeway
7 Sandringham Crescent, Harrow,
Middlesex HA2 9BW

LAGAN VALLEY CB CLUB

Poste Restante,
Gpo,
Lisburn,
N. Ireland

LEICESTERSHIRE CB'ers

Chairman: Crapshooter
c/o Modern Motoring Ltd.
68 Narborough Rd
Leicester LE3 0BR

THE MIDLANDS CITIZENS BAND RADIO CLUB (MCBRC)

Chairman: Keith Townsend
1163 Yardley Wood Road,
Birmingham B14 4LE

PRESTON CB CLUB

Chairman: F. W. McKeown,
29 Russell Avenue,
Preston,
Lancs.

STEEL CITY CB CLUB

Chairman: Alan Taylor
SSCBC PO Box 123, Reading

UNITED BREAKERS ASSOCIATION (UBA)

Chairman: Andy Donovan
50 Gaskell Street, Clapham SW4

UBA (ESSEX)

Chairman: Ted Cheneler
24 Bryony Close, Witham, Essex

UBA (NE)

Chairman: B. D. Low
53 Mayfield Avenue,
Lancaster

UNITED KINGDOM CITIZENS BAND CAMPAIGN

Chairman: Bernie Murray,
32 Downbank Avenue,
Barnehurst, Kent DA7 6RP.

THE WEYMOUTH CB CLUB

Chairman: Ray Howes
39 St Thomas Street, Flat 1,
Weymouth, Dorset

CB RADIO ACCESSORIES

The Largest distributors of CB accessories in the UK.

**SHOP
NOW
OPEN**

Come and see the biggest and best selection of CB radio

accessories including:-

**SWR METERS
including HANSEN**



**MICROPHONES by
TURNER-K40
G.C. ELECTRONICS**

**SUPPRESSION EQUIPMENT
PLUS MUCH MUCH MORE**

**ANTENNAS
by
HY-GAIN
SIRTEL
A.S.
HMP**



10% discount on presentation of this ad

Mura
Mura Electronics (UK) Ltd.

Blackpool: A.D.S. Electronics, 16 Warbeck Drive (Nth. Shore) Blackpool. Tel. 02353 57222/0263 21173; Edinburgh: Custom Equip., 131 Fountain Bridge, Edinburgh EH3. Tel. 031-229 9830; Stoke-on-Trent: HSEB, 27 Hope Street, Hanley, Stoke-on-Trent. Tel. 0782 273815; Wigan: Car Radio Wigan, 80 Darlington Street East, Wigan, Lancs. Tel. 0942 43101.

79 Church Road, Hendon, London NW4
Tel: 01 203 527718

THE #1 WIRE WOUND
AND MOST COPIED
ANTENNA IN THE WORLD!

**'Firestik'[®]
ANTENNAS**

**CITIZEN BAND
FIBREGLASS ANTENNAS
AND ACCESSORIES.**

Call or write for full information

WINTJOY LTD.

103 HIGH STREET, SHEPPERTON
MIDDX. TW17 9BL
Tel. Walton-on-Thames (STD
09322) 48145

ARE YOU INTO THE C.B. SCENE?

If so, a 9" x 4" s.a.e. will bring you free details of our carefully selected range of C.B. Accessories.

MAIL-ORDER ONLY

Post today to:

POLAR ENTERPRISES
2 SWORDS HOUSE
HIGH STREET
CROWTHORNE, BERKSHIRE
Tel. 03446-71714
(24-hr. Answering Service)

REMEMBER! UNTIL CB BECOMES LEGAL
WE DO NOT SELL RIGS

PETITION For Citizens Band Radio

Wherefore your Petitioners pray that the House Of Commons do introduce a Bill
To establish Citizens Band Radio in the United Kingdom.
And your Petitioners, as in duty bound, will ever pray, etc.

Please note

Please return to any branch
of TANDY UK Ltd

| Signature | Address |
|-----------|---------|
| 1 | |
| 2 | |
| 3 | |
| 4 | |
| 5 | |
| 6 | |
| 7 | |
| 8 | |
| 9 | |
| 10 | |
| 11 | |
| 12 | |
| 13 | |
| 14 | |
| 15 | |
| 16 | |
| 17 | |
| 18 | |
| 19 | |
| 20 | |

C.B. SCOTLAND

Scotland's first suppliers of C.B.
Accessories bring you: —

Aerials

Meters

In fact you name it

We stock it

But sorry, no rigs
Smokey Bear says negatory

VICTOR MORRIS

(Audio Visual) Ltd
340 Argyle St
Glasgow
041-221 8958

That's a big 10-4

C.B - C.B - C.B

AERIALS AND ACCESSORIES

| | |
|-----------------------------|--------|
| Cutter mount | £15.95 |
| Boot/Roof/Wing mount | £19.95 |
| Traditional Fibreglass Whip | £14.95 |
| AM/FM/CB Retractable | £25.95 |
| CB Electric Retractable | £29.95 |
| AM/FM/CB Electric Ret | £39.90 |
| Roof mount 20" Glass Whip | £19.95 |
| SWR/Power/F.S. Meter | £24.95 |
| SWR/Power Meter | £12.95 |
| Pre-Amp 20db gain | £19.95 |
| Splitter Box | £9.95 |
| Linear Amps from | £59.95 |
| 27 MHz Monitor + AM/FM | £18.65 |

These are a few of the items available

The latest from the U.S.A. PINBALL WIZARD

Still available
Featured in Nov. issue of E.T.I.
Home TV Game — B/W Kit

Basic Kit **£28.90**

Contains everything except box and controls
Box & Controls **£6.50**, P.S.U. **£3.90**
CEH Car Alarm Kit **£18.90**
Chroma Chime 24 tune door chimes kit **£10.75**, Built **£15.95**
SINCLAIR SC110 10MHz scope **£145.25**
PFM 200 Digital Frequency Meter **£52.00**
3" 5 MHz Oscilloscope **£113.85**
4" 5 MHz Oscilloscope **£139.90**
5" 10 MHz Oscilloscope **£169.90**

ATARI £138

ELECTRONIC GAMES

| | |
|------------------------------|---------|
| Star Chess T/V game | £63.35 |
| Database Prog T/V game | £89.95 |
| Chess Challenger 7 | £99.00 |
| Chess Challenger 10 | £160.00 |
| Voice Challenger | £230.00 |
| Chessmate 8 level | £59.95 |
| Zodiac Astrology Computer | £29.95 |
| Electronic Mastermind | £14.90 |
| Supersonic Mastermind. New | £21.00 |
| Mattel Subchase. New | £17.90 |
| Mattel Armor Battle. New | £17.90 |
| Enterprise 4 in 1 | £22.90 |
| Galaxy Invaders. New | £22.95 |
| Radio Control Models—Various | |

COMPUTERS—HOME BUSINESS, ETC

| | |
|---------------------------------------|---------|
| Pet 8k | £550.00 |
| Pet 16K | £670.00 |
| Pet 32K | £790.00 |
| Superboard 11 4K | £172.45 |
| UK101 kit 4K | £228.85 |
| UK 101 Built 4K | £286.35 |
| Superboard/UK101 case | £33.80 |
| Nascom 2 kit | £339.25 |
| Nascom 2 built | £420.00 |
| TRS80 16K Level II | £409.40 |
| H14 line printer kit | £410.00 |
| 5 1/4" disc drive for TRS80 | £287.50 |
| Computer Books | S.a.e. |
| Software - Pet/TRS80/Superboard, etc. | |
| Exody Sororor 16/32/48K from | £860.00 |
| Renumber prog. 101 | £4.00 |

Free - Advice/Demonstrations/Coffee

S.a.e Enquiries. Please allow up to 21 days for delivery. All prices inclusive



N.I.C

61 BROAD LANE, LONDON N.15 4DJ
Day 01-808 0377; Eve 01-889 9736



LCD ANALOGUE/DIGITAL

The best of both worlds with Casio's new watch

LCD Analogue Digital

Stopwatch

Countdown

12 or 24 hour display



Time display

Time calendar

Time display. Digital: Hours, minutes, seconds, am/pm. Analogue: Seconds
Time/date display. Digital: Hours, minutes, am/pm, date. Analogue: Seconds
Time/calendar display. Digital: Month, date, day. Analogue: Hours, minutes
Stopwatch. Measuring net, lap and first & second place times from 1/10 second to 59 minutes, 59.9 seconds.
Countdown. Measuring capacity 60 minutes, in 1/10 second units. Setting to the second. Countdown can be stopped and restarted for net time measurement.
Calendar. Auto calendar set at 28 days for February.
Case: Water resistant. Mineral glass. 39.6mmx35.8mmx8.3mm.
Battery: One lithium battery type BR-2016 gives approx. 2 years operation.

56QS-50B. Stainless steel. Available now. (£39.95) **£34.95**

56QS-38B. Chrome plated. Available soon (£27.95) **£24.95**

THE EXECUTIVE WATCH

For the man who doesn't want hands on his time

Alarm/Chronograph

Hourly chimes

Push-button calendar

Full month calendar

Tone control



Time and date display. Hours, minutes, seconds, am/pm, and date.
Calendar display. Day, date, month and year.
Monthly calendar display. From the year 1901 to the year 2099.
Stopwatch. Measuring normal, net, lap and first and second place times from 1/10 second to 11 hours, 59 minutes, 59.9 seconds.
Alarm time function. Displaying hours, minutes, and am/pm. 24 hour.
Time signal function. Chiming every hour, on the hour, when selected.
Tone control system. Tone pitch can be varied in 10 steps.
Calendar: Auto calendar pre-programmed to the year 2099.
Case: Stainless steel, water resistant. Mineral glass. 39.4mmx35.7mmx8.6mm.
Battery: One lithium battery, type BR-2016, lasts approx. 15 months.

79CS-51B Executive alarm chrono (£44.95) **£39.95**

81QS-35B Alarm Chronograph

Stainless steel. Mineral glass. Water resistant. 5 YEAR BATTERY. Hours, minutes, seconds, day. And day, date, month and year. 12 or 24 hour display. 24 hour alarm, hourly chimes. Stopwatch from 1/100 second to 7 hours, net lap and 1st and 2nd place times. (£34.95) **£29.95**



NEW MODEL, 81QS-40B. As above but heavy chrome plated case. (£27.95) **£24.95**

95QS-36B Chronograph. Similar to above but with dual time (12 or 24 hr.) in lieu of alarm and chimes. Stainless steel. (£22.95) **£19.95**

95QS-42B. As above but with stainless steel jacket. (£19.95) **£17.95**



83QS-41B Alarm Chronograph

S/S encased. Mineral glass. Water resistant. 3 YEAR BATTERY. Hours, minutes, seconds, date, am/pm, or hours, minutes, alpha day, date am/pm. 24-hour alarm, hourly chimes. Stopwatch from 1-10 second to 12 hours; net lap net lap and 1st and 2nd place. Nightlight. **ONLY £24.95**

F-80. As above but with black resin case/strap with S/S back and front trim. **£19.95**

PLEASE NOTE

Casio's guarantee is only valid if goods are purchased from an authorised dealer. Authorised dealers are easily recognised because they do not advertise goods below a minimum price (our price). Casio will ONLY supply authorised dealers.

Having said that, we will always try and beat a lower advertised price providing the advertiser has stocks.

Send for our FREE LEAFLET "The whole truth about digital watches."

CALCULATORS

WITH CLOCK, ETC.
 PW-81 £14.95. AQ-1500 £14.95. MQ-6 £19.95. MQ-12 £19.95. AQ-2200 £19.95. ML-71 £22.95. ML-81 £22.95. HR-10 £29.95.

SCIENTIFICS
 With check. FX-7100 £24.95. FX-800 £24.95.
 Others: FX-81 £12.95. FX-80 £13.95. FX-100 £15.95. FX-100 £15.95. FX-330 £15.95. FX-510 £19.95. FX-3200 £21.95.
FREE MASTER PACK (RRP) £17.95
 with FX-501P + F.A.-1 or FX-502P + FA-1. FX-501P £54.95. FX-502P £74.95. FA-1 £19.95.

ILLUSTRATED CATALOGUE

Casio and Seiko products. Send 25p to: TEMPUS (Information and Service Centre), 19-21 Fitzroy Street, Cambridge CB1 1EH.

111QS-34B

Superbly finished chrome plated case, mineral glass. Water resistant. Comprehensive display, hours, minutes, seconds, am/pm, day and date. Button for nightlight. £14.95 (£17.95) F-8C Black resin cased version. **£9.95**



F-200 Sports. Now only **£12.95**

C-80 Calculator Watch

(Finger-touch keyboard). Hours, minutes, seconds, am/pm, day. Day, date, month auto calendar pre-programmed to 2009. Professional 24 hour stopwatch: net, lap, 1st & 2nd place to 1/100 sec. Dual time. 8 digit calculator. Nightlight. Water resistant. Glass. Black resin case/strap. 44.9mmx35.8x10.2mm **ONLY £24.95**



LADIES' CASIO WATCHES

10 models, from £12.95 to £44.95

RICOH WATCHES

We are now authorised agents for these HIGH QUALITY Japanese analogue and digital watches. P.O.A.

RETURN OF POST SERVICE

Postal and telephone orders received before 4.00 p.m. will normally be despatched the same day by FIRST CLASS POST.

Send your order by FREEPOST (2nd class post — no stamp required). Please phone urgent orders or use first class mail.

PRICE includes VAT, P&P. Send your Company Order, Cheque or P.O. or phone your ACCESS or B'CARD number to:

TEMPUS

Tempus (Dept. HE)
 FREEPOST, 164-167 East Road
 Cambridge CB1 1BR. Tel. 0223 312866

Metronome

Just marking time? Feel the pulse with this easy-to-build project!

THIS PROJECT IS CHEAP, quick, easy . . . and you learn while you experiment!

Although designed as a metronome, producing regular 'clicks' (an invaluable aid to aspiring musicians), this handy little gadget can operate in a multitude of ways with just one or two simple circuit changes. To give you a hint, try changing the capacitor C1 for a much lower value one — say 10n. Now what do you hear?

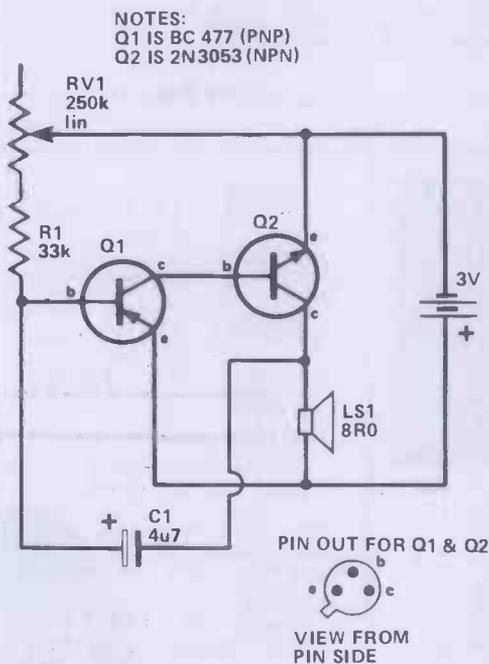


Fig. 1. Circuit diagram of the metronome. The circuit is drawn with the negative wire from the battery at the top of the diagram to make it easier to understand the operation of Q1.

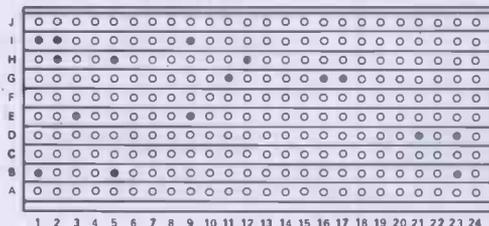


Fig. 2. Soldering guide for the veroboard, shown here copper side up. In this project it is not necessary to break any of the tracks.

CONSTRUCTION

Using our specially prepared drawings, and Hints for Constructors, building the unit is a cinch.

How it Works


When power is first applied to the circuit, both transistors are turned off and have a high resistance to current flow between their collectors and emitters. We can pretend that the loudspeaker isn't there for a moment (because the loudspeaker has a very low resistance compared with that presented by the collector-emitter junction of Q2 and the timing resistance of RV1 in series with R1).

Now we can see that when power is applied, C1 will begin to charge up as current flows into it via RV1 and R1. When the voltage across C1 reaches about -0.6 volts it is sufficient to begin to forward bias the base-emitter junction of Q1 and this transistor begins to 'turn on'. Current now flows through the collector-emitter junction of Q1, from the negative terminal back to the positive terminal of the battery.

When a current flows in the base-emitter junction of a transistor, a greater current is able to flow in the collector-emitter junction. So the current passing through the base-emitter junction of Q2 causes Q2 to 'turn on' and let current flow from the negative terminal of the battery through Q2 and LS1 to the positive terminal.

This surge of current makes the loudspeaker produce a 'click'. While Q2 is 'turned on', the voltage at its collector rises from being close to the positive terminal of the battery towards the negative terminal. This rise in voltage affects C1 which is connected to this point and causes it to charge via the base-emitter junction of Q1. As C1 reaches full charge, the current being drawn becomes too small to keep Q1 'turned on'. As Q1 'turns off', it causes Q2 to 'turn off' too and the voltage at Q2 collector falls back towards the positive terminal of the battery.

Of course, C1 is also affected by this voltage change and reflects it at the junction of C1, R1 and Q1 base. This point becomes about two volts positive of the positive terminal of the battery. This reverse-bias on Q1 base keeps Q1 and Q2 'turned hard off' and the cycle repeats as the voltage on C1 goes from $+2V$ to $-0.6V$ as current flows through RV1 and R1. The time between 'clicks' is determined by the resistance of RV1 in series with R1; the lower the resistance, the more current flows and the less time passes between each 'click'.

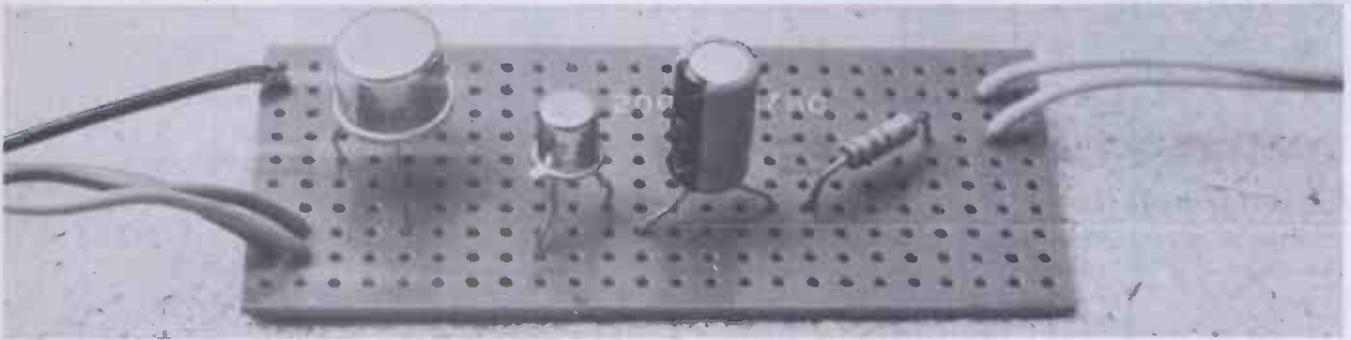

Parts List

| | |
|------------------------|----------------------------|
| RESISTOR (1/4W, 5%) | |
| R1 | 33k |
| POTENTIOMETER | |
| RV1 | 250k LIN |
| CAPACITOR | |
| C1 | 4 μ 7 16V Electrolytic |
| SEMICONDUCTORS | |
| Q1 | BC477 |
| Q2 | 2N3053 |
| MISCELLANEOUS | |
| LS1 | 8ohm Loudspeaker |
| 3V battery | |
| Knob for potentiometer | |
| Veroboard | |

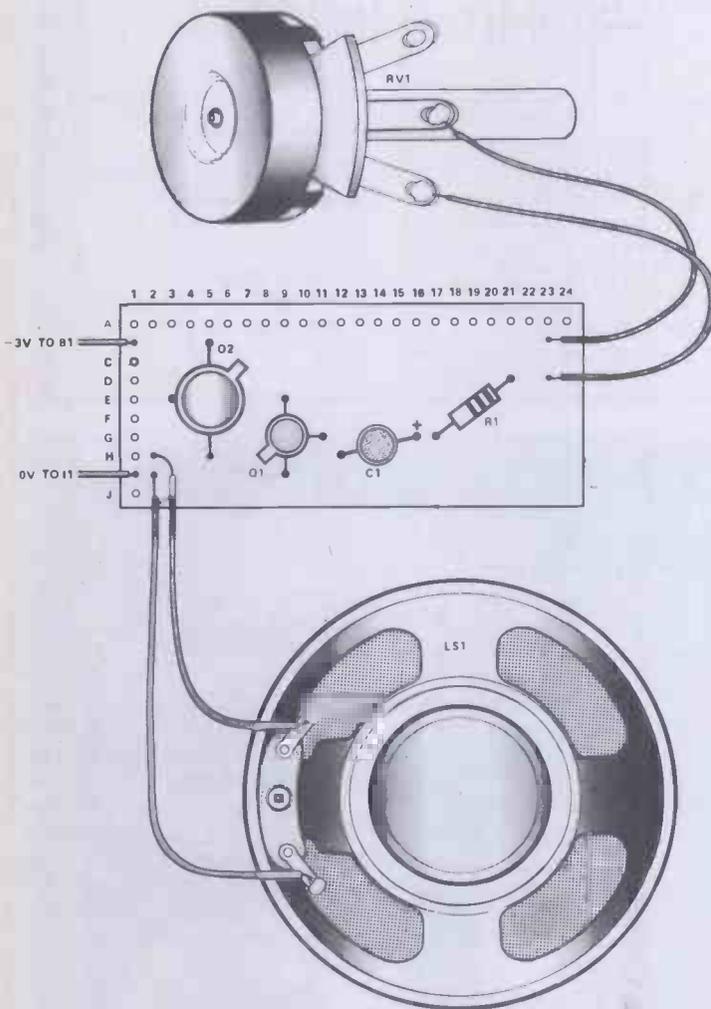


Fig. 3. Component layout of the metronome. A small 3V battery is connected with the positive terminal connected to track "1" and the negative terminal to track "2", as indicated.

Buylines

All of the components used in this project should be available from your usual supplier or from the larger mail-order companies.

The hints below apply generally to projects constructed on Veroboard. For this particular project the section "cutting the board" is not applicable.

HINTS FOR CONSTRUCTORS

Cutting the board. Rotate the "spot face cutter" while pressing gently to make the breaks in the copper track. If you do not have Vero's special tool, use a drill — 1/8" is about right. Always check that no bits of copper swarf are shorting to an adjacent track.

Inserting components. Long nose pliers come in handy for forming leads and inserting components. Do not bend the leads close to the body or they may break off. Check that components are not shorting to each other or to any wire links on the board.

Always insert the low profile components first: wire links, resistors, capacitors etc. Put the semiconductors in last.

Soldering. Make sure the component leads and the soldering iron are clean. If you use new components there should be no problem. Use a small soldering iron. 15 watts is ideal; 25 watts is really a safe maximum. Hold the components still when you solder them AND until the solder has set — about five seconds. Do not use too much solder or you may bridge the tracks and BE QUICK!

When the joint is cool, trim the lead with a pair of sidecutters.


Short Circuit

"HEADS" OR "TAILS"

This simple novelty circuit is designed to electronically simulate the tossing of a coin; randomly producing a "heads" or "tails" output. The output of the unit is displayed on two LEDs, one being marked "heads", and the other being given a "tails" legend. The unit has a push button switch which is briefly depressed in order to "toss the coin", and only one of the LEDs will be switched on when this switch is released, indicating the decision of the unit.

The circuit uses Q1 and Q2 in what is virtually a standard astable multivibrator circuit. The only deviation from the standard configuration is the inclusion of push button switch SW1 in the bias circuit for Q1. As the circuit stands there is no bias to Q1, and the circuit therefore fails to oscillate. However, if SW1 is operated the circuit can function normally. A roughly squarewave output is then produced at the collector of Q2, and the specified values give an operating frequency of many kilohertz.

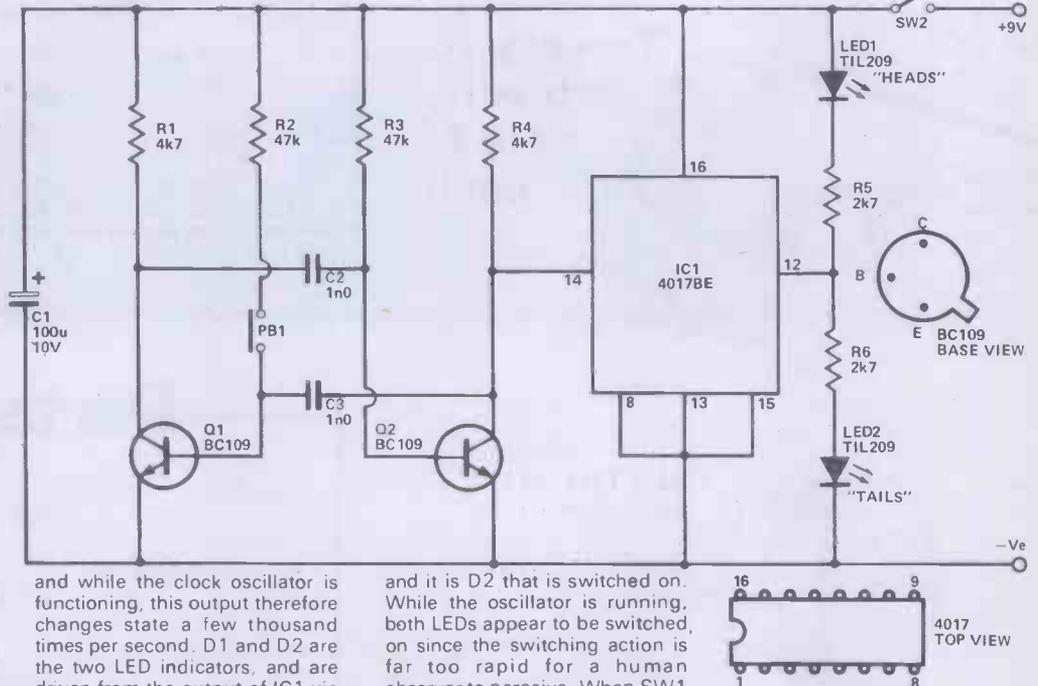This squarewave output is fed to a 4017 divide by ten circuit, which is used here effectively as a form of bistable circuit. After each five input cycles, the output of IC1 (pin 12) changes state,



and while the clock oscillator is functioning, this output therefore changes state a few thousand times per second. D1 and D2 are the two LED indicators, and are driven from the output of IC1 via current limiting resistors R5 and R6. When IC1's output is low, R6 and D2 are effectively short circuited by the output stage, but D1 will be switched on. Conversely, when the output is high, D1 and R5 are short circuited,

and it is D2 that is switched on. While the oscillator is running, both LEDs appear to be switched on, since the switching action is far too rapid for a human observer to perceive. When SW1 is released, and the oscillator stops, IC1 will stay in whatever output state it happened to have at the instant the oscillator stopped. There is, of course, no way of predicting which state this will be, and which of the LEDs will be

switched on. It is purely a matter of chance whether the unit indicates "heads" or "tails."

SW2 is the on/off switch. The current consumption of the circuit is only about 5 mA.

The NEW Marshall's 79/80 catalogue is just full of components

and that's not all . . .

. . . our new catalogue is bigger and better than ever. Within its 60 pages are details and prices of the complete range of components and accessories available from Marshall's.

These include Audio Amps, Connectors, Boxes, Cases, Bridge Rectifiers, Cables, Capacitors, Crystals, Diacs, Diodes, Displays, Heatsinks, I.C.s, Knobs, LEDs, Multimeters, Plugs, Sockets, Pots, Publications, Relays, Resistors, Soldering Equipment, Thyristors, Transistors, Transformers, Voltage Regulators, etc., etc.

Plus details of the NEW Marshall's 'budget' Credit Card. We are the first UK component retailer to offer our customers our own credit card facility.

Plus — Twin postage paid order forms to facilitate speedy ordering.

Plus — Many new products and data.

Plus 100's of prices cut on our popular lines including I.C.s, Transistors, Resistors and many more.

If you need components you need the new Marshall's Catalogue.

Available by post 65p post paid from **Marshall's, Kingsgate House, Kingsgate Place, London NW6 4TA**. Also available from any branch to callers 50p.



Retail Sales: London: 40 Cricklewood Broadway, NW2 3ET. Tel: 01-452 0161/2. Also 325 Edgware Road, W2. Tel: 01-723 4242. Glasgow: 85 West Regent Street, G2 2QD. Tel: 041-332 4133. And Bristol: 108A Stokes Croft, Bristol. Tel: 0272 426801/2.

OUT NOW!



Twenty-five projects at only 5p each!

£1.25

AUDIO PROJECTS

- Tantrum
- Audio Mixer
- Rumble Scratch Filter
- Constant Volume Amplifier
- Graphic Equaliser
- Envelope Generator

TEST GEAR

- Linear Scale Ohmmeter
- Analogue Frequency Meter
- White Noise Generator
- Transistor Tester

FOR THE HOME

- Digital Clock
- Ultrasonic Switch

- Drill Speed Controller
- Digibell
- Casanova's Candle
- FOR THE MOTORIST**
- LED Tachometer
- Parking Meter Timer
- MUSIC, GAMES**
- Hobbytune
- Touch Switch
- Push-Button Dice
- Photon Phone
- Starburst
- Photographic Timer
- Shark
- Multi-Option Siren

Send £1.25 + 30p (P&P) to Sales Office (Specials), Hobby Electronics, 145 Charing Cross Rd, London WC2H 0EE.

SPECIALS FROM MODMAGS

Send your orders to Sales Office (Specials), Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE.

ETI CIRCUITS

Books 1 & 2
Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal — hardly surprising when the circuits cost under 1p each!
£1.50 + 30p P&P each

ELECTRONICS TOMORROW

Comprised entirely of new material, the edition covers such diverse topics as Star Wars and Hi-Fi! The magazine contains projects for everyone — none of which have appeared in ETI — and a look at the future of MPUs, audio, calculators and video. How can you not read it?
75p + 30p P&P

TOP PROJECTS

Book 1 + 2 SOLD OUT! Book 3: SOLD OUT! Book 4: £1.00 + 30p P&P. Book 5: £1.00 + 30p P&P. Book 6: £1.00 + 30p P&P

TOP PROJECTS

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter, wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, 1B metal locator, electronic bongos, puzzle of the drunken sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit level.
Book 7: £1.25 + 30p P&P

ELECTRONICS — IT'S EASY

This very successful beginners' series has now been reprinted in one volume. The book covers just about every aspect of electronic theory and is ideal for anyone just starting out in this fascinating hobby.
£3.60 + 80p P&P

INTO ELECTRONICS PLUS

The complete series of Ian Sinclair's series Into Electronics Plus a selection of some of the most popular and informative articles from HE. Everything from Home Computing to making your own PCBs.
£1.00 + 30p P&P

Electronic Circuit Design

Selected Reprints from **electronics today** INTERNATIONAL

£1.25 + 30p EACH p&p

No. 1

| | |
|--|----|
| Contents | |
| CMOS | 4 |
| Audio Amplifiers | 27 |
| Power Supplies | 32 |
| Practical Guide to SCRs | 43 |
| Op Amps and Integrators | 51 |
| Electronic Speed Control for Motors | 54 |
| Op Amps | 59 |
| 3080 Circuits | 70 |
| CMOS to Mains | 71 |
| Practical Guide to Temperature Control | |

Contents

| | |
|----------------------------------|----|
| OP-AMPS | 4 |
| TRANSISTOR OPERATING POINT | 19 |
| 40 CMOS CLOCKS | 21 |
| PRACTICAL GUIDE TO REED SWITCHES | 29 |

No. 2

| | |
|------------------------------------|----|
| Contents | |
| V.F.E.T.S FOR EVERYONE! | 41 |
| CHOOSING AND USING TRANSFORMERS | 51 |
| DIGITAL ELECTRONICS BY EXPERIMENT | 55 |
| GAIN CONTROL | 83 |
| Designing and Using Active Filters | 4 |
| A Few Cheap Tricks! | 16 |
| Digital to Analogue Techniques | 21 |
| Using the LM3900N | 27 |
| Designing High(est)-Fi Amps | 33 |
| A Practical Guide to Triacs | 47 |

No. 3

| | |
|-----------------------------------|----|
| Contents | |
| Power Supplies | 4 |
| A Practical Guide to Zener Diodes | 16 |
| Modern Crystal Oscillators | 21 |
| High Voltage for Low Cost | 27 |
| Odd Dees | 33 |
| Designing Oscillators | 47 |


These three specials reprint the best 250+ pages of the almost 1500 ETI pages that have explained how to design your own electronic circuits. Take a look at the contents — together the three volumes from a comprehensive guide to most of the circuits you're likely to need.

BUY ALL THREE

Send £1.25 + 30p (P&P) for each volume required to Sales Office (Specials), Modmags Ltd, 145 Charing Cross Road, London, WC2H 0EE.

Short Circuit

RADIO 4 TUNER

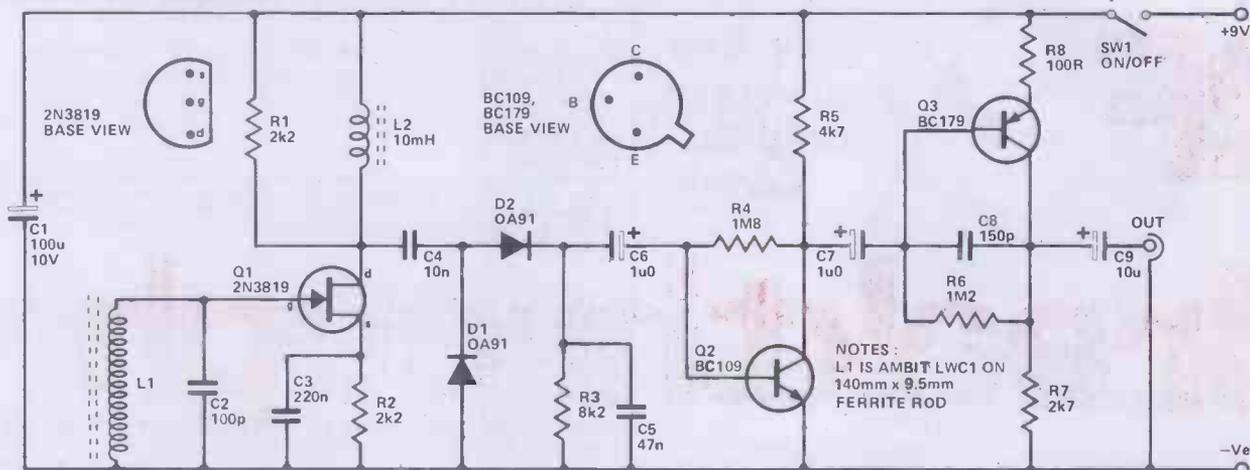

This tuner has primarily designed for use with a tuner/amplifier which does not have long wave coverage, and is therefore unable to receive the BBC Radio 4 LW transmission. However, it can also be used as a personal receiver for reception of Radio 4 if the output is fed to a crystal earphone or a pair of high impedance magnetic headphones.

Q1 is used as a JFET common source amplifier, and its gate terminal is fed direct from the ferrite aerial (L1). This is quite acceptable since a JFET has an

extremely high input impedance and will not place a significant degree of loading on the aerial. L1 is used to bias the gate of Q1 to the negative supply rail. C2 brings the ferrite aerial to resonance at approximately the Radio 4 frequency of 200kHz, and L1 is simply slid along the ferrite rod to tune the unit to precisely the correct frequency. L2 forms the main source load for Q1, but it was found to be necessary to damp this using R1 in order to prevent instability.

The amplified RF output from

Q1 is fed by C4 to a straight forward AM detector circuit which is comprised of D1, D2, R3, and C5. The demodulated AF signal is then coupled by C6 to a high gain, low noise, common emitter amplifier based on Q2.

This considerably boosts the signal, but it is still at an inadequate level to drive many amplifiers. A second common emitter stage using Q3 is therefore used to further boost the signal, and this gives an output amplitude of several hundred millivolts RMS. The full gain of

Q3 is not required, and R8 is therefore used to provide local negative feedback which produces the required reduction in gain. C8 rolls off the high frequency response of Q3. This aids stability and improves the signal to noise ratio of the unit.

The tuner only has one control, and this is on/off switch SW1. The current consumption of the unit is only about 2.5 mA. When the correct position on the ferrite rod for L1 has been located, it should be firmly taped or glued in this position.

Now, the hand-held 50MHz counter.

For £54.00
+15% VAT AND P&P. £63.83

Various accessories are also available.

It's true. Our new, diminutive frequency counter, the *Max 50 costs a mere £54.00. Which, when you consider its totally automatic performance, is quite outstanding.

Well, what would you normally expect to pay for a guaranteed frequency range of 100Hz to 50MHz; 6-digit LED display; auto-ranging, polarity, slope trigger and input level; and built-in overvoltage protection?

And there's even more. The high reliability of LSI circuitry; sensitivity of 30mV trigger threshold; 3ppm accuracy; choice of battery or a.c. mains operation, and optional antenna.

True value, and yours for the asking.

Just call us on Saffron Walden (0799) 21682 right away. Your own *Max 50 could be hand-held tomorrow!

Dealer enquiries also welcomed. *For a while, supplies will be labelled 'Mini-max'.

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited.

Dept 14F Unit 1, Shire Hill Industrial Estate.
Saffron Walden, Essex CB11 3AO
Telephone: Saffron Walden (0799) 21682
Telex: 817477

RF



Breakthrough


The evanescent (look it up in a dictionary) nature of most forms of RF interference to Hi-Fi equipment is often sufficient to cause an otherwise methodical, logical-acting and patient person to erupt into behaviour characteristic of a clockwork orange. "It's those furshlugginer CBers again! . . . !!!!!!" is not an uncommon cry. To suggest that the fault lies within the equipment is regarded as treasonous! Here's how to delete those expletives.

IF YOU HAVE EVER been aggravated by the sound of the local taxi service's radio in the middle of your favourite record, or if the nearest TV transmitter imprints its sound track on tape every time you make a recording, you have been struck by that infuriating phenomenon known as RF breakthrough.

With the huge number of broadcasting stations, taxi radios and CB freaks — among many others — now operating, the problem of radio frequency interference is a major headache. And the problem is not restricted to those with Hi-Fi equipment; public address systems, hearing aids and even electronic musical instruments all suffer. (We won't delve into the case of the man who claimed to pick up transmissions through a filling in his tooth!)

The cause of radio breakthrough into audio equipment is almost invariably within the suffering audio equipment. It's rarely caused by a fault within the transmitter, or even by faulty operational procedures.

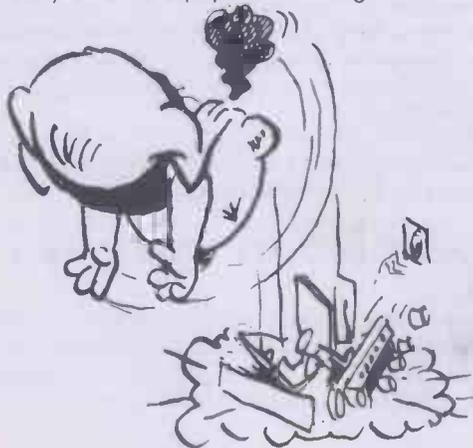The phenomenon is generally known as "audio rectification" because of the way the interference is picked up. In essence, the unwanted RF energy is picked up by some part of an audio system which acts as an antenna — speaker and interconnecting leads, or even an incorrectly earthed equipment casing.



The energy is passed on through the audio system until it strikes a component or suitable element which is operating non-linearly, which acts as a rectifier. This could be a valve, a transistor, an integrated circuit, or even a poorly soldered joint!

The rectified signal is then amplified by the remainder of the audio system. (In some cases the speaker leads may act as the antenna and a faulty connection on one of the speakers as the rectifier — as has happened with large and powerful PA systems).

Of course there are other causes than transmissions by radio stations, television channels or CBers. Electrical machines and appliances often behave as transmitters of spurious radio frequencies, sending noise instead of the more coherent transmissions from radio stations.

Regardless of what form the breakthrough takes — noise or regular broadcasts — radio frequencies may be carried to the audio equipment along two paths, through the air, or through the mains power supply. The main methods of controlling these two forms are: shielding for airborne radio frequencies and filtering for line-carried interference. The cure for one will have no effect on the other.

In most cases the causes of this type of interference are introduced into the early stages of a preamp, or are picked up and introduced by the power supply leads. To check that this is in fact so, just turn down the volume control when you notice the interference. If this does reduce the interference, it is being introduced before the volume controls, which are normally in the output stage of the preamp, or its equivalent in an integrated unit.

If the level of the interference remains constant when the volume control is turned down, the interference is probably being picked up in some stage after the volume control.

CONTROL-AFFECTED INTERFERENCE

If the volume control does affect the level of the interference, it is most likely that the signals are introduced in one of three places — via the mains cable, via the interconnecting leads between the main amp and the auxiliary equipment, or via the speaker leads themselves.

It may also be caused by a poor, or nonexistent earth connection — this should be checked thoroughly before looking further. To check this aspect, examine the continuity of wiring at the input and output sockets on the equipment, and also check the earthing facilities in the interconnecting cables themselves.

Having checked out all the earth connections, it is advisable next to check the speaker leads. Although it is hard to see how a signal picked up here would be of sufficient level to produce an audible output, or even be affected by the volume control, signals picked up by the speaker cables may be routed in such a way as to show these symptoms. If the RF signal is picked up in the speaker leads, it is fed back into the amplifier's circuitry through the negative feedback loop. And while feedback is applied after the volume control, some of the radio frequencies may be conducted back into the earlier stages of the preamp.

Sometimes the speaker leads can be of such a length that they actually resonate at the interfering frequency, in which case an instant cure may be obtained by shortening or lengthening the cables. Unfortunately, this may merely substitute one cause of interference for another, and the taxi company may simply be replaced by a local TV channel. Twisting the cables, or using shielded cable may also be effective here.

Another possible cure is to connect a capacitor across the amplifier's output terminals, or from each terminal to earth. The high audio frequencies will not be degraded if a capacitance of about 100nF (0.1µF) is used as the impedance is very low at this point in the circuit.

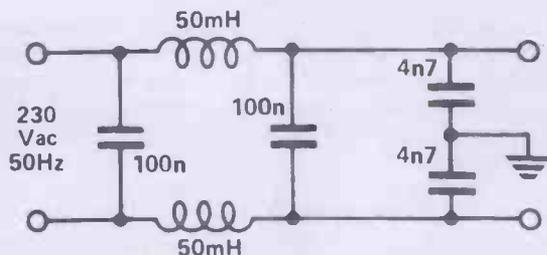


Fig 1. Circuit of a mains input filter which may be home made. If you do make it yourself it is essential to use capacitors rated for mains operation. Ceramic types rated at 400 VAC or, better still, 630 VAC, are recommended.

A capacitance of about 10nF is generally sufficient to remove radio frequencies, although it is best to use the smallest value that gives relief from the problems (provided sufficient capacitors are on hand to allow a few experiments). Always use ceramic capacitors for this purpose.

SIGNAL LEADS

If the checks already covered don't cure the problem, the next trouble spot to check is the signal leads. The quickest and easiest way to do this is to check all externally connected components, such as the turntable, tape deck or tuner. If the interference is eliminated when one of these leads is disconnected, then the cable connecting the component to the amplifier is not properly screened. The metallic shield or braid on the cable should be checked to see that it is complete, and that it makes a good earth contact at the component, and at the amp.

If one of these remedies has any result, check for line-carried interference by connecting a line filter in series with the incoming mains power line. These filters are available from some electronics suppliers, or a unit may be made as shown in Figure 1.

If you make this filter yourself, do not under any circumstances increase the values of the capacitors shown, and make absolutely certain that the capacitors are rated for at least 400 volts AC operation (preferably more for safety).

When the signal strength of the unwanted signal is very high, as it may be in areas close to transmitting antennas, the signal may find its way into the circuitry despite these precautions. This is most likely when the amplifier or the ancillary components do not have a metallic case, or when the metal cabinets are not correctly earthed. If a non-metallic case is thought to be the problem, the cure is an earthed shield — aluminium foil is suitable when securely earthed.

If the signal still finds its way into the system more drastic measures will be required. Firstly, check that there are no *dry joints* — joints where the solder has been incorrectly applied and has set around a conductor without making good electrical contact — for a dry joint can act as an almost perfect rectifier. If a visual examination shows any doubtful joints — if they look crystalline or grey — resolder them by giving them a touch with a hot soldering iron.


Electrolytic capacitors may cause problems because they tend to have high inductive reactance at radio frequencies, which may prevent them passing the unwanted radio frequencies to ground. Suspicious capacitors may be checked by temporarily wiring a 10nF (0.01 µF) capacitor in parallel. Permanent wiring of the additional capacitor may follow if this is found to cure the breakthrough problem.

If the problem remains after all these checks, it may be necessary to modify the amplifier as outlined below — not a job for the inexperienced.

UNAFFECTED BY VOLUME CONTROL

Sometimes the unwanted radio frequency breakthrough will be heard at a constant level, which is not affected by settings of the volume control. When this happens (or when all other attempted remedies have failed) it will be

RF Breakthrough

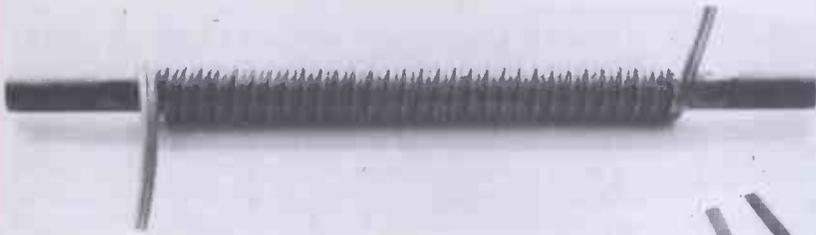

Interference pickup on speaker leads may be cut by winding part of the lead, nearest the amplifier terminals, on a ferrite rod — available at many parts suppliers.



An alternative method is to wind 'suspect' leads onto ferrite rings, well, it's worth a try anyway.



necessary to use some form of filtering at the input to the power amplifier. This is a job for those experienced in electronic matters as it involves knowledge of the input circuitry of the amp, and it should not be attempted by the Hi-Fi (or electronics) novice.

One way of providing this filtering, which has proved successful, is shown in the diagram. Unfortunately it is impossible to quote exact component values as these will be determined by the circuitry of the individual amplifier. However, it is important that the component values be chosen so that there is no audible change in the frequency response as a result of the modifications. Only in really severe cases which have withstood all possible solutions will it be necessary to trade off frequency response against interference removal. The capacitors used should be ceramics (not paper or polyester types) and inductor L1 may be a ferrite bead.

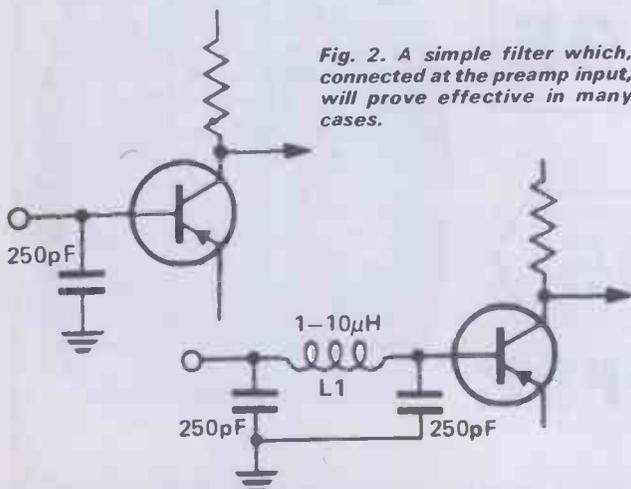


Fig. 2. A simple filter which, connected at the preamp input, will prove effective in many cases.

Fig. 3. Another simple filter, similar to that shown in Figure 2, but generally more effective in stubborn cases.

BREAKTHROUGH IN FM TUNERS

Electricity, the very thing that makes radio transmissions possible, also interferes with those transmissions. Although FM broadcasting has considerably reduced the problems, it is not totally immune, and breakthrough still occurs. As with stray noise picked up within the other components of the audio system, FM interference is also either airborne or line-carried.

Sometimes the same cures as are used in the rest of the system will be sufficient to remove unwanted

breakthrough, but it is also possible to remove the offending source in many cases, since a majority of the problems arise from household appliances.

Identifying the source may be the most baffling problem of all, as the cause may be as diverse as a car's ignition system, or a faulty fluorescent light fitting.

A car ignition system gives rise to a fast and steady popping type of interference. Most cars should be fitted with suitable suppressors, but older cars, or cars with faulty suppressors, may still cause serious problems for FM users near main roads.

A number of household appliances which are operated by electric switches cause irregular clicking — the switching of fridge thermostats is well known, and others like electric typewriters, adding machines or even relays in the lifts of high rise buildings can contribute.

Whining, or a steady level of scratchy noise often arises from electric motors which produce sparks in operation, and from electric generators. And a simple faulty fluorescent light fitting can give rise to a buzzing hum.

Obviously with devices such as these, the easiest cure may be the source — if you can find it.

WHERE DOES NOISE COME FROM?

It may seem strange that these useful and apparently harmless devices should cause problems by generating radio frequencies, but there are many ways in which they can develop such frequencies.

Any sharp pulse from switching, or somehow interrupting, an electric circuit contains some radio

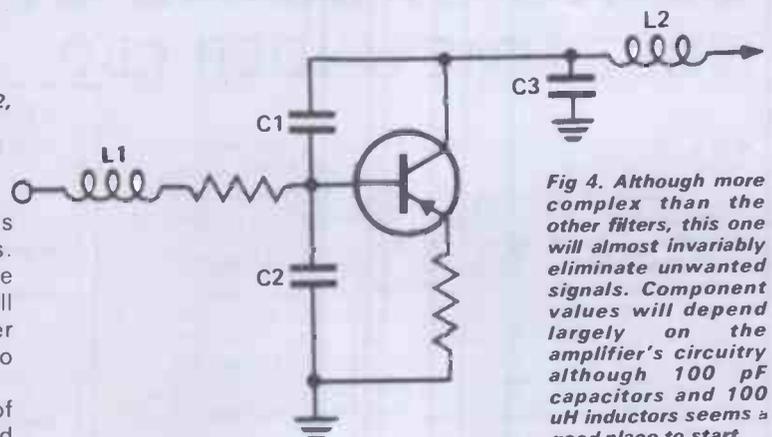


Fig. 4. Although more complex than the other filters, this one will almost invariably eliminate unwanted signals. Component values will depend largely on the amplifier's circuitry although 100 pF capacitors and 100 µH inductors seems a good place to start.

RF Breakthrough

frequency energy. Thus switches, thermostats and some motors cause problems. And any machine which causes sparks in operation is a likely candidate. After all, the very first radio transmissions were made with the aid of a spark transmitter, in which capacitors were allowed to discharge across a spark gap. Spark transmitters produce so much radio frequency energy that they can affect very wide areas of the RF spectrum and cause widespread interference to most receiving devices. Some electric motors are not so very different, and almost every electric switch in an ac circuit produces sparks in operation. An arc lamp is virtually an enormous spark generator.

When trying to eliminate RF noise in the FM tuner, it is necessary to find where the noise is coming from — power lines or through the air. A simple means of doing this is to disconnect the antenna and link the tuner's terminals to ground. If the noise persists, it is carried through the power lines; if it has disappeared, it is airborne.

If the noise is found to be airborne, and you have a directional outdoor antenna with a run of 300 ohm balanced feeder, it is possible that the noise is being picked up in the feeder cable. In this case a shielded feeder is essential — in spite of its extra cost — and this may reduce or completely eliminate the problem.

LINE CARRIED NOISE

If the noise is carried through the power lines, it is worth looking for a generating source within the home. When a

machine or appliance is suspected, it can be verified by having somebody turn the machine on and off while you listen to the noise on the audio system with the FM as source.

If you do manage to identify a source within your home, it is worth checking with the manufacturer of the appliance or machine to see whether radio frequency suppression is normally fitted, or is available. Unless the manufacturer has some simply-fitted device, it is best to consult an expert, as there are many different methods of applying the suppression.

Generally the method will depend on a bypass of the RF to ground via a capacitor. If you know the details of the machine's operation and have electronics experience, you may be able to decide where the capacitor should go and what value should be used. If you have any doubts at all, however, consult an expert.

When constructing a shield, make certain that it is well bonded at all joints and that the earth connection is firm.

If you cannot locate the noise source, it will be necessary to run through the same procedures as were used for eliminating breakthrough from the system as a whole.

If after taking every humanly possible measure you still suffer from radio frequency interference, you have only three options left: You can sell your equipment, you can sell your house, or you can blow up the offending source.

We cannot really recommend any of these.

HE



SEIKO CHRONOGRAPH

£39.95

ALL INC.

SEIKO ALARM CHRONOGRAPH

£49.95

ALL INC.



SEIKO SPECIAL OFFER FIRST TIME UNDER £50

Let's look at the simple Seiko first — a dependable chronograph with no nonsense operation. At the touch of a button you can select either the things that normal watches do i.e. telling the time or a stopwatch display with the usual split/lap time facility.

The next Seiko is a bit clever. It's an alarm chronograph with a locking facility. What does that mean, I hear you say. Buttons are prone to being pushed, especially buttons that reset the watch time. However, with this remarkable wrist piece you can just press the LOCK button and pushing all the other controls suddenly has no effect. Full chronograph and alarm facilities we also featured.

SEIKO WATCH OFFER

Name

Address

Please send me Seiko Chronograph(s) at £39.95 each.
..... Seiko Alarm Chronograph(s) at £49.95 each

I enclose a cheque/PO made payable to Modmags Ltd for £

Modmags Ltd.,
Sales Office (Ref. Seiko Offer),
145, Charing Cross Road,
London WC2H 0EE.

BOOKS BY BABANI

| BOOK NO | DESCRIPTION | £ p |
|---------|--|------|
| BP6 | Engineers & Machinists Ref. Tables | 0.50 |
| BP14 | 2nd Book Transistor Equivs & Subs | 1.10 |
| BP24 | 52 Projects Using IC741 (or equiv) | 0.95 |
| BP26 | Radio Antenna Book Long Distance Reception & Transmission | 0.85 |
| BP27 | Giant Chart of Radio Electronic Semi-conductor & Logic Symbols | 0.80 |
| BP32 | Build Metal & Treasure Locators | 1.00 |
| BP34 | Practical Repair & Renovation of Colour TVs | 1.25 |
| BP35 | Handbook of IC Audio Preampifier | 1.25 |
| BP36 | 50 ICs use Germ/Sil/ Zener Diodes | 0.75 |
| BP37 | 50 Projects using Relays /SCRs/Triacs | 1.25 |
| BP39 | 50 Field Effect Trans Projects | 1.25 |
| BP40 | Digital IC Equivs & Pin Connection | 2.50 |
| BP41 | Linear IC Equivs & Pin Connection | 2.75 |
| BP43 | How to make Walkie Talkies | 1.25 |
| BP44 | ICC555 Projects (Revised & Enlarged Edition) | 1.75 |
| BP45 | Projects on Opto-electronics | 1.25 |
| BP46 | Radio Circuits using ICs | 1.35 |
| BP47 | Mobile Discotheque Handbook | 1.35 |
| BP48 | Electronics Projects for Beginners | 1.35 |
| BP49 | Popular Electronic Projects | 1.45 |
| BP50 | IC LM3900 Projects | 1.35 |
| BP51 | Electronic Music & Creative Tape Recording | 1.25 |
| BP52 | Long Distance Television Reception (TV-DX) For the Enthusiast | 1.45 |
| BP53 | Practical Electronic Calculations & Formulae | 2.25 |
| BP55 | Radio Stations Guide | 1.45 |
| BP56 | Electronic Security Devices | 1.45 |
| BP57 | How to Build Your Own Solid State Oscilloscope | 1.50 |
| BP58 | 50 Circuits using 7400 Series ICs | 1.35 |
| BP59 | Second Book of CMOS IC Projects | 1.50 |
| BP60 | Practical Construction of Pre-amps/Tone Controls/ Filters & Artn | 1.45 |
| BP61 | Beginners Guide to Digital Techniques | 0.95 |
| BP62 | Elements of Electronics — Book I | 2.25 |
| BP63 | Elements of Electronics — Book II | 2.25 |
| BP64 | Elements of Electronics — Book III | 2.25 |
| BP65 | Single IC Projects | 1.50 |
| BP66 | Beginners Guide to Microprocessors & Computing | 1.75 |
| BP67 | Counter driver & numeral display projects | 1.75 |
| BP68 | Choosing & Using your Hi-Fi | 1.65 |
| BP69 | Electronic Games | 1.75 |
| BP70 | Transistor Radio Fault-Finding Chart | 0.50 |
| BP160 | Coil Design & Construction Manual | 0.75 |
| BP202 | Handbook of Integrated Circuits Equivs & Substitutes | 1.00 |
| BP211 | First Book of Diode Characteristics & Equivalents & Substitutes | 1.25 |
| BP213 | Electronic Circuits for Model Railways | 1.00 |
| BP215 | Shortwave Circuits & Gear for Experimenters & Radio Hams | 0.85 |
| BP217 | Solid State Power Supply Handbook | 0.85 |
| BP221 | 28 Tested Transistor Projects | 1.25 |
| BP224 | 50 CMOS IC Projects | 0.95 |
| BP226 | Build Advanced Short wave receivers | 1.20 |
| BP227 | Beginners Guide to Building Electronic Projects | 1.25 |
| RCC | Resistor Colour Code Disc | 0.20 |

BRACKETS

Right angle mounting brackets. Ideal for mounting, PCB, panels etcetera into boxes and cases.
 1BSWG — Mild steel — short face has silted hole 6.5cm x 3.7cm long face has 3.7cm diam hole
 O/NO: 1725 Height 15cm, length 15cm, width 10cm £0.05
 O/NO: 1727 Height 25cm, length 15cm, width 10cm £0.07

SWITCHES

| Description | No. | Price |
|--------------------------------------|------|-------|
| DPDT miniature slide | 1973 | £0.18 |
| DPDT standard slide | 1974 | £0.17 |
| Toggle switch SPST 1 1/2 amp 250V ac | 1975 | £0.38 |
| Toggle switch DPDT 1 amp 250V ac | 1976 | £0.48 |
| Rotary on-off mains switch | 1977 | £0.58 |
| Push switch — Push to make | 1978 | £0.16 |
| Push switch — Push to break | 1979 | £0.21 |

| Description | No. | Price |
|--|------|-------|
| Miniature SPST toggle 2 amp 250V ac | 1958 | £0.81 |
| Miniature SPST toggle 2 amp 250V ac | 1959 | £0.86 |
| Miniature DPDT toggle 2 amp 250V ac | 1960 | £0.92 |
| Miniature DPDT toggle centre off 2 amp 250V ac | 1961 | £1.09 |
| Push-button SPST 2 amp 250V ac | 1962 | £1.04 |
| Push-button SPST 2 amp 250V ac | 1963 | £1.09 |
| Push-button DPDT 2 amp 250V ac | 1964 | £1.38 |

| Description | No. | Price |
|---------------|------|-------|
| 1 pole 12 way | 1965 | £0.55 |
| 2 pole 6 way | 1966 | £0.55 |
| 3 pole 4 way | 1967 | £0.55 |
| 4 pole 3 way | 1968 | £0.55 |

| Description | No. | Price |
|---|------|-------|
| Plastic button gives simple 1 pole change over action Rating 10 amp 250V ac | 1970 | £0.29 |

ANTEX IRONS

| | | |
|------|---|-------|
| 1943 | 15 watt iron element ceramic fitted with 3/32" bit | £5.12 |
| 1947 | Replacement element for 1943 iron | £2.33 |
| 1944 | Iron coated bit 3/32" for 1943 iron | £0.58 |
| 1945 | Iron coated bit 1/8" for 1943 iron | £0.58 |
| 1946 | Iron coated bit 3/16" for 1943 iron | £0.58 |
| 1948 | General purpose 18 watt iron fitted with iron coated bit | £5.12 |
| 1952 | Replacement element for 1948 iron | £2.22 |
| 1949 | Iron coated bit 3/32" for 1948 iron | £0.58 |
| 1958 | Iron coated bit 1/8" for 1948 iron | £0.58 |
| 1951 | Iron coated bit 3/16" for 1948 iron | £0.58 |
| 1931 | Highly popular x 25 25 watt quality iron ceramic shafts to provide near perfect insulation breakdown voltage of 1500 volts AC and a leakage current of only 3-5uA and another shaft of stainless steel to ensure strength | £5.12 |
| 1935 | Replacement element for 1931 iron | £2.00 |
| 1932 | Iron coated bit 1/8" for 1931 iron | £0.58 |
| 1933 | Iron coated bit 3/32" for 1931 iron | £0.58 |
| 1934 | Iron coated bit 1/4" for 1931 iron | £0.58 |
| 1953 | SK1 kit contains 15 watt iron with a 3/16" bit plus two spare solder, heat-sink and a booklet 'How to solder', in presentation display box | £7.28 |

BIB HI-FI ACCESSORIES

| | | | | | |
|------|-----------------------|-------|------|----------------------|-------|
| 2201 | 2.5"x3.75" .1 Copper | £0.71 | 2211 | 2.5"x2.5" .15 Copper | £0.63 |
| 2202 | 2.5"x3.75" .1 Copper | £0.61 | 2212 | 3.75"x17" .15 Copper | £2.39 |
| 2203 | 2.5"x17" .1 Copper | £2.14 | 2213 | 3.75"x5" .15 Copper | £0.90 |
| 2205 | 3.75"x3.75" .1 Copper | £0.71 | 2217 | 3.75"x11.9" .1 Plain | £1.79 |
| 2206 | 3.75"x17" .1 Copper | £2.76 | 2218 | 3.75"x2.5" .1 Plain | £0.44 |
| 2207 | 4.75"x17.9" .1 Copper | £3.61 | 2219 | 5"x3.75" .1 Plain | £0.68 |
| 2208 | 2.5"x1" .5 lb pack | £0.85 | 2225 | 2.5"x3.75" .15 Plain | £0.37 |
| 2204 | 3.75"x5" .1 Copper | £0.79 | 2226 | 2.5"x3.75" .15 Plain | £0.56 |
| 2210 | 2.5"x5" .15 Copper | £0.64 | | | |

VEROBOARD

| | | |
|-----|---|-------|
| 806 | J Compact tape head cleaning kit | £1.22 |
| 810 | 23 Tape Editing kit | £2.66 |
| 811 | 24 Cassette Tape editing and joining kit | £2.76 |
| 813 | 29A Salvage cassette | £0.51 |
| 814 | 31 Cassette Head cleaning tape | £0.71 |
| 817 | 36A Record & Stylus cleaning kit | £0.46 |
| 818 | 41 8-track Cartridge tape head cleaner | £1.24 |
| 819 | 42 Groove Kleen auto metal record cleaner | £2.65 |
| 826 | 52A Cassette storage tray (holds 10) | £0.92 |
| 827 | 53 Hi-Fi stereo test cassette | £3.17 |
| 829 | 60 Chrome finish 'Groove Kleen' (plastic) | £2.12 |
| 834 | 69 Anti-static Hi-Fi cleaning liquid | £0.35 |
| 838 | 78 Cassette hand tape winder | £1.50 |

WIRE CONNECTORS

Entirely new range of connectors for Decra wire. Uniquely designed Wirepots soldered to the P.C. Board. A pre-stripped wire is inserted into the connector and easily locked by pressing the housing down. The wire is alternatively removed by lifting the housing. Tin alloy plated contacts ensure good as gold performance.
 Housing consists of Thermo plastic polyester.
 1728 Single connector in red/black or white £0.12 inc VAT
 1729 Three-way connector black ONLY £0.23 inc VAT
 1730 Four-way connector black ONLY £0.28 inc VAT

FUSE HOLDERS AND FUSES

| Description | No. | Price |
|--------------------------------|-----|-------|
| 20mm x 5mm chassis mounting | 506 | £0.18 |
| 1 1/4" x 1/4" chassis mounting | 507 | £0.14 |
| 1 1/4" car inline type | 508 | £0.18 |
| Panel mounting 20mm | 509 | £0.23 |
| Panel mounting 1 1/4" | 510 | £0.37 |

| QUICK BLOW 20mm | | | | | |
|-----------------|-----|------|-----|------|-----|
| Type | No. | Type | No. | Type | No. |
| 150mA | 610 | 1A | 615 | 6p | 3A |
| 250mA | 611 | 1.5A | 616 | 7p | 4A |
| 550mA | 613 | 2A | 617 | 6p | 5A |
| 800mA | 614 | 2.5A | 618 | 7p | 6A |

| ANTI-SURGE 20mm | | | | | |
|-----------------|-----|------|-----|-------|-----|
| Type | No. | Type | No. | Type | No. |
| 100mA | 622 | 1A | 625 | 2.5A | 628 |
| 250mA | 623 | 2A | 626 | 3.15A | 629 |
| 500mA | 624 | 1.5A | 627 | 5A | 630 |

| QUICK-BLOW 1 1/4" | | | | | |
|-------------------|-----|-------|-----|-------|-----|
| Type | No. | Type | No. | Type | No. |
| 250mA | 631 | 500mA | 632 | 800mA | 634 |

| NUTS AND BOLTS | | | | | |
|----------------|-----|------|-----|------|-----|
| Type | No. | Type | No. | Type | No. |
| 1A | 635 | 2.5A | 638 | 4A | 641 |
| 2A | 637 | 3A | 639 | 5A | 642 |

| BA BOLTS — packs of BA threaded cadmium plated screws slotted cheese head. Supplied in multiples of 50 | | | | | |
|--|-----|-------|-----------|-----|-------|
| Type | No. | Price | Type | No. | Price |
| 1in OBA | 839 | £1.38 | 1/2in 4BA | 846 | £0.37 |
| 1/2in OBA | 840 | £0.86 | 1/4in 4BA | 847 | £0.29 |
| 1in 2BA | 842 | £0.75 | 1in 6BA | 848 | £0.46 |
| 1/2in 2BA | 843 | £0.52 | 1/2in 6BA | 849 | £0.24 |
| 1/4in 2BA | 844 | £0.60 | 1/4in 6BA | 850 | £0.29 |
| 1in 4BA | 845 | £0.51 | | | |

| BA NUTS — packs of cadmium plated full nuts in multiples of 50 | | | | | |
|--|-----|-------|------|-----|-------|
| Type | No. | Price | Type | No. | Price |
| OBA | 855 | £0.83 | 4BA | 857 | £0.35 |
| 2BA | 856 | £0.55 | 6BA | 858 | £0.28 |

| RA WASHERS — flat cadmium plated plain stamped washers supplied in multiples of 50 | | | | | |
|--|-----|-------|------|-----|-------|
| Type | No. | Price | Type | No. | Price |
| OBA | 859 | £0.16 | 4BA | 861 | £0.14 |
| 2BA | 860 | £0.14 | 6BA | 862 | £0.14 |

| SOLDER TAGS — Hot tinned supplied in multiples of 50 | | | | | |
|--|-----|-------|------|-----|-------|
| Type | No. | Price | Type | No. | Price |
| OBA | 851 | £0.46 | 4BA | 853 | £0.25 |
| 2BA | 852 | £0.32 | 6BA | 854 | £0.25 |

AUDIO LEADS

| No. | Type | Price |
|-----|---|-------|
| 107 | FM, indoor Ribbon Aerial | £0.69 |
| 113 | 3.5mm Jack plug to 3.5mm Jack plug. Length 1.5m | £0.86 |
| 114 | 5 pin DIN plug to 3.5mm Jack connected to pins 3 & 5. Length 1.5m | £0.98 |
| 115 | 5 pin DIN plug to 3.5mm Jack connected to pins 1 & 4. Length 1.5m | £0.98 |
| 116 | Car aerial extension Screened insulated lead. Fitted plug and socket | £1.44 |
| 117 | AC mains connecting lead for cassette recorders and radios. 2 metres | £0.78 |
| 118 | 5 pin DIN phono plug to stereo headphone Jack socket | £1.21 |
| 119 | 2+2 pin DIN plugs to stereo Jack socket with attenuation network for stereo headphones. Length 0.2m | £1.04 |
| 120 | Car stereo connector. Variable geometry plug to fit most car cassettes. 8-track cartridge and combination units. Supplied with inlined fuse power lead and instructions | £0.69 |
| 123 | 5.5m Coded Guitar Lead Mono Jack plug to Mono Jack plug. Black | £1.73 |
| 124 | 3 pin DIN plug to 3 pin DIN plug. Length 1.5m | £0.86 |
| 125 | 5 pin DIN plug to 5 pin DIN plug. Length 1.5m | £0.86 |
| 126 | 5 pin DIN plug to Tinned open end. Length 1.5m | £0.86 |
| 127 | 5 pin DIN plug to 4 Phono plugs | £1.50 |
| 128 | 5 pin DIN plug to 5 pin DIN socket. Length 1.5m | £0.92 |
| 129 | 5 pin DIN plug to 5 pin DIN plug mirror image. Length 1.5m | £1.21 |
| 130 | 2 pin DIN plug to 2 pin DIN inline socket. Length 5m | £0.78 |
| 131 | 5 pin DIN plug to 3 pin DIN plug 1 & 4 and 3 & 5. Length 1.5m | £0.95 |
| 132 | 2 pin DIN plug to 2 pin DIN socket. Length 10m | £1.13 |
| 133 | 5 pin DIN plug to 2 Phono plugs. Connected pins 3 & 5. Length 1.5m | £0.86 |
| 134 | 5 pin DIN plug to 2 Phono sockets. Connected pins 3 & 5. Length 23cm | £0.78 |
| 135 | 5 pin DIN socket to 2 Phono plugs. Connected pins 3 & 5. Length 23cm | £0.78 |
| 136 | Coded stereo headphone extension lead. Black. Length 1.5m | £2.01 |
| 178 | AC mains lead for calculators, etc. | £0.52 |

TRANSFORMERS

| MINIATURE MAINS Primary 240V | | | |
|------------------------------|-----------------|-------|-----------|
| No. | Secondary | Price | |
| 2021 | 6V-0-6V 100mA | £1.04 | P & P 45p |
| 2022 | 9V-0-9V 75mA | £1.04 | P & P 45p |
| 2023 | 12V-0-12V 100mA | £1.29 | P & P 66p |

| MINIATURE MAINS Primary 240V with two independent secondary windings | | | |
|--|-----------------------|-------|-----------|
| No. | Type | Price | |
| 2024 | MT280-0-6V 0-6V RMS | £1.84 | P & P 86p |
| 2025 | MT150-0-12V 0-12V RMS | £1.84 | P & P 86p |

| 1 AMP MAINS Primary 240V | | | |
|--------------------------|-----------------|-------|-----------|
| No. | Secondary | Price | |
| 2026 | 6V-0-6V 1 amp | £2.88 | P & P 45p |
| 2027 | 9V-0-9V 1 amp | £2.30 | P & P 45p |
| 2028 | 12V-0-12V 1 amp | £2.99 | P & P 55p |
| 2029 | 15V-0-15V 1 amp | £3.16 | P & P 66p |
| 2030 | 30V-0-30V 1 amp | £3.97 | P & P 86p |

| STANDARD MAINS Primary 240V | | | |
|-----------------------------|---------|-------|-----------|
| No. | Rating | Price | |
| 2031 | 1/2 amp | £3.91 | P & P 86p |
| 2032 | 1 amp | £5.06 | P & P 86p |
| 2033 | 2 amp | £6.27 | P & P £1 |


240V Primary 0-55V @ 2A Secondary £7.30 P & P £1

SPECIAL OFFER
 2042 240V Primary 0-20V @ 2A Secondary. By removing 5 turns for each volt from the secondary winding any voltage up to 20V @ 2A is easily obtainable. Ideal for the experimenter
 £1.50 P & P 86p

CASES AND BOXES

| INSTRUMENT CASES. In two sections, vinyl covered top and sides, aluminium bottom, front and back | | | | | |
|--|--------|---------|---------|-------|--|
| No. | Length | Width | Height | Price | |
| 155 | 8in | 5 1/2in | 2in | £1.73 | |
| 156 | 11in | 6in | 3in | £2.92 | |
| 157 | 6in | 4 3/4in | 1 3/4in | £1.79 | |
| | | | | | |

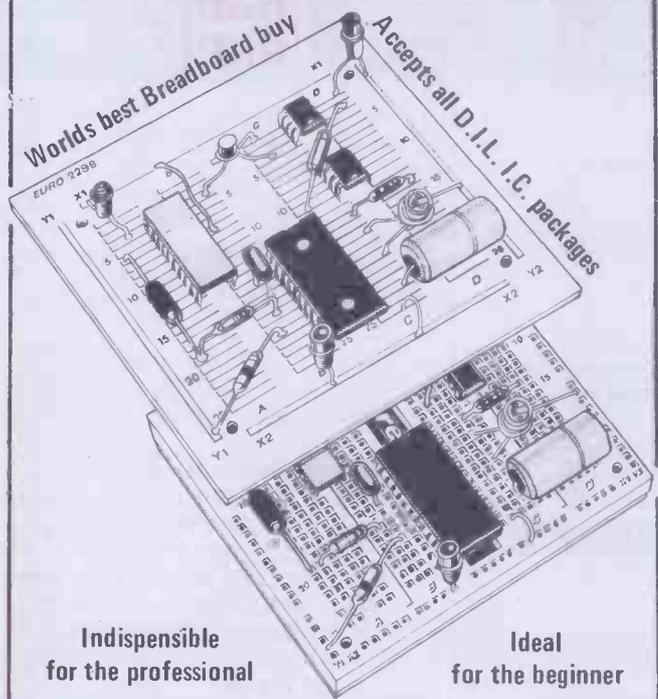First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-traced tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales, Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales, HE6

Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.

Please send me:-

- | | | | |
|-----------------------|----------|--------------------------|--------|
| 1 EuroBreadBoard | @ £ 6.20 | <input type="checkbox"/> | |
| or 2 EuroBreadBoards | @ £11.70 | <input type="checkbox"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="checkbox"/> | Tick |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="checkbox"/> | |


All prices are applicable from Jan. 1st 1980 and include VAT and PP but add 15% for overseas orders.

Name
Company
Address

Tel. No.
Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

GREENWELD

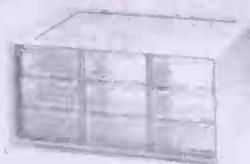443F Millbrook Road, Southampton SO1 0HX
All prices include VAT at 15% — Just add 40p post



COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors, diodes and i.c.s All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts!

All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 185mm with 9 drawers into which all parts can be neatly located.


If bought individually parts plus case would cost over £45 but we are offering this for ONLY £31.95 + £1 P&P. Simply send a cheque or PO for £32.95 for immediate despatch.

CONTENTS

- 200 1/4 watt resistors
- 20 Wire wound resistors
- 70 Ceramic Capacitors
- 70 Mylar Capacitors
- 50 Polyester Capacitors
- 56 Electrolytic Capacitors
- 61 Transistors
- 12 I.C.s
- 20 L.E.D.s
- 55 Diodes and rectifiers

Altogether 614 components

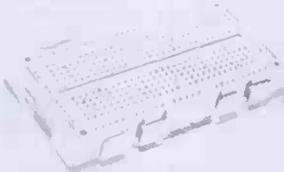Price includes current catalogue and Greenweld pen for reordering supplies. Plus free surprise gift.



VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocks can be joined together. Bus strips on X & Y axis — total 360 connection points for just £3.70.

VERO OFFCUTS

Packs of 100 sq ins of good size pieces about 4x2in. in the following types:
K5410 0.1in. copper clad £1.80
K544 0.1in. plain £1.80
Also pieces 2 1/2 x 1in. — 10/£1.20 100/£9. 17x3 1/4 in. x 0.1in. sheets, 10/£16.50

Large range of Standard Veroboard and boxes/cases in stock. Details in Catalogue.

SCOOP!!! Verobox type 2522, unused but has 3 1/2 in. holes in one end and 1 1/2 in. hole in the other, so instead of £3.96, we are selling these at £1.85.

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC Buzzer, all metal construction. 50mm dia. x 20mm 70p.
Z402. Miniature type, Buzzer, 6, 9 or 12V, only 22x15x16mm. Very neat. 53p.
Z450 Miniature 6V DC motor, high quality type. 32mm dia x 25mm high, with 12mm spindle. Only £1.
W892 Heavy duty 12V relay, ideal for car use — single 15A make contact. Coil 25R 85p.
W890 DIL reed relay SPCO 2.4-10V 200R coil. Only £2.20.

COMPONENT TRAY

Attractive yellow tray 285x165x42mm with clear hinged lid and moveable compartments. Up to 19 can be made from dividers supplied. As an added bonus, a selection of new surplus components are included, all for the special low price of £3.95.

THE NEW 1980 GREENWELD CATALOGUE

FEATURES INCLUDE

- 60p Discount Vouchers
 - Quantity prices for bulk buyers
 - Bargain List Supplement
 - Reply Paid Envelope
 - Priority Order Form
 - VAT inclusive prices
- All for only 40p + 20p post

EX-COMPUTER PANELS

Z528 Pack of boards containing 100s Rs. Cs diodes, including at least 50 transistors. Only £1.20.

Z529 TTL pack — Panels with 74 series on, together with code sheet. From simple gates to complex counters. 20 ICs £1. 100 ICs £4.

SCR PANEL & REED PANELS

Z525 Contains 11 800mA 60V 2N5061 SCR's, 11 6V8 zeners, 11 1N4004 diodes + Rs, Cs etc. Only £1.00.

Z527 2 x 6V reed relays, 6x2S030 or 2S230 6x400V reeds, + Rs. Only 50p.

AERIALS

X901 Telescopic 8 section 970mm long extended. 175mm collapsed. Swivel joint. 2BA fixing hole in base. 75p.

X904 Ferrite rod 140mm x 9mm LW/MW/coupling coils, each independently moveable 64p.

X905 As above, but LW/coupling coil together on moveable former 65p.

VU METERS

V002 Twin type. 2 metres 40x40mm and driver board, supplied with circuit and connexion data £3.50.

V003 New type, just in. Twin type moulded in one piece, 80x40mm (no driver board but suitable circuit supplied) £2.50.

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!!! Almost all are marked with type number — almost all are full spec. devices. Some have bent leads. Over 30 different types have been found by us including 8C184/212/238/307/32B, BF196/7; ZTX107/8/9/34Z/450/550, etc. Only available as a mixed pack at £3 per 100, £7 per 250; £25 per 1000.

£1 BARGAIN PACKS

All packs £1 EACH, ANY 25 PACKS £22

| Pack No. | Contents |
|----------|---|
| K101 | 15 BC239B transistors |
| K102 | 15 BC349A transistors |
| K103 | 10 BC546B transistors |
| K104 | 18 BC182B transistors |
| K106 | 18 BC184L transistors |
| K107 | 18 BC213L transistors |
| K108 | 8 2N5060 thyristors 30V 0.8A T092 case |
| K109 | 15 BC114 transistors |
| K110 | 4 BD131 transistors |
| K111 | 4 BD132 transistors |
| K112 | 12 3A 100B reeds, wire ended |
| K113 | 30 DA02 reeds, 150V 0.5A |
| K114 | 15 XK6116 (BF 241) transistors |
| K115 | 18 SP1218 (2N3702) transistors |
| K116 | 10 MPSL01 NPN 140V T092 |
| K117 | 10 BF450 PNP TV IF amp transistor |
| K118 | 16 ME4101 NPN 60V AF low noise |
| K119 | 10 2N5401 NPN 160V T092 |
| K120 | 6 prs 2S096/2S8496 AF OP sim to AC128/176 |
| K121 | 20 7V5 400mW zeners |
| K122 | 10 VR525 25V 2.2W zener |
| K123 | 10 56V 1W zener |
| K124 | 50 02µF disc ceramic |
| K125 | 200 1k 5A 1/4W carbon film resistors |
| K126 | 100 3000pF 63V polystyrene preformed caps |
| K127 | 25 47µF 25V axial lead caps |
| K128 | 25 15µF 40V do |
| K129 | 8 AA113 diodes |
| K131 | 10 VA1086 thermistor |
| K133 | 20 3-way 5A term blocks |
| K134 | 50 unmarked unused OC71 transistors |
| K135 | 30 0.7µF 10V radial elects |
| K136 | 4 AC187k transistors |
| K137 | 5 18µF 100V non-polarised caps |
| K138 | 30 1/4" coil former with slug |
| K139 | 40 .025µF 50V mylar caps |
| K140 | 30 .05 do |
| K141 | 40 0.01µF 400V axial caps (C296) |
| K142 | 25 wire ended neons std size, 90V |
| K143 | 200 squares mica insulation 25mm sq. |
| K144 | 30 1RS 3W wirewound resistors |
| K146 | 25 330µF 4V axial caps |
| K148 | 30 transformer former type X228 |
| K149 | 12 Ferrite rod type X038 |
| K150 | 10 switches type W430 |
| K151 | 12 0.125" red LEDs |
| K152 | 10 0.2" red LEDs |
| K154 | 15 5-pin 180° Din socket, clip fix |

The Egg Timer

HE proudly present the ultimate Egg Timer. Shake it and set it down, you can have either soft or hard-boiled. Yes folks it's all here — don't delay, build it today. . . .

OKAY, so you've got an egg timer. Odds on it's nothing like this one!

Conventional egg timers — the coloured-granules-in-a-three-minute-hour-glass variety — do their job efficiently, but silently. You have to watch them to see when your egg is ready. Either you stand and stare at it for the duration or you need sharp wits to instinctively 'know' when the time's up. Lack of audible indication on conventional egg timers is a consequence of inadequate design. Lack of sharp wits in the morning is a consequence of soft living.

This project tackles the first problem, the second is up to you!

FEATURES

Conventional egg timers (even electronic ones we've seen) lack the option of 'hard' or 'soft' timing. Even if the electronic ones have an audible indication, they have the disadvantage of including an on/off switch.

This egg timer project includes the hard/soft option, does not include an on/off switch and 'bleats' when your egg is ready. We could have had it go 'cluck, cluck'

or even 'cock-a-doodle-doo', but considered this a little *too* corny, and besides, it complicated the project unnecessarily!


Operation is very simple. First, you pick it up and shake it — the device lets you know with a soft bleep when it's been shaken enough. You then put it down on one end. Which end depends on whether you want a long time period (for a hard egg) or a shorter period (for — you guessed it — a runny one). After the appropriate period has elapsed the timer will issue a one second-long bleat and turn itself off until shaken awake again.

Has it got a microprocessor inside?

No, it's all done with one CMOS IC, a couple of transistors and fifty pence worth of mercury switch.

CONSTRUCTION

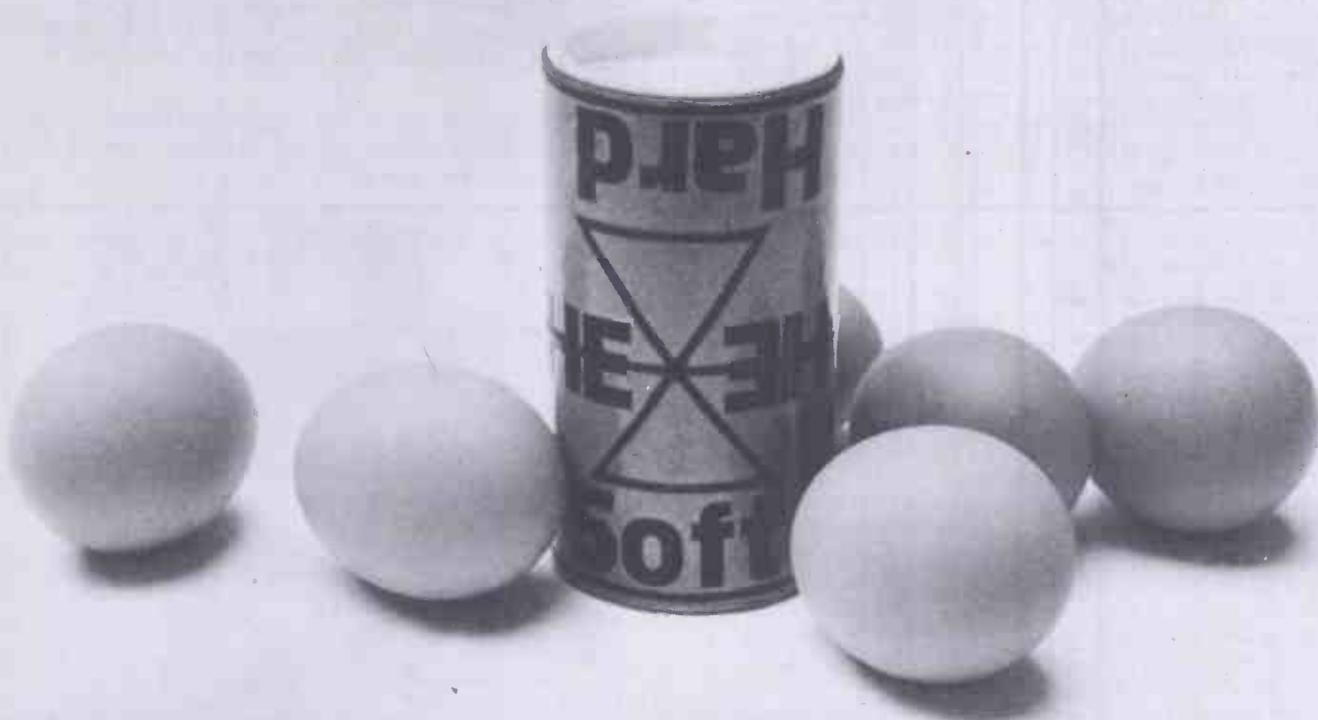The project is best constructed on the printed circuit board designed for it. Be sure to get the IC, transistor and diodes correctly oriented when inserting the components in the board. Take care also with the electrolytic capacitors.



Egg Timers come and go but now, with the HE Egg Timer at your disposal, you need never suffer from runny or hard-boiled eggs again. A quick shake is all you need, perfect eggs every time.

Parts List

RESISTORS (All 1/4W, 5%)

| | |
|----------|------|
| R1 | 2M2 |
| R2 | 4M7 |
| R3 | 1M8 |
| R4 | 1k |
| R5 | 1M5 |
| R6 | 4k7 |
| R7 | 22k |
| R8 | 100k |
| R9 | 10k |
| R10 | 1k8 |
| R11, R12 | 4k7 |
| R13 | 470k |

CAPACITORS

| | |
|----|------------------------|
| C1 | 10 μ 16 V tantalum |
| C2 | 220n ceramic |
| C3 | 1 μ 16 V tantalum |
| C4 | 47 μ 16 V tantalum |
| C5 | 47 μ 16 V tantalum |
| C6 | 10 μ 16V tantalum |
| C7 | 47 μ 16V tantalum |

SEMICONDUCTORS

| | |
|--------|------------------|
| D1-D6 | 1N914 or similar |
| Q1, Q2 | BC184 |
| IC1 | CD4049 |

MISCELLANEOUS

| | |
|----------------------------------|--|
| B1 | 9 volt, battery (PP3 or similar) |
| BZ1 | piezo electric buzzer (6 V operation) |
| SW1 | Mercury switch (see Buylines) |
| Suitable box, PCB, Battery Clip. | |

Buylines

None of the components should be difficult to obtain. The buzzer is a solid-state, piezo-electric device and is obtainable from Watford or Maplin. The mercury switch is available from Watford Electronics.

If you wish to copy our design you will need a cardboard mailing tube with end caps. We used a tube with 2in. diameter. Cut a length of about 6in. and paint it in polyurethane varnish to prevent it peeling. Find a scrap of PCB material and cut it to fit inside the tube, i.e. 6in. x 2in. The PCB is then attached to this board along with the buzzer and battery — see pictures for details. If you want to increase the volume of the buzzer you can cut a few holes in the side of the tube.

ADJUSTMENTS

If you like your eggs super hard — or perhaps extremely runny, or even somewhere between these extremes, the time periods may be changed by altering the value of R2 or R3 — one will alter the softness of the 'hard' egg, the other the density of the 'soft' egg. See 'How it Works' for an explanation of the circuit operation.

HE

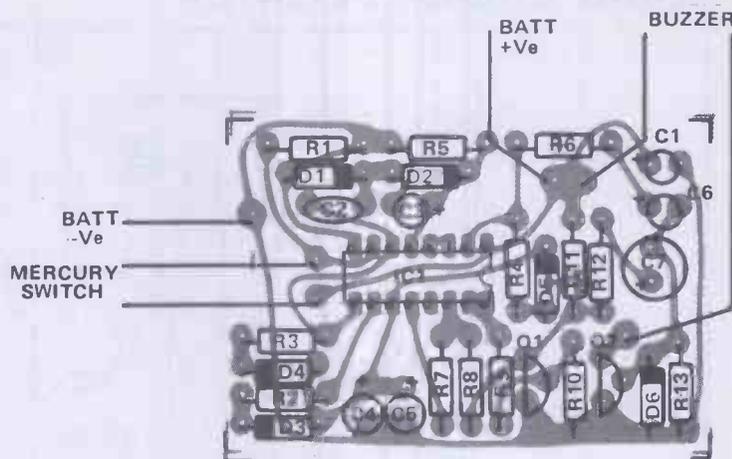


Fig. 2. Above — Overlay diagram of the Egg Timer. As usual take care when inserting polarised components.



The HE Egg Timer in its 'swish' case made from a cardboard mailing tube. All the components fit neatly onto the main board.


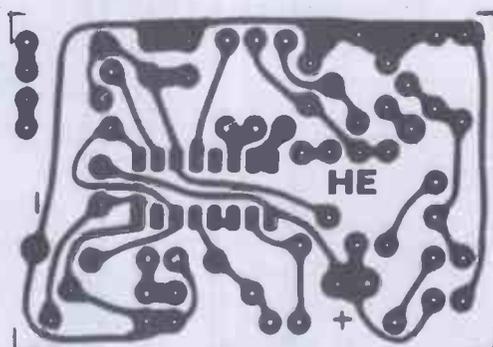


Fig. 3. PCB foil pattern. The design will shortly appear as a HOBBYPRINT rub-down transfer. If you've never used HOBBYPRINTS before then see the ad in this issue. First class results guaranteed every time.

Short Circuit

LIGHT CHANGE DETECTOR

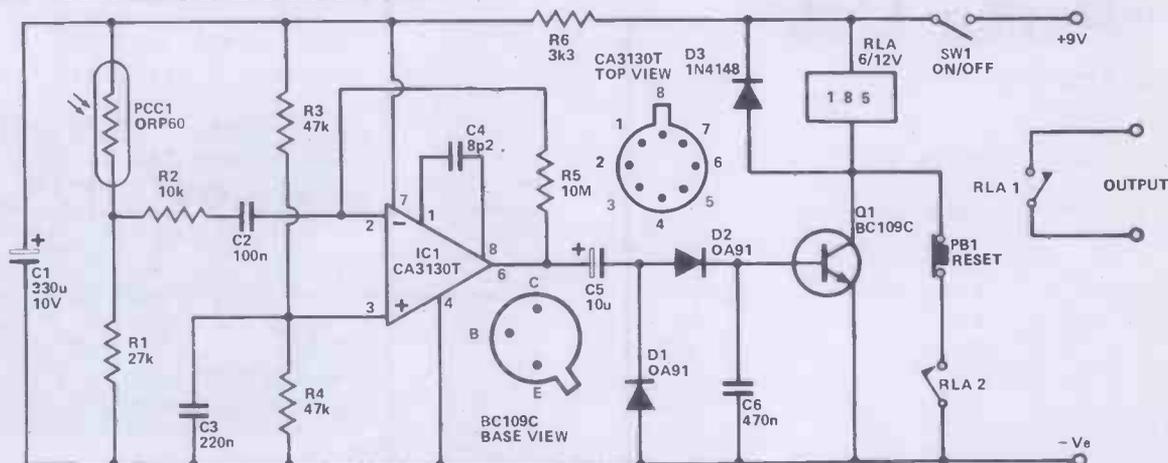

This simple light activated switch can be employed in intruder alarm systems, or in certain other applications where a proximity detector is required. It is not a light operated switch of the type which responds to some particular ambient light level, but instead, it responds to rapid changes in light level. It will, for example, trigger if a torch is shone on or near the photocell, or if someone passing in front of the unit casts a shadow onto the photocell. The unit is unaffected by natural, slow changes in light level.

The photocell used in the unit

is cadmium sulphide photo-resistor, PCC1, and together with R1 this forms a potential divider connected across the supply lines. The voltage at the junction of R1 and PCC1 depends upon the resistance of PCC1, which in turn depends upon the light level to which this component is subjected.

IC1 is an operational amplifier which is used here in the inverting mode. R2 and R5 form a negative feedback network which set the voltage gain of the circuit, and a high degree of gain is required in order to give the unit good sensitivity. The gain of the

amplifier is approximately equal to R5 divided by R2, or about 1,000 times (60dB.) in other words. The output from PCC1 and R1 is coupled to the input of the amplifier, but C2 provides DC blocking here, so that the DC output from these components is of no consequence. However, rapid changes in the output voltage from the photocell circuit will be passed to the input of the amplifier, and will appear greatly boosted at the output.

The output from IC1 is coupled by C5 to a smoothing and rectifier circuit consisting of D1, D2, and C6. When the unit is

activated, the positive bias produced across C6 is sufficient to bias Q1 into conduction, so that it energises the relay coil which forms its collector load. RLA2 then closes and maintains the supply to the relay coil, so that once triggered the circuit latches in the on state. The alarm or other controlled equipment is operated by RLA1.

SW2 can be used to break the supply to the relay, and thus reset the circuit. SW1 is merely the on/off switch. C4 is the compensation capacitor for IC1 and D3 is the normal protective diode. Current is 1.40mA.

EX-STOCK ONLY FROM US

J.V.C. BELT DRIVEN TURNTABLE

WITH STEREO MAGNETIC **FREE** CARTRIDGE



LIST PRICE OVER £50

J.V.C. Turntable supplied complete with Audio Technica AT10 stereo magnetic cartridge.

- * 'S' shaped tone arm.
- * Belt driven. Modern design
- * Full size 12" platter.
- * Precision calibrated counter balance weight (0.3 grms).
- * Anti-skate (bias) device. Nylon thread weight.
- * Cut-out template supplied. Size - 12 3/4" x 15 3/4" (approx.)

LIMITED STOCKS AT ONLY £25.99

PLUS VAT £3.89 Post £2.50

GEC HIGH QUALITY STEREO

10 + 10 watt AMPLIFIER WITH AM/FM STEREO TUNER IDEAL FOR THE HOME

A cancelled export order brings you this offer from the world-famous firm of G.E.C.

AM/FM Stereo Tuner Amplifier
Ready built, comprising of a tuner/pre-amp. board, and separate power supply/power amp. board.
Note: Interconnection wiring diagram supplied.
Rotary Controls: Tuning, on/off volume, balance, treble, bass, Stereo Beacon Indicator.
Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), LW, MW, SW.

Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.
Frequency Response: 60Hz-20KHz within ± 3dB.
Tape Sensitivity: Output - typically 150 mv. Input - 300 mv for rated output.
Disc Sensitivity: 100 mv (ceramic cartridge)
Radio: FM (VHF) 87.5MHz-108MHz.
Long Wave 145KHz-265KHz.
Medium Wave 520KHz-1620KHz.
Short Wave 5.8KHz-16MHz.
Size: Tuner - 2 1/4in. x 1 1/2in. x 7 1/4in. Approx. Power Amp - 2in. 7 1/4in. x 4 1/4in. Approx.



ON/OFF BALANCE TREBLE, BASS, MONO TAPE Phono AFC FM LW MW SW Tuning. Volume

Fully Guaranteed Ex-Stock

SUITABLE PAIR £19.95
SPEAKERS 10 WATTS INC. VAT

POST £2.50 Pair

ONLY £19.95
+ VAT £2.99
CARRIAGE £2.50

CAR STEREO CASSETTE MECHANISM made for MOTOROLA



- * Front loading 12 volt transistorised
- * Speed & Voltage control

- * Limited stocks
- * Size

ONLY £7.50
INC. VAT
POST 80p



HENRY'S

Phone (01) 723 1008/9
404 Edgware Road, London, W2, England



£1 BRINGS YOU

OUR 100-PAGE CATALOGUE

Reader Services

Backnumbers

June 79 Vol 1 No 8

PROJECTS: GSR Monitor, Envelope Generator, Drill Speed Controller.

FEATURES: Citizens Banned, Display Techniques, Electronics in Music.

July 79 Vol 1 No 9

PROJECTS: Shark, Baby Alarm, Points Controller, Linear Scale Ohmmeter.

FEATURES: Cassette decks and tapes, Binary Numbers, Fixed Resistors.

August 79 Vol 1 No 10

PROJECTS: Home Security System, LED Tacho, Injector/Tracer, CV Amp.

FEATURES: Security Installation, Variable Resistors, Tools, Satellite Power.

September 79 Vol 1 No 11

PROJECTS: Combination Lock, Light Dimmer, Starburst, Ultra Switch.

FEATURES: Electronic Timekeeping, Thyristors, Radio Control, FET Special.

October 79 Vol 1 No 12

PROJECTS: Tantrum, Hobbytune, Analogue Frequency Meter, Multi-Siren.

FEATURES: Home Computing, Electronic Games, Microwave Cooking.

December 79 Vol 2 No 2

PROJECTS: Saxelextric Controller, Ring Modulator, Bar Graph Voltmeter, HEBOT III.

FEATURES: TV Receivers, Project Fault Finding, Data Supplement.

January 80 Vol 2 No 3

PROJECTS: HEBOT III, Laser Crosshatch, Digi-Die.

FEATURES: Mini TV Survey CMOS Special, Spacelab.

February 80 Vol 2 No 4

PROJECTS: Passionmeter, Infra-Red Remote Control, Win Indicator.

FEATURES: Short Circuit Special, KEZY Does it, Power to the People.

March 80 Vol 2 No 5

PROJECTS: SW Radio, 25 Watt Module, PSU Module, Touch Switch.

FEATURES: Electronics on Wheels, PETting it Together.

April 80 Vol 2 No 6

PROJECTS: Hobbycom, CD Ignition, R/C Motor Controller, Frequency Meter.

FEATURES: NBTV, Solar Cells, Into Constructional Electronics.

Shown here are all of the back issues currently available. Each issue costs £1.00. (Surface mail anywhere in the world) Please specify the

Volume and issue number you require on the coupon below and send it, together with your remittance to:

Sales Office (Backnumbers), 145 Charing Cross Road, London WC2H 0EE

Hobbyprints

| | | |
|-------------------|-------------------|-----------------------|
| NOV 78 A 95 pence | MAY 79 G 95 pence | NOV 79 M 95 pence |
| DEC 78 B 95 pence | JUN 79 H 95 pence | DEC 79 N * (see note) |
| JAN 79 C 95 pence | JUL 79 I 95 pence | JAN 80 O * (see note) |
| FEB 79 D 95 pence | AUG 79 J 95 pence | FEB 80 P 95 pence |
| MAR 79 E 95 pence | SEP 79 K 95 pence | MAR 80 Q 95 pence |
| APR 79 F 95 pence | OCT 79 L £1.20 | APR 80 R 95 pence |

HOBBYPRINTS are the easiest way to make perfect PCBs every time. Simply place the transfer sheet over a cleaned, sized piece of PCB material and transfer the design by gently rubbing with a soft pencil. Once the pattern is safely in place immerse the board in a solution of

Ferric Chloride. From beginning to end should take no more than 15 minutes.

To order your **HOBBYPRINTS** write the appropriate code letter in the coupon below and send it, together with your remittance to:

Sales Office (HOBBYPRINTS), 145 Charing Cross Road, London WC2H 0EE.

*Please Note.

Print N is in two parts.
(a) All projects except HEBOT.
(b) HEBOT. (a) is 95 pence,
(b) is 45 pence.

Print O is in two parts.
(a) Lap Counter and PSU.
(b) Digi-Die, HEBOT Loop
Drive, Crosshatch Gen.

Subscriptions

As you can see from our Backnumbers ad, copies of HE sell out very quickly indeed. To avoid disappointment why not take out a postal subscription to HE? It costs

just £9.00 for one year. This covers postage for mainland UK and surface mail overseas. (Airmail rates on request) Send coupon below to:

SUBSCRIPTIONS, Hobby Electronics, PO Box 35, Bridge Street, Hemel Hempstead, Herts.

BACKNUMBERS

Please supply the following Backnumbers.....

Enclosed £.....
Name.....
Address.....

HOBBYPRINTS

Please supply me with Hobbyprint(s).....

Enclosed £.....
Name.....
Address.....

SUBSCRIPTIONS

I would like a postal subscription with HE commencing with the..... issue.

Enclosed £.....
Name.....
Address.....

Beasties

THOUGHT FOR THE MONTH:-
 THYRISTORS TURN ME ON -
 BUT THE NATIONAL GRID
 KEEPS ME GOING !!



RA '80

Beasties

WE HAD TO ABANDON THE
 WAVE ENERGY PROJECT.

THE POWER WE GENERATED
 WAS SO DAMP IT MADE ALL
 THE ELECTRICAL GEAR GO
 RUSTY !!

WHY?



RA '80

VARI WIPE

WIPER DELAY CONTROL

The Vari Wipe provides intermittent operation of the windscreen wipers with adjustable control to delay each wipe between 3 and 60 seconds. Set the control to suit the conditions to clear light drizzle, fog, snow, sleet or spray. Easily fitted to British, Continental & Japanese cars with 12 volt self park wipers. Complete kit contains all components, including timer chip, PCB, case, mounting panel, wire, etc., with full instructions.

VARI WIPE KIT £6.75 inc. P & P
ASSEMBLED £9.25 inc. P & P

or send large s.a.e. for details

Spimin DEVELOPMENTS
 Dept HE 3
 Card Holders Phone 0253 27244

FREEPOST Thornton Cleveleys, Blackpool FY5 2BR

OHIO SCIENTIFIC Superboard 2 Assembled 50 Hz model **£159.95** + 15% VAT post free. Colourboard 2 (the new colour version of Superboard 2) **£205** + 15% VAT.

★ Special offer: - If bought with Superboard or Colourboard these items are at the reduced price show first. ★

★ Also sold separately at the bracketed prices. Add 15% VAT. Modulator and power supply kit **£5.95** (E9.95). 4K extra ram **£19** (E24). Case **£19** (E21). ★

★ Cassette recorder **£13** (E15). ★

SINCLAIR PRODUCTS New 10MHz scope **£145**, pm200 **£51.95**, case **£2.07**, adaptor **£4.20**, connector kit **£13.95**. Microvision TV **£89**, adaptor **£8.88**, pm25 **£34.28**, adaptor **£4.20**, case **£2.07**. dm350 **£76.70**, dm450 **£102.17**, dm235 **£55.55**, rechargeable batts. i:8, adaptor **£4.20**, case **£9**. Enterprise prog. calculator + accessories **£19.95**.

COMPUTER GAMES Chess Champion 8 **£49.95**, Chess Challenger 7 **£84**, Philips G7000 home computer **£139**, Videopaks **£12.95**. Atari videocomputer **£129**. Cartridges **£14.85**. **COMPONENTS** 1N4148 0.9p. 1N4002 2.9p. 741 18p. bc182, bc184, bc212, bc214, bc648 **£5.5p**. Resistors 1/4W 5% £12 10R to 10M 1p, 0.8p for 50+ of one value. 16V electrolytics: 5, 1.2, 5, 10, 22mf 5p, 100mf 6p, 750mf 10p, 11b FeCl **£1.50**. Oalo pen 84p, 40 sq. ins. pcb 48p. Polystyrene capacitors **£12.63V** 10 to 1000pf 3p, 1n2 to 10n 4p. Ceramic capacitors **50V** **£6.22pf** to 47n 2p. Zeners 400mV **£24.2v** to 33v 7p.

TV GAMES AY-3-8500 + kit **£10.21**. AY-3-8600 + kit **£17.28**. Stunt Cycle chip + kit **£18.66**. AY-3-8603 chip **£13.63**.

TRANSFORMERS 6-0 6V 100ma 30p, 1 1/2a **£2.60**, 9-0 9V 75ma 80p, 1a **£2.40**, 2a **£3.94**, 12-0-12V 100ma **99p**, 1a **£2.90**.

IC AUDIO AMPS with pcb JCI12 6W **£2.08**, JC20 10W **£3.54**.

BATTERY ELIMINATORS 3-way type 6 7/7 1/2 9v 300ma **£2.84**, 100ma radio type with press-studs 5v **£3.57**, 9+9v **£4.79**. Car Converter 12v input, output 4 1/2 / 6 7/7 1/2 9v 800ma **£2.66**.

BATTERY ELIMINATOR KITS 100ma radio types with press-studs 4 1/2 v **£1.49**, 6v **£1.49**, 9v **£1.49**, 4 1/2 + 4 1/2 v **£1.92**, 6+6v **£1.92**, 9+9v **£1.92**. Stabilised 8-way types 3 1/4 v / 6 7/7 1/2 9v / 12 / 15 / 18v 100ma **£2.60**, 1Amp **£6.50**. Stabilised power kits 2-18v 100ma **£2.60**, 1-30v 1A **£6.75**, 1-30v 2A **£12.10**. 12v car converter 6 7/7 1/2 9v 1A **£1.35**.

T-DEC AND CSC BREADBOARD s-dec **£3.79**, t-dec **£4.58**, u-dec **£4.69**, u-dec **£7.16**, exp4b **£2.64**, exp30 **£6.61**, exp350 **£3.62**, exp325 **£1.84**.

BI-PAK AUDIO MODULES s450 **£25.06**, AL60 **£5.06**, pa100 **£17.33**, spm80 **£4.74**, bmt80 **£6.08**. Stereo 30 **£21.57**, AL30A **£4.08**.

SWANLEY ELECTRONICS
 Dept. HE, 32 Goldsel Rd., Swanley, Kent
 Post 35p extra. Prices include VAT unless stated.
 Official and overseas orders welcome. Lists 27p post free. Mail order only.

IONISER KIT

The Ioniser produces large quantities of negative ions in the air which many people find stimulating and refreshing. Price **£10**. Accessories and a case can be supplied as an optional extra.

H.E. KITS

- Crosshatch Generator Jan 80 **£11.25**
- Digi-Die Jan 80 **£5.50**
- Passionmeter Feb 80 **£5.00**
- Infra-red Remote Control Feb 80 **£19.35**
- Electronic Ignition April 80 **£18.25**

- INTERSIL**
- 3 1/2 Digit Meter Kit with P.C.B. **£21.00**
- I.C.L. 7106 EV (L.C.D.) **£18.50**
- I.C.L. 7107 (L.E.D.) **£18.50**

Callers please ring first to check availability of kits. C.B. C.B. C.B. Enthusiasts please let us know the I.C.'s, Transistors, etc., that you require. Orders. Please add 30p post and packing. Add 15% V.A.T. on total order.

T. POWELL

306 St. Paul's Road, Highbury Corner, London, N.1
 Telephone: 01-226 1489
ACCESS / VISA ACCEPTED
 Shop open: Mon. to Fri. 9-5.30; Sat. 9-4.30

JAY KIT DM-2

DIGITAL MULTIMETER
 DC Volts
 1mV to 1000V
 Ac Volts 1V to 500V
 DC Current
 0.1mA to 0.2A
 Resistance 1 to 20M
 3 1/2 digit LCD
 Auto low battery indication,
 Auto Polarity and Zero
 1% accuracy (DC volts)
 Designed around Intersil 7106C
 Includes cabinet and all parts
£27.30
 P&P £1.00 Add 15% VAT.



- Hobbscom April 80 **£28.60**
- Digital Frequency Meter **£27.75**
- R/C Speed Controller April 80 **£9.60**
- Kits supplied with PCB and case.

- Miniclock May 80 **P.O.A.**
- 5080 Preamp May 80 **P.O.A.**
- Track Cleaner May 80 **P.O.A.**

E PROMS

Surplus to requirements
 2708 **£5.00** each
 4716 **£25.00** each

Parts sent by return.
 Programming Service if required.
 Please add VAT (15%) and 30p P&P

BARINGLOCK LTD.

31 Ashdown Avenue
 Saltdean, Brighton
 Telephone: 01-686 1922

VMOS POWERFETS

- VMP4 (25W, 10dB at 200MHz, min.) **£12.50**
- VN67AF (15W, 2A, TO202) **75p**, 10 + **70p**
- VN10KM (1W, 1/2A, TO92) **55p**, 10 + **50p**
- BD512 (P-chan, 10W, 1 1/2A, TO202/3) **85p**, 10 + **80p**
- Heat clips, TO202 **12p**, TO92 **8p**. VN / VM Design Cat. **20p**
- TL081CP **29p**, 10 27p, 25 25p. TL082CP **55p**, 10 50p, 25 25p.

- CA3026 **70p**, 709C **15p**
- CA3080E **70p**, 710N **25p**
- CA3140E **38p**, 733N **50p**
- 2102 **80p**, 741 **18p**
- CD4011B **17p**, 78L05 **29p**
- 555 **25p**, 78L12 **29p**
- "MC1458" (unmarked, 100% good) **20p**
- Mini mains transformer 6v-0-6v, 100mA **75p**

6 WATT SIREN
 Modified design with touch control option and improved tone. Circuit, VN67AF and all components (excluding switch, board and speaker) **140p**

VOLTAGE CONTROLLED AMP
 0dB to more than 80dB attenuation. Fast slewing, very low distortion. All components and circuit **225p**

Brief data on everything in new lists. S.A.E. P&P 30p. Mail order only. Prices inc. Tel. 01-800 6667

J. W. RIMMER

367 GREEN LANES
 LONDON N4 1DY

Hobby Chit~Chat

In this month's 'Chit-Chat' Ray Marston takes a look at LEDs and LED displays

ONE OF THE MOST POPULAR types of project amongst the readers are LED display circuits, in which one or more LEDs (light-emitting diodes) repeatedly turn on and off in some pre-determined sequence and thereby generate a visually interesting pattern. These projects are so popular that we've decided to devote the whole of this month's 'Chit-Chat' feature to the topic and to present a variety of practical 'display' circuits.

BASIC LED CHARACTERISTICS

The most obvious thing about a LED is that it glows a pretty colour (either RED, ORANGE, YELLOW or GREEN) when current is passed through it. The brilliance of the glow increases with the current magnitude. In most practical applications, currents of 10 to 30 mA give adequate illumination. Approximately 2 volts are generated or 'lost' across the LED when it is passing forward current.

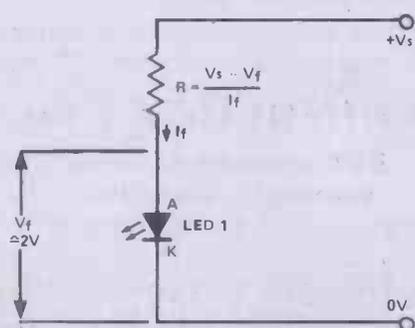


Fig. 1. Method of working out the 'R' value for a given V_s and I_f .

When you use a LED, you have to wire some form of current-limiting device in series with it, to set its operating current to the correct level. Fig 1 shows how to work out the value of resistance needed to give a particular current from a specific supply voltage. In practice, 'R' can be connected in either the anode or the cathode side of the LED.

You can use a LED as an indicator in an AC circuit by wiring a diode in inverse parallel with it, as shown in Fig 2, to prevent the LED being reverse biased. For a given brightness, the value of 'R' should be halved relative to that of a DC circuit.

One practical problem that you'll encounter when

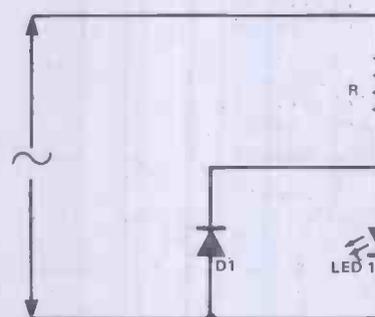


Fig. 2. Method of using a LED as an indicator in an AC powered circuit.

using a LED is that of identifying its polarity. Most LEDs have their cathode (K) identified by a notch or flat on the package, or by a short lead. This practice is not universal, however, so the only sure way to identify a LED is to test it in the basic circuit of Fig. 1. Try the LED both ways round: when it glows, the cathode is the most negative of the two terminals. It is always good practice to test a LED before soldering it into circuit. It is also good practice to check the LED's forward voltage, which should be less than 2.5 volts: a greater value than this indicates an 'out of spec' or second grade device.

If you ever need to drive a number of LEDs from a single source, note that this can be achieved by wiring a number of LED's in series, as shown in Fig 3. Note that the supply voltage used here must be significantly greater than the sum of the individual LED forward voltages. This circuit thus draws minimal total current, but is limited in the number of LEDs that it can drive. A number of these circuits can, however, be wired in parallel, so that almost any number of LEDs can be driven from a single source.

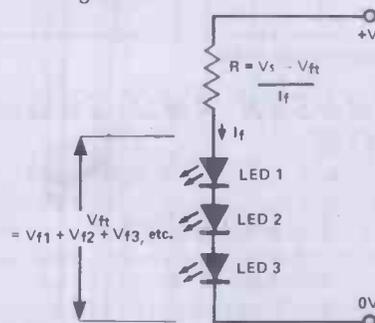


Fig. 3. Method of working out 'R' with LEDs in series.

4-LED circuit of Fig 8. Alternatively, the circuit can be made to give an intermittent display with a controlled number of 'off' steps by simply taking the appropriate one of the 'unwanted' outputs to the pin-15 RESET

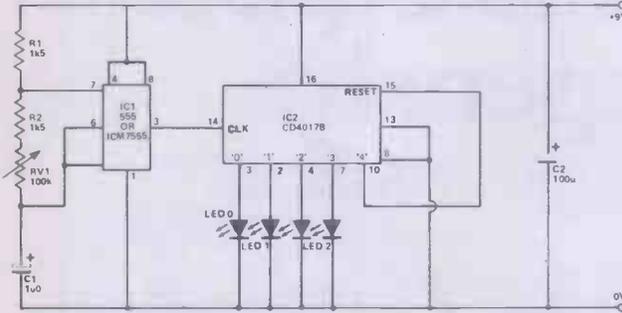


Fig. 9. 4-LED continuous Moving-dot display.


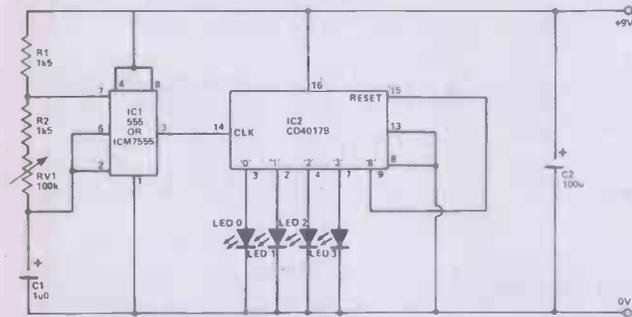


Fig. 10. 4-LED Intermittent Moving-dot display with 50% blank period.

terminal. In fig 9, for example, the LEDs 'display' for four steps and then 'blank' for four steps, after which the sequence repeats.

Finally, Fig 10 shows a rather unusual and very attractive 4-LED 5-step sequencer, in which all four LEDs are initially on but then turn off one at a time until eventually (in the 5th step all four LEDs are off: sequencing details are given in the table of Fig 11. Note in this circuit that the LEDs are effectively wired in series and that the basic circuit can not be used to drive more than four LEDs.

HE

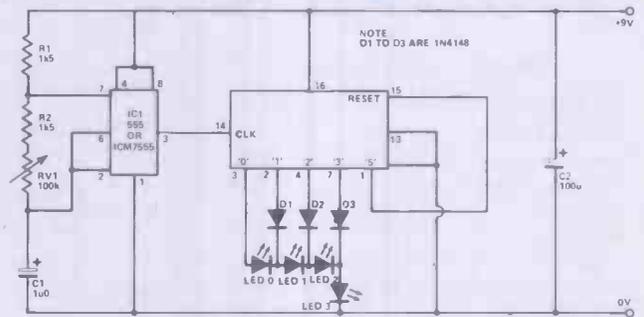

| | | | | | | |
|-------|-------------|-----|-----|-----|-----|----|
| LED 0 | ON | OFF | OFF | OFF | OFF | ON |
| LED 1 | ON | ON | OFF | OFF | OFF | ON |
| LED 2 | ON | ON | ON | OFF | OFF | ON |
| LED 3 | ON | ON | ON | ON | OFF | ON |
| | STEP NUMBER | | | | | |
| | 1 | 2 | 3 | 4 | 5 | 1 |

Fig. 11. Circuit and performance table of a 4-LED, 5-step sequential turn-off display.

WEST HYDE CASES FOR H.E. PROJECTS

- Power Supply Unit (May 1979) Order Code SWF 222L
- Digibell Project (May 1979) Order Code MIN 020 +020A
- Baby Alarm (July 1979) Order Code BOC 440
- Scalextric Lap Counter (January 1980) Order Code BOC 670
- Crosshatch Generator (January 1980) Order Code SAM 003
- System 5080A Amplifier Module (March 1980) Order Code ACE 100K
- System 5080A Power Supply (March 1980) Order Code MD4 01K
- Hobby Com (April 1980) Order Code PRB CTB1

PLEASE SEND FOR OUR FREE
80-PAGE CATALOGUE & PRICE LIST

SYSTEM 5080 PRE-AMP (MAY 1980). ORDER CODE ACE 300K.
L.C.D. CLOCK (MAY 1980). ORDER CODE BOC 706B.
CAR POWER BOOSTER. (JUNE 1980). ORDER CODE ACE 100K.

THE BIGGEST SELECTION OF CASES IN EUROPE



WEST HYDE

WEST HYDE DEVELOPMENTS LIMITED, UNIT 9, PARK STREET INDUSTRIAL ESTATE, AYLESBURY, BUCKS. TEL: 0296 20441

All the reliability, accuracy and style you would expect from the most expensive watches.

Metac have become synonymous with quality and extreme good value.

We are particularly proud of this reputation and preserve it by meticulously selecting and carefully checking every product we sell.

Our customers are consequently guaranteed a stylish, accurate and reliable timepiece which should cost considerably more than Metac's special offer prices.

24 hour despatch. This is another unique Metac service.

We don't believe, unlike other companies, that you really want to

wait 28 days for your watch, so we have opened a special 24 hours despatch centre.

The centre now guarantees that every order received by 3.30pm will be safely and securely on its way back to you the same day.

Guarantee. Every watch is guaranteed for one year.

And, as with all Metac products, we will be pleased to refund your money if you are not completely satisfied with the watch, and return it within 10 days.



Credit card holders may telephone 03272 76545 or (01) 723 4753 and place orders immediately, without completing the coupon.



M18 £15.95 inc p&p
Ladies quartz LCD Fashion Watch



M64 £14.95 inc p&p
Mans dual time quartz alarm chronograph with 6 digits, 5 indicators and 22 functions.

M18 Ladies quartz LCD Fashion Watch

Highly functional, but beautifully designed watch, suitable for those special occasions.

Displaying hours, mins, secs, day and date, the watch also has an auto calendar and a backlight.

The slim but strong bracelet is fully adjustable and is available in a silver or gold finish.

M64 Mans dual time quartz alarm chronograph with 6 digits, 5 indicators and 22 functions.

For business people with overseas contacts and responsibilities this is the ideal watch.

Local time is always visible, but in addition the watch can be set, and recall, a second time zone, in either 12 or 24 hour formats, and displays a day and date for each zone.

The chronograph/stopwatch displays up to 12 hours, 59 minutes and 59.9 seconds.

On command, the stopwatch display freezes to show intermediate (split/lap) time while the stopwatch continues to run and neither function affects the normal timekeeping.

The alarm can be set to any time within a 24 hour period.

To complete the functions, there is also a 4 year calendar and a fully adjustable stainless steel strap.



M15 Ladies quartz LCD Day Watch

This slender watch displays hours, mins, secs, day and date and has an auto calendar and a backlight.

Only 25mm X 20mm X 6mm thick this elegant watch has a bracelet, in silver or gold finish, and is fully adjustable to suit very slim wrists.

£9.95 inc p&p



£13.95
inc p & p

M17 Ladies quartz LCD Cocktail Watch

Only 6mm thick, the watch displays hours, mins, secs, day, date and has an auto calendar and backlight.

The fully adjustable bracelet has a bronze/gold or silver finish.



£19.95
inc p & p

M30 Mens dual time melody alarm chronograph with count-down timer, 34 functions

A very impressive new watch at a superbly low price and with so many useful functions.

There are 5 independent working modes; normal watch, count-down alarm, alarm, dual time zone, 1/100th sec. chronograph.

In addition, the watch can display the day of the week in French, German or English.

The count-down timer can be used for a variety of applications from boiling an egg to reminding you your parking meter time has expired. Both the count-down alarm and the normal alarm have a clear musical tone.

For the businessman the time zone feature could be a real advantage. Just programme the second time zone and it will be permanently recorded for easy reference.

And as a stop-watch here's a great timepiece for sporting events and for timing recordings.

There's the conventional stop/start counter plus a lap timer which enables first and second places to be timed.

Longer timing intervals, such as journey times can be recorded while the watch is reading its normal time.



Solar version
£12.95
inc p & p

M3 Mens quartz LCD with 6 digits and 11 functions

Only 7mm thick and with a fully adjustable stainless steel bracelet, this watch is ideal for all ages.

The normal functions are hours, mins, secs, day, date, and day of week.

But as a stop-watch, which does not affect normal timekeeping you also have 1/100th and 1/10th secs., split, lap and journey timing, a four year calendar and a backlight.

Also available is a solar version.

This is the same watch but incorporated is a solar energy panel which converts normal daylight into electricity.

During periods of darkness the watch instantly operates by battery without losing its accuracy.



£10.95
inc p & p

M4 Mens quartz LCD alarm with 6 digits and 9 functions

A very useful watch with an effective, loud alarm but still only 8mm thick.

The normal functions are hours, mins, secs, date, day of week, four year calendar and a backlight.

In addition, there is a 24-hour alarm, a 5-minute snooze feature and a 4 second pre-alarm conference bleep.

The conference signal is a bleep, 4 seconds before main alarm to give advance warning and the option to cancel.

After the main alarm stops the snooze repeater alarm sounds 5 minutes later, unless previously cancelled.

To complete the functions, there is also a 4 year calendar and a fully adjustable stainless steel strap.



Solar version
£18.95
inc p & p

£16.95
inc p & p

M16 Mens dual time quartz alarm chronograph with 6 digits, 5 indicators and 22 functions.

This watch has the same functions as M64 except the time is in the 24 hour format only.

A solar version is available.

This is the same watch but incorporated is a solar energy panel which converts normal daylight into electricity.

During periods of darkness the watch instantly operates by battery without losing its accuracy.

Metac

ELECTRONICS & TIME CENTRES

Callers may buy from our shops in:
London, 327 Edgware Rd, W2 Daventry, 67 High St, Northampton, St. Giles Square.

To: Metac Electronics & Time Centres,
24-hour Despatch Centre, 67 High Street,
Daventry, Northants.

Please send me the following watches:

Model No. Quantity Colour if applic.


I enclose PO/Cheque for £ _____

Barclaycard/Access No. _____

Name _____


Address _____

HE6

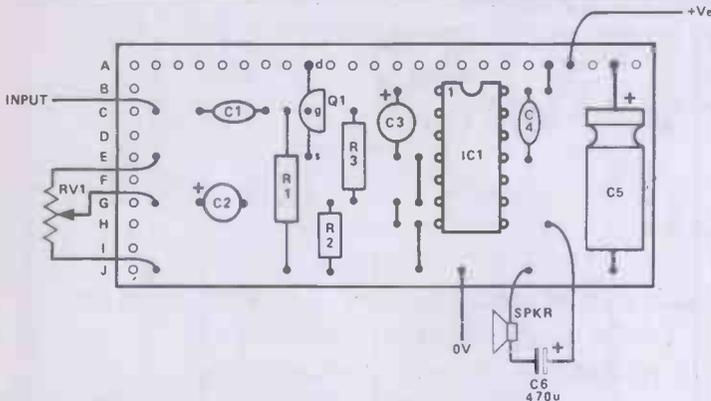

Above. Component insertion layout. Note the orientation of Q1 and IC1

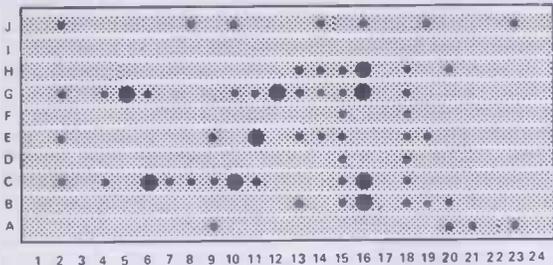Below. Underside of the Miniboard Amplifier. Ensure that cuts in the track are made in the correct places.



More Miniboards coming soon! Watch HE for details. If you have any suggestions for Miniboard circuits then why not let us know. **HE**

Parts List

RESISTORS (All 1/4W, 5%)

| | |
|----|-----|
| R1 | 10M |
| R2 | 15k |
| R3 | 10k |

POTENTIOMETER

| | |
|-----|---------|
| RV1 | 10k LIN |
|-----|---------|

CAPACITORS

| | |
|-------|------------------------|
| C1, 4 | 100n polyester |
| C2 | 1u0 25 V electrolytic |
| C3 | 10u 25 V electrolytic |
| C5 | 100u 25 V electrolytic |
| C6 | 470u 25 V electrolytic |

SEMICONDUCTORS

| | |
|-----|--------|
| Q1 | 2N3819 |
| IC1 | LM380N |

MISCELLANEOUS

| | |
|-------------|-----------------|
| Speaker | 8R0 |
| 1" x 2 1/2" | Veroboard panel |

Buylines

All the components used in this project are readily available

DISPLAY LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

DL1000K
This kit features a bi-directional sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.60**

DL2100K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**
Optional Opto Input **60p**



INTEGRATED CIRCUITS

| | |
|---|-------|
| 555 Timer | 21p |
| 741 Op. Amp | 18p |
| AY-5-1224 Clock | £2.60 |
| AY-5-1230/2 Clock/Timer | £4.50 |
| AY-3-1270 Thermometer | £8.20 |
| ICL7106 DVM (LCD drive) | £7.00 |
| LM377 Dual 2W Amp | £1.45 |
| LM3795 Dual 6W Amp | £3.50 |
| LM380 2W Audio Amp | 80p |
| LM382 Dual low noise pre-amp | £1.00 |
| LM386 250mW low voltage amp | 75p |
| LM1830 Fluid Level Detector | £1.50 |
| LM2907 f.v. Converter | £1.40 |
| LM2917 f.v. Converter | £1.60 |
| LM3909 LED Flasher/Oscillator | 55p |
| LM3911 Thermometer | £1.20 |
| LM3914 Dot/Bar Driver | £2.10 |
| MM74C91 14-digit display controller | £6.50 |
| MM74C915 7-segment-BCD converter | 96p |
| MM74C926 4-digit counter with 7-segment outputs | £4.50 |
| S5668 Touchdimmer | £2.50 |
| S9283 Touchswitch 16-way | £4.85 |
| SN76477 Complex Sound Generator | £2.52 |
| TBA800 5W Audio Amp | 85p |
| TBA810AS 7W Audio Amp | 85p |
| TDA1024 Zero Voltage Switch | £1.00 |
| TDA2020 20W Audio Amp | £2.85 |
| ZN1034E Timer | £1.80 |

All ICs supplied with data and circuits. Data sheets only 5p.

DIGITAL VOLTMETER/THERMOMETER KIT



Based on the ICL7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer, using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery) **£20.75**

24 HOUR CLOCK/APPLIANCE TIMER KIT



Switches any appliance up to 1kW on and off at preset times once per day. Kit contains AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac, PCBs & full instructions. **£14.90** white **£17.40** with **£22.50**

| | |
|-------------------|--------------|
| CT1000K Basic Kit | £14.90 |
| CT1000KB | white £17.40 |
| Ready Built | with £22.50 |

LEDs

| | |
|--------------------|-----|
| 0.1" Red | 9p |
| 0.1" Green | 12p |
| 0.1" Yellow | 12p |
| 0.2" Red | 9p |
| 0.2" Green | 12p |
| 0.2" Yellow | 12p |
| 0.2" clips | 3p |
| Rectangular Red | 18p |
| Rectangular Green | 20p |
| Rectangular Yellow | 21p |

CAPACITORS

| | | | |
|----------------|-----|------|-----|
| Polyester 250V | | | |
| 0.01 | 6p | 0.22 | 12p |
| 0.002 | 6p | 0.33 | 12p |
| 0.033 | 7p | 0.47 | 15p |
| 0.047 | 7p | 0.68 | 18p |
| 0.068 | 7p | 1.0 | 24p |
| 0.1 | 7p | 1.5 | 27p |
| 0.15 | 11p | 2.2 | 31p |

Electrolytics A Axial R Radial

| | | | | | |
|-----|--------|-----|-----|--------|-----|
| 63V | 1.0 R | 3p | 16V | 10 R | 3p |
| | 2.2 R | 3p | | 22 R | 3p |
| | 4.7 R | 4p | | 33 R | 3p |
| | 10 R | 5p | | 47 R | 4p |
| | 47 R | 8p | | 100 R | 5p |
| 25V | 22 | 6p | | 220 R | 6p |
| | 47 A | 6p | | 470 R | 9p |
| | 100 A | 7p | | 1000 R | 15p |
| | 110 A | 10p | | 47 A | 6p |
| | 470 A | 17p | | 100 A | 6p |
| | 1000 A | 20p | | 220 A | 7p |

| | | | | | |
|-----------------|------|-----|------|-----|-----|
| Tantalum (bead) | | | | | |
| 35V | 0.1 | 8p | 10V | 22 | 16p |
| | 0.22 | 8p | 6.3V | 33 | 18p |
| | 0.47 | 8p | | 47 | 24p |
| | 1.0 | 8p | 3V | 100 | 24p |
| 25V | 2.2 | 9p | | | |
| | 4.7 | 12p | | | |
| | 10 | 15p | | | |

DISPLAYS



| | |
|---|-------|
| DL304 Red 0.3" c.c. pin compatible with DL704 | 70p |
| DL307 Red 0.3" c.c. pin comp. | 70p |
| DL707 | 70p |
| DL847 Red 0.8" (pin comp. DL747) c.c. | £1.80 |
| DL850 Red 0.8" c.c. (pin comp. DL750) | £1.80 |
| DL727 Dual 0.5" c.c. Red | £1.50 |

MINI TRANSFORMERS



| | |
|------------------------------------|-----|
| Standard mains primaries 240V a.c. | |
| 100mA secondaries | 80p |
| 6.0-6V | 85p |
| 9.0-9V | 85p |
| 12.0-12V | 90p |

D.I.L. I.C. SOCKETS

| | | | |
|--------|-----|--------|-----|
| 8 pin | 8p | 18 pin | 17p |
| 14 pin | 12p | 28 pin | 24p |
| 16 pin | 14p | 40 pin | 36p |

Soldercon Pins 50p/100

VOLTAGE REGULATORS



Available in 5V, 1.2V & 15V versions.
78L series 100mA pos. 26p
79L series 100mA neg. 60p
78 series 1A pos. 52p

| | |
|---------------------------------|-------|
| LM317T adjustable 1.2V-37V 1.5A | £1.80 |
|---------------------------------|-------|

MINI KITS

These KITS form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB short instructions and all components.

TEMPERATURE CONTROLLER/THERMOSTAT
Uses LM3811 IC to sense temperature (50°C max.) and triac to switch heater. PCB (4 cm sq.) potentiometer, plus all other components included with instructions. **500W £3.20** **1KW £3.50**

SOLID STATE RELAY
Ideal for switching motors, lights, heaters etc. from logic. Opto isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

BAR/DOT DISPLAY
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.75**

BURST FIRE/PROPORTIONAL TEMPERATURE CONTROLLER
Based on the TDA1024 Zero Voltage Switch this kit contains all the components required to make a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. **1.5KW £5.25** **3KW £5.55**

BOXES

Moulded in high impact ABS. Supplied with lids and screws. Black or white.

| | |
|--------------------|-----|
| 82 95 x 71 x 35mm | 65p |
| 83 115 x 95 x 37mm | 78p |

RESISTORS

| | | |
|---------------------|-----|------------------------|
| ZENER DIODES | | 1/4W 22ohm-10M |
| 400mW 3V 3V 3V | 8p | Pack of 10 (one value) |
| 1.3W 7.5-27V | 15p | 10 Packs (10 values) |
| | | 80p |

TRIACS

| | | | |
|---------------------------|-----|-----|------|
| 400V Plastic Case (Texas) | | | |
| 3A | 49p | 16A | 90p |
| 8A | 58p | 20A | 165p |
| 12A | 85p | 25A | 180p |
| 8A with trigger | | | |
| 8A isolated tab | | | |
| Diac | | | |
| 85p | | | |
| 18p | | | |

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES PLUS 40p P&P. MAIL ORDER - CALLERS WELCOME BY APPOINTMENT.


TK Electronics

(H.E.), 106 STUDLEY GRANGE ROAD
LONDON W7 2LX. TEL. 01-579 9794



Short Circuit

CRYSTAL CALIBRATOR

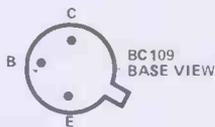

A problem with home-constructed short wave receivers is that of providing the finished unit with an accurately calibrated tuning dial. A crystal calibrator solves this problem by providing numerous calibration signals that enable the various dial frequencies to be marked on with good accuracy. A crystal calibrator is also useful for checking the calibration of a short wave receiver that has been in use for some time.

The calibrator circuit shown here has fundamental outputs at 1MHz and 100kHz. However, it does not merely provide calibration signals at these frequencies, but also at harmonics of these frequencies. Harmonics are merely multiples of the fundamental frequencies. The 1MHz output therefore provides calibration signals at 2MHz, 3MHz, 4MHz, etc., while the 100kHz output provides signals at 200kHz, 300kHz, 400kHz, etc.

These additional frequencies are produced because the circuit is designed to give an output signal that is not a sine wave, but instead has a very rapid risetime and is virtually a square wave. This gives a signal which is rich in harmonics at frequencies up to many megahertz. This circuit provides harmonics that are readily detectable up to 30MHz (the upper limit of the short wave spectrum) on any reasonably sensitive receiver.


Q1 is used in a simple 1MHz crystal oscillator, and it operates in the emitter follower mode. TC1 and C2 effectively form a tap on the crystal which acts as a parallel

tuned circuit. The output of Q1 is coupled into this tapping, and this gives the positive feedback path needed to produce oscillation. The circuit oscillates at the resonant frequency of the crystal since there is only an efficient feedback path at this frequency. There is a voltage step-up through the tuned circuit which ensures that there is sufficient feedback to produce strong oscillation and an output rich in harmonics. A crystal is used in the unit rather than an ordinary L-C tuned circuit as a crystal gives better accuracy and stability. The 100kHz output is obtained merely by feeding the 1MHz

signal to a CMOS 4017 divide by ten circuit.

TC1 must be adjusted to give optimum accuracy from the unit, and this is easily achieved by connecting a short lead to the 100kHz output and placing near to a radio tuned to the BBC LW 200kHz transmission. This will produce a low frequency beat note (heard as a cyclic rise and fall in the volume of the station), and TC1 is simply adjusted for the lowest attainable beat note. A beat rate of well under one per second should be easily obtained.

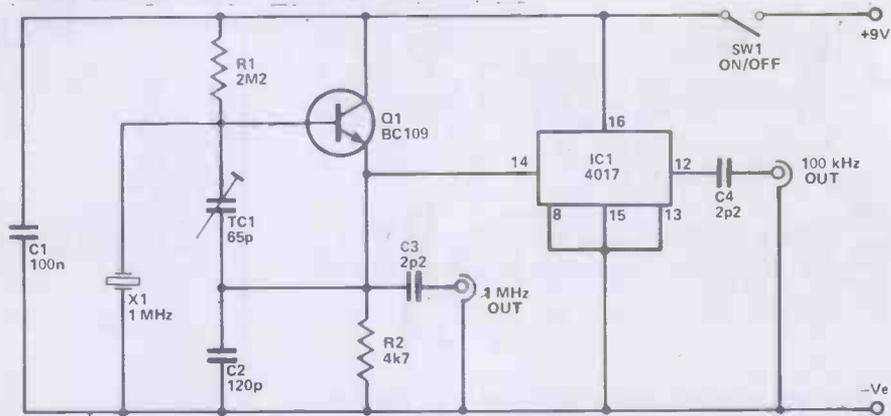The current consumption of the circuit is about 4 mA.



FM/AM STEREO TUNER AMPLIFIER CHASSIS

Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together.

Note Circuit diagram and interconnecting wiring diagrams supplied.

Rotary Controls Tuning, volume, balance, treble and bass.

Push Button Controls Mono, Tape, Disc, A.F.C., FM (VHF), LW, MW, SW.

Power Output 7 watts RMS per channel into 8ohms (10 watts music).

Tape Sensitivity output typically 150mv. Input 300mv for rated output.

Disc Sensitivity 100mv (ceramic cartridge).

Stereo Beacon Indicator LED or bulb.
Size Tuner — 2¼" x 15" x 7½"
 approx. Power amp. 2" x 7½" x 4½"
 approx.
Price £22.00 + £2.50 Postage and Packing.

J.V.C. TURNTABLE

J.V.C. Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

- ★ 'S' shaped tone arm.
- ★ Belt driven.
- ★ Full size 12" platter.
- ★ Precision calibrated counter balance weight (0.3 grms).
- ★ Anti-skate (bias) device. Nylon thread weight.

★ Cut-out template supplied.
Size — 12¾" x 15¾" (approx.).
Price £29.90 + £2.50 Postage and Packing.

B.K. ELECTRONICS

(Dept. HE), 37 Whitehouse Meadows
 Eastwood, Leigh-on-Sea
 Essex SS9 5TY

★ S.A.E. for components list etc. ★ Official orders welcome. ★ All prices include V.A.T. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam.

ELECTROVALUE

FOR COMPONENTS THAT COUNT



| | | |
|--|--|--|
| SIEMENS SEMI-CONDUCTOR CAPACITORS FERRITES | NASCOM MICRO COMPUTERS AND ANCILLARIES | VERO BOARDS CASES & KITS |
| ISKRA RESISTORS | RADIOHM POTENTIOMETERS | BREADBOARDS SOLDER TOOLS |
| | OPTO-ELECTRONICS | SWITCHES CATALOGUE 10 |

ALL GOOD PROJECTS START WITH CATALOGUE 10 IT'S FREE FOR THE ASKING

128 pages packed with almost everything everyone wants. There are attractive discounts and free postage in UK on orders £5.75 and upwards.

ELECTROVALUE LTD. HEAD OFFICE (Mail Orders)
 28(H) St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone: Egham 33603. Telex 264475.

NORTHERN BRANCH (Personal Shoppers Only)
 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone: (061) 432 4945.

Projects Special

from

Hobby Electronics



Graphic Equaliser

Another project for those interested in audio... an excellent companion to the Hi-Fi...

Analogue Audio Frequency Meter

in age... econ...

Constant Volume Amplifier

Linear Scale Ohmmeter

Hobbytune

Build a full feature monophonic organ for less than £100...

Casanova Candle




If Casanova were alive today he would have certainly soldered this project, history however does not record when...

Digibell Project

No more pressing go, the 'chime'...

Projects Special Volume 1

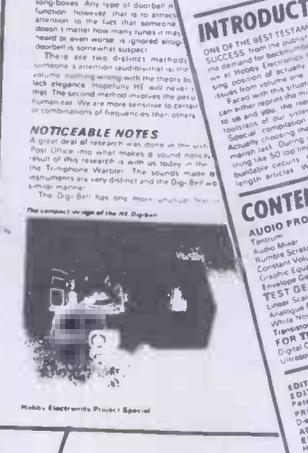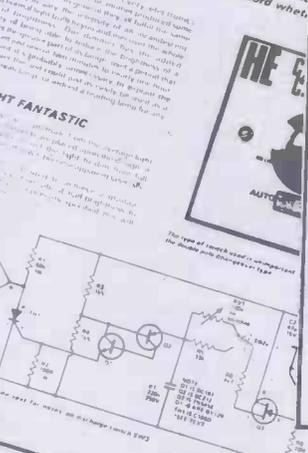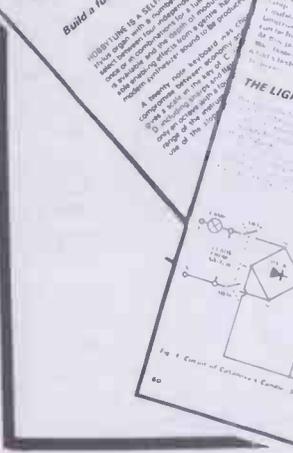From the publishers of Hobby Electronics Winter 1980



INTRODUCTION

ONE OF THE BEST TESTIMONIES TO A MAGAZINE'S SUCCESS... FROM THE PUBLISHERS OF HOBBY ELECTRONICS

CONTENTS

| | |
|---------------------------------|----|
| AUDIO PROJECTS | |
| Audio Mixer | 6 |
| Random Switch Filter | 12 |
| Constant Volume Amplifier | 18 |
| Graphic Equaliser | 21 |
| Envelope Generator | 25 |
| TEST GEAR | 31 |
| Analogue Frequency Meter | 36 |
| Linear Scale Ohmmeter | 37 |
| White Noise Generator | 41 |
| FOR THE HOME | 45 |
| Digital Clock | 47 |
| Ultrasonic Sensor | 51 |
| FOR THE WORKSHOP | |
| Drill Speed Controller | 54 |
| Digital Casanova's Candle | 64 |
| FOR THE MOTORIST | |
| LED Warning Lamp | 71 |
| Parking Brake Timer | 77 |
| MUSIC, GAMES AND GENERAL | |
| Hobbytune | 80 |
| Touch Switch | 83 |
| Push Button Dice | 85 |
| Smoothing Circuit | 88 |
| Photographic Timer | 93 |
| Diary | 95 |
| Multi-Option Switch | 96 |

Catalogue Survey

Time again for our annual catalogue survey. Is it cheaper to buy mail-order, who is the cheapest — find out now.



Three of the best. Nearly all the components you'll ever need can be brought through these companies.

MAIL-ORDER selling is a rapidly growing industry, the purpose of which is to supply goods to you, the customer, as swiftly and easily as possible. The Mail-Order Catalogue serves both seller and buyer. It enables a company to give a more comprehensive guide to its products than an advertisement alone could show, and it provides detailed information from which the prospective purchaser may make his choice.

Just as there is enormous variety between the size of companies and the range of goods they offer, so this is reflected in the kind of catalogues they produce. In all cases, however, the function of the brochure is the same — to entice and inform.


Last April we conducted a survey of several mail-order companies who advertised in HE. We invited them to send us an example of their current catalogue and we compared these in terms of number of pages, cost, guarantee/exchange etc. We thought it would be worthwhile to repeat the exercise again this year and to offer a quick and practical summary of the kind of catalogue available.

As is to be expected, the size and presentation of the catalogues varies considerably. The format ranges from

a few duplicated sheets to a publication approaching the proportions of a magazine. This, of course, is reflected in the price. Quality of reproduction does not necessarily mean that the goods advertised are in anyway superior, although the clearer and more informative the catalogue the more attractive the product may seem. It is more helpful if a photograph accompanies description and in each case this was so although the clarity did vary.

The size of the catalogues surveyed, ie the number of pages, also varied according to the size of the company and the range of components on sale. It should be borne in mind, however, that a catalogue, as well as giving information, needs to be well presented visually. A page of writing alone is neither as attractive, nor indeed as useful, as writing accompanied by illustration. The best of the larger catalogues included both.

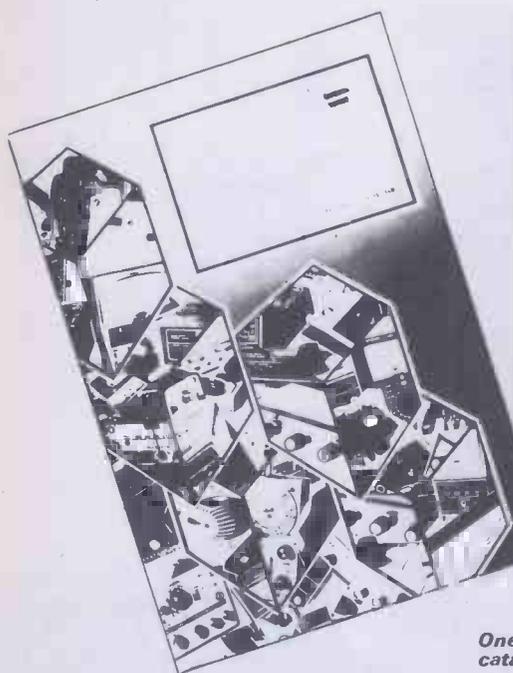The price of a catalogue will obviously depend on its size and the quality of its photographic content. Nevertheless, do not dismiss something merely because it is free — the information is still valid. Another thing to watch is VAT. Catalogues that include VAT in the price give a more accurate picture of just how much you can really expect to pay for your project or component. Some



One of the latest entries to the mail-order catalogue field, this looks most promising.

Three more of our favourite publications. Henry's above are particularly good at supplying 'unusual' or hard-to-get components and devices.

Electrovalue, above, specialists for semiconductors and other electronic components. This new catalogue is crammed full of useful IC pin-out data.

| SUPPLIER | FORMAT C = CATALOGUE L = LIST | NUMBER OF PAGES | COST OF CATALOGUE | VAT INC PRICE | POST & PACKING | GUARANTEE EXCHANGE | ADDITIONAL DATA | TRANSISTOR PIN-OUTS | NOTES | COMMENTS |
|--------------------------------|-------------------------------------|-----------------|-------------------|---------------|----------------|--------------------|-----------------|---------------------|-------|--|
| AUDIO ELECTRONICS | L | 40 | SAFE FREE | YES | NO | YES | NO | NO | - | AUDIO EQUIPMENT PLUS ACCESSORIES |
| AMBIT INTERNATIONAL | C | - | - | NO | - | YES | YES | NO | 1 | THREE SECTIONS |
| CATRONICS | C | 20 | - | YES | - | YES | YES | YES | - | |
| CONTINENTAL SPECIALITIES CORP. | C | 36 | FREE | NO | NO | YES | ON PRO-JECTS | - | - | INCLUDES MANY COLOUR LEAFLETS |
| ELECTROVALUE | C | 128 | - | NO | YES | YES | YES | - | - | VERY GOOD SELECTION & KEEN PRICES |
| GREENWALD | C | 52 | 40p | YES | NO | NO | SOME | SOME | - | GOOD SELECTION, FAIR PRICES |
| HENRYS | C | 118 | £1.00 | YES | NO | YES | NO | NO | - | BUMPER ISSUE PACKED WITH INFO |
| HAMLIN ELECTRONICS | C | 72 | - | - | - | - | - | - | - | EXCELLENT CATALOGUE |
| LOWE ELECTRONICS | C | 72 | - | - | - | - | - | - | - | BASIC INFO ON RANGE FOR TOP QUALITY RADIO PRODUCTS |
| MAPLIN | C | 280 | 75p | YES | FREE OVER £2 | - | - | - | - | SUPERB CATALOGUE, BEST THERE IS |
| MARSHALLS | C | 48 | 40p | YES | YES | YES | YES | YES | - | VAST SELECTION AT COMPETITIVE PRICES |

Catalogue Survey

TABLE 2 Comparison of prices of two recent projects from Hobby Electronics

| SUPPLIER | PROJECT 1 | PROJECT 2 | COMMENTS |
|---------------------|-----------|-----------|--|
| AMBIT INT. | £15.27 | £3.49 | All prices are not inclusive of Value added tax. So please add 15% to all totals |
| CHROMASONICS | £15.42 | £3.78 | |
| ELECTROVALUE | £15.39 | £3.22 | |
| GREENWELD | £15.53 | £3.24 | |
| MAPLIN | £15.47 | £3.56 | |
| MARSHALLS | £15.48 | £3.36 | |
| WATFORD ELECTRONICS | £15.71 | £3.39 | |

NOTE:
PROJECT 1; DIGITAL FREQUENCY METER
PROJECT 2;
TOUCH SWITCH
(not including PCB's, cases & knobs etc.)

companies in the survey included VAT, some did not. There was variation in the amount of post and packing added to the cost of an item. Some companies make no charge at all, others make no charge on orders over a certain amount. Some quote a P&P charge on each item. Again, if the exact charge is clearly shown, you will have a better and more immediate picture of total cost.

Not only is it important that the catalogue gives a clear and accurate indication of cost, but it is also essential that it gives as much information as possible about the product. Photographs are very helpful, and really should be obligatory, but in some cases, more detail is needed. This ought to, and in some cases did, mean pin-out diagrams of transistors and ICs as well as additional data.

As in last year's survey, we decided to conclude with a comparison of prices charged by the different companies. We did this by costing two projects from recent issues of HE and the results are shown in table 2. They should be taken as a rough guide to the companies' overall price structure, and are pretty well self-explanatory.

CONCLUSION





The mail-order catalogues we examined varied in size and price, and some were quite clearly better than others. However, we found all of them to be useful sources of information and worthwhile reading for anyone interested in buying. If you look at our tables you will get a pretty good idea of how and where the catalogues differ, as well as what kind of prices to expect from each company. We hope you find them helpful, but if you have any comments of your own to add, please let us know.

HE



BEASTIES

BY AH

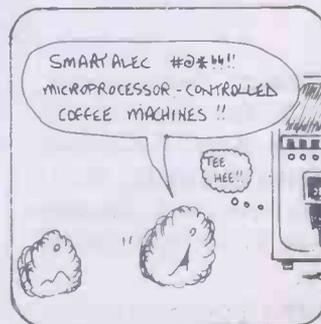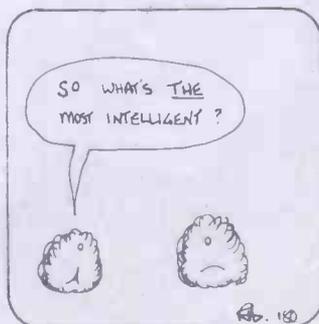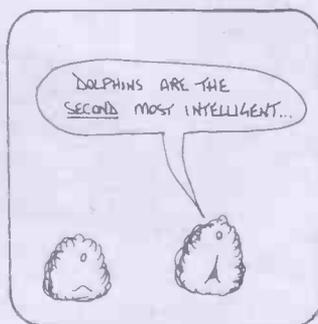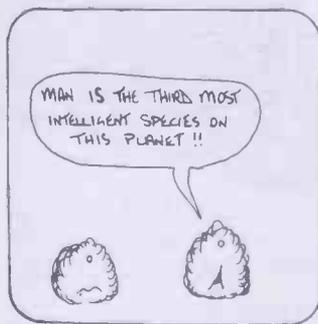

YOU'VE USED ETI CIRCUITS NO 1 YOU'VE USED ETI CIRCUITS NO 2 NOW USE:




**THIS IS ETI
CIRCUITS
NO 3**

ELECTRONICS DIGEST
No 1 reprints The Best Tech Tips From ETI Magazine. The Circuits are Classified By Type For Easy Access. So Don't Be Stuck For A Circuit — Use Instant Inspiration, Use Electronics Digest.

**IN
YOUR
NEWSAGENTS
MAY 17th**

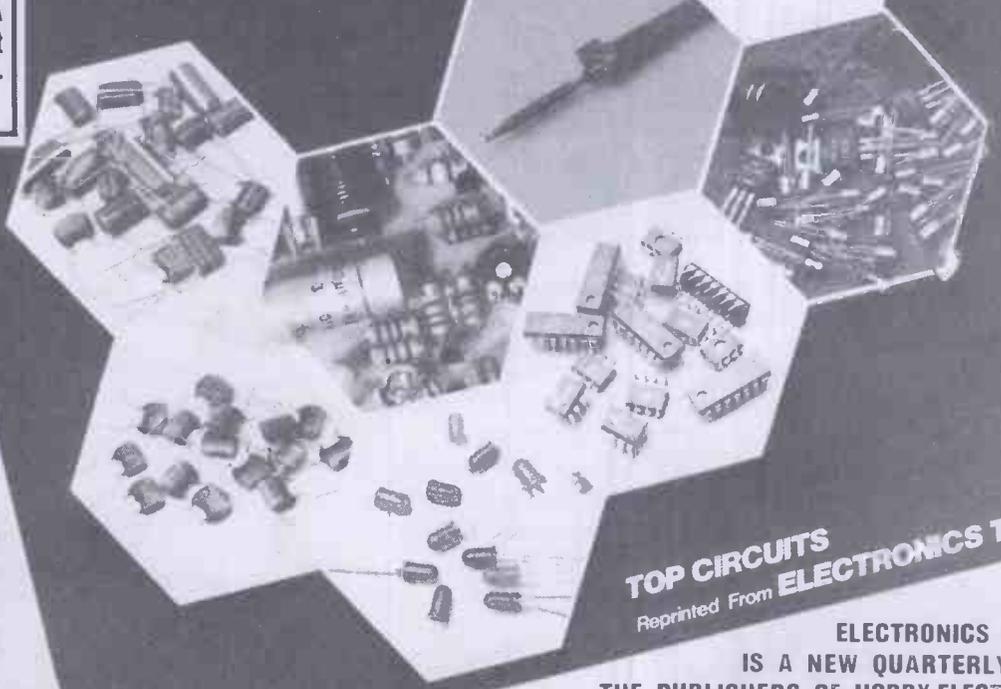At Your Newsagent, £1.50. Or Send £1.50 + 30p P&P To Sales Office (Specials), Modmags Ltd, 145 Charing Cross Rd, London WC2H 0EE.




TOP CIRCUITS
Reprinted From **ELECTRONICS TODAY**

ELECTRONICS DIGEST
IS A NEW QUARTERLY FROM
THE PUBLISHERS OF HOBBY ELECTRONICS

Short Circuit

TRANSISTOR CHECKER

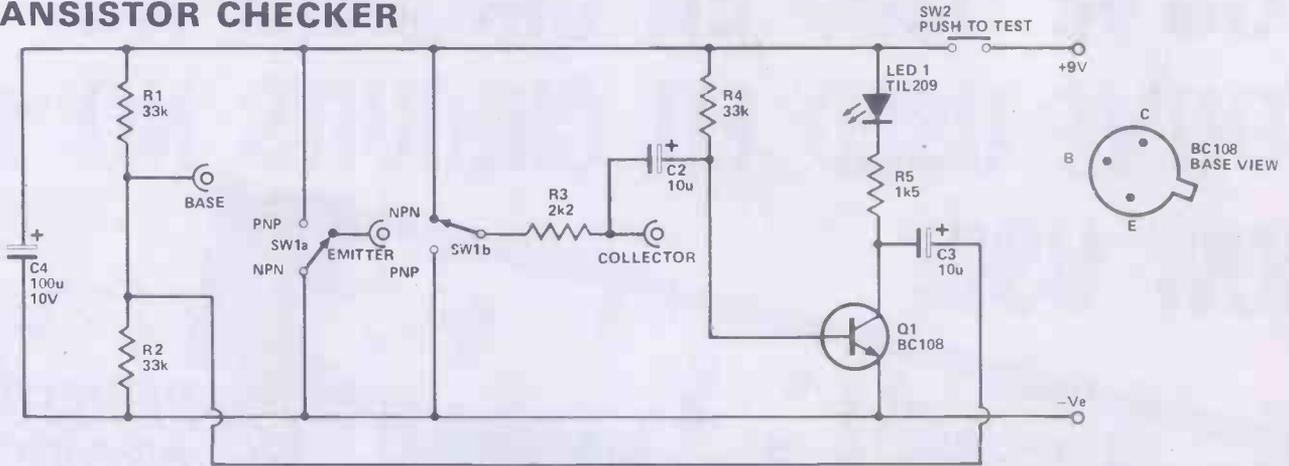

This device enables transistors to be quickly tested, and shows whether or not they are serviceable. To test a device it is first connected to three sockets on the front panel, ensuring that each lead connects to the correct socket, a switch is set to the PNP or NPN mode, as appropriate, and then a push button switch is depressed. If the test device is functional, a LED indicator will flash on and off at a rate of about two or three times per second. The LED will simply light up for the duration that the push button is pressed if the test device is a dud.

If we consider the circuit in the NPN mode first, it is basically just a standard astable multivibrator, with the test transistor acting as one of the transistors in the circuit. The test device is biased by R1 and has R2 as its collector load resistance. R2 shunts the base emitter terminals of the test device, but is too high in value to have any significant effect on the circuit. Q1 is used in the other section of the multivibrator, and it is biased by R4. LED indicator D1 and current limiting resistor R5 acts as its collector load. C2 and C3 provide the cross coupling between the two stages.

If the test device is functional, the circuit will of course oscillate, and the specified values give an operating frequency of about 2 to 3 Hertz. As Q1 switches on and off, D1 will be seen to flash on and off. If the test device is faulty, R4 will simply bias Q1 into conduction, resulting in D1 remaining switched on while SW2 is depressed and power is supplied to the circuit.

With SW1 switched to the "PNP" mode, the supply to the test device is altered to the correct polarity. R2 now biases the test device, and it is R1 that has no significant effect on the


circuit. Although a multivibrator would not normally use one PNP and one NPN device, the circuit operates very much as before.

The current consumption of the unit is about 6 mA. Three small wander sockets mounted in a triangular arrangement can be used as the test sockets, and provided they are mounted very close together, most small transistors will then plug into these without difficulty. A set of three test leads terminated in crocodile clips can be used to connect the unit to those that will not.


SW2 is a push-to-make switch.

S100-the British way

vero vero

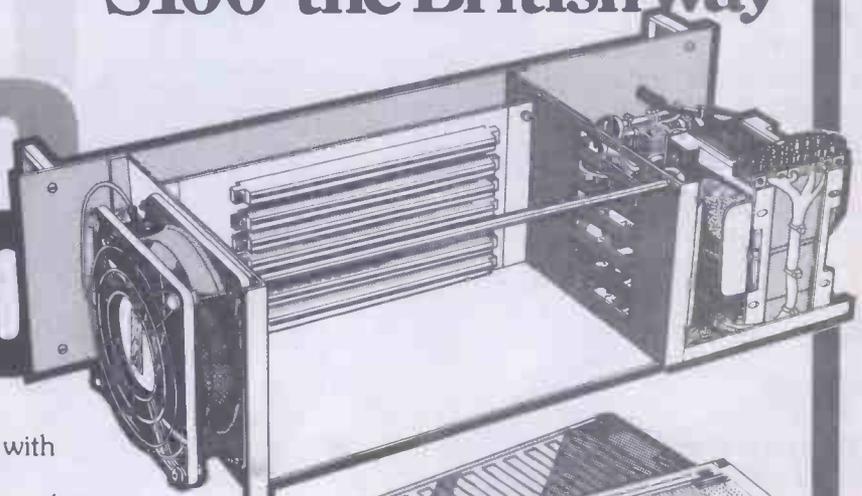

The Vero S100 Sub Rack is a 19" rack mountable development kit, complete with its own power supply and backplane motherboard, for the construction and evaluation of microprocessor based systems to the S100 format. The power supply provides three voltage levels — +8V, +18V and -18V. The Sub Rack has its own cooling fan providing airflow across the boards and the power supply. A full range of allied items to enable a complete system to be constructed are available.

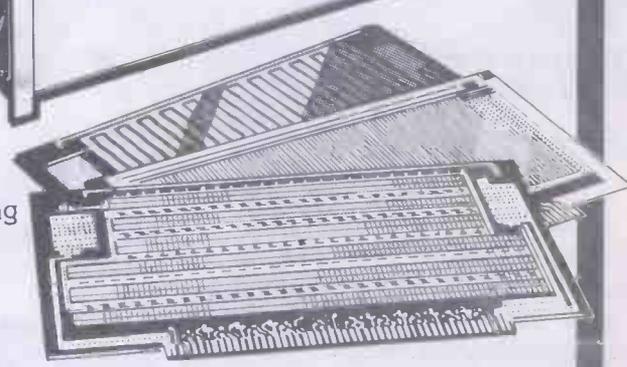

VERO ELECTRONICS LTD RETAIL DEPT.
 Industrial Estate, Chandler's Ford,
 Hampshire SO5 3ZR
 Tel: (04215) 62829

ETI JULY 1980

WHAT TO LOOK FORWARD TO
IN OUR JULY ISSUE! ON
SALE JUNE 6TH.


Next month ETI presents the definitive history of the spacecraft. Ian Graham - our permanently high spaceman - talks us through the hardware of the fastest man-made vehicles to date and takes a look at those which take flight only in our imaginations. For everyone who has looked up at the stars and longed.

Also, next issue we have the long awaited Image Co-ordinator which will allow you to do things with your stereo image that your mother wouldn't approve of! Moreover Tim Orr follows up his Handbook of this month, with another in similar vein, this time on his favourite subject, Active Filters - find out how to design them yourself in the July issue of ETI.

For the audio men there is a link at one of the rising stars of hi-fi, the 204 (110W) power amplifier. It can be bought as a fully built and working piece or as a kit. An example of their range is the 204 (110W) power amplifier by your speakers.

FROM THE PUBLISHERS OF HE

THE DJ's YEARBOOK 1980

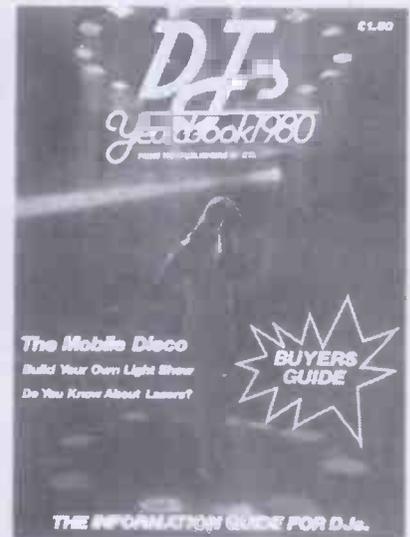

The DJ's Yearbook tells you what you need to know to make you a better DJ. It tells you how to make your own light show (two versions), how to manage the business side, how to operate, how to build a mixer-amplifier. The DJ's yearbook tells you about the Disc Jockeys' Federation, about insurance, about publicity. It contains the most-comprehensive-yet-published Directory of Manufacturers and Suppliers.

And if you're thinking of starting your own mobile disco business, the DJ's yearbook will set you off on the right lines.

At your newsagents. Or send £1.50 + 30p (P&P) to Sales Office (Specials) Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE.

INVASION FROM ANOTHER WORLD

NEWS

What's happening in the world of technology

THE WIRED CITY

Europe's new capital city will be wired for 21st Century living

QUAD FS-13 REVIEW

Superb response from a flat wall-panel loudspeaker

MORE THAN HUMANLY POSSIBLE

Should we be worried by robots?

WORLD WAR THREE

Newly-released papers show how electronics won the War

THE GROWTH OF INFORMATION

The explosion that took everyone by surprise

"MAD DOCTOR" APPREHENDED

Police in New York finally catch the infamous "Mad Doctor"

WHY THE NEWTON CRASHED

New information on a disaster that could have been avoided

MAKING RINGS AROUND OUR PLANET

It's not just high-technology manufacturing in Earth's orbit

ETI PSYCHOSYMPHONIA

Hear yourself think with this easy-to-build project for the musician

All across the nation ordinary citizens have been intrigued by the appearance of thousands of blue and silver folders. These folders first appear on the shelves of newsagents and quickly they find their way into the hands of innocent shoppers. These (previously normal) individuals have since reported the emergence from the folder of a colourful magazine-like object with the markings "ETI 1999" clearly visible in front aspect. Further inspection has shown a polyfolio structure with pages of fascinating articles and pictures from another world - a world both strange and uncannily familiar.

The latest development in the ETI 1999 story is the aggregation of a few thousand of the alien objects, withdrawn into their protective folders, at the Hobby Electronics office. Further, we have received a demand for thousands of pounds and instructions to send units of "ETI 1999" to anyone who sends £1.50 + 30p (P&P) to Sales Office (Specials), Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE.

ON-AIR, OFF-AIR

Will all broadcasting be banned in the near future?

MUSIC IN A DIGITAL WORLD

Recording studios aren't what they used to be

THE NEW MILLENIUM

What to look forward to for the next thousand years

HELLPROBE NEARS SUN

The space probe that's trying to get one up on Icarus

THE WORLD IN YOUR HAND

Call directly into a satellite phone link with this pocket Communicator

THE DRIVERLESS CAR

Public transport can do it and soon your private car will be able to do it

COMPUTERS CATCH COLD

Are software "viruses" weakening our computers?

EUROTOWER PICKS UP ETI?

ExtraTerrestrial Intelligence in the new Eurotower?

THE MAD PROFESSOR

Further scenes from the life of our funny friend

WIN A TRIP TO SKYLAB!

Another great contest from ETI

Detail of the Contents Page

Detail of the Contents Page

Fog Horn

Connect this little circuit up to our Miniboard Amplifier and you'll be able to lose all your friends in under one minute — you have been warned.

IF YOU LIVE ON the shores of a busy harbour, you have probably been woken occasionally in the early morning by the sound of a ship's fog horn. Before the advent of radar, fog horns were the only means ships' captains had of avoiding collisions. The distance and direction of the low-pitched sound gave an indication of another craft's position. Despite radar, many boats and ships still have fog horns in active service.

This project won't wake the household (or the neighbours!) but it certainly makes a realistic sound.

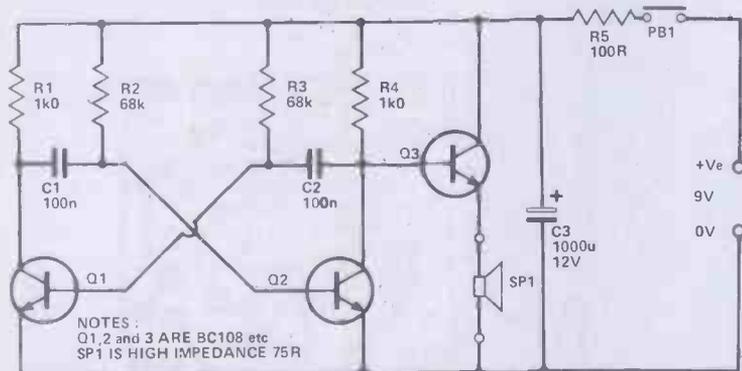


Fig. 1. Circuit diagram of the 'deafening' HE Fog Horn.

CONSTRUCTION

This circuit is simple enough to be constructed on matrix board or tag strips. However, we have used a printed circuit board. If you are not yet confident of getting all the connections right, we suggest you construct this project as we have.

No matter what method of construction you elect to use, as always, take care with the orientation of the transistors and the polarity of the battery connections. The speaker we used is rather an unusual item. Small speakers commonly have an impedance of either eight or 16 ohms. The one used here has an impedance of 75 ohms.

You can modify the sound of the fog horn if it is not quite to your satisfaction — normal component variations will produce differing results. You can vary the basic sound produced by the multivibrator by varying C1 and C2. Changing these by one standard value higher or lower will produce quite a gross variation in pitch. Smaller variations can be obtained by having several capacitors in parallel. Use a large value — close to that specified — and connect a smaller value capacitor in parallel, for each of C1 and C2.

The rising and falling pitch and volume is controlled by R5 and C3. The value of R5 can only be practically varied a small amount. You get a much more satisfactory result by varying the value of C3 or varying its discharge

How it Works

The fog horn consists of an oscillator, which generates the basic sound, and a speaker driver. The oscillator we used is known as a "multivibrator". This type of circuit is widely used — in one form or another — in electronics, it is one of the 'building blocks' used in many complex circuits.

The multivibrator here consists of Q1, Q2, C1, C2 and R1 to R4. To understand how it oscillates, we must first make an assumption: let us assume Q2 turns on when the push-button, PB1, is operated. One or other of the transistors, Q1 or Q2, will turn on first as no two devices are exactly the same.


Now, when PB1 is pushed, Q2 conducts and Q1 will be 'cut off' (not conducting). The collector voltage on Q1 will be at the supply voltage (about +9V) and the base of Q1 almost at zero volts as C1 will not be charged and the collector voltage on Q2 will be close to zero (as Q2 is on). C2 will charge via R1 and the base of Q2, keeping Q2 on while it charges. C1 will begin to charge via R2, and when the base voltage on Q1 has risen sufficiently, Q1

will commence to conduct. The collector voltage on Q1 will rapidly fall. This will cause the charge on C2 to reverse-bias the base of Q2, immediately turning it off. Thus, the collector voltage on Q2 will jump to the supply voltage and C1 will begin to charge via R4 and the base of Q1, holding it on while C1 charges.

However, C2 will begin to charge — in the opposite direction to which it was first charged — and the negative voltage on the base of Q2 (from C2) will decrease, pass through zero and rise in a positive direction. When it has risen sufficiently for the base of Q2 to conduct once more, Q2 will turn on.

And the whole business begins again. The charge on C1 will reverse bias Q1 which turns right off, C2 will charge via R1, driving Q2 further on . . . until C1 charges (via R4) sufficiently to turn Q1 on again, etc.

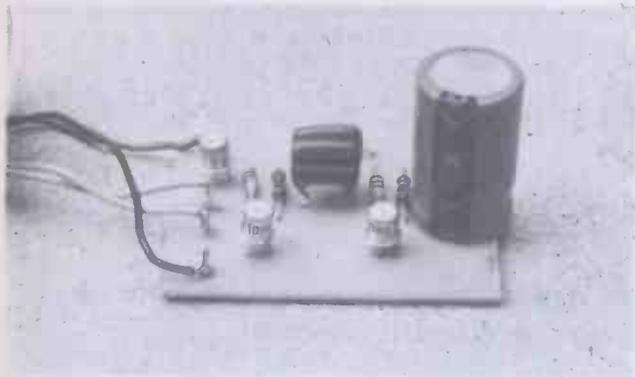Thus, the collector voltages on Q1 and Q2 will alternately rise, stay up for a period, fall and stay



Close-up of the 'business end'.

time. You can decrease the 'die away' period by putting a low-value resistor in parallel with C3, increasing the discharge current. Start experimenting with something like 680 ohms.

Parts List

RESISTORS (All 1/2W, 5%)

| | |
|--------|------|
| R1 | 1k |
| R2, R3 | 68k |
| R4 | 1k |
| R5 | 100R |

CAPACITORS

| | |
|--------|---------------------|
| C1, C2 | 100n |
| C3 | 1000µ, 12 V electro |

SEMICONDUCTORS


| | |
|-------|-----------------------------------|
| Q1—Q3 | BC548, BC108, DS548 or similar |
|-------|-----------------------------------|

MISCELLANEOUS

SP high impedance speaker, greater than 40 ohms.
PB1 push-to-make momentary push button.
9 V battery or suitable battery eliminator.

Buylines

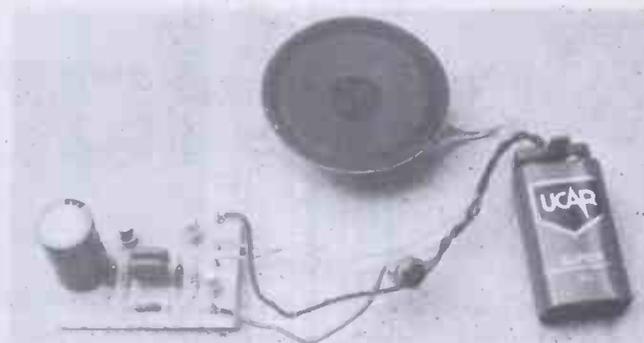All of the components are readily available. The mercury switch can be obtained from either Maplin or Watford Electronics for around 50 pence.



The HE Fog Horn connected up to the speaker, battery and switch.


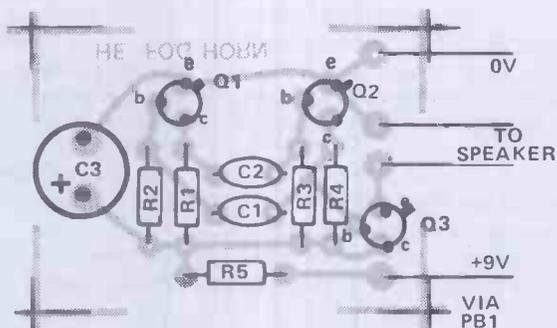


Fig. 2. (Above). Overlay diagram of the Fog Horn.

Fig. 3. (Below). PCB design.

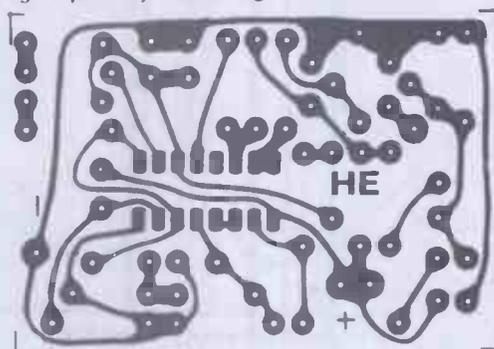

down for a period, then rise again — a square wave.

That's your basic, or common-garden-variety, multivibrator. The frequency of oscillation is dependent on the values (and thus the time-constant) of R1, C2 and R2, C1. An output can be taken from the collector of either Q1 or Q2. The signal on one collector will be the opposite phase to that on the other collector (while one collector is up, or 'high', the other collector is down, or 'low').

The output from the oscillator will not be able to drive the speaker directly. This is because the oscillator has a high impedance output and cannot supply enough current to drive the relatively low impedance of the speaker. To increase the available current, and lower the output impedance, we use an emitter follower, where the input is fed to the base of a transistor, Q3, and the output is taken from the emitter. The voltage output from the emitter follower is very close to the input voltage, but the current is amplified sufficiently to drive the speaker.

But what about the R5 and C3. Well, these help to give the oscillator its characteristic sound. The multivibrator generates the basic low pitch of the fog horn. But, if you listen carefully to a real fog horn, you will notice that the pitch and volume vary slightly as it sounds. Now, the frequency of a multivibrator depends on the supply voltage to a large extent. The lower the supply, the lower the frequency, and vice-versa. Also, the output, and thus the volume, is lower at lower supply voltages — vice-versa.

When PB1 is pushed, C3 will take a short while to charge and therefore the voltage supply to the oscillator (and speaker driver) will take a short while to rise. Thus, the sound from the speaker will have the characteristic rising pitch and volume of the first part of a fog horn's blast. When PB1 is released, C3 will take a short while to discharge and the sound level and pitch will die away.

In this way, the circuit simulates the characteristic sound of a ship's fog horn.

All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronic D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.



Fits all 12 v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED

Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE
ELECTRONIC IGNITION

Electronics Design Associates, Dept. HE/6
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

I enclose cheque/PO's for

X5 KIT £16.95

£

Cheque No.


ACCESS OR BARCLAY CARD No.

Send SAE if brochure only required

AUTO COMMAND REMOTE CONTROL

"Definitely the star of the show as far as gimmicks went."

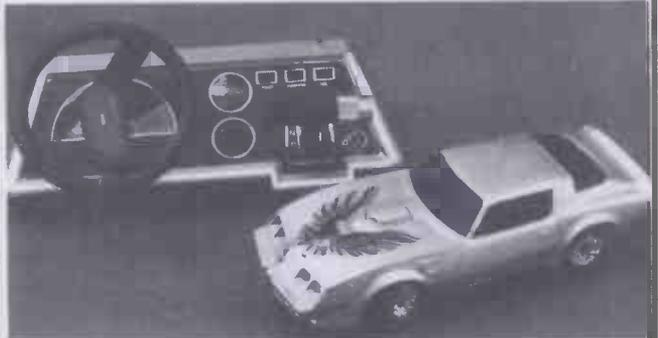HOBBY ELECTRONICS
Radio Control Model Survey



1. "The 7" by 15" fully operational dashboard that puts you in complete control of the Trans AM."
2. Magnificently detailed 12" long 1979 Firebird Trans AM.
3. True Proportional steering wheel.
4. Infinite speed control.
5. Realistic engine idle revving and acceleration roar — Directly from the car engine.
6. Key Start! Activate engine sound and dashboard light.
7. Gear Shift! Select drive neutral or reverse with stick mounted gear shift.
8. Accelerate! Rotate accelerator bar — hear the car engine roar louder as the car speeds away.
9. Steer it! Proportional steering and speed control tests your driving skills.
10. Built-in Accessories! Real working horn on steering wheel. Real working rev counter. Real working dashboard indicator.
11. Range 80 feet.

Scopes and multimeters available. Super-system III Chess Game £154 as mentioned in Hobby April '80. Chess Challenger 7 @ £84. S.A.E. for details.

Please send me Auto Command Remote Control Car: £55 + £2 p&p or details of Computer Chess, Scopes, Multimeters. (Delete as applicable.)

Name
Address

KRAMER & CO., 9 October Place, London, NW4 1EJ. Tel: 01-203 2473. Telex 888941 Attn. K7.

Callers welcome by appointment. Open Mon.-Fri. Sun. by appointment

Into Electronics Construction

PART 5

BY IAN SINCLAIR

Only one more month to go, by now you should have grasped the rudiments of electronics but now the one skill you have to master — soldering.

UP TILL NOW we've been building all of our circuits on the Eurobreadboard which lets us keep using the same components over and over again, and also allows us to experiment with changing component values without needing major surgery to the circuit. Every now and again, though, there's a circuit that you'll want to use permanently and which must then be built on a solderboard of some sort. That means soldering, and soldering is the subject of this part of the series.

Soldering means joining metals together with another metal, one which melts at a low temperature. There are all sorts of solders for all sorts of purposes, but the one which is of most interest to us is made from a mixture of sixty parts of tin to forty parts of lead. This is a type of solder which has a particularly low melting-point, and is the most suitable for electronics use. We have to avoid solders which have high melting points, because electronic components are easily damaged by high temperatures. The solder we use gets quite hot enough, and we certainly wouldn't want to use anything which melts at a higher temperature. Fortunately, we don't have to worry too much about details, since we don't have to make our own solder. We just buy a suitable "electrical" grade solder, and use it!

The important part of the soldering operation which has to be repeated over and over again is to join a component leadout wire to a strip of copper. The copper strip will be on some sort of solderboard — we'll look at these later in this Part. What we're trying to do is to make hot molten solder flow on to both of these metals (the leadout wire and the copper) so that it joins them, mechanically and electrically, then to let the solder solidify so that the metals stay joined.

HOT STUFF

Difficulty number one is to make the hot solder flow. Like water on a greasy plate, solder has an annoying habit of forming into little round drops which don't flow on to anything. All molten metals do this, in fact; it's caused by an effect called surface tension, and it's enemy number one as far as soldering is concerned. Fortunately, this problem has been licked — but you have to know how, else you'll never know how to solder really well.

The solution to the problem is similar to the solution to getting water to flow on a greasy plate — you add a "detergent". Now I wouldn't suggest that you should dip your soldering iron into Super Family Sudso (the fumes might choke you), but it's the same sort of thing. I've even used a cake of soap as a way of making solder flow before now when nothing else was to hand, but that's another story. The material which helps to make solder flow on to component leads and on to the copper strips of solderboards is called flux, and the correct flux is as important a part of soldering as the solder itself.

Time was when you had to buy flux separately, and coat everything you were going to solder with this thick goo. Those days are gone, and I still have a tin of flux I bought in 1948, because when you buy the genuine solder for electronics use it has the flux inside it. Yes — I said inside it — like the lettering in Blackpool Rock, the flux is a core inside the metal of the solder. Under a microscope it looks a bit like the drawing in Fig. 5.1.

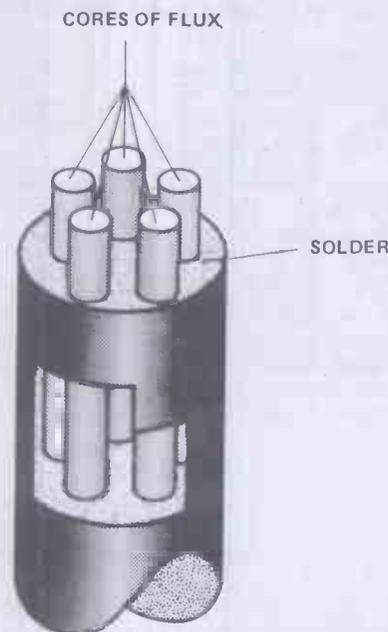


Fig. 5.1 A magnified view of a piece of five-cored solder. The five cores of flux will melt when the solder is heated.

Now if all that the flux did was to help the solder flow on to the joint (the two metals we want to join), that would be reason enough to be grateful, but it does another job as well. Solder is a mixture, as we've said, of the metals tin and lead, and both of these metals are attacked by the oxygen in the air. One effect of this attack, called oxidation, shows when you melt these metals. The bright surface of the molten metal soon becomes covered with a dull film of metal oxide. These oxides (of tin and of lead) don't conduct electricity too well in this form (though there is one conducting form of tin oxide), and they certainly don't stick to other metals, so that we need to avoid this oxidation of our hot solder. The flux does just that, by flowing over the surface of the solder and protecting it from the air. If you insist on keeping solder hot for a long time, though, the flux will burn away, leaving the solder unprotected, and that can spell disaster to your hopes of a good connection.

KEEP IT CLEAN

Of course there's not much point in having the solder kept clean and beautiful by the flux if the metals you're going to join are in a grotty state. Solderboards should be clean and free from grease; a wipe with a rag moistened with white spirit, dry cleaner fluid or lighter fuel will clean grease off, but be careful with all of these liquids. Component leadout wires sometimes benefit from being pulled through a bit of folded wet-or-dry emery paper (yes, that's what you ask for in the shop, wet-or-dry rubbing-down paper.). Apart from aluminium, which needs special solders and fluxes, the nickel-chromium-steels which are used for transistor leadout wires are the only metals which can present problems, and they need the most careful cleaning — but don't pull the leads out from the transistors!

The steps in making a good soldered joint are:

1. Heat the materials which you're going to join,
2. Melt the solder and its flux directly on to the place where you're making the joint.
3. Keep the lot hot until the solder has flowed properly,
4. Cool the joint down again before the flux burns away.

It all sounds pretty straightforward, so let's see how we go about it in practice.

GETTING STARTED

First of all, you'll need a soldering iron. Nowadays, with components getting smaller and smaller, a big old-fashioned iron is useless, and you'll need a miniature iron with a power rating of somewhere between 10 and 20 watts, preferably with a selection of interchangeable "bits", as the business end is called. People have their own preferences — mine is for a very nice little iron, the SRB, manufactured by SR Brewster of Plymouth, and widely advertised in the electronics magazines. It has enough power to cope with the occasional larger job, a good selection of different plug-in bits and, most important of all, a three-core cable so that it can be properly earthed through a three-pin plug and socket. I often work alone, and nothing will ever persuade me to use any electrical equipment which is not properly earthed — end of safety message.

Let's suppose, then, that we have an iron plugged in and getting hot, and a component leadout wire which is laid against a piece of solderboard. How do we go about soldering this lot? To start with, we have to make sure

that the bit of the iron is not clogged up with gungy old solder. The cleaning method is simple — a quick wipe with a damp cloth (and that's why I like the iron to be earthed!) Don't file or sandpaper the bits; they usually have a thin coating of iron nowadays, which will be removed if you file them, and that will greatly reduce the life of any bit. In addition, the damp-cloth method is much less messy. The cloth shouldn't be *wet*, just damp enough to steam slightly when the iron is touched against it.

With the bit of the iron clean, place it on to the joint. Ideally, the bit should touch both the component leadout wire and the copper track of the solderboard. Let them heat for a second (no more, otherwise the dreaded oxide will strike again), and then touch the end of the solder-wire against the bit of the iron just where it touches the copper track. There will be a puff of smoke from the flux, and after a little bit of hesitation, the solder will start to flow onto the copper and around the leadout wire. You can sometimes help it on its way round the wire by turning the iron around the wire, keeping the bit in contact all the time. Whenever the solder coats the wire and the copper track evenly (Fig 5.2), take the iron away — the joint has been made and heating it any longer will just cause oxidation. Now blow on the joint until the solder is cool, and take a good look. There should be an even coating of solder, no great blobs or gaping holes, and the surface should be reasonably bright, with no trace of burning. It doesn't matter if there's a brittle coating of something that looks like old varnish — that's the flux.

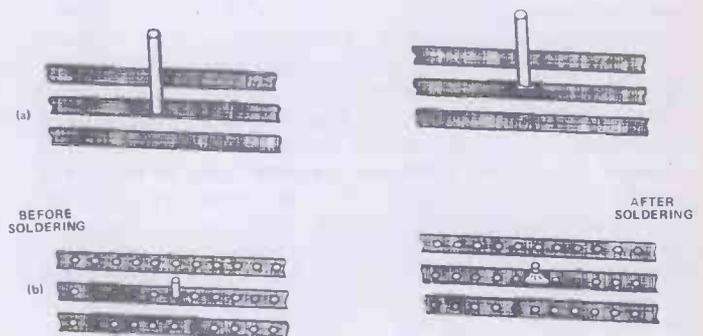


Fig. 5.2 Soldered joints. (a) Shows a joint made on to a plain board, such as the Euro 2298, (b) shows a joint made to a perforated board such as Veroboard.

Easy isn't it? What can possibly go wrong? One thing that can go wrong is that the leadout wire of the copper track is dirty, so that the solder simply refuses to flow. Another thing that can go wrong is that no flux gets to the joint, because you've melted some solder on to the iron and then carried it to the joint. You can also wreck a perfectly good joint by keeping the iron on for so long that the flux burns away, the solder oxidises, and the copper coating of the board becomes so hot that it pulls away from the board.

Now you've probably noticed that the procedure as laid down in these last few paragraphs needs a lot of hands, because with the iron in one hand and the solder in the other, it's a bit difficult to hold the solderboard and the component. There are several ways around this. Way

Into Electronics Construction

number one is to use some sort of clamp or jig for holding the solderboard and the component. It doesn't have to be very elaborate, a small vice, or C-clamp, even a Bulldog clip, and a lot of Blu-Tak works wonders.

The other way is a bit more subtle and needs more practice — it relies on the idea of tinning the board and the component leadout. 'Tinning' just means coating with solder, so that you put a film of solder onto the leadout wire and the copper strip before you try to solder them together. It's easy enough, just place the iron against the wire or track, touch the solder onto the place and wait until the molten solder spreads. Only two hands are needed, because the solder board can lie flat on the bench, while you hold the iron in one hand and the solder in the other; when you tin a component wire, the solder can lie coiled on the bench and the iron and component can be brought up to the solder.

Once both have been tinned, they'll solder together just by placing them together and applying the iron for one second, no more. If tinning the board has sealed up the hole through which the lead-wire has to come, just keep the wire pushed into the hole, it'll go through whenever the solder melts. This method often looks time consuming, but it makes sure that each part which has to be soldered is coated properly with solder, and that's the important part of soldering. Some printed circuit boards come ready-tinned, so that if the component leadout wires are also tinned, soldering is exceptionally easy.

HAVE A GO

That deals with the soldering, then. Now for what we're going to solder on to — the solderboards or PCB's themselves. PCB means printed circuit board — a board which is 'printed' with a pattern of copper tracks which give the correct connections for your circuit. At this stage, there's quite a lot of choice for you of readymade PCB's, or various stages of circuit board construction. The easiest (and most costly) method is to buy a ready-made board for the circuit you're going to build, or to buy a kit which includes the board ready to use. All you have to do then is to cut the component leads to the correct lengths, bend them so as to fit the board and solder them into place. It's too easy, really, a bit like shooting a sitting duck.

A less costly and more interesting method is to make use of your favourite magazine's Hobbyprints. The Hobbyprint is a method of producing a very professional looking PCB by your own efforts, and there's a Hobbyprint for most of the projects featured in HE. Hobbyprints produce a PCB in very much the same way as your ready-made boards are produced, by etching away the copper from a copper-coated board using an acid solution. The raw material is a plastic board (a material called SRBP — synthetic resin bonded paper) which is coated with copper. The board is often called 'laminated' and most of the component suppliers will sell you chunks of this material. You clean the surface free of dirt or grease, dry it thoroughly (watch for fingerprints — get a fingerprint on the board and you'll have to wipe it off with a rag moistened in lighter fuel), and then apply the Hobbyprint.

What's the Hobbyprint, I hear you ask? It's a dry transfer, in the exact pattern you need for a printed circuit, and you apply it to the copper in the same way as you apply any other dry transfer, by slapping it face

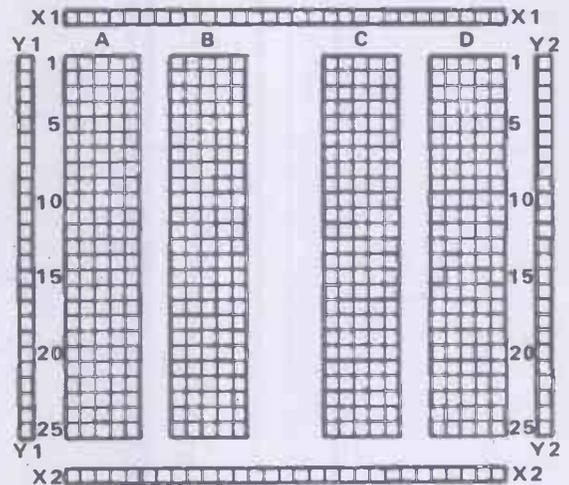


Fig. 5.3 The layout of the Euro 2298 board. This matches perfectly with the layout of the Eurobreadboard, so that you can make all your circuits in permanent soldered form.

down on the copper (ouch!) and rubbing the back all over with a pencil. You can use a soft pencil with a broad lead — I use a carpenter's pencil myself — to make sure that you have pencilled all over the back of the Hobbyprint. When you slowly and carefully remove the backing paper, you are left with a pattern of your PCB on the copper and a piece of paper which you can now throw away. Don't panic if it looks as if a bit hasn't stuck to the copper, just rub the back a bit more where the point is not transferring. If the worst happens and a piece refuses to stick (are you sure you cleaned the copper thoroughly?), then there's a repair kit with each Hobbyprint — they think of everything, these guys!

Now this is no ordinary dry transfer, because the material which is used for the Hobbyprint is acid-proof. Result is that if you now dip the whole sheet into an acid, the copper which is *not* covered by the Hobbyprint will be etched away and will disappear, but the copper which is covered by the Hobbyprint pattern is protected and will stay in place. This wouldn't work well if we used a really strong acid, so we don't, we use a weakly acid material — ferric chloride. Ferric chloride is a solid, reddish brown lump which dissolves in hot water to make up a solution which dissolves copper at a reasonable rate and doesn't affect the transfer material. The ferric chloride solution will work cold, but only very slowly. Make it up with hot water, as much material as possible in the amount of water you are going to use. Remember that the solution will have to cover the laminate board, and that you'll need to keep it in something. A cast iron pot is ideal, because it's unaffected by ferric chloride, but I wouldn't like to use it for cooking afterwards because stray copper isn't too good for you. I etch my boards in a photographic developing tray, and keep the solution hot by shining a 100W reflector lamp on it. I don't like working with ferric chloride on the cooker — the workshop is the place for this sort of thing!

With concentrated hot solution, the etching is complete in ten to fifteen minutes, and the PCB is ready whenever all the uncoated copper has just disappeared. The next step is hard work — you have to wash the board and then scrub off all the coating. Good ol' fashioned Vim and elbow-grease is the only way.



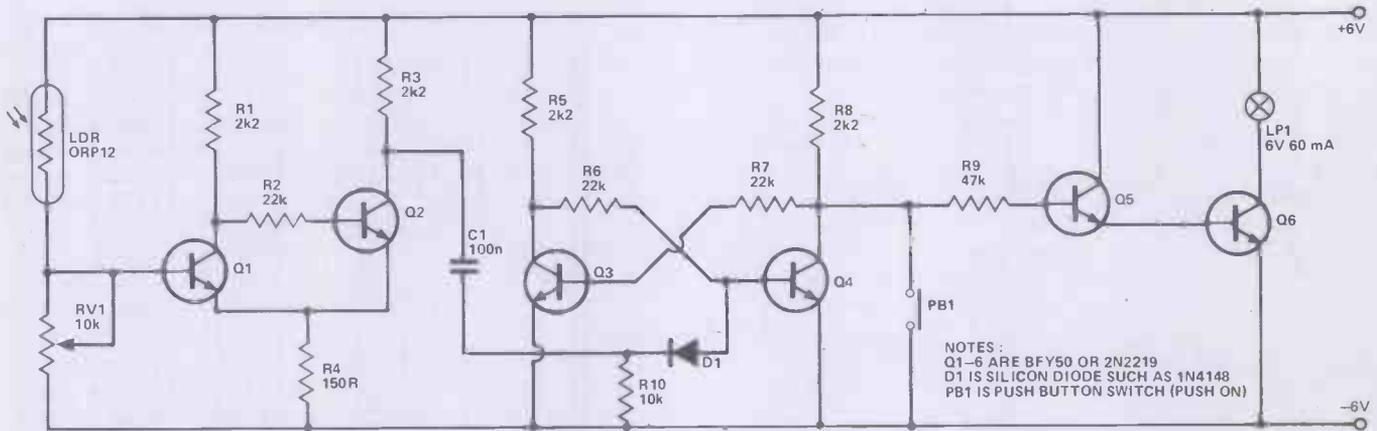


Fig. 5.4 The light alarm circuit. All the transistors are NPN types.

DO-IT-YOURSELF

All you have to do now is to drill the holes for the component lead out wires and remove any burns around your drill holes. It's an advantage if you have a small drill — a carpenter's brace is decidedly useless for this job. Result — one perfect PCB!

Suppose you don't have a Hobbyprint for the particular circuit you have? Don't panic, there are still lots of ways left. One way is to draw the pattern on the copper for yourself. You can use felt-pens which contain acid resistant varnish, or you can use draftsman's indian ink — some of the neatest work I've seen was done with a Rotring pen using indian ink. If you're not wildly keen on that sort of thing you can buy sheets of dry transfer lines, circles, and other shapes, and by cutting the bits you want end up with a transfer pattern which is just the shape of printed circuit you need. You can even buy rolls of thin sticky-tape which is a bit more durable.

Suppose you want to copy a circuit layout which you've used for the Eurobreadboard? Easy enough, you simply use a Eurosolderboard, or as they call it, Euro 2298. The Eurosolderboard is a solderboard which is etched in exactly the same pattern as the Eurobreadboard, and with the same numbering and lettering. Because the pattern is identical, you can use exactly the same layout of components, and to make life easier, the Eurosolderboard is used one way round, with no holes drilled through the tracks.

The idea is that you mount components onto the board in pretty much the same way as you work on the Euroboard. The plain side of the board is placed on the bench, the component lead-wires are tinned, and then the ends of the leads are held touching the correct strips of the board, with the leads point at right angles to the board. A drop of solder will then join the two together, as shown in Fig. 5.2(a), and the job is done. This is the only board you can buy which is lettered and numbered and even if you haven't tried out the circuit on the Eurobreadboard, the Eurosolderboard is a treat to work on.

Now for a really free-range idea. Take a piece of laminate board, a thick straight strip of steel, and a triangular file or a tile-cutter. Using this equipment, you

can cut gaps in the sheet to make a board with lots of parallel copper lines. You can then number and letter them, and use them without drilling, just solder the ends of the leads to the board on the same side as the track (Fig. 5.2(b) if anything you get a better soldered joint than when the component wire has had to come through a hole. When you make your own circuit boards this way, you can choose how close you want the tracks to be — you're not stuck with the 2.5 mm or 3.5 mm that all the manufactured strip boards turn out at. So far, we've had a pretty heavy session of soldering, and it's time now to look at a circuit, just one this month. It's a lot more elaborate than anything you've built so far, though, so you'll have to take your time over the Eurobreadboard layout.

The circuit is of a light-operated alarm — but one which is triggered by a light beam and which has to be reset by a switch. It's the basic circuit of a light-detecting burglar alarm, but for our purpose the alarm bell is replaced by a 6 V bulb so that we can see the action without summoning the police and fire-brigade.

The circuit is shown in Fig. 5.4; it uses six transistors, all NPN types, along with the LDR for light detecting and a 6 V 60 mA bulb for indicating what is happening at the output. It's easier to follow if we look at the transistors in pair, because each pair of transistors forms a circuit that we've used before.

Q1 and Q2 form a trigger circuit, the type called the Schmitt trigger. With no volts on the base of Q1, Q2 is kept conducting because of the current from the 6V supply through R1 and R2 into the base of Q2 a bit above zero, somewhere around 0.4 V. The collector voltage of Q2 will be low, around 0.6 V, because Q2 is conducting so easily.

Now because the emitters are connected together, the emitter voltage of Q1 is the same as the emitter voltage of Q2, around 0.4 V. If we keep the base voltage of Q1 low, then Q1 won't conduct — remember that you need to have the base voltage of an NPN transistor something like 0.5 V higher than its emitter voltage before it conducts. Because the emitter voltage of Q1 is around 0.4 V, we'll need to have the base voltage at around 0.9 V before Q1 can start to conduct.

Into Electronics Construction

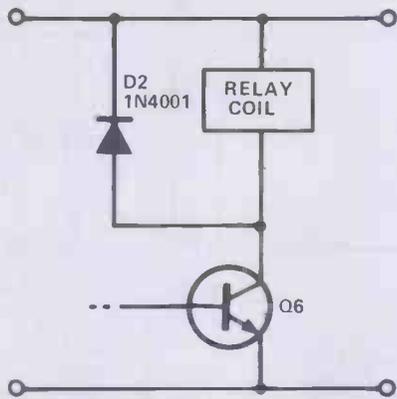


Fig 5.5 Connecting a 6 V 100 mA relay into the alarm circuit.

The base voltage of Q1 depends on how much light hits the LDR though. In darkness, the LDR resistance will be very high, and the voltage across RV1 will be very low, much less than 0.9 V. That makes sure that, in darkness, Q1 stays off and Q2 stays on. When a torch beam hits the LDR, or a light is switched on near it, however, its resistance drops to a much lower value, low enough to hoist the voltage across RV1 (depending on the setting of RV1) to something a bit above 0.9V.

The effect of that will be to switch Q1 on, making Q1 a good conductor, and causing its collector voltage to drop down to about 0.6V. There isn't enough voltage now at the collector of Q1 to keep current flowing into the base of Q2 because the emitter voltage is still at 0.4 V (the current through Q1 ensures that) and we would need something like 0.9 V at the collector of Q1 to switch Q2 on. With the light on, then Q2 stops drawing current.

This 'stop' is pretty sudden, so that the voltage at the collector of Q2 rises suddenly — what does that do to Q3 and Q4? These two are connected as a bistable which has been set by closing K1 and opening it again. When K1 was closed, the voltage at the collector of Q4 dropped to zero, so that no current could flow in Q3. With no current through Q3, the 6 V supply can pass current through R5 and R6 into the base of Q4, keeping this one switched on. When K1 is released, Q3 and Q4 stay as they are, there's no reason for them to change.

Now what happens when light hits the LDR? Nothing! When light hits the LDR it makes the voltage at the collector of Q2 shoot up. Because of C1, the voltage at the cathode of D1 will also shoot up, but D2 doesn't

conduct — it's the wrong way round for that, so that C1 just charges quietly through R10, and the base of Q4 is unaffected.

The real action takes place when the lights go off. By this time your actual burglar has decided that the place is safe and there aren't any alarms, but when the light goes off the LDR, the voltage at the collector of Q2 comes down with a thump. Result is a negative voltage at the base of Q4, and that will cause the voltage at the cathode of D1 to shoot down, go negative. This time the diode conducts, the voltage is the right way round, and so the base voltage of Q4 gets pulled down as well, and that shuts off Q4.

Current now flows through R8, R7 into the base of Q3, turning this transistor on. With Q3 conducting well, the voltage at its collector is low, so there's no voltage to keep Q4 on, and Q4 stays off.

There's another effect too. With Q4 off, current through R8 will also flow through R9 into the base of Q5, and so turn on Q6. Q6 will light the bulb Lp 1 which we're using to indicate an alarm. There's nothing to make Q4 switch back again — if the light goes on again, the voltage rise at the collector of Q2 can't switch Q4 on because D1 blocks current flow in this direction. Lp 1 will stay on until SW 1 is operated to stop the 'alarm' and reset the circuit. For a real alarm, you'll want Q 6 to operate a relay, and the circuit is then modified a bit, as shown in Fig. 5.5. It's quite a cunning circuit, because the alarm doesn't sound until the light has been switched on and then off again, and the alarm can't be stopped by switching on again.

Next month — a little bit of theory, something on amplifiers — and the end of the series! **HE**

ADDITIONAL SHOPPING LIST FOR PART 5

Resistors:



2 x 2k2
1 x 22 k

Semiconductors:

3 x Silicon NPN transistors BFY50 or 22N2219 (or equivalents)

BEASTIES

BY **AH**

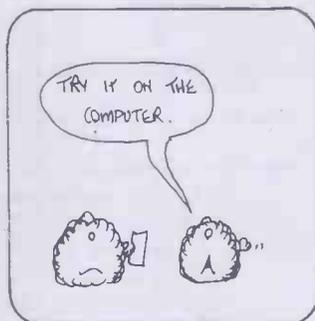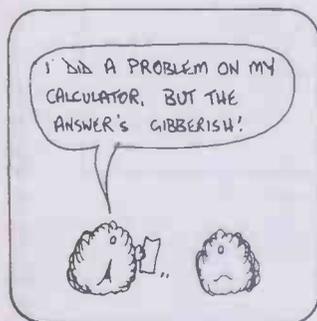


Short Circuit

CASSETTE-RADIO BOOSTER

This amplifier was primarily designed for use as a booster to enable output powers of around 4 to 5 watts RMS to be obtained from a radio/cassette unit. Using a portable radio or cassette unit as a signal source will not provide a Hi-Fi results, but using this set up in conjunction with a speaker of reasonable quality and efficiency gives quite good results at low cost. Of course, the amplifier is also suitable for other applications. It has an input sensitivity of approximately 350 mV. RMS into 10k for maximum output, and an output intended to feed an 8 ohm load.

The circuit uses a well known configuration which has common emitter input stage (Q1) direct coupled to common emitter driver stage (Q2), which is in turn direct coupled to the complementary emitter follower output stage (Q3-Q4). R7 provides virtually 100% negative feedback at DC, giving the circuit approximately unity voltage gain at DC. R1, R2 and R4 form a potential divider which bias the input of the amplifier to about half the supply potential, and the output is also biased to about this level due to the DC unity gain. This bias level gives the optimum unclipped output voltage swing.

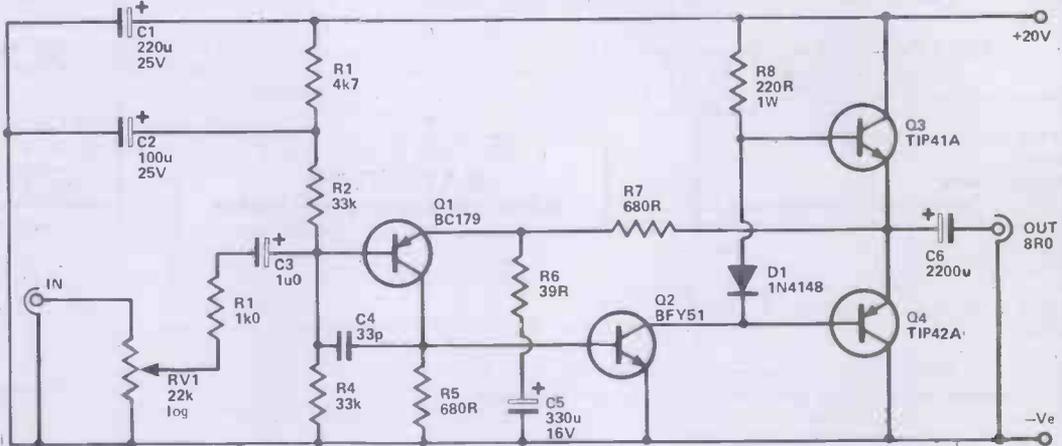

R1 and C2 filter out any hum or noise which might otherwise be coupled from the supply lines to the input via the bias circuit. R6 and C5 are used to decouple some of the feedback at audio frequencies, and thus give the unit a useful voltage gain at these frequencies.

D1 is used to give a small standing bias to the output transistors, and together with the fairly substantial amount of negative feedback used reduces cross-over distortion to an un-

noticeable level. The emitter follower output stage gives the circuit a low output impedance so that the low impedance load can be efficiently driven with the high output currents involved here. Q3 drives the speaker during positive going output excursions while Q4 drives the speaker during negative output excursions. C6 provides DC blocking at the output, and C3 provides the same function at the input. R1 and C4 aid the stability of the circuit. RV1 is a volume control,

and in the amplifiers intended application, results will probably be best if the volume control on the cassette radio is set for a fairly high output (but not so high as to cause clipping), and the volume is adjusted using RV1.

The circuit requires a stabilised supply of about 18 to 22 volts, and capable of providing up to 400 mA. Q2 should be fitted with a clip on TO-5 size heatsink. Q3 and Q4 are both fitted with commercially made, finned, bolt-on heatsinks.

CLASSIFIED INFORMATION

Semi-Display:—

- 1-3 insertions — £4.50 per single column centimetre
- 4-11 insertions — £4.00 per s.c.c.
- 12 insertions — £3.50 per s.c.c.

Classified:—

- 18 pence per word (minimum 25 words)
- Box number on application (Personal ads only)

ALL ADVERTISEMENTS IN THIS SECTION MUST BE PRE-PAID.
Closing date: 2nd Friday in month preceding publication.

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request).

Please insert the advertisement below in the next issue of Hobby Electronics for insertions. I enclose Cheque/P.O. for £..... (Cheques and Postal Orders should be crossed and made payable to Hobby Electronics).

| | | | |
|--|--|--|--|
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |
| | | | |

NAME

ADDRESS

Send to: Margaret Hewitt
HOBBY ELECTRONICS
145 Charing Cross Road,
London WC2H 0EE.
Tel. 01-439 7449.

MEMORY MART

'UK 101' Superboard 4K RAM
Memory Expansion £30 each
2114 1Kx 450 small ns £3.75 each
2708 UV prom 650 small ns £5.00 each

P&P 20p
C.O.O. 60p extra

MEMORY MART

19 Weatherby Gardens
Hartley Wintney, Hants

INTRODUCTION TO MICROPROCESSORS. A beginners book £2.30. Popular Electronic Projects £1.45. Single IC Projects £1.50. 28 Tested Transistor Projects £1.25. Add 35p p&p. — Educational Data & Technical Services, 59 Station Road, Cogenhoe, Northampton NN7 1LU.

ELECTRONIC COMPONENTS & ACCESSORIES:— We offer you a first class service at the right price, all orders processed the same day. Send now for 1980 catalogue 30p refundable on first order over £1.00 or return catalogue within 10 days for full refund to:— **LIGHTNING ELECTRONIC COMPONENTS**, 44 Grassholme, Stonydelph, Tamworth B77 4BZ.

ORIGINAL HI-FI PCB for 3 power: 25-50-100w. £3.50 with data. Free diagrams for 5 projects. Francisco Inverno, Rua Prof. Dr. Virgilio Machado, 25-5 Fr 2745 Queluz, Portugal. Cash with order, by International Money Order only please.

£5 OSCILLOSCOPE. Standard Junk Box Components plus approx. another £5 (total components approx. £12). This unit plugs into TV Aerial socket and converts TV to Oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

D.I.Y. ALARM MODULE



Positive and Negative loops. Negative loop also acts as 24-hr. monitor loop. Pressure mats do not need separate loop. * On/off switch loop N/C break to activate. * Inbuilt electronic siren, only speaker needed. Very low current consumption battery only. Converts to Mains/Battery, auto switching just by adding transformer (12v. A.C.). May be fitted in bell box. PRICE £16.75 inc. VAT and P&P.

ALSO AVAILABLE: Horn speaker, transformer, contacts, bells, mats, cable, bellboxes, etc. S.A.E. list.

SIMMONS DOMESTIC ELECTRICAL (647-5841)
79b-81a MANOR ROAD, WALLINGTON, SURREY

Top Quality, Pre-recorded Videocassettes, the latest films, free lists. From half recommended price. Write now for details. AUSHE, 76 Church Street, Larkhall, Lanarkshire.

FREE 1980 Amtron catalogue with new range of kits and equipment cabinets. Send s.a.e Amtron UK Ltd., 7 Hughenden Road, Hastings, Sussex TN34 3TG. Tel. Hastings 436004.

RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. SAE FOR LISTS. £1.25 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd., 2 Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS. 021-354 9764, or see them at TLC, 32 Cravens Street, Charing Cross, London WC2.

Cheaper than a visit to the pictures. Latest top quality films prerecorded on videocassettes from only £6. Full details from G.T. Technical Video Library (10a HE), 119 Oxford Street, London W1R 1PA.

BBC TV Producer would like to hear from anyone in the Midlands area interested in Robotics. Please contact: John Clarke, Pebble Mill, Birmingham. 021-472 5353 (ext. 2304).

AD INDEX

| | |
|------------------------|---------|
| AMBIT INTERNATIONAL | 2 |
| ARROW AUDIO CENTRE | 18 |
| BARINGLOCK LTD. | 48 |
| BI-PAK SEMICONDUCTORS | 41 |
| BK ELECTRONICS | 56 |
| C.S.C. | 36 |
| DAVID GEORGE SALES | 42 |
| E.D.A. | 66 |
| ELECTROVALUE | 56 |
| GREENWELD | 42 |
| HENRY'S RADIO | 46 |
| ILP | 4 & 5 |
| KRAMER & CO. | 66 |
| MAPLIN | 76 |
| MARSHALLS | 34 |
| METAC | 52 & 53 |
| MIDLAND TRADING CO. | 20 & 21 |
| MINIKITS | 10 |
| MODUS SYSTEMS | 18 |
| VICTOR MORRIS | 30 |
| MURA ELECTRONICS | 29 |
| NIC MODELS | 30 |
| POLAR ENTERPRISES | 29 |
| T. POWELL | 48 |
| POWERTRAN ELECTRONICS | 75 |
| J. W. RIMMER | 48 |
| R.T.V.C. | 9 |
| SPIMIN DEVELOPMENTS | 48 |
| SRU AUTOS | 25 |
| SWANLEY ELECTRONICS | 48 |
| SYMBOLYKA | 24 |
| TECHNOMATIC | 16 |
| TEMPUS | 31 |
| TK ELECTRONICS | 55 |
| VERO | 62 |
| WATFORD ELECTRONICS | 7 |
| WEST HYDE DEVELOPMENTS | 51 |
| WINTJOY LTD. | 22 & 29 |

PRINTED CIRCUITS

and

HARDWARE

Comprehensive range Constructors Hardware and accessories.

Selected range of popular components
Full range of HE printed circuit boards normally ex-stock, same day despatch at competitive prices
P.C. Boards to individual designs
Resist-coated epoxy glass laminate for the d.i.y. man with full processing instructions (no unusual chemicals required)

Affac range of etch resist transfers and other drawing materials for p.c. boards

Send 15p for catalogue.

RAMAR CONSTRUCTOR SERVICES
MASON ROAD
STRATFORD-ON-AVON
WARWICKS, Tm, 4879

CITIZEN BAND AERIALS. 27 Mhz roof/boot mounting, as radio telephone aerial, with cable PL259 plug, £17. Few left. See April H.E. for description. Also Gutter Mount, centre loaded, cable/PL259, £12. While stocks last. Send cheque/p.o., Unifax, 74 Amhurst Park, London N16 5AP.

AERIAL AMPLIFIERS: Improve wear VHF radio and television reception, price £6.00. S.A.E. for leaflets. Electronic Mail Order, Ramsbottom, Lancs. BLO 9AGP.

MAIL ORDER PROTECTION SCHEME

The Publishers of 'Hobby Electronics' are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader, readers are advised to lodge a claim with 'Hobby Electronics' within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will not be considered. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence. For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

BUY SELL EXCHANGE

WE CAN'T PRODUCE RABBITS BUT WE CAN PRODUCE RESULTS

& whether you are buying, selling or exchanging let HE's classified advertisement section work wonders for you.

Ring Margaret Hewitt
on
01-439-7449

Hobby Electronics Book Service



POPULAR ELECTRONICS BOOKS

| | |
|---|-------|
| Sinclair, I. R., Introducing Electronic Systems | £1.95 |
| Sinclair, I. R., Introducing Amateur Electronics | £1.65 |
| Sinclair, I. R., Electronic Fault Diagnosis | £3.55 |
| Sinclair, I. R., Repairing Pocket Transistor Radios | £2.60 |
| Sinclair, I. R., Oscilloscope In Use | £3.10 |
| Sinclair, I. R., Understanding Electronic Components | £4.20 |
| Sinclair, I. R., Understanding Electronic Circuits | £4.20 |
| Kitchen, H. T., Handtools For Electronic Workshop | £2.95 |
| Kitchen, H. T., Electronic Test Equipment | £5.20 |
| Capel, V., How To Build Electronic Kits | £2.35 |
| Oarr, J., How to test almost everything electronic | £3.70 |
| Brown, R. M., How to read electronic circuit diagrams | £5.60 |

AUDIO

| | |
|---|-------|
| Earl, J., Audio Technicians Bench Manual | £3.70 |
| Earl, J., Pickups and Loud Speakers | £3.70 |
| Earl, J., Tuners and Amplifiers | £3.20 |
| Earl, J., Cassette Tape Recorders | £5.40 |
| Earl, J., ABC of Hi-Fi | £4.35 |
| Capel, V., Microphones In Action | £3.15 |
| Capel, V., Improving Your Hi-Fi | £3.65 |
| Capel, V., Creative Tape Recording | £4.20 |
| Hellyer, H. W., Tape Recorders | £4.45 |
| Sinclair, I. R., Audio Amplifiers For Home Construction | £2.85 |

RADIO CONTROL

| | |
|---|-------|
| Drake, J., Radio Controlled Helicopter Models | £4.20 |
| Jeffries, C. R., Radio Control For Model Yachts | £3.85 |
| Safford, E. L., Radio Control Manual | £2.60 |

COOKBOOKS

| | |
|--|--------|
| Tracton, K., BASIC Cookbook | £4.10 |
| Lancaster, D., TTL Cookbook | £7.00 |
| Lancaster, D., RTL Cookbook | £4.65 |
| Lancaster, D., CMOS Cookbook | £8.20 |
| Jong, W., IC Op Amp Cookbook | £10.00 |
| Lancaster, D., T.V. Typewriter Cookbook | £7.75 |
| Lancaster, D., Cheap Video Cookbook | £7.00 |
| Jong, W., IC Timer Cookbook | £7.50 |
| Lancaster, D., Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business) | £4.95 |

QUESTIONS AND ANSWERS

SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.

| | |
|---|-------|
| Coker, A. J., Q & A On Electric Motors | £1.90 |
| Hellyer, H., Q & A On Radios and T.V. | £1.90 |
| Hibberd, R., Q & A On Integrated Circuits | £1.90 |
| Jackson, K., Q & A On Electricity | £1.90 |
| Brown, C., Q & A On Hi-Fi | £1.90 |
| Brown, C., Q & A On Transistors | £1.90 |
| Brown, C., Q & A On Electronics | £1.90 |
| Reddihough, J., Q & A On Colour T.V. | £1.90 |
| Miller, H., Q & A On Electric Wiring | £1.90 |

CONSTRUCTOR GUIDES

| | |
|--|-------|
| Graham, P., Simple Circuit Building | £2.70 |
| Colwell, M., Electronic Diagrams | £2.70 |
| Colwell, M., Electronic Components | £2.70 |
| Colwell, M., Printed Circuit Assembly | £2.70 |
| Ainslie, A., Practical Electronic Project Building | £2.70 |
| Colwell, M., Project Planning and Building | £2.70 |

BEGINNER'S GUIDE

| | |
|--|-------|
| Sinclair, I. R., Beginner's Guide To Tape Recording | £3.45 |
| Sinclair, I. R., Beginner's Guide To Integrated Circuits | £3.45 |
| Sinclair, I. R., Beginner's Guide To Audio | £3.45 |
| King, G. J., Beginner's Guide To Radio | £3.45 |
| King, G. J., Beginner's Guide To Television | £3.45 |
| King, G. J., Beginner's Guide To Colour T.V. | £3.45 |
| Guilou, F., Beginner's Guide To Electric Wiring | £3.45 |

PROJECT BOOKS

| | |
|---|-------|
| Marston, R. M., 110 Cosmos Digital IC Projects For The Home Constructor | £3.95 |
| Marston, R. M., 110 Wave Form Projects For The Home Constructor | £3.95 |
| Marston, R. M., 110 Op Amp Projects For The Home Constructor .. | £3.95 |
| Marston, R. M., 110 Semiconductor Projects For The Home Constructor | £3.95 |
| Marston, R. M., 110 Thyristor/SCR Projects For The Home Constructor | £3.95 |
| Marston, R. M., 110 Electronic Alarm Projects for The Home Constructor | £3.95 |
| Marston, R. M., 110 Integrated Circuits Projects For The Home Constructor | £3.95 |
| Marston, R. M., 20 Solid State Projects For The Car and Garage | £3.20 |
| Marston, R. M., 20 Solid State Projects For The Home | £3.20 |

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service,
Modmags Ltd,
145 Charing Cross Road,
London WC2H 0EE.

★ Prices may be subject to change without notice.

Chromatheque 5000

ETI 5 CHANNEL LIGHTING EFFECTS SYSTEM



Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

**COMPLETE KIT
ONLY
£49.50 + VAT**

BLACK HOLE

As Featured in *ELECTRONICS TODAY INTERNATIONAL* May issue

The **BLACK HOLE** designed by Tim Orr is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine **VIBRATO** (pitch modulation) and a **CHORUS** mode which gives a 'spacey' feel to the sound achieved by delaying the input signal and mixing it back with the original. **Notches (HOLES)**, introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An option of double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has variable sensitivity input, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.


COMPLETE KIT ONLY £49.80 + VAT (single delay line system)
De Luxe version (dual delay line system) also available for £59.80 + VAT

MANY MORE KITS!
including synthesizers, computer, hi-fi amps, tuners, etc.
in our **FREE CATALOGUE**

POWERTRAN

MPA 200

100 Watt Mixer-Amplifier

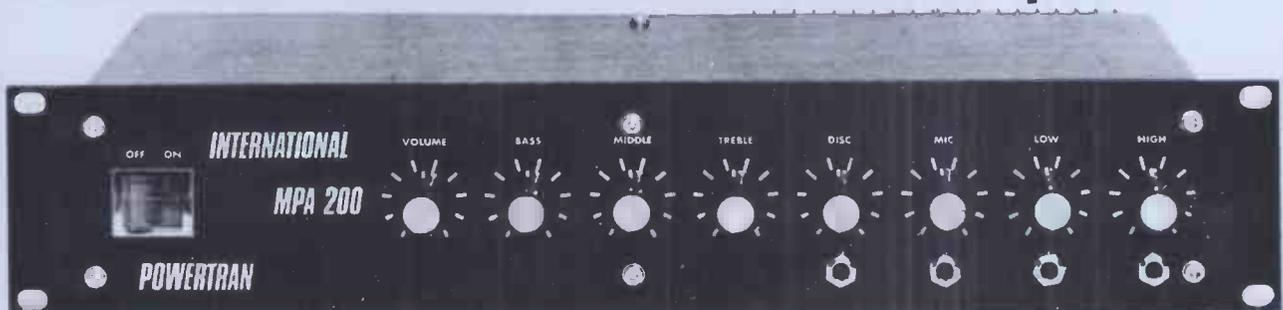

Panel size 19.0" x 3.5". Depth 7.3"

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, control, wire, etc. — complete down to the last nut and bolt.

**COMPLETE KIT
ONLY
£49.90 + VAT**

PRICE STABILITY: Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until July 31st, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m.-12 noon — 1-4.30 p.m. Monday-Thursday

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE
ANDOVER, HANTS SP10 3MM

ANDOVER
(STD 0264) 64455

STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**



Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____

ADDRESS _____



MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:-

P.O. Box 3, Rayleigh, Essex SS6 8LR.

Telephone: Southend (0702) 554155.

Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).

Telephone: Southend (0702) 554000.