

Open Channel News On UKCB Radio

ISSN 0142-6192

July '80  
50p

# Hobby Electronics

**Take Pictures  
Like This With  
Our Flash Trigger  
Project**




**18w Car  
Stereo Booster  
Amp**

**Electronics For The Master Spy**


**Hazard Flasher For Your Car**

**Push-Button Volume  
Control Project**

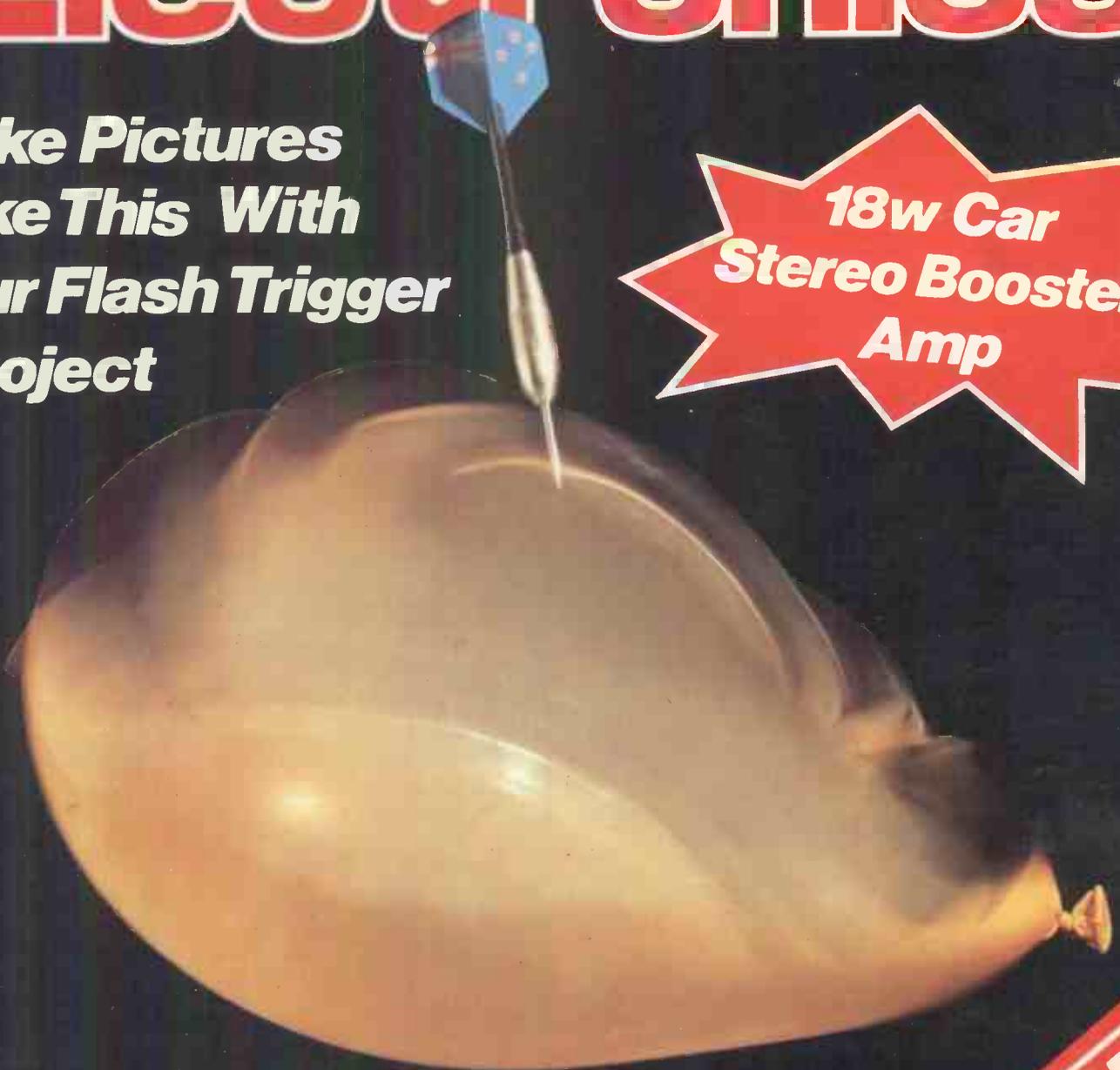

**Electronics In  
The New  
Cameras**

## Complete Audio/Tuner Kits

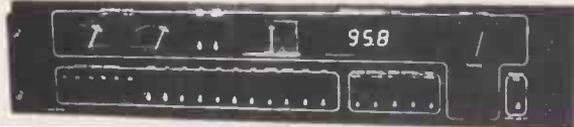

### Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mark III A series 'Reference series' tuner modules .....£171.35 inc.  
Mark III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder .....£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

### Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of preview comments, it seems that many of you are waiting to hear about the matching HMOSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC Input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit .....£178.25 inc. Carr. £5.

### Preamplifier

More features and facilities, thanks to DC switching and control design

Previewing the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape inputs, 2 low pass, 2 high pass active filters, genuine volume - rated loudness, 1dB channel matching, with DC volume, balance, bass and treble controls. Stable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N+, THD -75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

## Semiconductors

### Radio/Communications ICs

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST

CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TDA4420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.95	TDA1220	1.61	KB4413	2.24
TBA120S	1.15	TDA1083	2.24	KB4417	2.53
KB4406	0.80	TDA1062	2.24	MC3357P	3.16
SL1610	1.84	SL1626	2.80		
SL1611	1.84	SL1630	1.86		
SL1612	1.84	SL1640	2.17		
SL1613	2.12	SL1641	2.17		
SL1620	2.50	SL6600	4.31		
SL1623	2.80	SL6640	3.16		
SL1624	3.77	SL6690	3.68		
SL1625	2.50	MC1496	1.44		

### VARICAP DIODES.....

A section from our PL:

BA102	0.35	16:1 ratio AM tuning
BB204	0.41	KV1215 9v triple
BB105	0.41	KV1211 9v dual
BB109	0.31	KV1225 25v triple
MVAM2	1.93	BB212 9v dual

### POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).

2SK133 120v N-ch 100W MOSFET £6.33 2SJ48 Pch complement £6.33  
2SK135 160v N-ch 100W MOSFET £7.29 2SJ50 Pch complement £7.39  
PA101B Kit for 100W MOSFET PA less Heatsink £16.10 (£23 inc heatsink/bkt)

### ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!!). It comfortably supercedes discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. (Replaces HA1457) £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

### Radio Control ICs

We have various RC ICs, including NE544 NES044, and two new ones from OKI

KB4445 - 4 channel dig. prop. FM TX IC. 30mW out (amplifiable) - £2.30 inc  
KB4446 - 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. £2.65  
KB4445/6 pair: £4.75. New 8 page data-sheet 35p + SAE. More RC ICs in list

### CMOS, LPSNTTL, TTL, MPU: Listings in the new pricelist.

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

Coming Soon..... Contain yourselves, RF fans! Not yet ready for a full launch until autumn, but previewed here.

### SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source I/O or 2 IC Mullard synth (for instance) and RF PA for TX. OP. 0.2uV basic sensitivity in HF. Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

CATALOGUES 60p ea. All three for £1.60  
PRICES SHOWN HERE INCLUDE VAT  
POST/PACKAGE CHARGE NOW 75p

Please send an SAE with all enquiries. Phone orders by ACCESS but minimum £5. Callers welcome

**ambit**  
INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 5SG

## Radio/Audio/Communications Modules

### LW-MW-SW-DC tuned and switched

91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands  
MW/LW: £15.58 +1SW £16.73



### VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

### Pilot Cancel PLL Stereo decoders

944378-2  
£26.45

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output



### Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

### Various digital frequency displays

The World's largest range of receiver DFM's is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility - 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



## Components

### Crystal Filters

Most popular types are available ex-stock, and in quantity.

10.7MHz	25kHz Channel spacing 8pole	£16.67
	12½kHz	£17.82
	2.4kHz SSB	£19.78
	Monolithic dual roofing filter	£2.30
34.5MHz	1.3dB loss, 80dB stopband HF	
	first filter in synth. RX	£36.80
RC XTALS	FM pairs (no spilt)	£3.74
	AM pairs	£3.57
USB/LSB	Xtals for 10.7SSB filter	£2.88 ea



### Piezo Sounders

The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz). The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)

### Keyboard switches and caps

From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyboards, and data entry keyboard switches. The SCMB1101 is shown here, with the KT5 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCMB1101: 17p, KT5: 16p - or 29p/pair



### LCD CLOCKS

Clocks use 1.5v at 15uA only.

### LCD DVM

DVM 9v/1mA

CM161: 7mm LCD 12/24hr, alarms etc £11.44 each  
CM172: 13mm, 12hr, alarms, timer etc £14.32 each  
CM174: 13mm, 12hr, min/sec stopwatch £14.32 ea  
DVM 176: ICM7106 based LCD 3½digit £22.36 each



## WHAT'S NEW at AMBIT

### NEW PRICELIST/SHORTFORM:- 28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

### POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :

£1.50 each - or free with pairs of HMOS and the PA101B

Everything you should know about HMOSFET devices theory and applications.

Parts 1-3  
AMBIT catalogues  
60p ea, or  
£1.60 the lot.

# Hobby Electronics

**JULY 1980 Vol. 2 No.9**

**Editor:** Steve Braidwood, G3WKE.  
**Assistant Editor:** Rick Maybury.  
**Project Editor:** Keith Brindley  
**Art Director:** Diego Rincon



See page 15



See page 11



See page 23

**Technical Artists:** Paul Edwards, Tony Strakas.

**Advertisement Department:** Group  
 Advertisement Manager: Christopher Surgenor;  
 Advertisement Manager: Steve Rowe;  
 Advertisement Representative: Roy Perryment,  
 Advertisement Production Controller:  
 Sandie Neville.

**Editorial Secretary:** Halina Di-Lallo.

**Managing Director:** T. J. Connell.

## PROJECTS

- SOUND-OPERATED FLASH TRIGGER** ..... 11  
*Catch A Speeding Bullet, A Breaking Window, A Golf-Ball Being Struck, A Balloon Popping*
- 18W+18W CAR STEREO BOOSTER** ..... 23  
*Hear Your Stereo Over The Road Noise, Have A Party In Your Car, Entertain Your Neighbours*
- PUSH-BUTTON VOLUME CONTROL** ..... 37  
*Three Experimenter's Projects; A Voltage-Controlled Volume Control, A Push-Button Voltage Controller (For Interfacing With A Remote-Control System?), And A LED Voltage (Therefore Volume) Monitor.*
- CAR HAZARD FLASHER** ..... 62  
*A Solid-State Flasher To Give Turn Indication Or Hazard Flash.*
- SHORT CIRCUITS** ..... 20, 26, 42, 45  
*Infra-Red Intruder Alarm, Speech Processor, Table Lamp, Voice-Operated Fader.*

## FEATURES

- ELECTRONICS IN PHOTOGRAPHY** ..... 15  
*Cameras Are Changing, Fast, Thanks To Electronics. Phil Gerring Takes You Through The Viewfinder.*
- ELECTRONIC ESPIONAGE** ..... 28  
*Today's Spy Has Put Aside His Walther PPK And Taken Up His Soldering Iron.*
- KIT REVIEWS: TWO TANDY KITS** ..... 46  
*Pete Howells Builds A Push-Button Dimmer And An LED VU Meter.*
- BREAKER ONE-FOUR: OPEN CHANNEL** ... 49  
*Our 'Legalise CB' Campaign Isn't Over Yet. Read About Our Progress.*
- PIEZO ELECTRICITY** ..... 56  
*Sparks, Squeaks And Squeezes From Ian Sinclair.*
- INTO ELECTRONICS CONSTRUCTION** ..... 67  
*Another In Ian Sinclair's Beginners' Series.*

## NEWS & INFO

- MONITOR, We've Got News For You** ..... 6
- SPECIALS, Further Reading From Modmags** ..... 10
- HE AUGUST: In-Car Electronics, Teletext, Car Equaliser, Gas Detector, Photo Timer, Pass-The-Loop, Vibration Detector, Crimson Review** ..... 21
- SUBSCRIPTIONS, Make Sure Of Your Copy** ..... 26
- CLEVER DICK** ..... 35
- READERS OFFER** ..... 43
- ETI JULY** ..... 59
- CT JULY** ..... 60
- HOBBYPRINTS, BACK NUMBERS** ..... 65
- BINDERS** ..... 65
- BOOKS** ..... 74

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.


**Hobby Electronics**, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002.  
**Published** by Modmags Ltd.  
**Distributed** by Argus Distribution Ltd, 12-18 Paul St., London EC2A 4JS.  
**Printed** by QB Ltd, Colchester.

**Copyright:** All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing kits of the projects must be sought from the Publisher. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally.

© Copyright 1980  
 Modmags Ltd




# Simply ahead...

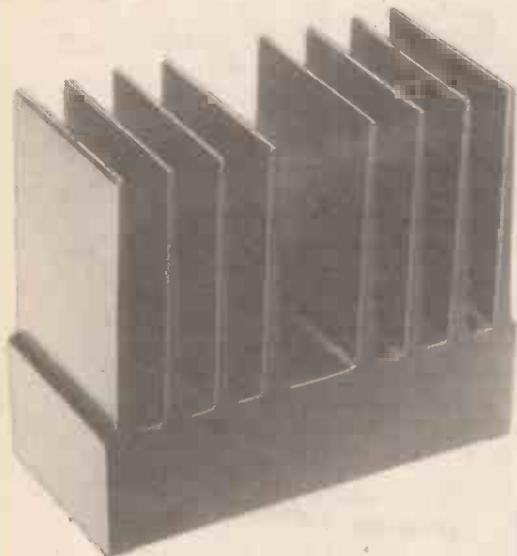

ILP PRE-AMPS ARE  
COMPATIBLE WITH ALL  
ILP POWER AMPS AND PSUs
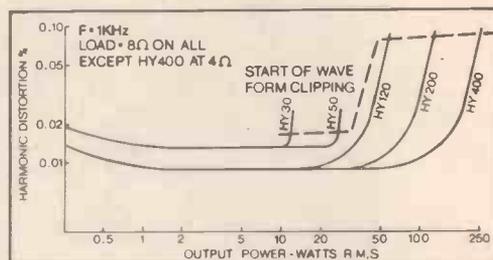
## POWER AMPLIFIERS

ILP Power Amplifiers are encapsulated within heatsinks designed to meet total heat dissipation needs. They are rugged and made to last a lifetime. Advanced circuitry ensures their suitability for use with the finest loudspeakers, pickups, tuners, etc. using digital or analogue sound sources.



Model	Output Power R.M.S.	Distortion Typical at 1KHz	Minimum Signal/Noise Ratio	Power Supply Voltage	Size in mm	Weight in gms	Price + V.A.T.
HY30	15 W into 8 Ω	0.02%	100 dB	-20 -0 +20	105x50x25	155	£6.34 + 95p
HY50	30 W into 8 Ω	0.02%	100 dB	-25 -0 +25	105x50x25	155	£7.24 + £1.09
HY120	60 W into 8 Ω	0.01%	100 dB	-35 -0 +35	114x50x85	575	£15.20 + £2.28
HY200	120 W into 8 Ω	0.01%	100 dB	-45 -0 +45	114x50x85	575	£18.44 + £2.77
HY400	240 W into 4 Ω	0.01%	100 dB	-45 -0 +45	114x100x85	115K g	£27.68 + £4.15

Load impedance - all models 4 Ω - ∞  
Input sensitivity - all models 500 mV  
Input impedance - all models 100K Ω  
Frequency response - all models 10Hz - 45KHz - 3dB

## POWER SUPPLY UNITS



ILP Power Supply Units with transformers made in our own factory are designed specifically for use with ILP power amplifiers and are in two basic forms - one with circuit panel mounted on conventionally styled laminated transformer, for smaller PSU's - in the other, for larger PSU's, ILP toroidal transformers are used which are half the size and weight of laminated equivalents, are more efficient and have greatly reduced radiation.

PSU 30 ± 15V at 100mA to drive up to 12 x HY6 or 6 x HY6-6 £4.50 + £0.68 VAT

THE FOLLOWING WILL ALSO DRIVE ILP PRE-AMPS

PSU 36 for 1 or 2 HY30's £8.10 + £1.22 VAT

PSU 50 for 1 or 2 HY50's £8.10 + £1.22 VAT

PSU 60 with toroidal transformer for

1 HY 120 £9.75 + £1.46 VAT

PSU 70 with toroidal transformer for 1 or

2 HY120's £13.61 + £2.04 VAT

PSU 90 with toroidal transformer for

1 HY200 £13.61 + £2.04 VAT




PSU 180 with toroidal transformer for

1 HY400 or 2 x HY200 £23.02 + £3.45 VAT



AVAILABLE ALSO FROM WATFORD ELECTRONICS, MARSHALLS AND CERTAIN OTHER SELECTED STOCKISTS.

# this time with two new pre-amps

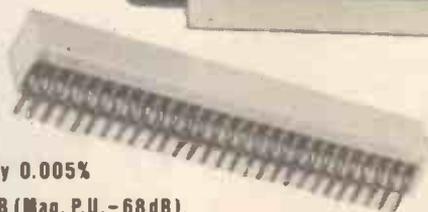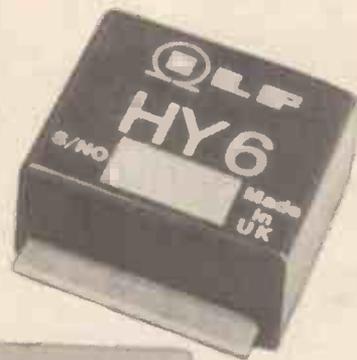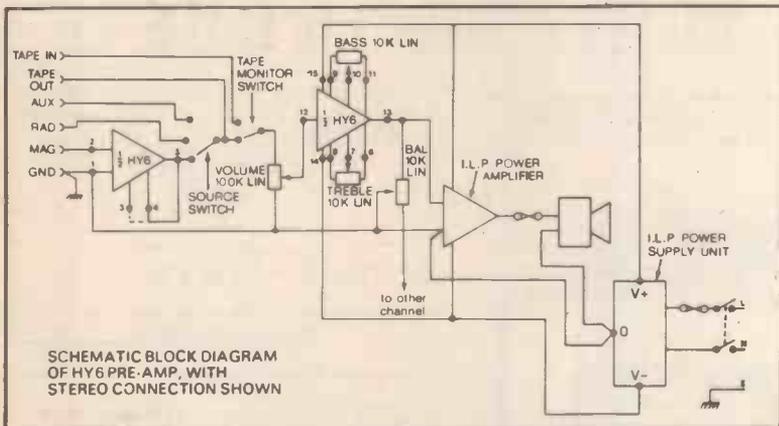

## HY6 mono HY6-6 stereo

When ILP add a new design to their audio-module range, there have to be very special reasons for doing so. You expect even better results. We have achieved this with two new pre-amplifiers – HY6 for mono operation, HY6-6 for stereo. We have simplified connections, and improved performance figures all round. Our new pre-amps are short-circuit and polarity protected; mounting boards are available to simplify construction.

Sizes – HY6 – 45 x 20 x 40 mm HY6-6 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity – Mag. PU – 3mV. Mic – selectable 1-12mV. All others 100mV. Tape O/P – 100mV. Main O/P – 500mV. Frequency response – D.C. to 100KHz – 3dB.

**HY6** mono

£5.60

+ VAT 84p

**HY6-6** stereo

£10.60

+ VAT £1.53

Connectors included

B6 Mounting Board

78p + 12p VAT

B6-6 Mounting Board

99p + 15p VAT

- LOW DISTORTION - Typically 0.005%
- S/N RATIO - Typically 90 dB (Mag. P.U. – 68 dB).
- HIGH OVERLOAD FACTOR – 38 dB on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS.
- REQUIRE ONLY POTS, SWITCHES, PLUGS AND SOCKETS.
- COMPATIBLE WITH ALL ILP POWER AMPS AND PSUs.
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$ V to  $\pm 50$ V.

NO QUIBBLE  
5 YEAR GUARANTEE  
7-DAY-DESPATCH ON ALL ORDERS  
BRITISH DESIGN AND MANUFACTURE  
FREEPOST SERVICE  
- see below

★ ALL U.K. ORDERS DESPATCHED POST PAID

### HOW TO ORDER, USING FREEPOST SYSTEM

Simply fill in order coupon with payment or credit card instructions. Post to address as below but do not stamp envelope – we pay postage on all letters sent to us by readers of this journal.



**ELECTRONICS LTD.**

FREEPOST 6 Graham Bell House, Roper Close,  
Canterbury, Kent CT2 7EP.  
Telephone (0227) 54778

Telex 965780

Please supply .....

..... Total purchase price £.....

Enclose Cheque  Postal Orders  International Money Order

Please debit my Access/Barclaycard Account No.....

NAME .....

ADDRESS .....

Signature .....

# Monitor

## WORZEL PROTECTION



If we'd expected any printable responses we'd have used this photo in a caption contest. The truth is the machine at the bottom left is a radio-controlled trolley which whisks Barbara Windsor through Southern Television's 'Worzel Gummidge' series. The photo is from Chromatronics of Harlow who protected Barbara from the effects of interference on the control channel.

## VIDEO VILLAINS

Two new cartridges for the Atari Video Computer this month. The first is entitled 'Superman' and jolly good fun it is too. The game is essentially for one player and involves what Atari aptly describe as an adventure. You, the player controls Superman. The game begins by Clark Kent walking the streets of Metropolis, suddenly a bridge blows up, Clark Kent has to find his way to a telephone kiosk to change into Superman. From then on you have a number of tasks to complete, Lex Luthor and his five henchmen must be rounded up, the bridge re-built and the deadly Kryptonite missiles must be avoided. If Superman comes into contact with this rather nasty (and noisy) stuff he must seek out Lois Lane to regain his powers. What makes this game unusual is the field of play, rather than restrict the characters to one screen area, you have the whole of the city of Metropolis to play in. You can move a block at a time by traversing the screen in any direction whereupon a new block appears. You can also

## REVOLUTIONARY METER

How about this portable digital tachometer, designed to work in areas of high ambient light? Made by Power Instruments Inc of the USA this instrument, designated 1893, costs around £165 from the UK importers. It will measure RPM instantly at between 1/4" to 30" distance from a rotating object, using a beam of reflected light. To make the measurement a small piece of reflective tape is attached to the object and the beam from the tachometer is pointed at the tape.



Accuracy is assured by the internal quartz controlled oscillator, typically this will be  $\pm 1$  RPM over the range 10-100000 RPM.

It comes complete with carrying case, marking tape, disc set and two feet of reflective tape. For more information contact: Electronic Brokers, 49/53 Pancras Road, London NW1 2QB.

travel around the city via the subway system. The game is played without a preset time limit but with a clock display in the screen area. So far the best time to complete all the tasks and return (as Clark Kent) to the Daily Planet Building is two minutes 52 seconds. That sounds quite impressive, and it is but the first time it was switched on our ace Superman, player took more than two hours to complete the game. This game is a real challenge and we defy anyone to get bored with it or beat 2 minutes 52 seconds.

Game number two is the long awaited version of Space Invaders. This cartridge has an amazing 112 variations on the Space Invaders theme ranging from a simple two player set-up, to a really nasty game involving invisible monsters. As usual both these cartridges are available from that well known purveyor of games NIC in Tottenham. Superman costs £23.95, Space Invaders £29.95.

## NOISE ANNOYS

This nifty, state-of-the-art little gadget looks set to help a lot of people lead quieter lives. It is the PMP-20 audio frequency test meter. It will measure very high levels of noise (-50 to 30dB) over the frequency range of 30Hz to 20 kHz. As you can see this instrument is fully portable and runs from its own internal batteries. The LCD display flashes about two hours before the batteries are exhausted, if the voltage drops any further the meter switches off to avoid giving false readings. More information is available from Wandel & Golterman (UK) Ltd, 40-48 High Street, Acton, London W3.

## HOBBYPRINTS


Since we're sure you've all rushed out to buy the Project Special, here are some things you should know about the Hobbyprints advert in it. Firstly, the listing is incomplete; Sheet 103 also has the Graphic Equaliser, and Sheet 105 also has the Photographic Timer. Second, if you want to build the Hobbytune, you'll also need Hobbyprint L (small), because that's where the keyboard and tuning board are.

As we are changing manufacturers, there will be some delay in the production of Hobbyprints S, T and U.
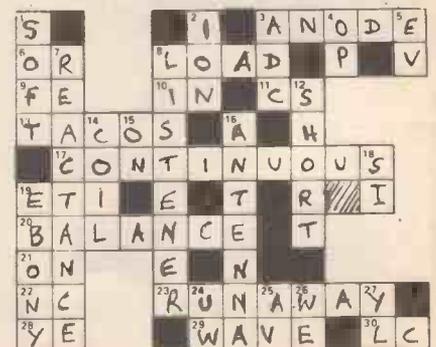
## HEATH CONTEST RESULT

Despite a few problems with the presentation of this contest we had a fabulous response, with approximately 500 correct entries. The contest was a little more difficult than we had planned due to a couple of non-essential clues going astray following production problems on the May issue. Some people were also concerned about the indeterminate status of the square down-one-and-one-to-the-left of square 18. This should be blacked-in or left blank. Still, it was a fair contest, everyone started with the same information.

The winning entry was drawn on Friday, May 16th, and the prize goes to Mr. T. N. Backler of Capel St Mary, Ipswich. He receives a Heathkit 1M-2215 hand held LCD multimeter kit, courtesy of Heath Electronics (U.K.) Ltd.



The correct Solution to our Crossword.

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P.P. Add 40p to ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE. ACCESS ORDERS WELCOME.

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.  
We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Bus Station: Watford High Street. Open Monday to Saturday. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type.  
400V: 1nF, 1n5, 2n2, 3n3, 4n7, 6n8, 10n, 15n 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 62p; 1µF 64p; 2µF 82p; 4µF 7 85p; 100V: 39F, 100n, 150n, 220n 11p; 330n, 470n 19p; 680n, 1µF 22p; 1µ5, 2µF 23p; 4µF 7 36p; 1000V: 10nF, 15n 20p; 22n 22p; 47n 26p; 100n 38p; 470n 53p; 1µF 175p.

**POLYESTER RADIAL LEAD CAPACITORS:** 250V.  
10n, 15n, 22n, 27n 5p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p; 680n 19p; 1µF 22p; 2µF 23p; 4µF 7 85p.

**ELECTROLYTIC CAPACITORS:** Axial lead type (Values are in µF). 500V: 10 50p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 8p; 15, 22, 47, 32, 50 12p; 63, 100, 200, 330, 500, 750, 50V: 50, 100, 220, 250, 470, 330 10p; 680, 40V: 22, 33, 10p; 100, 12p; 220, 330, 85p; 630, 85p; 35V: 33, 10p; 330, 47, 32p; 1000, 49p; 25V: 10, 22, 47, 30, 10p; 8p; 160, 220, 250, 330, 470, 25p; 64V: 100, 1000, 35p; 1500, 40p; 2200, 45p; 3300, 77p; 4700 85p; 18V: 10, 47, 68, 7p; 100, 125, 8p; 220, 330, 14p; 470, 20p; 1000, 150p, 30p; 2200, 34p.

**TANTALUM BEAD CAPACITORS:** 35V: 0.1µ, 0.22, 0.33, 0.47, 0.68, 1.0µ, 2µ, 3µ, 4.7, 25V: 10, 20, 20V: 6.8, 18V: 2µ, 4µ, 10, 15p, 18V: 22, 25p; 47, 100, 220, 200, 80V: 10V: 15, 22, 33, 24p; 100 35p; 6V: 47p; 68, 100 28p; 3V: 100 20p.

**MYLAR BEAD CAPACITORS:** 100V: 0.001, 0.002, 0.005, 0.01µF 6p; 0.015, 0.02, 0.04, 0.05, 0.056µF 7p; 0.1µF, 0.2µF, 50V: 0.47µF 12p.

**MINIATURE TYPE TRIMMERS:** 2.5-6pF: 3-10pF: 10-40pF: 5-25pF: 5-45pF: 60pF: 88pF

**COMPRESSION TRIMMERS:** 3-40pF: 10-80pF: 25-190pF: 100-500pF 45p 1250pF 33p

**POLYSTYRENE CAPACITORS:** 10pF to 1nF 8p; 1.5nF to 10nF 10p

**SILVER MICA (Values in pF):** 3-3, 4-7, 6-8, 10, 12, 18, 22, 33, 47, 50, 88, 75, 120, 85, 100, 120, 150, 180 11p each; 220, 250, 270, 300, 330, 360, 390, 600, 820 16p each; 1000, 1200, 1800, 2200 21p each.

**CERAMIC CAPACITORS 50V:** 0.5pF to 10nF 4p; 22n to 47n 5p, 100n, 7p.

**EURO BREADBOARD £5.20.**

**VOLTAGE REGULATORS**

1A	T03	+ve	-ve	
5V	7805	145p	7905	220p
12V	7812	145p	7912	220p
15V	7815	145p		
18V	7818	145p		
1A	TO220	Plastic Casing		
5V	7805	60p	7905	65p
12V	7812	60p	7912	65p
15V	7815	60p	7915	65p
18V	7818	60p	7918	65p
24V	7824	60p	7924	65p
100mA	TO92	Plastic Casing		
5V	78L05	30p	79L05	65p
6V	78L06	30p		
8V	78L08	30p		
12V	78L12	30p	79L12	65p
15V	78L15	30p	79L15	65p

**JACKSONS VARIABLE CAPACITORS**

**DIODES**

**ZENERS**

**NOISE**

**BRIDGE RECTIFIERS**

**TRIACS**

**DIAC**

**VERO BOARD**

**TTL 74**

7400	11	74125	45	74LS74	40	4021	105	4432	1050	LM390	80
7401	12	74126	55	74LS75	45	4022	95	4435	1050	LM381	145
7402	12	74127	55	74LS76	45	4023	25	4440	950	LM382	125
7403	14	74128	65	74LS83	105	4024	75	4450	350	LM386	99
7404	14	74129	65	74LS85	105	4025	25	4451	350	LM387	150
7405	18	74130	85	74LS90	50	4026	180	4452	-	LM1458	40
7406	48	74131	90	74LS92	75	4027	82	4490F	750	LM3900	60
7407	48	74132	90	74LS93	75	4028	105	4501	28	LM3909N	70
7408	22	74133	90	74LS95	115	4029	60	4502	125	LM3911	125
7409	22	74134	145	74LS96	180	4030	225	4503	75	LM3914	240
7410	22	74135	150	74LS107	45	4031	125	4506	75	M252	625
7411	25	74136	150	74LS109	75	4032	175	4507	60	M253AA	1150
7412	20	74137	75	74LS112	80	4033	210	4508	325	MCI304P	260
7413	33	74138	75	74LS113	65	4034	125	4510	99	MCI310	149
7414	52	74139	80	74LS114	48	4035	115	4511	150	MCI312P	195
7415	31	74140	185	74LS122	70	4036	365			MCI458	45
7416	31	74141	99	74LS123	95	4037	118			MCI488	85
7417	31	74142	99	74LS124	180	4038	360			MCI489	90
7418	31	74143	99	74LS125	60	4039	105			MCI495	350
7419	31	74144	99	74LS126	60	4040	80			MCI496	92
7420	26	74145	99	74LS127	60	4041	80			MCI500	79
7421	32	74146	120	74LS128	85	4042	95			MCI503AP	120
7422	32	74147	120	74LS129	85	4043	95			MCI504	120
7423	32	74148	120	74LS130	85	4044	95			MCI505	120
7424	32	74149	120	74LS131	85	4045	95			MCI506	120
7425	32	74150	120	74LS132	85	4046	95			MCI507	120
7426	32	74151	120	74LS133	85	4047	95			MCI508	120
7427	32	74152	120	74LS134	85	4048	95			MCI509	120
7428	32	74153	120	74LS135	85	4049	95			MCI510	120
7429	32	74154	120	74LS136	85	4050	95			MCI511	120
7430	32	74155	120	74LS137	85	4051	95			MCI512	120
7431	32	74156	120	74LS138	85	4052	95			MCI513	120
7432	32	74157	120	74LS139	85	4053	95			MCI514	120
7433	32	74158	120	74LS140	85	4054	95			MCI515	120
7434	32	74159	120	74LS141	85	4055	95			MCI516	120
7435	32	74160	120	74LS142	85	4056	95			MCI517	120
7436	32	74161	120	74LS143	85	4057	95			MCI518	120
7437	32	74162	120	74LS144	85	4058	95			MCI519	120
7438	32	74163	120	74LS145	85	4059	95			MCI520	120
7439	32	74164	120	74LS146	85	4060	95			MCI521	120
7440	32	74165	120	74LS147	85	4061	95			MCI522	120
7441	32	74166	120	74LS148	85	4062	95			MCI523	120
7442	32	74167	120	74LS149	85	4063	95			MCI524	120
7443	32	74168	120	74LS150	85	4064	95			MCI525	120
7444	32	74169	120	74LS151	85	4065	95			MCI526	120
7445	32	74170	120	74LS152	85	4066	95			MCI527	120
7446	32	74171	120	74LS153	85	4067	95			MCI528	120
7447	32	74172	120	74LS154	85	4068	95			MCI529	120
7448	32	74173	120	74LS155	85	4069	95			MCI530	120
7449	32	74174	120	74LS156	85	4070	95			MCI531	120
7450	32	74175	120	74LS157	85	4071	95			MCI532	120
7451	32	74176	120	74LS158	85	4072	95			MCI533	120
7452	32	74177	120	74LS159	85	4073	95			MCI534	120
7453	32	74178	120	74LS160	85	4074	95			MCI535	120
7454	32	74179	120	74LS161	85	4075	95			MCI536	120
7455	32	74180	90	74LS162	110	4076	95			MCI537	120
7456	32	74181	290	74LS163	100	4077	95			MCI538	120
7457	32	74182	88	74LS164	164	4078	95			MCI539	120
7458	32	74183	145	74LS165	165	4079	95			MCI540	120
7459	32	74184	145	74LS166	166	4080	95			MCI541	120
7460	32	74185	145	74LS167	167	4081	95			MCI542	120
7461	32	74186	145	74LS168	168	4082	95			MCI543	120
7462	32	74187	145	74LS169	169	4083	95			MCI544	120
7463	32	74188	145	74LS170	170	4084	95			MCI545	120
7464	32	74189	145	74LS171	171	4085	95			MCI546	120
7465	32	74190	135	74LS172	105	4086	95			MCI547	120
7466	32	74191	135	74LS173	105	4087	95			MCI548	120
7467	32	74192	135	74LS174	147	4088	95			MCI549	120
7468	32	74193	135	74LS175	110	4089	95			MCI550	120
7469	32	74194	105	74LS176	110	4090	95			MCI551	120
7470	41	74195	130	74LS177	110	4091	95			MCI552	120
7471	41	74196	130	74LS178	110	4092	95			MCI553	120
7472	31	74197	90	74LS179	125	4093	95			MCI554	120
7473	40	74198	195	74LS180	125	4094	95			MCI555	120
7474	34	74199	145	74LS181	295	4095	95			MCI556	120
7475	34	74200	145	74LS182	295	4096	95			MCI557	120
7476	41	74201	195	74LS183	295	4097	95			MCI558	120
7477	41	74202	195	74LS184	295	4098	95			MCI559	120
7478	41	74203	195	74LS185	295	4099	95			MCI560	120
7479	41	74204	195	74LS186	295	4100	95			MCI561	120
7480	41	74205	195	74LS187	295	4101	95			MCI562	120
7481	41	74206	195	74LS188	295	4102	95			MCI563	120
7482	41	74207	195	74LS189	295	4103	95			MCI564	120
7483	41	74208	195	74LS190	295	4104	95			MCI565	120
7484	41	74209	195	74LS191	295	4105	95			MCI56	

## News from the Electronics World

### SUITE YOURSELF



We could say that this is the new lightweight, all purpose anti-fallout sunbathing suit but we won't. Instead we'll tell you all, how, for just £400 you can enroll on the Underwater NDT Technicians Course at Fort Bovisand. NDT stands for Non-Destructive Techniques, presumably that means you won't be blowing things up, anyway it all sounds like good fun. At the end of the course, if you're still with it and have passed the exams you will qualify for the new CSWIP certificate that means you can go and do non-destructive things underwater. Contact The Plymouth Ocean Projects Limited, Fort Bovisand, Plymstock, Nr Plymouth in Devon for details.

### TECHNICAL QUERIES

We have decided to streamline our postal technical query service. In future all known errors and alterations will be filed on Data Cards, one per article or project. Whenever possible, queries will be answered by sending out a photocopy of the relevant card(s). Please bear the following points in mind:


- We can't help you if you just say "It doesn't work". Try to isolate which section of the circuit is giving you problems. Our article on Project Fault Finding in December '79 HE gives useful hints on this.
- Try to be concise. We can give you a better service if we don't have to play 'Spot the Query' with a six page letter.
- Our engineers have good reasons to use the components they do — so don't change them to unspecified types. Similarly we cannot answer queries about modifications you have made to our projects.
- We cannot answer enquiries on articles, etc, not from our magazines, and we cannot undertake design work of any sort for individuals.
- Please don't ask questions that can be answered by reading adverts in the magazine.
- Please enclose a stamped self-addressed envelope (preferably foolscap) or International Reply Coupons and write the name of the project or article on the back (e.g. "Electronic Ignition, April '80 HE"). Any enquiries without an sae will not get a personal replay.
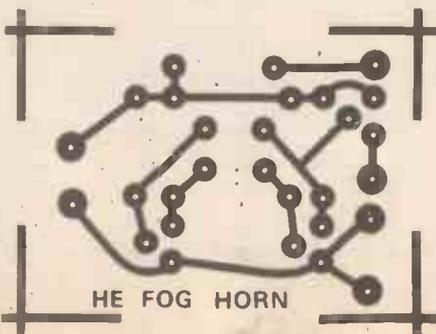
### NEW BUTTON BOX

Over the past few months there seems to have been a distinct lack of new calculators. We can remember back to last year when it seemed that Casio sent us news of at least five new calculators a month. Ah well, times have changed, the calculator market has been completely swamped (to say the least) and there really isn't too many more functions that can be crammed onto an IC. (Remember the days when it was actually considered to be really with it just because your calculator has a 'Constant' button. These days you couldn't hold your head up in decent company if you didn't have at least 200 scientific functions, bubble memory, alphanumeric display and thirty year battery life with solar powered back up systems for the nuclear pile).




It was therefore most intriguing to receive news of this innocuous looking little calculator from Commodore. Did it have an in-built miniature VDU, would the memory have the capacity to store all human knowledge in a chip the size of a pin head? Actually no, it is just a simple, honest to goodness calc called the LC4512. Nothing really remarkable, the 8+2 digit display will show you the results of all the in-built scientific functions and will cost around £15. Not startling really but then sometimes it does us good to appreciate just how much technology we have all come to take for granted in the last few years. Bring back the mechanical adding machine!


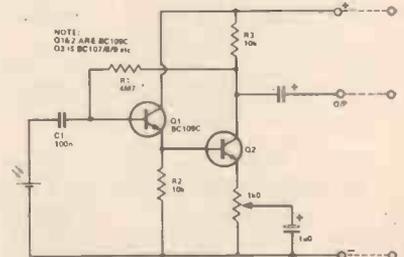
### NBTV

We received a letter from Doug Pitt the other day. He is the chairman of the Narrow Bandwidth TV Association, apparently he has received rather a lot of letters concerning the feature he wrote for us a couple of months ago. It seems that some of you noticed that Fig 11 in part two had some of the values missing. Poor Mr Pitt was actually blameless, it was all our fault, so by way of an apology we have the diagram printed below, this time with the missing values in their proper places.



### SILICON SOCCER

No, this hasn't got anything whatsoever to do with TV games, it concerns Leicester City Football Club using a microcomputer system to sort out all their ticketing problems.

The big bonus, as far as using a computer is concerned, will be the easing of paperwork for advance bookings and season tickets.

They acquired the computer for a £20 000 transfer fee from Geest Computer Services. This has one program that the fans will never see.

### CAPTION COMPETITION

Cease, desist, send us no more. The caption competition in the April Issue was meant to be a joke. You should have realised by the closing date (April 1st). Well, so many of you took the trouble to write in that we'll have to dish out a few prizes so we are sending the best five a Tee Shirt each. They are: Richard Small in Nottingham, M. Casey in Hendon, 'Micro Man', Berkshire, D. Green in Arundel and Campbell McKay, BFPO 10.

We won't be printing any of the entries because they are all disgusting (but funny!).

### ERRATA

It has come to our notice that someone switched the PCB foil pattern for the Fog Horn project last month (P65) for another Egg Timer PCB. The correct PCB is published left. If we ever catch those responsible you may be assured that the noises they will be making will be considerably louder than any Fog Horn!

You may have noticed the odd numbering of the diagrams in Hobby Chit-Chat last month. To correct this, add one to each reference in the text after Fig. 3, i.e. Fig. 4 becomes Fig. 5 and so on.

# SUPERIOR QUALITY AND RELIABILITY

## CASIO'S NEW EXECUTIVE WATCH

**79CS-51B ALARM CHRONOGRAPH**  
Full month calendar, tone control, hourly chimes



Hours, minutes, seconds, am/pm and date. Calendar display: Day, date, month and year. Monthly calendar from the year 1901 to 2099. 1/10 sec. stopwatch to 12hrs. Net, lap, 1st & 2nd. 24-hour alarm with 10 step tone control. Hourly chimes, backlight, lithium battery. Stainless steel case 8.6mm thick. Mineral glass, water resistant. (RRP £44.95)

**£39.95**

## OUR BEST-SELLING WATCH

**CASIO C-80 CALCULATOR WATCH**

(Finger-touch keyboard). Hours, minutes, seconds, am/pm, day, date, month, auto calendar pre-programmed to 2009. Professional 24-hour stopwatch: net, lap, 1st & 2nd place to 1/100 sec. Dual time. (24-hour). Nightlight, 8 digit calculator.

Water resistant. Glass. Black resin case/strap. 44.9mmx35.8x10.2mm

**ONLY £24.95**

Hundreds sold!



**F-80.** As above but with black resin case/strap with S/S back and front trim.

**£19.95**

**NOW AVAILABLE GOLD PLATED**

**83 QGS-41B (RRP £34.95)**

**£29.95**

F-8C £8.95; 111QS-34B £14.95; F-200 £12.95; 95QS-42B £17.95; 95QS-36B £19.95; 56QS-38B £24.95; 56QS-50B £34.95; 81QS-40B £24.95; 29CS-49B £29.95.


**LADIES' CASIO** 10 models from **£12.95**

## NEW 11-NOTE MELODY MAKER

**CASIO ML-82**


Clock, calendar, musical alarm, hourly chimes, 1/10 second stopwatch to 24 hours; net, lap and 1st & 2nd place. Calculator with musical keys, full memory, %, square roots. 9/32 x 2 1/2 x 4 3/4 inches. ONE YEAR BATTERIES (RRP £22.95)

**£19.95**

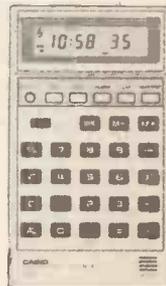

## NEW METRIC CONVERTER / CALCULATOR

**CASIO MC-34 CARD**

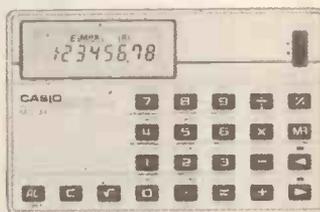

34 conversion functions, 17 metric, 17 reversible. Distances, weights; areas, volumes and temperatures. Calculator with GT memory, %, square roots, 1,100 hours batteries. 5/32 x 3 1/4 x 2 1/4 ins.

(£1.95) **£11.95**

Casio's guarantee is only valid if goods are purchased from an authorised dealer, who WON'T advertise lower prices than ours. Nevertheless we promise to BEAT (sensible) lower prices IF the advertisers have stocks.

Send for our FREE LEAFLET "The whole truth about digital watches."

## OUR BEST SELLING CALCULATOR



**FX-8100**

1 YEAR BATTERIES  
Hours, minutes, seconds, am/pm, day. Calendar pre-programmed to year 1999. 24-hour alarm. Alarm timer, interval timer, or 1/100 second stopwatch; net, lap, 1st and 2nd place. Fractions, %, cube roots, 5 levels parentheses, hyperbolics, standard deviations, co-ordinates, conversions. X to Y, X to M. 1/2 x 2 1/4 x 5 1/4" (RRP £27.95)

**ONLY £24.95**

**HUNDREDS SOLD!**

## OTHER CALCULATORS

WITH CLOCK, ETC.  
PW-81 £14.95; AQ-1500 £14.95; MQ-6 £19.95; MQ-12 £19.95; AQ-2200 £19.95; ML-71 £22.95; ML-81 £22.95; HR-10 £29.95.

SCIENTIFICS. With clock. FX-7100 £24.95. Others: FX-81 £12.95; FX-100 £15.95; FX-330 £15.95; FX-510 £19.95; FX-3200 £21.95.

# SEIKO

**PRICES SLASHED!**

## TS1 Alarm Chronograph



With countdown alarm. Hours, minutes, seconds, alpha day and date on upper display; and day, date, month, alarm and hourly chimes. Countdown alarm (upper display). Stopwatch from 1/100 sec to 12 hours; net, lap, and 1st and 2nd place times. Stainless steel. Glass.

**Only £44.95**

## TS7 Alarm Chronograph

100M Water Resistant. Suitable for swimming, water skiing etc. Hours, minutes, seconds, day, date and month. Programmable weekly alarm. Interval alarm timer up to 16 hours. Hourly chimes. Stopwatch, 1/100 second to 20 minutes, then seconds to 12 hours. Upper display — lap times. Lower display — Total time.



**ONLY £64.95**

## TS5 World Time / Alarm



Two Alarms, local and world time (dual tones). Hourly chimes. Normally displays hours, minutes, seconds, day; or optionally hours, minutes, day, date, month. World time mode displays an atlas with each of the 19 time zones highlighted when selected. Date and summer time functions.

**Stainless £59.95**  
**Gold Plated £84.95**

## TS4 Calculator Alarm

Hours, minutes, seconds, day, and day, date, month, am/pm. Alarm (2 tones), hourly chimes. 8 digit calculator with constants, delta %. Water resistant. 2 year battery with hatch. Approx. 9mm thick + 0.5mm for keys.



**Stainless £59.95**  
**Gold Plated £84.95**

## TS2 Alarm Chronograph



Comprehensive display of hours, minutes, seconds, day, date and month. 24 hour alarm and hourly chimes. Stopwatch from 1/100 second to 20 minutes, then seconds to 20 hours. Upper display-lap times. Lower display-total time. S/Steel encased—8mm thick plus front buttons

**Only £39.95**

## RETURN OF POST SERVICE

Postal and telephone orders received before 4.00 p.m. will normally be despatched the same day by FIRST CLASS POST.

Send your order by FREEPOST (2nd class post — no stamp required). Please phone urgent orders or use first class mail.

PRICE includes VAT, P&P. Send your Company Order, Cheque or P.O. or phone your ACCESS or B'CARD number to:

# TEMPUS

Tempus (Dept. ME)  
FREEPOST, 164-167 East Road  
Cambridge CB1 1BR. Tel. 0223 312866

# SPECIALS

Send your orders to Sales Office (Specials), Modmags Ltd,  
145 Charing Cross Road, London WC2H 0EE.

## ELECTRONICS DIGEST: SUMMER '80



Electronics Digest is a new quarterly from the Modmags Specials Department. The Summer 1980 issue reprints the best of Tech Tips from the last couple of years of ETI, and is, in fact, the third volume in the ETI Circuits series. Circuits are classified by type for easy access by the designer who needs inspiration.

£1.50 + 30p (p&p)

## DJ's YEARBOOK 1980



How to make your own light show (two versions), how to manage the business side, how to operate, how to build a mixer-amplifier. About the Disc Jockey's Federation, about insurance, about publicity. The most comprehensive yet-published Directory of Manufacturers and Suppliers. And if you're thinking of starting your own mobile disco business, the DJ's yearbook will set you off on the right lines.

£1.50 + 30p (p&p)

ETI 1999 is what we think a magazine will look like in 19 years time. Read about Europe's new capital city, the latest development in hifi loudspeakers, what's happening in space; and World War Three. This four-colour magazine comes in a special folder and makes an ideal gift for an SF or electronics enthusiast.

£1.50 + 30p (p&p)

## ETI 1999



Contents include Designing and Using Active Filters, A Few Cheap Tricks!, Digital to Analogue Techniques, Using the LM3900N, Designing High(est)-Fi Amps, A Practical Guide to Triacs, Power Supplies, A Practical Guide to Zener Diodes, Modern Crystal Oscillators, High Voltage for Low Cost, Odd Odes, Designing Oscillators.

£1.25 + 30p (p&p)

## ELECTRONIC CIRCUIT DESIGN No 3



## ELECTRONIC CIRCUIT DESIGN No 2

Contents include Op-Amps, Transistor Operating Point, 40 CMOS Clocks, Practical Guide to Reed Switches, V-FETS for Everyone!, Choosing and Using Transformers, Digital Electronics by Experiment, Gain Control.

£1.25 + 30p (p&p)



## ELECTRONIC CIRCUIT DESIGN No 1

Contents include CMOS, Audio Amplifiers, Power Supplies, Practical Guide to SCRs, Op Amps and Integrators, Electronic Speed Control for Motors, Op Amps, 3080 Circuits, CMOS to Mains, Practical Guide to Temperature Control.

£1.25 + 30p (p&p)

## HE PROJECTS SPECIAL

Tantrum, Audio Mixer, Rumble Scratch Filter, Constant Volume Amplifier, Graphic Equaliser, Envelope Generator, Linear Scale Ohmmeter, Analogue Frequency Meter, White Noise Generator, Transistor Tester, Digital Clock, Ultrasonic Switch, Drill Speed Controller,

Digibell, Casanova's Candle, LED Tachometer, Parking Meter Timer, Hobbytune, Touch Switch, Push-Button Dice, Photon Phone, Starburst, Photographic Timer, Shark, Multi-Option Siren.

£1.25 + 30p (p&p)

## INTO ELECTRONICS PLUS



The complete series of Ian Sinclair's series Into Electronics Plus a selection of some of the most popular and informative articles from HE. Everything from Home Computing to making your own PCBs.

£1.00 + 30p (p&p)

## ELECTRONICS IT'S EASY

This very successful beginners' series has now been reprinted in one volume. The book covers just about every aspect of

electronic theory and is ideal for anyone just starting out in this fascinating hobby. £3.60 + 80p (p&p)

## TOP PROJECTS No 7

ER II loudspeaker, CCD phaser, 3-channel tone control, bass enhancer, continuity tester, bench supply, LCD digital multimeter, digital frequency meter.

wide range oscillator, ETI wet, egg timer, house alarm, porch light, torch finder, light dimmer, 1B metal locator, electronic bongos, puzzle of the drunken

sailor, race track, ultrasonic switch, tic-tac radio, rev counter, Transcendent 2000, spirit-level.

Book 7: £1.25 + 30p (p&p)

## TOP PROJECTS No 6

Contents: Graphic Equalizer, RF Attenuator, ETI Watchdog, Sweep Oscillator, £2 Sound Improver, Stereo Simulator, Freezer Alarm, General Preamplifier, Stars &

Dots Game, GSR Monitor, Burglar Alarm, Headlight Reminder, Bench Amplifier, CCTV Camera, Audio-Visual Metronome, Expander, Compressor, Power Amplifier Modules, Digital Thermometer.

Headphone Adaptor, Hear & Tell Unit, LED Dice, Active Crossover, Marker Generator, Skeet Game, Flash Trigger, Disco Lightshow Unit, Pink Noise Generator, PCB Foil Patterns. £1 + 30p (p&p).

## TOP PROJECTS No 5

Contents: Five Watt Stereo, Stage Mixer, Disco Mixer, Touch Organ, Audio Limiter, Infra-Red Intruder Alarm, Train Controller, Reaction Tester, Headphone Radio, STD Timer, Double Dice, General Purpose Power Supply, Logic

Tester, Power Meter, Digital Volt Meter, Universal Timer, Breakdown Beacon, 1-2 Hour Timer, Heart Rate Monitor, Induction Balance Metal Locator, Temperature Meter, Slave Flash Unit. £1.00 + 30p (p&p)

## TOP PROJECTS No 4

Contents: Sweet Sixteen, Waa Waa, Ceramic Cartridge Preamplifier, Audio Level Meter, Expander - Compressor, Anti-Theft Alarm, Auto Amp, Headlight Reminder, Solid State Flasher,

Courtesy Light Extender, Flash Trigger, Exposure Meter, Photo Timer, Dual Tracking Power Supply, Simple CMOS Tester, Audio Millivoltmeter, Logic Probe, Logic Pulser, Basic

Power Supply, Thermocouple Meter, Intruder Alarm, Garden Watering, Touch Switch, Push Button Dimmer, Electronic Dice, High Power Beacon, Temperature Controllers, One Arm Bandit. £1 + 30p (p&p).

## ELECTRONICS TOMORROW

Star Wars and Hi-Fi projects for everyone - none of which have appeared in ETI - and a look at the future of MPUs, audio, calculators and video.

75p + 30p (p&p)

## ETI CIRCUITS No 1 ETI CIRCUITS No 2

Each volume contains over 150 circuits, mainly drawn from the best of our Tech-Tips. The circuits are indexed for rapid selection and an additional section is included which gives transistor specs, and plenty of other useful data. Sales of this publication have been phenomenal - hardly surprising when the circuits cost under 1p each!

£1.50 + 30p (p&p) each

# Sound Operated Flash Trigger


***Faster than a speeding bullet (almost),  
the HE Flash Trigger will produce those  
out-of-the-ordinary photos.***

If the photo on our cover caught your eye, this is the project for you. Though it uses less than twenty components, it offers the photographer an opportunity to instantaneously "freeze" the action and create fascinating photographs using just an ordinary camera and a simple electronic flash gun.

No special optics are required and you should be able to use even the simplest camera with this unit; a "pin-hole" camera would do! It is necessary to set up your camera in a darkened room, or conduct your experiments at night, with the shutter open. Most cameras have a "B" or "T" position on their speed selector dials. You may need to use a locking shutter release cable. Don't open the shutter until you are ready to take the picture. If you have a tripod you will find it helpful — otherwise you'll probably need an assistant to hold the camera or direct the action.

The electronic flash gun is positioned for best lighting and the unit can be switched on and connected. A control on the board enables you to adjust the unit's sensitivity to suit your application. Now, whenever the ambient sound exceeds the threshold level the unit will fire the flash gun. Remember that if the unit is set for high sensitivity, the flash gun is likely to go off when someone slams a door upstairs or when a flea jumps into the microphone! Experiment with the sensitivity setting, microphone positioning and lighting angle with a few trial-runs before you open the shutter and expose the film.

This unit will work with any electronic flash gun. Most of them have a flash duration of a thousandth of a second or less so you can "stop" slow motion — though you will not be able to "freeze" an insect's wings. (If you don't believe me, try it . . . but remember; bees sting!) For certain shots it is useful to be able to vary the delay between the sound-making event and the triggering of the flash. For the bursting balloon shot on our cover, for instance, this delay had to be precisely controlled. The

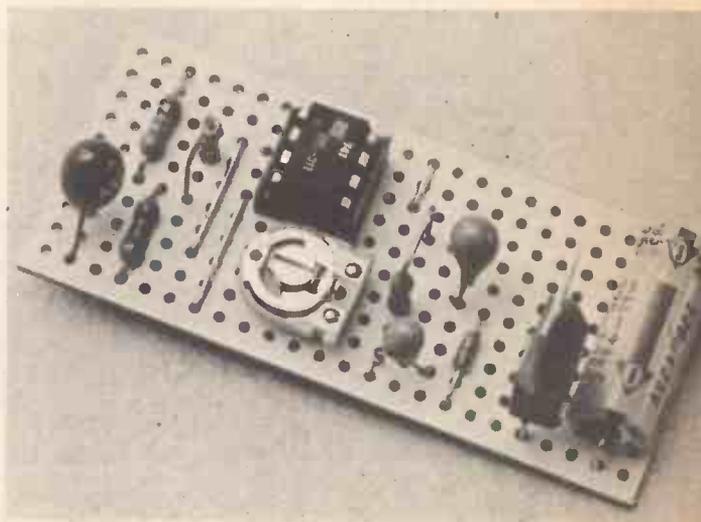

delay is proportional to the distance between the sound source and the microphone (approximately one thousandth of a second per foot).

The circuit as shown has a gain of at least 100. With high output crystal inserts you may find that there is too great a sensitivity. This can be reduced by changing the value of R4 from 100k to 10k or simply by replacing R4 with a piece of wire! When you come to connect the unit to your flash gun remember that thyristors only work "one way round". If it does not work first time, reverse the leads and try again. There may be a high voltage at the trigger terminal of an undischarged flash gun. Try not to discharge it through your finger or you may have a surprise!

## **CONSTRUCTION**

We used veroboard, though any method of construction may be used. A simple circuit like this lends itself to breadboarding. If you do use veroboard then just follow our drawings and check the "Hints For Constructors". Any nine volt battery will power the unit — we used a PP3. Keep the leads to the crystal microphone short or use screened cable (connect the screen to the junction of R1, R2, and C1).



You can try connecting other transducers in place of the crystal microphone. An LDR, for example the ORP12 cadmium-sulphide light dependent resistor, should make the unit sensitive to changes in light intensity. We have not tried it but experience has shown that LDRs usually work best at low light levels — so if you do try, mount the LDR at the end of a cardboard tube or make a light shield with some rolled up paper. Once you have the unit working, you can set the sensitivity to the required level and shoot away.

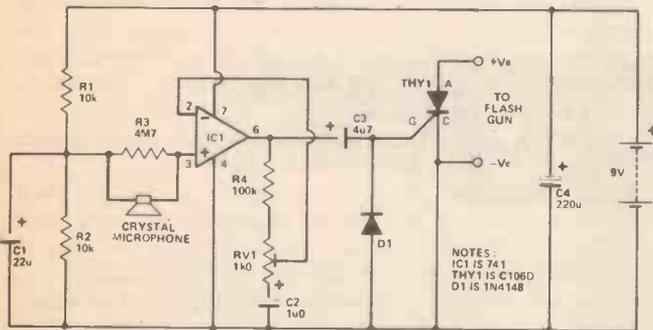


Fig. 1. The circuit diagram of the Flash Trigger.

## How it Works

Sound waves striking the microphone are transformed into electrical impulses and amplified by IC1. The gain of this stage is variable by adjustment of RV1. When there is no sound, the output of IC1 (pin 6) will be steady, at about four or five volts; roughly half the supply voltage. Capacitor C3 prevents current from flowing into the gate of the thyristor until a sound impulse causes the output of IC1 to swing towards the positive rail. Diode D1 provides a recharge path for C3.

The thyristor is an electronic switch. It will switch on very fast when the current flowing through the gate-cathode junction exceeds a certain value. The 'turn-on' current for the C106D is about 200uA (two ten thousandths of one amp). Once turned on, the thyristor will stay on, even if the gate current is removed, until the current from the anode to cathode falls below a few milliamps. This is a very useful feature in some circuits and causes no problem here as the flash gun discharges in a fraction of a second and the thyristor switches off again. Note that the thyristor will only conduct current in one direction. With the voltage across its terminals reversed, it behaves just like an ordinary diode and no current flows until the breakdown voltage of the device is exceeded.

## Buylines

All of the components used in this project should be available from your usual supplier or from the larger mail-order companies.

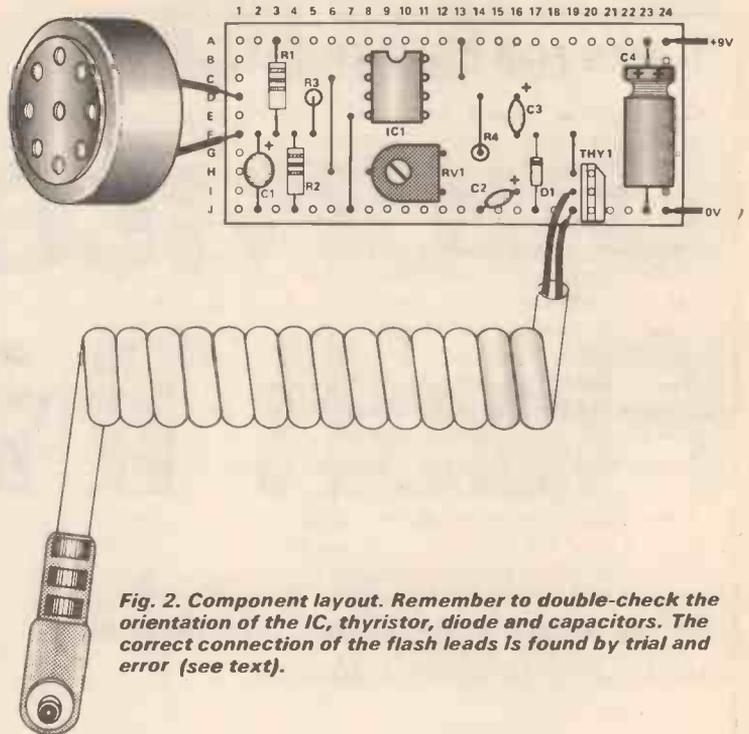


Fig. 2. Component layout. Remember to double-check the orientation of the IC, thyristor, diode and capacitors. The correct connection of the flash leads is found by trial and error (see text).

## Parts List

### RESISTORS (All 1/4W, 5%)

R1, 2	10k
R3	4M7
R4	100k

POTENTIOMETER 1kΩ LIN preset

### CAPACITORS

C1	22u 25V tantalum
C2	1u0 35V tantalum
C3	4u7 35V tantalum
C4	220u 25V electrolytic

### SEMICONDUCTORS

D1	1N4148
IC1	741
THY1	C106D

### MISCELLANEOUS

Crystal microphone  
9V battery (PP3)  
Flash extension lead  
1in x 2 1/2in Veroboard

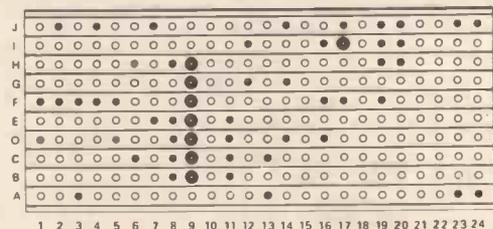


Fig. 3. The underside of the board. The large circles show where to cut the tracks, the dots are soldering points for the component leads.

# Sound Operated Flash Trigger

## HINTS FOR CONSTRUCTORS

**Cutting the board.** Rotate the "spot face cutter" while pressing gently to make the breaks in the copper track. If you do not have Vero's special tool, use a drill — 1/8" is about right. Always check that no bits of copper swarf are shorting to an adjacent track.

**Inserting components.** Long nose pliers come in handy for forming leads and inserting components. Do not bend the leads close to the body or they may break off. Check that components are not shorting to each other or to any wire links on the board.

Always insert the low profile components first: wire links, resistors, capacitors etc. Put the semiconductors in last.

**Soldering.** Make sure the component leads and the soldering iron are clean. If you use new components there should be no problem. Use a small soldering iron. 15 watts is ideal; 25 watts is really a safe maximum. Hold the components still when you solder them AND until the solder has set — about five seconds. Do not use too much solder or you may bridge the tracks and BE QUICK!

When the joint is cool, trim the lead with a pair of sidecutters.

## HOW I SHOT THE FRONT COVER PICTURE USING THE HE FLASH TRIGGER

*A day in the life of our cover photographer, Steve Crawley.*

For this shot I set the shutter to B (or T) with the camera on a tripod in a dark studio. I used an aperture of f16 and Kodak Ektachrome 200ASA EPD film.

Lighting was provided by one Metz 402 flash unit and a white reflector to fill in the shadows. The sensor on the flash was set to 200 ASA f16 and I placed the balloon 4ft in front of it. The duration of the flash is 1/25,000-1/30,000 of a second.

The balloon was blown up as hard as possible and placed in front of a black velvet background.

The position of the microphone is critical. I used Polaroid film to find the correct distance — in this case 2ft 3ins. With the microphone at 3ft the balloon is completely demolished leaving the dart in mid air!

After a few hours of experimentation, trial and error, and sheer luck I managed to come up with a few reasonable shots for the HE artists to shape into a cover. The actual shot chosen shows one of a series of smoke-filled balloons about 25% demolished. **HE**

# STEVENSON

## Electronic Components

STEVENSON

**AT LAST! OUR NEW 1980/81 CATALOGUE IS NOW AVAILABLE.**

Our new catalogue is just packed with components. It contains 100 illustrated pages detailing over 3000 line items. These include:

Amplifier modules	Connectors	Meters
Books	Desoldering tools	Ni-cad cells
Breadboards	Drills	Op-amps
Cabinets	Etching equipment	Rams
Cables	Heatsinks	Resistors
Capacitors	IC sockets	Switches
CMOS	Knobs	Tools
Crossovers	Mains Transformers	Triacs

Included with our catalogue you will receive:

- a reply paid envelope for your first order.
- a mail order form to facilitate rapid despatch
- a 50p discount voucher to be used against mail order purchases over £10.00.

Available now by post from the address below at a cost of 50p

Due to stock and administrative problems over the last few months, the quality of our service had suffered considerably. These problems have now been resolved and we are confident that we can now offer the quality of service we had been accustomed to. We wish to convey our apologies to any customers who have been inconvenienced.

All prices include VAT. Please add 50p carriage on orders below £15. Contact our sales office with your requirements on: **01-464 5770**



### OPTO

Red	0.125in.	0.2in.	
Green	TIL209	TIL220	10p
Yellow	TIL211	TIL221	16p
Clips	TIL213	TIL223	16p
			3p

DISPLAYS

DL704	0.3in	CC	130p
DL707	0.3in	CA	130p
FND500	0.5in	CA	100p

### TRANSISTORS

AC127	25p	BC547	8p	TIP30C	70p
AC128	25p	BCY71	18p	TIP2955	65p
AD161	40p	BD131	35p	TIP3055	60p
AD162	40p	BD132	35p	ZTX107	12p
BC107	10p	BD139	35p	ZTX108	12p
BC108	10p	BD140	35p	ZTX109	12p
BC109	10p	BFX29	25p	ZTX300	14p
BC147	9p	BFX84	26p	ZTX500	15p
BC178	16p	BFY50	23p	2N3053	25p
BC182	10p	BFY51	23p	2N3055	55p
BC182L	10p	MJ2955	98p	2N3702	9p
BC184	10p	TIP29C	60p	2N3703	9p
BC184L	10p			2N3704	9p
BC212	10p			2N3819	22p
BC212L	10p			2N3905	10p
BC214	10p			2N5777	50p
BC214L	10p				

### DIODES

1N914	4p	1N4148	3p
1N4001	4p	1N4002	5p
1N4006	7p	1N5401	14p

BZ788 series 8p each.

### LINEAR

741	18p.	LM324	52p	MM57160	650p
747	70p	LM339	55p	NE531	140p
748	40p	LM348	100p	NE555	23p
7106	850p	LM377	170p	NE556	60p
CA3046	70p	LM378	230p	NE567	120p
CA3080	75p	LM380	80p	RC4136	100p
CA3130	100p	LM381	140p	SN76477	230p
CA3140	60p	LM382	120p	TBA800	80p
LF347	170p	LM386	90p	TBA810	110p
LF351	45p	LM387	120p	TDA1022	630p
LF353	90p	LM1458	40p	TLO81	45p
LF356	95p	LM1830	180p	TLO82	85p
LM301A	30p	LM3900	60p	TLO84	125p
LM318	85p	LM3909	72p	XR2206	390p
		LM3911	120p	ZN414	80p
		LM3914	320p	ZN425E	475p
		LM3915	320p		

### PACKS

Specially designed packs intended for development work at a considerable saving.

1/4w resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 530p each.

1/2w resistors. 10 of each value 4.7ohm to 1 Mohm. a total of 650 resistors. 875p each.

Presets. Pack of 5 of each value from 100ohms to 1 Megohm. a total of 65 presets. 390p each.

LED's. Pack containing 10 of each colour LED 0.2 size. Total of 30 Led's + clips. 450p each.


Zeners. Pack of 5 of each value from 2U7 to 33V A total of 130 zeners. 880p each.

### CMOS

4001	25p	4025	25p	4072	25p
4002	25p	4026	150p	4081	30p
4006	95p	4027	50p	4082	30p
4007	25p	4028	90p	4085	85p
4011	30p	4029	110p	4093	80p
4013	45p	4040	110p	4095	110p
4015	85p	4042	85p	4510	90p
4016	48p	4046	110p	4511	100p
4017	80p	4048	60p	4518	90p
4018	90p	4049	50p	4520	110p
4020	110p	4050	50p	4527	165p
4022	100p	4052	80p	4528	100p
4023	25p	4060	120p	4532	125p
4024	60p	4066	63p	4543	170p
		4068	25p	4583	80p
		4069	25p	4585	115p
		4070	25p		
		4071	25p		

### SKTS

8 pin	9p	22pin	20p
14pin	11p	24pin	22p
16pin	12p	28pin	26p
18pin	16p	40pin	38p
20pin	18p		

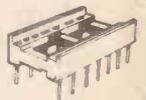

### SWITCHES

TOGGLE			
Standard	SPST	40p	DPDT 55p
Miniature	SPDT	80p	DPDT 90p
Subminiature	SPST	65p	DPDT 85p
SLIDE	Standard DPDT	17p.	Miniature 16p each.
PUSH	Push to make	16p.	Push to break 22p.

### TTL

7400	15p	7447	65p	74123	50p
7401	15p	7448	65p	74125	60p
7402	15p	7472	35p	74126	60p
7404	16p	7473	38p	74132	70p
7406	38p	7474	36p	74141	95p
7408	22p	7475	40p	74145	90p
7410	18p	7476	40p	74150	120p
7413	35p	7483	80p	74154	110p
7414	56p	7485	80p	74157	80p
7420	16p	7486	35p	74164	120p
7427	30p	7490	45p	74165	120p
7430	30p	7492	55p	74174	100p
7432	35p	7493	45p	74175	95p
		7494	70p	74190	100p
		7495	70p	74191	100p
		7496	70p	74192	100p
		7497	70p	74196	100p

# 76 College Road, Bromley, Kent BR1 1DE.



# Electronics In Photography

**Latest developments exposed by Phil Gerring, HE's hot-shoe, hot-shot photographer.**


SINCE JOSEPH NIEPCE produced the first photographic image in 1826 the science of photography has advanced beyond all recognition. Indeed Niepce, confronted with a modern SLR compact, would be at a loss to know what it is — let alone how to use it. Niepce's first photograph took eight hours to expose; today the same scene can be captured in 1/1000 of a second (at a far better quality).

The camera manufacturers are continually bringing out new models incorporating the latest technology. Photography is such big business that Kodak, the world's longest photographic company, spend more (world wide) on advertising than the U.S. do on defence.

This article follows and explains the development of electronics as applied to photography, and looks into the future.


## EXPOSURE METERS

As far back as 1873 a guy by the name of Willerby Smith noticed that the conductivity of a piece of selenium varied with the amount of light falling on it. Despite this early instance of photo-conductivity, it wasn't until the 1930s that the first commercial electric light meter was developed. Since then there have been many advances and developments. In the late 40s germanium and silicon were applied to photo-voltaic and photo-conductive uses. In the 50s light meters became a permanent fixture on cameras and in the 60s 'Through the Lens' metering was instituted on both semi-automatic and fully automatic cameras.

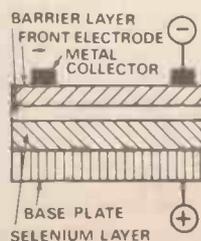

**Fig. 1. Structure of the selenium cell. This was used in the first commercial exposure meter and is still popular today.**

There are four different types of photocell used in exposure meters. The first of these are selenium cells or barrier layer cells (Fig. 1). They generate their own electricity (photovoltaic) and use a sensitive galvanometer attached to a mechanical calculating dial. Their sensitivity is limited and dependent on the area of cell exposed to the light. The light meter uses a baffle to limit the acceptance angle to that of the camera lens employed. Its advantages are that it requires no power supply and is relatively inexpensive. It is, however, too large to be incorporated inside the camera and does not perform very well in low light levels.

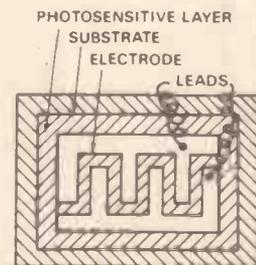

**Fig. 2. The cadmium sulphide cell, with leads for the external power supply. Its sensitivity allows its use in TTL metering.**

The cadmium sulphide cell (CdS) is a photosensitive cell and an increase in light reduces its resistance to a flow of electricity, thus increasing the flow of current from a battery across the cell (Fig. 2). A sensitive galvanometer is used to calculate the exposure setting (see Fig. 4). It is usually employed as a 'Through The Lens' light meter (TTL) as it is very compact. It is more sensitive than the selenium cell and responds well in low light levels. Its disadvantages are that it tends to retain or memorize a light level (it is slow to respond to a new one) and it is also very sensitive to red light which results in under-exposure of red subjects.

Silicon cells (Si) are solid state photodiodes (Fig. 3) that generate a minute current (photovoltaic). This is then amplified to obtain a useful output and an op-amp is used as a current-to-voltage converter with a suitable

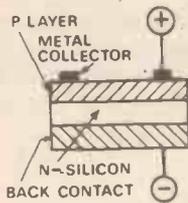


Fig. 3. Silicon cells are extremely fast reacting and very small.

feedback resistor to give high output voltage in proportion to the incident light on the cell. This then gives a significant response even at low light levels and also a linear response over a wide range with an almost instantaneous response to changing levels. As these cells are small and reliable, they are used in common camera bodies. Being very sensitive to red light, they are often fitted with blue filters and called Silicon Blue Cells (SBC) which give a better acceptance of the spectrum. However, the cell becomes unreliable in temperature extremes.

The fourth type is the gallium arsenide phosphide cell (GaAsP). This is a fast-reacting compact photocell and provides reliable readings in blue and red light. It also responds well in low light levels and is not over sensitive to temperature extremes. It is similar to the Silicon cell in that it responds about 1000 times faster than the CdS cell. It is, however, a fairly recent innovation and is not at the moment in common use.

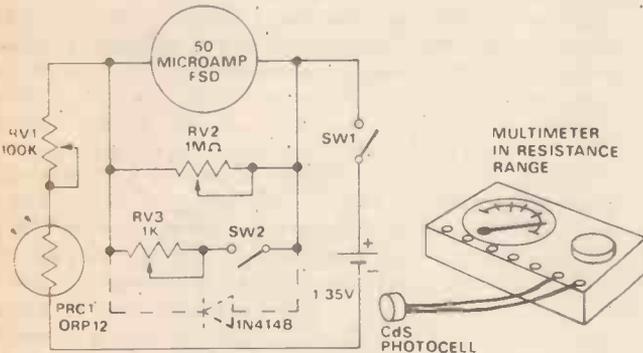


Fig. 4. Circuit diagram of a basic hand-held CdS lightmeter. This version has two ranges which are individually calibrated by RV2 and RV3.

## SEMI AUTOMATIC CAMERAS

A practical semi-automatic system first became possible with the development of a compact photosensitive resistor which could be installed in or on the camera. The next development was to directly link the light meter circuitry to the shutter, aperture and film speed controls. This was achieved using a series of variable resistors. By the mid-70s the cameras used a moving coil meter with a needle as an indicator.

There are two basic metering systems. One uses a two needle system. A "match" needle is linked to the ASA film speed which is directly linked to the metering coil. The aperture and shutter are linked to the other needle, which may have a ring attachment at its end. The photographer adjusts the ring until it is aligned with the needle by altering the shutter speed and aperture controls.

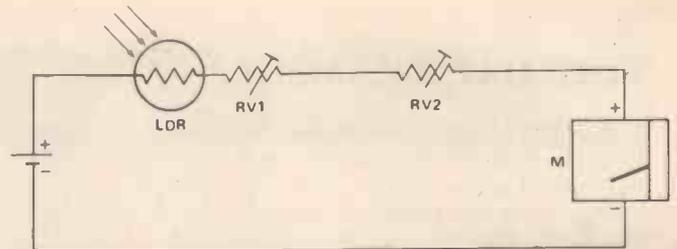


Fig. 5. An early design for an in-camera exposure meter. RV1 and RV2 are connected to the shutter speed and film speed respectively.

The other major system uses the needle centre method (Fig. 5). All the exposure controls as well as the light-dependent resistor are connected to a single needle which is situated at the side of the viewfinder and is free to swing between two markings. If the needle swings towards the +ve end of the scale this indicates that the picture will be over-exposed and conversely, if it swings the other way it will be under-exposed. The photographer can then adjust his aperture and/or shutter speed accordingly.

The drive circuits for the integral systems, as described above, in modern 35mm cameras can be very basic arrangements. For example, the single-ended circuit operates a meter by measuring the amount of light falling on the LDR through the lens of the camera. As the ASA of the film and the shutter speed are preset, the meter can be centred by adjusting the aperture ring. (Note: The aperture is not connected to the circuit.)

This circuit arrangement has disadvantages and can be unreliable because it is dependent on a constant voltage supply from the battery. So if the battery voltage fluctuates above or below its normal it is going to result in a faulty meter reading and consequently affect the exposure.

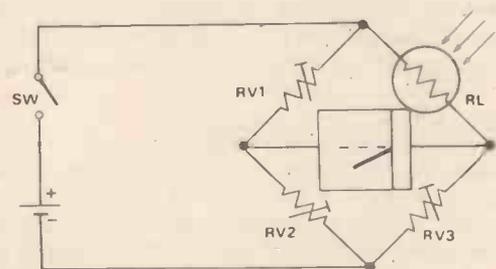


Fig. 6. A Wheatstone bridge arrangement.

A more reliable circuit is achieved by using a Wheatstone bridge arrangement (Fig. 6), which operates independently of any fluctuations in the battery voltage.

The sensitivity of the microammeter in the metering system of semi-automatic cameras is so crucial that should it get damaged the whole metering system would have to be replaced and this can be very expensive. So when LEDs first appeared on the market, camera manufacturers were quick to see the obvious advantages of these solid state devices, and they began developing them for application in photography. Linked to a drive 'chip', these devices have many advantages over the old moving coil metering system. The most common display arrangement used is a vertical column of three LEDs. The top and bottom LEDs glow red to indicate either over- or under-exposure. When the exposure is correct the middle LED glows green.

# Electronics In Photography

## AUTOMATIC CAMERAS

In the 50s crude forms of automatic exposure meters were being built into cameras but these were mainly mechanical systems designed for the amateur market.

They were not always reliable and had a fixed shutter speed. The aperture was adjusted electro-mechanically. A photo-voltaic cell would measure the incident light and power a servo motor which then adjusted the aperture using a series of geared wheels.

Another popular system in early 'automatic' cameras used the needle trap method. A meter is used to read the output from a photocell and then the meter needle is clamped into position (which doesn't do a microammeter much good). Then on depressing the shutter button a lever travels to the position at which the needle was trapped and adjusts the aperture as it moves. This system is accurate but easily damaged. It can, however, incorporate a range of resistors which allows for a variety of shutter speeds.

By the early 60s microcircuitry was beginning to come into its own and in 1968 Konica brought out the first fully-automatic electronic 35mm SLR. All the other major manufacturers soon followed with their own versions.

Most of these early auto cameras have an 'aperture priority' control whereby the photographer sets the film speed on the dial which is in turn linked to the exposure calculator circuitry. Then, by moving the aperture control only, the camera works out the correct shutter speed to go with the chosen aperture. This is done using a comparator chip which can accept the output from the photoelectric cell and the variable resistances from the aperture and film speed settings.

Most of the recent auto-exposure cameras use electro-magnetic aperture control with a direct electronic link made to the timing circuitry giving faster and more accurate exposures. The early versions had automatic aperture controlled by levers and servos.

Micro-electronic developments, such as more 'intelligent' and compact chips as well as flexible circuit boards and greatly increased reliability, have made it possible for cameras to have more than one auto-exposure mode. As well as manual operation they are capable of aperture priority or, with the flick of a switch, shutter speed priority. This dual mode feature coupled with an increased reliability is particularly attractive to professional photographers.

Some modern cameras are pre-programmed by the manufacturer so that if there is either too much or too little light for the exposure even after the shutter or aperture has gone to its limits, the camera will take over the setting. These alterations are usually displayed in the viewfinder so that a check can be made in case the settings are not close enough to get the desired effect.

Some cameras make use of stepped programmes. These are mainly incorporated in compact 35mm cameras in the higher price range. The exposure rating is staggered between the aperture and exposure settings, thus giving the photographer a balanced setting between depth of field (aperture) and fast exposure (shutter speed).

Using electronic shutters and apertures enables cameras to operate with continuous exposure values to give more accurate and more consistent exposures. There are some recent fully automatic cameras where the light reading is taken partly off the actual surface of

the film emulsion. So with fast-reacting electronics a shutter speed or aperture can be corrected in mid-exposure. In compact cameras a stepless exposure works only above 1/100th of a second so that camera shake problems are minimised.

## ELECTRONIC SHUTTERS

Polaroid produced the first commercially-available electronic shutter to operate efficiently in the small body of a camera. The other major manufacturers soon followed but with more professional systems. The development of mechanical shutters had attained a high standard by the time electronic shutters appeared on the scene and initially there were no real advantages in using an electronic shutter except where weather conditions were extreme.

The electronic systems gained the advantage though when they were linked to the automatic exposure systems. In 1971 Asahi Pentax introduced the Pentax ES (electronic shutter) and this set the route by which the electronic shutter was going to develop.

There are two basic types of shutter used in cameras, they are the 'between-the-lens shutter' (ie between the elements of a compound lens) and the 'focal plane shutter.'

Between-the-lens arrangements have appeared in many different forms from a single blade type as found in the simpler cameras such as Instamatic cameras, and the lower-priced Rangefinder Compacts. More expensive cameras use a between-the-lens arrangement with more than one blade. This system has fewer operating problems than the focal plane shutter because it allows an even one step illumination over the whole film area. The first form of electronic shutter which appeared in the 60s was the electronically operated spring-loaded diaphragm shutter. This shutter uses an electromagnet to attract a lever which moves a collar attached to the shutter leaves. The electromagnet is connected to a switch and a power supply, normally a small battery.

When the exposure button is depressed, this energizes the coil which attracts the lever and a capacitor-resistance network starts timing. When the exposure is completed, the electromagnet is de-energized and the shutter is closed by the force of a spring acting on the lever. Another arrangement of shutter control is by the use of permanent magnets in place of the spring. The use of magnets reduces mechanical moving parts and also closes the shutter more efficiently than a spring. Automatic exposure systems can be linked to this shutter by exchanging the resistor network with a silicon cell device which can judge the exposure while light is landing on the film surface.

Mechanical timing arrangements were used at first to control these shutters, but microcircuitry has made it possible to incorporate an electronic timer. When the electro-magnet in the shutter is activated it also trips a switch which allows a capacitor to charge at a predetermined rate, controlled by a variable resistor or by a resistor series network. This is linked to the shutter speed setting on the camera and when the voltage in the capacitor attains a critical level a transistor switching circuit will take over and cut off the current to the solenoid allowing the shutter to close.

The focal plane shutter is not situated in the lens but directly in front of the film plane. One blade shuts out the light. When the shutter is released it slides across. When the film has been exposed for the correct length of time a second blade follows across to complete the exposure.

The most common type of electric shutter is a spring loaded system which is attached to and cocked by the film wind-on lever. The electronics are similar to those in the between-the-lens shutter, using a capacitor charged via a variable resistor (Fig. 7). By pressing the shutter release trigger, switch (SW2) is closed and this allows current to pass through an op amp which in turn charges a solenoid. The charged solenoid pulls a spring tensioned lever up to the electromagnet and at the same instant releases a catch allowing the first shutter blade to shoot along its track close to the focal plane. At the same instant, the resistor and capacitor circuit starts timing the shutter. After the set time the op amp switches off and discharges the solenoid. The lever is then released and the spring returns to its starting point at the same time releasing the second blade and covering the film again.


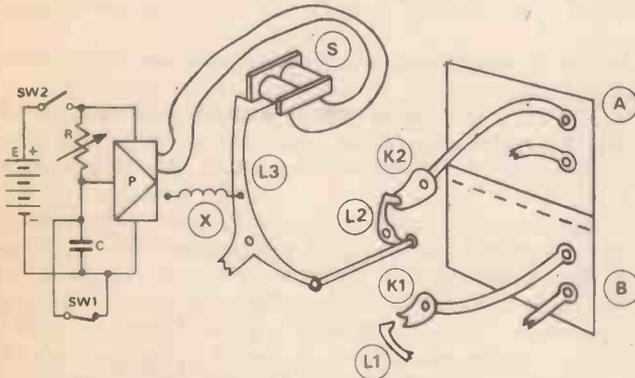


Fig. 7. Many electronic shutters still require complex lever arrangements to function.

There are several types of electronic timing used in conjunction with electronic shutters, the most popular being the Schmitt trigger and the SCR. In the Schmitt circuit (Fig. 8), the capacitor is charged up to a level predetermined by the resistor R. When the trigger voltage is reached, the 'off' and 'on' transistors are switched over. The SCR circuit (Fig. 9) can operate using very low power levels. The SCR starts out as an open circuit. When the power is connected, the first shutter blade is released and the capacitor charges up to a low gate voltage which then triggers the SCR (to a closed circuit). This puts a voltage across the solenoid which in turn attracts the lever releasing the second blade of the shutter.

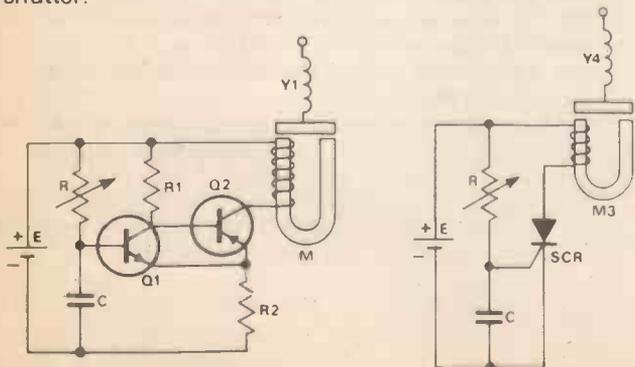

Figs. 8, 9. The Schmitt trigger and SCR timers.

## AUTOFOCUS

Cameras have developed rapidly in recent years with the aid of high technology electronics. Cameras can decide and set their own shutter speed, aperture and even film speed controls to give you fully automatic operation. The next stage was the development of autofocus, so that a camera could calculate the distance of the subject from the lens to bring it into focus.

The first autofocus camera was developed by Canon in 1963 but autofocus cameras did not actually come onto the market until 1978 with an autofocus camera designed by Konica. There are now three systems used. The first, and at the moment most predominant, system is based on the Honeywell Visitrone Autofocus Module. This uses a system of comparing the contrast of light on a subject as viewed by two banks of light sensitive cells.

The second is a system used by Polaroid. This sends out an ultrasonic wave (sonar type) at the subject for automatic focusing. The third and newest system is one used by Canon which bounces an infra red light beam off the subject.

In the Honeywell system light from the subject passes through two windows on the front of the camera and is reflected by a series of mirrors into the autofocusing module. Here the two light sensitive panels (silicon photocells) compare the lighting contrast from the two views of the subject. The contrast is a maximum at the point of exact focus and falls away on each side of it.

The sonar system employed in Polaroid cameras works on the same principle as that used by submarines. A transducer sends out and later receives the sound waves and converts them into electrical energy. The transducer sends out a chirp lasting about 1/100 sec towards the subject. The chirp contains four ultrasonic frequencies between 50 and 60 kHz. A crystal oscillator clock times how long it takes for the chirp to rebound onto the camera and a chip calculates the focal setting from this information, a servo motor adjusting the lens accordingly.

The Canon autofocus system uses an infra red light beam to assess the correct focus. It works using an IRED (infra red light emitting diode) which sends out a beam of invisible light of about 900 nm (nanometres) wavelength. The camera has two rangefinder-style windows. The infra red leaves one window and scans the subject scene from left to right through an angle of about 10°. When the receiving sensor is receiving the maximum signal, the IC electronics informs the lens of the correct setting, and all this takes about 120 milliseconds.

Each system has its advantages and disadvantages. The Honeywell is compact and for the first time afforded quick, easy, sure, sharp automatic focusing for all photographers. It does, however, have a slight 'memory' whereby it retains previous focal settings and does not function very dependably in dim light or low contrasting light (and is therefore inadequate for flash). It can also have trouble focusing on small repetitive patterns.

The advantage of the ultrasonic or sonar system is that it does not depend on bright lighting of the subject and so can focus in absolute darkness. The only drawback is if a solid object such as a window lies between the subject and the camera, as the sonar cannot then judge the distance to the subject.

# Electronics In Photography

The infra red system works in almost any situation in which the Honeywell system does not and it can focus even in total darkness. It can also focus through glass. The only drawback to the system is that it may not work well on subjects with low reflectance characteristics. It is the infra red system which will probably predominate autofocusing systems in cameras during the 80s.

## ELECTRONIC FLASH

1851 saw the first electronic flash when Fox-Talbot, an early photographic pioneer, borrowed equipment from Faraday and demonstrated the use of an electric spark as an artificial light. But it wasn't until the 20th century that electronic flash became available as a convenient light source. Flash guns require a DC power supply, capacitors, flash tube, triggering circuit and a reflector. Modern flash guns have flash tubes filled with xenon surrounded by a toughened glass envelope. This is connected to a capacitor which has been specifically designed for flash guns and similar instruments, and these are called either energy storage or auto flash types.

There are three types of flash guns which make use of varying sizes of capacitor depending on the application. Low power amateur flash guns make use of capacitors charged from 180-500 volts. Portable studio guns use 500-1500 volts and industrial giants can use 1500-15000 volts. As thousands of volts are discharging through the flash circuit, there will be several hundred amps moving along the flash tube for 1/250th to 1/1000th of a second. Therefore the power produced can be as high as a 100kW at the peak of the flash.

In modern portable flashguns the capacitor requires a power pack running from a few 1.5 pencil batteries. The small 1.5 volt cells can charge the capacitor up to sufficiently high voltage by using a transistor 'inverter' circuit (Fig. 10). This circuit oscillates at an audio frequency (this accounts for the whining noise heard as the flashgun charges up). The oscillator produces an AC voltage which is stepped up by a transformer and the high-voltage AC is then converted back to DC by a rectifying diode, and goes to charge the storage capacitor via a current limiting resistor. The flash gun then has to be fired to release the stored charge.

It is critical that the flash synchronizes precisely with the shutter. A synchronizing switch is built into the camera. This switch cannot directly handle the flash current, so it is used to trigger a thyristor in the flash unit.

Charge control circuits are built into flashguns to ensure constantly bright flashes regardless of the state of the batteries. This circuit fully charges the capacitor before switching off to conserve the battery power. But if the voltage drops below a certain % level the circuit will automatically switch itself back on again to keep the flash at a consistent level. A small neon light is included in the circuit and lights up to indicate when the flash gun is fully charged.

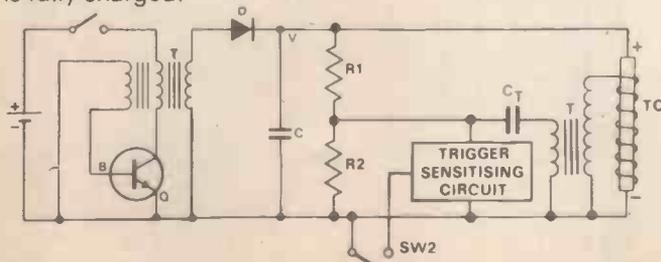


Fig 10. Basic diagram of a manual flashgun.

In recent years automatic flashguns have become keenly competitive with ordinary flashguns (as described above). The automatic flashguns use a fast acting photocell such as a silicon photodiode. These cells operate so quickly that they are able to calculate the correct exposure setting while taking the light reading off the subject. In the flashgun the cell is used to read the amount of light reflected from the object and transfer the information to an integrated circuit which works out when enough light has been reflected to register on the film. It then shuts off the flash by cutting the power supply.

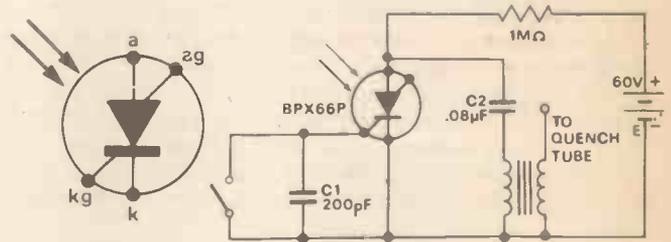


Fig. 11. The extra circuitry required for an automatic flashgun.

The auto flashes of the 60s used a system called 'Dump Quenching' which meant that when the integrated circuit decided that there had been enough light emitted it would cut out the flash by shorting the remainder of the power in the capacitor to the negative rail. The system worked well but wasted a lot of power, so in the early 70s a 'Blocking Quench' system was introduced (Fig. 11). This used a silicon sensor and integrated circuit as before but instead of shorting the circuit it used a faster thyristor which cut the power from the capacitor to the flash gun thus leaving the capacitor still partially charged.

On some recent auto exposure cameras there is a special connection for flash guns made by the same manufacturer (for the really dedicated) whereby the exposure calculation circuitry controls the flash power directly and also has an LED readout in the viewfinder informing the photographer of the state of readiness of the flash gun and also whether there was enough light to illuminate the subject correctly.

Recent innovations in portable flash photography include double flash heads on one body — one a low power flash and the other high power, for bounce diffused lighting. Rollei have recently introduced their latest flash which has an illumination range of 80 feet for an average speed film. The development in their flash is that it has an LED readout — and when the ASA film speed and aperture used are fed in it works out the distance the flash can cover.

This gives some idea of the way in which electronic flash photography is rapidly developing. The flashguns these days can even switch the cameras electronic shutters to the speeds required to take flash pictures.

All the figures illustrating this article are reproduced from "Electronics And The Photographer" by T. D. Towers, and appear by permission of the publishers, Focal Press. We recommend this book to anyone wanting to read further on this subject. It is available from your bookshop at £6.95. (If you have any difficulty obtaining it write to Focal Press, 31, Fitzroy Square, London W. 1. enclosing £6.95 plus 80p p + p).

# Short Circuit

## INFRA-RED INTRUDER ALARM

This intruder alarm is of the type where the alarm sounds when an invisible beam of infra-red light is broken by the intruder. The circuit is intended to feed an existing burglar alarm system, and units of this type are not usually used as the only method of intruder detection. The system is very simple, and requires no special lenses or filters for operation over distances of about 2 metres or less. A short range is usually sufficient to cover entrances to rooms, span corridors, etc.

The unit actually consists of two separate circuits, one being used to produce an infra-red beam, and the other being used to detect this beam and sound the alarm if there is a break in the signal. In common with most systems of this type, a pulsed infra-red beam is used. Unless of high power, it would be difficult to produce a continuous beam circuit that would give good reliability and a useable range, since the beam would otherwise tend to be swamped by the ambient infra-red level. A modulated beam can easily be differentiated from the ambient infra-red radiation, enabling a low power beam to be employed.

The transmitter is based on the popular 555 timer IC, and it is used in the standard astable mode. R1, R2, and C2 are the timing components, and these give an operating frequency of roughly 5.25kHz. A standard 555 oscillator does not produce a true squarewave output, as the output is in the high state for a longer period than it is in the low state. This is due to the fact that

the output goes high during the time that C2 charges up through the relatively high resistance of R1 plus R2 in series, and low while C2 discharges through the low resistance of R2 and an internal transistor of IC1. The values used in this case give an output which is in the low state for only about 10% of the time.

During these brief negative output excursions Q1 is pulsed on by the base current it receives via R3. It then passes a current of about 500 mA. to infra-red LED1 by way of current limiting resistor R4. Of course, the average current through LED1 is only about 50 mA., and this system therefore gives fairly strong pulses of infra-red together with a reasonably low average current drain. There is no output from LED1 in the visible light spectrum.

At the receiver the pulses of infra-red are detected by photodiode LED1. This is fed from the supply rails via load resistor R1. The



pulses of infra-red cause the leakage current through LED1 to increase momentarily, giving a series of small voltage pulses at the junction of R1 and LED1. These are fed by C2 to the input of a straight forward high gain amplifier which uses Q1 and Q2 in a conventional two stage direct coupled arrangement. C2 and C4 are purposely given low values so that the circuit has a poor response at low frequencies. This gives good rejection of 50 Hertz signals produced by LED1 picking up the infra red radiation from mains powered lighting. The circuit has high gain at the much higher operating frequency of the transmitter circuit though.

The output from the amplifier is coupled by C5 to a rectifier and smoothing circuit which utilizes D1, D2, C6, and R6. The positive bias produced by this circuit is fed to one input of operational amplifier IC1. The other input is fed with a bias voltage by R7 and R8. Normally the fixed bias to the inverting (-) input will be higher

than the bias fed to the non-inverting (+) input. IC1 is used as a comparator, and under these conditions its output goes high, energising the relay coil with discrete buffer stage Q3 being used to provide the fairly high drive current required. If an intruder breaks the beam momentarily, the charge on C6 rapidly decays, taking the voltage fed to the non-inverting input of IC1 below that at the inverting input. IC1's output then goes low, the relay is switched off, and relay contacts RLA1 open so that the main alarm system is triggered.

The system is fail-safe in that if the power to either the transmitter or receiver should cease, or be switched off, the relay contacts will open and trigger the main alarm system.

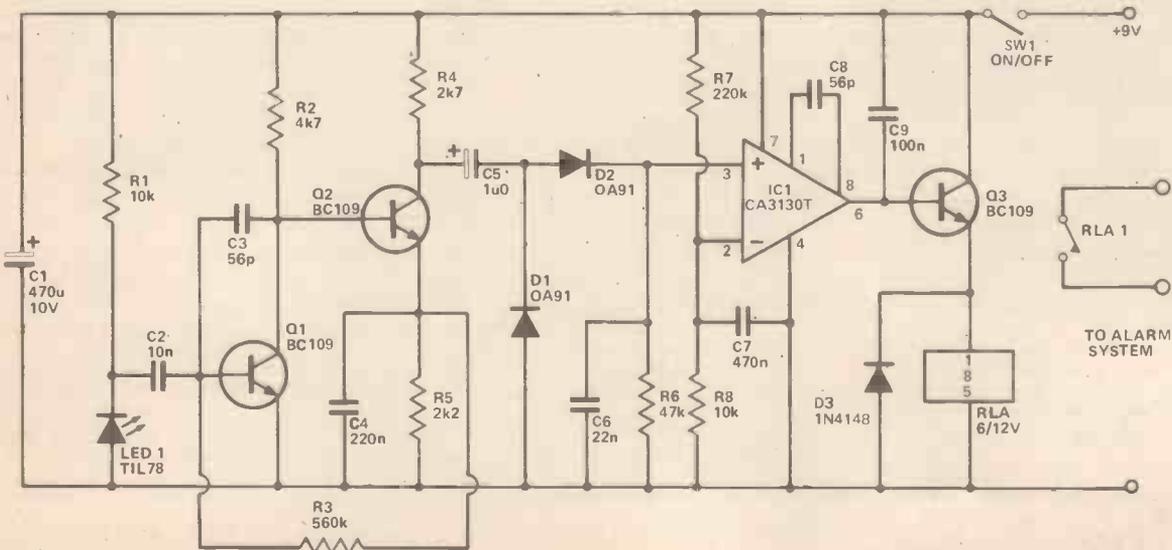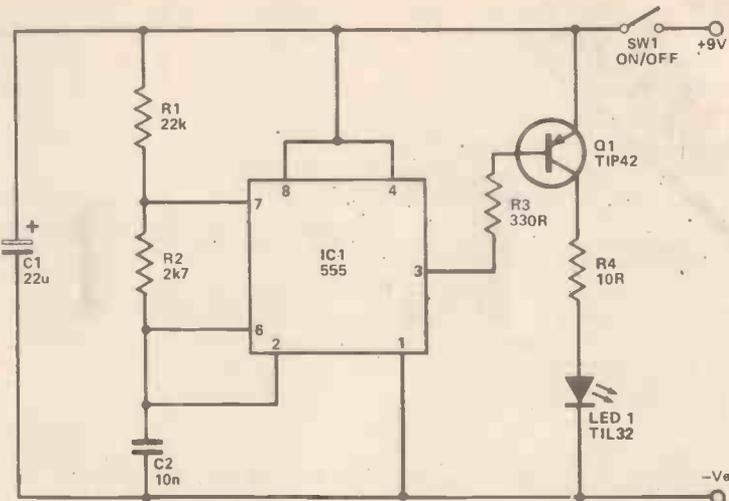The current consumption of the circuit is about 45 mA. when the relay is switched on, and about 3 mA. when it is switched off.




**Next  
Month**

# Hobby Electronics
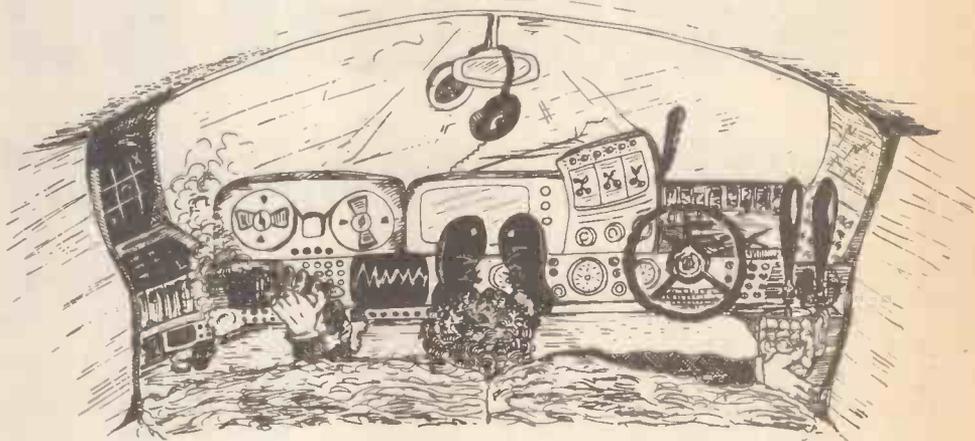
## PASS THE LOOP

Time again for another of HE's famous game projects. This time we have taken the ageless 'pass the loop' game where a steady hand and nerves of steel are needed to thread a wire loop over a complex wire shape. We have brought it bang up to date with a variable timer, a noise generator to tell you when you've succeeded and some clever circuitry that will tell you when you have failed.

This elegant little circuit is an ideal fundraiser for fetes, fairs or just good old fashioned fun at parties. The circuitry is extremely simple, ideal for 'old hands' and newcomers alike.



## VIBRATION DETECTION

Bothered by burglars then this has got to be for you! The HE vibration detector is sensitive enough to detect a fly tip-toeing across the sensor or adjusted to respond to the heavy tread of a villain going through your drawers. Protect your property with this revolutionary little circuit, we even connected our prototype to the office copies of HE, whoever is pinching them will be in for a surprise! However you decide to use it don't miss next month's issue for full constructional details.

## ICE

Or, to put it another way, In Car Entertainment. The world's leading Hi Fi manufacturers are now looking to the car to be the big 'boom' market for the eighties. Next month Terry Bentley, a leading motoring journalist looks at some of the equipment currently available. Is it

worth spending £500 on a radio cassette player, can the small speakers ever match up to large devices used in domestic Hi Fi, what about the acoustics of the small metal boxes we drive? All these questions and more will be answered next month.

## EQUITONE

In conjunction with our stereo booster we proudly present the 'Equitone', this cunningly simple device will allow you to make more of your existing car Hi Fi system. Three fully independent tone filters to control Bass, Mid and Treble. It has got to be heard to be believed.

## TELETEXT

Tired of watching ordinary TV programmes? These days the BBC and IBA transmit something like 1000 'pages' of information with the existing TV signal. If you have the correct decoder these pages are available completely free. Currently you can call up information about the latest weather reports, Stock Market information, what's on at your local cinema to the number of seats available on airline flights.

The system was pioneered by engineers at

the BBC during the late sixties and early seventies, so we thought it would be appropriate to ask the BBC to tell us all about Teletext. One of the BBC's top engineers puts pen to paper next month, exclusively for HE, in what must be one of the most informative articles ever written about Teletext, past, present and future! Plus, we have news of some of the latest developments that have yet to be announced see it first in HE next month.

---

# The August issue will be on sale July 11th

---


The items mentioned here are those planned but unforeseen circumstances may affect the actual contents.

# Don't buy a digital watch until you read this report

There are so many digital watches on the market, with varying functions, that the average person is bound to feel somewhat confused.

A new survey of the electronic watch industry has been produced to clarify this confusion and to give an unbiased and objective answer to the many questions that are constantly being raised.

by Trevor Raven.  
 C.Eng. AMBIM. MIERE

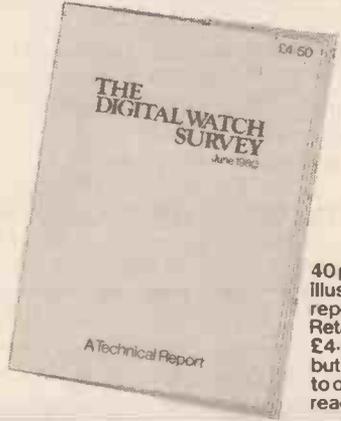

40 page illustrated report. Retail price £4.50 but just £1 to our readers.

- \* How accurate are electronic watches?
- \* Who makes Seiko's?
- \* What is the importance between brand names?
- \* Is solar power worth the extra money?
- \* What are the most important features in a watch?
- \* When will prices stop falling?

The survey answers all of these questions and tells you what to look for in a quartz watch; how they work; why the prices vary so much; what the future holds.

**SPECIAL OFFER**

Send today for this technical report, plus news of a unique Metac offer to beat all special offers.

Complete the coupon below and send it FREEPOST (no stamp required) and we will post, Same Day Despatch, the technical report giving you all you need to know about electronic watches and details of our special offer.

## Which is the best watch?



These four watches are very different in price, durability and functions. How would you choose between them?

This unbiased and objective report helps you to make this decision and gives you a deeper insight into the rapidly changing and exciting world of the micro-chip.


For your free copy of the report complete and return the coupon to: Metac Electronic & Time Centres, 24-hour Despatch Centre, FREE-POST, 47A High St., Daventry, Northants.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_  
 \_\_\_\_\_

HE7
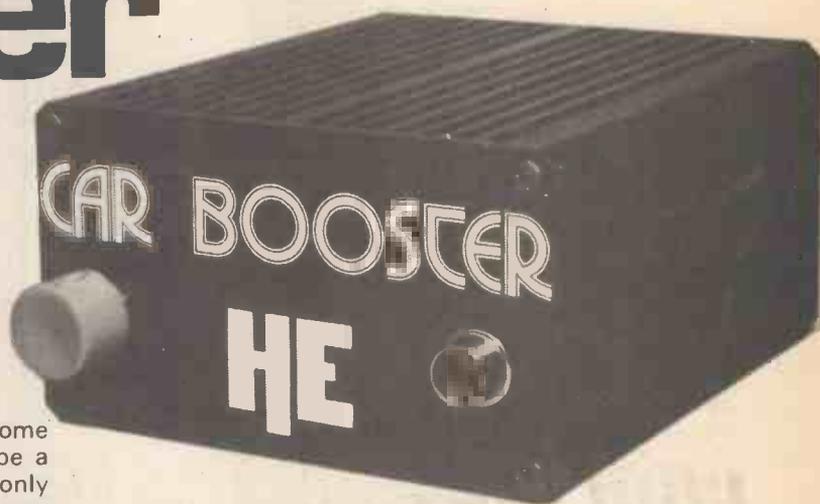
# Car Booster

*Have a quickstep in the carpark,  
discos in the drive or merely  
freak out on the freeway  
with the HE Car  
Power Booster.*



EVERY ONCE IN A WHILE, the HE Project Team come up with a design that is virtually guaranteed to be a winner. And we feel that this project is just that! Not only is it easy to build, but it looks good, sounds even better and is cheap! Now, we can't be any fairer than that, can we?

The HE Car Booster consists essentially of two small printed circuit boards (one per channel for stereo), each of which holds the circuitry for an 18-watt power amplifier. The "18-watts" is not 18-watts "music power," "peak power", or "any old-power" that some equipment manufacturers specify when they talk of their devices but 18-watt true RMS into speakers of 4Ω impedances. In actual fact when we put the finished booster to test in our lab we recorded a full 22 watts RMS per channel — and that is loud!

Because the amplifier circuit contains the almost unbelievable sum of only 13 components, the PCB is consequently very small (less than three square inches), and it really is incredible that so few can sound so loud. The credit for this efficiency can be taken by the use of a purpose designed IC — The Hitachi HA 1388 which is a 12-pin, Single-in-line, plastic package and it really does all the donkey work. This chip brings in-car audio boosters to the amateur electronics world with a bang and anybody with a soldering iron and a steady hand is within reach of constructing their own.

Readers of May's HE may remember us saying that we were going to use the stylish SINK BOX case again, after it was used so successfully in the 5080 Stereo System. Well, here it is, holding the HE Car Booster, in a 100 millimetre length — a good 50% or more smaller than available ready-built units of similar power and performance. Because of its small size the booster is mountable either behind the dashboard of your car so as not to be seen, or simply fastened to the existing cassette/cartridge player or radio whose output is to be boosted.

All you need is the HE Car Booster, a pair of 20-watt speakers (more on them later) and a signal from your sound source (be it cassette, radio or whatever) and you can be enjoying about 40 watts of Hi-Fi audio inside your car. That means even in a car with the noisiest of engines we reckon you'll have enough volume there to blow your roof off.

## CONSTRUCTION

The low component count of the circuit means construction is very simple. The only thing to watch is the correct polarisation of capacitors so follow the overlay carefully.

The metal tab of the IC should of course go to the outside of the board to make contact with the case. There is no need to use isolating washers between the IC and case as the metal tab of the IC is at ground potential, if your car is negative earth.

Switch SW1 connects in series with the positive supply line and LED 1 with series resistor R<sub>3</sub>, go across the supply connections to one of the boards.

The two boards bolt to the bottom of the case, facing each other and slightly offset, so that the large capacitors C10 on each board do not touch any component on the other board.

All connections, the on/off switch SW1, and the LED go onto the end panels. We suggest the use of spring-loaded connections to the speakers. Phono sockets are best for the I/P from your cassette player and either a heavy duty (over 4 amps) power connector, or simply flying leads, for supply connections. Remember that all speaker connections should be isolated from earth, if you short any one of the four leads to 0 V that channel will cease to operate.

It is not necessary to adapt your existing cassette/cartridge player/radio if you don't want to. The HE Car Booster is designed to accept a signal from the speaker O/Ps of the source. A simple paralleled connection somewhere along the speaker line, either from the existing speaker end or the existing sound source end, will suffice. If you want to make a plug in/out connection you can put a couple of Phono sockets into your cassette player but this is not essential. You must however make sure that the grounded lead of each speaker connection is taken to the ground I/P of the corresponding channel of the booster and the signal lead to the signal I/P. Figure 4 gives suggestions how to connect the Booster.

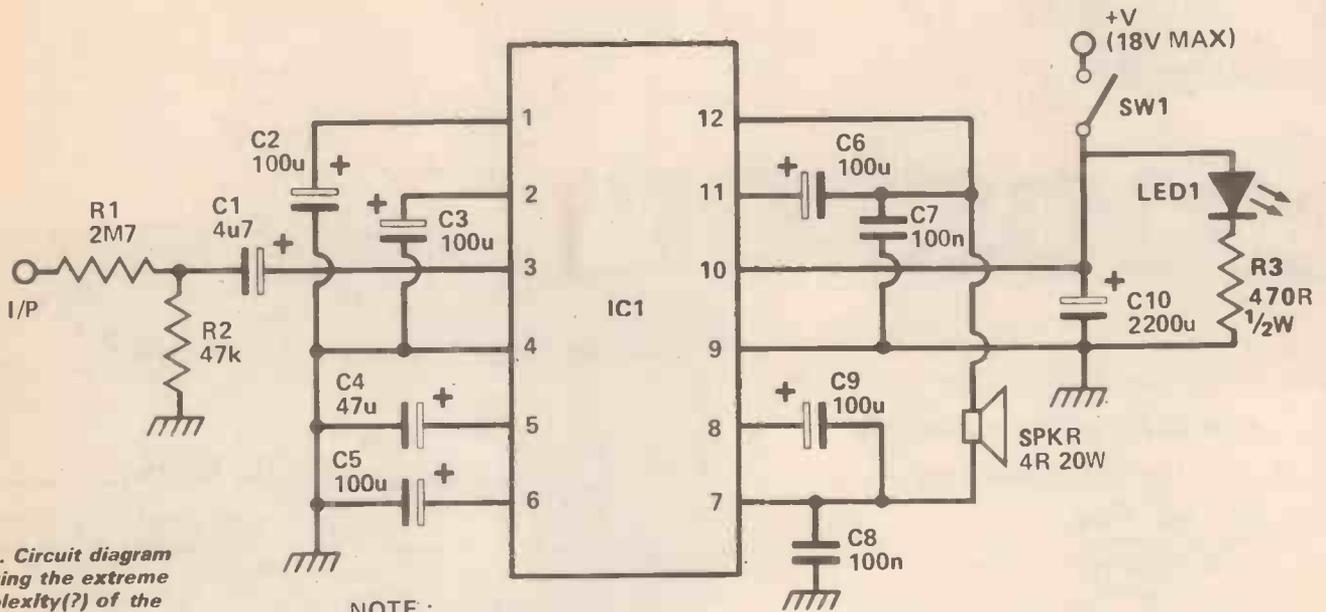


Fig. 1. Circuit diagram showing the extreme complexity(?) of the HE Car Booster — one channel.

NOTE :  
IC1 IS HA1388

## How it Works

The HA 1388 is an 18-watt amplifier IC designed and manufactured specifically for use in car amplifiers.

A normal power amplifier, operating from the voltage available on a car electrical system i.e. nominal 13 volts DC can only produce an output voltage swing of no more than 6 volts amplitude (12 volts peak to peak) across the load. The maximum RMS power available is 4.5 watts.

However, the HA 1388 has two such amplifiers in the IC which operate out of phase with each other. Figure shows the concept of the design. AMP 1 acts as a non-inverting amplifier, whose O/P is fed to the speaker and the inverting I/P of AMP 2. The outputs of the two amplifiers are therefore completely out of phase, producing voltage swings of 24 volts peak to peak (12 volts amplitude) across the speaker. This doubling of voltage quadruples the power available from 4.5 to 18 watts.

It should be noted that neither speaker terminal is at ground potential, unlike the input to the amplifier, or the outputs of the car cassette player. Care should be taken therefore to isolate them from ground.

## Parts List

### RESISTORS (ALL 1/4W, except where stated otherwise)

R1	2M7
R2	47K
R3	470R, 1/2W

### CAPACITORS

C1	4u7 16V Tantalum
C2,3,5	100u 6V3 Tantalum
C4	47u 6V3 Tantalum
C6,9	100u 10V Tantalum
C7,8	100n Ceramic
C10	2200u 16V P.C. Mounting Elect.

### SEMICONDUCTORS

IC1	HA 1388
LED	RED LED

### MISCELLANEOUS

SW1 Single pole, latching push button  
 4 Spring action terminals, 2 red, 2 black  
 2 Phono sockets  
 In-line fuse holder and 3 amp fuse.  
 Case.


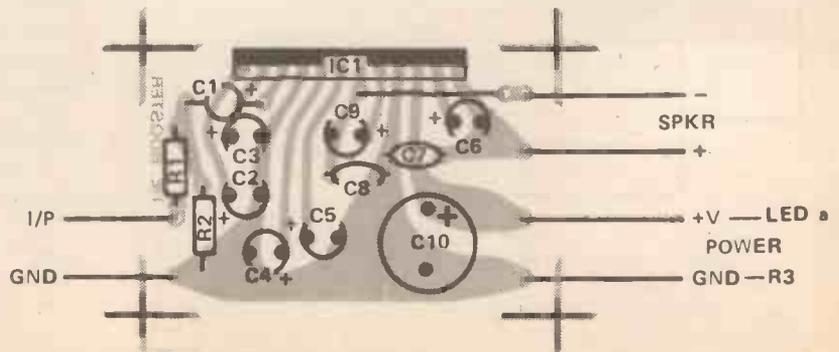
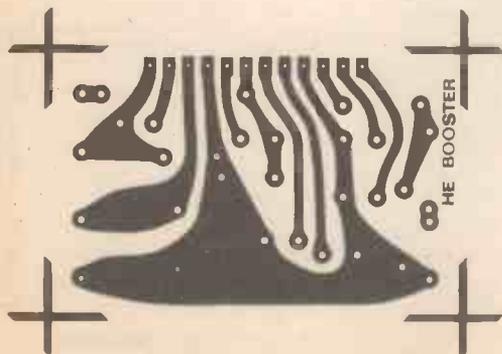


Fig. 2. PCB overlay.

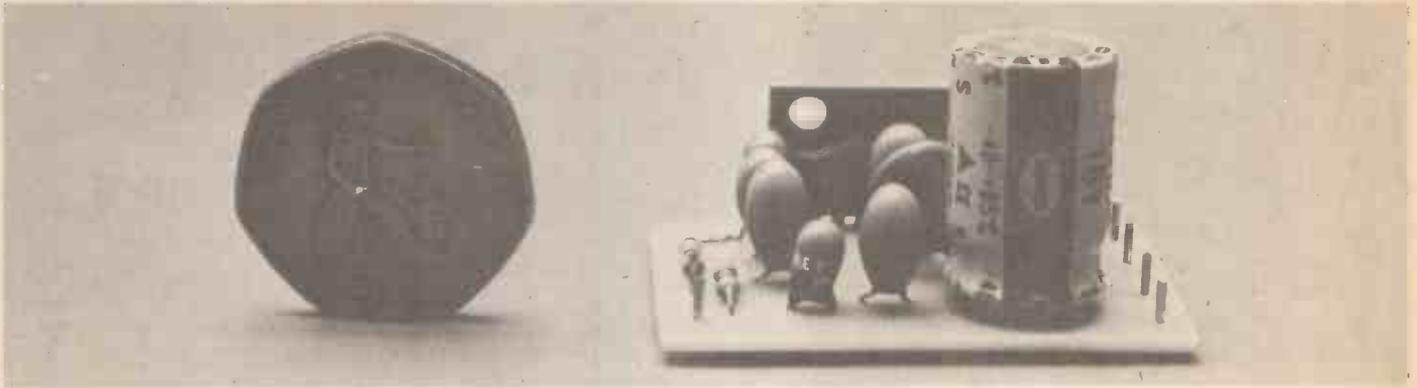

## Buylines

Ambit International are stocking the HA 1388 power amplifier IC and to our knowledge are the only suppliers this side of the Rising Sun.

The case is, of course from our old friends, West Hyde Developments and is the Sink Box in a 100mm length.

Although quite a few mail order companies hold car speakers in their stock, after a great deal of research and painful earache we found the exceptional range stocked by Tandy to be worth a close look. Their door-mounting speakers, no. 12-1855 were the cheapest we could find to handle the power but overall, the pod speakers, no. 12-1853 were the best value for money and of a very, very good quality. We have used Tandy before and have never been disappointed by their goods or their service.

All other components will be easy to come by.


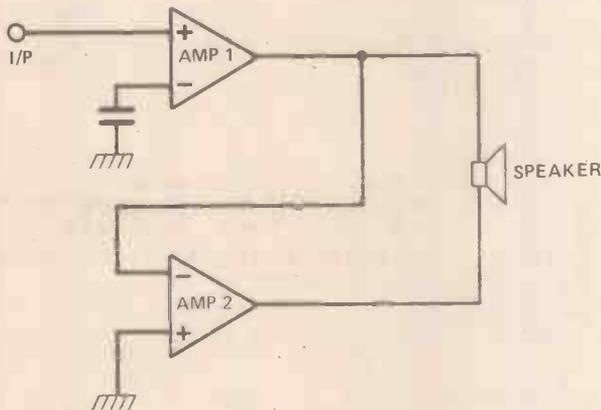


Fig. 3. Simplified internal circuitry of the HA 1388.

Fig. 4. Diagram showing permanent connection between the sound source and the HE Car Booster (for plug/socket connections in broken lines).

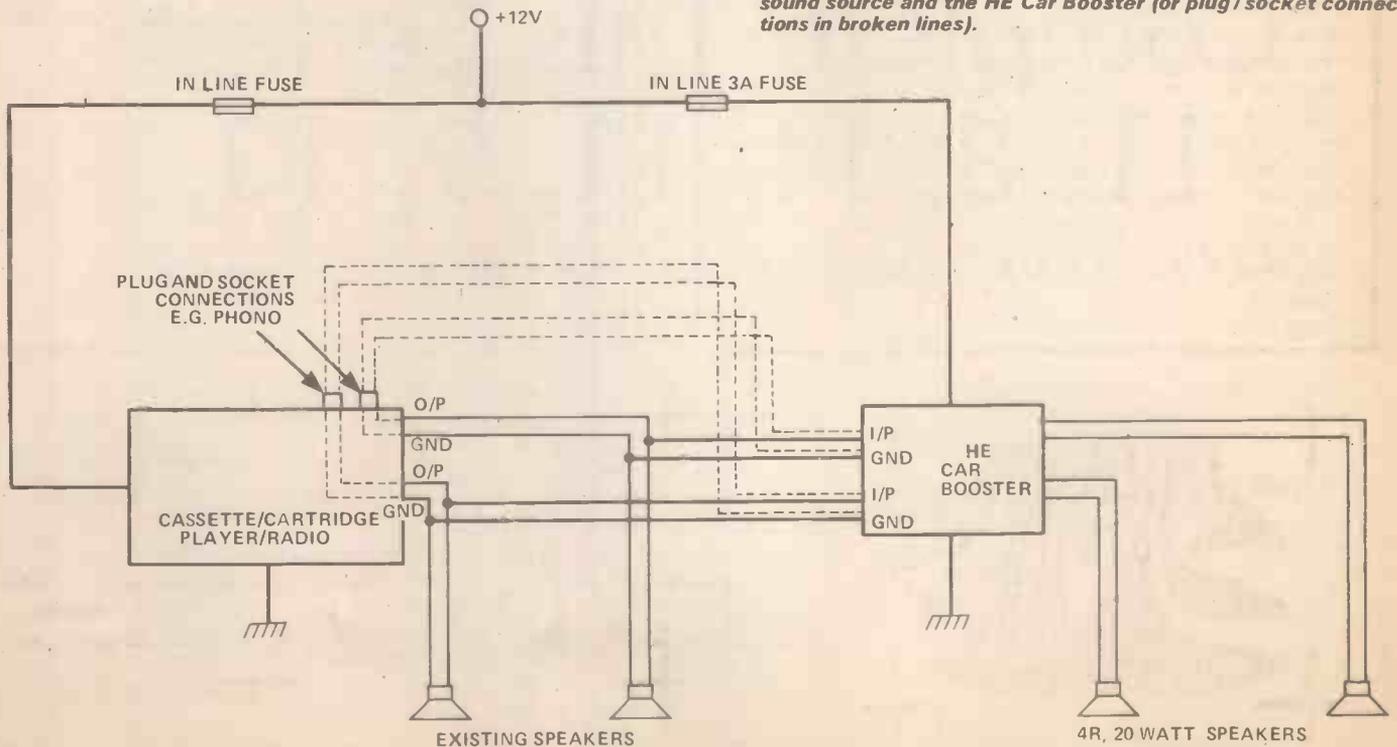

# Short Circuit

## SPEECH PROCESSOR

Speech processors are primarily used in radio transmitting equipment, but can be used in public address systems, disco equipment, etc., where it is necessary for a speech signal to be as effective as possible.

Bass frequencies do not aid the intelligibility of speech, and treble frequencies are of little help either. The signal can therefore be made more effective by attenuating the higher frequencies (above about 3kHz) and the

lower frequencies (below about 250Hz), and then boosting the signal to compensate for the reduction in its amplitude.

A speech signal has a rather spikey waveform, and the average signal amplitude is rather low in comparison to the peak level. The signal is given considerably more "punch" if the peak levels are reduced, but the lower levels are not compressed.


In this circuit the signal from the (50k impedance) microphone is amplified by a two stage pre-amplifier using Q1 and Q2 in the

common emitter mode. RV1 is microphone gain control. The output from the preamplifier is coupled by C6 to a simple clipping circuit which uses D1 and D2 to clip the signal at about  $\pm 0.5$  V. In use the output from the preamplifier will be somewhat higher than this, and so signal peaks will be severely reduced in amplitude by the clipping circuit, but signals below  $\pm 0.5$  V. will not be affected.

This gives the required compression, but also distorts the signal and generates high frequency distortion com-

ponents. These are considerably attenuated by an active low pass filter based on Q3 and having a nominal 18dB. per octave roll off rate. This gives a reasonably "clean" signal, and provides the required high frequency attenuation. The low frequency attenuation is obtained by using low value coupling capacitors in the circuit.

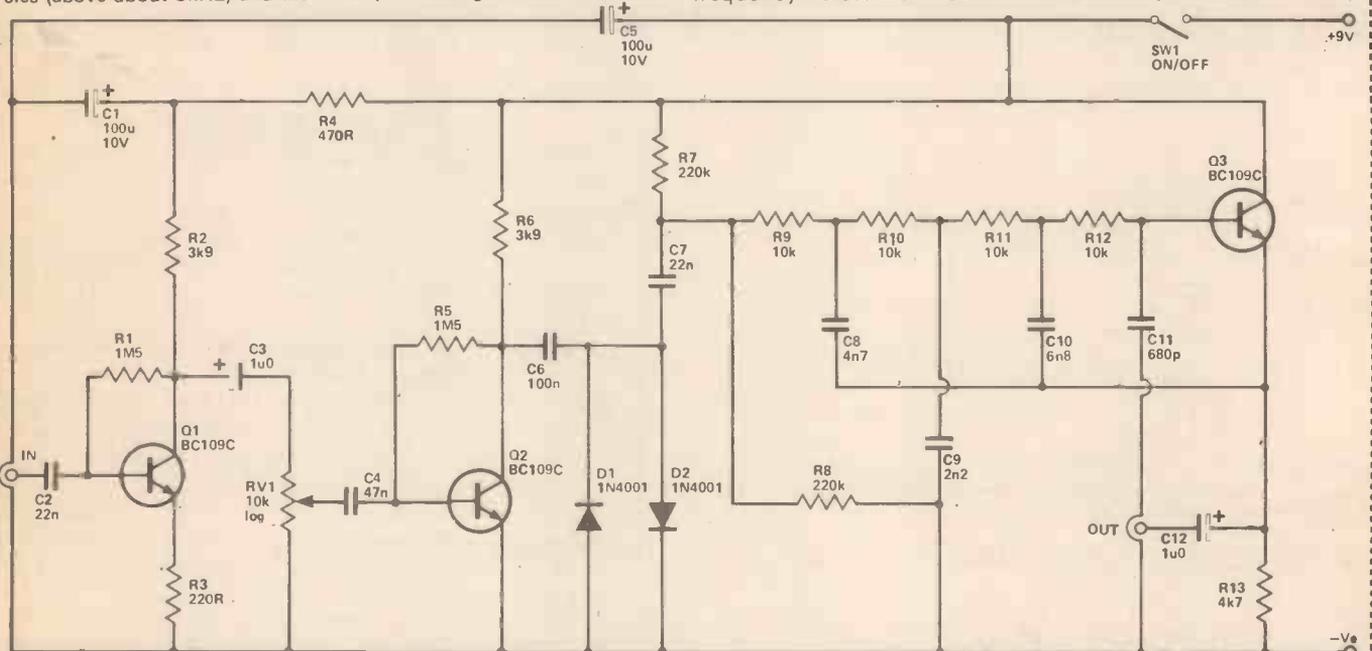RV1 is adjusted to give the desired amount of compression, and should not be advanced too far as this would cause the output to be severely distorted.



# Complete This Series:

## 11, 8, 14, 11, 9, 13,

•••, •••, •••, •••, •••, •••, •••,

Send to: Subscriptions Department,  
Hobby Electronics  
PO Box 35, Bridge Street,  
Hemel Hempstead, HERTS.

Dear Hobby Electronics, please send me a copy of each issue as soon as it is published. I enclose a cheque for £9.

Name .....

Address .....

Tricky, isn't it. Here's the answer: 11, 8, 12 and 10, 14, 12. Any wiser?

The key is that these are the days when you have to be in your newsagents this year to get your copy of Hobby Electronics on the day of publication. Remember the series: 11, 8, 14, 11, 9, 13, 11, 8, 12, 10, 14, 12. But don't internalise it too well — the numbers will be different next year.

Got a headache, yet? Here's relief: there is a way you can ensure copies of Hobby Electronics automatically — no need to remember dates, no need to rush to the newsagents, no need to impose on your friends to get you a copy when you go abroad. It couldn't be simpler; just write your name and address on the coupon below and send it to us with a cheque for £9.

# BI-PAK

**SEMICONDUCTORS SEND YOUR ORDERS TO**  
**DEPT. HE7, PO BOX 6, WARE HERTS**  
**VISIT OUR SHOP AT: 3 BALDOCK ST., WARE, HERTS.**  
**TEL: 0920 3182. TELEX: 817861**

## TRANSISTORS

## THYRISTORS

## LEDS

AC126	£0.21	BC148	£0.08	BC549	£0.12	BU105	£1.84	ZTX108	£0.12
AC127	£0.18	BC149	£0.08	BC550	£0.16	BU105/02	£2.24	ZTX109	£0.12
AC128	£0.30	BC157	£0.12	BC556	£0.16	BU204	£1.61	ZTX300	£0.14
AC128K	£0.30	BC158	£0.12	BC557	£0.15	BU205	£1.61	ZTX500	£0.15
AC132	£0.23	BC159	£0.12	BC558	£0.14	BU208/02		2N1613	£0.23
AC134	£0.23	BC167	£0.14	BC559	£0.16			2N1711	£0.23
AC137	£0.23	BC168	£0.14	BD115	£0.58	MJE2955	£1.04	2N1889	£0.52
AC141	£0.25	BC169	£0.10	BD116	£0.92	MJE2955	£0.69	2N1890	£0.52
AC141K	£0.25	BC169C	£0.12	BD121	£0.78	MJE3440	£0.60	2N1893	£0.35
AC142	£0.30	BC170	£0.10	BD124	£0.81	MPF102	£0.40	2N2147	£0.86
AC176	£0.21	BC171	£0.10	BD131	£0.40	MPF105	£0.40	2N2148	£0.81
AC176K	£0.30	BC172	£0.10	BD132	£0.40	MPSA06	£0.23	2N2192	£0.44
AC178	£0.29	BC173	£0.10	BD133	£0.46	MPSA06	£0.23	2N2193	£0.44
AC179	£0.29	BC177	£0.18	BD135	£0.40	MPSA06	£0.23	2N2194	£0.44
AC190	£0.23	BC178	£0.18	BD136	£0.40	MPSA85	£0.23	2N2217	£0.25
AC180K	£0.32	BC179	£0.18	BD137	£0.40	MPSA85	£0.23	2N2218	£0.25
AC181	£0.23	BC180	£0.29	BD138	£0.41	OC22	£1.73	2N2218A	£0.23
AC181K	£0.32	BC181	£0.10	BD138	£0.41	OC23	£1.73	2N2219	£0.23
AC187	£0.21	BC182L	£0.10	BD140	£0.41	OC24	£1.55	2N2219A	£0.28
AC187K	£0.32	BC183	£0.10	BD155	£0.92	OC25	£1.15	2N2904	£0.21
AC188	£0.21	BC183L	£0.10	BD175	£0.69	OC26	£1.15	2N2904A	£0.21
AC188K	£0.32	BC184	£0.10	BD176	£0.69	OC28	£0.92	2N2905	£0.24
AD140	£0.69	BC207	£0.13	BD177	£0.78	OC29	£1.09	2N2905A	£0.23
AD142	£0.98	BC208	£0.13	BD178	£0.78	OC35	£1.03	2N2906	£0.18
AD143	£0.86	BC209	£0.14	BD179	£0.86	OC36	£1.03	2N2906A	£0.21
AD149	£0.69	BC212	£0.10	BD203	£0.92	OC70	£0.28	2N2970	£0.25
AD161	£0.40	BC211	£0.10	BD204	£0.92	OC71	£0.17	2N2926G	£0.11
AD182	£0.40	BC213	£0.10	BDY20	£0.92	TIC44	£0.33	2N2926Y	£0.09
AD161	£0.40	BC213L	£0.10	BF457	£0.43	TIC45	£0.40	2N2926Y	£0.09
162MP	£0.81	BC214	£0.10	BF458	£0.43	TIP29A	£0.46	2N2926Y	£0.09
AF124	£0.35	BC214L	£0.10	BF459	£0.44	TIP29B	£0.48	2N2926Y	£0.09
AF125	£0.35	BC237	£0.18	BF594	£0.35	TIP29C	£0.51	2N3053	£0.20
AF126	£0.35	BC238	£0.18	BF596	£0.32	TIP30A	£0.46	2N3054	£0.46
AF127	£0.37	BC251	£0.17	BF939	£0.28	TIP30B	£0.48	2N3055	£0.46
AF139	£0.40	BC251A	£0.18	BF940	£0.29	TIP30C	£0.51	2N3055	£0.46
AF186	£0.58	BC301	£0.32	BF979	£0.32	TIP31A	£0.46	2N3614	£1.15
AF239	£0.44	BC302	£0.33	BF980	£0.32	TIP31B	£0.48	2N3615	£1.21
AL103	£1.38	BC303	£0.32	BFX29	£0.25	TIP31C	£0.51	2N3646	£0.10
AL103	£1.03	BC304	£0.44	BFX32	£0.26	TIP32A	£0.45	2N3702	£0.09
AU104	£1.61	BC327	£0.18	BFX84	£0.25	TIP32B	£0.45	2N3703	£0.09
AU110	£1.61	BC328	£0.17	BFX85	£0.28	TIP32C	£0.51	2N3704	£0.08
BU113	£1.61	BC337	£0.17	BFX86	£0.29	TIP41A	£0.51	2N3705	£0.08
BU107A	£0.09	BC338	£0.17	BFX87	£0.25	TIP41B	£0.52	2N3706	£0.08
BC107B	£0.10	BC440	£0.35	BFX88	£0.25	TIP41C	£0.55	2N3707	£0.08
BC107C	£0.12	BC441	£0.35	BFY50	£0.26	TIP42A	£0.51	2N3708	£0.08
BC108A	£0.10	BC460	£0.44	BFY51	£0.20	TIP42B	£0.53	2N3709	£0.08
BC108B	£0.11	BC461	£0.44	BFY52	£0.20	TIP42C	£0.55	2N3710	£0.08
BC108C	£0.12	BC462	£0.44	BFY53	£0.20	TIP2955	£0.69	2N3711	£0.08
BC109A	£0.09	BC478	£0.23	BP120	£0.44	TIS43	£0.25	2N3712	£0.08
BC109B	£0.10	BC479	£0.23	BP119	£0.44	TIS90	£0.21	2N3819	£0.21
BC109C	£0.12	BC547	£0.12	20MP	£0.82	T146	£0.22	2N3820	£0.40
BC147	£0.08	BC548	£0.12	BRY39	£0.51	ZTX107	£0.12		

Volts No.	Price	Volts No.	Price
10 THY600ma/10v	£0.17	50 THY7A/50	£0.55
20 THY600ma/20v	£0.18	100 THY7A/100	£0.58
30 THY600ma/30v	£0.23	200 THY7A/200	£0.65
50 THY600ma/50v	£0.25	400 THY7A/400	£0.71
100 THY600ma/100v	£0.29	600 THY7A/600	£0.89
200 THY600ma/200v	£0.44	800 THY7A/800	£0.05
400 THY600ma/400v	£0.51		
Volts No.	Price	Volts No.	Price
50 THY1A/50	£0.30	50 THY10A/50	£0.55
100 THY1A/100	£0.32	100 THY10A/100	£0.65
200 THY1A/200	£0.37	200 THY10A/200	£0.71
400 THY1A/400	£0.44	400 THY10A/400	£0.80
600 THY1A/600	£0.52	600 THY10A/600	£1.13
800 THY1A/800	£0.67	800 THY10A/800	£1.40
Volts No.	Price	Volts No.	Price
50 THY3A/50	£0.32	50 THY16A/50	£0.62
100 THY3A/100	£0.35	100 THY16A/100	£0.66
200 THY3A/200	£0.48	200 THY16A/200	£0.71
400 THY3A/400	£0.58	400 THY16A/400	£0.88
600 THY3A/600	£0.58	600 THY16A/600	£1.03
800 THY3A/800	£0.75	800 THY16A/800	£1.59
Volts No.	Price	Volts No.	Price
50 THY5A/50	£0.51	50 THY30A/50v	£1.36
100 THY5A/100	£0.57	100 THY30A/100v	£1.64
200 THY5A/200	£0.51	200 THY30A/200v	£1.87
400 THY5A/400	£0.65	400 THY30A/400v	£2.06
600 THY5A/600	£0.79	600 THY30A/600v	£4.03
800 THY5A/800	£0.93		

O/no	Size	Colour	Price
1501	125	RED	£0.10
1502	125	GREEN	£0.16
1503	125	YELLOW	£0.16
1504	2	RED	£0.10
1505	2	GREEN	£0.16
1506	2	YELLOW	£0.16
1509	2	CLEAR	£0.12
(Ill Red)			
SUPER 'Hi' Brine' Type			
1521	125	RED	£0.11
1522	2	RED	£0.11
1514	ORP 12	Light dependent resistor	£0.70
1520	OCPT1	Photo transistor	£0.40

### CLIPS

1508/125	pack of 5	125 clips	£0.17
1508/2	pack of 5	2 clips	£0.20

### DISPLAYS

DL307	7 segment D.P. left (0.3" height) common anode single digit	O/NO 1523	£0.80
DL707	7 segment D.P. left (0.3" height) common anode single digit	O/NO 1510	£0.92
DL727	RED. 7 segment D.P. right (0.5" height) anode. Two-digit reticulator	O/NO 1524	£1.95
DL727	RED. 7 segment O.P. right (0.5" height) common anode. Two-digit light pipe	O/NO 1512	£2.83
DL747	RED. 7 segment D.P. right (0.5" height) common anode. Single-digit light pipe	O/NO 1511	£1.72

## SILICON RECTIFIERS

200MA	Price	10 Amp	Price
IS920 50v	£0.07	IS10/50 50v	£0.21
IS921 100v	£0.08	IS10/100 100v	£0.24
IS922 150v	£0.09	IS10/200 200v	£0.26
IS923 200v	£0.10	IS10/400 400v	£0.40
IS924 300v	£0.11	IS10/600 600v	£0.48
1 Amp	Price	30 Amp	Price
IN4001 50v	£0.05	IS30/50 50v	£0.64
IN4002 100v	£0.05	IS30/100 100v	£0.79
IN4003 200v	£0.07	IS30/200 200v	£1.06
IN4004 400v	£0.08	IS30/400 400v	£1.43
IN4005 600v	£0.09	IS30/600 600v	£2.02
IN4006 800v	£0.10	IS30/800 800v	£2.23
IN4007 1000v	£0.11	IS30/1000 1000v	£2.65
1.5 Amp	Price	50 Amp	Price
IS015 50v	£0.10	IS50/50 50v	£0.86
IS020 100v	£0.11	IS50/100 100v	£0.96
IS021 200v	£0.12	IS50/200 200v	£1.38
IS022 300v	£0.14	IS50/400 400v	£2.01
IS026 600v	£0.16	IS50/600 600v	£2.58
IS027 800v	£0.18	IS50/800 800v	£2.87
IS029 1000v	£0.28	IS50/1000 1000v	£3.45
IS031 1200v	£0.28		
3 Amp	Price	10 amp Plastic	Price
IN5400 50v	£0.16	400 TR110A/100	£0.88
IN5401 100v	£0.17	400 TR110A/200	£1.06
IN5402 200v	£0.18	400 TR110A/400	£1.29
IN5404 400v	£0.19		
IN5406 600v	£0.24		
IN5407 800v	£0.28		
IN5408 1000v	£0.34		

## OPTO-ISOLATORS

Isolation Breakdown - Voltage 1500 - continuous two current 100mA  
 CIL74 Single-channel 6 pin DIP standard type - optically coupled pair with infra-red LED emitter and NPN silicon photo transistor O/NO 1497 £0.57  
 CIL74A Multi-channel 8 pin DIP two isolated channels O/NO 1498 £1.15  
 CIL74B Multi-channel 16 pin DIP four isolated channels O/NO 1499 £2.53

## SECOND GRADE LED PACK

A pack of 10 standard sizes and colours which fail to perform to their rigid specification but which are ideal for amateurs who do not require the full spec.  
 O/NO 1507 £1.04

## SOCKETS

1611	8 pin DIL	£0.09	1615	28 pin DIL	£0.26
1612	14 pin DIL	£0.11	1723	40 pin DIL	£0.34
1613	16 pin DIL	£0.12	1616	TO18 transistor	£0.13
1614	18 pin DIL	£0.18	1617	TO3 transistor	£0.37
1721	20 pin DIL	£0.20	16117	TO3 transistor	£0.13
1722	22 pin DIL	£0.22	1724	14 pin DIL Wire wrap	£0.25
1614	24 pin DIL	£0.24		gold plated Cambion	£0.25

## G.P. SWITCHING TRANSISTORS

TO18am to 2N706/3 5Y27 2B 95A All useable devices, no open and shorts ALSO available in PNP amp to 2N290 BCY70 20 to 57p; 50 for £1.15; 100 for £2.07; 500 for £8.20; 1,000 for £16.10. When ordering state NP/PNP

## G.P. SILICON DIODES

300mW 40VPI (min) sub min. FULLY TESTED Ideal for Organ builders  
 30 for 57p; 100 for £1.72; 500 for £5.75; 1,000 for £10.35

## VOLTAGE REGULATORS

Positive Case	Price	uA7912	TO220	£0.85	
uA7805	TO220	£0.75	uA7915	TO220	£0.85
uA7812	TO220	£0.75	uA7924	TO220	£0.85
uA7815	TO220	£0.75	uA7918	TO220	£0.85
uA7824	TO220	£0.75	72723	14 pin DN	£0.52
uA7818	TO220	£0.75	uA723C	TO98	£0.52
			LM309K	TO3	£1.72
Negative Case	Price	ZTK	338	£0.12	
uA7905	TO220	£0.85			

## ZENER DIODES

400 mw (Bzy88) DO7 Glass encapsulated range of voltages available 1.3v, 2.2v, 2.7v, 3.3v, 3.9v, 4.3v, 4.7v, 5.1v, 5.6v, 6.2v, 6.8v, 7.5v, 8.2v, 9.1v, 10v, 11v, 12v, 13v, 15v, 16v, 18v, 20v, 22v, 24v, 27v, 30v, 3

# Electronic

***Rick Maybury has been snooping around this month into the dark and devious world of Electronic Espionage. It seems that these days anyone with a secret worth knowing can be liable to some kind of 'Surveillance' if you're being bugged then don't miss the section on anti-bugging techniques.***

WHISPER WHISPER HE WHO DARES, a bug's been planted under the stairs. (Apologies to A A Milne). Planting bugs under stairs is not actually such a good idea as we will see later. Today the Microbug, star of countless spy films means more than just an FM transmitter. The spy industry can now offer a bewildering range of devices that can be anything from a straight 'bug' to a device the size of a small suitcase that will analyse the integrity of up to twelve telephone lines simultaneously. A lot has been happening since the rather clumsy attempt at Watergate, nowadays though, most of the blame for these intrusions into privacy can be squarely laid at the door of the microelectronics industry.

Until the advent of the IC in commercial quantities (in the early 70s) the would-be spy had a relatively limited choice of equipment. The FM transmitter was (and still is) the favourite method of eavesdropping. These very simple circuits, sometimes nothing more than a couple of transistors, can be easily built by amateurs, the circuits are freely available (even in this country). With care they can transmit an almost Hi-Fi like quality signal over a distance of a mile or so and still fit into a matchbox.

Luckily such devices are very easy to locate and

immobilise, indeed, much of the equipment on sale in this country is aimed at the 'anti-bug' market. Most bug detectors are nothing more than wide band receivers (usually from 1 to 500 MHz) which locate the transmitter by setting up an RF feedback path to induce the characteristic 'Howl Round' that will increase in amplitude as the receiver is brought closer to the bug's microphone.

Strangely enough it is quite legal to import and sell bugs in this country, as anyone who has an interest in CB radio will tell you the Government introduced legislation in 1967 to prevent the import of cheap 27 MHz walkie talkies. For some reason best known to the Government of the day this left a gaping loophole that permits the sale but not the use, of a large range of transmitting equipment. Take a look sometime through the pages of one of those national classified advertising magazines, you should see scores of small ads offering 'Cordless Microphones', 'Wireless Baby Alarms' or even a blatant 'Miniature FM Wireless Microphone', and they call CB a 'menace'.

The ease of availability of these bugs and their low price has made virtually anyone with a secret a potential target for bugging. If you think that you could be a candidate then at the end of this article we'll give you a



***'Counterspy', the anti-bugging shop in London. They can be found just around the corner from the American Embassy!***

# Espionage

few hints on what to look for, in the meantime let's look at the Telephone, it must rate as the most popular target for eavesdroppers.

## BUZBY BLUES

The beauty of the 'phone, from the spys point of view, is its position in a room or office. The 'phone is usually placed on a desk or table around which potentially interesting conversations are bound to occur. The 'phone can be bugged in one of three ways. The most obvious method is to 'tap' the line. In its simplest form a tap will just consist of a couple of wires linked in parallel to the line at some vantage point within the building or at an outside distribution box in the street. If the tap is likely to be a long term affair the usual plan is to connect the wires to a tape recorder via a VOX (Voice Operated) switch, the tap can then be left unattended, save for an occasional visit to change the tapes. The much publicised Home Office tapping operation at Ebury Bridge House is actually quite interesting though mostly sensationalistic journalism. The suggestion that they have the ability to transcribe the conversations directly into a print out is actually nonsense, as any computer buff will tell you. Even the best voice recognition systems have only a 50% success rate, and that is with clearly spoken English. Mind you, you can be quite sure that someone somewhere is working day and night to improve on that!

Detecting a straight Tap is quite straightforward, a device called a 'Blanched Line Voltage Analyser' will tell you if any unauthorised connections have been made to your line, however, it's not much good against an 'authorised' or professional tap at the exchange for instance.



*Subminiature bug detector, the LED on top blinks when a bug is operating in the room.*

Aside from a physical connection to the line the 'phone offers a couple of other interesting alternatives. Because of the in-built power supply it is ideal for RF bugs, the problem of expiring batteries has always made RF bugs a bit limited. (It was suggested that high levels of RF energy beamed at the American Embassy in Moscow was an attempt by the Russians to re-charge the batteries in their bugs.) Because these bugs are essentially RF, detection again is no real problem.

The third, and probably most elegant (from an electronics point of view) method of phone tampering is the 'Infinity Transmitter'. This cunning little device is little more than a narrow band tone filter and a couple of reed relays. Once implanted inside the phone the spy has only to dial up the phone (on the pretext of a wrong number) wait for the receiver to be replaced and blow a whistle, this activates the relays which keep the line open and the microphone (in the handset) in circuit. There are several, more advanced, variations on the Infinity Transmitter theme, one specimen can be activated without the bell ringing. The use of STD equipment on an international scale makes it theoretically possible to overhear conversations in Australia from the comfort of your armchair in England, mind you, you'll still get large 'phone bills.

## BASIC BUGS

Lower down the scale in terms of complexity, but still valid from the effectiveness point of view is the 'Hard Wire' bug. This is usually nothing more than a concealed microphone connected up to an amplifier. The beauty of this system is that, it's almost impossible to detect, the spy is at a disadvantage though, it is much more difficult



*A complete anti bug system. The suitcase contains a tap detector, a tap defater, telephone monitor and scrambler.*



Wide band surveillance receiver. This model will tune over the range of 1 to 1500 MHz, a built in oscilloscope shows the devices bandwidth and the presence of any other bugs on other frequencies.


to conceal long runs of cable and unless he or she incorporates a tape recorder with a VOX switch it requires almost constant attendance. Several stories however about Hard Wire bugs being built-into buildings during construction sound quite plausible, the Americans in particular have some stories to tell on this score, or so we're told.

### LIGHT LISTENING

Bang up to date now, it's not surprising that our old friend the Laser should pop up somewhere (didn't someone once say that the Laser was an invention looking for an application?). It is now possible to buy yourself a gadget called a Laser Bounce Surveillance Receiver. Operation again is wonderfully simple, sound waves in a room act upon glass imparting minute vibrations onto the glass in sympathy with any speech. A laser (usually outside the visible spectrum) is beamed onto the glass and the reflections, modulated by the vibrations in the glass, bounce back to the receiver to be decoded into speech. It is quite likely that buildings up to a mile away could be 'surveyed' in this way. One further thought, with the trend of modern architects to use mirrored glass in office buildings we suspect that the efficiency of Laser bounce has been improved dramatically.
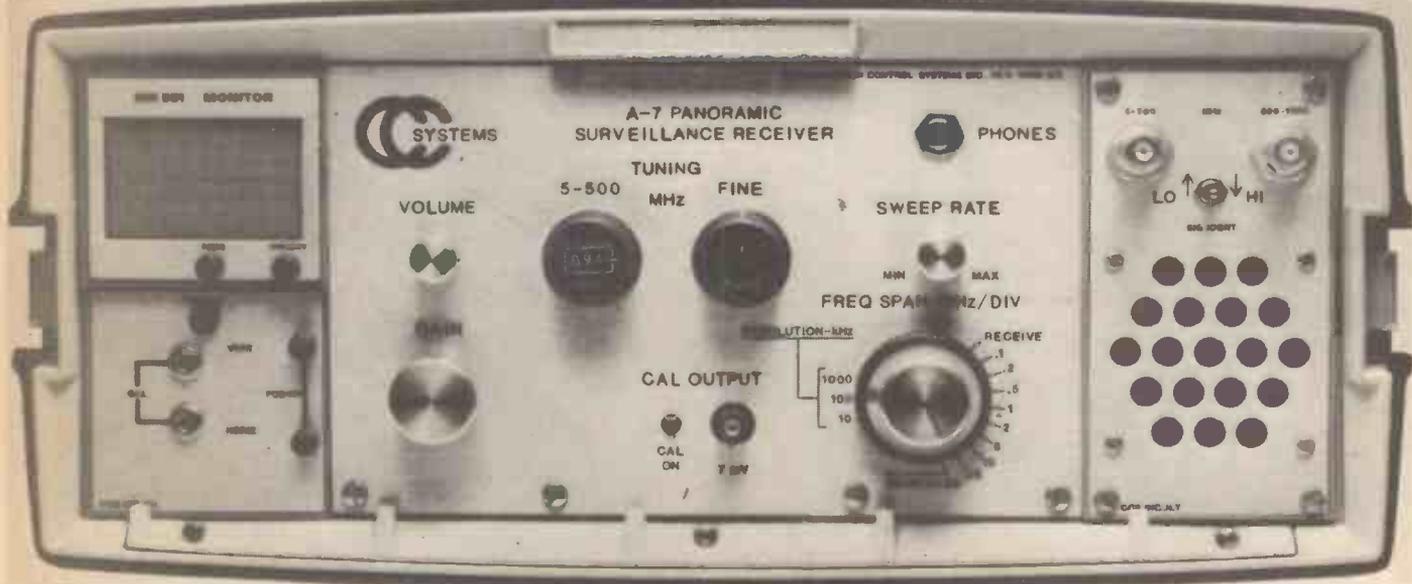
### VIDEO BUGS

With all the improvements in IC technology it's not surprising that video cameras can now be reduced to the size of a five pence piece. Indeed the latest CCD (Charged Coupled Device) cameras, with a couple of ancillary IC and a simple transmitter circuit, can now fit comfortably inside a matchbox. The lens is usually the single largest component! We are led to believe that these cameras operate in extremely low light conditions and quite conceivably in colour. Although we haven't actually seen a system that small, it is clear from our research that you can buy over the counter a 'Video Bug'



# Electronic Espionage

complete with camera, monitor and microwave link for 'remote applications' . . . .

## **SPEAK THE TRUTH**

Latest gadget from across the big pond has the sinister title of a Voice Stress Analyser. Basically this is a device that was developed during the Vietnam War by the Americans to 'humanely' interrogate prisoners. It works by detecting so called 'microtremors' in the voice that are said to occur when the subject is under stress. It remained pretty much a curiosity for several years until some bright spark brought the size of all the gubbins down to IC level. Now you can freely buy (in the States) VSAs that slip into suitcases, the publicity blurb proudly claims that . . . it is ideal for assessing the integrity of prospective employees . . . . The implications are quite clear, conventional skin resistance type lie detector (polygraphs) work mainly on variations of skin resistance brought about by sweating (stress). The VSA has no physical connections to the subject, and because it only requires an easily hidden microphone to use, it is easily hidden. Not only can a conversation be analysed 'live' it is also possible to tape the conversation and study it later. The latest type of Voice Stress Analyser even works over the telephone, presumably you can bug someone via your Infinity Transmitter and at the same time tell whether they are telling the truth or not. . . .

## **DE-BUG YOURSELF**

Now as promised we present the Hobby Electronics guide to anti-bugging procedures. Firstly we shall look for RF bugs, assuming that you are dealing with a run-of-the-mill type spy it's a fair bet that any RF bug will be an FM VHF type. Arm yourself with an FM receiver and set it up in the middle of the room. Turn the volume full up and scan up and down the band. Because of the presence of broadcast stations in the middle portion of the band any bug will be either at the lower end or the



*Portable Voice Stress Analyser capable of working over the telephone. The results can be displayed either as a two digit display or a hard copy on the integral printer.*

*A larger device, this has an IC doing most of the work, it will fit neatly inside a telephone.*



*A watch bug, the aerial is inside the strap, it can pick up a conversation 20 to 30 feet away and transmit it for up to a mile and a half.*



# Electronic Espionage

upper end, they would be very stupid to tune it in the police band!

Listen for a distinct 'dead' spot, if the room is quiet you'll hear the background noise. Having located a possible carrier walk round the room whistling, this sounds a bit daft but this should help you set up a feedback loop. If the radio suddenly starts oscillating turn the volume down and try to find out in which direction the oscillations get louder. Once you have narrowed it down you should be able to find it with a careful visual examination. The two main types of bug likely to be encountered are the disguised bug, one that has been placed inside an inconspicuous looking object, look at anything that may be new on your desk, a stapler for instance or even the phone. The second type of bug is usually hidden in a place that would not normally be examined, the underside of desks, air conditioning vents, inside the cushion of chairs, behind polystyrene tiling etc.

If you're clear of FM bugs (that doesn't include bugs operating on other frequencies though, you'll need a specialised receiver for that), you should now look at the telephone as a potential source of trouble. The best way to protect yourself against infinity transmitters is to have all your calls routed through a switchboard, direct lines are out. Have you had a visit from any phone engineers lately? If you have then it's a simple matter to check up with the phone company to check credentials. Taking the phone apart to look for bugs is not advisable. Apart from the person who placed the bug knowing straight away that the device has been discovered (you may wish to feed them "duff" information). The Post Office take a pretty dim view of anyone mucking about with their equipment. They are probably the best people to investigate, or you could get in touch with one of the many

firms that now offer a comprehensive de-bugging service. That goes for taps too (unless it is the authorities placing a legitimate tap on your phone in which case they probably wouldn't tell you anyway).

Laser bounce is a bit more tricky to counter, you could go to the expense of fitting low reflectivity glass and double glazing or 'deadening' the glass with a thin film of plastic sheet. Video bugs will be even harder to trace, the obvious give-away will be the lens, it will have to be quite large (a couple of cm across at least) to be effective and it would have a nearby microphone (not all spys can lip-read). Because of bandwidth problems in transmitting video, the RF will be at a very high frequency, again a specialised receiver will be needed. If the video bug has been hard wired then you must look for tell-tale wires, remember too that a cunning spy could use telephone wire, check it out with the PO. If the building you occupy is relatively new then any bug installed at the building stage could be almost impossible to detect, the only answer here is to build a room within a room, this can be used when discussing especially sensitive matters. The Russians apparently do this as a matter of course in all their foreign embassies. If after all these precautions you are still troubled by bugs then the only people who can help you are Rentokill.

HE

**We would like to make it clear that 'Counterspy' DO NOT sell bugging devices. However, if you want to see what is available on the 'anti-bugging' market you could do worse than pay them a visit.**

The author would like to thank 'Jo Ann O'Neil and the staff of 'Counterspy' (62 South Audley St, London, W1) for their help in preparing this article.




*A wide band surveillance receiver. This portable device will bleep when the probe is brought near a bug.*
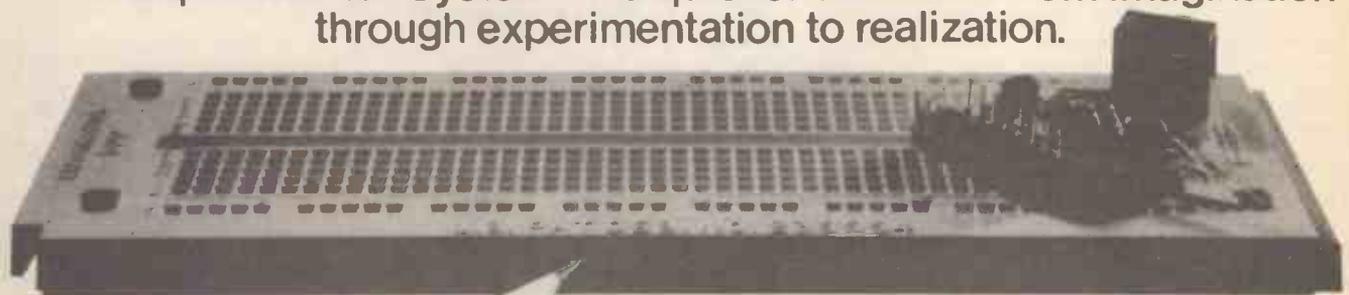
# You can't beat The System.

See us on Stand 161  
at SCOTELEX


The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.



Experimentor Scratchboard™ workpads.

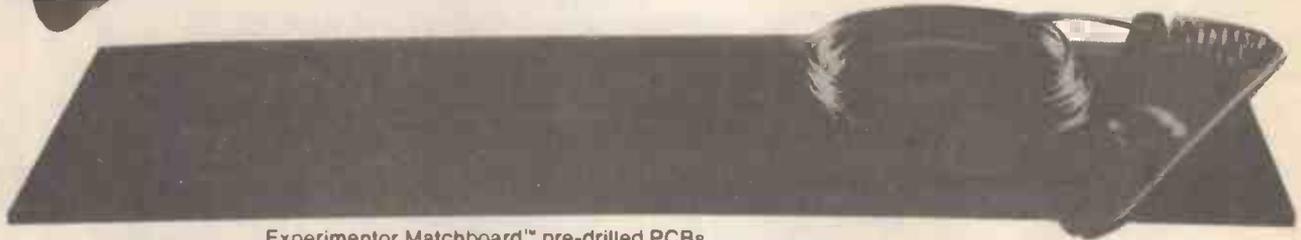

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.32.

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

<b>1.</b> EXP-300PC, which includes one item A Matchboard pre-drilled PCB. <b>£1.32</b>	<b>2.</b> EXP-302, which includes three items Three 50-sheet Scratchboard workpads <b>£1.68</b>	<b>3.</b> EXP-303, which includes three items: Two Matchboards and an EXP-300 solderless-breadboard. <b>£8.60</b>	<b>4.</b> EXP-304, which includes four items Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad. <b>£9.30</b>
---	---	--	---

CONTINENTAL SPECIALTIES CORPORATION



**C.S.C. (UK) Limited, Dept. 14W**  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex. CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477.

CONTINENTAL SPECIALTIES CORPORATION. DEPT. 14W

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

Name \_\_\_\_\_

Address \_\_\_\_\_

Inc P&P and 15% VAT

1.EXP 300PC <b>£2.38</b>	Qty. Reqd.	2. EXP 302 <b>£2.79</b>	Qty. Reqd.
3. EXP 303 <b>£11.04</b>	Qty. Reqd.	4. EXP 304 <b>£11.85</b>	Qty. Reqd.

FREE Catalogue tick box

I enclose cheque/ PO for

£ \_\_\_\_\_

Phone your order with Access, Barclaycard or American Express

Card No. \_\_\_\_\_ Expiry date \_\_\_\_\_

# MITRAD

MITRAD

QUARTZ L.C.D.s AT THEIR BEST

MITRAD

## GENT'S MELODY ALARM CHRONO DUAL TIME

This watch is super slim. Only 7mm thick, but has 5 independent working modes. (1) Normal watch. Hours, Mins., Secs., A.M./P.M. and mode square indication. The weekday can be set in any of three different languages, French, English and German.

(2) Countdown Alarm: Presetable to 24 hours, with the musical tune playing for 1 minute. (3) Ordinary alarm which can be set within a 24-hour period and lasting for 60 seconds.

(2) Dual timing facilities.

(4) Chronograph: This runs to a 1/100s. Freeze and split and lap mode facilities are standard.

This watch is finished in 3 micron gold and comes with a closed strap.

Back Light.



**SPECIALY PRICED AT £14.95**

## ZEON DIGITAL ANALOGUE ALARM

★ EXCLUSIVE ★

We are proud to be able to offer you this scoop purchase. One of the finest pieces of modern technology.

The analogue section can be set as a conventional hand watch and is totally independent of the L.C.D. section.

The digital part of the watch has the following functions:

1. Constant display of Hours, Mins. and Seconds.
2. Optional Display of Date, Month and Weekday.
3. A unique alarm system, which can be set to any time within 24 hours, and is actuated for a full 40 seconds. A five-minute snooze is also available.

The watch is finished off with a Backlight and an infinitely adjustable stainless-steel strap.

**BUY NOW  
AT £34.95**



## GENT'S CHRONOGRAPH SOLAR ALARM

The slimmest Chrono Solar Alarm in the World. Only 7mm thick.

This watch has a genuine solar panel. You can take the battery out and the watch will still function as normal. Battery hatch. Mineral glass.

Constant display of Hours, Mins. and Secs. with Date Flag. Optional display of Hours, Mins. and Date.

The alarm can be set to any time within a 24-hour period and is actuated for a full 60 seconds.

The chrono runs to a 1/10th Sec. with a maximum capacity of 24 hours. Lap Time and Freeze Facilities are available.

Dual timing facilities are readily available.

Back Light. Fully adjustable stainless-steel strap.

This watch is available in gold or silver.

**OFFERED AT £19.95**



## GENT'S MELODY MULTI-CHIME ALARM CHRONO

Latest technology! Constant display of hours, mins and secs, week-day, date and month with mode and chime indication display. The musical alarm once actuated plays the tune "Oh Suzanna". Two further alarm systems are incorporated in this outstanding watch: (i) 24-hour alarm; (ii) count-down alarm. The watch can be set to chime on every full hour. A 1/100th sec chrono is standard to the watch. Can be switched off. Mineral glass face. The watch also has a battery hatch backlight and infinitely adjustable stainless steel strap.

**VALUE AT £19.95**



MITRAD

THE UNRIVALLED RANGE

MITRAD

We are able yet again to offer you the above watches plus a complete quartz watch range. All at unrivalled prices. Just look at the following points:

- (i) 48-hour despatch guaranteed on both retail and trade orders.
- (ii) Full instructions and 12 month manufacturers guarantee.
- (iii) Our own free back-up service.
- (iv) 10-day full money refund if not completely satisfied.
- (v) Free felt presentation case with each watch.

**M  
I  
T  
R  
A  
D**

★ FULL COLOUR CATALOGUE NOW AVAILABLE ★

Write or phone for your free copy. Trade lists on application.

Earn £££s selling watches to all your friends. P/P per item 85p which includes insurance. Cheques or P.O.s made payable to Mitrad and sent to (Dept. HE1), 58 Windmill Avenue, Kettering, Northants, NN16 8PA.

**Telephone (0536) 522024**

# Clever Dick



**The problem of detecting wood-worm in furniture crops up again this month. We need some help with a bee-detector circuit and a useful mod for the Hobbycom. It's all in CD this month.**

IT LOOKS AS IF THE WORM HAS TURNED, the wood-worm man Cliff Robertson (see CD March) has written to us again.

Dear Dick,

I was pleased to see that my suggestion about wood-worm detection was not entirely a damp squib. It is hardly surprising that Barry Hayton's friend received everything within earshot in his experiment at the church, he was clamping his mike to a very large receiving diaphragm. However, it prompted me to try the idea out on my piano — it has a suspended fret carrying the pedals where I have noticed the wood champings on the carpet. An 1710 Akai recorder was handy, and having fixed a rubber shield over the end of one of the microphones, I applied it to the affected part! There was also the unmistakable, irregular gnawing noise. The fret is now in my workshop soaking in Rentokil, after a suitable execution I will have another listen. If you can ask one of your older friends for the loan of a reel-to-reel tape recorder I will send you the tape.

By the way, Cliff Robertson was a film star, I'm just an ancient monument.

Cliff Robertson,  
Isle Of Wight.

PS. My first contribution to the electronics world was in *Amateur Wireless* magazine No. 14, dated September 9th, 1922. It was signed 'CF' which was a severe blow to my pride but the cheque for 10/6 arrived just the same.

Well, what can we say, times have obviously changed. It transpires that *Amateur Wireless* went out of business soon after your letter was published, an omen for us perhaps? Actually we're willing to take the chance and send you a HE Binder worth £3.8s.6d (about right allowing for inflation).

By the way, what's a reel-to-reel tape recorder?

Is Mr Williams having us on? Read on.

Dear Dick,

I am interested in Beekeeping and have heard of a device for detecting the change of tone of the bees just prior to swarming.

I would be most obliged if you could give me some information about this instrument or give me the address of someone who could help.

Daniel Williams,  
Gwynedd.

Come on you lot, how about some more of those weird and wonderful ideas you keep having!

Back to more down-to-earth matters now with this letter from someone who declined to send us their name. We'll call him Mr X.

Dear CD,

Whilst looking through my local library for electronics books I came across '104 Easy Transistor Projects' by Robert Brown.

The problem is that this book is American, the projects that I wish to build use transistors that I have not been able to find in any of the ads in either HE or ETI. Any suggestions? They are: 2N105, 2N1573 and 2N370. Could you advise me of any substitutes or any shops that stock them. Ace Mag, keep up the good work.

Mr X,  
Edmonton, London.

No sooner said than done. The famous 'Towers International Transistor Selector' to the rescue.

2N105 = AC107N,  
2N1573 = BFY65,  
2N370 = AF124,  
OK?

Now for a reply to the letter from Mr Harrington who had a problem with a nearby radar station interfering with his equipment (electronic that is).

Dear Dick,

As I live in a high-rise block of flats I have the reverse problem to that of Mr Harrington. I find that I am unable to receive transmissions due to the screening effect of the metal reinforcements of the structure.

May I suggest to Mr Harrington that screening might help to stop his interference. This could be made from cooking foil hung on a wooden frame sited between him

and the radar station. It would of course have to be earthed.


Ray Pearce,  
Southampton.

Well, that's one suggestion, how about 'papering' your walls with aluminium foil, it would also help keep your heating bills down.

Rupert Goodwins has a simple modification for the Hobbycom, it goes something like this:

Dear Dick,

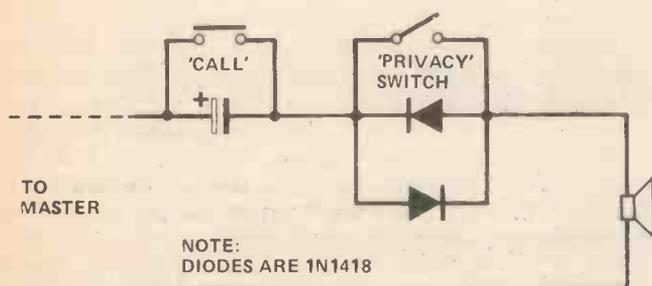A fault on the original Hobbycom is that a sub-station can be operated without it being realised. A simple modification to overcome this problem is as follows.



The diodes (1N1418) allow the call tone or voices from the main station to be heard but the minute voltages from the sub-station speaker are not enough to turn the diodes on.

Rupert Goodwins,  
Southway.

That looks pretty good to us. If anyone else has any modifications or suggestions for our projects then why not let us know about it.

Our last letter this month comes from young Paul Collins over there in Chipping Sodbury.

Dear Dick,

Owing to money problems, would it be possible to adapt the Travelling Alarm Clock in the May issue to a LED Display, possibly with the help of a few ICs?

I don't mind if any of the functions are missing provided the Alarm is still there.

Paul Collins,  
Chipping Sodbury.


Dear Paul,

Sorry mate, the display is part of the module, even if you used another clock IC you would still need a rather large battery to keep the display going, then you really would have money problems. Stick to our design, at least it works.

Thanks for your letters, keep them coming. See you next month.

HE
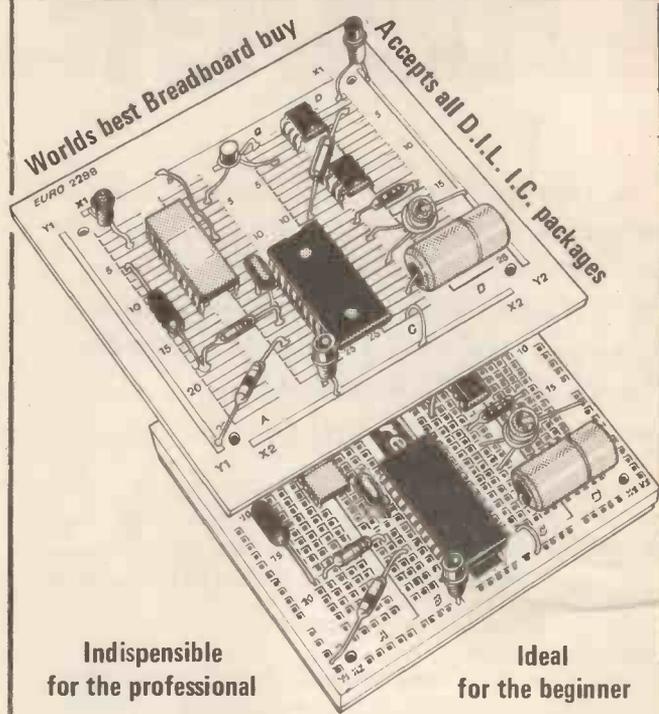
## First the EuroBreadBoard Now the EuroSolderBoard



Indispensible  
for the professional

Ideal  
for the beginner

Design on a EuroBreadBoard — Instal on a EuroSolderBoard

### First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths.

All rows and columns numbered or lettered for exact location indexing (ideal for educational projects)

Long life, low resistance (<10m ohms) nickel silver contacts

£6.20 each or £11.70 for 2

### Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern.

Four 2.5mm dia fixing holes.

£2.00 for set of three ESB's

### And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales,  
Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

### David George Sales, HE7

Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.

Please send me:—

- |                       |          |                       |        |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard      | @ £ 6.20 | <input type="radio"/> |        |
| or 2 EuroBreadBoards  | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick   |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> |        |

All prices are applicable from Jan. 1st 1980 and include VAT and PP but add 15% for overseas orders.

Name .....

Company .....

Address .....

Tel. No .....

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

# Push-Button Volume Control

**A project for the HI-FI buff, experimenter and electronics 'loon'. It's a gadget that lets you control the volume of a stereo amplifier via a single push-button switch; any number of such switches can be wired in parallel and used to control the volume from different parts of the room.**

THIS UNIQUE project enables the conventional ganged volume control of a stereo amplifier to be replaced by a single push-button switch. The switch is coupled to a sophisticated IC which processes the push-duration information and then controls the volume of the amplifier (via an electronic module) in accordance with that information.

If the switch is simply closed for a brief period (60 to 400 mS) the volume merely switches from ON to OFF (Mute) or vice versa, depending on the previous state. A longer switch closure (greater than 400 mS) causes the volume level to cycle slowly from minimum to maximum or vice versa for the duration of the closure, taking about seven seconds to span the full volume range: when the switch is released the prevailing volume level is 'remembered' and maintained indefinitely. At switch off or Mute (a brief switch closure) the chosen volume level is 'stored': this volume is automatically set again at switch-on (another brief switch closure).

## REMOTE CONTROL

A single push-button switch thus enables the volume to be turned on or off or set to any desired level, as

required. In practice, any number of push-button switches can be wired in parallel: these switches can, if desired, be located remotely from the main amplifier, enabling the volume to be remotely controlled from any number of points.

Our push-button volume control project uses three individual circuits, each built up on its own PCB. The main circuit uses five ICs and is used to generate a DC output control voltage via the push-button switch. This output is used to control an electronic stereo 'pot' circuit that is designed around a single IC and built on a small PCB. The third PCB circuit is a LED bargraph voltage-level indicator, which is intended to mount on the front panel of the stereo amplifier to give a visual indication of the amplitude of the DC control voltage.

The two small PCB modules are powered from a 15 volt regulator that is built into the main PCB, which in turn can be powered from any 18 to 30 volt positive supply that is available in the existing stereo amplifier and capable of supplying currents up to about 150 mA. The three modules are intended to be built into an existing stereo amplifier. Figure 1 shows how the three PCBs are interconnected.

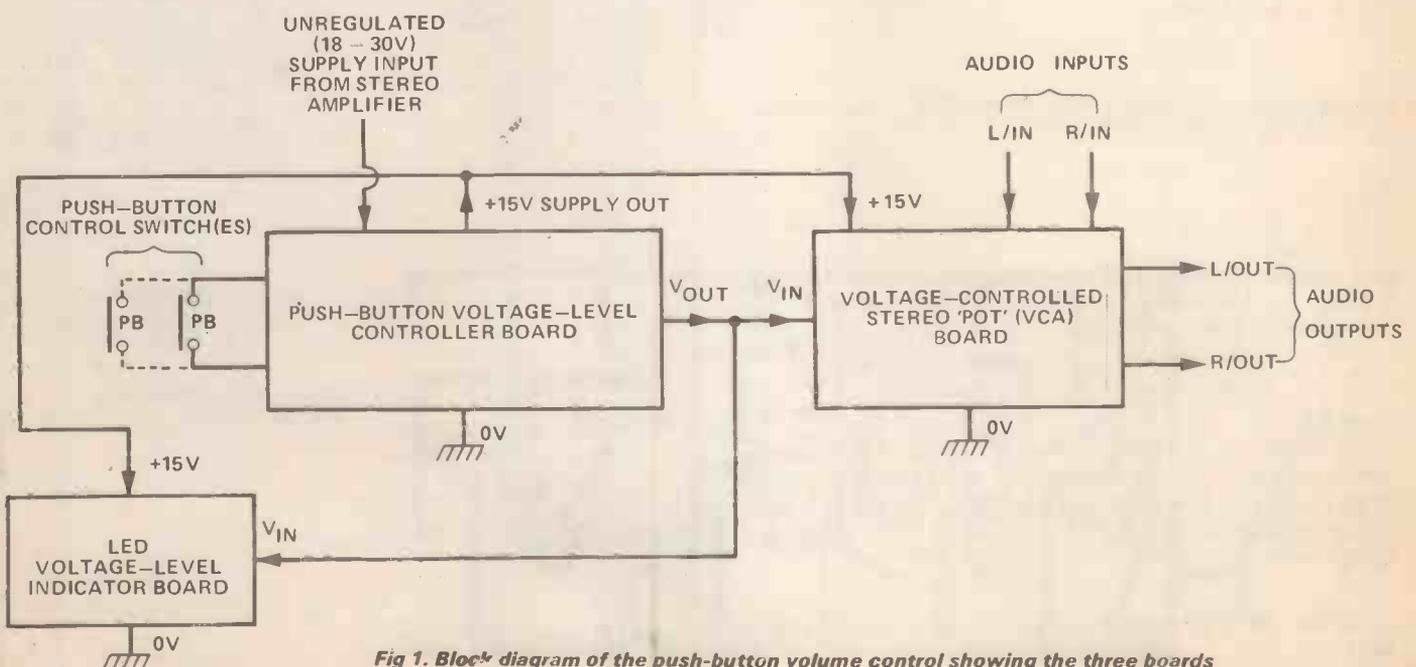


Fig 1. Block diagram of the push-button volume control showing the three boards

## CONSTRUCTION AND TEST

The project is built up on three individual PCBs, each of which can be used as a self-contained project. Construction of the boards should present few problems if the usual care is taken to observe the polarities of all semiconductors and electrolytics and to follow the overlay details. We recommend that all ICs be fitted in suitable sockets.

Start construction by building the large push-button voltage-level controller unit. Note that IC4 is a Siemens S566B touch-dimmer IC and must not be confused with the similarly numbered NE566N voltage controlled oscillator IC. When construction of the unit is complete, connect it to a suitable power supply, fit PB1 in place, connect a voltmeter between ground and the  $V_{out}$  terminal and give the circuit a functional test by operating PB1: it should be possible to ramp the voltage up and down or switch it to zero via PB1, as already described.


Next, build up the LED voltage-level indicator board,

taking special care to test all LEDs before soldering them into place on the PCB. When construction is complete, connect the circuit to the 'push-button' circuit board as shown in Fig 1 and check that an illuminated line of LEDs can be ramped up and down via PB1.



Finally, build up the voltage-controlled stereo 'pot' board and then connect it up as shown in Fig 1. Connect suitable audio input signals to the board and check that the output volumes can be varied or set via PB1, as already described. This completes the construction of the system, which can then be installed in a suitable stereo amplifier.
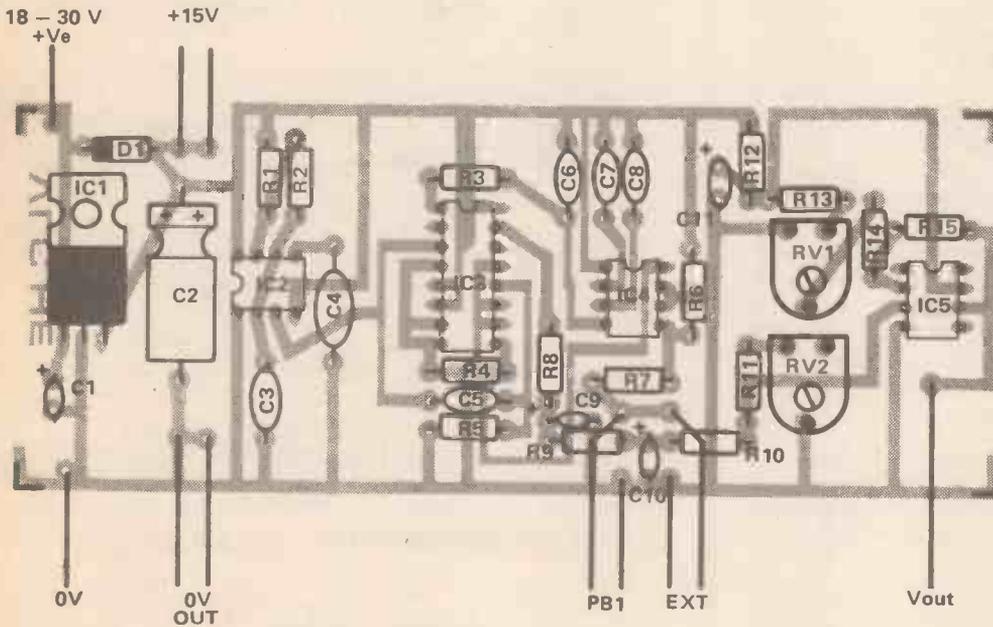
## USING THE SYSTEM

The system is intended to be built into an existing stereo amplifier unit and to be powered from the amplifier's positive supply rail (18 to 30 volts at up to 150 mA). The LED display should be visible on the front panel and placed adjacent to the PB1 control switch. The 'push-



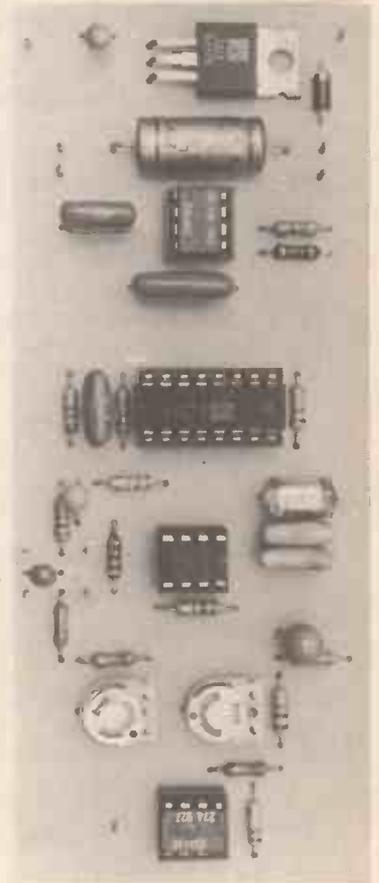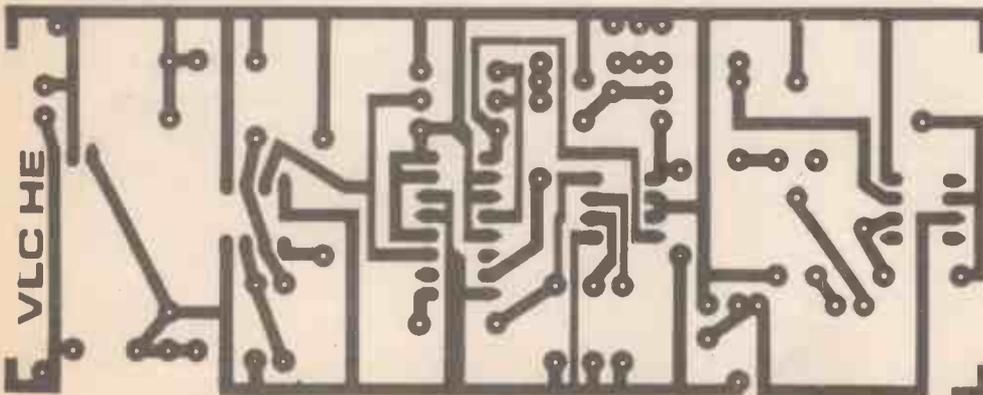Above Component overlay for the voltage level controller board. Below: PCB design



Above: The voltage level controller board

# Push-Button Volume Control

button' board and the stereo 'pot' board can be fitted in any convenient space: the input and output leads of the redundant stereo pot should be connected to the inputs and outputs of the 'pot' board.

It should be noted that the 'push-button' board generates a good deal of RFI: if you intend to use the board in a unit that includes an LW or MW radio tuner, the board may have to be fitted into a screened case.

When installation is complete, give the system a functional check and get used to the action of control button PB1. The two pre-sets on the 'push-button' board can be adjusted in conjunction with PB1 to give limited 'dead' ranges of control at the max and min volume settings of the system and are adjusted to suit individual tastes. The pre-set on the LED voltage-level indicator board should be adjusted so that all LEDs illuminate under the 'maximum control voltage' condition. Finally, you can, if you wish, connect any number of remotely located push-button switches in parallel with PB1, enabling the volume to be remotely controlled. **HE**

## Parts List

### PUSH-BUTTON-CONTROLLER

#### RESISTORS (All 1/4W 5%)

R1	4k7
R2	82k
R3, 4	100k
R5, 8	33k
R6	1M0
R7	47k
R9	10k
R10, 14	56k
R11	68k
R12	270R
R13	15k
R15	150k

#### POTENTIOMETERS

RV1	10k min horiz preset
RV2	47k min horiz preset

#### CAPACITORS

C1	1u0 Tantalum
C2	100u Electrolytic
C3	100n Polyester
C4	150n Polyester
C5	10n Polyester
C6	2n2 Polystyrene
C7, 8	47n Polyester
C9, 10	2u2 Tantalum
C11	22u Tantalum

#### SEMICONDUCTORS

IC1	7815
IC2	ICM7555
IC3	CD4027B
IC4	S566B
IC5	CA3140
D1	1N4001

## Parts List

### STEREO 'POT'

#### RESISTORS (All 1/4W 5%)

R1, 2, 3	22k
R4, 5	47k

#### CAPACITORS

C1, 7	220n Polyester
C2, 5, 6	100n Polyester
C3, 8	33p Polystyrene
C4, 9	2u2 Tantalum




#### INTEGRATED CIRCUIT

IC1	NE570N
-----	--------
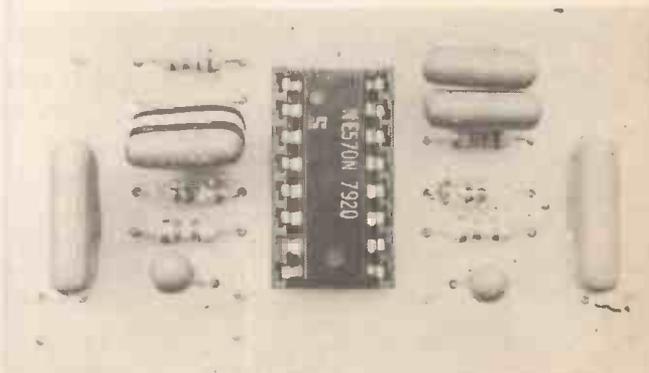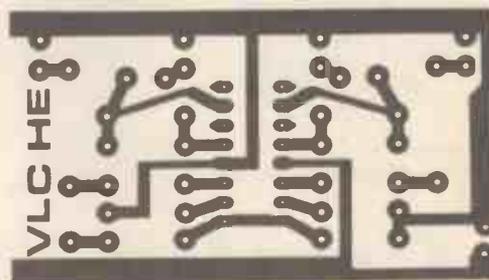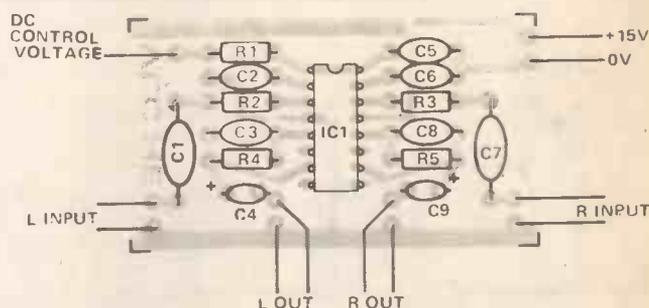
## Buylines

The NE570 is available from Watford Electronics

The S566B is available from Electrovalve.



The voltage-controlled stereo pot board

# How it Works

## THE SYSTEM

This project consists of three independent circuit modules. The largest module is a push-button-activated DC voltage generator, which produces an output that can be varied over the range 0 to 12 volts via a single push-button switch. This voltage is used to control the gain of a dual voltage-controlled amplifier (VCA), which acts as a stereo 'pot'. The third circuit module is a LED bargraph voltage-level indicator, which is intended to give a visual indication of the amplitude of the DC control voltage.

## THE PUSH-BUTTON VOLTAGE LEVEL CONTROLLER


The heart of the push-button voltage-level controller circuit is IC4, a sophisticated Siemens S566B chip that is specifically designed for use in touch-controlled lamp dimmer applications, in which the 50Hz mains is used to provide a 'clock' signal to the IC. In our present application, IC4 is again clocked at 50 Hz, but in this case the clock signal is derived as follows:—

IC2 is a 100 Hz astable multivibrator circuit, designed around a CMOS version of the 555 timer chip. The 100 Hz output of this astable is fed to one half of dual flip-flop IC3, which divides the input frequency by two and produces a 50 Hz output (at pin 1) which is used to clock pin 4 of IC4 via R3-C6. The other half of IC3 is used to process the outputs of IC2 and IC4 and produce a composite output signal at pin 15.



The net effect of the actions of IC2-IC3-IC4 is that a 100 Hz rectangular waveform normally appears at output pin 15 of IC3. The mark/space ratio (and thus the mean voltage) of this waveform can be varied over a wide range or reduced to zero by suitably operating push-button switch PB1, as already described. This output waveform is converted to pure DC via dual low-pass filter network R8-C9-R9-C10 and then further processed by IC5 to enable the final DC output signal to span the full range of zero to 12 volts.

Most of the 'logic' of the circuit is built into IC4, which processes the PB1 push-duration information and then produces an output signal in accordance with that information. If PB1 is held closed, the final DC output voltage of the unit ramps slowly from zero to 12 volts, or vice versa, for the duration of the switch closure: when the switch is released the prevailing voltage level is 'remembered' and maintained indefinitely. The output can be switched alternately between the prevailing level and zero, or vice versa, by momentary closure of PB1.

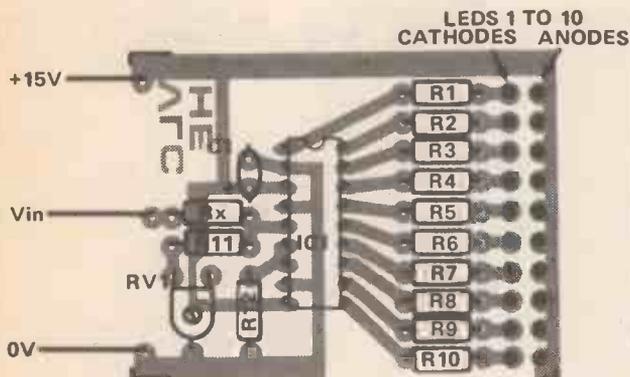The 'push button' circuit is powered from a 15 volt supply derived from the stereo amplifier's supplies via IC1, a 3-terminal voltage regulator IC. The output of IC1 can also be used to power the two remaining modules of the 'volume control' system: the input of IC1 can be fed from any 18 to 30 volt DC supplies that are capable of supplying 150 mA or so.



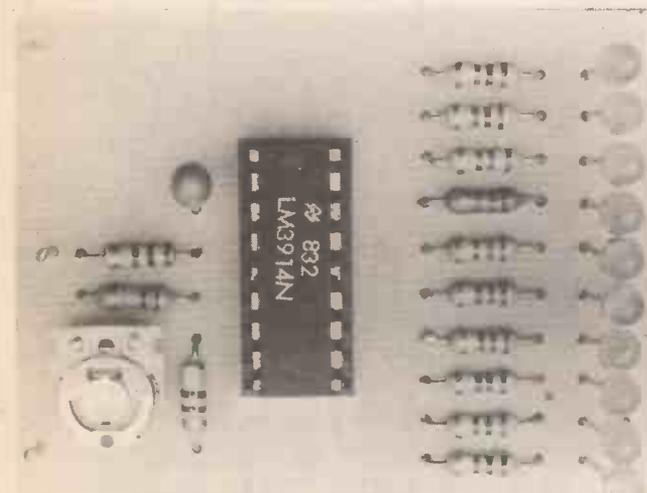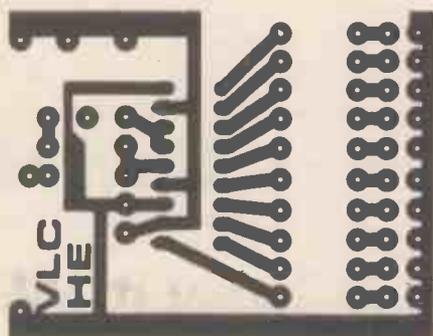Above: Component overlay for the LED bargraph indicator board. Right: PCB design for the LED bargraph indicator. Below: Photo of the indicator board



## Parts List

### DISPLAY BOARD

RESISTORS (All 1/4W 5%)

R1 to 10	1k2
R11	100k
R12	820R
Rx	see text
POTENTIOMETER	
RV1	47k min horiz preset
CAPACITOR	
C1	2u2 Tantalum
INTEGRATED CIRCUIT	
IC1	LM3914
Leds 1 to 10	Any LED

# Push-Button Volume Control

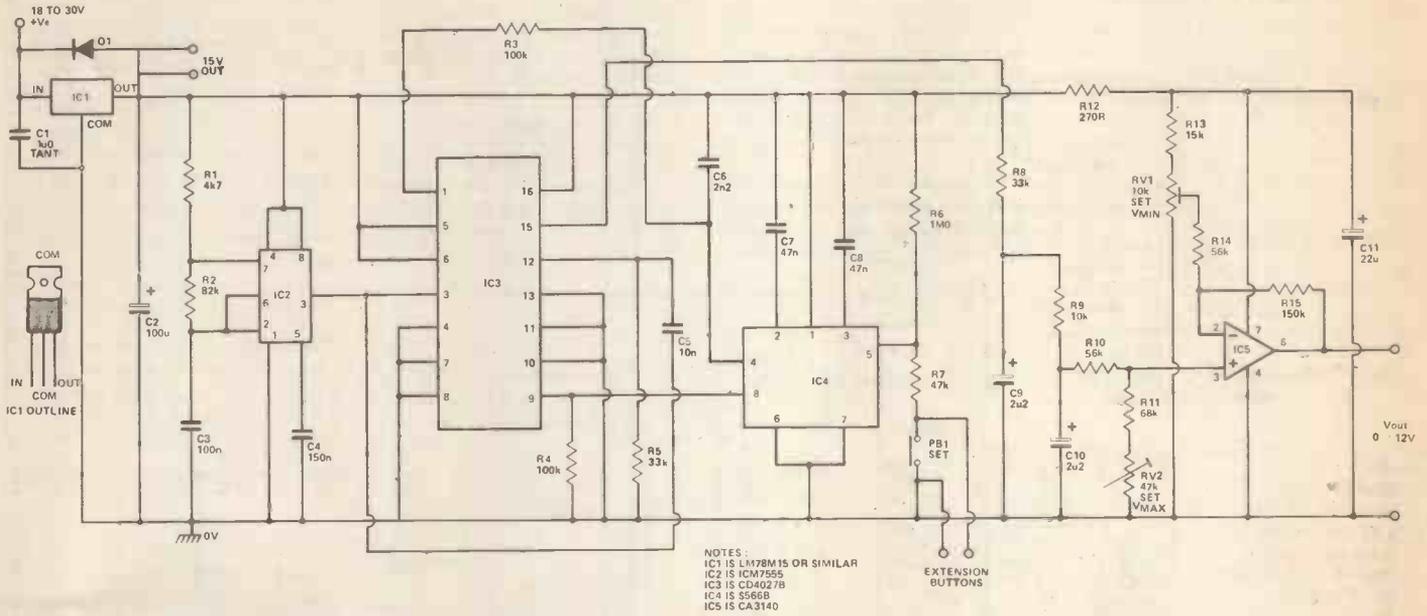


Fig. 2. Circuit diagram of the push-button voltage level controller

## How it Works

### THE VOLTAGE-CONTROLLED STEREO 'POT'

The NE570N IC used in this module can be regarded as a dual voltage-controlled amplifier. Audio signal inputs are fed to pins 3 and 14 and outputs are taken from pins 7 and 10: the amplifier gains can be controlled by DC voltages fed to pins 1 and 16. In our application, both halves of the IC are gain-controlled by the same DC voltage and the 'gain' can be varied from roughly minus 80 dB at zero volts to plus a few dB at 12 volts. The IC produces negligible audio distortion and can thus be used as a voltage-controlled stereo 'pot'. The circuit is powered from a 15 volt supply derived from the main 'push-button' circuit board.

## How it Works

### THE LED BARGRAPH INDICATOR

This module is designed around an LM3914 LED dot/bar voltmeter IC. In our application, the circuit is configured so that all LEDs illuminate ('bar' display) at full-scale indication. The circuit indicates full scale with an input of roughly 11-12 volts with the component values shown. The sensitivity can be varied over a limited range via RV1: the sensitivity can also be changed by using an alternative value of  $R_x$ .

The bargraph circuit is intended to give a visual indication of the output control voltage of the 'push-button' circuit. The circuit draws roughly 100 mA with all LEDs illuminated and is powered from a 15 volt supply derived from the main 'push-button' circuit board.

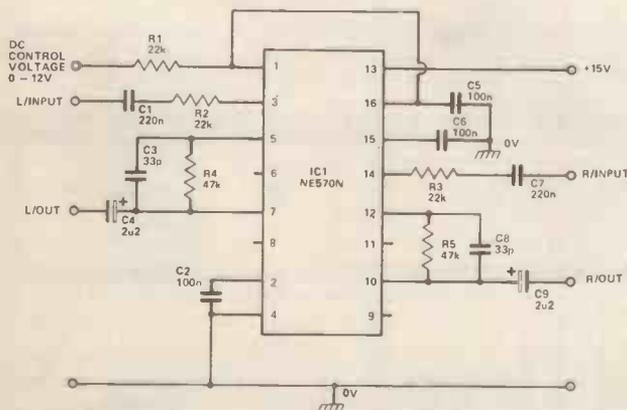


Fig. 3. Circuit diagram of the voltage-controlled stereo pot

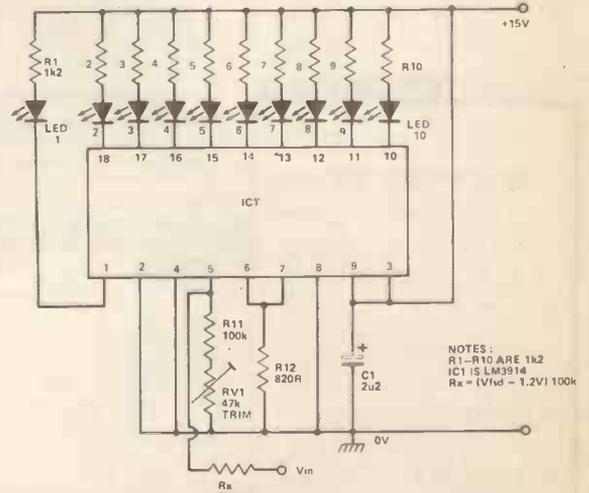


Fig. 4. Circuit diagram of the LED bargraph indicator

# Short Circuit

## TABLE LAMP

This circuit is for a decorative table lamp that produces a slowly changing background colour. The unit has a number of light-bulbs of different colour, that are slowly varied in brightness. However, they are each modulated at a different rate, giving a constantly changing blend of colour.

The circuit is powered from the mains via a stabilised power supply. T1 provides safety isolation and a voltage step down. The mains supply connects to its primary through on/off switch S1, and its centre tapped secondary feeds a straightforward

push-pull smoothing and rectifier network. The resultant DC supply is fed to regulator device IC1, which gives a stabilised 15 volt output. C2 and C3 are decoupling components and should be mounted physically close to IC1.


The remaining circuitry is used to control one lamp. This must be duplicated for each additional lamp, and for best results at least

three lamps should be used. There is no need to duplicate the power supply which can power up to five lamp circuits.

IC2 is a 555 device which is used in the astable mode. This type of circuit normally operates by the timing capacitor (C4) charging up to 2/3 V+ via both timing resistors (R3 and R4). The device is then triggered and discharges the capacitor through

one of the timing resistors (R4) to 1/3 V+, whereupon the device reverts to its original stage and the capacitor starts to charge again. The circuit continuously oscillates in this way. In this case R1 and R2 have been used to raise the two threshold voltages from their normal levels in order to make the unit more efficient. The roughly sawtooth waveform produced across C4 is used to control the lamp by way of a triple Darlington buffer stage.

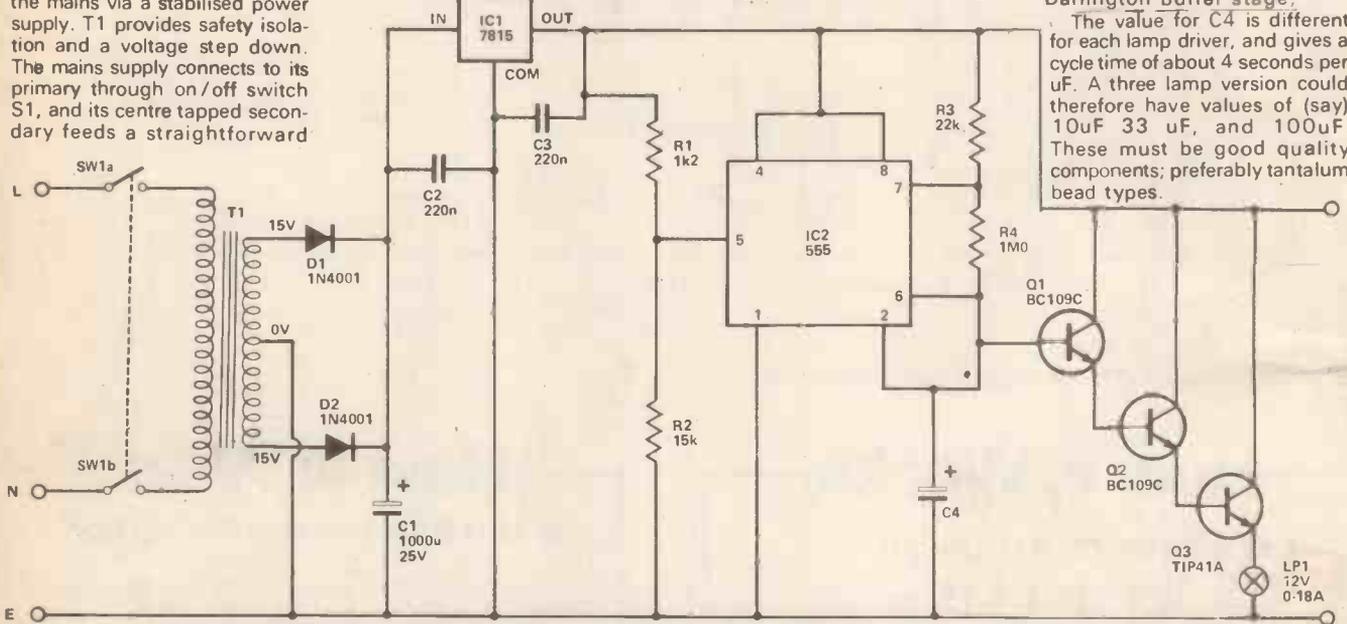The value for C4 is different for each lamp driver, and gives a cycle time of about 4 seconds per uF. A three lamp version could therefore have values of (say) 10uF, 33 uF, and 100uF. These must be good quality components; preferably tantalum bead types.



## DISPLAYS



DL304 Red 0.3" c.c. pin comp. compatible with DL704 **70p**  
DL307 Red 0.3" c.c. pin comp. DL707 **70p**

DL847 Red 0.8" (pin comp. DL174) c.c. **£1.80**  
DL850 Red 0.8" c.c. (pin comp. DL750) **£1.80**  
DL727 Dual 0.5" c.a. Red **£1.50**

## LEDS

LEDS  
0.1" Red **9p**  
0.1" Green **12p**  
0.1" Yellow **12p**  
0.2" Red **9p**  
0.2" Green **12p**  
0.2" Yellow **12p**  
0.2" clips **3p**  
Rectangular Red **18p**  
Rectangular Green **20p**  
Rectangular Yellow **21p**

## O.V.M. THERMOMETER KIT

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). **£20.78**

## MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

**MK1 TEMPERATURE CONTROLLER / THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. **500W £3.20** **1KW £3.50**

**MK2 SOLID STATE RELAY**  
Ideal for switching motors, lights, heaters, etc. from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.60**

**MK3 BAR/DOT DISPLAY**  
Displays an analogue voltage on a linear 10-element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 8-20V supply. **£4.78**

**MK4 PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the TDA1024 Zero voltage switch, this kit may be wired to form a "burst fire" power controller or a "proportional temperature" controller enabling the temperature of an enclosure to be maintained to within 0.5°C. **1.5KW £5.25** **3KW £5.55**

**MK5 MAINS TIMER**  
Based on the ZN1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. **£4.50**

## TOUCH CONTROL LIGHTING KITS

These KITS replace light switches and control up to 300 Watts of lighting. No rewiring, fit plaster depth boxes, insulated touchplates. Easy to follow instructions.

**TD300K TOUCHDIMMER**. Single touchplate with alternate action. Brief touch switches lamp on and off, longer touch dims or brightens lamps. Neon lamp helps find the switch in the dark. **£6.50**

**TDE/K Extension Kit for TD300K for 2-way switching, etc.** **£1.80**

**TSD300K TOUCHSWITCH & DIMMER**. Single touchplate, small knob controls brightness. **£6.80**

**TSA300K TIME DELAY TOUCHSWITCH**. Turns off after preset delay (2 secs. to 3½ mins.) **£4.30**

**LD300K Conventional Lightdimmer** **£2.90**

## INTEGRATED CIRCUITS

555 Timer **21p**  
741 Op. Amp. **19p**  
AY-51224 Clock **£2.60**  
AY-51230/2 Clock/Timer **£4.50**  
AY-3-1270 Thermometer **£6.20**  
ICL7106 DVM (LCD drive) **£7.00**  
LM3377 Dual 2 W Amp **£1.45**  
LM3795 Dual 6W Amp **£3.50**  
LM380 2W Audio Amp **80p**  
LM382 Dual/low noise Preamp **£1.00**  
LM386 250mW low voltage Amp **75p**  
LM1830 Fluid Level Detector **£1.50**  
LM2907 V Converter (8 pin) **£1.40**  
LM2917 V Converter (14 pin) **£1.80**  
LM3909 LED Flasher/Oscillator **85p**  
LM3911 Thermometer **£1.20**  
LM3914 Dot/Bar Driver **£2.10**  
MM74C911 4 digit display controller **£6.50**  
MM74C915 7 segment-BCD converter **96p**  
MM74C926 4 digit counter with 7 seg.o/p. **£4.50**  
S5668 Touchdimmer **£2.50**  
S9263 Touchswitch 16-way **£4.85**

## DO MAGAZINE REMOTE CONTROL PROJECTS MAKE YOU SEE INFRA RED?

How many times have you considered building a remote control project but were put off by the dozens of ICs, special coils, lenses and other hard to get components, not to mention the need for a well equipped lab. to set the unit up? T.K. ELECTRONICS have changed all that. Three ICs can build a sophisticated system that requires only a capacitor and resistor to set the clock frequency (which can drift up to 20% without affecting performance). Control radios, Hi-fi (including bass, treble and volume), lighting, toys, garage doors, etc. Still not convinced? Then look at the prices!

LD271 IR Emitting Diode **38p**  
SFH205 Photodiode Detector **95p**  
SL480 IC Pulse Amplifier **£1.40**  
SL490 Keyboard Controlled Encoder/Transmitter **£2.40**

ML922 10-channel Receiver and 3 Analogue Outputs **£4.20**  
ML926 16-channel Receiver (4 Momentary binary outputs) **£1.40**  
ML928 16-channel Receiver (4 Latched binary outputs) **£1.40**

Data sheets (per device) **5p**

These ICs can also be used with ultrasonic and radio links, depending on range, cost and speed of operation. For more details, why not give us a ring — we will be pleased to advise you.

If you do not require a sophisticated multi-channel remote control, we have developed a simple single-channel ON/OFF infra red transmitter and receiver. The transmitter unit comes complete with a hand held box and requires a PP3 (9V) battery. The receiver includes a triac capable of switching up to 500W at 240V a.c. and comprises a preamplifier, bistable latch and a mains power supply, making the unit completely self-contained. The small size of the receiver enables the unit to be "built into" all kinds of equipment from lamps to tape recorders. The minimum range is 20 feet.

ONLY £12.00 (Order as RC500K)

## INTEGRATED CIRCUITS

SN76477 Complex Sound Generator **£2.82**  
TBA800 5W Audio Amp **58p**  
TBA810AS 7W Audio Amp **85p**  
TDA1024 Zero Voltage Switch **£1.20**  
TDA2020 20W Audio Amp **£2.85**  
ZN1034E Timer **£1.80**

All ICs supplied with data sheets  
Data Sheets only 5p each device.

## TRIACS

400V Plastic Case (Texas)

3A	49p	16A	90p
8A	58p	20A	165p
12A	85p	25A	190p
6A with trigger			80p
8A isolated tab			65p
Diac			18p

## SPECIAL OFFERS

orders must be received by 30.6.80

10X8pin sockets	65p	10X555	£1.80
10X14pin sockets	£1.00	10X741	£1.60
10X16pin sockets	£1.15	25X0.2" Red Leds	£1.50
10X18pin sockets	£1.40	ORP12	50p
100X Soldercon pins	40p	2N3055	40p

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION, ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER — CALLERS WELCOME BY APPOINTMENT




**TK Electronics**

(H.E.), 106 STUDLEY GRANGE ROAD  
LONDON W7 2LX. TEL. 01-579 9794



# SPECIAL OFFER

## TEN YEARS OF

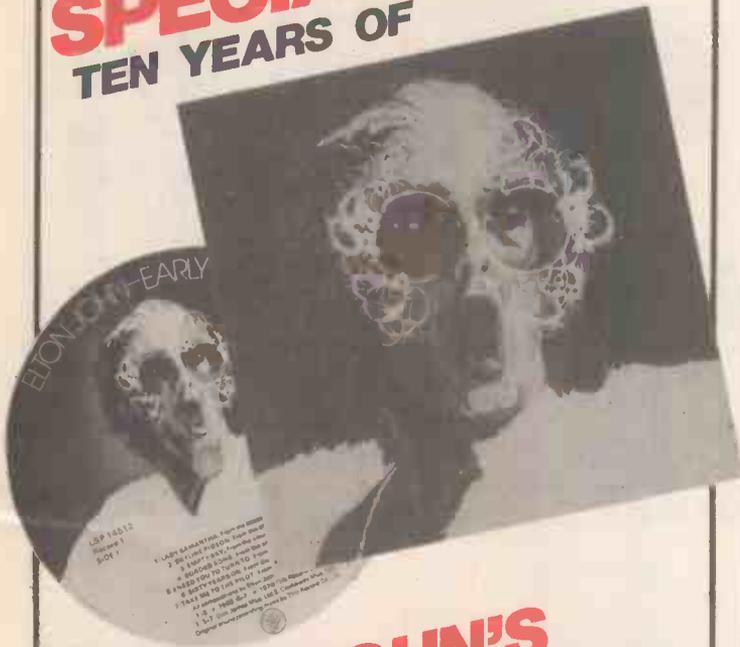

# ELTON JOHN'S GREAT HITS

Yes, 10 years of Elton John's Great Hits in 5 superb albums beautifully boxed and supplied together with a full-sized, full-colour pop art poster. For the Elton fans this is a must!

### EARLY YEARS:

Includes: Lady Samantha: Take me to the Pilot: Country Comfort: Friends.

### ELTON ROCKS:

Includes: The Bitch is Back: Crocodile Rock: Pinball Wizard: Saturday Nights Alright for fighting.

### SINGLES:

Includes: Daniel: Lucy in the Sky with Diamonds: Philadelphia Freedom: Rocket Man.

### MOODS:

Includes: Sweet Painted Lady: Love Song: High Flying: Bird: Blues for my Baby and me.

### CLASSICS:

Includes: We all fall in love sometimes: Curtains: Love lies Bleeding: Captain Fantastic and the Brown Dirt Cowboy.

To obtain your boxed Album complete the coupon below and send it together with your cheque/P.O. made payable to Modmags Ltd. Allow 21 days for despatch.

**£12.50**  
including post,  
packing & V.A.T.

Please send me . . . . . Elton John Albums  
@ £12.50 each incl. post & packaging.  
I enclose my cheque/PO No. . . . .

NAME . . . . .

ADDRESS . . . . .

Send coupon and cheque/PO to:  
MODMAGS LIMITED  
Sales Office (Ref: REC)  
145, Charing Cross Road,  
London WC2H 0EE.

# All these advantages...

- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

## ..in kit form

SPARKRITE X5 is a high performance, top quality inductive discharge electronic ignition system designed for the electronics D.I.Y. world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1-2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built-in static timing light systems function light and security changeover switch. Will work all rev counters.



**Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.**

### THE KIT COMPRISE EVERYTHING NEEDED

Die pressed case, Ready drilled aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

# Sparkrite

HIGH PERFORMANCE  
ELECTRONIC IGNITION

Electronics Design Associates, Dept. HE/7  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 614791

Name \_\_\_\_\_  
Address \_\_\_\_\_

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQ'D.

I enclose cheque/PO's for

X5KIT £16.95

£

Cheque No.

ACCESS OR BARCLAY CARD No.

Send SAE if brochure only required.

**MONEY SAVING BARGAIN  
EX-STOCK FROM US**

**J.V.C. BELT DRIVEN  
TURNTABLE  
WITH STEREO MAGNETIC  
AUDIO TECHNICA  
CARTRIDGE**



**LIST PRICE OVER £50**

J.V.C. Turntable supplied complete with Audio Technica AT10 stereo magnetic cartridge. Belt driven

- \* 'S' shaped tone arm.
- \* Modern design
- \* Full size 12" platter.
- \* Calibrated counter balance weight (0.3 grms).
- \* Anti-skate (bias) device.
- \* Size — 12 3/4" x 15 3/4" (approx)

AT ONLY  
**LIMITED STOCKS £25.99**  
PLUS VAT £3.89 Post £2.50

**GEC HIGH QUALITY STEREO**


**10 + 10 watt AMPLIFIER  
WITH AM/FM STEREO TUNER  
IDEAL FOR THE HOME**

A cancelled export order brings you this offer from the world-famous firm of G.E.C.

AM/FM stereo Tuner Amplifier  
Ready built. Comprising of a tuner/pre-amp. board and separate power supply/power amp. board with wiring diagram.  
Rotary Controls: Tuning, on/off volume, balance, treble, bass Stereo Beacon Indicator.  
Push-button Controls: Mono, Tape, Disc, A.F.C., F.M. (VHF), LW, MW, SW.

Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music.  
Frequency Response: 60Hz-20KHz within ± 3dB.  
Tape Sensitivity: Output — typically 150 mv. Input — 300 mv for rated output.  
Disc Sensitivity: 100 mv (ceramic cartridge)  
Radio: FM (VHF) 87.5MHz-108MHz.  
Long Wave 145KHz-255KHz  
Medium Wave 520KHz-1620KHz  
Short Wave 5.8KHz-16MHz.  
Size: Tuner — 2 1/2in. x 1 1/2in. x 7 1/2in. Power Amp — 2in. x 7 1/2in. x 4 1/2in.

**LOW PRICE OFFER**

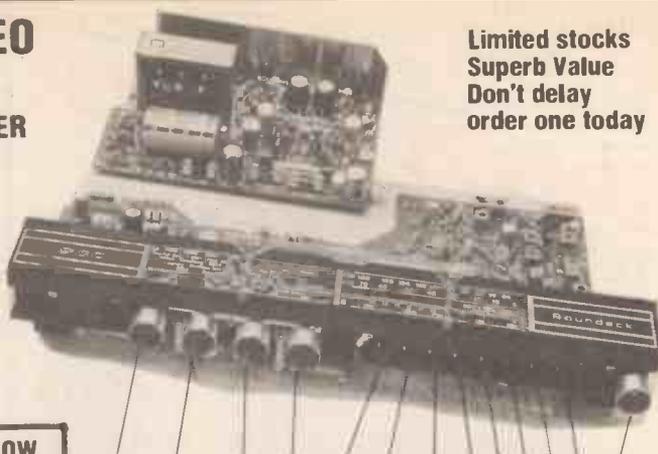

ON/OFF BALANCE, TREBLE, BASS, MONO TAPE Phono AFC FM LW MW SW Tuning. Volume

**Fully Guaranteed Ex-Stock**

**SUITABLE SPEAKERS IN CABINETS PAIR 10 WATTS**

**£19.95** POST £2.50 Pair  
INC. VAT

**ONLY £19.95**  
+ VAT £2.99  
CARRIAGE £2.50



**CAR STEREO CASSETTE MECHANISM made for MOTOROLA**

- \* Front loading 12 volt transistorised
- \* Speed & Voltage control
- \* Ex-equipment — Tested O.K.
- \* Limited stocks
- \* Size
- \* Takes standard C60 cassette

**ONLY £7.50**  
INC. VAT  
POST 80p

PRO M25 Professional capacitor boom-arm microphone by Eagle.  
A graceful 60 cm boom-arm capacitor studio microphone using a cardioid capsule. A high standard of finish for in-vision use and yet robust enough to withstand long periods between maintenance. Supplied complete with 1 red and 1 black windshield and 6 metres of twin screened cable terminating at the microphone and in an XLR connector.  
Impedance: 600 ohms (floating). Response: 20-18,000 Hz. Sensitivity: — 70 dBV.  
Cable: 6 metres two conductor shielded. Connector: XLR 3-11C. Battery type: HP7.

**LIST PRICE £37.40**  
**OUR PRICE £19.95**  
inc VAT  
POST £1.50



**Henry's**  
Phone (01) 723 1008/9  
404 Edgware Road, London W2, England I.E.D.



**Marshall's**

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA  
Industrial Sales: 01-328 1009  
Mail Order: 01-624 8582  
Also retail shops: 325 Edgware Road, London W2  
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow.  
108A Stokes Croft, Bristol.

**CAPACITORS:**  
Mullard Ceramic 63v range ~ 1pF to 10,000pF E. 24 range all at £0.06 each  
Siemens Ceramic 63v B37448/9 .01: .022: .033: .047mF @ £0.06  
.068: .1mF @ £0.08: .22mF @ £0.11  
CSF High Voltage Ceramic Discs Prices £0.07 to £0.18 Range 100pF to 10,000pF Voltage range up to 6Kv. See catalogue for details.  
Comprehensive range Siemens Layer Polyester Caps: .001 to 3.3mF Prices £0.07 to £0.63. See catalogue for details.  
Large range of Mullard/Siemens Electrolytic Axial/Radial Capacitance values 1.0mF to 10,000mF Voltage ranges 25v: 40v: 63v: 100v: Prices and types as catalogue Also Mullard C280; Siemens B32231/4 and B32110. All prices net + VAT and postage/packaging.

**BOXES & CASES**  
See catalogue for full range. Aluminium boxes 13 sizes. Rexine Covered boxes 7 sizes. **NEW RANGE TMEC CASES** Send S.A.E. for details & types Price range, £14.04 to £ 17.00  
**ABS PLASTIC BOXES**  
3" x 2 1/4" x 1 3/8" Prices as catalogue  
3 3/4" x 2 3/4" x 1 3/8"  
4 1/2" x 3 3/4" x 1 1/2"  
8" x 4 3/4" x 3"  
**BAZELLI INSTRUMENT CASES** 5 sizes.  
Miscellaneous hardware including Vero Board: Superstrips: Vero Breadboard. Vero boxes (see catalogue for full range).  
Card Frames: Fliptop boxes: etc etc.



**TOOLS BAHCO**  
Side Cutter with Bezel.  
Side Cutter without Bezel.  
End Cutter without Bezel.  
Vero Metal Shears.  
Other items as catalogue.

**1980 CATALOGUE**  
U.K.: 65p post paid  
Europe 85p post paid  
Rest of World £1.25 post paid  
Mail order: 01-624 8582



**TTL see catalogue for full range**

SN7400N	EO.14	SN7491AN	EO.54
SN7401N	EO.14	SN7492N	EO.31
SN7402N	EO.14	SN7493N	EO.32
SN7403N	EO.14	SN7494N	EO.80
SN7404N	EO.14	SN7495N	EO.55
SN7405N	EO.15	SN7496N	EO.34
SN7406N	EO.54	SN7497N	EO.80
SN7407N	EO.26	SN74100N	EO.10
SN7408N	EO.15	SN74107N	EO.21
SN7409N	EO.55	SN74108N	EO.76
SN7410	EO.15	SN74119N	EO.20
SN7411N	EO.15	SN74121N	EO.25
SN7412N	EO.20	SN74122N	EO.48
SN7413N	EO.28	SN74123N	EO.42
SN7414N	EO.47	SN74124N	EO.53
SN7416N	EO.22	SN74125N	EO.40
SN7417N	EO.22	SN74141N	EO.50
SN7420N	EO.15	SN74145N	EO.64
SN7423N	EO.18	SN74148N	EO.05
SN7425N	EO.19	SN74150N	EO.79
SN7426N	EO.19	SN74151N	EO.55
SN7427N	EO.19	SN74153N	EO.55
SN7430N	EO.15	SN74154N	EO.90
SN7432N	EO.17	SN74155N	EO.60
SN7437N	EO.21	SN74157N	EO.59
SN7438N	EO.21	SN74160AN	EO.70
SN7440N	EO.15	SN74161AN	EO.70
SN7441AN	EO.52	SN74162AN	EO.70
SN7442N	EO.40	SN74163AN	EO.70
SN7445N	EO.66	SN74164AN	EO.80
SN7446AN	EO.48	SN74165N	EO.80
SN7447AN	EO.48	SN74167N	EO.20
SN7448N	EO.45	SN74174N	EO.80
SN7450N	EO.15	SN74175N	EO.63
SN7451N	EO.15	SN74176N	EO.74
SN7453N	EO.15	SN74177N	EO.73
SN7454N	EO.15	SN74180N	EO.70
SN7460N	EO.15	SN74181N	EO.65
SN7470N	EO.26	SN74182N	EO.83
SN7472N	EO.24	SN74184N	EO.29
SN7475N	EO.25	SN74185AN	EO.10
SN7474N	EO.25	SN74186N	EO.35
SN7475N	EO.31	SN74188AN	EO.84
SN7476N	EO.26	SN74189N	EO.26
SN7480N	EO.39	SN74190N	EO.74
SN7481N	EO.71	SN74191N	EO.79
SN7482N	EO.65	SN74192N	EO.79
SN7483N	EO.60	SN74193N	EO.79
SN7484N	EO.95	SN74196N	EO.74
SN7485N	EO.70	SN74197N	EO.74
SN7486N	EO.25	SN74198N	EO.09
SN7489N	EO.56	SN74199N	EO.09
SN7490AN	EO.33		

**SOLDERING EQUIPMENT**  
**IRONS-ANTEX**  
15 watt C15 £3.95  
15 watt CCN £4.20  
17 watt CX17 £4.20  
25 watt X25 £4.20  
Stand £1.50  
**DESOLDERING TOOL**  
Solder £6.50

**SINCLAIR INSTRUMENTS**  
Digital Multimeter  
" " PDM35 £ 34.50  
" " DM235 £ 52.50  
" " DM350 £ 72.50  
" " DM450 £ 99.00  
Digital Frequency Meter PFM200 £ 49.80  
Low Power Oscilloscope SC110 £139.00

**CRIMSON ELEKTRIK HI FI MODULES**  
CE608 Power Amp £18.26  
CE1004 " " £21.30  
CE1008 " " £23.91  
CE1704 " " £30.43  
CE1708 " " £30.43  
CPS1 Power Unit £16.96  
CPS3 " " £20.43  
CPS6 " " £26.09  
CPR1 Pre Amp £29.57  
CPR1S Pre Amp £38.70  
All prices + VAT + postage/packaging



# Short Circuit

## VOICE OPERATED FADER

The purpose of a voice operated fader is to mix two signals, and to automatically fade out one of these to some predetermined level when a signal is present in the other channel. Normally the control signal is a commentary of some kind and the controlled signal is music. Units of this type are used in discos, and in similar applications.

In this circuit, with no control


input signal, the controlled signal is fed via C5 and R8 to one input of a conventional two input mixer which is based on IC1.

Some of the control signal is applied to the other input of the mixer, and the rest is fed to a common emitter amplifier based on Q1. The output of this is fed to a rectifier and smoothing circuit comprised of C3, R4, D1, D2, R5 and C4. Normally Q2 is cut off,

and R6 strongly reverse biases Jfet Q3. Q3 therefore has a very high drain to source resistance (typically about 1,000 megohms), and has no significant effect on the circuit. However, in the presence of a suitable control input signal, the negative bias produced by the smoothing and rectifier circuit switches Q2 hard on, and eliminates the reverse bias on Q3. The drain to source resistance of Q3 then falls to only about one

hundred ohms or so, and causes greatly increased losses through R8. Thus the required automatic fade out action is obtained. R7 can be adjusted to give any level of fade out from about -6dB. to about -60dB.

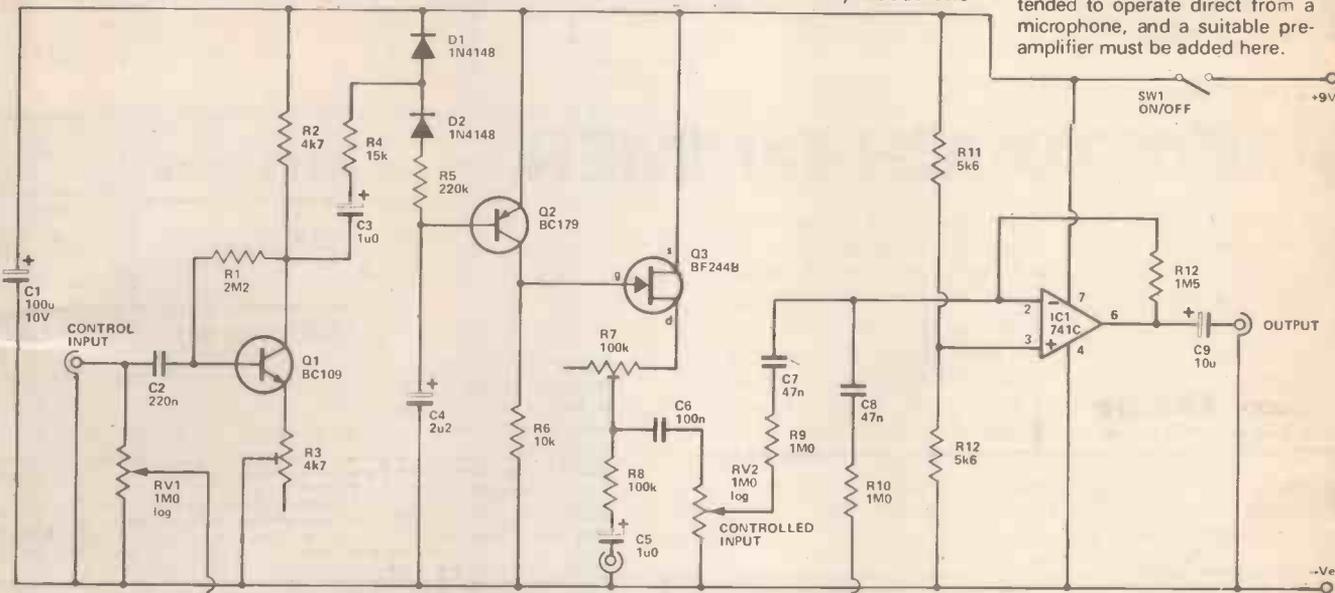R3 controls the voltage gain provided by Q1, and in practice is adjusted for the lowest gain (highest resistance) that gives reliable operation of the unit. Note that this input is not intended to operate direct from a microphone, and a suitable pre-amplifier must be added here.



### FM/AM STEREO TUNER AMPLIFIER CHASSIS

Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together.

**Note** Circuit diagram and inter-connecting wiring diagrams supplied.  
**Rotary Controls** Tuning, volume, balance, treble and bass.

**Push Button Controls** Mono, Tape, Disc, A.F.C., FM (VHF), LW, MW, SW.

**Power Output** 7 watts RMS per channel into 8ohms (10 watts music).

**Tape Sensitivity** output typically 150mv. Input 300mv for rated output.

**Disc Sensitivity** 100mv (ceramic cartridge).

### GEC QUALITY




#### 240v/50Hz Operation

**Stereo Beacon Indicator LED** or bulb.  
**Size** Tuner - 2 3/4" x 15" x 7 1/2" approx. Power amp. 2" x 7 1/2" x 4 1/2" approx.

**Price** £21.50 + £2.50 Postage and Packing.

### J.V.C. TURNTABLE

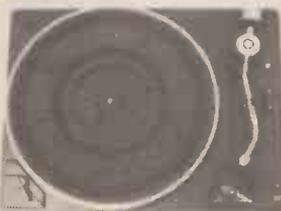

★ 240v/50Hz Operation

J.V.C. Turntable supplied complete with an Audio Technica AT10 stereo magnetic cartridge.

- ★ 'S' shaped tone arm.
  - ★ Belt driven.
  - ★ Full size 12" platter.
  - ★ Precision calibrated counter balance weight (0.3 grms).
  - ★ Anti-skate (bias) device. Nylon thread weight.
  - ★ Cut-out template supplied.
- Size** - 12 3/4" x 15 3/4" (approx.).  
**Price** £29.00 + £2.50 Postage and Packing.

## B.K. ELECTRONICS

(Dept. HE), 37 Whitehouse Meadows  
Eastwood, Leigh-on-Sea  
Essex SS9 5TY


★ S.A.E. for equipment list etc. ★ Official orders welcome. ★ All prices include V.A.T. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam.

# Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

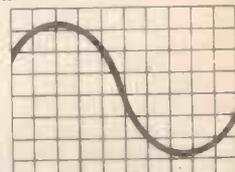Learn the technology of the future today in your own home.



### TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name \_\_\_\_\_

Address \_\_\_\_\_

Block Caps. Please

Post now, without obligation to:

HE7  
**British National Radio & Electronics School.**

**FREE BROCHURES**

No previous knowledge is necessary.  
- Just clip the coupon for a brochure

P.O. Box 156, Jersey, Channel Isles

# Kit Reviews

*Pete Howells builds a couple of kits from Tandy*

## TANDY TOUCH DIMMER

DIMMER SWITCHES have been around for quite some time now and are easily available in practically all electrical stores, retailing for around £5 each. This kit from Tandy, however, adds that extra bit of novelty that makes it worth a second glance, in that it can be controlled by a touch sensitive plate rather than by the conventional potentiometer. The idea here is that short touch to the sensor will turn a light on or off, and that a longer, sustained touch will put the light through a dim/bright cycle until the touch is removed; it will then maintain this intensity until turned off. One more thing — when it's turned on again the intensity will be the same as when it was turned off, hence the "built-in memory" designation.



The kit itself consists of the circuit board, drilled, printed with component locations and laquered, the components and the instructions. Now, the instructions are a real gem. You may have thought that the literacy of contributors in this magazine left something to be desired, but please wait until you read these instructions: "This IC is a C-MOS IC, and is very sensible by static charges . . . use a soldering iron with small currency." That bit's easy. Try figuring out how it works. Oddly the English translation takes up about two thirds of the space that those in other languages use, and one can't help wondering about what's been left out. Perhaps the translator couldn't cope with some of the words and just didn't bother. Mind you, he (or she) didn't cope too well with what was left in. Considering how sensible a CMOS IC is, it would have been sensible to include an IC socket, and although there isn't one in the kit it is worth forking out a few pence on one yourself.

The components can be thrown together on the PCB without any problems, and although the instructions don't say anything about the orientation of polarised components this could be worked out from the markings on the board by anyone familiar with electronic components. A beginner might well end up in trouble, though.

Again the instructions fall down when it comes to telling you what to do with the thing once you've built it. Bear in mind that you're playing with mains currents and that a moment's thought before doing anything rash is in order. No mention is made of safety considerations and the wiring is described in a not too copiously labeled diagram. If you're going to fix it into a light switch plate you must make sure that none of the components foul the metal casing at any point.

Eventually there comes a time when everything is in place and the power is turned on. You put your finger to

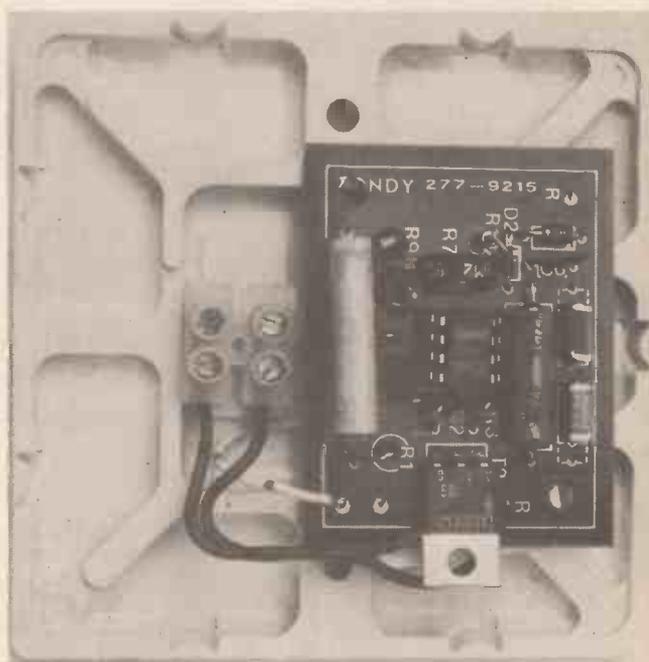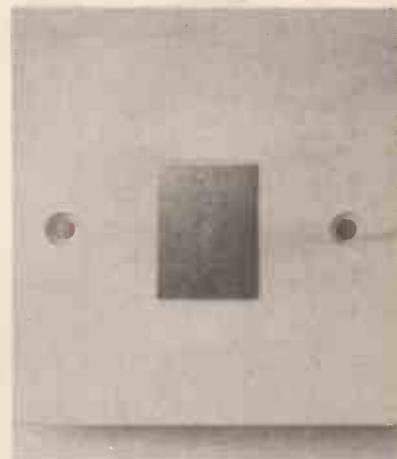
**Right: The dimmer installed on the back of a light switch plate. Sticky pads are a wonderful thing. Below: And from the front — the sensor plate is available from Maplin or Watford.**



the touch plate and — nothing happens. This was very peculiar because two days later it worked perfectly, though at the time no amount of coaxing could make the device sensitive enough to respond to the touch sensor unless it was directly earthed. Since then there have been no problems, and no one has been able to explain why it didn't work at first. Radio interference is very low even with no suppression added. A choke and a capacitor are suggested, though not supplied with the kit; according to the instructions, "This work is depressing parasites."

To make a working unit a couple of extra bits are needed; a connector block (Mains circuits shouldn't be soldered direct into this board), a touch plate (quite neat ones can be bought from most components suppliers) and some form of mount for the inhole gubbins — if it's going to control a room light, a blanking plate (see photo), which is ideal for the job, is quite cheap to buy. Most highly recommended is an eight pin DIL socket for the "sensible" CMOS IC. The kit itself costs £9.95 and with the other bits the total cost will come to something like £11.

## TANDY VU METER

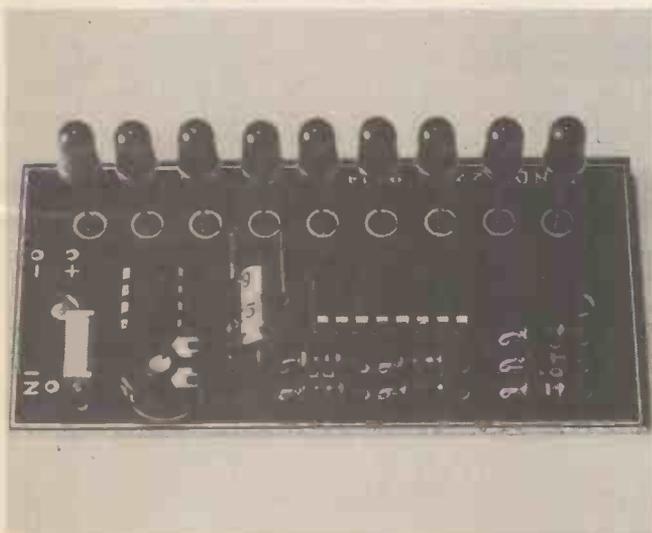

**Above: The completed board — four wires to connect (12V supply and signal). Below: A picture of Pete's Revox which was used to test the meter.**

THE MAJOR PROBLEM when recording audio signals on magnetic tape has always been the difficulty of treading the narrow path between the level of noise inherent in the medium and the level at which the recorded signal saturates the tape. A similar problem arises when running audio amplifiers towards the limits of their performance, when the disturbing phenomenon of clipping occurs. Virtually every tape recorder available today is equipped with a meter to indicate the level of the signal going onto the tape, and a significant number of

amplifiers now also boast this feature. The VU (for Volume Unit) meter is marked with an arbitrary scale, with zero corresponding to the maximum usable signal; the recording level, when using a tape recorder, is set so that the indicator never exceeds this point.

Traditionally the VU meter is a mechanical device and as such it is subject to inertia (the tendency of a moving object not to change its state). The electrical signals being measured, however, are not subject to this restraint and may change strength by several orders of magnitude instantaneously. The initial striking of a string in a piano, for instance, is very much louder than the subsequent resonance and this is faithfully reproduced by the signal passing through an amplifier. A meter measuring this signal will only have had time to set its needle in motion before the signal has died away. At this point technology, in the form of solid state electronics, comes to the rescue.

By using Light Emitting Diodes (LEDs) to replace the coil meter, the mechanics, along with inertia, are eliminated. This kit from Tandy uses the UAA170L IC, specifically designed for this purpose, to control a row of nine LEDs which act as a VU indicator. For your money you get the PCB, components and a set of instructions in four languages. The English translation is slightly dubious —

All the components can be thrown onto the drilled, printed and laquered board without too much fuss, although you've got to be careful with the polarised ones; the instructions don't contain any diagrams. Mounting the LEDs, in particular, needed a second glance as the component locations printed on the PCB were a bit unclear and it was difficult to tell which way round the flat side of the LED should go.

At this point the constructor is left to his own ingenuity. You need a 12 V DC power supply, the chosen signal source, and some means of calibrating the meter (which is sensitive to inputs of from 20 mV to 6 V at full scale deflection). To set up the kit for an amplifier you can use an oscilloscope and a signal generator: connect the generator, set to 1 kHz, to the amplifier input at a suitable level, take the output from the amplifier to the oscilloscope. Adjust the output of the amplifier to the point where clipping just starts (this can be seen on the scope as a flattening of the peaks of the signal waveform) and then adjust the trimmer on the meter so that it indicates a maximum reading. With a tape recorder that already has a VU meter fitted the calibration can be made by feeding in a signal from, again, a signal generator at 1 kHz, adjusting the recording level to maximum using the conventional VU, and then setting the kit can also give a maximum reading.

The kit worked first time and produced a satisfying dancing spot of light (only one LED is lit at any time, as opposed to the system where 'lower' LEDs remain lit; this produces a 'bar' of light which varies in length). The only real quibble that I can think of is that the LEDs supplied were all red: it would have been much prettier, and more useful, to have eight green ones and a single red one at the top of the line.

The completed kit consists of a PCB on which the LEDs are mounted and anyone with the time to drill nine holes in a panel should have little trouble installing it in some existing equipment. A little knowledge (however dangerous it may be) will be required in finding, or manufacturing, a suitable 12 V power source and a point from which to tap the signal. If you want a stereo pair you'll have to buy two kits — they cost £9.95 each. **HE**

# CB ANTENNAS AND ACCESSORIES

We are pleased to announce that we are now main distributors for antenna specialists

**'Firestik'<sup>®</sup>**  
**ANTENNAS**

*Citizen Band Fibreglass Antennas and Accessories for Marine, RV, Truck, Auto, Van and Motorcycle.*

Watch for the new film  
**"SMOKEY AND THE BANDIT II"**  
starring **BURT REYNOLDS** and  
**'Firestik'<sup>®</sup> ANTENNAS!**

*Shakespeare<sup>®</sup>*

## CB MOBILE ANTENNA SERIES

and the Shakespeare fibreglass Super Big Stick™ base station antenna



SWR METERS, NOISE SUPPRESSION FILTERS, T.V.I. FILTERS, CO-PHASORS, ANTENNAS, LEADS AND NUMEROUS OTHER ACCESSORIES.



Microphones, Power Supplies, SWR Meters, Linear Amplifiers, Preamplifiers, Antennas, Frequency Counters etc., etc. . . . .

**TELEX<sup>®</sup>** MICROPHONES AND HEADSETS

**TURNER<sup>®</sup>** ANTENNAS AND MICROPHONES

**hy-gain<sup>®</sup>** CB MOBILE AND BASE STATION ANTENNAS

**K40** SPEECH PROCESSORS AND BASE LOAD ANTENNAS

WE ARE UK DISTRIBUTORS FOR THE MANUFACTURERS LISTED ABOVE AS WELL AS MANY OTHER COMPANIES. WE BUY DIRECT FROM THEM WITHOUT ANY MIDDLEMEN SO THE PRICES WE CAN OFFER ON THEIR PRODUCTS ARE SOME OF THE BEST IN THE COUNTRY AND THEIR RANGE IS VAST. COME AND SEE US . . . . . IT MAKES SENSE!

★★ SEND £1 FOR A COMPREHENSIVE CATALOGUE ★★

**WINTJOY**

Ltd.

*103 High Street, Shepperton,  
Middlesex TW17 9BL, England.*

*Tel:*

*Walton-on-Thames (STD 09322) 48145*

COMMUNICATIONS EQUIPMENT DISTRIBUTORS

UK RETAIL OUTLETS IN SELECTED AREAS STILL BEING SOUGHT

★★ UNTIL RIGS BECOME LEGAL WE ARE UNABLE TO SUPPLY THEM ★★

# Breaker One Four

**We're almost there, Open Channel looks set to become our very own CB service but the fight is far from won. Rick Maybury investigates.**

CB HAS NOT BEEN LEGALISED — YET. In the words of Mr William Whitelaw the Home Secretary, in a reply to Mr Patrick Wall MP asking "whether he has completed his examination of the possibility of introducing Citizens Band Radio in the United Kingdom," he replied:

*"We have concluded that we favour in principle the introduction of a facility of this general kind.*

*The scheme which I am considering would however differ in certain respects from that advocated by those whose ideas are based on the experience of other countries and we are proposing to call it Open Channel. It would take some time to introduce, because current developments in Europe and elsewhere have to be taken into account, and because further work is necessary, for example, to establish a precise frequency band and appropriate technical specification.*

*I therefore think it important that the general public should have the opportunity to consider the implications of the sort of scheme that might be possible, and to express their views. Accordingly I intend to publish a discussion document on Open Channel within the next few weeks, and I shall take the public reaction to this into account in reaching the final decisions."*

That was on Wednesday the 7th of May 1980. It sounds very impressive, but there are one or two little passages that are quite significant.

"It would take some time to introduce. . . ."

We ask, how long? It is not unheard of for a discussion document (Green Paper) to take up to two years to be acted upon!

"...further work is necessary, for example, to establish a precise frequency band and appropriate technical specifications. . . ."

We took the trouble to phone up the Home Office the day after the announcement, a spokesman told us that:

"We have been carrying out extensive research in our laboratories and have finalised the specifications."

Wait a minute, I thought we were going to be asked?

That aside, the announcement has generated an incredible amount of rumour-mongering. Currently we are receiving up to a dozen phone calls a day suggesting that Open Channel (more about the name later) is going to be anywhere from halfway along the Medium Wave to a frequency that could only be received by NASA.

Favourite at the moment is around 900 MHz, not actually too unconvincing but we'll say no more! We supposedly have a chance to make our views known, and that is exactly what everyone should do. Hopefully we will have the Green Paper in our possession by next month. All being well we'll have some suggestions of our own to make.

Now for that name. Open Channel, say it to yourself a few times, it all sounds terribly British. A quick poll around the BOF office gained mixed reaction, tell us what you think about it.

Last few words before we get back to business, as we said in the first line of this article, CB has not been legalised, it is still important that our feeling be made known, demonstrations are still being organised, the emphasis now is not so much 'We want CB' as 'WE WANT CB NOW.' See you in Trafalgar Square on July 6th.

## CLUBS

In the directory last month we said that Andy Donovan was the Chairman of the UBA, in fact he is the President, sorry Andy.

## HANDLE DIRECTORY

Yes, we are still going ahead with the Directory of Handles, names are still pouring in by the hundred. This has got to be the last month for entries, closing date is now June 20th. Publication will hopefully be in the September issue, well, part one at least, judging by the number of names we've got already.



● C.B. AERIAL ● EVERYTHING BUT RIGS ● PLUGS ● SWR METERS ●

MOBILE ANTENNAE



BOOST 20RF  
IMPEDANCE MATCHER

**MOBILE STEREO**  
Dept. HE, 360 York Road, London, SW18  
Telephone 01-870 7362  
Free fitting on all units purchased from us

★ Come and have a cup of coffee while we fit your stereo  
★ Wide range of fitting kits and aeriels ★

● BASE ANTENNAE ● RAIN CAPS ● MICROPHONES ● CB SUPPRESSORS

# C.B.

Antennas & Accessories  
We stock all leading brands, e.g. Turner, K40, Firestik, Shakespear, HMP, Hy-Gain, A.S.P.

Power supplies, ext. speakers  
P.A. Speakers, Base Station  
Antennas, Coax, Filters  
Connectors, Books, etc., etc.

Open 7 days

## SPARES 'N' REPAIRS

79 Far Gosford Street  
Coventry (0203) 29567



### LONDON PETITION

Here we have (above) Dave and Jeff from the Harrow and Wembley CB Group handing over their petition to Richard Town and Bernie Murray of the NATCOLCIBAR steering committee down at County Hall in London on May 13th. The petition contained nearly 6000 signatures. All the signatures are from Londoners, more power to their elbows.

### HE PETITION

If you're wondering what to do about the petition we published last month, don't worry, the wording is still relevant. Fill them in and return them either to us or to any branch of Tandy. Remember they must be back by June 30th in time for the July 6th demo. We still haven't got CB!

# CB RADIO ACCESSORIES

The Largest distributors of CB accessories in the UK.

**SHOP  
NOW  
OPEN**

**SWR METERS  
including HANSEN**



Come and see the biggest and best selection of CB radio accessories including:-

**MICROPHONES by  
TURNER-K40  
G.C. ELECTRONICS**

**SUPPRESSION EQUIPMENT  
PLUS MUCH MUCH MORE**

**ANTENNAS  
by  
HY-GAIN  
SIRTEL  
A.S.  
HMP**



10% discount on presentation of this ad

**Mura**  
Mura Electronics (UK) Ltd.

Blackpool: A.D.S. Electronics, 16 Warbeck Drive (Nth. Shore) Blackpool. Tel. 02953 57222/0253 21173; Edinburgh: Custom Equip., 131 Fountain Bridge, Edinburgh EH3. Tel. 031-229 8830; Stoke-on-Trent: MSBC, 27 Hope Street, Hanley, Stoke-on-Trent. Tel. 0782 273815; Wigan: Car Radio Wigan, 80 Darlington Street East, Wigan, Lancs. Tel. 0942 43101.

79 Church Road, Hendon, London NW4  
Tel: 01 203 5277/8



## OPEN CHANNEL

Now, about that name, 'Open Channel', the first time we heard it our immediate impression was that it would be just one channel. It's that sort of name, now, reason tells us that there is absolutely no-way that we would get just one channel (Is there ???). After saying it to ourselves a few times it has slightly grown on us.

## T-SHIRT COMPETITION

Thanks for all the entries to our CB Tee-shirt competition, closing date for entries will be 30th June. If we still haven't received your masterpiece then hurry, there's still time.


## SEATCOVER OF THE MONTH

We know how much you lot like having your photographs taken, we can tell by all the people skulking behind the tea hut at the London demos as soon as we get our cameras out. So, we thought, how about you sending us a picture of your 'seatcover', (girlfriend to all non male chauvenists, we know it's not a very endearing term but it's all we've got).

We would like to brighten up the pages of HE with the odd (not too odd please) picture of a young lady. We won't guarantee instant stardom or a ready made modelling career but who knows. Anyway how about it, any of you breakers want to get your lady into print?

You don't have to be too specific about names and addresses but if you want the photos back please include an SEA.

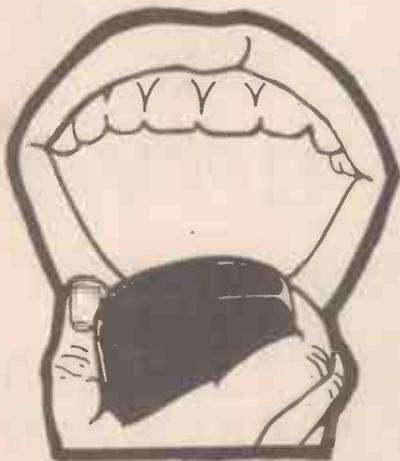*HE&BOF's first Seatcover Of The Month was sent in by Glen Hall. She's Jillie Newham, 22, a Trainee Computer Operator from Guildford.*



# CB Equipment Specialists

the U.K.'s leading CB equipment supplier..!

All types of antennae — disguise, tri-band, DV27, DX27, B27, T27, dipoles, twins — every possible type/position of mount. We're approved distributors for antenna specialists. We also sell burners (50-1000 watts), pre-amps, SWR meters, mikes, test equipment, suppression gear, plus, connectors, books, etc. In fact, anything to do with CB EXCEPT RIGS. Special pledge — we will match or beat any genuine price anywhere in the UK.

Mail order expressed by Red Star, all goods returnable if not satisfied.

Phone your requirements, quoting your Access or Barclaycard number for immediate despatch. We'll help with any problems, by phone if at all possible.

*10-21 breakers*

*Woking (04862) 67944 Mon-Sat.*

**MIKE EVANS**



A year ago only two campaign groups were known nationally, namely the CBA and UKCBC, from these sprang such clubs as the 10-4 Club, the UBA, CBNE and many many more.

Today if you stop Mr and Mrs Joe Public in the street and ask them about citizens band radio, I would estimate that 45 per cent of them would say "Yes", they had seen it on the television, heard about it on the radio or even read it in the national or local press, but who do not regard it as a necessary thing.

A year ago it was all "CB can save your life, keep you awake during long-distance driving, keeps you out of traffic jams", in fact the English were becoming very Americanised with these statements. Today the Home Office are looking for more realistic cases, facts and figures which relate to the UK. It is a basic personal freedom to be able to communicate freely with each other.

Not so long ago radio amateurs and radio modellers were very anti-CB, they are less so now due to the possibility of new technology and a break away from 20 year old technology namely 27 MHz. Which we feel 55 per cent of our readers feel must take place if a CB system tailor made for the UK is ever to be envisaged.

In early 1979 there were very few prosecutions brought to the eyes of the general public, in fact CB was well under the carpet. Today with the illegal operators on 27 MHz — and without them where would we be! — it is constantly being brought in the public's attention as to date there have been 1,142 cases.

A year ago most policeman didn't know what a DV27 or rig looked like, but now with memorandums from the Customs and Excise people circulated to all stations, it is a bigger cat and mouse game than it ever was.

Before the Conservative Government was elected last May nobody had heard of the All Party Group of MPs who were looking at the whole question of CB radio — was this the beginning of a more forward looking campaign?

In fact a year ago we never thought we would be bringing you a publication called "Bandstand", reporting on newspaper, television and radio coverage, as well as the demonstrations that have been held this year, and producing articles and letters with such deep feeling on CB from our readers.

A year ago Timothy Raison wasn't such a well known figure, nor I should imagine did he realise that the general public were so passionately in favour of CB radio, and that he would receive over 8,000 pieces of correspondence on the subject.

A year ago who would have dreamed that the GLC would publish a consultative paper on CB radio and ask Londoners for their views on the subject, who would have thought that a National Committee would be formed to promote the legislation of citizens band radio!

The above has all happened, what does the future hold. With all this pressure from so many quarters where are we going! Not having a crystal ball, but reading between the lines, are we to be given a CB system at all? Are we going to get a purely British VHF system? Or are we going to be another Australia? We believe it will be a matter of forgetting 27 MHz and like the British electronics industry have done in the past look around for the best money making system tailored towards financial gain and with this in mind this is the system we will get.

**HE MICROBE R/C**

Basic Kit **£19.90**  
(2 PCB's and all PCB components)

**C.B - C.B - C.B**

**AERIALS AND ACCESSORIES**

- Cutter mount **£15.95**
- Boot / Roof / Wing mount **£19.95**
- Traditional Fibreglass Whip **£14.95**
- AM / FM / CB Retractable **£25.95**
- CB Electric Retractable **£29.95**
- AM / FM / CB Electric Ret **£39.90**
- Roof mount 20" Glass Whip **£19.95**
- SWR / Power / F.S. Meter **£24.95**
- SWR / Power Meter **£12.95**
- Pre-Amp 20db gain **£19.95**
- Splitter Box **£9.95**
- Linear Amps from **£59.95**
- 27 MHz Monitor + AM / FM **£18.65**

\*These are a few of the items available\*

The latest from the U.S.A.

**PINBALL WIZARD**

\*Still available\*

Featured in Nov. Issue of E.T.I.  
Home TV Game — B/W Kit

Basic Kit **£28.90**

- Contains everything except box and controls
- Box & Controls **£6.50**, P.S.U. **£3.90**
- CEH Car Alarm Kit **£18.90**
- Chroma Chime 24 tune door chimes kit **£10.75**, Built **£15.95**
- SINCLAIR SC110 10MHz scope **£145.25**
- PFM 200 Digital Frequency Meter **£52.00**
- 3" 5 MHz Oscilloscope **£113.85**
- 4" 5 MHz Oscilloscope **£139.90**
- 5" 10 MHz Oscilloscope **£169.90**

**ATARI £138**

**ELECTRONIC GAMES**

- Star Chess T/V game **£63.35**
- Database Prog T/V game **£89.95**
- Chess Challenger 7 **£99.00**
- Chess Challenger 10 **£150.00**
- Voice Challenger **£230.00**
- Chessmate 8 level **£59.95**
- Zodiac Astrology Computer **£29.95**
- Electronic Mastermind **£14.90**
- Supersonic Mastermind. New **£21.00**
- Mattel Subchase. New **£17.90**
- Mattel Armor Battle. New **£17.90**
- Enterprise 4 in 1 **£22.90**
- Galaxy Invaders. New **£22.95**
- Radio Control Models—Various

**COMPUTERS—HOME BUSINESS, ETC**

- Pet 8k **£550.00**
- Pet 16K **£670.00**
- Pet 32K **£790.00**
- Superboard 11 4K **£172.45**
- UK101 kit 4K **£228.85**
- UK 101 Built 4K **£286.35**
- Superboard / UK101 case **£33.80**
- Nascom 2 kit **£339.25**
- Nascom 2 built **£420.00**
- TRS80 16K Level II **£409.40**
- H14 line printer kit **£410.00**
- 5 1/4" disc drive for TRS80 **£287.50**
- Computer Books **S.a.e.**
- Software - Pet / TRS80 / Superboard, etc.
- Exody Sororor 16 / 32 / 48K from **£80.00**
- Renumber prog. 101 **£4.00**

Free — Advice / Demonstrations / Coffee

S.a.e. enquiries. Please allow up to 21 days for delivery. ALL PRICES INCLUSIVE



**N.I.C.**

61 BROAD LANE, LONDON N.15 4DJ  
Day 01-808 0377; Eve 01-889 9736



**CB CITY**

PROUDLY PRESENT



**ACCESSORIES CATALOGUE SHOWROOM**

Telephone:  
**ALDRSHOT**  
**0252 318141**

Monday-Saturday  
9 a.m.-6 p.m.

**(NO RIGS)**



**KEITH TOWNSEND**

MCBRC was formed almost by accident as the result of a "bust" which occurred during the local filming of a "nationwide" article on CB. The resultant newspaper publicity culminated in a meeting of just fifteen people with the vague idea that "something should be done". Two local newspapers had recently featured articles about CB and both proved very sympathetic to our aims, even offering suggestions as to how we might test local support.

Our next meeting, a month later, was attended by over fifty people and the club was well under way. The first tangible results of our campaign were the requests for interviews and phone-ins from the various local radio stations. I was interviewed by one pretty lady who was surprised to discover that we were not in fact running a Caroline style pop pirate station. Our initial letter campaign met with a very mixed response which included some surprises such as the letter of tacit support from the local Police Federation. As the result of a request from ROSPA for further information we contacted REACT in Chicago who sent copious details which are currently being studied by the Society. Like many other clubs we received only negative replies from both the AA and RAC.

As the result of some expert conning we obtained free stand space at the Birmingham Custom Car Show in late October. During the four days of this show our membership increased dramatically and the Post Office made handsome profit from the five thousand or so postcards sent to Momma Maggie and Whitehall Willie, whilst the local Rates Dept. got a boost from our parking tickets.

Following our various contacts with other clubs we were proud to host the first national CB Conference in early December, which, after a great deal of discussion resulted in the formation of the National CB Committee. The mere existence of this committee has generated a great deal of media interest in CB while the committee itself has achieved a great deal of respect in official circles.

During these last twelve months we have kept up a steady stream of letters to the Home Office (not all of which have received answers) and pestered as many local MPs as would stop and listen to us. One of our proudest possessions is a letter to a member from the Minister of Transport saying that he believes that the possible advantages of CB outweigh the possible disadvantages.

We have had our good times (the club dance) and our bad times (the night the beer ran out) and our membership, which is open to anyone

interested in CB now exceeds 750 including our honorary lady members.

As I write this I and a number of my buddies are experiencing terminal nervous breakdowns, trying to organise Britain's first CB Campaign Carnival.

Hopefully the next one will be to celebrate legalisation.

**Keith Townsend, Midlands Citizens Band Radio Club, 1163 Yardley Wood Road, Birmingham B14 4LE.**

*Next month our old friend Glyn Hall of WintJoy fame tells us his life story.*

**CB ORGANISATIONS**

**BANDSTAND MAGAZINE**

FLAGSTONES  
WEST HEATH LANE  
SEVENOAKS, KENT

**NORTHERN IRELAND CITIZENS BAND INFORMATION CENTRE**

93 CASTLEREACH ROAD  
BELFAST  
BELFAST 31614

**NATIONAL COMMITTEE FOR THE LEGALISATION OF CB RADIO (NATCOLCIBAR)**

GLC  
COUNTY HALL  
LONDON

**'Firestik' ANTENNAS**

**MODEL KW2 £14.40**

2' 5/8 + wave 3dB gain. Fire-power rating — 100AM watts, 200 SSB.

**MODEL KW3 £15.55**

3' 5/8 + wave 6dB gain. Fire-power rating — 300AM watts, 600 SSB.

**MODEL KW4 £16.70**

4' 5/8 + wave 6dB gain. Fire-power rating — 400AM watts, 800 SSB.

**MODEL KW5 £17.55**

5' 5/8 + wave 6dB gain. Fire-power rating — 500AM watts, 1000 SSB.

**MODEL KW7 £20.15**

7' 3/4 + wave 6dB gain. Fire-power rating — 700AM watts, 1400 SSB. + Base/Cable.

● 27MHz = 120 Channel Plus Tunable to 10 Meters.

UNTIL C.B. IS LEGALISED WE DO NOT SUPPLY RIGS.

**Shakespeare**

**REBEL 500 £10.95**

We stock a very large selection of CB Accessories. If what you require is not in stock we will gladly order.

- DV27
- DX27
- 5/8 HELICAL WHIPS
- FULLY DISGUISED ANTENNAE
- BASE STATION ANTENNAE
- STARDUSTER ETC.
- SWR METERS
- POWER METERS
- POWER SUPPLIES
- SLIDE MOUNTS
- SUPPRESSION KITS
- MAGIC MIKES
- POWER MIKES
- ANTENNAE MATCHERS
- SPLITTER BOXES

- C.B. BOOKS
- Big Dummy's Guide £2.75
- CB Lingo Bible £2.75
- Best Book on CB £3.95
- CB Yearbook 1980 £2.25
- + 25p per book p&p.



Citizen Band, Antennas and Accessories for Marine, RV, Truck, Auto, Van Motorcycles . . . Mobile and Indoor / Outdoor Base Applications  
**10-4 Good Buddies**

**Come to us for your Car Spares — Accessories — Customizing Equipment**

**TEL: CHERTSEY (STD 09328) 62556**  
**229 CHERTSEY ROAD**  
**ADDLESTONE, SURREY**

# A HISTORY OF CB

IT WAS THE ROMANS WHO FIRST BROUGHT CB TO OUR SHORE

THEY CALLED IT BANDUS CITIZENICUS OR BC!

THIS IS JULIUS 55 BC

THE ANCIENT BRITONS DIDN'T HAVE MUCH USE FOR ANYTHING ROMAN...

LET'S HAVE ONE FOR THE WOAD!

... AND OFTEN INTERRUPTED THEIR FREQUENCIES

SEVERAL HUNDRED YEARS LATER KING ARTHUR RECEIVED A 40-BAND RIG FROM THE LADY OF THE LAKE ...

... AND A NEW AGE WAS BORN

SOON KNIGHTS ALL OVER ENGLAND WERE GATHERING TOGETHER

HEY~ WE GOT US A CONVOY!

CHIVALRY BECAME THE ACCEPTED FORM OF BEHAVIOUR

WANNA CUT THE RUG, BEAVER?

OLD WILL SHAKESPEARE HIMSELF CONSIDERED WRITING A PLAY IN CB LINGO

CB? OR NOT CB?

ADMIRAL NELSON BROUGHT THE PITIFUL LACK OF NAVAL CB TO THE PUBLIC'S ATTENTION WITH HIS HEROIC STAND AT WATERLOO (OR WAS IT EUSTON? ANYWAY IT WAS ON THE NORTHERN LINE)

I HEAR NO SHIPS

YET IT WASN'T UNTIL THE INDUSTRIAL REVOLUTION THAT CB WAS SEEN BY THE MASSES

OOH~ LOOK STEAM RADIO

AND IT'S ONLY IN RECENT YEARS THAT OUR ENLIGHTENED GOVERNMENT HAS SHOWN SIGNS OF RESPONDING TO PUBLIC PRESSURE ABOUT CB ...

THESE CB-ERS ARE GETTING UPPITY~ WE'LL HAVE TO TOSS THEM A CRUMB...

FIRST WE MAKE IT LEGAL TO OWN A RIG~ BUT NOT TO OPERATE IT...

YEA YEA

VERILY

FORSOOTH

THEN WE CAN TAX THEM FOR OWNING IT ~ THE NEXT STEP (DROOL~DROOL) IS TO TAX THEM FOR LOOKING AT IT AND THINKING ABOUT USING IT!

THEN WE CAN STOP THEM FROM READING ABOUT IT (GLOAT, GLOAT) AND MAYBE...

YEA

STROKE OF GENIUS

MAKE HIM P.M.

GET THE PICTURE? THAT'S HOW IT IS ~ UNTIL PERHAPS SOME ENLIGHTENED BRITON FOLLOWS THE EXAMPLE OF HIS DISTANT ANCESTORS!

HEH HEH

FLETCH

THE #1 WIRE WOUND  
AND MOST COPIED  
ANTENNA IN THE WORLD!

**'Firestik'<sup>®</sup>**  
**ANTENNAS**

**CITIZEN BAND  
FIBREGLASS ANTENNAS  
AND ACCESSORIES.**

Call or write for full information

**WINTJOY LTD.**

103 HIGH STREET, SHEPPERTON  
MIDDX. TW17 9BL  
Tel. Walton-on-Thames (STD  
09322) 48145

# CB MONITOR

40 channels, 8 transistors. Noise blanking circuitry with switch. Uses normal car radio antenna. Connects and works off your normal AM car radio. Can be installed in under five minutes with no tools.

Available from:

**WINTJOY LTD.**

103 High Street, Shepperton  
Middx. TW17 9BL, England

Tel. Walton-on-Thames  
(STD 09322) 48145

YOUR NEAREST INTERNATIONAL

Mobile Moonraker<sup>®</sup>

The  
MOON-  
FANTOM  
AV-200



SOLE AGENTS FOR:-

Avanti's<sup>®</sup>  
Astro-Fantom  
Goes Where  
No CB  
Antenna  
Has Gone  
Before!

AV-200



From the AVANTI Research laboratories comes a sleek, 22" full 1/2 wave antenna, so unique that it mounts on glass, transmits through glass and receives through glass... yet requires no grounding to metal as do conventional 1/4 wave antennas. No holes to drill, no clamps, clips or magnets to ever mar or scratch your car's finish! No pinched cables to run in through doors, windows or trunk. No more leaks. The Astro-Fantom is a handsome, low profile antenna that provides the ultimate in convenience!

# C.B. SUPPLIER

DEALERS REQUIRED

AVANTI ANTENNAS MOBILE & HOME BASE  
SOMMERKAMP AMATEUR & MARINE RADIOS  
STALKER RANGE  
C.T.E. POWER SUPPLY UNITS, ALL ACCESSORIES & AERIALS.

Replace your present antenna with a new Avanti Mobile Moonraker



avanti



MOONRAKER AV-211M

A New Direction in Fiberglass Antenna Whips! From Avanti



The Avanti Skinny Stick.

AV-110




ASTRO-FANTOM AV-200



Form 21053

MOONRAKER 4

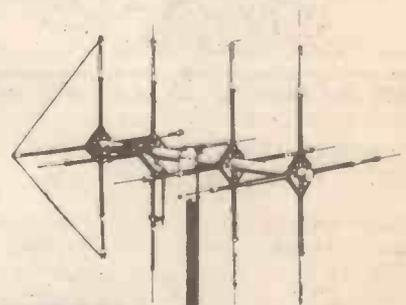

**T.V.E.S. LTD.** 12/13 Greenpark Road, Bray, Co. Wicklow, Ireland.  
Tel: 860077, 868727, Telex: EI. 31539

Northern Ireland Office: DunDonald 2941


"WHILST WE CANNOT SELL RIGS TO THE U.K. AT THE MOMENT, WHY NOT SEND FOR DETAILS OF OUR RANGE IN PREPARATION FOR LEGISLATION"

# Piezo Electricity

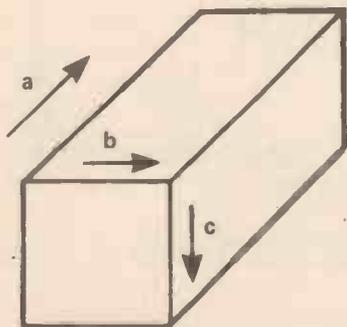***It sparks when you hit it. Well, thats not an altogether bad description of the Piezo Electric effect, but these crystals can do a whole lot more as Ian Sinclair explains.***

PIEZO ELECTRICITY HAS been with us for some time, and yet we seem to keep meeting new applications of this remarkable effect. How is it that we can use the crystals to generate sparks, to convert vibration into electrical waveforms, to stabilise the frequency of oscillation, or to make precise electrical wave-filters? Here's how — just switch off that soldering iron for a minute or two.

By this time, you should be getting used to the idea that most materials form crystals. Crystals are regular arrangements of atoms, probably the most perfect structures we know, but that doesn't mean that the structures are exactly alike in each direction. The key word here is isotropic. An isotropic crystal has the same properties in any direction (Fig. 1). Properties in this case means measurable quantities like electrical conductivity, heat conductivity, expansion coefficient, elasticity and all the other measurable quantities which fundamentally depend on how atoms are arranged.



1. An isotropic crystal gives the same readings for quantities like expansivity, resistivity, etc., in any direction along the crystal, a, b, or c.

## CRYSTAL CLEAR

An isotropic material is mercifully easy to make measurements on, because you don't have to choose any special direction in the material. The materials we call anisotropic (meaning not isotropic) aren't like this, though, how they behave depends on which direction we choose to work on. Wood is a simple example, everyone who has ever worked on a piece of wood knows how differently wood cuts across the grain as compared to along the grain.

Many crystals are anisotropic, because the spacings between atoms are quite different in different directions

along the crystal. The result is that each quantity that we can measure will have different values, depending on the direction that we choose in the crystal.

Now when a crystal is anisotropic, it usually behaves in a peculiar way in a strong electric field. Any material will be affected by a strong electric field; usually what happens is that the material has some electrons separated off, starts to conduct, then sparks across. Some very anisotropic crystals behave differently, their atomic spacings re-arrange themselves a bit. When this happens there is no way the crystal can be the same size as it was before, because the size of the crystal is decided by the size of the atoms and the way they are arranged. Usually what happens is that the atoms move slightly closer to each other *in one direction* so that the crystal becomes slightly shorter in that direction. The dimensions of the rest of the crystal may remain unchanged. These changes of length are very small, but they're certainly not undetectable.

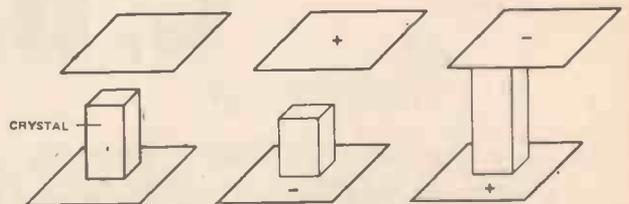


Fig. 2. The drawing's an exaggeration, of course, but it shows the idea. Piezo-electric crystals become shorter in one direction of electric field and longer when the field is reversed.

What makes the process more interesting is that if an alternating electric field is applied to the crystal, it will become longer and shorter alternately, in phase with the field. How do we apply an alternating field? Simple enough, we simply sandwich the crystal between metal plates and connect an alternating voltage between the plates. Since we usually want the distance between the plates to be very small, the usual way of achieving this is to deposit a metal, usually silver, on opposite faces of the crystal, making sure that we have chosen the right direction in the crystal.

With a crystal treated in this way, an alternating voltage across the metal conducting will cause vibration, with the crystal length becoming longer and shorter at the frequency of the AC. This is a piezoelectric transducer, which will vibrate at the frequency of the AC signal and pass on the mechanical vibration to any-


# Piezo Electricity

thing in contact with the crystal. Cementing one face of the crystal to a diaphragm creates a piezoelectric tweeter, a loudspeaker unit which will give out a sound wave from the large surface of the diaphragm which is being vibrated by the crystal.

## FAST MOVERS

There's no reason to stick to frequencies in the audio range of 30 Hz—20 kHz though. The crystals themselves can vibrate quite happily at much higher frequencies, even up to several MHz. In this way we can have ultrasonic tweeters, giving out invisible beams of air vibration like sound but at frequencies too high to hear. The favourite frequency range is around 35—65 kHz, because the vibration of the crystal can be transferred to air reasonably easily in that frequency range.

Any material that is in contact with the crystal will be vibrated along with it, though, so that this ultrasonic vibration has many applications. One is non-destructive testing. A piezoelectric crystal vibrates a sample, perhaps a metal casting, and the path of the beam of vibration through the material is traced, using another piezoelectric crystal as a detector. An invisible flaw inside the material causes the beam path to be unaccountably shifted, so that the material can be rejected. This principle is used widely, along with X-ray methods, for detecting holes and faults in metal casting, particularly if the casting is valuable or if its failure could cause likes to be in danger. They don't bother too much with things like the kick-start cranks of motor bikes, though!

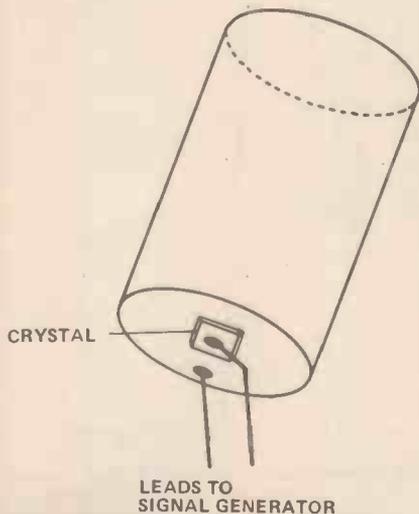


*Fig. 3. An ultrasonic cleaner. The metal beaker has a piezoelectric crystal soldered to the base. Leads to the beaker and to a contact on the face of the crystal are fed with high frequency signals from a generator. The vibrations of the crystal cause the liquid in the beaker to vibrate.*

## CLEAN SOUND

Ultrasonic cleaning is another widespread use of ultrasonics. A piezoelectric crystal is mounted on the base of a metal beaker, so that it will vibrate any liquid in the beaker — the liquid can be water or any grease solvent like benzene, and anything placed in the vibrating liquid will be thoroughly cleaned with no need for scrubbing. Of course, you've all got HE offer digital watches and probably don't remember the old fashioned tick-tock type, but ultrasonic cleaning was the standard method

for cleaning these things. Using an ultrasonic cleaner meant that the watch didn't have to be taken apart, so saving an immense amount of time and skilled work.

A piezoelectric crystal with quite a different type of application is the quartz crystal. Quartz crystals are prepared in just the same way as the barium titanate crystals of ultrasonic cleaners, but the aim is not to harness the mechanical vibration but to make use of the electrical behaviour of the crystal. Any insulator with a couple of metal contacts on opposite faces is a capacitor, but the materials we usually make into capacitors are not piezoelectric, so that the capacitor behaves, well, just like a capacitor.

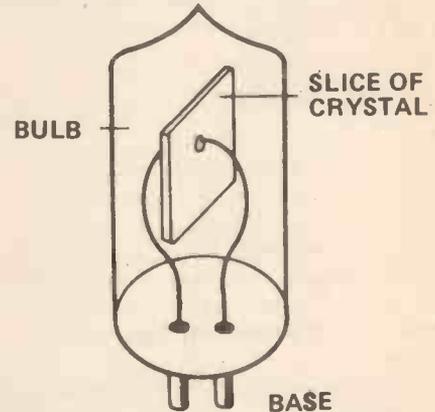

*Fig. 4. A quartz crystal inside an evacuated bulb. This is a type of mounting used for crystals that control radio transmitter frequencies.*


A capacitor made from a piezoelectric material is rather special, though, because electrical energy is converted into mechanical energy of vibration when the crystal is driven by an alternating voltage. This, in turn, alters the electrical behaviour. A good comparison is a loudspeaker speech coil which may measure 6 ohms on a meter, but whose apparent resistance, equal to AC volts divided by AC amps, can change considerably from one frequency to another because of the transfer of energy from the coil to the core.

The crystal and the loudspeaker also show the effects of resonance. At one particular frequency, the energy converting process is very much more efficient than it is at other frequencies, so that a very large amount of vibration can be caused by a very small amount of electrical energy. Now this resonance is the same sort of effect as we get when an inductor and a capacitor are connected together, either in series or in parallel, but with one important difference. Mechanical resonances are usually very sharply tuned, with a very small bandwidth, a quantity which is measured by the 'Q' factor of a tuned circuit. Q factors of 100 to 250 are considered pretty good by the standards of electrical tuned circuits, but mechanical resonances can achieve Q values of 30,000 or more.

## CRYSTAL GAZING

All of that prepares us for the fact that the quartz crystal behaves electrically like an incredibly efficient tuned circuit. At a frequency well below the frequency of mechanical resonance, the whole thing behaves like a capacitor, with a value of reactance which decreases as the frequency is increased, and a 90° phase shift, current leading voltage. This behaviour keeps up until near the frequency of resonance, when the crystal starts

to behave as if it had a resistor connected in parallel with the capacitor, allowing more current to flow, and reducing the phase shift. At the first peak of resonance, the crystal behaves for AC like a small value resistor, with no phase shift. This peak is called the series resonant peak. As the frequency of the signal across the crystal terminals is raised, the resistance rises, the phase shifts violently again and at a frequency a few kHz higher than the series resonant frequency another resonance occurs. This time the crystal behaves like a parallel resonant circuit, and at the peak of resonance the resistance appears now to be very high, once again with no phase shift. At higher frequencies still, the crystal behaves like a capacitor again, with a 90° phase shift, current leading voltage.

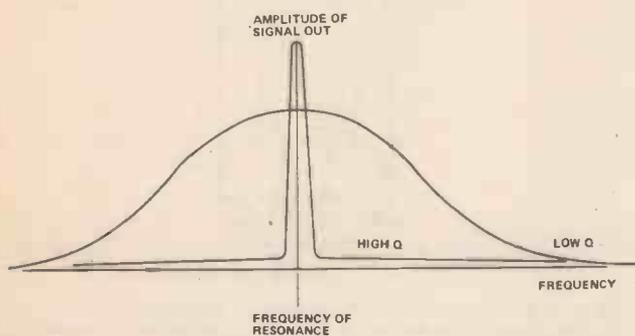


**Fig. 5. Q-factor of a tuned circuit. A high-Q tuned circuit tunes sharply to one frequency, so that there is very little output at other frequencies.**

All of this leads to crystals being used in oscillator circuits which can maintain a very precise frequency—used for applications as diverse as digital watches and radio transmitters. In addition, crystal filters can be designed which will pass only a very small bandwidth around a selected frequency.


Quartz crystals intended for oscillators are never driven very hard—too much vibration could split the crystal—but the vibration can be used. The piezoelectric effect can work both ways however, particularly in ceramic crystals and if we put a second set of electrode plates onto a ceramic crystal then a mechanical vibration of the crystal will cause an alternating voltage to appear across these additional plates. This arrangement can be used as a very efficient filter, passing only a narrow band of frequencies around the resonant frequency of the crystal. This can permit the use of untuned (IC) amplifiers, with just a couple of these ceramic filters providing the tuning. In addition, the removal of unwanted frequencies is much easier than when coil-capacitor tuned circuits are used.

The fact that the effect works the other way around—with mechanical vibration causing an electrical output—has, of course been the basis of ceramic gramophone pickups for many years. Less well known is the application of the same transducers to measure speed and acceleration of aircraft and missiles. The transducers give a voltage proportional to acceleration, and analogue computers transform this into readings of speed and distance. In addition, the transducers which

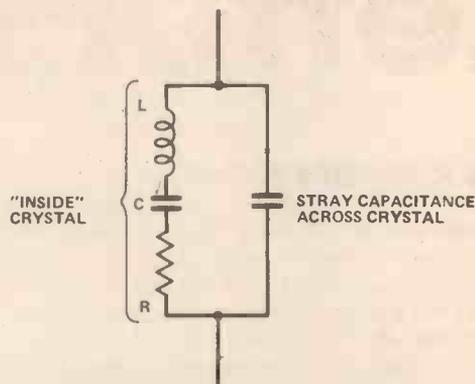

**Fig. 6. Equivalent circuit of a crystal — this circuit would behave electrically just like a crystal if we could ever get suitable components for L, C and R.**

are used as ultrasonic sources can also be used as receivers for the same frequency, so that ultrasonic burglar alarms are possible.

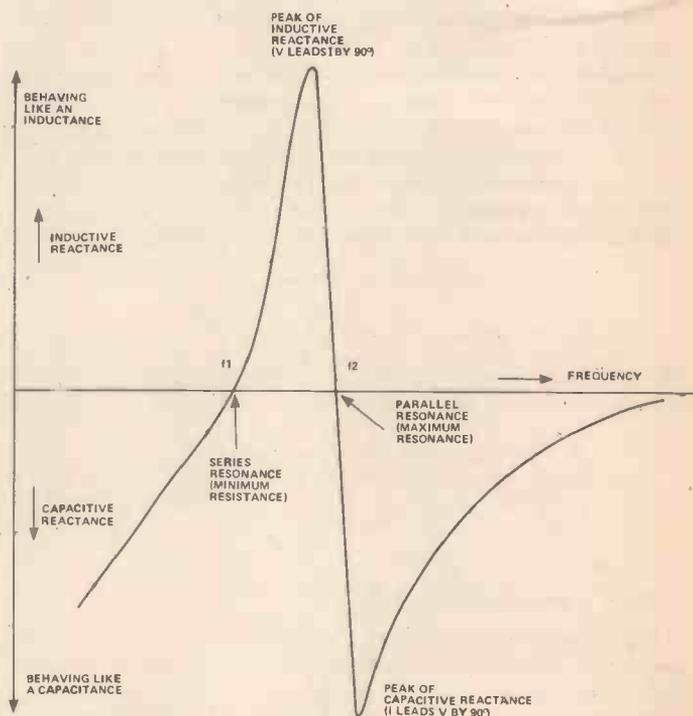

**Fig. 7. Electrical behaviour of a crystal. At low frequencies, the crystal behaves like a capacitance, with its reactance decreasing until it reaches zero at  $f_1$ , the frequency of series resonance. Just about this frequency, the crystal behaves like an inductor, reaching a peak of reactance which then reduces to zero again at  $f_2$ , the frequency of parallel resonance. The crystal then behaves like a capacitor again, with a peak of reactance occurring before the normal capacitor reactance curve is resumed.**

The familiar piezoelectric gas lighter is yet another example of these crystals in use. A barium zirconate crystal can give an enormous voltage, 20kV or more, when it is hit hard enough. These gas lighters pull a hammerhead back against a spring and then suddenly release the lot on the unsuspecting crystal. Result is a sudden pulse of voltage, enough to produce a spark across a gap. Sparks, squeaks and squeezes; they're all part of the piezoelectric story!

HE

# Letters

## CB for the Elderly

I'm coming up to 79 years of age, and was a ham in the 20's—2LO days. Your expose re CB is of vital interest to me, having fallen on hard times. No, I am not asking for a handout — just technical help — so here goes. I am a disabled person with invalid carriage, trying to live on Soc Sec. I live in a block of holiday flats, so have no neighbours with a phone — the nearest is ¼ mile away, if it's not vandalised.

I have my own phone now purely to call the doctor or clinic, or for any other emergency help. Now, I have just paid my phone bill — £25 for six months! I have to go without a lot to pay this, no daily paper, or television or cinema, etc etc.

Can I build some sort of a rig to contact someone somewhere! I had visions of contacting the AA, police, ambulance service, or even the fire

brigade, just to pass on a message, but of course this is out! Mine is certainly a case for CB.

F. E. W., Bridport

## Freebies

If any educational authority or club has need of electronic and electro-mechanical devices including two record decks, I would be glad to let them go for free as long as they are collected.

My phone number is 01-455 0540 and I can be contacted between 17:30 and 18:30 most evenings.

David St George, G4 IOY

## Photomultiplier warning

I am sure that your articles on NBTV have aroused a lot of interest so this information should be of use to your readers, and could save them expense and disappointment.

You mentioned the use of photomultipliers but state that they are expensive. One company advertises these as "G31A Photo Multiplier in stainless steel container with window and built-in resistor network £2 each". This would seem very attractive and would suggest that the devices only need a power supply to be put to immediate use. In the case of the two I bought, this would have meant immediate destruction of the power supply, for the gel in which the whole thing is potted was saturated with electrolyte from the capacitors in the unit (the aluminium cans of these being corroded right through). I thus decided to dismember one of these in order to extract the G31A, which is the important part. The G31A was "soft". Examination of the other unit through the window proved it to be in the same useless condition.

J. G., Calne, Wilts.

# computing today

THE JULY ISSUE  
WILL BE ON SALE  
JUNE 13th

## UART PROJECT

This month we present a companion board to the popular modem project with our UART board. Simple, powerful and flexible were the requirements and that's exactly what it is — so if you have interfacing problems connect to the next issue.

## COMPUCOLOR REPORT

The Compucolor II never really took off in this country despite the glowing reviews it received. As a colour graphics machine it offers a variety of functions that are both unique and powerful and our users report contains a detailed discourse in the machines defence. It also provides an interesting insight into the problems that can occur when you try and order machines from abroad, caveat emptor has seldom been more applicable!

## MAILING LIST PROGRAM

Is your tongue fed up with sticking all those stamps, envelopes and things? Use CTs mailing list implementation as the basis for your small business, office, club, user group etc etc and save your secretary that feeling of "gummy tongue".

## TAKE A TEST

Computerisation and the classroom are thorny subjects but there is a real and ready-made application in the multiple choice type of exam. Our regular contributor, A.P. Stephenson, presents his ideas and programs on this subject. Book your classroom micro for a test with next months educational CT.

## HEX A TRUSTY 80

Are you hexed about Hex? Do you know what to do with it when you've got it? Read how one of our readers struggled through the Hex jungle and emerged triumphant with the knowledge. Seriously though, if you are having problems understanding how to link machine code routines to BASIC programs then this is a must for you. TRS-80 owners are advised to queue for this issue as it is going to be much in demand!

The items mentioned here are those planned but unforeseen circumstances may affect the actual contents

# BARGAIN CORNER

Show us that you could have purchased for less within one month of your purchase and we will refund the difference!

## MULTIMETERS:



● **DT 1314 A** superb 38 range meter. Special features include 50K $\Omega$ /VDC movement, 10 amp DC Scale, resistance up to 100 M $\Omega$ , 2 ranges for testing batteries, long extraflex leads, batteries included. Usually sold for £35. **FOR LIMITED PERIOD £25 + 70p post.**



● **DT1004 20** K $\Omega$ /VDC movement, 16 ranges and off position, mirror scale, protected movement, battery included. Usually sold for £16, our price £12 + 70p post.

## CAR AUDIO:



● **New Model Stereo Cassette/Radio M.W.**, stereo FM and stereo cassette player. 8 Watts per channel, fast forward and autostop, includes fitting kit and **FREE SPEAKERS**. Sold elsewhere for up to £85 (believe it or not). Our price £45 + £1.40 post. (For negative earth cars only).

● **End of line clearance** LW/MW stereo cassette players. 8 watts per channel. Fast forward and autostop, usually sold for between £45 and £65. Limited number at £34 + £1.20 post. (For negative earth only). Manual car radios 5 watts, includes fitting kit and speaker. Neg. or pos. earth. £9 + £1.20 post.



## METAL DETECTORS:


● **Induction Balance Model.** Highly sensitive model with speaker and meter, 7-inch search head and telescopic stem. Usually sold for £39.95. Our price £24.50 + £1.20 post.

● **BFO Model** Due to importer clearing stocks we can offer this standard model for the incredible price of £11.50 + £1.20 post.

All goods guaranteed one year. 10 day money back offer on all undamaged goods. Goods ex-stock at time of going to press. Send S.A.E. for details.

**MINIKITS ELECTRONICS LTD**  
HOBBY  
84 HAINAULT ROAD  
LEYTONSTONE  
LONDON E11 1EH

# Beasties

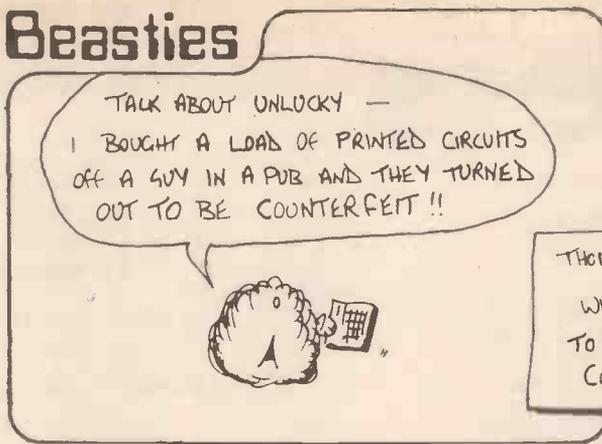

THOUGHT FOR THE MONTH: -  
WHAT DID BUREAUCRATS HAVE TO BLAME THINGS ON BEFORE COMPUTERS WERE INVENTED?



A. 80

## NEWS

# ETI NEXT MONTH

ON SALE JULY 4th

## 100W MOSFET Amplifier

Yet another in the long line of top line audio projects from ETI. Next month we give you a 100 + 100W power amp with bargraph output display, separate PSUs for each channel and a brilliant sound that puts this unit at the very top end of audio today. You will find it costs a lot less than you think to build, too.

## Electromagnetic Pulse Effect.

Never heard of it eh? Most people haven't — yet EMP could be the deciding factor in a nations fight for survival during nuclear attack. With the international situation steadily worsening around us, the facts ETI has turned up about Britain's susceptibility to EMP are very, very disturbing and make mandatory reading for anyone concerned with keeping civilisation alive in the age of the Bomb!

As an indication of the situation, did you know that in 1958 a small warhead test in the Johnstone Islands produced power systems failure in Hawaii, SOME 1000 KM FROM THE EXPLOSION, due to EMP? (The British Isles are approx. 800 km in length).

## Video Today — And Tomorrow

Next month ETI takes a detailed look at the expanding world of home video and offers a buyers guide to inform the intending purchaser. In addition we have a look at the next 12 months from Richard Dean (editor — TV and Home Video) — probably the leading writer in the field today.

## Circuits Appetiser

How many times have you glanced at book titles all neatly aligned on a shelf and wondered just how interesting they really are? Well, as of next month maybe we can help. "110 Timer Circuits for the Home Constructor" has just been released by Newnes and ETI is publishing a chapter from it next month. Circuits galore and full details of this very nifty little volume. It is hoped that more books will receive this treatment in the future.

## Projects, Projects, Projects, Projects.

In addition to that truly amazing MOSFET AMPLIFIER we have a further four constructional projects for you next month. There is an excellent VCA module which fits in with Project 80 if you're following it. Also we give full details of an ULTRASONIC BURGLAR ALARM which could ensure than any visitors you get are at least invited. Two test gear "quickness" are featured in the shape of a LINEAR CAPACITANCE METER with good accuracy and easy construction and a very versatile LOGIC PROBE to allow you to hunt out those missing bits. With all this how can you possibly not buy ETI next month?

Articles mentioned herein are in an advanced state of preparation, however, circumstances may dictate charges to the final contents.

# New from Newnes Technical Books

## Beginner's Guide to Digital Electronics

Ian Sinclair

Digital electronics affects us all — pocket calculators, digital watches, T.V. games, microprocessors and computers all make use of digital technology. This book provides a readable introduction to the methods, circuits and applications of digital electronics, with practical hints and exercises.

1980                      192 pages                      0 408 00449 5  
£3.25                      US\$7.50

## Electronics — Build & Learn

R A Penfold


An introduction to basic electronics theory for beginners by means of practical experiments: 'learning by doing'. Full instructions are given for building a circuit demonstrator unit; electronics components are then described one by one and used in simple circuits that can be set up on the unit. This is an ideal first book for hobbyists.

1980                      112 pages                      0 408 00454 1  
£2.80                      US\$6.50


**Newnes Technical Books**  
Borough Green, Sevenoaks, Kent TN15 8PH
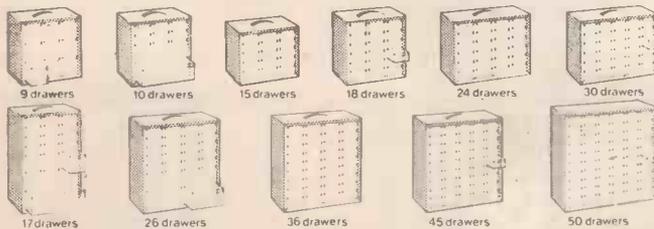
## Akro-Mils offer a new and improved range of low cost-high value storage organisers in steel frame cabinets.

These eleven storage cabinets come wrapped in an eye catching full colour presentation sleeve each individually illustrated. The cabinets are of hard wearing steel frame design in a bright blue metallic finish. They are made to stack together or be wall mounted and ten are fitted with an unbreakable carrying handle. The drawers of transparent crystal styrene are in various arrangements of four sizes shown below. These cabinets for their quality of construction and presentation are very competitively priced indeed. Write now to AKRO-MILS for colour brochure and full details.



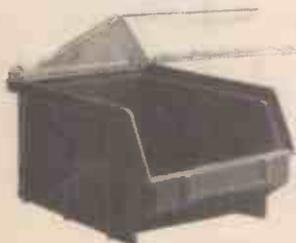These cabinets will fulfil a multitude of small part storage requirements in the Home, Office and Workshop.



## AKRO-MILS **STORABIN**

A wall hung storage system for the safe keeping of all small parts. They are made in two sizes and are of high-impact polystyrene with transparent hinged lids. They come packed in tens complete with hanging rails and illustrated label.



For full details of these and other products, write now or phone



AKRO-MILS (U.K.) LTD. LEWCOS INDUSTRIAL ESTATE, 210, CHURCH RD. LEYTON, LONDON E10 7JH. TELEPHONE: 01-558 1203 4 5

# Hazard Flasher

*The HE Hazard Warning Indicator lets you flash around the streets. Adapt your car lighting system with it.*

IF YOUR CAR does not feature hazard warning indicators, then this project is for you. It can replace the existing indicator control, still providing the normal indicator functions but giving the added bonus of hazard control, where all four indicator bulbs are illuminated simultaneously.

With the connection of a small 64 ohm impedance speaker an audible warning can be obtained, to warn the driver that the indicator lights are flashing. The frequency of this tone changes when in the hazard mode so that the driver can instantly tell that the feature is operational. Also the standard dash board lamp can be controlled by the unit giving a visual indication of operation.

A single IC does the majority of the work, controlling the rate at which the lights are illuminated, and the frequency of the audible tone. Power Darlington transistors are used as high current electronic switches and the whole circuit is mounted on a small neat printed circuit board which can be fitted either straight under the dash or inside a small case. Personal choice decides the latter.

The existing indicator switch in the steering column should be adaptable into the circuit without problem and the only item extra to the circuit will be the hazard ON/OFF switch itself, which you can mount virtually anywhere.


## CONSTRUCTION

Absolutely nothing special in construction here, apart from the two power transistors. As they tend to run warm they need a substantial heatsink (we used the diecast metal box in which the project was mounted).






The transistors can be mounted on the underside of the board with the leads bent up and carefully soldered on. We have used this method of construction before and it provides a useful way of heatsinking the transistors while holding the board steady. Heat sink compound and insulating washers must, however, be used to insulate the transistors from the case.

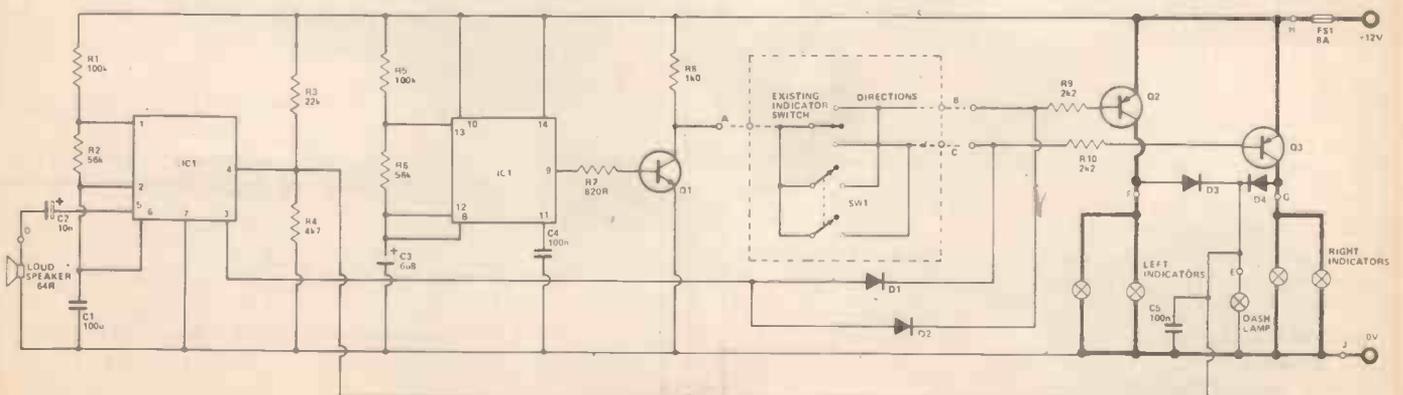If you wish, the case can be primed and painted with aerosol sprays, but this is really not essential as the unit will probably be fitted behind the dashboard and therefore will be out of sight.



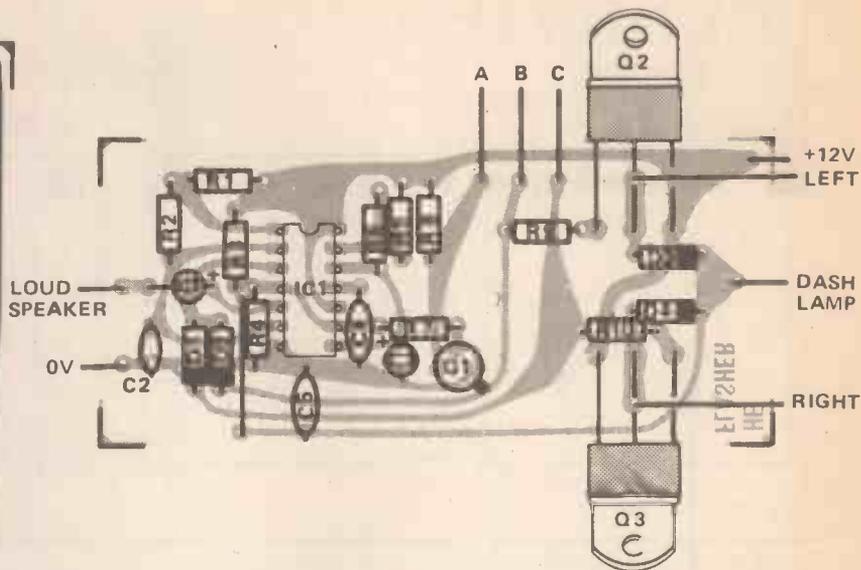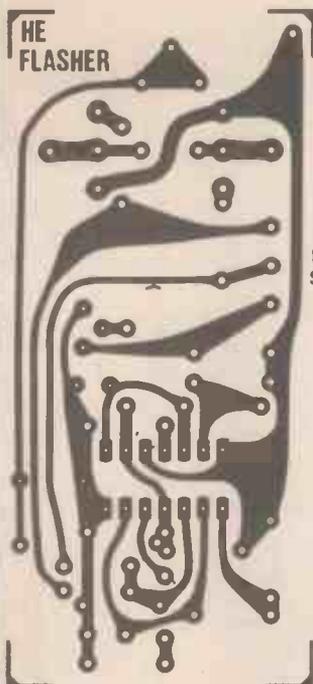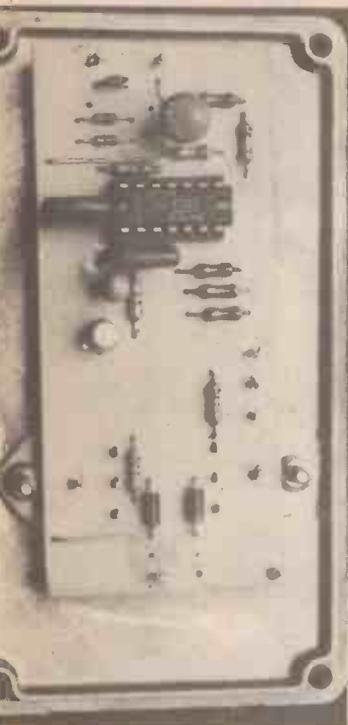Above: Full circuit diagram of the Hazard Flasher unit.



Above: The Flasher installed on the lid of a diecast box.

Right: Component overlay for the Hazard Flasher.

'Crimp-on-connectors' provide the easiest method of connection to the car electrical circuit, but remember in the positive power supply line to include an in-line fuseholder and 8 A fuse.

HE

## How it Works

The second half of IC1, a dual 555 type timer IC is connected as an astable multivibrator, oscillating at approximately 1Hz.

Q2 and 3 form the power switches necessary to turn the indicator bulbs on and off and are power Darlington transistors. The heavy current path is shown on the circuit diagram as thick black lines.

The transistors are turned on and off by the pulse from the astable oscillator coupled through either the existing indicator switch (which turns either Q2 or Q3 on and off) or the hazard switch which turns both Q2 and Q3 on and off.

The dash board indicator lamp is illuminated via current D3 and/or D4 whenever either of the transistors Q2 or Q3 turn on.

The first half of IC1 is an astable running at an audio frequency variable by the control voltage at pin 3, which is taken from Q2 and 3 bases via D1 and D2. These two diodes control the voltage at pin 3, such that with only one power transistor on the multivibrator has a higher frequency than when both transistors are on. A different tone is therefore obtained for the hazard flasher and the individual direction indicator.

Finally, the astable is enabled by the voltage across the dashboard light — when the lamp is on i.e. when a voltage appears across it, pin 4 of IC1 is taken high which turns on the astable.

## Parts List

### RESISTORS (All 1/4W, 5%)

R1, 5	100k
R2, 6	56k
R3	22k
R4	4k7
R7	820R
R8	1k
R9, 10	2k2

### CAPACITORS

C1	10u 16V Tantalum
C2	10n Ceramic
C3	6u8 16V Tantalum
C4, 5	100n Polyester

### SEMICONDUCTORS







IC1	556
Q1	BC 109
Q2, 3	TIP 146
D1, 2	1N 4148
D3, 4	1N 4001

### MISCELLANEOUS

64 ohm miniature loudspeaker, in-line fuseholder + 8A fuse, SW1 DPST toggle switch, diecast box 4 1/2" x 2 1/2" x 1 1/4"
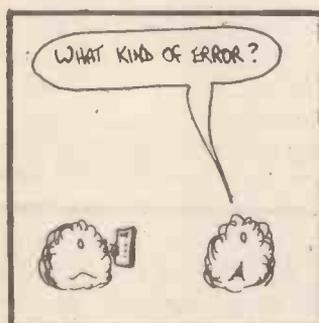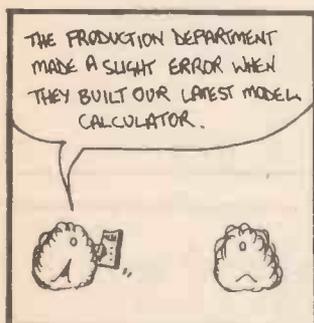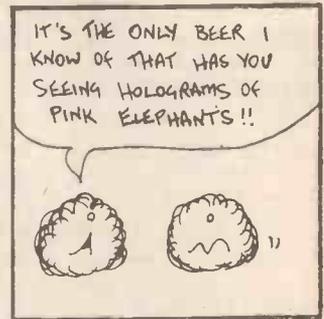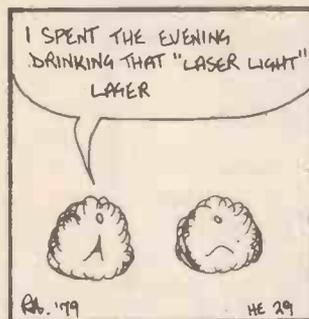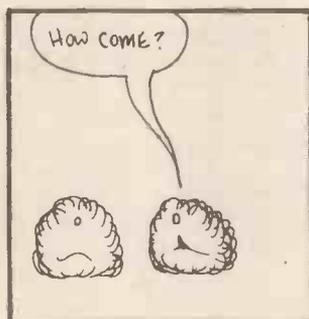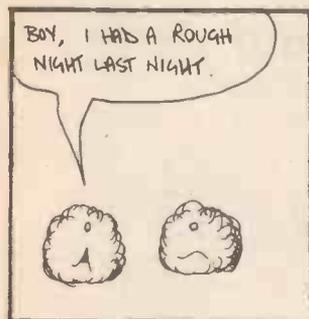
## Buylines

We can't foresee any problems in obtaining the components for this project. The usual mail order companies advertising in this issue should have all of the components even if your local stockist hasn't.



## Card Frames

vero  
vero



Our 19" Card frame will house your projects in a 'professional' manner. It is designed to take Eurocards or Modules and offers facilities for interconnection through 2 - part DIN 41612 or direct edge connectors.

A full range of compatible items are available — all selected from the established range of industrial products — boards, accessories, cases etc. Just send 40p. and we'll send you our catalogue by return — it's got the lot!

VERO ELECTRONICS LTD RETAIL DEPT.  
Industrial Estate, Chandler's Ford,  
Hampshire SO5 3ZR  
Tel: (04215) 62829



# Backnumbers

June 79 Vol 1 No 8

**PROJECTS:** GSR Monitor, Envelope Generator, Drill Speed Controller.

**FEATURES:** Citizens Banned, Display Techniques, Electronics in Music.

July 79 Vol 1 No 9

**PROJECTS:** Shark, Baby Alarm, Points Controller, Linear Scale Ohmmeter.

**FEATURES:** Cassette decks and tapes, Binary Numbers, Fixed Resistors.

August 79 Vol 1 No 10

**PROJECTS:** Home Security System, LED Tacho, Injector/Tracer, CV Amp.

**FEATURES:** Security Installation, Variable Resistors, Tools, Satellite Power.

September 79 Vol 1 No 11

**PROJECTS:** Combination Lock, Light Dimmer, Starburst, Ultra Switch.

**FEATURES:** Electronic Timekeeping, Thyristors, Radio Control, FET Special.

October 79 Vol 1 No 12

**PROJECTS:** Tantrum, Hobbytune, Analogue Frequency Meter, Multi-Siren.

**FEATURES:** Home Computing, Electronic Games, Microwave Cooking.

December 79 Vol 2 No 2

**PROJECTS:** Scalextric Controller, Ring Modulator, Bar Graph Voltmeter, HEBOT III.

**FEATURES:** TV Receivers, Project Fault Finding, Data Supplement.

January 80 Vol 2 No 3

**PROJECTS:** HEBOT III, Crosshatch Digi-Die.

**FEATURES:** Mini TV Survey CMOS Special, Spacelab.

February 80 Vol 2 No 4

**PROJECTS:** Passionmeter, Infra-Red Remote Control, Win Indicator.

**FEATURES:** Short Circuit Special, KEZY Does it, Power to the People.

March 80 Vol 2 No 5

**PROJECTS:** SW Radio, 25 Watt Module, PSU Module, Touch Switch.

**FEATURES:** Electronics on Wheels, PETting it Together.

April 80 Vol 2 No 6

**PROJECTS:** Hobbycom, CD Ignition, R/C Motor Controller, Frequency Meter.

**FEATURES:** NBTV, Solar Cells, Into Constructional Electronics.

Shown here are all of the back issues currently available. Each issue costs £1.00. (Surface mail anywhere in the world) Please specify the

Volume and issue number you require on the coupon below and send it, together with your remittance to:

Sales Office (Backnumbers), 145 Charing Cross Road, London WC2H 0EE

# Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately twelve issues and is attractively bound and blocked with the HOBBY ELECTRONICS logo.

Price U.K. £3.95 including postage, packing and VAT, overseas orders add 30p. Why not place your order now and send the completed coupon below with remittance to:-

EASIBIND LTD., 4, UXBRIDGE STREET, LONDON W8 7SX

Please allow 3/4 weeks for fulfillment of order.

it's easy with **EASIBIND**

Easibind Ltd., 4 Uxbridge St., London, W8 7SZ.

Nat. Giro No. 5157552.

## Order Form

HOBBY ELECTRONICS

I enclose p.o./cheque value .....

for ..... binders

Years required .....

**BLOCK LETTERS PLEASE**

Name .....

Address .....

.....

Date .....

Registration No. 307469.



# Hobbyprints

\*Please Note. Print N is in two parts.  
(a) All projects except HEBOT.  
(b) HEBOT. (a) is 95 pence,  
(b) is 45 pence.

Print O is in two parts.  
(a) Lap Counter and PSU.  
(b) Digi-Die, HEBOT Loop Drive, Crosshatch Gen.

NOV 78	A 95 pence	MAY 79	G 95 pence	NOV 79	M 95 pence
DEC 78	B 95 pence	JUN 79	H 95 pence	DEC 79	N * (see note)
JAN 79	C 95 pence	JUL 79	I 95 pence	JAN 80	O * (see note)
FEB 79	D 95 pence	AUG 79	J 95 pence	FEB 80	P 95 pence
MAR 79	E 95 pence	SEP 79	K 95 pence	MAR 80	Q 95 pence
APR 79	F 95 pence	OCT 79	L £1.20	APR 80	R 95 pence

HOBBYPRINTS are the easiest way to make perfect PCBs every time. Simply place the transfer sheet over a cleaned, sized piece of PCB material and transfer the design by gently rubbing with a soft pencil. Once the pattern is safely in place immerse the board in a solution of Ferric Chloride. From beginning to end should take no more than 15 minutes.

To order your HOBBYPRINTS write the appropriate code letter in the coupon below and send it, together with your remittance, to:

Sales Office (HOBBYPRINTS), 145 Charing Cross Road, London WC2H 0EE.

## BACKNUMBERS

Please supply the following Backnumber(s) .....

Enclosed £ .....

Name .....

Address .....

## HOBBYPRINTS

Please supply me with Hobbyprint(s) .....

Make sure  
of your  
Heathkit  
catalogue...  
write now.



Keep up to date with the world's finest electronic kits—with the Heathkit catalogue. 48 product packed pages contain photographs and specifications of the widest possible range of kits. Everything from doorbells to digital clocks, multimeters to microcomputers.

Heathkit make it easy to build, easy on your pocket, and, as with 13 million Heathkit builders over 34 years, your success is guaranteed.

Make sure of your copy of the Heathkit catalogue. Send the coupon today, plus 25p in stamps and beat the demand.

To: Heath Electronics (U.K.) Limited, Dept (HE 7)  
Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue.

I enclose 25p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_

Soldering  
Iron offer  
FREE

N.B. If you are already on the Heathkit mailing list you will automatically receive a copy of the Heathkit catalogue without having to use this coupon. When you receive your catalogue you will get details of this free offer.

**HEATHKIT** HEATH  
ZENITH

### IONISER KIT

The Ioniser produces large quantities of negative ions in the air which many people find stimulating and refreshing. Price £10. Accessories and a case can be supplied as an optional extra £8.


### H.E. KITS

Crosshatch Generator .....  
Jan 80 £11.25  
Digi-Die ..... Jan 80 £5.50  
Passionmeter Feb 80 £5.00  
Infra-red Remote Control  
..... Feb 80 £19.35  
Electronic Ignition .....  
April 80 £18.25  
Microbe June '80 P.O.A.  
Metranome June '80 P.O.A.  
Egg Timer June '80 P.O.A.  
2 watt Amplifier .....  
June 80 P.O.A.  
Foghorn June '80 P.O.A.

### JAY KIT DM-2
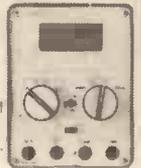
#### DIGITAL MULTIMETER

DC Volts ..... 1mV to 1000V  
Ac Volts 1V to 500V  
DC Current ..... 0.1mA to 0.2A  
Resistance 1 to 20M  
3 1/2 digit LCD  
Auto low battery indication.  
Auto Polarity and Zero  
1% accuracy (DC volts)  
Designed around Intersil 7106C  
Includes cabinet and all parts



£27.30

P&P £1.00 Add 15% VAT.

Hobbcom ..... April 80 £28.60  
Digital Frequency Meter .....  
£27.75  
R/C Speed Controller .....  
April 80 £9.60  
Kits supplied with PCB and  
case.  
Miniclock ..... May 80 P.O.A.  
5080 Preamp .....  
May 80 P.O.A.  
Track Cleaner May 80 P.O.A.

Callers please ring first to check availability of kits.

C.B. C.B. C.B. Enthusiasts please let us know the I.C.'s, Transistors, etc., that you require.

Orders. Please add 30p post and packing. Add 15% V.A.T. on total order.


## T. POWELL

306 St. Paul's Road, Highbury Corner, London, N.1  
Telephone: 01-226 1489

ACCESS / VISA ACCEPTED

Shop open: Mon. to Fri. 9-5.30; Sat. 9-4.30

### STEREO FUNCTION MODULE CP-FG1

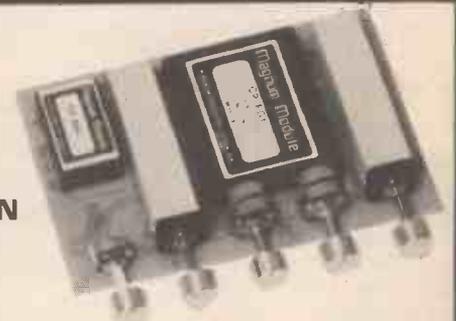

For comprehensive hi and lo filtering and control of stereo separation (image width) mount a CP-FG1, 2 switches and 3 pots on a Magnum CP-MPC2 Interconnection Board. This fully encapsulated function module incorporates some unique features. Two stereo filters ("rumble" and "hiss") are provided, each with its own slope control and choice of three cut-off frequencies. Stereo separation control allows variation of the apparent image width to suit listening conditions — if you can't place your speaker where it really ought to be, let the CP-FG1 do it for you! All modules are, of course, available separately — Magnum boards aren't essential but coupled with their specially designed P.C. mounting pots and switches, they are an easy way to build the system of your choice.

CP-FG1—£13.55 inc. (U.K.) £15.55 inc. (Export).

Also available: Pre-Amplifiers, Filters, Power Amplifiers, Peak Programme Monitors, Compressor/Expander Active Crossovers, Power Supplies, plus all pots, switches, etc.

## MAGNUM AUDIO Ltd.

DEPT. HE7, 13 HAZLEBURY CRESCENT  
LUTON, BEDS. LU1 1DF  
TELEPHONE: 0582 28887  
SEND LARGE SAE FOR DETAILS

# Into Electronics Construction

## PART 6

BY IAN SINCLAIR

*All good things come to an end. Ian Sinclair ties up a few loose ends this month with some hints on fault-finding and a look at an amplifier circuit.*

WE'VE COME QUITE A LONG WAY since we started this series, assuming at the start that you didn't know a resistor from a capacitor and had never put a circuit together. This is the last part of this series, and it's a good opportunity to tidy up a bit, and deal with some things which had been left aside earlier. We're still keeping to the idea that this is a series for the apprentice constructor, but a bit of knowledge of theory is now the most pressing item on the list, because without it you're eternally stuck with other people's circuits and no idea what to do if things go wrong.

One of the most useful bits of electrical theory is Ohm's Law — it's simple to remember and simple to use, yet it's quite incredibly valuable to us. To understand it properly, though, we have to be very clear about what happens in an electrical circuit, so pin your eyebrows up and take this lot on board.

### OHM TRUTHS

An electrical circuit is a load of connections which allow electric current to flow in a complete loop, ending up where it started. There also has to be something which causes the electric current to flow, something which pushes it along. That something, as far as our circuits are concerned will be a battery or a mains power supply unit.

How much current will flow when we connect a battery into a circuit? That depends on two quantities — the voltage generated by the battery (often referred to in textbooks as the EMF, Electromotive Force) and the resistance of the circuit. The voltage of the battery is printed on it — 9 V or 6 V for the batteries we've used in this series, for example. The resistance of the whole circuit will be a quantity which can be measured in units called ohms, or if the resistance is large in units of kilohms. The kilohm or k is just 1000 ohms, and we use k in place of ohms just to avoid having to work with large numbers. Now we can answer the question of how much current flows — it's equal to the battery voltage divided by the total circuit resistance. If we used ohms as a measure of resistance, the current will be a number of amperes (amps); if we used kilohms to measure resistance, the current will be a number of milliamps. The milliamp (mA) is one thousandth of the amp or  $10^{-3}$ A. Most electronic circuits have high resistances and use low amounts of current, so that these units of kilohms

and milliamps are more common than the ohms and amps we would use in large-scale electrical circuits. What we've used here is one form of Ohm's Law, which can be written as —

$$\text{current in mA} = \frac{\text{voltage in Volts}}{\text{resistance in k}}$$

For example, if we have 9 V across a 6k8 resistor (value 6.8k, remember) then the current is

$$\frac{9}{6.8},$$

which is around 1.32mA.

That's not the end of it, though. Suppose we know, by measurement, how much current a circuit takes, and we also know the battery voltage. We can use these two bits of information to find out what the resistance of the circuit is — it's simply:

$$\frac{\text{voltage of battery}}{\text{current}}$$

If, as usual, we know the battery voltage in units of volts and the circuit current in milliamps, then the value of resistance we calculate is in kilohms. For example, using a 6 V battery and measuring a 4mA current means that the resistance of our circuit is

$$\frac{6 \text{ V}}{4 \text{ mA}}$$

= 1.5k or 1k5.

There's a third form of the law. Suppose we have a supply whose voltage is *not* known, but we know the circuit resistance (in k) and the current (in mA) which flows. We can then calculate what the voltage is — it's equal to current x resistance. For example, if a current of 2.5mA flows through a 3k resistance; then the voltage which is pushing it is  $3 \times 2.5 = 7.5$  V. Easy really.

One very old-fashioned way of remembering these effects is to use letters to represent the quantities: V for voltage, R for resistance and I for current, and then we can write Ohm's law in the form of equations:

$$I = V/R$$

$$R = V/I$$

$V = R \cdot I$  — and Fig. 6.1 shows a method which countless generations of apprentices have used to help them remember which way round the equations go. 



Fig. 6.1 The ancient and extremely useful method of remembering Ohm's law.

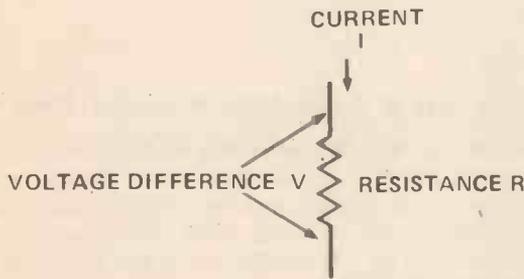


Fig. 6.2 A voltage difference caused by a current flowing through a resistor.

## ODD OHMS

Now that's just one use of Ohm's law — relating the voltage of a battery to the current it causes in a circuit — but it applies equally well to any part of a circuit. Suppose we have a resistor which is part of a circuit, as shown in Fig. 6.2. If there's a current flowing through this resistor, then there's a voltage across it, and the voltage just has to be equal to current x resistance. If for example, we have a 2k $\Omega$  resistor with 2 mA flowing through it, then there's a voltage difference of  $2.2 \times 2 = 4.4$  V across the resistor. Why should there be a voltage? This is a resistor, after all, not a battery! The answer is that this is a bit of the battery voltage being used to force current through this resistor. If we didn't have this voltage, there wouldn't be any current. Ohm's law applies exactly to all the resistors in a circuit — if you find that your measurements don't agree with the theory, then it's likely that your measurements are wrong!

There's one very important part of an electronic circuit which doesn't obey Ohm's law, though, and that's the transistor itself, along with its close relative, the diode. The voltage between the collector and emitter of a transistor doesn't have much relation to the current which flows between these points, because the current between collector and emitter is controlled by the base current. Similarly, the voltage between the base and the emitter is almost constant while the transistor is passing current, something between 0.5 V and 0.6 V most of the time, even when the current varies by quite a bit. Definitely not according to the ways of Ohm sweet Ohm! By using Ohm's law for the resistors, though, and what we know of how transistors behave, we can sort out circuits which are misbehaving, so that you now have as much theory as you're going to need for quite a time. What you need now for trouble shooting exercises is some way of measuring these important quantities, voltage and current, and that brings us to meters and measurements.

## TEST GEAR

If you're serious about this electronics business, if the smell of hot solder had got to you, if it's not good enough just to build one bit every year, then its odds on you're going to be able to make use of a meter. Now you have to be a bit fussy about what sort of meter you buy. Don't for example, be tempted by some of the 'bargain offers' which you see in the advertising pages of papers. These things may be fine for measuring the voltages of a car battery, but they're useless for any sort of electronics circuit apart from the old fashioned valve-operated radios of many years ago. What you have to look for is a device described as a multimeter, and which has a 'figure-of-merit' of *at least* 10000 ohms per volt. Don't let anyone mystify you by talking of the dozens of ranges on the meter he's trying to sell you — your concern is for the ohms per volt figure. Even if every knob is gold plated and it comes with a thousand year guarantee, it's no use if its ohms per volt is less than 10000 and nowadays, 20000 is a much more useful figure. Why? Well, this figure of merit measures how much resistance the meter itself has when you're using it to measure voltages. If the meter has too low a resistance, then it's going to cause quite a large change in the circuit when you connect it, and it certainly won't give you much of a clue about what voltage was there *before* you connected it. It's better to have a good quality meter with 20000 ohms per volt and only a few ranges than one with 5000 ohms per volt, dozens of ranges, flashing dials and an instruction book in Russian/Chinese/Turkish/Finnish.

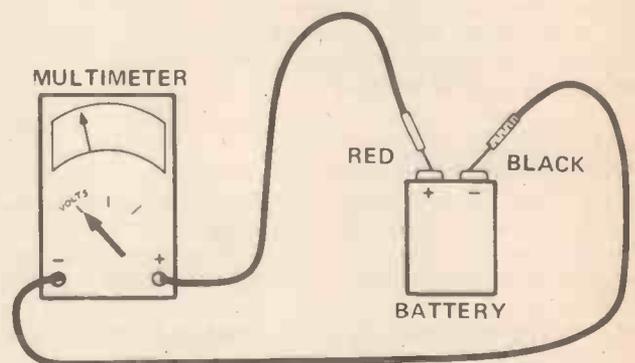


Fig. 6.3 Measuring a battery voltage. The meter must be set to a VOLTAGE range high enough to cope with the battery voltage.

How exactly can you make use of such a meter? Let's start by looking at how you connect a meter in circuit — then we'll see why! The most useful scales are the voltage scales, mainly because they're simple to use. Most circuits have the negative line of the battery connected to all the circuit metal work — it's then called the earth line. If you clip the negative lead from the meter to this earth line or to battery negative if the circuit has no metalwork around it, then you can measure every voltage in the circuit. Start with the battery voltage itself — if the battery is reasonably fresh, then the battery voltage should be pretty close to the voltage which is marked on the battery — 6 V for a PP1, 9 V for a PP9. If the battery is getting near to the end of its life, though, this voltage may be quite a bit lower, especially when the battery is delivering current to a circuit. If you find that

# Into Electronics Construction

your battery voltage shoots down when the circuit is switched on, then it's time to renew the battery — a good rule of thumb is to renew a 6 V battery when it reads 4.5 V and renew a 9 V battery when it reads 6 V. Incidentally, if you take the battery out and measure its voltage you'll usually find that it looks quite normal — a duff battery in its early stages shows up only when it's in circuit and passing current.

## MEASUREMENTS

You can do a lot more with a multimeter than just checking batteries, though, you can check every part of a circuit. Suppose you have the situation, which every constructor has to face at some time or another, of a circuit which you've built which simply doesn't work. How do you go about getting it to work? The hard way, of course, is to check every part of the circuit, looking for bad soldered joints, wrong connections, open circuits but that won't find a faulty component for you. The satisfactory method is to make intelligent use of a meter to indicate what's wrong. It's a skill which you learn mainly by experience, but here are a few hints for the sort of battery-operated circuits we've been building.

First of all, if you've just connected up a battery to find that nothing happens, check the battery voltage. Switch the multimeter selector switch to a DC voltage range which is higher than the normal battery voltage (for example, the 12 V range for checking 9 V or 6 V batteries), then clip the negative lead to battery negative and the positive lead to battery positive. Take the voltage reading with the battery also connected to the circuit. If the voltage looks too low, you need a new battery. Make sure that you're reading the right scale — obviously if you've set the range switch to 12 V, then you should be reading on a scale which is marked from zero to 12 — it looks obvious but a lot of people don't seem to realise this!

If the battery voltage looks OK, then check the current which the circuit is drawing. This is quite a different type of reading which needs a different sort of connection. Remove the positive lead which runs from the circuit to the battery, and connect the positive lead of the meter to the battery positive terminal. Now switch the meter to its highest current range, which is usually several amps,

Fig. 6.4 Measuring the amount of current that a circuit takes.


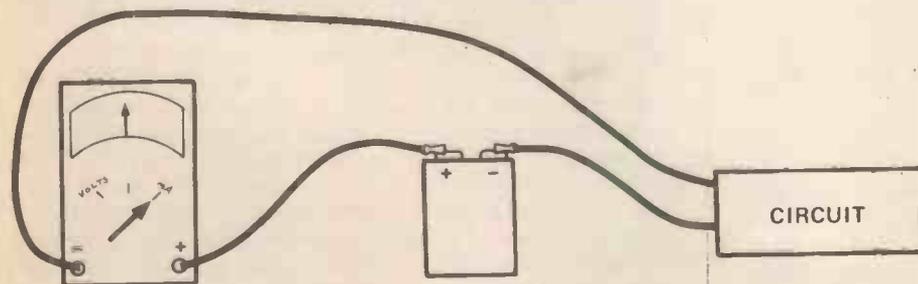



Fig. 6.5 Where to measure the collector voltage of a transistor. The meter must be switched to a voltage range as high as that used for measuring battery voltage.

and connect the positive lead from the circuit to the meter negative lead. This makes the meter part of the circuit. Your circuit probably takes very little current, so that the amount hardly shows on the largest current range, but if you now switch one at a time, to the lower current ranges, you should find a reading in one range. If the current reading is zero or very small, then there's something missing — the circuit isn't conducting. Either some connections are not properly connected, or a transistor is not conducting — you'll have to check or make further tests to find out which; but at least you have some clue as to what you're looking for.

Suppose everything's OK so far, but the circuit still doesn't work! Put it back the way it was, and prepare the meter for making voltage readings again. That means switch back to the voltage scale you used for reading the battery voltage, and clip the meter negative lead to the battery negative lead. You can now use the meter positive lead to measure voltages in each part of the circuit, and the most obvious places to start with are the transistors. Start by measuring the collector voltages. If the collector voltage of a transistor is about equal to the battery positive voltage, then it's certain that transistor isn't conducting. On the other hand, if the collector voltage of the transistor is so low that it hardly causes the needle of the meter to move, then the transistor is conducting all right, it's conducting so well that it has hardly any resistance. Now compare these discoveries with a description of what the circuit ought to be doing — should we have any transistors cut off, or conducting hard (bottomed)? Once again, the meter has indicated where to check.

It doesn't, of course, tell us why these transistors are cut-off or bottomed, and the next step is to check the voltage between the base of each transistor and its emitter. If each emitter is connected to battery negative, of course, you don't need to make any alterations; keep the meter negative lead fastened to battery negative. If the emitter connects to negative through a resistor, then you'll have to clip the meter negative to each emitter and then take a reading by connecting the meter positive to the base of each transistor, one at a time. For a transistor which is cut-off, the base-to-emitter voltage should be around 0.5 V or less. If your transistor is cut-off (no

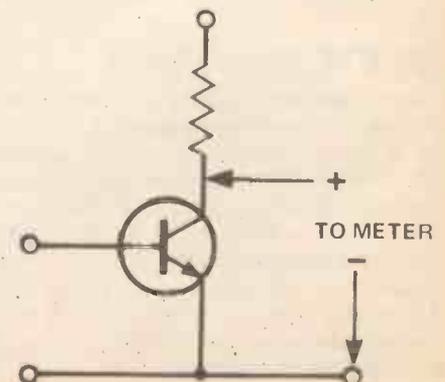

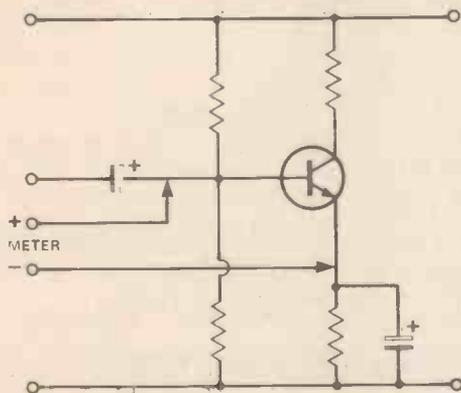


**Fig. 6.6** Measuring the voltage between base and emitter. A meter with a good "figure of merit" is needed for this measurement.

current flowing, collector voltage high) with a base emitter voltage of 0.6 V or more than it looks suspiciously like a duff transistor you've got there. On the other hand, if you have a transistor which is bottomed, and yet its base-to-emitter voltage is less than 0.5 V, that's another indication of a fault — a different type of fault to be sure, but one which is equally effective at stopping the transistor from working. It's at times like this when you find that you've put the transistor in the wrong way round, and what you thought was the collector is in fact the emitter or the base.

These simple tests take you a long way in checking out the non-worker, and by experience you will soon learn to spot signs of faults. Several circuits, for example, show what the 'normal' voltage at each point should be, so that by checking each of the voltages — nearly always measured with the meter negative connected to battery negative — you can see if there's one which is way out. Small differences (except between emitter and base) don't usually matter too much, they're caused by the tolerances of components values. A 10k resistor, for example, can have a true value anywhere between 8k and 12k, so that circuits which use several resistors can often have voltage readings which differ quite a bit between one sample of the circuit and another. The big differences, more than 20%, usually indicate a fault somewhere, though, and this sort of voltage reading exercise is a very valuable method of fault-finding.

## AWKWARD AMPS

Just to end with, we're going practical again. There's one type of circuit we haven't looked at up till now, and that's a voltage amplifier — the sort of circuit you might use between a microphone and a cassette recorder, for example, to boost the performance of the microphone. The reason we've left it is that the amplifier circuit doesn't have an action which can be made visible — it doesn't flash lights — and it's not nearly so easy to check that it's working correctly. The best method, in fact, is by taking voltage measurements, and we may have to make some adjustments to the circuit to get it operating correctly.

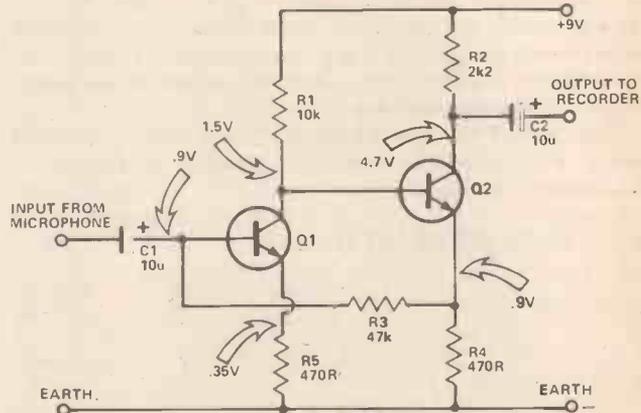

**Fig. 6.7** The amplifier circuit. The figures in circles are the "design voltages" for the circuit; actual readings should not be too greatly different.

The circuit is shown in Fig. 6.7. This is a type of amplifier which is called a voltage amplifier, because its job is to make a copy of a signal but with a greater voltage. A signal, as far as an amplifier like this is concerned, is a continual cycle of change of voltage, going from zero to some positive voltage, back to zero, then to a negative voltage and back to zero again. The frequency of such a signal is equal to the number of these complete cycles of change which take place in a second. The amplitude of the signal is the maximum voltage it reaches on each side of zero.

Where do we get these signal voltages from? We get them when we convert any varying quantities into an electrical signal. A microphone, for example, converts sound waves into signals of this sort, and we also get these signals from recordings, using pickup cartridges or tape-heads. A TV camera converts pictures into electrical signals which are a lot more complicated than the simple signals we get from microphones, but the idea of the signal is the same. Amplifying a signal means making a larger-scale copy of the signal, with more volts, but at the same frequency. Very often this amplification mustn't change the shape of the signal — a graph of signal voltage plotted against time should look the same for the output signal as it does for the input. If this is so, then the amplifier gets the name of a linear amplifier; if it doesn't then the amplifier is distorting the signal.

In the circuit shown in Fig. 6.7 two transistors, both NPN types are used. Each of these has to have bias voltage at its base — enough to keep the transistor conducting, but not so much that the transistor is bottomed. Why? Because the signal will cause the voltage at the base of the first transistor to change, up and down as the signal voltage changes — if the transistor cuts off or bottoms, then its output voltage can't be an exact copy of the input.

The important bias component of the amplifier in Fig. 6.7 is the resistor R3, and this one may have to be altered to make the amplifier bias correct, because we can't select exactly what transistors or other components we shall use. Let's take a close look at the circuit.

The signal comes in from the microphone at C1. This signal is very small, less than a millivolt, which is why it

# Into Electronics Construction

needs to be amplified. We need the capacitor because the microphone mustn't have any DC across its terminals, but the transistor must, and the capacitor separates the two — it lets signal voltages through, but it prevents direct current from flowing out of the amplifier circuit into the microphone.

The base of the first transistor has a current flowing into it through R3, from the emitter of Q2. This arrangement is deliberate, it's a type of circuit arrangement called feedback bias, and it causes enough current to flow in Q1 to keep the collector voltage of Q1 pretty low, around 1.5 V. It's that potential divider type of circuit in action again. The collector of Q1 is connected directly to the base of Q2, so that this part is also at 1.5 V DC. Note that these are the steady voltages, before any signal voltage exists. With 1.5 V on the base of Q2, the emitter has to be at a voltage of around 0.9 to 1.0 V — and that in turn keeps current flowing into the base of Q1.

The arrangement keeps itself self-adjusting providing that the correct values are used in the first place. Imagine, for example, what happens if the voltage at the base of Q1 went down. Q1 would conduct less well, so the voltage at its collector would rise. Because the base of Q2 is connected to the collector of Q1, the base voltage and the emitter voltage (0.5 V or so between them, remember) of Q2 would rise — and now more current would flow through R3, causing the base voltage of Q1 to rise again. This sort of self-correcting circuit is what we mean by negative feedback — it's a phrase you will keep coming across in this electronics business.

The negative feedback keeps the bias currents flowing correctly in each of the transistors, then, even if resistor values change, or transistors are replaced. The only thing we have to be sure of is that the circuit is correct in the first place. The circuit of Fig. 6.7 has been designed so that it should automatically be correct, and if you have no meters you'll simply have to take it on trust. If you have a meter, though, measure the voltage at the collector of Q2, with the negative lead of the meter connected to battery negative. This voltage should be somewhere around 4.7 V — that was the 'target' voltage at the design stage. As long as the voltage is between 4.0 and 5.5 the circuit will work reasonably well.

Now what happens when a signal from a microphone is connected into C1? The tiny signal voltage, one millivolt or so causes the voltage at the base of Q1 to vary, a millivolt or so up and a millivolt or so down. This variation makes the current between collector and emitter vary, and so causes the collector voltage to rise and fall in sympathy. At the collector, though, the rise and fall of voltage is several times as great as that at the input.

This is an amplified signal, and it's also affecting the base of Q2. Here again we have the same process, causing the current of Q2 to rise and fall (much more than that of Q1) and so causing a signal voltage at the collector of Q2. This signal voltage can pass through C2, though direct current can't, so that we can connect other circuits to the output at C2 without disturbing the steady voltage on the collector of Q2. The amount of gain from the circuit as it's shown isn't very good, less than a hundred times, but it's quite adequate to make a very noticeable difference when it's connected between a microphone and another unit, such as the input of a

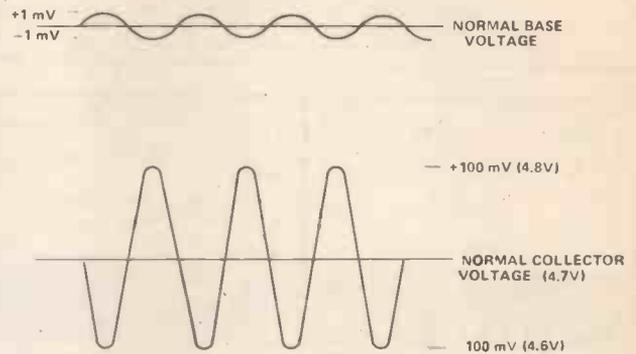


Fig. 6.8 The action of the amplifier. The wave at the output of the amplifier is an enlarged copy of the wave at the input.

cassette recorder (remember that an earth connection is also needed — no one-wire connections if you please!)

To get a much larger value of gain, there's just one very simple modification — connect a 220 $\mu$ F 6 V (or more) capacitor across R4, with its positive terminal towards the emitter of Q2. This will now give you a lot of gain — probably more than you can handle!


## AND FINALLY . . .

And now it's farewell. In these six parts we've tried to give you an entry into the fascinating world of electronics' construction, and also some idea of how much more there is waiting for you when you begin to understand what it's all about. Where do you go from here? There's the book "Into Electronics" for starters, which is the next step on in electronics circuit theory, and then the other follow-ups of the Into-series. After that — it's up to you. By that time you'll probably have decided that your interests lie in one particular branch of electronics, and you'll be looking for the more specialised titles in the HE list. One thing is sure — you'll find all you need in these pages!

See you next month with a new series.

HE

## Beasties

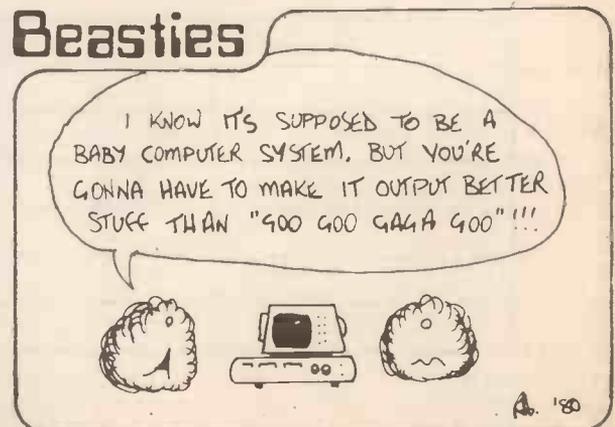



## BUZZERS 12v ELECTRONIC


Typical 85db, 30 mA. Operate down to less than 6 volts.  
80p each + 20p p.p. post free over £5.

### HAMCAM LTD.

Millsborough House, Millsboro Road, Redditch,  
Worcs. Tel: Redditch 67932

If it's a case of making your project  
look good, then use one of ours.

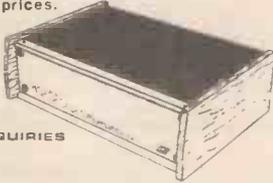Simply send a S.A.E. for  
Details and prices.



TRADE ENQUIRIES  
INVITED.

### H.M. ELECTRONICS

271a/275a Fulwood Road,  
Broomhill  
Sheffield S10 3BD

**TOP QUALITY PRE-RECORDED VIDEO-  
CASSETTES**, the latest films, free lists. From  
half recommended price. Write now for de-  
tails, AUSHE, 76 Church Street, Larkhall,  
Lanarkshire.

**CHEAPER THAN A VISIT TO THE PIC-  
TURES.** Latest top quality films prerecorded  
on videocassettes from only £6. Full details  
from G.T. Technical Video Library (10a HE),  
119 Oxford Street, London W1R 1PA.

**£5 OSCILLOSCOPE.** Standard Junk Box  
Components plus approx. another £5 (total  
components approx. £12). This unit plugs  
into TV Aerial socket and converts TV to  
Oscilloscope. Circuit and plans £3. Kerr, 27,  
Coles Road, Milton, Cambridge, CB4 4BL.

**AERIAL BOOSTERS** improve weak VHF  
radio and television reception, price £6. SAE  
for leaflets. Electronic Mail Order Ltd., 62  
Bridge Street, Ramsbottom, Bury, Lancashire  
BLO 9AGP.

## BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED LED DIGITAL ALARM CLOCKS



(1) (2) (3)

Returned to Service Department within guarantee  
period.

- (1) With alarm repeat — S.R.S.P. of £17.00 offered at  
£3.95 inc. VAT.
- (2) With luxury lamp and repeat alarm as featured in  
most major U.K. Mail Order catalogues, S.R.S.P.  
£31.00—offered at £7.95 inc. V.A.T.
- (3) With integral luxury light and repeat alarm also as  
featured in most major U.K. Mail Order catalogues.  
S.R.S.P. of £32.00—offered at £7.45 inc. V.A.T.

These will be sold as received from our customers with  
the existing fault(s) and without guarantee.

UK ONLY

Discounts available on large bulk purchases

**PRESCOTT CLOCK AND  
WATCH COMPANY LIMITED**

Prescott House, Humber Road, London NW2 6ER

**12 BAND PATHFINDER RADIOS**, with  
HF 530KHz to 30MHz, VHF 66 to 174MHz,  
UHF 430 to 470MHz, AM, FM, LSB, USB,  
CW, Reception, RF Gain, Squelch, Controls,  
Tuning Meter, mains, battery, 12VDC opera-  
tion. £139 inclusive. PLH Electronics, 20  
Vallis Road, Frome, Somerset. Tel: (0373)  
61831.

**INTRODUCTION TO MICROPROCES-  
SORS.** A beginners book £2.30. Popular  
Electronic Projects £1.45. Single IC Projects  
£1.50. 28 Tested Transistor Projects £1.25.  
Add 35p p&p. — Educational Data & Techni-  
cal Services, 59 Station Road, Cogenhoe,  
Northampton NN7 1LU.

### MEMORY MART

'UK 101' 'Superboard' 4K RAM ..... £30 each  
Memory Expansion ..... £3.75 each  
2114 1Kx 450 small ns ..... £5.00 each  
2708 UV prom 650 small ns

P&P 20p  
C.O.D. 60p extra

### MEMORY MART

19 Weatherby Gardens  
Hartley Wintney, Hants

**BACK ISSUES!** Hobby and Electronics  
magazines. Bought/sold/exchanged. State  
requirements and request quotation.  
Denstone Educational Publications, 1 Water-  
foot Avenue, Southport PR8 3TE.

## MULTIPLEX

### RECHARGEABLE NICAD BATTERIES

4000 mAh size D £2.60 inc. VAT  
(Normal price £3.34 inc. VAT)  
1200 mAh size sub C £1.60 inc. VAT  
500 mAh size AA pen cells £1.05 inc.  
VAT.

Post & carriage extra

Minimat Technical LTD

55 Cornwall Street Birmingham B3 2DH

Tel 021-236-1328

Dealers Enquiries invited

**ELECTRONIC SYSTEMS ADVANCED  
LEVEL G.C.E.?** Join south east London  
School sixth form. Full range advanced level  
courses available. Details: 01-692 1803.  
Mornington Road, London, SE8 4BL.

**FREE 1980 Amtron catalogue** with new range of  
kits and equipment cabinets. Send s.a.e Amtron  
UK Ltd., 7 Hughenden Road, Hastings, Sussex  
TN34 3TG. Tel. Hastings 436004.

**ELECTRONICS.** Learn an interesting hobby,  
cheaply and with full practical back-up.  
Taught as a hobby not as a career and tailored  
to suit each person's needs with specialist  
courses for the more advanced, e.g. Com-  
puters. S.a.e. for full details to: Teach-a-  
tronics, 100 Quarry Street, Woolton, Liver-  
pool 25.

## RECHARGEABLE BATTERIES

TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE. S.A.E. FOR LISTS. £1.45 for Booklet. "Nickel  
Cadmium Power" plus Catalogue. Write or call: Sandwell Plant Ltd., 2  
Union Drive, BOLDMERE, SUTTON COLDFIELD, WEST MIDLANDS.  
021-354 9764, or see them at TLC, 32 Cravens Street, Charing Cross,  
London, W.C.2.

## PRINTED CIRCUITS and HARDWARE

Comprehensive range Constructors Hardware  
and accessories.

Selected range of popular components  
Full range of HE printed circuit boards  
normally ex-stock same day despatch at  
competitive prices  
P.C Boards to individual designs  
Resist-coated epoxy glass laminate for the  
diy man with full processing instructions (no  
unusual chemicals required)

Allfac range of etch resist transfers, and other  
drawing materials for p.c boards

Send 15p for catalogue.

### RAMAR CONSTRUCTOR SERVICES

MASONS ROAD  
STRATFORD-ON-AVON  
WARWICKS, Tel. 4879

## AD INDEX

AKRO-MILS .....	61	MINIKITS .....	60
AMBIT INTERNATIONAL .....	2	MOBILE STEREO .....	49
ARROW AUDIO CENTRE .....	72	MURA ELECTRONICS .....	50
BI-PAK SEMICONDUCTORS .....	27	NIC MODELS .....	52
BK ELECTRONICS .....	45	T. POWELL .....	66
B.N.R.S. ....	45	POWERTRAN COMPUTERS .....	75
BUTTERWORTHS .....	61	J. W. RIMMER .....	72
C.B. CITY .....	52	SPARES 'N' REPAIRS .....	50
C.S.C. ....	33	SRU AUTOS .....	53
DAVID GEORGE SALES .....	36	C. N. STEVENSON .....	13
E.D.A. ....	43	SWANLEY ELECTRONICS .....	72
HEATH ELECTRONICS .....	66	SYMBOLYKA .....	51
HENRY'S RADIO .....	44	TECHNOMATIC .....	14
ILP .....	4 & 5	TEMPUS .....	9
MAGNUM AUDIO .....	66	TK ELECTRONICS .....	42
MAPLIN .....	76	T.V.E.S. LTD. ....	55
MARSHALLS .....	44	VERO .....	64
METAC .....	22	WATFORD ELECTRONICS .....	7
MIDLAND TRADING CO. ....	34	WINTJOY LTD. ....	40 & 55

# Books from the HE Book Service

## 28 Tested Transistor Project

Richard Torrens. The projects can be split down into simple building blocks which can be recombined for ideas of your own.

**Electronic Projects for Beginners** £1.65  
F. G. Rayer. Divided into 'No Soldering Projects', Radio and Audio Frequency, Power Supplies and Miscellaneous.

**Practical Electronic Calculations and Formulae** £2.55  
F. A. Wilson. A valuable reference for the home and laboratory, containing all the most frequently used, and some of the less well-known electronic formulae and calculations.

**Popular Electronic Projects** £1.75  
R. A. Penfold. A collection of the most popular types of circuits and projects using modern, inexpensive and freely available components.

## POPULAR ELECTRONICS BOOKS

Sinclair, I. R., *Introducing Electronic Systems* £1.95  
Sinclair, I. R., *Introducing Amateur Electronics* £1.65  
Sinclair, I. R., *Electronic Fault Diagnosis* £3.55  
Sinclair, I. R., *Repairing Pocket Transistor Radios* £2.60  
Sinclair, I. R., *Oscilloscope In Use* £3.10  
Sinclair, I. R., *Understanding Electronic Components* £4.20  
Sinclair, I. R., *Understanding Electronic Circuits* £4.20  
Kitchen, H. T., *Handtools For Electronic Workshop* £2.95  
Kitchen, H. T., *Electronic Test Equipment* £5.20  
Capel, V., *How To Build Electronic Kits* £2.35  
Darr, J., *How to test almost everything electronic* £3.70  
Brown, R. M., *How to read electronic circuit diagrams* £5.60

## AUDIO

Earl, J., *Audio Technicians Bench Manual* £3.70  
Earl, J., *Pickups and Loud Speakers* £3.70  
Earl, J., *Tuners and Amplifiers* £3.20  
Earl, J., *Cassette Tape Recorders* £5.40  
Earl, J., *ABC of Hi-Fi* £4.35  
Capel, V., *Microphones In Action* £3.15

## Digital IC Equivalents and Pin Connections

Adrian Michaels. Covers most popular types and gives details of packaging, families, functions, country of origin and manufacturer.

**Radio Stations Guide** £1.75  
B. Babani and M. Jay. An invaluable aid to everyone with a radio receiver helping them to obtain maximum entertainment, value and enjoyment from their set.

**IC 555 Project** £2.05  
E. A. Parr. Circuits are given for the car, model railways, alarms and noise makers. Also covers the related devices 556, 55B and 559.

**Second Book of CMOS IC Projects** £1.80  
R. A. Penfold. Following in the success of the original CMOS projects book we present the second volume covering all aspects of CMOS technology from multivibrators to triggering devices.

Capel, V., *Improving Your Hi-Fi* £3.65  
Capel, V., *Creative Tape Recording* £4.20  
Hellyer, H. W., *Tape Recorders* £4.45  
Sinclair, I. R., *Audio Amplifiers For Home Construction* £2.85

## RADIO CONTROL

Drake, J., *Radio Controlled Helicopter Models* £4.20  
Jeffries, C. R., *Radio Control For Model Yachts* £3.85  
Safford, E. L., *Radio Control Manual* £2.60

## COOKBOOKS

Tracton, K., *BASIC Cookbook* £4.10  
Lancaster, D., *TTL Cookbook* £7.00  
Lancaster, D., *RTL Cookbook* £4.65  
Lancaster, D., *CMOS Cookbook* £8.20  
Jong, W., *IC Op Amp Cookbook* £10.00  
Lancaster, D., *T.V. Typewriter Cookbook* £7.75  
Lancaster, D., *Cheap Video Cookbook* £7.00  
Jong, W., *IC Timer Cookbook* £7.50  
Lancaster, D., *Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business)* £4.95

## Electronic Security Devices

R. A. Penfold. Full of constructional circuits covering the most basic security systems to the Ultrasonic and Doppler Shift systems

## How To Build Your Own Solid State Oscilloscope

F. G. Rayer. The book contains concise practical instructions so that even an inexperienced hobbyist can construct a fairly sophisticated instrument with the minimum of difficulty and expense.

**50 FET (Field Effect Transistor) Project** £1.55  
F. G. Rayer. Contains something of interest for every class of enthusiast. Short Wave Listener, Radio Amateur, Experimenter or audio devotee.

**Linear IC Equivalents and Pin Connections** £3.10  
Adrian Michaels. Gives most essential data for popular devices.

## QUESTIONS AND ANSWERS SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.

Coker, A. J., *Q & A On Electric Motors* £1.90  
Hellyer, H., *Q & A On Radios and T.V.* £1.90  
Hibberd, R., *Q & A On Integrated Circuits* £1.90  
Jackson, K., *Q & A On Electricity* £1.90  
Brown, C., *Q & A On Hi-Fi* £1.90  
Brown, C., *Q & A On Transistors* £1.90  
Brown, C., *Q & A On Electronics* £1.90  
Reddihough, J., *Q & A On Colour T.V.* £1.90  
Miller, H., *Q & A On Electric Wiring* £1.90

## CONSTRUCTOR GUIDES

Graham, P., *Simple Circuit Building* £2.70  
Colwell, M., *Electronic Diagrams* £2.70  
Colwell, M., *Electronic Components* £2.70  
Colwell, M., *Printed Circuit Assembly* £2.70  
Ainslee, A., *Practical Electronic Project Building* £2.70  
Colwell, M., *Project Planning and Building* £2.70

## BEGINNER'S GUIDE

Sinclair, I. R., *Beginner's Guide To Tape Recording* £3.45

## Essential Theory for the Electronics Hobbyist

G. T. Rubaroe gives the hobbyist a background knowledge tailored to meet his specific needs.

## Beginners Guide to Building Electronic Projects

R. A. Penfold. Covers component identification, tools, soldering, constructional methods and examples of simple projects are given.

## 50 Projects using IC CA3130

R. A. Penfold. Describes audio projects, RF project, Test Equipment, Household and miscellaneous circuits.

## 50 Circuits Using 7400 Series ICs

R. N. Soar. The author has managed to compile no less than 50 interesting and useful circuits using this range of devices, covering many different aspects of electronics.

Sinclair, I. R., *Beginner's Guide To Integrated Circuits* £3.45  
Sinclair, I. R., *Beginner's Guide To Audio* £3.45  
King, G. J., *Beginner's Guide To Radio* £3.45  
King, G. J., *Beginner's Guide To Television* £3.45  
King, G. J., *Beginner's Guide To Colour T.V.* £3.45  
Guilou, F., *Beginner's Guide To Electric Wiring* £3.45

## PROJECT BOOKS

Marston, R. M., *110 Cosmos Digital IC Projects For The Home Constructor* £3.95  
Marston, R. M., *110 Wave Form Projects For The Home Constructor* £3.95  
Marston, R. M., *110 Op Amp Projects For The Home Constructor* £3.95  
Marston, R. M., *110 Semiconductor Projects For The Home Constructor* £3.95  
Marston, R. M., *110 Thyristor/SCR Projects For The Home Constructor* £3.95  
Marston, R. M., *110 Electronic Alarm Projects For The Home Constructor* £3.95  
Marston, R. M., *110 Integrated Circuits Projects For The Home Constructor* £3.95  
Marston, R. M., *20 Solid State Projects For The Car and Garage* £3.20  
Marston, R. M., *20 Solid State Projects For The Home* £3.20

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service  
Modmags Ltd  
145 Charing Cross Road  
London WC2H 0EE

\* Prices may be subject to change without notice.

# Chromatheque 5000

ETI 5 CHANNEL LIGHTING EFFECTS SYSTEM



Panel size 19.0" x 3.5". Depth 7.3"

This versatile system featured as a constructional article in *ELECTRONICS TODAY INTERNATIONAL* has 5 frequency channels with individual level controls on each channel. Control of the lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward.

Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!

COMPLETE KIT  
ONLY  
£49.50 + VAT

## BLACK HOLE

MUSIC EFFECTS DEVICE AS FEATURED IN  
*ELECTRONICS TODAY INTERNATIONAL*

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effects to be added. The device is floor standing with foot switch controls, LED effect selection indicators, has a variable sensitivity input, has high signal/noise ratio obtained by an audio compander and is mains powered — no batteries to change! Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.

COMPLETE KIT ONLY £49.80 + VAT (SINGLE DELAY LINE SYSTEM)

De Luxe version (dual delay line system) also available for £59.80 + VAT.




# POWERTRAN

**MANY MORE KITS!**  
including synthesizers, computer, hi-fi amps, tuners, etc.  
in our FREE CATALOGUE

## MPA 200

### 100 Watt Mixer-Amplifier

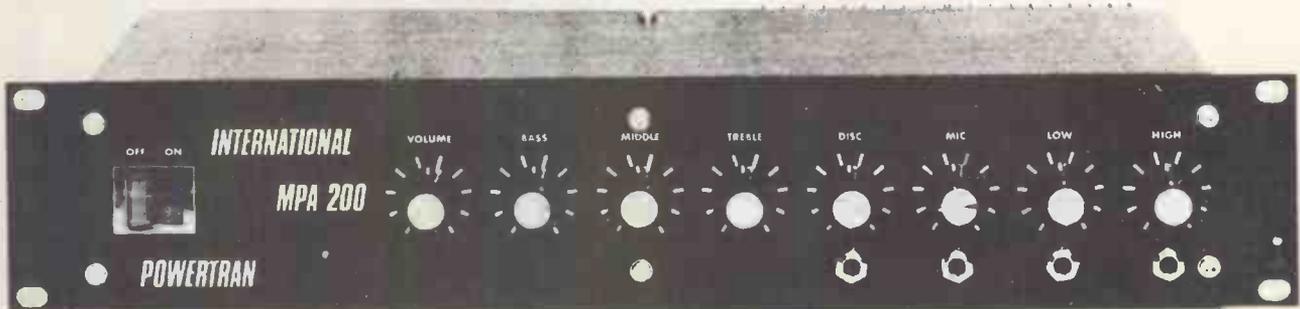

Panel size 19.0" x 3.5". Depth 7.3"

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, control, wire, etc. — complete down to the last nut and bolt.

COMPLETE KIT  
ONLY  
£49.90 + VAT

**PRICE STABILITY:** Order with confidence. Irrespective of any price changes we will honour all prices in this advertisement until August 31, 1980, if this month's advertisement is mentioned with your order. Errors and VAT rate changes excluded.

**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1 handling and documentation.

**U.K. ORDERS:** Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed.

**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.

**SALES COUNTER:** If you prefer to collect kit from the factory, call at Sales Counter. Open 9 a.m. - 12 noon — 1.4.30 p.m. Monday-Thursday.

OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

## POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3MM

ANDOVER  
(STD 0264) 64455

# STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

Send the coupon for your copy  
and **STEP UP TO  
MAPLIN SERVICE  
NOW**




Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

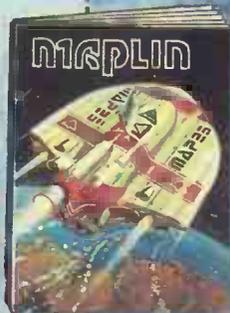

# MAPLIN

**ELECTRONIC SUPPLIES LTD**

All mail to:-

**P.O. Box 3, Rayleigh, Essex SS6 8LR.**

**Telephone: Southend (0702) 554155.**

**Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).**

**Telephone: Southend (0702) 554000.**