

**ELECTRONIC GAMES - 10 OF THE BEST**

# Hobby Electronics

**January '81**

ISSN 0142-6192

**55p**

**For A Down-To-Earth Approach To Electronics**



**COMPETITION**  
-WIN A  
ROWTRON  
PROGRAMMABLE  
TV GAME  
-SEE INSIDE

**DISCO LIGHTS**  
Build Our *SPECIAL*  
Sound-into-Light Project!

**Chuffer Sound Project**  
-bring your model  
trains alive

**Rev-counter**  
-put your car engine revs  
on display



# Ever wondered who buys electronics today? You'd be surprised!

The electronics market is rapidly expanding. Whether it's antique radio equipment, accessories or what have you, it's becoming increasingly difficult to keep up with the latest developments. Or to get them.

That's where we come in. We probably have just what you're looking for and a lot more besides. We stock all the top makes... at prices that will just make you love us. Simply phone, write or telex

WINTOY Ltd., 103 High Street, Shepperton, Middlesex TW17 9 BL, England, Tel. Walton-on-Thames (STD 09322) 48145 and find out.



Or just simply call us.



**TON AHLERS  
ELEKTRONIKA B.V.**

Aalsmeerderdijk 349, 1436 BH Rijnsenhout -  
Holland, tel. 010 31 2977-2 86 11 (4 lines),  
telex 15181 tonel nl. (near Schiphol Airport).

Even the old boys circuit is getting electronicized. With our help.

# Hobby Electronics

JANUARY 1981  
Vol. 3 No. 3

Editor: Hugh Davies  
Assistant Editor: Rick Maybury Editorial Assistant: Tina Boylan Project Editor: Keith Brindley  
Drawing Office Manager: Paul Edwards Group Art Editor: Paul Wilson-Patterson B.A.  
Managing Editor: Ron Harris B. Sc.




## PROJECTS

<b>SOUND-INTO-LIGHT CONVERTER</b> . . . . .	11
<i>Light fantastic?</i>	
<b>CAR REV COUNTER</b> . . . . .	27
<i>A revolutionary design</i>	
<b>BENCH AMPLIFIER</b> . . . . .	37
<i>A sound idea</i>	
<b>CAR SPEEDOMETER (PART 2)</b> . . . . .	42
<i>Digital speed</i>	
<b>NICAD CHARGER</b> . . . . .	50
<i>Versatile volts</i>	
<b>CHUFFER</b> . . . . .	54
<i>Soundly on track</i>	

## FEATURES

<b>MONITOR</b> . . . . .	6
<i>Latest news</i>	
<b>TEN OF THE BEST</b> . . . . .	19
<i>Ten electronic games</i>	
<b>COMPETITION</b> . . . . .	23
<i>Win a TV game</i>	
<b>WHAT'S IN A NAME</b> . . . . .	25
<i>Listen to this!</i>	
<b>O LEVEL Q &amp; A</b> . . . . .	32
<i>Study time again</i>	
<b>BUILDING SITE</b> . . . . .	39
<i>Do it properly</i>	
<b>INTO DIGITAL ELECTRONICS</b> . . . . .	45
<i>Count on it!</i>	
<b>INDEX VOLUME 2</b> . . . . .	52
<i>The year's here</i>	
<b>FREEDOM PHONE OFFER</b> . . . . .	58
<i>Cordless telephone</i>	
<b>BREAKER ONE FOUR</b> . . . . .	61
<i>CB 4 UK</i>	

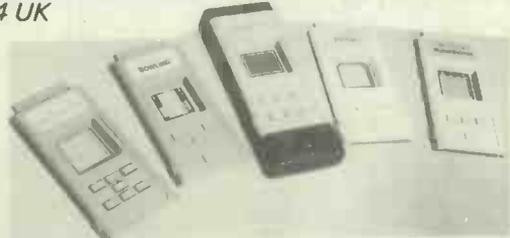

## NEWS & INFO

<b>HE Next Month</b> . . . . .	8
<b>ETI Next Month</b> . . . . .	56
<b>Citizens Band Magazine</b> . . . . .	60
<b>Hobbyprints</b> . . . . .	64
<b>PCB foil patterns</b> . . . . .	65
<b>Classified Ads</b> . . . . .	66

Advertisement Manager: Stephen Rowe Advertisement Representative: Roy Perryment  
Creative Director: Diego Rincón  
Managing Director: T. J. Connell

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.  
Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Published by Modmags Ltd. Distributed by Argus Distribution Ltd, 12-18 Paul St., London EC2A 4JS. Printed by QB Ltd., Colchester. Covers printed by Alabaster Passmore.

Copyright: All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing of kits of the projects must be sought from the Publisher. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally. ©Copyright 1980 Modmags Ltd ABC Member of Audit Bureau of Circulation.



**SIMPLY AHEAD**  
and staying there

# The range grows bigger... better...

## New Profile Amplifiers - Two New Series

### MOSFET


**CHOOSE AN I.L.P. MOSFET POWER AMP** when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETs, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02



### BIPOLAR

**CHOOSE AN I.L.P. BIPOLAR POWER AMP** where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple - via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£6.34 + 95p
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.24 + £1.09
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£15.20 + £2.28
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£18.44 + £2.77
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£27.68 + £4.15

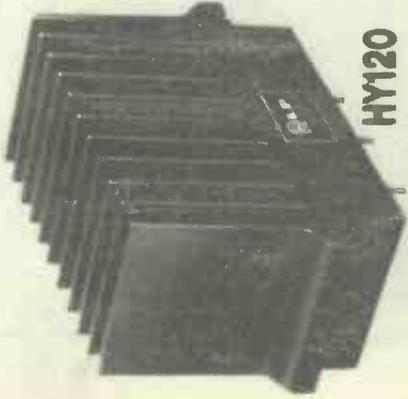


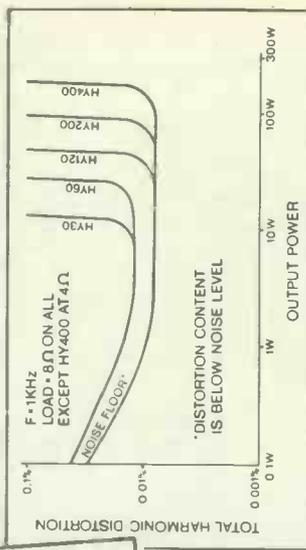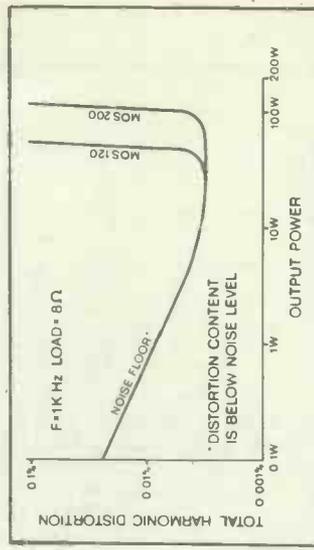**I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE**



Load impedance both models 40-∞ Input impedance both models 100KΩ  
Frequency response both models 15Hz-100KHz - 3dB

**THE NEW PROFILE EXTRUSIONS**  
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages. - Research shows they provide optimum thermal dissipation and stability. - Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. - Surfaces are matt black, anodised for lower thermal conductivity. - Extrusions vary in size according to module number.

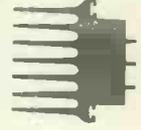

# NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide  $\pm 12$ dB cut and boost. Inputs Sensitivity - Mag. PU, -3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV. Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.


HY6 mono £5.60 + 84p VAT Connectors included

HY66 stereo £10.60 + £1.39 VAT Connectors included

B6 Mounting Board for one HY6 78p + 12p VAT

B66 Mounting Board for one HY66 99p + 15p VAT

COMPATIBLE WITH ALL ILP MODULES

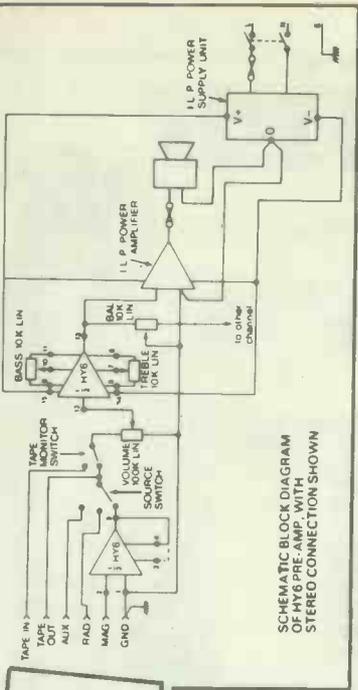

SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP WITH MAIN STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U., -68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY  $\pm 15$  to  $\pm 60$ v

# NEW POWER SUPPLY UNITS


Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembling buildings. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

- PSU30  $\pm 15$ V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS £8.10 + £1.22 VAT
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU36 for use with 1 or 2 HY30's £9.75 + £1.46 VAT
- PSU50 for use with 1 or 2 HY60's £9.75 + £1.46 VAT
- PSU60 for use with 1 HY120 £9.75 + £1.46 VAT
- PSU65 for use with 1 MOS120 £13.61 + £2.04 VAT
- PSU70 for use with 1 or 2 HY120's £13.61 + £2.04 VAT
- PSU75 for use with 1 or 2 MOS120 £13.61 + £2.04 VAT
- PSU90 for use with 1 HY200 £14.75 + £2.21 VAT
- PSU95 for use with 1 MOS200 £23.02 + £3.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £24.20 + £3.63 VAT
- PSU185 for use with 1 or 2 MOS200
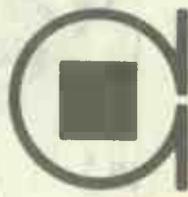
## ★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



# ELECTRONICS LTD.

FREEPOST 5 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.  
Telephone (0227) 54778 (Technical (0227) 64723) Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

# 1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.


# BRITAIN'S FASTEST GROWING MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD. CANTERBURY CT2 7EP

Please supply..... Total purchase price £.....  
 I enclose Cheque  Postal Orders  International Money Order   
 Please debit my Access/Barclaycard Account No.....

NAME.....  
 ADDRESS.....  
 Signature.....

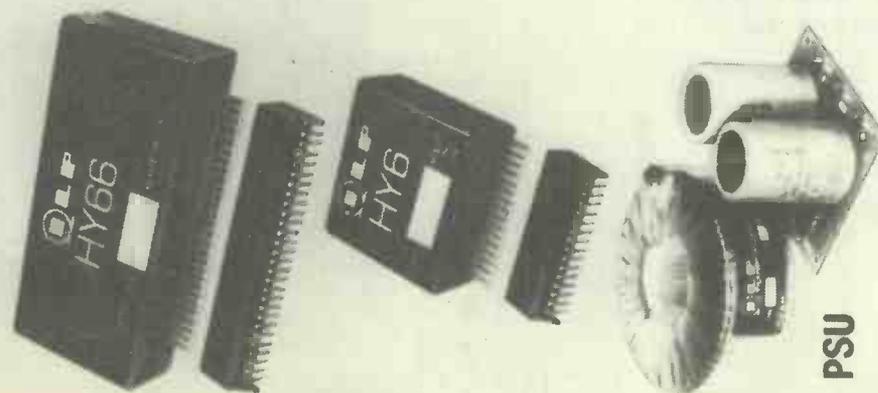NO QUIBBLE 5 YEAR GUARANTEE  
 7-DAY DESPATCH ON ALL ORDERS  
 BRITISH DESIGN AND MANUFACTURE  
 FREEPOST SERVICE



PSU

ALL U.K. ORDERS DESPATCHED FREEPOST

# EDITORIAL

# Monitor

**STEALTHILY**, over the last three months, changes have been taking place in Hobby Electronics. Some of these have been in response to comments from the many readers who took the trouble to fill in and return our Survey form (HE August 1980).

You will have noticed, no doubt, that the cover and Contents page haven't been spared: what about the magazine itself?

Judging by the response to our Survey — and the constant flow of letters that we receive — HE is meeting most of our readers' needs. But there's room for a few improvements and we've already started on these.

First the projects: we're aiming to make them more interesting and useful without at the same time making them *too* clever or *too* expensive. We'll try and keep the balance between simple projects for those starting from scratch to more expensive ones for our more experienced (or ambitious) readers. Whatever the project, we'll help you understand how it works and guide you on how to build it without getting submerged in technicalities.

Second the features: we'll try and dish up some interesting general articles for you and polish up some of the regular ones.

On some magazines the editorial staff sit in an ivory tower detached from their readers, apart from the odd letter of complaint. In the Modmags plastic tower in Charing Cross Road we're right in the middle of things and get plenty of support (and criticism) from our readers. The subject of electronics is exciting and an exciting part of an uncertain future. We aim to present this subject in a digestible form and make it an interesting and absorbing hobby for you.

As one of our readers in South Africa rounded off his letter to us recently, so I will end this Editorial:

Yours — in electronics  
Hugh Davies  
EDITOR


## Tiny Tape 11

Following our exclusive report last month on the amazing Technicolor miniature video cassette recorder we have news of yet another mini VCR, this time from Hitachi.

Unlike the Technicolor machine the Hitachi recorder is still experimental but it does have the advantage of having a video camera built-in to the case. This new machine has been provisionally called the MAG Camera and as you can see from the picture it's not much larger than an 8 mm camera.

The MAG uses  $\frac{1}{4}$ " tape in a compact cassette-type box, and we would hazard a guess that this is the same tape as used by the Technicolor machine which also uses compact cassette-sized tape units. Up to 2 hours recording time is available on this unit, and internal rechargeable batteries power both the recorder and solid-state camera. All-up weight of the unit is just 2.6 kg (5.7 lbs) which should prevent too much muscle strain.

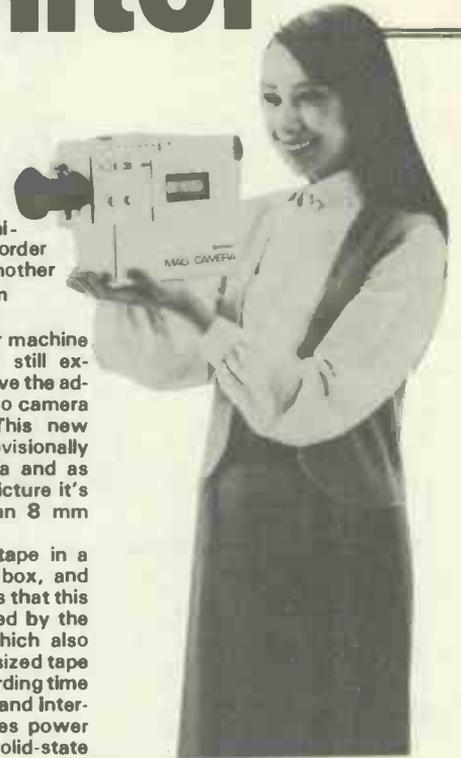As yet Hitachi haven't announced price or probable launch date: this they claim will not be until there have been some international agreements on standardisation. It would seem to us that the battle of the new formats is going to be as bloody as the one currently being waged over VHS and



Betamax. In the end no-one will win — it'll be the poor old consumer that has to make the unenviable choice of risking money on a system that might or might not become redundant. We just wish these companies would agree on standards before they launch their products and not wait until poor old Joe Public has spent his hard earned cash.

## And again . . .

This is getting monotonous. Here we have yet another tiny stereo cassette player, this time from Hanimex. You all know the score by now so we'll just content ourselves with the price, which is £39.95 and the name, which is HC 300S. At the moment there are around six or seven of these

little units on the market (or there will be in the very near future — in time for Christmas no doubt). We have yet to see one that rivals the Sony Stowaway, and certainly none sound as good. Watch this space: we'll tell you when we see one!

For more information contact Hanimex UK Ltd. Faraday Road, Dorcan, Swindon.





## CHEAP CHESS

If you've been holding back on buying a chess computer then now may be the time. We have been playing with the cheapest and neatest chess computer we've ever seen. It comes from an American company called Tryrom Inc and is called — rather uninspiringly — Electronic Chess Game. Our resident wizard reports that the game is every bit as good as

the current crop of chess machines costing up to £100. The machine has eight levels of difficulty ranging from beginner to expert. Facilities include position verification, automatic castling, change sides and piece selection. All of this is contained in a calculator-sized box with a small travelling set of magnetic chess pieces and a wooden chess board. Each game can commence with a number of classic openings or alternatively a random opening once your strategy has been decided.

Taken overall this is an excellent little machine and the incredibly low price of just £29.95 including board and pieces represents just about the best possible value for a chess computer. For more details of this machine and a fine selection of other games contact Kramer & Co., 9 October Place, Holders Hill Road, London NW4.

## Staggering Statistic

Have you ever wondered how many colour TV transmitters the BBC operate? No? Well, we'll tell you anyway, on the 7th of

November the BBC opened their one-thousandth transmitter at Hedlyhope in County Durham. Makes you think about the £34 licence, almost seems cheap doesn't it?

## Tune Your Guitar By Cassette

Our Guitar Tuner Project (HE November 1979, pp 61 to 62) inspired one company — Tutchings Electronics — to come up with what it claims to be the first guitar tuner on cassette tape in the world.

While our tuner produces six preset tones, each corresponding to the pitch of one of the guitar strings, this cassette, called simply 'Guitar Tuner', contains recordings of tones and string sounds for classical, acoustic, electric and 12-string instruments. According to Tutchings, most pupils find it difficult to tune up their guitars by simple tones, and prefer to hear the actual strings. The recordings are backed up by a string-by-string commentary.

Side one of the tape contains classical and acoustic sections, interspaced by what is described as: '... the frequency tone of the tuning A — 440 Hz — which lasts for 3½ minutes. The main purpose of this is to assist in finding the acoustic guitar section. It can, of course, also be used for tuning other instruments.'

For classical, acoustic and electric guitars you get a 10 second tone of each note, starting with the high E, followed by: '... the striking of each string four times

on an accurately tuned guitar'. Each section is repeated. Tuning for the 12-string guitar is more complicated, starting with 'first pair: D in unison' down to 'sixth pair: D covered ... now D covered, octave up'. A chord played on all strings is included at the end of each section.

We tested this cassette on a Phillips N2534 machine, and used the recordings to tune-up a classical guitar and an acoustic guitar. After the tune-up, both were checked against harmonic (open string) tuning, aided with an A (440 Hz) tuning fork. The check showed the tape method to be reasonably accurate, but it must be borne in mind that very few cassette players are capable of running precisely the same speed without some, however slight, 'wow' and 'flutter'. Such irregularities are usually imposed by the transport mechanism. (By the way, the continuous 440 Hz recorded tone was found useful for checking for such irregularities!)

Although not necessarily of hi-fi quality, the tape worked well as a tuning aid. We thought it ideal for the beginner, because most have difficulties with tuning-up (especially after fitting a new set of strings). Guitar Tuner costs £2.50 including post and packing, and is available from: Tutchings Electronics Ltd., 3 Grange Road, Bournemouth BH6 3NY

## TV Game In Court

An interesting story has been drifting across the Atlantic for the past few weeks. It concerns a number of disgruntled software engineers working for Atari. Apparently the gentlemen who used to write the games programs for Atari left the company some months ago to start a company of their own. They formed a small outfit called Activision, specifically to manufacture cartridges for the Atari TV game. Naturally Atari was a little bit unhappy about all this, after all it invented the Video Computer System and saw no reason why somebody else should move in on its territory, particularly ex-employees. Atari proceeded to slap a 20 million dollar lawsuit on Activision. Much of the legal wrangling centred on the name used for one of the cartridges which

had been registered by Atari. The fuss caused by the lawsuit has given Activision an immense amount of free publicity which helped its sales no end. Now it appears the Activision cartridges are soon to be sold on this side of the big pond. Already we have had a couple of samples in the HE offices. We can safely say that they are every bit as good as the original Atari cartridges. The fact they will cost about 20% less than comparable Atari cartridges will no doubt assure their popularity over here too. Currently there are four games available: Fishing Derby, Checkers, Boxing and Dragster. In the spring we can expect another two cartridges called Skiing and Bridge. Recommended retail price is likely to be around £16.95 each. It will no doubt comfort owners of Atari machines to know that the quality of these cartridges is such that Atari hasn't actually claimed that these new games will damage its machines. We wonder what will happen when they go on sale over here.



EXT MONTH. NEXT MONTH. NEXT MONTH. NEXT MONTH. NEXT MO

# Hobby Electronics

ON SALE JANUARY 16th

## First Report

Just hours before we went to press on this issue of Hobby Electronics the 1980 Breadboard Show opened its doors. We couldn't resist showing you a couple of pictures of the proceedings. Within minutes of the show opening hundreds of eager enthusiasts were milling around the dozens of stands crammed with electronic goodies. Look out for a full picture report next month, right here in Hobby Electronics.



Yes, that is Brian Rix (third from right) with Ron Harris (right) Editor ETI, Geoff Arnold (Editor PW), Mike Kennard (Editor EE) and Jim Connell (Managing Director Modmags)



You can't actually see it but there are some Space Invader machines on our stand drawing the crowds

## Doppler Burglar Alarm

No, it's not a special alarm system for doppler thieves but a highly-sensitive ultrasonic project which uses the doppler principle to detect moving objects entering a field of inaudible sound. It provides a low-cost method of home protection and has other interesting uses.

## High-impedance Voltmeter

Standard multimeters have a nasty habit of 'damping' high-impedance electronic circuits when you try to measure component voltages: the meter impedance is just too low. The meter in this project has an impedance in excess of 11 million ohms and will give a true reading of DC voltages in most high-impedance circuits.

## Signal Generator

Ever wanted an audio-frequency tone to test your amplifier or other audio project? This generator will enable you to select signals over the audio spectrum.

Items mentioned here are those planned, but unforeseen circumstances may affect the actual contents.

## Train Sound Generator

Yes — a follow-up to the Chuffer in the January issue. But we're not prepared to say what the sound is this time. So, all you model train enthusiasts, wait until the February issue for the secret to be revealed!

## Miniature MW Radio

This is the set you can tuck away in your top pocket (or wherever) and tune into . . . whatever's your fancy. Definitely personal pleasure at low cost.

## Background Noise Source

Background *what?* This is an HE special, a project to soothe your nerves, help you cope with the frantic pace of life in the 80's and relax as you read HE. More details next month.

## Oscilloscopes

The oscilloscope is probably the most versatile piece of test equipment available to the amateur constructor. That much we all know, but how many of us know exactly how they work? Well, we're going to put that right next month with possibly the most comprehensive feature on oscilloscopes ever published. If there are any questions you ever wanted answered about 'scopes then you'll find everything you want to know, right here next month — don't miss it!

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

**ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 40p TO ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE. ACCESS ORDERS WELCOME.**

**VAT** Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 16% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground, Nearest Underground/BR Station: Watford High Street. Open Monday to Saturday, 9 a.m. to 6 p.m. **Ample Free Car Parking** space available.

**POLYESTER CAPACITORS:** Axial lead type  
400V: 1nF, 1n5, 2n, 3n, 4.7, 6.8, 10n, 15n 9p; 18n 10p; 22n, 33n 11p; 47n, 68n 14p; 100n 17p; 150n, 220n 24p; 330n, 470n 41p; 680n 52p; 1µF 64p; 2.2µF 82p; 4.7µF 85p  
160V: 39pF, 100n, 150n, 220n 11p; 330n, 470n 19p; 680n, 1µF 22p; 1.5, 2µF 32p; 4µF 36p  
1000V: 10nF, 15n 20p; 22n 22p; 47n 28p; 100n 38p; 470n 80p; 1µF 175p

**POLYESTER RADIAL LEAD CAPACITORS: 250V:**  
10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n 10p; 220n, 330n 13p; 470n 17p; 680n 19p; 1µF 22p; 1.5µF 30p; 2µF 34p; 4µF 70p.

**ELECTROLYTIC CAPACITORS:** Axial lead type (Values are in µF)  
500V: 10 50p; 47 78p; 250V: 100 65p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3, 4.7, 6.8, 8, 10, 15, 22, 47, 32, 50 12p; 63, 100, 27p; 50V: 50, 100, 220, 25p; 470, 32p; 1000, 80p; 40V: 22, 33, 10p; 100, 12p; 2200, 330p, 85p; 4700, 98p; 35V: 33, 10p; 330, 47p; 32p; 25V: 10, 22, 47, 100 8p; 150, 220, 250, 15p; 470, 25p; 680, 100n, 35p; 1500, 40p; 2200, 54p; 3300, 77p; 4700 85p; 16V: 10, 47, 68, 7p; 100, 125, 8p; 220, 33p, 16p; 470, 20p; 1000, 150p, 30p; 2200, 36p.  
**TAG-END TYPE:** 450V: 100µF 180p; 70V: 4700, 185p; 64V: 3300 150p; 2500 110p; 50V: 3300 135p; 2200 99p; 40V: 4700 130p; 4000 92p; 3300 93p; 2500, 2200 90p; 2000+2000 120p; 30V: 4700 195p; 2200 25V; 15000 470p; 6400 120p; 4700 100p; 3300 85p; 2200 60p.

**TANTALUM BEAD CAPACITORS:**  
35V: 0.1µ, 0.22, 0.33, 0.47, 0.68, 1.0, 1.5, 2.2, 3.3, 4.7, 25V: 10, 20p; 20V: 2.2, 3.3, 4.7, 10, 20p; 16V: 2.2, 3.3, 4.7, 10, 20p; 10V: 1.5, 2.2, 3.3, 4.7, 10, 20p; 6V: 4.7, 6.8, 10, 20p; 3.3, 100 23p; 100 23p.

**MYLAR FILM CAPACITORS:**  
100V: 0.001, 0.002, 0.005, 0.01µF 6p  
0.015, 0.02, 0.04, 0.05, 0.056µF 7p  
0.1µF 8p; 50V: 0.47µF 12p

**MINIATURE TYPE TRIMMERS:**  
2.5-6pF: 3.10pF, 10 40pF 28p  
5-25pF: 5-45pF; 60pF; 88pF 35p

**COMPRESSION TRIMMERS:**  
3-4pF, 10-80pF; 25-190pF 33p  
100-500pF 45p; 1250pF 58p

**POLYSTYRENE CAPACITORS:**  
10pF to 1nF 8p; 1 nF to 10nF 10p

**SILVER MICA (Values in pF):** 3.3, 4.7, 5.6, 10, 12, 18, 22, 33, 47, 56, 68, 75, 82, 85, 100, 120, 150, 180, 11n each; 220, 250, 270, 300, 330, 360, 390, 470, 600, 800, 820 16p each; 1000, 1200, 1800, 2200 26p each.

**CERAMIC CAPACITORS 50V: 0.5µF to 10nF 4p; 22n to 47n 6p; 100n, 7p.**

**EURO BREADBOARD £5.20.**

**VOLTAGE REGULATORS**

1A TO3	4.7	7905	220p
5V 7805	145p	7912	220p
12V 7812	145p		
15V 7815	145p		
18V 7818	145p		

1A TO220 Plastic Casing  
5V 7805 80p 7905 65p  
12V 7812 60p 7912 65p  
15V 7815 60p 7915 65p  
18V 7818 60p 7918 65p  
24V 7824 60p 7924 65p

100mA TO92 Plastic Casing  
5V 78L05 30p 79L05 65p  
6V 78L06 30p 79L06 65p  
8V 78L08 30p 79L08 65p  
12V 78L12 30p 79L12 65p  
15V 78L15 30p 79L15 65p

**JACKSONS VARIABLE CAPACITORS**

Dielectric: 0.2 365pF with slow motion Drive 450p  
500pF 250p 00 208/176 with 6 1 Ball Drive  
4511/DAF 145p slow motion drive 410p  
Dial Drive 4103  
6-1/36-1 775p CB04-5pF: 10, 15;  
Drum 54mm 55p 25, 30pF 250p  
0-1.365pF 325p 80p 92p 65p  
00-2.365pF 395p 00.3x25pF 725p

**DENCO COILS**  
DP VALVE TYPE  
Range 1 to 5 Bl.  
Rd. Tl. Wh. 10p  
6-7 Brn 95p  
15 Green 130p  
T type 1 to 5, Bl.  
Rd. Wh. Yl. 130p  
B9A Valve Holder  
125p  
RD2 35p  
MW/SFR 112p  
MW/LW SFR 134p

**VEROBOARD** 0.1 0.15 0.15 (copper clad) (plain)

2 1/2 x 3 1/2	66p	59p	34p
2 1/2 x 5	75p	69p	39p
3 1/2 x 3 1/2	75p	69p	39p
3 1/2 x 5	85p	92p	65p
2 1/2 x 17	202p	195p	
3 1/2 x 17	296p	260p	178p
4 1/2 x 17	387p		280p

Pkt of 36pins 20p 'DIP' Board 32p  
Spot face cutter 107p 'VQ' Board 144p  
Pin insertion tool 147p VeroBoard 35p

**DIODES**

BA100	16	BA100V	16
BY126	12	BY127	12
CR033	158	CR033	158
OA9	45	OA7	12
OA70	10	OA70	10
OA91	15	OA85	15
OA91	8	OA95	8
OA200	9	OA202	9
IN541/1	6	IN541/2	6
IN4001/2	5	IN4003	6
IN4004/5	6	IN4007/7	7
IN4148	4	IN5401/2	17
IN5403/4	20	IS44	20
3A/100V	18	3A/200V	44
3A/400V	20	3A/600V	27
3A/1000V	30	VM18 DIL 50	

**ZENERS**  
Range: 2V7 to 39V 400mW  
Range: 3V3 to 33V, 1.3W  
15p each

**NOISE**  
Z5J 180p

**BRIDGE RECTIFIERS** (plastic case) p

1A/50V	20	2A/100V	22
1A/200V	25	2A/400V	25
1A/400V	29	2A/600V	34
1A/600V	34	2A/100V	35
2A/100V	44	2A/200V	46
2A/400V	53	2A/600V	65
2A/100V	73	6A/100V	73
6A/200V	78	6A/400V	85
6A/600V	85	6A/1000V	90
12A/100V	90	12A/200V	98
12A/400V	100	12A/600V	100
12A/100V	110	16A/100V	110
16A/200V	115	16A/400V	120
16A/600V	120	25A/100V	120
25A/200V	120	25A/400V	120
25A/600V	120	25A/1000V	120

**SCRs Thyristors**

0.6A/200V	30	0.8A/100V	30
0.8A/200A	35	1A/200V	42
1A/100V	42	1A/200V	47
1A/500V	42	1A/600V	43
5A/300V	35	5A/600V	43
8A/300V	48	8A/600V	48
12A/300V	55	12A/500V	92
12A/500V	92	15A/700V	195
2N4444	140	BT106	150
BT107	150	BT108	150
BT109	150	BT110	150
BT111	150	BT112	150
BT113	150	BT114	150
BT115	150	BT116	150
BT117	150	BT118	150
BT119	150	BT120	150
BT121	150	BT122	150
BT123	150	BT124	150
BT125	150	BT126	150
BT127	150	BT128	150
BT129	150	BT130	150
BT131	150	BT132	150
BT133	150	BT134	150
BT135	150	BT136	150
BT137	150	BT138	150
BT139	150	BT140	150
BT141	150	BT142	150
BT143	150	BT144	150
BT145	150	BT146	150
BT147	150	BT148	150
BT149	150	BT150	150
BT151	150	BT152	150
BT153	150	BT154	150
BT155	150	BT156	150
BT157	150	BT158	150
BT159	150	BT160	150
BT161	150	BT162	150
BT163	150	BT164	150
BT165	150	BT166	150
BT167	150	BT168	150
BT169	150	BT170	150
BT171	150	BT172	150
BT173	150	BT174	150
BT175	150	BT176	150
BT177	150	BT178	150
BT179	150	BT180	150
BT181	150	BT182	150
BT183	150	BT184	150
BT185	150	BT186	150
BT187	150	BT188	150
BT189	150	BT190	150
BT191	150	BT192	150
BT193	150	BT194	150
BT195	150	BT196	150
BT197	150	BT198	150
BT199	150	BT200	150

**TRIACS**

3A/100V	48	3A/200V	48
3A/400V	48	3A/600V	48
3A/100V	54	6A/100V	54
6A/200V	54	6A/400V	54
6A/600V	54	12A/100V	54
12A/200V	54	12A/400V	54
12A/600V	54	16A/100V	54
16A/200V	54	16A/400V	54
16A/600V	54	25A/100V	54
25A/200V	54	25A/400V	54
25A/600V	54	25A/1000V	54
25A/100V	54	25A/200V	54
25A/400V	54	25A/600V	54
25A/1000V	54	25A/1000V	54

**DIAC** ST2 25 T280000 480

**TTL 74**

7400	11	74126	45	74LS75	45	4021	90	4422	570	LM390	80
7401	11	74128	65	74LS10	65	4022	85	4432	1050	LM381	145
7402	11	74130	55	74LS11	65	4023	24	4433	995	LM382	125
7403	14	74131	75	74LS12	65	4024	60	4434	850	LM386	99
7404	14	74132	185	74LS13	65	4025	24	4440	999	LM387	120
7405	18	74133	250	74LS14	65	4026	180	4450	350	LM387	120
7406	36	74134	80	74LS15	65	4027	45	4451	350	LM387	120
7407	36	74135	150	74LS16	65	4028	92	4452		LM387	120
7408	17	74136	125	74LS17	65	4029	98	4490F	350	LM387	120
7409	20	74137	100	74LS18	65	4030	98	4480V	350	LM387	120
7410	17	74138	100	74LS19	65	4031	185	4501	28	LM390	60
7411	25	74139	70	74LS20	65	4032	125	4502	105	LM391	125
7412	20	74140	120	74LS21	65	4033	175	4503	65	LM391	125
7413	32	74141	75	74LS22	65	4034	213	4504	75	LM391	125
7414	38	74142	150	74LS23	65	4035	95	4505	48	LM391	125
7415	38	74143	150	74LS24	65	4036	275	4506	325	LM391	125
7416	38	74144	150	74LS25	65	4037	115	4510	95	LM391	125
7417	30	74145	99	74LS26	65	4038	110	4511	98	LM391	125
7418	19	74146	99	74LS27	65	4039	299			LM391	125
7419	38	74147	99	74LS28	65	4040	85			LM391	125
7420	25	74148	120	74LS29	65	4041	90	2102-2	225	LM391	125
7421	28	74149	120	74LS30	65	4042	70	2108	495	LM391	125
7422	28	74150	120	74LS31	65	4043	60	2109	495	LM391	125
7423	28	74151	120	74LS32	65	4044	80	4116	290	LM391	125
7424	32	74152	205	74LS33	65	4045	175	6502	650	LM391	125
7425	43	74153	205	74LS34	65	4046	96	6800	700	LM391	125
7426	43	74154	205	74LS35	65	4047	98	709C 8 pin	35	LM391	125
7427	32	74155	205	74LS36	65	4048	85	710	67	LM391	125
7428	35	74156	205	74LS37	65	4049	35	741C 8 pin	17	LM391	125
7429	19	74157	375	74LS38	65	4050	38	747C	78	LM391	125
7430	27	74158	100	74LS39	65	4051	86	748C	36	LM391	125
7431	36	74159	82	74LS40	65	4052	86	753	150	LM391	125
7432	36	74160	82	74LS41	65	4053	66	810	150	LM391	125
7433	36	74161	82	74LS42							

# Now you can have **LINEAR REGRESSION** at your fingertips!

With the **FX-3500P**, Casio's new low-cost programmable scientific. An abundance of built-in functions, including Linear Regression. Prov. price: **UNDER £30.**

## THE ULTIMATE WATCHES

★ **STAR BUY FOR 1980** ★

Our best selling watch

### LCD ANALOGUE/DIGITAL

**Alarm Chronograph with countdown**  
**Analogue.** Independent hours and minutes with synchronous digital seconds. Dual time ability.  
**Digital.** Hours, minutes, seconds, day and date.  
**Stopwatch.** 1/100 second to 12 hours. Net Jap and 1st and 2nd place. Start/stop and 10 minute signals.  
**Alarm.** For 30 seconds with carousel display.  
**Countdown Alarm.** Normal and net times to 1 hour with amazing "Star Burst" flashing display.  
**Time Signal.** Half-hourly and hourly chimes. Tone control. Lithium battery. Light. Water-resistant case. B. 65mm thick. Mineral glass.



**AA81**  
Analogue Display



**AA82**  
Digital Display

### 12 MELODY ALARM CHRONOGRAPHS

Countdown alarm. Date memories.

Hours, minutes, seconds, am/pm, 12 or 24 hour. Day, date and month auto calendar.  
**Alarm.** 7 melodies, one for each day of the week.  
**Hourly time signal.** With "Big Ben" type tune.  
**Date memory.** Select either "Wedding March" or "Trinkled" to be played.  
**Birthday and Christmas Memory.**  
**Countdown alarm.** From 1 second to 1 hour. After zero count continues positively.  
**Stopwatch.** 1/10 second to 1 hour. Net, lap, etc.  
 Picturesque moving display of notes played. Light. Lithium. Glass. Water-resistant cases. **M-12** Resin, s/s trim. **M-1200** all s/s 9.0 mm thick.

**AA81** Chrome plated **£29.95**  
**AA81G** gold plated **£49.95**  
**AA82** stainless steel **£39.95**  
**AA83** Dress watch, s/s **£44.95**



**£24.95**



**£29.95**

for around 40 functions

### 100 METRE WATER RESISTANT

**Alarm chronographs with countdown**  
 Amazing 5-year lithium battery life. Hours, minutes, seconds, am/pm, day, date and month. 12 or 24 hour. Time is always visible regardless of display mode.  
**Stopwatch.** 1/100 second to 1 hour. Net, lap, and 1st and 2nd. Start/stop signal. 10 minute signal.  
**Alarm.** Sounds for 30 seconds.  
**Countdown Alarm.** Normal and net times to 12 hours. Start/stop and 10 minute signals.  
**Time signal.** Half-hourly and hourly chimes.  
**W-100.** All resin. **W-150B** All s/s. **W-150C** (not illustrated) s/s case/resin strap. **£29.95**



**£19.95**



**£32.50**

**A250.** As above but with standard water-resistant case

**S220.** As above but with dual tune in lieu of alarms and chimes

**F300 Sports Chronograph** (right). 8 digits, hours, minutes, seconds, date and day indicator. 1/100 second stopwatch: net, lap and 1st and 2nd place times, to 12 hours. Resin case, s/s trim. Water-resistant. Glass. Light.

**110QS-37B** Metal version **£17.95**

**F81 Alarm Chronograph** (far right). 8 digit display of hours, minutes, seconds, am/pm and date. 24-hour alarm; hourly chimes, 1/10 second stopwatch to 12 hours; net, lap, 1st & 2nd place. Resin case/strap. Water resist. Mineral glass. Nightlight.

**83QS-41B.** S/s jacket version **£19.95**



**£12.95**



**£15.95**

**OTHER CASIO WATCHES** Remember we will **BEAT** lower prices by 5% \*

8 digit basic watches. **F7C** £8.95. **111QS-34B** £14.95.

Chronographs. **95QS-36B** £19.95. **56QS-38B** Digital/analogue £14.95.

Calculator/Chronographs. **C80** £24.95. **C801** £29.95.

Alarm chronos. **B1QS-35B** all s/s £29.95. **83QGS-41B.** Gold plated. £29.95.

**B1QGS-35B** Gold plated £29.95. **79QS-39B** calendar. £29.95. **79CS-51B** Calendar. all s/s £39.95.

### LADIES' MODELS with stopwatch or dual time.

**87QGL-13B** gold plated £24.95. **B7QL-13B** chrome £16.95. Other ladies' models from £10.95 to £34.95.

**Ladies' Alarm Watches.** Hourly chimes, calendar.

**LA550** all s/s £24.95. **LA551.** chrome £19.95.

Details on request.

\* Providing the advertiser has stocks and we make a small profit!

**CHRISTMAS POST** Our return of post service means that orders received by 18th December should reach you in time for Christmas, subject to availability.

Send 25p for our illustrated catalogue of latest Casio and Seiko products. Offers are subject to availability.

Price includes VAT and P&P. Send your company order, cheque, P.O. or phone your **ACCESS** or **BARCLAYCARD** number to:

# TEMPUS

Dept. HE, FREEPOST  
 164-167 East Road,  
 Cambridge CB1 1DB  
 Tel: 0223 312866


## RETURN OF THE SUPERCALCS!

★ **NEW MODEL! FX-6100**

Clock. Hours, minutes, seconds, am/pm.  
 Alarm. Alarm signal at pre-set time.  
 Hourly chimes. Every hour, on the hour. Easily switched off.  
 Countdown alarm. (Repeater time).  
 Stopwatch. Normal, net, and lap times to 1/100 second.  
 Calculator. 39 scientific functions. True algebraic logic. 5 level parenthesis, cube roots, standard deviations, R-P and P-R coordinate conversions, sexagesimal conversions, full memory, %.  
 Approx. 14 months on 2 penlight batteries (AA type). 3/4 x 3 x 5 1/2 inches. (RRP £22.95). **£19.95**

**FX-7100.** Card version of above with kiss-touch keys. 3/16 x 2 1/2 x 3 3/8. (€27.95). **£24.95**

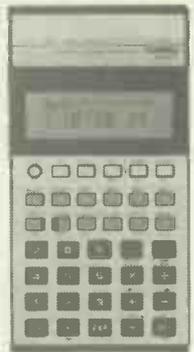**FX-8100.** Specifications as above plus permanently programmed calendar (1976-1999), day, date, month and year. Also has hyperbolics. 1/4 x 2 1/2 x 5 1/2. **£24.95**



## CASIOTONE KEYBOARDS

★ **NEW MODEL! CT-301 Domestic Keyboard**

Polyphonic playing of 14 instruments plus 16 rhythm voices. Dimensions, etc are similar to the CT-201. Woodgrain only. Provisional price; under **£300.**

**CT-201.** 29 polyphonic instruments over 4 octaves, 4-sound memory function. 3 x 33 1/2 x 9 1/2. Weight 15 lbs. Integral amplifier and speaker. AC only. (€285) **£245**

## THE SPACE INVADERS ARE BACK!

This time right in your pocket. An action-packed speed game that will give you hours of skilful entertainment and chair-gripping excitement. Never another dull spare moment. Also an 11-note melody calculator, pre-programmed "When The Saints Go Marching In". Full memory, %. Auto power-off facility.

**MG-880** (left)

1/4 x 2 1/2 x 4 1/2"

**£10.95**  
(€12.95)

**MG-770** (right)

Kiss touch keys.

5/32 x 3 3/8 x 2 1/2"

**£12.95**

(€14.95)



## 12 PRE-PROGRAMMED MELODIES

Clock, calendar, 11-note melody maker, calculator, square roots, %. Alarm 1; 7 tunes, one for each day. Alarm 2; a fixed tune. Hourly chimes. Date memories; 4 anniversary tunes.  
**MQ-1200** (below). Desk or bedside. Built-in speaker, Volume control. Nightlight. Powered by three AA size batteries. 1 9/16 x 6 x 2 1/4 inches.

**£19.95**  
(€22.95)



**ML-90** (right)

Kiss keys

Stopwatch

7/32 x 2 1/2 x 4 1/2"

**£19.95**

(€22.95)



Other Casio calculators, P.O.A. Remember, we will **BEAT** lower prices by 5%

## SEIKO ALARM CHRONOGRAPHS FROM **£37.50**



**£37.50**

**DFT 048** (left) Alarm, countdown alarm, hourly chimes, stopwatch to 1/100 second; net, lap, 1st & 2nd.

**DFT 038** 100 metre water-resistant version

**£49.95**

**DER 048** Solar powered (right). Weekly programmable alarm, 16-hour interval countdown alarm timer, hourly chimes, 1/100 second stopwatch.

**DER 018** 100 metre water-resistant version.

**£69.95**



**£52.50**

**DUO DISPLAY Analogue/digital watches from £57.50**

# Sound-into-Light Module

No ordinary sound-into-light display this: by creating a pulsating, rising-and-falling light show it will transform your party or disco. Designed by Magenta Electronics



OH NO, NOT another boring old sound-into-light converter — well yes and no. Yes, it is a sound-into-light converter but no, it certainly is *not* boring, in either appearance or design. By constructing the HE Ladder-of-Light as a modular design you will be the owner of a very versatile project. The simplest module (as shown here) will drive ten 100 W bulbs either in bar mode (in a line increasing from one end) or dot mode (one bulb at a time) according to the volume of music. All that's required is to connect the Ladder-of-Light to your amplifier or speakers.

By filtering the audio signal through a low-pass, a high-pass or an all-pass filter, the converter is controlled by bass, treble or middle frequencies allowing the display to pulsate in time with music or vocal etc. An adjustable sensitivity level means that most amplifiers regardless of output power, can be used with the project.

The display of bulbs is triac-controlled with zero-cross detection and triggering to prevent radio frequency interference (RFI), and with no heatsinking ten 100 W bulbs can be used without the triacs overheating. If you wish, the triacs can be fitted with heatsinks thus taking power handling up to the triacs maximum of 1k2 W per bulb,

but it is outside the scope of this article to show how this can be done. If you want to increase power handling, remember that the total current consumption of the converter and display must not exceed that available from mains (ie 13 A). Style of the display is largely a matter of personal choice and so we only give suggestions for its constructional details, but designs could be in the form of a line of bulbs, a circle, a spiral etc.

More intricate and eye dazzling displays can obviously be built if more than one module is used so that different coloured bulbs can be used, for bass and treble for example, adding a new dimension.

## Construction


Unlike most mains-powered projects (especially those which control mains voltages via triacs and thyristors etc) we have not used a PCB for constructional purposes, but Veroboard. The main reason for this is that the only mains connection to the board is a *neutral* connection. However, we must stress that while we have taken every precaution in the wiring of the project, if the mains wiring of the particular application is incorrect (ie

the live and neutral connections are reversed), then the mains and triac board will be *potentially live* — and prying fingers might pry no more. So take care!

Construction starts with the Veroboard — a larger-than-usual piece — 26 strip by 50 holes, 0.1" matrix. We are assuming that builders of this projects are not beginners so we need not explain *all* stages of build-up of the board, just remember to make the breaks in the track first. Use pins in the board for all external connections — in this way the board can be fixed in position into the case using *plastic* mounting brushes (for insulation) before wiring-up starts.

Drill the case for all switches, the pot, neon, cable holder, triac and main board mounting holes, transformers, connector blocks and a rectangular slot in the back panel to allow the cables from all lamps to enter the case. Grommet strips should be put around the slot to prevent chaffing of the cables. Your project can now start to go together as in the connection diagram of Fig. 5 which should provide you with details of the full project minus only the triac board. This is a piece of paxolin on which the ten triacs, 10 fuseholders and the



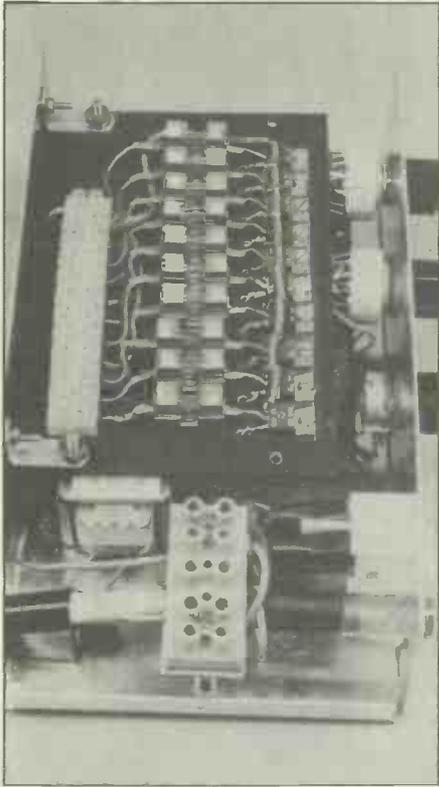

12-way connecting block fit as you can see in the photograph. These must all be firmly mounted on the paxolin. Solder all 10 triac MT1 terminals together, using a suitable length of single-core, tinned wire and insulate this adequately with sleeving. Each MT2 terminal of the triacs goes to the corresponding fuseholder (again insulated). The final triac connections — the 10 gate terminals — should be taken to the corresponding output of the LM3914 on the main board. Figure 1 connection diagram shows their order.

The other sides of the fuseholders go to the first 10 terminals on the connecting block. The final two terminals of the block are neutral connections, one to the mains input connecting block and one to the main board. These two terminals are joined and then taken to the ten MT1 terminals of the triacs. Figure 1, summarises all connections on this board. Now fasten this board to the back panel using angle brackets and make sure no short circuit might occur between the triac circuitry and the rest of the project.

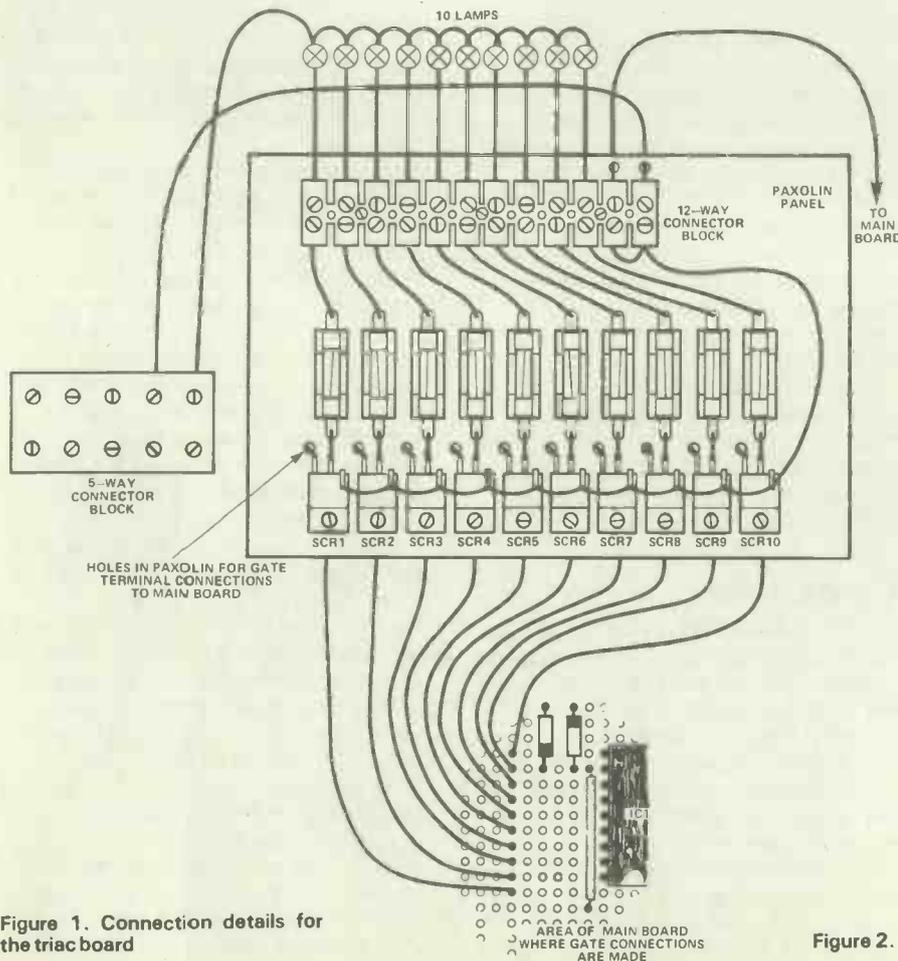



Figure 1. Connection details for the triac board

A second paxolin panel should be used over the triac board to prevent the lid from shorting out the connections underneath, if for instance, the case is accidentally damaged.

The project is ready for testing now, with ten bulbs and an audio source. The live connection for each bulb is taken from the mains terminal block and connected to the bulbs in turn.
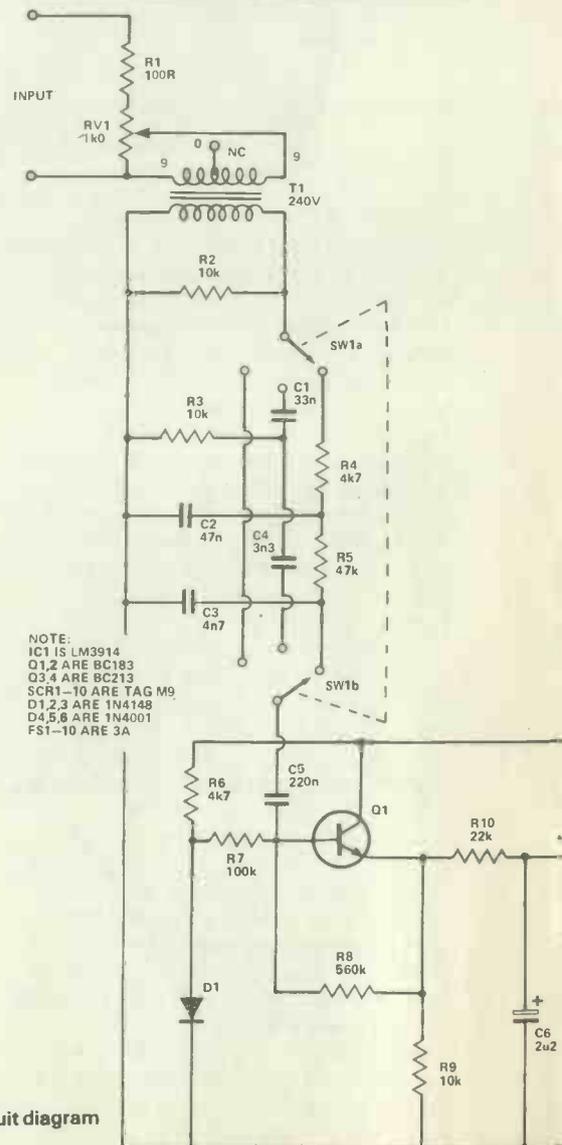
## Buylines

All the components are reasonably easy to obtain, but Magenta Electronics are producing a full kit of parts for those readers who can't be bothered to buy individual components. This kit is also very reasonably priced at £30.38 inclusive of case, VAT and postage — all you need is a plug. Not bad, eh? As an added incentive, Magenta have included in this price the circuit for Strobe and Chase facilities. You will find their advertisement on page 24 this month.



NOTE:  
 IC1 IS LM3914  
 Q1,2 ARE BC183  
 Q3,4 ARE BC213  
 SCR1-10 ARE TAG M9  
 D1,2,3 ARE 1N4148  
 D4,5,6 ARE 1N4001  
 FST-10 ARE 3A

Figure 2. Circuit diagram

# Sound-into-Light Module

## How It Works

The HE Ladder-of-Light controls each bulb in the display, according to the amplitude of the applied audio signal. The 10 bulbs are turned on and off by triacs SCR 1 to 10 in Fig. 2. These triacs can be considered as being electronic switches which are operated by pulses at their gates. The block diagram shown in Fig. 3 shows such a switch capable of turning on one bulb. Although we have only shown one triac, there are ten in the project.

The gate pulse to operate the triac comes from the dot/bar voltmeter IC1, an LM3914, which as our 'regulars' will know (we have used it once or twice before) drives either a bargraph or dot display, where the number of 'dots' illuminated depends on the applied DC voltage at its input. The LM3914 is most often associated with a 'line of LEDs' display, but this application sees it driving a line of triacs directly.

The DC voltage at the input of the LM3914 voltmeter is derived from the audio input, taken directly from your amplifier output. Transformer T1 is used as an isolating transformer to electrically separate the amplifier circuit from the Ladder-of-Light circuit (only magnetic coupling takes place). From here the signal is switched through a bank of filters (low-pass, high-pass or all-pass) by SW1, which means that various frequency bands — either bass, treble or middle — are used to control the light.

As the audio signal is AC and the required control voltage at the LM3914 is

DC, the signal must be rectified and Q1 with its associated components performs this function. The resultant DC voltage of 0 V to 1.2 V is stored by capacitor C6.

Now, if a triac is turned on half-way through a mains cycle, radio frequency interference (RFI) can occur, because of the sharp edge on the wave — Fig. 4 shows such a waveform. The obvious

way to prevent RFI from occurring, therefore, is to switch on the triac at the beginning of the mains cycle. The block diagram shows a section dedicated to detecting when the mains voltage crosses 0 V, the zero-crossing detector formed by Q2,3,4 along with associated components. Whenever this 0 V state occurs the LM3914 is allowed (given the right control voltage) to turn on the triacs.


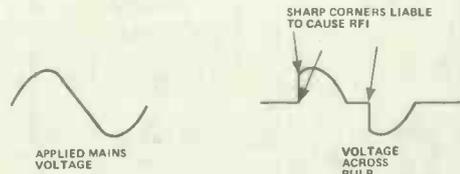
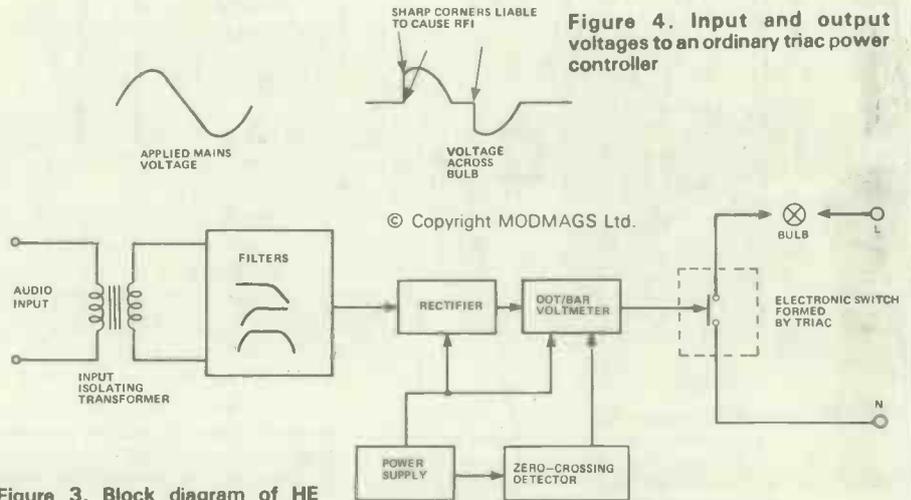


Figure 4. Input and output voltages to an ordinary triac power controller

© Copyright MODMAGS Ltd.

© Copyright MODMAGS Ltd.

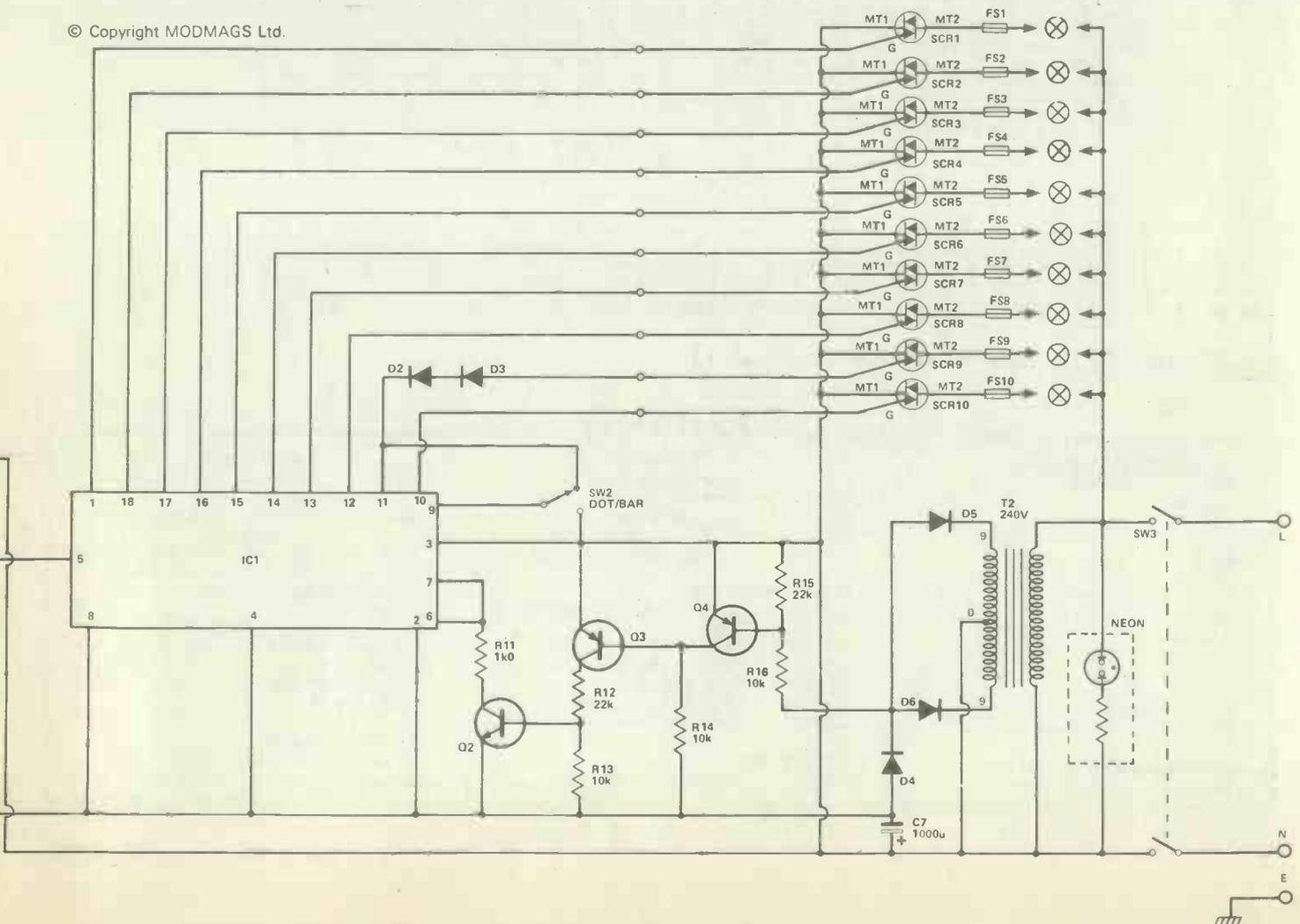

# Sound-into-Light Module

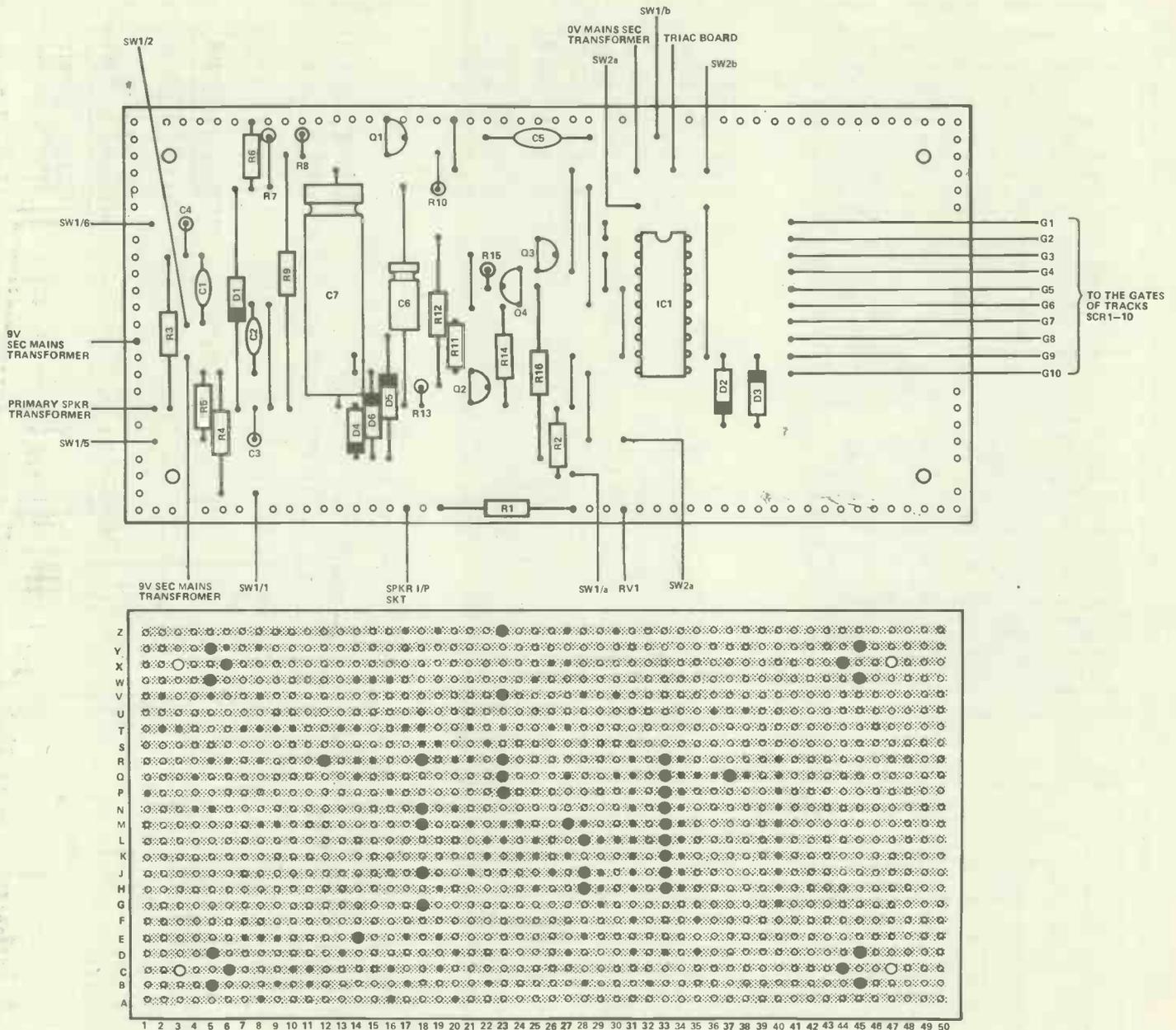


Figure 5. Veroboard layout and underside view showing track breaks

## Parts List

### RESISTORS (All 1/4 W, 5%)

R1 100R  
 R2,3,9,13,14,16 10k  
 R4,6 4k7  
 R5 47k  
 R7 100k  
 R8 560k  
 R10,12,15 22k  
 R11 1k0

### POTENTIOMETER

RV1 1k0 linear

### CAPACITORS

C1 33n polyester

C2 47n polyester  
 C3 4n7 polystyrene  
 C4 3n3 polystyrene  
 C5 220n polyester  
 C6 2u2, 16 V electrolytic  
 C7 1000u, 16 V electrolytic

### SEMICONDUCTORS

IC1 LM3914 dot/bar display driver  
 Q1,2 BC183 NPN transistor  
 Q3,4 BC213 PNP transistor  
 D1,2,3 1N4148 diode  
 D4,5,6 1N4001, 1 A diode  
 SCR1-10 TAG M9 triac

### MISCELLANEOUS

SW1 two-pole, three-way

SW2 rotary switch one-pole, two-way rotary switch  
 SW3 single-pole, single-throw rocker switch  
 T1,2 9-0-9 V mains transformer  
 FS1-10 3 A fuse + fuseholders  
 neon with integral resistor  
 cable grip  
 12-way connecting block (2 A)  
 5-way connecting block (10 A)  
 speaker DIN socket  
 IC socket (18 pin)  
 knobs to suit  
 case to suit  
 2 x angle brackets  
 26 strip x 50 hole 0.1" Veroboard  
 2 x paxolin panels of suitable size.

TTLs by TEXAS			
7400	11p	74293	150p
7400	60p	74298	200p
7401	12p	74365	100p
7402	12p	74366	100p
7403	14p	74367	100p
7404	14p	74368	100p
7405	18p	74390	200p
7406	36p	74393	200p
7407	36p	74490	225p
7408	17p	74495	4030
7409	19p	74500	14p
7410	15p	74502	16p
7411	24p	74503	18p
7412	20p	74504	16p
7413	30p	74505	25p
7414	40p	74508	22p
7414	40p	74509	21p
7416	27p	74510	20p
7417	27p	74511	40p
7420	17p	74513	40p
7421	40p	74514	50p
7422	22p	74520	20p
7423	34p	74521	40p
7425	30p	74527	38p
7426	40p	74530	20p
7427	34p	74531	27p
7428	36p	74537	30p
7430	17p	74538	38p
7432	30p	74542	70p
7433	40p	74547	75p
7437	35p	74551	24p
7438	35p	74559	30p
7440	17p	74573	50p
7441	70p	74574	27p
7442A	60p	74575	36p
7443	112p	74576	45p
7444	112p	74583	70p
7445	100p	74584	40p
7446A	93p	74586	40p
7447A	75p	74590	40p
7448	80p	74592	70p
7450	17p	74593	60p
7451	17p	74596	110p
7453	17p	74510	45p
7454	17p	74509	80p
7456	17p	74511	40p
7470	36p	745113	90p
7472	30p	745114	45p
7473	34p	745122	80p
7474	34p	745123	60p
7475	38p	745124	60p
7476	32p	745125	50p
7480	50p	745126	50p
7481	100p	745132	60p
7482	84p	745133	30p
7483A	90p	745136	55p
7484	100p	745137	55p
7485	110p	745139	75p
7486	34p	745145	120p
7489	210p	745147	220p
7490A	30p	745148	175p
7491	80p	745151	80p
7492A	46p	745152	60p
7493A	36p	745154	200p
7494	84p	745155	80p
7495A	70p	745156	90p
7496	65p	745157	60p
7497	180p	745158	60p
74100	130p	745163	75p
74107	34p	745161	75p
74109	55p	745162	140p
74116	200p	745163	100p
74118	130p	745164	90p
74119	210p	745165	140p
74120	110p	745166	120p
74121	34p	745173	110p
74122	48p	745174	100p
74123	60p	745175	100p
74125	75p	745181	320p
74126	60p	745190	100p
74128	75p	745191	100p
74132	75p	745192	100p
74136	75p	745193	100p
74137	50p	745195	140p
74141	50p	745196	120p
74142	200p	745197	90p
74145	90p	745221	120p
74147	190p	745222	120p
74148	150p	745241	175p
74150	130p	745242	170p
74151A	70p	745243	170p
74153	70p	745244	150p
74154	120p	745245	250p
74155	90p	745247	140p
74156	90p	745251	140p
74157	70p	745253	90p
74159	190p	745257	90p
74160	100p	745258	160p
74161	100p	745259	160p
74162	100p	745266	100p
74163	100p	745273	170p
74164	120p	745279	140p
74165	130p	745283	90p
74166	120p	745298	160p
74167	200p	745323	200p
74170	240p	745324	200p
74172	450p	745348	200p
74173	120p	745365	48p
74174	90p	745367	70p
74175	85p	745368	100p
74176	90p	745373	150p
74177	90p	745374	150p
74178	160p	745375	120p
74180	83p	745377	160p
74181	160p	745378	140p
74182	90p	745390	120p
74184A	150p	745392	160p
74185	150p	745399	200p
74186	500p	745445	140p
74188	325p	745670	400p
74190	120p	4000 SERIES	
74191	100p	4000	15p
74192	100p	4001	16p
74193	100p	4002	20p
74194	120p	4006	95p
74195	95p	4007	20p
74196	95p	4008	80p
74197	60p	4009	40p
74198	150p	4010	45p
74199	150p	4011	40p
74201	160p	4012	25p
74202	160p	4013	25p
74203	110p	4015	45p
74204	110p	4016	45p
74205	110p	4017	70p
74206	110p	4018	89p
74207	110p	4019	45p

93 SERIES		74S SERIES	
9301	160p	74500	60p
9302	175p	74504	60p
9308	316p	74505	75p
9310	278p	74508	75p
9311	275p	74510	75p
9312	165p	74520	60p
9314	165p	74530	60p
9316	225p	74532	90p
9321	225p	74537	90p
9322	150p	74564	60p
9334	380p	74574	60p
9335	250p	74585	300p
9370	300p	74586	180p
9374	200p	745112	120p

LINEAR ICs		MEMORIES	
AY1-0212	600p	LM13600	125p
AY1-1313	668p	MB3712	150p
AY1-1320	320p	MC1310P	150p
AY1-5050	140p	MC1458	45p
AY3-1270	840p	MC1495L	35p
AY3-8917	650p	MC1496	35p
AY5-1224A	240p	MC3340P	120p
AY5-1315	600p	MC3340P	120p
AY5-4007D	520p	MC3340P	120p
CA3019	80p	MC3340P	120p
CA3048	70p	MC3340P	120p
CA3080E	72p	MC3340P	120p
CA3086	48p	MC3340P	120p
CA3089E	225p	MC3340P	120p
CA3090AQ	375p	MC3340P	120p
CA3130E	90p	MC3340P	120p
CA3140E	50p	MC3340P	120p
CA3161E	140p	MC3340P	120p
CA3162E	450p	MC3340P	120p
CA3189E	300p	MC3340P	120p
CA3280	160p	MC3340P	120p
DACT408-B	200p	MC3340P	120p
FX209	750p	MC3340P	120p
HA1388	850p	MC3340P	120p
ICL7106	280p	MC3340P	120p
ICL8038	300p	MC3340P	120p
ICM7555	80p	MC3340P	120p
LF1331	310p	MC3340P	120p
LF3561	95p	MC3340P	120p
LM3048	425p	MC3340P	120p
LM301A	27p	MC3340P	120p
LM311	70p	MC3340P	120p
LM319	225p	MC3340P	120p
LM324	45p	MC3340P	120p
LM339	75p	MC3340P	120p
LM348	95p	MC3340P	120p
LM358P	90p	MC3340P	120p
LM377	175p	MC3340P	120p
LM380	75p	MC3340P	120p
LM381AN	180p	MC3340P	120p
LM386	95p	MC3340P	120p
LM393	100p	MC3340P	120p
LM709	36p	MC3340P	120p
LM710	50p	MC3340P	120p
LM725	350p	MC3340P	120p
LM733	100p	MC3340P	120p
LM741	18p	MC3340P	120p
LM747	70p	MC3340P	120p
LM748	35p	MC3340P	120p
LM749	75p	MC3340P	120p
LM2917	250p	MC3340P	120p
LM3302	140p	MC3340P	120p
LM3909	70p	MC3340P	120p
LM3911	130p	MC3340P	120p
LM3914	225p	MC3340P	120p
LM3915	225p	MC3340P	120p

VOLTAGE REGULATORS		CPU's	
Fixed Plastic TD-220		1600	1200p
1A	+ve	7815	60p
5V	+ve	7816	60p
15V	+ve	7817	60p
18V	+ve	7818	60p
24V	+ve	7819	60p
100mA	TO-92	7820	60p
5V	78L05	7821	60p
12V	78L12	7822	60p
15V	78L15	7823	60p

OPTO-ELECTRONICS		OPTO-ISOLATORS	
2N5777	45p	TL111	100p
OC711	90p	TL112	100p
ORP12	120p	TL116	90p
IL074	130p	TL117	100p
MCT26	100p	TL118	90p
MCS2400	190p	TL119	90p

LEDS		DISPLAYS	
IL125	0.2"	3015F	200p
TL122	55p	DL704	140p
TL1209 Red	13p	DL707 Red	18p
TL1211 Red	20p	FDN357	120p
TL1212 Ye	25p	FDN500	110p
TL1216 Red	18p	FDN507	110p
TL1220 Red	16p	MAN3640	175p
TL1222 Gr	18p	MAN4640	200p
TL1228 Red	22p		
TL1229 Red	22p		
TL1232 Red	22p		
TL1233 Red	22p		
TL1234 Red	22p		
TL1235 Red	22p		
TL1236 Red	22p		
TL1237 Red	22p		
TL1238 Red	22p		
TL1239 Red	22p		
TL1240 Red	22p		
TL1241 Red	22p		
TL1242 Red	22p		
TL1243 Red	22p		
TL1244 Red	22p		
TL1245 Red	22p		
TL1246 Red	22p		
TL1247 Red	22p		
TL1248 Red	22p		
TL1249 Red	22p		
TL1250 Red	22p		
TL1251 Red	22p		
TL1252 Red	22p		
TL1253 Red	22p		
TL1254 Red	22p		
TL1255 Red	22p		
TL1256 Red	22p		
TL1257 Red	22p		
TL1258 Red	22p		
TL1259 Red	22p		
TL1260 Red	22p		
TL1261 Red	22p		
TL1262 Red	22p		
TL1263 Red	22p		
TL1264 Red	22p		
TL1265 Red	22p		
TL1266 Red	22p		
TL1267 Red	22p		
TL1268 Red	22p		
TL1269 Red	22p		
TL1270 Red	22p		
TL1271 Red	22p		
TL1272 Red	22p		
TL1273 Red	22p		
TL1274 Red	22p		
TL1275 Red	22p		
TL1276 Red	22p		
TL1277 Red	22p		
TL1278 Red	22p		
TL1279 Red	22p		
TL1280 Red	22p		
TL1281 Red	22p		
TL1282 Red	22p		
TL1283 Red	22p		
TL1284 Red	22p		
TL1285 Red	22p		
TL1286 Red	22p		
TL1287 Red	22p		
TL1288 Red	22p		
TL1289 Red	22p		
TL1290 Red	22p		
TL1291 Red	22p		
TL1292 Red	22p		
TL1293 Red	22p		
TL1294 Red	22p		
TL1295 Red	22p		
TL1296 Red	22p		
TL1297 Red	22p		

# Clever Dick



Do you like our new cartoon? Good, well we're stuck with it for the next few months. Anyway down to business with this month's rather interesting selection of letters

I've heard some pretty feeble excuses from people trying to extract valuable binders from the HE staff but this one takes the biscuit. It's so cheeky that Ian Malcolm might just get one, if I remember.

Dear Mr C Dick,

In my capacity as Chief Tester for the National Binder Inspection Board, I would be very grateful for a sample of your HE binders for close scrutiny.

While I'm writing I may as well ask about the feasibility of constructing a communications system between myself and a pillion passenger fortunate enough to experience the thrill of roaring down the High Street on my big, fast Yamaha.

Most helmets cannot be easily adapted for such a system so your suggestions would be most welcome. I believe that the number of bikers on the road today would justify such a circuit.

Please don't forget the binder — we have a duty to protect the consumer and it is your interest to ensure your binder's get the Board's approval.

Ian Malcolm  
County Armagh

First things first, the helmet intercom is quite practical, in fact they are manufactured commercially. If you want to make your own then all you'll need are two small amplifiers (we've published many in the past few months) and a helmet headphone/mike kit from Wintjoy Ltd. See the inside back cover for the address. Now, your request for a binder has been considered at length. We've weighed all the pro's and cons (I've know all about cons) and have decided to submit a binder to the Board for testing but we require a 4000 word report by return of post plus £3.95 to cover our expenses.

Back across the Irish Sea and up a bit, we have this letter from Steven Johnson who says:

Dear Clever Dick,  
Here are a few questions:

(1) Where can I obtain a 240 volt/12 volt 6 VA transformer for use in the Battery Eliminator project in the November issue?

(2) What's happened to Short Circuits?

(3) Are HE Tee Shirts still available and if so how much do they cost?

(4) Have you ever produced an HE diary?

Thank you for such a magnificent magazine.

PS How's HEBOT?  
PPS Your Binders look nicelll  
Steven Johnson  
Co Durham

(1) Nothing special about the transformer, try Watford Electronics, Maplin, Magneta etc. etc.

(2) They're back next month after a short holiday.

(3) The old HE T-shirts have sold out but the NEW design will be on sale shortly: keep your eyes open for details.

(4) No, but you never know, we just might.

Thank you for such a nice letter.

PS HEBOT is okay and sends his regards to everyone.

PPS Yes they do don't they, why not buy one?

Back in London, Martin Green also asks about the absent Short Circuits.

Dear CD

A few questions:

(1) Where did Short Circuits go, they were brilliant.

(2) Problem: I had a subscription to HE from March '79 to February '80. In January I renewed my subscription, so far I have received every issue except the April issue. Can you help me?

PS Am I HE's youngest reader at 13? Do I deserve a binder?

PPS Thanks for the superb mag  
Martin Green  
London

As I said earlier Short Circuits are back next month. Sorry about the missing issue, but by the time you read this one should have been sent. I don't think you are our youngest reader but if you are we will certainly send you a binder. If any of you lot are younger than Martin drop us a line but remember to get your parents to put a note on the letter so we can be sure you're not having us on.

YO HO HO, Hobby Electronics certainly gets around. WEMN C. Phillips currently floating around somewhere has a 'messy' problem.

Dear Clever Dick,

Being in the Royal Navy and living in a Mess with 29 other people I have a problem. We are all fed up with answering the Mess door only to find that the person required is not in. Could you please design a Mess call-up system. The following idea is proposed.

Each Mess member has a personal number. The caller requiring, for example, Number 18 taps out the number required on a keypad at the door. Inside the Mess two 0.5 inch digit LED displays show the number and a siren sounds for about 5 seconds. To answer the called a Mess member presses either a 'Yes Wait' or a 'No' button which will illuminate one of a pair of LEDs on the door. In the event of the

Mess being empty the 'No' light should come on after 30 seconds and reset for further use.

WEMN C. Phillips  
BFPO  
Ships  
London

Well, that all sounds a little complicated to me. How about a simple intercom like the Hobbycom for instance. We can't really think of anything off hand but our readers have a reputation for coming up with brilliant ideas. If any of you have a suggestion for WEMN Phillips then could you send it to us and we'll forward them. By the way what does WEMN stand for?

Our penultimate letter this month comes from David Livings. David has been having difficulties in obtaining some batteries. This problem took quite some time to sort out.

Dear CD,  
Is it still possible to obtain 45, 60 and 90 volt dry batteries for valve equipment? If so could you please tell me

where I can obtain them and a rough idea about cost. If you can answer this question I will be very grateful.  
David Livings  
Herts

The problem with this question was that we assumed that such batteries were no longer produced. After several hours head scratching and looking through catalogues from the Vintage Wireless Company we suddenly had the bright idea of looking through the Ever-Ready catalogue. Lo and behold they still make high tension batteries for valve equipment. The nearest ones we could find were the B101 at 67.5 volts. B126 for 90 volts. For the 45 volt battery we suggest two B122s (22.5 V) or one B123 (30 V) and one B121 (15 V) in series. As these batteries are for specialist applications you may have to order them through your local retailer.

Just time for one last letter this month, it comes from Colin Mills who is having Multi Option Siren Problems.

Dear CD,  
Just a quick one this. I built the Multi Option Siren in the October '79 issue and something seems to be wrong. I can only get a variable oscillation. I remember seeing a correction on it, and after going through all my back copies I find someone has swiped my November '79 issue so I bet it was there. Can you help.  
Colin Mills  
Rotherham

Of course we can. The problem was on the overlay diagram (Figure 3). The connection for SK1 was mixed up with the connection for SW1. The wire coming from the junction of R12c and R13 should be marked SK1 not SW1.

Times up once again. Thanks for the hundreds of letters each month, I'm just sorry we can't answer them all. Remember the best chance of being answered is to keep your letters as short as possible. See you next month.

HE

# Marshall's

A. Marshall (London) Ltd., Kingsgate House,  
Kingsgate Place, London NW6 4TA  
Industrial Sales: 01-328 1009  
Mail Order: 01-624 8582 24hr. service  
Also retail shops: 325 Edgware Road, London W2  
40 Cricklewood Broadway, London NW2 85 West Regent St. Glasgow  
108A Stokes Croft, Bristol

We now supply the extremely reliable and cost conscious LEADER range of testgear.

SINGLE TRACE OSCILLOSCOPES	
LBO 510A 5" 4MHz 20mV	£125.00
LBO 512A 5" 10MHz 10mV	£170.00
LBO 513A 5" 10MHz 10mV	£215.00
LBO 507A 5" 20MHz 10mV	£239.00

DUAL TRACE OSCILLOSCOPES	
LBO 308S 3" 20MHz 2mV	£419.00
LBO 508A 5" 20MHz 10mV	£299.00
LBO 520A 5" 35MHz 5mV	£475.00
LNO 514 5" 10MHz 5mV	£255.00

T.V. RADIO TEST GEAR	
LSG 16 Signal Generator	£ 49.00
LSG 231 FM Stereo Signal Generator	£169.00
LCG 397U PAL-B Pattern Generator	£189.00

AUDIO TEST GEAR	
LAG 26 Audio Generator	£ 60.00
LAG 120A Audio Generator	£119.00
LDM 170 Distortion Meter	£225.00
LFM 39A Wow/Flutter Meter (Dist)	£249.00
LFM 39A Wow/Flutter Meter (Dist)	£299.00
LAV 191 Audio Tester	£249.00
LAC 125 Low Distortion Audio Generator	£229.00

GENERAL TEST GEAR	
LCH 740 LCR Bridge	£135.00
LTC 906A Transistor Checker	£ 90.00
LVT 72 Fet Transistor Checker	£119.00
LTC 907 Transistor Checker	£139.00
LAT 47 Attenuator	£135.00
LAT 45 Attenuator	£ 75.00
LFG 1300 Sweep Function Generator	£299.00

AMATEUR RADIO	
LDM 815 DIP Meter	£ 43.00
LIM 870A Antenna Impedance Meter	£ 41.00
LPM 880 RF Power Meter	£ 69.00
LPM 885 SWR Watt Meter	£ 44.00
LAC 895 Antenna Coupler	£ 85.00
LAC 896 Antenna Coupler	£ 41.00
LAC 897 Antenna Coupler	£ 41.00

Please send large SAE for special catalogue. All prices exclusive VAT/carriage.

The new Marshall's 80/81 catalogue is now available. A veritable treasure house of components, test gear, tools, etc.



Lots of old friends, but also many new products including leader test gear, Crimson Hi Fi Modules, Rechargeable Ni Cad batteries and chargers (very competitive). More components including SN74ALS series, new tools etc. Available by post, UK 75p post paid: Europe 95p post paid: Rest of world £1.35 post paid.

## SINCLAIR INSTRUMENTS

Digital Multimeter	
"	PDM35 £ 34.50
"	DM235 £ 52.50
"	DM350 £ 72.50
"	DM450 £ 99.00
Digital Frequency Meter	
	PFM200 £ 49.80
Low Power Oscilloscope	
	SC110 £139.00

## NEW

TF200	Frequency Meter	£145.00
TGF105	Pulse Generator	£ 85.00

## CRIMSON ELEKTRIK HI FI MODULES

CE608	Power Amp	£20.09
CE1004	"	£23.43
CE1008	"	£26.30
CE1704	"	£33.48
CE1708	"	£33.48
CPS1	Power Unit	£19.52
CPS3	"	£23.52
CPS6	"	£30.00
CPR1	Pre Amp	£32.17
CPR1S	Pre Amp	£42.52

All Prices + VAT + postage/packaging

Don't forget! We also carry an impressive range of semi-conductors, passive components, electro mechanical components, tools etc.

GUITAR PHASER	ZD85	Sept. '80	£9.60	HOBBYTUNE	ZD34	Oct. '79	£18.00
BENCH POWER SUPPLY UNIT	ZD87	Sept. '80	£25.00	MULTI OPTION SIREN	ZD36	Oct. '79	£10.50
DEVELOPMENT TIMER	ZD86	Sept. '80	£8.75	ANALOGUE AUDIO			
TOUCH SWITCH (on Vero)	ZD84	Sept. '80	£4.50	FREQUENCY METER	ZD35	Oct. '79	£15.00
AUTO PROBE	ZD83	Sept. '80	£3.00	COMBINATION LOCK	ZD29	Sept. '79	£12.50
REACTION TIMER	ZD82	Sept. '80	£26.50	★STARBURST	ZD30	Sept. '79	£14.50
MICROMIXER (on Vero)	ZD81	Sept. '80	£8.50	LAMP DIMMER	ZD31	Sept. '79	£6.50
EQUITONE CAR EQUALISER	ZD52	Aug. '80	£13.30	ULTRASONIC SWITCH	ZD32	Sept. '79	£21.00
GAS DETECTOR	ZD55	Aug. '80	£22.00	CONSTANT VOLUME AMPLIFIER	ZD28	Aug. '79	£11.50
PASS THE LOOP GAME	ZD56	Aug. '80	£12.00	INJECTOR TRACER	ZD27	Aug. '79	£4.50
RADIO TIMER (on Vero)	ZD57	Aug. '80	£5.50	LED TACHOMETER	ZD26	Aug. '79	£14.75
MOVEMENT ALARM (on Vero)	ZD54	Aug. '80	£5.00	BABY ALARM	ZD25	July '79	£13.50
OP. AMP CHECKER (on Vero)	ZD53	Aug. '80	£4.00	POINTS SWITCH	ZD24	July '79	£12.50
CAR BOOSTER (no speakers)	ZD50	July '80	£18.00	LINEAR SCALE OHMMETER	ZD23	July '79	£14.00
HAZARD FLASHER	ZD48	July '80	£10.50	SHARK	ZD22	July '79	£22.75
★PUSH-BUTTON VOLUME				G.S.R. MONITOR	ZD19	June '79	£10.50
CONTROL	ZD47	July '80	£19.50	ENVELOPE GENERATOR	ZD20	June '79	£11.79
SOUND FLASH TRIGGER (on Vero)	ZD49	July '80	£3.50	DRILL SPEED CONTROLLER	ZD21	June '79	£7.00
2 WATT AMPLIFIER (on Vero)	ZD46	June '80	£3.90	WHITE NOISE EFFECTS UNIT	ZD18	May '79	£16.85
METRONOME (on Vero)	ZD51	June '80	£3.50	PARKING METER TIMER	ZD17	May '79	£6.70
MICROBE R/C SYSTEM				DIGIBELL PROJECT	ZD16	May '79	£5.00
(less Servos)	ZD45	June '80	£17.50	VARIABLE POWER SUPPLY			
FOG HORN	ZD44	June '80	£4.50	0.30V 1 AMP	ZD15	May '79	£30.00
★EGG TIMER	ZD43	June '80	£6.50	TRANSISTOR GAIN TESTER	ZD76	April '79	£6.50
MINI CLOCK	ZD10	May '80	£26.00	CISTERN ALARM	ZD75	April '79	£5.50
5080 PRE-AMP	ZD11	May '80	£32.00	MODEL TRAIN CONTROLLER	ZD74	April '79	£26.00
TRACK CLEANER	ZD12	May '80	£7.75	PHOTOGRAPHIC TIMER	ZD73	March '79	£14.50
★R/C SPEED CONTROLLER	ZD3	April '80	£9.60	TONE CONTROL	ZD72	March '79	£9.00
HOBBY COM	ZD8	April '80	£28.60	CASANOVA'S CANDLE	ZD71	March '79	£7.50
ELECTRONIC IGNITION	ZD2	April '80	£18.25	SHORT WAVE RADIO	ZD66	Feb. '79	£12.50
DIGITAL FREQUENCY METER	ZD9	April '80	£27.75	SINE/SQUARE WAVE			
SHORT WAVE RADIO	ZD80	March '80	£19.50	GENERATOR	ZD67	Feb. '79	£22.50
TOUCH SWITCH	ZD79	March '80	£5.00	SCRATCH AND RUMBLE			
5080 PSU MODULE	ZD78	March '80	£29.50	FILTER MONO	ZD68	Feb. '79	£22.50
SYSTEM 5080A	ZD77	March '80	£15.00	SCRATCH AND RUMBLE			
PASSION METER	ZD6	Feb. '80	£5.00	FILTER STEREO	ZD69	Feb. '79	£25.00
WIN INDICATOR	ZD42	Feb. '80	£9.00	CAR ALARM	ZD70	Feb. '79	£8.50
INFR RED REMOTE CONTROL	ZD7	Feb. '80	£19.35	FLASH TRIGGER (less flash gun)	ZD65	Jan. '79	£10.50
SCALEXTRIC CONTROLLER	ZD41	Jan. '80	£52.50	TOUCH SWITCH	ZD63	Jan. '79	£5.50
CROSSHATCH GENERATOR	ZD4	Jan. '80	£11.25	VARI-WIPER	ZD64	Jan. '79	£8.00
DIGI-DIE	ZD5	Jan. '80	£5.50	GRAPHIC EQUALISER	ZD62	Jan. '79	£25.00
RING MODULATOR	ZD1	Dec. '79	£8.50	PUSH-BUTTON DICE	ZD61	Dec. '78	£6.00
SCALEXTRIC CONTROLLER	ZD39	Dec. '79	£21.50	AUDIO MIXER	ZD14	Dec. '78	£20.30
BARGRAPH CAR VOLTMETER	ZD40	Dec. '79	£6.60	BEDSIDE RADIO	ZD58	Nov. '78	£12.50
GUITAR TUNER	ZD38	Nov. '79	£8.50	STEREO AMPLIFIER (HOBIT)	ZD59	Nov. '78	£52.50
★R2 D2 RADIO	ZD37	Nov. '79	£8.60	WAA-WAA PEDAL	ZD60	Nov. '78	£30.00
TANTRUM	ZD33	Oct. '79	£37.50				

**IONISER KIT: ZD13.** This negative ion generator gives you power to saturate your home with millions of refreshing ions, without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain filling your room. The result? Your air feels like fresh ocean air, crisp and wonderfully refreshing. All parts p.c.b. and full instructions £10. A suitable case including front panel neon switch, etc., available at £8 extra.

### LATE EXTRA

Watchdog Intruder Alarm	ZD89	OCT. '80	£15.75
Temperature Controlled Soldering Iron	ZD90	OCT. '80	£9.00
Freezer Alarm (on Vero)	ZD91	OCT. '80	£8.50
Tug O' War Game	ZD94	OCT. '80	£12.50
Nobell Doorbell	ZD93	OCT. '80	£9.75
Kitchen Timer (on Vero)	ZD92	OCT. '80	£5.50
Light Dimmer	ZD88	OCT. '80	£5.00

All kits contain components as specified plus Texas I.C. sockets, where required, also connecting wire.

**FAIRCHILD FLV150 red. 2 LEDs, 10 for £1.00, 100 for £7.50**  
**DALY ELECTROLYTIC CAPACITORS 2000uF 100v £1.50**  
**PHILIPS SCOPE Tube 5" CV2191/DG-13-2 £10**

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of kits.

# T. POWELL

306 ST. PAULS ROAD, Highbury Corner  
 LONDON N1. 01-226 1489

SHOP HOURS:  
 MON.-FRI. 9-5.30 p.m.  
 SAT. 9-4.30 p.m.



Minimum telephone Orders £5  
 Minimum Mail Order £1

# Top Ten Electronic Games

Looking for an electronic game? Rick Maybury has been playing with over 100 of them recently and reports on his special selection

THE HE OFFICES have been looking like Santa's grotto for the last few months as a result of our latest special 'Gadgets and Games'. We thought it would be a good idea, with Christmas just a few weeks away, to have an exclusive mini-survey, just for Hobby Electronics. From the hundred or so games we've looked at we have selected just ten. The ten games in our list are those we consider to offer the best value for money, are fun to play with and offer the most in terms of challenge and playability: we'll deal with all of these factors in turn.

## Value For Money

This was possibly the hardest criteria to establish. Not all of us are multimillionaires, not least those working for Hobby Electronics. This is especially hard for us to judge as our games are supplied free (though we have to give them back . . . eventually!). The games we have chosen are those that we would probably buy ourselves if we had the money to spare. This may sound rather hypocritical with one game costing nearly £200 and a couple of others close to £100 but we sincerely believe that they are worth that kind of money, as much as our cheapest game costing £10.95 is worth every penny.

Most of the games we've reviewed are, quite frankly, a rip-off. Electronic games manufacturers sometimes seem to think that a couple of flashing LEDs and a squeaking noise can justify a £30 price tag. We don't. We know all about modern technology and how much it costs.

## Fun Factor

To scientifically establish whether a game is fun to play or not we lent our sample games to a group of carefully selected juveniles (the HE and ETI staff) and listened to their comments. For the most part it was incoherent babble but a clear pattern did emerge. If the game was beaten too quickly a flood of tears resulted in the game being thrown against the nearest wall and a replacement demanded with equal ferocity. If the game was a success then the combined efforts of the

Editor and Assistant Editor were needed to prise the game from its tearful player. This expert panel was also used to judge the value for money of each game. After each game had been returned (one way or another) the gameless employee often enquired how much of his pocket money would be needed to buy one. If our reply was returned with just one swear word the game was cheap. If two or three expletives came forth then it was a reasonable buy. If he or she had to be physically restrained then it was classed as poor value for money and if they laughed then we had to assume the game was considered over priced.

## Playability

Again our expert panel's comments were used to classify each game. For this test we divided our testers into three groups roughly proportional to intelligence. This we assumed would give us an idea as to how easily each game could be beaten. The three groups were as follows: Editorial staff (naturally the most intelligent), Artists, (quick on the uptake now and again) and Advertisement department (most of them know how to tie their bootlaces). Each game was given to

the Ad Department first. Most of the 100 games completely baffled this group. Those games that were left unbeaten (or survived intact) were then passed on to the artists. Again the most of the games left met with a dismal fate. Those that were unbeaten were passed on to the Editorial staff (noted for having large brains and heads to match). After exhaustive testing and much head scratching we came up with our final selection.


## The Games

Our ten games have been divided into two groups: the hand-held or table-top games and the TV or video games. We'll look at the hand-held games first.
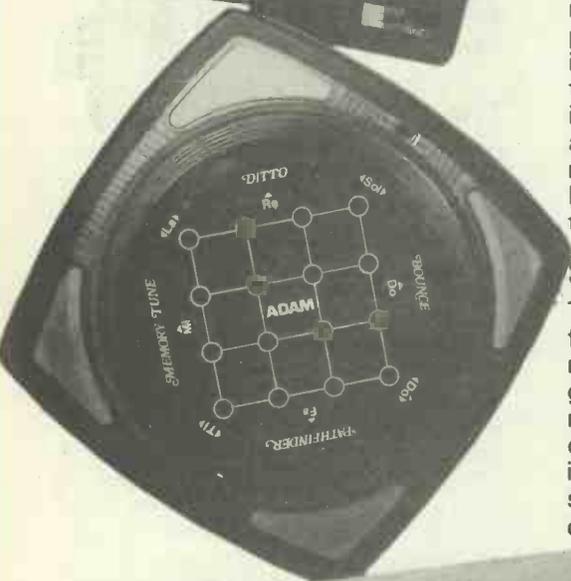
## MICROVISION

Not to be confused with titchy tellies this game is the first cartridge-programmable hand-held game. It comes in two parts, the display and control module and the memory cartridge that is needed for each game. The display module is unusual in that it uses a 2" liquid crystal display (LCD) element for each game. All of the graphics are based upon hundreds of square blocks, this may not sound very





dramatic but believe us, it is. Some very clever design work has gone into this device.

The Microvision comes with just one cartridge as standard called 'Blockbuster' and is better known by the name of 'Breakout' in its more usual video format. Other games include 'Four In A Row', a logical sequence game similar to a board game of the same name. The three remaining games include a space game, 'Shooting Star', 'Bowling' and 'Pinball', both of these are dexterity games based on the pastimes of the same names.

Microvision is currently on sale for £40.00, this price includes the Blockbuster cartridge. Each additional cartridge costs £12.95. Our initial reaction was that this game was overpriced but after prolonged 'field tests' it has become more than apparent that the difficulty of the Blockbuster game is such that it has yet to be mastered by anyone in the HE office. For that reason alone it looks as though it will be played here regularly for quite some time to come.

## SPACE INVADERS

There are something like twenty different space invader games on the market ranging from superb video games to quite disgusting hand-held rubbish purporting to be something other than the ten bob's worth of LEDs it actually is. Our choice for a hand-held space invader game comes from a new company called Entex. This version compares quite favourably with the genuine pub or arcade video game. All

of the familiar elements are there including the flying saucer that flits across the screen from time to time offering bonus points when hit. The limitations of the LED display have meant that the aliens are limited in number but this does not detract from the overall game that is both fast and furious and constantly being played with. Price for this game is around £22.95.

## ADAM

Adam is not new. In fact, like the first Adam, it is getting quite long in the tooth by now. It is a table-top unit that can play four different compelling games. Game number one is called 'Ditto'. This is a sequence game that relies on the player(s) memory to repeat and ever growing sequence of sounds and lights on the four coloured playing keys. If the player fails to get the right combination Adam responds with an electronic 'raspberry' noise. The sequence is, as far as we can tell, limitless. Our best score on Ditto is a 20-note sequence and we're quite proud of that.

The second game is called Pathfinder and involves the player finding their way out of a hidden maze, again by using the four keys to denote direction of movement of the LED 'man'.

Game number three is called Bounce this is a two or four player reaction game. The players have to press their nearest control key when one of a row of LEDs lights up in the appropriate order. This game is particularly suited to parties where a number of people can join in.

The fourth and final game is not really a game at all. It is called Memory Tune and makes use of the four player keys to record and replay up to 36 notes and spaces. Each of the four individual keys and combinations thereof can be used to create the usual 'doh' 'ray' 'Me' etc. notes and the accompanying song book lists dozens of simple tunes that can be played on Adam's keyboard.

Adam is available under a variety of different names but in general we have found the original Adam to be the cheapest. You can expect to part with £19.95 for this game.

## RAISE THE DEVIL

This game is rather inappropriately named because it is actually a LED pinball game. It is an electronic interpretation of the mechanical pinball table that was popular before the video machines took over. This game also comes from Entex (just like Space Invaders) and is well designed and built,

sufficiently so to stand up to the harsh treatment metered out by our assessment panel.

Basically the game board consists of an array of LEDs that variously represent the ball, bumpers or flippers. The game is played in exactly the same way as the full-size pinball and the scoring is displayed on a two-digit, seven-segment display at the top end of the table.

It's worth shopping around for this game: if you're lucky you can pick one up for as little as £19.95.

## ENTERPRISE

Like Adam, Enterprise has been around for quite some time. It is basically a full function calculator that plays games. Three games are included the first two being 'Speedway', a simple reaction game and 'Brain Drain', a hidden code game that bears more than a passing resemblance to the very popular Mastermind game. The third game is called 'Pontoon': we think it is really the gambling game Blackjack but you'll know what we mean if you manage to get your hands on one.

Overall each of the three games is fun to play, and that alone is a good recommendation. Couple this up with a proficient calculator and you have one of the best deals ever for just £19.95.

## CASIO MG-880

Our last hand-held game is another game/calculator combination, ideal for whiling away boring business meetings or school lessons. Unlike the Enterprise the Casio MG-880 has just one game but its a good 'un.

The calculator is an LCD full-spec machine that has a musical note assigned to each key so that even sim-


ple sums can become quite jolly. In the game mode the player has to 'destroy' an army of alien digits that try to cross the display. To destroy a digit the player has to match the randomly-generated alien digit by pressing a button marked 'aim'. This controls the player's gun digit, and each press of the aim button increments the gun digit up by one. When the gun digit and the alien digit match the 'fire' button is pressed and the alien is destroyed. The game starts slowly but gradually speeds up to the point where the expert Editorial button pushers were giving up. At just £10.95 this is a cheap calculator: with the game its a bargain.

## Video Games

The last four games are all video games. They all rely upon a domestic television receiver that can be used as a display. All of these games are in colour and only work on PAL encoded 625 line receivers. That's unfortunate if you've only got a 405 line black-and-white set but then if you're old fashioned enough to still use an old set like that some new fangled electronic gizmo like a TV game won't be of much interest to you will it?
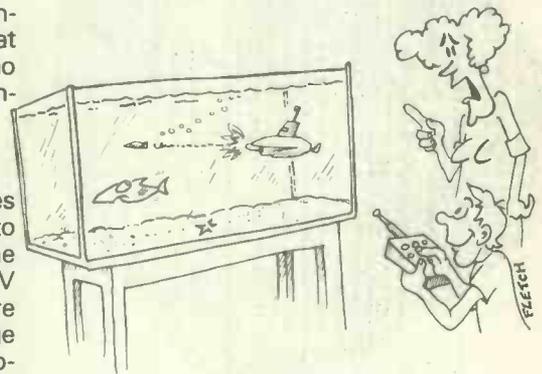
## MATELL INTELLIVISION

There really aren't enough superlatives in the English language to do justice to this amazing piece of design work. The Intellivision is quite simply the best TV game ever. It is expensive but so are Rolls Royces and there's no shortage of customers for them. We're not going to bore you with long descriptions of how marvellous each game is or how versatile it can be when coupled up to a keyboard unit. All we'll say is find £200, go to your nearest stockists and buy one: we promise you won't regret it.



"I TOLD YOU TO LEAVE THE FISH ALONE!"



# Top Ten Electronic Games

## ATARI VIDEO COMPUTER SYSTEM

If you haven't just rushed out to buy an Intellivision because you are not lucky enough to have £200 (and that's the only permissible excuse) then the Atari programmable TV game is a reluctant second choice. The Atari has been around for a couple of years now so again we'll omit the boring details. Price for the basic unit is currently around £99.00. For that you get the main console plus an Air-Sea battle game. There are something like 32 other cartridges available costing from £15 to £35. Worth looking out for are the Space Invaders games, Surround, Maze, Chess and Superman. The game is well established, new cartridges appear on a monthly basis and at least one other company is producing cartridges for this machine so there is little chance you'll ever get bored with it providing you can keep it fed with new games.

## ROWTRON TV GAME

We've included this TV game for two reasons. Firstly it is British designed and built (we're nothing if not patriotic) and secondly the games are unusually fun to play. Unlike the Atari machine more thought seems to have been put into the 'thinking games', games that don't rely purely on manual dexterity. Although only a few cartridges are available at the moment it would seem that Rowtron are busily writing new games right here in this country.

The actual games unit is rather old fashioned looking by contemporary standards and the graphics are not quite up to the excellent Intellivision standards. It is nonetheless an excellent attempt by British industry to regain the market now dominated by American and Oriental machines. (We are sufficiently impressed with this machine to offer it as a prize in our January competition.)

But back to the game: our favourites are undoubtedly the Four In A Row and Maze games. These require a great deal of logical thinking and quick reactions to play. Overall we have no hesitation in recommending this, because the £69.95 price tag for the game and £11.95 for each cartridge makes it an attractive buy for rich dads.

## BINATONE 6

At the low end of the TV game market is the last of our ten games. It is the Binatone 6. The machine is based squarely on the General Instruments AY38500 games chip developed in Scotland about four years ago. It uses the familiar 'ball and paddle' graphics to play Soccer, Table Tennis, Squash and Solo. The rather wicked looking gun supplied with it is used for the two shooting games that make up the fifth and sixth games.

This game is in colour and can be mains powered via an optional adaptor. The sound effects do not come out on the TV speaker! instead they are fed to a speaker within the games console. This game is tried and tested, comes from a reputable manufacturer and above all is almost in the 'pocket money' price bracket. You should be able to find it for as little as £18.95 complete with the gun.

As you may have gathered the ten games we have chosen are a personal choice. That aside our selection has been arrived at after looking at something like 150 different electronic games. You may have noticed that we have left out specialised games like chess, backgammon and bridge — we felt that they were only of interest to those people who regularly play those games.

All that remains now is to wish you happy times with the game of your choice and if you're still undecided then why not have a look at a copy of Gadgets and Games for some more hints and tips on how to buy electronic games.



"LOOKS LIKE GRANDAD WON AT 'KING OF THE JUNGLE' AGAIN!"



"...AND THIS ONE'S ON SPECIAL 'COS WE CAN'T FIGURE OUT HOW TO PLAY IT!"

# COMPETITION



Fast, furious and frantic, that's how we've been for the past couple of weeks. Why? Well, we've been compiling our super famous, stupendous Christmas Competition.

As you can see the theme is electronic games. Our prizes include the amazing new Rowtron programmable TV game and a selection of cartridges, and remember: this game's British.

Our second prize is the very popular Space Invader game from Entex. This is certainly the best hand-held Invader game we've ever seen.

The twenty runners up will all receive the latest Hobby Electronics T-Shirt, never before worn in public. These are strictly limited edition so they'll certainly become collectors' items in the next fifty years or so.

Now how do you win these fabulous prizes? Simple, all you have to do is answer the six simple questions below, complete the phrase and send the answer form, not forgetting your T-Shirt size, to the address below.

Here are the questions:

- 1) Which component is used as a 'White Noise' generator in the Chuffer project this month?
- 2) What is the maximum power rating of each channel in the Sound-To-Light project?
- 3) How many times is the word 'games' used in this month's feature on electronic games?
- 4) Who sells the cheapest BC109 amongst the advertisers in this month's HE?
- 5) What is the maximum number of 'revs' that can be displayed on the HE Tachometer project?
- 6) What is the impedance of the High-Impedance Voltmeter that will be appearing in next month's HE?

Complete the following limerick

Right in the middle of Modmags  
 Clever Dick was opening his mail  
 As he opened on pack  
 It made a loud 'crack'

.....

Name ..... (1) .....

Address ..... (2) .....

..... (3) .....

..... (4) .....

T-Shirt size (S,M or L) ..... (5) .....

..... (6) .....

My suggestion for the last line is: .....

.....



Send this form to: Hobby Electronics Competition. 145 Charing Cross Road, London WC2H 0EE.

All entries should arrive no later than 1st January 1981. Winners will be notified by post. No correspondence regarding this competition will be entered in to. The Editors decision is final.

# MAGENTA ELECTRONICS LTD.

## H.E. PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL THE ELECTRONIC+ AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project — you will need to order the Instruction reprint as an extra 45p each.

DIGITAL SPEEDO, Dec. '80	£35.89
MODEL #RAIN CONTROLLER, Dec. '80	£16.86
BATTERY CHARGE MONITOR, Dec. '80	£4.91
JACK LEAD TESTER, Dec. '80	£1.99
STEREO POWER METER, Dec. '80	£18.98
PARTY GRENADE, Nov. '80	£7.98
TRANSISTOR TESTER, Nov. '80	£5.57 inc. test leads
DOUBLE DICE, Nov. '80	£13.80
GUITAR PRE-AMP, Nov. '80	£5.65 case (diecast) extra £2.99
BATTERY ELIMINATOR, Nov. '80	£14.88
NOBELL DOORBELL, Oct. '80	£11.98
INTRUDER ALARM, Oct. '80	£17.83
FREEZER ALARM, Oct. '80 with probe	£9.42
TUG O' WAR, Oct. '80	£16.98
KITCHEN TIMER, Oct. '80 (2% resistors)	£7.34
MICROMIX, Sept. '80	£7.82
AUTO PROBE, Sept. '80	£3.67 less case
TOUCH SWITCH, Sept. '80	£2.34 less case & contacts
GUITAR PHASER, Sept. '80	£13.84
DEVELOPMENT TIMER, Sept. '80	£11.93
BENCH PSU, Sept. '80	£28.50
EQUITONE CAR EQUALISER, Aug. '80	£14.98
GAZTEC GAS DETECTOR, Aug. '80	£24.98
OP AMP CHECKER, Aug. '80	£4.55
MOVEMENT ALARM, Aug. '80	£5.68
RADIO TIMER, Aug. '80	£6.98
PASS THE LOOP GAME, Aug. '80	£13.98
SOUND OPERATED FLASH TRIGGER, July '80, no skt.	£4.59
18W+18W CAR STEREO BOOSTER, July '80	£29.98 (stereo)
FOG HORN, June '80	£5.65
EGG TIMER, June '80	£8.99 less case
5080 PRE-AMP, May '80	£39.98
SPEED CONTROLLER FOR R/C, April '80	£14.92 less case
DIGITAL FREQUENCY METER, April '80	£35.78
HOBBYCOM: TWO WIRE INTERCOM, April '80	£33.95 (Master)
Sub Station	£3.58 each
ELECTRONIC IGNITION (CD), April '80	£20.87
25-WATT MODULE (5080), Mar. '80	£17.98
PSU MODULE (5080), Mar. '80	£33.75
WIN INDICATOR, Feb. '80 (with switches)	£13.92
DIGI-DICE, Jan. '80	£9.98
BARGRAPH CAR VOLTMETER, Dec. '79	£7.33 less case
RING MODULATOR, Dec. '79	£12.95
GUITAR TUNER, Nov. '79	£10.98
FRANTRUM STEREO AMPLIFIER, Oct. '79	£79.50
HOBBYTUNE, Oct. '79	£26.98
ANALOGUE FREQUENCY METER, Oct. '79	£15.52
MULTI-OPTION SIREN, Oct. '79	£15.98
STARBU' RST, Sept. '79	£19.98 less case
ULTRASONIC SWITCH, Sept. '79	£28.85 less 3 pin mains socket
HOME SECURITY UNIT, Aug. '79	£28.56 less siren
SIREN	£5.09 less case
LED TACHOMETER, Aug. '79	£17.98
INJECTOR TRACER, Aug. '79	£4.34
CONSTANT VOLUME AMPLIFIER, Aug. '79	£15.60
LINEAR SCALE OHMMETER, July '79	£15.98
SHARK, July '79	£25.98
GSR MONITOR, June '79	£9.63
ENVELOPE GENERATOR, June '79	£14.98
PARKING METER TIMER, May '79	£8.79
WHITE NOISE EFFECTS UNIT, May '79	£17.74
TRANSISTOR GAIN TESTER, April '79	£9.98
PHOTOGRAPHIC TIMER, Mar. '79	£16.45
CAR ALARM, Feb. '79	£10.98
SCRATCH/RUMBLE FILTER, Feb. '79	£25.48 Mono £29.98 Stereo
SINE/SQUARE WAVE GENERATOR, Feb. '79	£25.78
GRAPHIC EQUALISER, Jan. '79	£28.68
PUSH BUTTON DICE, Dec. '78	£6.98
AUDIO MIXER, Dec. '78	£25.98
BEDSIDE RADIO, Nov. '78	£16.99
STEREO AMPLIFIER (HOBIT), Nov. '78	£59.50

LATEST KITS: S.A.E. OR PHONE FOR PRICES

## 80/81 ELECTRONICS CATALOGUE

KITS  
ICs  
TRANSISTORS  
CAPACITORS

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery by FIRST-CLASS POST. Send 70p in stamps for your copy (7 x 10p or 5 x 14p).

TOOLS  
RESISTORS  
HARDWARE  
CASES

## ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects — including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S Dec and the components for the projects. Adventures With Electronics £1.75. Component pack £16.72 less battery.

## ADVENTURES WITH MICROELECTRONICS

Same style as above book. 11 projects based on integrated circuits — includes dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes Bimboard 1 plug-in breadboard and the components for the projects. Adventures with Microelectronics £2.35. Component pack £27.95 less battery.

## H.E. LADDER OF LIGHT, JAN. '81

Complete kit for this novel project includes all components and case for the control module. 10 individual outputs EXTRA included with our kit only: additional circuit and components for strobe and chase features. LADDER OF LIGHT, JAN '81 £29.98 + 40p p&p.

## H.E. MEMORY BANK — SYNTHESISER NOV. '80

Complete kit for this exciting project, includes i.c. with socket, 2 pcbs, case etc. The custom designed i.c. at the heart of this project generates musical sounds which can be stored in its own memory. Features include memory erase, vibrato, speed and depth controls, variable pitch, chord and tremolo etc. 'Synthesiser' Nov. '80 + Dec. '80 £33.95

## INTO DIGITAL ELECTRONICS

Current H.E. series. Part 1 in Sept. '80. Covers digital electronics from the basics. Circuits are built on a plug-in Eurobreadboard. Reprints of back issues available 45p each. Eurobreadboard and components for series £18.95 less battery. Components only £12.75.

## INTO ELECTRONICS CONSTRUCTION

H E 6-part Series: Feb. '80 to July '80. COVERS THE BASICS OF ELECTRONICS — LOTS OF PRACTICAL WORK. Circuits are built on a plug-in Eurobreadboard. REPRINTS AVAILABLE, 45p each part. Eurobreadboard and Components for Series £15.63. Components only £9.43.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR £10.50  
ANTEX SOLDERING IRON 25W £9.98.  
SOLDERING IRON STAND £1.98.  
SPARE BITS. Small, standard, large 65p each.  
SOLDER. Handy size 98p.  
EUROBREADBOARD £6.20.  
LOW COST LONG NOSE PLIERS £1.68.  
LOW COST CUTTERS £1.69.  
P.C.B. ASSEMBLY JIG £11.98.  
P.C.B. ETCHING KIT £4.98.  
AM-FM AIRCRAFT BAND PORTABLE RADIO £9.98.  
WIRE STRIPPERS AND CUTTERS £2.48.  
MULTIMETER TYPE 1. 1,000 o.p.v. with probes 2 x 3½ x 1 £6.66.  
MULTIMETER TYPE 2. 20,000 o.p.v. with probes 5 x 3½ x 1¼ £11.52.  
TELEPHONE PICK-UP COIL 72p.  
CRYSTAL MICROPHONE INSERT 58p.  
SPEAKERS MINIATU' E, 8 ohm 87p. 64 ohm 98p. 80 ohm £1.56.  
PILLOW SPEAKER, 8 ohm 98p.  
EARPIECES, Crystal 85p. Magnetic 18p.  
MONO HEADPHONES, 2K Padded, Superior sensitive £2.98.  
HEAT SINK TWEEZERS 15p.

### 3 BAND S.W. RADIO

Simple T.R.F. Design. Covering most Amateur Bands and Short Wave Broadcast Bands. Five controls. Bandset, Bandspread Reaction, Wavechange and Attenuator. Coil section is by Wavechange Switch. Use with Headphones or a Crystal earpiece. Kit contains all the components required including the P.C. Board and Case. Instructions are included with this kit. KIT £18.97. Headphone extra £2.98.

SOLDER BOBBIN 30p.  
DESOLDER PUMP £5.98.  
CROC CLIP TEST LEAD SET. 10 leads with 20 clips 98p.  
CONNECTING WIRE PACK. 5 x 5 yd. coils 65p.  
VERO SNOT FACE CUTTER £1.21.  
RESISTOR COLOUR CODE CALCULATOR 21p.  
STEREO HEADPHONES. 6 ohm. Padded £4.35.  
DESOLDERING BRAID 69p.

## MAGENTA ELECTRONICS LTD.

HE 5, 98 CALAIS ROAD, BURTON-ON-TRE' +, STAFFS, DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI. MAIL ORDER ONLY

ADD 40p P.&P. TO ALL ORDERS. ALL PRICES INCLUDE 15% V.A.T. OFFICIAL ORDERS FROM SCHOOLS ETC. WELCOME. ENQUIRIES MUST INCLUDE S.A.E. OVER-EAS: SEND ORDER WITH 3 INTERNATIONAL POSTAL COUPONS WE WILL QUOTE EXACT PRICE BY AIR MAIL. EIRE & BFPO ORDERS U.K. PRICES — LESS 10% (COVERS V.A.T. REF+ND & EXPORT DOCUMENTS). PAYMENT: STERLING U.K. BANK DRAFT, U.K. POSTAL ORDERS OR U.K. CHEQUE. ENQUIRIES: ENCL0+ 2 INTERNATIONAL POSTAL COUPONS.



# What's In A Name

This month's sense is sound: Rick Maybury describes some of the devices for producing it


LAST MONTH, you may remember we began a short series looking at electronic systems and components that duplicate our own five senses. For the next two months we shall be looking at the subject of Audio Electronics — components or devices that respond to or generate sound. This month we shall look at devices that make noises.

To understand the action of the electronic counterparts of our vocal chords, it is first necessary to have some idea of what sound actually is.

Sound is basically a mechanical vibration that can travel through any medium (though not a vacuum) whether it is solid, liquid or gaseous. The old analogy of ripples on a pond is still the best way of visualising a sound wave. If we throw a stone into a still pond then a series of ripples spread outwards from the centre. If we compare this with the action of sound in air we can see that the high point of each ripple or wave corresponds to a peak of air pressure, the trough or low point of each wave corresponding to an area of low air pressure.

You can perhaps understand this better if I tell you the story of a lunatic Frenchman at the turn of the century. He devised and built an enormous whistle, many feet long and several feet wide. A huge blast of compressed air down the whistle produced a note that was only a couple hertz in frequency. It was said that one of his assistants standing in front of the whistle was killed instantly. Although the note was too low to be heard by human ears the pressure wave was so great that, at the high-pressure peak, his body was literally enveloped in compressed air and a quarter of a second later it was subjected to a partial vacuum as he was hit by the low pressure wave. His body was literally sucked apart — a nasty way to go!

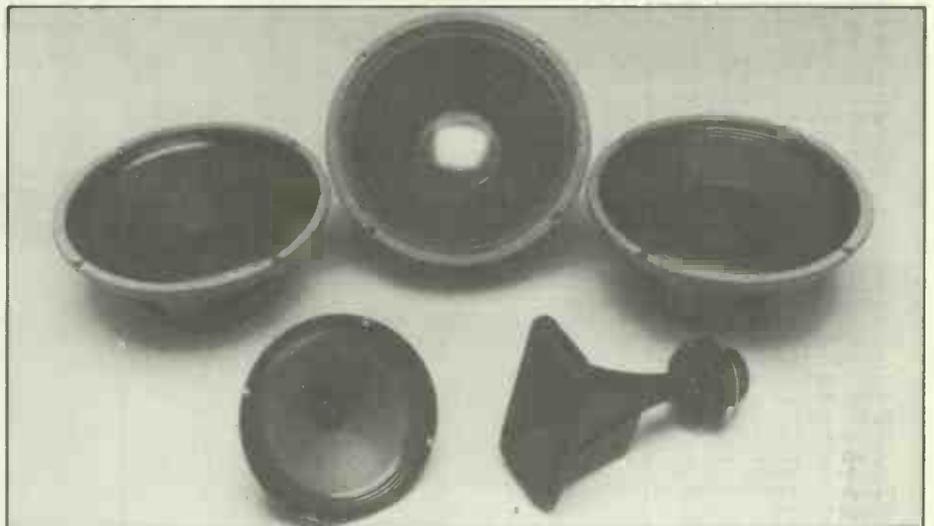If we want to generate sound electronically we have to devise some way of creating high and low pressure waves in the air. The simple way is to take a large flat surface, couple it in the centre to a strong electromagnet and pass an alternating current through the coil of the electromagnet. This will have the effect of moving the flat surface forwards and backwards thus



creating an alternating pattern of high- and low-pressure waves. The idea has been refined and improved upon mechanically by exchanging the flat surface for a shallow cone supported in a circular metal frame. We all know this as our old friend the loudspeaker.

The speaker isn't the only device that can make noises. On a smaller scale headphones and earphones use a variety of moving coil, piezo-electric or electrostatic devices to vibrate the acoustic surfaces or diaphragms. The use of the piezo-electric effect in earphones relies upon the mechanical distortion of quartz crystal when a voltage is applied across the face of the crystal. The crystal is then coupled mechanically to the diaphragm. Electrostatic loudspeakers and head-

phones use the attractive and repulsive properties of high-voltage charges on two plates in close proximity to each other. In some older types of loudspeaker the cone was attached to a permanent magnet that was inside an open-wound electromagnet: not surprisingly these are known as moving-magnet loudspeakers. As you can imagine there are dozens of ways electrically and electronically generating sound: the one thing to remember, however, is that all rely upon a mechanical action to create waves of varying air pressure. Next month we'll look at how we can turn these sound waves back into electrical signals and also the similarities between our own ears and electronic microphones.

HE

# TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians  
Radio, T.V. Electronics Technicians  
Radio Amateurs  
Electrical Installation Work

## Diploma Courses

Colour T.V. Servicing  
CCTV Engineering  
Electronic Engineering & Maintenance  
Computer Engineering and Programming  
Radio, T.V. and Audio, Engineering & Servicing  
Electrical Engineering, Installations & Contracting

## Other Career Courses

A wide range of other technical and professional courses are available including GCE.

**FREE BOOK**

To ICS, Dept. Z263, Intertext House,  
London SW8 4UU

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_


**ICS**

To ICS, Dept. 263C, Intertext House,  
London SW8 4UJ  
or telephone 01-622 9911 (all hours)

7 SEGMENT DISPLAY HEWLETT-PACKARD High Efficiency "Ultra bright" half inch rad. Common anode type 5082-7650 (similar to D1707). Gamma Cathode version 5082-7653 (similar to D1704). OUR PRICE BRAND NEW £1. Set of six of either type. £5 incl. VAT.		HALF PRICE OFFER
FAIRCHILD PHOTO 0.25" Mini rad 7 segment display. Common anode. 50p 5 for £2.50		
<b>LP1171 &amp; LP1179 MODULES MULLARD</b>		
LP1171 and LP1179 tuning heart and IF modules which form the basis of a quality AM/FM tuner. Full medium long-wave and VHF coverage. May be used as the basis of a quality portable or tuner. Supply 6V at 15mA output 70mV at 20K. Pair £9.75. SUPPLIED COMPLETE WITH DATA		
LP1157 Medium & Long Wave Tuner, module heart £2.50 LP1186 Vericap £5.00		
<b>5+5 Watt Car Stereo Amplifier made for Motorola</b>		
★ WITH pre-amplifier and M. & Long Wave assembly. ★ 5+5 watt stereo amplifier 12/14 volt 4 x 2 x 1". ★ Supplied as two built and tested units. ★ Complete with circuit, data and connection diagrams. ★ R.F. and L.F. stereo pre-amplifier and radio 4 x 2 x 1". ★ Limited quantity available. ex-stock.		
<b>EX-MOTOROLA Only £9. Post 50p</b>		
PRO 825 Professional capacitor boom-arm microphone by Eagle. A graceful 50 cm boom-arm capacitor ribbon microphone with a cardioid capsule. A high standard of finish for in-venue use and yet robust enough to withstand long periods between maintenance. Supplied complete with 170d and 1 black windshield and 6 metres of twin screened cable terminating at the microphone end in an XLR connector. Impedance: 600 ohms (floating). Response: 20-18,000 Hz. Sensitivity: -70 dBV. Cable: 6 metres two conductor shielded. Connector: XLR 3-11C. Battery type: NP7.		LIST PRICE £37.40 OUR PRICE <b>£19.95</b> inc. VAT POST £1.50
DRYFIT RE-CHARGEABLE BATTERY, 6 volt 4.5 amp/h. Size 6" x 3 1/4" x 1 1/4" at half price. Brand new £7.50, post 50p   MIN. EDGE INDICATORS WITH LAMP, 0-100 MICRO AMP 6 for £8.50 INDICATOR METERS, 200 Micro, 1 1/4" x 1 1/4" x 1/4", 6 for £5		
TRANS. AMPLIFIERS. Contains two Feeder type moving coil, mikes/earphones, V/C and switches as used on aircraft for passenger listening. £1.50 P.P. 25p 10 for £12.50 SANGAMO HOUR METER, 9999.8 non reset. £4.50. 1 1/2" sq. 2" deep		
MANS TRANSFORMERS all 200/250V input.		MULLARD TB4000, IC audio amplifier, £1. RCA CA3098, FM IF £1.50. RCA CA3090AQ, FM decoder £2.50. BU208 TEXAS, £1.50 min. 10 for £12. BU208 T03 Texas TV power transistor, 10 for £15. 100 for £120. MULLARD AD161-AD162, Matched pair 80p, 10 pairs £8. 100 pairs £50. Carbons at 600 pairs £250 EX-STOCK. 5 or 12 volts TB4625 ATES voltage regulators 50p ea. 1000s/amps (1099) per 10 £4.50. CA3098 RCA POSITIVE VARIABLE 5 volt 100m amp variable. 18/24V 95p ea. TEXAS 10 WATT, C. Amp SA76016 5-pin package £1.20. 10 for £10. TA4081B (14 pin DIL) IC TV sound amplifier-detector by ATES as a circuit, other parts. Complete with data. 60p. 10 for £5. 100 for 40p ea.
2W MIN. W/W VOL. CONTROLS 10K-47K. 10 for £6		
10 TURN POTS. 47K 100K. 10 for £17.50		
STEREO CASSETTE TAPE HEAD, High quality replacement for most machines record/record with mounting bracket £2.95		EX12 E307 Erase 675 ohms 2mA ..... £9.98 EX20 E302 Erase 90 ohms 90mA ..... £9.98 MiniMax Tape Heads 1/4 Track NMG Erase ..... £2.25 KMS-T with Mini-metal screen ..... £2.50 WMS-T with Mini-metal screen ..... £2.50 L76 Erase head ..... £5.99 D/RP/1/3 Record/Play 1/4 track head ..... £0.85 NR-RP Single track Record/Play head 0.2H at 60/75, 60 KHz impedance of 50 Kc/s. 600 current 2005A ..... £0.55
XRPS (X240P 10), 1/4 track, Rec./Play medium imp. £3.25 XRPS36 (X240P36), 1/4 track Record/Play low imp. £4.00 XES11 (X240E31 1) 1/4 track erase for XRPS series £1.25 EX-RP/63 1/4 track Record Play Head (black/red) £2.25 EX12E343 1/4 track Erase Head for above £1.25 EX11 E308 Erase 675 ohms 2mA ..... £8.88		
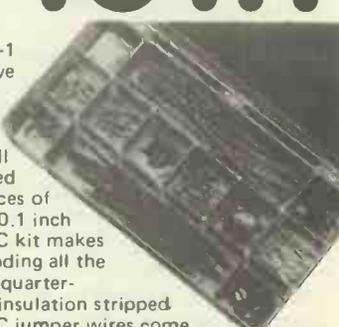
# JUMP TO IT!

Climb aboard the breadboarding bandwagon with CSC's new WK-1 wire jumper kit - just what you've always wanted to make breadboarding easier and quicker than ever before. Here, in one neatly compartmented box, are all those different lengths of insulated hook-up wire you need - 25 pieces of each, in 14 lengths ranging from 0.1 inch to 4 inches. What's more, the CSC kit makes your job even easier by colour-coding all the different lengths and providing a quarter-inch length at each end with the insulation stripped off and bent through 90°. So CSC jumper wires come ready to plug straight into your quick-test sockets, bus strips or breadboard system. No more fiddling around with wire cutters, strippers or pliers - everything you need in one box. Take the plunge right now by filling in the CSC coupon.



CSC (UK) Ltd., Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: (0799) 21682. Telex: 817477.

Unit price inc. P&P 15% VAT £6.90 Only Read!

Please deduct £1 postage from each additional order.

I enclose cheque/PO for £ \_\_\_\_\_  
or debit my Barclaycard, Access, American Express card

No. \_\_\_\_\_ Exp. date \_\_\_\_\_  
or Tel: (0799) 21682 with your card number and your order will be in the post immediately.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CONTINENTAL SPECIALTIES CORPORATION

CSC

FREE catalogue tick box

Continental Specialties Corporation (UK) Limited, Dept. 14RR  
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

## TOMORROW'S TOOLS TODAY

Hobby Electronics, January 1981

# Car Rev Counter




Yet another application of the now famous LM3914 dot/bar voltmeter chip — this tachometer project is designed to complement our Digital Speedo in both style and size — fit them both into the same case or use them individually.

NO, IT'S NOT true! We haven't got shares in National Semiconductor, the manufacturer of the LM3914. Neither do we accept bribes (unless they are in cash — used £1 notes — and handed to us in a plain brown envelope). The simple fact of the matter is that the LM3914 is so versatile and adaptable that literally thousands of projects can be built around it, so it is no wonder that we do tend to use it a lot (see our Sound-to-Light Converter in this issue). The HE Rev Counter uses two LM3914s coupled in series mode, so that not just the normal ten LEDs (associated with the chip) but *twenty* LEDs give indication of engine revs in a direct-reading, linear display.

You will see from the photographs that we built our model into the same case as the Digital Speedo — that is the reason for the cut-out in the Speedo display board — so that a neat combination of digital-speed and 'line of LED' — revs readouts is obtained which is good enough to take pride of place in either your Metro or your Silver Spirit. Alternatively both projects can be constructed and used individually (and then you can put one in each car!).

For adaptability, the Rev Counter has been designed so that it can be used with most car engines; ie 4-cylinder 4-stroke; 6-cylinder 4-stroke; 8-cylinder 4-stroke, but it is possible that the device may function with other engines. A simple

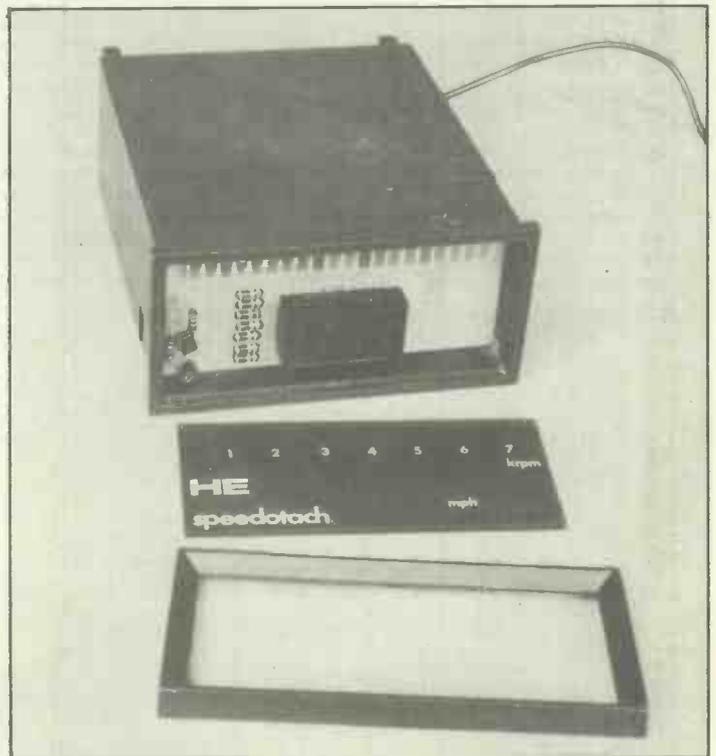The HE Car Rev Counter in the same case as the HE Speedo. Another name for a rev counter is a tachometer - hence the HE Speedotach




calculation tells you if your engine will suit: you need to know the number of cylinders of the engine (n) and how many strokes each cylinder makes between ignition cycles (m). Next, divide the value of n by that of m.

Taking, for example a 4-cylinder 4-stroke engine the calculation is:

$$\frac{4}{4} = 1.$$

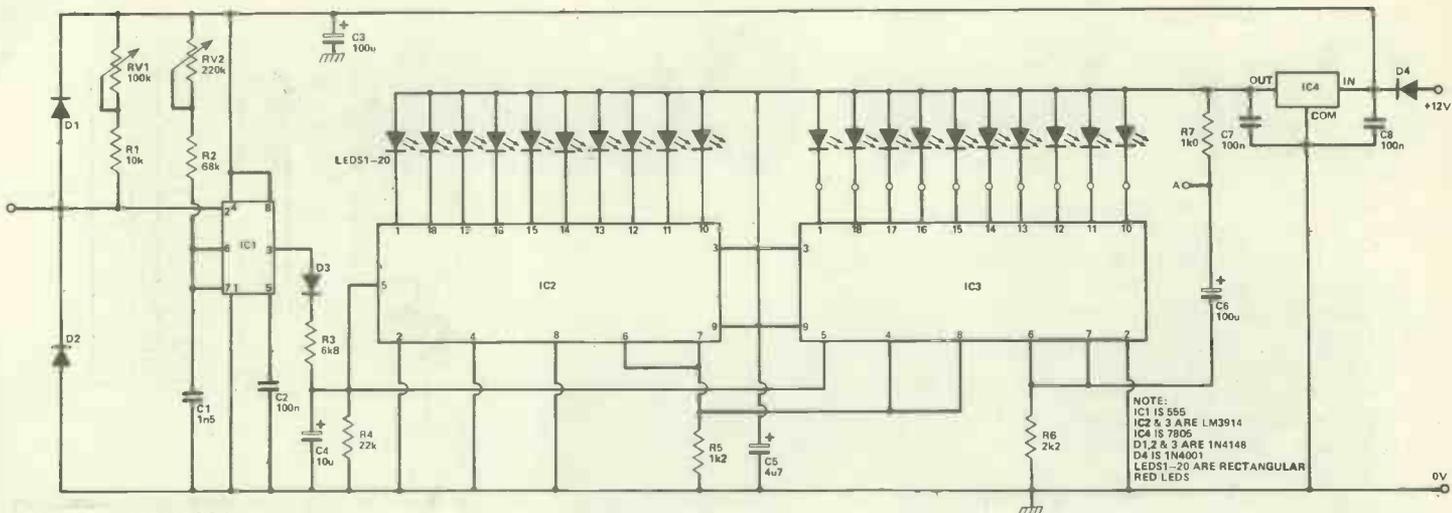The answer for the chosen engine must fall (as in the above example) within the range 1 to 2. If so, the engine suits the Rev Counter. One final point is that the engine must be petrol-driven as diesel types do not have the necessary ignition circuitry.



© Copyright MODMAGS Ltd.

Figure 1. Circuit diagram of the HE Car Rev Counter

## How It Works

A standard car engine relies on the combustion of an explosive mixture of petrol and air within a confined chamber. The combustion is brought about by a spark generated at the spark plug gap with a very high voltage across it. A particular engine might have two of these explosions per revolution of the engine, thus at say 1000 RPM there will be 2000 high voltage pulses every minute, generated by the electrical system of the car. Thus, the number of pulses gives a direct measure of the revolution rate of the engine.

Now, a change of voltage within a length of conductor, such as the main high tension lead from the car's coil to distributor, creates a changing magnetic field around the conductor. Similarly, if another length of conductor is placed in

close proximity to the first, the changing magnetic field produces a secondary changing voltage in the second conductor. (Incidentally, this is the principle of operation of all transformers — see last month's *O Level Q & A*).

The HE Rev Counter uses this secondary pulse to trigger a monostable multivibrator, built around IC1, a 555. Figure 2 shows input and output waveforms of this part of the circuit. From this you will see that no matter how often the input pulses occur (two per engine revolution), the output waveform has an 'on' time which does not change — the output pulses simply get closer together or further apart depending on the input frequency. Capacitor C1 and resistors RV1 and RV2 define the 'on' time, the larger the values the longer the 'on' time. It can


also be seen from this diagram that the average voltage at the output of IC1 will be at a maximum when the pulses are close together and at a minimum when the pulses are far apart. Consequently, as the RPM rate goes up so does the average output voltage. The resistor/capacitor combination R3, 4 and C4 smooths out the voltage so that a steady DC voltage, which changes only with engine speed, is obtained across C4.

The remainder of the circuit, formed by two LM3914s and associated components, is a bargraph voltmeter. This simply measures the voltage across C4 and illuminates a line of LEDs. The higher the voltage, the more LEDs in the line light. Preset RV2 is adjusted so that at a known engine speed the correct LED just lights up.

By connecting point A on the PCB to one of the LED cathodes by a wire link, a facility is used whereby the LEDs in the upper half of the display flash whenever the voltage corresponding to the LED is exceeded. For example, if A is connected to the LED which indicates 5000 RPM, whenever the engine speed reaches 5000 RPM the LEDs in the upper half flash to warn the driver that he is over-revving the engine. If the Tacho is scaled (as ours was) up to 7000 RPM then any engine speed in the range 4000 to 7000 RPM can be used to trigger this flashing display.

Finally, IC4 is a voltage regulator which provides a stable 5 VDC supply for the LEDs and IC2 and IC3.

Figure 2. Waveforms of the circuit

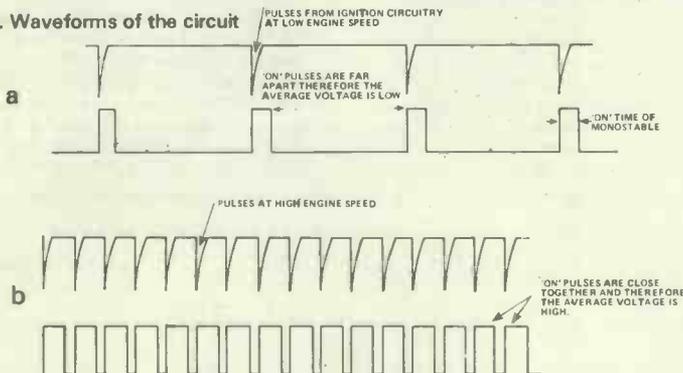


## Construction

Construction of the PCB is reasonably straightforward. Insert the four links first followed by resistors, capacitors and IC sockets. All semiconductors (except LEDs) should be put in next, noting correct polarity. Bend the pins of voltage regulator IC4 at right angles, about 1/8" from the body and mount it flush to the board.

The leads of LEDs 1 to 20 need to

be shaped correctly so that they all fit onto the edge of the board. We used rectangular LEDs which are exactly 0.15" on their narrowest width, so 20 fit along a 3" length of board. Each LED fits up to the edge of the board with the cathode above the board and the anode below. Following the diagram in Fig. 3, and using a good pair of fine, long-nosed pliers, bend the leads at right angles at exactly the distances shown and

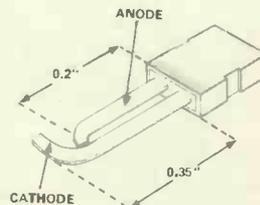

© Copyright MODMAGS Ltd.

Figure 3. The leads of all 20 LEDs need to be bent to fit the board

then cut off the excess leads as in the diagram. These measurements are fairly critical to enable the LEDs to fit on the board. When the leads are correctly shaped each LED can then be inserted — this is a fiddly job, so take care not to damage the devices. Solder them in place, making sure they all line up perfectly.

The final thing to do on the PCB is to link up point A to whichever LED you require the flashing display to occur on. If you don't want this facility, simply omit this link.

When completed, the board will slide directly into its case — the DIN style case used in the Digital Speedo. Each circuit, the Speedo or the Rev Counter will work individually so they can be built into separate cases if you wish, but for a really neat project both fit in the same case with excellent results which you can see in the photographs. Note that for correct operation (ie with the LED display reading from left to right), the Rev Counter PCB needs to be 'upside-down' — with the component side facing down.

Only three connections are made to the board, power supply (via an in-line 1 A fuse and holder) through the ignition switch circuitry, and the sensor. The sensor is simply a length of thin multi-strand wire which goes from the PCB to the high tension lead between the car's coil and distributor. There is *no* electrical connection involved — the pick-up is purely electromagnetic. Cable ties can be used to hold the wires.

The procedure for setting up is reasonably easy. Presets RV1 and RV2 are adjusted fully clockwise. Then, with the car engine running at tick-over speed, RV1 is slowly adjusted anti-clockwise until the line of LEDs burst into life. The preset adjusts the threshold of the Rev Counter and its setting is not in the slightest critical (about mid-position should suit most applications) but it can be used to prevent spurious triggering in certain applications.

Preset RV2 is now adjusted so that a particular LED lights up at a known engine speed. Ideally, for this purpose you will need a calibrated tachometer or rev counter to compare yours with, operating at a set speed of say 3000 RPM. As a last resort (if you can't obtain a calibrated tacho) you can simply adjust RV2 at tick-over till the first couple of LEDs in the line are lit. This is, however, only an approximate calibration and cannot be as accurate as the suggested method.

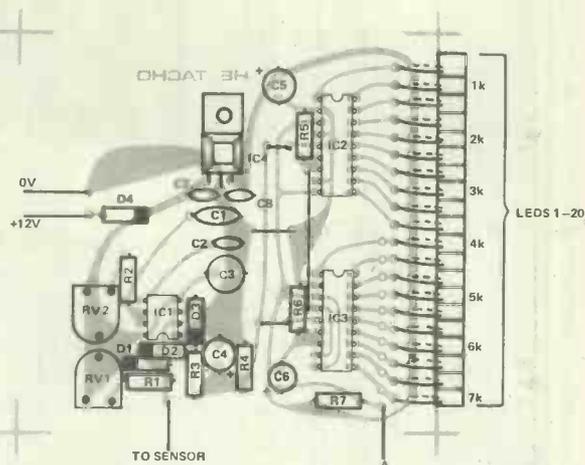


Figure 4. Overlay of the circuit board

## Parts List

### RESISTORS (All ¼ W, 5%)

R1	10k
R2	68k
R3	6k8
R4	22k
R5	1k2
R6	2k2
R7	1k

### POTENTIOMETERS

RV1	100k miniature horizontal preset
RV2	220k miniature horizontal preset

### CAPACITORS

C1	1n5 polystyrene
C2,7,8	100n resin dipped ceramic

C3,6	100u 16 V printed circuit electrolytic
C4	10u 35 V tantalum
C5	4u7 35 V tantalum

### SEMICONDUCTORS

IC1	555 timer
IC2,3	LM3914 dot/bar display driver
IC4	7805 5 V, 1 A voltage regulator
D1,2,3	1N4148 diode
D4	1N4001 1 A diode
LED 1-20	rectangular red LEDs

### MISCELLANEOUS


case to suit (see Buylines)  
in-line fuse holder + 2A fuse

## Buylines

All parts for our Rev Counter are fairly standard and should be easily obtained. The approximate cost of all components (excluding as usual, the case and PCB) should be around £18 — the most expensive items being the 20 LEDs. The rectangular LEDs can be replaced by ordinary circular LEDs if you wish, but they must measure no more than 0.15" in diameter, or they will simply not fit the

board.

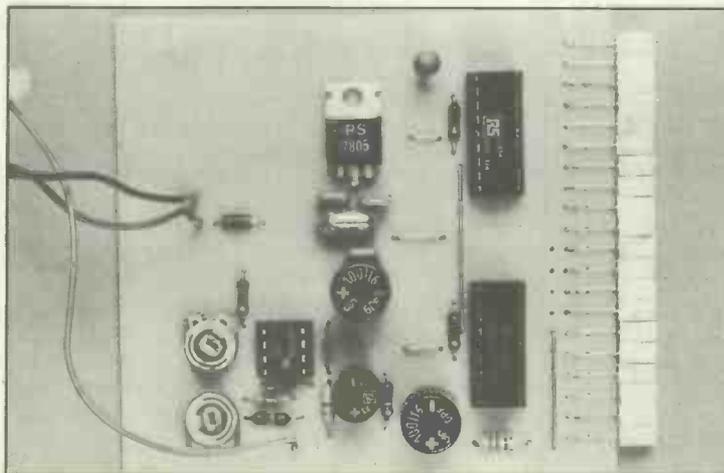The case is the same as used in the HE Digital Speedo (see this and last month's issue) and is RS Components stock number 508-683. Your local component supplier should be able to obtain it for you. Of course, if you are building both projects they will fit in the same case, saving the need to buy two.



# hobbikits from vero



Electronic Kits from the British company that has always believed the Electronics Hobbyist deserves the same high quality as our industrial customers. Choose from a wide range of Hobbikit projects, that include an Ultrasonic Trnsmitter and receiver, Smoke and Gas Detector, Continuity Tester, Model Train Controller, and a complete Stereo Amplifier System that you can build up in modules.



**look** for the **vero** where you buy your electronic components

## DO YOU EVER NEED A FEW MORE HANDS? ABSONGLEN ANNOUNCES THE NEW MINIBENCH 2\* WITH THE MINIBENCH SYSTEM



- Just a squeeze needed to clamp or release the circuit board.
- Adjustable minimum jaw aperture.
- Jaws flip over for work on either side of circuit board.
- Rubber-lined jaws for circuit board protection and maximum grip
- Single wing nut adjusts friction control and jaw attitude.
- Crocodile clips mounted on flexi-arms hold components exactly where needed.
- Crocodile clip can be used as heat shunt.
- Lens similarly mounted is ideal for close work and spotting those solder bridges.
- Flexi-arms are mounted on the jaw assembly to keep station with the circuit board.
- 6 separate flexi-arm mounting positions.
- A typical configuration would consist of 2 flexi-arms with clips and one with lens.
- Attractive two-tone stove enamelled finish.
- Built to last a lifetime.



★ Trade Mark

Patented

TO: ABSONGLEN LTD. DEPT. HE

Name .....

Address .....

Post Code .....

Please supply:

Minibench 11 £12.95

Flexi-arms with Clips @ £4.75 ent.

Flexi-arms with Lens @ £5.75 ent.

Postage and packing - £2.00

★ Price applicable to Minibench purchasers only

Remittance enclosed for

**ABSONGLEN LTD, DEPT. HE**  
THE FORGE, STAPLOW  
LEDBURY, HEREFORDSHIRE HR8 1NP

# AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

## LINEAR ICs - NUMERIC LISTINGS

TBA1205	1.00	KB4413	1.95
L200	1.95	KB4417	1.80
U27B	1.28	TDA4420	2.25
U27B	1.28	KB4420B	1.09
U257B	1.28	KB4423	2.30
U267B	1.28	KB4424	1.65
LM301H	0.67	KB4431	1.95
LM301N	0.30	KB4432	1.95
LM308H	0.96	KB4433	1.52
LM308N	0.65	KB4436	2.53
LM339N	0.66	KB4437	1.75
LM348N	1.86	KB4438	2.22
LF351N	0.38	KB4441	1.35
LF353N	0.76	KB4445	1.29
LM374N	3.75	KB4446	2.75
LM380N-14	1.00	KB4448	1.65
LM380N-8	1.00	NE5044N	2.26
LM381N	1.81	NE5532N	1.85
ZN419CE	1.95	SD6000	3.75
NE544N	1.80	SL6270	2.03
NE555N	0.30	SL6310	2.03
NE556N	0.50	SL6600	3.75
NE560N	3.50	SL6640	2.75
NE562N	4.05	SL6690	3.20
NE564N	4.29	SL6700	2.35
NE565N	1.00	ICL8038CC	4.50
NE566N	1.60	MSL9362	1.75
NE570N	3.85	MSL9363	1.75
SL624	3.28	HAI1211	1.95
TBA651	1.81	HAI1223	2.15
UA709HC	0.64	HAI1225	1.45
UA709PC	0.36	HAI2002	1.45
UA710HC	0.65	HAI2017	0.80
UA710PC	0.59	HAI2402	1.95
UA741GH	0.66	HAI2411	1.20
UA741CN	0.27	HAI2412	1.55
UA747CN	0.70	LF13741	0.33
UA748CN	0.36	SN7660N	0.80
UA753	2.44		
UA758	2.35		
TBA810AS	1.09		
TBA820M	0.75		
TC940E	1.80		
TD102B	2.11		
TD102P	2.11		
TD105A	1.45		
TD106E	1.95		
TD107E	2.69		
TD1074A	5.04		
TD1083	1.95		
TD1090	3.05		
HAI137	1.20		
HAI196	2.00		
HAI197	1.00		
TD1220	1.40		
LM1303	0.99		
LM1307	1.55		
MCI310P	1.90		
MCI330	1.20		
MCI350	1.20		
HA1370	1.90		
HA1388	2.75		
TD1490	1.86		
MCI496P	1.25		
SL1610P	1.60		
SL1611P	1.60		
SL1612P	1.60		
SL1613P	1.89		
SL1620P	2.17		
SL1621P	2.17		
SL1623P	2.24		
SL624C	3.28		
SL1625P	2.17		
SL1626P	2.44		
SL1630P	1.62		
SL1640P	1.89		
SL1641P	1.89		
TDA2002	1.25		
TDA2020	3.00		
ULN2242A	3.05		
ULN283B	1.00		
CA3080E	0.70		
CA3089E	1.84		
CA3090AQ	3.35		
CA3123E	1.40		
CA3130E	0.80		
CA3130T	0.90		
CA3140E	0.46		
CA3189E	2.20		
MC3357P	2.35		
LM3900N	0.60		
LM3909N	0.68		
LM3914N	2.80		
LM3915N	2.80		
KB4400	0.80		
KB4406	0.60		
KB4412	1.95		

## FREQUENCY DISPLAY & SYNTHESIS ICs

SAA1056	3.75
SAA1058	3.35
SAA1059	3.35
11C900D	14.00
LNL232	19.00
LNL242	19.00
MSL2318	3.84
MSM5223	11.30
MSM5224	11.30
MSM5225	7.85
MSM5226	7.85
MSM5227	9.75
MSM52271	9.75
ICM7106CP	9.55
ICM7107CP	9.55
ICM7216B	19.25
ICM7217A	9.50
SP8629	3.85
SP8647	6.00
95H90PC	6.00
HDL0551	2.45
HDM4015	4.45
HDL2009	6.00
HDM4752	8.00

## CMOS 4000 SERIES

4001	0.17
4000	0.17
SL624C	3.28
SL1625P	2.17
SL1626P	2.44
SL1630P	1.62
SL1640P	1.89
SL1641P	1.89
TDA2002	1.25
TDA2020	3.00
ULN2242A	3.05
ULN283B	1.00
CA3080E	0.70
CA3089E	1.84
CA3090AQ	3.35
CA3123E	1.40
CA3130E	0.80
CA3130T	0.90
CA3140E	0.46
CA3189E	2.20
MC3357P	2.35
LM3900N	0.60
LM3909N	0.68
LM3914N	2.80
LM3915N	2.80
KB4400	0.80
KB4406	0.60
KB4412	1.95

## TTL N and LSN

7400N	0.13	7443N	1.15
74LS00	0.20	7444N	1.12
7401N	0.13	7445N	0.94
74LS01	0.20	7446N	0.94
7402N	0.14	7447N	0.89
74LS02	0.20	7448N	0.56
7403N	0.14	7449N	0.99
74LS03	0.20	7450N	0.99
7404N	0.14	7451N	0.17
74LS04	0.24	7452N	0.24
7405N	0.18	7453N	0.17
74LS05	0.26	7454N	0.17
7406N	0.28	7455N	0.24
7407N	0.38	7456N	0.24
7408N	0.17	7457N	0.17
74LS08	0.24	7458N	0.28
7409N	0.17	7459N	0.28
74LS09	0.24	7460N	0.32
7410N	0.15	7461N	0.38
74LS10	0.24	7462N	0.38
7411N	0.20	7463N	0.27
74LS11	0.24	7464N	0.28
7412N	0.17	7465N	0.38
7413N	0.30	7466N	0.38
7414N	0.51	7467N	0.38
74LS15	0.24	7468N	0.48
7416N	0.30	7469N	0.86
7417N	0.30	7470N	0.69
7420N	0.16	7471N	1.05
74LS20	0.24	7472N	0.64
7421N	0.29	7473N	0.54
74LS21	0.24	7474N	0.99
7422N	0.27	7475N	0.99
7425N	0.27	7476N	0.80
7427N	0.27	7477N	0.67
74LS27	0.44	7478N	0.55
7428N	0.35	7479N	0.38
74LS28	0.32	7480N	0.78
7430N	0.17	7481N	0.20
74LS30	0.24	7482N	0.82
7432N	0.25	7483N	1.30
74LS32	0.24	7484N	0.92
7437N	0.40	7485N	0.78
7438N	0.33	7486N	1.18
74LS38	0.24	7487N	1.85
7440N	0.17	7488N	1.04
74LS40	0.24	7489N	0.63
7441N	0.74	7490N	0.38
7442N	0.70	7491N	0.54
74LS42	0.99	7492N	0.70
		7493N	0.68

## VOLTAGE REGULATORS

78series	0.95
79series	1.00
78Mseries	0.65
79Lseries	0.35
79L05	0.85
78M02C	1.75
79M02C	1.75
723CN	0.65
L200	1.95
TDA1412	0.75
NE555N	1.25
LM317MP	1.48
LM337MP	1.48
4043	0.85
4044	0.80
4046	1.30
4047	0.99
4049	0.52
4050	0.55
4051	0.65
4052	0.65
4053	0.65
4063	1.09
4066	0.56
4068	0.25
4069	0.20
4070	0.20
4071	0.20
4072	0.20
4073	0.20
4075	0.20
4076	0.90
4077	0.20
4078	0.20
4082	0.20
4093	0.78
4175	0.95
4503	0.69
4506	0.51
4510	0.99
4511	1.49
4512	0.98
4514	2.55
4518	1.03
4520	1.09
4521	2.36
4522	1.49
4529	1.41
4539	1.10
4549	3.50
4554	1.53
4560	2.18
4566	1.59
4568	2.18
4569	3.03
4572	0.30
4585	1.10

## MICROMARKET

8080A/2	7.50
8212	2.30
8214	3.50
8216	1.95
8224	3.50
8251	6.25
8255	5.40
6800P	7.50
6810	5.95
6820	7.45
6850	4.90
6852	4.85
MC2708	7.50
2114	6.50
4027	5.78
2102	1.70
2112	3.40
2513	7.54
HM4716	4.50
81LS97	1.25

## 74LS112 0.38

74LS112	0.38
74LS113	0.38
74LS114	0.38
74118N	0.83
74120N	1.15
74121N	0.42
74122N	0.46
74123N	0.73
74LS124	1.75
74125N	0.38
74LS125	0.44
74126N	0.57
74LS126	0.44
74LS127	0.74
74132N	0.73
74LS132	0.78
74LS136	0.40
74LS138	0.60
74141N	0.56
74142N	2.65
74143N	3.12
74144N	3.12
74LS145	0.97
74147N	1.75
74148N	1.09
74LS148	1.19
74150N	0.99
74LS151	0.55
74LS151	0.84
74LS151	0.64
74LS152	0.54
74154N	0.96
74LS155	1.10
74156N	0.80
74157N	0.67
74LS157	0.55
74LS158	0.60
74159N	2.10
74160N	0.82
74LS160	1.30
74161N	0.92
74LS161	0.78
74LS162	1.30
74163N	0.92
74LS163	0.78
74164N	1.04
74LS164	1.30
74165N	1.05
74LS165	1.04
74167N	2.50

## 74LS169 2.00

74LS169	2.00
74170N	2.30
74LS170	2.00
74LS174	1.20
74175N	0.87
74LS175	1.10
74176N	0.75
74177N	0.78
74LS181	1.65
74LS181	3.50
74LS183	2.10
74184N	1.35
74185N	1.34
74LS190	0.92
74192N	1.05
74LS192	1.80
74193N	1.05
74LS193	1.80
74194N	1.05
74196N	0.99
74LS196	1.10
74LS197	1.10
74198N	1.50
74199N	1.60
74LS247	0.93
74LS257	1.08
74LS260	1.53
74LS279	0.52
74LS283	1.20
74LS293	0.95
74LS365	0.49
74LS366	0.49
74LS367	0.43
74LS368	0.49
74LS374	1.80
74LS377	1.95
74LS379	1.30
74LS393	1.40

## VARICAP

BA102	0.30
BA121	0.30
ITT210	0.30
BB204B	0.36
BB105B	0.36
BB109	0.27
MM125	1.05
BB212	1.95
KV1210	2.45
KV1211	1.75
KV1226	1.95
KV1225	2.75
KV1215	2.55
KV1225	2.75

# O Level Q & A

It's time for some semiconductors. Nick Walton describes how diodes work and how they can rectify, detect, light up and . . . break down

THIS MONTH we continue our examination of the London Board's Alternative O level Electricity and Electronics syllabus with a look at the way conduction takes place in metals and semiconductors, and this leads us to consider the simplest semiconductor device of them all, the diode. As we will see it is found in many forms and fulfils many functions.

Detailed scientific theories on conduction are complicated and not needed for any O or A level, so what follows is just an outline of the scene. As you know, conduction of electricity occurs when the negatively-charged electrons move from one atom to the next pushed by voltage (looked on, remember, as energy in joules supplied to the charge expressed in coulombs). These electrons are the same as those involved in chemical reactions and when performing this chemical role are called valency electrons. They can have differing amounts of energy and these energy values are known collectively as the valence band of energies. But before they can actually leave a particular atom to drift off and help conduct current they need to enter another series of energy levels called the conduction band.

An insulator has its conduction band well above its valence band so in no way will an electron be able to find the energy to move up from valence to conduction band, hence the lack of conduction electrons and high electrical resistance. Metals on the other hand conduct well because the two bands are close together, sometimes even overlapping, so it is easy for an electron to find its way into the conduction band (Figs. 1a and b). You could say that an insulator holds tight to its electrons while a metal is more permissive and lets them roam.

In between these two extremes come our friends the semiconductors, most commonly silicon and germanium. They do have a distinct gap between the valence and the conduction band (Fig. 1c), and at low temperatures electrons just cannot find the energy to jump the gap. But as things warm up it becomes easier. Ac-

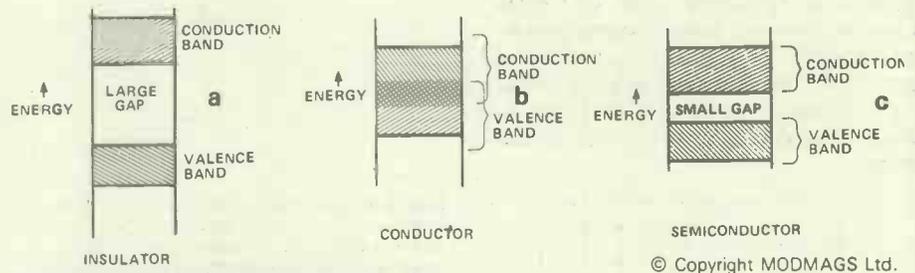


Figure 1. Conduction bands for a) insulators (well separated), b) metal (very close) and c) semiconductors (small gap)

ording to Bennett in 'Electricity and Modern Physics' (Arnold), at room temperatures 1 in every  $10^{11}$  electrons are in the 'high' state where they are capable of shifting from the valence band into the conduction band.

## Moving Holes

Perhaps a little surprisingly this leads not to one type of conduction but two. Clearly the energetic electron that has jumped up into the conduction band is now able to flow, but consider what it has left behind. The atom from which it came now has an unoccupied space or 'hole' which can be filled by an electron from somewhere else. Now this somewhere else can be the valence band (not the conduction band) of a neighbouring atom, to which the hole would now be transferred. Thus a hole can move around and make its own contribution to conduction separate from the electron that left home in the first place. For practical purposes we can regard this hole movement as that of positively charged particles, each unit having a charge equal to that of the electron but positive not negative.

In a pure semiconductor this naturally occurring conduction is described as 'intrinsic'. But the production of conduction electrons and the equivalent number of positive holes does not occur in sufficient quantities for practical advantage. The real use comes about when you increase either the number of conduction electrons or the number of positive holes. This is achieved by a process known as 'doping' which involves putting a different type of atom into your

silicon or germanium crystal. Both these elements have four valence electrons and form a type of pyramid-structured crystal (Fig. 2a), like diamond, in which each atom is double-bonded to four other atoms by a pair of shared valency electrons. This is shown in Fig. 2b, which is just one unit of the crystal and you have to reckon that all the many silicon atoms are attached to four others. If now an atom of comparable size takes the position of one of the silicon atoms in the crystal, and if that atom (eg antimony or arsenic) has five valency electrons, it will use up four of these electrons in the bonding. The fifth is now free to roam the lattice as a conduction electron. Thus the impurity atom appears as a donor of electrons and we have what is called an n-type semiconductor (electrons being negative).


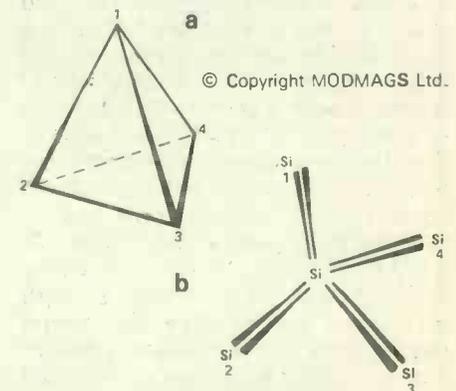


Figure 2. Semiconductor crystal: a) 'diamond' structure (pyramid-like) form in which silicon and germanium crystallise, b) central silicon is bonded to four others, one at each apex of the pyramid

Conversely if an impurity with only three valency electrons (eg gallium or indium) were to take the place of a silicon atom in the crystal there would be a tendency to complete the electron structure, perhaps from a neighbouring electron thus creating a hole. Since holes are regarded as positive, this type of semiconductor with an impurity which accepts electrons (an 'acceptor' impurity) is called p-type. Now what happens when you have some n-type and p-type semiconductor together in a single crystal? The answer is that you have what is called a p-n junction diode and that it conducts in one direction but not in the other.

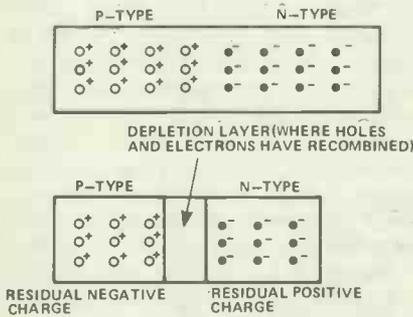

© Copyright MODMAGS Ltd.


**Figure 3. p-n material:** a) holes in p-type and electrons in n-type single crystal before any interaction, b) depletion layer formed because of the recombination of electrons and holes, leaving residual negative charge in the p-type region and residual positive charge in the n-type region

### p-n Junction Diode

Consider Fig. 3a with p-type semiconductor on the left. It contains positive holes (represented as  $o^+$ ) drifting around though, of course, the net charges balance out. On the right is the n-type material with electrons (represented as  $e^-$ ) drifting around. Sooner or later an electron is going to drift into the left-hand region and fall into a hole, or a hole might drift right and meet up with an electron. Notice that each time an electron moves into the p-type region, it makes it negative and leaves a residual positive charge in the n-type region it has left. Thus a situation develops where at the junction of p-type and n-type, holes and electrons have combined leaving a region depleted of current carriers. This is called the 'depletion layer' and being without carriers it has a high resistance. Furthermore, the n-type region now has a residual positive charge and the p-type a negative charge due to the electron and hole movement.


It might help to picture this imbalance of charge as having the same effect as an imaginary cell connected

up as shown in Fig. 4a. If now an external cell B is connected to our p-n junction with connections shown as in Fig. 4b, the voltage at the positive terminal of this external cell will push the positive holes towards the junction and that of the negative terminal will push the electrons also towards the junction, effectively narrowing the depletion layer and letting current flow. This state is called 'forward

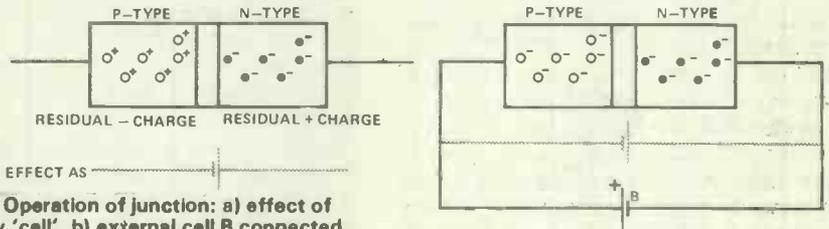


**Figure 4. Operation of junction:** a) effect of imaginary 'cell', b) external cell B connected to p-n junction in 'forward bias'. The imaginary cell appears to be connected to assist current flow

© Copyright MODMAGS Ltd.

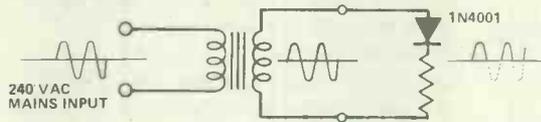


**Figure 5. Rectifying action of a diode (half wave rectification)**

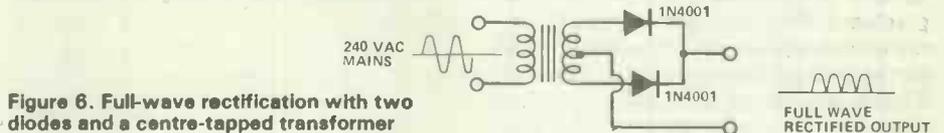

**Figure 6. Full-wave rectification with two diodes and a centre-tapped transformer**

© Copyright MODMAGS Ltd.

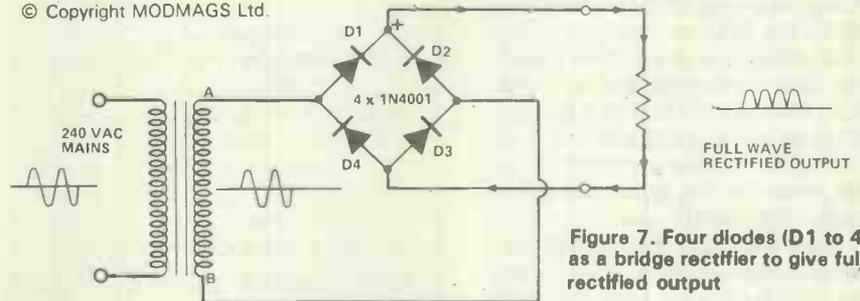

**Figure 7. Four diodes (D1 to 4) used as a bridge rectifier to give full-wave rectified output**

### Rectification

Perhaps the most important and widespread use of the diode (circuit symbol  $\rightarrow|$ ) occurs in rectification; that is, changing AC to DC. If you apply AC to a diode the current is only allowed to flow one way. Thus a single diode will only let one half of the AC wave through and, for the AC input shown in Fig. 5, the result is the loss of the lower half of the wave. It is necessary to include the resistor (a value of between 100R to 1kR will do for this) to limit the current flow. If you want to measure the waveforms indicated in Fig. 5, then connect an oscilloscope first across the secondary winding of the transformer (or other 10 VAC source used) and then across

the resistor. Because you end up with just half the wave across the resistor this process is called *half-wave* rectification. Apart from demonstrations it is hardly ever used. The reason is that full-wave rectification is easy to achieve with two diodes from a transformer with a centre tap (Fig. 6).

You can save the cost or inconvenience of the centre tap if you use four diodes in a configuration called a bridge (Fig. 7). When the output of transformer A is at positive voltage relative to B then current flows in the diodes D1 and D3 and is blocked by D2 and D4. When B is positive relative to A, D2 and D4 conduct and D1 and D3 block. So the (conventional) current always flows in the resistor from top to bottom.



## Smoothing Out the Bumps

Thus we get squirts of DC. The flow builds up from nothing and then drops to nothing, rather like the flow you get when you milk a cow. Putting in a capacitor which takes time to charge up and discharge has the effect of smoothing out the bumps as shown in Fig. 8 and you only get what is called a ripple which is as good an approximation to DC as we require.

© Copyright MODMAGS Ltd.

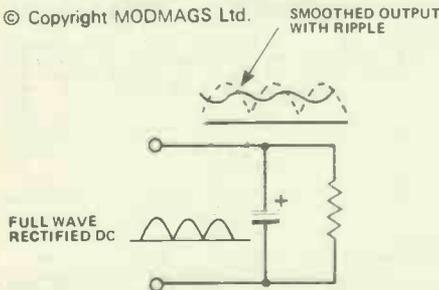


Figure 8. Action of a capacitor in smoothing full-wave rectified DC

## Diodes for Detection

Another widespread use of the diode is in radios in the process called detection or demodulation. To understand this we need to take a very potted view of what happens in a (non-FM) radio. radio signals are carried at high frequencies: for instance, BBC Radio 4 is transmitted at a frequency of 200 kHz — that's 200,000 waves every second, and what we hear comes about by changing (modulating) the amplitude (size) of our high-frequency carrier wave, a process called 'amplitude modulation' or AM. Suppose a flute was being broadcast playing a note of frequency 500 Hz. The carrier wave would have its amplitude changed at a frequency of 500 Hz as shown in Fig. 9, though if we wanted to be entirely accurate we would need to draw 400 complete carrier waves for each complete flute wave. Before

THE CARRIER WAVE HAS ITS AMPLITUDE MODULATED AT THE FLUTE'S FREQUENCY OF 500 Hz

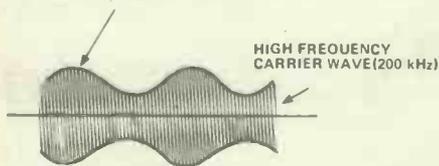


Figure 9. Amplitude modulation of a radio-frequency carrier wave

© Copyright MODMAGS Ltd.

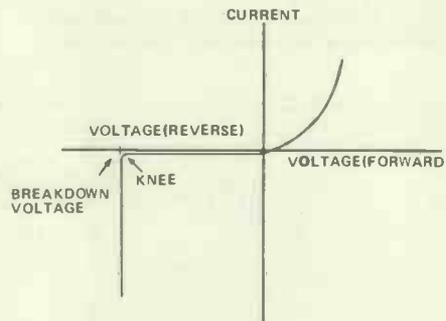


Figure 10. Effect of a diode in demodulating a radio signal before it is fed into the audio amplifier

this can be fed into the audio amplifier and be heard, the bottom part of the signal has to be chopped off and this is done by means of a diode. The result is shown in Fig. 10. The action of the diode here is called detection or demodulation.

## Breaking Down a Zener

We have seen that a diode allows current to flow one way but not the other. But any diode will break down if you apply a big enough reverse voltage. With an ordinary diode that is usually the end of its useful life but there is a special sort — a zener diode — which is made so that it breaks down at a precisely-defined voltage and without damage. It has a current-voltage graph as shown in Fig. 11, and the important aspect is the 'knee' on the reverse voltage side. This indicates that when this reverse voltage is reached the diode conducts more and more current rather than change voltage. Obviously it can be damaged if you try hard enough and exceed its power rating.



© Copyright MODMAGS Ltd.

Figure 11. Current-voltage curve for a zener diode

The zener diode finds widespread use when a fixed voltage is needed somewhere, for instance in a power supply. Its action can be readily demonstrated with a variable voltage (eg by using a potentiometer) connected across the zener diode in series with a resistor as in Fig. 12. As the voltage is raised from zero the zener will exhibit a high resistance and most if not all of that voltage will appear across it. At 4.7 V (zeners, like resistors, come in preferred values) it will suddenly start to conduct and it will go on conducting whatever current is necessary to keep the voltage across it fixed at 4.7 V.

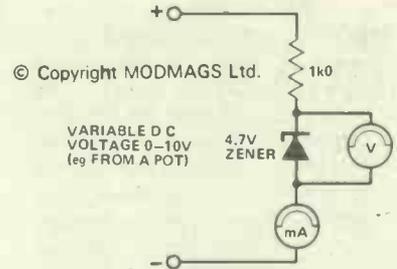


Figure 12. Circuit to demonstrate action of a zener diode

## Luminous Diodes

There is one other type of diode we cannot overlook and that is because it actually emits light at us from places like the luminous display of a calculator. I do not mean the liquid crystal (non-luminous) display but the red or green type still common. The device is actually called a light-emitting diode or LED. When an electron jumps down into a hole it gives up energy and for a pn junction diode made of heavily-doped gallium arsenide (GaAs) the light emitted is infra-red. The addition of phosphorus to the compound (GaAs P) brings the light into the visible region of the spectrum. The most restful colour for the eye is green, achieved with a GaAs P and some nitrogen. You can also get LEDs that produce green, orange or yellow light but as yet manufacturers have not been able to produce a blue LED. If they could, they would have red, green, and blue — the primary colours which could lead to interesting possibilities with mixtures. Each numeral in the display on your calculator is merely seven individual long-shaped LEDs arranged in a square figure of eight and each segment can be switched on and off separately (see Fig. 13a). Thus for instance the number six is obtained by having all segments lit except the top right upright, as shown in Fig. 13b.



Figure 13. Seven-segment display in a calculator: a) make-up of display, b) to generate a 6, all segments are lit up except the top right upright

That just about switches off the display for this month. I hope you managed to recover from the misprints in the November issue. Thanks for staying with me — you must have done or you wouldn't be reading this now—and we'll meet again next month. HE

### TRANSISTORS

AC126	£0.23	BC149	£0.08	BC550	£0.16	BU105	£1.84	ZTX109	£0.12
AC127	£0.23	BC157	£0.12	BC556	£0.16	BU105/02	£2.24	ZTX109	£0.12
AC128	£0.22	BC158	£0.12	BC557	£0.15	BU204	£1.81	ZTX300	£0.14
AC128K	£0.30	BC159	£0.12	BC558	£0.14	BU205	£1.61	ZTX500	£0.15
AC132	£0.23	BC167	£0.14	BC559	£0.16	BU208/02		ZN1613	£0.23
AC134	£0.23	BC168	£0.14	BC115	£0.58			ZN1711	£0.23
AC137	£0.23	BC169	£0.10	BD116	£0.92	MJE2955	£1.04	ZN1889	£0.52
AC141	£0.25	BC169A	£0.12	BD121	£0.75	MJE3055	£0.69	ZN1890	£0.52
AC141K	£0.35	BC170	£0.10	BD124	£0.81	MJE3440	£0.60	ZN1893	£0.35
AC142	£0.23	BC171	£0.10	BD131	£0.40			ZN2147	£0.86
AC176	£0.21	BC172	£0.10	BD132	£0.40	MFF104	£0.40	ZN2148	£0.81
AC176K	£0.30	BC173	£0.10	BD133	£0.46	MFF105	£0.40	ZN2192	£0.44
AC178	£0.29	BC177	£0.18	BD135	£0.46	MPSA05	£0.23	ZN2193	£0.44
AC179	£0.29	BC178	£0.18	BD136	£0.40	MPSA06	£0.23	ZN2194	£0.44
AC180	£0.23	BC179	£0.18	BD137	£0.40	MPSA55	£0.23	ZN2217	£0.25
AC180K	£0.32	BC180	£0.29	BD138	£0.41	MPSA56	£0.23	ZN2218	£0.25
AC181	£0.23	BC181	£0.10	BD138	£0.41	OC22	£1.73	ZN2218A	£0.23
AC181K	£0.32	BC182L	£0.10	BD140	£0.41	OC23	£1.73	ZN2219	£0.23
AC187	£0.23	BC183	£0.10	BD155	£0.92	OC24	£1.55	ZN2219A	£0.28
AC187K	£0.32	BC183L	£0.10	BD175	£0.69	OC25	£1.15	ZN2904	£0.21
AC188	£0.23	BC184	£0.10	BD176	£0.69	OC26	£1.15	ZN2904A	£0.24
AC188K	£0.32	BC207	£0.13	BD177	£0.78	OC28	£0.92	ZN2905	£0.21
AD140	£0.69	BC208	£0.13	BD178	£0.78	OC29	£1.09	ZN2905A	£0.23
AD142	£0.98	BC209	£0.14	BD179	£0.86	OC35	£1.03	ZN2906	£0.19
AD143	£0.88	BC212	£0.10	BD203	£0.92	OC36	£1.03	ZN2906A	£0.21
AD149	£0.89	BC212A	£0.10	BD204	£0.92	OC70	£0.28	ZN2907	£0.23
AD161	£0.40	BC213	£0.10	BDY20	£0.92	OC71	£0.17	ZN2926G	£0.11
AD162	£0.40	BC213L	£0.10	BF457	£0.43	TIC44	£0.33	ZN2926J	£0.09
AD161	£0.40	BC214	£0.10	BF458	£0.43	TIC45	£0.40	ZN2926K	£0.09
162MP	£0.81	BC214L	£0.10	BF459	£0.44	TIP29A	£0.46	ZN2926L	£0.09
AF124	£0.35	BC227	£0.18	BF594	£0.35	TIP29B	£0.48	ZN2926R	£0.09
AF125	£0.35	BC238	£0.18	BF596	£0.32	TIP29C	£0.51	ZN2926S	£0.09
AF126	£0.35	BC251	£0.17	BF597	£0.25	TIP29D	£0.48	ZN3053	£0.20
AF127	£0.37	BC251A	£0.18	BF840	£0.29	TIP30A	£0.46	ZN3054	£0.46
AF139	£0.40	BC301	£0.32	BF879	£0.32	TIP30B	£0.48	ZN3055	£0.46
AF186	£0.58	BC302	£0.33	BF880	£0.32	TIP31A	£0.46	ZN3614	£1.15
AF239	£0.44	BC303	£0.32	BFX29	£0.25	TIP31B	£0.48	ZN3615	£1.21
AL102	£0.33	BC304	£0.32	BFX30	£0.35	TIP31C	£0.51	ZN3616	£1.21
AL103	£0.36	BC327	£0.18	BFX31	£0.35	TIP32A	£0.46	ZN3702	£0.09
AU104	£1.61	BC328	£0.17	BFX32	£0.28	TIP32B	£0.48	ZN3703	£0.09
AU110	£1.61	BC337	£0.17	BFX86	£0.28	TIP32C	£0.48	ZN3703	£0.09
AU113	£1.61	BC338	£0.17	BFX87	£0.25	TIP32C	£0.48	ZN3704	£0.08
BC107A	£0.09	BC440	£0.35	BFX88	£0.25	TIP41A	£0.51	ZN3705	£0.08
BC107B	£0.10	BC441	£0.35	BFY50	£0.20	TIP41C	£0.55	ZN3707	£0.09
BC107C	£0.12	BC460	£0.44	BFY51	£0.20	TIP42A	£0.51	ZN3708	£0.08
BC108A	£0.10	BC461	£0.44	BFY52	£0.20	TIP42B	£0.53	ZN3709	£0.08
BC108B	£0.11	BC477	£0.23	BFY90	£0.95	TIP42C	£0.55	ZN3710	£0.08
BC108C	£0.12	BC478	£0.23	BP19	£0.44	TIP2955	£0.69	ZN3711	£0.08
BC109A	£0.09	BC479	£0.23	BP20	£0.44	TIS43	£0.25	ZN3819	£0.21
BC109B	£0.10	BC546	£0.12	BP19	£0.44	TIS90	£0.21		
BC109C	£0.12	BC547	£0.12	70MP	£0.92	UT46	£0.23		
BC147	£0.08	BC548	£0.12	8R39	£0.51	ZTX107	£0.12		
BC148	£0.08	BC549	£0.12						

### THYRISTORS

Volts No	Price	Volts	Price
10 THY600ma/10v	£0.17	50 THY7A/50	£0.55
20 THY600ma/20v	£0.18	100 THY7A/100	£0.58
30 THY600ma/30v	£0.23	200 THY7A/200	£0.65
50 THY600ma/50v	£0.25	400 THY7A/400	£0.71
100 THY600ma/100v	£0.29	600 THY7A/600	£0.89
200 THY600ma/200v	£0.44	800 THY7A/800	£0.05
400 THY600ma/400v	£0.51		
Volts No	Price	Volts No	Price
50 THY1A/50	£0.30	50 THY10A/50	£0.58
100 THY1A/100	£0.32	100 THY10A/100	£0.65
200 THY1A/200	£0.37	200 THY10A/200	£0.71
400 THY1A/400	£0.44	400 THY10A/400	£0.80
600 THY1A/600	£0.48	600 THY10A/600	£1.13
800 THY1A/800	£0.67	800 THY10A/800	£1.40
Volts No	Price	Volts No	Price
50 THY3A/50	£0.32	50 THY16A/50	£0.62
100 THY3A/100	£0.35	100 THY16A/100	£0.66
200 THY3A/200	£0.37	200 THY16A/200	£0.71
400 THY3A/400	£0.48	400 THY16A/400	£0.88
600 THY3A/600	£0.58	600 THY16A/600	£1.03
800 THY3A/800	£0.75	800 THY16A/800	£1.59
Volts No	Price	Volts No	Price
50 THY5A/50	£0.41	50 THY30A/50v	£1.36
100 THY5A/100	£0.51	100 THY30A/100v	£1.67
200 THY5A/200	£0.57	200 THY30A/200v	£1.87
400 THY5A/400	£0.65	400 THY30A/400v	£2.06
600 THY5A/600	£0.79	500 THY30A/600v	£4.03
800 THY5A/800	£0.93		

### LEDs

O/no	Size	Colour	Price
1501	125	RED	£0.10
1502	125	GREEN	£0.16
1503	125	YELLOW	£0.10
1504	2	RED	£0.10
1505	2	GREEN	£0.16
1506	2	YELLOW	£0.16
1509	2	CLEAR (III Red)	£0.12

**SUPER 'Hi Brn' Type**

1521	125	RED	£0.11
1522	2	RED	£0.11
1524	2	RED	£0.11
1524	125	RED	£0.11
1525	125	RED	£0.11
1526	125	RED	£0.11

**CLIPS**

1508/125	pack of 5	125 clips	£0.17
1508/2	pack of 5	2 clips	£0.20

**DISPLAYS**

DL307	+	segment D.P. felt (0.3" height) common anode single digit	O/N0 1523	£0.80
DL707	RED	7 segment D.P. left (0.3" height) common anode single digit	O/N0 1510	£0.92
DL727	RED	7 segment D.P. right (0.5" height) common anode 2-digit rectifier	O/N0 1524	£1.95
DL727	RED	7 segment D.P. right (0.5" height) common anode 2-digit light pipe	O/N0 1521	£2.53
DL747	RED	7 segment D.P. left (0.6" height) common anode Single-digit light pipe	O/N0 1511	£1.72

**OPTO-ISOLATORS**

Isolation Breakdown — Voltage 1500 — continuous two current 100mA

CL174 Single-channel 6 pin DIP standard type — optically coupled pair with infra-red LED emitter and NPN silicon photo transistor O/N0 1497

£0.57

CL174 Multi-channel 8 pin DIP two isolated channels O/N0 1498

£1.15

CL174 Multi-channel 16 pin DIP four isolated channels O/N0 1499

£2.53

### SILICON RECTIFIERS

200MA	Price	10 Amp	Price
IS920 50v	£0.07	IS10/50 50v	£0.21
IS921 100v	£0.08	IS10/100 100v	£0.24
IS922 150v	£0.09	IS10/200 200v	£0.26
IS923 200v	£0.10	IS10/400 400v	£0.40
IS924 300v	£0.11	IS10/600 600v	£0.58
IS925 600v	£0.16	IS10/800 800v	£0.69
IS927 800v	£0.18	IS10/1000 1000v	£0.79
IS929 1000v	£0.23		
IS931 1200v	£0.28		
3 Amp	Price	30 Amp	Price
IS5400 50v	£0.16	IS30/50 50v	£0.64
IS5401 100v	£0.17	IS30/100 100v	£0.79
IS5402 200v	£0.18	IS30/200 200v	£1.06
IS5403 400v	£0.24	IS30/400 400v	£1.43
IS5404 600v	£0.28	IS30/600 600v	£2.02
IS5405 800v	£0.34	IS30/800 800v	£2.23
IS5406 1000v	£0.34	IS30/1000 1000v	£2.65
IS5407 1200v	£0.34	IS30/1200 1200v	£3.31
1.5 Amp	Price	60 Amp	Price
IS1015 50v	£0.10	IS70/50 50v	£0.86
IS1020 100v	£0.11	IS70/100 100v	£0.98
IS1021 200v	£0.12	IS70/200 200v	£1.38
IS1022 400v	£0.14	IS70/400 400v	£2.01
IS1023 600v	£0.16	IS70/600 600v	£2.58
IS1024 800v	£0.18	IS70/800 800v	£2.87
IS1025 1000v	£0.18	IS70/1000 1000v	£3.45
IS1026 1200v	£0.18		
IS1027 800v	£0.18		
IS1028 1000v	£0.23		
IS1029 1200v	£0.28		
IS1030 1200v	£0.28		

### SECOND GRADE LED PACK

A pack of 10 standard sizes and colours which fail to perform to their rigid specification but which are ideal for amateurs who do not require the full spec O/N0 1507

£1.04

### SOCKETS

1611	8 pin DIL	£0.09	1615	28 pin DIL	£0.26
1612	14 pin DIL	£0.11	1623	40 pin DIL	£0.34
1613	16 pin DIL	£0.12	1624	TO18 transistor	£0.13
1614	18 pin DIL	£0.18	1617	TO3 transistor	£0.37
1615	20 pin DIL	£0.20	1618	TO5 transistor	£0.13
1616	22 pin DIL	£0.22	1619	14 pin DIL Wire wrap	£0.13
1617	24 pin DIL	£0.24	1620	gold plated Cambion	£0.25

### TRIACS & DIACS

2 amp TO5 case	Price	10 amp	Price
100 TR12A 100	£0.36	100 TR110A 100	£0.88
200 TR12A 200	£0.59	200 TR110A 200	£1.06
400 TR12A 400	£0.82	400 TR110A 400	£1.29
6 amp	Price	10 amp Plastic	Price
100 TR16A 100	£0.59	400 TR110A 400P	£1.29
200 TR16A 200	£0.70		
400 TR16A 400	£0.88		
DIACS	Price	DIACS	Price
BR100	£0.23	D32	£0.23

### G.P. SWITCHING TRANSISTORS

TO18mm to 2N706/3 SV27 28 95A. All useable devices, no open and shorts ALSO available in PNP sum to 2N290 BCY70 20 for 87p; 50 for £1.15; 100 for £2.07; 500 for £9.20; 1,000 for £16.10. When ordering state NP/PNP

### G.P. SILICON DIODES

300mW 40VPI (min) sub min. FULLY TESTED Ideal for Organ builders

30 for 87p; 100 for £1.72; 500 for £5.75; 1,000 for £10.35

### BRIDGE RECTIFIERS

SILICON 1 amp	Price	SILICON 2 amp	Price
100v RMS BR1 50	£0.25	50v RMS BR2 50	£0.52
100v RMS BR1 100	£0.25	100v RMS BR2 100	£0.55
200v RMS BR1 200	£0.29	200v RMS BR2 200	£0.60
400v RMS BR1 400	£0.41	400v RMS BR2 400	£0.67
SILICON 10 amp	Price	SILICON 25 amp	Price
50v RMS BR10 50	£1.73	50v RMS BR25 50	£2.19
200v RMS BR10 200	£1.96	200v RMS BR25 200	£2.53

### VOLTAGE REGULATORS

Positive Case	Price
---------------	-------

# 2 SUPERB NEW KITS!

Special Offer -  
**£2 OFF!**



## C300/ES200

high performance electronic ignition, to add power, economy, reliability, sustained smooth peak performance, instant all weather starting, to your car.

Surefire has sold in its thousands in ready made form from big name accessory firms, but it is now available in quality kit form to fit all vehicles with coil ignition up to 8 cylinders.

**ES200.** A high performance inductive discharge ignition incorporating a power integrated circuit (special selection): electronic variable dwell circuit (maximises spark energy at all speeds): pulse processor (overcomes contact breaker problems). Coil governor (protects coil). Long burn output. Negative earth only. Compatible with all rev. counters.

**C300.** In it's ready built form (C3000) it came top of all systems tested by an independent national authority July '79. A high energy capacitive discharge ignition incorporating a high output short circuit proof inverter, top grade Swedish output capacitor, pulse processor circuit, transient overload protection. Fast rise bidirectional output ideal for fuel injection, sports carburation, oily engines. Compatible with most rev. counters. (Low cost adaptors available for rare cases. Application list enclosed with each kit. Note: Vehicles with Smiths/Jaeger rev. counters code RVI on dial will require adaptor type TCI).

**What's in the kits.** Surefire's own precision anodised aluminium extruded case. P.C. mounted security changeover switch, static timing light. Special selection Motorola semi-conductors. Capacitors, resistors etc. selected after 5 years experience. Glass fibre pcb, solder, complete down to last washer. Fully illustrated comprehensive instructions and full technical back up service.



Suretron Systems (UK) Ltd. Dept. HE1  
Bayer Buildings, Lower Bristol Road, Bath, BA2 3EF. Tel: Bath (0225) 332317

Name: \_\_\_\_\_  
Address: \_\_\_\_\_

\*Phone order with Access/Barclaycard  
VAT and P & P inc.

Quantity  
required

ES200: Neg	£13.95	£11.95	
C300: Pos	£17.95	£15.95	
C300: Neg	£17.95	£15.95	
Tacho Adapt. TCI		£3.90	

I enclose  
chq/PO's  
£  
Chq No.

# CAR ENTERTAINMENT BARGAINS

Show us that you could have purchased for less within one month of your purchase and we will refund the difference!

● **STEREO CASSETTE/RADIO.** MW and Stereo FM radio and Stereo Cassette Player, 8 watts per channel, lockable fast forward and autostop. Includes fitting kit and **FREE SPEAKERS.** Sold elsewhere for up to £85 (believe it or not). **OUR PRICE £45 (+ £1.50 post).** (For negative earth cars only).



● **PYE 7-CHANNEL STEREO GRAPHIC EQUALISER/BOOSTER AMPLIFIER.** 17 watts R.M.S. per channel. Frequency response 20Hz to 30,000Hz ± 12dB cut/boost on each channel. Complete with fitting kit. You would pay at least £45 elsewhere. **OUR PRICE £28 (+ £1.20 post).**

● **SUITABLE SPEAKERS FOR EQUALISER.** Adjustable angle, shelf-mounting, power handling 30 watts max. **OUR PRICE £16 per pair (+ £1.20 post).**



● **ELECTRIC ANTENNA.** Wing mounting, including switch and fitting kit. **OUR PRICE £10 (+ £1.20 post).**

**PLEASE NOTE:** These goods are ready built units. All goods guaranteed one year. 10-day money back offer on all undamaged goods. Goods ex-stock at time of going to press. Send SAE for details.

**MINIKITS ELECTRONICS LTD.**  
88H Hainault Road, Leytonstone, London E11 1EH



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages. Bound in stiff linen. Cover size 8 1/2 in x 5 in. Price £10.00 per set (we pay the postage)

- Book 1. Introducing Electronics
- Book 2. Resistors/Capacitors
- Book 3. Inductors/Diodes
- Book 4. Meters/Voltage-dividers
- Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value. This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals. Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order Now:  
Selray Book Company  
11 Aspen Copse,  
Bromley,  
Kent. BR1 2NZ

**OUR 100% GUARANTEE**  
Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £ \_\_\_\_\_  
Name: \_\_\_\_\_  
Address: \_\_\_\_\_ HE1

# Bench Amplifier

Just the project you need — cheap, simple to build and a very useful piece of audio test gear



Beginners in electronics often assume that the more complex equipment is the more useful it is likely to be in the workshop. In fact it tends to be the more simple pieces of equipment that get worn-out! Probably the most useful items of equipment are a multimeter, power supply unit, a signal source of some kind and a simple amplifier such as the one described here.

Maximum output power of the HE Bench Amplifier is around 150 mW RMS, which should be sufficient for normal test purposes. An output power of about 1 W RMS can be achieved if an 8 Ω impedance speaker is used in place of the specified high-impedance type, but a large 9 V battery (PP9) or a mains power supply would then be necessary as the current consumption would average over 100 mA at high volume levels. The amplifier should not be found lacking in sensitivity since only about 2.5 mV RMS into 47k is needed for maximum output, and even low-level signal sources such as guitar pick-ups and microphones will drive it fully.
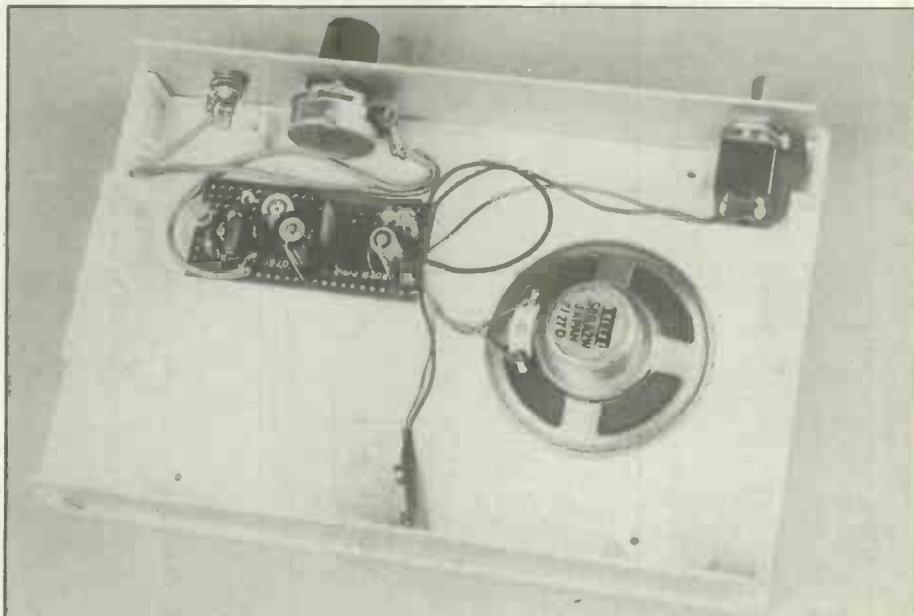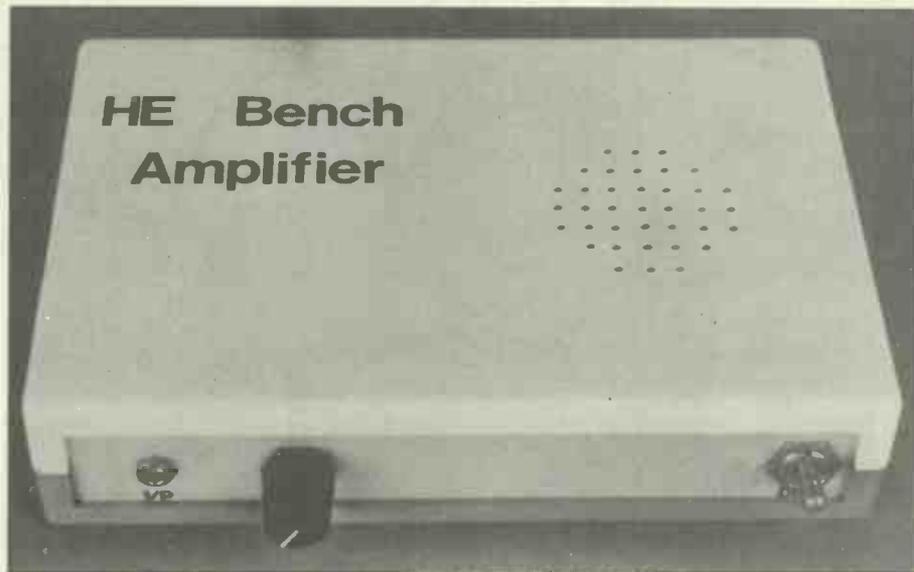
## Construction

The circuit can be built onto one of our standard Veroboards using the component layout and wiring shown in Fig. 2. Break the tracks where indicated using a spot-cutting tool or a hand-held  $\frac{1}{8}$ " drill bit. Hold the tool onto the hole in question and gently rotate it clockwise until the track breaks cleanly. The component layout is very compact, but there should be no problems here, provided modern miniature components are used, and care is taken to avoid accidental solder bridges between the copper strips.

As with any high-gain amplifier, it is advisable to use screened leads at the input so that stray feedback and pick-up is minimised. Using a metal



case also helps to avoid stray pick up of mains hum, etc, but a plastic one like we used is satisfactory for most purposes. The input leads and speaker leads should be kept reasonably well separated so that stray feedback is avoided.

A speaker grille must be made in the case, and this can simply consist of a matrix of small holes about 3 to 5 mm in diameter. This is not as easy as you might think, and must be

done very carefully if a neat finish is to be obtained. The loudspeaker is glued in place using one of the more powerful adhesives that are available (such as an epoxy or cyanoacrylate type), making sure that none of the adhesive is smeared onto the speaker's diaphragm (or on your fingers!).

The circuit is powered by a PP6-sized battery, which uses the standard PP3 type battery connector.

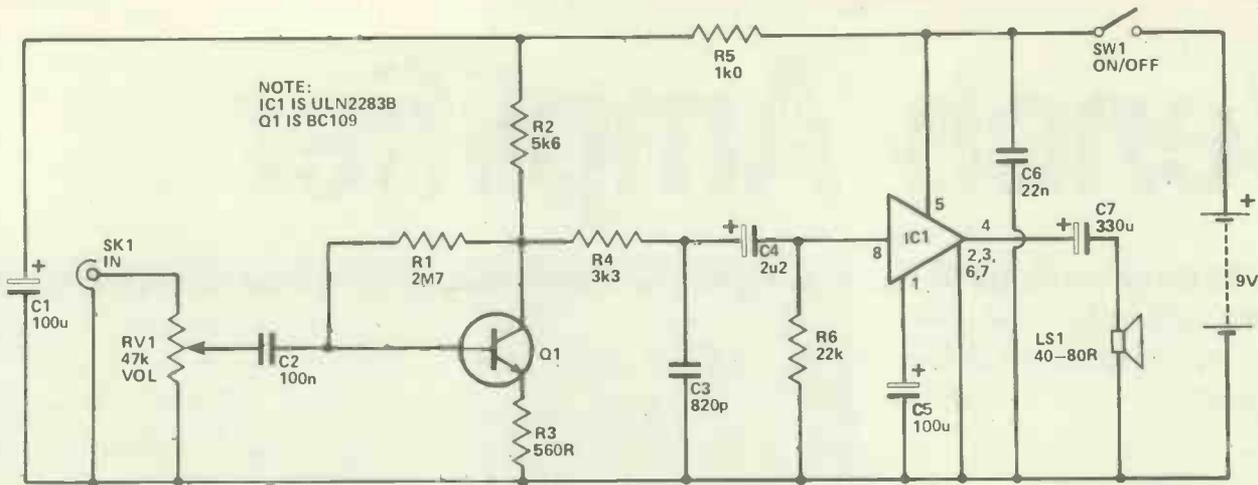


Figure 1. Circuit diagram

© Copyright MODMAGS Ltd.

### Parts List

<b>RESISTORS</b> (all 1/4 watt 5%)		C6	22n ceramic
R1	2M7	C7	330u electrolytic
R2	5k6	<b>SEMICONDUCTORS</b>	
R3	560R	IC1	ULN2283B power amplifier
R4	3k3	Q1	BC109 NPN transistor
R5	1k	<b>MISCELLANEOUS</b>	
R6	22k	SW1	single-pole, single-throw toggle
<b>POTENTIOMETER</b>		SK1	3.5 mm jack socket
RV1	47k log carbon	10 strip by 24 hole Veroboard	
<b>CAPACITORS</b>		40-80R miniature speaker case to suit	
C1	100u 10 V electrolytic	battery and clip	
C2	100n polyester	knob to suit	
C3	820p ceramic		
C4	2u2 63 V electrolytic		
C5	100u 10 V electrolytic		

### How It Works

The circuit uses an integrated circuit power amplifier stage preceded by a single transistor preamplifier, as can be seen from the circuit diagram in Fig. 1. A ULN2283B device is used for IC1, which has its voltage gain set at approximately 43 dB (140 times) by an internal negative feedback circuit. Capacitor C6 decouples the supply, aiding the stability of IC1, and C5 decouples the supply to the input stages of IC1; also aiding stability. Capacitors C4 and C7 merely provide DC blocking at the input and output. Resistor R6 provides bias for IC1.

Transistor Q1 is used as a low-noise emitter-follower amplifier which boosts the sensitivity of the circuit by a factor of ten. The innate voltage gain of the circuit is far higher than is required here, and R3 is therefore used to provide negative feedback which boosts the input impedance of the stage and reduces its voltage gain to the appropriate figure. The input signal is applied straight to volume control RV1, and C2 is used to couple the signal from the volume control to the input of Q1.

Because of the very high gain of the circuit it is necessary to roll-off the response at high frequencies to avoid instability. Together, R4 and C3 form a simple low-pass RC filter which is included in the signal path between Q1 and IC1.

The output stage of IC1 is in class AB, and the quiescent current consumption of typically 12 mA increases significantly (to a maximum average value of about 40 mA) at high output levels. It is therefore necessary to decouple the preamplifier stage from the main supply with R5 and C1 so that low-frequency instability due to feedback through the supply lines is avoided.

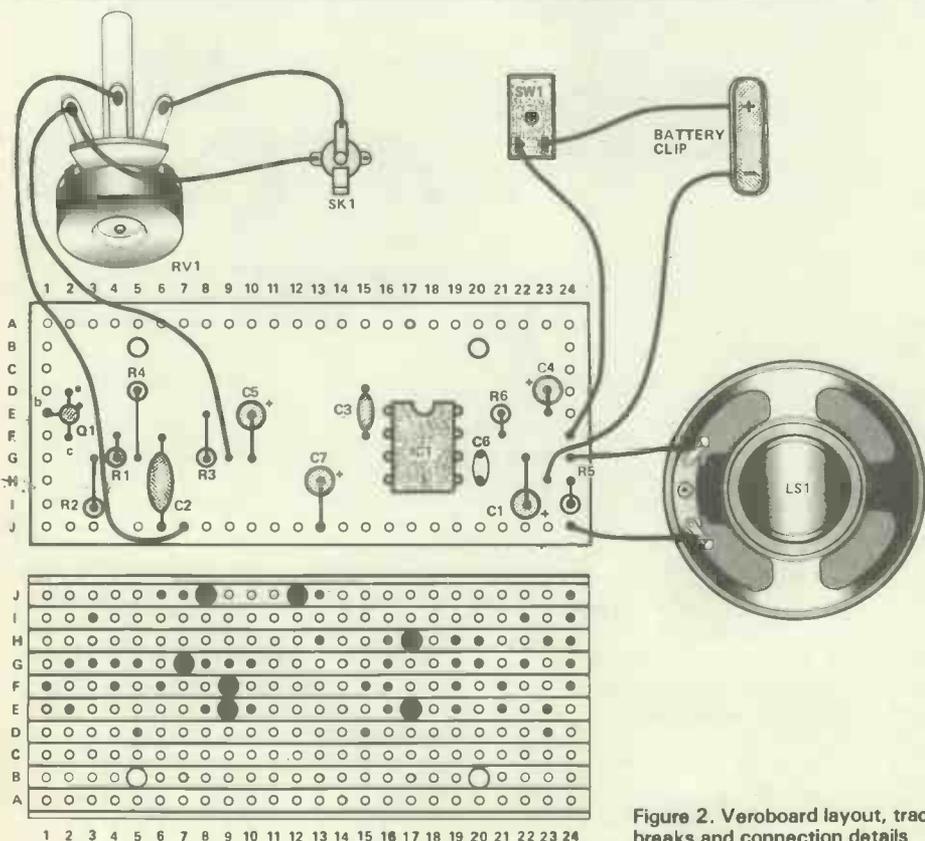


Figure 2. Veroboard layout, track breaks and connection details


### Buylines

All components are common types with the exception of the ULN2283B device used for IC1. This is available from Ambit International, 200 North Service Road, Brentwood, Essex, CM14 4SG. Approximate price for the project (excluding case) should be about £6.
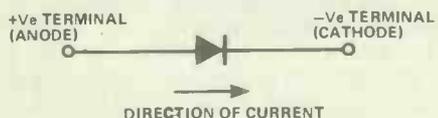
# Building Site

What to do with diodes — important practical advice for project builders from HE's Project Editor

NOW, BEFORE WE START I want to make one thing clear! I'm not going to bore anyone with any theory of what a diode is and/or how it works — you can find that out in any number of textbooks on electronics. (It's worth looking at this month's O Level Q & A too.) I'm going to talk about *how* we use a diode rather than *why*. So the only thing to remember as far as we're concerned here is that electric current will flow through a diode in one direction but if the diode is turned round *no* current will flow — simple, isn't it? The symbol used to represent a diode (see Fig. 1) is a graphical portrayal of this. You can think of it as an arrow head with a bar across the tip of the arrow. The direction of current which will flow (from +ve to -ve) is the same as the arrow head, from anode to cathode. (The terms 'anode' and 'cathode' originated with thermionic diodes.) If the diode is turned round so that the cathode is +ve and anode -ve, nothing will happen — it's as if the current has come up against a barrier (the bar in the diode symbol) which prevents it from flowing.



© Copyright MODMAGS Ltd.  
Figure 1. The symbol for a diode

Manufacturers of diodes quite often carry this symbolic representation of a diode over to the markings on the actual diode itself. The two diodes used most often in HE projects are good examples — the 1N4001 and the 1N4148. Figure 2 shows a photograph of these two devices and you can see the bar marked at one end of their bodies. The end with the bar is, of course, the cathode, although it isn't necessary to think of a diode in terms of 'cathode' and 'anode' as long as its body is marked with this bar. All you need to do with such a diode is line up the bar so that it is the same way round as indicated in the circuit diagram.

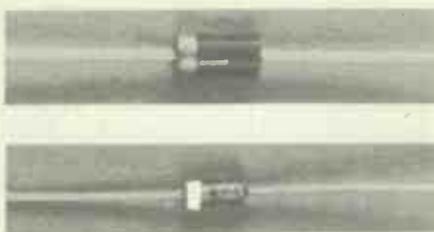


Figure 2. A 1N4001 diode (above) and a 1N4148 diode

## Diode Ratings

How does one diode differ from another? Usually in terms of only two parameters: the maximum forward current and the maximum reverse voltage which the diode can handle. For instance, the 1N4001 has a maximum forward current of 1 A, and a maximum reverse voltage of 50 V, while the values for 1N4148 are 75 mA and 75 V. So you'd obviously use the 1N4001 in a large-current circuit, say a power supply, and the 1N4148 in a circuit demanding less current, say an audio circuit or logic circuit, although the 1N4148 can operate under higher reverse voltage conditions.


## Branching Out

Although the above type of diode is the most important, it is by no means the only member of the semiconductor diode family tree. There are a number of different types of diode (tunnel, Gunn, photodiode, to name just a few), but only two are of *real* importance to the hobbyist. The first is the zener diode and the second is the LED (light-emitting diode). Fundamental to the action of a zener diode is that, in the *reverse* mode, it maintains a constant voltage across itself, regardless (within limits) of the current being passed through it.

A typical circuit using a zener diode is shown in Fig. 3. Note that the diode appears to be the 'wrong way round' (ie its cathode is positive). Look at the symbol for the zener diode — it's the same as an ordinary diode but with one edge of the bar bent down, signifying that it has a 'breakdown' or constant

voltage. This can be used to advantage as a voltage reference — a very stable DC voltage. The applied voltage at the input to the circuit may vary quite considerably but the output voltage is fixed, and it depends entirely upon the breakdown voltage of the zener.

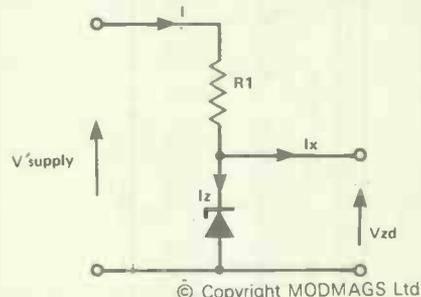Zeners are sold by two main ratings, their breakdown voltage and the maximum power they can dissipate. Individual diodes can be selected according to their breakdown voltage, and these vary from about 3 V to over 30 V in approximately ½ V steps.



© Copyright MODMAGS Ltd.  
Figure 3. Typical circuit using a zener diode

The power which a zener diode dissipates should never exceed its power rating and simple calculations can be used to check this. If, in the example shown in Fig. 3, the zener voltage is, say 4 V and resistor R1 is 100R, then the current I through the resistor is, from Ohm's Law equal to:

$$I = \frac{V}{R1}$$

Where:

$$I = \frac{12 - 4}{100} = \frac{8}{100}$$
$$= 0.08 \text{ A} \quad (80 \text{ mA}).$$

If no current ( $I_x$ ) is taken by any following circuitry then all the current flowing through the resistor will flow through the zener.

Therefore,  
 $I_z = I$ ,  
and the power P dissipated by the diode is given by:

$$P = IV,$$

or


$$0.08 \times 4 = 320 \text{ mW}.$$

A device should be chosen whose power rating is more than this, eg 400 mW.

Normally, the breakdown voltage of the zener diode will be printed on its body, for example 6V3 — meaning 6.3 V (9V1 would be 9.1 V). Otherwise the device will probably look identical to any other semiconductor diode and thus have a bar at the cathode end. Remember that a zener diode appears to go the 'wrong way round' in a circuit! If you insert it so that the cathode is negative you may well damage it, because the forward current rating of the zener is quite small.
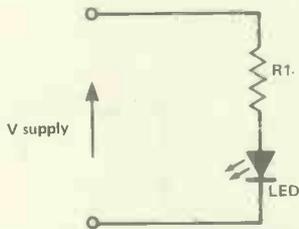
## LEDs

The other important diode-based device is the LED. This produces a coloured glow (of one of three colours, red, green or yellow/amber — although a blue LED is currently being developed), when a forward current is applied through it. A typical LED circuit is shown in Fig. 4 and you can see that the symbol of a LED is that of a standard diode but with arrows to indicate that it emits light.



© Copyright MODMAGS Ltd.

Figure 4. An LED in circuit

Light intensity of LEDs increases with applied current but the manufacturer will state a maximum forward current

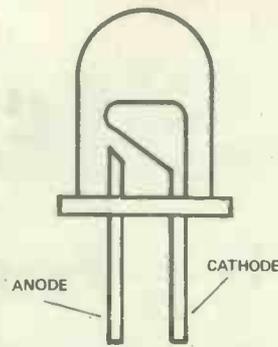


Figure 5. By holding the LED up to a bright light the junction can be seen

beyond which damage may occur. As a rule-of-thumb, a current of 20 mA produces adequate illumination from any of the commonly available LEDs.

Cathodes and anodes of LEDs are marked in a number of ways, depending on the manufacturer. Typical identification marks are painted spots, a notch or flat on the body, or different-length leads, denoting which lead is cathode and which is anode. These methods are quite standard. What is not standard, however, is whether it is the cathode or the anode which has been denoted by one of these markings: one manufacturer may mark the anode while another may mark the cathode. Don't despair, though, the puzzle is soon solved by a quick check of the published data usually supplied with these devices.

If you have a LED but have no data, there is a simple way of working out for yourself which lead is which. Hold the LED up to a bright light and look through the body. You will see the junction between the two leads where the light is emitted (see Fig. 5). The

feature to note is that one side of the junction (the cathode) appears to lean over the other.

To confuse the issue at this point, I'm going to add that the rectangular kind of LED used in the HE Rev Counter project this month (see page 27) has an opaque white plastic shield around the body of the LED (to prevent emission of light from the sides). This means that you can't work out cathode and anode just by looking at it. All is not lost however — with a battery (say a PP3) and a 2k2 resistor for R1, you can build up the circuit shown in Fig. 4 simply by holding the resistor, LED and battery, in series in your hands — whichever way round the LED lights is correct and then you can mark or just remember cathode and anode. You can use this technique for any LED (see Fig. 6).

It's worth noting that LEDs aren't usually as easily damaged as zeners, so if you still are uncertain which lead is which, put it in circuit — if it doesn't work, turn it round — you shouldn't damage it.

## Cracking Up

Finally, a word concerning the insertion of a diode into a circuit board. Many types of diode (such as the 1N4148, most zeners and some LEDs) have a brittle body. If you bend the leads to fit the board with your fingers, you may crack the casing and the devices can literally fall apart. Using a pair of fine, long-nosed pliers you can prevent damage by holding the diode firmly and bending the lead at the far side of the nose of the pliers. (see Fig. 7).


Diodes with all-glass bodies are also easily damaged by too much heat, so be careful when soldering them into circuits. A good hint is to let the whole area cool down after soldering one lead, before tackling the other. You may waste a minute of your time waiting for the diode to cool, but it could save you the expense and bother of renewal.

HE




Figure 6. By holding a LED, resistor and battery in series you can find out which lead is which

Figure 7. Use a fine pair of pliers to hold the diode while you bend the lead

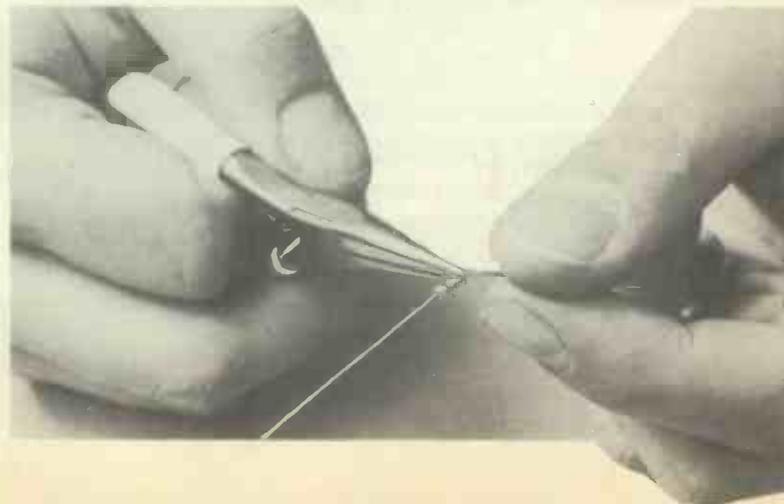
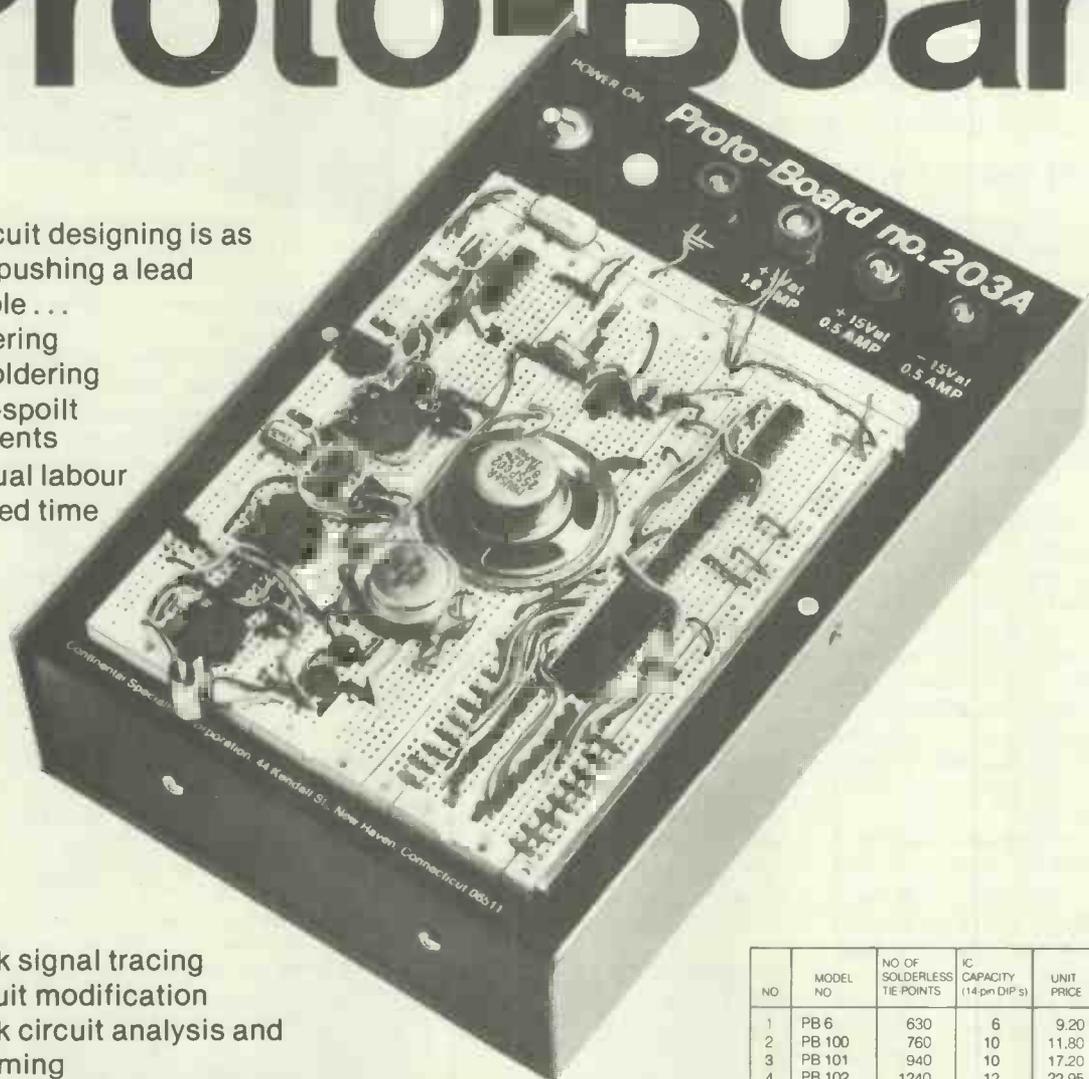
# The Proto-Board<sup>®</sup>

Now circuit designing is as easy as pushing a lead into a hole . . .  
 No soldering  
 No de-soldering  
 No heat-spoilt components  
 No manual labour  
 No wasted time



For quick signal tracing and circuit modification  
 For quick circuit analysis and diagramming  
 With or without built-in regulated power supplies  
 Use with virtually all parts — most plug in directly, in seconds.  
 Ideal for design, prototype and hobby

NO	MODEL NO	NO OF SOLDERLESS TIE-POINTS	IC CAPACITY (14-pin DIP's)	UNIT PRICE	PRICE INC P&P 15% VAT	OTHER FEATURES
1	PB 6	630	6	9.20	11.73	Kit
2	PB 100	760	10	11.80	14.72	Kit
3	PB 101	940	10	17.20	21.21	
4	PB 102	1240	12	22.95	27.83	
5	PB 103	2250	24	34.45	41.34	
6	PB 104	3060	32	45.95	54.56	
7	PB 203	2250	24	55.15	65.14	5V @ 1A
8	PB 203A	2250	24	74.70	87.63	5V ± 15V
9	PB 203AK	2250	24	59.00	69.57	5V ± 15V & Kit

## Tomorrow's tools for today's problems

CONTINENTAL SPECIALTIES CORPORATION

C.S.C. (UK) Limited, Dept. 14U, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.



1	Qty Req	2	Qty Req	3	Qty Req	4	Qty Req	5	Qty Req	6	Qty Req	7	Qty Req	8	Qty Req	9	Qty Req
---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------	---	---------

Name \_\_\_\_\_ Address \_\_\_\_\_

I enclose Cheque/P.O. for £ \_\_\_\_\_ or debit my Barclaycard, Access, American Express card no. \_\_\_\_\_ exp. date \_\_\_\_\_

FOR IMMEDIATE ACTION — The C.S.C. 24 hour 5 day a week service Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately tick box

C.S.C. (UK) Limited, Dept. 14U  
 Unit 1, Shire Hill Industrial Estate,  
 Saffron Walden, Essex. CB11 3AQ.  
 Telephone: Saffron Walden (0799) 21682  
 Telex: 817477

For FREE catalogue

# Digital Speedo-2

Part two of our Speedo project deals with final construction and suggests methods of connecting the pickup sensor to your car



After following last month's construction advice builders should, by now, have reached the stage where they possess two made-up boards which need only to be connected with 10 jump leads between the two. **Figure 1** shows where all interboard connections are to be made — leads of about 4" length are OK. You can then either cable-tie them or simply leave them all floating.

That almost concludes the building side of the project. After drilling the case at the back and inserting grommets for the power lead and sensor wire, the main board can be inserted into the case between the bottom pair of PCB grooves — which leaves the display board to drop in the front. The acrylic panel should now fit into the front and when the rectangular bezel is clipped in place, all boards should be firmly held in the case.

So far so good, but now we move on to the tricky bit — positioning the pickup sensor on the car. As we explained in the last issue the operation of the sensor relies on the fact that magnets, going past a coil, induce a current in it. From this seemingly simple statement we can see that the magnets need to be positioned on some rotating shaft which rotates with a velocity proportional to the vehicle's linear velocity. It happens that the drive shaft of a car does just that — so the magnets (four in all) are positioned on the shaft in a similar manner to that shown in **Fig. 3**. They should, ideally, be equidistant around the shaft and first secured with pads of double-sided adhesive foam. The centripetal force which they encounter (remember that at 70 MPH the shaft will rotate at approximately 70 Hz) will be quite large and so the pads should be only a temporary fixing while you fasten the magnets permanently with cable ties. Although the circumference of the shaft will be more than the length of one cable tie, two or more can be con-

nected together to make a longer one.

Two separate bands of ties should be used to hold the magnets to the shaft.

The positioning of the sensor along the length of the drive shaft needs also to be considered and obviously, is dependent on the individual car. Somehow the coil has to be fixed on the body of the car so that it is close enough (within 2") to the magnets. The rear axle is, of course liable to vertical movement and hence, the drive shaft at the rear is too. So the pickup is best positioned toward the front of the drive shaft. Position the coil so that the magnets are never further away than 2" from the coil. Care should also be taken to ensure that the coil isn't too close (say less than 1/2") to the magnets to prevent actual contact under bumpy road conditions!


The diagrams give an idea of how we fixed the sensor to the car used. The car had a central, fixed point to the drive shaft (which was actually part of the body) and so the coil was fastened

to a length of aluminium bar, shaped to fit and bolted at each end, to the car floor panel. This is the area where readers may need to put on their thinking caps and use a bit of ingenuity — the problems encountered will depend on the particular make and model of car used — we can obviously only give general guidelines for a solution.

In summary, however, it doesn't seem to make any difference to the operation of the Speedo in what polar direction the magnets are travelling. The coil appears to pick up an adequate signal for the circuit to process as long as it is within 2". The main point, though, is that the central soft metal core of the coil should be perpendicular to the face of the magnets.

It only remains to run a length of screened lead from the coil to the inside of the car and to the Speedo. Power is connected to the Speedo via an in-line fuse (1 A) and the ignition switch and your project is complete.

The two Speedo boards with that of the Rev Counter

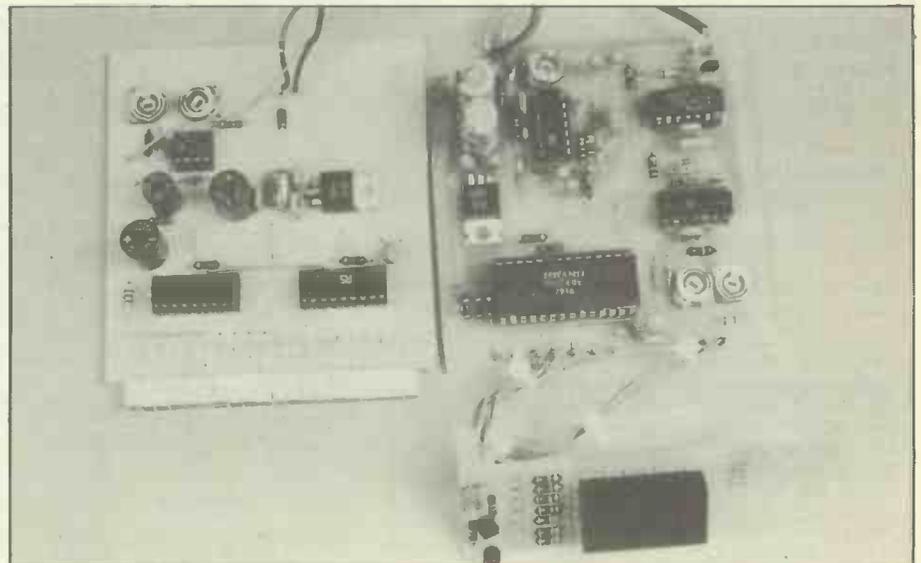

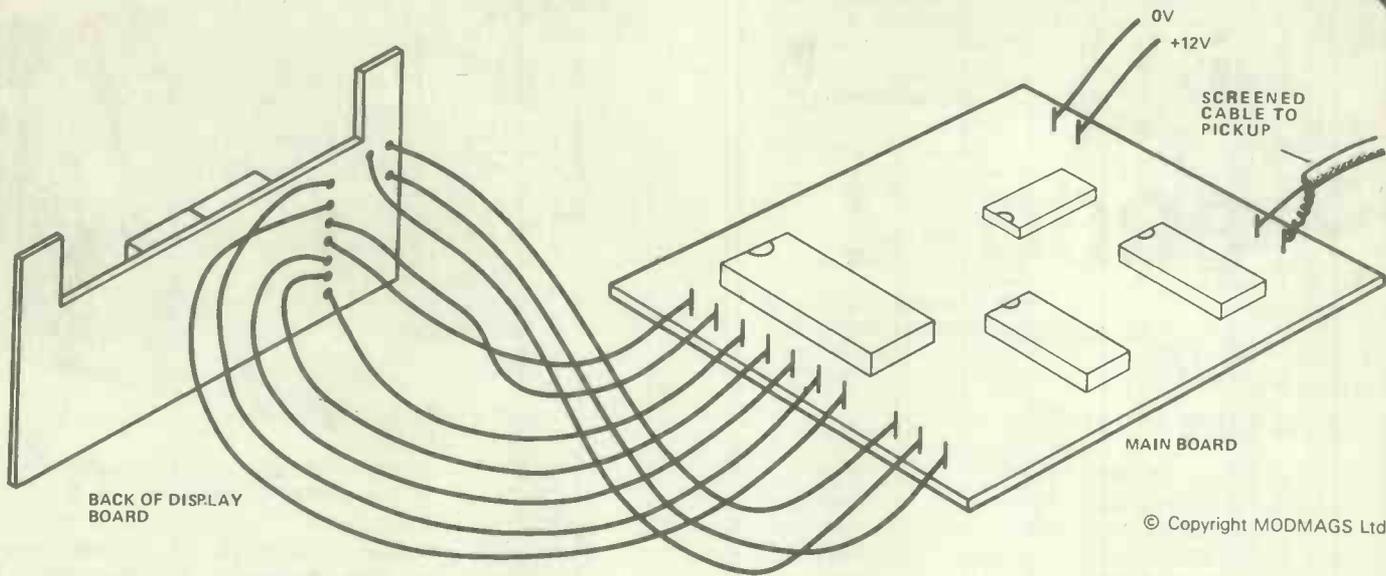


Figure 1. Connection details of the two boards of the Speedo

## How It Works

The operation of the pickup sensor depends on the electromagnetic effect of a changing magnetic flux in the vicinity of a conductor — causing a current to flow in that conductor. This effect is also used in the pickup of the HE Tacho project in this issue.

As the magnet approaches the coil in a particular direction a current is induced in it, producing a voltage across the coil as shown in Fig. 2. The voltage increases first in one direction and then reverses as the magnet passes the coil (the magnetic flux changes direction). The output is approximately sinusoidal around the area (waveform a).

If the magnet rotates with a faster velocity the sinusoidal 'blips' occur closer together and (because the change of magnetic flux is more rapid) a larger voltage is produced (waveform b).

The output voltage from the coil is passed onto the rest of the circuit for processing as explained last month.

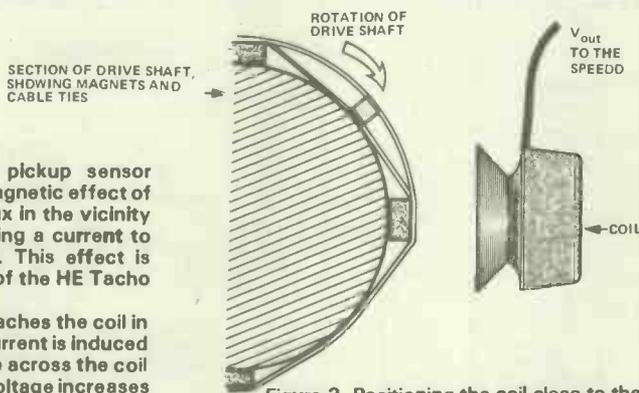


Figure 2. Positioning the coil close to the drive shaft results in the waveforms below

SINUSOIDAL-TYPE 'BLIPS' CAUSED BY A MAGNET PASSING THE COIL AT SLOW SPEED

© Copyright MODMAGS Ltd.



NEAT-SINUSOIDAL WAVEFORM OF SENSOR AT HIGH SPEED

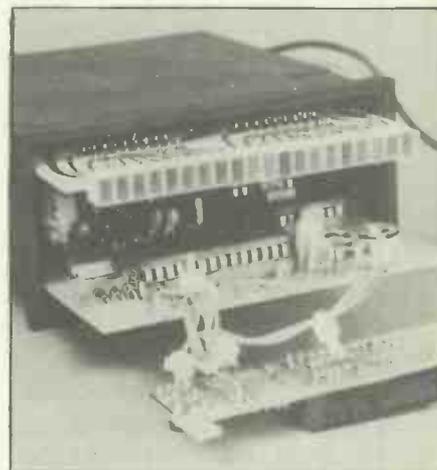


Figure 3. It's a tight fit — but all three boards of the Speedo and the Rev Counter do fit in the case

## Parts List

### MISCELLANEOUS

4 small magnets (reed switch type)  
telephone pickup coil — Altai TC200  
cable ties

## Buylines

The magnets are standard reed switch operating types and should be available at any good component stockist. Likewise the telephone pickup coil should be no problem — we only specify the particular variety mentioned in the Parts List because it was the first we could lay our hands on. You may like to experiment with other types if you can't obtain that one.

The cable ties are made by Vero.


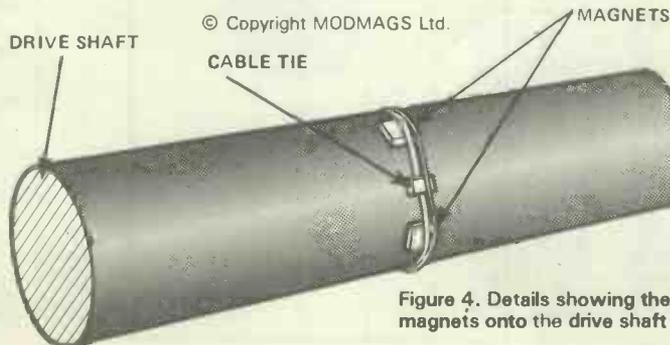


Figure 4. Details showing the positioning of magnets onto the drive shaft

HE
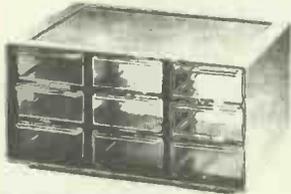
# GREENWELD

443 MILLBROOK ROAD, SOUTHAMPTON SO1 0HX  
All prices include VAT—just add 40p post. Tel (0703) 772501



## COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors, diodes and I.C.s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts. All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 165mm with 9 drawers into which all parts can be neatly located. If bought individually parts plus case would cost over £50 but we are offering this for ONLY £33.95 + £1 p. & p. Simply send a cheque or P.O. for £34.95 for immediate despatch.

- CONTENTS:**
- 200 1/2 watt resistors
  - 20 Wire wound resistors
  - 70 Ceramic Capacitors
  - 70 Mylar Capacitors
  - 50 Polyester Capacitors
  - 56 Electrolytic Capacitors
  - 61 Transistors
  - 12 I.C.s
  - 20 L.E.D.s
  - 55 Diodes and rectifiers
- Altogether 614 components  
Plus FREE surprise gift.

### EX-COMPUTER PANELS

Z527 2 x 6V reed relays, 6 x 2S030 or 2S230 6 x 400V rects. + Rs. Only 50p.  
Z529 TTL pack — Panels with 74 series on, together with code sheet. From simple gates to complex counters, 20 ICs £1; 100 ICs £4.

### COMPONENT TRAY

Attractive yellow tray 285 x 165 x 42mm with clear hinged lid and movable compartments. Up to 15 can be made from dividers supplied. As an added bonus, a selection of new surplus components are included, all for the special low price of £4.35.

### BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia x 20mm 85p.  
Z402 Miniature type buzzer, 6, 9 or 12V. only 22 x 15 x 16mm. Very neat 85p.  
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. Only £1.

Z459 115-230V ac high torque motor with geared reduction down to 60 rpm. Sturdy construction, 70mm dia x 20mm. Spindle 6mm dia x 20mm long. Only £2.  
WB92 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket 85p.  
WB90 DIL Reed relay SPCO 2.4-10V. 200R coil. Only £2.20.  
WB47 Low profile PC mntg 10 x 33 x 20 mm 6V coil, SPCO 3A contacts. 93p.

### VEROBLOC BREADBOARD

New from Vero, this versatile aid for building and testing circuits can accommodate any size of IC. Blocs can be joined together. Bus strips on X & Y axis — total 360 connexion points for just £4.15.

## ELECTRONICS A NEW AND EXCITING HOBBY!!

BIG WELL ILLUSTRATED BOOK  
Ideal for beginners — gives lots of general information — explains how to build lots of projects — Intercom, Rain Alarm, Radios, Organ, Parking Light etc. All parts supplied and can be re-used on special deck provided, so NO SOLDERING is required. Just needs 4½V battery.

£17.50 inc. VAT & Post

Also ADVENTURES WITH MICROELECTRONICS — Explore the world of silicon chips — All components & Deck, £27.95 inc. VAT & Post.

## THE SPECTACULAR 1981 GREENWELD Component Catalogue

Bigger and better than ever!!!

- \* 60p discount vouchers
  - \* First Class reply paid envelope
  - \* Free Bargain List
  - \* Priority Order Form
  - \* VAT inclusive prices
  - \* Quantity prices for bulk buyers
  - \* Free IC Data Sheet
- SEND 75p (inc. post) FOR YOUR COPY NOW!!

## BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST, VAT INCLUSIVE PRICES.

K001 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1,000pF, total 210. £4.80.  
K002 Extended range 22pF to 0.1µF, 330 values £7.66.

K003 Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ, 110 altogether for £5.40.

K004 Mylar capacitors, min 100V type 10 each all values from 1,000pF to 10,000pF. Total 130 for £4.70.

K007 Electrolytic capacitors 25V working small physical size, 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.59.  
K008 Extended range, as above, also including 220, 470 and 1000µF. Total of 100 for £6.35.

K021 Miniature carbon film 5% resistors CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors £5.95.

K022 Extended range. Total 850 resistors from 1R to 10M £8.20.

K041 Zener diodes, 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for £15.95.

NEW K051 LEDs — 10 each red, green & yellow 3mm & 5mm, with clips. Total 60 LEDs for £8.95

### REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110 x 82 x 33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: 1/2 Output voltage 0-28V

1/2 Output current 20mA-2A

1/2 Source impedance 0R1

Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. Only £7.75

### TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number — almost all are full spec. devices. Some have bent leads. Over 30 different types have been found by us including BC184/212/238/307/328, BF196/7, 21x107/8/9/34Z/450/550, etc. Only available as a mixed pack at £3 per 100, £7 per 250, £25 per 1,000.

### ELECTRONIC AIR FRESHENER KIT



- Battery Operated
- Replaceable Fragrance
- Continuous Air Freshening
- Robust Construction

This novel kit contains everything you need to make one of the most advanced air fresheners of its kind. Styled to take its place in any room in your home and do its job quietly and unobtrusively.



The automatic timing circuit switches on a fan for a few seconds at regular intervals to send an odour neutralising fragrance into every corner of your room.

The kit includes components for EITHER a 4 or 15 minute timing circuit, miniature D.C. motor and moulded parts in high impact styrene to provide an easily maintained, elegant appearance.

ONLY £7.95.



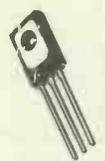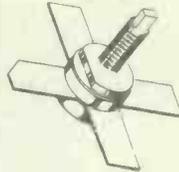RUBBER DUCK CALLING LOGI BAIRD — "SAY MAC WHERE DO I GET R.F. TRANSISTORS 2.30 MHz, CIRCUIT BOARDS AND APPLICATION NOTES?"



GAILAN OF COURSE!! THEY'VE ALWAYS GOT WHAT I WANT, MOTOROLA, M.R.F. AND JAPANESE REPLACEMENT TYPES



BURDETT ROAD, WISBECH  
CAMBS PE13 2PS

TEL: 0945 63281  
TELEX 32630

# TELEVISION SOUND IS GOOD!

Yes it's true—but you'll need to listen through a Minim Television Sound Tuner to be convinced. Music, wildlife, even the news suddenly comes to life when you can hear all the detail that you expect from High Fidelity equipment.

Connect the Minim Television Sound Tuner to the amplifier or music centre or listen directly on headphones so as not to disturb others.

Further information will only cost you 12p — stamp out poor television sound!

Name .....

Address .....

HE1

Minim Audio Limited, Lent Rise Road, Burnham,  
Slough SL1 7NY. Tel: Burnham 63724

## Minim Audio


make a note of our name!

# Into Digital Electronics

More advanced circuits this month as Ian Sinclair describes how to use binary counter ICs, a seven-segment display and SISO, PIPO, PISO and SIPO shift registers

A BCD COUNTER, a we've seen, can be made from four flip-flop units, with a gate for detecting the ten (1010) output and operating the reset. This BCD counter arrangement is so common that all its flip-flops and gates are manufactured in IC form, ready for use. There are several BCD counter ICs, but the one we'll use is a very common variety, the 74LS90.

The pinout of the 74LS90 is shown in Fig. 5.1. The four outputs are labelled QA-QD, QA being the lowest significant digit (the one on the right hand side when we write a binary number) and QD the highest significant digit. There are two counting inputs, A and B. The A input is an input to one of the flip-flops, whose output, reasonably enough, is QA. The B input is to the remaining chain of three flip-flops, which are gated so that they divide by five. For a BCD count, therefore, a connection has to be made from QA to input B, and the signals to be counted are taken to the A input.

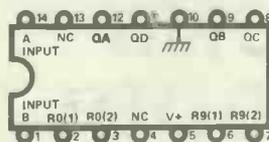


© Copyright MODMAGS Ltd.

Figure 5.1 Pinout for the 74LS90 BCD/binary counter chip

There are also four reset terminals. The two terminals marked RO will reset the 74LS90 to zero when both are allowed to go high. For normal counting, therefore, at least one of these inputs must be earthed. Similarly, the inputs marked R9 will reset the counter to nine (1001) unless one of these terminals is earthed. By making use of gating and these reset terminals, various count numbers can be obtained, but the 74LS90 is practically always used just as a straightforward decade (scale of ten) counter with BCD outputs.

We can try it all out quite easily using the Eurobreadboard. Remove the J-K flip-flops from the board, and plug in the 74LS90 (a 14-pin IC) with its pin 1 on line 10A and pin 14 on line 10B.

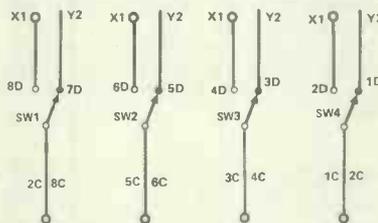Keep your 74LS132 oscillator in place to provide clock pulses, and make sure that all the switches are wired as they were at the beginning, so that up gives logic 1 and down gives logic 0 — Fig. 5.2 is a reminder of this switch wiring.



© Copyright MODMAGS Ltd.

Figure 5.2 The conventional switch arrangement — a reminder

Now make the connections which are needed to use the 74LS90 as a decade counter, displaying its count on the LED's. The circuit is shown in Fig. 5.3. One of the spare gates of the 74LS132 is used to control the clock pulses, so that SW1 acts as a count/wait switch. Switch SW4 is wired to the reset (0), terminal, so that the counter can be reset with this switch up.

When the wiring is complete, switch on and use SW4 to reset. This counter, like any device containing flip-flops, will always give an unpredictable output at switch on, so that it must always be reset after switching on. Circuits (such as computers) which contain a large number of flip-flops need what is called an 'initialisation procedure' which resets all the flip-flops, otherwise the circuits would be unusable.

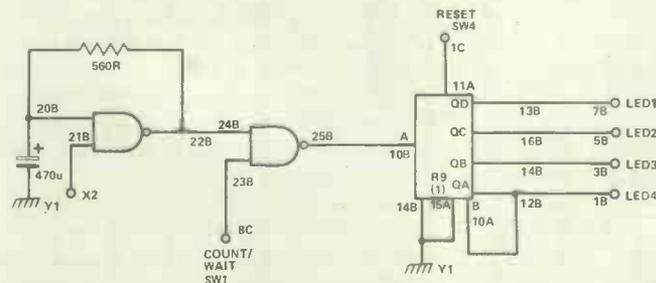


Figure 5.3 A clock-pulse oscillator driving the decade counter through a gate. The outputs of the counter are taken to LEDs

Now watch the LEDs as you switch SW1 up to start the count. The wiring given in the diagram has been arranged so that the LEDs are in the correct order to show a binary number, with QD indicated on the left-hand side and QA on the right-hand side.

## Decimal Readouts

All this binary readout with LEDs is very interesting, but for most readouts we want to see decimal numbers which we're accustomed to. To show a decimal digit there are several types of display systems, but by far the most common is the LED seven-segment display. The arrangement of a seven-segment display is shown in Fig. 5.4, and it consists of seven bars of LED material arranged in a figure eight pattern. There is often an eighth segment, a decimal point, but this is not activated by the decade counter so we'll ignore it for the moment.

Now at this point we have a problem of a type which gets more familiar (and more complicated) as we go on with digital electronics. There are four outputs from the 74LS90 counter and there are seven segments to drive. In addition, the signals from the counter are TTL signals, 0 V or +5 V, and the signal needed at the display to make a segment glow is about 2 V. We need some method of converting BCD signals into seven segment signals, and TTL levels into LED segment levels. This sort of problem is an interfacing problem, and like most interfacing problems it's solved by using another IC.

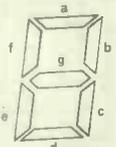


Figure 5.4 Layout of a seven-segment display. The lettering which is shown against the segments is always used to indicate these segments

The other IC is a BCD-to-seven-segment decoder. Its inputs are the BCD signals from the counter and its outputs are the seven segment lines. These will still deliver signals at TTL levels, so we connect the decoder outputs to the display inputs by resistors, which will limit the amount of current. Without these resistors, the display would be bright, but not for long!

It's straightforward so far, then, but there is one minor complication. There are two varieties of seven-segment displays using LEDs. Each LED in a display has an anode and a cathode. We don't need to have separate connections to each anode and cathode, so we can connect one lot together.

Common-cathode LED displays have one cathode terminal, and the inputs are the separate anode terminals. Common-anode LED displays have one anode terminal, and the inputs are to the separate cathode terminals. Because the display glows when an anode is taken positive or a cathode negative, the two types must use different decoders, or one decoder type, with seven inverters for the opposite type of display.

For our board, the most convenient display is the DL728, available from Maplin (order number FR38R). This is a common-cathode display, and the decoder which goes with it is the 74LS48. We're using 470R resistors to limit the current in each segment to about 6 mA. This is more out of consideration for your power supply than for the display, which could take quite a bit more, up to 20 mA per segment.

### Counter Circuit

The circuit for the complete counter and display is shown in Fig. 5.5. We've used quite a lot of the board for this, and several new components. The 74LS48 is placed with its pin 1 in line 18C and pin 16 in line 18D, replacing a 74LS76. Note that this is a 16-pin chip. Incidentally, the 74LS48 is sometimes quite hard to get — lots of people advertise it but can't necessarily supply it. If you're unlucky, just reorder for the 7448 instead — it will take more current but it operates in the same way. The display is mounted on columns C and D of the Eurobreadboard. The pinout, looking from the top, is shown in Fig. 5.6 and the mounting position is with pin 1 in line 10C and pin 14 in line 10D. The connections are then as shown in Fig. 5.5. Check your connections before testing the circuit, and then set SW1 down (to isolate the clock) and SW4 up (to reset the counter). Switch SW2 is con-

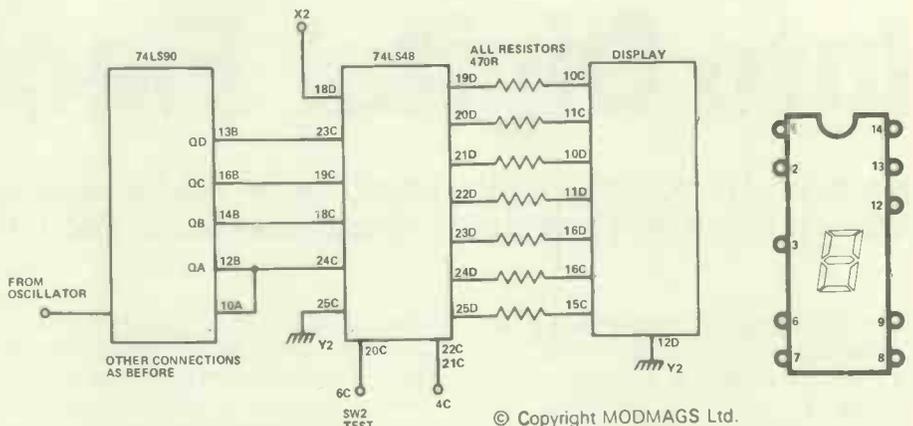


Figure 5.5 Counter-decoder-display circuit. Connections to the 74LS90 counter are the same as they were in Fig. 5.3, but the outputs Qa to Qd are connected to the decoder inputs, and the decoder outputs are connected through 470R resistors to the display

nected to the LAMP TEST pin of the 74LS48 (line 20C) and SW3 is connected to the RB input (lines 22C, 21C). Indicator LED 1 on the board is connected to the RB output pin of the 74LS48 — we'll explain these RB inputs and output later on. For the moment, keep the SW2 up and SW3 down.

Switch on, and you should be rewarded with a zero on the display, since the counter is reset to zero. With SW2 down, the remaining segment will light up, because the 'LAMP TEST' input does just that — it switches on each segment of the LED display. That way, you can test displays without having to watch each stage of a count. Put SW2 up again, so that the zero shows, and switch SW1 up, to start the count. The display should now start to go through a normal counting sequence 1, 2, 3 and so-on up to 9. On the next clock pulse, the gates in the 74LS90 will reset the counter so that the zero shows again.

Suppose you wanted to display tens and hundreds? It's just a matter of repeating these circuits, and the method is shown in Fig. 5.7, though we haven't room to construct it. The units counter has its QD output connected to the A-input of the next counter, and the ripple-blanking input to the next output as shown. Each counter has its own decoder and seven-segment display.

Ripple-blanking? That's a useful feature of the 74LS48 which we don't need in our circuit, but which is handy when we connect up a lot of counting units together. When the RB connections are 'daisy-chained' (Fig. 5.7) then the display suppresses leading

© Copyright MODMAGS Ltd.

### DISPLAY

74LS48	PIN	FUNCTION
1.QB INPUT	1	ANODE F
2.QC INPUT	2	ANODE G
3.LAMP TEST	3	NO PIN
4.RB OUT	4	CATHODE
5.RB IN	5	NO PIN
6.QD INPUT	6	ANODE E
7.QA INPUT	7	ANODE D
8.EARTH	8	ANODE C
9.E OUTPUT	9	ANODE DP
10.D OUTPUT	10	NO PIN
11.C OUTPUT	11	NO PIN
12.B OUTPUT	12	CATHODE
13.A OUTPUT	13	ANODE B
14.G OUTPUT	14	ANODE A
15.F OUTPUT		ONLY ONE CATHODE CONNECTION NEED BE USED
16.+5V		

Figure 5.6 Pinouts for the display and for the 74LS48 decoder

zeros. In plain English, that means it would never, for example, show 0012, only 12. The zeros which come before any other numbers are simply not displayed — the ripple-blanking input acts to gate them off.

Before we leave counting, there's one important point about the 74LS48. At each of the possible input binary numbers from 0000 to 1111, there is a different set of digits on the seven output lines. This is a simple form of read-only memory chip, because a definite output is always obtained for each input. If we thought of the 74LS48 as a memory circuit, the inputs A, B, C, D would be called the 'address', and the outputs the data. For example, an address of 1000 (eight) gives a data output of 1111111 (all segments lit). Why read-only? Well, there's nothing we can do to change the data which comes out of the 74LS48. An input of 1000 will always give an output of 1111111, and we can't make it 1010101 by any sort of juggling with the chip. The memory circuits for microprocessors are also circuits which will output a different set of bits at each input address, and if you're familiar with chips like the 74LS48, then memory circuits don't seem quite so unfamiliar.

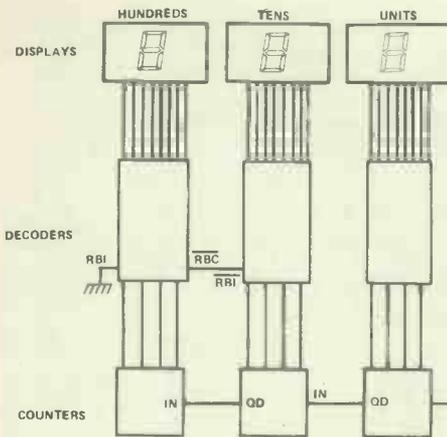


Figure 5.7 How a count of up to 99 can be achieved. Each digit needs one 74LS90, equivalent to one 74LS48 decoder, and a seven-segment display. The Qd of the units counter is connected to the input of the tens counter, and the Qd of the tens counter is connected to the input of the hundreds counter. The hundreds and tens decoders have their ripple-blanking connections made so that leading zeros are suppressed

## Back to the Beautiful Movers

Decimal counting and display is just a brief interlude in a lot of binary circuits, and we need now to return to shift registers. We make a shift register from four J-K flip-flops, but nowadays, a shift register would be bought as a complete IC. Shift registers, despite the name, aren't used just for shifting, and we need to know a bit more about their uses nowadays, because microprocessors contain a lot of shift registers.

There are four basic types, labelled SISO, PIPO, PISO, and SIPO. As usual, the letters are the first letters of words, S for serial, P for parallel, I for input, O for output, and the letters therefore describe how each shift register can be used. In the descriptions which follow, remember that a bit means a binary digit, 0 or 1.

### SISO

The SISO shift register is serial in, serial out. A register of this type would have one input and one output, with a clock terminal. A bit at the input is shifted in by a clock pulse, and won't appear at the output until several clock pulses later. How many? That depends on how many flip-flops are in the register, a complete shift through the register will take as many clock pulses as there are flip-flops. It's a useful way of delaying a set of bits on their way through a circuit, or of storing bits for a set number of clock pulses.

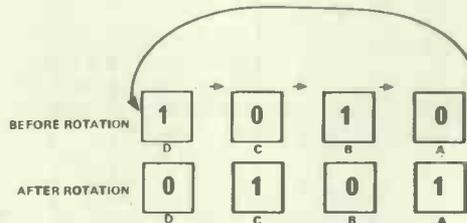


Figure 5.8 Rotating a set of bits with a shift register

© Copyright MODMAGS Ltd.

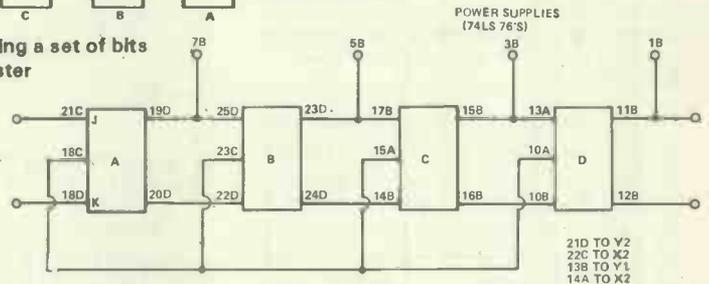


Figure 5.9 Basic shift register layout. The display and the 74LS48 have been removed from the board, and the 74LS76s replaced, wired as shown. The next series of diagrams will consist of additions to this basic scheme

### PIPO

The opposite extreme is the PIPO register, parallel in and parallel out. We can use this one without ever applying clock pulses, simply as a latch to hold some data bits. If a serial input is also provided, this can rotate a set of bits (Fig. 5.8), so that the bits which you read out are not in the same positions as they were when you put them in. It, too, has its uses.

### SIPO & PISO

The SIPO and PISO are both extremely useful forms of registers. The PISO is parallel in, serial out, so that a complete group of bits can be stored in the register, using one line for each bit, and then read out one by one along a single line. This is how information in groups of bits (like the eight bit unit, or byte, which is used by most microprocessors) can be sent along a single wire to a video terminal, a printer or a cassette recorder. The PISO register is, of course, only a part of the whole system but its part is the important one — conversion from parallel eight bits to serial one-at-a-time.

A SIPO register is the gubbins you need for the opposite conversion. When you have bits in serial form coming along a single line, and you want to assemble them into groups to deliver to some system which deals with groups (display, microprocessor or whatever), then the SIPO register provides the method. The bits enter the serial inputs, are shifted along the register at each clock pulse, and can be read at the parallel outputs after the correct number of clock pulses. We've simplified all this, of course, because there are usually other problems to solve. You have to be sure that when you send bits out serially, each of them is doing something. There's no point, for example, in sending bits at a rate of 100,000 bits per second to a printer

which can cope with only a few hundred bits per second. Taking another example, if you're reading serial bits into a register, you have to make sure that you are grouping them correctly, and not taking some bits from the end of one group and some from the start of the next. There are several ways of ensuring that these actions go smoothly: one of them is the use of bits to identify stop and start, but we don't need to go into these problems right now.

### Practical Shifting

What we do need, however, is some first hand experience with a shift register. We could use various IC shift registers to demonstrate all of these actions, or even use a 74LS295, which has both serial and parallel inputs and outputs to demonstrate all four types of registers, but the easiest and least pricy method is just to use the 74LS76s which we already have. After all, it's the actions we want to show, not the look of the IC.

To start off with, then, place the two 74LS76 ICs back on the Eurobreadboard. Integrated circuit ICA should have its pin 1 in line 10A and pin 16 in line 10B and ICB should have its pin 1 in line 18C and pin 16 in line 18D. We'll need the 74LS132 as well, with its pin 1 on line 19A and pin 14 on line 19B. The power supply connections are as shown in Fig. 5.9 and all the switches are connected conventionally: a reminder is also shown in Fig 5.2.

With these preliminaries over, we can start. The board should now contain the three chips, with power supply links; but no interconnections. Link up the J and K inputs to the Q and Q outputs in the usual form of a shift register (Fig. 5.9) and we now have the basic unit which we'll use to demonstrate all the types of shift register.

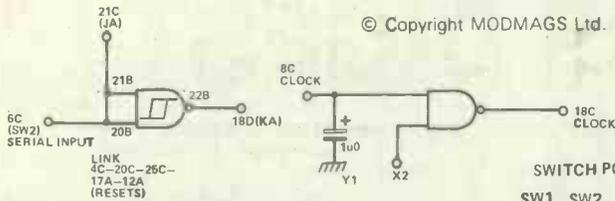


Figure 5.10 The additions to the basic shift register circuit for implementing a SISO register

Start off with SISO. For this one we want to be able to place bits in serially at the input of F/FA. To do this, we need an inverter between JA and KA, and one of the gates of the 74LS132 can be pressed into service for this task. We'll use a switch to clock the register, SW1, and another of the gates of the 74LS132 is used as a simple debounce circuit for the switch. Switch SW2 is now used to provide the serial input, and LED4 indicates the serial output at QD (Fig. 5.10).

With four flip-flops in the register, any bit placed at the input using SW2 will need four clock pulses from SW1 to complete its movement through the shift register. We must first ensure that all the flip-flops are cleared, and that SW3 has been arranged to do this.

With the circuit wired as shown, turn on the 5 V supply, and reset all the flip-flops, using SW3. Switch SW2 up to place a 1 on the input, and operate SW1 once to shift this 1 to QA. Switch SW2 down so that the input now remains at zero, and operate SW1 three more times. This should result in a 1 appearing at the output (LED4).

The PIPO shift register needs a different set of switch connections, but the NAND gates are not required. Three switches, SW2, SW3, SW4 are used to set the flip-flops, and one to reset (SW1). The switches have been deliberately arranged so that no flip-flop can have both set and reset terminals earthed simultaneously (Fig. 5.11).

All four of the LEDs are now used to indicate the state of the register, LED 1, for flip-flop A, 2 for B, 3 for C and 4 for D. With the wiring shown, reset by pushing the slider of SW1 down.

Push the sliders of switches SW2, 3, 4 so as to select one flip-flop to set — Fig. 5.12 shows how the switches are set for each flip-flop. Switch SW1 is then pushed up to set that flip-flop. Unless SW1 is pushed down again, the flip-flops which have been set, indicated by the LEDs, will remain set — which is the principle of the PIPO register. We haven't used clock pulses — for this sort of application we don't need them.

© Copyright MODMAGS Ltd.

Figure 5.11 The switch modifications for a PIPO register. The connections made in Fig. 5.10 must be removed first

SWITCH POSITIONS				—SETTINGS—			
SW1	SW2	SW3	SW4	A	B	C	D
L	X	X	X	0	0	0	0
H	H	X	H	1	0	0	0
H	H	X	L	0	1	0	0
H	L	H	X	0	0	1	0
H	L	L	X	0	0	0	1

Figure 5.12 Table of switch operations for Fig. 5.11

Next on the list is the PISO. With our ration of four switches, we can't set the flip-flops individually and still have the register free to be clocked. Figure 5.13 shows the circuit, SW3 and 4 are used for setting, and SW2 selects set or reset. Switch SW1 lets you isolate the set and reset so that the register can be clocked, using the slow clock pulse generator formed by one of the 74LS132 gates. Indicator LED4 is used to show the state of QD which is the serial output JA = 0, KA = 1, so that the first flip-flop is reset when the clock pulses start. This ensures that the register is emptied by four clock pulses. One of the NAND gates is connected so that clocking starts when the set inputs are isolated.

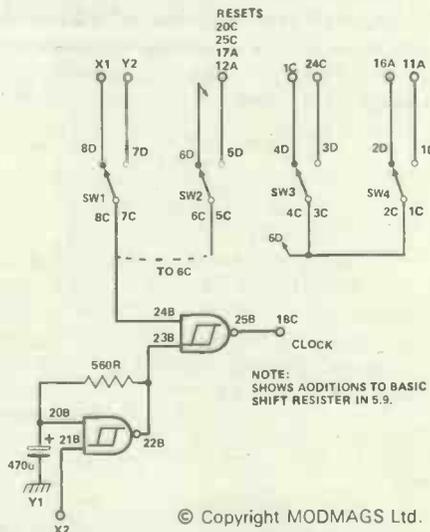


Figure 5.13 Connections for a PISO register. The connections shown in Fig. 5.11 are removed: the diagram shows the additions to the basic circuit in Fig. 5.9

Wire up, switch on, and use SW2 (down) and SW1 (down) to reset the flip-flops. Now switch SW1 up to isolate the set/reset inputs, and SW2 up to select set. Switches SW3 and SW4 can now be arranged so that either 1 and 3 or 2 and 4 will be set when SW1 is pushed down again. Whenever SW1 is pushed up again, the clock pulses will start to operate

© Copyright MODMAGS Ltd.

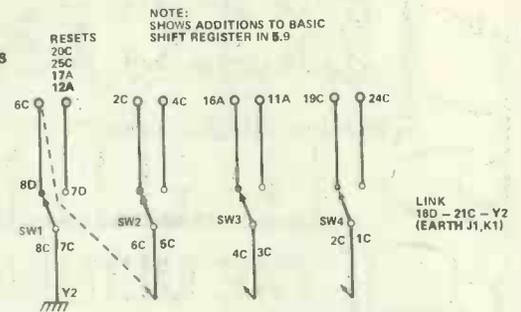


Figure 5.14 The SIPO register connections. Once more, this shows the additions to the circuit in Fig. 5.9, with previous additions removed. This also restores the switches to normal operation for the next set of operations to be described next month

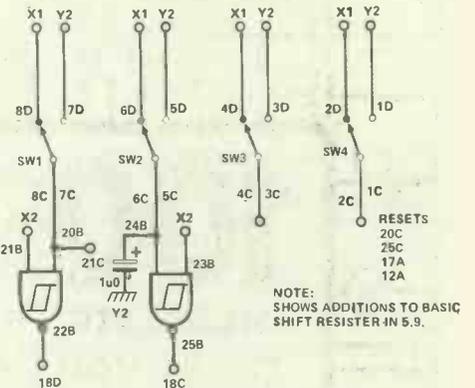


Figure 5.14 The SIPO register connections. Once more, this shows the additions to the circuit in Fig. 5.9, with previous additions removed. This also restores the switches to normal operation for the next set of operations to be described next month

the flip-flops, and the bits which have been set will shift right at each clock pulse. After four clock pulses, all the original bits have been shifted out (remember that some of the original bits were zero) and the register is filled with zeros.

The SIPO shift register is easier on switches (Fig. 5.14). This time each LED shows the state of one of the flip-flop outputs, and the 'signals' are fed in at each clock pulse. Switch SW4 resets the flip-flops, SW1 is used to switch the serial input high or low, and SW2 is used as the clock pulse generator, along with its debouncing circuit, one of the NAND gates of the 74LS132.

Wire up, switch on, and use SW4 to reset, so that all of the LEDs are extinguished. Now use SW1 to place a 0 (down) or 1 (up) at the input, and load this in with a complete switch cycle (up to down) of SW2. Pick another value (0 or 1) for SW1, and use SW2 again. At each load, a value will feed into F/F A, and the previous value will be shifted along to F/F B. After four clock pulses, the register will be full, ready to read out its content over four lines.

By now we've covered most of the really important basic digital circuits with one important exception — the adder. We'll keep that for next month.

HE

# ELECTRONICS DIGEST

**THE ULTIMATE DATA BOOK?**

**No  
3  
£1.50**

**100** pages packed with pin-outs, circuits, characteristics, equivalents, formulae etc. — in fact everything electronic you ever needed to know but had no-one to ask.

Details from Modmags Ltd.  
145 Charing Cross Road,  
London WC2H 0EE

## AVOID DANGER from RADIATION WITH OUR RADIATION DETECTOR

Recommended for: Civil  
Defence, Fire, Hospital,  
Medical and general use

### General Information:

Pocket dosimeters provide an accurate, reliable and immediate method of measuring the integrated dose of radiation received by those exposed to ionising radiation. The dose may be read at any time and in any place, providing a source of light is available.

### Principle:

The dosimeter is an ionisation chamber type using a quartz fibre electroscope as the indicating element. A microscope is used to project the image of the moving quartz fibre element on to a graticule scale. The quartz fibre is mounted on a wire electrode, which in turn is supported by a high quality insulator. When the instrument is charged, positive charges distribute themselves over the wire electrode and quartz fibre causing the fibre to bend away from the electrode. The fibre will take up a position depending on the amount of charge on the system.

When the surrounding air in the ionisation chamber is ionised negative ions will be attracted to the positively charged electrode thereby reducing its charge. The resulting fibre movement will be related directly to the quantity of radiation producing the ionisation. The fibre movement can thus be calibrated directly in roentgen units and the rate of movement of the fibre will be proportional to the roentgens received per unit time.

### Construction:

The microscope, electroscope and ionisation chamber are housed in an outer skin which may be of brass or aluminium. At one end of the tubular case is fixed a charging assembly, and at the other an eye-piece window.

Each dosimeter is provided with protective end cap translucent window so that the cap need not be removed for reading.

Dosimeters meet vibration, drop, salt spray, humidity, water-immersion and temperature tests.


- BE PREPARED, EVERY HOME SHOULD HAVE ONE ●

YOU CAN'T SEE IT  
HEAR IT  
FEEL IT  
BUT YOU CAN DETECT IT

WILL READ X-RAY  
& GAMMA RADIATION
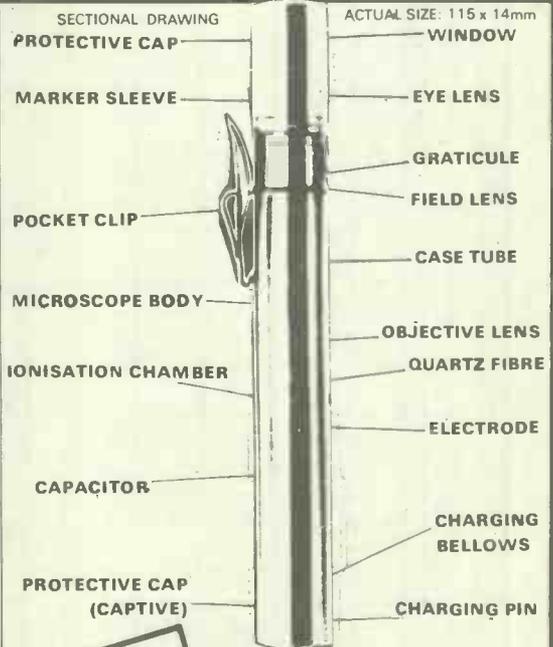
### Features:

- THESE UNITS WILL READ AUTOMATICALLY THE AMOUNT OF RADIATION IN THE AIR
- THIS INSTRUMENT IS ONLY A LITTLE LARGER THAN A FOUNTAIN PEN
- CLIPS ON TO YOUR TOP POCKET
- WEIGHT LESS THAN 3 OZ.
- CONTAINS THREE LENSES
- FULLY CHARGED, TESTED AND GUARANTEED
- BRITISH DESIGN AND MANUFACTURE, RUGGED CONSTRUCTION
- MANUFACTURER'S LIST PRICE OF SIMILAR MODEL IS OVER £25
- BUY NOW WHILST STOCKS AVAILABLE. DELIVERY BY RETURN POST



**SAVE  
£ POUNDS**

**£6.75**  
inc. VAT  
+p/p 50p

Manufacturer's current list price similar model is over £25



**HENRY'S**

Mail Order Division  
404 Edgware Road, London W2, England I.E.D.

TELEX 262284  
REF. 1400




Supplied complete with  
Data and Information on  
radiation and detectors.

All units are checked and tested just  
prior to despatch by first-class mail in  
proper protective packing.

VIEW  
THRU  
LENS



# Nicad Charger

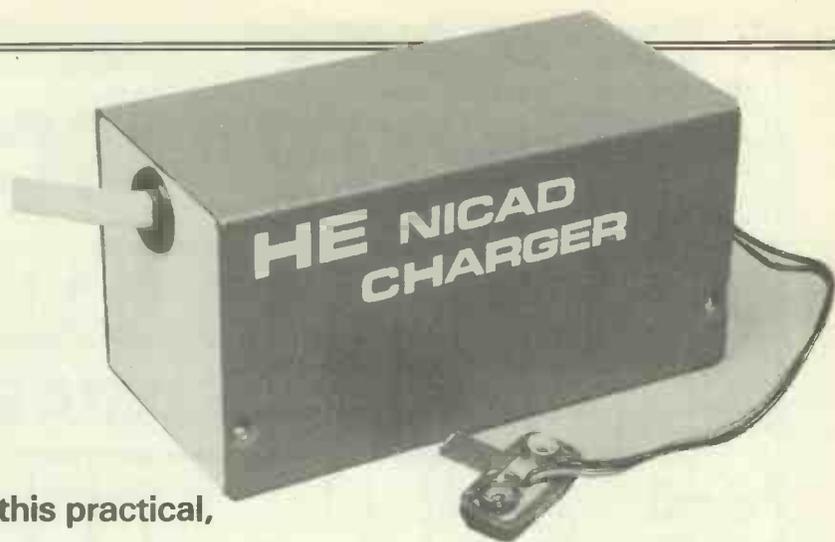

Recharge your vital equipment with this practical, money saving device from HE

ISN'T IT SAD — just when you want to listen to your favourite radio programme on your little tranny, you inevitably find the batteries are defunct. And don't they cost a lot to replace? Well, here is the answer to all your problems — rush out and buy some nicad cells for your battery-powered calculator, transistor radio or cassette player etc. Although they are more expensive initially, you can recharge them again and again on the HE NICAD Charger, thus saving £££££s overall! With this project whenever your batteries run down an overnight charge will revitalise them to their full vigour.

Nicad cells can be recharged many hundreds of times but they need a regulated charge current. Our charger provides this regulation and, in the mode shown in Fig. 2, it will handle up to six AA sized (HP7 type) cells. It can be easily modified to suit other sizes as described below.

Nicads need a constant current charge. For example AA cells need about a 65 mA charge, for a set period (normally 12 hours and so an overnight charge is ideal). For other sizes of cells, different charge currents are required. The table in Fig. 1 shows typical values of current required for various-sized cells. Altering our charger to suit other cells is a cinch, as the output current is set solely by R1.

Its value in ohms is equal to:  
0.65

the required charge rate in amps  
So, for any required charge current, choose the nearest preferred value of resistor to the calculated value.

Output currents of more than 80 mA will require a larger mains transformer because this should have a secondary current rating at least 20 mA more than the charge current.

Higher charge currents might also make it necessary to fit Q1 with a more substantial heatsink.

## Construction

The components are mostly assembled on one of our standard-size (24 holes by 10 strips) 0.1" pitch stripboards as can be seen from the wiring diagram of Fig. 3. Transformer T1 is not mounted on the board, but is bolted to the inside of the case. For reasons of safety the case should be a type having a screw-on lid, and must not be a clip-on type. If a metal case is used it must be connected to the mains earth. It is likely that T1 will have flying leads rather than tags, and a connector block will then be needed to facilitate the connections between the mains lead and T1. The earth lead to the component panel can also be taken via this block. Connector blocks are usually sold in twelve-way strips, and the required three-way

block can be cut from one of these using a sharp knife.

The output of the unit can be taken to a PP3-type battery connector, making quite sure that it is connected with the correct polarity. Plastic battery holders for AA (HP7) size cells are readily available, and these have a PP3-type connector. These holders connect the batteries in series (connected '+' to '-') — the batteries must never be connected in parallel ('-' to '-' and '+' to '+').

Q1 may become quite hot in use and should be fitted with a small heatsink.

SIZE OF CELL	CHARGE CURRENT (FOR 12hr CHARGE)
PP3	100mA
AAA	20mA
AA	65mA
C	250mA
D	500mA

Figure 1. Table of charge currents for various cells.



## Parts List

### RESISTORS (All 1/2 watt 5%)

R1 10R  
R2 680R

### CAPACITOR

C1 100u 25 V electrolytic

### SEMICONDUCTORS


Q1 TIP41A NPN power transistor

Q2 BC109 NPN Transistor  
D1, D2 1N4002
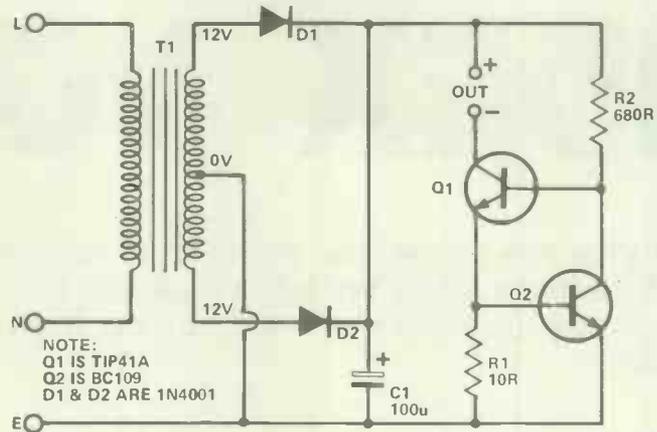
### MISCELLANEOUS

T1 12-0-12 V 100 mA mains transformer

10 x 24 hole 0.1" Veroboard case, battery holder, battery clip, mains lead, connector block, fitted heatsink, etc.



© Copyright MODMAGS Ltd.

Figure 2. Circuit diagram

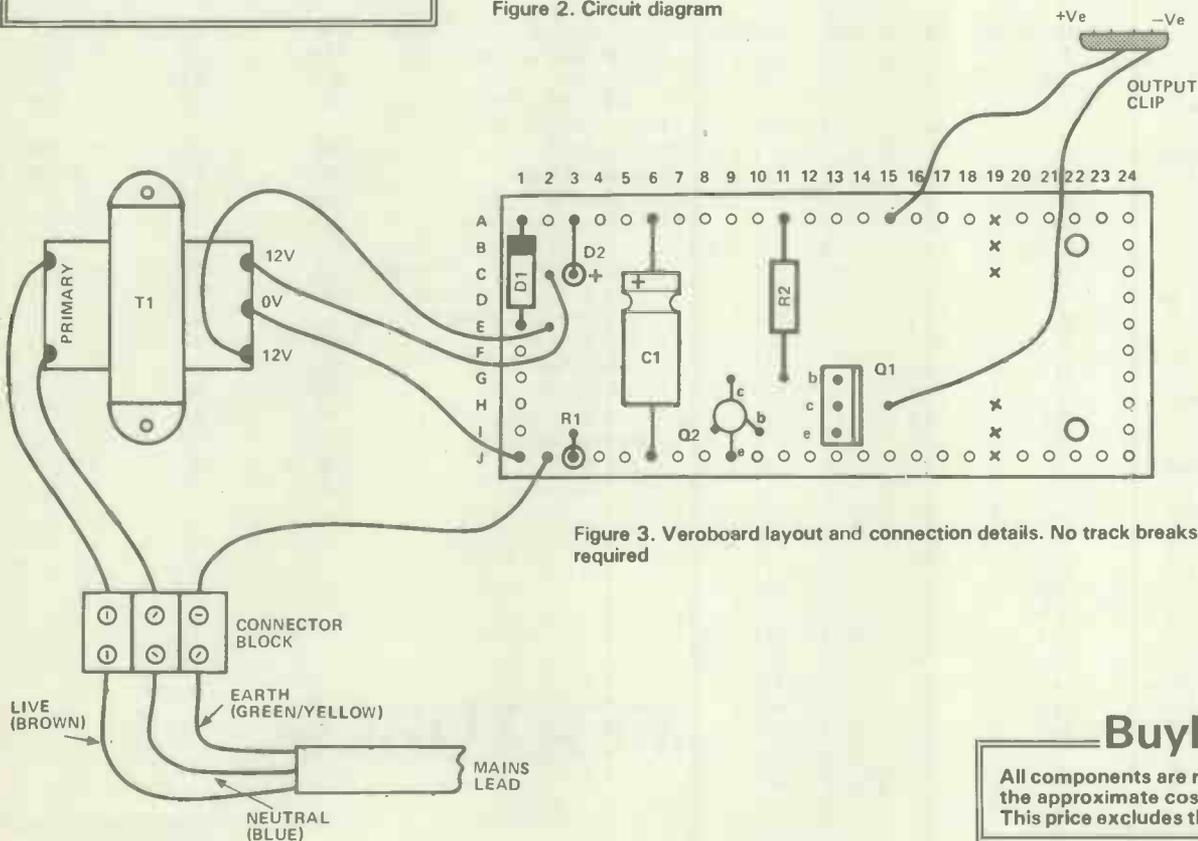


Figure 3. Veroboard layout and connection details. No track breaks are required

## Buylines

All components are readily available and the approximate cost will be around £5. This price excludes the case, of course.

## How It Works

The mains voltage is stepped down to a more suitable potential by transformer T1, with D1, D2, and C1 then full-wave rectifying and smoothing the output of T1 to give a low voltage (about 14 V under load) DC supply. This supply cannot be connected directly across the nicad cells as these have an extremely low internal resistance, and would place virtually a short circuit across the supply. The supply in turn would damage the cells, which should not be charged at a higher current than that recommended by the manufacturer, and would also result in the destruction of the supply circuit!

A current regulator must be included to ensure that the cells are charged correctly, and this is the purpose of Q1, Q2, R1 and R2, which are used in a conventional constant-current generator configuration. Transistor Q1 is biased hard into conduction by R2, and a current therefore flows through R1, Q1, and the cells being charged. The current is limited to a safe level by Q2 which becomes biased into conduction by the potential developed across R1. The results in Q2 tapping off some of the base current for Q1, so that the impedance of Q1 increases.

Therefore, even with a low im-

pedance across the output, such as that of the nicad cells, the output current passed by Q1 is stabilised by Q2 at a safe level, since Q2 can reduce the bias on Q1 to practically zero if necessary. As Q2 is a silicon device it requires a base bias voltage of about 0.65 V to bring it into normal conduction, and so the circuit stabilises with about this potential across R1. From Ohm's Law it can be seen that about 65 mA flows through R1, Q1, and the cells under charge (0.65 V divided by 10R gives 0.065 A, or 65 mA), which is about the correct charge for AA size cells.

# INDEX VOL. 2

Another year has passed, so it's time once again for the annual HE alphabetical Index. Here we have a complete listing of all of the major features, projects and short circuits from Volume 2 of Hobby Electronics.

## PROJECTS

TITLE	MONTH	YEAR	NO	PAGE
2 Watt Amplifier	Jun	80	8	54
18 W + 18 W Stereo Amplifier	Jul	80	9	23
5080 25 Watt Amplifier Module	Mar	80	5	11
5080 Loudspeaker	May	80	7	64
5080 Preamp	May	80	7	28
Audio Power Meter	Dec	80	2	59
Autoprobe	Sep	80	11	37
Battery Charge Indicator	Dec	80	2	41
Battery Eliminator	Nov	80	1	24
Bench PSU	Sep	80	11	63
Chuffer Sound	Jan	81	3	54
Crosshatch Generator	Jan	80	3	31
Development Timer	Sep	80	11	53
Digi-Dice	Jan	80	3	47
Digital Frequency Meter	Apr	80	6	33
Digital Speedometer	Dec	80	2	13
Double Dice	Nov	80	1	65
Egg Timer	Jun	80	8	43
Electronic Ignition	Apr	80	6	11
Equitone	Aug	80	10	21
Fog Horn	Jun	80	8	64
Freezer Alarm	Oct	80	12	40
Gaztec	Aug	80	10	57
General Purpose Amplifier	Jan	81	3	37
Guitar Phaser	Sep	80	11	49
Guitar Preamp	Nov	80	1	35
Hazard Flasher	Jul	80	9	62
Hebot Part 3	Jan	80	3	56
Hobbycom	Apr	80	6	17
Infra-Red Remote Control	Feb	80	4	27
Intruder Alarm	Oct	80	12	59
Jack Lead Tester	Dec	80	2	49
Kitchen Timer	Oct	80	12	13
Light Dimmer	Oct	80	12	33
Metronome	Jun	80	8	32
Microbe Radio Control System	Jun	80	8	11
Micromix	Sep	80	11	19
Micromix	Sep	80	11	19
Miniboard Siren	Mar	80	5	54
Minicock	May	80	7	11
Minisynth	Nov	80	1	13
Minisynth II	Dec	80	2	27
Movement Alarm	Aug	80	10	49
NiCad Battery Charger	Jan	81	3	50
Nobell Doorbell	Oct	80	12	67
Op-Amp Checker	Aug	80	10	62
Party Grenade	Nov	80	1	41
Passionmeter	Feb	80	4	10
Pass The Loop	Aug	80	10	41

Push Button Volume Control	Jul	80	9	37
PSU Module (5080)	Mar	80	5	19
Radio Timer	Aug	80	10	29
Railway Track Cleaner	May	80	7	45
Radio Control Speed Controller	Apr	80	6	49
Reaction Timer	Sep	80	11	25
Rev Counter	Jan	81	3	27
Scalextric Lap Counter	Jan	80	3	9
Short Wave Radlo	Mar	80	5	57
Sound Operated Flash Trigger	Jul	80	9	11
Sound-To-Light Converter	Jan	81	3	11
Temperature Controlled Soldering Iron	Oct	80	12	49
Touch Switch	Sep	80	11	45
Touch Switch	Mar	80	5	44
Train Controller	Dec	80	2	66
Transistor Tester	Nov	80	1	53
Tug O'War	Oct	80	12	24
Win Indicator	Feb	80	4	59

## FEATURES

TITLE	MONTH	YEAR	NO	PAGE
Catalogue Survey	Jun	80	8	58
CMOS Special	Jan	80	3	23
Electronic Espionage	Jul	80	9	28
Electronics in Photography	Jul	80	9	15
Electronics On Wheels	Mar	80	5	38
Home Electronics	Oct	80	12	44
Intellivision TV Game	Sep	80	11	29
In Car Entertainment	Aug	80	10	11
KEZY Does It	Feb	80	4	38
Microprocessors Are Easy	Aug	80	10	53
Miniature TV Survey	Jan	80	3	15
Narrow Bandwidth Television Pt 1	Apr	80	6	40
Narrow Bandwidth Television Pt 2	May	80	7	54
PETting It Together	Mar	80	5	24
Piezo Electricity	Jul	80	9	56
Power To The People	Feb	80	4	51

Radio Control Model Survey	May	80	7	20
RF Breakthrough	Jun	80	8	37
Solar Cells	Apr	80	6	27
Spacelab	Jan	80	3	38
Story Behind Stereo	Nov	80	1	18
Teletext Explained	Sep	80	11	12
Ten Of The Best	Jan	81	3	18
View Into Video Discs	Dec	80	2	18

## GENERAL FEATURES

TITLE	MONTH	YEAR	NO	PAGE
Breaker One Four	Jan	80	3	61
"	Feb	80	4	63
"	Mar	80	5	63
"	Apr	80	6	61
"	May	80	7	35
"	Jun	80	8	23
"	Jul	80	9	49
"	Aug	80	10	65
"	Sep	80	11	67
"	Oct	80	12	71
"	Nov	80	1	71
"	Dec	80	2	71
"	Jan	81	3	61
Building Site	Aug	80	10	26
"	Sep	80	11	57
"	Oct	80	12	30
"	Nov	80	1	46
"	Dec	80	2	63
"	Jan	81	3	39
Chit-Chat	Mar	80	5	49
"	Apr	80	6	55
"	Jun	80	8	49
Clever Dick	Jan	80	3	21
"	Feb	80	4	14
"	Mar	80	5	17
"	Apr	80	6	15
"	May	80	7	17
"	Jun	80	8	19
"	Jul	80	9	35
"	Aug	80	10	46
"	Sep	80	11	60
"	Oct	80	12	63
"	Nov	80	1	27
"	Dec	80	2	25
"	Jan	81	3	16
Into Linear ICs Part 7	Jan	80	3	65
Into Electronics Construction 1	Feb	80	4	65
" 2	Mar	80	5	67
" 3	Apr	80	6	67
" 4	May	80	7	67
" 5	Jun	80	8	67
" 6	Jul	80	9	67
Into Digital Electronics Pt 1	Sep	80	11	30
" Part 2	Oct	80	12	17
" " 3	Nov	80	1	29

" " 4	Dec	80	2	35
" " 5	Jan	81	3	45
Kit Review : R/C Servo	Feb	80	4	45
" : Tuner/Amplifier	Mar	80	5	29
" : Touch Dimmer	Jul	80	9	46
" : VU Meter	Jul	80	9	47
O Level Q & A	Sep	80	11	22
"	Oct	80	12	52
"	Nov	80	1	49
"	Dec	80	2	45
"	Jan	81	3	32
Talking Design	Sep	80	11	41
"	Oct	80	12	55
"	Nov	80	1	59
"	Dec	80	2	53
What's In A Name	Aug	80	10	35
"	Sep	80	11	35
"	Oct	80	12	37
"	Nov	80	1	39
"	Dec	80	2	33
"	Jan	81	3	25

## SHORT CIRCUITS

TITLE	MONTH	YEAR	NO	PAGE
Audio Limiter	Jan	80	3	18
Automatic Fader	Feb	80	4	20
Car Cassette Power Supply	Jan	80	3	44
Cassette-Radio Booster	Jun	80	8	72
Christmas Tree Lights Flasher	Feb	80	4	21
Class A Amplifier	Apr	80	6	23
Crystal Calibrator	Jun	80	8	56
Doorbuzzer	Feb	80	4	17
General Purpose Amplifier	Feb	80	4	18
Infra-Red Intruder Alarm	Jul	80	9	20
LED VU Meter	Apr	80	6	48
Metronome	Feb	80	4	18
Morse Practice Oscillator	Feb	80	4	17
Noise Gate	Jan	80	3	71
One Armed Bandit	Mar	80	5	72
Radio 4 Tuner	Jun	80	8	36
Simple MW Radio	Feb	80	4	21
Simple SW Radio	Feb	80	4	16
Sound Operated Switch	Mar	80	5	33
Speech Processor	Jul	80	9	26
Supply Splitter	Apr	80	6	48
Table Lamp	Jul	80	9	42
Thermostat	Mar	80	5	52
Transistor Checker	Jun	80	8	62
Transistor Tester	Mar	80	5	33
Ultrasonic Receiver	Feb	80	4	19
Ultrasonic Transmitter	Feb	80	4	19
Waa-Waa Unit	Jan	80	3	44
Water Alarm	Feb	80	4	20
Voice Operated Fader	Jul	80	9	45
ZN1034E Timer	Mar	80	5	23
10 to 30 MHz Preselector	Apr	80	6	23

# Chuffer



## Add realistic sound effects to your world of trains with this circuit. First of a series of 'funny noises' for model railway enthusiasts

OVER THE NEXT couple of months HE intends to devote project space to the model railwayites — that odd breed of beings who choose to sit at home in the attic or spare bedroom, surrounded by miles of track and scaled-down trains, stations and scenery. And what do they hear as they sit there? Certainly nothing resembling *real* train sounds.

Now, this sub-world can be made more complete by building some of our model train sound effects starting with the HE Chuffer, a device designed to simulate the sound of a steam train. A preamplified output means that the device can be plugged into an external amplifier (this month's Bench Amplifier is ideal) and preset controls allow it to be used with a wide range of train systems, to give the required sound. The project is purpose-designed to complement the HE Train Controller of last month's issue although it will also perform well with standard (variable resistor type) controllers.

The two IC and three transistor circuit picks up and measures the voltage applied to the track by the controller and converts this into a varied rate of 'chuffs'. The higher the

voltage, the faster the chuff rate. When the train is stationary only a faint background or 'parking' hiss is heard, but as soon as the train pulls away, the chuffs commence — slowly at first, until full power is applied, when chuffs are fast and furious as the train hurtles round the track.

### Construction

The circuit is built up on a 16-strip by 26-hole piece of Veroboard. Although this method of construction is very convenient for the hobbyist you must remember that certain procedures must be followed if the project is to be fault-free. The copper strips or track must be broken in the correct places as shown in the underside diagram of the board in Fig. 3. This can be accomplished using a hand-held  $\frac{1}{8}$ " drill bit (if you haven't got the proper tool for the job) but in either case make sure that no loose bits of copper swarf bridge nearby tracks.

Next, insert and solder the wire links into the board as in the overlay diagram. Resistors and capacitors can then be soldered in. Polarised

capacitors need to be inserted the right way round — check them carefully before soldering! IC sockets should be inserted and soldered now.

Finally, all semiconductors should be put in, but like polarised capacitors they should be checked for correct insertion before soldering.

We have included no details of casing the project this month as it is our intention to house it and forthcoming model train sound effects in one case, later.


### Setting Up

First set the three preset resistors at mid-position. Connect the circuit to an amplifier and a battery or 9 VDC power supply. Switch on. By adjusting RV3, a white noise signal of up to 100 mV should be available to the amplifier. The setting of RV3 will be best found by experience and personal choice but as a rough guideline only, adjust it till just a faint hiss is heard from the amp.

Now, connect the input of the circuit to your model train track and set a train running around the track at medium speed. Readjusting RV3 should now give a variable output of white noise from sharp clonking pulses to a continuous hiss — choose the best overall sound.
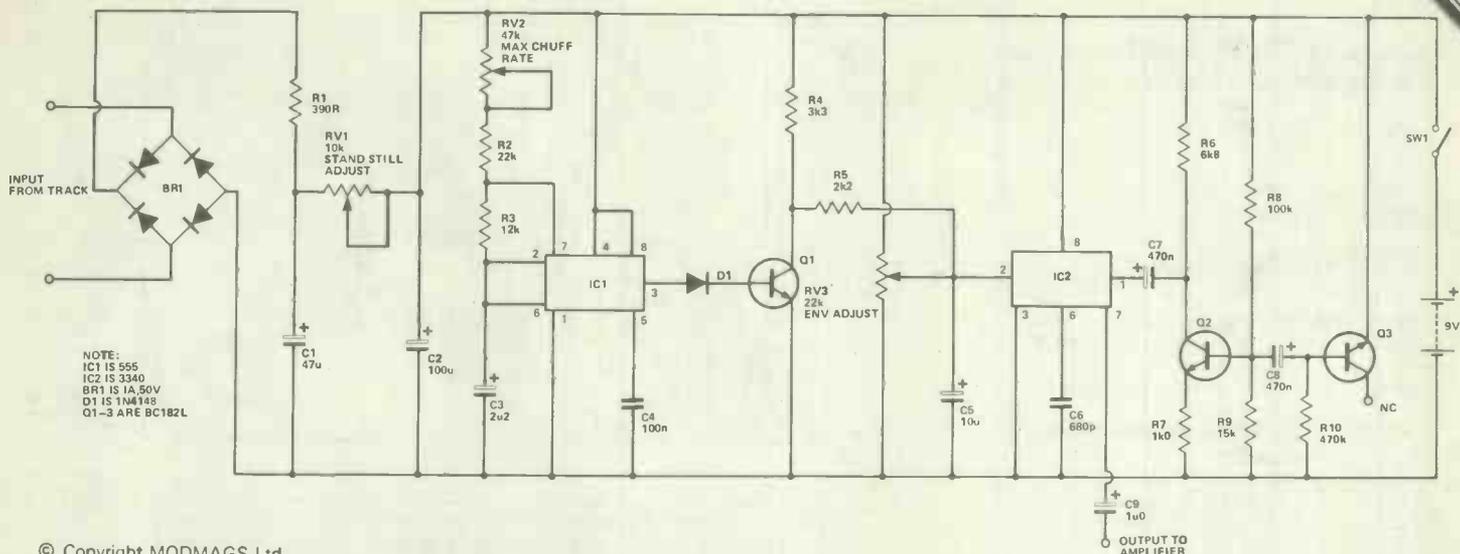
### Buylines

All components are common types and should cause no difficulty. The approximate cost of parts will be around £8.



© Copyright MODMAGS Ltd.

Figure 1. Circuit diagram of the HE Chuffer

## How It Works


The main sound generated by a (full-sized) steam train is a more or less equal mixture of all frequencies — in electronics this sort of sound is known as white noise, so called because of this mixture of *all* audible frequencies (analogous to white light). One way of electronically producing white noise is with a transistor connected as Q3 in the main circuit diagram in Fig. 1. You will see that its collector is open-circuit and its emitter is, unusually, taken positive relative to its base. Connected so, Q3 acts as a zener diode, maintaining a con-

stant voltage across itself. A white noise signal occurs at its base which is amplified by Q3 and fed to IC2.

The 'chuff-chuff' sound required of the circuit is formed by adding an envelope to the white noise. Figure 2 shows this in diagrammatical form. As can be seen, the enveloped white noise means that the noise increases from zero, maintains this maximum level for a while, then decreases back to zero — forming a resounding 'chuff' sound. By repeating this envelope every so often


as the train goes round the track, the required sound is obtained.

The rest of the circuit is designed to trigger the envelope at a rate which corresponds to the speed of the train; ie, at full speed the chuffs are rapid and at standstill, only a background hiss is heard to simulate a stationary steam engine. To do this the voltage present on the railway track is rectified and smoothed by BR1, R1, RV1, C1 and C2, to produce a DC voltage which increases and decreases with the speed of the train. This changing voltage is used to power an astable oscillator (IC1—a 555). As its power supply increases and decreases so does its oscillation rate. Preset RV2 gives overall control of oscillation rate (the chuff rate). Transistor Q1 buffers and inverts this pulse which is then used to trigger the envelope described above.

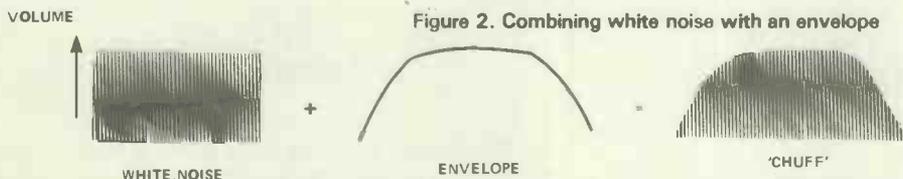

Using the train controller, stop the train. Adjustment of RV1 should provide a 'turn-off point' when no modulated noise is available (ie when the train is stationary — no 'chuffs' are heard). Fine readjustment of RV3 will now give a background gentle hiss at this stage, simulating a stationary steam train.

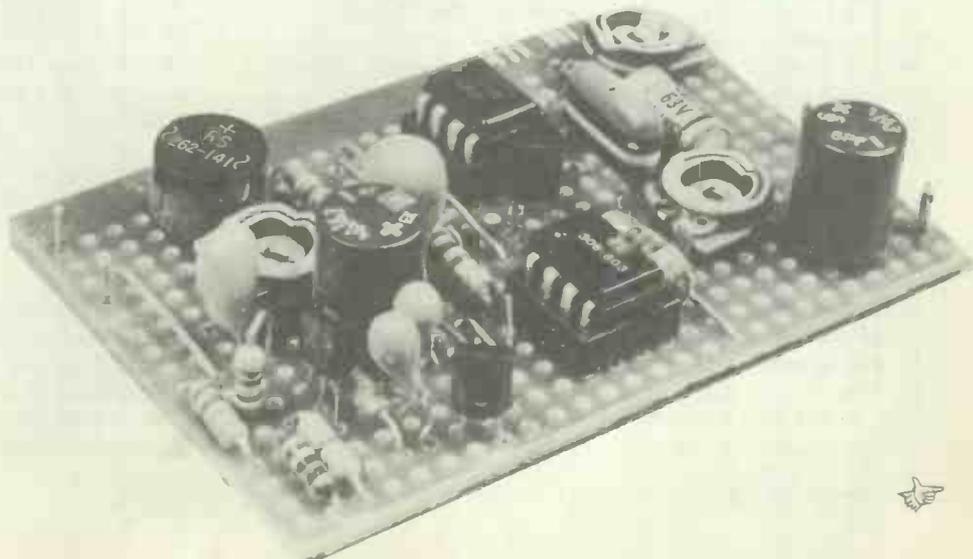Finally, run the train at maximum speed and adjust RV2 until the required maximum 'chuff rate' is found. It may be necessary to retrim the presets until the best combination of background hiss, stationary turn-off and maximum chuff rate is obtained.



## Parts List

### RESISTORS (All 1/4 W, 5%)

R1	390R
R2	22k
R3	12k
R4	3k3
R5	2k2
R6	6k8
R7	1k
R8	100k
R9	15k
R10	470k

### POTENTIOMETERS

RV1	10k miniature horizontal preset
RV2	47k miniature horizontal preset
RV3	22k miniature horizontal preset

### CAPACITORS

C1	47u 10 V, tantalum
C2	100u 6V3, tantalum
C3	2u2 16 V, electrolytic
C4	100n polyester
C5	10u 16 V, printed circuit mounting electrolytic
C6	680p polystyrene
C7,8	470n 35 V, tantalum
C9	1u 16 V, printed circuit mounting electrolytic

### SEMICONDUCTORS

IC1	555 timer
IC2	MC3340 voltage controlled attenuator
BR1	1 A, 50 V bridge rectifier
Q1,2,3	BC182L NPN transistor
D1	1N4148 diode

### MISCELLANEOUS

SW1	single-pole, single-throw toggle switch
16 strip x 26 hole Veroboard	
battery clip	
IC sockets	

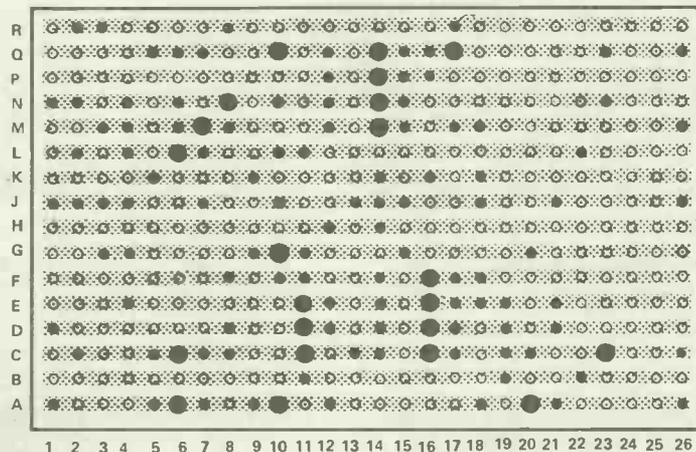
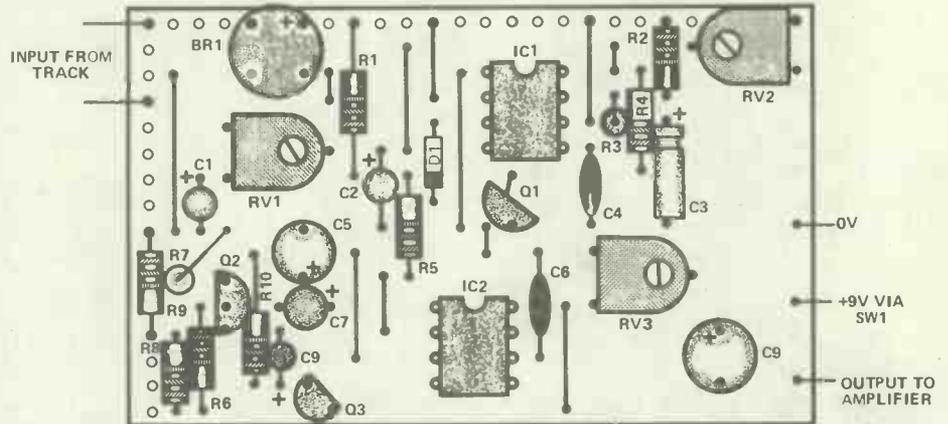


Figure 3. Veroboard layout and underside view, showing track breaks

HE

# electronics today

INTERNATIONAL

**NEXT  
MONTH**

Look out for the February issue  
on sale January 2nd

## Digital Designers' Circuit Supplement

In only 10 years digital circuits have shifted from simple single-function chips to microprocessors and horrific dedicated multifunctional devices — creating increasing problems for the digital designer. Tim Orr's Digital Designers' Circuit Supplement helps you make sense of this digital nightmare.

## Roulette

At last: a hand-held battery-powered project that brings you the thrills of the casino. ETI's roulette has a circle of LEDs and gives you the choice of biased (in favour of the house) or unbiased (no house) options. It even has sound effects.

## IR Beam Alarm

ETI's IR Beam Alarm features a dual beam IR link. The two beams, a few inches apart, must be broken simultaneously to activate the alarm. So it won't trigger falsely when a fly lands on the transmitter or receiver. The link has a 10 m range and could form the basis of a house alarm system.

## SPL Meter

This is a first for a UK electronics magazine: an accurate, calibrated Sound Pressure Level Meter based on a special-purpose, but modestly-priced precision microphone insert. The SPL can be used to check absolute levels of sound level or loudness: use it to set up the graphic equaliser in your hi-fi system!

Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.



**ELECTROVALUE**  
CATALOGUE '81

68  
LARGE  
PAGES

POTENTIOMETERS • SEMI-CONDUCTORS • SWITCHES • CONNECTORS

The larger Catalogue that means  
FREE POSTAGE IN U.K.  
ADDITIONAL DISCOUNTS  
KEEN PRICES  
GUARANTEED SATISFACTION  
GOOD STOCKS  
We pay postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety  
• Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

**ELECTROVALUE**

**FREE FOR THE ASKING**

ELECTROVALUE LTD. (Dept. ME2), 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.  
Telephone: (STD 0784) (London 87) 33603. Telex: 264475

**ETCH RESIST TRANSFER KIT SIZE 1:1**  
Complete kit 13 sheets 6in. x 4 1/2in. £3, with all symbols for direct application to P.C. board. Individual sheets 30p each. (1) Mixed Symbols (2) Lines 0.05 (3) Pads (4) Fish Plates and Connectors (5) 4 Leads and 3 Lead and Pads (6) DILS (7) BENDS 90° and 130° (8) 8-10-12 T.O.S. Cans (9) Edge Connectors 0.15 (10) Edge Connectors 0.1 (11) Lines 0.02 (12) Bends 0.02 (13) Quad in Line.

**MAIL ORDER PC BOARD**  
2" x 8" 12 pieces for ..... £1.00 post 50p  
3" x 8" 7 pieces for ..... £1.00 post 50p  
4" x 8" 6 pieces for ..... £1.00 post 50p  
6" x 8" 4 pieces for ..... £1.00 post 50p  
8" x 8" 3 pieces for ..... £1.00 post 50p  
Some double-sided, same price also 3/32" ss

**PLAIN PAXOLIN INSULATION BOARD**  
1/32" 4" x 8" 10 pieces for ..... £1.00 post 50p  
1/16" 4" x 8" 6 pieces for ..... £1.00 post 50p

**FRONT AND REAR PANEL TRANSFER SIGNS**  
All standard symbols and wording. Over 250 symbols, signs and words. Also available in reverse for perspex, etc.. Choice of colours, red, blue, black or white. Size of sheet 12" x 9". Price £1.20.

**GRAPHIC TRANSFERS WITH SPACE ACCESSORIES**  
Available also in reverse lettering, colours red, Blue, black or white. Each sheet 12" x 9" contains capitals, lower case and numerals 1/8" kit or 1/4" kit, £1.20 complete. State size.

All orders despatched promptly. All post paid

Shop and Trade enquiries welcome. Special Transfers made to order  
E. R. NICHOLLS  
**P.C.B. TRANSFERS**  
DEPT. ET12, 46 LOWFIELD ROAD  
STOCKPORT, CHESHIRE. 061-480 2179

**24HR. CLOCK/APP. TIMER KIT**  
Switches any appliance up to 1KW on and off at preset times once per day Kit contains AY 5 1230 IC, 0.5" LED display mains supply display drivers switches LED's triac PCBs & full instructions.  
CT1000KB with white box (56.131 x 71mm) £17.40  
CT1000K Basic Kit £14.90 Ready Built £22.80

**DVM THERMOMETER KIT**  
Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). £19.50

**MINI KITS**  
These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.  
**MK1 TEMPERATURE CONTROLLER / THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater 1 KW £4  
**MK2 SOLID STATE RELAY**  
Ideal for switching motors lights heaters etc from logic Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range £2.80  
**MK3 BAR/DOT DISPLAY**  
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply £4.75  
**MK4 PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the TDA1024 Zero voltage switch this kit may be wired to form a burst fire power controller or a proportional temperature controller enabling the temperature of an enclosure to be maintained to within 0.5°C 3KW £5.85  
**MK5 MAINS TIMER**  
Based on the ZN1034E Timer IC this kit will switch a mains load on or off for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW £4.50

**DISCO LIGHTING KITS**  
Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.  
**DL1000K**. This kit features a bi-direction sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. £14.80  
**DL21000K**. A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. £8.00  
Optional Opto Input, DLA1 £1.80

**INTEGRATED CIRCUITS**  
555 Timer 21p  
741 Op Amp 19p  
AY-5-1234 Clock £2.60  
AY-3-1270 Thermometer £8.20  
ICL7106 DVM (LCD drive) £7.00  
LM377 Dual 2 W Amp £1.45  
LM3795 Dual 6W Amp £3.50  
LM380 2W Audio Amp £1.60  
LM382 Dual/low noise Preamp £1.00  
LM386 250mW low voltage Amp 75p  
LM1830 Fluid Level Detector £1.50  
LM2907 I-V Converter (8 pin) £1.40  
LM2917 I-V Converter (14 pin) £1.60  
LM3909 LED Flasher/Oscillator 60p  
LM3911 Thermometer £1.20  
LM3914 Dot/Bar Driver £2.10  
MM74C911 4 digit display controller £6.50  
MM74C915 7 segment-BCD converter 96p  
MM74C915 4 digit ctr with 7 sep o-p £4.50  
S566B Touchdimmer £2.50  
S9283 Touchswitch 16-way £4.85  
SN76477 Complex Sound Generator £2.82  
TB800 5W Audio Amp 68p  
TB810AS 7W Audio Amp £1.00  
TDA1024 Zero Voltage Switch £1.20  
TDA2020 20W Audio Amp £2.85  
ZN1034E Timer £1.80  
All ICs supplied with data sheets.  
Data Sheets only 10p each device.

**TRIACS**  
400V Plastic Case (Texas)  
3A 49p 16A 95p  
8A 58p  
12A 85p  
6A with trigger 80p  
8A isolated tab 65p  
Diac 18p

**AND NOW A DIMMER THAT MAKES TOUCH DIMMERS OBSOLETE**

Two years ago TK Electronics launched a touchdimmer kit the TD300K which made knob controlled dimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW TK have designed a touch dimmer kit with an Infra-Red Remote control enabling you to switch and control the brightness of your lights from the comfort of your armchair etc. (as well as manually by touching the frontplate or by using the TDE/K extension kit). As with all our kits these come complete with all components including RFI suppression frontplate, a neon to help you find the switch in the dark and a neat box for the transmitter. The plastic frontplate has no metal pads to touch ensuring complete safety and enabling the plate to be covered with a decorative finish to blend with your room decor.

We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.

In two years time everyone will be selling remote control dimmers but you can have your TDR300K kit NOW for only £14.30 for the dimmer unit and £4.20 for the transmitter.

For the more athletic of you the TD300K is still available at £6.50 and the TDE/K at £2.00. DON'T FORGET to add 40p P&P and 15% VAT to your total purchase.

**REMOTE CONTROL KITS**

**MK6**—Simple Infra Red Transmitter. A pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. £4.20  
**MK7**—Infra Red Receiver—Single channel, range approximately 20ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, can be modified for use with 5-15V dc supplies and transistor or relay outputs. £9.00  
\*SPECIAL PRICE\* MK6 and MK7 together. Order as RCS00K £12.50  
**MK8**—Coded Infra Red Transmitter—Based on the SL490, the kit includes two IR LEDs, measures only 6x2x1.3 cms. Requires a 9V (PP3) battery. £5.90  
**MK9**—4-way Keyboard for use with the MK8 kit, to make a 4-channel remote control transmitter. £1.90  
**MK10**—16-way Keyboard for use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML928 receiver (MK12 kit). £5.40  
**MK12**—16 Channel IR Receiver—for use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML928 or ML928 is specified. Includes its own mains supply. £11.95  
Size: 9x6x2 cms, excluding transformer.

**ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 40p P&P MAIL ORDER — CALLERS WELCOME BY APPOINTMENT. SEND SAE WITH ALL ENQUIRIES.**

**TK Electronics**  
(H.E.), 11 Boston Road, London, W7 3SJ  
Tel: 01-579 9794

# CORDLESS PHONE SPECIAL OFFER

Imagine the luxury of having use of a phone in every room. This is now possible with this month's very special offer from Modmags. We are now in a position to offer to you, at a never-to-be-repeated price the fabulous Freedom Phone FF1 500. This brilliantly engineered little device consists of a base station transponder and a cordless handset. Facilities include full duplex two-way transmission, incoming and outgoing calling, push-button dialling with memory and re-chargeable nickel cadmium batteries for low operating costs.

The range of the Freedom Phone is in excess of 200 yards, enough for even the largest back-garden: it will enable you to be in telephone contact at all times. Never again will you miss that all-important business call and the built-in paging facility will allow anyone to get in touch with you, no matter where you are within the transmission area.

Each unit comes complete with the base station transponder/charger plus secondary charger, full fitting instruction (only two wires to the existing phone line), re-chargeable batteries and the personal handset. Price for each unit (including post, package, etc) is just £125.00.



**SEND YOUR CHEQUE/POSTAL ORDER TO:  
PHONE OFFER, Modmags Ltd., 145 Charing  
Cross Road, London WC2H 0EE.**

Please note that these devices are at present not licenceable for use in the UK.

I enclose a cheque/postal order for £ .....

for ..... Freedom Phone/s

Name .....


Address .....

.....

.....


**PLEASE MENTION  
HOBBY ELECTRONICS  
WHEN REPLYING  
TO ADVERTS**

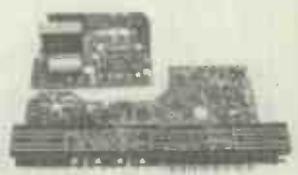**GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS.** Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc, AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within  $\pm 3$ dB. **Tape Sensitivity:** Output — typically 150 mV. Input — 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio: FM (VHF), 87.5MHz — 108MHz. Long wave, 145kHz — 108kHz. Medium wave,**



520kHz — 1620kHz. Short wave. 5.8MHz — 16MHz. **Size:** Tuner — 2 3/4in. x 1 1/2in. x 7 1/2in. approx. Power amplifier — 2in. x 7 1/2in. x 4 1/2in. approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £21.50 plus £2.50 postage and packing.**

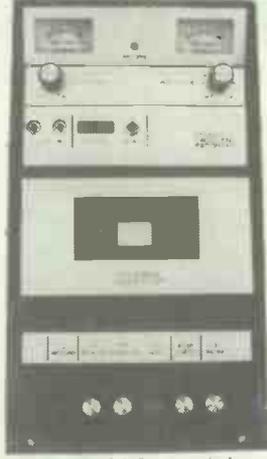**STEREO CASSETTE TAPE DECK ASSEMBLY.** Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. For horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. **Features:** Pause control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual level controls, twin mic, input sockets, AC erase system, LED record indicator. (Separate power amplifier required). **Input Sensitivity:** 6 mV (with level control set at max.). **Input Impedance:** 47kOhms. **Output Level:** To both left and right-hand channels 150 mV. **Output Impedance:** < 10K. **Signal to noise ratio:** 45 dB nominal. **Power Supply Requirements:** 12V AC at 300mA. **Connections:** All connections to the unit are via a wander lead terminated with nine-pin plug (socket provided). **Dimensions:** Top panel — 11 1/2in. x 6 1/2in. Mechanism fits through a cut out 5 1/4in. x 10 1/2in. Clearance required under top panel 2 1/4in. Supplied complete with circuit diagram etc. **Price £30.50 plus £2.50 postage and packing. Suitable 12V mains transformer £3.00.**



**B.K. ELECTRONICS**  
37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY  
BARCLAYCARD  
VISA  
\* SAE for current lists \* Official orders welcome \* All prices include VAT \* Mail order only \* All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please telephone 0702 527572.  
We welcome Access

**OHIO SCIENTIFIC COMPUTERS** New series 2 Challenger C1P p.o.a. New Series 2 disc version Challenger C1PMF p.o.a. New Superboard 3 £159 + 15% VAT post free, with free power supply and modulator kit. Kits for use with old Superboard 2 (Add 15% VAT). Guard band kit £8. 4K extra ram £17.50. Display expansion kit approx 30 lines x 54 characters £20. Case £26. Colour conversion board kit £45 or built £65. CEGMON improved monitor rom £29.50. Cassette recorder £18.  
**SINCLAIR PRODUCTS SC110** 10 MHz Scope £145. PFM £51.95  
**TV GAMES, AY-3-8600 + kit** £12.98. Stunt cycle chip + kit £20.95.  
**IC AUDIO AMPS** with pcb. JC12 6W £2.50. JC20 10W £3.54.  
**BATTERY ELIMINATORS.** 3-way type 6/7 1/2/9V 300ma £3.50. 100ma radio type with press studs 9v £4.77, 9+9V £5.99. Car converter 12v input, output 4 1/2/6/7 1/2/9v 800ma £3.04.  
**BATTERY ELIMINATOR KITS** 100ma radio types with press studs 9v £1.84, 9+9v £2.30. Stabilized 8-way types 3/4 1/2/6/7 1/2/9/12/15/18v 100ma £3.12, 1Amp £8.10. Stabilized power kits 2.18v 100ma £3.12, 1.30v 1A £8.30, 1.30v 2A £14.82, 12v car converter 6/7 1/2/9v 1A £1.62.  
**T-DEC AND CSC BREADBOARDS** s-dec £3.79, t-dec £4.59, exp4b £2.64, exp300 £6.61.  
**TRANSFORMERS** 6-0-6V 100ma 96p, 1 1/2a £3.32, 9-0-9v 75ma 96p, 1a £3.08, 2a £4.93.

12-0-12v 100ma £1.20, 1a £3.70.  
**SHARP COMPUTERS**



Add 15% VAT to these prices. Sharp M280K Computer with Basic tape and a free tape of approx 50 programs: — 20K version £438, 48K version £486. M280 I/O £83. M280P3 £499. M280FD £772. PC1211 I/O £83. CE121 £12. PRINTERS 800MST £359. Oki Microline 80 £349. Free interface and word processor for Superboard 2 included. Add 15% VAT.

**SWANLEY ELECTRONICS**  
Dept HE, 32 Goldsai Rd, Swanley, Kent  
Post 40p extra. Prices include VAT unless stated  
Official and overseas orders welcome. Lists 27p post free. Telephone Swanley 64851.

# It's easy to complain about advertisements.

Every week, millions of advertisements appear in the press, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice and are legal, decent, honest and truthful.

But if you find one that, in your opinion, is wrong in some way, please write to us at the address below.

We'd like you to help us keep advertising up to standard.



**The Advertising Standards Authority.**  
**If an advertisement is wrong, we're here to put it right.**

A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.

# NEW from Modmags


CITIZENS BAND is the new monthly magazine for all CB enthusiasts. Every month we publish all of the latest news, views and information. Our team of technical reviewers bring you test reports of all of the latest equipment. Our project team get together to design simple and cheap to build projects that are of interest to both CBers and radio enthusiasts alike. And for people with something to say our regular monthly forum 'CB Soapbox' gives anyone a chance to publicly air their views. For those still unsure of the working of CB we have a new monthly feature called 'Inside CB' in which we explain in a simple down-to-earth way how CB works.

CITIZENS BAND will be on sale on the third Friday of each month price just 50 pence. If YOU are interested in CB then you just can't afford to miss CITIZENS BAND'

GADGETS & GAMES is the answer to all of your problems. Inside this Special edition from Hobby Electronics we have reviewed over 100 of the best electronic Gadgets and Games on the market. From the simplest hand-held LED game to the ultra sophisticated video games right up to the most powerful chess computers, they're all here.

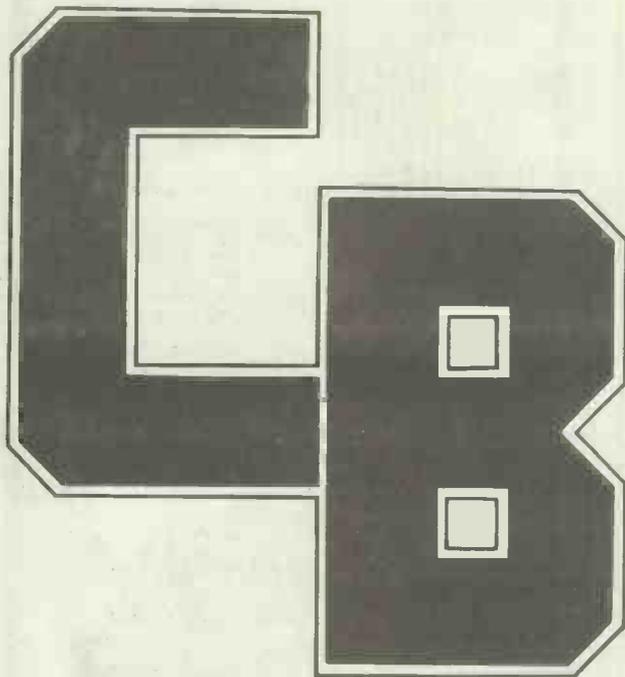In the Gadgets section we have put together a selection of the most fascinating, innovative and revolutionary gadgets, from the smallest television set in the world to the world's first talking language translator. As a special bonus we have also compiled a list of hundreds of software games that can be played on your home computer. All this for just 85 pence. In your local Newsagent NOW.





# Breaker One Four

---

The publishers of HOBBY ELECTRONICS would like to point out that it is at present a contravention of the Wireless Telegraphy Act of 1949 and 1968 to use, manufacture, install or import CB transmitting equipment. It is not the intention of Modmags Ltd to incite, encourage or condone the use of such equipment.

---

With issue number one of **CITIZENS BAND** on the bookstalls and the **Breadboard** show underway it's been a very busy month. Rick Maybury has the latest news

THIS HAS been the busiest month we can remember for a long time. With the first edition of Citizens Band now on sale and number two just about going to press we've hardly had time to breathe.

The Government Green Paper has just about done its stuff: closing date for replies was a couple of weeks ago, and it now remains for the Home Office to make some kind of recommendation about CB in this country. Whatever it decides will make absolutely no difference to the present situation, because we now reckon there are some 500,000 rigs in the country at the moment and in our opinion that means *we have CB*. The fact that it is not a legal system is neither here nor there. It is working and seen to be working: we are hearing more and more reports of channel 9 being used for emergency calls and these being acted upon by the Police and Ambulance services. To our rather uncertain knowledge at least three lives have been saved in the past month by the quick actions of CBers. At least one Police force has unofficially admitted that CB has been a help to them on several occasions. The 24-hour monitoring service in London and a couple of other large cities more than justifies the existence of CB.

What happens now will largely depend upon how much notice the Home Office takes of public opinion. Most CBers will agree that 27 MHz is at best a compromise. It is a noisy and to an extent unreliable waveband. We're sure that most CBers are law abiding citizens and would welcome a legal waveband that embodied all of the advantages of 27 MHz without the attendant problems of noise and interference. We could have it tomorrow and it wouldn't cost any more to buy a rig than it does to obtain a 27 MHz rig on the black market. We need a frequency *now*. Time and time again it has been proven that 928 MHz is totally unsuitable.

We have proved that the VHF band on 41 to 49 MHz would be suitable for such a service. Industry has agreed that the equipment could be manufactured in this country with the consequent improvement in the UK unemployment situation. So why are we waiting? A new series of demonstrations will be starting by the time you read this. You **MUST** make your feelings known. We know that most of these demos will be arguing for 27 MHz. That's OK but we must admit to ourselves that this cannot really be the final answer. Push for 27 MHz by all means but let the Home Office know that you want a quality system, a system that will give this country a chance to become a world leader in personal communications. OK, enough table-thumping for one month, back to the news scene to see what's been happening.

## Mass Eyeball

Cast your minds back a couple of months to the November edition of BOF. You may remember we mentioned the Midlands Radio Fare and Mass Eyeball which was held on the 9th of November. It turned out to be an enormous success, so much so in fact that already the organisers are planning three more functions in the next five months. They are:

Sunday, January 18th 1981 at the Festival Inn, Trowell, Notts. (Same venue as first Mass Eyeball)

Sunday March 8th 1981 at the Lincolnshire Exhibition Centre, Lincoln.

Easter Sunday, April 19th 1981 at the Festival Inn, Trowell, Notts.

If you would like further details of these events then write to TVC Ltd., Station Road, Long Eaton, Nottingham or phone Long Eaton 62247.



**Multitesters 100,000 opv**

AC volts:- 0 - 5 - 10 - 250 - 1000  
 DC volts:- 0 - 05 - 25 - 10 - 50 - 250 - 1000  
 DC current:- 0 - 10ua - 25ua - 500ua - 0 - 5 ma - 50 ma  
 - 500 ma - 10 amp

AC current:- 10 amp  
 Resistance:- 0 - 20 ohms - 200 ohms - 5 K ohms - 200 K ohms - 50 K ohms - 200 K ohms - 5 meg ohms - 50 meg ohms

As a transistor tester

HFE:- 0 - 5 (NPN) - PNP  
 ICO:- 0 - 5 ua (NPN) - PNP  
 Dims:- 178 x 140 x 70 mm

Please add 30p P.P. per unit order as MT 20

**Multitester 1,000 opv**

AC volts:- 0 - 5 - 150 - 500 - 1000  
 DC volts:- 0 - 15 - 150 - 500 - 1000  
 DC current:- 0 - 1 ma - 150 ma  
 Resistance:- 0 - 25 K ohms - 100 K ohms  
 Dims:- 90 x 61 x 30 mm

Please add 30p P.P. per unit order as MT

**Multitester 20,000 opv**

AC volts:- 0 - 10 - 50 - 100 - 250 - 500 - 1000  
 DC volts:- 0 - 0.5 - 5 - 25 - 125 - 250 - 500 - 1000  
 DC current:- 0 - 50 ma - 0.5 ma - 250 ma  
 Resistance:- 0 - 3 K ohms - 300 K ohms - 3 meg ohms  
 Deibels:- -20 to +63 db  
 Dims:- 127 x 90 x 32 mm

Please add 30p P.P. per unit order as MT 7

**Headphones**

High velocity mylar diaphragms. Coiled lead. Finished in a combination of bright aluminium.

Impedence:- 8 ohms  
 Frequency response:- 15 - 22000 HZ  
 Weight:- 350 gms

Please add 30p P.P. per unit order as PH 12

**ARROW AUDIO CENTRE**  
 20 NORTH BAR BANBURY OXON OX16 0TF.  
 TELEPHONE BANBURY (0295) 3677  
 TERMS: CHEQUE/PO WITH ORDER. CALLERS WELCOME

**HE MICROBE R/C**  
 Basic Kit £19.90  
 (2 PCB's and all PCB components)

**G.B - C.B - C.B**  
**AERIALS AND ACCESSORIES**

Cutter mount £15.95  
 Boot/Roof/Wing mount £19.95  
 Traditional Fibreglass Whip £14.95  
 AM/FM/CB Retractable £25.95  
 CB Electric Retractable £29.95  
 AM/FM/CB Electric Ret £39.90  
 Roof mount 20" Glass Whip £19.95  
 SWR/Power/F.S. Meter £24.95  
 SWR/Power Meter £12.95  
 Pre-Amp 20db gain £19.95  
 Splitter Box £9.95  
 Linear Amps from £59.95  
 27 MHz Monitor + AM/FM £18.65

\*These are a few of the items available\*

The latest from the U.S.A.  
**PINBALL WIZARD**  
 \*Still available\*  
 Featured in Nov. issue of E.T.I.  
 Home TV Game - B/W Kit  
 Basic Kit £28.90

Contains everything except box and controls  
 Box & Controls £6.50. P.S.U. £3.90  
 CEH Car Alarm Kit £18.90  
 Chroma Chime 24 tune door chimes kit £10.75. Built £15.95  
 SINCLAIR SC110 10MHz scope £145.25  
 PFM 200 Digital Frequency Meter £52.00  
 3" 5 MHz Oscilloscope £113.85  
 4" 5 MHz Oscilloscope £139.90  
 5" 10 MHz Oscilloscope £169.90

**ATARI £138**

**COMPUTERS—HOME BUSINESS, ETC**

Pet 8k £458.85  
 Pet 16K £573.85  
 Pet 32K £790.00  
 Superboard 11 4K £172.45  
 UK101 kit 4K £228.85  
 UK 101 Built 4K £286.35  
 Superboard/UK101 case £33.80  
 Nascom 2 kit £339.25  
 TRS80 16K Level II £409.40  
 H14 line printer kit £410.00  
 5 1/4" disc drive for TRS80 £271.40  
 Computer Books S.a.e.  
 Software - Pet/TRS80/Superboard, etc.  
 Exody Sorcerer 16/32/48K from £860.00  
 Renumber prog. 101 £4.00  
 Free - Advice/Demonstrations/Coffee

**ELECTRONIC GAMES**

Star Chess T/V game £63.35  
 Database Prog T/V game £89.95  
 Chess Challenger 7 £95.00  
 Chess Challenger 10 £160.00  
 Voice Challenger £230.00  
 Chessmate 8 level £59.95  
 Zodiac Astrology Computer £29.95  
 Electronic Mastermind £14.90  
 Supersonic Mastermind. New £21.00  
 Mattel Subchase. New £17.90  
 Mattel Armor Battle. New £17.90  
 Enterprise 4 in 1 £22.90  
 Galaxy Invaders. New £22.95  
 Radio Control Models—Various

Ball Clock as H.E. offer. Kit £24.95, or ready-built £29.95.

S.a.e. enquiries. Please allow up to 21 days for delivery. ALL PRICES INCLUSIVE

**N.I.C.**  
 UNIT 6  
 61 BROAD LANE, LONDON N.15 4DJ  
 Day 01-808 0377; Eve 01-889 9736

**CBCBCB**

**ACCESSORIES ACCESSORIES  
 LARGEST STOCKS IN THE MIDLANDS  
 WHOLESALE + RETAIL  
 SUPPLIED**

**YES WE CARRY LARGE STOCKS OF CB Equipment including over 50 TYPES of ANTENNA, SWRS, BURNERS, SPEAKERS, POWER SUPPLYS, SUPPRESSORS, PRE-AMPS, CABLES, ETC. PLUS LOTS LOTS MORE!!!**

**THIS MONTH'S SPECIAL OFFERS**

Fully retractable AM/FM/CB Antenna with Splitter. Only £18.95  
 3/5 amp Power Supply. Only £16.95

DV27 Only £5.95  
 Magmount Antenna Complete £8.95

**\*TRADE ENQUIRIES INVITED\***

**\*REMEMBER - We are Direct Importers and therefore can offer the BEST PRICES AROUND**

**EM AUDIO VISUAL**

27 HOPE STREET  
 HANLEY  
 STOKE-ON-TRENT ST1 5BT  
 Telephone: 0782 273815





## Club Corner

Literally dozens of new clubs are springing up all over the place. If you've read **CITIZENS BAND** you'll know that we have published the most comprehensive club listing ever and we will continue to do so every month. Here is this month's selection of new clubs:

- |   |  |
|---|--|
| <b>WORTH VALLEY BREAKERS</b><br>B. Widsop<br>c/o 19 Woodhouse Road,<br>Keighly,<br>Yorks.           | <b>COPY CAT CLUB</b><br>Martholme Grange,<br>Altham,<br>Accrington,<br>Lancashire. |
| <b>AIRE VALLEY BREAKERS</b><br>Call Ch 19 AM or 30 USB.   | <b>REDDITCH AREA CB CLUB</b><br>80 Heronfield Road,<br>Churchill,<br>Redditch      |
| <b>CB MUSKETEERS</b><br>PR. J.L. Smith,<br>61 Gibbwin<br>Great Linford,<br>Milton Keynes,<br>Bucks. | <b>ST HELENS CB CLUB</b><br>33 Broadway,<br>St Helens,<br>Merseyside.              |



Two sneak previews of this year's Breadboard show. Above some of the CB goodies on the Wintjoy stand. Below, Glyn Hall (Wintjoy) menacing the customers asking if he sells rigs.



## CB Books

Our last item this month concerns the sudden increase in the number of books about CB. As you might expect most of these works are of American origin and as such can be slightly irrelevant to our own needs. That aside a couple of books we've seen recently are actually applicable to any CB system working on 27 MHz. Best so far is called *Modern CB Radio*

servicing. It is published by Hayden and is being imported by NIC. This book costs £4.60 and believe us, it's worth every penny. The book contains step-by-step instructions that will enable any competent, electronically-minded person to carry out simple repairs on all kinds of common CB rigs. Mind you, we can't actually encourage anyone to do such a thing — after all CB is illegal and no one really has any rigs that might go wrong. . . . .

## Shop Scene

Walthamstow is fast becoming the North London CB centre as it now boasts two specialist CB accessory dealers. Latest arrival is called *Globe Communications*. Previously *Globe* were TV aerial specialists but within the last two months they have turned their attention to selling CB gear. Already they have built up a strong local reputation for low prices and I must admit they're certainly the lowest I've seen in London. *Globe* is run by Jack Glover, Mick Dingley, (they're the governors) and ably assisted by Jim Wild and Steve Dingley (Mick's son). *Globe* can be found at 110 Hoe Street, Walthamstow. Phone 521-7221 for details.

## And Finally . . . . .

Just in case you ever wondered how large some CB clubs can get the UBA now boast a membership in excess of 70,000. Impressive eh? Stay Lucky and see you next month. **HE**

# Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately twelve issues and is attractively bound and blocked with the **HOBBY ELECTRONICS** logo.

Price U.K. £3.95 including postage, packing and VAT, overseas orders add 30p. Why not place your order now and send the completed coupon below with remittance to:-

**EASIBIND LTD., 4, UXBRIDGE STREET, LONDON W8 7SX**

Please allow 3/4 weeks for fulfillment of order.

*it's easy* with **EASIBIND**

Easibind Ltd., 4 Uxbridge St., London, W8 7SX.  
Nat. Giro No. 5157552.

### Order Form

**HOBBY ELECTRONICS**

enclose p.o./cheque value .....

for ..... binders

Years required .....

**BLOCK LETTERS PLEASE**

Name .....

Address .....

.....

Date .....

Registration No. 307469.



## HOBBYPRINTS

If you have never used HOBBYPRINTS before, then you don't know what you've been missing. HOBBYPRINTS are an etch-resistant rub-down transfer. Just place the appropriate HOBBYPRINT over a clean piece of copper clad PCB material and rub. It's as simple as that. Once the design has been transferred, immerse the board into the Ferric Chloride. 15 minutes later you will be rewarded with a perfect PCB prepared from our original artwork, so you can have no worries about making a mistake. By the way, HOBBYPRINTS are ideal for making PCBs by Ultra-Violet exposure.

For your HOBBYPRINT refer to the chart above and send your cheque or postal order to:  
HOBBYPRINTS,  
Modmags Sales Office,  
Hobby Electronics,  
145 Charing Cross Road,  
London WC2H 0EE.

**HOBBYPRINT SHEETS ARE AVAILABLE FOR ISSUES FROM NOV. 78 RIGHT UP TO THIS ONE. ALL SHEETS COST £1.20 ALL INCLUSIVE OF POST AND PACKING AND VAT. ORDER BY SHEET LETTER AND ISSUE MONTH (SEE BELOW).**

ISSUE	SHEET REF.
Nov. 78	A
Dec. 78	B
Jan. 79	C
Feb. 79	D
Mar. 79	E
Apr. 79	F
May 79	G
Jun. 79	H
Jul. 79	I
Aug. 79	J

ISSUE	SHEET REF.
Sept. 79	K
Oct. 79	L
Nov. 79	M
Dec. 79	N
Jan. 80	O
Feb. 80	P
Mar. 80	Q
Apr. 80	R
May 80	S
Jun. 80	T

# ELECTRONIC GAMES

## ATARI

SPECIAL PRICE



£86 + VAT

## SPACE INVADERS



HAND HELDS + CARTRIDGES  
ATARI ACETRONIC  
PRINZTRONIC  
RADOFIN - DATABASE etc.  
We keep a full range!  
Send for cartridge lists stating which machine you own.

MAIL ORDER SERVICE - Free postage & Packing

TELEPHONE & MAIL ORDERS - accepted on:

Access \* Barclaycard \* American Express \* Diners Club

CALLERS WELCOME - at our shop in Welling - Demonstrations daily  
Open from 9am-5pm Mon-Sat (9am-1pm Wed)

GUARANTEE - Full 12 months + After Sales Support!

We have comprehensive brochures on all products. Please let us know what you are interested in and we will send you detailed brochures AND our own 32 page catalogue covering most games on the market.

## INTELLIVISION MATTEL



£173.87 + VAT

Available August 1980  
This is the most advanced TV game in the world. Expandable next year into a full microcomputer. COLOUR CATALOGUE AVAILABLE WITH DETAILS ON ALL THE CARTRIDGES

## BRIDGE


COMPUTER



- \* Plays 1/2/3 or 4 Hands
- \* Problem Mode
- \* Audio Feedback
- \* Instant Response
- \* Auto scorekeeping

## DRAUGHTS

COMPUTER

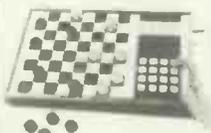

- \* Solves Problems
- \* Rejects illegal moves
- 2 level machine £43 + VAT
- 4 level machine £77.78 + VAT

## CHESS

COMPUTERS



Send for further details.

NEW RANGE AVAILABLE AUGUST 1980  
We specialise in computer chess machines & stock over 13 different models from £20 to £300

## BACKGAMMON

COMPUTERS



From £38 to £108. Send for further details.

OMAR 1  
OMAR 2  
CHALLENGER  
GAMMONMASTER

## LEISURE

- \* CHEAP TV GAMES
- \* TELEPHONE ANSWERING MACHINES
- \* AUTO DIALERS
- \* CALCULATORS
- \* DIGITAL WATCHES
- \* PRESTEL
- \* HAND HELD GAMES

## TELETEXT



RADOFIN  
TELETEXT  
Add on Adaptor

£173 + VAT

## 24-TUNE DOOR BELL

£13.65 + VAT




## FREE CATALOGUE

For a free copy of our 32 page catalogue, send a 12p stamp to Silica Shop Ltd or Telephone 01-301 1111

## SILICA SHOP

SILICA SHOP LTD., Dept. HE1  
1-4 The Mews, Hatherley Road  
Sidcup, Kent, DA14 4DX  
Tel: 01-301 1111

# PCB FOIL PATTERNS

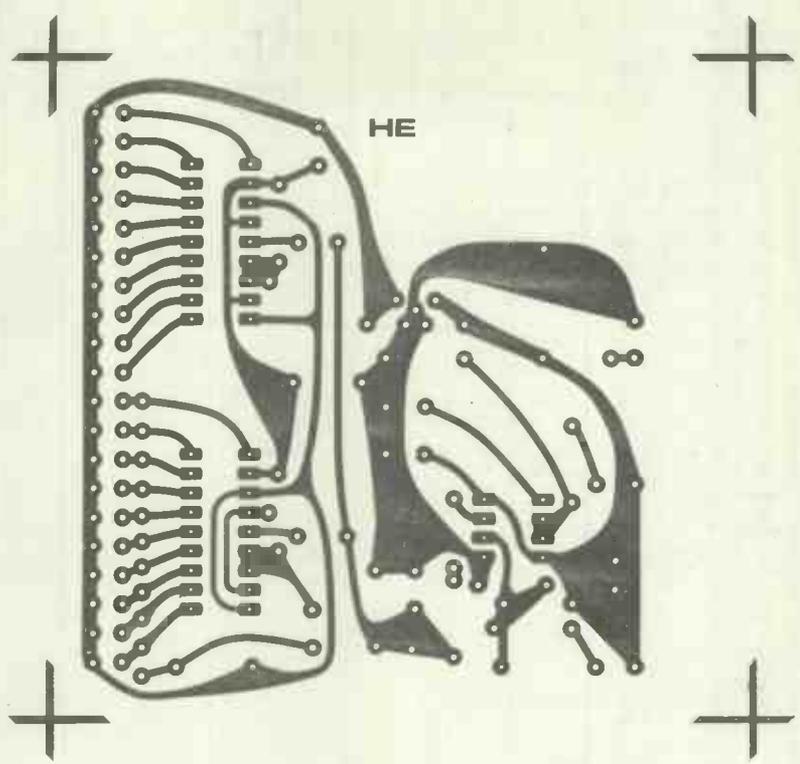

Only one foil pattern this month: the HE Car Rev Counter

Complete This Series:  
11, 8, 14, 11, 9, 13,  
.../ .../ .../ .../ .../ .../ .../

Send to: Subscriptions Department,  
Hobby Electronics  
PO Box 35, Bridge Street,  
Hemel Hempstead, HERTS.

Dear Hobby Electronics, please send me a copy of each issue as soon as it is published. I enclose a cheque for £9.

Name .....

Address .....

Tricky, isn't it. Here's the answer: 11, 8, 12 and 10, 14, 12. Any wiser?

The key is that these are the days when you have to be in your newsagents this year to get your copy of Hobby Electronics on the day of publication. Remember the series: 11, 8, 14, 11, 9, 13, 11, 8, 12, 10, 14, 12. But don't internalise it too well — the numbers will be different next year.

Got a headache, yet? Here's relief: there is a way you can ensure copies of Hobby Electronics automatically — no need to remember dates, no need to rush to the newsagents, no need to impose on your friends to get you a copy when you go abroad. It couldn't be simpler; just write your name and address on the coupon below and send it to us with a cheque for £9.

## ● MAIL ORDER CB!

Want to get into CB, but don't know much about it? Try our beginner's package, one 40-channel CB rig (Sam, President or Cobra, usually), one DV27 car aerial (56in. fibreglass whip), plus SWR meter, plus full instructions plus beginner's book *The Big Dummy's Guide to CB*, package price **£99.95** plus **£2.50** carr. (Roadline). Red Star delivery to your local station **£2.50** extra. Home base station package: one rig, as above, plus M-117 or GPA27 base aerial (pole mounting), plus 20 yards coax cable, plus SWR meter, plus 12v. power unit (mains transformer), plus instructions, plus books (as above), **£159.95** plus **£3.50** carriage (Roadline). Red Star **£2.50** extra. Heavy-duty chimney lashing kit, plus 5ft. x 1 1/2in. pole, or heavy-duty wall bracket, plus 5ft. 1 1/2in. pole, suitable for mounting M-117 or GPA27 base station antennas, **£9.95** plus **£2.50** carriage. Red Star **£2.50** extra. President Adams 240-channel sideband rigs, **£165** each plus **£2.50** carriage; many other bargains in antennas and accessories. Too many to list here. Walkie-talkies, 100 milliwatt 49 MHz models with MW radio incorporated (approx. 100-200 yds. range), **£33.75** pair plus **£1.25** postage; 1 watt 29MHz units, 1-5 miles range reported by customers, **£108.75** pair plus **£1.25** postage. Please ring for prices on your other requirements; sorry, no price lists or brochures at present, as stock is moving too quickly. Access and Barclaycard accepted by phone on all items. Send postal orders or bankers cheque for same-day despatch, cheque orders 3-4 days delay for clearance. **Castlegate TV and Radio, 64 Castlegate, Grantham. Tel. 0476 65869.**

**150 ASSORTED RESISTORS £1. 100 Assorted Capacitors £1. 100 1N4148 £1. P. & p. 20p.** S.A.E. lists of components, mikes, meters.—Dept. H, D.B. Products, 1 Holly Tce., York YO1 4DS.

**BURGLAR ALARM KIT.** Contents include control module and steel box, steel bell box (pvc coated), keyswitch 106dB FBI siren, 6 contacts, attack button, 3 pressure pads, batteries, cable clips, screws, instructions. **£83.30** inclusive Sigma Security Systems, 13 St Johns Street, Oulton, Leeds LS26 8JT. W. Yorks.

**OSCILLOSCOPE. £12.** Easy build converter plugs into TV aerial socket and converts to large screen oscilloscope. (Components cost under £12). Circuit and plans **£3.** — Kerr, 27 Coles Road, Milton, Cambridge CB4 4BL. (Callers by appointment).

**ZX80 GAMES.** Free Game sent on request. Send s.a.e.: Mastercode, Simon Says, Dr. Who, Alien Invader. The 4 on cassette, **£3.** —Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

## AMAZING ELECTRONIC PLANS

Lazers, Burning, Cutting, Rifle, Light Shows.

Ultra-sonic Force Fields. Weaponry, Satellite TV, Giant Tesla, Split the Atom. Lots more. Catalogue 75p

## PLANCENTRE

ST. JOHN STREET  
BRIDGENORTH, SHROPSHIRE

## DIGITAL WATCH BATTERY REPLACEMENT KIT



These watches all require battery (power cell) replacement at regular intervals. This kit provides the means. We supply eyeglass, non-magnetic tweezers, watch screwdriver, case knife and screwback case opener. Also one doz. assort. push-pieces, full instructions and battery identification chart. We then supply replacement batteries — you fit them. Begin now. Send **£9** for complete kit and get into a fast-growing business. Prompt despatch.

**BOLSER INSTRUMENT CO. HE1**  
11 Percy Avenue, Ashford, Middx. TW15 2PB

# CLASSIFIED

## RATES

1-3 insertions **£5** per scc  
4-11 insertions **£4.50** per scc  
12 insertions **£4** per scc  
18p per word (Min. 15 words)  
Box No on application

All advertisements in this section must be pre-paid  
Closing Date: 1st Fri. month preceding publication

Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

SEND TO: HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 26

## £1 BARGAIN PACKS

All packs **£1** each; any 12 for **£19**. Post 25p  
All top grade new components—no rubbish

PC1 12 BC107	PC9 10 T03 sockets
PC2 14 BC108	PC10 15 0.1/35V variacs
PC3 12BBC109	PC11 14 3mm red LED's
PC4 3 2N3055	PC12 12 5mm red LED's
PC5 7 8F51	PC13 8 741
PC6 16 BC182	PC14 6 555
PC7 60 1N4148	PC15 15 12V zeners
PC8 25 1N4003	PC16 100 1k 1/4W 5% R's

Send s.a.e. for 8-page list/enquiries. Mail only.

**PC ELECTRONICS, 2 Thornhill, Romsey Road Whiteparish, Salisbury SP5 2SD**

## GLOBAL ELECTRONIC CONSTRUCTION KITS SUPER CHIP 1

Construct this easy-to-build one-chip radio using the Ferranti ZN414 integrated circuit plus one transistor. This highly sensitive radio giving full m/w coverage works for months on a 1.5v. battery, and its own ready-wound ferrite rod aerial means no external aerial req. Case measures only 10.5cm. X 7cm. X 4cm and comes complete with Xtal earpiece and all necessary parts to build. It including Easy Build Plans and Instructions. Total cost **£6.95**; p.p. 55p.

## SUPER CHIP 2

As above, but with loudspeaker. **£8.25** + 65p p.p.

Catalogue on request 55p

Cheques and P.O.s payable to  
**GLOBAL ELECTRONIC ENTERPRISES**  
Dept. H.E., St. John's Works, St. John's, Bedford

Humidity Switch .....	£1.25	Small Reed Switch .....	10p
Electronic Timers .....	49p	Changeover Type .....	50p
Door Viewer .....	£1.50	Large Reed Switch .....	16p
Bleeb IC Boards .....	40p	Changeover Type .....	35p
Enamelled Copper Wra. 32, 34, 36		Magnets .....	8p & 15p
38, 40 SW6 .....	1p ft.	Reed Relay 3-9v DC .....	40p
4 Car Telephone Spring Leass. 45p		Tape Recorder Motor, Reg 9v DC 1 1/2" x 2"	85p
Alert Project Bar .....	40p	10 Ass'd. 1 1/2A Diodes .....	40p
4 Pin Trans Shts .....	10p	40 Ass'd. Springs .....	50p
Slide Switch S.P.C.D. ....	10p	50 Ass'd. Resistors .....	40p
Mercury Switch .....	75p	10 Ass'd. LEDs .....	£1.20
Fire Alarm Sensor .....	55p	20 Ass'd. C280 Caps .....	50p
Robber Mats .....	11p	5 Ass'd. Micro Switches .....	£1
Resistors 1/4W 5% .....	2p	30 Ass'd. Untested ICs .....	35p

Prices include VAT, add 25p postage, List 15p

## GRIMSBY ELECTRONICS

17 Beesley Road, Grimsby, South Humberside  
Callers to our Lambert Road Components Shop

**£99 SYNTHESISER D.I.Y.** Professional results, easy-build.—S.A.E.: Dewtron, 254 Ringwood Road, Ferndown, Dorset BH22 9AR.

**PRINTED CIRCUITS.** Make your own simply cheaply and quickly! Golden Fotolak Light Sensitive Lacquer—now greatly improved and very much faster. Aerosol cans with full instructions, **£2.25**. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board, approx. 1mm thick **£1.75** sq. ft. Post/packing 60p.—White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

## Earn £20-£100 p.w. in your spare time

by introducing the revolutionary new **Flip-Caller** telephone to your friends. Features micro-chip controlled push-button dialling and memory recall. Sells itself. Generous commission. For details write to Dept. ET1


## IDL SUPERPHONE

P.O. Box 31, Twickenham TW2 5RL



If it's a case of making your project look good, then use one of ours.

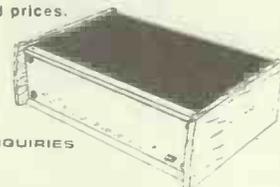Simply send a S.A.E. for Details and prices.



TRADE ENQUIRIES INVITED.

## H. M. ELECTRONICS

271a/275a Fulwood Road, Broomhill Sheffield S10 3BD

## SPARE PARTS

SERVICE MANUALS  
PHONE ORDERS NOW  
Most makes inc. Sony, J.V.C., Hitachi etc.

**HI-FI HOSPITAL (GRS) LTD.**  
100 Uxbridge Road, W7 0T-840 1890

# AD INDEX

ABSONGLEN LTD .....	30
AHLERS ELECTRONIKA .....	2
AMBIT INTERNATIONAL .....	31
ANGLIA COMPONENTS .....	44
ARROW AUDIO CENTRE .....	62
BI-PAK SEMICONDUCTORS .....	35
BK ELECTRONICS .....	59
C.S.C. ....	26, 41
ELECTROVALUE .....	57
E.M. AUDIO VISUAL .....	62
GREENWELD .....	44
HENRY'S RADIO .....	26, 49
ICS .....	26
ILP .....	4 & 5
MAGENTA ELECTRONICS .....	24
MAPLIN .....	68
MARSHALLS .....	17
MINIKITS .....	36
MINIM AUDIO .....	44
E.R. NICHOLLS .....	57
NIC MODELS .....	62
T. POWELL .....	18
SELRAY BOOK CO. ....	36
SILICA SHOP .....	64
SURETRON SYSTEMS .....	36
SWANLEY ELECTRONICS .....	59
TECHNOMATIC .....	15
TEMPUS .....	10
TK ELECTRONICS .....	57
VERO ELECTRONICS .....	30
WATFORD ELECTRONICS .....	9
WINTJOY LTD .....	67

# CB ANTENNAS AND ACCESSORIES



## CB and monitor antennas CB Accessories



Citizen Band Fibreglass Antennas and Accessories  
for Marine, RV, Truck, Auto, Van and Motorcycle.

Watch for the new film  
"SMOKEY AND THE BANDIT II"  
starring BURT REYNOLDS and  
**Firestik** ANTENNAS!



### CB MOBILE ANTENNA SERIES

and the Shakespeare fiberglass Super  
Big Stick™ base station antenna



SWR METERS, NOISE SUPPRESSION FILTERS, T.V.I. FILTERS, CO-  
PHASORS, ANTENNAS, LEADS AND NUMEROUS OTHER  
ACCESSORIES.



Microphones, Power Supplies, SWR Meters, Linear Amplifiers, Preamplifiers,  
Antennas, Frequency Counters etc., etc. . . . .

## **TELEX** MICROPHONES AND HEADSETS

## **TURNER** ANTENNAS AND MICROPHONES

## **hy-gain** CB MOBILE AND BASE STATION ANTENNAS

## **K40** SPEECH PROCESSORS AND BASE LOAD ANTENNAS

For further information call Teledata on 200-0200.

We are now a Tandy Stockist  
UK Retail outlets in selected areas still  
being sought



103 High Street, Shepperton,  
Middlesex TW17 9BL, England.

Tel:

Walton-on-Thames (STD 09322) 48145

COMMUNICATIONS EQUIPMENT DISTRIBUTORS




# The new MAPLIN CATALOGUE is out on December 5th

A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.
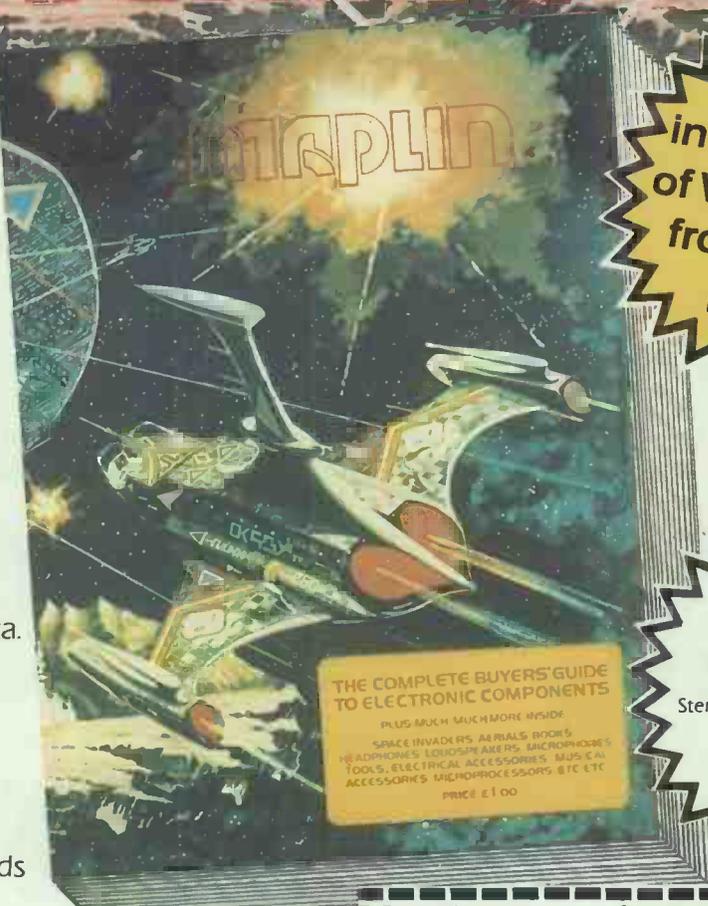
# MAPLIN

Maplin Electronic Supplies Ltd.  
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Telephone: Southend (0702) 554155. Sales (0702) 552911.  
Shops:  
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.  
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.  
Both shops closed Mondays.



On sale  
in all branches  
of W H Smith  
from Dec 5th  
price £1

**PLUS LOW PRICES**  
such as  
Resistors from 1½p  
Multimeters from £4.25  
Ni-Cads from £1.15  
Stereo Headphones from £3.49  
Radios from £2.95  
Over 300 Books  
21 Different ranges  
of capacitors, etc.,  
etc., etc.,

Post this coupon now for your copy of our 1981 catalogue price £1.  
Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.

I enclose £1.25

Name \_\_\_\_\_

Address \_\_\_\_\_

HE181