

Hobby Electronics

March '81

ISSN 0142-6192

60p

For A Down-To-Earth Approach To Electronics

BEGINNINGS OF REAL TV

**We trace
the origins
of modern
television**



**ALSO
INSIDE FOR YOU
TO BUILD**

**PORTABLE PUBLIC
ADDRESS AMPLIFIER -
Make yourself heard outdoors**



Special-offer kit



**Speedometer
for your bicycle
-no moving parts**



**Guitar FUZZ Box
-musical distortion
for under £10**

Ever wondered who buys electronics today? You'd be surprised!

The electronics market is rapidly expanding. Whether it's antennas, test equipment, accessories or what have you, it's becoming increasingly difficult to keep up with the latest developments. Or to get them.

That's where we come in. We probably have just what you're looking for and a lot more besides. We stock all the top makes... at prices that will just make you love us. Simply phone, write or telex

WINTOY Ltd., 103 High Street, Shepperton, Middlesex TW 7 9 BL, England, Tel. Walton-on-Thames (STD 09322) 48145 and find out.



Or just simply call us.



**TON AHLERS
ELEKTRONIKA B.V.**

Aalsmeerderdijk 349, 1436 BH Rijsenhout -
Holland, tel. 010 31 2977-2 86 11 (4 lines),
telex 15181 tonel nl. (near Schiphol Airport).

Even the old boys circuit is getting electronicized. With our help.

Hobby Electronics

MARCH 1981
Vol. 3 No. 5

Editor: Hugh Davies
Assistant Editor: Keith Brindley Editorial Assistant: Tina Boylan
Drawing Office Manager: Paul Edwards Group Art Editor: Paul Wilson-Patterson B.A.
Managing Editor: Ron Harris B. Sc.

BEGINNINGS OF REAL TV

We trace the origins of modern television

ALSO



This month's cover shows three notable receivers from the history of TV. Left is a cut-away Colorstar TV made by Ferguson in 1968 (on show in Science Museum). Centre is a Baird prototype made by the Plessey Company in 1928. It had a 30-line, vertically-scanned picture with a frame rate of 50 frames/second, and is on view at the ITA Gallery, Brompton Road, London. In the background is an elegant model 702 receiver made by Marconiphone in 1938 (also on show in Science Museum). More details on these TVs is given under *The Beginnings Of Real TV* on page 18.

FEATURES

MONITOR	6
<i>News, news, and nothing but the news</i>	
MOVE TOWARDS MICROCASSETTES	10
<i>A special feature on the smallest of audio cassettes</i>	
THE BEGINNINGS OF REAL TV	18
<i>Before ICs, before trannys, before valves</i>	
COMPETITION RESULTS	24
<i>The winners of our January competition</i>	
BUILDING SITE	27
<i>To help you connect</i>	
CLEVER DICK	41
<i>A lively selection of letters</i>	
INTO DIGITAL ELECTRONICS	43
<i>Delving deeper into micros</i>	
O LEVEL Q & A	48
<i>All about test gear</i>	
WHAT'S IN A NAME	53
<i>You can't touch it</i>	
BREAKER ONE FOUR	61
<i>Citizens on the air</i>	

PROJECTS

PUBLIC ADDRESS AMPLIFIER	
<i>Now you can really be a loud-mouth</i>	13
WINDSCREEN WIPER CONTROLLER	
<i>Just the thing for bad weather</i>	30
STEAM LOCO WHISTLE	
<i>Last part of our train sound effects series</i>	33
BICYCLE SPEEDOMETER	
<i>A digital delight</i>	37
SHORT CIRCUIT	
<i>Experimenters' corner</i>	46
FUZZBOX	
<i>Controllable guitar distortion</i>	54
PHOTOGRAPHIC TIMER	
<i>Built in a flash?</i>	58
PCB FOIL PATTERNS	
<i>Right at the bottom of the projects</i>	65



NEWS & INFO

HE Next Month	8
Hobbyprints	64
SPECIAL OFFER SUBSCRIPTIONS	66
Classified Ads	66

Advertisement Manager: Stephen Rowe Advertisement Representative: Sally Holley
Creative Director: Diego Rincón
Managing Director: T. J. Connell

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Published by Modmags Ltd. Distributed by Argus Press Sales & Distribution Ltd, 12-18 Paul St., London EC2A 4JS. Printed by QB Ltd., Colchester. Covers printed by Alabaster Passmore.
Copyright: All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing of kits of the projects must be sought from the Publisher. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally. © Copyright 1981 Modmags Ltd ABC Member of Audit Bureau of Circulation.



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET


CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connections via five pins on the underside. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02


BIPOLAR

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fidelity and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shouldered connections are simple, via five pins on the underside and with our new pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£9.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

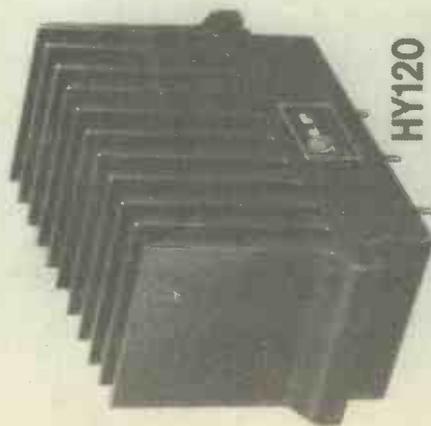

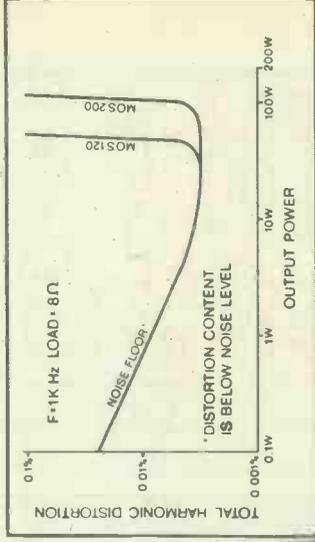I.L.P. POWER AMPS ARE ENCAPSULATED FOR THERMAL STABILITY AND LONGER LIFE




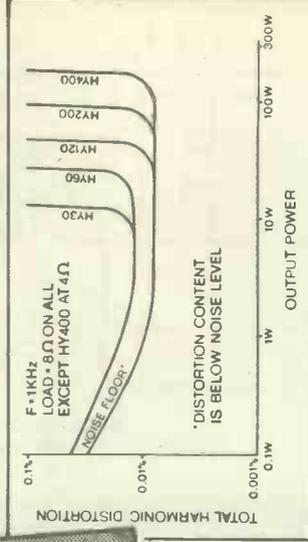Load impedance both models 4Ω-∞ Input sensitivity both models 100KΩ. Frequency response both models 15Hz-100KHz - 3dB



Load impedance all models 4Ω-∞ Input sensitivity all models 100KΩ. Frequency response all models 15Hz-50KHz - 3dB

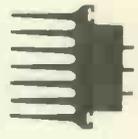THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages. Research shows they provide excellent thermal dissipation and stability. Slotting provides easy mounting. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity - Mag. P.U. - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
 HY66 stereo £12.19 + £1.83 VAT Connectors included
 B6 Mounting Board for one HY6 78p + 12p VAT
 B66 Mounting Board for one HY66 89p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.


- PSU30 ± 15 V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS £8.10 + £1.22 VAT
- PSU36 for use with 1 or 2 HY30's
- ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS
- PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.32 + £2.45 VAT
- PSU95 for use with 1 MOS200 £21.34 + £3.20 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.46 + £3.22 VAT
- PSU185 for use with 1 or 2 MOS200

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER

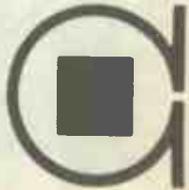
Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



ELECTRONICS LTD.

FREEPOST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780

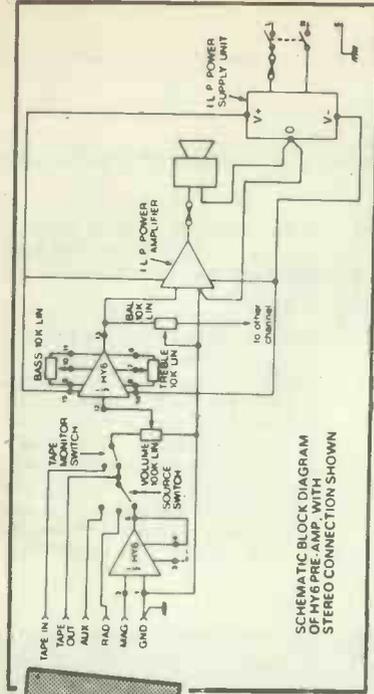Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers



SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP WITH STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 V

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factories, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply.....

..... Total purchase price £.

I enclose Cheque Postal Orders International Money Order


Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

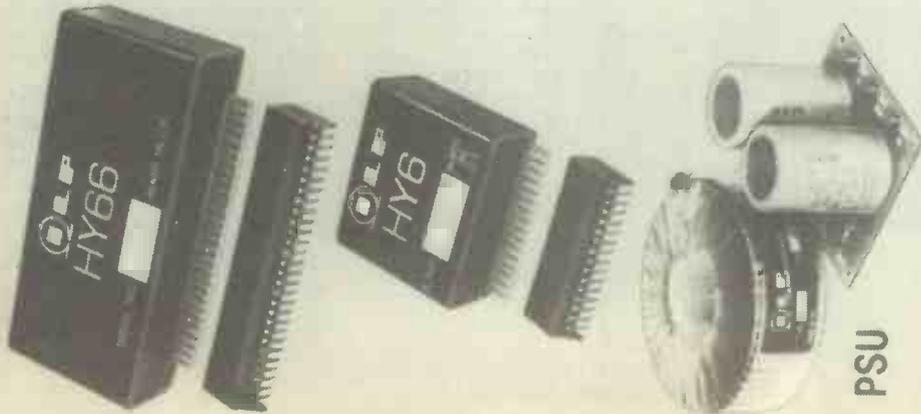NO QUIBBLE 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE



PSU

ALL U.K. ORDERS DESPATCHED FREEPOST

Monitor



50th Model Engineer Exhibition — Record Attendance

To the surprise of the organisers, attendance at this year's Model Engineer Exhibition, the 50th in its 73-year history, exceeded 81,000. (And we thought just over 17,000 was a large turn-out for Breadboard 80!)

It was also the largest exhibition since it started in 1907 and for this reason it was held at the Wembley Conference Centre, running from 1 to 3, 5 to 10 January.

HE visited the exhibition on Friday 9 January, and although most of the exhibits on display were mechanical or electro-mechanical in operation, we still thought it well worth the visit.

No sooner had we gained entry to the Centre we found ourselves surrounded by every conceivable type of model: from locomotives to sailing ships and from aeroplanes and cars to military models.

Of particular interest to electronics enthusiasts were the radio-controlled models, and plenty of

space was allocated to these. Provision had been made in the lecture theatre for indoor 'round the pole' flying of model aircraft and for racing of model cars. (A safety net had been fitted between the stage and the auditorium.) On the roof outside the concourse a pool had been installed for model boats. Visitors were encouraged to enter competitions with their own models.

Stands in the exhibition catered for every need of the hobbyist, ranging from raw materials to the finished items. And if you didn't have a fully-equipped machine shop in the shed at the bottom of your garden then you could buy one of the many different varieties of model kits, some with pre-finished and pre-painted components.

For the die-hards who insist on making even the last nut and bolt, there were tools. If you wanted a lathe or a drilling machine, they were there. If you wanted a jeweller's vice or a set of miniature screwdrivers, they were there too. But most important of all, there was help. Many

if they were the result of shrinking powder applied to the full-scale models — such was the attention to fine detail.

Lord Gretton, president of The Society of Model and Experimental Engineers, was to have opened the exhibition but, unfortunately, was ill in hospital at the time. His son, John Gretton, who is a keen locomotive enthusiast himself, took his place.

Possibly because it followed a Bank holiday, Friday 2 January was almost the busiest day — but it was just beaten by the final Saturday.

Now we had some idea of how



Tiger Moth on show at MEE. It was built by Ron Chivrell, who took Championship Cup for aircraft models. Detail extends to the tail trim system and cockpit instruments. Ron flew the real machine at Fair Oaks, Surrey

of the staff on the stands are hobbyists themselves and were keen to help and advise on visitors' problems.

Even the electronics enthusiast would benefit from a visit to the ME exhibition because of the wide selection of tools on show. In common with most exhibitions there were some interesting offers. And even the casual visitor must have been impressed by the care that had gone into those models. Some of the locomotives, for example, looked as

busy this exhibition was by the length of the queue on the Friday we made our visit. If you are interested, it would be better to get your tickets in advance and stroll past the queue in a leisurely manner. They are advertised during November and December in MAP model magazines, namely: Aeromodeller, Clocks, Military Modelling, Model Boats, Model Engineer, Model Railways, Radio Control Models, Radio Modeller, Popular Crafts, Scale Models, and Woodworker.



Stable Supply From Italy

This could be the kind of mains power supply offer you can't refuse ... imported from Italy. Model BRS27 is made by Breml and gives a regulated fixed output of 13.8 VDC at 3 A maximum.

Stability is specified as being better than 0.1% with mains variations of 10% or load variations from 0 to 2.5 A. It includes an electronic current limiter, and ripple is specified as being 1 mV with 2.5 A load.

The supply comes in a robust black-finished steel box 173 mm wide by 90 mm high by 138 mm deep. Output sockets, mains switch

and red indicator lamp are mounted on the front panel.

According to George Philips, managing director of the supplier, Open Channel Telecommunications, N. London, cost of the BRS27 is likely to be '£16.95 or under'.

He mentioned that another power supply, having the same electrical specification as the BRS27 but with lighter gauge steel for the box will be available shortly and will cost only £6.75.

What would you use 13.8 VDC at around 2.5 A for? One obvious application which comes to mind is equipment intended for mobile use, such as Citizens' Band rigs when these become legal.

Contact Open Channel Telecommunications, 407 Lordship Lane, London N17. Tel. 01-808 5656.



Tiny Tape Recorders

Two miniature hand-held recorders, models D6700 and D6710, are due for release by Philips Audio in March 1981.

Unlike Philips' Pocket Memo Range, which uses minicassettes giving 15 minutes playing time on each side, these two use *microcassettes*, which double this

playing time.

Full details of these machines, and of the likely impact of microcassettes on the market are given in this month's special news feature of page 10.

Further details on the D6700 and D6710 are available from: Philips Audio, PO Box 298, City House, 420 to 430 London Road, Croydon, Surrey CR9 3QR.

Can You Design For The Disabled?

We're giving you, as a reader of HE the opportunity to design a project for a disabled person — and a chance to win a prize for your entry.

Did you know that at least 10% of the population of any country suffers from some form of physical or mental disability?

Now, 1981 has been proclaimed by the United Nations General Assembly as the International Year of Disabled Persons (IYDP).

So, in the April issue we are running a Design Competition to enable readers to do their bit and try to help the UN in its aims. We reckon that with all the brain potential out there, some of you will have



ideas and designs which must help somebody.

The idea is that your design should aid a disabled or handicapped person — any aid — any handicap.

You stand to win large cash prizes, so you can't afford to miss it, can you? Remember to order your April copy of HE early, to make sure of your entry form and details.

Wire Up Your Boards With A Pencil

Looking a little like a red plastic carrot with an obliquely set metal probe at its tip, the Vector Wiring Pencil model p-173 can be used for point-to-point wiring of circuit boards. It is supplied with two 20 mm diameter metal bobbins of fine-gauge coated copper wire, each with a different-coloured coating for identification.

One of the bobbins is loaded into the cap of the tool and the wire is threaded out through the probe tip. The wire feed can be controlled by hand pressure on the bobbin, the rim of which protrudes slightly from the cap.

Wire is routed around the circuit board (plain board, that is, the type having no laminated copper strips) from component-to-component or pin-to-pin. At each connection point, the wire is wrapped around the wire-end or pin and soldered in place (the coating melts when a soldering iron is applied to it).

Although we can't recommend it for HE projects, which generally make use of PCBs or Veroboard, the pencil could be useful for our more

ambitious readers who may like to experiment with breadboards. Certainly, the wire gauge is much too fine and delicate for permanent hook-ups. (See this month's Building Site for guidance on the right choice of wire for the job.)

Main feature of the wiring pencil is its light weight: our sample was only 25g (0.88 oz) including the bobbin. Cost, including two bobbins of wire and instructions, is £5.

Another wiring tool available from the supplier, J.H. Equipment, Lancs., strips the coating from the wire before it is wrapped. Thus there is no need for soldering. John Hancock, managing director, described this as more of an industrial tool, costing £16.

Both tools are imported from Vector Electronic Co. Inc., California, USA. Hancock said that he hoped to offer a kit soon comprising the p-173 Wiring Pencil and some circuit boards.

J.H. Equipment Ltd., 91 Redbrook Road, Timperley, Trafford, Lancs.

New Catalogue From Heath

Heath Electronics (UK) has produced its winter 1980-81 catalogue which is filled, as usual, with a mouth-watering selection of electronic kits.

One new kit is the Heathkit Ultrasonic Minuteman II security alarm system. This enables property to be protected inside and outside. Up to three ultrasonic detectors can be used, together with indoor/outdoor loudspeakers, key operators, magnetic door controls and window foil or other closed-circuit detector devices. Master ultrasonic control/detector GD-1800E protects an area up to 300 sq. ft. and the kit costs £141. Accessories include 'slave' ultrasonic kits at £52 each, key operators (for doors, closed-circuit loops etc) at £24.50 each and an all-weather alarm ('sounds loud wail') at £23 each.

Another new kit is the GC-1720

digital wall clock, 5 1/4" high by 7 1/2" wide by 1 1/2" deep (133 by 181 by 38 mm). Accuracy is claimed to be + 1 minute a year, and the clock is claimed to run for two years on one 1.5 V alkaline cell. Time is displayed on four 1" liquid-crystal displays in 12 or 24 hour format. The GC-1720 costs £43.70.

Four new electronic weather forecasting aids include the ID-1890, a microprocessor-based digital wind computer and clock/calendar. Wind direction is displayed on a 16-point compass dial, and speed can be converted and displayed in MPH, KPH or knots. It will even store 'gust information', in terms of wind speed, direction and the time at which the gust occurred. Definitely for the serious sailor, the ID-1890 kit costs £158 (£253 assembled).

Heath is also offering some more teach-yourself courses, and these include weather forecasting (£55), optoelectronics (£46.50) and programming in COBOL (£90).

WINTER 1980-81

Digital Barometer and Clock/Calendar — see page 12

Digital Wall Clock — see page 47

NEW!

More new products in this catalogue
 NEW! Computer Operating Systems, Languages and Software — see page 2.
 NEW! Electronic Ignition Tester — see page 16.
 NEW! Charging System Tester — see page 16.
 NEW! Basic Electricity Course — see page 21.
 NEW! Optical Switching Course — see page 28.
 NEW! Ultrasonic Car Alarm — see page 28.

Hobbyprint Erratum

It has come to our notice, this month, that Hobbyprint Y (December 1980) has the Minisynth Keyboard printed on it at 60% full size. If you remember, we had to reduce it in size to get it on the foil pattern page, but somebody forgot to enlarge it again for the Hobbyprint. Do not despair, the error is being rectified!

Hobby Electronics

Look for the April issue. You can't afford to miss it!

Anatomy Of The Space-Shuttle

A special HE report on the forthcoming NASA Space-Shuttle launch. We investigate what the technical problems have been, why it's overdue, and give you a timetable running up to the launch and beyond

Tremolo

Just the effect you want for your guitar to complement the Fuzzbox in the March issue, although it will work with any electronic musical instrument. Simple-to-build, even simpler-to-use yet it won't burn a hole in your pocket

Russian Roulette

A novelty game designed to eliminate the players — without any mess whatsoever

----- STOP PRESS ----- STOP PRESS ----- STOP PRESS -----
- COMPETITION - STOP - NEXT MONTH'S ISSUE OF HOBBY ELECTRONICS
- STOP - PROMOTING THE UNITED NATION'S INTERNATIONAL YEAR OF
THE HANDICAPPED PERSON - STOP - QUERY - DO YOU THINK YOU CAN
DESIGN AN ELECTRONIC AID TO HELP A HANDICAPPED PERSON - STOP -
ANY ELECTRONIC AID - SOLID-STATE, COMPUTER PROGRAM, EVEN VALVE
- ANY ELECTRONIC AID - STOP - ANY HANDICAP - STOP - PRIZES TO
WIN - STOP
----- STOP PRESS ----- STOP PRESS ----- STOP PRESS -----

High Fidelity Comes To HE

Announcing a special audio project for HE: a hi-fi, high-power amplifier system which you can tailor according to your budget by making use of our special-offer kits. We start with the pre-amplifier in the April issue. This pre-amp requires *no wiring* except for the leads to the power supply! You can use it with your own amplifier too

Windscreen Washer Alarm

For the motorist who's fed up with cleaning his windscreen by hand because his washer bottle has run dry. As soon as the fluid drops below a predetermined level a 're-fill me' alarm is displayed

Plus:

News, views and info on CB, circuits, recent developments in electronics — everything for the electronics enthusiast and hobbyist — things you can't afford to miss. Get It!

Items mentioned here are those planned, but unforeseen circumstances may affect the actual contents.

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 40P TO ALL ORDERS UNDER £10. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to all prices.

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest underground/BR Station. Watford High Street. Open Monday to Saturday, 9 a.m. to 6 p.m. Ample Free Car Parking space available.

POLYESTER CAPACITORS:
400V: 1nF, 1.5n, 2.2n, 3.3n, 4.7n, 6.8n 1p; 10n, 15n, 18n, 22n 1p; 33n, 47n, 68n 1p; 100n 150n 20p; 220n 330n 470n 470n 680n 60p; 1µ F 85p; 2µ 2.82p; 4µ 7.85p.
150V: 10nF, 12n, 10n 11p; 150n, 220n 1p; 330n, 470n 30p; 680n 38p; 1µ F 42p; 1µ 5.45p; 2µ 2.48p; 4µ 7.85p.
1000V: 1nF 17p; 10n 30p; 15n 40p; 22n 38p; 33n 42p; 47n 42p; 100n 42p; 470n 98p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10nF, 15n, 22n 7p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p.
330n, 470n 13p; 680n 18p; 1µ F 23p; 1µ 5.40p; 2µ 2.48p; 4µ 7.85p.

ELECTROLYTIC CAPACITORS: (Values are in µF). 500V: 10 82p; 47 78p; 250V: 100 65p; 83V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3 8p; 4.7 9p; 5.8, 10 10p; 15, 22 12p; 33 15p; 47 12p; 100 19p; 1000 70p; 50V: 47 12p; 68 20p; 220 24p; 470, 32p; 2200 80p; 40V: 4.7, 15, 22 9p; 3300 90p; 4100, 120p; 85p; 1.5, 6.8, 10, 22, 33, 47 8p; 100 11p; 150 12p; 220 15p; 330 22p; 470, 25p; 680, 1000 34p; 2200 50p; 3300, 76p; 4700 82p; 18V: 40, 100 2p; 150 2p; 220 12p; 330, 470, 20p; 680 34p; 1000 27p; 1500, 31p; 2200, 36p; 3300 74p; 4700 78p.
TAG-END TYPE 450V: 100V 85p; 70V: 4700, 248p; 64V: 3300 198p; 2200 139p; 50V: 3300 154p; 2200 110p; 40V: 4700 180p; 25V: 10,000 324p.

TANTALUM BEAD CAPACITORS:
35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.88, 1.0, 1.5 15p; 2.2, 3.3 18p; 4.7, 6.8 18p; 10, 22 20p; 33, 47 22p; 100 25p; 220 30p; 330 30p; 470 30p; 1000 35p; 1500 35p; 100 55p; 220 55p; 330 55p; 470 55p; 1000 55p; 1500 55p; 100 75p; 220 75p; 330 75p; 470 75p; 1000 75p; 1500 75p; 100 100p; 220 100p; 330 100p; 470 100p; 1000 100p; 1500 100p; 100 150p; 220 150p; 330 150p; 470 150p; 1000 150p; 1500 150p; 100 200p; 220 200p; 330 200p; 470 200p; 1000 200p; 1500 200p; 100 300p; 220 300p; 330 300p; 470 300p; 1000 300p; 1500 300p; 100 500p; 220 500p; 330 500p; 470 500p; 1000 500p; 1500 500p; 100 1000p; 220 1000p; 330 1000p; 470 1000p; 1000 1000p; 1500 1000p; 100 1500p; 220 1500p; 330 1500p; 470 1500p; 1000 1500p; 1500 1500p; 100 2000p; 220 2000p; 330 2000p; 470 2000p; 1000 2000p; 1500 2000p; 100 3000p; 220 3000p; 330 3000p; 470 3000p; 1000 3000p; 1500 3000p; 100 4000p; 220 4000p; 330 4000p; 470 4000p; 1000 4000p; 1500 4000p; 100 5000p; 220 5000p; 330 5000p; 470 5000p; 1000 5000p; 1500 5000p; 100 10000p; 220 10000p; 330 10000p; 470 10000p; 1000 10000p; 1500 10000p; 100 15000p; 220 15000p; 330 15000p; 470 15000p; 1000 15000p; 1500 15000p; 100 20000p; 220 20000p; 330 20000p; 470 20000p; 1000 20000p; 1500 20000p; 100 30000p; 220 30000p; 330 30000p; 470 30000p; 1000 30000p; 1500 30000p; 100 40000p; 220 40000p; 330 40000p; 470 40000p; 1000 40000p; 1500 40000p; 100 50000p; 220 50000p; 330 50000p; 470 50000p; 1000 50000p; 1500 50000p; 100 100000p; 220 100000p; 330 100000p; 470 100000p; 1000 100000p; 1500 100000p; 100 150000p; 220 150000p; 330 150000p; 470 150000p; 1000 150000p; 1500 150000p; 100 200000p; 220 200000p; 330 200000p; 470 200000p; 1000 200000p; 1500 200000p; 100 300000p; 220 300000p; 330 300000p; 470 300000p; 1000 300000p; 1500 300000p; 100 400000p; 220 400000p; 330 400000p; 470 400000p; 1000 400000p; 1500 400000p; 100 500000p; 220 500000p; 330 500000p; 470 500000p; 1000 500000p; 1500 500000p; 100 1000000p; 220 1000000p; 330 1000000p; 470 1000000p; 1000 1000000p; 1500 1000000p; 100 1500000p; 220 1500000p; 330 1500000p; 470 1500000p; 1000 1500000p; 1500 1500000p; 100 2000000p; 220 2000000p; 330 2000000p; 470 2000000p; 1000 2000000p; 1500 2000000p; 100 3000000p; 220 3000000p; 330 3000000p; 470 3000000p; 1000 3000000p; 1500 3000000p; 100 4000000p; 220 4000000p; 330 4000000p; 470 4000000p; 1000 4000000p; 1500 4000000p; 100 5000000p; 220 5000000p; 330 5000000p; 470 5000000p; 1000 5000000p; 1500 5000000p; 100 10000000p; 220 10000000p; 330 10000000p; 470 10000000p; 1000 10000000p; 1500 10000000p; 100 15000000p; 220 15000000p; 330 15000000p; 470 15000000p; 1000 15000000p; 1500 15000000p; 100 20000000p; 220 20000000p; 330 20000000p; 470 20000000p; 1000 20000000p; 1500 20000000p; 100 30000000p; 220 30000000p; 330 30000000p; 470 30000000p; 1000 30000000p; 1500 30000000p; 100 40000000p; 220 40000000p; 330 40000000p; 470 40000000p; 1000 40000000p; 1500 40000000p; 100 50000000p; 220 50000000p; 330 50000000p; 470 50000000p; 1000 50000000p; 1500 50000000p; 100 100000000p; 220 100000000p; 330 100000000p; 470 100000000p; 1000 100000000p; 1500 100000000p; 100 150000000p; 220 150000000p; 330 150000000p; 470 150000000p; 1000 150000000p; 1500 150000000p; 100 200000000p; 220 200000000p; 330 200000000p; 470 200000000p; 1000 200000000p; 1500 200000000p; 100 300000000p; 220 300000000p; 330 300000000p; 470 300000000p; 1000 300000000p; 1500 300000000p; 100 400000000p; 220 400000000p; 330 400000000p; 470 400000000p; 1000 400000000p; 1500 400000000p; 100 500000000p; 220 500000000p; 330 500000000p; 470 500000000p; 1000 500000000p; 1500 500000000p; 100 1000000000p; 220 1000000000p; 330 1000000000p; 470 1000000000p; 1000 1000000000p; 1500 1000000000p; 100 1500000000p; 220 1500000000p; 330 1500000000p; 470 1500000000p; 1000 1500000000p; 1500 1500000000p; 100 2000000000p; 220 2000000000p; 330 2000000000p; 470 2000000000p; 1000 2000000000p; 1500 2000000000p; 100 3000000000p; 220 3000000000p; 330 3000000000p; 470 3000000000p; 1000 3000000000p; 1500 3000000000p; 100 4000000000p; 220 4000000000p; 330 4000000000p; 470 4000000000p; 1000 4000000000p; 1500 4000000000p; 100 5000000000p; 220 5000000000p; 330 5000000000p; 470 5000000000p; 1000 5000000000p; 1500 5000000000p; 100 10000000000p; 220 10000000000p; 330 10000000000p; 470 10000000000p; 1000 10000000000p; 1500 10000000000p; 100 15000000000p; 220 15000000000p; 330 15000000000p; 470 15000000000p; 1000 15000000000p; 1500 15000000000p; 100 20000000000p; 220 20000000000p; 330 20000000000p; 470 20000000000p; 1000 20000000000p; 1500 20000000000p; 100 30000000000p; 220 30000000000p; 330 30000000000p; 470 30000000000p; 1000 30000000000p; 1500 30000000000p; 100 40000000000p; 220 40000000000p; 330 40000000000p; 470 40000000000p; 1000 40000000000p; 1500 40000000000p; 100 50000000000p; 220 50000000000p; 330 50000000000p; 470 50000000000p; 1000 50000000000p; 1500 50000000000p; 100 100000000000p; 220 100000000000p; 330 100000000000p; 470 100000000000p; 1000 100000000000p; 1500 100000000000p; 100 150000000000p; 220 150000000000p; 330 150000000000p; 470 150000000000p; 1000 150000000000p; 1500 150000000000p; 100 200000000000p; 220 200000000000p; 330 200000000000p; 470 200000000000p; 1000 200000000000p; 1500 200000000000p; 100 300000000000p; 220 300000000000p; 330 300000000000p; 470 300000000000p; 1000 300000000000p; 1500 300000000000p; 100 400000000000p; 220 400000000000p; 330 400000000000p; 470 400000000000p; 1000 400000000000p; 1500 400000000000p; 100 500000000000p; 220 500000000000p; 330 500000000000p; 470 500000000000p; 1000 500000000000p; 1500 500000000000p; 100 1000000000000p; 220 1000000000000p; 330 1000000000000p; 470 1000000000000p; 1000 1000000000000p; 1500 1000000000000p; 100 1500000000000p; 220 1500000000000p; 330 1500000000000p; 470 1500000000000p; 1000 1500000000000p; 1500 1500000000000p; 100 2000000000000p; 220 2000000000000p; 330 2000000000000p; 470 2000000000000p; 1000 2000000000000p; 1500 2000000000000p; 100 3000000000000p; 220 3000000000000p; 330 3000000000000p; 470 3000000000000p; 1000 3000000000000p; 1500 3000000000000p; 100 4000000000000p; 220 4000000000000p; 330 4000000000000p; 470 4000000000000p; 1000 4000000000000p; 1500 4000000000000p; 100 5000000000000p; 220 5000000000000p; 330 5000000000000p; 470 5000000000000p; 1000 5000000000000p; 1500 5000000000000p; 100 10000000000000p; 220 10000000000000p; 330 10000000000000p; 470 10000000000000p; 1000 10000000000000p; 1500 10000000000000p; 100 15000000000000p; 220 15000000000000p; 330 15000000000000p; 470 15000000000000p; 1000 15000000000000p; 1500 15000000000000p; 100 20000000000000p; 220 20000000000000p; 330 20000000000000p; 470 20000000000000p; 1000 20000000000000p; 1500 20000000000000p; 100 30000000000000p; 220 30000000000000p; 330 30000000000000p; 470 30000000000000p; 1000 30000000000000p; 1500 30000000000000p; 100 40000000000000p; 220 40000000000000p; 330 40000000000000p; 470 40000000000000p; 1000 40000000000000p; 1500 40000000000000p; 100 50000000000000p; 220 50000000000000p; 330 50000000000000p; 470 50000000000000p; 1000 50000000000000p; 1500 50000000000000p; 100 100000000000000p; 220 100000000000000p; 330 100000000000000p; 470 100000000000000p; 1000 100000000000000p; 1500 100000000000000p; 100 150000000000000p; 220 150000000000000p; 330 150000000000000p; 470 150000000000000p; 1000 150000000000000p; 1500 150000000000000p; 100 200000000000000p; 220 200000000000000p; 330 200000000000000p; 470 200000000000000p; 1000 200000000000000p; 1500 200000000000000p; 100 300000000000000p; 220 300000000000000p; 330 300000000000000p; 470 300000000000000p; 1000 300000000000000p; 1500 300000000000000p; 100 400000000000000p; 220 400000000000000p; 330 400000000000000p; 470 400000000000000p; 1000 400000000000000p; 1500 400000000000000p; 100 500000000000000p; 220 500000000000000p; 330 500000000000000p; 470 500000000000000p; 1000 500000000000000p; 1500 500000000000000p; 100 1000000000000000p; 220 1000000000000000p; 330 1000000000000000p; 470 1000000000000000p; 1000 1000000000000000p; 1500 1000000000000000p; 100 1500000000000000p; 220 1500000000000000p; 330 1500000000000000p; 470 1500000000000000p; 1000 1500000000000000p; 1500 1500000000000000p; 100 2000000000000000p; 220 2000000000000000p; 330 2000000000000000p; 470 2000000000000000p; 1000 2000000000000000p; 1500 2000000000000000p; 100 3000000000000000p; 220 3000000000000000p; 330 3000000000000000p; 470 3000000000000000p; 1000 3000000000000000p; 1500 3000000000000000p; 100 4000000000000000p; 220 4000000000000000p; 330 4000000000000000p; 470 4000000000000000p; 1000 4000000000000000p; 1500 4000000000000000p; 100 5000000000000000p; 220 5000000000000000p; 330 5000000000000000p; 470 5000000000000000p; 1000 5000000000000000p; 1500 5000000000000000p; 100 10000000000000000p; 220 10000000000000000p; 330 10000000000000000p; 470 10000000000000000p; 1000 10000000000000000p; 1500 10000000000000000p; 100 15000000000000000p; 220 15000000000000000p; 330 15000000000000000p; 470 15000000000000000p; 1000 15000000000000000p; 1500 15000000000000000p; 100 20000000000000000p; 220 20000000000000000p; 330 20000000000000000p; 470 20000000000000000p; 1000 20000000000000000p; 1500 20000000000000000p; 100 30000000000000000p; 220 30000000000000000p; 330 30000000000000000p; 470 30000000000000000p; 1000 30000000000000000p; 1500 30000000000000000p; 100 40000000000000000p; 220 40000000000000000p; 330 40000000000000000p; 470 40000000000000000p; 1000 40000000000000000p; 1500 40000000000000000p; 100 50000000000000000p; 220 50000000000000000p; 330 50000000000000000p; 470 50000000000000000p; 1000 50000000000000000p; 1500 50000000000000000p; 100 100000000000000000p; 220 100000000000000000p; 330 100000000000000000p; 470 100000000000000000p; 1000 100000000000000000p; 1500 100000000000000000p; 100 150000000000000000p; 220 150000000000000000p; 330 150000000000000000p; 470 150000000000000000p; 1000 150000000000000000p; 1500 150000000000000000p; 100 200000000000000000p; 220 200000000000000000p; 330 200000000000000000p; 470 200000000000000000p; 1000 200000000000000000p; 1500 200000000000000000p; 100 300000000000000000p; 220 300000000000000000p; 330 300000000000000000p; 470 300000000000000000p; 1000 300000000000000000p; 1500 300000000000000000p; 100 400000000000000000p; 220 400000000000000000p; 330 400000000000000000p; 470 400000000000000000p; 1000 400000000000000000p; 1500 400000000000000000p; 100 500000000000000000p; 220 500000000000000000p; 330 500000000000000000p; 470 500000000000000000p; 1000 500000000000000000p; 1500 500000000000000000p; 100 1000000000000000000p; 220 1000000000000000000p; 330 1000000000000000000p; 470 1000000000000000000p; 1000 1000000000000000000p; 1500 1000000000000000000p; 100 1500000000000

Move Towards Microcassettes

You may have heard of microcassettes being used in dictating machines. Hugh Davies looks at how they could come to compete with compact cassettes in hi-fi recording

During the last year, a revolution in miniature has been taking place in the recording tape industry over the smallest audio cassette of all — the microcassette. From the results of development work in Japan on metal-powder tapes, microcassettes are to become available for high-quality (if not high-fidelity) recording.

To put this in perspective, a microcassette is only half the size of the popular compact cassette (the compact cassette is 100 by 64 by 12 mm compared with only 50 by 30 by 8 mm for the microcassette).

Microcassettes are not new: Matsushita and Olympus, working closely together, produced the first one in 1974. That's over six years ago, so why the revolution? The reason is that it is only in the last few months that the tapes have had any claim to high-quality reproduction. Standard ferro (iron-oxide) microcassettes are only suitable for speech or medium-quality audio reproduction, and for this reason their use has been restricted to hand-held recorders suitable for use as miniature dictating machines.

During 1980, some of the leading Japanese tape recorder manufacturers, principally Matsushita and Sony, showed that microcassettes, using special metal-coated tape, were capable of producing high-quality sound, approaching the performance of 'metal' compact cassettes. (Metal-coated

tapes have a very high signal-to-noise ratio, and allow true hi-fi recording in cassette form.) Matsushita, for instance, has been working on its Angrom metal tape for microcassettes. The metal coating is evaporated onto a plastic base using what Peter Hamblin, Marketing Manager of Panasonic (part of Matsushita), described as 'a highly complex production process'. Playing time for this tape, he claimed, is 90 minutes/side at 2.4 cm/s (half the speed of a compact cassette), or 3 hours at 1.2 cm/s. (Most microcassette recorders offer both of these speeds.)

He said that a high-frequency (treble) response approaching 14 kHz was possible, although the problem of getting adequate low-frequency (bass) response had yet to be resolved.

The tapes look exciting, but what is there to play them on? The answer is very little — in the UK. It appears that because all the development work has taken place in Japan, all the really interesting machines are being held there for the time being. But that is not to say that the rest of the world has been left in suspense. It is understood that Sanyo demonstrated a mains-operated microcassette deck at the Hi-fi show in Dusseldorf, Germany as long ago as August 1980. Matsushita claims to have demonstrated a similar machine in the recent Tokyo exhibition. And Sony, which claims to hold 50% of the market for microcassette dictating machines, has also been active.

Microcassettes In the UK

Somehow, in the UK, we always seem to have to wait longer than everyone else for new ideas. It looks like being several months before high-quality or even hi-fi microcassettes and their recorders reach Britain. But meanwhile some of the currently-available minicassette 'hardware' using the standard tape is interesting in itself. Unlike compact cassettes, ferro and metal microcassettes can be played on the same machine *without any need for re-adjustment of recording bias*.

Microcassette recorders currently available in the UK are battery-powered and hand-held, and the playback quality of standard microcassettes is acceptable in such applications. Up till now, the machine market has obviously been dominated by Japanese manufacturers such as National Panasonic, Olympus, Sanyo, Sony and Sharp. But now the Dutch giant Philips has entered the market with two new recorders, with microcassettes compatible with the Japanese microcassettes to match. These products are due for release in March 1981. What is significant about this move is that it was Philips which produced the compact cassette back in the 60's, and it has ignored short-lived wonders such as 8-track and EL cassettes until microcassettes came along.

A Philips' spokesman told HE that: 'Phillips are not known to back losers' adding that the microcassette could take off as did its big brother the compact cassette.

Microcassette Construction

A microcassette is a truly scaled-down version of the compact 'cassette' because, like the compact cassette, the tape is moved by a pinch wheel (a similar mechanism is used on open-reel recorders). Thus the tape moves at a constant speed as it is transferred from one reel to the other.

Another type of cassette, slightly larger than the microcassette, is the *minicassette*. This has been used mainly in dictating machines such as those in Philips' Pocket Memo range, but because the tape drive is indirect (the tape is moved by rotation of one of the cassette sprockets), tape speed is not constant over its length. This method of drive is known as 'rim drive'.

Comparison of microcassette and compact cassette





Microcassette (left) and minicassette

Philips' D6700 and D6710

The D6710 is a hand-held microcassette recorder 130 by 65 by 24.8 mm with a built-in electret microphone. We tested a sample D6710 at HE and found the microphone to be extremely sensitive. You didn't have to clutch the machine to your mouth (as was necessary with a sample 0085 Pocket Memo we tried) but could, under quiet conditions, leave it on the table to record a conversation. Sound output, specified as being 0.22 W maximum, was quite adequate too, considering that the recorder runs from only 3 VDC, supplied by two HP7- or AA-sized cells. It is claimed by Philips that the energy requirements, compared with an equivalent compact cassette machine, are cut by more than 50% — starting, presumably, with the need for only two cells. (Compact cassette recorders, providing loudspeaker output, usually need four or six cells.) Sockets are provided for external 3 VDC supply, earphone/line output and microphone/line input.

Two standard playing speeds (1.2 and 2.4 cm/s) can be selected, and other features include a 'silent' tape stop, a three-digit counter and an automatic recording level control.

Price for the D6710 is estimated by Philips to be £64.95. A similar model, the D6700, is due for release around the same time and is likely to be about £10 cheaper. It will have no automatic tape stop, no counter and will have a cheaper finish. These two machines will enable Philips to 'test the market' for microcassettes.

Sanyo M5850

One combined microcassette recorder and FM/AM radio released a few months ago is the M5850FG from Sanyo. Although the radio section is restricted to VHF (88 to 108 MHz) and MW (525 to 1605 kHz) and it may lack the sensitivity and sound output of a similar-sized radio receiver, the microcassette section has the same functions as Philips' D6710. It runs from 4.5 VDC, supplied by three HP7- or AA-sized cells. A 'beat 1 and 2' switch is included to allow the erase oscillator frequency to be shifted should it produce a heterodyne note with an incoming radio signal. Apart from having a press-button dial light, indicators are provided for battery/power and recording.

If the D6710 costs you about £65 then the M5850FG will cost you around £25 more for the radio facility.

Approximate weight (with batteries) of the M5850FG is 450 g (1 lb) compared with 280 g (10.25 oz) for the D6710.

What Is To Come

The above machines are examples of what is available for microcassettes at present, but what about the future? Japanese companies are working to perfect metal tape to meet hi-fi standards, and present progress looks encouraging. What we are likely to see from equipment manufacturers are more miniature radio receiver/microcassette combinations, with the strong possibility of stereo versions appearing later this year. It is also likely that microcassette equipment will become available for use in the car.

When Sony was asked about its plans for microcassette hardware, it said that it had nothing comparable with Sanyo's microcassette radio/recorder at present. Sony would prefer to include long-waves with the MW and VHF wavebands on any microcassette radio recorder it introduced to the UK market. It is likely to concentrate only on recorders for the next 12 months. A new range of 'budget to top-end' recorders is planned for the Spring and Summer.

Meanwhile, at HE, we'll keep an eye on the progress of microcassettes and we aim to produce a feature article in a few months time on the cassettes and the equipment available for playing them.




Philips D6710 microcassette recorder, Sanyo M 5850FG microcassette recorder/radio and Philips 0085 pocket memo. Microcassette and minicassette tapes are shown side-by-side in the foreground

HE

TLTs by TEXAS 7400 11p 74293 150p 4020 110p 7400 60p 74298 200p 4022 110p 7401 12p 74385 100p 4023 27p 7402 12p 74386 100p 4024 27p 7403 14p 74387 100p 4025 20p 7404 14p 74388 100p 4026 130p 7405 18p 74390 200p 4027 50p 7406 36p 74393 200p 4028 84p 7407 36p 74490 225p 4029 100p 7408 17p 74LS SERIES 4030 55p 7409 15p 74LS02 16p 4031 200p 7410 15p 74LS02 16p 4034 200p 7411 24p 74LS03 18p 4035 110p 7412 20p 74LS04 16p 4036 295p 7413 30p 74LS05 25p 4040 100p 7414 40p 74LS06 22p 4041 80p 7415 30p 74LS09 20p 4041 80p 7416 27p 74LS10 20p 4042 80p 7417 27p 74LS11 20p 4043 90p 7420 17p 74LS13 40p 4044 90p 7421 40p 74LS14 50p 4048 110p 7422 22p 74LS20 20p 4047 100p 7423 34p 74LS21 40p 4048 55p 7425 30p 74LS27 38p 4049 45p 7426 40p 74LS30 20p 4050 45p 7427 34p 74LS32 27p 4051 80p 7428 34p 74LS37 27p 4052 80p 7430 17p 74LS38 38p 4053 80p 7432 30p 74LS42 70p 4054 150p 7433 40p 74LS47 75p 4055 125p 7437 35p 74LS51 24p 4056 135p 7438 35p 74LS55 30p 4059 60p 7440 170p 74LS57 27p 4060 115p 7441 70p 74LS74 27p 4063 110p 7442A 60p 74LS75 36p 4066 50p 7443 112p 74LS76 45p 4067 45p 7444 112p 74LS83 70p 4069 27p 7445 100p 74LS85 70p 4070 27p 7446 75p 74LS90 40p 4071 25p 7448 75p 74LS92 70p 4072 25p 7450 17p 74LS93 60p 4073 25p 7451 17p 74LS96 60p 4074 25p 7453 17p 74LS107 45p 4076 107p 7454 17p 74LS109 80p 4081 27p 7460 17p 74LS112 40p 4082 27p 7470 36p 74LS113 90p 4086 72p 7472 36p 74LS114 45p 4093 70p 7473 34p 74LS122 60p 4094 250p 7474 30p 74LS123 60p 4094 250p 7475 38p 74LS124 180p 4095 95p 7476 32p 74LS125 50p 4096 95p 7480 50p 74LS126 50p 4098 120p 7481 100p 74LS130 30p 4099 200p 7482 84p 74LS133 30p 4099 200p 7483A 90p 74LS136 55p 40100 220p 7484 100p 74LS138 65p 40101 132p 7485 110p 74LS139 75p 40102 180p 7486 34p 74LS145 20p 40104 95p 7489 210p 74LS146 220p 40104 95p 7490A 30p 74LS148 175p 40105 120p 7491 80p 74LS151 80p 40106 90p 7492A 46p 74LS153 50p 40107 60p 7493A 36p 74LS154 200p 40108 40p 7494 84p 74LS155 80p 40109 100p 7495A 70p 74LS156 80p 40110 300p 7496 65p 74LS157 60p 40114 250p 7497 180p 74LS158 60p 4052 120p 74100 130p 74LS160 90p 4503 70p 74107 34p 74LS162 140p 4508 290p 74109 55p 74LS162 140p 4508 290p 74116 200p 74LS163 100p 4510 90p 74118 130p 74LS164 90p 4511 120p 74119 210p 74LS166 140p 4512 80p 74120 110p 74LS166 180p 4512 80p 74121 34p 74LS173 100p 4515 300p 74122 48p 74LS174 100p 4516 110p 74123 60p 74LS175 100p 4518 100p 74125 75p 74LS181 320p 4520 100p 74126 60p 74LS190 100p 4521 250p 74128 75p 74LS191 100p 4521 250p 74132 75p 74LS192 100p 4527 150p 74136 75p 74LS193 100p 4528 100p 74137 50p 74LS195 140p 4532 140p 74142 200p 74LS196 120p 4534 550p 74145 90p 74LS197 90p 4538 375p 74147 190p 74LS204 175p 4543 180p 74148 150p 74LS241 175p 4553 320p 74150 130p 74LS242 170p 4556 72p 74151A 70p 74LS243 170p 4560 200p 74152 34p 74LS244 150p 4569 250p 74154 120p 74LS245 250p 4572 40p 74155 90p 74LS247 140p 4583 110p 74156 90p 74LS251 140p 4584 90p 74157 70p 74LS253 90p 4585 150p 74159 190p 74LS257 60p 4587 90p 74160 100p 74LS258 160p 40097 90p 74161 100p 74LS259 160p 14411 1100p 74162 100p 74LS266 100p 14412 1100p 74163 100p 74LS273 170p 14433 1100p 74164 20p 74LS285 80p 14434 100p 74165 130p 74LS283 90p 14599 290p 74166 120p 74LS298 160p 14599 290p 74167 200p 74LS323 400p ADS36A ICs 74170 240p 74LS324 200p ADS16J 1400p 74172 450p 74LS325 200p AD732A 600p 74173 120p 74LS385 80p DM8123 175p 74174 90p 74LS367 70p DM8131 375p 74175 85p 74LS368 100p DPR304 450p 74176 90p 74LS373 150p DS8835 250p 74177 90p 74LS375 150p DS8836 150p 74178 160p 74LS377 160p MCL488 75p 74180 93p 74LS377 160p MCL488 75p 74181 160p 74LS378 140p MCL489 75p 74182 90p 74LS390 120p MC3446 300p 74185 150p 74LS393 120p 25510 350p 74186 500p 74LS445 400p 75107 160p 74188 325p 74LS670 400p 75150 175p 74190 120p 4000 SERIES 75154 175p 74192 120p 4000 SERIES 75182 230p 74193 100p 4001 22p 75322 300p 74194 120p 4006 95p 75324 375p 74195 95p 4007 20p 75363 400p 74196 80p 4008 80p 75385 200p 74198 400p 4009 40p 75451 2 72p 74199 150p 4010 80p 75491 2 70p 74201 160p 4012 25p 8776 160p 74251 140p 4013 50p 8195 180p 74259 250p 4014 84p 8797 160p 74278 290p 4015 84p 81LS95 120p 74283 140p 4017 70p 81LS96 140p 74284 360p 4018 89p 81LS98 140p 74285 360p 4019 45p 9602 220p				93 SERIES 9301 160p 74500 60p 74S114 120p 9302 175p 74504 60p 74S124 300p 9306 316p 74508 75p 74S132 160p 9310 275p 74508 75p 74S133 75p 9311 275p 74510 60p 74S138 225p 9312 160p 74520 60p 74S139 225p 9314 165p 74530 60p 74S157 250p 9316 225p 74532 80p 74S174 250p 9321 225p 74537 90p 74S175 320p 9322 150p 74564 60p 74S194 350p 9334 360p 74574 90p 74S241 450p 9368 250p 74585 300p 74S242 60p 9370 300p 74586 120p 74S373 500p 9374 200p 745112 120p 74S374 500p				74S SERIES 74S114 120p 74S124 300p 74S132 160p 74S133 75p 74S138 225p 74S139 225p 74S157 250p 74S174 250p 74S175 320p 74S194 350p 74S241 450p 74S242 60p 74S373 500p 74S374 500p				TRANSISTORS AC126 25p AC127/8 25p AC176 25p AC177/8 25p AF116 50p AD149 70p AD161/2 45p AU107 200p BC107/8 11p BC109 11p BC117 20p BC147/8 9p BC149 10p BC157/8 10p BC184 11p BC189 12p BC192 12p BC177/8 17p BC179 18p BC182/3 10p BC184 11p BC187 30p BC212/3 11p BC214 12p BC237 15p BC239 15p BC337 16p BC338 16p BC481 36p BC477/8 30p BC517/8 40p BC547/8 16p BC548 18p BC557 18p BCY103/4 50p BD31/2 22p BD37/1 50p BD135/6 54p BD139 56p BD189 60p BD232 95p BD233 75p BD235 85p BD241 70p BD247 60p BDY56 200p BF200 32p BF244 35p BF258 70p BF257/8 32p BFY103/4 50p BFY109 25p				BFR40 25p BFR41 25p BFR79 25p BFR80 25p BFR21 25p BFR29 40p BFX30 34p BFX84/5 40p BFX87 30p BFX88 30p BFY10 90p BFY50 30p BFY51/2 30p BFY56 35p BFY90 90p BR39 33p BSX19/20 20p BU104 225p BU105 190p BU108 250p BU109 225p BU126 150p BU180A 120p BU205 200p BU208 200p BU406 145p E300 50p E308 50p E310 50p MJ2501 225p MJ2955 18p MJ301 225p MJ340 50p MJE2955 100p MJE3055 70p MPF102 45p MPF103/4 50p MPF105/6 40p MP56531 50p MP56534 50p MPSA06 30p MPSA12 30p MPSA20 50p MPSA42 50p MPSA43 50p MPSA45 50p MPSA56 32p MPSA70 30p MPSU06 63p MPSU07 63p MPSU45 78p MPSU65 78p OC128 30p OC35 130p TIP29A 40p TIP29C 55p				TIP30A 48p TIP30C 60p TIP31A 85p TIP31C 82p TIP32A 68p TIP32C 82p TIP33A 90p TIP33C 114p TIP34A 110p TIP34S 120p TIP35A 225p TIP35C 270p TIP36A 290p TIP36C 340p TIP37A 300p TIP41C 70p TIP42A 70p TIP42C 82p TIP54 160p TIP122 130p TIP142 130p TIP2955 78p TIP4055 78p TIP2958 145p TISB3 30p TX108 12p TX300 13p TX500 15p TX5172 27p TX519 90p TX501 90p TX5194 90p TX5245 45p TX5296 55p TX5401 50p TX5457 45p TX5459 40p TX5484 60p TX5485 44p TX5490 27p TX5492 27p TX5493 27p TX5494 27p TX5495 27p TX5496 27p TX5497 27p TX5498 27p TX5499 27p TX5500 27p TX5501 27p TX5502 27p TX5503 27p TX5504 27p TX5505 27p TX5506 27p TX5507 27p TX5508 27p TX5509 27p TX5510 27p TX5511 27p TX5512 27p TX5513 27p TX5514 27p TX5515 27p TX5516 27p TX5517 27p TX5518 27p TX5519 27p TX5520 27p TX5521 27p TX5522 27p TX5523 27p TX5524 27p TX5525 27p TX5526 27p TX5527 27p TX5528 27p TX5529 27p TX5530 27p TX5531 27p TX5532 27p TX5533 27p TX5534 27p TX5535 27p TX5536 27p TX5537 27p TX5538 27p TX5539 27p TX5540 27p TX5541 27p TX5542 27p TX5543 27p TX5544 27p TX5545 27p TX5546 27p TX5547 27p TX5548 27p TX5549 27p TX5550 27p				3N204 120p 40290 250p 40360 40p 40361/2 75p 40364 120p 40408 90p 40409 100p 40410 100p 40411 300p 40594 120p 40595 120p 40673 75p 40841 90p 40871/2 100p 40872 100p BY127 12p BY336-300 27p CA4 9p OA81 15p OA85 15p OA90 9p OA91 9p OA95 9p 2N4123/4 18p 2N4125/6 18p 2N4407/3 27p 2N4547 45p 2N4871 60p 2N5087 27p 2N5089 27p 2N5172 27p 2N519 90p 2N5194 90p 2N5245 45p 2N5296 55p 2N5401 50p 2N5457 45p 2N708 30p 2N918 45p 2N930 18p 2N1131/2 38p 2N6027 48p 2N1711 25p 2N2102 70p 2N2160 350p 2N2219A 30p 2N2222A 30p 2N2329A 30p 2N2484 30p 2N2646 45p 2N2904/5 30p 2N2906A 30p 2N2907A 30p 2N2926 9p 2N3053 40p 2N3054 65p 2N3055 48p 2N3442 140p 2N3563 240p 2N3585 30p 2N3584 250p 2N3643/4 48p 2N3703/3 12p 2N3704/5 12p 2N3706/7 14p 2N3708/9 12p 2N3773 300p 2N3819 25p 2N3820 50p 2N3823 70p 2N3866 90p 2N3902 70p 2N3903/4 18p 2N3905/6 20p 2N4037 65p 2N4038 65p 2N4060 12p 2N4061/2 18p 2N4123/4 18p 2N4125/6 18p 2N4407/3 27p 2N4547 45p 2N4871 60p 2N5087 27p 2N5089 27p 2N5172 27p 2N519 90p 2N5194 90p 2N5245 45p 2N5296 55p 2N5401 50p 2N5457 45p 2N708 30p 2N918 45p 2N930 18p 2N1131/2 38p 2N6027 48p 2N1711 25p 2N2102 70p 2N2160 350p 2N2219A 30p 2N2222A 30p 2N2329A 30p 2N2484 30p 2N2646 45p 2N2904/5 30p 2N2906A 30p 2N2907A 30p 2N2926 9p 2N3053 40p 2N3054 65p 3N201 110p				6A 50V 80p 6A 100V 100p 6A 400V 120p 10A 400V 200p 25A 400V 400p ZENERS 2 7V 33V 160p 400mW 9p 1W 15p TRIACS PLASTIC 3A 400V 60p 6A 400V 70p 6A 500V 88p 6A 400V 75p 8A 500V 95p 12A 400V 85p 12A 500V 105p 16A 400V 110p 16A 500V 130p T2800D 130p THYRISTORS 1A 50V 70p 1A 400V 90p 1A 400V 100p 6A 600V 140p 12A 400V 160p 16A 100V 160p 16A 400V 180p BT106 110p CI160 45p MCR101 36p TIC44 27p 2N3525 130p 2N4444 140p 2N5060 34p 2N5064 40p LOUD-SPEAKERS 1A 100V 20p 1A 100V 25p 1A 600V 30p 2A 50V 30p 2A 100V 35p 2A 400V 45p 3A 200V 60p 3A 600V 72p 4A 100V 95p 4A 400V 100p ZERO INSERTION FORCE BKT 24 pin 67 HEADER PLUGS 14 pin 50p 16 pin 80p 16 pin 100p 16 pin 275p SOFTY: Ideal Software/Hardware Development Tool. Using SOFTY you can develop your Programmes, Debug/Verify and then commit them to EPROM KIT £100 BUILT AND TESTED £125 Also available Expansion Board for Programming single floppy (+5V) EPROMS. Ready built £40 MINI FLOPPY DISC DRIVE MECHANISM Tead Type FD-50A 40 track 5 1/4" Double/Single Density drives £140 FLOPPY DISC CONTROLLER: FD1771 £24, FD1791 £36, FD1691 £15, 2143 £5.50. EPROM ERASERS: Type UV140. Will erase up to 14 EPROMS in approx. 20 mins. Has slide-in tray for safe use. MAINS and ERASE INSTRUCTIONS £61.50 NANOCOMP MICROPROCESSOR TRAINER. As described in WW, January 1981. A complete kit of parts available (excluding PCB and the case). The kit includes pre-programmed 2716, sockets for all ICs and PSU parts as well. Price £54 inc. VAT and P&P. VEROBOARDS D1 2.5x3.75" (copper 65p) 7.0MHz 300p 7.168MHz 300p 8.0MHz 300p 8.8MHz 300p 10.0MHz 300p 10.7MHz 300p 12.0MHz 350p 16.0MHz 350p 18.0MHz 300p 18.432MHz 325p 2.0MHz 325p 2.45760MHz 325p 3.276MHz 300p 3.579MHz 175p 4.0MHz 250p 4.194MHz 290p 4.43MHz 125p 5.0MHz 325p 6.0MHz 300p 6.144MHz 300p 7.0MHz 300p 7.168MHz 300p 8.0MHz 300p 8.8MHz 300p 10.0MHz 300p 10.7MHz 300p 12.0MHz 350p 16.0MHz 350p 18.0MHz 300p 18.432MHz 325p 19.68MHz 390p 26.690MHz 350p 27.145MHz 325p 38.666MHz 350p 48.0MHz 300p 55.5MHz 400p 116.0MHz 350p ANTX SOLDERING IRONS C-15W 415p CX-17W 425p CCN-15W 440p X25 SPARE BITS Spot of 100s 50p Pin cutter 80p Pin insertion tool 110p Vero Wring Pen 200p CFX/CCN SPARE ELEMENTS C/CX/X25 180p CCN 200p COUNTERS 74C925 550p 74C926 550p ICM7216B 2000p ICM7217A 850p ZN1040E 700p TTL & ECL MC4024 325p MC4044 325p 10116 350p 10231 350p			
---	--	--	--	--	--	--	--	---	--	--	--	--	--	--	--	---	--	--	--	---	--	--	--	--	--	--	--	---	--	--	--

Public Address Amplifier

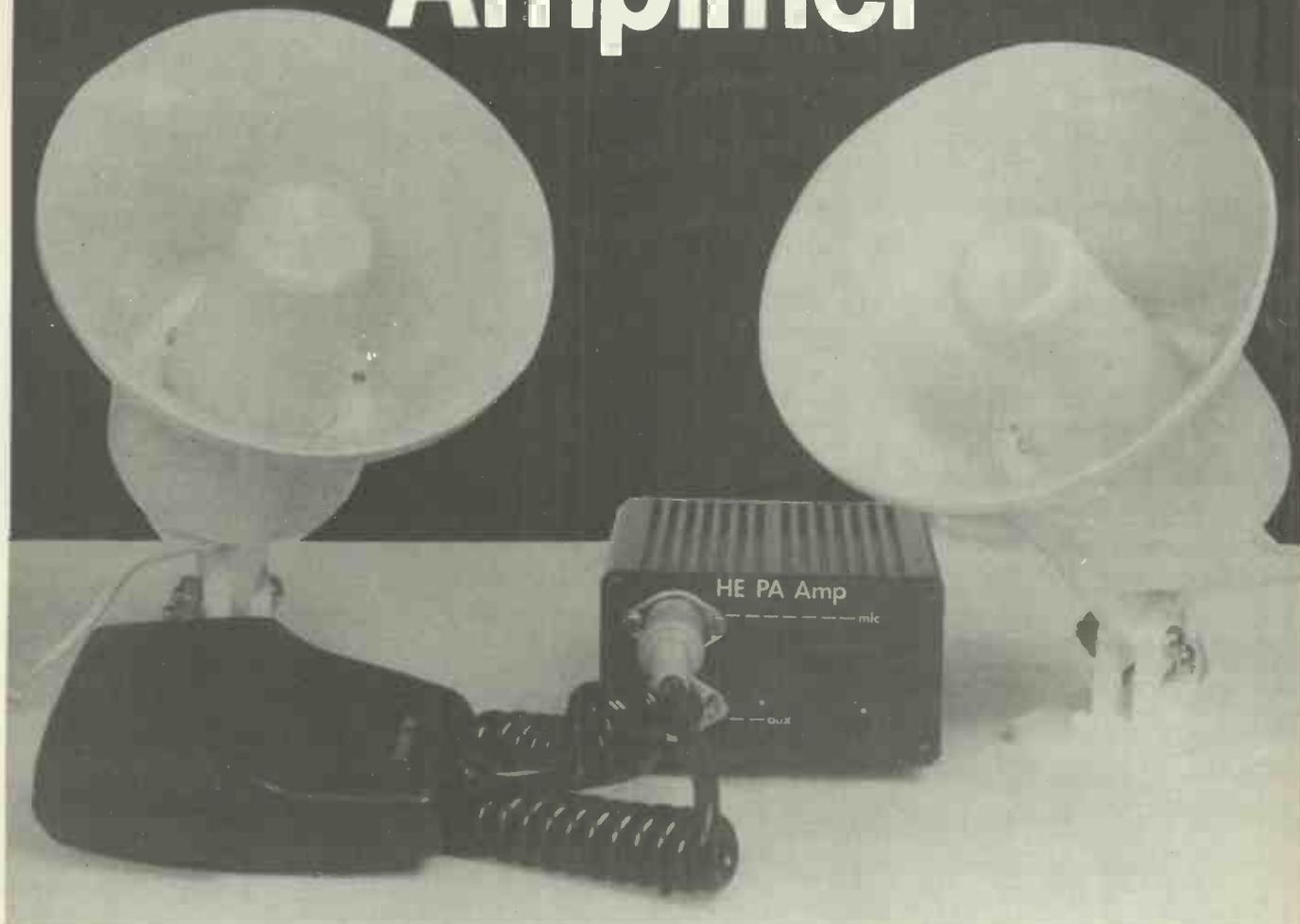

Make yourself heard above the crowd with this high-power, battery-operated, low-cost amplifier — ideal for any public gathering. A kit is available at a special-offer price

SPRING IS THE TIME of year when fêtes, fairs, garden parties and other outside gatherings start to be organised, so we reckoned that now was the time to launch this project to help defeat the problem of trying to address *every* member of a large crowd. You won't have to shout your voice hoarse anymore once you've built the HE Public Address Amplifier because with suitable horn speakers and a microphone (see Buylines for a suggested source) your voice will be lifted above the merry throng to an almost ear-piercing level.

A simple circuit provides 18 watts RMS into 4R-impedance speakers, the

supply being a standard 12 V car battery. Power also can be taken directly from a nearby car's electrical circuit, say by plugging into the lighter socket. Alternatively a 240 V operated 12 V power supply can be used if you have access to mains.

There are two inputs — for a microphone and an auxiliary line — each with an individual volume control to allow mixing of voice with, say, background music or a guitar or other instrument.

Based around an IC, the HA1388, the whole circuit is constructed neatly on Veroboard which can then be built into a 100 mm Sink Box. Way back in

July 1980 you may remember that we used both the HA1388 and the Sink Box in our popular Car Booster amplifier. The IC provides a high-power audio output, with a low-voltage power supply and the box provides a rugged housing — both are ideal for car or mobile use.

Construction

Take extreme care when building up your project. We show details for Veroboard but there is nothing to stop you designing your own PCB if you want a smaller board: just remember that parts of the circuit require large

amounts of current so keep the tracks wide. If you use Veroboard make all track breaks first in the usual way and then solder in the links.

Insert and solder all components, resistors first, followed by capacitors and finally semiconductors, leaving IC1 till last. Figure 1 shows the insertion details of IC1. Unusually, it is

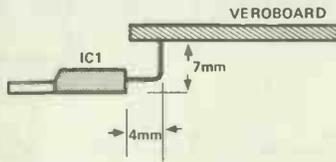


Figure 1. Correct mounting procedure for IC1, below the board.

mounted *underneath* the board and needs to be the correct distance from it, as shown. This positions the IC in the correct place for bolting it onto the underneath of the case so that the metal surface of the Sink Box can act as a heatsink and dissipate the large amount of heat which the IC generates at full output. You must take care when mounting the chip on board to ensure you don't damage it. That finishes construction of the

Veroboard itself, although if you wish you can use connecting pins to help when making the off-board connections.

Next comes the job of fixing the board into the case. The box is all metal of course, and so the underneath of the Veroboard needs to be insulated from it, by glueing two small strips of paxolin or plastic to the case bottom. Also, two similar pieces can be glued to the sides thus providing a guide rail for the board to slide into. Two bolt holes should be drilled to enable the IC to be fastened down. No insulation measures need to be taken here as the metal plate on the back of the IC is internally connected to 0 V, thus the whole box will be at this potential. (This is a point you should bear in mind if your vehicle is of the positive-earth type. If so, insulate the box from the car chassis rather than the IC from the box).

Mark and drill the two end panels for input and output sockets, potentiometers and power cable and then fit all controls and sockets ready for final wiring-up. Carefully follow the details in Fig.2 and solder all connections. Note that screened cable should be used at the input.

Parts List

RESISTORS (All 1/4 W, 5%)

R1,5	100k
R2,6,8,9	47k
R3,7	4k7
R4	220k
R10,11	2R2

POTENTIOMETERS

RV1	100k logarithmic with single-pole, single-throw switch
RV2	100k logarithmic potentiometer

CAPACITORS


C1,2,13,14	100n polyester
C3,5	220n polyester
C4	10u, 16 V
C6,9	100u, 6 V
C7	100u, 16 V
C10,11	100u, 10 V
C8	47u, 6 V
C12	2200u, 16 V

SEMICONDUCTORS

IC1	HA1388, power amplifier
Q1	BC184 NPN transistor
D1	1N5401, 3 A diode

MISCELLANEOUS

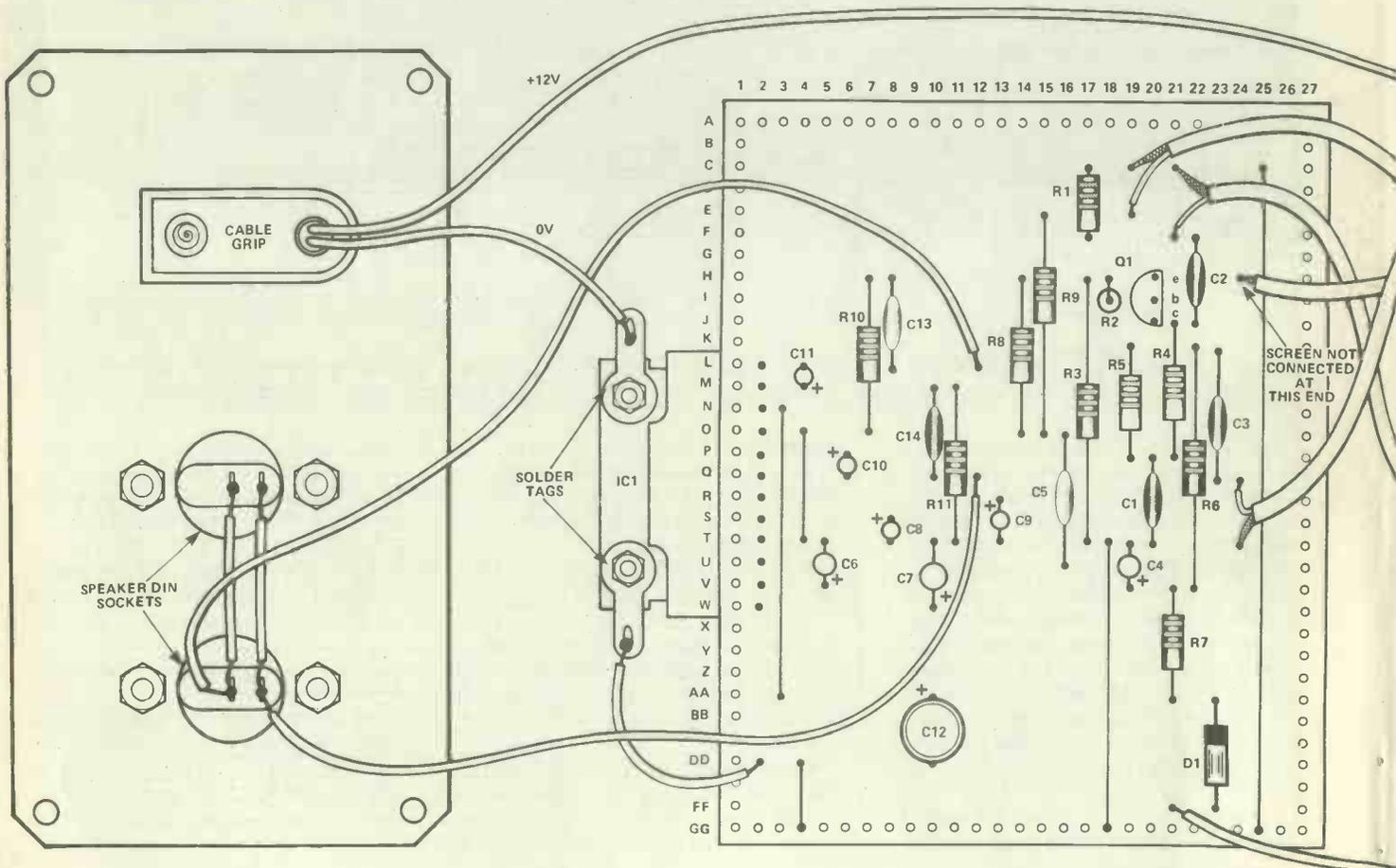Case to suit (see Buylines)
Knobs
2 x 5-pin, 180° DIN sockets
2 x speaker DIN sockets
Cable grip, in-line fuse holder + 3 A fuse
27 hole x 33 strip 0.1" Veroboard
Microphone and speakers to suit (see Buylines)



Note also that fairly heavy-gauge cable is necessary for the power and output connection because a lot of current will be flowing through them at times. Use of fine-gauge wire will result in loss of power and possible audible instability. Use sleeving, if you have any, to cover all soldered connections thus helping to prevent short circuits.

Finally make sure you connect an in-line fuseholder with a 3 A slow-blow fuse in the power lead, then if things *do* go wrong with all this current flowing around, damage to the circuit can be avoided.

From this photograph of the back of the Sink Box you can see how IC1 is bolted to the bottom of the case. This provides both excellent heatsinking and a good earth point for the solder tags



How It Works

Integrated circuit IC1, the HA1388 is a high-gain, high-output power amplifier which requires a low-voltage power supply of 8 to 18 VDC maximum to operate. Maximum output power is 18 watts RMS at 13.2 VDC, this being the approximate voltage present in a car electrical system. The IC will drive a speaker/speaker system of 4R minimum impedance with full power output.

Sensitivity of the amplifier is exceptionally good, only a few mV at its input terminal (pin 3) being required to drive the output to full power. It also has a reasonably high input impedance which

enables it to be driven directly from most signal sources.

The signal from a microphone is amplified by Q1 and associated components R1 to 7, C1 to 4, by a factor of 10 so it is about the same amplitude as the line input signal (auxiliary) from say, a cassette player or even an electric guitar. Both input signals are then mixed by RV1 and RV2 and applied to the main amplifier IC.

Diode D1 is in circuit to ensure that no damage will occur if power is inadvertently connected in reverse and capacitor C12 helps to smooth out the many voltage fluctuations which often are inherent in mobile applications.

HE

Buylines


The only two out-of-the-ordinary parts for this project are the main IC and the case. The HA1388 is now available from a number of sources, Ambit International, Technomatic etc and the Sink Box comes from West Hyde.

Special Offer Kit


If you wish to buy all parts for the Public Address Amplifier together, Magenta Electronics will supply everything (case, Veroboard, pots, knobs, components etc.) down to the last nut and bolt, for the special offer price of £16.56 inc VAT. Please add p&p at a standard rate of 40p.

We also obtained our two rear-entrant horn speakers and the hand mike from Magenta. The speakers cost £6.83 each and the mike is priced at £4.40. Remember the 40p standard charge for p&p applies whatever the total cost of your order.

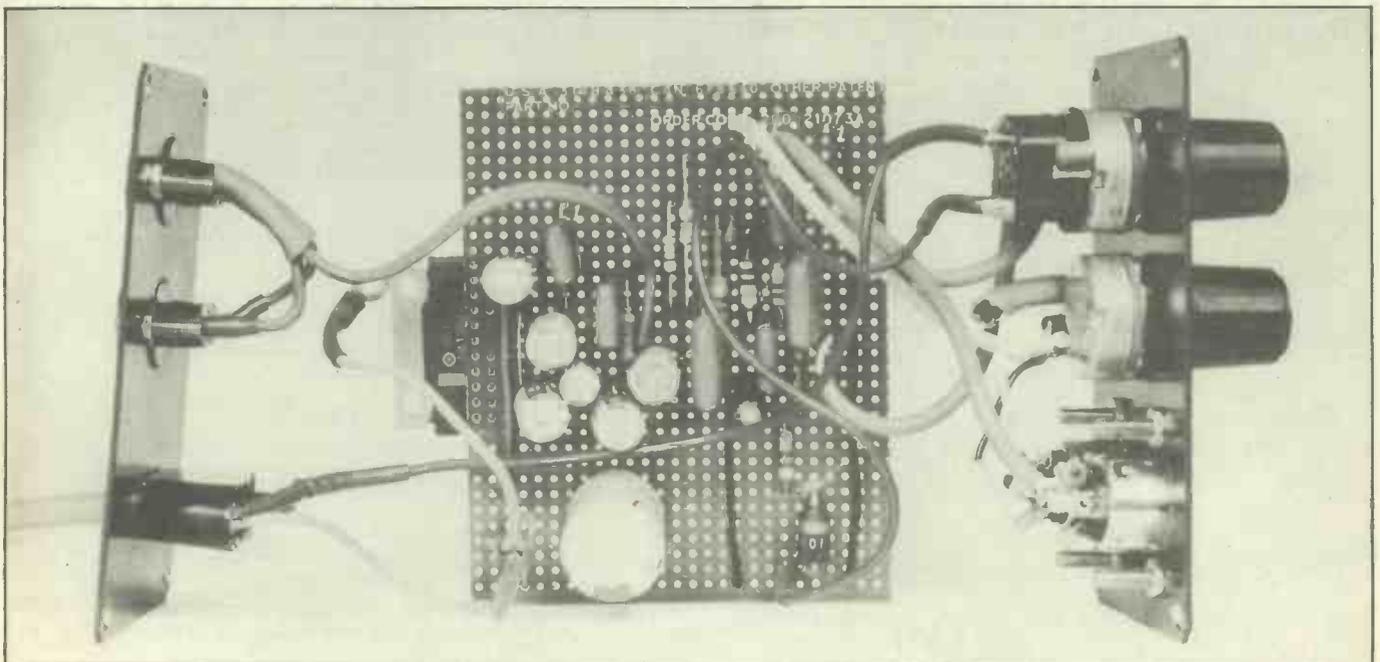Below you can see the insides of the HE Public Address Amplifier. Keep the wiring as neat as you can and use sleeving at connection points




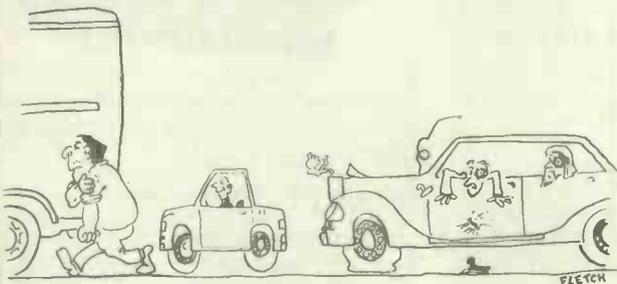Example of HE Public Address Amplifier in use



BUILDING YOUR OWN HI-FI SYSTEM?

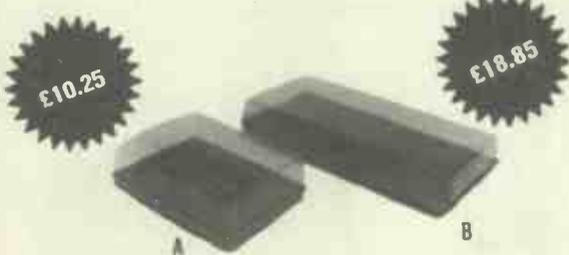GET A PROFESSIONAL FINISH TO YOUR OWN TAILOR-MADE SYSTEM BY PURCHASING A SMOKED ACRYLIC LIFT-OFF LID WITH CONTRASTING BLACK ABS LEATHER GRAINED BASE DIRECT FROM THE MANUFACTURER BY POST.



INTERNAL SIZES:

MODEL A
Lid: 17 3/4" x 12 1/2" x 3 3/4"
TAPERING TO 3"
Base: 17 3/4" x 12 1/2" x 3"

MODEL B
Lid: 31 1/2" x 14 3/8" x 3 1/2"
Base: 31 1/2" x 14 3/8" x 2 3/8"

State model required and send cheque or P.O. for the amount quoted (VAT & Postage paid) to:

TAURUS PLASTICS LTD. 2 CHARLES ST. WALSALL WEST MIDLANDS

BIORHYTHMS ARE BACK!

With just about everything else except the kitchen sink

CASIO BQ-1100 BIOLATOR/WATCH



Clock, calculator, 2 alarms, countdown alarm stopwatch, time memory, three date memories, biorhythm and date calculations, calculator. Clock: Hours, minutes, seconds, am/pm. Day/date. Universal calendar. Pre-programmed 1901 to 2099. Day, date, month and year display. Alarm. Two separate alarms. 24-hour system. Countdown alarm. 1/10 second to 24 hours, or Stopwatch 1/10 second to 24 hours. Net times, or Time memory. Dual time facility. 24-hour system. Calculator. 8 digits. Full memory. Sq roots, %. Date calculations. Any monthly calendar from 1901 to 2099 can be displayed and utilised. Biorhythm calculations. Forecast your physical, emotional and intellectual performance potential. Chart your peak, ebb and critical days and reschedule to avoid mistakes. Two silver oxide batteries last approx 1 year. Dims: 1/4 x 2.7/16 x 4 1/4 inches. Leatherette wallet.

ALL THIS FOR ONLY £14.95

CASIO'S AMAZING NEW FX-3500P

Statistical regression and integrals. Non-volatile memories and stores.

38 functional (non-volatile) steps. 2 programme storage capability. Unconditional and conditional jumps. 7 (non-volatile) memories; one independent, 8 constant memories. 18 pairs of parentheses, nestable in 6 levels.

61 built-in functions, including: Integrals (Simpson's rule). Linear regression, logarithmic regression, exponential regression and power regression.

Hyperbolic, sexagesimal and co-ordinates conversions. 10 digit mantissa or 10+2 exponent. Two silver oxide batteries give approximately 1,000 hours continuous use with power-saving automatic cut-off, with data and memory protection.

Dims: 9/32 x 2 1/8 x 5 1/4 inches. Supplied with leatherette wallet.

ALL THIS FOR ONLY £22.95



FX180P. Hand held version without hyperbolic. 2 x AA batteries, 3/4x3x5/8" £19.95
FX-2700P. As FX3500P but 8+2; without integrals, regression, 1 program £19.95
New melody alarm clock calculators. ML2000 £22.95, UC360 £19.95, UC365 £19.95.

★ star buy for 1981 ★ Our best selling watch

With around 40 functions

LCD ANALOGUE/DIGITAL

Alarm Chronograph with countdown

Analogue. Independent hours K d minutes with synchronous digital seconds. Dual time ability.
Digital. Hours, minutes, seconds, day and date.
Stopwatch. 1/100 second to 12 hours. Net lap and 1st and 2nd place. Start/stop and 10 minute signals.
Alarm. For 30 seconds with carousel display.
Countdown Alarm. Normal and net times to 1 hour with amazing "Star Burst" flashing display.
Time Signal. Half-hourly and hourly chimes. Tone control. Lithium battery. Light. Water-resistant case. 8.65mm thick. Mineral glass.



AA81
Analogue
Display

AA82
Digital
Display

AA81 Chrome plated £29.95

AA81G Gold plated £49.95

AA82 Stainless Steel £39.95

12 MELODY ALARM CHRONOGRAPHS with countdown alarm. M-12 resin case/strap £24.95. M1200 all stainless steel £29.95

100 METRE WATER RESISTANT Alarm chronographs with countdown alarm. W100. Resin case/strap £19.95. W150C Stainless steel case/resin strap. £25.95. W150B Stainless steel case/bracelet £32.50.

CASIOTONE KEYBOARDS. New model: CT 301 14 Instruments and 16 rhythm voices (RRP £325) £275. CT201 £245. M10 £89.

SEIKO. New Calculator watch/stopwatch/Five alarms. £69.95.

Send 25p for our illustrated catalogue of Casio and Seiko

PRICES

Include VAT and post and packing. Remember, we will beat any lower advertised price by 5% providing the advertiser has stocks and we still make a small profit! Just send details and your remittance for the lower amount.

Send cheques, PO or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. HE, Beaumont Centre, 164-167 East Road, Cambridge, CB1 1DB. Tel: 0223 312866.

The Beginnings of Real TV

Modern TV has origins dating back to the last century. Ian Sinclair traces some of the surprising milestones on the way

Try asking a number of people if they know who invented TV. If they come up with a name at all, it certainly won't be the name of any of the true pioneers of television as we know it today. Would you yourself recognise the names of Nipkow, Rosing or Campbell-Swinton? As we'll see, no one man invented TV but of all the contenders, Campbell-Swinton comes nearest to being the inventor of the system we know, even though the technology of the day was unable to permit him to demonstrate how correct his ideas were.

Let's look, then, at the long chain of events which shaped the TV system of today and the men whose efforts made it all possible. We could start with Berzelius in 1817, whose discovery of selenium introduced the first photoconductive element to us. Alternatively, we could choose Becquerel who investigated photovoltaic cells in 1839 and, incidentally, also discovered radioactivity. Probably the best start, though, is in 1873 with the first engineering advances, as distinct from purely scientific discoveries. In that year, the telegraph engineer, Willoughby Smith, published brief details of a remarkable discovery — that selenium was photoconductive. Selenium had been known since Berzelius' discovery of it in 1817, but it had not been put to any practical uses. Berzelius had noted that it conducted electricity, though very poorly: so that his discovery ranks as the first discovery of a semiconductor. Willoughby-Smith's interest was in using selenium to make high-resistance values for use in measuring instruments. His assistant had noticed that these instruments gave different readings as the light falling on them varied, and had gone on to discover

that the resistance of selenium decreased when the material was exposed to light.

Selenium In Image Transmission

At this time, Graham Bell was working on the device which he was to announce in 1875 — the telephone. The two ideas prompted many inventors to put forward ideas for devices which would transmit images over telephone lines, facsimile transmission as we call it today. One scheme, devised by Carey in 1875 was for a large set of selenium cells linked to a corresponding set of electric lights by cables. It would probably have worked, but needed a large number of parallel lines, one for each cell. An alternative idea which he suggested used only a single wire for transmission, and included, for the first time, the principle of scanning the cells at the 'transmitter'. The scanning mechanism was clockwork, and though the transmitter could have worked, there was no way of syn-

chronising the receiver so that it would correctly 'unscramble' the information coming over the wire.

Need For Scanning

A working model of a facsimile machine was demonstrated in 1881, by Selford Bidwell, to the Royal Institution in London. The transmitter used a single selenium cell, and the image was formed by a pinhole in one end of the box containing the selenium cell. The position of the pinhole could be varied by a set of cams, so scanning different parts of the image in turn over the selenium cell. At the receiver, a picture was re-constituted by electrochemical action using paper moistened with chemicals which changed colour when a current passed through them. It worked — but the synchronisation was purely mechanical — the receiver was connected by a revolving shaft to the transmitter. The

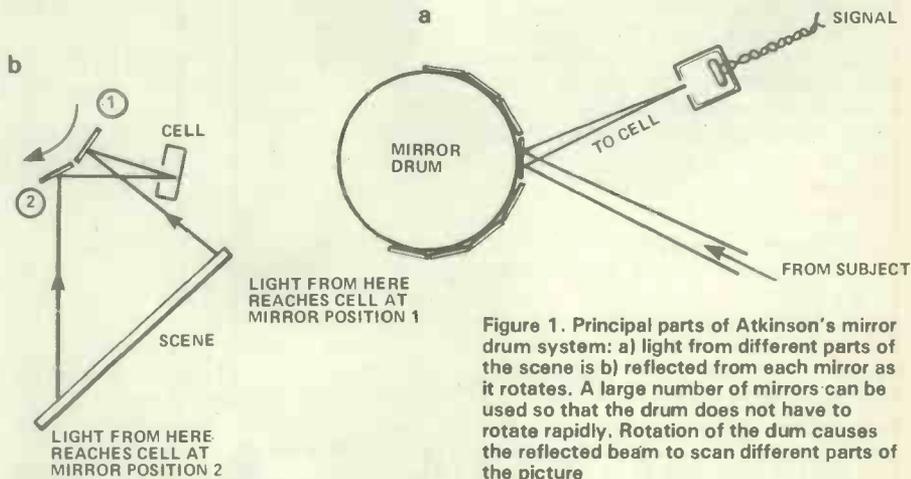


Figure 1. Principal parts of Atkinson's mirror drum system: a) light from different parts of the scene is b) reflected from each mirror as it rotates. A large number of mirrors can be used so that the drum does not have to rotate rapidly. Rotation of the drum causes the reflected beam to scan different parts of the picture

whole machine is in the Science Museum, which acquired it in 1908.

The need for scanning had been recognised, and by the mid-1880s, two important mechanical methods of scanning were well known. Atkinson's mirror drum (1882) used a set of flat mirrors mounted around the outside of a drum. As the drum was rotated, each mirror caused light from a reflected image to scan across a cell (Fig. 1). The Nipkow disc of 1884 used a wheel with holes drilled in it to provide both horizontal and vertical deflection at the same time (Fig. 2), and his Patent of 1884 contained all the details of the apparatus which Baird would later use.

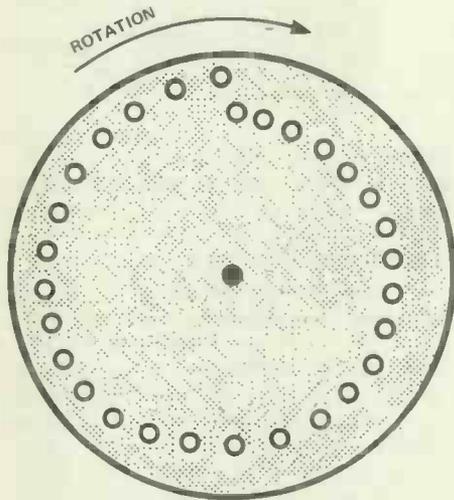


Figure 2. Nipkow disc, the scanning system used by most of the mechanical TV systems

Beyond Selenium

The practical problem which prevented these pioneers from producing a 30-line TV picture in the 1880s was their use of selenium. Like so many photoconductive materials, selenium has a long time-constant, so that scan rates of more than a few bits (fragments of picture information) per second were impossible. For slow facsimile work, this was of little importance, but for the transmission of any sort of moving picture, the time-constants were impossibly long. For that reason alone, mechanical TV systems were developed no further at that time, and no new suggestions were put forward.

By 1897, the possibility of all-electronic TV came flickering onto the horizon. In that year, Karl Braun developed a workable cathode ray tube which contained most of the essentials of the tube of today. Although the electron beam was

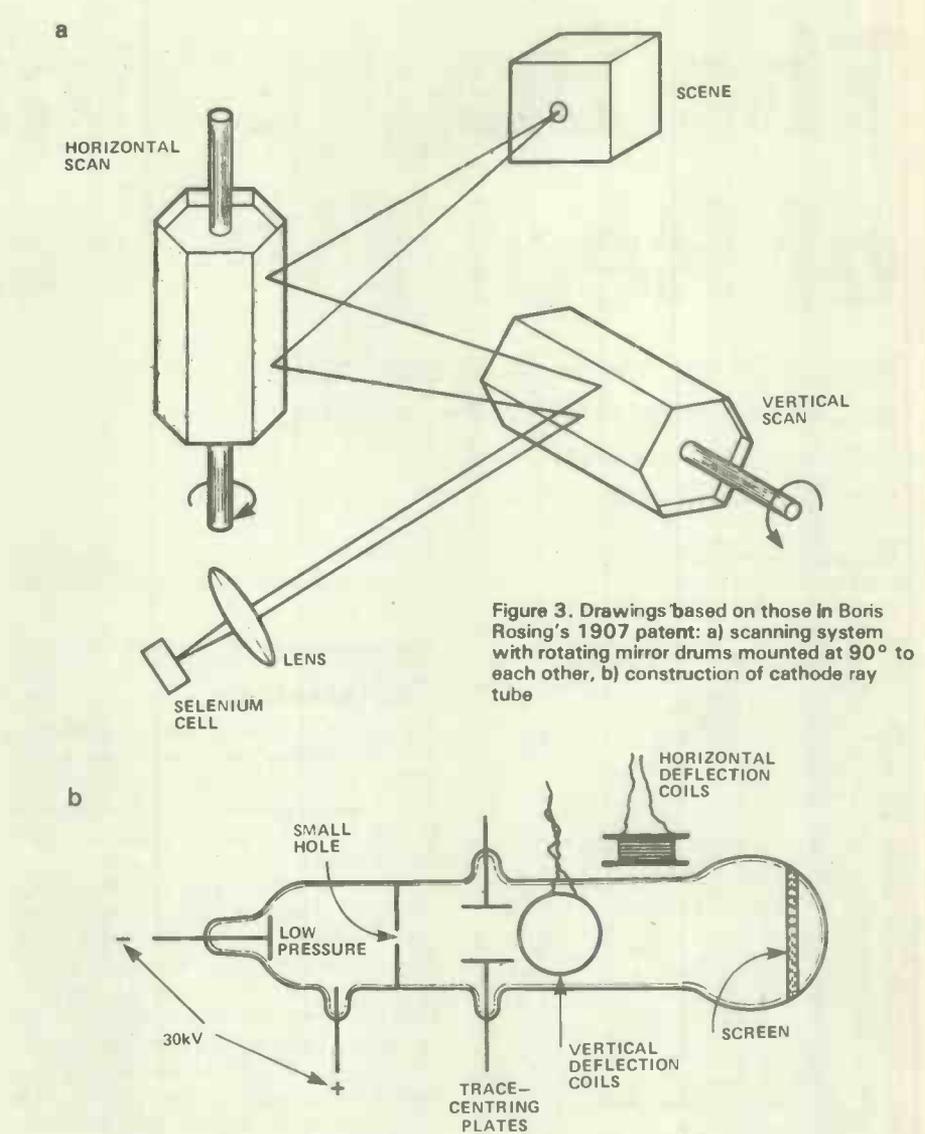


Figure 3. Drawings based on those in Boris Rosing's 1907 patent: a) scanning system with rotating mirror drums mounted at 90° to each other, b) construction of cathode ray tube

generated by passing current through a gas at low pressure rather than by thermionic emission, the deflection system and fluorescent screen were virtually the same as those we would recognise today. The possibilities which were opened up by this invention were immediately recognised by research physicists, who seized on the new device as a method of displaying alternating voltages. Engineers took a bit longer to see what might be achieved.

The first recorded suggestion that a cathode ray tube could be used for television seems to have come from Boris Rosing.

Rosing was a teacher with the St. Petersburg Technological Institute, and he wasted no time in applying for a British Patent for his invention. Rosings' TV system used mechanical scanning at the transmit-

ter, by mirror drums mounted at 90° to each other (Fig.3a). One drum revolved fast to provide line scan, while the other revolved slowly to provide frame scan. The cathode ray tube (Fig.3b) was used at the receiver, with its deflection coils fed from generators. The scheme was unworkable because the signals from the transmitter were much too feeble to operate the receiver: no amplification was then possible.

Insight Into Modern TV

At about the same time, A. A. Campbell-Swinton, an engineering consultant, had become interested in television and had concluded that mechanical systems were too primitive. In a letter written to the journal *Nature* (which is still where you'll find the first reports of significant new

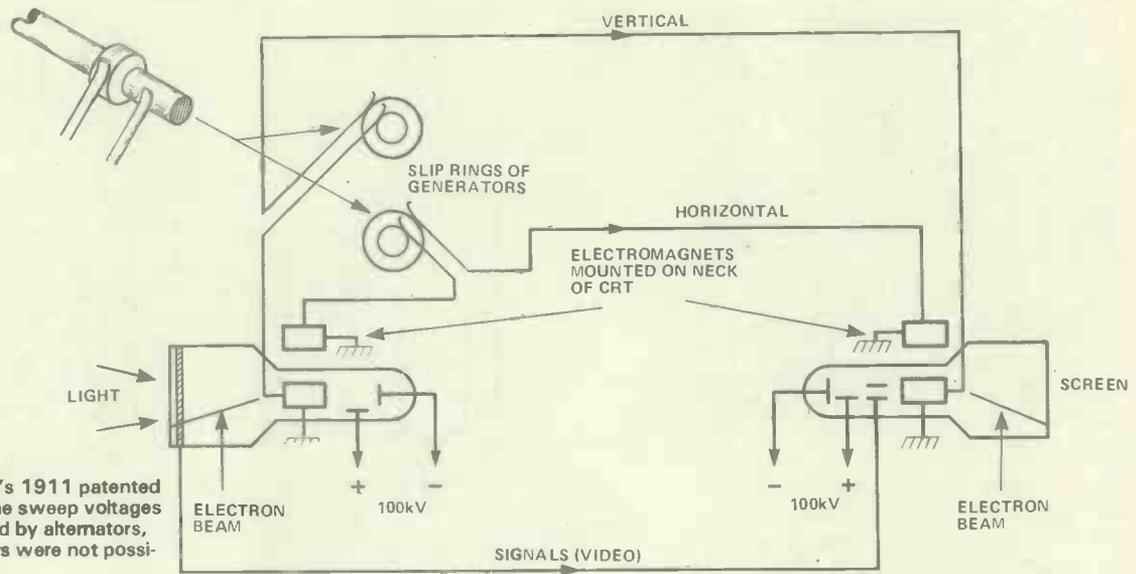


Figure 4. Campbell-Swinton's 1911 patented sketch in simplified form. The sweep voltages were to have been generated by alternators, because electronic oscillators were not possible at that time

discoveries) he described in outline all the details we would recognise as essential to all-electronic TV. An extract from the letter shows how far ahead his thinking was: '... employment of two beams of cathode rays (one at the transmitting and one at the receiving station) synchronously deflected by the varying fields of two electromagnets placed at right angles to one another and energised by two alternating electric currents of widely different frequencies, so that the moving extremities of the two beams are caused to sweep synchronously over the whole of the required surfaces within the one-tenth of a second necessary to take advantage of visual persistence. Indeed, so far as the receiving apparatus is concerned, the moving cathode beam has only to be arranged to impinge on a sufficiently sensitive fluorescent screen, and given suitable variations in its intensity to obtain the desired result. The real difficulties lie in devising an efficient transmitter

It takes only slightly more modern wording to be used as an acceptable description of TV today, yet this was published in 1908. Campbell-Swinton recognised that there was much to do, but in 1911 he took out a patent, and also delivered a lecture to the Rontgen Society in which he gave more details about his proposal. Campbell-Swinton's patented sketch, in simplified form, is shown in Fig. 4.

Need For Amplification

As it happened, one of the problems which made early TV experiments impractical was being solved — DeForest

had developed his Audion, the first radio valve, and had shown that amplification of signals was possible. Though Campbell-Swinton was unable to build a working model at the time, Marconi constructed one in 1937 to Campbell-Swinton's original plans, and it was exhibited at the Science Museum.

The first World War put an end to television experiments as such, but had the side-effect of causing a rapid development of radio and in particular the use of amplifying valves. Amplification was no problem in the post-War era, and the ideas which Campbell-Swinton had so clearly stated were picked up once again. The brilliant engineer, Vladimir Zworykin, who had escaped from Russia to the USA, developed the use of cathode ray tubes for receivers, and also filed a patent for a camera tube which was later developed into the Iconoscope. Philo Farnsworth, working on more conventional lines, developed another type of camera tube which he called the Image Dissector. Every part of Campbell-Swinton's scheme could now be assembled — but electronic TV didn't appear.

Looking back, the reason must be the immense publicity which accompanied Baird's experiments: Using the mechanical system of Nipkow and Atkinson, Baird was able to produce crude pictures. Other experimenters, knowing the limitations of the mechanical system, dismissed these results but to the uninformed public, Baird had produced television and no one else had. Work on electronic television suddenly became a secret operation, hindered rather than helped

by secrecy, and with funds always in short supply as speculators preferred to put their money into something they could see working. Television today exists because of the far-sightedness of several large companies who refused to jump on the Baird bandwagon and who recognised that Campbell-Swinton's scheme represented the only true TV system which could eventually be sold to the public. EMI and Marconi in the UK and RCA in the USA must share the credit for the remarkable developments which took place between 1923 and 1936. Because of the secrecy which surrounded the work of the two main teams who were developing electronic TV, it looks likely that neither was really aware of what the other was doing, but the basic scheme which had been laid down by Campbell-Swinton ensured that both were, in fact, working along very similar lines.

Need For An Electronic Camera

In the USA, the team at RCA was led by Vladimir Zworykin, and his interest in television had been aroused in a very direct way — he had been a pupil of Boris Rosing at St. Petersburg before his army service. After his escape to the USA in 1919, when so many army officers were being butchered for alleged lack of sympathy with the revolution, Zworykin joined the Westinghouse Research Laboratories. At Westinghouse, his research project was the construction of an electronic camera tube on the lines which had been proposed by

The Beginnings of Real TV

Campbell-Swinton, though Zworykin has said that at the time he was quite unaware of the work of Campbell-Swinton.

Zworykin realised that such a tube would have to incorporate the normal CRT electron gun and deflection coils, but in place of a fluorescent screen it would need to have a 'target' of photosensitive material. The method which Zworykin chose was a photoemissive layer, using a material which emits electrons when struck by light. This isn't the place to look closely at the way in which this tube worked, but briefly the idea was to use the light of an image to cause electrons to be emitted from a set of small insulated dots of photoemissive material. These electrons were then replaced as the beam from the electron gun scanned the target, and the current caused by the replacement of the electrons constituted the signal. Zworykin called this tube 'Iconoscope', and first attempted to take out a patent in 1923. At that time, however, a working model could not be constructed and the patent was not, in fact, granted until 1938. Zworykin had also put a considerable amount of work into the development of the receiver CRT, moving from a device which used both electrostatic and magnetic deflection (Fig. 5) to one which in all but dimensions resembles the tube of today.

EMI And The Choice Of Lines

In the UK the research and development effort centred round the newly-formed EMI group. This was a company formed by a merger of the Gramophone Company, Columbia Gramophone Company and a few other smaller companies, and this group had already achieved a mechanical system using 150 lines. At the time of the merger, Isaac Schoenberg, another Russian citizen who had studied at Kiev and had escaped to Britain (in 1915) was appointed as Director of Research. This was probably one of the best arrangements since Rolls met Royce, for Schoenberg had a remarkable ability for spotting engineering genius and for getting ideas put into practice. Two of his team have made their names many times over, A. D. Blumlein, who had the distinction of holding more patents in electronics circuitry than anyone before or since, and Dr. J. D. McGee, who is now Professor at Imperial College, and who then was concerned

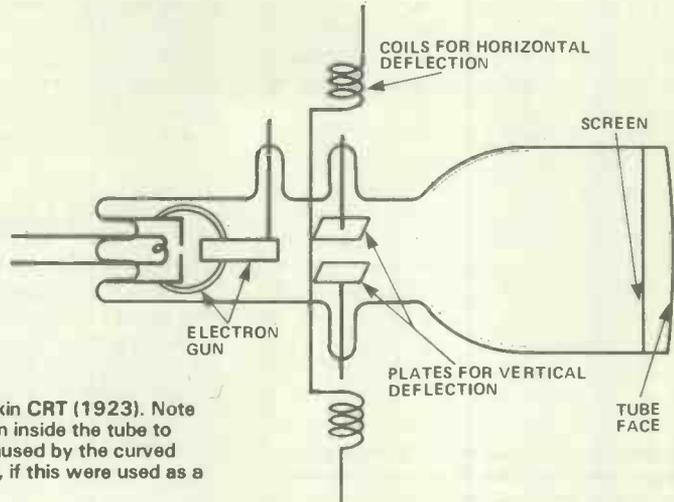


Figure 5. Early Zworykin CRT (1923). Note the use of a flat screen inside the tube to avoid the distortion caused by the curved outer face of the tube, if this were used as a screen

with the development of the Emitron camera tube.

When the EMI research team was originally formed, its first brief in 1931 was to improve the mechanical system, which was in fact done, first to 180 lines and then to 243 lines. By 1932, however, the engineers were convinced that the mechanical system had too many limitations to be considered seriously and the EMI team, like Zworykin's team at RCA started to concentrate exclusively on electronic methods. The Emitron camera tube was a considerably improved version of the original Iconoscope design, and the work which Blumlein did on such circuitry as timebases, synchronising pulses, video amplifiers and VHF circuits ensured rapid progress. It's worth remembering that *everything* was novel, there was no experience of such circuitry to draw on. In addition, the handicap of secrecy surrounded the project. There were several reasons for this. Shareholders of the company who had seen the mechanical system wondered why EMI did not put something on the market to counter Baird's efforts. Secondly, no-one was quite sure how far the US efforts had reached. Finally, there was a small but noisy group of left-wing MPs who opposed all forms of research which used money in times of hardship.

Fortunately, Schoenberg was able to persuade EMI's directors of the potential of his system. It's as well for us that he did, because the work of Blumlein on TV circuitry was the pioneering effort which enabled us to develop radar in such a remarkably short time. Incidentally, the development of the Merlin aero engine which

was later to power the Spitfire was also carried out under strong opposition from left-wing MPs, and the project would probably have collapsed but for money donated by Lady Houston. Not surprisingly, the opposition collapsed when Germany invaded Russia!

By 1935, the EMI team had succeeded to a point where an awkward decision had to be made. They could either market a 240 line system there and then, or work on to develop a higher-definition system. Schoenberg took the brave step of deciding to go for a 405 line interlaced scan system, once again plunging into the unknown. It was a remarkably brave step, because the BBC had been broadcasting on the Baird System since 1929, and the longer EMI waited, the more difficult it would have been to overturn the established system.

Once again, Schoenberg's judgement was correct. A Parliamentary Committee had been set up in 1934 to consider the various TV systems which were available, and to decide if any could be made the basis for regular public-service broadcasting. The Baird transmissions were still experimental, and the BBC was entrusted with the job of putting out the EMI system signals as well.

Once again, EMI was stepping into the unknown. The Baird system, being low-definition and sequentially scanned (no interlace) needed a comparatively small bandwidth and could be broadcast on the short-wave band. The EMI system needed a much greater bandwidth, and had to be transmitted on VHF — a band which was little used. No-one had ever transmitted or received TV waveforms

The Beginnings of Real TV

on these frequencies before, and no-one was quite certain whether it could be done or not. The transmitter side of the problem was handled by Marconi's Wireless Telegraph Company (as it was called then!).

The companies found themselves in a two-horse race. Baird's company was using three camera systems. One was a mechanically-scanned camera, using 240 lines with 25 frames per second. The second system used film as a method of televising scenes which the Baird camera could not tackle — which was most of them! The mechanical camera required the whole studio to be in darkness except for a brilliantly-lit subject, so that only face close-ups could really be televised live. The intermediate-film system was designed to patch up this immense handicap by filming the live scenes, developing and fixing the film in a time of one minute, and then using the film in a mechanical TV scanner, in which intense lighting could be used. Baird's third camera was an electronic one developed under licence from Philo Farnsworth but not sufficiently advanced to match the EMI equipment.

The tests started on 2nd November, 1936 at 3.30 PM — and there is a joke in EMI that the last joint was soldered at 3.29! Certainly, the

EMI team was working frantically right up to the last moment to perfect their 405-line 50-field system which was immensely superior in quality to the pictures which the Baird system could offer. Each system was used for a week, alternating between the two.

Arrival Of Modern TV

There was little doubt about which system was superior, but in any case the Baird Company suffered a disaster — a fire at the Crystal Palace destroyed all the equipment, including the Farnsworth camera. The EMI-Marconi system was chosen at about the same time as Zworykin at RCA was announcing the 525-line system which is still used in the USA. Television as we know it had arrived.

It hasn't exactly looked back. Schoenberg, always aiming to improve the system, had discussed with McGee the possibility of a greatly improved camera tube, the Super-Emitron. Once again, late working became the normal way of life in the Research Department and the Super-Emitron was ready for the Coronation broadcasts in 1937. This event provided so many 'firsts' for TV that there isn't room to list them. Every camera

which could possibly be used was pressed into service and the result was an immense success. Despite the fact that there was only one transmitter, at Alexandra Palace, some 23,000 receivers were in use by 1939, and pictures were being received at distances which no-one had believed possible, from Clacton to Brighton.


Then it all ended. The Second World War shut down all work on TV in Europe, and most of it in the USA. The techniques which had been worked out in that breathless period in the 30s were turned to radar use. Tragically, A.D. Blumlein was killed when an aircraft, in which he was conducting radar trials, crashed.

After the war, TV in Britain shakily started again on 405 lines. It seems out of character that Schoenberg should not have insisted on going to a higher line standard then, but the 405 line system seemed adequate at the time, and we are, after all, only saying farewell to it now.

Who invented television, then? It's a complex story, but I'll put my money on Campbell-Swinton, whose scheme was the launching pad on which the EMI team assembled their rocket. Without his vision, we might well have had to import the whole of the technology from the USA.



View into back of Marconiphone TV receiver, model 702, 1938 (also shown at beginning of article). It has a 12" (300 mm) picture tube mounted vertically, which is viewed by means of a surface-silvered mirror mounted in the lid. This was common practice in early receivers, where the tube was too long to be housed horizontally. The tube had an EHT voltage of 5kV, was electromagnetically deflected but electrostatically focussed

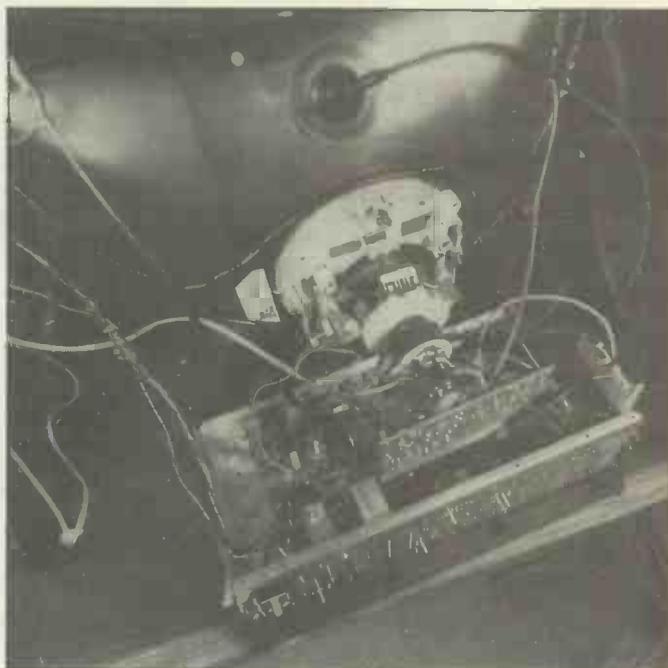

Rear view of Ferguson colourstar TV, 1968. This was the first all-transistor colour TV in the world, and it uses a 25" (635 mm) Thom-Mazda tube. It features modular construction: printed-wiring panels are removable for easier servicing. It was manufactured by Thom Consumer Electronics in Enfield, Middlesex

Both receivers are on view in the Science Museum, London

BI-AND SAVE SALE-81

DIODES

AA119	£0.06	OA70	£0.06	IN4005	£0.07
BA100	£0.06	OA79	£0.06	IN4006	£0.06
BA148	£0.13	OA81	£0.06	IN4007	£0.09
BA173	£0.13	OA90	£0.06	IN5400	£0.12
BAX13	£0.05	OA91	£0.06	IN5401	£0.12
BAX16	£0.06	OA95	£0.06	IN5402	£0.15
OA200	£0.06	IN34	£0.06	IN5404	£0.15
OA202	£0.07	IN60	£0.07	IN5406	£0.19
BY100	£0.18	IN4148	£0.05	IN5407	£0.23
BY126	£0.12	IN4002	£0.06	IN5408	£0.28
BY127	£0.14	IN4003	£0.05	IS44	£0.03
OA47	£0.06	IN4004	£0.06		

AUDIO AMPLIFIER

5 watt Audio Amplifier Module.

Special Clearance Offer

O/No. AL20. £2.50

CAPACITOR PAKS

16201	18 electrolytics	4.7uF-10uF
16202	18 electrolytics	10uF-100uF
16203	18 electrolytics	100uF-680uF

AM 3 in SPECIAL PRICE OF £1.30

16160	24 ceramic caps	22pF-82pF
16161	24 ceramic caps	100pF-380pF
16162	24 ceramic caps	470pF-3300pF
16163	24 ceramic caps	4700pF-0.047pF

All 4 in SPECIAL PRICE OF £1.80

RESISTOR PAKS

Order No.			
16213	60 $\frac{1}{2}$ W	100ohm-820ohm	
16214	60 $\frac{1}{2}$ W	1K-8.2K	
16215	60 $\frac{1}{2}$ W	10K-82K	
16216	60 $\frac{1}{2}$ W	100K-820K	
16217	40 $\frac{1}{2}$ W	100ohm-820ohm	
16218	40 $\frac{1}{2}$ W	1K-8.2K	
16219	40 $\frac{1}{2}$ W	10K-82K	
16220	40 $\frac{1}{2}$ W	100K-820K	

Any 4 in SPECIAL PRICE OF £1.80

SPECIAL OFFER

MJ2955 (PNP Complementary to 2N3055) TO3	£0.75
ZN414	£0.75
ORP12	£0.50

SEE OUR SPECIAL INCLUSIVE APRIL ANNOUNCEMENT IN PRACTICAL ELECTRONICS, PRACTICAL WIRELESS, EVERYDAY ELECTRONICS

POPULAR (CMOS)

CD4001	} 1 of each, normal price £1.80 for 5 — Our price £1.30 for 5
CD4007	
CD4011	
CD4017	
CD4081	

O/No. SJ1245

P.C.B.

O/NO:1609 PCB Etch Resist Pan	£0.55
SJ138 Paper PCB 5-pieces — approx. 200 sq. ins.	£1.75
SJ139 Glass Fibre PCB 5-pieces — approx. 200 sq. ins.	£2.25
SJ140 Mixed PCB single-sided paper — single and double-sided Glass Fibre — 5-pieces — approx. 200 sq. ins.	£2.00

CAPACITORS

SJ11	150 Caps. mixed types & values.	£0.50
SJ12	60 Electrolytics all sorts mixed.	£0.50
SJ13	40 Polyester/polystyrene capacitors mixed.	£0.50
SJ14	50 C280 type capacitors mixed.	£1.00
SJ15	Polystyrene Caps 1, 160v	£0.60
SJ16	40 Low volts electrolytics mixed values up to 10v.	£0.50

TRANSFORMERS

MINIATURE MAINS Primary 240v

No. Secondary		
2021	6v-0-6v 100mA	£0.75
2023	12v-0-12v 100mA	£0.95
2035	240v Primary 0-55v 2A Secondary	£5.50

BC108 FALLOUTS

50 NPN BC107/108 SJ124 £1

Manufacturers out of spec on volts or gain or neither — Metal TO18 case — You test.

50 PNP BC177/178 SJ1244 £1

UJTs & FETs

UT46/TIS43	£0.18	2N4860	£0.40
BRV56	£0.25	2N4220	£0.30

Silicon Fast Switch

NPN — like 2N706/2N2369

You select by test!

O/No. SJ125.50 for £1

Special Introductory Offer

COMPUTER ICs

EPROM 2516	£3.00
EPROM 2716	£6.00
D.RAMS 4116	£2.25

SPECIAL OFFER LINEAR ICs

NE555	5 for £0.90
741P	5 for £0.80
NE556	5 for £2.50
LM380	5 for £3.50
72723 14 pin	5 for £1.75
CA3085	1 for £0.75

ASSORTED GERM. TRANS.

SJ135 20 Assorted Germanium Transistors — All New and Coded types include ACs — 2Gs — GETs-ACs, etc. £1.00

FM TUNER

SJ141 FM Tuner (Front End) with AM twin gang capacitor 87.109MHZ 5-10 volts supply — data sheet supplied. £2.60

AERIALS

FM Indoor Tape/Ribbon Aerial

O/No. 107.40p each

HI-FI CAR AERIAL

4-section fully retractable & locking **SPECIAL PRICE.**

O/No. 109. £1.40 each

BI-PAK'S OPTO BARGAIN!

Valued at over £10 — Normal Retail

We offer you a pack of 25 Opto devices to include LED's large and small in Red, Green, Yellow and Clear, 7 segment Displays both Common Cathode and Common Anode PLUS bubble type displays — like DL-33 Photo Transistors — similar to OCP71 and Photo Detectors — like MEL11-12. This whole pack of 25 devices will cost you just —

£4!

and we guarantee your money back if you are not completely satisfied.

Full data etc included

O/No. SJ120.

IC SOCKET PAKS

SJ36	14	8 pin	SJ41	6	22 pin
SJ37	12	14 pin	SJ42	5	24 pin
SJ38	11	16 pin	SJ43	4	28 pin
SJ39	8	18 pin	SJ44	3	40 pin
SJ40	7	20 pin			

ALL AT ONLY £1 each

VOLTAGE REGULATORS

Cast TO220

Positive	Negative		
uA7805	£0.65	uA7905	£0.70
uA7812	£0.65	uA7912	£0.70
uA7815	£0.65	uA7915	£0.70
uA7818	£0.65	uA7918	£0.70
uA7824	£0.65	uA7924	£0.70

GERM. TRANSISTORS

The last of the Germanium PNP-OC71-71-75 etc. Mullard Black/Glass Type — You test (5 could cost you that!)

O/No. SJ126. 50-pcs £1.

GERM. POWER TRANS

AD149-OC26-AD140 £0.50 each

AD142-OC28-2N3614 £0.65 each

GENUINE MULLARD TRANSISTORS

AF118	£0.40	AC187	£0.20
AF118	£0.45	AC187K	£0.35
OC71	£0.12	AC188	£0.20
OC75	£0.25	AS217	£0.60
OC76	£0.30	BC148C	£0.07
OC79	£0.35	BC149C	£0.07
OC42	£0.18	BC157	£0.08
OC44	£0.20	BC159	£0.08
OC45	£0.18	OC71	£0.30

DISC CERAMIC CAP

100 Disc Ceramic Cap. Mixed values covering complete range 3PF-4,700PF.

SUPER VALUE

O/No. SJ121. £1

SWITCHES

Push-to-make, 6mm panel mounting.

O/No. SJ131. 5 for £0.50

Push-to-break as above.

O/No. SJ132. 4 for £0.50

Silicon Heat Sink Compound 3ml in syringe 25p

SJ134 Slide Switches Low voltage and mains types 12 for £1.00

Semiconductors from Around the World

100 A collection of Transistors, Diodes, Rectifiers, Bridges, IC's, SCR's, Triacs both Logic and Linear + Opto's all of which are current everyday usable devices. **100**

Guaranteed Value over £10 at Normal Retail Price yours for only £4.00

Data etc in every pak. Order No. SJ220

SILICON TRANS.

SJ25	100 Silicon NPN transistors all perfect & coded — mixed types with data & equivalent sheet — no rejects	£2.50
SJ26	100 Silicon PNP transistors all perfect & coded — mixed types and cases, data & equivalent sheet	£2.50
SJ27	50 Assorted pieces of SCR's, diodes & rectifiers incl. stud types, all perfect — no rejects, fully coded — data incl.	£2.50

TTLs

SJ28 20 TTL74 series gates — assorted 7401-7460

£1.00

Mixed DTL ALL New and Coded

330-9999 our mix 18 for £1.00

O/NO-SJ133

RESISTORS

SJ1	200 Resistors mixed values.	£0.50
SJ2	200 Carbon resistors $\frac{1}{2}$ watt preformed.	£0.50
SJ3	100 $\frac{1}{2}$ watt miniature resistors mixed values.	£0.50
SJ4	60 $\frac{1}{2}$ watt resistors mixed values.	£0.50
SJ5	50 1-2 watt resistors mixed pot values.	£0.50
SJ7	30 1-2 watt wirewound resistors mixed.	£0.50

CASSETTES

SUPER VALUE & A GREAT SAVING!!!

C120 Dinky Cassettes — Low noise — astounding value and sound.

O/No. SJ32. 10 for £3.50

PRECISION VOM MULTIMETER

20,000 ohms/volts DC. Complete with test leads & instructions.

OUR SPECIAL OFFER PRICE £11 each

O/No. 1323

Use your Barclay or Access Card!

NPN TRANSISTORS

SJ68	30 ZTX300 type transistors pre-formed for P/C Board colour coded Blue — all perfect.	£1.00
SJ70	25 BC107 NPN TO106 case transistors code Green Spot.	£1.00
SJ71	25 BC177 PNP TO106 case transistors code C1395.	£1.00
SJ72	4 2N3055 silicon power transistors TO3	£1.00

POTENTIOMETERS

16173	15 Assorted Pots	£1.00
SJ54	20 Assorted Slider Pots	£1.00
SJ56	10 100 K Lin Slider Pots 40mm	£0.50
16186	25 Pre-sets Assorted	£0.50
SJ49	8 Dual gang carbon pots log and lin mixed values	£1.00
SJ50	20 Assorted slider knobs — chrome/black.	£1.00

TRIACS

4A	400v TO-202 non-isolated	
TAG136D		£0.40
8A	400v TO-202 isolated	
TAG425		£0.60
Diac D32/BR100		£0.15
SCR C106D	plastic case	£0.30

LED.

2nd Quality Paks

1507	10 Assorted colours & sizes	£0.65
S122	10 125 RED	£0.50
S123	10 2 RED	£0.50

LED CLIPS

1508/125 125	5 for £0.10
1508/2 2	5 for £0.12

MISCELLANEOUS

SJ137 Assorted Cable Grips and Cabinet Feet 50 pieces for £1.00

SJ135 Nickel Cadmium rechargeable Cell 3500D. HP2 size

Calculator Chip Type: GOM2-C500 24-pin MOX with Data

2015 IC Insertion — Extraction Tool

£0.50

£0.52

ODDMENTS

16170	50 metres asst. colours single strand wire.	£0.50
16187	30 metres stranded wire mixed colours.	£0.50
16178	5 Main slider switches assorted.	£0.50
SJ76	1 Board containing 2x5-pin DIN sockets 180° & 2x2-pin DIN loud-speaker sockets.	£0.30

KNOBs

SJ62	5 15mm chrome knobs standard push fit.	£0.50
SJ63	Instrument knob — black winged (29x20mm) with pointer. $\frac{1}{2}$ " standard screw fit.	£0.15
SJ64	Instrument knob — black/ivory aluminium top (17x15mm) $\frac{1}{2}$ " standard screw fit.	£0.12

BI-PAK

Send your orders to: Dept. 'HE 3, BI-PAK, PO BOX 6, WARE, HERTS. SHOP AT: 3 BALDOCK ST, WARE, HERTS. TERMS: CASH WITH ORDER, SAME DAY DESPATCH, ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL: (0920) 3182. GIRO 388 7006 ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING.

Results of HE Electronic Games Competition

We're pleased to announce the results of the competition published in the January 1981 issue of HE. You will remember that first prize was the exciting new programmable TV game from Rowtron, with a selection of cartridges for good measure. Second prize was the hand-held Space Invader game from Entex. We offered one of the latest HE T-shirts to each of the 20 runners-up.

Now for the bad news. No, we haven't lost the entries (or the prizes!) but out of the 400-odd entries we received, only 17 (4.25%) got *all* the answers right! So there was no need for us to worry about using your suggested last line to our limerick in a 'tie-breaker'.

The Winners

1st Prize Anthony Clarke, Spondon, Derby

2nd Prize Jeff Jones, Risca, Gwent

Runners-up

Tufail A. Ansari, Southall, Middlesex
Derek Blamire, Llandudno, North Wales
R.W. Chandler, Adel, W. Yorks
P.C. Clift, Sharness, Gloucestershire
Andrew Donaldson, Harpenden, Herts
D.F. Downing, Ashford, Kent
G.U. Fenton, Falsgrave, Scarborough
T. Holt, Codsall, Staffs
Bruce C. Joslin, Henleaze, Bristol
M. Moore, Peterborough, Cambs
G.F.P Room, Corringham, Essex
John Sedgeman, Sherburn Rd. Est., Durham
E.L. Stock, Pontypridd, Mid Glamorgan
Stephen Walls, Stockton, Cleveland
David St. George, London

As you can see from the picture right, Sally Holley, HE's new Advertisement Representative, was chosen to draw the winning entries. The draw took place on Thursday 8 January, and we're glad to say that only two entries came in after the closing date of 1 January.

The Answers

Now, before the arguments start, printed below are the original questions together with the *correct* answers. As we said on the entry form, no correspondence regarding the competition will be entered into, AND the Editor's decision is final.

1) Which component is used as a 'White Noise' generator in the Chuffer project this month?

Q3 (Note that 'a BC182L transistor' or just 'a transistor' was not sufficient)

2) What is the maximum power rating of each channel in the Sound-To-Light project?
1.2kW

3) How many times is the word 'games' used in this month's feature on electronic games?
50

4) Who sells the cheapest BC 109 amongst the advertisers in this month's HE?

Watford Electronics (Note BC109 not BC109A or other gain derivatives, nor bulk buys or assortments)

5) What is the maximum number of 'revs' that can be displayed on the HE Tachometer project?
7000

6) What is the impedance of the High-impedance Voltmeter that will be appearing in next month's HE?

In excess of 11 million ohms (also correct: over 11 million ohms, over 11 MΩ, or even > 11 x 10⁶Ω)



The moment of truth: HE's Sally Holley takes the plunge for the 1st-prize winner

At last, after a few tries, out comes the winning entry



The Limerick

Most entrants had a go at the last line to this, and we must thank David St. George, one of the runners-up, for his observation: 'This is not a limerick! The last words of the 1st and 2nd lines should rhyme!'

This was confirmed by the Concise Oxford Dictionary, which states: 'Kind of humorous verse, esp. five-line form often epigrammatic or indecent, with rhymes *aabba...*'

Well, ours wasn't indecent (nor did anybody supply an indecent ending) but it was in *abccb* form.

Enough of these technicalities: we'll simply present a selection of endings below and leave *you* to judge which are the best ... or the worst.

Right in the middle of Modmags
Clever Dick was opening his mail
As he opened one pack
It made a loud crack

.....
(You'll notice that we've corrected the 'on pack' error in the original)

And now he reads "H.E." using brail
Dan Gillham, Guildford, Surrey

And out popped [!] a man from Mars
V. Stanley, Cambridge

It couldn't have been fitted with 'safe fail'
C.T. Hearne, Chalfont St Peter, Bucks

Now Modmags has something for sale
David Melvin, Sherborne, Dorset

And out fell "A PET" minus tail
Max York, Mundlesley, Norfolk

And his false teeth fell into a pail
D. Powell, Prescott, Lancs

And a voice said 'HE is now on sale'
J. Burns, Ewell, Surrey

That's a new kind of programming in brail
M. Souter, Sevenoaks Weald, Kent

And out popped Fletch with a wail
A. Woodward, Coppull, Lancs

And promptly blew off all his nails
S. O'Callaghan, Guildford, Surrey

He found a party grenad [!] from Iraq
Andrew Hodson, Kendal, Cumbria

And exploded with a siren-like wail
J. Madigan, Crick, Northampton

And his desk was awash with real ale
B. Fuller, Keighley, W. Yorks

Good Lord, its [!] short circuits, they're back!
Pete Hodges, Tyseley, Birmingham

IC said CD, and he shouted for joy,
A motto, a hat and a toy
Paul A. White, Cookridge, Leeds

'Twas a spaceship in graphic de-tail
N.N. Lindsey, Reading, Berks

Rolled over and said "Hows That!"
Nigel Schwarz, Temple Cloud, Nr Bristol

And he hosed himself down with Pale Ale
Robert Hannah, Feltham, Middlesex

And blew the Editor to rags!
P.W. Dix, Enfield, Middlesex

And out popped a little alien
Who was burnt and all black
Adrian Hallas, Midlothian, Scotland

Now his electronics are hung on a nail
Bobby Grindlay, West Calder, West Lothian

Went he as pale as a pail of pale ale!
Winston Harratt, Congleton, Cheshire

And shorted his 'Chuffer' to the rail
H. Edwards, Stockport, Cheshire

And out fell a crate of brown ale
David Shea, Old Windsor, Berks

An 'HE' project that didn't fail
D.F. Downing, Ashford, Kent

Perhaps we'll make it easier next time: see under Monitor this month for details of our next competition.

GREENWELD

443F MILLBROOK ROAD, SOUTHAMPTON SO1 0HX
All prices include VAT—just add 40p post. Tel (0703) 772501



COMPONENT CABINET IDEAL FOR THE NEWCOMER TO ELECTRONICS

Contains hundreds of brand new resistors, capacitors, transistors, diodes and I.C.s. All useful values, carefully chosen to help the new constructor pursue his hobby without finding himself short of some vital parts. All parts contained in clearly marked bags in a plastic storage cabinet 232 x 121 x 185mm with 9 drawers into which all parts can be neatly located. If bought individually parts plus case would cost over £50 but we are offering this for **ONLY £33.95** + £1 p. & p. Simply send a cheque or P.O. for **£34.95** for immediate despatch.

CONTENTS:

- 200 1/4 watt resistors
- 20 Wire wound resistors
- 20 Ceramic Capacitors
- 70 Mylar Capacitors
- 50 Polyester Capacitors
- 56 Electrolytic Capacitors
- 61 Transistors
- 12 ICs
- 20 LEDs
- 55 Diodes and rectifiers
- Altogether 614 components.
- Plus FREE surprise gift.

P.C. ETCHING KIT M4-V

The best value in etching kits on the market — contains 100 sq in copper clad board, Ferric Chloride, Etch resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. **All for £4.95.**

CALC CHIPS 80pi1

New full spec, supplied with data. Type MK50321 — full function inc. memory. **Only 80p**

DISPLAYS

8 and 9 digit 7-segment bubble type for above chips — most have minor faults, dud segment, etc. Mixture of 2 or 3 different types with data. 5 for **£1.**

EX-COMPUTER PANELS

Z527 2 x 6V reed relays, 5 x 25030 or 25230 6 x 400V reeds. + Rs. **Only 50p.**
Z529 TTL pack — Panels with 74 series on, together with code sheet. From simple gates to complex counters. 20 ICs **£1;** 100 ICs **£4.**

BUZZERS, MOTORS & RELAYS

Z401 Powerful 6V DC buzzer, all metal construction. 50mm dia x 20mm **85p.**
Z402 Miniature type buzzer, 6, 9 or 12V, only 22 x 15 x 16mm. Very neat **65p.**
Z450 Miniature 6V DC motor, high quality type 32mm dia x 25mm high, with 12mm spindle. **Only £1.**
Z459 115-230V ac high torque motor with geared reduction down to 60 rpm. Sturdy construction, 70mm dia x 20mm Spindle 6mm dia x 20mm long. **Only £2.**
W892 Heavy Duty 12V relay, ideal for car use — single 15A make contact. Coil 25R in sealed metal can with mounting bracket **85p.**
W890 DIL Reed relay SPCO 2.4-10V. 200R coil. **Only £2.20.**
W847 Low profile PC mtg 10 x 33 x 20mm 6V coil. SPCO 3A contacts. **93p.**

VEROBLOC BREADBOARD

New from Verob, this versatile aid for building and testing circuits can accommodate any size of IC. Blocs can be joined together. Bus strips on X & Y axis — total 360 connexion points for just **£4.15.**

ELECTRONICS

A NEW AND EXCITING HOBBY!!

BIG WELL ILLUSTRATED BOOK

Ideal for beginners — gives lots of general information — explains how to build lots of projects: Intercom, Rain Alarm, Radios, Organ, Parking Light etc. All parts supplied and can be re-used on special deck, provided NO SOLDERING is required. Just needs 45V battery.

£17.50 Inc. VAT & Post

Also **ADVENTURES WITH MICROELECTRONICS** — Explore the world of silicon chips — All components & Deck, **£27.95** Inc. VAT & Post.

THE SPECTACULAR 1981 GREENWELD Component Catalogue

Bigger and better than ever!!!

- * 60p discount vouchers
- * First Class reply paid envelope
- * Free Bargain List
- * Priority Order Form
- * VAT inclusive prices
- * Quantity prices for bulk buyers
- * Free IC Data Sheet
- * **SEND 75p (inc. post) FOR YOUR COPY NOW!!**

BUY A COMPLETE RANGE OF COMPONENTS AND THESE PACKS WILL HELP YOU

ALL PACKS CONTAIN FULL SPEC. BRAND NEW MARKED DEVICES — SENT BY RETURN OF POST, VAT INCLUSIVE PRICES.

- K001** 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1,000pF, total **£4.80.**
- K002** Extended range 22pF to 0.1µF, 330 values **£7.66.**
- K003** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µ, 110 altogether for **£5.40.**
- K004** Mylar capacitors, min 100V type 10 each all values from 1,000pF to 10,000pF. Total 130 for **£4.70.**
- K007** Electrolytic capacitors 25V working small physical size, 10 each of these popular values 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for **£3.59.**
- K008** Extended range, as above, also including 220, 470 and 1000µF. Total of 10 for **£8.35.**
- K021** Miniature carbon film 5% resistors CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors **£5.95.**
- K022** Extended range, Total 850 resistors from 1R to 10M **£8.20.**
- K041** Zener diodes 400mW 5% BZY88, etc. 10 of each value from 2.7V to 36V, E24 series. Total 280 for **£15.85.**
- NEW K051** LEDs — 10 each red, green & yellow 3mm & 5mm, with clips. Total 60 LEDs for **£8.95.**

REGULATED PSU PANEL

Exclusive Greenweld design — better spec. than anything on the market being offered at the price. Panel 110x82x33mm high contains all components including bridge rectifier and smoothing capacitor. Ready built and tested — just add a 30V 2A transformer and two pots for a fully variable voltage and current supply.

SPEC: Output voltage 0-28V
Output current 20mA-2A
Source Impedance 0R1

Open circuit ripple 10mV

Send SAE for full details of the many ways this useful module can be used, together with price list of parts for various options. **Only £7.75**

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number — almost all are full spec. devices. Some have bent leads. Over 30 different types have been found by us including BC184/212/238/307/328. BF196/7: 21x107/8/9/342/450/550, etc. Only available at a mixed pack at **£3 per 100, £7 per 250, £25 per 1,000.**

ELECTRONIC AIR FRESHENER KIT



- Battery Operated
- Replaceable Fragrance
- Continuous Air Freshening
- Robust Construction

This novel kit contains everything you need to make one of the most advanced air fresheners of its kind. Styled to take its place in any room in your home and do its job quietly and unobtrusively. The automatic timing circuit switches on a fan for a few seconds at regular intervals to send an odour neutralising fragrance into every corner of your room.

The kit includes components for EITHER a 4 or 15 minute timing circuit, miniature O.C. motor and moulded parts in high impact styrene to provide an easily maintained, elegant appearance.

ONLY £7.95.

★ POWERFET AMPLIFIERS ★

Conservatively rated, high quality designs with substantial heatsink/mounting bracket.

PFA 80
80w into 8Ω.
THD < 0.008%.
S/N 120dB.
Kit **£13.95**
Built **£15.95**

PFA 120
120w into 8Ω.
THD < 0.005%.
S/N 120dB.
Kit **£21.55**
Built **£23.85**

Post & packing 75p

CA3080E	70p
CA3140E	45p
MC3401	30p
TL081	29p
TL082	35p
2102	80p
2114	340p
4001B	17p
4011B	17p
4013B	40p
4016B	40p
555	25p
709	15p
710	25p
733	50p
741	18p
78L05	29p
78L12	29p

POWERFETS
8D512 (60V, 1 1/2A, Pchan.) 85p
8D522 (60V, 1 1/2A, Nchan.) 80p
VN67AF (60V, 2A, Nchan.) 75p
2S149 (140V, 100W, Pchan.) 340p
2SK134 (140V, 100W, Nchan.) 340p

HI-FI ON TWO CHIPS

HA12017 (Preamp 0.001% distortion 83dB S/N in phono application) 80p
HA1397 (Poweramp 200 watts in 8Ω, 0.02% distortion (typ) 195p)
Both with data and circuits

SCOPE TRACE DOUBLER P.C.B.
Built C/W shift, chan. select, chopper controls and instructions. Useful display from DC to 10MHz. Runs from 9V battery **£9.95**
CAR AMP I.C. HA1388 Bridge amp delivers 18W 195p.
Heatsink for above **40p.**

VCA High quality design offers attenuation from 0dB to -90dB. S/N 90dB. THD 0.01%, B.V. DC to 100KHz. Complete components set and circuit **£2.50**

J. W. RIMMER

Technical enquiries to 367 Green Lanes, London N4 1DY. Tel 01-800 6667

P&P 35p Mail orders to 148 Quarry Street, Liverpool L25 6HQ. Tel 051 428 2651.

PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded/coloured and colour coded.

£1-00 per hundred mixed. (Min 10 per value)
£8-50 per thousand mixed. (Min 50 per value)


Special stock pack, 60 values, 10 off each **£5-50**

DIODES: IN4148 3p each. Min order quantity — 15 items.
£1-60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base — solve those programming problems.
4 Way 86p each. 6 Way **£1-00** each. 8 Way **£1-20** each.

DIL SOCKETS: High quality, low profile sockets:
8 pin — 10p. 14 pin — 13p. 16 pin — 15p. 18 pin — 19p. 20 pin — 25p.
22 pin — 29p. 24 pin — 35p. 28 pin — 39p. 40 pin — 57p.

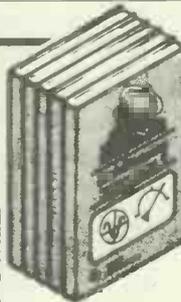ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN. ORDER — UK £1-00. OVERSEAS £5 — CASH WITH ORDER PLEASE



ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages. Bound in stiff linen. Cover size 8 1/2 in x 5 in. Price **£10.00** per set (we pay the postage)

- Book 1. Introducing Electronics
- Book 2. Resistors/Capacitors
- Book 3. Inductors/Diodes
- Book 4. Meters/Voltage-dividers
- Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order Now:
Selray Book Company
11 Aspen Copse,
Bromley,
Kent. BR1 2NZ

OUR 100% GUARANTEE

Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £

Name:

Address:

HE3

Building Site

What's important about wire? Keith Brindley advises you on the correct types to use in your projects

IF YOU HAVE read the article on the HE Public Address Amplifier project this month then you will have come across the reference (page 13) to different types of wire (screened cable at the input and heavy gauge wire at the output and for the power supply connections). If you are an enquiring reader (and judging by the letters we receive, many of you are), then you may ask why we use one type of wire in one place and yet an entirely different type elsewhere. After all, surely the only *real* purpose of a piece of wire is to join parts of a circuit electrically, so that a low resistance exists between two points? So why are different varieties used? Well, I gave the clue when I said *low* resistance. You see, NO wire of any length can have zero resistance. A wire will always possess a finite resistance, however small, perhaps only a thousandth of an ohm (0.001R). Now, resorting to a bit of electronics theory, Ohm's Law states clearly the relationship between voltage, current and resistance, given by:

$$V = I \times R,$$

where V is the voltage, I the current and R the resistance. Putting a few numbers in this equation, say a length of wire has an overall resistance of 0.1R and the current through it is 5 A. The voltage between one end of the wire and the other will be:

$$\begin{aligned} V &= 5 \times 0.1 \\ &= 0.5 \text{ volts (0.5 V).} \end{aligned}$$

Now, 5 A may seem to be a very large current and you could be forgiven for thinking that none of your projects would ever pass such an amount, but you would be wrong. Take the PA Amplifier for instance: although it probably draws an *average* current of only a few hundred milliamps (mA), during large-volume peaks the current *surges* can be around and over 5 A. So, with this project, it is possible that 0.5 V could be easily 'lost' along a length of cable having the above specifications.

A voltage on the connecting wire means that a voltage *drop* occurs between the two circuits connected by the wire and Fig. 1 shows this graphically. In this example, two leads are connected between a power supply and a

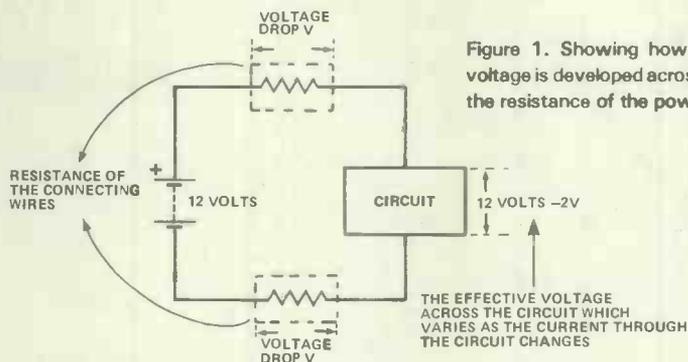


Figure 1. Showing how less than the original voltage is developed across the circuit because of the resistance of the power supply leads

circuit. Any voltage drop across one lead will be mirrored in the other, because they both have about the same resistance and not all the power available is passed onto the following circuit. The result is that not only does the voltage across the circuit vary with current flow, but the earth rail of the circuit (which should be at 0 V) changes in voltage: thus it is 'floating'. In an amplifier, particularly one producing more than a couple of watts output, a floating earth can result in instability and unwanted noises from the loudspeaker.

The only solution to the above problem is to use the correct thickness of wire for the job. Make sure you choose the wire by its current rating, such as 1 A, 2 A etc. Figure 2 shows a selection of wires ranging from 0.5 A rating to 10 A rating.

The wire recommended for most HE projects is multi-strand wire, which is a collection of strands of the conducting material grouped together and covered with insulating material. The wire can be classified by the number of strands in the group and the thickness of each one (e.g. 10/0.1 — a group of ten strands, each 0.1 mm thick). However, another category is the single-strand type, which is, as its name suggests, one single length of wire. Inevitably, single-strand wire is more brittle than its multi-strand counterpart, so if you use it to wire up one of your projects, be warned that if any movement of a connection occurs, the wire might break. I would always advise you to use only multi-

strand wire to wire-up a project. You should certainly *never* use single-strand for wiring to mains plugs.

So where *do* you use single-strand? There are three main places, each using a different variety or single-strand wire:

- on a breadboard (see Fig. 3) where connections are made from one socket to another. You shouldn't use multi-strand here because the thin strands tend to break off and get stuck inside the sockets
- as a link on a circuit board. Tinned copper, single-strand uninsulated wire is ideal and makes really neat links
- to make a coil. Certain circuits require an inductor and often these can be hand-made by winding a number of turns of single-strand wire on an insulated former. To prevent short-circuits between the turns, the wire needs to be insulated, and the standard procedure is to use coated wire which has a layer of polyurethane on it. Making the connections at the ends is easy: you can either scratch off the last ¼" or so of insulation with a sharp knife (watch your fingers) or, with a hot soldering iron, melt it off

Finally we come to screened leads, which are normally used at the inputs of high-gain amplifiers to help prevent interference. The main cause of the interference is *capacitive* pickup and Figs. 4 & 5 show the principle of its action and how to prevent it. In the examples shown, a high-gain amplifier is used to raise the output signal of a microphone to the level required to drive a loudspeaker. The two connec-

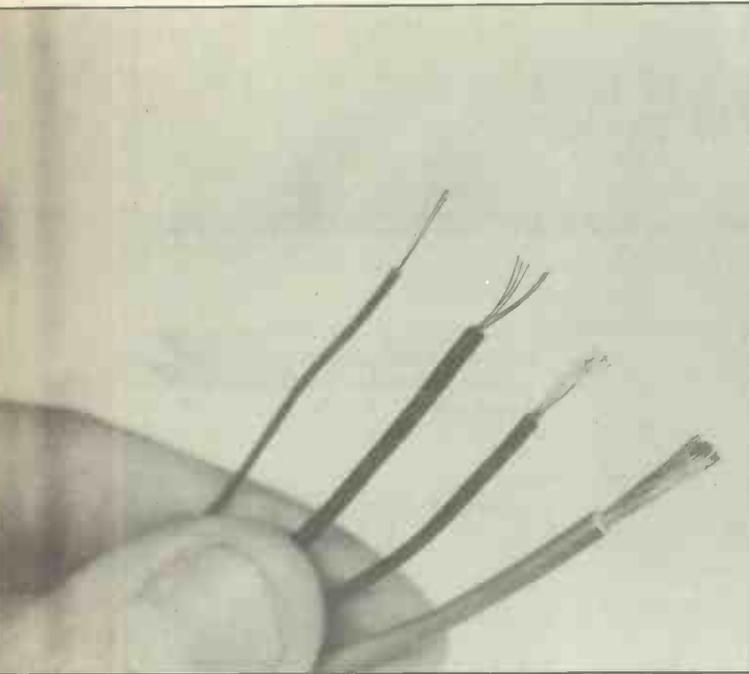


Figure 2. Examples of some different thicknesses of wire with current ratings of 0.5 A, 1 A, 2.5 A and 13 A

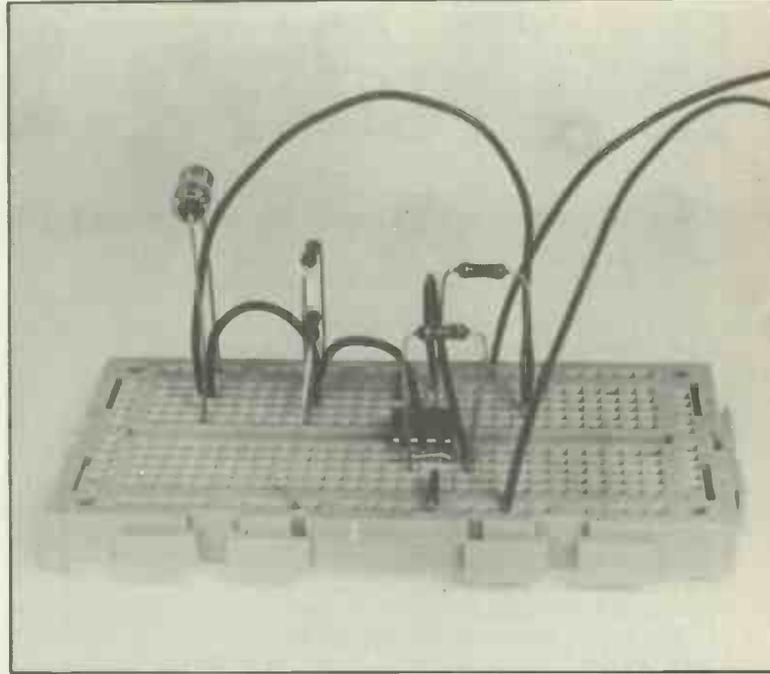


Figure 3. A breadboard circuit which uses single strand wire for all connections

ting leads are separate pieces of wire. In an ideal world this simple circuit would work but, especially in electronics, the world is far from ideal. You see, any two

wires *not* in electrical contact but lying close beside each other form a capacitor — usually represented by two conductive plates separated by an in-

ductor. So between our two amplifier leads and also between the signal lead and the mains lead in Fig. 4, capacitances exist and are indicated by capacitor symbols. These two capacitors form a potential divider and a small part of the mains voltage is superimposed on the signal lead. The amplifier, as you would expect, amplifies this with the result that a 50 cycle-per-second (Hz) 'hum' is heard from the loudspeaker. This frequent problem is called 'mains hum'.

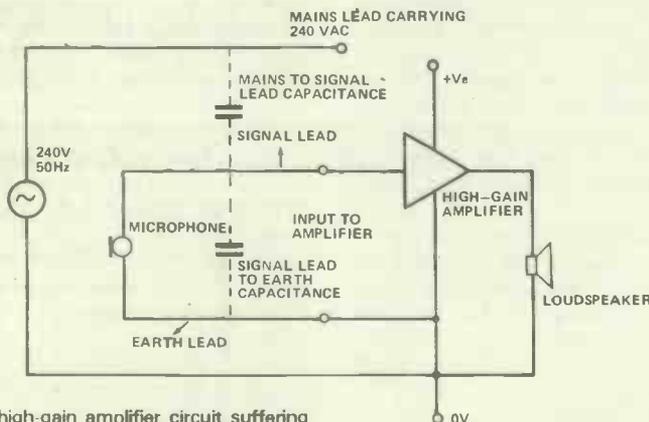


Figure 4. A high-gain amplifier circuit suffering from capacitive pickup

The earthed screen of screened cable effectively eliminates (or at least greatly reduces) the capacitance between the signal lead and mains lead because of the electrical barrier it places between the two. Thus very little superimposed mains voltage exists on the signal lead.

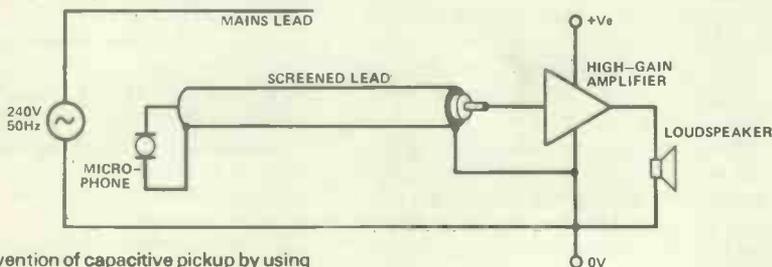


Figure 5. Prevention of capacitive pickup by using screened cable

You might ask why we don't use screened cable everywhere, say for the speaker leads: surely they pick up interference too? Well, of course they do but remember it's just a tiny amount which won't be heard through the speaker. It's a different story at the amplifier output — any tiny amount picked up is *amplified* until it is large enough to be heard.

Well, that about wraps it up for this month. We've seen most of the sorts of wire we're likely to meet in projects. The important thing is to use the right kind of wire at the right place; follow any guidance given in the text and you shouldn't go wrong

HE

MAGENTA ELECTRONICS LTD.

H.E. PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project - you will need to order the instruction reprint as an extra 45p each.

HEARTBEAT MONITOR, Feb. '81	£21.28
HIGH IMPEDANCE VOLTMETER, Feb. '81	£8.98
AUDIO SIGNAL GENERATOR, Feb. '81	£17.21
BACKGROUND NOISE SIMULATOR, Feb. '81	£6.43
TWO-TONE TRAIN HORN, Feb. '81	£4.77 less case
MEDIUM WAVE RADIO, Feb. '81	£6.98
BENCH AMP, Jan '81	£9.19
NICARD CHARGER, Jan '81	£6.98
CHUFFER, Jan '81, less case	£6.44
CAR REV COUNTER, Jan 81, less case	£21.20
Case extra	£5.98
DIGITAL SPEEDO, Dec. '80	£35.89
MODEL TRAIN CONTROLLER, Dec. '80	£16.86
BATTERY CHARGE MONITOR, Dec. '80	£4.91
JACK LEAD TESTER, Dec. '80	£1.99
STEREO POWER METER, Dec. '80	£18.98
PARTY GRENADE, Nov '80	£7.98
TRANSISTOR TESTER, Nov '80	£5.57 inc. test leads
DOUBLE DICE, Nov '80	£13.80
GUITAR PRE-AMP, Nov 80	£5.65 case (dilecast) extra £2.99
BATTERY ELIMINATOR, Nov '80	£14.88
NOBELL DOORBELL, Oct. '80	£11.98
INTRUDER ALARM, Oct. '80	£17.83
FREEZER ALARM, Oct. '80 with probe	£9.42
TUG O' WAR, Oct. '80	£16.98
KITCHEN TIMER, Oct. '80 (2% resistors)	£7.34
MICROMIX, Sept. '80	£7.82
AUTO PROBE, Sept. '80	£3.67 less case
TOUCH SWITCH, Sept. '80	£2.34 less case & contacts
GUITAR PHASER, Sept. '80	£13.84
DEVELOPMENT TIMER, Sept. '80	£11.93
BENCH PSU, Sept. '80	£28.50
EQUITONE CAR EQUALISER, Aug. '80	£14.98
GAZTEC GAS DETECTOR, Aug. '80	£24.98
OP AMP CHECKER, Aug. '80	£4.55
MOVEMENT ALARM, Aug. '80	£5.68
RADIO TIMER, Aug. '80	£6.98
PASS THE LOOP GAME, Aug. '80	£13.98
SOUND OPERATED FLASH TRIGGER, July '80, no skt.	£4.59
18W+18W CAR STEREO BOOSTER, July '80	£29.98 (stereo)
FOG HORN, June '80	£5.65
EGG TIMER, June '80	£8.99 less case
5080 PRE-AMP, May '80	£39.98
SPEED CONTROLLER FOR R/C, April '80	£14.92 less case
DIGITAL FREQUENCY METER, April '80	£35.78
HOBBYCOM: TWO WIRE INTERCOM, April '80	£33.95 (Master)
Sub Station	£3.38 each
ELECTRONIC IGNITION (CD), April '80	£20.87
25-WATT MODULE (5080), Mar. '80	£17.98
PSU MODULE (5080), Mar. '80	£33.75
W/N INDICATOR, Feb. '80 (with switches)	£13.92
DIGI-DICE, Jan. '80	£9.98
BARGRAPH CAR VOLTMETER, Dec. '79	£7.33 less case
RING MODULATOR, Dec. '79	£12.95
GUITAR TUNER, Nov. '79	£10.98
TANTRUM STEREO AMPLIFIER, Oct. '79	£79.50
HOBBYTUNE, Oct. '79	£26.98
ANALOGUE FREQUENCY METER, Oct. '79	£15.52
MULTI-OPTION SIREN, Oct. '79	£15.98
STARBURST, Sept. '79	£19.98 less case
ULTRASONIC SWITCH, Sept. '79	£28.85 less 3 pin mains socket
HOME SECURITY UNIT, Aug. '79	£28.56 less siren
SIREN	£5.09 less case
LED TACHOMETER, Aug. '79	£17.98
INJECTOR TRACER, Aug. '79	£4.34
CONSTANT VOLUME AMPLIFIER, Aug. '79	£15.60
LINEAR SCALE OHMMETER, July '79	£15.98
SHARK, July '79	£25.98
GSR MONITOR, June '79	£9.63
ENVELOPE GENERATOR, June '79	£14.98
PARKING METER TIMER, May '79	£8.79
WHITE NOISE EFFECTS UNIT, May '79	£17.74
TRANSISTOR GAIN TESTER, April '79	£9.98
PHOTOGRAPHIC TIMER, Mar. '79	£16.45
CAR ALARM, Feb. '79	£10.98
SCRATCH/RUMBLE FILTER, Feb. '79	£25.48 Mono £29.98 Stereo

OUR PRICES INCLUDE VAT

80/81 ELECTRONICS CATALOGUE

KITS
ICs
TRANSISTORS
CAPACITORS

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery by FIRST-CLASS POST.
Send 70p in stamps for your copy (7 x 10p or 5 x 14p).

TOOLS
RESISTORS
HARDWARE
CASES

ADVENTURES WITH ELECTRONICS

By Tom Duncan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, Intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S Dec and the components for the projects.
Adventures With Electronics £1.90
Component pack £16.72 less battery.

ADVENTURES WITH MICROELECTRONICS

Same style as above book. 11 projects based on integrated circuits - includes dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes Bimboard 1 plug-in breadboard and the components for the projects.
Adventures with Microelectronics £2.35
Component pack £27.95 less battery.

H.E. LADDER OF LIGHT, JAN. '81

Complete kit for this novel project includes all components and case for the control module.
10 individual outputs
EXTRA included with our kit only: additional circuit and components for strobe and chase features. LADDER OF LIGHT, JAN '81 £29.98 + 40p p&p.

H.E. MEMORY BANK - SYNTHESISER NOV. '80

Complete kit for this exciting project, includes i.c. with socket, 2 pcbs, case etc. The custom designed i.c. at the heart of this project generates musical sounds which can be stored in its own memory. Features include memory erase, vibrato, speed and depth controls, variable pitch, chord and tremolo etc.
'Synthesiser' Nov. '80 + Dec. '80 £33.95

INTO DIGITAL ELECTRONICS

Current H.E. series Part 1 in Sept. '80. Covers digital electronics from the basics. Circuits are built on a plug-in Eurobreadboard. Reprints of back issues available 45p each. Eurobreadboard and components for series £18.95 less-battery. Components only £12.75.

INTO ELECTRONICS CONSTRUCTION

H.E. 6-part Series: Feb. '80 to July '80. COVERS THE BASICS OF ELECTRONICS - LOTS OF PRACTICAL WORK. Circuits are built on a plug-in Eurobreadboard. REPRINTS AVAILABLE, 45p each part. Eurobreadboard and Components for Series £15.63. Components only £9.43.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR £10.50.
ANTEX SOLDERING IRON 25W £4.98.
SOLDERING IRON STAND £1.98.
SPARE BITS. Small, standard, large 65p each.
SOLDER Handy size 99p.
EUROBREADBOARD £6.20.
LOW COST LONG NOSE PLIERS £1.68.
LOW COST CUTTERS £1.69.
P.C.B. ASSEMBLY JIG £11.98.
P.C.B. ETCHING KIT £4.98.
AM-FM AIRCRAFT BAND PORTABLE RADIO £8.98.
WIRE STRIPPERS AND CUTTERS £2.48.
MULTIMETER TYPE 1, 1,000 o.p.v. with probes 2" x 3/2" x 1" £6.66.
MULTIMETER TYPE 2, 20,000 o.p.v. with probes 5" x 3/2" x 1/4" £11.52.
TELEPHONE PICK-UP COIL 72p.
CRYSTAL MICROPHONE INSERT 58p.
SPEAKERS MINIATURE, 8 ohm 87p. 64 ohm 98p. 80 ohm £1.56.
PILLOW SPEAKER, 8 ohm 98p.
EARRPIECES, Crystal 65p. Magnetic 18p.
MONO HEADPHONES, 2K Padded, Superior, sensitive £2.98.
HEAT SINK TWEEZERS 15p.

3 BAND S.W. RADIO

Simple T.R.F. Design. Covering most Amateur Bands and Short Wave Broadcast Bands. Five controls. Bandset, Bandspread Reaction, Wavechange and Attenuator. Coil section is by Wavechange Switch. Use with Headphones or a Crystal earpiece. Kit contains all the components required including the P.C. Board and Case. Instructions are included with this kit.
KIT £18.97. Headphone extra £2.98.

SOLDER BOBBIN 30p.
DESOLDER PUMP £5.98.
CROC CLIP TEST LEAD SET. 10 leads with 20 clips 99p.
CONNECTING WIRE PACK. 5 x 5 yd. coils 65p.
VERO SPOT FACE CUTTER £1.21.
RESISTOR COLOUR CODE CALCULATOR 21p.
STEREO HEADPHONES. 6 ohm. Padded £4.35.
DESOLDERING BRAID 69p.

MAGENTA ELECTRONICS LTD.

HF7, 98 CALAIS ROAD, BURTON-ON-TRENT, STAFFS, DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI. MAIL ORDER ONLY
ADD 40p P&P. TO ALL ORDERS. ALL PRICES INCLUDE 15% V.A.T. OFFICIAL ORDERS FROM SCHOOLS ETC. WELCOME.
ENQUIRIES MUST INCLUDE S.A.E.
OVERSEAS: SEND ORDER WITH 3 INTERNATIONAL POSTAL COUPONS WE WILL QUOTE EXACT PRICE BY AIR MAIL
EIRE & BFPO ORDERS
U.K. PRICES - LESS 10%
(COVERS V.A.T. REFUND & EXPORT DOCUMENTS). PAYMENT: STERLING U.K. BANK DRAFT, U.K. POSTAL ORDERS or U.K. CHEQUE.
ENQUIRIES: ENCLOSE 2 INTERNATIONAL POSTAL COUPONS.



Windscreen Wiper Controller

An easy-to-build project for the car owner, to stop those smeary windscreens at the flick-of-a-switch




YES, ITS YET another design for a windscreen wiper controller, but in addition to giving single, intermittent wipes, this one can also be used to give several sweeps of the windscreen followed by a pause for a similar length of time. This second mode of operation can be very useful under certain conditions where single strokes of the wipers just tend to smear the screen, possibly even making things worse rather than better.

This circuit is suitable for use with 12 V positive- or negative-earth systems. The wipers are controlled by a pair of normally-open relay contacts which are wired across the ordinary wiper switch, and adding the wiper controller does not affect the operation of this switch. Continuous operation of the wipers can therefore be obtained by using the wiper switch in the usual way.

Construction

The component layout and wiring of the wiper controller are shown in Fig.2. As you can see, we have used one of our usual 10 by 24 hole pieces of 0.1" matrix Veroboards, and so the unit is constructed using the usual techniques.

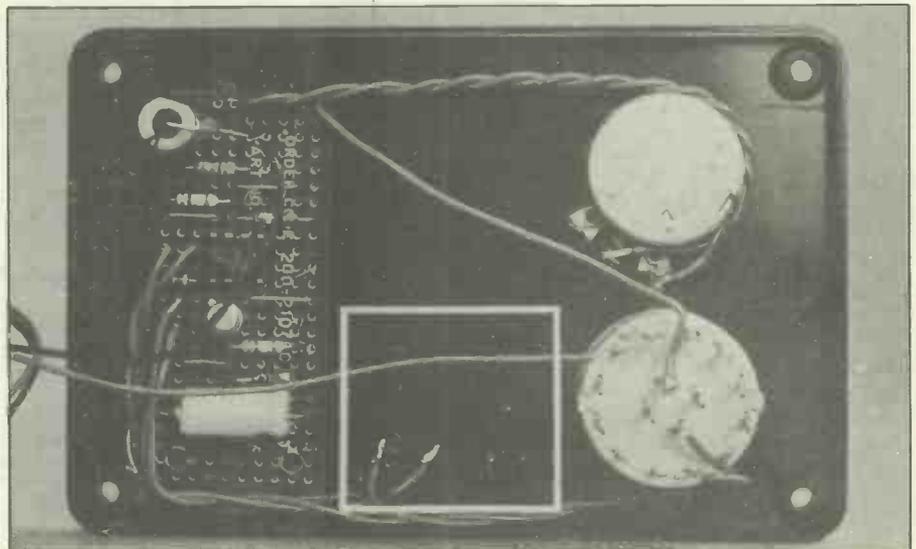The unit is small enough to fit into virtually any of the numerous plastic cases that are available these days. The relay is not mounted on the component panel, but is mounted on the case instead. Modern relays normally have plastic housings, and the most convenient way of mounting these is to simply glue them in place using a really strong adhesive such as an epoxy type.



How It Works

The circuit diagram of the wiper controller is given in Fig. 1, and the unit is based on an operational amplifier used in a simple oscillator circuit.

A popular type of oscillator is used, and with switch SW1 in the position shown there is a square wave output from the oscillator at pin 6 of the IC1. The circuit operates by first charging C2 from the output of IC1 via RV1 and R4, and then discharging it through the same path. Thus the charge (IC1 output high) and discharge times (IC1 output low) are equal, and the square wave output is generated. Integrated circuit IC1 is used to drive the relay by way of Q1. This device is used as an emitter-follower buffer stage that provides the relatively high operating current required by the relay compared with the current drawn by the rest of the circuit. A pair of normally-open relay contacts operate the wipers during the periods when the output of IC1 is high, but switch them off during the periods when IC1's

output is low, giving the required intermittent operation.

If SW1 is switched to its central position, D1 and R3 are connected across RV1 and R4 and thus affect the timing of the circuit. The discharge time of C2 is not significantly affected because D1 blocks any current flow in this direction, but D1 permits a charge current to flow through R3. Because of the low value of R3 this gives a reduced charge time (and time for which the output of IC1 is high) of only about half a second. Thus the relay is only briefly pulsed on, and single, intermittent wipes of the screen are provided.

Potentiometer RV1 controls the time between single wipes of the screen, and in the other mode of operation it governs both the on and off times of the wipers. It gives a range of approximately 5 seconds to 50 seconds.

The third position of SW1 is used to switch the unit off.


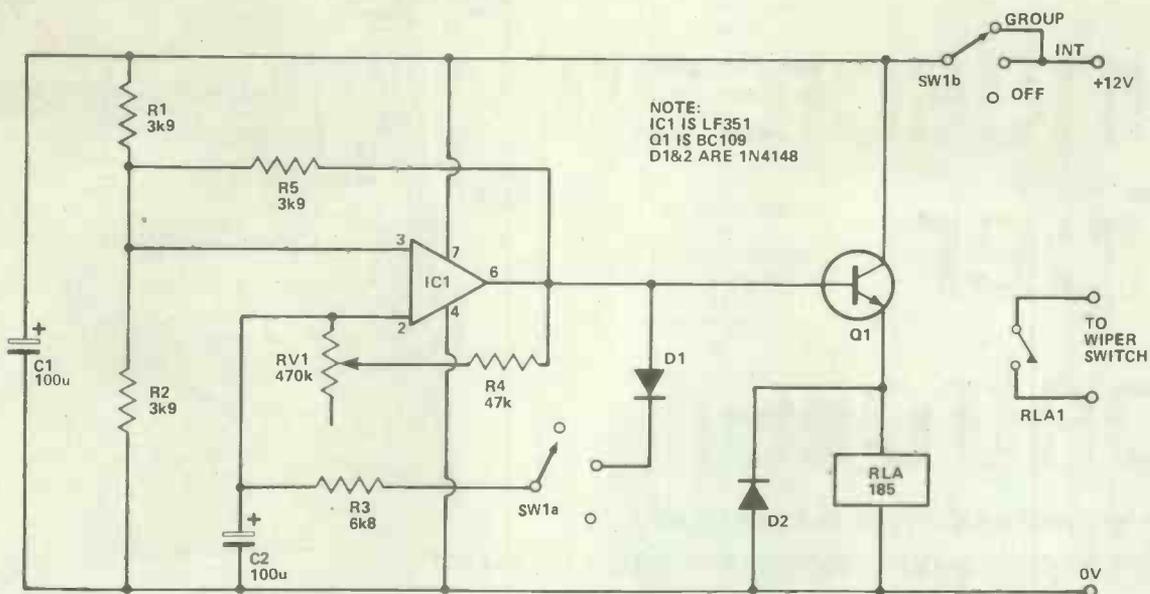


Figure 1. Circuit diagram of the HE Windscreen Wiper Controller

Figure 2. Veroboard layout, underside view and connection details

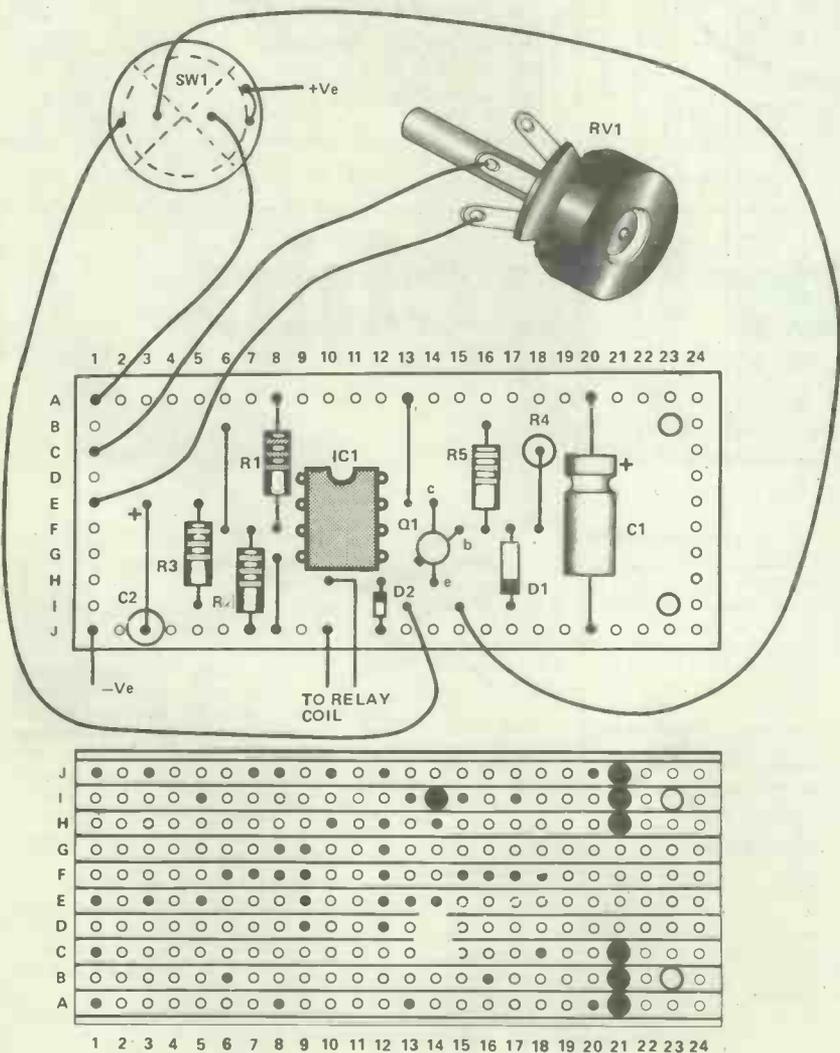

Parts List

RESISTORS (All 1/4 W, 5%)

R1,2,5	3k9
R3	6k8
R4	47k

POTENTIOMETER

RV1	470k linear potentiometer
-----	---------------------------

CAPACITORS

C1,2	100u, 10 V electrolytic
------	-------------------------

SEMICONDUCTORS

IC1	LF351 or TL081CP, bifet operational amplifier
D1,2	1N4148, diode
Q1	BC109, NPN transistor

MISCELLANEOUS

SW1	four-pole, three-way rotary switch
RLA	12 V relay 185R, with at least one set of heavy-duty, normally-open contacts

Case to suit
10 strip x 24 hole, 0.1" Veroboard
Knobs

Buylines

All the components are straightforward types with the possible exception of the relay. This should have a coil operating voltage of 12 V and a resistance of about 185 R or more. It must also have at least one make contact (or a changeover contact used as a make type) having a current rating of 4 A or more at 12 VDC. Suitable types are available from Maplin (eg the 'Relay Flat 12 V').

The parts for your project will cost you about £7 excluding the case.

HE



68
LARGE
PAGES

The larger
Catalogue
that means

FREE POSTAGE
IN U.K.

ADDITIONAL
DISCOUNTS

KEEN PRICES

GUARANTEED
SATISFACTION

GOOD STOCKS

We pay postage

Semi-Conductors • I.C.s • Opto-
devices • Rs and Cs in great variety
• Pots • Switches • Knobs •
Accessories • Tools • Materials •
Connectors


ELECTROVALUE

FREE
FOR THE
ASKING

ELECTROVALUE LTD. (Dept. HE4) 28 St. Jude's Road, Englefield Green, Egham, Surrey
TW20 0HB Telephone: (STD 0784) (London 87) 33603. Telex: 264475



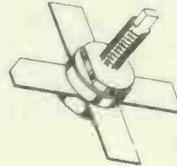RUBBER DUCK CALLING LOGI
BAIRD — "SAY MAC, WHERE DO
I GET R.F. TRANSISTORS.



GAILAN OF COURSE!! THEY'VE
ALWAYS GOT WHAT I WANT,
MOTORLA MRF AND JAPANESE
REPLACEMENT TYPES.



BURDETT ROAD, WISBECH
CAMBS PE13 2PS

TEL: 0945 63281
TELEX 32630

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

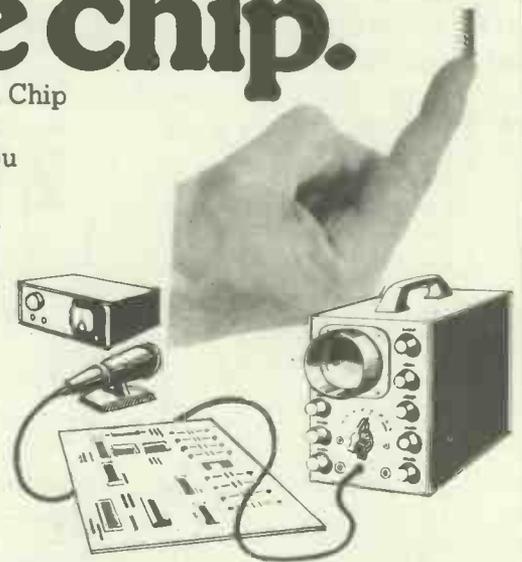- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



Please send your FREE brochure without obligation to -

Name

Address

.....

.....

.....

.....

.....

I am interested in -

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS

(Please state your interest!)

.....

.....

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS. HE/3/813

Steam Loco Whistle



This third and final part of our model train sound effects series. We provide details of how to combine steam whistle, two-tone horn and chuffer projects in one box

OUR LAST MODEL train sound generator of this very popular series (see January and February issues for Chuffer and Diesel Horn projects) is a realistic steam locomotive whistle, created electronically.

Four transistors are used to generate the whistle sound and a single integrated circuit mixes this sound with that produced by our two previous train sound effects circuits.

The whistle can be built and used individually or as an integral part of a complete sound effects unit, built in one case like ours.

Construction

The whistle is built on a printed circuit board (PCB) so construction is very

easy. Follow the layout in Fig. 1 inserting and soldering each component in turn, starting with the resistors followed by capacitors and finally semiconductors. The IC is cheap (a 741) so you may not feel it worth the cost of a holder. If so, solder it carefully, allowing each pin to cool before soldering the next.

Connection details for this project are given also in Fig. 1 and this shows where the other two sound effects are connected if you put them all together in one case, as we did. Drill the case for all connections and switches and simply parallel connect the power supply ie the 9 V battery, to each circuit at the board side of the on/off switch. The output lead from the whistle board to the output jack socket should be a screened lead, with the shielding taken to 0 V.

If you intend to connect your projects together, you will need to make a slight change to the Two-tone

Train Horn board, and this modification is shown in Fig. 3. Simply unsolder and take out capacitor C5 and insert the two resistors Rx and Ry as shown. The output from this board was originally fed to a loudspeaker and the resistors simply act as a potential divider, dropping this output level to one which suits the input of the mixer formed by IC1.



Buylines

All components should be easily obtained and the total cost (excluding case and PCB) should be around £12.

The case we used is from the Samos range stocked by West Hyde and its number is 006.


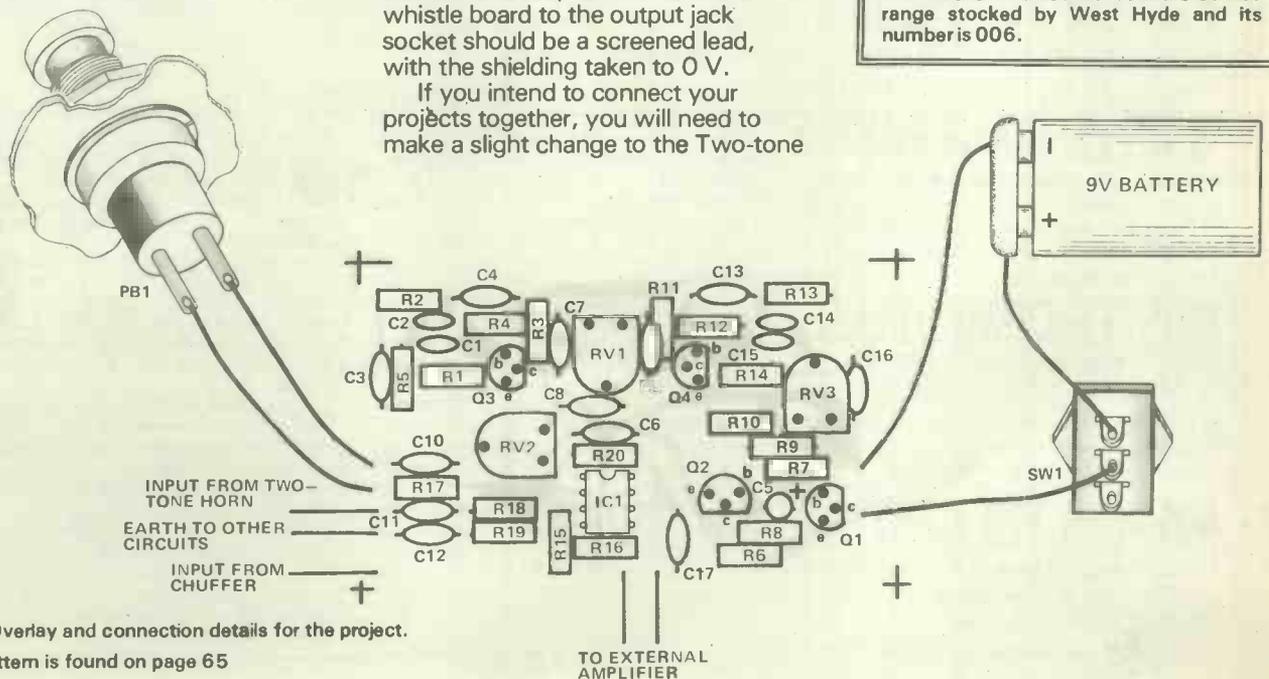


Figure 1. Overlay and connection details for the project.

The foil pattern is found on page 65

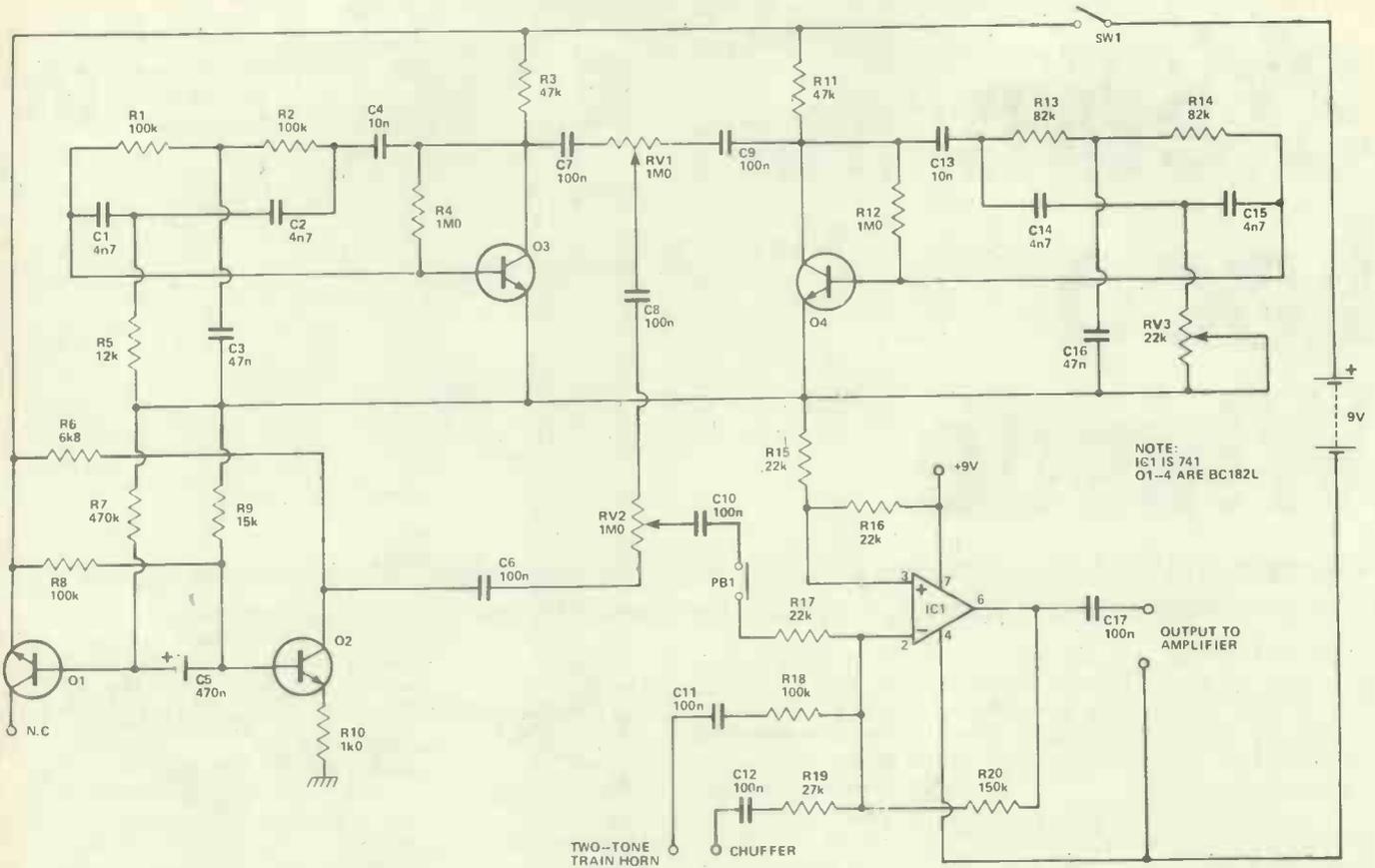

Parts List

RESISTORS (All 1/4 W, 5%)

R1, 2, 8, 18	100k
R3, 11	47k
R4, 12	1M0
R5	12k
R6	6k8
R7	470k
R9	15k
R10	1k
R13, 14	82k
R15, 16, 17	22k
R19	27k

POTENTIOMETERS

RV1, 2	1M0 miniature horizontal preset
RV3	22k miniature horizontal preset

CAPACITORS

C1, 2, 14, 15	4n7 ceramic
C3, 16	47n ceramic
C4, 13	10n polyester
C5	470n, 35 V tantalum
C6, 7, 8, 9, 10, 11, 12, 17	100n polyester

SEMICONDUCTORS


IC1	741 operational amplifier
Q1-4	BC182L NPN transistor

MISCELLANEOUS

SW1	single-pole, single-throw toggle switch
PB1	push-to-make switch
Case to suit (see Buylines)	
Battery + clip	

Figure 2. Circuit diagram of the Steam Loco Whistle

Figure 3 (right). The modification to the Two-Tone Train Horn board — take out C5 and insert Rx and Ry

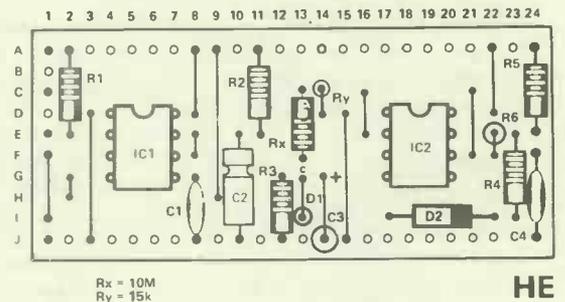

Rx = 10M
Ry = 15k

HE

How It Works

The waveform of a steam whistle is a complex combination of two main things: white noise and an audio frequency oscillation. Both are fairly easy to recreate electronically.

White noise is usually made by a 'noisy' zener diode, the output being amplified to the required level. The generator we used is of the same type as in the 'Chuffer' project of January's issue; i.e. a transistor (Q1) biased into zener mode and a simple transistor amplifier (Q2).

The audio frequency oscillation is a straightforward mixture of two similar (but not identical) sinewaves, which after their addition produces a more complex waveshape than either of the two individual waves. The sinewave generators are known as 'Twin-T' oscillators because the feedback components (eg R1, 2 and C3, and C1, 2 and R5) around the transistor (Q3) are in the shape of two letter Ts. The frequency is set by the values of the feedback components and

in this circuit is fixed. The other oscillator frequency is variable because one of the resistors is replaced by a preset (RV3). At RV3's mid-position the frequency is about the same as that of the other oscillator.

Preset RV1 mixes the two sinewaves so that an appropriate waveform is obtained. Similarly, RV2 mixes this waveform with the white noise produced elsewhere in the circuit. Adjustment of the three presets will result in the required sound.

Integrated circuit IC1 is an operational amplifier used as a simple mixer/amplifier which combines the steam whistle, chuffer, and two-tone horn sounds into one, suitable for amplification by an external amplifier (say your stereo system).

The gain of the mixer is determined by the ratio of R20 to the input resistances, R17, 18 or 19, of the channel concerned and so by varying the chosen resistor the levels of the individual sounds in the mix can be altered to suit.

Get a great deal from Marshall's

CRIMSON ELEKTRIK HI FI MODULES

CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48
CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00
CPR1	Pre Amp	£32.17
CPR1S	" "	£42.52

SINCLAIR INSTRUMENTS

Digital Multimeter	
"	PDM35 £ 34.50
"	DM235 £ 52.50
"	DM350 £ 72.50
"	DM450 £ 99.00
Digital Frequency Meter	
"	PFM200 £ 49.80
Low Power Oscilloscope	
"	SC110 £139.00
TF200 Frequency Meter	
"	£145.00
TGF105 Pulse Generator	
NEW	£ 85.00
LCD Multimeter	
"	TM351 £99.00
LCD Multimeter	
"	TM352 £49.95
Prescaler	
"	TP600 £37.50

ILP HI FI MODULES

Power Amplifiers

HY30	£ 7.29
HY50	£ 8.33
HY120	£17.48
HY200	£21.21
HY400	£31.83

Pre Amplifiers

HY6	£ 6.44
HY66	£12.19

Power Supplies

PSU30	£ 4.50
PSU36	£ 8.10
PSU60	£13.04
PSU70	£15.92
PSU180	£21.34

MULTIPLEX NICKEL CADMIUM CELLS

Type S101 (HP4)	£0.98
Type SubC (HP11)	£1.75
Type SubD (HP2)	£1.95
Friwo Chargers for above	
Penlight 4: accommodates	
1-4 size HP7	£5.50
Combibox FW611:	
accommodates	
HP7, HP11	£13.25

NOTE ALL PRICES NET. EXCLUDING VAT. POSTAGE/PACKING

New


Presensitised PC Boards, Developer. U.V. units.

Toyo miniature Fans 230v AC £9.95

Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95

Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

Just one of the exciting Leader range

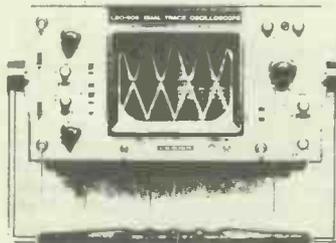

£299 + VAT

LB0508A OSCILLOSCOPE
With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.


A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA.
Industrial Sales: 01-328 1009
Mail Order: 01-624 8582 24hr service.

Also retail shops: 325 Edgware Road, London W2.
40 Cricklewood Broadway, London NW2. 85 West Regent St., Glasgow. 108A Stokes Croft, Bristol.

ARE YOU INTERESTED IN ELECTRONICS?

THEN YOU SHOULD KNOW ABOUT VERO.

We manufacture a wide range of products for the electronics industry and can make available to you a selection suitable for project work. We offer you a large choice of Veroboard and circuit board accessories, including the latest solderless breadboard — VEROBLOC, which enables you to use those valuable components time and time again. Use a piece of Veroboard to save a successfully completed circuit and choose a box or instrument case from our vast range to give your project that professional touch.

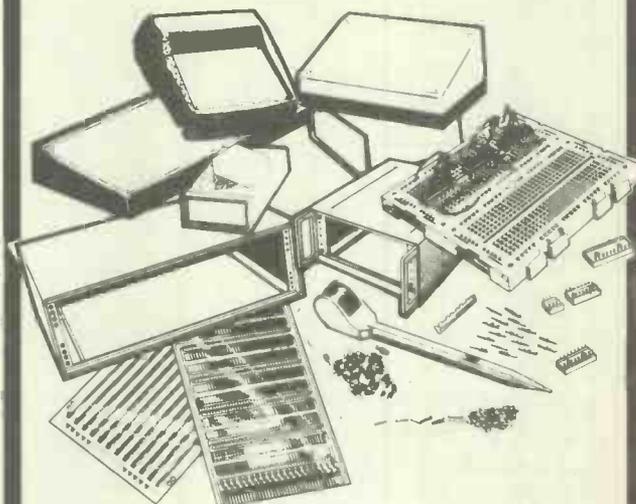

For further details and a copy of the brochure please fill in the coupon below.

Verob Electronics Ltd.
Retail Department.
Industrial Estate,
Chandler's Ford.
Hampshire. SO5 3ZR.
Tel. (042 15) 62829

**vero
vero
vero**

Verob Hobbyist Brochure.
I enclose 40p. for package and postage

Name _____

Address _____

POPULAR KITS AND PARTS

TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox - all electronic parts and circuit £2.30.

RADIO MIKE

Ideal for discos and garden parties. allows complete freedom of movement. Play through FM radio or tuner amp £6.50.

SAFE BLOCK

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit £1.95.

LIGHT CHASER

Gives a brilliant display - a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase-patterns and a strobe effect. Total output power 750 watts per channel. Complete kit. Price £18. Ready made up £4 extra.

FISH BITE INDICATOR

enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loud speaker emits a shrill note. Kit. Price £4.90.

6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit, includes case materials, six transistors, and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy, if you have an amplifier to connect it to on a pair of high resistance headphones. Price £11.95.

SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (give best results) £3.75. Kit includes chassis and front but not case.

RADIO STETHOSCOPE

Easy to fault find - start at the aerial and work towards the speaker - when signal stops you have found the fault. Complete kit £4.95.

INTERRUPTED BEAM KIT

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components - relay, photo transistor, resistors and caps, etc. Circuit diagram but no case. Price £2.30.

OUR CAR STARTER AND CHARGER KIT has no doubt saved many motorists from embarrassment in an emergency you can start off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, diode switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

G.P.O HIGH GAIN AMPSIGNAL TRACER. In case measuring only 5 1/4in x 3 3/4in x 1 1/4in is an extremely high gain (70DB) solid state amplifier designed for use as a signal tracer on GPO cables etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4 1/2v battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp etc. An absolute bargain at only £1.85. Suitable 80 ohm, earpiece 69p.

VU METER

Edgewise mounting through hole size 1 3/4" x 1/8" approx. These are 100 micro amps f.s.d. and fitted with internal 6 volt bulb for scale illumination, also have zero reset. The scale is not calibrated but has very modern appearance. Price £2.88.

BALANCE METER. Edgewise mounting 100 UA centre zero. Price £2.30.

1 7/8in SQUARE PANEL METER. Eagle full vision plastic front, 50 UA. Price £4.60. 1mA Price £4.03.

WATERPROOF HEATING WIRE. 60 ohms per yard. This is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses - around water pipes, under grow boxes, in gloves and socks. 23p metre.

DIAL INDICATOR. As used in toolmaking and other precision measuring operations, the famous John Bull accurately shows differences of 0.1mm. A beautifully made precision instrument, price in most toolshops would be £12-£15. We have a fair quantity. Price £9.20.

COMPONENT BOARD Ref. W0998

This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including four 3 amp 400v types (made up in a bridge), 8 transistors, type BC107 and 2 type BF511, electrolytic condensers, SCR ref. 2N 5062 25 Out 100V DC and 100uF 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

FRUIT MACHINE HEART. 4 wheels with all fruits, motorised and with solenoids for stopping the wheels with a little ingenuity you can defy your friends getting the "jackpot". £9.95 + £4 carriage.

DESOLDERING PUMP

Ideal for removing components from computer boards as well as for service work generally. Price £6.35.

4-CORE FLEX CABLE

White pvc for telephone extensions, disclights, etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

MUGGER DETERRENT

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

HUMIDITY SWITCH

American made by Honeywell. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch. Very sensitive breathing on it for instance, will switch it on. Micro 3 amp at 250V a.c. Only £1.95.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings-2000 o.p.v. mirrored scale.

11 instant ranges measure:

DC volts 10, 50, 250, 1000.

AC volts 10, 50, 250, 1000.

DC amps 0-100 mA.

Continuity and resistance 0-1 meg ohms in two ranges.

Complete with Test Prods and instruction book showing how to measure capacity and inductance as well.

Unbelievable value only £6.75 + 50p post and insurance.

FREE Amps ranges kit to enable you to read DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini-tester and would like one, send £2.50.

SUPER HI-FI SPEAKER CABINETS.

Made for an expensive Hi-Fi outfit will suit any decou. Resonance free cut-outs for 8in woofer and 4in tweeter. The front material is carved Dacron, which is thick and does not need to be stuck in and the completed unit is most pleasing. Colour black. Supplied in pairs. Price £6.90 per pair (this is probably less than the original cost of one cabinet). Carriage £3 the pair.

RADIO CHASSIS BARGAIN

3 waveband radio with stereo amplifier. Made for incorporation in a high-class radiogram, this has a quality of output which can only be described as superb. It is truly hi-fi. The chassis size is approximately 14". Push buttons select long, medium, short and gram. Controls are balance, volume, treble and bass. Mains power supply. The output is 6+6 watts. Brand new and in perfect working order, offered at less than value of stereo amp alone, namely £6.90. Post £2.00.

MULLARD UNILEX

A mains-operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy-to-assemble modular form this should sell at about £30 - but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16 including V.A.T. and postage. **FREE GIFT** - Buy this month and you will receive a pair of Good-man's elliptical 8" x 5" speakers to match this amplifier.

THIS MONTH'S SNIP

THERMOSTAT ASSORTMENT


10 different thermostats, 7 bi-metal types and 3 liquid types. There are the **CURRENT STAT**s which will open to protect devices against overload, short circuits etc. or when fitted say in front of the element of a blower heater, the heat would trip the stat. **APPLIANCE STAT**s, one for high temperatures, others adjustable over a range of temperatures which could include 0-100C. There is also a **THERMOSTATIC POD** which can be immersed, an oven stat, a calibrated **BOILER STAT**, finally an **ICE STAT** which fitted to your waterproof heater element up in the loft could protect your pipes from freezing. Separately these thermostats would cost around about £15 - however, you can have the parcel for £2.50.

WALL MOUNTING THERMOSTAT.

The Danfoss, a handsome 2 tone, intended for living rooms but is just as efficient in a greenhouse or store. It is suitable for normal air temperature range 32F-80F. Price £4.60.

TANGENTIAL HEATER UNIT

A most efficient and quiet running blower-heater by Solatron - same type as is fitted to many famous name heaters - comprises mains induction motor, long turbo fan, split 2kw heating element and thermostatic safety trip. Simply connect to the mains for immediate heat. Mount in a simple wooden or metal case or mount direct onto base of say, kitchen unit. Price £5.95, post £1.50. Control switch to give 2kw, 1kw, cold blow or off available 60p extra, 3kw model £6.95. Control switch 95p.

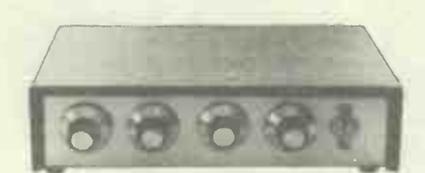

3KW MODEL £6.95 + £1.50 P & P

3-CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2,000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for Disco work. This unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting. Fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £12.95 in kit form or £7.95 assembled and tested.

SUPER CONSTRUCTOR'S SNIP

Here's a super bargain for you. 100 twist drills, regular toolshop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic, etc. from the tiniest holes in P.C.B. right up to about 5mm. Don't miss this snip - send your order today.

TERMS: Cash with order - but orders under £10 must add 50p to offset packing, etc.

BULK ENQUIRIES INVITED - PHONE HAYWARDS HEATH 54563 ACCESS & BARCLAYCARD WELCOMED

J. BULL

(Electrical) LTD.

(Dept. HE), 34-36 AMERICA LANE HAYWARDS HEATH, SUSSEX, RH16 3QU

IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived - often bargains which sell out before our advertisement can appear - It's an interesting list and it's free - just send S.A.E. Below are a few of the Bargains still available from previous lines.

DUE TO THE HIGH & RISING PRICES OF FUEL many companies and probably many householders are looking around for ways of saving some of this cost. One Company bought a number of fans from us and fitted these in the ceiling of their workshops where the hot air tends to collect and they blow this hot air downwards. Another Company has bought fans from us to suck the exhaust fumes through a central heater through a zig-zag of asbestos pipes, the asbestos pipes being in a separate chamber which becomes a hot air chamber, the hot air from this is blown through ducting to wherever it is needed. Basically, they have cut out the normal chimney and replaced this with one of our high power extractor fans. If you have any other good ideas on heat cost saving, let us know and we will pass it on to other readers.

EXTRACTOR FANS

Ex-computer made by Woods of Colchester, ideal also as blower, central heating systems, fume extraction, etc. Easy fixing through panel, very powerful 2,500 r.p.m. but quiet running. Choice of 2 sizes, 5" £5.50, 6" £6.50, post £1 per fan. All mains operated.



PING PONG BALL BLOWER-UPPERS

Have you got to organise a party or charity fund-raising event? Then one always popular way is to have ping pong balls going up and down and being caught. We have some powerful blowers and these would be ideal for this, and of course for more serious purposes. They are 4-stage blowers, coupled to synchronised AC mains motors of approximately 1/8 h.p. They have a terrific suction as well as a high velocity blow. Ex-computers, price £26.

RECHARGEABLE SOLID GEL BATTERY. 12V 5AH, new and unused, made by or for Eplow Corporation of California. Dimensions 6in. long, 3 3/4in. high and 2 1/2in. wide. Regular price of similar batteries, R.S. Components, is £26. Limited quantity available at £15.80.

E.H.T. UNITS. One of our specialities has always been E.H.T. transformers, and we probably have bigger stocks than most of our contemporaries. It is surprising what uses these high voltages can be put to - killing flies and weeds, lighting central heating boilers, lifting paper, extracting dust, etc. A new one this month is 14.5 KV (d.c.) 0.5mA. Made by ADVANCE ELECTRONICS, this unit is completely enclosed and has input and output sockets - size of the unit is approximately 6in. x 3in. x 3 3/4in. Price is £15.38, post £1.

To remind you of the E.H.T. Transformers we stock, here is a list:

3-4 KV	3 mA	ex equipment	£2.90
5 KV	5 mA	ex new equipment	£7.15
5 KV	5 mA	with outer casing	£9.45
8.5 KV	10 mA	totally enclosed with E.H.T. outlets	£15.50

LEDS are used increasingly and are now being recommended for nearly all indicators and for games and novelties. Due to a fortunate purchase, this month we are able to offer 10 red led's for £1. These are the small ones equivalent to the TL 209. Bulk price £60.00 per 1,000 + V.A.T.

FIG. 8 FLEX is always in demand. We are able to offer white Fig. 8.5 amp type on 50 metre roll for £2.00, ditto but dark grey with tracer lead, suitable for speaker extensions, 50 metres £3.38.

300 WATT MERCURY VAPOUR LAMP. Mazda, ref 90-5104 MAT/V blended. These give a really powerful light but, of course, have to be used with their correct control gear. We are expecting to get this control gear early in the New Year. Price of the lamp is £38 + 25p. Post 50p.

ANTI-FROST THERMOSTAT. The normal refrigerator type thermostat switches off as the temperature falls and so is not suitable for anti-frost devices. However, we have the ice-stat - this switches on as the temperature falls and is set to switch on just above freezing point. It is a skeleton type stat so would require boxing but the price is modest at £1.10.

THIN CONNECTING WIRE 500 metre drums, 7 stranded copper core p.v.c. covered available in 10 different colours. Price £7.15.

SUPER BREAKDOWN PARCEL with free gift of a desoldering pump, perhaps the most useful breakdown parcel we have ever offered. Consists of 50 nearly all different computer panels on which you will find: over 300 ICs, over 300 diodes, over 200 transistors and many hundred other parts, resistors, condensers, multi turn pots, rectifiers, SCR etc. etc. for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel, +£1.27 VAT +£2 post (it's a big parcel).

TIME SWITCH BARGAIN. Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs £2.50.



EXTENSION LEAD BARGAIN. We all know how especially in the cold weather, p.v.c. leads lose a lot of their flexibility, in fact some poor grade p.v.c. can be quite stiff and awkward, and will not stay put. We have an extra flexible twin round cable. This is highly suitable for lead lamps, vacuum cleaners, in fact any portable device which does not need an earth. The regular price of this very flexible cable which is suitable for up to 7.5 amps is 30p per metre, and that is buying 1,000 metres at a time. However, this month you can buy 50 metres for £5.00 + 75p + 60p post or 250 metres for £22.00 + £3.30 + £3.00 post.

EXTRA LIGHTWEIGHT HEADPHONES. Stereo, but these weigh only 50 grams (approx. 2oz.). Intended for use whilst playing your instrument in a band, or in normal headphones operation. Japanese made, and extremely good quality. £7.00 + £1.10.

COMPUTER CORNER. PRINTER TERMINAL UNIVAC reference DCT1000, this is a floor standing mains operated printer, which takes a 14" wide paper complete with electronics - in a good clean condition, but untested. Price: £75 + £11.25, plus delivery at cost.

8-BIT PUNCH AND READER UNIVAC. Combined is a neat case, this is their model no. 0925-15. Made by the Roytron Company of America, Roytron number being 572-1. This is a desk standing instrument with input and output leads made for 115v operation. The case has a perspex view window and drawer below to hold the tape. Complete with electronics and in very clean condition. Price £25 + £3.75. Post £4.50.

UNIVAC KEYBOARD MODEL NO. F1308-00. A neat keyboard, probably made to be used with the 8 bit punch and reader. Has 57 encoded keys and 10 function switches on a line along the top. The legends on these switches are: auto-manual, monitor off, run-stop, on-line-off-line, keyboard off, printer off, reader off, punch-off, card reader-off, card punch-off. We have only a few of these, in a new condition. Price £20 + £3. Post £2.

BIG ELECTROLYTICS. Bargain parcel of big electrolytics 8 for £3.30 inc. VAT & P.P.

Bicycle Speedometer

0 — 99 MPH in sixty minutes — that's how long it will take you to build this all electronic, solid-state speedo



WITH PETROL getting dearer, the world's oil supply running out and gas disappearing in a puff of smoke, it can't be long now before pedal-power makes a comeback. We can see it now; CB freaks with pillion-mounted rigs and six-foot whips on the back. Of course there will be lots of research into optimum wheel size, cruising speed etc. That's where this dandy little project will come to your aid. Featuring a two-digit readout, bright red LED display with 1 MPH resolution updated every few seconds it can be built in a trice (ideal if your bike has three wheels) and powered from a single 9 V battery.

Swift And Silent

There have been many bike speedo designs published over the years but never before has so much been brought to so many with so little. Yes, only Hobby Electronics can do this for you! No seriously, before this gets totally over the top, we'll explain. Only three ICs are required plus the two displays and a handful of passive components. The whole thing is very easy to put together so you can assemble it whichever way you like best. The speedometer works by detecting each revolution of the bike's wheel using magnetically-sensitive reed switches with one or more bar magnets mounted on the wheel. The faster you go, the more pulses are counted and the speed displayed increases. The display blanks out while the counters are advancing to avoid a distracting flicker and the count period is set up by adjustment of a single resistor when the speedo is mounted on your bike.



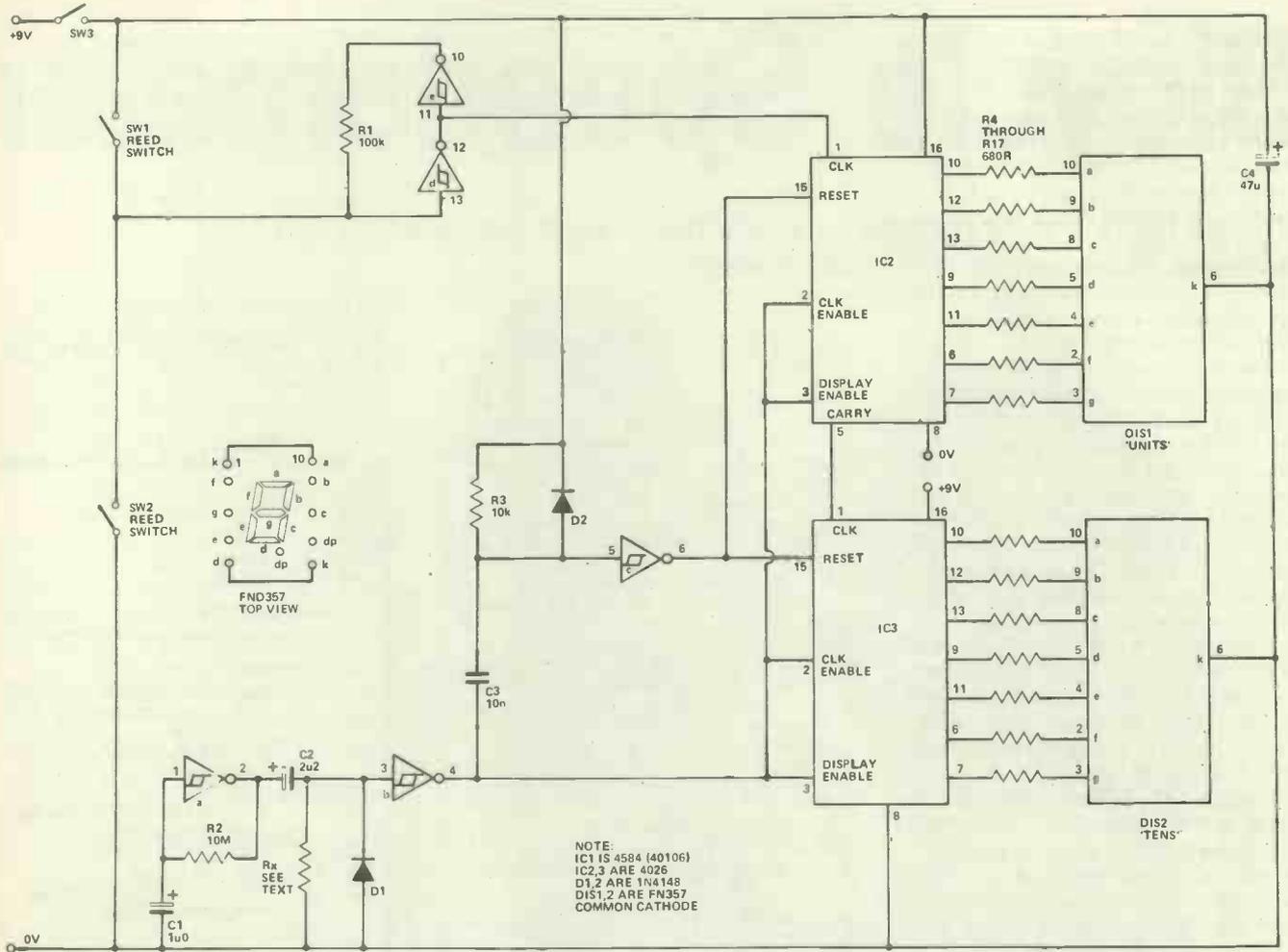


Figure 1. Circuit diagram of the HE Bicycle Speedometer

Okay, so it doesn't speak your weight, but it won't burn a hole in your pocket either!

Construction/Setting Up

Nothing to cause any problems here. As usual we'd recommend you use sockets for the ICs. If you use our PCB design you should have success first time though the circuit is simple enough to be put together on Veroboard or whatever comes to hand . . . except for the original breadboard which went out of fashion when ICs arrived. You try knocking nails into a piece of wood the size of a postage stamp and anyway, you would look silly with a breadboard between the handlebars!

Reed switches come with two main switch actions, either single-pole, single-throw or single-pole, double-throw (changeover). You can use two of the former or simply one of the latter (with its centre contact connected to the common point on

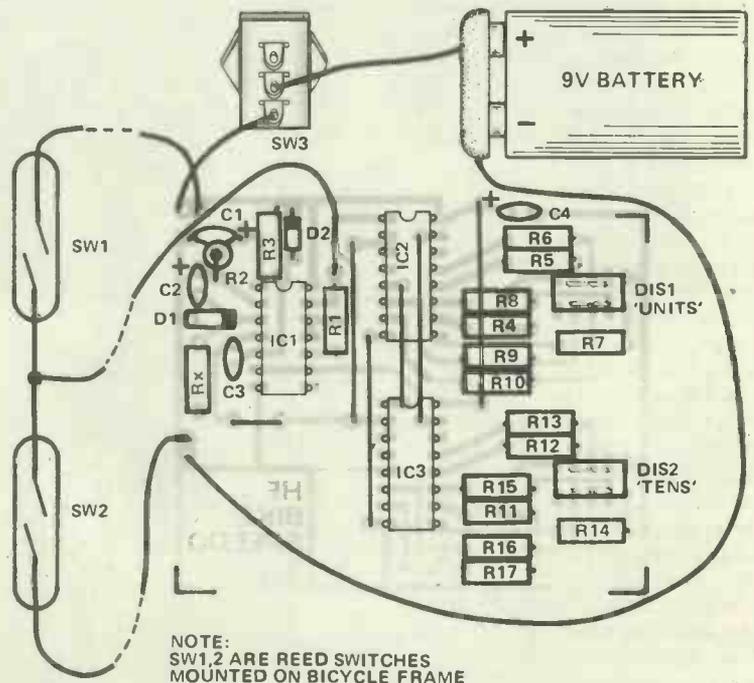


Figure 2. Overlay and connection details. Remember that SW1 and SW2, the reed switches, can be combined as one changeover type reed switch

the circuit board for the two switches (see Fig.2).

Reed switches are usually supplied as glass tubes with the switch contacts brought out to tags at either end. For better protection against the elements we used a single-pole, double-throw type which is sealed inside a waterproof housing (see Buylines). This is more expensive than the open-wired types, but it comes complete with a moulded mounting tab.

The relationship between wheel diameter, gate period and number of magnets required is not a simple one. Toy bikes and bikes with 'baby' wheels will get away with one or two magnets. To obtain a reasonable gate period with larger wheels you'll need to use more magnets. In practice, fix between five and 10 small magnets (the type usually supplied with reed switches) around the rim of the wheel (the more the merrier). To stop them falling off it's best to glue them in place or secure them with pads of double-sided foam tape. Once fixed, a dab of paint or varnish will prevent them from going rusty.

Connect a 1MΩ potentiometer or preset at the Rx position, get on your bike and adjust the pot until you get the right speed reading. Now, measure its value and make it up from fixed value resistors or just fasten the pot or preset onto the board — there's plenty of room.

If you use separate reed switches, make sure that both are never on at once or the battery will be short — circuited through them. To safeguard against this you can connect 10k resistors in series with the wires from the battery.

Ideally you'll need a box with a clear lid (like ours — see Buylines) so you can see the display without having to cut holes in the box, which would let in water. It's best to mount the box using a Terry Clip, centrally on the handlebars so that, if the bike takes a tumble no damage will be done. Lacquer the back of the board so that if any condensation appears in the box no shorts will result. The circuit takes about 40 mA of current when running so two batteries in parallel are advisable and there's just enough room under the PCB to site them.

Alternatively, you might like to make a proper fascia panel to hold a whole set of instruments (oil pressure, ammeter, etc!?) Watch this space!

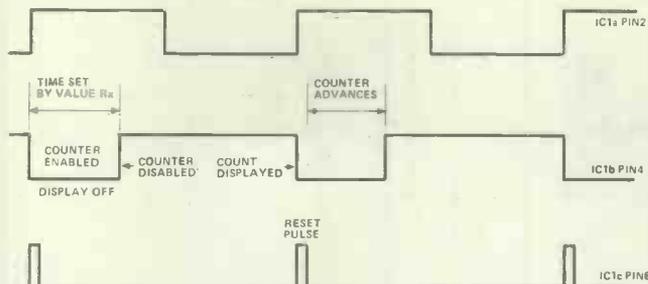


Figure 3. Waveforms within the circuit, not to scale

How It Works

A low-frequency astable oscillator provides the master clock for the circuit. IC1a, R2, C1 take care of this. Pulses are then differentiated and squared up by IC1b and IC1c to provide clock enable and reset signals. Figure 3 shows this in detail.

Integrated circuits IC2 and 3 form a two-digit counter and display driver, which needs only correct timing and clock pulses to operate both 7-segment displays. While IC1b's output is low the counters are enabled and clock pulses from IC1d cause the counters to advance. When IC1b goes high the counters are disabled and the count is displayed on the 7-segment displays. The combination of IC1d and IC1e forms a simple but effective debouncing circuit. Some form of signal conditioning circuit like this is nearly always required when mechanical switches are interfaced to digital counters. Resistors R4 through R17 limit the current in the displays and C4 provides overall decoupling.

Buylines

The semiconductors for this project are obtainable from Technomatic. All other parts should be easily found. One exception could be the hermetically-sealed reed switch mentioned under Construction/Setting Up. This is an RS Components type but it can be ordered through your component stockist. Stock number 339-213.

Approximate price for components (excluding case) is between £10 and £15. The case we used is from West Hyde Developments (tel no. Aylesbury 0296 20441) and is type BOC 430G.

Parts List

RESISTORS

R1	100k
R2	10M
R3	10k
R4-R17	680R

POTENTIOMETER

Rx	1MΩ linear potentiometer
----	--------------------------

CAPACITORS

C1	1u0, 16 V tantalum
C2	2u2, 16 V tantalum
C3	10n ceramic
C4	47u, 16 V tantalum


SEMICONDUCTORS


IC1	4584 or 40106 hex inverting, Schmitt trigger
IC2,3	4026
D1,2	1N4148 diode
DIS1,2	FND357, common cathode, 7-segment displays

MISCELLANEOUS

SW1,2	reed switch inserts
SW3	single-pole, double-throw toggle switch
Magnets	
Battery and clip	
Case to suit	

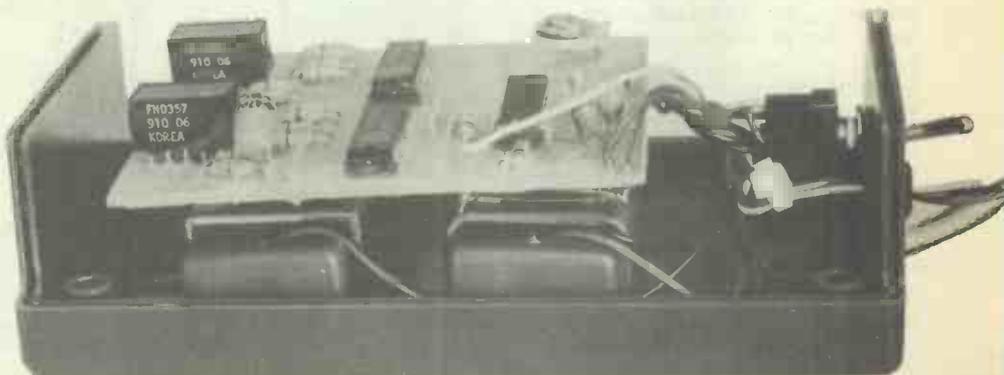Side view of speedometer, showing the two batteries mounted under the PCB



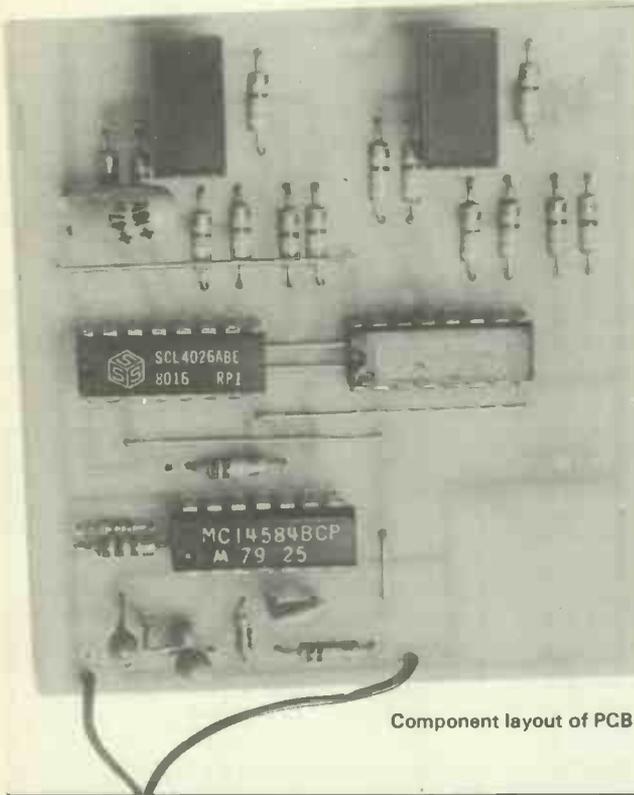

Component layout of PCB



Rider's view of speedometer

HE

The 2001 sweeps the board at only £75*



Get all the waveforms you need — 1 Hz to 1 MHz in five overlapping ranges: stable, low-distortion sine waves, fast rise/fall-time square waves, high linearity triangle waves — even a separate TTL square wave output. Plus high- and low-level main outputs.

An applied DC Voltage at the Sweep input can shift the 2001's frequency: or sweep up to 100: 1 with an AC signal. A pushbutton activates the DC Offset control, which shifts the output waveform up or down on command.

For value for money the 2001 sweeps the rest off the board.

For immediate action — The C.S.C. 24 hour, 5 day a week service
Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately or just clip out the coupon.

*price excluding P&P and 15% VAT

CONTINENTAL SPECIALTIES CORPORATION



C.S.C. (UK) Limited Dept. 14HH
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ
Tel: Saffron Walden (0799) 21682 Telex: 817477

Continental Specialties Corporation (UK) Limited Dept. 14HH, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ			
Model 2001 Sweepable Function Generator	£87.98. (inc. P&P and 15% VAT)	Qty Reqd.	For FREE catalogue tick box <input type="checkbox"/>
Name		Address	
I enclose PO/Cheque for £.....		or debit my Barclaycard/Access/American Express No	
		exp date	

Clever Dick



A good variety this month: from geiger counters to motor bikes, and from Bristol to black chips

Letters, letters, letters, still flooding in . . . I must ask HE's Editor to add 50p to my weekly wage for the trouble.

Let's start off with a nice friendly one from someone who really *appreciates* HE:

To whom it may concern,

My wife purely by an accidental, act of fate bought Hobby electronics instead of E.T.I. Man I have never read such rubbish. Who the hell wants to build a 'background noise simulator', the idea is totally useless and as for the Heart beat Monitor that has to be operated by a push Button Switch, well!

And what about that stupid idiotic cartoon that page could have been used for adverts of which there are already 1/3 of the magazine given over to.

Then there's the "pocket" M.W. Radio, very novel 1/2 foot long, two 109s and cost £7?

Why is your magazine made up from Everyday electronics throw outs?

The only thing worth looking at was the T-shirt ad. and even she was a flop! D.S. Nightingale, Essex

All I can say is that, in a forthcoming issue, we'll have an *electronic* probe for use with the Heartbeat Monitor project. And no, our magazine is *not* made up from Everyday Electronics' throw-outs — we're sure EE can't *afford* to throw its articles away.

The next letter definitely 'cheered' us up:

Dear CD,

In your February edition of HE you printed my letter and called me a nutter — you also told me next time I was feeling rich to send my money to your beer fund, so here it is: it should be enough to buy someone a pint. Onto more serious matters — In your electronics digest volume 1 number 1 (p.67) you show the circuit for a geiger counter. I have built it but cannot find a Geiger tube. Please tell me who sells them. (Type CV2249) M. Broughton S. Yorks

You've embarrassed us with your contribution to our fund: cheers.

As to who sells a Geiger tube, we found that Henry's, 404 Edgware Road, London W2 1ED, stocks two types: CV2246 and CV2247. We understand that they are both 350 VDC working and cost £3 each.

On to two wheels for the next one:

DEAR Richard of the High I.Q.

I have a single cylinder 4-stroke motor cycle with a six volt electrical set-up. Is there any way I can adapt your car speedometer or tachometer to work on my bike It need onley work in top gear, the speedo that is.

K. Lawry

Bristol

P.S. Thanks for a great mag.

P.P.S. Letter short enough?

First things first: no, the speedometer circuit won't work from a 6 V supply because its pre-amplifier is biased for 12 V operation. But the rev counter (tachometer) will work from 6 VDC. (Why onley in *top* gear we wondereyd.)

Second: yes, nice and short thanks very much.

The next one has been buried under the heap for a few weeks, but I thought it worth including as a comment on the 'why are ICs black?' debate.

Dear C.D.

I have long suspected that the alleged superiority of you whiteys is a load of bluff and adequately described as 'white noise!' Will your ego be upset if a poor ignorant black girl from South Africa puts you right on black ICs?

The modern ICs are part of a world of fantasy and if a member of this world says "That is a black IC" it is merely a part of his mode of living since black is not a colour and as such his claim to see it is balmy. As I know from personal experience a matt black package has the advantage/disadvantage of reducing the temperature differential between the inside and outside.

I know of at least three types of binder but your type will suit me well.

Ms. S. Mayekiso

South Africa

I think that explanation deserves a long-distance binder.

Finally, another one from Bristol:

Dear C.D.

Are you a Circuit Diagram?, or maybe a C.M.O.S., I.C. (e.g CD 4001) Or are you just some common or garden reserchist sitting in an office staring at boring letters written by readers?

Anyway, down to the question, Does R. behind a resistor value stand for ohms? and if so why not just put Ω or ohms? Question number 2, is there a simpler way of inserting a C.M.O.S. I.C than using an insertion tool? If so please specify. I think Beasties are superb and want to see more. Thanks for an Excellent mag.

A. Ellis

Bristol

P.S. I don't suppose there is an easier way of getting a binder than spending all that money? (Hint, Hint)

Where a resistor is specified as, for example, 10R then yes, the R stands for 'ohms'. On the other hand, the R can take the place of a decimal point, such as in 2R2 (equivalent to 2.2 ohms). The R is clearer than the Ω (omega) sign for low values and decimal points have a habit of disappearing.

You *can* insert CMOS devices without an insertion tool: most modern CMOS devices are a lot less susceptible to damage by static or other electrical discharges to their pins than some of the earlier types. To be safe, make use of the plastic holder or conductive foam in which the device is supplied. Full details were given in Building Site, HE, September 1980, pages 57 to 58.

We may see Beasties again in HE. True: there isn't usually an easier way of getting a binder than spending all that money.

And that's it for this month. Perhaps next month we'll try and assess from all the letters we've received who *is* HE's youngest reader. Cheers for now. **HE**

CAMBRIDGE LEARNING

Self Instruction Courses

Microcomputers are coming - ride the wave! Learn to program.

Millions of jobs are threatened but millions will be created. Learn BASIC - the language of the small computer and the most easy-to-learn computer language in widespread use. Teach yourself with a course which takes you from complete ignorance step-by-step to real proficiency, with a unique style of graded hints. In 60 straightforward lessons you will learn the five essentials of programming: problem definition, flowcharting, coding the program, debugging, and clear documentation.



BOOK 1 Computers and what they do well; READ, DATA, PRINT, powers, brackets, variable names; LET; errors; coding simple programs. BOOK 2 High and low level languages; flowcharting; functions; REM and documentation; INPUT, IF...THEN, GO TO; limitations of computers, problem definition. BOOK 3 Compilers and interpreters; loops, FOR...NEXT, RESTORE; debugging; arrays; bubble sorting; TAB BOOK 4 Advanced BASIC; subroutines; strings; files; complex programming; examples; glossary.

Also **THE BASIC HANDBOOK (BHB) £11.50** An encyclopaedic guide to the major BASIC dialects. A must if you use other peoples' programs

and: **ALGORITHM WRITER'S GUIDE (AWG) £4.00** Communicate by flow chart! Learn to use Yes/No questions for: procedures, system design, safety, legislation etc.

Understand Digital Electronics

Written for the student or enthusiast, this course is packed with information, diagrams, and questions designed to lead you step-by-step through number systems and Boolean algebra to memories, counters, and simple arithmetic circuits; and finally to an understanding of the design and operation of calculators and computers



BOOK 1 *Decimal, Octal, hexadecimal, and binary number systems and conversion between number systems; negative numbers; complementary systems.* BOOK 2 *OR and AND functions; multiple-input gates; truth tables; De Morgan's Laws; canonical forms; logic conventions; Karnaugh mapping; three-state and wired logic.* BOOK 3 *Half, full, serial, and parallel adders; subtraction; processors and ALU's; multiplication and division.* BOOK 4 *Flip flops; shift registers; asynchronous, synchronous, ring, Johnson, and exclusive-OR feedback counters; ROMs and RAMS.* BOOK 5 *Structure of calculators; keyboard encoding; decoding display-data; register systems; control unit; PROM; address de-coding.* BOOK 6 *CPU; memory organisation character representation; program storage; address modes; input/output systems; program interrupts; interrupt priorities; programming, assemblers; computers; executive programs; operating systems.*

DIGITAL COMPUTER LOGIC & ELECTRONICS. (DCL) £7.50 A course covering the material in italics above, but at a slower pace. (4 vols)

GUARANTEE - No risk to you. If you are not completely satisfied your money will be refunded without question, on return of the books in good condition.

PLEASE SEND ME:-

- CPB (£10.00)
- BHB (£11.50)
- AWG (4.00)
- DDS (£13.50)
- DCL (7.50)

Quantity

FOUR WAYS TO PAY:

- 1) A U.K. cheque or a U.K. postal order (Not Eire or overseas)
- 2) A bank draft, in sterling on a London bank (available at any major bank)
- 3) Please charge my Access/M.Ch Barclay/TrustC/Visa Am. Exp. Diners
- 4) Or phone us with these credit card details - 0480 67446 (ansaphone) 24 hour service.

Card No. _____ Signed _____
THESE PRICES COVER THE COST OF SURFACE MAIL WORLDWIDE. AIRMAIL:
 Eur. N.Af. Mid.E. add 1/3 to price of books; Jpn. Aus. N.Z. Pcfcc add 1/2; elsewhere add 1/2

Name _____
 Address _____

U.K. Delivery: up to 21 days
 Cambridge Learning Ltd., Unit 80, Rivermill Site, FREEPOST
 St. Ives, Huntingdon, Cambs. PE17 4BR, England
 Reg. in Eng. No. 132B762



Multitesters 100,000 opv
 AC volts:- 0 - 5 - 10 - 250 - 1000
 DC volts:- 0 - 05 - 25 - 10 - 50 - 250 - 1000
 DC current:- 0 - 10ua - 25ua - 500ua - 0 - 5 ma - 50 ma - 500 ma - 10 amp
 AC current:- 10 amp
 Resistance:- 0 - 20 ohms - 200 ohms - 5 K ohms - 200 K ohms - 50 K ohms - 200 K ohms - 5 meg ohms - 50 meg ohms
 As a transistor tester
 HFE:- 0 - 5 (NPN) - (PNP)
 ICO:- 0 - 5 ua (NPN - PNP)
 Dims:- 178x 140 x 70 mm
 Please add 30p P.P. per unit order as MT 20



Multitester 1,000 opv
 AC volts:- 0 - 5 - 150 - 500 - 1000
 DC volts:- 0 - 15 - 150 - 500 - 1000
 DC current:- 0 - 1 ma - 150 ma
 Resistance:- 0 - 25 K ohms - 100 K ohms
 K ohms
 Dims:- 90 x 61 x 30 mm
 Please add 30p P.P. per unit order as MT



Multitester 20,000 opv
 AC volts:- 0 - 10 - 50 - 100 - 250 - 500 - 1000
 DC volts:- 0 - 0.5 - 5 - 25 - 125 - 250 - 500 - 1000
 DC current:- 0 - 50 ma - 0.5 ma - 250 ma
 Resistance:- 0 - 3 K ohms - 300 K ohms - 3 meg ohms
 Deibels:- -20 to +63 db
 Dims:- 127 x 90 x 32 mm
 Please add 30p P.P. per unit order as MT 7




Headphones
 High velocity mylar diaphragms. Coiled lead. Finished in a combination of bright aluminium.
 Impedance:- .8 ohms
 Frequency response:- 15 - 22000 HZ
 Weight:- 350 gms
 Please add 30p P.P. per unit order as PH 12

ARROW AUDIO CENTRE

20 NORTH BAR BANBURY OXON OX16 0TF.
TELEPHONE BANBURY (0295) 3677
TERMS: CHEQUE/PO WITH ORDER. CALLERS WELCOME

GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. Note: Circuit diagram and interconnecting wiring diagrams supplied. Rotary Controls: Tuning, on/off volume, balance, treble, bass. Push-button controls: Mono, Tape, Disc, AFC, FM (VHF), LW, MW, SW. Power Output: 7 watts RMS per channel, at better than 2% THD into 8 ohms, 10 watts speech and music. Frequency Response: 60Hz-20kHz within ±3dB. Tape Sensitivity: Output - typically 150 mV. Input - 300 mV for rated output. Disc Sensitivity: 100mV (ceramic cartridge). Radio: FM (VHF), 87.5MHz - 108MHz. Long wave 145kHz - 108kHz. Medium wave.

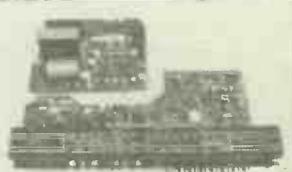

520kHz - 1620kHz. Short wave. 5.8MHz - 16MHz. Size: Tuner - 2 3/4in. x 1 5/8in. x 7 1/2in approx. Power amplifier - 2in. x 7 1/2in. x 4 1/2in. approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. Price £21.50 plus £2.50 postage and packing.

STEREO CASSETTE TAPE DECK ASSEMBLY. Comprising of a top panel assembly and tape mechanism coupled to a record/play back printed board assembly. For horizontal installation into cabinet or console of own choice. Brand new, ready built and tested. Features: Pause control, auto stop, 3 digit tape counter, illuminated twin VU meters with individual level controls, twin mic. input sockets, AC erase system, LED record indicator. (Separate power amplifier required). Input Sensitivity: 6 mV (with level control set at max.). Input Impedance: 47kOhms. Output Level: To both left and right-hand channels 150 mV. Output Impedance: < 10K. Signal to noise ratio: 45 dB nominal. Power Supply Requirements: 12V AC at 300mA/A. Connections: All connections to the unit are via a wander lead terminated with nine-pin plug (socket provided). Dimensions: Top panel - 11 1/2in. x 6 1/2in. Mechanism fits through a cut out 5 1/4in. x 10 1/2in. Clearance required under top panel 2 1/4in. Supplied complete with circuit diagram etc. Price £30.50 plus £2.50 postage and packing. Suitable 12V mains transformer £3.00.

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

BARCLAYCARD

* SAE for current lists * Official orders welcome * All prices include VAT * Mail order only in All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please telephone 0702 527572.

VISA



Into Digital Electronics

This is the seventh — and last — part of this series. To round it off, Ian Sinclair outlines the operation of the microprocessor

The microprocessor is the big chip of all digital chips, and although it's way and above all others in its complication, we've reached the stage where we can understand what it does. This final part, then, is devoted to the microprocessor. There's no practical work this month, because we would need a lot more space to describe a practical layout. One way to get thoroughly acquainted with practical microprocessing would be to refer to the series 'MPUs by experiment' in back numbers of Computing Today. This series ran from July 1979 to June 1980.

What is a microprocessor then? It's a chip which is filled with gates and registers arranged in groups of eight (usually), and with lots of internal connections. What makes it so useful is that the gates can be controlled by signals fed into the microprocessor and can then in turn decide what happens to the next signal or signals along. Everything about a microprocessor is arranged to fit a time sequence, controlled by clock pulses. The sequence never changes — it consists of a set of eight signals which open some gates and close others, followed by more signals which then pass through the open gates. The first set of eight signals is a program instruction, the next lot is data. What's the difference? Only the sequence!

First Mouthful

A group of eight digital signals is called a byte. There's no special reason for having eight. Pocket calculators operate quite happily with four bits at a time, but things can operate faster when we deal with 8 at a time. Large computers deal with 16, 32 or even 64 bits at a time,

which speeds some operations up a lot more. Eight just happened to be a useful increase from four without needing a lot more pins on the package.

What can you do with eight bits, then? The answer is eight times as much as you can do with one. You can carry out eight ANDs, eight ORs, add eight-bit numbers, shift left or right — just the sort of digital operations we should be accustomed to by now. Everything the microprocessor does is based on these straightforward digital operations plus one more — the ability to copy a set of eight bits from one register to another. There's nothing novel about the copying (or transfer) action either, it's just an example of using the output of one register as the input of another.

Force-feeding

The microprocessor, then, doesn't do anything which wasn't done by separate chips previously but it takes up a lot less space and costs a lot less as well. For the guy who was familiar with the way computers were designed long before ICs came along, the microprocessor is a simple way of doing what needed a whole lot of circuitry before. When you've come along a different path, however, from linear ICs into digital ICs, it all looks a bit (sorry!) bewildering, with a language of its own which was borrowed from computing. Let's explain, simplify, and cast a little light.

Suppose you want to AND two bits. Simple, use a two-input AND gate (Fig. 7.1a) and the job is done. If you want to AND eight lots of two bits it just means that you use eight lots of AND gates which will have a total of sixteen inputs and eight outputs, as shown in Fig. 7.1b.

That's 24 pins to be connected to a PCB, 24 joints to go wrong and probably two chips on the board. Now the key to the difference between this conventional digital method of gating and the use of a microprocessor is the timing. With eight 2-input AND gates, you can put in all of your sixteen signals together — you'll have to, otherwise the gates won't operate correctly. The microprocessor will accept only eight

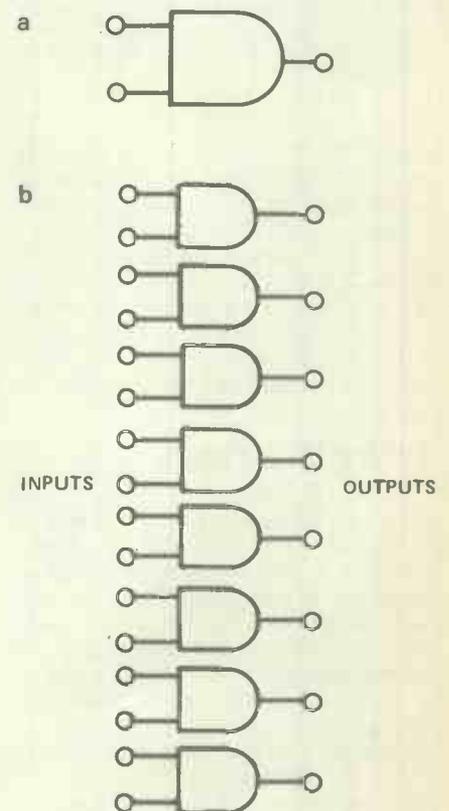


Figure 7.1 One operation — ANDing. A single AND gate (a) can AND two bits. To AND a set of eight bits (b) would need eight AND gates, with sixteen inputs and eight outputs

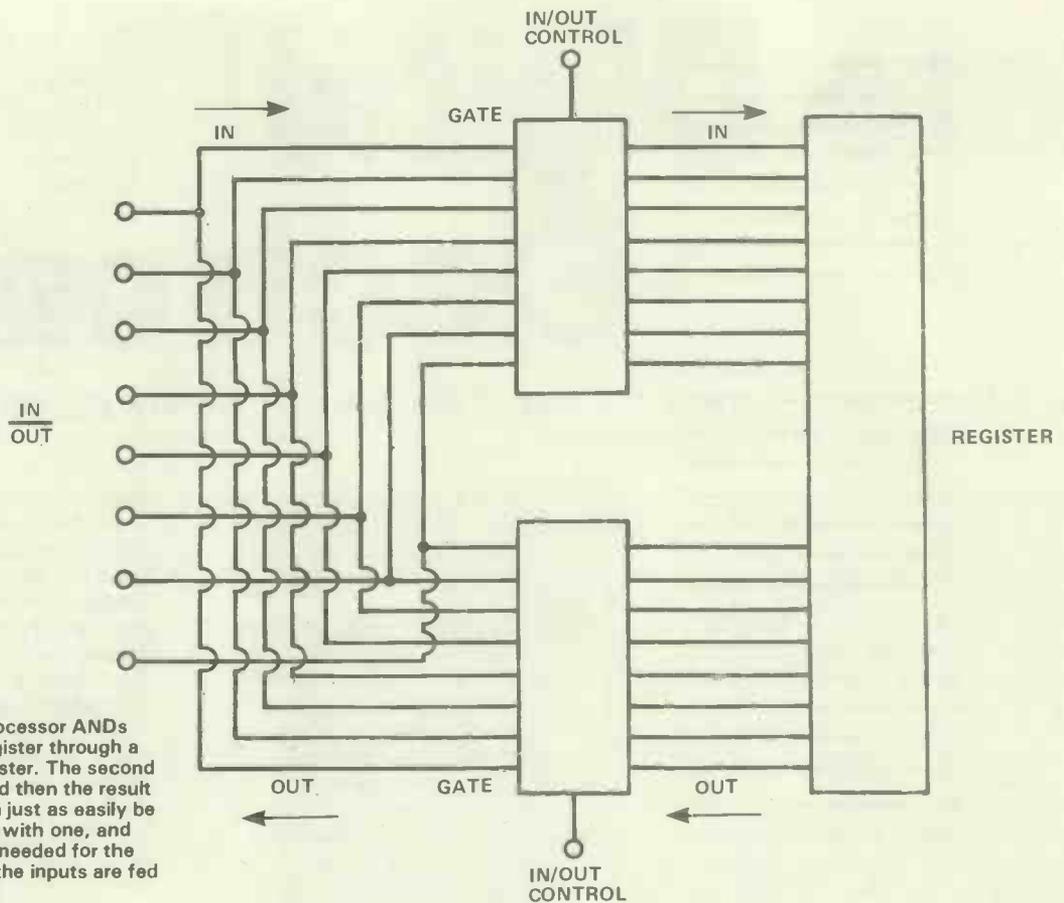


Figure 7.2 How the microprocessor ANDs bits. One bit is fed in to a register through a gate and is stored in the register. The second bit is then fed in, ANDed, and then the result is fed out. The operation can just as easily be performed with eight bits as with one, and only the eight input pins are needed for the inputs and output, because the inputs are fed in at different times

signals at a time, so the only way we can AND two lots of eight is to feed in one lot, store it in a register, feed in the next lot of eight, store that, and then AND the two lots, and feed the results out. It sounds complicated but in a lot of ways it's simpler. For one thing, we need only eight pins for our eight bits, and we can feed in or out of the same set of eight pins (see Fig. 7.2).

Timing The Feeds

Let's look in detail at what has to be done to AND two lots of eight bits. First of all we need to store the first set of eight bits, the first byte of the mouthful, in a register. There has to be an instruction for this, which will open the correct gates within the microprocessor to transfer our first byte into a register (see Fig. 7.3). For this operation, the register will usually be the main working register of the microprocessor and is called the accumulator. One instruction byte will therefore prepare the path from the eight data pins to the accumulator, and the next byte will be our first set of eight bits which are to be ANDed. Having loaded them in,

we now need to tell the microprocessor what it has to do next. The next byte is therefore another instruction which calls on the microprocessor to AND the bits in the accumulator register with the next set of bits which will be fed in, and to store the result in the accumulator. Quite a mouthful that, so we abbreviated it to AND-immediate.

Following that instruction, the microprocessor expects to find the next set of bits we want to AND with the first lot.

The last operation is to deliver the results, so another instruction has to be sent to the microprocessor calling

on it to connect the accumulator to the eight pins which we used to enter each byte, and so transfer the resulting byte out again. At the end of this instruction, the byte appears on the eight pins (the data pins) and the process is completed. The total score is three instructions in, two bytes of data (the bytes we wanted to AND) input and one byte (the result) output: a total of six steps.

Now, for ANDing two bytes of bits together, you might think that six steps of microprocessor action is a pretty poor exchange for just having a couple of AND chips working on two lots of eight bits. You would be

1. INSTRUCTION: Read a set of data bits
2. DATA (8 bits = 1 byte) IN
3. INSTRUCTION: AND this byte with the next set
4. DATA (second byte) IN
5. INSTRUCTION: STORE — send the result out
6. DATA (byte sent out) OUT

Figure 7.3 Sequence of operations for an 8-bit AND. A similar sequence would be used for any other 8-bit logical operation

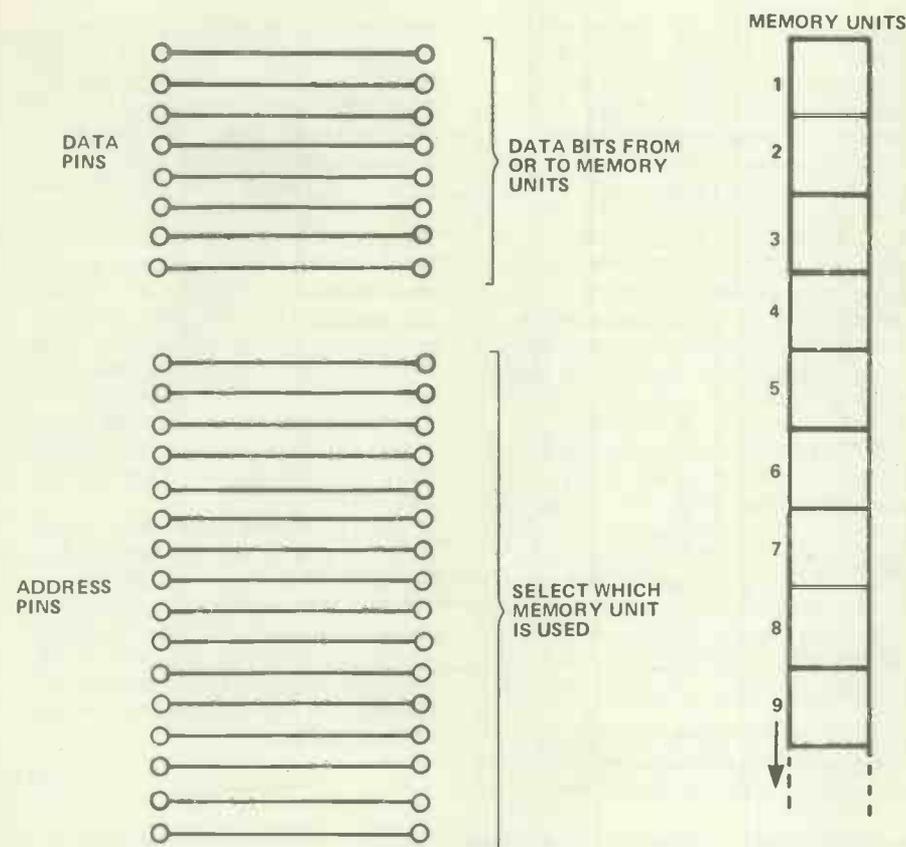


Figure 7.4 Using memory to ensure that instructions and data follow each other in the correct sequence. It is impossible to tell without knowing the sequence, whether a byte is an instruction or data

quite correct, it is a pretty poor exchange, and if you only ever had to AND two bytes together you'd be a mug to go to all the expense and bother of setting up a microprocessor to do it.

Where the microprocessor starts to score is in applications which need more than just a couple of bytes ANDed together. A lot of machine-control units would need several boards full of ICs just to carry out one of the operations which they do. Because the microprocessor operates on instructions, you can add more tasks just by adding more instructions. In addition, you can change the instructions without having to change the microprocessor. If you have a digitally-controlled machine which turns out one part, and the controller uses separate gates, then to make it turn out a new part means swapping boards around. That's what's called a hardware exercise. If the same machine were microprocessor-controlled then only the instructions would need to be changed, and that can be a whole lot simpler.

Once Upon A Time

You'll have started to suspect that this microprocessor caper probably calls for close timing, a bit of the old strict tempo. How right you are! Each stage of microprocessor action is started by a clock pulse, and the clock pulse generator is usually a crystal-controlled oscillator working at 1 MHz or more, so that the instructions are carried out pretty quickly. Now that speed, gratifying though it is, leads to further complications. Remember what the sequence of events was? First of all came the instruction (load) which set up the accumulator to receive the first data byte, then the data, another instruction (AND-immediate), more data, the output instruction and data out. If the clocking rate is as high as a 1 MHz oscillator suggests, how do we make sure that we are feeding the correct byte on to the pins at the correct time? Whether we are feeding in an instruction or a piece of data, it's just one byte at a time, and so the sequence just has to be right. How is it all synchronised?

Thanks For The Memory!

Memory is the answer to the problem. Memory is not something mysterious and new, it's just a word for a set of registers. As far as most microprocessor circuits are concerned, a memory will consist of a set of 8-bit registers, with gates to ensure that only one set of eight bits is connected to the data lines at one given time. The gating system is called addressing, so that when we talk of addressing memory what we mean is passing signals to gates so that one particular register is connected and eight bits can be stored in it or copied from it (see Fig. 7.4).

In the early days, addressing was rather primitive and a lot of memories used a sequence principle, so that the first byte stored in was the first byte out, and the rest followed in sequence. We still use this idea for cassette-tape storage — you start at the beginning of the tape and you record or replay until you are finished. For a lot of purposes, though, it can be very much more useful if you can pick a byte out of any part of memory without having to go through all the bytes which were placed there earlier. This idea is called 'random access', and all the IC chip memories that we use nowadays have random access.

It's addressing which makes this random access possible. If you make your gates so that each binary number placed on a set of inputs — the address inputs — will connect a different register on to a set of data lines, then you have the random access you need, because you don't need to go through the binary numbers in sequence. The old memory system which didn't use address lines (one byte was connected in or out at each clock pulse) is never used these days.

Getting It All Together

Now we can start to see how the microprocessor can carry out its instructions. To start with, all the signals which it's going to need will be stored in memory chips. Taking our example of the ANDing of two bytes, we would need all six bytes stored in memory. The simplest way to do this would be to store them in the same order as they are used, with the 'load first byte' instruction first and the 'store answer' byte last. All we need then is some method of arranging that a byte is connected to



the data lines of the microprocessor at each clock pulse, and this is done by 'address lines' from the microprocessor. The address lines come out on pins, usually sixteen of them, which can be connected inside the microprocessor to various counting registers. Their job is to signal to memory which memory byte is wanted.

Sixteen lines allow us to use binary numbers of up to 16 digits, which in familiar terms means a range of 0 to 65,536. Being able to select up to 65,536 different bytes sounds good, and most microprocessor systems need a lot less, but it's worth remembering that large computers need a lot more memory, which is why microprocessor chips with 24 or even 32 address lines are being developed.

For our ANDing, then, we could arrange things so that the first instruction was connected to the data lines of the microprocessor when the address was 1. (You don't want me to write out fifteen 0s and a 1, do you? I'll stick to ordinary

scale-of-ten if you don't mind!) This address is obtained by a counting register inside the microprocessor whose name is, appropriately enough, program counter. At each clock pulse, the program counter simply advances by one digit unless we instruct it otherwise. When the 'load a byte' instruction has been digested, therefore, the next clock pulse will advance the program counter to 2, and this has to be the memory address for the first of the two bytes we want to AND. At the count of three, the byte which is stored is the AND—immediate instruction, and address number four brings in the second byte to be ANDed. At step 5 another instruction comes in — an instruction which has quite a different effect, because it commands the microprocessor to send a byte out on the next clock pulse. Clock pulse number 6, then causes a byte to be stored — in this example in memory location number 6.


How do the registers tell the difference between sending a byte from memory to microprocessor

(reading) and sending a byte from microprocessor to memory (writing)? Easy, there's a pin which carries a read/write signal. The signal from this pin is normally logic 1, so that the microprocessor reads from whichever part of memory has been activated by the address signals. When the WRITE instruction is received the next clock pulse puts the read/write pin to logic 0, and holds it like that until another clock pulse restores it. That way, a similar pin on each memory chip can be held low to ensure that the gates inside the memory chips are arranged to receive a signal (at the register inputs) rather than send one out (from the register outputs).

Yes, of course there's a lot more to it, but this outline should dispel some of the mystery and explain some of the new words which fly around the microprocessor business. The important point is that once you have swallowed the ideas of digital electronics, microprocessors are just one more byte!

HE

Short Circuit

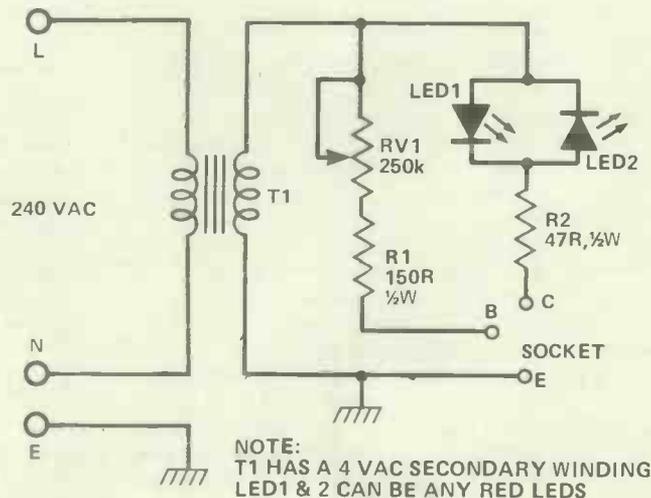

Diode-Transistor Tester

No apologies are made for including this circuit — there is nothing particularly new about it, but it is very useful when checking diodes and

transistors and can save a great deal of time.

Potentiometer RV1 is kept at maximum resistance when a transistor is plugged into the socket, then slowly decreased until one of the LEDs glows brightly depending on the type of transistor (NPN or PNP). If both LEDs light up, the transistor has a short-circuit: if neither

LEDs light the device has an open-circuit.

The same method applies to diodes. If the two leads of the diode are plugged into E and C (anode to E) the PNP LED will light up. If reversed the other LED will glow. As with transistors, if both LEDs light the diode is open-circuit.

By plugging in a new transistor

with a known gain and observing the brightness of the LED and the position of RV1, you will get a rough idea of the gain of unknown devices.

If a metal box is used to house this project then it should be connected to the earth point in the circuit.

GUITAR PHASER	ZD85	Sept. '80	£9.60	HOBBYTUNE	ZD34	Oct. '79	£18.00
BENCH POWER SUPPLY UNIT	ZD87	Sept. '80	£25.00	MULTI OPTION SIREN	ZD36	Oct. '79	£10.50
DEVELOPMENT TIMER	ZD86	Sept. '80	£8.75	ANALOGUE AUDIO			
TOUCH SWITCH (on Vero)	ZD84	Sept. '80	£4.50	FREQUENCY METER	ZD35	Oct. '79	£15.00
AUTO PROBE	ZD83	Sept. '80	£3.00	COMBINATION LOCK	ZD29	Sept. '79	£12.50
REACTION TIMER	ZD82	Sept. '80	£26.50	★STARBURST	ZD30	Sept. '79	£14.50
MICROMIXER (on Vero)	ZD81	Sept. '80	£8.50	LAMP DIMMER	ZD31	Sept. '79	£6.50
EQUITONE CAR EQUALISER	ZD52	Aug. '80	£13.30	ULTRASONIC SWITCH	ZD32	Sept. '79	£21.00
GAS DETECTOR	ZD55	Aug. '80	£22.00	CONSTANT VOLUME AMPLIFIER	ZD28	Aug. '79	£11.50
PASS THE LOOP GAME	ZD56	Aug. '80	£12.00	INJECTOR TRACER	ZD27	Aug. '79	£4.50
RADIO TIMER (on Vero)	ZD57	Aug. '80	£5.50	LED TACHOMETER	ZD26	Aug. '79	£14.75
MOVEMENT ALARM (on Vero)	ZD54	Aug. '80	£5.00	BABY ALARM	ZD25	July '79	£13.50
OP. AMP CHECKER (on Vero)	ZD53	Aug. '80	£4.00	POINTS SWITCH	ZD24	July '79	£12.50
CAR BOOSTER (no speakers)	ZD50	July '80	£18.00	LINEAR SCALE OHMMETER	ZD23	July '79	£14.00
HAZARD FLASHER	ZD48	July '80	£10.50	SHARK	ZD22	July '79	£22.75
★PUSH-BUTTON VOLUME CONTROL	ZD47	July '80	£19.50	G.S.R. MONITOR	ZD19	June '79	£10.50
SOUND FLASH TRIGGER (on Vero)	ZD49	July '80	£3.50	ENVELOPE GENERATOR	ZD20	June '79	£11.79
2 WATT AMPLIFIER (on Vero)	ZD46	June '80	£3.90	DRILL SPEED CONTROLLER	ZD21	June '79	£7.00
METRONOME (on Vero)	ZD51	June '80	£3.50	WHITE NOISE EFFECTS UNIT	ZD18	May '79	£16.85
MICROBE R/C SYSTEM				PARKING METER TIMER	ZD17	May '79	£6.70
(less Servos)	ZD45	June '80	£17.50	DIGIBELL PROJECT	ZD16	May '79	£5.00
FOG HORN	ZD44	June '80	£4.50	VARIABLE POWER SUPPLY			
★EGG TIMER	ZD43	June '80	£6.50	0.30V 1 AMP	ZD15	May '79	£30.00
MINI CLOCK	ZD10	May '80	£26.00	TRANSISTOR GAIN TESTER	ZD76	April '79	£6.50
5080 PRE-AMP	ZD11	May '80	£32.00	CISTERN ALARM	ZD75	April '79	£5.50
TRACK CLEANER	ZD12	May '80	£7.75	MODEL TRAIN CONTROLLER	ZD74	April '79	£26.00
★R/C SPEED CONTROLLER	ZD3	April '80	£9.60	PHOTOGRAPHIC TIMER	ZD73	March '79	£14.50
HOBBY COM	ZD8	April '80	£28.60	TOUCH CONTROL	ZD72	March '79	£9.00
ELECTRONIC IGNITION	ZD2	April '80	£18.25	CASANOVA'S CANDLE	ZD71	March '79	£7.50
DIGITAL FREQUENCY METER	ZD9	April '80	£27.75	SHORT WAVE RADIO	ZD66	Feb. '79	£12.50
SHORT WAVE RADIO	ZD80	March '80	£19.50	SINE/SQUARE WAVE GENERATOR	ZD67	Feb. '79	£22.50
TOUCH SWITCH	ZD79	March '80	£5.00	SCRATCH AND RUMBLE FILTER MONO	ZD68	Feb. '79	£22.50
5080 PSU MODULE	ZD78	March '80	£29.50	SCRATCH AND RUMBLE FILTER STEREO	ZD69	Feb. '79	£25.00
SYSTEM 5080A	ZD77	March '80	£15.00	CAR ALARM	ZD70	Feb. '79	£8.50
PASSION METER	ZD6	Feb. '80	£5.00	FLASH TRIGGER (less flash gun)	ZD65	Jan. '79	£10.50
WIN INDICATOR	ZD42	Feb. '80	£9.00	TOUCH SWITCH	ZD63	Jan. '79	£5.50
INFR RED REMOTE CONTROL	ZD7	Feb. '80	£19.35	VARI-WIPER	ZD64	Jan. '79	£8.00
SCALEXTRIC CONTROLLER	ZD41	Jan. '80	£52.50	GRAPHIC EQUALISER	ZD62	Jan. '79	£25.00
CROSSHATCH GENERATOR	ZD4	Jan. '80	£11.25	PUSH-BUTTON DICE	ZD61	Dec. '78	£6.00
DIGI-DIE	ZD5	Jan. '80	£5.50	AUDIO MIXER	ZD14	Dec. '78	£20.30
RING MODULATOR	ZD1	Dec. '79	£8.50	BEDSIDE RADIO	ZD58	Nov. '78	£12.50
SCALEXTRIC CONTROLLER	ZD39	Dec. '79	£21.50	STEREO AMPLIFIER (HOBIT)	ZD59	Nov. '78	£52.50
BARGRAPH CAR VOLTMETER	ZD40	Dec. '79	£6.60	WAA-WAA PEDAL	ZD60	Nov. '78	£30.00
GUITAR TUNER	ZD38	Nov. '79	£8.50				
★R2 D2 RADIO	ZD37	Nov. '79	£8.60				
TANTRUM	ZD33	Oct. '79	£37.50				

IONISER KIT: ZD13. This negative ion generator gives you power to saturate your home with millions of refreshing ions, without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain filling your room. The result? Your air feels like fresh ocean air, crisp and wonderfully refreshing. All parts p.c.b. and full instructions £10. A suitable case including front panel neon switch, etc., available at £8 extra.

LATE EXTRA

Watchdog Intruder Alarm	ZD89	OCT. '80	£15.75
Temperature Controlled Soldering Iron	ZD90	OCT. '80	£9.00
Freezer Alarm (on Vero)	ZD91	OCT. '80	£8.50
Tug O' War Game	ZD94	OCT. '80	£12.50
Nobell Doorbell	ZD93	OCT. '80	£9.75
Kitchen Timer (on Vero)	ZD92	OCT. '80	£5.50
Light Dimmer	ZD88	OCT. '80	£5.00

All kits contain components as specified plus Texas I.C. sockets, where required, also connecting wire.

FAIRCHILD FLV150 red. 2 LEDs, 10 for £1.00, 100 for £7.50
DALY ELECTROLYTIC CAPACITORS 2000uF 100v £1.50
PHILIPS SCOPE Tube 5" CV2191/DG-13-2 £10

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of kits.

T. POWELL

306 ST. PAULS ROAD, Highbury Corner
 LONDON N1. 01-226 1489

SHOP HOURS:
 MON.-FRI. 9-5.30 p.m.
 SAT. 9-4.30 p.m.



Minimum telephone Orders £5
 Minimum Mail Order £1

0 Level Q&A

Test gear's the topic this month, and Nick Walton discusses moving coil meters and oscilloscopes

We will take a rest from high flying theory this month and consider test gear, in other words the basic instruments used by the hobbyist or the electronic engineer, namely the ammeter, voltmeter, and the ohmmeter as well as that highly versatile and useful device the 'scope or cathode ray oscilloscope to give its full mouthful.

Moving-coil Meters

The most common type of meter today (apart from the ever-increasing range of electronic digital meters) is based on the moving-coil movement. This consists of a small coil of wire free to twist within the magnetic field of a permanent magnet. When the current passes through this coil you will know from a previous article that it creates its own magnetic field. This interacts with the permanent field, resulting in the movement indicated by the pointer. One such meter widely used has a coil resistance of 1000 ohms and a full scale deflection produced by a current of 0.1 mA. This, by Ohm's law, implies a required voltage of 0.1 V for full deflection.

Measuring Amps, Volts and Ohms

You use this basic meter to give you an ammeter which reads currents greater than 0.1 mA by connecting a low value of resistance (called a shunt) in parallel with the coil. For instance, to read up to 1 mA you would choose a shunt resistance value which, for 0.1 V, took all the current except the 0.1 mA you wanted through the coil (see Fig. 1).

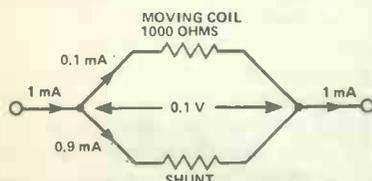


Figure 1. To convert a moving-coil meter into an ammeter, you connect a low-value resistance in parallel with it

Thus if the shunt has to take 0.9 mA for a voltage of 0.1 V it works out to be 111 ohms. Measurement of higher current would need lower-resistance shunts whose value can again be

calculated by using Ohm's law.

Whereas the moving coil meter becomes an ammeter by adding a low resistance in parallel, it can be used as a voltmeter by adding a high resistance in series. For instance, to measure a voltage of up to 1 V, we need the resistance in series to account for 0.9 V to leave the desired 0.1 V across our coil. The current in this resistor, which remember is in series with our meter, must be 0.1 mA and the voltage across it is 0.9 V, all of which is shown in Fig. 2. So again with the help of George Simon Ohm we can deduce that it needs to have a resistance of 9k.

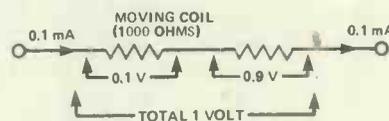


Figure 2. To convert a moving-coil meter into a voltmeter, you add a high-value resistance series with it

When it comes to making connections in the circuit, it is the ammeter you need to be most careful with. A mistake with it can cost you the instrument, whereas with a voltmeter connected wrongly nothing very much happens. You need not think very deeply to realise why the ammeter is vulnerable. When you want to measure a current in a circuit as in Fig. 3, it is as though you need to cut the wire and rejoin it through the ammeter. Since you do not want to reduce the current by the act of measuring it the ammeter must have as low a resistance as possible (ideally zero, though in practice this cannot be achieved) and this really is the trouble.

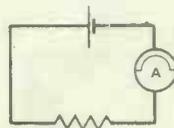


Figure 3. How an ammeter is connected into the circuit

For instance, suppose as previously you needed only 0.1 V to drive the pointer to full-scale deflection and in a moment of aberration you connected it across the resistor where there existed a voltage of 5 V, you would be putting

5 V across a meter designed to take 0.1 V; ie, fifty times too much. This would be the sad end of your instrument so watch out. Actually many ammeters these days are protected by two diodes connected across the ammeter as shown in Fig. 4. At first sight this looks pretty pointless till you remember that even in forward bias a diode needs a definite voltage to make it conduct, for example 0.3 V. Given that the little coil of the meter still needs 0.1 V for full scale deflection, it could probably survive being overloaded to 0.3 V for short periods. Any further overloading will result in one of the diodes conducting quite heavily if necessary thus protecting the instrument itself. But remember the law of nature (Sod's Law) which, when applied here, says that the one ammeter you overload is the one that is unprotected.

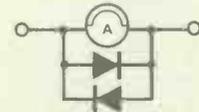


Figure 4. An ammeter fitted with diode protection

The voltmeter is not vulnerable like the ammeter. Since voltage is a difference in potential between two points you always connect it in parallel with the component across which the voltage exists. But there is a problem you need to watch and it is called the loading effect. It is tied up with the fact that connecting everything (even a high resistance voltmeter) in parallel with a component does actually provide an alternative route for the current and on occasions this can lead to damage resulting from a bigger current flow than was intended.

Suppose for instance you had a transistor with a resistance of 20k on the base to keep down the base current to, say, 0.1 mA. If you put your voltmeter — whose resistance could be 20k — across the 20k resistor, between A & B in Fig. 5, the resistance of the combination (voltmeter in parallel with R1) will be only 10k. This could allow too much base current to flow into the transistor which could cause damage. Manufacturers specify what they call a 'figure of

merit' for voltmeters which is expressed in terms of ohms per volt and is actually the reciprocal of current at full-scale deflection. Generally, the ohms per volt rating needs to be much higher (at least, say, ten times) than the value of any resistance across which you might want to measure a voltage. The higher the ohms per volt rating of a voltmeter the more it costs, but electronic voltmeters are now available with figures of merit in excess of 1 Megohm per volt (ie a million ohms per volt).

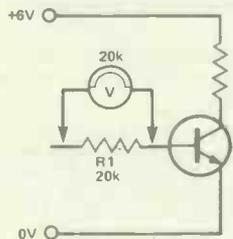


Figure 5. A voltmeter 'loading' the base resistor of a transistor

Ohmmeters are also useful things to have around and the simplest can work using Ohm's Law in the following way. Looking at the circuit in Fig. 6 the unknown resistance is connected between A & B. Suppose the meter reads up to 1 mA, then if there is no resistance between A and B (ie A and B connected together) the pointer will indicate 1 mA (1 V from the battery and 1k in the circuit). So this will be marked out on the scale as zero. If the resistance across AB is now 1k, the total resistance in the circuit will be 2k so the current will be 0.5 mA on the scale which is where 1k will be marked on it. It turns out that the scale is back-to-front and not evenly spaced. Even-spacing on an ohmmeter scale needs sophisticated electronics and costs a lot.

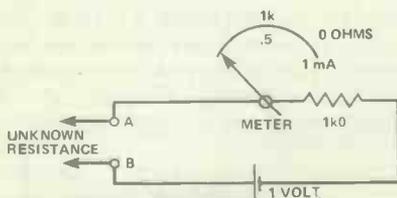


Figure 6. A design for a simple ohmmeter

Oscilloscopes

Our final topic is the cathode ray oscilloscope and the fact that it can fulfil so many functions is what makes it so useful. (See The Oscilloscope, HE, February 1981, pp 18 to 22.) Cost varies from about £100 to several thousand pounds. If you're thinking of buying one then it would be worth look-

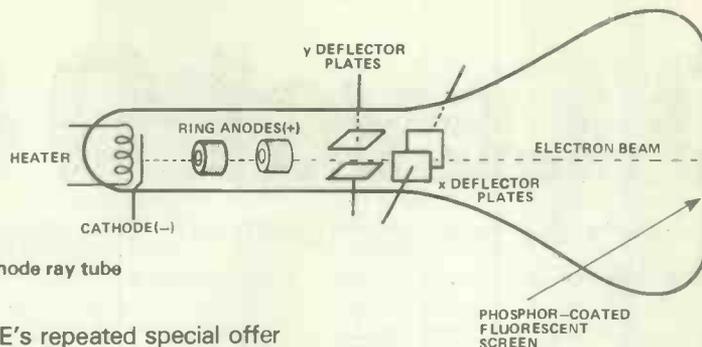


Figure 7. A cathode ray tube

ing out for HE's repeated special offer next month.

Common to every scope is the cathode ray tube which is illustrated in Fig. 7. At the left-hand end you have a heated cathode from which you are boiling off electrons. Persuade these to move in a stream by applying a high positive voltage at the anode and you have what the early workers called cathode rays (since they originated from the cathode.) Now you play a dirty trick on the electrons which were so keen to reach the attracting anodes. The anodes are in fact ring shaped so the electrons go flying through and hit the screen which is coated with a phosphor compound and which emits light when struck by an electron. The function of the second ring is for focusing purposes.

Deflecting The Spot

Having got a sharp little point on the screen, what shall we do with it? Move it around. Indeed it is the movement which lies behind its usefulness. The movement is achieved by the two pairs of deflector plates. If you know the fundamental principle of electrostatics, namely that unlike charges attract, (that is, a positive charge attracts a negative charge) and that like charges repel, then you will have no difficulty in understanding how the deflector plates do their job. If you apply a voltage between a pair of plates, then this is actually identical to putting some excess positive charge on one plate and negative charge on the other. So when the (negative) electrons of the beam enter this region (called, incidentally, an electric field) they will be attracted to the positive side and repelled from the negative side. Looking at Fig. 7 once again, if we suppose the first set of

plates are charged so that the top plate is positive and the bottom negative then the electrons will be deflected upwards. They will not actually hit the deflector plates because they are travelling too fast and are out of the field before they have undergone any more than a few degrees change of course. The first pair of plates is called the Y-plates after the graph-drawing convention which says that when plotting a graph of y against x the vertical axis is y and the horizontal axis is x. Thus you can see from Fig. 7 that the second set of plates is positioned to deflect the plate horizontally which is why they are called the X plates. Thus the two knobs marked 'X shift' and 'Y shift' on the front panel of the instrument (see Fig. 8) simply alter the voltage on the X and Y plates.

But the story does not quite end there and we need to consider refinements to both these controls. In most applications the spot is actually swept across the screen from left to right. It then nips back very smartly and repeats rather like the motion of your eyes as you read this article. The control responsible for this is called the timebase and its settings indicated on the front panel by the control knob are expressed in terms of time taken to cover one centimetre. For instance, a typical setting might be labelled 2 ms/cm which means that the spot takes two milliseconds (that's two thousandths of a second) to cover one centimetre of the screen. Mathematical geni will notice that the units are the reciprocal of speed and it is fun to work out how fast the dot is travelling — in this example a mere 500 cm per second. On good oscilloscopes the maximum timebase setting is around one microsecond (ie a millionth of a second) per centimetre. Faster than about 50 ms/cm the dot just appears as a solid line as your eye cannot keep up



Figure 8. Front panel of an oscilloscope (Kikusui 538A) showing the various controls

with it. It's the timebase control which enables you to time things since you can relate distance across the screen to time in seconds, milliseconds or microseconds. In one particular application shown in Fig. 9 the bunched-up waves on the left hand side of the screen indicate the time for which a hammer was in contact with a metal rod. Contact ceased when the trace went flat. The bunched-up waves occupy 4 cm of screen and, on a timebase setting of 100 us/cm we can conclude that 4 cm across the screen accounts for 400 us, the contact time for the hammer.

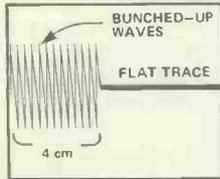


Figure 9. Using an oscilloscope to time how long a hammer was in contact with a metal rod

Additionally if you measure time intervals, you can measure the time for one complete wave to be displayed on the screen, from which you can find the frequency.

You can also measure voltage on the oscilloscope by using what is called the voltage sensitivity control. This control is calibrated in volts per centimetre on the front panel and it simply indicates how far the spot is deflected for a given voltage. So if you were on 5 V/cm setting and the spot jumped up a couple of centimetres as a result of a signal you put in, you would know you had a voltage of $5 \times 2 = 10$ V.

Two great advantages of the oscilloscope as a voltmeter are that it has a high resistance (about a megohm) and secondly that it does not care whether it is looking at DC or AC (any frequency). Perhaps you can see now why anyone with any serious interest in electronics would find an oscilloscope so useful.

That just about rounds things off for this month. Space and time do not permit me to cover logic even though our syllabus requires knowledge or the NOT gate together with the AND, OR, NAND and NOR gates. These are superbly dealt with by Ian Sinclair in the October 1980 issue of HE. Similarly, the multivibrator (astable and bistable) will be dealt with elsewhere in HE, so there's lots to read. Cheers!

CORRECTIONS

The gremlins were going strong in the November 1980 article and corrections should read as follows:

The resistance R_{AB} of two resistors R_1 and R_2 in parallel should read:

$$\frac{1}{R_{AB}} = \frac{1}{R_1} + \frac{1}{R_2}$$

The Ohms' rating (reactance) of a capacitor is given by:

$$\frac{1}{2\pi fC}$$

where $\pi = 3.14$ as in circles, f is the AC frequency and C is the capacitance.

Also,

$$\text{Farads} = \frac{\text{coulombs}}{\text{volts}}$$

$$C = \frac{Q}{V}$$

A microfarad is one millionth of a farad, and in the December 1980 article the formula relating impedances to turns ratio should read:

$$\frac{Z_1}{Z_2} = \left(\frac{N_1}{N_2}\right)^2$$

and in the resonant frequency formula, a square root sign escaped, and it should read:

$$f = \frac{1}{2\pi\sqrt{LC}}$$

HE

GLOBAL ELECTRONIC ENTERPRISES

ELECTRONIC CONSTRUCTION KITS

<p>SUPER CHIP 2</p> <p>Full M/W coverage, uses I.C. ZN414+2 transistors, easy to build diagrams. Good beginners project complete with case and loudspeaker. £8.26 + P&P 65p</p> <p>SUPER CHIP 1</p> <p>Pocket earpiece radio. Performance and looks as above, complete with easy build plans. £6.95 + P&P 55p</p> <p>CRYSTAL RADIO</p> <p>For beginners, no batteries required, complete with case and easy build plans. £2.25 + P&P 50p</p> <p>Money refunded if not satisfied provided goods are returned undamaged.</p> <p>Post and packing included unless stated.</p> <p>All units are checked and tested prior to despatch.</p>	<p>CAR RADIO Manual with speaker/fixing kit £9.25</p> <p>OCEAN CAR STEREO, with built-in auto stop £15.95</p> <p>STEREO Headphones, 8 ohm £6.95</p> <p>POCKET RADIO AM/FM/AIR band with speaker £7.75</p> <p>POCKET RADIO AM/FM with speaker and E/P £6.95</p> <p>HAND ELECTRONIC Football Game £10.95</p> <p>QUARTZ HALOGEN Handheld spotlamps £8.75</p> <p>800 watts Mains Dimmer with magic eye facility £4.95</p> <p>SITCO CASSETTE Recorder D/C, small size £17.95</p> <p>B.S.R. C179 Auto Turntable with ceramic cartridge £18.95</p> <p>B.S.R. C182 with A.D.C. cartridge plinth and cover £38.50</p> <p>LLOYTRON Professional Headphones 4-16 ohm coiled cord, vol./control £12.95</p>
--	---

P/Os and Cheques made payable to:
GLOBAL ELECTRONIC ENTERPRISES
 St. John's Works, St. John's, Badford

OHIO SCIENTIFIC COMPUTERS New series 2 Challenger C1P. Cheapo 4K version £202. Ohio 8K version £259. Special offer: Superboard 3 with free power supply and modulator kit and guard band kit (gives 32x32 extended display, 1200 and 300 baud tape speeds, 50% higher computing speed and 50 Hz conversion) £159 the lot. Guard band kit also sold separately £10. 4K extra ram £18.95. Case £27. Cassette recorder £16. Cagmon Improved monitor rom £28.50. Assembler/Editor £25. Word processor £10. Display expansion kit, 30 lines x 54 characters for Superboard 2 £20.

SHARP M280K COMPUTER with free tape of 50 programs 20K £415. 36K £437. 48K £459.

PRINTERS supplied with free interface and word processor for Superboard and UK101. Seikosha GP80 £250. Oki Microline 80 £349. Base 2 800MST £299.

SINCLAIR PRODUCTS SC110 £145. PFM200 £51.95. DM450 £109. PDM35 £32.50.

TV GAMES AY-3-8600 + kit £12.98. AY-3-8550 + kit £9.28.

BATTERY ELIMINATORS 3-way type 6/7 1/2/9V 300ma £3.50. 100ma radio type with press studs 9V £4.77. 9+9V £5.99. Car converter 12v input, output 4 1/2/6/7 1/2/9V 800ma £3.04.

MEMORIES 2114 450ns £2.15. 4116 200ns £2.83. 4027 £1.30. All low current.

BATTERY ELIMINATOR KITS 100ma radio types, with press studs 9V £1.84. 9+9V £2.30. Stabilized 8-way types 3/4 1/2/6/7 1/2/9/12/15/18V 100ma £3.12. 1Amp £8.10. Stabilized power kits 2-18V 100ma £3.12. 1-30V 1A £8.30. 1-30V 2A £14.82. TTL and computer supplies 5V stabilized 2A £8.38. 4A £14.16. 12v car converter 6/7 1/2/9V 1A £1.62.

T-DEC AND S-DEC BREADBOARDS s-dec £3.79. i-dec £4.59. exp4b £2.64. exp300 £8.61.

BI-PAK AUDIO MODULES AL30A £4.53. AL60 £5.62. SPMB0 £5.28. BMT80 £8.36.

IC AUDIO AMPS with pcb. JC12 6W £2.50. JC20 10W £3.64.

SWANLEY ELECTRONICS

Dept HE, 32 Goldale Rd, Swanley, Kent

Post 40p extra. Add VAT except on sections marked * Lists 27p post free. Phone Swanley 64851. Official and overseas orders welcome.

The DT400 Series are designed and manufactured by SAFGAN in England

SAFGAN Presents DT-400 Series from £169 + VAT

HIGH QUALITY DUAL TRACE OSCILLOSCOPES

A BRITISH PRODUCT EVERYONE CAN AFFORD


Model DT-410	4" CRT	5mV	10MHz	@ £169 + VAT
Model DT-412	4" CRT	5mV	12MHz	@ £175 + VAT
Model DT-415	4" CRT	5mV	15MHz	@ £188 + VAT

SPECIFICATION FOR ALL MODELS

<ul style="list-style-type: none"> * CH1, CH2: 5mV/div-20V/div in 12 Cal. 1/2/5/steps * BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412) * BANDWIDTH: 15MHz (DT-415) * TIME BASE: 0.5us/div-200ms/div in 18 cal 1/2/5 steps. X5 Expansion to 100 ns/div X5 Multiplier to 1s/div * XY FACILITY: Matched Inputs X=CH1, Y=CH2 	<ul style="list-style-type: none"> * TRIGGER: Level Control, ± Slope Bright Line AUTO NORMAL, TV Triggering CH1, CH2 0.5div, EXT Trig. 100mv * Z Modulation * Graticule blue, ruled 8x10div (6.4x8cm²) * Size: H215mm W165mm D280mm. Weight 4.5kg. * Cal. O/P IVIKM2 PROBE (X1-REF-X10) £11.50 + VAT
--	--

Orders to: **SAFGAN ELECTRONICS LTD.** (Goods & P&P £3.50 or P. & Parcel Service £5.50 + 15% VAT)
 56 BISHOPS WOOD, ST. JOHNS, WOKING, SURREY GU21 3QB. Tel: WOKING 69560
 London Stockist: **AUDIO ELECTRONICS**, Edgware Road, London 01-724 3564

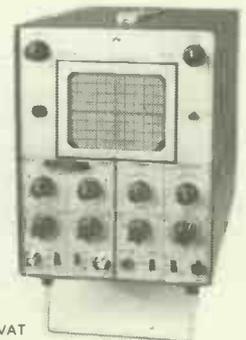DT-400 Series
Official Government and Educational orders accepted






HI THERE, H.E. MEN!
WE'RE OFF TO SEE ANOTHER READER'S INVENTION

THIS TIME WE'RE IN THE BIG CITY...

WHERE VIOLENCE AND VANDALISM REIGN SUPREME

TUFF STREET

SO THEY SAY... WHAT ROT?

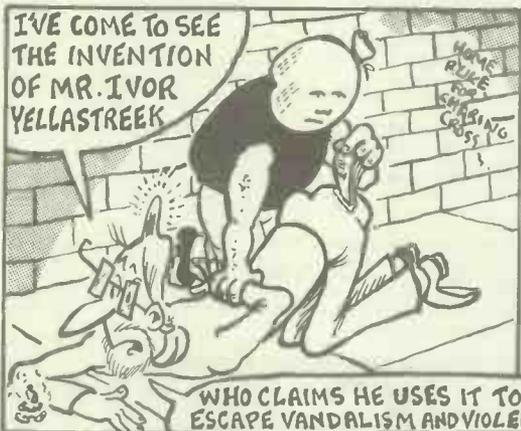

I'VE COME TO SEE THE INVENTION OF MR. IVOR YELLASTREEK

WHO CLAIMS HE USES IT TO ESCAPE VANDALISM AND VIOLENCE




GO AWAY

AH! HERE'S HIS HOUSE NOW

NO CALLERS

THIS MEANS YOU!

I'LL CALL THE POLICE!

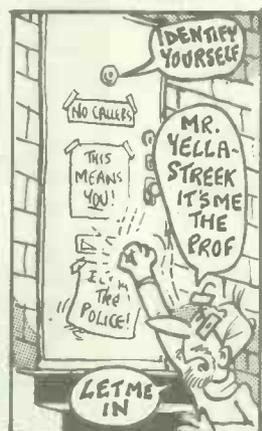

IDENTIFY YOURSELF

MR. YELLA-STREEK IT'S ME THE PROF

NO CALLERS

THIS MEANS YOU!

I'LL CALL THE POLICE!

LET ME IN



HMMM... DOESN'T DO YOU JUSTICE

SEE-HERE'S A PICTURE OF ME

NO CALLERS

THIS MONTH'S HOBBY MAT!



PLEASED TO MEET YOU MR. YELLASTREEK

HELLO

THEY WON'T HIT ME?

NOW WOULD YOU EXPLAIN YOUR NEW INVENTION TO OUR READERS



THERE IT IS...

THAT'S A SUBMARINE! DID YOU BRING ME TO THIS FOUL NEIGHBOURHOOD TO SEE A SUBMARINE!

DON'T HIT ME



IT'S NOT A SUBMARINE - IT'S A SUB-TERRAIN!!

COME FOR A TEST RUN

BUT DON'T HIT ME



WE'RE IN CLAY STRATA NOW...

IT WILL TRAVEL THROUGH ANY SOLID

...USING THIS I CAN GO TO THE LIBRARY SAFELY


YOU PROMISE YOU WON'T HIT ME?



BY USING THE EXCAVATOR ROTORS I CAN EVEN DIG A TUNNEL AND WALK MY DOG!

GRRARR (DON'T HIT ME)

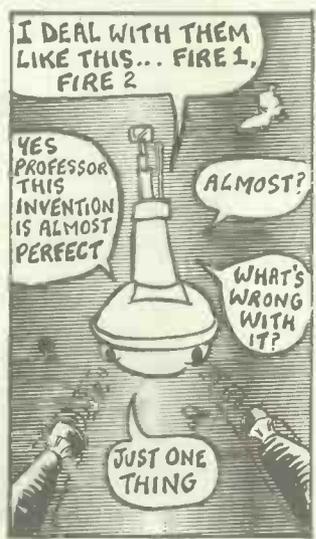FASCINATING MR. YELLASTREEK - BUT WHAT IF SOME VANDALS GET HOLD OF ANOTHER SUBTERRAIN??



I DEAL WITH THEM LIKE THIS... FIRE 1, FIRE 2

YES PROFESSOR THIS INVENTION IS ALMOST PERFECT

ALMOST?

WHAT'S WRONG WITH IT?

JUST ONE THING



IT'S NOT (GLUB GLUB)

WATERTIGHT

YOU SAID YOU WOULDN'T HIT ME!

AAAH

RADIATION DETECTORS

QUARTZ FIBRE DOSIMETER

Recommended for
CIVIL DEFENCE ● FIRE SERVICES ● MEDICAL ● HOSPITAL & General use.

- RADIATION CANNOT BE HEARD, SEEN OR SMELT.
- THIS DOSIMETER WILL AUTOMATICALLY DETECT THE AMOUNT OF RADIATION IN THE AIR.
- UNIT IS SIZE OF FOUNTAIN PEN AND WILL CLIP IN TOP POCKET.
- PRECISION INSTRUMENT, METAL CASED, WEIGHT 40 GRAMS.
- CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION.
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.

Be prepared, buy whilst available.

HENRY'S

404 EDGWARE ROAD, LONDON W2 1ED
Tel: 01-723 5095 Telex: 262284 Ref 1400



COMPLETE WITH DATA

Standard model


£6.95 inc. VAT
Post & Packing 60p

Industrial model O-150R
£10.95 incl. Post Paid



ELECTRONIC IGNITION SAVES PETROL

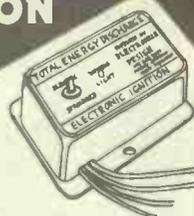More and more new cars use electronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.



TOTAL ENERGY DISCHARGE gives all the advantages of the best capacitive discharge ignitions:

- ★ Peak Performance—higher output voltage.
- ★ Improved Economy—consistent high ignition performance.
- ★ Better Starting—full spark power even with low battery.
- ★ Accurate Timing—prevents contact wear without 'contactless' errors.
- ★ Smooth Performance—immune to contact bounce effects.

PLUS

- SUPER HIGH POWER SPARK**—3½ times the energy of ordinary C.D. systems.
- OPTIMUM SPARK DURATION**—to get the very best performance and economy with today's lean carburettor settings.
- DESIGNED IN RELIABILITY**—with the 'ultimate insurance' of a changeover switch to revert instantly to standard ignition.

TECHNICAL DETAILS

- HIGH EFFICIENCY INVERTER.** A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4 volts.
- SUPERB DISCHARGE CIRCUIT.** A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the H.T. system.
- SOPHISTICATED TRIGGER CIRCUIT.** This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

IN MONEY-SAVING KIT FORM at £14.85 Inc. V.A.T. and P. & P.

All you need is a small soldering iron and a few basic tools — everything else is supplied with easy-to-follow instructions.

FITS ALL 6/12-volt NEGATIVE EARTH cars

ELECTRONIC DESIGN

2 Hillside Road, Four Oaks
Sutton Coldfield, West Midlands, B74 4QD
Phone 021-308 5877

A NEW ADVENTURE IN COOKING! COMPONENTS AND CHIPS FROM

Fast Service — Low Prices

Great Menu

ELECTRONICS

COMPUTER GRADE HIGH RIPPLE CAPS					TTLICs				Type N LS S				XTALS				'D' RANGE CONNECTORS				TRANSISTORS					
MF	Volts	Dim mm	Price	PP	Type	N	LS	S	74107	32p	—	—	Frequency	Case	Price	Ways	Plug	Socket	2N697	22p	AD162	40p	BC251A	15p		
1500*	100	80 x 35	70p		7400	10p	15p	25p	74109	50p	—	—	19.20 KHz	HCGU	300p	9	103p	126p	2N689	35p	BC108	10p	BC252	16p		
2200	40	50 x 25	150p		7401	12p	—	—	74112	—	—	90p	38.40 KHz	HCGU	400p	15	117p	201p	2N708A	25p	BC109	10p	BC237	13p		
3300	25	50 x 25	150p		7402	12p	15p	14p	74114	—	—	45p	100.00 KHz	HCGU	300p	25	172p	258p	2N1136A	25p	BC147	7p	BC337	13p		
3300*	63	115 x 35	80p		7403	14p	—	16p	74116	195p	—	—	100.00 KHz	HCGU	300p	37	235p	414p	2N2646	45p	BC148	7p	BC338	14p		
3300*	150	100 x 65	120p		7404	14p	—	—	74118	75p	—	—	110.00 KHz	BTG	400p	50	290p	545p	2N2904	23p	BC149	7p	BC346	15p		
4700	75	115 x 35	190p		7405	18p	—	—	74121	28p	—	—	1.00 MHz	HCGU	320p	25	WAY RIGHT ANGLE P.C.B.	PLUG 255p, SOCKET 295p	2N2926	7p	BC159	10p	BC548	8p		
11000	25	68 x 50	180p		7406	32p	—	—	74122	41p	—	—	2.00 MHz	HCGU	280p	—	—	—	2N3053	25p	BC167	10p	BC549	9p		
15000	16	80 x 35	180p		7407	32p	—	—	74123	45p	60p	—	4.00 MHz	HC18	280p	—	—	—	2N3058H	60p	BC170	10p	BCY33A	120p		
15000	40	115 x 35	190p		7408	17p	22p	—	74125	53p	—	—	5.00 MHz	HC18	280p	—	—	—	2N3440	60p	BC170A	11p	BD242C	80p		
20000	16	80 x 50	220p		7409	22p	—	—	74128	73p	—	—	6.00 MHz	HC18	280p	—	—	—	2N3702	8p	BC171	10p	BF258	35p		
22000	25	115 x 35	250p		7410	15p	19p	—	74132	68p	—	—	8.00 MHz	HC18	280p	—	—	—	2N3703	8p	BC171A	11p	BFW22	20p		
28000	25	105 x 70	270p	80p	7411	—	38p	—	74133	—	25p	—	10.00 MHz	HC18	280p	—	—	—	4006-4	95p	BC172A	10p	BF750	20p		
34000	50	145 x 75	350p	80p	7413	30p	—	—	74147	180p	—	—	11.20 MHz	HC18	280p	—	—	—	4027	375NS	350p	BC172B	10p	MJ1000	85p	
64000	40	115 x 75	590p	80p	7414	50p	—	—	74148	103p	—	—	20.00 MHz	HC18	280p	—	—	—	*4116	200NS	200p	BC172C	10p	MJ4030	225p	
68000	16	115 x 60	575p	80p	7416	27p	—	—	74150	98p	—	—	DIL XTAL OSC 9.600 MHz	4517	—	—	—	—	5101L	450NS	495p	BC172D	10p	MPU131	25p	
138.000	10	145 x 75	600p	80p	7417	20p	—	—	74151	60p	100p	—	5000 XTALS. EX-STOCK	7417	—	—	—	—	TMS3114SH REG	140p	BC172	10p	MPU131	25p		
160.000	30	220 x 75	750p	120p	7420	17p	19p	18p	74153	65p	—	—	PHONE YOUR FREQUENCY	7423	30p	—	—	—	*4116 8tor	1995p	BC207B	15p	TIP31	26p		
					7427	34p	—	—	74155	60p	—	—		7428	35p	—	—	—	*2114 8tor	2250p	BC212L	8p	ZTX108	8p		
					7428	35p	—	—	74157	60p	65p	—		7430	17p	20p	—	—	—	—	2N5449	12p	BC207B	15p	TIP31	26p
					7430	17p	20p	—	74161	90p	—	—		7432	28p	30p	—	—	—	—	2N5943	55p	BC212L	8p	ZTX108	8p
					7432	28p	30p	—	74163	80p	—	—		7437	35p	—	—	—	—	—	2N6385	125p	BC213A	8p	ZTX314	20p
					7437	35p	—	—	74164	120p	110p	—		7438	30p	35p	—	—	—	—	AD161	40p	BC251	14p		
					7438	30p	35p	—	74166	120p	—	—		7439	30p	—	—	—	—	—	—	—	—	—		
					7439	30p	—	—	74170	235p	—	—		7440	17p	19p	—	—	—	—	—	—	—	—		
					7440	17p	19p	—	74172	445p	—	—		7441	50p	—	—	—	—	—	—	—	—	—		
					7441	50p	—	—	74173	110p	—	—		7442	55p	—	—	—	—	—	—	—	—	—		
					7442	55p	—	—	74174	85p	—	—		7445	120p	—	—	—	—	—	—	—	—	—		
					7445	120p	—	—	74175	80p	100p	—		7447	45p	—	—	—	—	—	—	—	—	—		
					7447	45p	—	—	74180	92p	—	—		7450	17p	—	—	—	—	—	—	—	—	—		
					7450	17p	—	—	74181	150p	—	—		7451	—	22p	—	—	—	—	—	—	—	—		
					7451	—	22p	—	74182	—	90p	—		7454	17p	23p	—	—	—	—	—	—	—	—		
					7454	17p	23p	—	74190	85p	—	—		7470	33p	—	—	—	—	—	—	—	—	—		
					7470	33p	—	—	74191	85p	—	—		7472	28p	—	—	—	—	—	—	—	—	—		
					7472	28p	—	—	74193	85p	95p	—		7473	34p	—	—	—	—	—	—	—	—	—		
					7473	34p	—	—	74194	85p	—	—		7474	28p	32p	36p	—	—	—	—	—	—	—		
					7474	28p	32p	36p	74197	75p	—	—		7475	28p	—	—	—	—	—	—	—	—	—		
					7475	28p	—	—	74198	140p	—	—		7476	35p	—	—	—	—	—	—	—	—	—		
					7476	35p	—	—	74241	150p	—	—		7485	90p	—	—	—	—	—	—	—	—	—		
					7485	90p	—	—	74256	—	95p	—		7486	34p	35p	—	—	—	—	—	—	—	—		
					7486	34p	35p	—	74273	265p	—	—		7489	200p	—	—	—	—	—	—	—	—	—		
					7489	200p	—	—	74279	80p	—	—		7490	28p	—	—	—	—	—	—	—	—	—		
					7490	28p	—	—	74283	155p	—	—		7492	50p	—	—	—	—	—	—	—	—	—		
					7492	50p	—	—	74284	400p	—	—		7493	28p	—	—	—	—	—	—	—	—	—		
					7493	28p	—	—	74285	400p	—	—		7495	65p	—	—	—	—	—	—	—	—	—		
					7495	65p	—	—	74298	180p	—	—		7496	60p	—	—	—	—	—	—	—	—	—		
					7496	60p	—	—	74366	95p	—	—		7497	175p	—	—	—	—	—	—	—	—	—		
					7497	175p																				

What's In A Name

To end this series, Rick Maybury discusses electronic equivalents to our sensation of touch

THIS MONTH we look at systems and components that duplicate our sense of touch. From the outset it must be said that touch is a fairly empirical term: for instance, it includes the ability to detect temperature change and to sense changes in pressure. By comparison, electronic detectors allow these changes to be *measured*. Although these measurements may be accurate, they are crude compared with the total sensation of touch at the fingertips. The information transmitted from the fingertips through the nervous system to the brain enables us to *process* these minute sensations, localise them and, for example, set limits on the temperatures or pressures that we can safely endure. The built-in alarm system associated with these limits is pain!

In this final part of the What's In A Name series we will look at one electronic equivalent of touch sensation, namely that of pressure.

We can detect very small pressure changes with our own senses. For example, we can 'feel' a feather as it is brought in contact with the hand. (Our response to small changes in atmospheric pressure is another example.) Electronic devices have the edge on our own sensitivity, because devices known as strain gauges which detect *movement* due to a change of pressure or force can measure down to about one millionth of a gram or less. We'll have a look at these first.

Sadly, most electronics enthusiasts will never make use of strain gauges. Sad because these devices are highly versatile measuring transducers which could have many interesting applications for the hobbyist. (Perhaps we'll think of one or two for you to build as future projects in HE.) The most common form of *industrial* strain gauge uses the now familiar piezo-electric effect. You may remember that we dealt with piezo-electric devices when we looked at microphones. The transducer works by mechanically transmitting movement to a piece of quartz crystal. The structure of the crystal is such that any distortion 'frees' a number of electrons, within the structure, which can then be fed to an electronic circuit for measure-

ment. The number of electrons, or current, that will flow is directly proportional to the amount of movement so we can obtain a direct measure of that movement.


Leaving aside piezo-electric transducers there are a number of other quite familiar components that can be used to detect the movement due to a force. Our old friend the potentiometer is actually a case in point. In its most usual form it can measure a rotary motion in terms of changing resistance. Simple mechanical linkages can change the motion into a linear (straight line) or angular motion that is directly measured as a resistance.

Pressure or force can also be detected simply with the common-or-garden mechanical switch. Of course, a push button or toggle switch will not tell you *how* much force is being exerted but it will tell you whether the force is there or not. Simple microswitches, for instance, are used in their millions on many types of machinery that require some kind of sensor to detect a predic-

table force and that is in essence what the basic touch receptors found on our own bodies do.


The last type of detector we shall look at is not exactly a purely electronic device but it is worth a mention because of the incredibly small changes it is capable of measuring. The interferometer uses the properties of coherent light to resolve unbelievably small movements between two optical sensors. At present it is possible to detect a movement less than 0.1 μm . That's difficult to imagine, isn't it? In terms we *can* understand, it will measure a movement between two bodies about the size of an atom. Human senses are pretty efficient but it is doubtful whether anybody could feel an individual atom falling onto their skin! We do have one advantage however, the touch receptors in our own skin are about the size of a pin head, and even the wizardry of the silicon chip has a long way to go before it can come up with a transducer as small as that.

HE

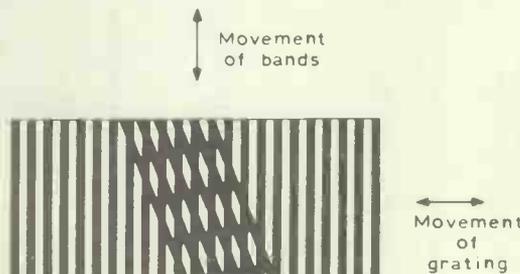

Left. Measurement of movement by optical means. Two gratings placed above one-another will produce interference patterns that can be used to determine movement

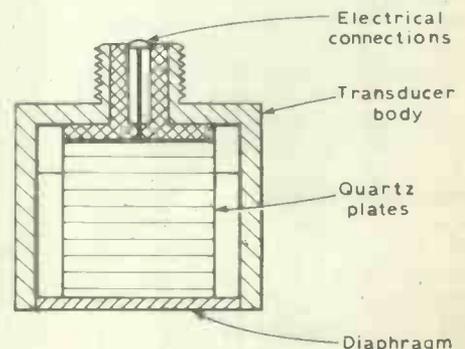A piezo-electric pressure sensor. Any movement on the diaphragm will be mechanically transmitted to the piezo-electric elements which in this case are made of quartz. The electrical signal is monitored at the top of the transducer



Guitar Fuzz Box

Produce delightful distortion from your electric guitar in a novel way. A cheap and simple-to-build project with foot-pedal control



THE STORY GOES that the first group to use a 'fuzz' effect in their music was the Kinks. Apparently, one of their loudspeaker cones was split and they couldn't afford to replace it so they simply made use of it — and fuzz was born.

Now whether the story is true or not, we don't really know. One thing for sure is that the effect has been recreated electronically in many different ways, but none with the controllability, or the simplicity of the HE Fuzzbox.

The design of our fuzz evolved with a lot of thought. We studied how the effect is normally made and all the consistent disadvantages with such methods, till eventually we came up with a new concept around which our design is built. A single integrated circuit, of the operational amplifier family, together with only a handful of passive components (ie resistors and capacitors) are used in the fuzz unit to produce a very 'smooth' sound which we feel is much superior to the usual harsh fuzz.

From the photographs you will see that our prototype is housed inside a brand-new style of box, complete with a pedal to operate an internal switch. We just couldn't resist being the first magazine to use it for a project and a fuzz box seemed ideal.



There's just enough room inside to fit the circuit, battery, a jack socket and controls, and we can tell that it's going to be a very popular type of housing for projects, particularly in the musical effects line.

Quiescent current drain of the HE Fuzzbox is only 2 mA, so long battery life can be expected and a single PP3-type battery should last for months with normal use.

Because our Fuzzbox operates in an unusual manner we have been able to design it as a low-distortion (hi-fi quality) preamplifier which will amplify the guitar signal level to about four times its original size — this can be useful in itself.

Construction

The usual constructional precautions should be taken, consistent with the use of Veroboard (ie make track breaks where indicated and check that no short circuits between adjacent tracks occur). Breaks in track can be made by gently twisting either the correct tool for the job, or alternatively a hand-held, small drill bit (about 1/8"), against the hole in question until a neat break is formed through the copper strip and the two sides are no longer in electrical contact.

Insert and solder all the components, starting with resistors,

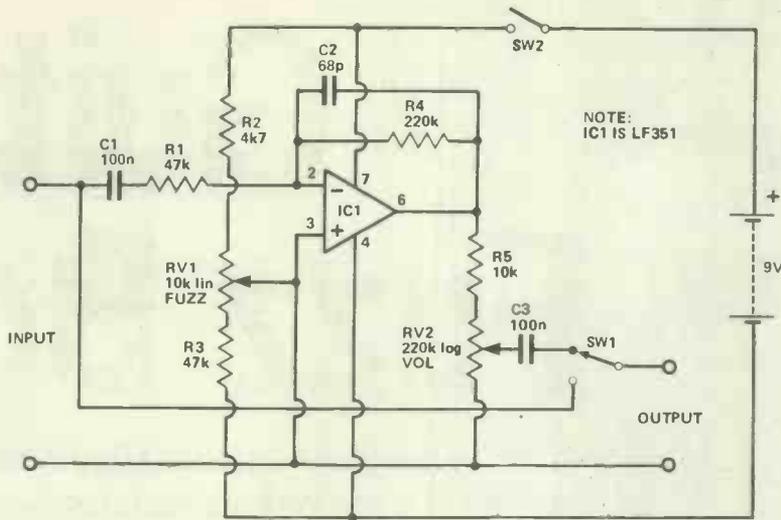


Figure 1. HE Fuzzbox circuit diagram. The simplicity of the project makes it ideal for the beginner

Figure 2 (below). Veroboard layout, connection details and underside view of the board showing track breaks

Parts List

RESISTORS (All 1/4 W, 5%)

R1,3	47k
R2	4k7
R4	220k
R5	10k

POTENTIOMETERS

RV1	10k linear potentiometer
RV2	220k logarithmic potentiometer

CAPACITORS


C1,3	100n ceramic
C2	68p polystyrene

SEMICONDUCTORS

IC1	LF351 JFET operational amplifier
-----	----------------------------------

MISCELLANEOUS


SW1	single-pole, double-throw slide switch (included in case - see Buylines)
SW2	single-pole, single-throw toggle switch
2 x 1/4" jack sockets (only one needed if case is used)	
Battery and clip	
Knobs	
Case to suit (see Buylines)	
10 strip x 24 hole, 0.1" Veroboard	

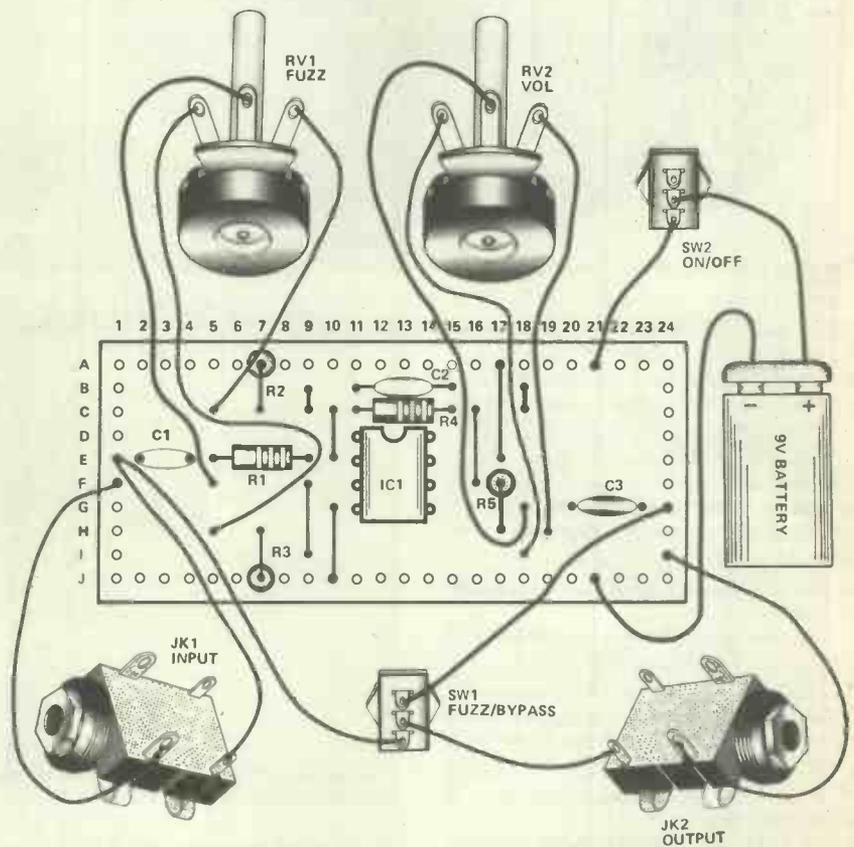

then capacitors and finally the IC as shown in Fig.2. Wiring up should be done as per connection details and then you can test your project. There is little to go wrong so providing your constructional skills are up to scratch the fuzz should work first time.

Although this project was designed to suit the case featured it will, with care, fit into almost any small case. In the connection diagram in Fig.2 we have included a jack socket for output, but this is optional. If you use the same case as us which comes complete with output lead, the second jack socket is not necessary, just connect the lead to SW1 as shown.

Guitar Fuzz Box

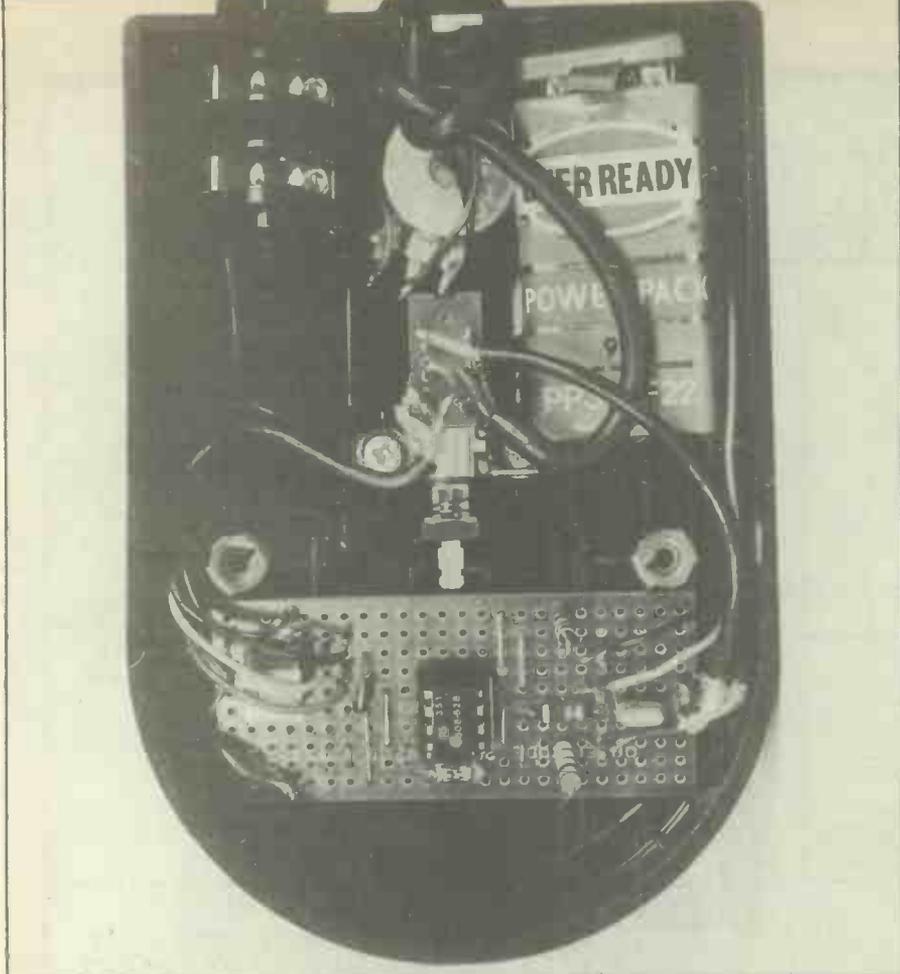

Internal photograph of the project showing how tight a fit it all is. Everything should fit neatly into the case with care

Use screened lead for input and output connections (the screen should be connected to 0V) thus keeping interference to a minimum

Buylines

The components for this project should cause few problems. IC1, the LF351, will be obtainable from most mail order companies. The smart case which we used can be bought from Magenta Electronics, and the price, which is complete with lead, plug and switch is £5.65 (inc. VAT), p&p 40p.

Magenta can also supply a complete kit of parts (including case) for HE Fuzzbox for £9.41. This price includes VAT but please add 40p for p&p.

How It Works

Most fuzz circuits use a high-gain amplifier to boost the output signal of your guitar to a greater level than the amplifier can supply without severe distortion. Figure 3 shows this effect graphically. Distortion (fuzz) occurs purely because the output is clipped by the amplifier saturating and cutting off. Two distinct disadvantages occur with this method — the distortion is very harsh and a lot of background noise can get in the way because of the amplifier's high gain.

Now, it might seem odd to you that we're complaining about too much distortion and noise in a circuit, that at first sight should do nothing but create distortion and noise. The reason for our complaint lies in the fact that the device is supposed to be a *musical* effect. If you distort the sound *too* much the musical part of it is overshadowed by the harshness.

So, a fuzz with not quite the distortion (or at least a more controlled distortion) and preferably lower amplification (to keep down the level of background noise), is required. HE Fuzzbox is just that!

Integrated circuit IC1 is an operational amplifier (op amp) connected as an inverting amplifier with a gain of about five. This means that for an input signal of say, 10 mV from your guitar, the IC's output is 50 mV. The potential divider of R5 and RV2 reduces this to a variable amount of between zero and about four times.

Potentiometer RV1 biases pin 3 (the

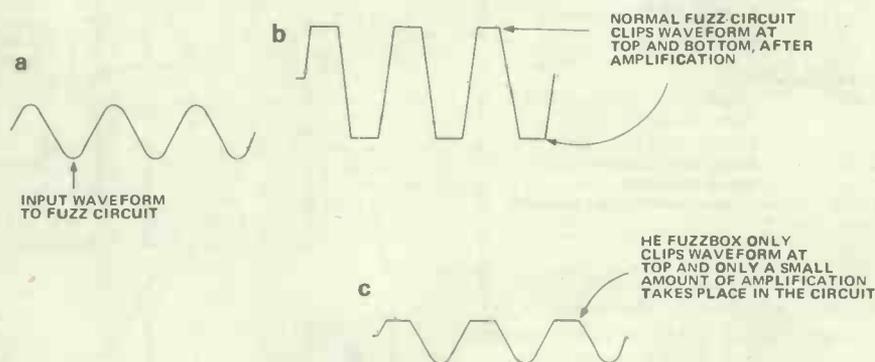


Figure 3. a) A possible input signal b) The output of a conventional fuzz circuit c) The output of the HE Fuzzbox

non-inverting input) of the amplifier and hence the amplifier itself, into AC operation, and also provides an earth point for the input and output. By altering the position of RV1 the circuit's earth moves in relation to the power supply rails and therefore the AC signal at the output of the op amp moves up and down with a DC bias. At the lower end of the pot, ie fuzz effect at minimum, the output signal suffers no restrictions from amplifier saturation. The output is merely an inverted, amplified replica of that at the input — and the device functions as a pre-amplifier. As the fuzz control is

moved clockwise the earth moves positive until the output become clipped on the larger positive half-cycles. Figure 3 shows this effect. Further increases in earth voltage, as the pot is turned more clockwise causes an increase in the clipping effect.

The important points to note are that no further gain is required to increase the fuzz effect and clipping only occurs on one half cycle of the waveform. A very 'clean' and controllable distortion occurs which is more musical and more adaptable to the needs of the individual guitarist.

HE

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5. Callers welcome


200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194.AMBIT G POSTCODE CM14 4SG

SSB transceiver module - based on G4CLF designs

- * High level mixer
- * 8 pole filter

- * 1 W AF on the PCB

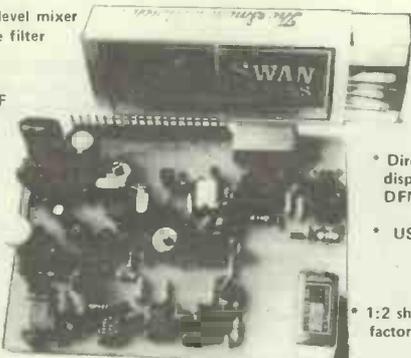

- * Direct freq. display with DFM7

- * USB/LSB

- * 1:2 shape factor

Add an LO and the RF selectivity, and you have a very simple yet high performance signal processing 'heart' of an SSB transceiver in the range 100kHz to 1000MHz (with the correct LO/RF stages). The Ambit 91600 costs just £44 +vat, and includes an 8 pole SSB crystal filter, SL1600 signal processing circuitry, double balanced schottky diode mixer and full USB/LSB electronic switching.

The use of 10.7MHz, instead of 9MHz (as in the original unit) now enable direct connection to an AMBIT DF7 for 1kHz frequency readout with far greater ease and accuracy than can be achieved with mechanical dial systems. Buy them both and save 15%. DFM7+91600= £69.46 inc.

The AMBIT catalogue - now with the new Part 4 for 1981
The most complete range of specialist radio components in Europe.

- * VHF tunerheads

- * Stereo decoders
- * Frequency synthesis
- * Block LPFs
- * keyswitches
- * DC audio control ICs
- * Ultimate HiFi



- * Crystal filters (& theory)

- * Ceramic filters for AM/FM
- * Mechanical filters
- * Fixed chokes
- * MC meters
- * CMOS/TTL
- * NBFM IFs
- * WBFM IFs
- * flat top LEDs
- * Variable chokes
- * Piezo sounders
- * potentiometers
- * 24 bit NC plotters
- * low noise RIAA ICs
- * UHF Helical filters
- * miniature electrolytics
- * 30Mb hard disks

The state of the art in radio and audio

You need all three sections for a complete picture. Each section is revised on a triennial cycle - so this year the part 4 contains the revised remnants of the original part 1 - plus all the many new items for 1981. £1.75 for the lot, or 60p each for parts 2 & 3, and £0.75p for the bumper part four section. (prices include postage).

Special Offers... each catalogue is supplied with a 'special offer' order form that will enable you to save the cost of the catalogues with your first few purchases.

Radio Control Systems

As well as the parts for constructing sophisticated digital proportional radio control systems, we offer kits of parts for complete receivers and transmitters (now including hardware). Only state-of-the-art FM systems, readily adapted to 35MHz if required.

- * Dual IF ceramic filters
- * gold plated servo connector

- * single IC transmitter/encoder
- * prewound coils for easy alignment



- * FM crystals extra

The RCRX4	8 channel FM receiver with triple ceramic filtering, complete with case..	£16.10
94445	4 channel FM transmitter based on ET1 October 1980 system	£8.57
94446	5 channel FM receiver, based on ET1 October 1980 system (inc case)	£14.26
TX Case	Complete transmitter case hardware, with two joystick controllers	£26.62
SD1	NE544 based servo driver electronics kit (no mechanics)	£3.28

- * Matching 'Signal', 'Tune' and 'VU' scales.

- * Custom scales OA



Moving coil indicator meters: over 10,000 in stock for immediate delivery. The new part 4 catalogue lists many of the stock designs, but a much wider range is available to order (subject to minimum requirements). Meters for nearly all occasions, including precision voltmeter and ammeters.

- * Signal level
- * 'tuning'
- * VU

NEW: Miniature electrolytics 0.01CV leakage

- * smaller than tants
- * vastly lower priced



* many standard types

Miniature PC mounting 12v relays 2A/24v contacts, single or dual changeover types available

SPDT: £1.65
DPDT: £1.85


- * sealed against flux



- * ideal antenna changeover etc

- * Clock timer switching

The Mark III Series of DIY HiFi.

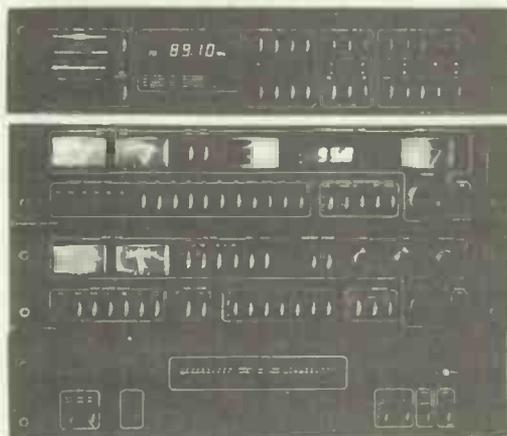

The Mark III series of HiFi is the ultimate DIY audio system. There are probably more features and facilities to the square inch of front panel than any other commercial HiFi around - let alone DIY systems. From the twin 500VA PSUs of the HMOFET 100W power amp, to the 1dB tracking of the DC controlled preamp and the versatility of the CMOS MPU controlled tuner, there is no match for performance, style or sound quality - come and hear for yourself in our foyer.

Mark III synthesised tuner	£175.00 + vat
Mark III B FM-only tuner	£185.00 + vat
Mark III DC controlled signal preamp	£175.00 + vat
Mark III 100W rms/channel MOS PA	£160.00 + vat



LCD modules: including various clock/timer/alarm systems, DVM, serial data decoder/displays. The clock shown is the CM161 - 12/24 hrs, day/date, alarm, backlight. All for just £11.44 including VAT.

The FC177 (alongside) displays AM/LO's up to 3.9999MHz directly - and with the prescaler unit (DFM7) the system displays SW and VHF in 1kHz and 10kHz resolution resp. FC177: £26.16; DFM7: £36.22 (prices include VAT)



Photographic Timer

You won't get caught in the dark with this one — time your photographs to perfection with this cheap-to-build, simple project

We could not be accused of overcomplication with this simple photographic timer project, which uses only about half a dozen components. The unit has a LED indicator which flashes regularly at one second intervals, and it can be employed as a simple enlarger timer, to time exposures lasting several seconds with the camera set to 'B' or 'T'. There are many other uses for this timer.

It is inexpensive and extremely simple to construct, being well within the capabilities of even a complete beginner: it makes an ideal first project.


Construction

The few components fit easily onto one of our standard size (24 holes by 10 strips) 0.1" pitch Veroboards, as shown in Fig. 2. Building the component panel could not be easier, but be careful to connect LED1, Q1 and C1 the correct way round, and be sure to connect the battery clip with the right polarity.

Practically any small metal or plastic case should be adequate to house the timer. Indicator LED1 is mounted on the front panel using one of the special panel holders available for the device. This panel holder can provide the mounting for the component board.

Potentiometer RV1 is given the correct setting by trial and error, comparing the flash rate of LED1 against a clock or watch which gives seconds' indication. In use the unit is started by closing SW1. The shutter is opened or the enlarging lamp is switched on at the first flash, and then the appropriate number of flashes are counted. On the last count, the shutter is closed or the enlarging lamp switched off. The period from switch-on to the first flash is slightly more than one second, and should not be used as part of the timing period.

The HE Photographic Timer will fit into any suitable-sized small case and when finished will be a valuable addition to the darkroom

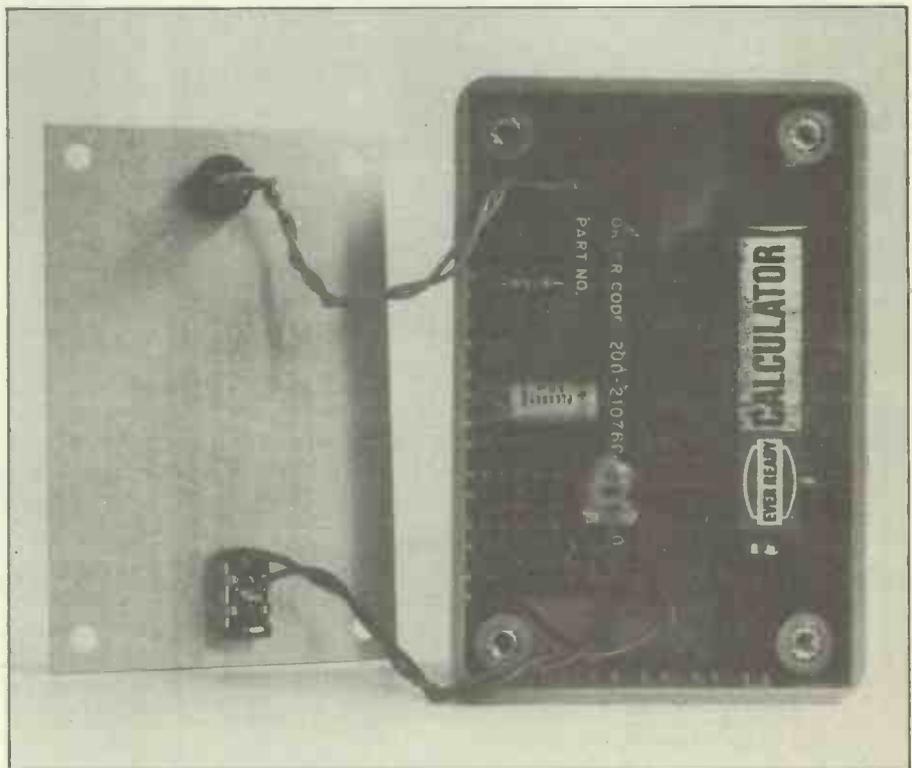


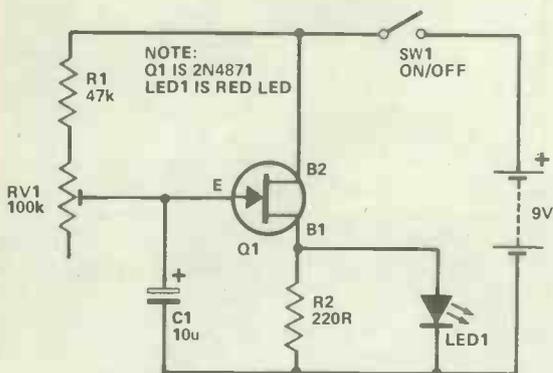


Figure 1 (left). Circuit diagram of this simple project

Figure 2 (below). Veroboard layout, underside view and connection details. Note there are no track breaks

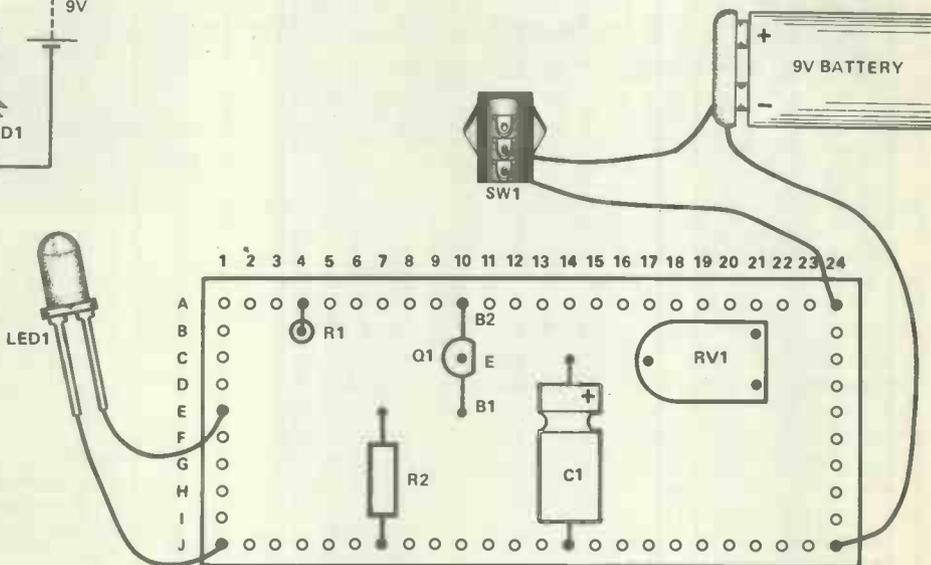

Parts List

RESISTORS (All 1/4 W, 5%)

R1 47k
R2 220R

POTENTIOMETER

RV1 100k miniature horizontal preset

CAPACITORS

C1 10u, 25 V electrolytic

SEMICONDUCTORS

Q1 2N4871 unijunction transistor
LED1 0.2" red LED

MISCELLANEOUS

SW1 single-pole, double-throw toggle switch

Case to suit

10 strip x 24 hole 0.1" Veroboard
Battery and clip

Buylines

All the components used in this project are standard readily obtainable items, and the total price (excluding the case) should be approximately £4.

How It Works

A unijunction relaxation oscillator makes a good basis for a project of this type since it gives the necessary short pulses of current required to give brief flashes of a LED indicator, and it does not need a stabilised supply to give good frequency stability. A circuit of this type is also simple, as can be seen from the circuit diagram (Fig. 1).

There is normally a resistance of a few thousands of ohms between the base 1 and base 2 terminals of a unijunction transistor, and a potential divider circuit is therefore formed by the unijunction device Q1 and resistor R2. Because of the comparatively low resistance of R2 the voltage appearing across this component is well below the threshold voltage of LED1, and the latter will not light up. The input impedance at the emitter of a unijunction is

very high under normal operating conditions, and at switch-on C1 charges by way of R1 and RV1.

Capacitor C1 continues to charge until it reaches a charge voltage of about 80% of the supply voltage, and Q1 then triggers. This results in the emitter-to-base 1 impedance of the device dropping to a level of just a few ohms. A rapid discharge takes place through Q1 and the parallel impedance of R2 and LED1, the latter being brought into the state of conduction by the current flow through R2 and the consequent rise in the voltage across this resistor. Because of the low impedance of C1's discharge path its charge diminishes very rapidly to the point where Q1 is no longer maintained in the 'triggered state',

and Q1 quickly reverts to its original state. Thus there is only a brief pulse of current through LED1, and it produces only a brief flash.

With Q1 back in its original state C1 is free to charge up once again, but the charge on this component soon reaches the trigger potential of Q1 once again, causing the device to trigger and discharge C1. This cycle is repeated indefinitely, giving a regular series of flashes from LED1. Potentiometer RV1 controls the charge rate of C1 and in practice it is adjusted to give the required flash rate of one per second.

The current consumption of the circuit is only about 1 to 2 mA, and each PP3-size 9 V battery gives many hours of use.

We're giving away this soldering iron worth over £10.



Choose any of 10 selected kits from the Heathkit catalogue as your first order, and we'll give you a superb soldering iron worth over £10. Plus a 10% discount!

These kits have been specially designed with first-time kit builders in mind. So even if you've never built an electronic kit before you won't find it difficult. In fact, the simple to follow step-by-step instructions make it easy to build any Heathkit kit.

And with your special offer discount you can afford to see just how easy it is.

Full details of this FREE offer are available in the Heathkit 48 page catalogue. So send the coupon for your copy now.

To: Heath Electronics (UK) Limited. Dept. (HE3), Bristol Road, Gloucester. GL2 6EE.

Please send me a copy of the Heathkit catalogue. I enclose 25p in stamps.

Name _____

Address _____


NB: If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.



HEATHKIT

HEATH
ZENITH

DIGITAL VOLTMETER MODULE

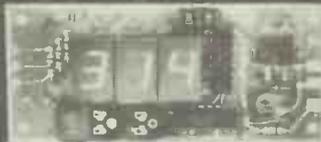

Fully built and tested, ONLY

£11.95 + VAT

- ★ Reads positive and negative voltages with a sensitivity of 0 - +999mV and 0 - -99mV
- ★ Requires only single supply between 7 & 12 volts (220mA)
- ★ High accuracy +0.1% +1 digit
- ★ Large bright 0.43" high efficiency displays
- ★ 4 readings per second sampling rate
- ★ Size only 41 x 95 x 10mm
- ★ Supplied with full data & applications information

This brand new, quality module manufactured by Autona Limited (who are one of the U.K.'s largest module manufacturers) means you can build accurate test equipment, multi-meters, thermometers, etc. easily and at a fraction of the cost of ready-made equipment. Full details are provided showing how to measure A.C. voltage, current, resistance and temperature.

Send your cheque or P.O. (£11.95 + £1.79 V.A.T. + 50pp. & p. = £14.24) now to:-

Dept. HE1
RISCOMP LIMITED
21 Duke Street
Princes Risborough
Bucks HP17 0AT

BUCKINGHAMSHIRE'S NEW COMPONENT SHOP
For all your Electronic Component needs
Telephone: (084 44) 6326



EX-STOCK DELIVERY



EVERCO

Multiband Receiver plus 40-channel CB Monitor. Frequency coverage:
54- 87 MHz 145-176 MHz
88-108 MHz Plus H1 40 CB Channels
108-145 MHz

This unit has a telescopic antenna and squelch control, sockets for earphone and external DC power source.

£21.95 inc. VAT + 75p P&P



The latest from the U.S.A.

PINBALL WIZARD

★ Still available ★
Featured in Nov. issue of E.T.I.
Home TV Game — B/W Kit

Basic Kit £28.90

Contains everything except box and controls

Box & Controls £6.50, P.S.U. £3.90

CEH Car Alarm Kit £18.90

Chroma Chime 24 tune door chimes kit

£10.75. Built £15.95

HE MICROBE R/C

Basic Kit £19.90
(2 PCBs and all PCB components)

ELECTRONIC GAMES

Star Chess T/V game	£63.35
Database Prog T/V game	£89.95
Chess Challenger 7	£99.00
Chess Challenger 10	£160.00
Voice Challenger	£230.00
Chessmate 8 level	£59.95
Zodiac Astrology Computer	£29.95
Electronic Mastermind	£14.90
Supersonic Mastermind. New	£21.00
Mattel Subchase. New	£17.90
Mattel Armor Battle. New	£17.90
Enterprise 4 in 1	£22.90
Galaxy Invaders. New	£22.95
Radio Control Models—Various	

Ball Clock as H.E. offer. Kit £24.95, or ready-built £29.95.

S.a.c. enquiries. Please allow up to 21 days for delivery. ALL PRICES INCLUSIVE



UNIT 6 **N.I.C.**
61 BROAD LANE, LONDON N.15 4DJ
Day 01-808 0377; Eve 01-889 9736



CB

Breaker One Four

The publishers of HOBBY ELECTRONICS would like to point out that it is at present a contravention of the Wireless Telegraphy Act of 1949 and 1968 to use, manufacture, install or import CB transmitting equipment. It is not the intention of Modmags Ltd to incite, encourage or condone the use of such equipment.

Rick Maybury reports on the response to the Open Channel Green Paper. He has some interesting news snippets too

I'M NOT NORMALLY given to rumour-mongering. In fact, as I've said on many previous occasions, I'm dead against it. But for once, I'm going to do a little crystal gazing, based on several very interesting snippets that have found their way into the HE office. It would seem that our friends in the good old Home Office are a little tired of CB. To them it is a nagging irritant that is not going to disappear: their Open Channel proposal fell on totally uninterested ears. The response to the Green Paper was, according to the HO, in the region of 12,000 responses. This figure is made up of group responses, clubs etc which only count as one response, so the overall figure is probably much higher.

The responses fell roughly into two categories, those from potential industrial and commercial users and those from private individuals. Not surprisingly the commercial and industrial users were not wholly against the infamous 928 MHz OC system, so we might see some developments in that area after all. The responses from private individuals, clubs etc were also predictable in their content. They were almost unanimously in favour of using a 27 MHz system.

Now, the two other snippets that connected together concerned the recent introduction of a CB system in France, very similar to the Dutch system introduced last year, and the hint from someone well connected with the HO that an internal directive had been issued to 'sort it out fast'. The two broadcasting organisations that still occupy the 41 to 49 MHz band (ie the IBA and BBC 405-line TV transmissions) have made it clear that they will not discontinue their service before the appointed date — sometime in 1985 — so it doesn't take much intelligence to work out that there are only a limited number of options open to the authorities.

The most logical step now would be for them to follow the French and Dutch with a rationalised CB system on 27 MHz using a low power output (possibly 2 watts?) and to ease the problems of interference, adopt FM (frequency modulation). It is also worth pointing out that both the French and Dutch have

opted for a limited number of channels, around 20 or 22.

Now, all this is pure conjecture: if I'm wrong I apologise but my sources indicate that some kind of announcement will be made around February or March. I'll say no more, just sit back and wait with everything crossed.

Club Happenings

Back to the more mundane matters now with a round-up of the month's events. Just around early January the Big E club from Tottenham held a 'Come As Your Handle' fancy dress party. The results were, as you can imagine, pretty incredible. I had hoped to show you some pictures of the event but they did not arrive in time. As a postscript to this story, the caterers hired for the party presented the club with an enormous cake complete with a rig made out of icing. Rather than eat it themselves, and I'm sure the temptation was enormous, they generously donated it to the Great Ormond Street Hospital for Children.

'A simple call of
'Hey, Waiter', would have
been more than enough, Sir!'



ELECTRONIC GAMES

ATARI

SPECIAL PRICE



£86 + VAT

INTELLIVISION MATTEL



£173.87 + VAT

This is the most advanced TV game in the world. Expandable this year into a full microcomputer. COLOUR CATALOGUE AVAILABLE WITH DETAILS ON ALL THE CARTRIDGES

CHESS



Send for further details.

COMPUTERS

NEW RANGE AVAILABLE AUGUST 1980
We specialise in computer chess machines & stock over 13 different models from £20 to £300

TELETEXT



RADOFIN TELETEXT Add on Adaptor

£173 + VAT

BRIDGE

COMPUTER



- ★ Plays 1/2/3 or 4 Hands
- ★ Problem Mode
- ★ Audio Feedback
- ★ Instant Response
- ★ Auto scorekeeping

BACKGAMMON


COMPUTERS



OMAR 1
OMAR 2
CHALLENGER
GAMMONMASTER

From £38 to £108. Send for further details.

SPACE INVADERS

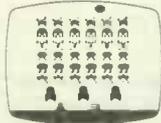


HAND HELDS + CARTRIDGES
ATARI - ACETRONIC
PRINZTRONIC
RADOFIN - DATABASE etc.

We keep a full range!
Send for cartridge lists stating which machine you own.

DRAUGHTS

COMPUTER

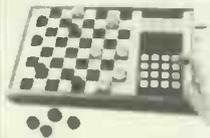

- ★ Solves Problems
- ★ Rejects illegal moves
- ★ 2 level machine £43 + VAT
- ★ 4 level machine £77.78 + VAT

LEISURE

- ★ CHEAP TV GAMES
- ★ TELEPHONE ANSWERING MACHINES
- ★ AUTO DIALERS
- ★ CALCULATORS
- ★ DIGITAL WATCHES
- ★ PRESTEL
- ★ HAND HELD GAMES

24-TUNE DOOR BELL

£13.65 + VAT



FREE CATALOGUE

For a free copy of our 32 page catalogue, send a 12p stamp to Silica Shop Ltd or Telephone 01-301 1111

MAIL ORDER SERVICE - Free postage & Packing
TELEPHONE & MAIL ORDERS - accepted on:
Access * Barclaycard * American Express * Diners Club
CALLERS WELCOME - at our shop in Sidcup - Demonstrations daily
Open from 9am-5pm Mon.-Sat. (9am-1pm Wed.)

GUARANTEE - Full 12 months + After Sales Support!

We have comprehensive brochures on all products. Please let us know what you are interested in and we will send you detailed brochures AND our own 32 page catalogue covering most games on the market.

SILICA SHOP
SILICA SHOP LTD., Dept. HE3
1-4 The Mews, Hatherley Road
Sidcup, Kent, DA14 4DX
Tel: 01-301 1111

It's easy to complain about advertisements.

Every week, millions of advertisements appear in the press, on posters or in the cinema.

Most of them comply with the rules contained in the British Code of Advertising Practice and are legal, decent, honest and truthful.


But if you find one that, in your opinion, is wrong in some way, please write to us at the address below.

We'd like you to help us keep advertising up to standard.

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.

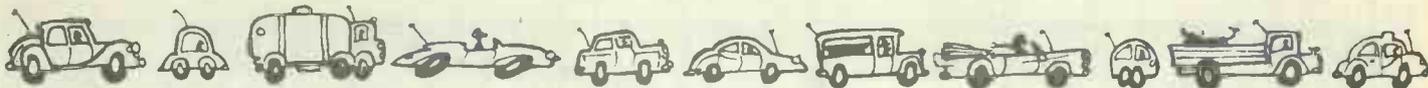A.S.A. Ltd., Brook House, Torrington Place, London WC1E 7HN.





Still with the clubs, the Colwyn Bay CB Club organised a New Years' Day pram race and swim. The proceeds from the sponsored swim went to a local childrens' home. In the pictures below you can see the intrepid contestants nearing the end of the race.

We now have well over 100 CB clubs on our files and for a complete list of the major clubs see the club directory in this month's edition of Citizens' Band magazine.



Competitive Accessory Prices

The accessory scene is really hotting up now. An average of two shops each week open up in London alone. This is obviously good news for the breakers as the inevitable price-cutting war has led to some impressive bargains. Only a year ago the average price for a DV27 antenna was around £15.00. Now you can pick one up for as little as £5.75. Inflation does not seem to be affecting this particular part of the British economy. Anyway, the point of all this is to offer a small prize to the sender of the price of the cheapest DV27 currently available. A genuine HE tee shirt will be dispatched to the sender of the name and address of the company that offers this popular antenna under the cheapest price tag — any offers?

Press Support For CB

Last item this month concerns the impressive coverage given to CB by one of this country's leading daily papers. Many of you will have seen the campaign published in the Star newspaper. The small petition form is a step in the right direction but there is one nagging doubt, are they just jumping on the bandwagon. Their inestimable help would have been much more appropriate six months ago. Oh well, any publicity is good publicity so thanks to the people concerned at the Star and I hear that Andy Donovan (Disco One), president of the UBA, had a hand in this particular campaign — well done to all concerned.

Time's up once again, keep your fingers crossed and with a little luck I'll have some good news for you next month.

Is CB worth this? Galloping breakers compete in Colwyn Bay CB Club's New Year pram race

Hope there's not a rig in that handbag! Club members hurtle toward the end of the pram race



HOBBYPRINTS

If you have never used HOBBYPRINTS before, then you don't know what you've been missing. HOBBYPRINTS are an etch-resistant rub-down transfer. Just place the appropriate HOBBYPRINT over a clean piece of copper clad PCB material and rub. It's as simple as that. Once the design has been transferred, immerse the board into the Ferric Chloride. 15 minutes later you will be rewarded with a perfect PCB prepared from our original artwork, so you can have no worries about making a mistake. By the way, HOBBYPRINTS are ideal for making PCBs by Ultra-Violet exposure.



HOBBYPRINT SHEETS ARE AVAILABLE FOR ISSUES FROM NOV. 78 RIGHT UP TO THIS ONE. ALL SHEETS COST £1.20 ALL INCLUSIVE OF POST AND PACKING AND VAT. ORDER BY SHEET LETTER AND ISSUE MONTH (SEE BELOW).

ISSUE	SHEET REF.
Nov. 78	A
Dec. 78	B
Jan. 79	C
Feb. 79	D
Mar. 79	E
Apr. 79	F
May 79	G
Jun. 79	H
Jul. 79	I
Aug. 79	J

ISSUE	SHEET REF.
Sept. 79	K
Oct. 79	L
Nov. 79	M
Dec. 79	N
Jan. 80	O
Feb. 80	P
Mar. 80	Q
Apr. 80	R
May 80	S
Jun. 80	T

For your HOBBYPRINT refer to the chart above and send your cheque or postal order to:
HOBBYPRINTS,
Modmags Sales Office,
Hobby Electronics,
145 Charing Cross Road,
London WC2H 0EE.

PCB FOIL PATTERNS

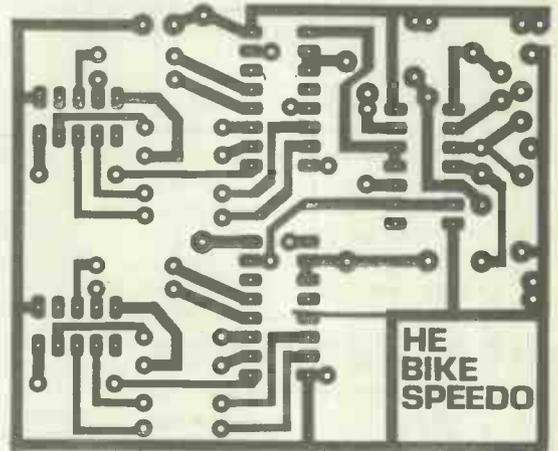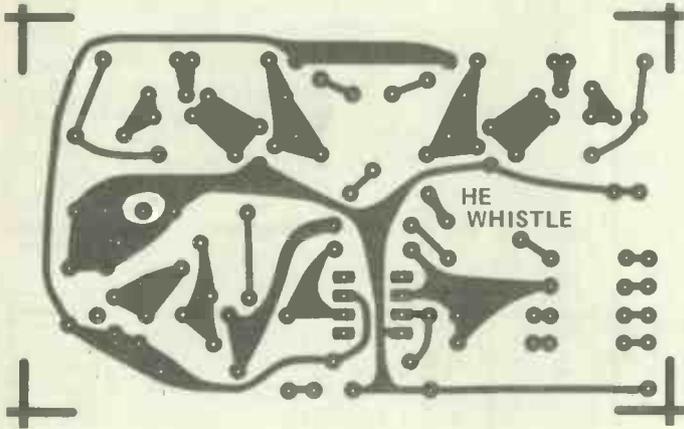

Above: The PCB foil pattern of the HE Bicycle Speedometer

Left: The HE Steam Loco Whistle foil pattern

HE

24HR. CLOCK/APP. TIMER KIT

Switches any appliance up to 1KW on and off at preset times once per day. Kit contains AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triac PCBs & full instructions.

CT1000KB with white box (56, 131 x 71mm) **£17.40**
 CT1000K Basic Kit **£14.90** Ready Built **£22.50**

DVM THERMOMETER KIT

Based on the ICL 7106. This kit contains a PCB, resistors, presets, capacitors, diodes, IC and 0.5" liquid crystal display. Components are also included to enable the basic DVM kit to be modified to a Digital Thermometer using a single diode as the sensor. Requires a 3mA 9V supply (PP3 battery). **£19.50**

AND NOW A DIMMER THAT MAKES TOUCH DIMMERS OBSOLETE

Two years ago TK Electronics launched a touchdimmer kit, the TD300K, which made knob controlled dimmers obsolete. This was such a great success that many magazines and more retailers soon produced similar designs. SO THAT OTHERS MAY FOLLOW, TK have designed a touch dimmer kit with an Infra Red Remote control enabling you to switch and control the brightness of your lights from the comfort of your armchair etc. (as well as manually by touching the frontplate or by using the TDE/K extension kit).

As with all our kits, these come complete with all components including RFI suppression, frontplate, a neon to help you find the switch in the dark and a neat box for the transmitter. The plastic frontplate has no metal pads to touch ensuring complete safety and enabling the plate to be covered with a decorative finish to blend with your room decor.

We have designed the light dimmer unit to fit a standard wall box, the transmitter to fit your hand and the price to fit your pocket.

In two years time everyone will be selling remote control dimmers but you can have your TDR300K kit NOW for only **£14.30** for the dimmer unit and **£4.20** for the transmitter.

For the more athletic of you the TD300K is still available at **£6.50** and the TDE/K at **£2.00**. DON'T FORGET to add 40p P&P and 15% VAT to your total purchase.

MINI KITS

These kits form useful subsystems which may be incorporated into larger designs or used alone. Kits include PCB, short instructions and all components.

MK1 TEMPERATURE CONTROLLER/THERMOSTAT

Uses LM3911 IC to sense temperature (80°C max) and triac to switch heater. 1 KW **£4**

MK2 SOLID STATE RELAY

Ideal for switching motors, lights, heaters etc from logic. Opto-isolated with zero voltage switching. Supplied without triac. Select the required triac from our range. **£2.80**

MK3 BAR/DOT DISPLAY

Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators etc. May be stacked to obtain 20 to 100 element displays. Requires 5.20V supply. **£4.75**

MK4 PROPORTIONAL TEMPERATURE CONTROLLER

Based on the TDA1024. Zero voltage switch, this kit may be wired to form a burst fire power controller or a proportional temperature controller enabling the temperature of an enclosure to be maintained to within 0.5°C. **3KW £5.85**

MK5 MAINS TIMER

Based on the ZN1034E Timer IC, this kit will switch a mains load on (or off) for a preset time from 20 minutes to 35 hours. Longer or shorter periods may be realised by minor component changes. Maximum load 1KW. **£4.50**

TRIACS

400V Plastic Case (Texas)		
3A	49p	16A 95p
8A	58p	
12A	85p	
6A with trigger	80p	
8A isolated tab	65p	
Diac	18p	

DISCO LIGHTING KITS

Each unit has 4 channels (rated at 1KW at 240V per channel) which switch lamps to provide sequencing effects, controlled manually or by an optional opto isolated audio input.

DL1000K. This kit features a bi-direction sequence, speed of sequence and frequency of direction change being variable by means of potentiometers. Incorporates master dimming control. **£14.80**

DL21000K. A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a preset pot. Outputs switched only at mains zero crossing points to reduce radio interference to minimum. **£8.00**
 Optional Opto Input, DLAI **£1.60**

INTEGRATED CIRCUITS

555 Timer	21p
741 Op. Amp	19p
AY-5-1224 Clock	£2.60
AY-5-1230/2 Clock/Timer	£4.50
AY-3-1270 Thermometer (ICL7106 DVM (LCD driver))	£8.20
LM377 Dual 7 W Amp	£7.00
LM3795 Dual 6W Amp	£1.45
LM380 2W Audio Amp	£3.50
LM382 Dual 'low noise Preamp	80p
LM386 250mW low voltage Amp	£1.00
LM1830 Fluid Level Detector	75p
LM2907 1v Converter (5 pin)	£1.50
LM2917 1v Converter (14 pin)	£1.40
LM3909 LED Flasher, Oscillator	£1.60
LM39-1 Thermometer	60p
LM3915 - Dot Bar Driver (Log)	£1.20
MM74C911 4 digit display controller	£2.20
MM74C915 7 segment BCD converter	£6.50
MM74C915 4 digit ctr. with 7 sep. o.p.	98p
S5668 Touchdimmer	£4.50
SL440 A.C. Power Control	£2.50
SN76477 Complex Sound Generator	£1.75
TB800 5W Audio Amp	£2.52
TB810AS 7W Audio Amp	88p
TDA1024 Zero Voltage Switch	£1.00
TDA2020 20W Audio Amp	£1.20
ZN1034E Timer	£2.85
All ICs supplied with data sheets. Data Sheets only 10p each device.	£1.80

REMOTE CONTROL KITS



MK6—Simple Infra Red Transmitter. A pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **£4.20**

MK7—Infra Red Receiver—Single channel, range approximately 20ft. Mains powered with a triac output to switch loads up to 500W at 240V ac, can be modified for use with 5-15V dc supplies and transistor or relay outputs. **£9.00**

* SPECIAL PRICE* MK6 and MK7 together. Order as RC500K **£12.50**

MK8—Coded Infra Red Transmitter—Based on the SL490, the kit includes two IR LEDs, measures only 6x2x1.3 cms. Requires a 9V (PP3) battery. **£1.90**

MK9—4 way Keyboard for use with the MK8 kit, to make a 4-channel remote control transmitter. **£5.90**

MK10—16 way Keyboard for use with the MK8 kit, to generate 16 different codes for decoding by the ML929. **£1.90**

MK12—16 Channel IR Receiver—for use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. Size: 9x4x2 cms, excluding transformer. **£11.95**

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. ADD VAT AT CURRENT RATE TO ABOVE PRICES. 50p P&P MAIL ORDER - CALLERS WELCOME BY APPOINTMENT. SEND SAE WITH ALL ENQUIRIES.




TK Electronics
 (H.E.), 11 Boston Road, London, W7 3SJ
 Tel: 01-579 9794



THE CB ANTENNA
THAT REALLY "ZAPS"
IT OUT

'Firestik'[®]
ANTENNAS

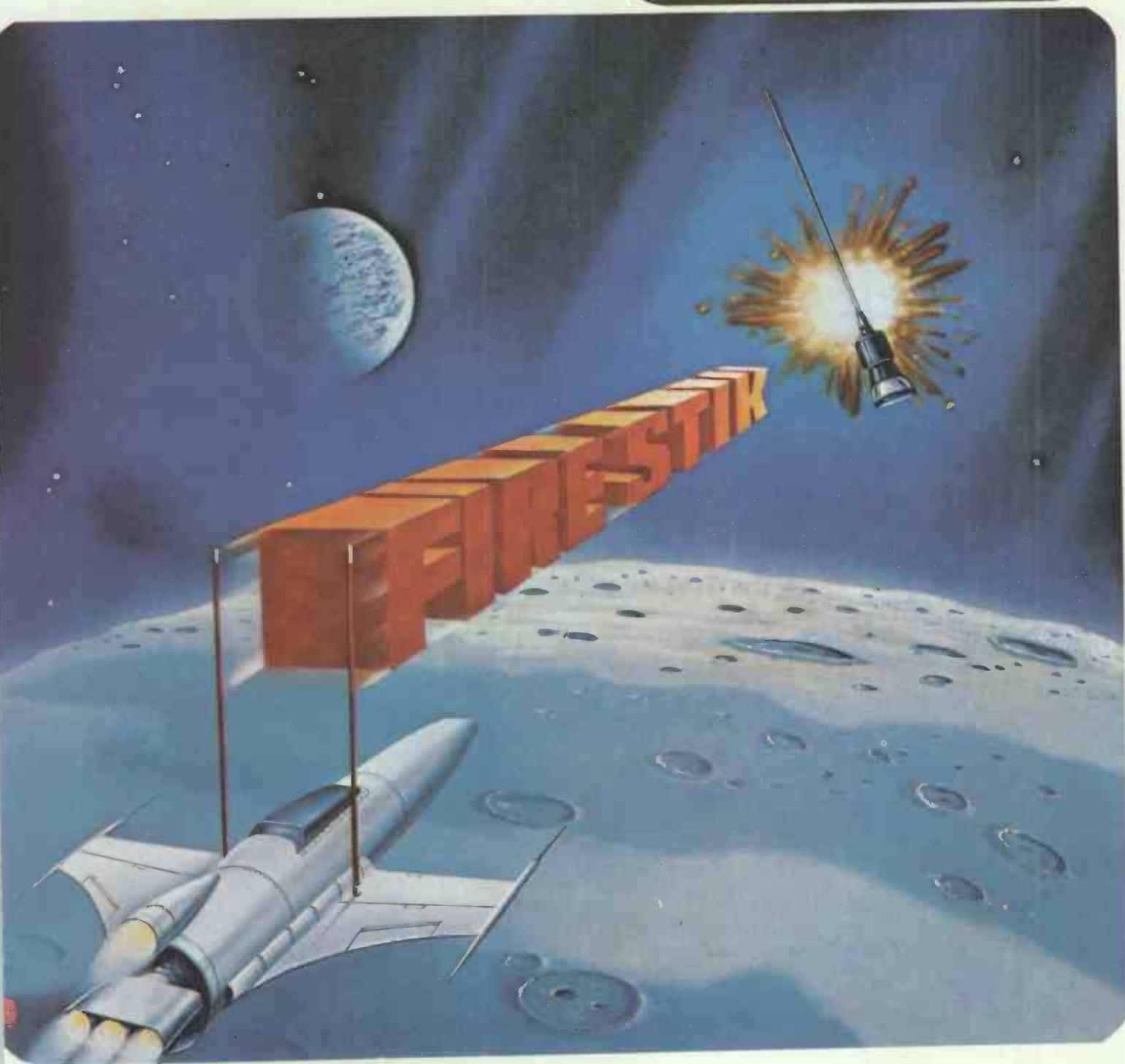


WINTJOY
THE 'CB' PEOPLE

WRITE OR CALL FOR FULL INFORMATION FROM:

WINTJOY LTD. TEL. WALTON-ON-THAMES
103 HIGH STREET (STD 09322) 48145
SHEPPERTON
MIDDLESEX TW17 9BL
ENGLAND

For 24-hr. Answer
Service ring
Teledata on
01-200 0200

Make it for a Song!

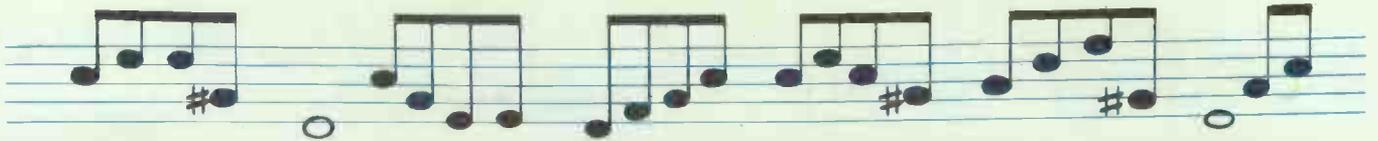

The New **Maplin in Matinée**

Amazing Value
For Only

£299.95 + £99.50 for cabinet if required.

Easy to build. Latest technology — means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices on drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard. Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money. Full construction details will be in *Electronics & Music Maker* magazine.



The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't afford to be without.

Post this coupon now for your copy of our 1981 catalogue price £1.
Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.
I enclose £1.25.

Name _____

Address _____

HE381

MAPLIN

Maplin Electronic Supplies Ltd.
All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR
Telephone: Southend (0702) 554155. Sales (0702) 552911.

Shops:
159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926
284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000
Both shops closed Mondays.

Catalogue now on sale in all branches of WHSMITH  Price £1.00