

FREE

GADGETS, GAMES & KITS SUPPLEMENT INSIDE

Hobby Electronics

JUNE '81

ISSN 0142-6192

60p

For A Down-To-Earth Approach To Electronics

Power Amplifier


over 100 watts/channel

- easy to build
- special kit offer



Radio-

its discovery, development and operation

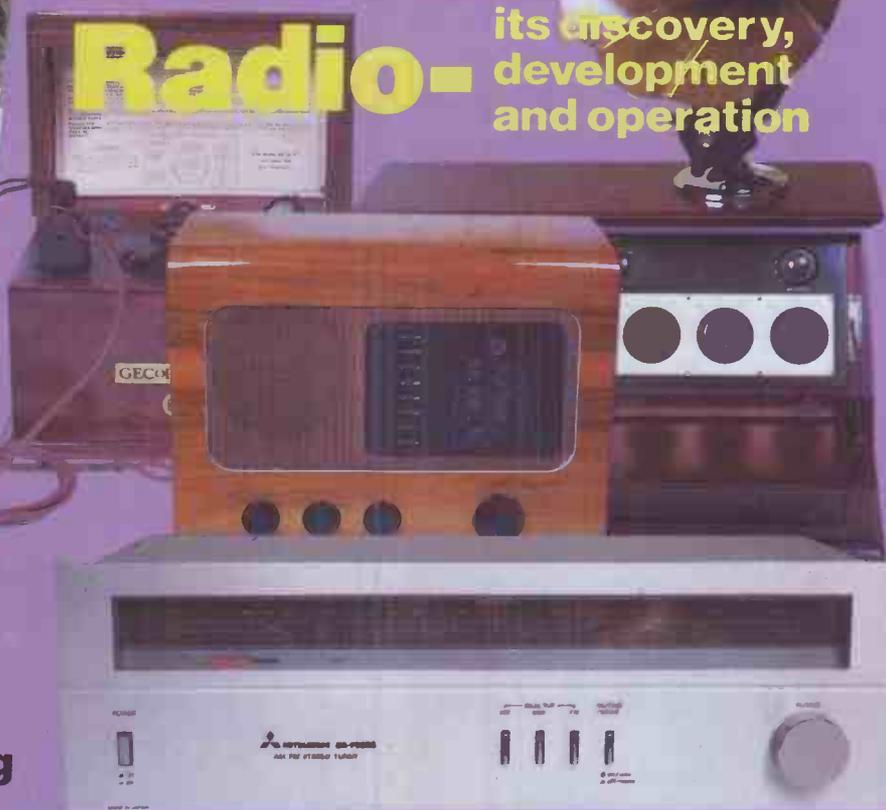

Continuity Checker

- use it for circuit fault finding
- kit under £5

PLUS

Other Projects & CB News Inside

How To Use An Oscilloscope
Special Practical Feature

LINEAR ICs	4000 series	4000 series	TTL	N'	L'PSN'	TTL	N'	L'PSN'	TTL	N'	L'PSN'	TTL	N'	L'PSN'	MICROMARKET	LEDS	LEDS								
TLA120S	1.00	SL1610P	1.60	HA11223	2.15	4A000	0.18	4068	0.25	TTL	N'	L'PSN'	TTL	N'	L'PSN'	TTL	N'	L'PSN'	8224	3.50	STD DOMED TYPES				
L200	1.95	SL1611P	1.60	HA11225	1.45	4001	0.18	4069	0.25	7400	0.13	0.20	7454	0.20	0.30	74128	0.74	74194	1.05	8251	6.25	5mm RED	12p		
U237B	1.28	SL1612P	1.60	HA12002	1.45	4002	0.24	4070	0.30	7401	0.13	0.20	7455	0.20	0.30	74132	0.73	74196	1.34	8255	5.40	3mm RED	clr 15p		
U247B	1.28	SL1613P	1.89	HA12017	0.80	4007	0.30	4071	0.24	7402	0.14	0.20	7460	0.20	0.20	74136	0.40	74197	1.10	6800P	7.50	3mm RED	15p		
U257B	1.28	SL1620P	2.17	HA12402	1.95	4008	0.80	4072	0.24	7403	0.14	0.20	7463	0.20	1.24	74138	0.75	74199	1.60	6810	5.95	2.5x5 YL	17p		
U267B	1.28	SL1621P	2.17	HA12411	1.20	4008AE	0.80	4073	0.24	7404	0.14	0.24	7470	0.40	0.40	74141	0.75	74207	1.60	6820	7.45	5mm GRN	15p		
LM301H	0.67	SL1623P	2.44	HA12412	1.55	4009	0.98	4075	0.25	7405	0.18	0.26	7472	0.30	0.30	74142	0.65	74247	1.60	6850	4.90	3mm GRN	clr 16p		
LM301N	0.30	SL1624C	3.28	LF13741	0.33	4010	0.58	4076	0.90	7406	0.36	0.36	7473	0.35	0.45	74143	3.12	74257		6852	4.85	3mm GRN	16p		
LM308TC	0.65	SL1625P	2.17	SN7660N	0.80	4011AE	0.24	4077	0.35	7407	0.38	0.24	7474	0.35	0.35	74144	3.12	74260		MC2708	6.00	5mm YL	15p		
LM324	0.64	SL1626P	2.44	FREQ. DISPLAY DEVICES		4011B	0.24	4078	0.30	7408	0.19	0.24	7475	0.56	0.45	74145	1.75	74279		2114	6.50	5mm YL	16p		
LM339N	0.66	SL1630P	1.62	AND SYNTH.		4012	0.55	4082	0.28	7409	0.21	0.24	7476	0.41	0.45	74146	1.75	74283		4027	5.78	3mm YL	clr 16p		
LM348N	0.89	SL1640P	1.89	AND SYNTH.		4013	0.55	4093	0.86	7410	0.18	0.24	7478	0.50	0.50	74148	1.09	74293		2102	1.70	3mm YL	18p		
LF351N	0.49	SL1641P	1.89	AA1055	3.75	4015	0.95	4175	1.15	7411	0.26	0.32	7480	0.52	0.40	74149	0.99	74365		2112	3.40	5mm ORA	20p		
LF353N	1.81	TA24202	1.65	SA1058	3.35	4016	0.52	4593	1.15	7412	0.27	0.32	7482	0.75	0.70	74153	0.70	74367		2513	7.54	5mm ORA	20p		
LM374N	3.75	ULN2242A	3.05	SA1058	3.35	4017	0.80	4506	0.68	7413	0.52	0.52	7485	0.40	0.99	74154	1.30	74368		HM4716	4.00	5mm ORA	clr 29p		
LM380N-14	1.00	ULN2282B	1.00	SA1059	3.35	4019	0.60	4510	0.99	7414	0.51	0.51	7485	1.04	0.99	74154	1.30	74368		81LS97	1.25	3mm ORA	19p		
LM380N-8	1.00	CA3080E	0.70	11C900C	14.00	4020	0.98	4511	1.49	7415	0.30	0.40	7486	0.40	0.40	74155	0.75	74374		1.80	2.5x5 ORA	24p			
LM381N	1.81	CA3095E	1.94	LN1232	19.00	4021	0.82	4512	0.98	7416	0.30	0.30	7486	2.05	0.90	74156	0.80	74377		1.90	5mm Infra Rd	50p			
ZM130CE	1.98	CA3090AO	3.35	LN1242	19.00	4022	0.96	4514	2.55	7417	0.30	0.24	7489	0.42	0.90	74157	0.78	74378		2.15	5mm Infra Rd	50p			
NE544N	1.80	CA3123E	1.40	MSL2318	3.84	4023	0.25	4518	1.03	7420	0.19	0.24	7491	0.85	0.25	74158	0.78	74393		1.40	5mm Infra Rd	50p			
NE555N	0.30	CA3130E	0.80	MSM5523	11.30	4024	0.76	4520	1.09	7421	0.38	0.24	7492	0.50	0.78	74159	2.10								
NE555E	0.50	CA3130T	0.90	MSM5524	11.30	4025	0.25	4521	2.36	7422	0.27	0.28	7493	0.57	0.99	74160	0.99	1.30							
NE560N	3.50	CA3140E	0.46	MSM5526	7.85	4026	1.30	4522	1.49	7423	0.27	0.27	7494	0.85	1.15	74161	0.99	0.98							
NE662N	4.05	CA3189E	2.20	MSM5526	7.85	4028	0.79	4529	1.61	7427	0.32	0.35	7494	0.95	1.20	74163	0.99	0.95							
NE664N	4.29	CA3240	1.27	MSM5527	9.75	4029	1.04	4539	1.28	7428	0.35	0.26	7496	0.58	1.20	74163	0.99	0.95							
NE665N	1.00	MC3357P	0.85	MSM5527	9.75	4030	0.59	4549	3.50	7430	0.17	0.26	7497	1.85	0.45	74164	1.20	1.30							
NE665N	1.60	LM3900N	0.80	MSL2312	3.84	4035	1.20	4554	1.73	7432	0.32	0.28	74107			74165	1.20	1.45							
NE570N	3.85	LM3909N	0.68	SP8629	3.85	4040	0.98	4560	2.18	7437	0.40	0.35	74109	0.63	0.45	74165	1.20	1.45							
SL624	3.28	LM3914N	2.80	SP8647	6.00	4042	0.85	4566	1.59	7438	0.33	0.28	74110	0.54	0.40	74169	2.10								
TB4651	1.81	LM3915N	2.80	95H90PC	7.80	4043	0.85	4568	2.18	7440	0.20	0.28	74111	0.68	0.40	74170	2.30	2.88							
uA709HC	0.64	KB4400	0.90	HD10551	2.45	4049AE	0.83	4569	3.03	7441	0.74	0.99	74113	0.70	0.75	74175	0.87	1.10							
uA709PC	0.65	KB4406	0.60	HD44015	4.40	4044	0.34	4572	0.30	7442	0.70	0.99	74112	0.85	0.40	74176	0.80								
uA710HC	0.65	KB4412	1.95	HD12009	6.00	4046	1.30	4585	1.00	7443	1.15	0.99	74114	1.15	0.40	74176	0.80								
uA710PC	0.59	KB4413	1.95	HD44752	8.00	4047	0.99	7444	1.12	7444	1.12	0.89	74118	0.85	0.99	74177	0.84								
uA741CH	0.66	KB4417	3.80	MC145181	12.45	4049	0.52	7445	1.05	7445	1.05	0.99	74120	1.15	0.99	74181	2.80	3.50							
uA741CN	0.27	KB4420B	2.09	MC145166	8.75	4050	0.55	7446	0.66	7447	1.32	0.25	74121	0.48	1.80	74182	2.80	2.98							
uA747CN	0.70	TD4420	1.65	MIC		4051	0.78	7447		7447		0.89	74122	0.46	1.80	74184	1.35								
uA748CN	0.36	KB4423	2.30	ICM7106CP	9.55	4052	0.79	7448	0.66	7448	0.66	0.99	74123	0.73	1.80	74185	1.34								
uA753	2.44	KB4424	1.65	ICM7107CP	9.55	4053	0.78	7449		7449		0.99	74124	2.30	1.80	74190	0.92								
uA758	2.35	KB4431	1.95	ICM7216BP	19.50	4063	1.18	7451	0.20	7451	0.20	0.25	74125	0.55	0.46	74192	1.20	1.80							
TB4820M	0.78	KB4432	1.95	ICM7555	0.94	4066	0.57	7453	0.20	7453	0.20		74126	0.57	0.46	74193	1.42	1.80							
TC9A40E	1.80	KB4433	1.52																						
TD1028	1.11	KB4436	2.53																						
TD1029	2.11	KB4437	1.75																						
TD1054	1.45	KB4438	2.22	32.768kHz	2.70	10.245	2.00	RC XTALS																	
TD1062	1.95	KB4441	1.35	100kHz	3.85	10.6985	2.50	AM TX/RX																	
TD1072	2.69	KB4445	1.29	455kHz	5.00	10.700	2.00	FM TX																	
TD1074A	5.04	KB4446	2.75	1.000MHz	2.95	10.7015	2.50	3rd or 30pF																	
TD1083	1.95	KB4448	1.65	3.2768	2.70	11.00	2.00	HC25U	1.65																
TD10A90	3.05	NE5044N	2.26	4.000	2.00	11.115	2.00	FMTX: Fund																	
HA1137	1.20	NE5532N	1.85	4.1934	2.00	11.520	2.00	20pF HC25U																	
HA1136	2.00	S00000	1.85	4.096	2.00	8.9985	2.00	3rd or 30pF	1.85																
HA1197	1.00	SL6270	2.03	4.032	2.00	9.0015	2.00	PAIRS..AM	3.10																
LM1220	1.40	SL6310	2.03	4.433619	2.00	21.000	2.00	PAIRS..FM	3.25																

Hobby Electronics

JUNE 1981
Vol 3 No 8

Editor: Hugh Davies Assistant Editor: Keith Brindley Editorial Assistant: Judith Jacobs
Drawing Office Manager: Paul Edwards Group Art Editor: Paul Wilson-Patterson BA
Managing Editor: Ron Harris B Sc

PROJECTS

- ★ **POWERAMP**
High-power, high-quality, high-fidelity amplifier 10
- CONTINUITY CHECKER**
Connected or unconnected, this project gives audible warning 20
- ELECTRONIC ORGAN**
Second part of our superb organ project 43
- ENVELOPE GENERATOR**
Electronic musical effect to alter your instrument's sound . 51
- INFRA-RED CONTROLLER**
A hand-held transmitter to match last month's receiver . . 60
- PCB FOIL PATTERNS**
At the bottom of the projects 64




The radio receivers on this month's cover include three from the Science Museum. Left is a GECophone crystal set, which cost £5.50 in 1923. Next to it is a Marconiphone 81, a 'straight-eight' luxury TRF receiver. It used triode valves, and cost £49.50 (plus £5 royalty) in 1925. In front of these is a Murphy A52. This had nine valves, and was a double-superhet. It cost £18.50 when it was introduced in 1938.

In the foreground is the latest AM/FM stereo tuner from Mitsubishi, the DA-F630E. This contains four ICs, 24 discrete transistors and 20 diodes, including six LEDs. It costs around £97.

FEATURES

- ★ **HOW TO USE AN OSCILLOSCOPE**
John Strong tells you how to use a 'scope 15
- ★ **RADIO**
Early discoveries and developments 24
- YOUR LETTERS**
Readers' correspondence 29
- GADGETS, GAMES & KITS**
FREE pull-out supplement 31
- BUILDING SITE**
Front panel lettering — how we do it 39
- O LEVEL Q & A**
A teach-in on op amps and systems 47
- CLEVER DICK**
CD answers back 55
- FAMOUS NAMES**
Heinrich Hertz — the man who discovered radio waves . . 56
- ★ **VIDEO DISC UPDATE**
Latest news on video disc systems 59
- BREAKER ONE FOUR**
Report on FM CB specification 62

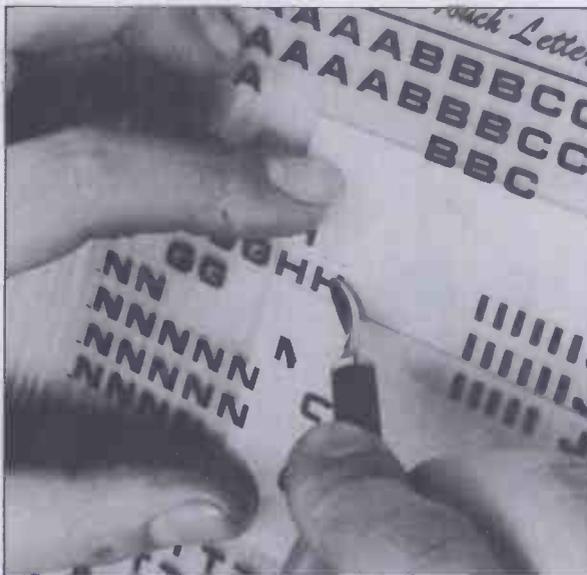

NEWS & INFO

- Monitor 6
- HE Next Month 8
- ★ Oscilloscope Offer 18
- ★ Citizens Band Exhibition 40
- Books From HE 42
- Backnumbers 64
- Subscriptions 65
- Classified Ads 66



Advertisement Manager: Stephen Rowe Advertisement Representative: Sally Holley Creative Director: Diego Rincón Managing Director: T. J. Connell

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01 437 1002. Telex No 881 1896. Published by Modmags Ltd.
Distributed by Argus Press Sales & Distribution Ltd, 12-18 Paul St, London EC2A 4JS. Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.
Copyright: All material in this publication is subject to world-wide copyright protection. Permission to reproduce printed circuit board patterns commercially or marketing of kits of the projects must be sought from the Publisher. All reasonable care is taken in the preparation of the magazine to ensure accuracy but Modmags cannot be held responsible for it legally. ©Copyright 1981 Modmags Ltd **ABC** Member of Audit Bureau of Circulation.



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of crossover distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS and are easier to mount. Connections are five pin through hole. I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLIEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.



Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR

(Standard O-P Transistors)


CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fidelity and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

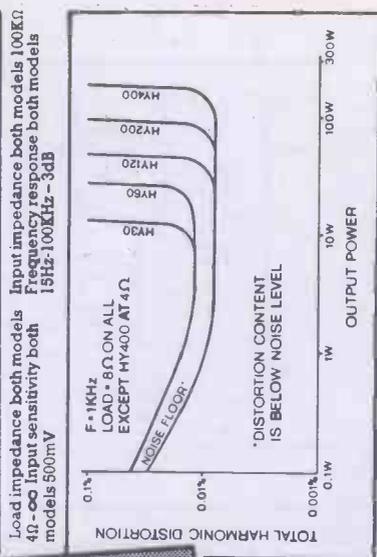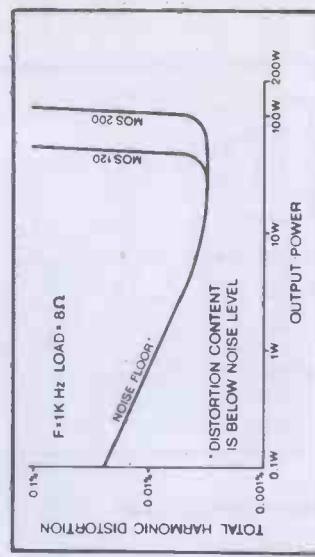

Load impedance both models 4Ω - ∞ Input sensitivity both models 500mV
Frequency response both models 15Hz-100KHz - 3dB

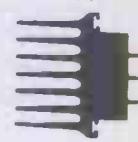Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages:—
Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting, standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes - HY6 - 45 x 20 x 40 mm. HY66 - 90 x 20 x 40 mm. Active Tone Control circuits provide ± 12 dB cut and boost. Inputs Sensitivity - Mag. PU. - 3mV; Mic - selectable 1-12mV; All others 100mV. Tape O/P - 100mV; Main O/P - 500mV; Frequency response - D.C. to 100KHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
 HY66 stereo £12.19 + £1.83 VAT Connectors included
 B6 Mounting Board for one HY6 78p + 12p VAT
 B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.


- PSU30 + 15V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
- PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
- PSU50 for use with 1 or 2 HY30's £10.94 + £1.64 VAT
- PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
- PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
- PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
- PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
- PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
- PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
- PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
- PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT

★ Freepost facility

When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER

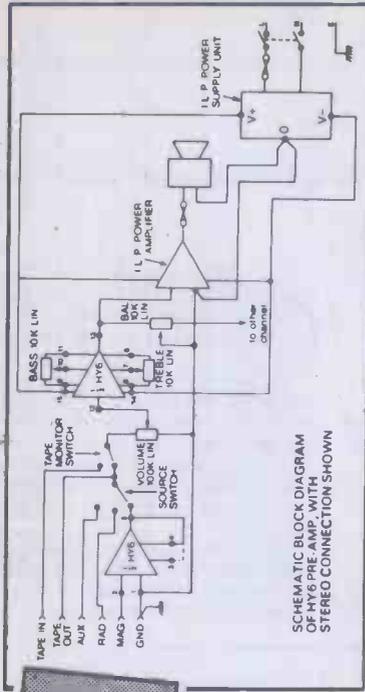Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



SCHEMATIC BLOCK DIAGRAM OF HY6 PRE-AMP WITH STEREO CONNECTION SHOWN

- DISTORTION TYPICALLY 0.005 %
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ± 15 to ± 60 V

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

1971-1980 TEN YEARS OF PLANNED PROGRESS

When, in 1971, Ian L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P. are simply ahead and staying there.

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply

..... Total purchase price £.

I enclose Cheque Postal Orders International Money Order


Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature

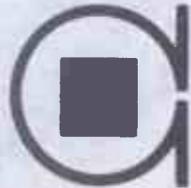NO QUIBBLE 5 YEAR GUARANTEE
 7-DAY DESPATCH ON ALL ORDERS
 BRITISH DESIGN AND MANUFACTURE
 FREEPOST SERVICE



I.L.P. ELECTRONICS LTD.

FREE POST 4 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
 Telephone (0227) 54778 | Technical (0227) 64723 | Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

UK ORDERS DESPATCHED FREE

Monitor

HEATHKIT®



NEW Heathkit products in this catalogue

- J-Matic™ Memory Keyer
- Hand-held Digital Capacitance Meter
- Antenna Tuner with Wattmeter/SWR Bridge
- FORTRAN, Microedit™ BASIC™ and PASCAL™ Programming Courses
- Hi-Fi Audio Products
- Ultrasonic Car Alarm

Lower Prices In Heathkit Catalogue

Some of the general-purpose test instruments featured in Heathkit's Spring/Summer '81 catalogue have been reduced in price.

Among the test meters, the SM2215 hand-held digital multimeter, which has a liquid-crystal display and a maximum accuracy of 0.03% of full scale, now costs £76 assembled or £63.25 in kit form (original price was £87.40).

Hand-held frequency counter SM2400, which has a range of 50 Hz to 512 MHz and typical input sensitivity of 10 mV RMS, now costs £89 assembled or £85.10 as a kit (original price £102.35).

High-quality Sound . . . All Round The House

SoundLink is a new product from a new company, IMP Electronics of Cambridge. It enables you to relay music from most hi-fi systems to an extension loudspeaker — without trailing cables.

Based on what is described by IMP as the 'established principle of FM mains transmission', the system is supplied as a pair of ready-built circuit board modules.

For the system to operate, it is first necessary to connect the input module to your hi-fi system

Function generator SG1271, covering 1Hz to 1MHz, is now £125 assembled or £121.90 as a kit (original price £143.75).

And among the power supplies, the SP2718 tri-output power supply (5 VDC fixed and 2 x 0 to 20 VDC variable) has been priced at £99 assembled, or £66.70 as a kit (original price £113.85).

Emphasis is placed on digital electronics in this catalogue, with 16 of its 64 pages dedicated to computer hardware, software and programming courses.

HE hopes to review a couple of Heathkit's courses in a future Gadgets, Games & Kits supplement.

The catalogue is available (send 25p in stamps) from: Heath Electronics (UK) Ltd, Bristol Road, Gloucester GL2 6EE or The London Heathkit Centre, 233 Tottenham Court Road, London W1P 9AE.

and to connect the output module to an extension speaker. (Additional output module and speaker combinations can be added as required.) But that's not the complete story — some additional hardware is required, including two mains transformers, two potentiometers, two switches and, of course, the extension speaker.

HE hopes to review the SoundLink system in a future Gadgets, Games & Kits supplement.

SoundLink is available for £45.50 from IMP Electronics, 34 Caraway Road, Fulbourn, Cambridge CB1 5DU (tel 0223 881105).

Sussex Mobile Rally

A second Sussex Mobile Rally is to be held at Brighton Race Course on Sunday 19 July 1981. The event, organised by six amateur radio clubs in the Sussex area, will run from 10.30 am to 6 pm.

Last year nearly 3,000 people attended the rally, with more than 100 stands under cover. This year the rally will be larger (over 20,000 sq ft of display area) with more trade stands dealing with all forms of electronics including amateur radio, microprocessors, components and CB.

This rally will cater for the family, with free trips to the sea front by minibus, restaurant and bar facilities and many attractions.

Entrance charge will be 50p (including draw ticket), with no charge for disabled persons or for children under 14 years.

Parking space for more than 4,000 cars will be available, together with an area for caravan parking.

More details are available from: A.K. Baker (G4GNX), 38 Elphick Road, Newhaven, Sussex (tel 07912 5327 evenings).

HE COMPETITION — Project Design for IYDP

Come on! You're not trying hard enough! The response so far to HE's electronic project design competition for the International Year of Disabled Persons, announced in the April '81 issue, has been disappointing. Or perhaps your project entries will all come in at the last moment!

Just think of a physical or mental handicap, or of a disabled person you know and then think: 'What ingenious device can I come up with to help cope with that handicap or aid that person?'

As stressed in the April issue, no design is too small — and the first prize is big — £200 in cash. So if you have any difficulties

or questions, give Hugh Davies a ring on 01 437 1002 or drop him a line at HE, Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE. Please head your envelopes 'Competition'.

Next month we plan to run a special article on electronic aids for the disabled.



Clean Up Your Video Head

Cleaners in cassette form have been available for some years for audio tape heads: now one has been produced specifically for tape heads in video recorders. Intended for use with tape head systems in BETA-MAX recorders, the Bib Videophile Edition tape head cleaner is claimed to have sufficient tape for 20 cleaning operations, covering 800 hours of playing.

After each 40-hour period of playing, the cassette is inserted in the normal way and run for 15 seconds. No portion of tape, once run through the machine, should be replayed.

Recommended retail price for the cleaner is £8.98, including VAT.

Bib Hi-Fi Accessories, Kelsey House, Wood Lane End, Hemel Hempstead, Herts HP2 4RQ (tel 0442 61291).



PETs On Show

The Second International PET Microcomputer show will be held at the West Centre Hotel, London SW6, from June 18 to 20.


The show, open to the public from 1.00 pm to 7.00 pm on Thursday 18 June, 10.00 am to 7.00 pm on Friday 19 June and 10.00 am to 5.00 pm on Saturday 20 June, will enable visitors to see about 300 PET computers showing off their tricks.

Among the estimated 100 exhibitors will be companies from all over Europe and the US. Also exhibiting will be PET user club groups.

Apart from computer systems and applications for business, medicine, education and engineering, products and programs for the home will be on show.

Of particular interest to HE readers will be the Commodore VIC colour home computer, which can be connected to a TV and is likely to cost under £200.

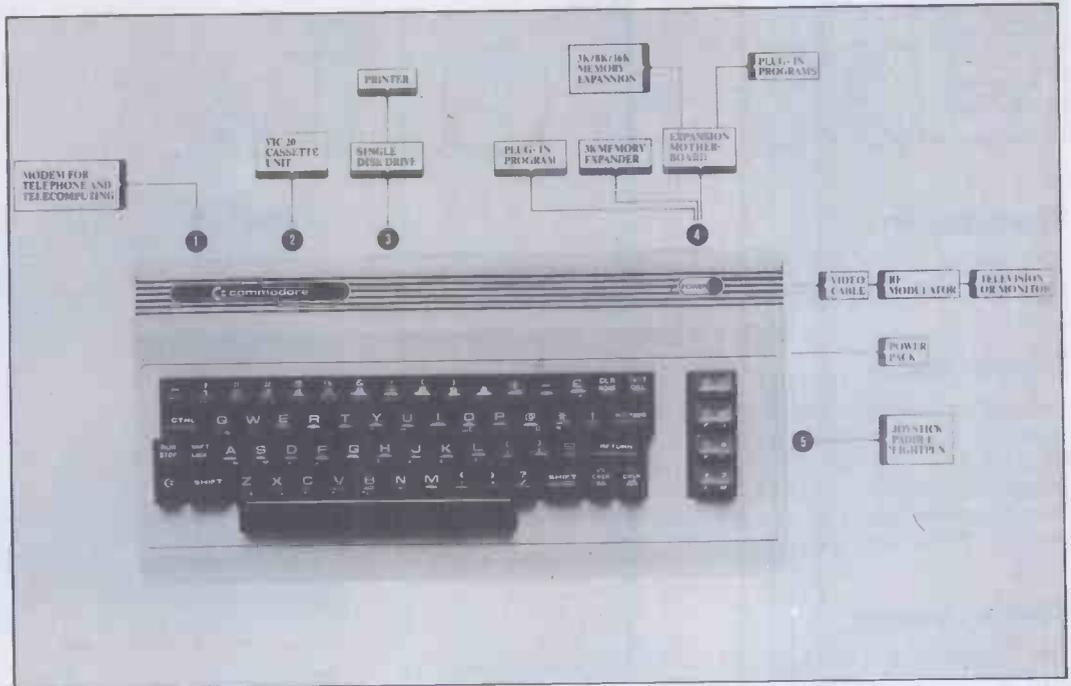HE hopes to report on this event in a coming issue.



Commodore VIC 20 computer

Keep A Hold On Your Cells

Two new holders are available from Magenta Electronics for RM401 mercury cells. The first, priced at 22p, holds a single 1.4 V cell, while the other, priced at 27p, takes two cells side-by-side.


Despite their small size (about 28 mm long by about 11 mm diameter) RM401 cells have a remarkable capacity — 800 mA/h. Shelf life to 75% of full capacity is *three years*. These cells are available from Magenta at 64p each.

Most cells are difficult items to connect or solder leads to, and are equally difficult to anchor down to a circuit board. The

holders are fitted with solder terminals and have pre-drilled holes for mounting.

In common with most other mercury cells, the case of the RM401 is positive (+ve) while the tip is negative (-ve). So the springs in the holders go to the case-ends while the studs go to the tips. Each holder has a small picture of a cell between the terminals as a guide. However, as pointed out by Magenta, because the holders were originally intended for another type of battery having the same case size as the RM401, it is best to ignore the pictures and be guided by the spring and stud connections instead.

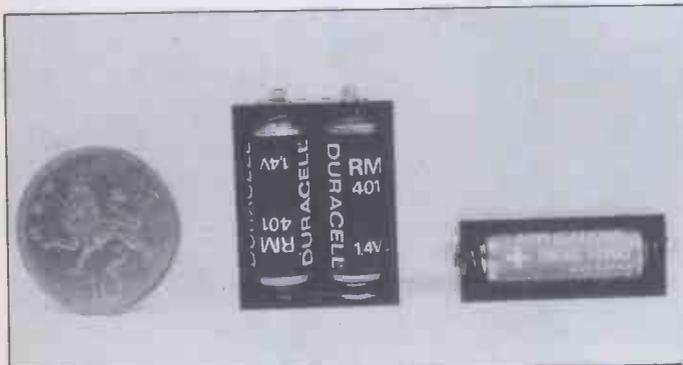Add 40p with each order placed with Magenta Electronics Ltd., 135 Hunter St., Burton-on-Trent, Staffs DE14 2ST (tel. 0283 65435).



Vintage Radio

Readers who have an interest in radio can do two things this month: first, read *Radio*, the special feature starting on page 24 in this issue; and second, take a subscription to the *Antique Wireless Newsheet*.

This A5-sized booklet is published by The Vintage Wireless Company in Bristol. The company, run by Tudor Gwilliam-Rees, specialises in vintage radio (or should we say 'wireless') receivers and all the associated hardware and nostalgia.

Gwilliam-Rees told HE that the most sought-after sets are the BBC period models from the early 1920s. These have a type-approval stamp, with the letters 'BBC' in a circle, and with 'type approval by the Post Master General' printed around the circle.

He said that, at present, most collectors are on the look-out for sets from the 1930s. The more unusual they look the better: square-box sets have little value unless they possess some exceptional technical qualities. It appears, however, that even these vintage sets have not escaped

the ravages of the recession, because their value has dropped in recent months.

Gwilliam-Rees is at present restoring some receivers for the company which originally made them in the early-to-mid 1930s — Clarke-Atlas.

Subscription to the *Newsheet* is £2.50 per year (£5.00 for overseas via airmail). It is issued 12 times a year.

The Vintage Wireless Company is based at 64 Broad Street, Staple Hill, Bristol BS16 5NL (tel. 0272 565472).

The Vintage Wireless Company
 IMPORT EXPORT
 OBSOLETE ELECTRONIC
 RADIO, T.V. & INDUSTRIAL
 VALVES
 ANTIQUE WIRELESS

OFFICE & SHOWROOM AT:
 64 Broad Street, Staple Hill, Bristol BS16 5NL, Gt. Britain.
 Telephone: Bristol (0272) 565472. VAT Reg. No. 130 9018 47.

THE ANTIQUE WIRELESS NEWSHEET

Number 68
 An article on the 'Golden Era' of your collection has appeared with this issue...
 U.K. & E. Post - £2.50 per year.
 Overseas via airmail - £5.00 per year.

THE TRUTH ABOUT THE WIRELESS MARKET

The Truth, the whole Truth and nothing but the Truth.

If your set gives you poor quality, it is telling lies about the Broadcast Station. If it fails to transmit the low bass notes, it is concealing part of the truth. You want true reception, you are entitled to it. So is your family. There is a way to get the truth in wireless reception —

FERRANTI

The following back numbers of the *Antique Wireless Newsheet* are still available, free upon receipt of a suitable stamped addressed envelope: No's 07, 08, 09, 10, 11, 12, 13, 14, 15, 16, 17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, 30, 31, 32, 33, 34, 35, 36, 37, 38, 39, 40, 41, 42, 43, 44, 45, 46, 47, 48, 49, 50, 51, 52, 53, 54, 55, 56, 57, 58, 59, 60, 61, 62, 63, 64, 65, 66, 67, 68, 69, 70, 71, 72, 73, 74, 75, 76, 77, 78, 79, 80, 81, 82, 83, 84, 85, 86, 87, 88, 89, 90, 91, 92, 93, 94, 95, 96, 97, 98, 99, 100.

Buying in old dealers' shops, etc., is often a waste of time. It is always preferable to find the 'odd' circuit diagram, service sheet, valve, etc. Often the only way to get the form of old instructions, etc. Recently however, we found a 'post' box... and a blue enamel found and having the title of 'Radio'... complete in their presentation.

Hobby Electronics

THE JULY ISSUE IS ON SALE JUNE 12th



Roger Jefcoate demonstrating the TCL Lightwriter, an electronic aid for the handicapped

Next month

Here are just a few of the things we have planned for the July issue of Hobby Electronics.

Burglar alarm

A simple-to-build yet very effective thief detector, designed to stop burglars in their tracks. HE Ultrasound Burglar Alarm uses the tried and tested Doppler effect along with ultrasonic sound waves, in a low-cost *battery operated* circuit, which means you won't have to spend all the money you are trying to protect on building it.

Treble booster

The next project in our series of complementary guitar effects is a good-looking, and even better-sounding treble booster. It has two switched boost options — a 'normal' boost, identical to that from other circuits and a 'super' boost for real ear-splitting treble from your guitar. It is housed in the same style case as two previous projects, the Fuzzbox, and this month's Envelope Generator.




Doorbuzzer

Commercial doorbells and buzzers usually operate along electromagnetic lines. Typically they need a low-voltage transformer too. Our doorbuzzer is different — it's battery operated for a start (a single PP3-sized battery should give around six months' operation) and it features a solid-state design (ie, there are no moving parts to wear out). Total cost of this project should be around a fiver. With those specifications and that price, what more could we offer?

Electronic aids for the disabled

How many projects have you built that have been fun for a while and then have been either left to gather dust or just be discarded? Hugh Davies spoke to Roger Jefcoate, consultant assessor and lecturer on technical aids for disabled people and was made aware that many electronic projects, some of them very simple, can be of great benefit to the disabled. This article describes some projects in use, looks at computer-controlled aids and opens the way for *your* ideas.

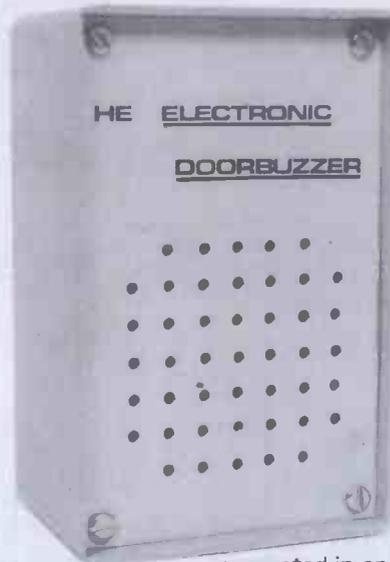

Plus

News and information, circuits, projects, regular features, your views — all presented in an understandable and down-to-earth fashion.

Keep up with the rapidly changing world of electronics with Hobby Electronics — the magazine that's written for the electronics enthusiast and hobbyist.

Items mentioned here are those planned, but unforeseen circumstances may affect the actual contents

Power Amplifier

Designed to match the HE Pre-amplifier, this project allows you to choose power output level to suit your own requirements. Modular construction makes it easy-to-build



HAVE YOU EVER heard 300 W of power (ie 150 W per channel into speakers of 4R impedance) at a distance of only 6 ft? It's loud.

Pardon?

I SAID IT'S LOUD! In fact, after we had tested the HE Power Amplifier in our project laboratory it took two hours before our hearing had returned to normal and we could hear anybody knocking on the door to ask what it was.

No, really, joking apart, 150 W per channel *is* loud and for those readers who want a very good quality amplifier system but with not quite that power output, there is an option to lower the output to the more manageable figure of 60 W per channel.

Whatever output power rating you choose, your finished amplifier will be a high quality device. Distortion is very low, meaning that the amplifier will faithfully reproduce at its output an amplified version of whatever signal is applied to the input, without adding any extra bits of its own. Its frequency range limits are well below and above the limits of hearing, so whatever you can hear, the amplifier can amplify with no problem.

Other Uses

The amplifier is suitable not only for home use but, because of its high output power option, is ideal as a high-power disco amplifier, a group instrument amplifier for guitar, organ, etc, or a high quality public address (PA) amplifier for on-stage use in, say, a theatre. In most

situations, the amplifier will be limited only by the other equipment, eg pre-amplifier, speakers, etc, used with it.

Stylish Appearance

Apart from extremely good technical specifications the power amplifier is also aesthetically pleasing, being housed in a sleek, low-profile, black plastic-coated steel case.

The modular format of the project means that even those readers who aren't too sure of their capabilities should be able to build it. The case is available ready to use, pre-formed and punched to fit all hardware. The most difficult job is the wiring-up and we'll take you through that stage, step-by-step, next month.

Table 1 is a list of the specifications of the complete amplifier.

Bandwidth	10 Hz to 70 kHz (± 3 dB)
Input sensitivity	775 mV (variable by RV1)
Input impedance	10k
Harmonic distortion	<0.06%
Signal-to-noise ratio	100 dB
Damping factor	minimum 100

Table 1.
Power Amplifier electrical specification

Construction


You have to decide at this point which power rating you want. As supplied, the amplifier printed circuit boards (PCBs) are complete and ready for operation in their higher power option. To derate

them to 60 W amplifiers, the following procedure should be adhered to.

Desolder and remove the middle two power transistors on the heatsink. Then desolder and take out R34 and R35. Replace the two resistors with wire links. You now have a 60 W power amplifier PCB.

The remainder of this month's work concerns the case hardware.

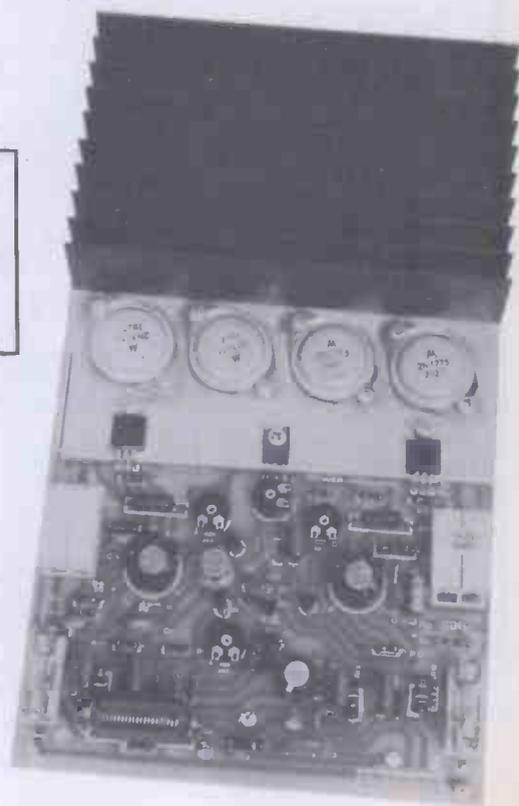First, locate and fit all the rear panel components onto the blank chassis of the case: three fuseholders, two phono sockets, a 5-pin DIN socket, four 4 mm sockets, the power supply cable clamp, and the small false panel. Figure 1 shows where each part is positioned.




Next fasten the mains on/off switch and neon to the inside front panel. Leave the false front panel aside for the time being, safe from harm.

Locate and fit the inside hardware, as shown in Fig. 2, by bolting from the underside of the chassis.

Two special points to note are:

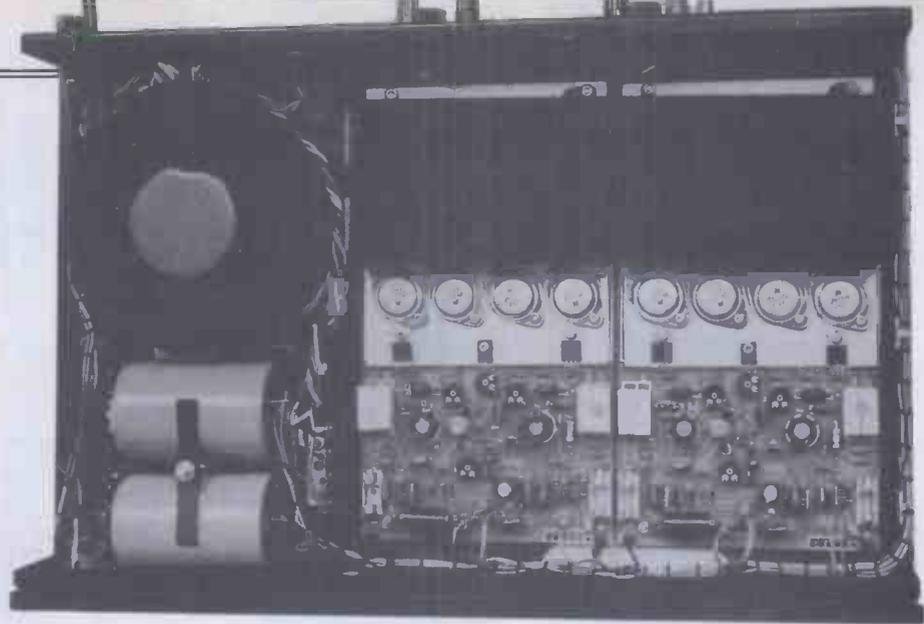- the 12-way terminal block is held by two self-tapping screws
- both PCBs are mounted as follows: Fasten eight nuts and bolts (one per corner of each board) to the chassis bottom. Put a nylon washer over the end of each bolt. Insert the two PCBs into the chassis so that the bolts go through the ready-drilled holes in the corners of the boards. Fasten the boards down with a nut on each bolt



Internal view of the completed project. Below you can see details of the chassis and all parts.

Next month we shall describe the wiring-up procedure of the project.

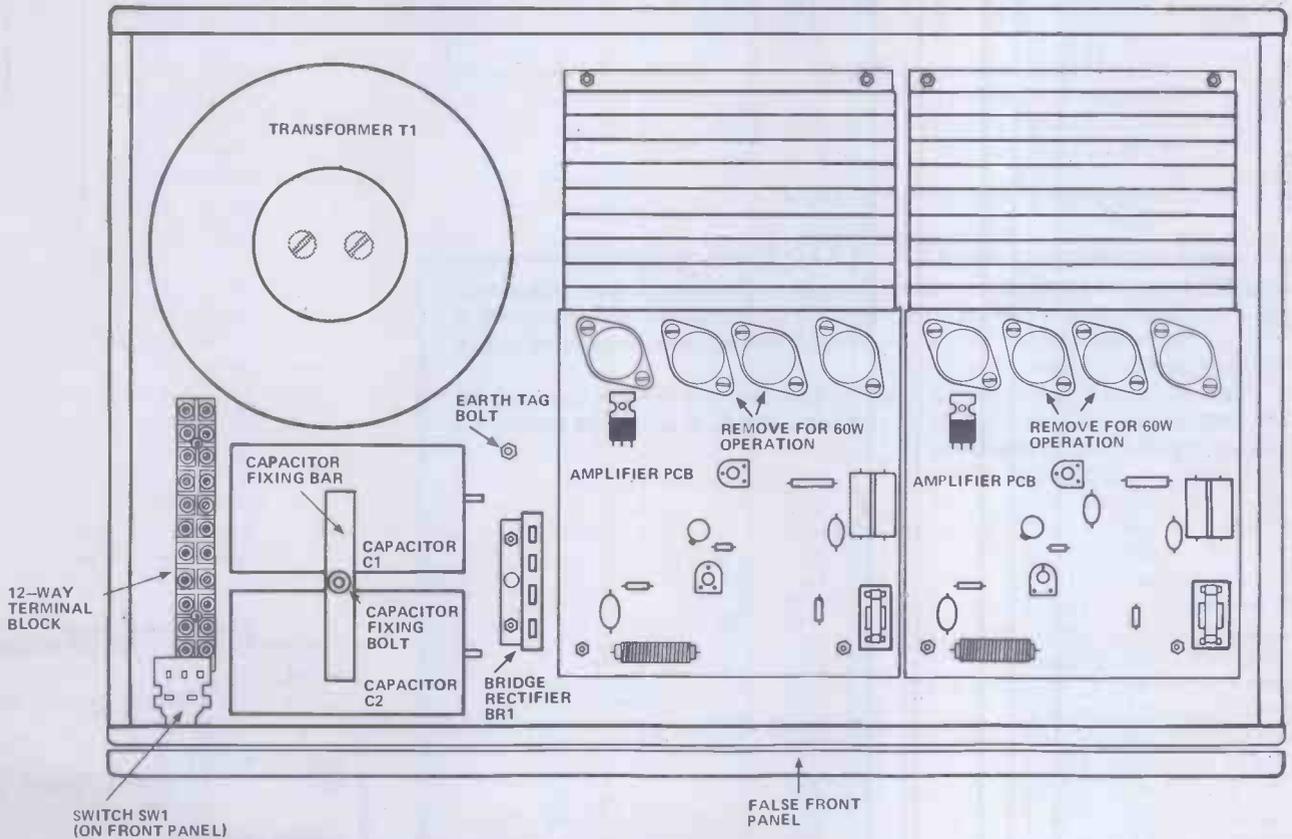


Figure 1. Positioning details of the major parts within the chassis of the HE Power Amplifier

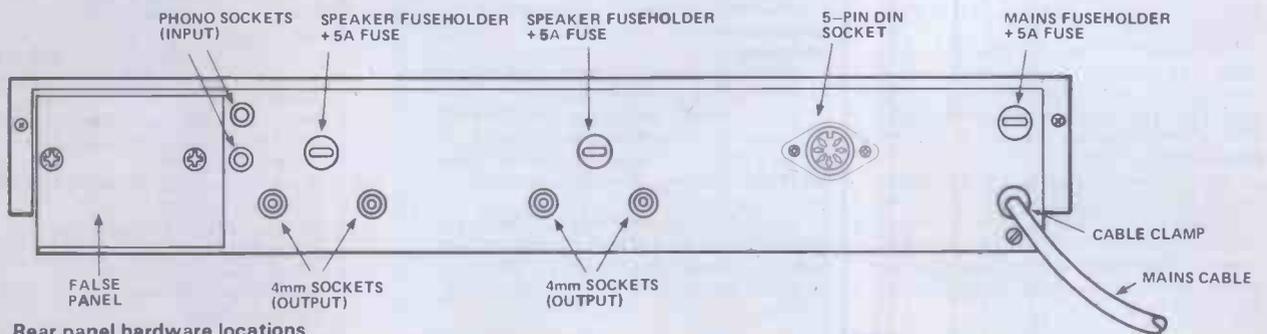


Figure 2. Rear panel hardware locations


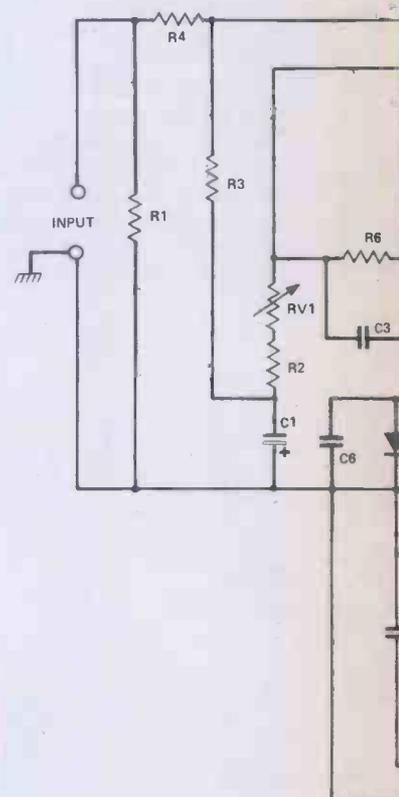
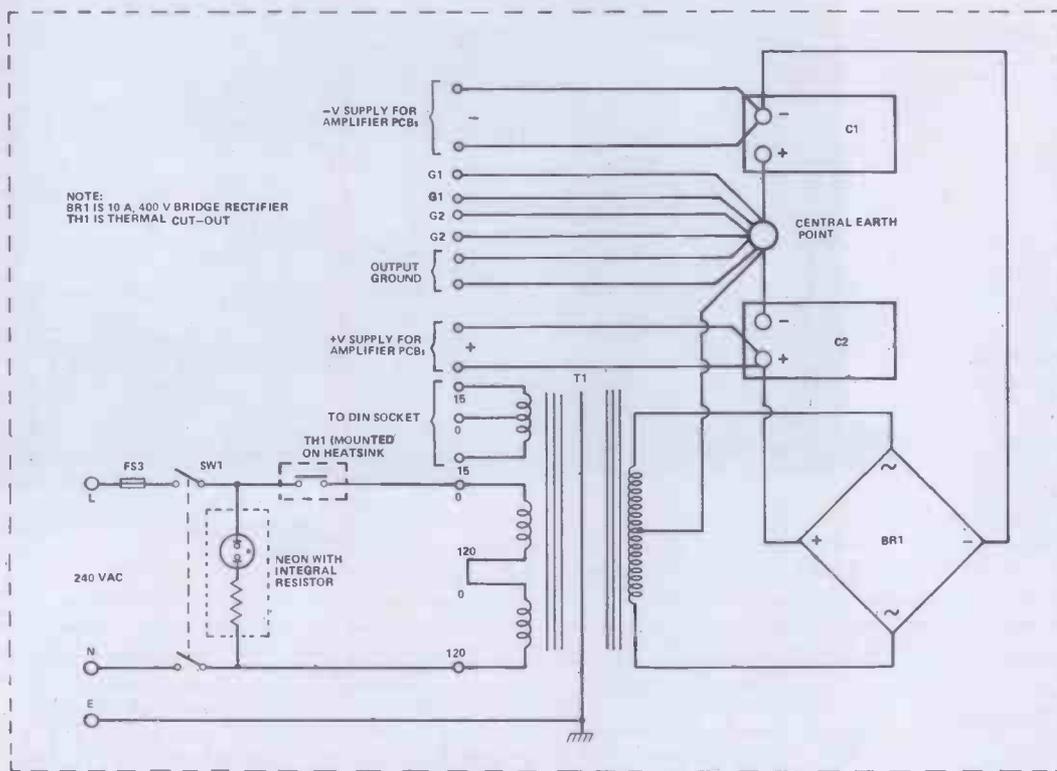


Figure 3. Circuit of the power supply used in this project

How It Works

The HE Power Amplifier consists of three main stages: an input stage which allows simple gain adjustments, a driver stage which provides the power necessary to drive the output stage, and an output stage formed by high-power transistors.

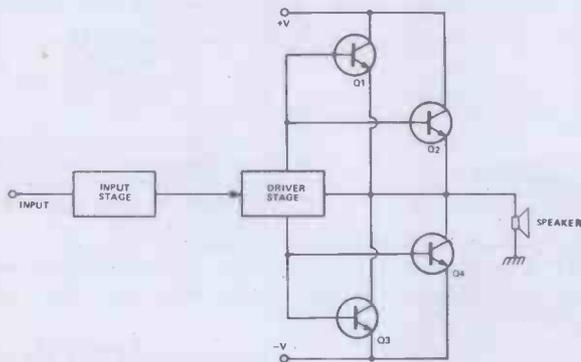Four output transistors (two pairs in parallel) are used in the 150 W amplifier option. Derating the amplifier to 60 W is a simple matter of removing one pair of transistors.



Integrated circuit IC1 and associated components form the input stage of the power amplifier. The IC presents a fairly high impedance to whatever signal source is used, thus acting as a buffer amplifier. This stage's gain, and in turn the whole amplifier's gain, is set by preset RV1.

One of the purposes of the driver stage is to produce DC standing voltages on the bases of the output stage transistors turning them partially on at all times. The standing voltages are set by the voltage across Q9 and can be varied by RV2.

The AC signal to be amplified is superimposed onto the standing voltages.

Final amplification in this stage is performed by Q6 to Q8, and Q10.

The power stage in the Power Amplifier is formed by transistors Q11 to Q14. By removing Q12 and Q14 the amplifier can only deliver about half of the maximum power.

From the output of the amplifier there is a feedback loop via R6 to the input of the operational amplifier IC1. This is a negative feedback loop and defines the overall gain of the complete amplifier.

Parts List

CAPACITORS

C1, 2 4700u (or greater), 63 V electrolytic

SEMICONDUCTOR

BR1 10 A, 400 V bridge rectifier

MISCELLANEOUS

SW1 double-pole, double-throw push-button switch
 T1 120/240 V primary, 50-0-50 + 15-0-15 V secondary transformer

Case to suit
 Neon with integral resistor
 3 x fuseholder + fuse (all 5 A)
 5-pin DIN socket
 4 x 4 mm socket (2 red, 2 black)
 2 x phono socket
 Mains cable + entry clamp
 2 x ready-built PCB
 12-way terminal block
 Mounting hardware
 Cable harness


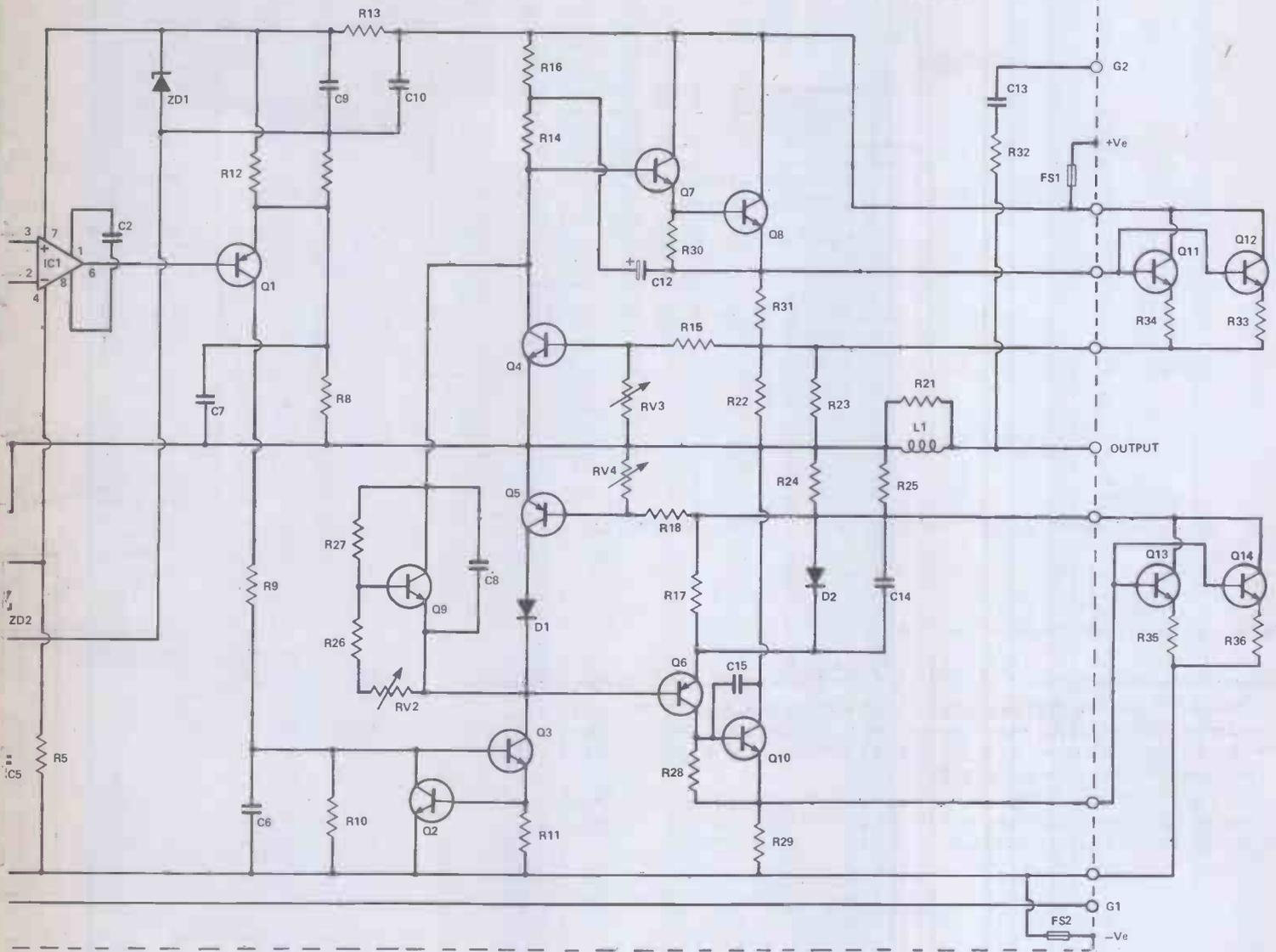


Figure 4 Circuit of the 150 W power amplifier, reproduced by courtesy of Capricorn Electronics. Two identical circuits are used on ready-built PCBs in the HE Power Amplifier

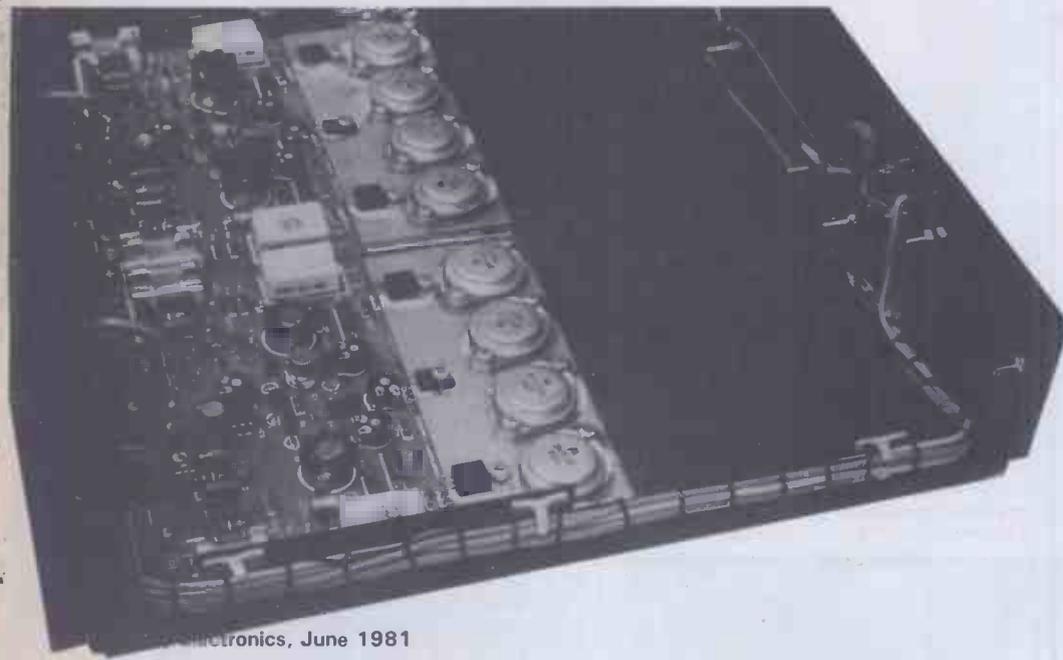

Buylines

A complete kit of parts for the HE Power Amplifier project is available from:
 Capricorn Electronics,
 281 Balmoral Drive,
 Hayes, Middlesex UB4 8HD
 (Tel: 01 573 1566)

for £155.

If you prefer to build the amplifier into a case of your own choice, Capricorn can supply all parts (excluding the case) for £125.

Please add £1.50 to your order to cover p&tp.

All components and parts are also obtainable individually from Capricorn.

HE

TTLs by TEXAS	74365	100p	4021	110p	931	160p	74S00	50p	74S114	120p
7400	11p	74368	100p	4022	9302	175p	74S04	60p	74S124	300p
7401	12p	74368	100p	4023	9308	316p	74S05	75p	74S133	75p
7402	12p	74390	200p	4025	9310	275p	74S08	75p	74S138	225p
7403	14p	74393	200p	4026	9312	160p	74S10	60p	74S139	250p
7404	14p	74490	225p	4027	9314	185p	74S30	60p	74S163	500p
7405	18p			4028	9316	225p	74S32	90p	74S174	250p
7406	30p			4029	9321	225p	74S37	90p	74S175	320p
7407	30p	74LS SERIES	4030	55p	9322	150p	74S64	90p	74S194	350p
7408	17p	74LS00	14p	4031	9334	360p	74S74	90p	74S241	450p
7409	19p	74LS02	18p	4034	9368	250p	74S85	304p	74S267	70p
7410	15p	74LS03	18p	4035	9370	300p	74S86	180p	74S373	500p
7411	24p	74LS04	18p	4036	9374	200p	74S112	120p	74S374	500p
7412	20p	74LS05	25p	4039						
7413	30p	74LS08	22p	4040						
7414	40p	74LS09	21p	4041						
7415	30p	74LS10	20p	4042						
7416	27p	74LS11	40p	4043						
7417	27p	74LS13	40p	4044						
7420	17p	74LS14	50p	4046						
7421	40p	74LS20	20p	4047						
7422	22p	74LS21	40p	4048						
7423	34p	74LS27	38p	4049						
7425	30p	74LS30	20p	4050						
7426	40p	74LS32	27p	4052						
7427	34p	74LS33	30p	4052						
7428	36p	74LS38	38p	4053						
7430	17p	74LS42	70p	4054						
7432	30p	74LS47	60p	4055						
7433	40p	74LS51	24p	4056						
7437	35p	74LS55	30p	4059						
7438	35p	74LS73	40p	4061						
7440	17p	74LS74	27p	4063						
7441	70p	74LS75	36p	4066						
7442A	60p	74LS76	45p	4067						
7443	112p	74LS83	70p	4068						
7444	112p	74LS85	80p	4070						
7445	100p	74LS86	80p	4071						
7446A	93p	74LS90	40p	4071						
7447A	75p	74LS92	70p	4072						
7448	80p	74LS93	50p	4073						
7450	17p	74LS96	110p	4075						
7451	17p	74LS107	45p	4076						
7453	17p	74LS109	80p	4081						
7454	17p	74LS112	40p	4082						
7460	17p	74LS113	90p	4086						
7470	36p	74LS114	45p	4089						
7472	30p	74LS122	80p	4093						
7473	34p	74LS123	60p	4094						
7474	30p	74LS125	60p	4095						
7475	38p	74LS125	50p	4096						
7476	32p	74LS126	60p	4097						
7480	50p	74LS132	60p	4098						
7481	100p	74LS133	30p	4099						
7482	84p	74LS136	55p	4100						
7483A	90p	74LS137	40p	4101						
7484	100p	74LS139	55p	4102						
7485	110p	74LS145	120p	4103						
7486	34p	74LS147	220p	4104						
7489	210p	74LS148	175p	4105						
7490A	30p	74LS151	50p	4107						
7491	80p	74LS153	60p	4107						
7492A	46p	74LS154	200p	4108						
7493A	36p	74LS155	80p	4109						
7494	84p	74LS156	90p	4110						
7495A	70p	74LS157	60p	4114						
7496	65p	74LS158	60p	4115						
7497	180p	74LS160	40p	4503						
74100	130p	74LS161	75p	4507						
74107	34p	74LS162	140p	4508						
74109	55p	74LS163	60p	4510						
74116	100p	74LS164	90p	4511						
74118	100p	74LS165	80p	4512						
74119	120p	74LS166	180p	4514						
74120	110p	74LS173	110p	4515						
74121	34p	74LS174	100p	4516						
74122	48p	74LS175	75p	4518						
74123	60p	74LS181	200p	4520						
74125	75p	74LS187	80p	4521						
74126	60p	74LS191	80p	4526						
74128	75p	74LS192	80p	4527						
74132	60p	74LS193	80p	4528						
74136	60p	74LS195	140p	4532						
74137	50p	74LS196	120p	4534						
74141	50p	74LS197	80p	4536						
74142	200p	74LS221	120p	4538						
74145	90p	74LS240	140p	4543						
74147	190p	74LS241	120p	4553						
74148	150p	74LS242	120p	4556						
74150	130p	74LS243	120p	4559						
74151A	70p	74LS244	100p	4562						
74153	70p	74LS245	150p	4572						
74154	120p	74LS247	140p	4583						
74155	90p	74LS251	140p	4584						
74156	90p	74LS253	90p	4585						
74157	70p	74LS257	90p	4724						
74158	190p	74LS258	160p	4097						
74160	100p	74LS259	160p	14411						
74161	100p	74LS266	100p	14412						
74162	100p	74LS273	130p	14433						
74163	100p	74LS279	90p	14500						
74164	120p	74LS283	90p	14599						
74165	130p	74LS291	160p	14599						
74166	200p	74LS323	400p							
74167	200p	74LS324	200p							
74170	240p	74LS348	200p							
74172	450p	74LS365	48p							
74173	120p	74LS368	100p							
74174	90p	74LS368	100p							
74175	85p	74LS373	150p							
74176	90p	74LS374	150p							
74177	90p	74LS375	120p							
74178	160p	74LS377	160p							
74180	93p	74LS378	160p							
74181	160p	74LS390	90p							
74182	90p	74LS393	90p							
74184A	150p	74LS399	200p							
74185	150p	74LS445	140p							
74186	500p	74LS670	400p							
74188	325p									
74190	120p									
74191	120p									
74192	100p	4000 SERIES								
74193	100p	4000	15p	75150						
74194	120p	4001	15p	75154						
74195	95p	4002	20p	75182						
74196	95p	4006	95p	75234						
74197	80p	4007	20p	75361						
74198	150p	4008	80p	75363						
74199	150p	4009	40p	75365						
74200	150p	4010	40p	75367						
74201	150p	4011	20p	75419/2						
74202	150p	4012	25p	8726						
74203	150p	4013	40p	8728						
74204	150p	4014	84p	8795						
74205	150p	4015	84p	8797						
74206	150p	4016	84p	8799						
74207	150p	4017	6							

How To Use An Oscilloscope

John Strong describes some simple tests and measurements that can be done with an inexpensive oscilloscope

AN OSCILLOSCOPE is probably the most informative instrument that anyone interested in electronics can possess. Used properly it can give a visual indication of what a circuit is doing, and often it can show what is going wrong quicker than any other instrument.

As with most things, the more money you spend, the better the equipment you can get. However, for the average hobbyist, equipment cost cannot be allowed to get out of proportion with the hobby itself. For this reason it is better to start with a simple and inexpensive 'scope rather than an elaborate and expensive one. As knowledge and finances improve, you can move on to more 'professional' equipment.

Getting Started

It is best to start with a single-channel, single-timebase oscilloscope. Such an instrument has the advantage of being fairly inexpensive (new ones can be bought for around £100) and it will have the minimum of controls.

Regular readers should have some idea of how a 'scope works (see *The Oscilloscope*, HE February 1981, pp18 to 22) but as a reminder, Fig. 1 shows a basic 'scope in block form.

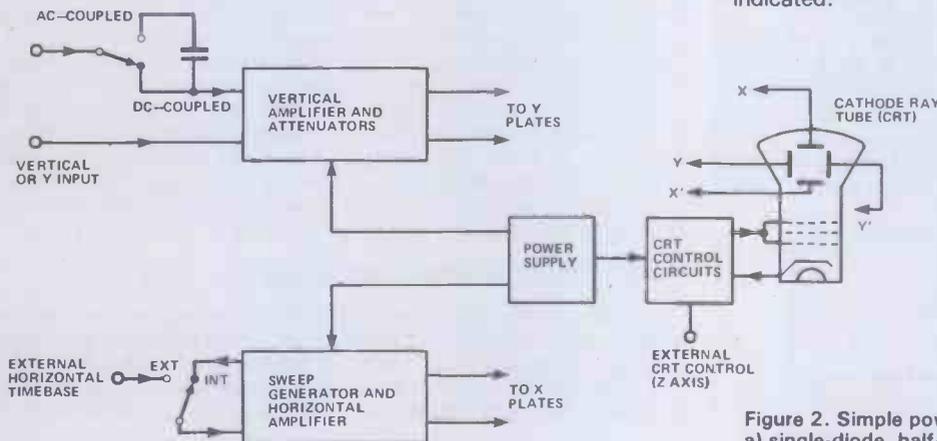


Figure 1. Principal stages of a simple oscilloscope

To make use of your 'scope it is best to follow the same procedure every time. Even those who make regular use of 'scopes can make mistakes by assuming that the controls are set correctly.

The following steps should serve as a guide.

1) Turn the horizontal gain fully up, and make sure that the sweep range control is *not* set to an external input position.

2) With no signal applied to the 'scope, adjust the position controls so that a continuous horizontal line is displayed across the centre of the screen. Check that the intensity and focus controls are correctly set at this stage. If the intensity control is set to high then there is a danger that the life of the CRT (cathode ray tube) will be shortened.

3) Check that the input voltage does not exceed the maximum value specified for the 'scope or of any probe used with the 'scope.

4) Check that the vertical gain (attenuator) control is set to, or above, the voltage of the signal to be measured. If in any doubt, start with maximum attenuation (highest voltage set-

ting, equivalent to least sensitivity) and work down the range until the correct setting is reached.

5) Check that the vertical input selector is set to the correct mode (that is, DC- or AC-coupled).

6) Check that the timebase and vertical amplifier controls are in their 'calibrated' positions (if these settings are provided).

Remember that the CRT is the most expensive single component in a 'scope so keep beam intensity down to the minimum required for a particular test. Take care to 'turn down the glare' on slow sweep speeds or if the 'scope is being used in the external horizontal timebase mode, as described later. When using the 'scope in this mode, avoid displaying a stationary bright 'dot' for any length of time. Once the phosphor coating has been burned from any part of the CRT screen the only remedy is to renew the CRT.

Practical Measurements

Rather than plunge into the depths of complicated circuits, it's best to start with something simple such as some rectifying and smoothing circuits. Figures 2a to 2d show various transformer, rectifier, capacitor and load resistor combinations, with test points indicated.


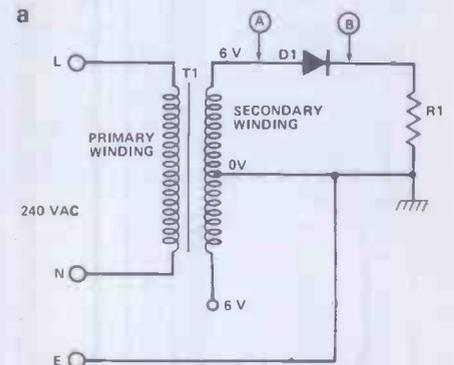


Figure 2. Simple power supplies. Figs. 2c and 2d are shown overleaf a) single-diode, half-wave rectified circuit, with resistive load.

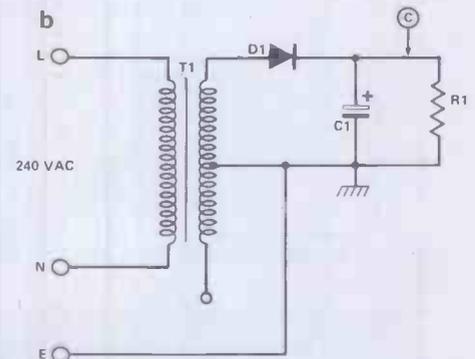

b) as circuit a, with smoothing capacitor.

Nothing is critical about the components used in these circuits; suggested values are given in Table 1. When wiring up the

transformer, take care to insulate the primary winding connections to avoid the chance of any electric shocks from exposed 'live' points. It is also advisable to 'breadboard' the components; that is, to mount the diodes, capacitor and resistor so that they can be easily rearranged for each configuration shown.

Power Supply Components

Transformer	Low-current type (say 50 mA) with 240 V primary and 6 V/6 V centre-tapped secondary
Diodes D1 and D2	1N4001 or similar
Capacitor C1	1000 μ , 10 V electrolytic
Resistor R1	1k Ω , 1/4 W

Table 1. Suggested components for circuits shown in Figs. 2a to 2e

It is also worth mentioning that a valuable aid when making oscilloscope measurements is a pair of probes. If you have an inexpensive 'scope then you won't need a deluxe probe set with built-in compensation components, variable gain and a kitchen sink built in. For most measurements, two lengths of ordinary insulated wire are sufficient. However, you will probably like to invest in a set of ordinary test leads, the black or earth lead having a crocodile clip or similar on one end, and the red or signal probe lead with a test prod or probe at its end.

Switch the 'scope to DC-coupled mode and adjust the trace to the centre of the screen before making measurements. Connect the clip of the earth probe to the point on each circuit marked with the earth symbol (ie, \perp)

With the circuits shown in Figs. 2a and 2b only one half of the secondary winding is used (centre tap and one 6 V tap). Both windings are used in the other two circuits, with the centre tap earthed.

When the probe is applied to point A in the circuit shown in Fig. 2a, trace A in Fig. 3 should be obtained. This represents an AC voltage with a frequency of 50 Hz (mains frequency).

The waveform of trace B at point B in Fig. 2a shows the effect of diode D1; that is, only the positive half-cycles are allowed to pass through to the load resistor R. This waveform represents DC in its crudest (unsmoothed) form. This kind of rectification is used, for example, in simple battery charger circuits.

Moving on to the circuit in Fig. 2b, capacitor C has been added in parallel across the resistor. The smoothing action at point C is indicated in trace C.


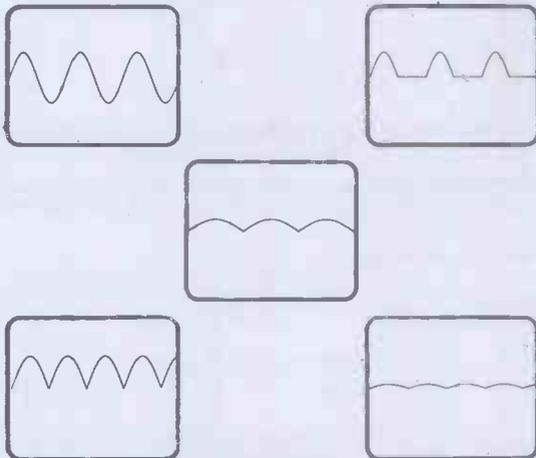



Figure 3. Traces that should be obtained from points A to E in circuits in Fig. 2

Figures 2c and d both show a full-wave rectified circuit. Here, two diodes are used to extract both half-cycles, giving the continuous line of 'humps' shown in trace D. With the capacitor in circuit as shown in Fig. 2d, a smoother trace is obtained: much smoother than obtained with the single-diode circuit.

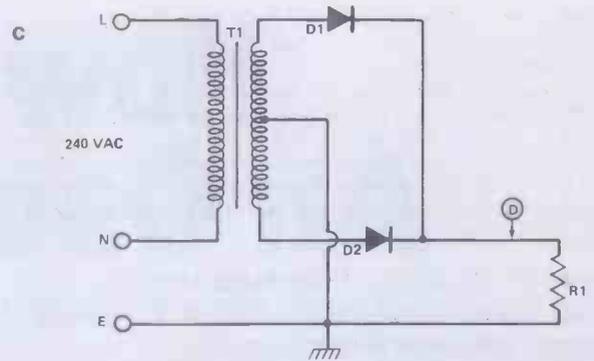You will notice that even the best smoothed circuit has some ripple (trace E). Pure DC from a battery would, by comparison, give



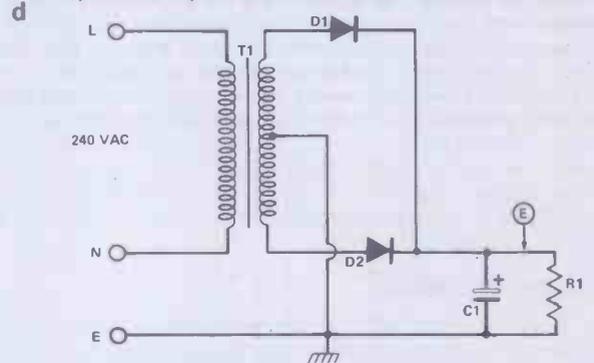c) two-diode, full-wave rectified circuit, with resistive load.



d) as circuit c, with smoothing capacitor.

a straight line on the 'scope. In the DC-coupled mode, the displayed line simply moves up the screen in proportion to the DC voltage. Thus the 'scope enables you to 'see' the presence of any ripple, which is the part of the AC voltage which, after rectification by the diodes, escapes smoothing by the capacitor. If the load were increased by reducing the value of R, then the ripple would be worse. If the ripple is observed with the 'scope in the AC-coupled mode, then the sensitivity of the vertical amplifier can be increased to allow the amount of ripple to be measured without the trace shifting out of view. This power supply ripple is an important consideration when designing some circuits and can, for example, produce an unwanted buzzing sound from an audio amplifier when it is run from a supply with a high ripple content.

Amplifier Measurements

To observe the response of an amplifier at various frequencies you will need, in addition to the 'scope, an audio-frequency generator similar to the one described in HE February 1981, pp 36 to 38.

The instruments are connected to the amplifier as shown in Fig. 4. Connect the generator, set to its lowest output voltage, to the

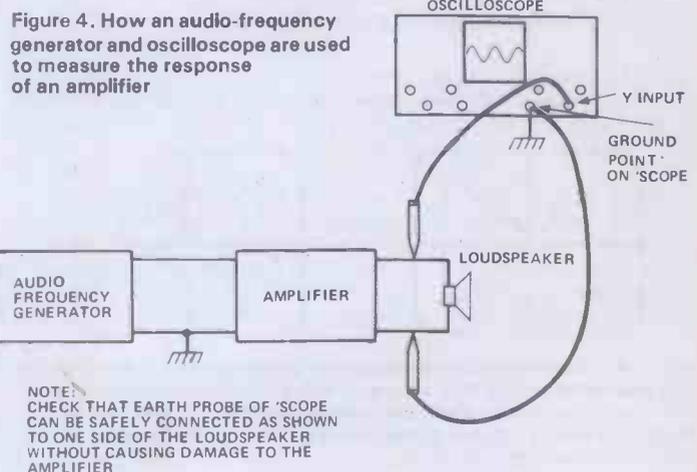


Figure 4. How an audio-frequency generator and oscilloscope are used to measure the response of an amplifier

input terminals of the amplifier, and connect the output of the amplifier to the vertical input terminals of the 'scope. Adjust the input attenuator and timebase controls to obtain a display. With the output signal from the generator held constant, try varying the generator frequency over the range of interest while adjusting the timebase controls to display only a few cycles of the waveform. The response of the amplifier at chosen frequencies can be observed, and the probe can be moved from the output of the amplifier back to the input to make comparisons of the shape and size of the signals at these points.

Simple Frequency Measurements

A display of what are called Lissajous figures can be useful for measuring the frequency of signals, particularly where no indication of time or frequency is given on the 'scope. Lissajous figures are obtained by feeding two different signals at the same time into the 'scope, one into the vertical input and the other into the horizontal input. Under these conditions, the timebase is switched off (that is, it is set to external horizontal timebase). The waveforms can be used to measure frequency if one of the signals has a known frequency while the other has an unknown frequency.

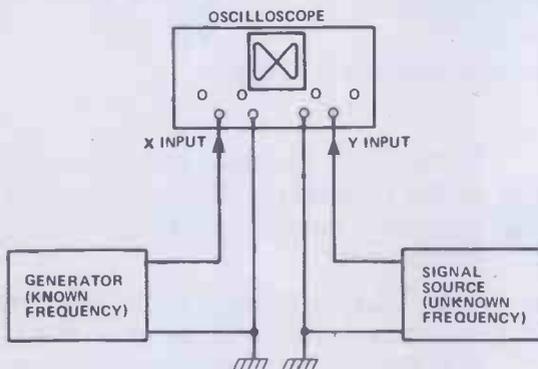


Figure 5. How a signal generator, providing a signal with known frequency and a signal source of unknown frequency, are connected to an oscilloscope to produce Lissajous figures

Connect the 'scope as shown in Fig. 5 and adjust the gain and position controls to centre the trace on the screen. Apply the unknown frequency to the vertical input and adjust the gain control to give a convenient sized display. Then adjust the generator frequency for a stationary display. The unknown frequency can then be calculated as follows:

$$\text{Unknown frequency} = \frac{\text{Number of crossing points over the horizontal scale line}}{\text{Number of crossing points over the vertical scale line}} \times \text{Known frequency from generator.}$$

For example, let's assume that the generator frequency is 1 kHz. If the trace in Fig. 6a is obtained, then the unknown frequency will be:

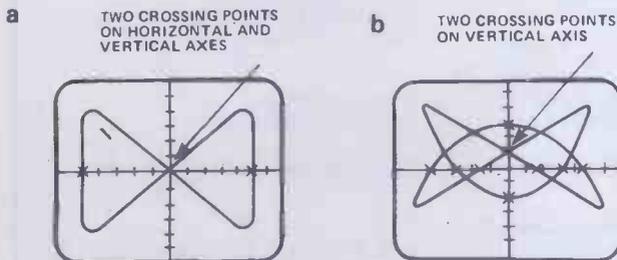


Figure 6. Lissajous figures produced by signals applied to the vertical and horizontal inputs of a 'scope: a) trace crosses horizontal axis at four points (twice at centre of screen) and vertical axis at two points (both at centre of screen), b) six crossing points on horizontal axis and four on vertical axis

$$\frac{4}{2} \times 1000 = 2 \text{ kHz.}$$

If the trace in Fig. 6b is obtained, then the unknown frequency will be:

$$\frac{6}{4} \times 1000 = 1.5 \text{ kHz.}$$

Reading The Scale

All the measurements described so far have been based on observation of the displayed image, and this method is satisfactory for most purposes. Often, the 'scope is used as an 'eye' to see what is going on in a circuit, and with experience much can be gained from correct interpretation of what is displayed. For example, if you are putting a pure sinewave signal into an amplifier and you get a flat-topped waveform from its output, then 'clipping' is taking place in the amplifier as the result of over-driving one of its stages. (See O Level Q & A, HE May '81, page 55 for a description of this effect.)

Sometimes, however, you may need to take measurements of units such as frequency and voltage *direct from the screen*. To do this, you will need to know what each little square on the screen means in terms of time and voltage. An example is given in Fig. 7.

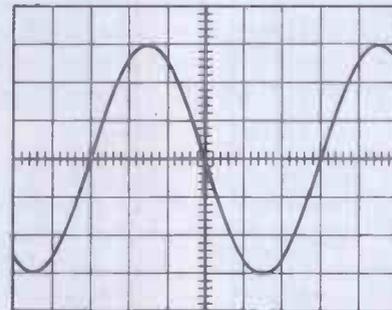


Figure 7. Example of sine wave signal displayed on typical oscilloscope screen. Timebase has been set to 5 ms/cm and vertical attenuator to 1 V/cm

A sine wave signal has been applied to the 'scope's vertical input, with the timebase set to 5 ms/cm and the vertical attenuator set to 1 V/cm. Therefore, the period of the waveform, measured over a full cycle, will be six divisions along the horizontal axis, equivalent to:

$$6 \times 5 \text{ ms} \\ \text{or } 6 \times 0.005 \text{ s} = 0.03 \text{ s.}$$

OK, you may say, what does 'period' mean? Let's convert it to frequency f (number of full cycles per second), by taking its reciprocal, where

$$f = \frac{1}{\text{Period in seconds.}}$$

Therefore,

$$f = \frac{1}{0.03} = 33 \text{ cycles/second or } 33 \text{ Hz.}$$

What about the voltage? Counting the vertical divisions between the peaks gives:

$$6 \times 1 \text{ V} = 6 \text{ V.}$$

Thus we have a 6 V peak-to-peak sine wave signal with a frequency of 33 Hz. All this calculation may seem a trifle complicated but you will soon get a 'feel' for it, and you can often do a rough calculation of frequency or voltage in your head.

Remember that the more practice you get in using a 'scope the more useful it will become.

HE

OSCILLOSCOPE EXCLUSIVE OFFER last chance for HE readers



THIS is the last chance to own the most valuable aid to the electronics hobbyist — AN OSCILLOSCOPE. With a screen size of 75 mm and a bandwidth of DC to 5 MHz the Kikusui 538A will enable you to 'see' how circuits are working *instantly*.

Apart from the CRT, semiconductors are used throughout the circuit: the 'scope is ready to operate in under 20 seconds. It comes complete with operating manual containing full details of operation, maintenance, calibration and circuits. (Probes not supplied.)


All-inclusive cost of the 538A, *delivered to your door*, is only **£95**. Each 'scope carries a full one-year guarantee.

Such was the response to our advertisements for the 538A in the February and April '81 issues that stocks quickly disappeared. Our supplier has allocated one last consignment to HE at the above price, so don't miss this chance to own a high-quality 'scope.

Pay by Barclaycard or cheque:



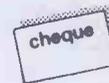Enter your Barclaycard number in the space provided on the coupon, add your signature, name and address — and we'll do the rest.



Enter your name, address and the amount in the coupon and send it with your cheque, made payable to Modmags Ltd.

Please also specify the number of 'scopes you require

SEND ALL ORDERS TO:

**HE Scope Offer,
Modmags Ltd.,
145 Charing Cross Road,
LONDON WC2H 0EE**

Please note that the offer applies to UK mainland only: allow 28 days for delivery

VISA

I WISH TO PAY
BY BARCLAYCARD
PLEASE CHARGE TO MY ACCOUNT
MY BARCLAYCARD NUMBER IS:

--	--	--	--	--	--	--	--	--	--

I enclose a cheque for
for Kikusui 538A Oscilloscope/s

SIGNATURE

NAME
(BLOCK CAPITALS)

ADDRESS

BRIEF SPECIFICATION

Vertical Deflection	
Voltage sensitivity	< 10 mV/division
Bandwidth	AC 2 Hz to 5 MHz DC DC to 5 MHz within -3dB
Input impedance	1M0 ± 5% within 35 pF
Ext. Horizontal Amplifier	
Voltage sensitivity	< 250 mV/division
Input impedance	1M0 10% within 35pF
CRT	75 mm (2.95") round screen, green phosphor
Power Requirements	
Voltage	100, 110, 117, 220, 230, or 240 VAC, 50 to 60 Hz
Wattage	about 10 VA
Dimensions	202 mm wide by 160 mm high by 305 mm deep. (7.9 by 6.3 by 12")

STEREO RECORD-PLAYER

£39.95 incl. V.A.T. + £2 p. & p.

- ★ Stereo Record-Player with Speakers
- ★ 5 + 5 Watts Music Power
- ★ 2-speed Semi-transcription Deck
- ★ Durable White Vinyl with Perspex Cover

7-day MONEY-BACK GUARANTEE

ADJUSTABLE POWER SUPPLY KIT

£25.00 all incl.

- ★ Complete Kit
- ★ Fully adjustable from 1.25V. to 30V.
- ★ 100% Output Shortcircuit Protection
- ★ Automatic Current Limiting
- ★ Thermal Shutdown
- ★ 1 Amp, 3 Amp or 5 Amp (please specify)

ELECTRONIC THERMOMETER

£18.50 all incl.

- ★ Complete Unit
- ★ Remote Temperature Sensor
- ★ 33 Metres Cable Fitted
- ★ Temperature Dial Reads 0.50° C.
- ★ PP3 Battery not supplied

INSTRUMENT CASES

Easy Slide-in Assembly with extra slots for PC boards, etc. Anodised aluminium with leather textured finish to top and base.

Size in inches	Width	Height	Depth	Price
	12 x 2½	x 5in.		£11.75
	12 x 3½	x 9in.		£14.25
	12 x 5½	x 9in.		£16.25

Other sizes available, please enquire.

CAR CLOCK MODULE, Green Display..... £9.95

CAR WASHER BOTTLE LEVEL SENSOR..... £4.95

ALARM CLOCK MODULE, 24-hour, Red LED..... £5.00

7-SEGMENT LED DISPLAYS:

0.3in. comm. anode..... £0.85

0.5in. c. an/c. cath., dual digit package..... £1.50

0.6in. c. an/c. cath..... £1.20

SOCKETS:

Low Profile, dual-in-line. Low price. Send s.a.e.

ALL PRICES EXCLUDE V.A.T. UNLESS STATED. POST AND PACKING ADD 40p

TO ALL ORDERS UNDER £10.

SEND S.A.E. FOR PRODUCT INFORMATION AND PRICES TO:

TWO + ONE

COMPONENTS LTD.

P.O. BOX 77, GERRARDS CROSS, BUCKS, SL9 0NT
TELEPHONE: 02-407 3568

TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

City & Guilds Certificates

Telecommunications Technicians
Radio Amateurs
Electrical Installation Work

Certificate Courses

Colour TV Servicing
Electronic Engineering and Maintenance
Computer Engineering and Programming
Radio, TV, Audio Engineering and Servicing
Electrical Engineering, Installation
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

To: International Correspondence
Schools

ICS Dept. 262H Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest _____

Name _____


Address _____

Tel. _____

Get a Grip on the state of your I.C.'s

The Logic Monitor 2 by GSC provides greater versatility and precision in testing all types of digital circuits.

It incorporates a fully isolated power supply which means that there is no loading of a circuit under test; avoids logic level shifts, false triggering and power supply loading. The self contained power supply in conjunction with I.C. comparators provides constant current drive to LEDs and ensures a uniformly bright display. A logic family selection switch enables the precise selection of logic thresholds and provides more accurate measurement of I.C.'s under test.

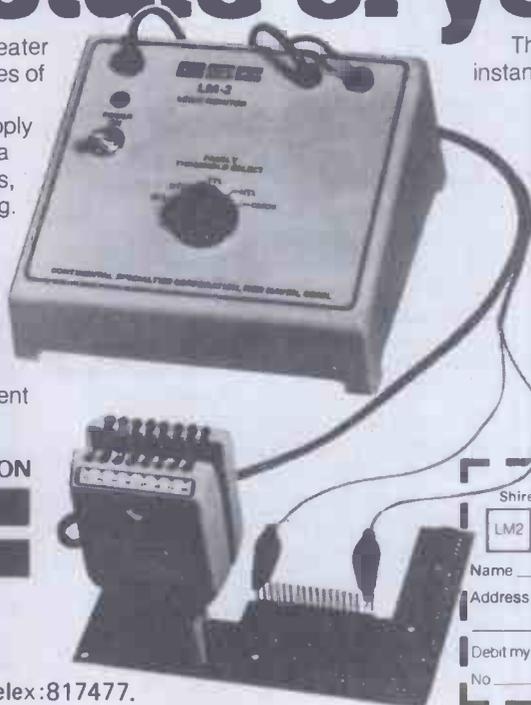

The LM2 just clips over the I.C. and displays instantly and automatically the logic state of the I.C. elements.

If you want to hear more of this gripping story then just send the coupon off or better still place an immediate order with your Access, American Express or Barclaycard.

£65.00 (excluding P&P and 15% VAT).

For immediate action

The G.S.C. 24-hour 5-day a week service.

Tel: (0799) 21682 and give us your Access, American Express, Barclaycard number and your order will be in the post immediately.

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 14DD
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.

Tel: Saffron Walden (0799) 21682 Telex: 817477.

G.S.C. (UK) Limited, Dept. 14DD, Unit 1,
Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

LM2 £76.47 (inc. P&P and 15% VAT) Qty Read For FREE catalogue tick box


Name _____

Address _____

_____ I enclose cheque/PO for £ _____

Debit my Barclaycard, Access, American Express

No _____ Exp. date _____

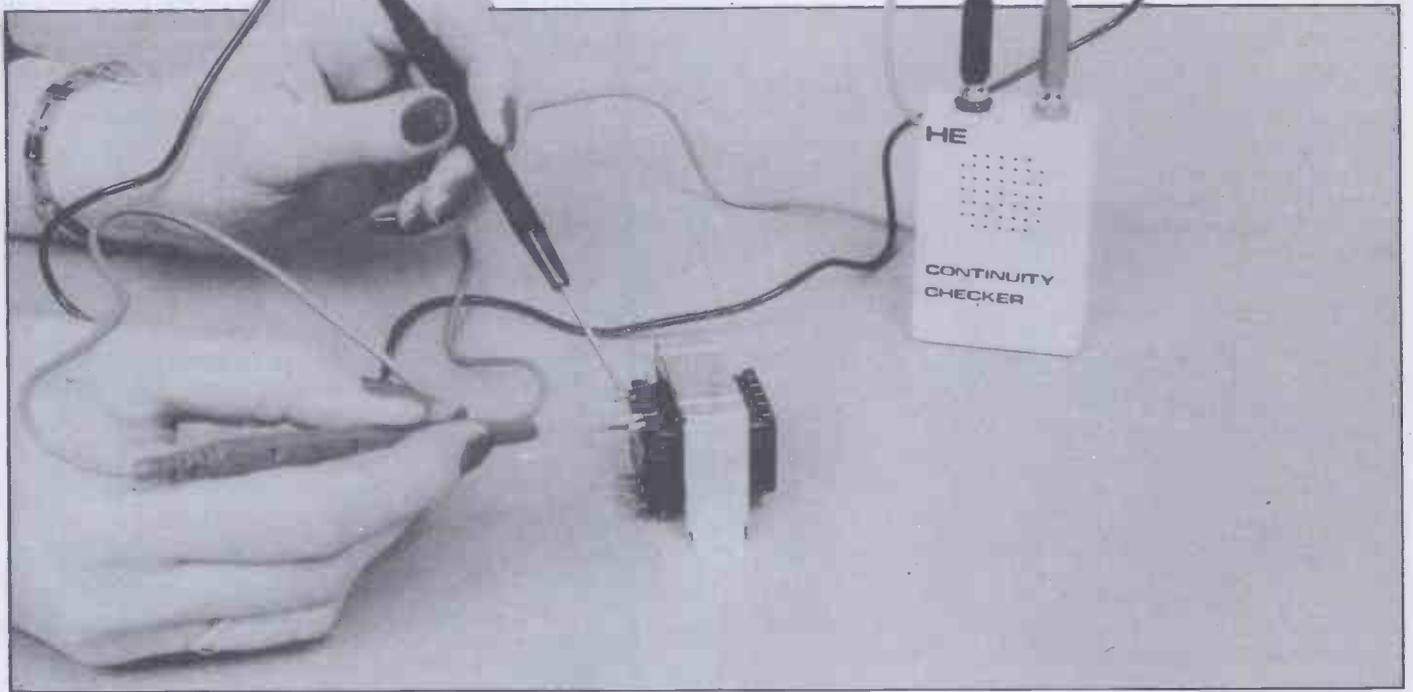

Continuity Checker

Here's an ideal project for you to build — it's cheap, simple-to-build and very useful

THERE ARE MANY times in the electronics hobbyist's life when a need arises for a quick and simple test to check fuses, coils, circuit boards etc, for short or open circuits. Normally this means searching for a multimeter (only to find that the internal battery is long dead) or diving into the junkbox to look for a battery, bulb and holder, and suitable wire (and then struggling to hold all connections in place between your knees while trying to position the probes onto whatever you're testing). The HE Continuity Checker is a project to end all of that. In fact, once you have built it you won't know how you ever managed without it. Housed in a small, hand-held case it combines usefulness with good looks. Total cost is around £5 so the project won't burn a large hole

in your pocket, and it is very easy to build.

The circuit is formed around a single IC, the LM3909, which directly drives a miniature loudspeaker with an audio frequency tone. The frequency of this tone varies with the resistance between the two probes — the lower the resistance, the higher the frequency. We reckon that, with a bit of practice, the 'experienced' ear should be able to distinguish easily between short circuits, open circuits or rough values of resistance from about 10 to 220R. The audio tone generated also means that you don't need to look away from the object under test (as would be necessary with a meter) while holding the probes in position on that object.

When the Continuity Checker is

connected to a loudspeaker, the speaker under test (if it works) will also emit the tone, so giving a good/bad speaker acoustic test.

No on/off switch is necessary because when the probes are disconnected battery drain is *nil* and battery life of the project (using an RM401 battery) should be a matter of years with average use. These batteries are specified as having a capacity of 800 mA/hours and a battery shelf-life, to 75% of full capacity, of 3 years.

Construction

Start construction by making the four breaks in track, on the underside of the Veroboard beneath IC1, as indicated in Fig. 2.

Next, insert and solder the links, followed by an 8-pin IC holder for IC1. Now insert and solder R1 and C1 making sure that you polarise C1 correctly, and then push IC1 into its socket.

Mark and drill the case for the two 4 mm probe lead sockets, also drill a number of holes in the front panel to act as a loudspeaker grille. Glue the speaker into position, being careful not to get glue on its cone, and fasten the two probe sockets into their positions.

Finally, wire together the speaker, battery holder, Veroboard and 4 mm sockets as shown in Fig. 2 using short lengths of connecting lead, and then fasten the board and the battery holder

into the case using double-sided adhesive pads. Insert the battery, seemingly the wrong way round (ie +ve to the spring) into its holder. The construction of these batteries is such that their *outer* case is positive, unlike most batteries of similar size, and consequently they should be inserted into the holder the opposite way round.

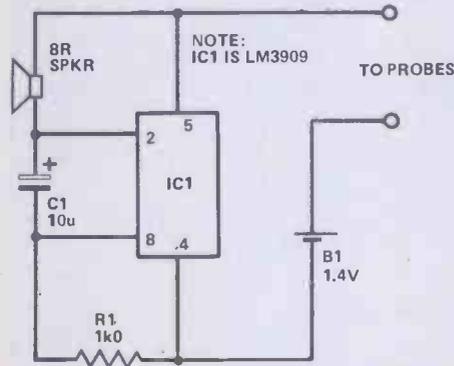


Figure 1. Circuit of the Continuity Checker


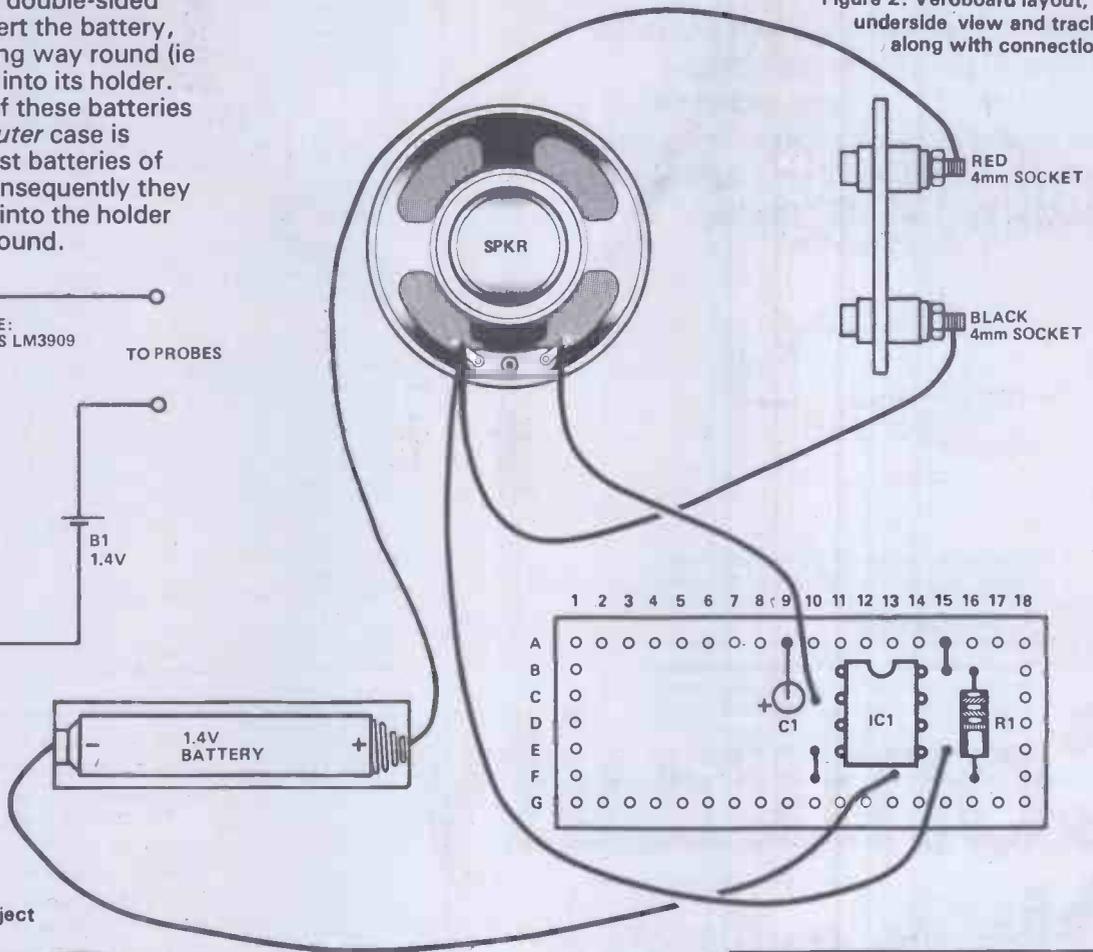


Figure 2. Veroboard layout, showing underside view and track breaks, along with connection details

Internal view of the project

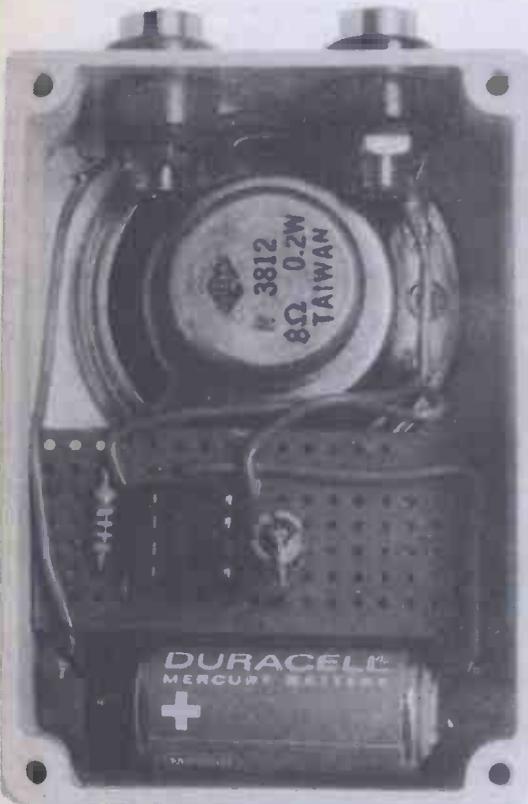


Parts List

- RESISTOR** (¼W, 5%)
R1 1kΩ
- CAPACITOR**
C1 10µ, 10 V electrolytic
- SEMICONDUCTOR**
IC1 LM3909 LED flasher/oscillator
- MISCELLANEOUS**
Case to suit (Vero type 202-21025K)
RM401 battery + holder
8-pin DIL IC socket
2 x 4 mm probe sockets (red and black)
2 x probes (red and black)
8R speaker
Veroboard, 7 strips x 18 holes, 0.1" matrix

Buylines

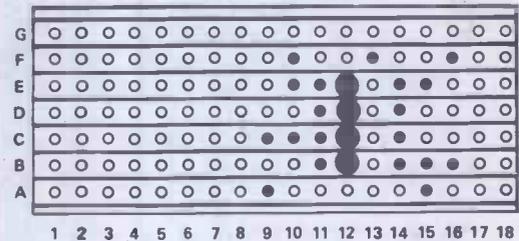
A complete kit of parts for the Continuity Checker is available from Magenta Electronics for £4.86 including VAT, probes and battery.
RM401 batteries are available separately for 64p each, the holders cost 22p each and LM3909s cost 79p each, all from Magenta.
Please add 40p p&p, whatever the total order price.



Continuity Checker

How It Works

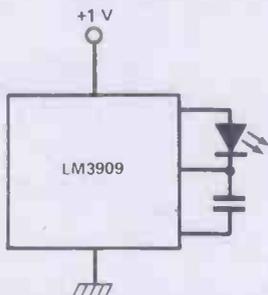Integrated circuit IC1 is a purpose-designed oscillator requiring a minimum of only one external component, a capacitor, to operate. Its main function is as a low-voltage (as low as 1 V) LED flasher.



The output stage of the circuit is quite powerful and a small 8R loudspeaker can be driven directly, replacing the LED in the above circuit.

Oscillator frequency is dependent on supply voltage, so if the probe leads are made part of the supply line then whatever resistance is in between the probes will determine the voltage across the IC and hence the oscillator frequency.

HE

Beasties

.... AND THEN THERE WAS THE IRISH RADIO ASTRONOMER WHO TRIED TO CASH A CHEQUE AT JODRELL BANK...



Beasties

DON'T YOU THINK THAT 250 VOLTS MIGHT BE A BIT RICH FOR THESE BABY COMPUTERS??

♪ THERE'S AN OLD MILL BY THE ♪
ZZTREAM, NELLIE DEAN...



THE PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project - you will need to order the instruction reprint as an extra 45p each.

Reprints available separately 45p each + p&p 40p
LATEST KITS: S.A.E. OR PHONE FOR PRICES

AUDIO MILLVOLT METER, May '81	£16.98
VOICE OPERATED SWITCH, May '81	£9.43
Microphone extra	£2.29
SUPER SIRON, Apr '81	£17.75
DOORBELL MONITOR, Apr '81	£2.99
GUITAR TREMOLO, Apr '81	£11.33
WINDSCREEN WASHER ALARM, Apr '81	£5.26
RUSSIAN ROULETTE GAME, Apr '81	£8.31 less case
PUBLIC ADDRESS AMPLIFIER, Mar '81	£16.56
Extras - horn speakers	£6.83 each
PA mic	£4.40
FUZZBOX, Mar '81	£9.41
WINDSCREEN WIPER CONTROLLER, Mar '81	£6.98
STEAM LOCO WHISTLE, Mar '81	£11.15
PHOTOGRAPHIC TIMER, Mar '81	£2.99
HEARTBEAT MONITOR, Feb '81	£21.28
HIGH IMPEDANCE VOLTMETER, Feb '81	£8.98
AUDIO SIGNAL GENERATOR, Feb '81	£17.21
BACKGROUND NOISE SIMULATOR, Feb '81	£6.43
TWO-TONE TRAIN HORN, Feb '81	£4.77 less case
MEDIUM WAVE RADIO, Feb '81	£6.98
BENCH AMP, Jan '81	£9.19
NICARD CHARGER, Jan '81	£6.98
CHUFFER, Jan '81, less case	£6.44
CAR REV COUNTER, Jan 81, less case	£21.20
Case extra	£5.98
DIGITAL SPEEDO, Dec. '80	£35.89
MODEL TRAIN CONTROLLER, Dec. '80	£16.86
BATTERY CHARGE MONITOR, Dec. '80	£4.91
JACK LEAD TESTER, Dec. '80	£1.99
STEREO POWER METER, Dec. '80	£18.98
PARTY GRENADE, Nov '80	£7.98
TRANSISTOR TESTER, Nov '80	£5.57 inc. test leads
DOUBLE DICE, Nov '80	£13.80
GUITAR PRE-AMP, Nov 80	£5.65 case (diecast) extra £2.99
BATTERY ELIMINATOR, Nov '80	£14.88

3 Channel Sound to Light
500 watts per channel. Independent controls for bass, middle and treble. Full wave output via PL552 socket and PL551 plug. Complete with p.c.b. and case.
Instructions included £18.98.

Chaser
A psychedelic light show. 3 modes of flashing - two chase patterns and a strobe effect. 3 channel - total output power 750W per channel. Supplied with plug and socket for output to the bulbs.
Instructions included £19.98.

Sound Pressure Level Meter
Featured in Feb. 81 E.T.I. Uses a precision ceramic microphone. Portable. Moving coil panel meter. 30-120dB sound level. Internal network gives A weighted (loudness) response or flat response for absolute measurements. Suitable for domestic, schools, industrial or disco use.
Instructions Included £45.75.

Printed Circuit Boards - Hobby Electronics
Fully etched, drilled and roller tinned p.c.b.s available for most Hobby Electronics projects - send s.a.e. for p.c.b. price list.

Public Address Amplifier 18 watts 12 volt

As featured in H.E. March 81. Make yourself heard with this high powered amplifier. Two inputs - one for microphone and an auxiliary line - each with its own level control - allows mixing of music with announcements, etc. Compact unit built in a black anodised aluminium 'sink box'. Uses a 12 volt d.c. supply - so can be powered from a car battery or a mains powered 12V supply. Uses a special audio i.c. to deliver 18 watts into 4 ohms (2x8 ohms in parallel). P.A. Amplifier kit £16.58. Extras: P.A. Mic £4.40; 8 ohm horn speakers £6.83 each.

Guitar Fuzz Box. H.E. March 81
Produce delightful distortion from your electric guitar in a novel way. A simple to build project with foot pedal control. This unit produces a very smooth sound. Circuit is housed in a 'brand new' style of box - complete with a pedal to operate an internal switch. Features more controlled distortion and less background noise than most other designs. Guitar Fuzz Box, Mar 81 £9.42.

1981 ELECTRONICS CATALOGUE

**KITS
ICs
TRANSISTORS
CAPACITORS**

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery. Send 70p in stamps or add 70p to your order.

**TOOLS
RESISTORS
HARDWARE
CASES**

ADVENTURES WITH MICROELECTRONICS

Same style as above book: 11 projects based on integrated circuits - includes: dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a bim-board, 1 plug-in breadboard and the components for the projects.
Adventures with Microelectronics £2.35. Component pack £26.95 less battery.

ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages, ideal for beginners. No soldering. Uses an 'S-Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec and the components for the projects.
Adventures With Electronics £1.90. Component Pack £16.72 less battery.

MAGENTA ELECTRONICS LTD.

NOBELL DOORBELL, Oct. '80.....	£10.98
INTRUDER ALARM, Oct. '80.....	£17.83
FREEZER ALARM, Oct. '80 with probe.....	£9.42
TUG O' WAR, Oct. '80.....	£15.98
KITCHEN TIMER, Oct. '80 (2% resistors).....	£7.34
MICROMIX, Sept. '80.....	£7.82
AUTO PROBE, Sept. '80.....	£3.67 less case
TOUCH SWITCH, Sept. '80.....	£2.34 less case & contacts
GUITAR PHASER, Sept. '80.....	£13.84
BENCH PSU, Sept. '80.....	£28.50
EQUITONE CAR EQUALISER, Aug. '80.....	£14.98
OP AMP CHECKER, Aug. '80.....	£4.55
MOVEMENT ALARM, Aug. '80.....	£5.68
RADIO TIMER, Aug. '80.....	£6.98
PASS THE LOOP GAME, Aug. '80.....	£13.98
SOUND OPERATED FLASH TRIGGER, July '80, no skt.....	£4.59
18W+18W CAR STEREO BOOSTER, July '80.....	£29.98 (stereo)
FOG HORN, June '80.....	£5.65
SPEED CONTROLLER FOR R/C, April '80.....	£14.92 less case
DIGITAL FREQUENCY METER, April '80.....	£35.78
HOBBYCOM: TWO WIRE INTERCOM, April '80.....	£33.95 (Master)
Sub Station.....	£3.38 each
ELECTRONIC IGNITION (CD), April '80.....	£20.87
WIN INDICATOR, Feb. '80 (with switches).....	£13.92
DIGI-DICE, Jan. '80.....	£9.98
BARGRAPH CAR VOLTMETER, Dec. '79.....	£7.33 less case
RING MODULATOR, Dec. '79.....	£12.95
GUITAR TUNER, Nov. '79.....	£10.98
HOBBYTUNE, Oct. '79.....	£26.98
ANALOGUE FREQUENCY METER, Oct. '79.....	£15.52
MULTI-OPTION SIREN, Oct. '79.....	£15.98
ULTRASONIC SWITCH, Sept. '79.....	£28.85 less 3 pin mains socket
HOME SECURITY UNIT, Aug. '79.....	£28.56 less siren
SIREN.....	£5.09 less case
LED TACHOMETER, Aug. '79.....	£17.98
INJECTOR TRACER, Aug. '79.....	£4.34
CONSTANT VOLUME AMPLIFIER, Aug. '79.....	£15.60
LINEAR SCALE OHMMETER, July '79.....	£15.98
GSR MONITOR, June '79.....	£9.63
ENVELOPE GENERATOR, June '79.....	£14.98
WHITE NOISE EFFECTS UNIT, May '79.....	£17.74
TRANSISTOR GAIN TESTER, April '79.....	£9.98
PHOTOGRAPHIC TIMER, Mar. '79.....	£16.45
CAR ALARM, Feb. '79.....	£10.98
SCRATCH/RUMBLE FILTER, Feb. '79.....	£25.48 Mono £29.98 Stereo
PUSH BUTTON DICE, Dec. '78.....	£6.98

INTO DIGITAL ELECTRONICS

Current H.E. series Part 1 in Sept. '80. Covers digital electronics from the basics. Circuits are built on a plug-in Eurobreadboard. Reprints of back issues available 45p each. Eurobreadboard and components for series £18.95 less battery. Components only £12.75.

INTO ELECTRONICS CONSTRUCTION

H.E. 6-part Series: Feb. '80 to July '80. COVERS THE BASICS OF ELECTRONICS - LOTS OF PRACTICAL WORK. Circuits are built on a plug-in Eurobreadboard. REPRINTS AVAILABLE, 45p each part. Eurobreadboard and Components for Series £15.63. Components only £9.43.

H.E. LADDER OF LIGHT, JAN. '81

Novel 'sound to light' project. Creates a pulsating, rising and falling light show. Will drive up to 10 100W light bulbs either in bar mode - In a line increasing from one end; or in dot mode - one bulb at a time. Filter allows selection of bass, treble or middle frequencies. Extra with our kit only - additional circuit and components for strobe and chase features. Ladder of Light Jan '81 £29.98. Reprint extra 45p.

MEMORY BANK SYNTHESIZER

Miniature synthesiser featuring vibrato, envelope tempo, volume and pitch controls. Uses 24 push button switches in a keyboard style layout. Based on a custom designed I.C. The accessible memory stores a 32 beat length sequence of notes and spaces. Can be played 'live'. Fitted with an internal speaker. Jack socket allows the use of an external amplifier if wished.

Memory Bank Synthesiser £33.85

3 BAND S.W. RADIO

Simple T.R.F. Design. Covering most Amateur Bands and Short Wave Broadcast Bands. Five controls. Bandset, Bandspread Bands. Wavechange and Attenuator. Coil reaction is by Wavechange Switch. Use with Headphones or a Crystal earpiece. Kit contains all the components required including the P.C. Board and Case. Instructions are included with this kit. KIT £18.97. Headphone extra £2.98.

MAGENTA ELECTRONICS LTD.

HH9, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS, DE14 2ST. 0283-65435. 9-4 MON.-FRI. MAIL ORDER ONLY

ADD 40p P&P TO ALL ORDERS

All prices include 15% VAT. (except where stated)



Irish Republic & B.F.P.O. Europe deduct 10% from prices shown. Payment must be in sterling. Access and Barclaycard (Visa) orders accepted by phone or post.

The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

The Instructor is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the Instructor and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk. 2. Circuits are built on a plug-in Eurobreadboard. Kit is available with or without the breadboard. INSTRUCTOR COMPONENT PACK: Including Eurobreadboard £27.85, or less Eurobreadboard £21.85. INSTRUCTOR COURSE NOTES AND OPERATING INSTRUCTIONS £2.96 extra.

C106D..... 56p	2N5457..... 58p	BFY51..... 24p	LINEAR ICs	LM3900N..... 85p
TIC46..... 49p	2N5484..... 63p	BFY52..... 23p	555..... 32p	LM3909N..... 79p
OA47..... 11p	40673..... 98p	BFX88..... 32p	556..... 79p	LM3911N..... £1.55
OA90..... 9p	AC128..... 29p	BRY39..... 48p	741..... 28p	LM3914N..... £2.89
OA202..... 16p	AC141..... 38p	MPSA65..... 39p	748..... 55p	LM3915N..... £2.98
W0.05..... 33p	AC176..... 37p	RPY58A.....	CA3080..... £1.21	MC3340..... £1.15
W06..... 47p	BC182..... 11p	TIP31A..... 52p	CA3085A..... £1.32	TBA820..... £1.05
Z5J..... £2.92	BC182L..... 11p	TIP32A..... 83p	CA3130T..... £1.12	TL064..... £2.59
1N4001..... 5 1/2p	BC183..... 11p	TIP33A..... 94p	CA3140E..... 57p	UZT37B..... £1.69
1N4005..... 6p	BC184..... 11p	TIP121..... £1.12	HA1388..... £2.85	ULN2838B.....
1N4148..... 5p	BC184L..... 11p	TIP2955..... 69p	ICL7611..... £1.04	ICL8038CC.....
1N5404..... 18p	BC212..... 11p	TIP3055..... 69p	ICL8038CC.....	ZN1034E..... £2.19
1N5408..... 19p	BC212L..... 11p	TIS43..... 38p	ICM7555..... £1.19	ZN414..... £1.09
BF244B..... 45p	BC213..... 11p	TPSA13..... 35p	LF351..... 58p	ZN419CE..... £2.59
MPF102..... 69p	BC214..... 11p	2N3053..... 25p	LF353..... 96p	ZN424E..... £2.14
TIS88A..... 57p	BC214L..... 11p	2N3055..... 59p	LF356..... 99p	ZN425E..... £5.98
VN67AF.....	BD131..... 48p	2N3702..... 11p	LM301AN..... 79p	C.MOS
..... £1.21	2N3819..... 28p	2N3704..... 11p	LM309K..... £2.99	4001..... 27p
2N3820..... 78p	BFY50..... 25p		LM317K..... £3.56	4011..... 28p
			LM317T..... £2.55	4013..... 55p

1/4W, carbon film resistors, E12 series, 1R-10M, 1/2p each. Min. horiz. presets 100R-4M7, 12p each. Midget pots, Linear, 470R-4M7, 37p each. Log 4k7-2M3, 38p each. Switched pots, 4k7-1M, Lin. 75p. Log. 76p.

Polyester (C280) capacitors 250V 10nF; 15nF; 22nF; 33nF; 47nF 7p ea. 68nF; 100nF 8p. 150nF; 220nF 12p. 330nF 15p. 470nF 20p. 680nF 28p. 1uF 33p. 1.5uF 49p. 2.2uF 65p.

Sub miniature plate ceramics 63V. Values in pF: 2.2; 3.3; 4.7; 5.6; 6.8; 8.2; 10; 15; 22; 33; 47 & 56pF 7p each. 68pF; 100pF 7p each. 150; 220; 330pF 11p. 390pF; 470pF; 1000pF 5p. 2200pF 6p. 3300pF; 4700pF 7p. 10nF 13p. 100nF 22p. 47nF 14p.

Electrolytic capacitors, AXIAL leads:- 1uF/16V 11p; 1uF/63V, 1uF/100V 12p; 2.2uF/63V, 3.3uF/63V, 4.7uF/63V 12p; 10uF/16V 11p; 10uF/63V 12p; 22uF/25V 12p; 22uF/63V 15p; 33uF/40V, 47uF/25V 12p; 47uF/25V 15p; 47uF/40V 15p; 47uF/63V 18p; 100uF/16V 12p; 100uF/25V 15p; 100uF/40V 18p; 100uF/63V 29p; 220uF/10V 15p; 220uF/25V 19p; 470uF/16V 29p; 470uF/25V 36p; 470uF/40V 55p; 680uF/16V 32p; 1000uF/10V 30p; 1000uF/16V 33p; 1000uF/25V 46p; 1000uF/40V 58p; 1000uF/63V 79p; 2200uF/10V 39p; 2200uF/25V 64p; 2200uF/63V £1.10. RADIAL leads:- 0.47uF/25V 8 1/2p; 10uF/16V, 22uF/16V, 47uF/16V, 100uF/16V, 100uF/25V 12 1/2p; 220uF/63V 39 1/2p; 1000uF/16V 35 1/2p; 220uF/16V 64 1/2p.

Switches
Min. toggle: spst 59p; spdt 69p; dpdt 79p. Min. push on 18p; push off 22p. Footswitch all action: spco £1.39; dpco £1.88. Rotary switches: 1p 12 way, 2p 6w, 3p 4w, 4p 3w 69p each. 12V 185R dpco relay £2.98.

Soldering
Jewell X25 soldering Iron, 25W £4.98. Soldering iron stand £1.99. spare bits (for X25) small, std, large 64p each. How to solder sheet 12p. Solder bobbin 30p. Desolder pump £5.98. Desolder braid 69p. Solder, handy size 98p. Heat sink tweezers 15p.

Opto
BXP25..... £2.24
2N5777..... 60p
ORP12..... 99p
TIL32..... 81p
TIL78..... 74p

L.e.d.s with clips
3mm: Red 15p; Green 18p; Yellow 20p. 5mm; Red 16p; Green 19p; Yellow 21p. Flashing L.e.d. 78p. Rectangular red 58p. Mains panel neon 32p.

Zener diodes 400mW, BZY88. Range 2V7 to 33V 12p each.

L.c. sockets
8 pin..... 16p 18 pin..... 22p
14 pin..... 17p 24 pin..... 48p
16 pin..... 18p 28 pin..... 45p

Jackson
300pF dilecon £2.36. 500pF dilecon £2.92. C804 var. capac. 10pF £2.28; 25pF £2.46; 50pF £2.48; 100pF £2.83; 150pF £3.48. '01' 365pF £3.48; '02' 365pF £4.49; '02' 208+176pF £3.98. 4511 DAF 6.1 drive £1.74.

Low cost long nose pliers £1.68. Wire strippers and cutters £2.48. P.c.b. assembly jig £1.98. P.c.b. etching kit £4.98. Plastic tweezers 69p. Eurobreadboard £6.20. Bimboard 1 £6.48. S. Dec £3.98.

Speakers miniature, 8 ohm 87p; 64-75 ohm 89p. Crystal earpiece 65p. Magnetic earpiece 15p. Mono headphones £2.98. Stereo headphones £4.35. Telephone pick-up coil 72p. FM aerial 49p. Min. buzzers 6V 50p; 9V £1.10; 12V 65p.

PP3 clips 10p; PP9 clips 11p. Panel meters 60x45mm £4.99 each. 50uA, 100uA, 1uA, 1A, 25V.

Veroboard 0.1" copper
10 strips, 24 holes £1.20 per 5. 24S 37H 78p. 24S 50H 89p. 36S 37H 89p. 36S 50H 99p. Terminal pins 48p/100. Pin insertion tool £1.69. Spot face cutter £1.23.

Multimeter type 1, 1000opv with probes, 2"x3 1/2"x1 1/2".....	£6.66
Multimeter type 2, 20,000opv inc. transistor tester.....	£14.75
Croc clip test lead set, 10 leads with 20 clips.....	95p
Connecting wire pack, 5x9yd coils.....	69p
Resistor colour code calculator.....	21p
Towers International Transistor Selector.....	£10.35
AM-FM aircraft band portable radio.....	£8.98
2 station desk intercom.....	£7.48 3 station.....
Plug-in power supply, 4.5V, 6V, 9V, 300mW.....	£3.89
Dimmer switch.....	£3.98
PVC tape - 3 reels.....	34p
Dentists inspection mirror.....	£2.85
Jewellers eyeglass.....	£1.50
Hand magnifier, 3".....	£2.99
Illuminated magnifier, 1 1/2".....	£1.14 3"..... £3.19

Radio

Even in this age of microelectronics, radio still has its appeal. Ian Sinclair traces its development and describes wave propagation, reception and simple receivers

"THERE WAS A TIME" quavered the old man, his stick trembling slightly, "when every recruit to the ranks of electronics as a hobby would have started by making his own radio receiver."

It would have been, of course, a simple receiver, not the sort of miracle-box which automatically tunes Radio Tokyo for you at 7.25 each morning, but a receiver which at least you had built with your own fair hands. In those days, too, we could take it for granted that everyone who started that way knew a fair bit about radio, because there wasn't much else to electronics in the early days.

Things have changed a lot. Radio is just one tiny part of the whole electronics scene, although one which looks as if it might make quite a comeback as an amateur activity when legal CB comes into operation later this year. Many people nowadays join this hobby of ours without ever coming into contact with radio, and that's a pity. Perhaps this article will help put some of that right.

Early Discoveries

The best place to start is always the beginning, and the beginning was, as so often happens, a bit of a false start. In 1864, James Clark Maxwell, a physicist of considerable distinction, put forward the idea, backed by theory, that light was an electrical wave. (See Famous Names, pp 63 to 64 in last month's HE.) He also said that it should be possible to generate similar but invisible electrical waves which would travel through space with the speed of light and which, unlike the telegraph or telephone, would need no wires to connect the transmitter with the receiver. His ideas were met with polite disbelief, his calculations were thought to be unrealistic, and because no-one had succeeded in producing any detectable waves by electrical methods, Maxwell's Electromagnetic Theory, as it was called, remained just a theory. Like all true research, however, it was not wasted. In 1888, some nine years after Maxwell had died, a researcher called Heinrich Hertz succeeded in producing the waves that Maxwell had predicted — and that's why we use the word hertz today for the unit of frequency. A brief look at Hertz's achievements is given in this month's Famous Names, on page 56.

Why had it been so difficult to produce radio waves? To answer that, we must know something of what was needed (as Maxwell knew) and also why it could not be achieved easily. What was needed was an alternating voltage which alternated at a high frequency. Alternating voltages had, of course, been around for several years (even in the 1860s), because an alternating voltage is

what you get when you spin a coil of wire between the poles of a magnet. The voltage between the ends of the wire is alternately positive, zero, negative, zero and positive again in each revolution of the coil. The frequency of the alternating voltage is the number of times per second that it goes through this complete cycle of changes. When the alternating voltage is generated by a coil rotating between the poles of a magnet, the frequency of alternation is easily found — it's the same as the rate of turning in revolutions per second. In the 1860s, it was reasonably straightforward to build generators which could rotate at around 3,000 revolutions per minute. That's 50 revolutions per second, giving a frequency of 50 Hz, the frequency we still use for mains supplies today.

Now it wasn't at all obvious from Maxwell's equations that the frequency of an alternating voltage should be an important factor in deciding whether or not it could be used for radio. Nevertheless, the information was there and several researchers found it and drew the correct conclusions — that the amount of radio wave which could be radiated from a piece of wire would be immensely greater if the frequency of the AC voltage on the wire was higher, much higher than 50 Hz. As it happens, the frequency of a radio wave is very closely related to another quantity called wavelength. The wavelength is, as the name suggests, the distance between two neighbouring wave peaks (Fig. 1), when the wave is travelling through space. Wavelength multiplied by frequency of a wave gives wave speed, and for all electrical waves — and that includes light — the speed is constant at around 300 million metres per second. By comparison, Concorde at full speed manages to cover just 630 metres per second. Because the speed of all types of radio waves is constant and of known value (in space), we can find the wavelength for any frequency by dividing the speed by the frequency.

For a 50 Hz wave, for example, the wavelength is

$$\frac{300 \text{ million}}{50}$$

which is a wavelength of 60 million metres, a distance equal to 15 times around the earth.

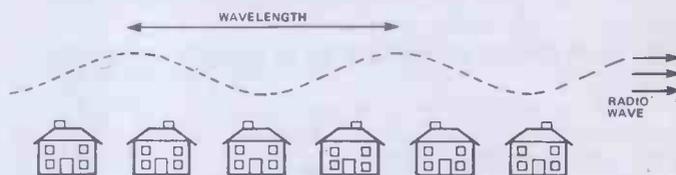


Figure 1. Wavelength. As the radio wave travels through space, there is a measurable distance between wavepeaks. This distance is the wavelength

Now Hertz and several others reckoned that an alternating voltage on a wire would cause a radio wave to be launched only if the wire was long compared with the wavelength — and no-one was likely to come up with a wire long enough to launch a 50 Hz wave. Hertz therefore concentrated on trying to generate much shorter wavelengths, which meant much higher frequencies. That, in turn, meant forgetting about rotating machines, because no alternator could stay in one piece at the frequencies Hertz was trying to generate; that is, frequencies of several thousands of millions of hertz. He solved the problem by using spark-gaps to generate high-frequency signals (see Fig. 1 on page 56), and radio was born at last.

Shift To Thermionic Valves

Radio has changed a lot since that momentous discovery by Hertz, and the work of Marconi, Tesla, Popov and many others who developed Hertz's laboratory experiments into a workable method of communication. Radio at the start of this century was still primitive — an induction coil to develop a high voltage, a spark-gap to cause high-frequency oscillations, and an aerial. The only control that was possible was to switch the induction coil on and off, using a telegraph key so that Morse code could be transmitted. To distinguish this from the 'normal' method of telegraphy, transmitted along wires, it was christened 'wireless telegraphy', and that's where the word 'wireless' comes from.

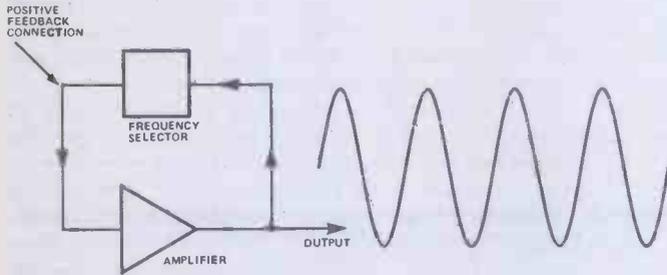


Figure 2. Block diagram of an oscillator

As a way of communicating short or emergency messages spark-gap transmitters were effective, and they were carried as emergency transmitters on ships right up to the '50s. But radio broadcasting needed something much more electronic in nature, and that came when thermionic valves were developed during the early years of this century. The thermionic valve was the device that dominated electronics for half a century. It could rectify (convert AC into current in one direction only), amplify (create a large-scale copy of an alternating voltage) and, most important of all, oscillate. Oscillation means creating an alternating voltage, and the important difference between a valve oscillator and a rotating generator is that the valve, like the transistor, has no mechanical moving parts. That in turn means that higher frequencies were at last simple to generate (as long as they were not *too* high!). It also meant that transmitters could operate at last on set frequencies.

That last remark needs some explaining. An oscillator, whether it uses a valve or a transistor, consists of three parts: an amplifier, a frequency selector and a positive feedback circuit (see Fig. 2). The amplifier has an input terminal and an output terminal, and produces at its output a large-scale copy of the alternating voltage — the signal — at its input. A frequency selector is a circuit which, as its name suggests, picks out one frequency of signals and rejects all others. A positive feedback circuit connects the output of an amplifier back to its input so that the amplifier provides its own input signal and doesn't need any other signals. Put these three components together and you have the kind of oscillator that is useful for radio. Because of the frequency selector, though, the signal from such an oscillator is a sine wave which has a single frequency, a frequency which can be changed only by altering the frequency selector circuit.

The old spark-gap transmitters lacked such refinements, and in the early days of radio no-one needed them anyway. As more and more transmitters were built, however, it became important to prevent them from in-

terfering with each other (as they did because the spark-gap created signals which comprised a huge mixture of frequencies). Valve oscillators allowed different transmitters to operate on different frequencies, not interfering with each other. They also permitted something else — modulation.

Controlling The Waves

Modulation means 'control', and in radio it means the control of the high-frequency oscillations of the radio wave or carrier wave. Morse code is a simple type of modulation, on or off, a digital signal long before its time. Why would we want to modulate a carrier wave? In the early days the most important reason was the ability to carry speech rather than Morse code. The human voice (yes, I include even DJ's) produces sound waves in air. Microphones can then convert these into electrical waves which have the same frequency and waveshape (Fig. 3) as the sound waves, so that we can amplify the electrical waves, something we can't do with sound waves. We cannot, however, transmit these electrical waves through space because their frequencies are too low — most voice signals are in the range of 300 Hz to 2000 Hz. The solution that was found simultaneously by several pioneers of radio was to make the high-frequency signals produced by an oscillator carry these low-frequency signals — the audio frequency signals, as they were later called. To do this it was necessary for the audio signals to *control* some feature of the high-frequency radio signals. In other words, the audio signals were used to *modulate* the radio signals.

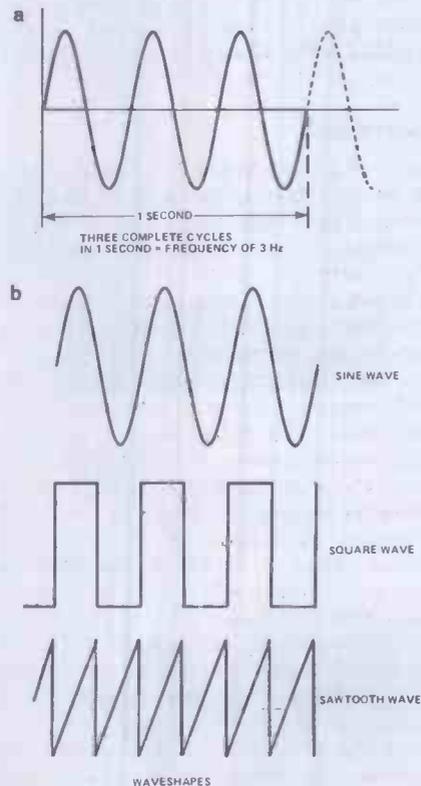


Figure 3. Frequency and waveshape. Frequency (a) is the whole number of complete cycles of a wave which happen each second. The waveshape is the shape of the graph of the wave plotted against time. For a sound wave, the quantity that is plotted is air pressure, and for an electrical wave, voltage is plotted



The idea had been around for a long time. In 1903, Valdemar Poulsen (who invented tape recording) patented a way of modulating the output of a spark-gap transmitter. It was called the 'singing arc' and it was necessary to speak directly into the spark. There were no volunteers for DJ duties — not surprising, when the spark was a foot long and generated by nearly 100,000 V!

The use of valves as oscillators made possible a comparatively simple method of modulation, known as amplitude modulation. The amplitude of an oscillation is the voltage of the signal measured from one peak of the wave to the opposite one (Fig. 4): strictly speaking, this is peak-to-peak amplitude, because there are other ways of measuring amplitude. The idea of amplitude modulation is to use the audio signal to control the amplitude of the carrier wave, so that the carrier wave has its normal amplitude only when the audio wave voltage is zero.

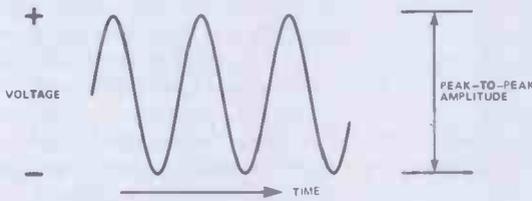


Figure 4. Peak-to-peak amplitude for a wave

When the audio wave is at its negative peak the carrier wave amplitude is reduced, and when the audio wave is at its positive peak the amplitude of the carrier wave is greater than normal. In this way (Fig 5), the outlines of the carrier wave are a copy of the waveshape of the audio wave — the carrier has been modulated. The carrier wave is still a radio frequency wave, so that it can be transmitted easily. At the same time it carries the information of the audio wave with it.

Band On The Side

A curious thing happens when a carrier wave is modulated. Before modulation, a carrier which is a sine-wave consists of one frequency only. When it is modulated other frequencies are present, equal to carrier

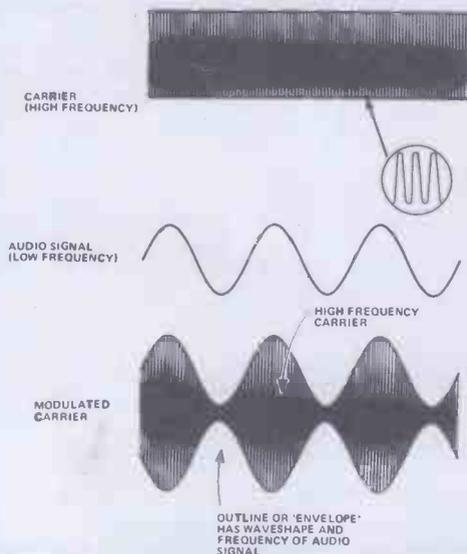


Figure 5. Modulating a radio-frequency carrier so that it carries an audio frequency wave. The frequency of the carrier must be much higher than the frequency of the audio wave

frequency plus audio frequency and carrier frequency minus audio frequency. For example, if the carrier frequency were 100 kHz, then before modulation only a frequency of 100 kHz would be present. When this same carrier is modulated with, for example, a 5 kHz sine wave, then four frequencies are present. One is the carrier frequency of 100 kHz, another is the audio frequency of 5 kHz. In addition, however, there are frequencies of 105 kHz (carrier + audio) and 95 kHz (carrier - audio) present, and these are called sidebands. The reason for the name? If we draw a graph of signal amplitude plotted against frequency, these two new frequencies lie on each side of the line that represents the carrier frequency (Fig. 6).

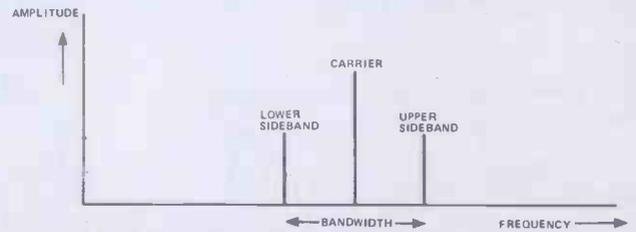


Figure 6. Sidebands. A carrier alone has a single value of frequency. When it is modulated by a low-frequency signal, the result is two new frequencies, the upper and lower sidebands

Why should this be important? For one thing, it limits the range of frequencies that we can use for radio transmitters. We can't, for example, have one transmitter operating at 100 kHz and another at 105 kHz if they are both being modulated with audio frequencies up to 5 kHz. If we did, then any receiver which was tuned to receive the complete signal (carrier plus sidebands) from one transmitter would also receive some of the sidebands of the other transmitter (see Fig. 7). This overlap causes interference, so that clear reception of either transmitter is not possible.

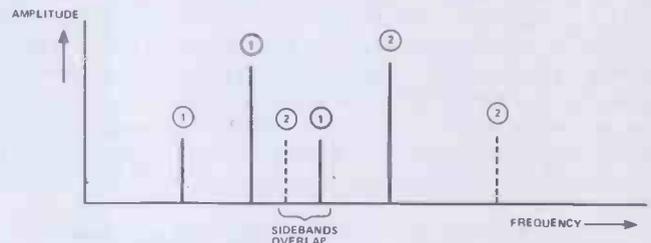


Figure 7. Interference is caused when the sidebands of two transmitters overlap, even though the carriers are separated

The sidebands have another effect. We have assumed so far that the radio transmission has been at a single frequency, the carrier frequency, so that a receiver which could receive only that frequency would suffice. Because a modulated carrier contains sidebands, however, a receiver for a modulated signal must be able to pick up and amplify the full range of frequencies from the lower sideband frequency to the upper one: this is the range of frequencies that we call the bandwidth.

Capturing Signals With A Ferrite Rod

Receiving a radio wave starts with catching a chunk of the modulated radio wave which has been sent out from the transmitter. The traditional way of doing this was to use a long piece of wire (Fig. 8), the aerial, slung between insulators and well clear of buildings. The radio wave is both

an electric and magnetic wave, and the electric part of the wave will produce an alternating voltage between the ends of any wire in its path. The voltage is greatest if the length of the wire is equal to a quarter of the wavelength of the wave, and that is the principle that we use for TV (operating at ultra high frequencies) and FM radio (operating at very high frequencies). For transmissions at medium wave, where the wavelength is several hundred metres, a quarter-wavelength aerial is usually impractical.

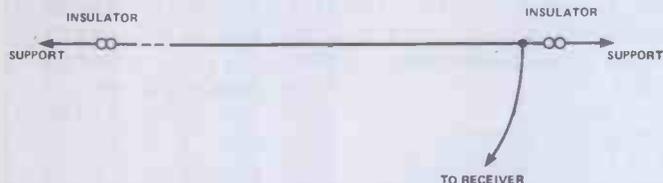


Figure 8. The traditional aerial, a long piece of wire insulated from its supports

The alternative to a long-wire aerial is to detect the magnetic part of the wave, using a coil. This method has been used for many years (it was called a frame aerial in the early days of radio) but was given a tremendous boost in the late '50s by the use of ferrite rods. Ferrite is a non-metallic magnetic material which, like all magnetic materials, has the ability to concentrate magnetism (see Fig. 9). By winding a coil round a ferrite rod, the magnetic portion of the transmitted wave can be made to provide an alternating signal between the ends of the coil, and because of the concentrating effect of the ferrite this signal can be as large as would be obtained from quite a long aerial wire. In addition, the ferrite rod is *directional*, because it is the magnetic waves approaching the *ends* of the ferrite rod that are most concentrated by the rod. Other magnetic materials, incidentally, are useless for this purpose because they are conductors, and the signal current flows within the material rather than in the coil — we had to wait for non-conducting ferrite before this method became really useful.

Now that we have a radio signal between the ends of a coil, what do we do with it? There are two important requirements. One is to select the signal we want from the thousands which are sent out from transmitters all over the world. The other is to amplify the signals, and extract the modulating audio signals from them.

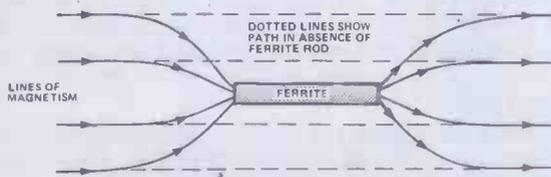


Figure 9. How ferrite concentrates magnetism. The dotted lines show what the tracks of the magnetic lines would be if no ferrite were present

Sorting Out The Signals

Selection is not quite so difficult as it sounds. Of all these thousands of signals, many are so faint that we can forget about them, and the stronger ones, providing they are all on different carrier frequencies, can be separated by using resonant circuits. A resonant circuit in its most familiar form consists of a coil (inductor) and a capacitor (Fig. 10a). The most usual form of this circuit in

amplitude-modulated radios is the parallel one, and that's the one we will look at.

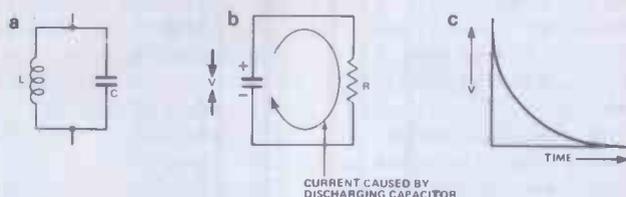


Figure 10. The resonant (tuned) circuit (a). This is a parallel type. If the capacitor were charged and connected to a resistor (b), then the capacitor would rapidly discharge through the resistor (c)

Imagine, to start with, a charged capacitor. If we connect this capacitor to a coil, the charge will flow from the positively charged plate of the capacitor through the coil to the negatively charged plate: this movement of charge is a current. If we had simply connected a resistor to the charged capacitor the current through the resistor (Fig. 10b) would heat up the material of the resistor, the heat would be lost to the air around, and once the capacitor was discharged that would be the end of the process. In other words, the energy of the charged capacitor has been changed to heat energy and lost. When the capacitor is connected to a coil which has a very low resistance, however, things are very different. The action of a coil, an inductor, is to keep current flowing, because the energy of the current goes into creating magnetism rather than heat, and magnetism does not flow away. Even when the voltage that has caused the current to flow is at zero the current does not stop, because the magnetism converts back into current, pouring charge back into the capacitor, this time charging it up in the opposite direction (Fig. 11). It can't stop there as the coil is still connected to the capacitor, so that the capacitor discharges again, sending current through the coil in the opposite direction this time. Once again the coil keeps the current flowing so that the capacitor ends up charged again, almost as it was in the beginning, and will then start to discharge again. This see-saw action keeps going at a rate which is set by the value of the capacitor and the inductance of the coil, but it can't go on forever because the coil has resistance which causes some of the electrical energy to be converted into heat and lost.

We have to leave the story of Radio at this point, but next month we'll continue the saga starting with the waveform obtained from a circuit such as that in Fig. 11.

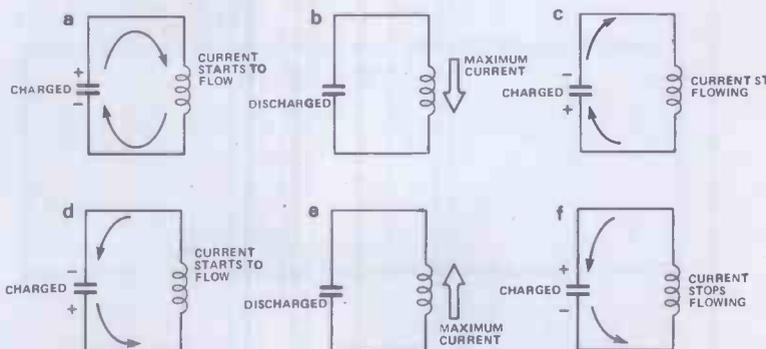


Figure 11. A charged capacitor in a resonant circuit. Figures 11a to 11f show how the charge produces a current which then charges the capacitor in the opposite direction, reversing the current until the charge is almost at its original value

HE

GUITAR PHASER	ZD85	Sept. '80	£9.60	HOBBYTUNE	ZD34	Oct. '79	£18.00
BENCH POWER SUPPLY UNIT	ZD87	Sept. '80	£25.00	MULTI OPTION SIREN	ZD36	Oct. '79	£10.50
DEVELOPMENT TIMER	ZD86	Sept. '80	£8.75	ANALOGUE AUDIO			
TOUCH SWITCH (on Vero)	ZD84	Sept. '80	£4.50	FREQUENCY METER	ZD35	Oct. '79	£15.00
AUTO PROBE	ZD83	Sept. '80	£3.00	COMBINATION LOCK	ZD29	Sept. '79	£12.50
REACTION TIMER	ZD82	Sept. '80	£26.50	★STARBURST	ZD30	Sept. '79	£14.50
MICROMIXER (on Vero)	ZD81	Sept. '80	£8.50	LAMP DIMMER	ZD31	Sept. '79	£6.50
EQUITONE CAR EQUALISER	ZD52	Aug. '80	£13.30	ULTRASONIC SWITCH	ZD32	Sept. '79	£21.00
GAS DETECTOR	ZD55	Aug. '80	£22.00	CONSTANT VOLUME AMPLIFIER	ZD28	Aug. '79	£11.50
PASS THE LOOP GAME	ZD56	Aug. '80	£12.00	INJECTOR TRACER	ZD27	Aug. '79	£4.50
RADIO TIMER (on Vero)	ZD57	Aug. '80	£5.50	LED TACHOMETER	ZD26	Aug. '79	£14.75
MOVEMENT ALARM (on Vero)	ZD54	Aug. '80	£5.00	BABY ALARM	ZD25	July '79	£13.50
OP. AMP CHECKER (on Vero)	ZD53	Aug. '80	£4.00	POINTS SWITCH	ZD24	July '79	£12.50
CAR BOOSTER (no speakers)	ZD50	July '80	£18.00	LINEAR SCALE OHMMETER	ZD23	July '79	£14.00
HAZARD FLASHER	ZD48	July '80	£10.50	SHARK	ZD22	July '79	£22.75
★PUSH-BUTTON VOLUME				G.S.R. MONITOR	ZD19	June '79	£10.50
CONTROL	ZD47	July '80	£19.50	ENVELOPE GENERATOR	ZD20	June '79	£11.79
SOUND FLASH TRIGGER (on Vero)	ZD49	July '80	£3.50	DRILL SPEED CONTROLLER	ZD21	June '79	£7.00
2 WATT AMPLIFIER (on Vero)	ZD46	June '80	£3.90	WHITE NOISE EFFECTS UNIT	ZD18	May '79	£16.85
METRONOME (on Vero)	ZD51	June '80	£3.50	PARKING METER TIMER	ZD17	May '79	£6.70
MICROBE R/C SYSTEM				DIGIBELL PROJECT	ZD16	May '79	£5.00
(less Servos)	ZD45	June '80	£17.50	VARIABLE POWER SUPPLY			
FOG HORN	ZD44	June '80	£4.50	0.30V 1 AMP	ZD15	May '79	£30.00
★EGG TIMER	ZD43	June '80	£6.50	TRANSISTOR GAIN TESTER	ZD76	April '79	£6.50
MINI CLOCK	ZD10	May '80	£26.00	CISTERN ALARM	ZD75	April '79	£5.50
5080 PRE-AMP	ZD11	May '80	£32.00	MODEL TRAIN CONTROLLER	ZD74	April '79	£26.00
TRACK CLEANER	ZD12	May '80	£7.75	PHOTOGRAPHIC TIMER	ZD73	March '79	£14.50
★R/C SPEED CONTROLLER	ZD3	April '80	£9.60	tone CONTROL	ZD72	March '79	£9.00
HOBBY COM	ZD8	April '80	£28.60	CASANOVA'S CANDLE	ZD71	March '79	£7.50
ELECTRONIC IGNITION	ZD2	April '80	£18.25	SHORT WAVE RADIO	ZD66	Feb. '79	£12.50
DIGITAL FREQUENCY METER	ZD9	April '80	£27.75	SINE/SQUARE WAVE			
SHORT WAVE RADIO	ZD80	March '80	£19.50	GENERATOR	ZD67	Feb. '79	£22.50
TOUCH SWITCH	ZD79	March '80	£5.00	SCRATCH AND RUMBLE			
5080 PSU MODULE	ZD78	March '80	£29.50	FILTER MONO	ZD68	Feb. '79	£22.50
SYSTEM 5080A	ZD77	March '80	£15.00	SCRATCH AND RUMBLE			
PASSION METER	ZD6	Feb. '80	£5.00	FILTER STEREO	ZD69	Feb. '79	£25.00
WIN INDICATOR	ZD42	Feb. '80	£9.00	CAR ALARM	ZD70	Feb. '79	£8.50
INFR RED REMOTE CONTROL	ZD7	Feb. '80	£19.35	FLASH TRIGGER (less flash gun)	ZD65	Jan. '79	£10.50
SCALEXTRIC CONTROLLER	ZD41	Jan. '80	£52.50	TOUCH SWITCH	ZD63	Jan. '79	£5.50
CROSSHATCH GENERATOR	ZD4	Jan. '80	£11.25	VARI-WIPER	ZD64	Jan. '79	£8.00
DIGI-DIE	ZD5	Jan. '80	£5.50	GRAPHIC EQUALISER	ZD62	Jan. '79	£25.00
RING MODULATOR	ZD1	Dec. '79	£8.50	PUSH-BUTTON DICE	ZD61	Dec. '78	£6.00
SCALEXTRIC CONTROLLER	ZD39	Dec. '79	£21.50	AUDIO MIXER	ZD14	Dec. '78	£20.30
BARGRAPH CAR VOLTMETER	ZD40	Dec. '79	£6.60	BEDSIDE RADIO	ZD58	Nov. '78	£12.50
GUITAR TUNER	ZD38	Nov. '79	£8.50	STEREO AMPLIFIER (HOBIT)	ZD59	Nov. '78	£52.50
★R2 D2 RADIO	ZD37	Nov. '79	£8.60	WAA-WAA PEDAL	ZD60	Nov. '78	£30.00
TANTRUM	ZD33	Oct. '79	£37.50				

IONISER KIT: ZD13. This negative Ion generator gives you power to saturate your home with millions of refreshing ions, without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain filling your room. The result? Your air feels like fresh ocean air, crisp and wonderfully refreshing. All parts p.c.b. and full instructions £10. A suitable case including front panel neon switch, etc., available at £8 extra.

PLEASE NOTE OUR NEW ADDRESS

LATE EXTRA

Watchdog Intruder Alarm	ZD89	OCT. '80	£15.75
Temperature Controlled Soldering Iron	ZD90	OCT. '80	£9.00
Freezer Alarm (on Vero)	ZD91	OCT. '80	£8.50
Tug O' War Game	ZD94	OCT. '80	£12.50
Nobell Doorbell	ZD93	OCT. '80	£9.75
Kitchen Timer (on Vero)	ZD92	OCT. '80	£5.50
Light Dimmer	ZD88	OCT. '80	£5.00

All kits contain components as specified plus Texas I.C. sockets, where required, also connecting wire.

FAIRCHILD FLV150 red. 2 LEDs, 10 for £1.00, 100 for £7.50
DALY ELECTROLYTIC CAPACITORS 2000uF 100v £1.50
PHILIPS SCOPE Tube 5" CV2191/DG-13-2 £10

If you do not have the issue of H.E. which contains the Project, we can supply a reprint at 40p extra. Please add 30p post and packing. Add 15% VAT to total order.

Callers please ring to check availability of kits.

T. POWELL

ADVANCE WORKS
44 WALLACE ROAD, LONDON, N.1



SHOP HOURS:
 MON.-FRI. 9-5.30 p.m.
 SAT. 9-4.30 p.m.

Minimum telephone Orders £5
 Minimum Mail Order £1

Your Letters

A selection of your letters to the Editor

IT IS ALWAYS frustrating to have reached the final stages of project construction . . . and to be stuck for one vital component. This was certainly the experience of David White in our first letter.

Dear Sir,

From your October 1980 HE issue, in my schools Electronics Club, I have built the "Intruder Alarm". But, I am unable to complete it because two ICs used in the circuit I cannot obtain. So could you tell me where I can get it and how much they cost or an equivalent as the project has already cost me £9.

The IC's number is JCL 7611. Maplin and Watford do not stock it.
David White
Hornchurch, Essex

True, the ICL 7611 is not a widely-stocked device. However, a quick check by 'phone revealed that it is available directly from Magenta Electronics, 98 Calais Road, Burton-on-Trent, Staffs for £1.31 plus 40p postage and packing.

The next two letters relate to circuit boards.

Dear Sir,

I am wondering if you could explain the Hobby Prints and also generally how P.B.C. is constructed.
R.G. Bannocks
Leytonstone

The Your Letters page is the wrong place to answer your two queries in sufficient depth. I would suggest that you read Building Site in the November '80 issue of HE, on pages 46 and 47. A good description is given of how to use Hobbyprints and of the different stages in the production of a PCB. (I assume it was PCB that you were referring to.)

Dear Sir,

I am very interested in H.E. projects. I found it difficult to follow mounting of components on P.C.B. given for the 'Watchdog' Alarm (H.E. October 1980).

Since I am a beginner and keen on H.E. projects, would you please help me to mount components on Veroboard layout, which I find much easier to follow. In most of your projects you do give Veroboard layouts but on this occasion you gave it on P.C.B.
D.L. Rao
London N18

When I looked at the component overlay in Fig. 3, page 61 of the October '80 Issue, I could appreciate your problem. We try, wherever possible, to show a faint pattern of the copper track — appearing as if the board were translucent (see Light Dimmer, Fig. 4, on page 35 of the same issue). Around that time we were experimenting to see if the overlay could be shown without the pattern. One problem associated with including the pattern is that, when the board contains

many components and connection points, inclusion of an outline of the track on the overlay can make the overall picture confusing. Most designs published since October '80 have, however, included the pattern.

Some projects are more suited to PCB layout while others are better suited to Veroboard. A few readers have told us that they have tried to use Veroboard in place of our PCB patterns but have become confused in the process, because of the cross-linking required. We will continue to use both methods: Veroboard for the simpler projects and PCBs for the complicated ones (or where space-saving is important).

Finally, a call for some information on electronic components.

Dear Sir,

I am a pupil at Tunbridge Wells Technical High School. I am undertaking an English Study on Electronics.

I would be very pleased if you could send me some information on how components are made and work. It is a beginners study so I need information on resistors, capacitors, diodes and transistors etc.
Ian Scholey
Edenbridge, Kent


We plan to take a careful look at the fundamental components of electronic circuits in a few issues' time. Meanwhile, you might like to refer to Into Electronics Plus, a booklet which gives broad coverage of electronic components. It is available, price £1.30 (including post and packing) from the Hobby Electronics Book Service, Modmags Ltd, 145 Charing Cross Road, London WC2H 0EE. HE

FIVE NEW BOOKS

in the Newnes


constructors projects series

Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting-up and trouble-shooting problems may be solved. The skilful use of colour in the text helps to clarify operation and circuit board layouts are suggested. Shopping lists of components are drawn up for each project. Each book measures 216 x 135mm and has 96 pages.

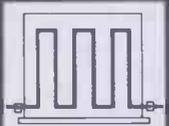


Electronic Projects for Home Security

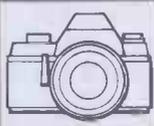Owen Bishop
0 408 00535 1
Describes electronic alarms to detect and deter intruders or give warnings of gas or fire



Electronic Projects in Photography

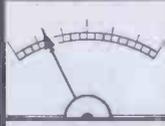R A Penfold and
J W Penfold
0 408 00500 9
Contains fifteen electronic projects for the photographer or electronics enthusiast




Electronic Test Equipment Projects

Alan C Ainslie
0 408 00528 9
The projects described in this book will assist in the construction or development of audio and radio frequency circuits as well as logic and control instrumentation



More Electronic Projects in the Home

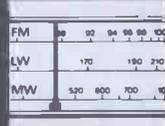A J Flind
0 408 00501 7
Contains a selection of circuits which will be useful around the home, including electronic switches, alarms and intercoms.



Projects in Amateur Radio and Short Wave Listening

F G Rayer - G30 GR
0 408 00502 5
Describes receivers and other aids which will be useful to the licensed amateur and to the short wave listener.

AVAILABLE NOW!

from your local bookshop

or in case of difficulty direct from us:

Please tick the books you need. This coupon can be cut out and returned to Patricia Davies at the address below.

Please send me _____ copy/ies as marked above. I enclose cheque/PO for £ _____ in total payment or debit my credit card account as follows (please tick)

Access Master Barclaycard American & other Express

My Credit Card No. is _____

Signature _____

Date _____

Name _____

Address _____

all at
£2.95
each

Already well established in the constructors projects series

Electronic Game Projects

F G Rayer 0 408 00379 0

Electronic Projects in the Home

R A Penfold 0 408 00338 3

Electronic Projects in the Car

M George 0 408 00386 3

Electronic Projects in Hobbies

F G Rayer 0 408 00354 5

Electronic Projects in the Home

Owen Bishop 0 408 00346 4

Electronic Projects in the Workshop

R A Penfold 0 408 00383 9

Electronic Projects in Music

A J Flind 0 408 00391 X

Projects in Radio and Electronics

Ian R Sinclair 0 408 00345 6

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH (HE/6.81)

ELECTRONI-KIT

Introducing our new

CHIP SHOP KITS

Each CHIP SHOP KIT is complete in every way and contains all the components necessary to build and operate the project described. All you need is a Soldering Iron (see Kit No. 2) and a 9v battery. Each kit includes step-by-step instructions on construction and detailed educational notes about the individual circuit, together with advice about soldering techniques.

Kit. No. 2 - SOLDERING IRON - contains a high quality British soldering iron; a 1Amp fuse and solder together with straightforward instructions upon how to handle your soldering iron and the best techniques for its use and maintenance.

Kit No. 3 - ELECTRONICS TOOLS - contains a selection of useful tools for anyone starting in electronics, together with instructions about the use and care of your equipment.

SOLDER is included with every kit.

Kit. No.		Price
1(a)	Morning Call plus	
1(b)	Transistor Tester	£5.00
2	Soldering Iron	£5.00
3	Electronics Tools	£4.50
4	Electronic Organ	£3.50
5	Morse Code Trainer and Siren Oscillator	£4.00
6	Light Operated Burglar Alarm	£4.00
7	Buzzer - Aircraft	£3.00
8	Light and Sound Alarm	£3.00
9	Lie Detector	£3.00
10(a)	Lamp Flasher plus	
10(b)	Sleep Inducer	£4.50
11(a)	Cat Sound plus	
11(b)	Night Light Reminder	£4.50
12(a)	Bicycle Horn plus	
12(b)	Electronic Shocker	£5.00
13(a)	Light Sensitive Alarm plus	
13(b)	Electronic Lamp	£5.00
14	2-Transistor Radio	£4.00
15	Morning Alarm	£4.00
16	American Police Siren	£4.00
17	Flashing Dual-tone Horn	£3.50
18	Two-way Interphone	£5.00
19	4-Transistor Radio	£5.00
20	Clicker-Helicopter Oscillator	£3.00

All kits packed individually in attractive boxes. Loudspeakers are included with each kit (except nos. 2, 3, 14 where they are not required).

Kit nos. 1, 10, 11, 12, 13 contain two separate projects.

These kits are becoming available in Hobby and Electronics Stores all over the Country - look out for the CHIP SHOP DISPLAY in your local store.

If you cannot locate a stockist please order direct from Electroni-Kit Ltd. Please add 50p per kit for postage and packing.

Trade and Educational Enquiries welcomes.

Cheque/P.O./Access/Barclaycard (or 23p for full-colour illustrated literature) to DEPT. HECS.

ELECTRONI-KIT LTD.
RECTORY COURT, CHALVINGTON,
E.SUSSEX, BN27 3TD (032 183 579)

Chess Computers
TV Games
Hand Held Games

EGS

The Electronic Games Shop
A DIVISION OF CIRCOLEC

WE TRY THE HARDEST!

We sell a comprehensive range of chess computers and TV Games from Atari, Mattel, Chess Challenger, Videomaster, CGL, Grandstand and others. A fast mail order service is offered but demonstrations can be arranged with pleasure at our head office in Tooting - please telephone to arrange if necessary.

PRICE EXAMPLES

Atari VCS Console	£99	Jet Fighters	£22.95
Mattel Intellivision	£199	Including free mains adaptor	
Philips G7000 Console	£93.75	Galaxy Invader 1000	£22.95
Videomaster Database	£54	Including free mains adaptor	
All including free cartridge.		Earth Invader	£24.95
Chess Challenger '7'	£78	Game and Watch (Vermin, Fire, etc)	£17.95
Voice Sensory Challenger	£243	Colour Cartridge T.V. Game	
Sensory 'B' Challenger	£113	c/w 4 cartridges and adaptor	£34.80

All prices include VAT and postage

All cartridges available for programmable games listed. Please write or telephone for details of other games. Money immediately refunded if out of stock.

Please make cheques payable to CIRCOLEC and send order to FREEPOST (no postage required), LONDON SW17 8BR.




TELEPHONE
01-767 1233



Credit Orders
Welcome



GEC AM/FM STEREO TUNER AMPLIFIER CHASSIS. Originally designed for installation into a music centre. Supplied as two separate built and tested units which are easily wired together. **Note:** Circuit diagram and interconnecting wiring diagrams supplied. **Rotary Controls:** Tuning, on/off volume, balance, treble, bass. **Push-button controls:** Mono, Tape, Disc, AFC, FM (VHF), LW, MW, SW. **Power Output:** 7 watts RMS per channel, at better than 2% THD into 8 ohms. 10 watts speech and music. **Frequency Response:** 60Hz-20kHz within ± 3 dB. **Tape Sensitivity:** Output - typically 150 mV. Input - 300 mV for rated output. **Disc Sensitivity:** 100mV (ceramic cartridge). **Radio:** FM (VHF), 87.5MHz - 108MHz. Long wave 145kHz - 108kHz. Medium wave,

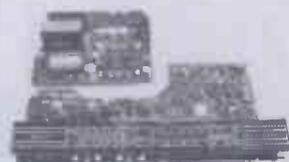

520kHz - 1620kHz. Short wave. 5.8MHz - 16MHz. **Size:** Tuner - 2 1/4 in. x 1 1/2 in. approx. Power amplifier - 2 in. x 7 1/2 in. x 4 1/2 in. approx. 240V AC operation. Supplied complete with fuses, knobs and pushbuttons, and LED stereo beacon indicator. **Price £21.50 plus £2.50 postage and packing.**

Stereo Cassette Tape Deck Module comprising of a top panel and tape mechanism coupled to a record/play-back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready-built and tested. Smart black and silver finish.

Features: Three digit tape counter, Auto-stop, Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input sensitivity** 100mV to 2V. **Input impedance** 68K. **Output level** 400mV to both left and right-hand channels. **Output impedance** 10K. **Signal to noise ratio** 45dB. **Wow and flutter** 0.1%. **Power supply requirements** 18V D.C. at 300mA. **Connections** the left and right-hand stereo inputs and outputs are via individual screened leads all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2 in. x 1 1/2 in., clearance required under top panel 2 1/4 in.

Supplied complete with circuit diagram and connecting diagram. **Price £26.70 + £2.50 postage and packing.** Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY



* SAE for current lists * Official orders welcome * All prices include VAT * Mail order only * All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please telephone 0702 527572.



GGADGETS GGAMES & KITS

Here is the second free GG&K supplement to HE. Last month we reviewed the Tantel adaptor for connecting you and your TV to Prestel. This month we look at the Radofin TAD110 adaptor, which enables your TV to display CEEFAX and ORACLE teletext transmissions. We also review three hand-held games, install a car radio/cassette combination and try our hand at a portable electronic chess game

Time For Teletext

We had a look at Tantel, Tangerine Computer Systems' Prestel adaptor, last month. The other sort of TV information service is teletext — but again, you need an adaptor. This month we look at one available from Silica Shop.

There isn't the amount of information available on teletext (about 700 pages) that there is on Prestel (nearly 200,000 pages at present) and the speed of page recall is much slower. One point in teletext's favour, however, is that any information received is completely free. All the on-screen data which you can read is already there (on the received TV signal) and you only need an adaptor to decode it into a readable form. The cost of using Prestel, on the other hand, can be quite high, because you are billed (on your telephone bill) for telephone time and also for certain (not all) pages of information. You pay your money. . . .

The Radofin TAD110 Teletext Adaptor comes complete with the necessary leads and instructions. All you need to supply is a plug, a TV and a good aerial signal. You take out the aerial plug, which goes to the back of your TV, and put it in the back of the adaptor, where it says 'To aerial'. Next, you plug the lead from the adaptor's 'To TV' socket into your TV. Last, you switch on and go.

Selecting Pages

Your TV needs to be tuned to channel 36 and the adaptor must be tuned to your usual received TV stations. This procedure is a bit tricky, but the instruction booklet tells you how to do it step-by-step.

You now have three complete magazines under your remote control (at the end of a long lead). The two Beeb stations — 1 and 2 — have a 100-page magazine each, under the name CEEFAX, while the ITV version is called ORACLE and has about 500 pages.

When you first switch on, the adaptor automatically looks for and displays page 100 — the index page (except for BBC2, which has it on page 200). After this, requesting any particular page is a simple matter of entering the number of the page onto the keypad. After a few seconds' delay, due to the fact that the pages are broadcast in sequence, your requested page will appear on the screen. And so it goes on.

You can choose between teletext

or television via your hand controller, or have a mix of the two on the screen, at any one time. An 'alarm clock' facility, using the highly accurate clocks transmitted by the broadcasting companies in the TV signal, can produce a chosen page or signal onto the screen at a preset time, if you want. You can also use one of the clocks as (would you believe) a digital clock to tell the time by.

Useful Machine?

We found the adaptor very simple to operate, and extremely useful in obtaining news headlines or sport updates, looking for what's on at theatres, cinemas, and of course TV programmes. It's ideal if, like us, you're a gadget-lover, button-pusher or gimmick-freak. If you are, then you'll have hours of fun, entertainment and interest with one of these.

Radofin TAD110 Teletext Adaptor is available for £199 including VAT from Silica Shop Ltd, 1-4 The Mews, Hatherley Road, Sidcup, Kent.



Multitesters 100,000 opv
 AC volts:- 0 - 5 - 10 - 250 - 1000
 DC volts:- 0 - 0.5 - 25 - 10 - 50 - 250 - 1000
 DC current:- 0 - 10ua - 25ua - 500ua - 0 - 5 ma - 50 ma - 500 ma - 10 amp
 AC current:- 10 amp
 Resistance:- 0 - 20 ohms - 200 ohms - 5 K ohms - 200 K ohms - 50 K ohms - 200 K ohms - 5 meg ohms - 50 meg ohms

As a transistor tester
 HFE:- 0 - 5 (NPN) - PNP
 ICO:- 0 - 5 ua (NPN) - PNP
 Dims:- 178x 140 x 70 mm
 Please add 30p P.P. per unit order as MT 20

Multitester
 1,000 opv
 AC volts:- 0 - 5 - 150 - 500 - 1000
 DC volts:- 0 - 15 - 150 - 500 - 1000
 DC current:- 0 - 1 ma - 150 ma
 Resistance:- 0 - 25 K ohms - 100 K ohms
 Dims:- 90 x 61 x 30 mm
 Please add 30p P.P. per unit order as MT

Multitester
 20,000 opv
 AC volts:- 0 - 10 - 50 - 100 - 250 - 500 - 1000
 DC volts:- 0 - 0.5 - 5 - 25 - 125 - 250 - 500 - 1000
 DC current:- 0 - 50 ma - 0.5 ma - 250 ma
 Resistance:- 0 - 3 K ohms - 300 K ohms - 3 meg ohms
 Deibels:- -20 to +63 db
 Dims:- 127 x 90 x 32 mm
 Please add 30p P.P. per unit order as MT 7

Headphones
 High velocity mylar diaphragms. Coiled lead. Finished in a combination of bright aluminium.
 Impedence:- 8 ohms
 Frequency response:- 15 - 22000 HZ
 Weight:- 350 gms
 Please add 30p P.P. per unit order as PH 12

ARROW AUDIO CENTRE
 20 NORTH BAR BANBURY OXON OX16 0TF.
 TELEPHONE BANBURY (0295) 3677
 TERMS: CHEQUE/PO WITH ORDER. CALLERS WELCOME

ELECTRONIC IGNITION SAVES PETROL



More and more new cars use electronic ignition to give the best performance and economy. Bring YOUR CAR up to top specification by fitting the latest TOTAL ENERGY DISCHARGE electronic system.

- TOTAL ENERGY DISCHARGE** gives all the advantages of the best capacitive discharge ignitions;
- ★ **Peak Performance**—higher output voltage.
 - ★ **Improved Economy**—consistent high ignition performance.
 - ★ **Better Starting**—full spark power even with low battery.
 - ★ **Accurate Timing**—prevents contact wear without 'contactless' errors.
 - ★ **Smooth Performance**—immune to contact bounce effects

- PLUS**
- SUPER HIGH POWER SPARK**—3½ times the energy of ordinary C.D. systems.
 - OPTIMUM SPARK DURATION**—to get the very best performance and economy with today's lean carburettor settings.
 - DESIGNED IN RELIABILITY**—with the 'ultimate insurance' of a changeover switch to revert instantly to standard Ignition

TECHNICAL DETAILS
HIGH EFFICIENCY INVERTER. A high-power, high efficiency, regulated inverter provides a 400-volt energy source—powerful enough to store twice the energy of other designs and regulated to provide full output even with the battery down to 4 volts.

SUPERB DISCHARGE CIRCUIT. A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the Ignition delay associated with lower power 'long burn' inductive systems. In addition this circuit maintains the correct output polarity, thereby preventing unnecessary stress on the H.T. system.

SOPHISTICATED TRIGGER CIRCUIT. This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

IN MONEY-SAVING KIT FORM at £14.85
Also MOTORCYCLE TWIN OUTPUT KIT at £22.94

Inc. V.A.T. and P. & P.

All you need is a small soldering iron and a few basic tools — everything else is supplied with easy-to-follow instructions.

FITS ALL 6/12-volt NEGATIVE EARTH VEHICLES
ELECTRONIZE DESIGN
 2 Hillside Road, Four Oaks
 Sutton Coldfield, West Midlands, B74 4DQ
 Phone 021-308 5877

HH/857
 Multiband Receiver plus 40-channel CB Monitor. Frequency coverage:
 54- 87 MHz 145-176 MHz
 88-108 MHz Plus H1 40 CB Channels
 108-145 MHz
 This unit has a telescopic antenna and squelch control, sockets for earphone and external DC power source.
£21.95 inc.

The latest from the U.S.A.
PINBALL WIZARD
 ★ Still available ★
 Featured in Nov. issue of E.T.I.
 Home TV Game - B/W Kit
 Basic Kit **£28.90**
 Contains everything except box and controls
 Box and Controls **£6.50**. P.S.U. **£3.90**
 CEH Car Alarm Kit **£18.90**
 Chrome Chime 24-tune door chimes kit **£11.50**. Built **£15.95**

HE MICROBE R/C
 Basic Kit **£19.90**
 (2 PCBs and all PCB components)

ELECTRONIC GAMES

Star Chess TV Game	£63.35
Database Prog. TV Game	£89.95
Chess Challenger 7	£89.00
Voice Challenger	£230.00
Chessmate 8 level	£59.95
Zodiac Astrology Computer	£29.95
Electronic Mastermind	£14.90
Supersonic Mastermind, new	£21.00
Basketball	£24.95
UFO Masterblaster	£19.95
Soccer	£24.95
Boxing	£24.95
Jet Fighter, new	£22.95
Galaxy Invaders, new	£22.95
Radio Control Models—Various	

Ball Clock as H.E. offer. Kit **£24.95**, or ready-built **£29.95**.

S.a.e. enquiries. Please allow up to 21 days for delivery. ALL PRICES INCLUSIVE

UNIT 6 **N.I.C.**
 61 BROAD LANE, LONDON N.15 4DJ
 Day 01-808 0377; Eve 01-889 9736

ADVENTURES with ELECTRONICS

ADVENTURES WITH ELECTRONICS

UNILAB. KIT

A complete Kit, including S-Dec, wire & battery, for the 16 projects described in Tom Duncan's book 'Adventures in Electronics' published by John Murray. No soldering. Adopted for class use in many schools: and a welcome gift for ages 11 upwards.

With book, **£23.82**
 Without book, **£21.97**

Clear pictorial instructions for making the following: RAIN DETECTOR, INTERCOM, MORSE BUZZER, BURGLAR ALARM, 3 TYPES OF RADIO, PARKING LIGHT, FLASHING LAMP, ELECTRONIC ORGAN, METRONOME, SIREN, TIMER, COUNTER, FIRE ALARM.

And now available:
ADVENTURES WITH MICROELECTRONICS
 A similar Kit including 'Bimboard' and Integrated Circuits. Suitable for the complete beginner, or those who have already enjoyed 'Adventures with Electronics'.

With book, **£36.36**
 Without book, **£34.16**

Conversion Kit:
 With book, **£29.51**
 Without book, **£27.31**

Cash or cheque with order, please, to

UNILAB © UNILAB LTD. Clarendon Road, Blackburn, BB1 9TA, England. Telephone (0254) 57643 (59)

Prices include carriage and VAT and are correct at time of going to press.



Three In Hand

Here we have three neat little hand-held games from Computer Games Ltd: Galaxy Invader 1000, Grand Prix and Jet Fighters. All of them are battery-operated and so are great for carrying with you on the long journeys which seem to be an inevitable part of the family summer holiday. To cut down the cost of batteries, mains adaptors are available as an optional extra at £4.95 for Galaxy Invader 1000 and Jet Fighters. It is not possible to use a mains adaptor with Grand Prix: it uses only three AA-size batteries, and Computer Games considers that the game is unlikely to be played for long periods.

Galaxy Invader 1000

If you like space attacker games, then Galaxy Invader 1000 should appeal to you. It is housed in a particularly attractive yellow and black casing shaped like a missile, with an equally eye-catching three-column LED (light emitting diode) display in green and red. The graphics are neat and easily definable, consisting of standard space attacker-type figures of monsters (in green) and UFOs (in red). The invaders appear at random on the display, moving sideways and down towards your missile base. The UFOs appear only on the top row of the screen and disappear again if you don't manage to hit them. A maximum of two invaders and one UFO appear on the screen at any time.

You are given three missile laun-

chers for each game and shooting down a UFO will gain you 10 points on the accumulating scoreboard on the top of the display. Shooting down an invader will give you between one and five points depending on how far down the screen it gets before you blast it into infinity. When you have accumulated 700 points on the scoreboard you will automatically gain an extra missile launcher and 50 missiles. The game is over when either you have reached 1,000 on the scoreboard and repelled the invasion, or if all your missile launchers are destroyed, or if the invaders capture your missile pad. It also comes to an end if you have fired the maximum of 250 missiles.

There are sound effects with this machine which simulate the firing of your missiles or the demise of your enemy.

The controls of the game are simple: on the left of the case is a rudder for lateral movement across the display, on the right is the 'fire' button and in the middle is the on/off/reset switch and a skill control which can be set to three different levels, depending on how good you get.

In all, this is a very attractive game, well thought out and straightforward to use. It can stretch the abilities of the most skilled invaders player with its three skill levels and is as authentic as you can get for such a small machine. The case is sturdy enough to stand the wear and tear it is likely to get. At £22.95 including VAT it should prove to be a very popular game — particularly as with this version you can *actually beat them!*

Grand Prix

The second CGL offering is a game called Grand Prix. It is a car racing simulation game and this game's case is cunningly shaped like a Formula 1 racing car, made of good solid material.

The display of this game differs from that of the other two in that it is an LCD (liquid crystal display), the type preferred in most new digital watches. The black and grey display shows the three lanes of the race track and indicators for speed, time and lap. On the left of the case is the accelerator lever and on the right the steering key for changing between the lanes.

When playing the game, your car does not in fact move; it is the other cars which whizz past as you dodge them. The speed at which they pass you is determined by your use of the accelerator. There are sound effects to simulate the sound of your exhaust — and the sound of your car crashing! When the inevitable crashes occur your car will disappear for two seconds for repairs.

There are two modes which you can play in: 'lap' mode and 'time' mode. Playing in 'lap' mode will tell you how many laps you have completed in the fixed time of 140 seconds. In 'time' mode, you are told how many seconds it takes you to drive the distance of 800 kilometres.

This is an absorbing game: although you can't actually win, you can improve your reflexes. The display is a little unusual being an LCD, which seems to cause a few problems. LCD displays are notorious for being slow to change, unlike LEDs which are simply on or

ELECTRONIC GAMES

COLOUR CARTRIDGE T.V. GAME



SEMI-PROGRAMMABLE T.V. GAME
+ 4 Cartridges + Mains Adaptor
Normal Price £73
NOW REDUCED TO: **£39.50**
inc. VAT

DATABASE T.V. GAME



FULLY PROGRAMMABLE CARTRIDGE T.V. GAME
14 Cartridges available
Normal Price £87.86
NOW REDUCED TO: **£59**
inc. VAT

ATARI T.V. GAME



The most popular T.V. Game on the market with a range of over 40 cartridges including SPACE INVADERS with over 112 games on one cartridge.
Normal Price £198.90
NOW REDUCED TO: **£98.90**
inc. VAT

SPACE INVADERS



Hand-held Invaders Games available £19.95
+ Invaders Cartridges available to fit ATARI/RADOFIN/ACETRONIC/PHILIPS G7000
+ Cartridges also available for MATTEL/TELENG/ROWTRON/DATABASE/INTERTON

CHESS COMPUTERS




We carry a range of over 15 different Chess computers:

Electronic Chess **£29.95**
Chess Traveller **£49.95**
Chess Challenger 7 **£79.00**
Sensory 8 **£119.00**
Sensory Voice **£259.00**

SPECIAL OFFERS:
VOICE CHESS CHALLENGER
Normal Price £245 NOW **£135.00**
SARGON 2.5/BORIS 2.5
Normal Price £273.70 NOW **£199.95**
All prices include V.A.T.

TELETEXT

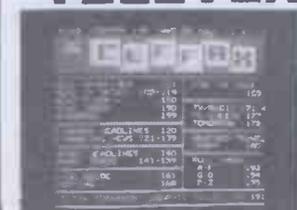

ADD-ON ADAPTOR £199

THE RADOFIN TELETEXT ADD-ON ADAPTOR

Plug the adaptor into the aerial socket of your colour T.V. and receive the CEEFAX and ORACLE television information services.

THIS NEW MODEL INCORPORATES:

- Double height character facility
- True PAL Colour
- Meets latest BBC & IBA broadcast specifications
- Push button channel change
- Unnecessary to remove the unit to watch normal TV programmes
- Gold-plated circuit board for reliability
- New SUPERIMPOSE News Flash facility

SPEAK & SPELL



Normal Price £49.95
NOW REDUCED TO:

£39.50 inc. VAT

Teach your child to spell properly with this unique learning aid. Fully automatic features and scoring. Additional word modules available to extend the range of words.

ADDING MACHINE OLYMPIA HHP 1010



Normal Price £57.21
NOW REDUCED TO:

£34 inc. VAT

Uses ordinary paper
No need to buy expensive thermal paper!
Fast add listing PRINTER/CALCULATOR 2 lines per second, 10 digit capacity.
Uses normal adding machine rolls. Battery or mains operated.
Size 9 1/4" x 4 1/4" x 2 1/4"
(Mains adaptor extra)

24 TUNE ELECTRONIC DOOR BELL



Normal Price £19.70
NOW REDUCED TO:

£12.70 inc. VAT

Plays 24 different tunes with separate speed control and volume control. Select the most appropriate tune for your visitor, with appropriate tunes for different times of the year!

MATTEL T.V. GAME




The most advanced T.V. game in the world. 20 cartridges available. Add-on KEYBOARD coming **£199.95** inc. VAT soon to convert the MATTEL to a home computer with 16K RAM, fully expandable and programmable in Microsoft Basic. Other accessories will be available later in the year.

THE OLYMPIA — POST OFFICE APPROVED

TELEPHONE ANSWERING MACHINE

WITH REMOTE CALL-IN BLEEPER

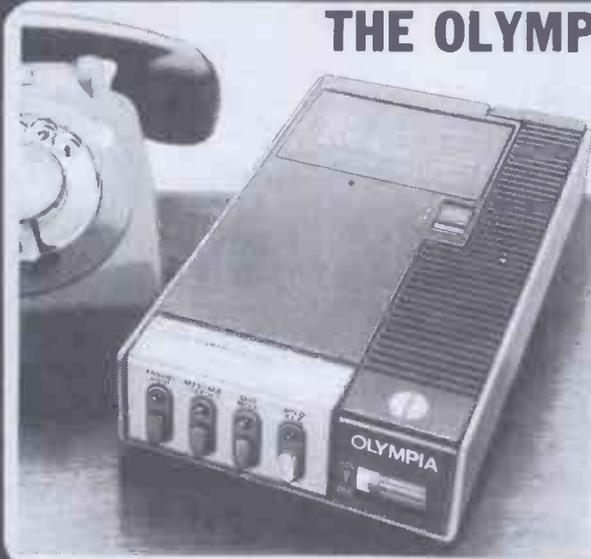

£135 inc. VAT

This telephone answering machine is manufactured by Olympia Business Machines, one of the largest Office Equipment manufacturers in the U.K. It is fully POST OFFICE APPROVED and will answer and record messages for 24 hours a day. With your remote call-in bleeper you can receive these messages by telephone wherever you are in the world. The remote call-in bleeper activates the Answer/Record Unit, which will at your command repeat messages, keep or erase them, and is activated from anywhere in the world, or on your return to your home or office. The machine can also be used for message referral, if you have an urgent appointment, but are expecting an important call, simply record the 'phone number' and location where you can be reached. With optional extra beepers (£13 each) this facility can be extended to colleagues and members of the family. Using a C90 standard cassette you can record as many as 45 messages. The announcement can be up to 16 seconds long and the incoming message up to 30 seconds long.

The machine is easy to install and comes with full instructions. It is easily wired to your junction box with the spare connectors provided or alternatively a jack plug can be provided to plug into a jack socket. Most important, of course, is the fact that it is fully POST OFFICE APPROVED.

The price of £135 (inc. V.A.T.) includes the machine, an extra-light remote call-in Bleeper, the microphone message tape, A/C mains adaptor. The unit is 9 3/4" x 6" x 2 1/4" and is fully guaranteed for 12 months. The telephone can be placed directly on the unit — no additional desk space is required.

FOR FREE BROCHURES — TEL: 01-301 1111



For free illustrated brochures and reviews on our range of electronic games, please telephone 01-301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/BARCLAYCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48hr delivery service available.

CALLERS WELCOME — Demonstrations daily at our Sidcup shop open from 9am-6pm, Monday-Saturday (Early Closing Thursday 1pm - Late opening Friday 8pm)

2 YEAR GUARANTEE — All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee

MONEY BACK UNDERTAKING — If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund

AFTER SALES SERVICE — Available on all machines out of guarantee

COMPLIANT PRICES — we are never knowingly undersold

HELPFUL ADVICE — Available on the suitability of each machine


CREDIT FACILITIES — Full credit facilities available over 12, 24 or 36 months at competitive rates of interest

PART EXCHANGE SCHEME — available on 2nd hand machines

ACCESS — Barclaycard, Owners Clubs, American Express

CREDIT CARDS WELCOME

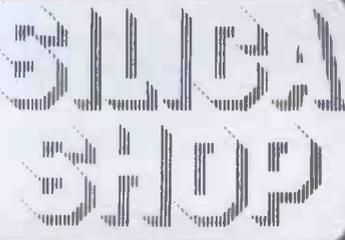SILICA SHOP LIMITED Dept. HE6
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX
Telephone: 01-301 1111 or 01-309 1111



off. This means that it is sometimes difficult to judge exactly where your opponent's car is when you are travelling at very high speeds, so you crash, thinking the car is somewhere else. This game needs quite a lot of skill to play, and is great fun, and a number of people can compete for the best times. This game is the most expensive of the three at £26.95, including VAT.

Jet Fighters

Game number three is Jet Fighters, and it looks like the controls of a missile launcher. The relevance of this will become clear as you read on. The game itself is based on the same concept as Galaxy Invaders. The difference is that the enemy takes the form of jet fighters and warships, and you have a missile

launcher to beat off their attack. Unlike Galaxy Invaders, this game is played sideways-on with your launcher on the right and the enemy coming at you from the left. The principle of the game is to shoot down the jet fighters before they shoot you down or land on your base. The warships appear only momentarily, and then disappear if you don't hit them. Like the Galaxy Invader 1000 game, you gain points which are accumulated on the scoreboard. You score three, two or one points for exterminating a jet fighter, depending on its position on the screen, and 10 points for a warship, up to a maximum of 199 points. There are sound effects built in to simulate explosions etc, and a little tune to signify your destruction or your victory. There is a choice of

skill levels and you can be a Private, Captain or General, which you choose depending on how good you are.

Comparatively speaking, this game did not seem as impressive as the other two. The case is not so well finished and the controls didn't seem terribly accurate. The display flickers rather a lot as well (very straining on the eyes), and although it is very similar to Galaxy Invaders it is not quite so addictive. When your launcher is hit you disappear from the screen for a couple of seconds, so when you reappear you are frequently just in the right place to be hit by another missile! Jet Fighters costs £21.95 and could really do with a few improvements to bring it up to the very high standard of the other two games.

Computer Games Ltd., 214-220 Maybank Rd., Woodford, London E18 1EX (tel 01-504 2255).

Car Radio Do-it-yourself Kit From Blaupunkt

As mentioned in Monitor in the May issue, Blaupunkt (Robert Bosch in the UK) was poised to launch four of its car radio and radio/cassette combinations in do-it-yourself installation packs. The four models, supplied along with loudspeakers, wiring, fitting kits and instructions are the Hamburg, Tempelhof CR, Hamburg CR and Mannheim CR. It was the Mannheim CR that HE had an opportunity to review.

After the contents of the yellow take-away box were emptied out on the carpet (radio, two speakers, leads, plastic fascia panels, packets of screws and knobs and instruction leaflets), we were ready to go.

The car chosen for the installation was a Ford Escort (1600 Sport), which already had a radio installed.

Instructions

It is worth commenting on the main instruction booklet supplied with the kit. This eight-page booklet contains most of the information you are likely to need for the installation, together with some general information. It starts with details of the tools you will need, lists the contents of the box and follows with a teach-in on radio waves, reception and the automatic suppression unit (ASU) included in all Blaupunkt radios and radio/cassette combinations. The



next four pages or so deal with the installation, including 28 illustrations. Radio interference and its suppression is dealt with in the final part of the booklet and diagrams showing how to connect an extra pair of speakers are given on the back page.

Installation

As mentioned earlier, the Escort Sport 1600 comes with a radio fitted (not a particularly good one was fitted to our test vehicle). This made the job easier, because the supply cables, aerial and its cable and the suppression components were already in place.

We could bend the rear retaining lug on the existing metal carrier to allow for the slightly longer case of the Mannheim CR. The components supplied with the kit would have made mounting possible had this 'modification' not been possible.

Once mounted in place on the 1600's plastic dash extension, the various connections were made to the back of the Mannheim CR, including the earth lead supplied with the kit.


With the mounting and wiring completed, the speakers were laid on the floor of the car and the radio was tested on all functions.

BECOME AN INSTANT MUSICIAN NO EXPERIENCE NECESSARY

Create your own music with a VL-TONE. You combine the sound, rhythm and tempo and the VL-TONE plays it back... beautifully!

CASIO VL-TONE (VL-1)

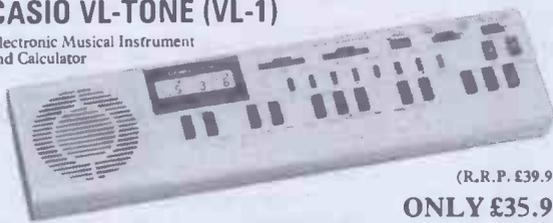Electronic Musical Instrument and Calculator



(R.R.P. £39.95)

ONLY £35.95

VL-1: Utilises Very Large Scale Integrated circuit advanced technology. This complete 29-note synthesiser records and plays back. The octave shift switch expands the range of the keyboard to almost 5 octaves.

Preset sounds: Piano, Violin, Flute, Guitar, Fantasy and ADSR (sound wave that can be varied in over 80 million ways).

Auto play: ONE-KEY or MANUAL playing can be recorded and will be played back in the form of a melody.

Auto rhythm: 10 built-in rhythms, with variable tempo and balance, can be incorporated in manual playing or added to your recording.

Built-in melody: Pre-programmed German Folk Song with rhythm accompaniment. Play it any time and practice tempo changes.

Facilities: LCD numerical display shows pitch, including sharps and programming information. Built-in amplifier and speaker. Output jack.

Calculator: 8 digits, +, -, ×, ÷, square roots, %, and full memory.

Power source: Four AA size batteries or AC adaptor (price £5).

Dimensions: 30mm x 300mm x 75mm (1 1/8" x 11 3/4" x 3").

This compact, battery powered lightweight (438g, 15.4oz.) can be played anywhere.

Available May

A CLASSIC IN ITS TIME

Battery powered, it is ideal for car, caravan, boat, lounge, kitchen, bedroom, office, or as a pocket watch, using the eyelet and leatherette pouch supplied.

PQ-20 ALARM CLOCK

(R.R.P. £14.95)

**ONLY
£12.95**



Large LC Display of full digital time. Symphonic alarm (Mozart, No. 40), or-buzzer, with snooze facility. Hourly time signal option. Integral speaker and amplifier. Rapid setting. Accuracy +/- 15 secs./month. One lithium battery lasts approx. 12 months. Dims.: 9.3 x 108 x 48mm (3/8 x 4 1/4 x 1 7/8"). 53g (1.9oz.).

MA-1 Battery Alarm Clock

Similar to PQ-20 but has blue LC display, nightlight, 3-position volume control. 3 AA batteries last 15 months approx. Dims.: 43 x 115 x 76mm (1 3/4 x 4 1/2 x 3 inches). Ivory coloured case. (R.R.P. £11.95) **ONLY £9.95.**

OUR BEST-SELLING SCIENTIFIC

CASIO FX-3500P

Statistical regression and integrals. Non-volatile memories and stores. 38 functional (non-volatile) steps. 2 programme storage capability. Unconditional and conditional jumps, 7 (non-volatile) memories; one independent, 6 constant memories. 18 pairs of parenthesis, nestable in 6 levels.

61 built-in functions, including: Integrals (Simpson's rule). Linear regression, logarithmic regression, exponential regression and power regression.

Hyperbolics, sexagesimal and co-ordinates conversions.

10 digit mantissa or 10 + 2 exponent. Two silver oxide batteries give approximately 1,000 hours' continuous use with power-saving automatic cut-off, with data and memory protection.

Dims.: 9/32 x 2 7/8 x 5 1/4 inches. Supplied with leatherette wallet.

ALL THIS FOR ONLY £22.95*

* PRICES

We will BEAT any lower advertised price by 5% providing we still make a profit! Prices include V.A.T. and P. & P. Return of post service subject to availability. Send your order FREE: POST; no stamp required.

Send cheques, P.O., or phone your ACCESS or BARCLAYCARD number to:

TEMPUS

Dept. HE, FREEPOST
164-167 East Road
Cambridge CB1 1DB
Tel. 0223 312866

THESE SPACE INVADERS WILL ALARM YOU

The price won't

CASIO'S MOST AMAZING WATCHES EVER

Display: Hours, minutes, seconds, a.m./p.m., day and date. 12- or 24-hour format.

Auto Calendar: Day, date, month, year.

Alarm: 24-hour, with "on" symbol.

Hourly Chimes: Time signal every hour, on the hour. Easily switched on or off.

Professional Stopwatch: Lap times, etc., from 1/100 second to 24 hours.

Dual Time: Second time zone.

Calculator: 8 digits, four functions, with constants and display symbols, and FINGER-TOUCH KEYBOARD.

DIGITAL SPACE INVADER GAME with sound effects and scoring.

Water resistant case. Mineral glass.

CA-90: 46 x 36 x 10.55mm. Black resin.

CA-901: 40.5 x 35.2 x 10.5mm. Metal.



CA-901 (R.R.P. £34.95)

ONLY £29.95



The random digital invaders attack from the bottom right and move across the display. Every time you tap AIM your missile number, top right, progresses by 1. When your missile number coincides with an invader, tap FIRE and that spaceship will disappear, adding to your score. The game is over if 3 of the 16 spaceships in an encounter penetrate your defences.

There are 2 stages, each stage having 9 encounters. In stage 1 the game speeds up with each encounter and in stage 2 the invaders attack from a closer position. After stage 2 the game reverts to stage 1 but the score, displayed after each encounter, is incremental.

CA-90 (R.R.P. £27.95)

ONLY £24.95

SUMMER TIME!

Now is the time to buy a Sports Watch for your holidays and outdoor activities. These models (except HV027) are WATER-RESISTANT TO 100 METRES and suitable for swimming, snorkelling, sailing and most other outdoor sports.

SEIKO DUAL DISPLAY

Analogue display of time with sweep second hand. Independent digital display of time (12- or 24-hour format); day/date calendar; 24-hour alarm function; hourly time signal; 1/100 second stopwatch. Instant setting. Luminous dial. 2-year battery life. Battery life indicator. Stainless steel case. HARDEX glass. JET 088. Black outer bezel. 100-metre W/R case, 36 x 40 x 9mm approx.

JET 088

100m
Water Resistant

**SAVE
£35!**

**ONLY
£94.50**



HV027

Water
Resistant

**SAVE
£17!**

**ONLY
£72.50**



CASIO ALARM CHRONOGRAPHS

100-metre water resistant



W150C
Stainless-
steel case
black resin
strap
£25.95



W150
All stainless
steel
£32.50



W100
All black
moulded
resin
£19.95

All have an easily-read display of full time and calendar, with half-hourly time signals which can be switched on or off. Easy-to-use functions include: 24-hour alarm. Professional stopwatch measuring lap times, etc., to 1/100 second. Countdown alarm timer with repeater memory function. The time is always visible regardless of the display mode. One-touch selection of 12- or 24-hour format. Micro light for night viewing. ±15 seconds/month accuracy. Amazing 5-year battery life. 9.65mm thick case with mineral glass face.

Loudspeaker Mounting

Under Loudspeaker Fitting in the instructions, the opening paragraph begins: 'Great care must be taken in fitting the loudspeakers'. The choice was in the rear parcel shelf, in the kick pads in the driver and passenger footwell areas or in the doors. The instructions then say: 'If the door assembly can accommodate the depth of the speaker then this is a particularly good place to site them since the door area acts as a sound chamber'.

Fine, we thought, the doors are where they shall be fitted. Investigation showed the depth to be right, so the panel was removed, marked out and a hole was cut using the paper template supplied with each speaker as a guide. A convenient hole was found in the door (made by the undersealers) for the cable and everything went like a dream — until we came to fit the window-winding handle. We discovered what many a motorist has discovered too late; that is, when the speaker cover was snapped into place, it was too proud to miss being caught by the inside edge of the handle as it was rotated. The choice was simple: either leave the handle off, or remove the speaker. We took the second choice and were left with a hole in the door.

On Test

With a couple of box-mounted

speakers, the Mannheim CR performed well. Apart from the fact that it does not have push-button station selection, the sound quality was very pleasant and of adequate volume. Pressing the Db noise limiter button helps to cut down noise from cassettes.

Problem Solving

HE spoke to Robert Bosch about the speaker problem. Surely flush-mounting speakers could have been supplied with the kit? Ron Sherwood, UK product manager of Robert Bosch, said that flush-mounting speakers from the Quick Fit range had been considered, but they were more expensive. Quick Fit model 723 speakers cost £9.55 plus VAT each, compared with £6.15 plus VAT for each of the model 555 speakers supplied with the kit.

So, if you want to fit door-mounted speakers, beware: check that you have sufficient clearance between the window-winding handle and your speaker. Alternatively, you could buy the Quick Fit 723s at extra cost and, as Ron Sherwood suggested, use the speakers supplied with the kit to make up a four-speaker system.

The 723s, by the way, are only available through specialist outlets for Blaupunkt. We'll try and report on a pair in the next GG&K supplement.

specific openings and simple position verification.

The pieces are of the peg variety, fitting into holes on the chessboard with extra holes for the captured pieces in a game. Positions and moves are entered using the multi-function keyboard and the whole thing is protected with a tinted plastic cover which clips onto the base during play.

In use, the Chess Traveler is simple and straightforward as far as keying in the moves is concerned. Unfortunately the pieces themselves are quite small and awkward to move — they fit rather snugly in the holes, which, although of obvious

Blaupunkt Kits

A rough guide to the radios in the four kits is given below.

Hamburg

An AM car radio. The Hamburg has five push-buttons for station selection, one for long wave and four for medium wave. Power output is 7 W and it has a variable tone control. Kit cost is around £53.50 plus VAT.

Tempelhof CR

An AM car radio with stereo cassette player. The Tempelhof CR has manual tuning of medium and long wave. Power output is 9 W/channel and it has a variable tone control. The cassette player has electronic speed control, lock-on fast forward wind and rewind and cassette ejection. It switches to radio when the tape ends. Kit cost is around £88.60 plus VAT.

Hamburg CR

An AM car radio with stereo cassette player. The Hamburg CR has push-button selection of five medium wave stations and one long wave station. Output power is 9 W/channel and it has a variable tone control. Cassette player functions are as the Tempelhof CR but the cassette player has a luminescent aperture outline for easier access in darkness. Kit price is around £113.60 plus VAT.

Mannheim CR

An AM/FM car stereo radio and stereo cassette combination. The Mannheim CR has manual station tuning on long, medium and VHF wavebands. Output power is 9 W/channel and it has a variable tone control. Cassette functions are as the Tempelhof CR and Hamburg CR. It features a push-button Db Noise Limiter system for use on cassette playback. Kit price is around £122.70 plus VAT.

Robert Bosch Ltd., PO Box 166, Rhodes Way, Watford WD2 4LB (tel 92 44 233).

Moves On The Move

With many people contemplating summer holidays at the moment, the Chess Traveler has appeared on the market at just the right time. This is a machine to while away the long hours of your journey to the sun!


It is a small hand-held chess computer, and as its name suggests is suitable for playing more or less anywhere. It runs for 9 to 10 hours on alkaline batteries, or a mains adaptor is available as an optional extra. The price is £39.95 plus a further £4.95 for the adaptor.

This machine has all the functions you would expect to find on many of the larger machines, including eight skill levels, castling, pawn promotion, and en passant. It accepts special board positions and solves mate-in-two problems, as well as having a multi-move key for

advantage in a portable chess machine, means that you tend to knock the surrounding pieces off the board when you make a move! The pieces are also not very easy to identify. For example, the bishops and the pawns are very similar.

In all, this would be quite a nice machine for a beginner to learn on as it is straightforward to use, but it's also capable of playing a mean game of chess at its higher levels. Despite any reservations about the pieces it is probably the best sort of design for balancing on your knee as you're whizzing through the verdant countryside on an Inter-City 125!

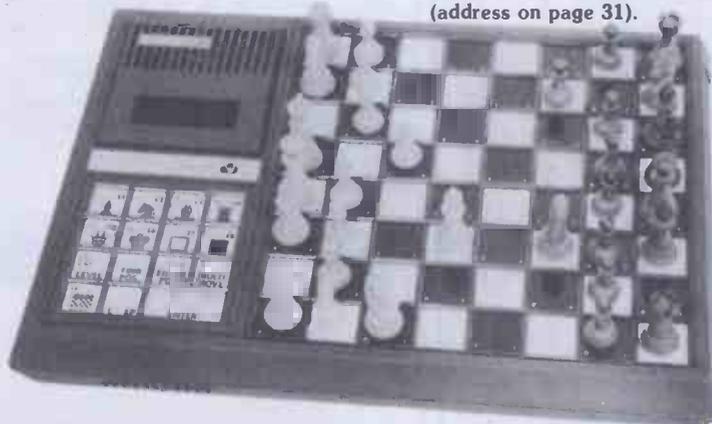Chess Traveler is available from Silica Shop (address on page 31).



HE

PLUGS AND SOCKETS

1625	2mm Plug RED	£0.16
1626	2mm Plug BLACK	£0.16
1628	2mm Socket RED	£0.16
1629	2mm Socket BLACK	£0.16
1634	4mm Plug BLACK	£0.16
1637	4mm Plug RED	£0.16
1640	4mm Socket BLACK	£0.16
1643	4mm Socket RED	£0.16
1652	2 Pin DIN Chassis Socket	£0.08
1654	5 Pin 180° DIN Chassis Socket	£0.12
1655	5 Pin 240° DIN Chassis Socket	£0.12
1656	2.5mm Chassis Socket	£0.10
1657	3.5mm Chassis Socket	£0.10
1658	Metal Std. Jack Chassis Socket (mono)	£0.18
1659	Metal Std. Jack Chassis Socket (stereo)	£0.24
1660	Single Phono socket	£0.09
1661	Double Phono Socket	£0.12
1662	Coax surface socket	£0.22
1663	Coax Flush Socket	£0.22
1664	Plastic Std. Jack Socket (mono)	£0.20
1665	Plastic Std. Jack Socket (stereo) for headphones	£0.32
1666	Car Aerial Chassis Socket	£0.18
1667	AC Chassis Socket	£0.16
1668	4 Way Phono Chassis Socket	£0.22
1669	Plastic Std. Jack Chassis socket stereo switched	£0.32
1670	AC switched non rev. socket	£0.32
1672	2 Pin DIN line socket	£0.10
1674	5 Pin 180° DIN line socket	£0.17
1675	5 Pin 240° DIN line socket	£0.20
1676	2.5mm Plastic line socket	£0.12
1677	3.5mm Plastic line socket	£0.12
1678	Std. jack plastic line socket (mono)	£0.17
1679	Std. jack metal line socket (mono)	£0.30
1680	Std. jack plastic line socket (stereo)	£0.22
1681	Std. jack metal line socket (stereo)	£0.38
1682	Phono in line metal socket	£0.16
1684	Coax line socket	£0.34
1685	Coax back-back socket	£0.14
1686	AC line socket (2 pin USA Type)	£0.18
1687	Phono in line plastic socket	£0.12
1688	Phono back-back socket	£0.20
1689	2 Pin DIN plug	£0.10
1692	5 Pin 180° DIN plug	£0.14
1693	5 Pin 240° DIN plug	£0.14
1696	2.5mm Plug (Metal)	£0.15
1697	3.5mm Plug (Plastic)	£0.12
1698	3.5mm Plug (Metal)	£0.16
1699	Std. Plastic Jack Plug (Mono)	£0.30
1700	Std. Metal Jack Plug (Mono)	£0.30
1701	Std. Metal Jack Plug (Stereo)	£0.35
1702	Plastic Phono Plug	£0.11
1703	Car Aerial Plug	£0.24
1704	Coax TV Plug	£0.22
1705	Right Angle Jack Plug (Mono)	£0.20
1706	2.5mm Plastic Plug	£0.12
1707	Std. Plastic Jack Plug (Stereo)	£0.22
1708	Metal Phono Plug	£0.14
1709	2.1mm DC Plug	£0.12
1710	2.5mm DN Plug	£0.12
1711	AC Plug (2 pin USA Type)	£0.16
1712	AM Aerial Plug	£0.17
1713	Cassette AC Input Plug	£0.15
1714	FM Aerial Plug	£0.13
1715	PL 259 Plug	£0.40
1716	SO239 Socket 4 hole fixing	£0.38
1717	SO239 Socket single hole fixing	£0.40
1718	PL259 Double Ended Female Coupler	£0.40
1719	NC555 Reducer for PL259 (Small)	£0.16
1720	NC556 Reducer for PL259 (Large)	£0.16
1721	M359 Right Angle Coupler PL259 SO239	£0.75
1722	M358 T Connector Female-Male-Female	£0.85
1723	NC583 Inline Coupler PL259 x 2	£0.60
1724	BNC15 50 ohm standard plug	£0.64
1725	BNC1502 Chassis mounting socket	£0.75
1726	BNC1503 Chassis mounting socket single hole fixing	£0.70
1727	BNC1520 BNC male to SO239 female	£0.85
1728	BNC1521 BNC female to PL259 male	£0.85
1729	Junction Box one in two out	£0.80
1730	Low loss splitter	£1.00

AERIALS		
105	Adjustable Aerial Gutter Mount	£3.00
106	C.B. Mobile Antenna	£9.50
107	FM Indoor Ribbon Aerial	£0.50
108	4 Section Car Aerial (Stainless)	£2.16
109	4 Section Car Aerial (Chrome)	£1.80
110	8 Section 1200mm Telescopic Aerial	£2.00
111	8 Section 750mm Telescopic Aerial	£2.60
112	5 Section 570mm Telescopic Aerial	£2.64
113	Roof Mounting Aerial	£3.80

AUDIO LEADS		
114	5 pin-3.5mm 3 & 5 connected	£0.65
115	5 pin-3.5mm 1 & 4 connected	£0.65
116	Car Aerial Ext. Lead	£1.00
117	Mains Cassette Lead	£0.48
119	2 x 2 pin plug in In Line Stereo Jack Socket	£0.74
120	Universal Car Adaptor Plug	£0.52
122	20ft. Coiled Guitar Lead	£0.72
125	5 pin to 5 pin DIN	£0.65
126	5 pin to DIN to open ends	£0.65
127	5 pin to DIN to 4 Phono Plugs	£1.00
128	5 pin Plug to 5 pin socket	£0.75
129	5 pin to 5 pin Plug (Mirror image)	£0.72
130	2 pin Plug to 2 pin Line Socket 5 mtrs.	£0.55
132	2 pin Plug to 2 pin Line Socket 10 mtrs.	£0.85
133	5 pin Plug to Phono Plug	£0.65
136	Headphones ext. lead 7 mtrs.	£1.50

DON'T FORGET YOUR NEW BI-PAK CATALOGUE! OUT NOW! ONLY 75p PLUS 25p P.&P.

COMPONENT PACKS

C26	300 Preformed carbon resistors mixed 1-10w	£1.00
C27	50 2-10 watt wire wound resistors mixed	£1.00
C28	300 Approx Resistors mixed values (count by weight)	£1.00
C29	200 Approx Capacitors mixed values and types (count by weight)	£1.00
C30	50 Precision Resistors 1-5% tol	£1.00
C31	100 Approx 1/8 watt min Resistors mixed values	£1.00
C32	6 Pieces Ferrite Rods	£1.00
C33	60 Metres Single strand wire assorted colours	£1.00
C34	15 Reed switches glass type	£1.00
C35	5 Micro switches assorted types including min.	£1.00
C36	6 Assorted Audio jack sockets and plugs	£1.00
C37	100 Disc ceramic caps mixed values	£1.00
C38	20 Assorted pots	£1.00
C39	40 C280 type capacitors metal foil	£1.00
C40	60 Electrolytics assorted	£1.00
C41	50 Assorted polyester/polystyrene	£1.00
C42	60 Low voltage Electrolytics mixed values up to 10v.	£1.00
C43	15 Assorted slider pots	£1.00
C44	10 Dual gang pots log and lin assorted	£1.00
C45	1 Pack assorted Handwired pots/bolts etc.	£1.00
C46	10 Assorted switches slide/rocker/mains	£1.00
C47	3 Relays 24v coil	£1.00
C48	20 Assorted knobs push, screw and slider types	£1.00
C49	20 Assorted Tag strips and panels	£1.00
C50	4 Wave change switches rotary	£1.00
C51	1 Pack of assorted PVC sleeving and markers	£1.00
C52	100 4 Watt resistors mixed values	£1.00
C53	35 Presets assorted type and values	£1.00
C54	40 Metres stranded wire assorted colours	£1.00
C55	10 Assorted Din/sockets/Coax/speakers/phone	£1.00
C56	10 Assorted plugs Din/coax/speakers/etc.	£1.00
C57	10 Metres assorted cable. Mains/speaker/coax/microphone	£1.00
C58	100 sq in copper clad board single side paper	£1.00
C59	75 sq in copper clad fiberglass board	£1.00

BABANI BOOKS

No.	TITLE	PRICE
BP160	Coil Design and Construction Manual	1.25
BP202	Handbook of Integrated Circuits (IC's) Equivalents & Substitutes	1.45
BP205	First Book of Hi-Fi Loudspeaker Enclosures	0.95
BP207	Practical Electronics Science Projects	0.75
BP208	Practical Stereo and Quadraphony Handbook	0.75
BP211	First Book of Diode Characteristics Equivalents and Substitutes	1.25
BP213	Electronic Circuits for Model Railways	1.00
BP214	Audio Enthusiasts Handbook	0.85
BP218	Build Your Own Electronic Experiments Laboratory	0.85
BP219	Solid State Novelty Projects	0.85
BP220	Build Your Own Solid State Hi-Fi and Audio Accessories	1.25
BP221	28 Tested Transistor Projects	1.25
BP222	Solid State Short Wave Receivers for Beginners	1.25
BP223	50 Projects Using IC CA3130	1.25
BP224	50 CMOS IC Projects	1.25
BP225	A Practical Introduction to Digital ICs	1.25
BP226	How to Build Advanced Short Wave Receivers	1.20
BP227	Beginners Guide to Building Electronic Projects	1.25
BP228	Essential Theory for the Electronics Hobbyist	1.25
BP5	Engineers and Machinists Reference Tables	0.70
BP7	Radio and Electronic Colour Codes and Data Chart	0.35
BP14	Second Book of Transistor Equivalents and Substitutes	1.10
BP23	First Book of Practical Electronic Projects	0.75
BP24	52 Projects Using IC41	0.95
BP27	Grant Chart of Radio Electronic Semiconductor and Logic Symbols	0.60
BP28	Resistor Selection Handbook (International Edition)	0.60
BP29	Major Solid State Audio Hi-Fi Construction Projects	0.85
BP32	How to Build Your Own Metal and Treasure Locators	1.35
BP33	Electronic Calculator Users Handbook	1.25
BP34	Practical Repair and Renovation of Colour TVs	1.25
BP35	Handbook of IC Audio Pre-amplifier & Power Amplifier Construction	1.25
BP36	50 Circuits Using Germanium, Silicon and Zener Diodes	0.75
BP37	50 Projects Using Relays, SCRs and TRIACs	1.25
BP38	Fun and Games with Your Electronic Calculator	0.75
BP39	50 (FET) Field Effect Transistor Projects	1.50
BP40	Digital IC Equivalents and Pin Connections	2.50
BP41	Linear IC Equivalents and Pin Connections	2.75
BP42	50 Simple L.E.D. Circuits	0.95
BP43	How to Make Walkie-Talkies	1.75
BP44	IC555 Projects	1.25
BP45	Projects in Opto-Electronics	1.35
BP46	Radio Circuits Using ICs	1.25
BP47	Mobile Discotheque Handbook	1.35
BP48	Electronic Projects for Beginners	1.35
BP49	Popular Electronic Projects	1.45
BP50	IC LM3900 Projects	1.35
BP51	Electronic Music and Creative Tape Recording	1.25
BP52	Long Distance Television Reception (TV-DX) for the Enthusiast	1.95
BP53	Practical Electronic Calculations and Formulae	1.25
BP54	Your Electronic Calculator and Your Money	1.75
BP55	Radio Stations Guide	1.45
BP56	Electronic Security Devices	1.75
BP57	How to Build Your Own Solid State Oscilloscope	1.50
BP58	50 Circuits Using 7400 Series ICs	1.35
BP59	Second Book of CMOS IC Projects	1.50
BP60	Practical Construction of Pre-amps, Tone Controls, Filters & Attn.	1.45
BP61	Beginners Guide to Digital Techniques	0.95
BP62	Elements of Electronics - Book 1	2.25
BP63	Elements of Electronics - Book 2	2.25
BP64	Elements of Electronics - Book 3	2.25
BP65	Single IC Projects	1.50
BP66	Beginners Guide to Microprocessors and Computing	1.75
BP67	Counter, Driver and Numerical Display Projects	1.75
BP68	Choosing and Using your Hi-Fi	1.65
BP69	Electronic Games	1.75
BP70	Transistor Radio Fault-Finding Chart	0.50
BP71	Electronic Household Projects	1.75
BP72	A Microprocessor Primer	1.75
BP73	Remote Control Projects	1.95
BP74	Electronic Music Projects	1.75
BP75	Electronic Test Equipment Construction	1.75
BP76	Power Supply Projects	1.75
BP77	Elements of Electronics - Book 4	2.95
BP78	Practical Computer Experiments	1.75
BP79	Radio Control for Beginners	1.75
BP80	Popular Electronic Circuits - Book 1	1.95

BUDGET STEREO HEADPHONES

BLACK WITH PADDED EARCUPS
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
30-18,000 HZ
WEIGHT 300gms O/N 885 £4.20

GOOD QUALITY STEREO HEADPHONES

DOUBLE PADDED HEAD BAND
CIRCULAR VENTED PADDED
EARPIECES
BLACK AND ALUMINIUM FINISH
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
20-19,000 HZ
WEIGHT 350 gms O/N 884 £8.25

SUPERIOR QUALITY STEREO HEADPHONES

WIDE BLACK PADDED HEAD
BAND AND MATT
ALUMINIUM EARCUPS
IMPEDANCE 8 ohms
FREQUENCY RESPONSE
15-25,000 HZ
WEIGHT 290 gms O/N 883 £15.85

ENAMEL COPPER WIRE 2 oz.

365	40 swg	£1.00
366	38 swg	£0.88
367	36 swg	£0.90
368	34 swg	£0.82
369	32 swg	£0.80
370	30 swg	£0.76
371	28 swg	£0.74
372	26 swg	£0.74
373	24 swg	£0.66
374	22 swg	£0.62
375	20 swg	£0.60
376	18 swg	£0.60
377	16 swg	£0.52
378	14 swg	£0.52

TINNED COP. WIRE 4oz.

379	24 swg	£0.94
380	22 swg	£0.83
381	20 swg	£0.88
382	18 swg	£0.90
383	16 swg	£0.78

HARDWARE IN PACKS OF 25

839	OBA 1/4in. Bolt	£0.70
840	OBA 1/2in. Bolt	£0.40
842	2BA 1in. Bolt	£0.35
843	2BA 1/2in. Bolt	£0.30
844	2BA 3/4in. Bolt	£0.32
345	4BA 1/4in. Bolt	£0.28
846	4BA 1/2in. Bolt	£0.20
847	4BA 3/4in. Bolt	£0.18
848	6BA 1/4in. Bolt	£0.24
849	6BA 1/2in. Bolt	£0.18
850	6BA 3/4in. Bolt	£0.20
851	OBA Solder Tags	£0.20
852	2BA Solder Tags	£0.16
853	4BA Solder Tags	£0.14
854	6BA Solder Tags	£0.12
855	OBA Full Nut	£0.42
856	2BA Full Nut	£0.26
857	4BA Full Nut	£0.18
858	6BA Full Nut	£0.18
859	OBA Washer	£0.12
860	2BA Washer	£0.09
861	4BA Washer	£0.09
862	6BA Washer	£0.09

FUSE HOLDERS

506	20mm Chassis Fuse Holder	£0.14
507	1 1/4in. Chassis Fuse Holder	£0.14
508	1 1/4in. Car in line Fuse Holder	£0.12
509	20mm Panel Fuse Holder	£0.26
510	1 1/2in. Panel Fuse Holder	£0.32

TRANSFORMERS

2021	6-0-6v 100mA	£0.90
2022	9-0-9v 100mA	£0.90
2023	12-0-12v 100mA	£1.15
2024	0-6v 0-6v, 280mA	£1.60
2025	0-12v 0-12v 150mA	£1.30
2026	6-0-6v 1 Amp	£2.40
2027	9-0-9v 1 Amp	£2.00
2028	12-0-12v 1 Amp	£2.50
2029	15-0-15v 1 Amp	£2.75
2031	Multi tap 5 Amp	£3.40
2032	Multi tap 3 Amp	£4.80
2033	Multi tap 2 Amp	£6.40
2034	0-35v 17 Amp	£4.90
2035	0-55v 2 Amp	£6.65
2036	0-17v 750mA	£2.85
2037	Min Audio output	£0.25
2038	Min Audio Driver	£0.36
2040	0-45-55v 1.5 Amps	£6.45
2041	0-55-65v 2 Amp	£8.45
2042	0-25v 2 Amps	£4.50
2043	15-0-15 150mA	£2.40

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182. All prices exclude V.A.T., add 50p postage per order. Terms: C.W.O., cheques, Postal Orders payable to Bi-Pak.

Building Site

This month, Keith Brindley proves how easy it is to give your projects a professional appearance. Front panel lettering is easy when you know how

A FINISHED PROJECT is only as good as it looks. It doesn't matter how well it works, how undistorted a thingummy is or how many flashing LEDs an electronic wotsit has got, if it doesn't look good. I mean you can't show it off to the neighbours or to friends if it looks as though it has been dragged through an electrified barbed wire fence backwards, can you? It's the finishing touches which make or break the appearance of your project.

One of the best ways to 'professionalise' your project is to label it, showing the functions of all switches, pots etc, and to give it an individual title. Take a look at some of the projects in HE this month and imagine them without labelling — see what I mean?

How Do We Do It?

We label all our projects by making use of dry transfer lettering systems. A variety of types can be seen in Fig.1. Letraset, Chartpak, Mecanorma and Blick are just a few of the trade names you will find associated with dry transfer systems. Many readers will know what they consist of — semi-opaque or transparent film sheets, with dry ink letters on the underside. The idea is to lay the sheet on the surface to be lettered and then to rub down the required letter, transferring it from the sheet onto the surface. That's all there is to it really.

You should be able to buy at least one variety of dry transfers at any graphics or drawing office supplier. A lot of booksellers also sell them, so you probably won't have to go far to get what you want.

There are literally hundreds of different typefaces (styles of letters) to choose from. The most popular ones are



Figure 2. Transferring characters from the sheet to the front panel. Here a burnisher is shown in use

duplicated on all manufacturers' systems. The typefaces we use most on our projects are Eurostyle Bold and Eurostyle Bold Extended. But *you* don't have to use the same type. In fact you can 'personalise' your project by using a typeface of your own choice.

You can also choose the size of the letters which suits you best. The letters are measured by what is known as their point size (for example, 12pt and 20pt). As a general guide, the larger the point size, the larger the letter. We normally use 10pt for labelling around switches and knobs, and 18pt for titles, etc. A single sheet of each size will provide sufficient letters and numbers for quite a few projects.

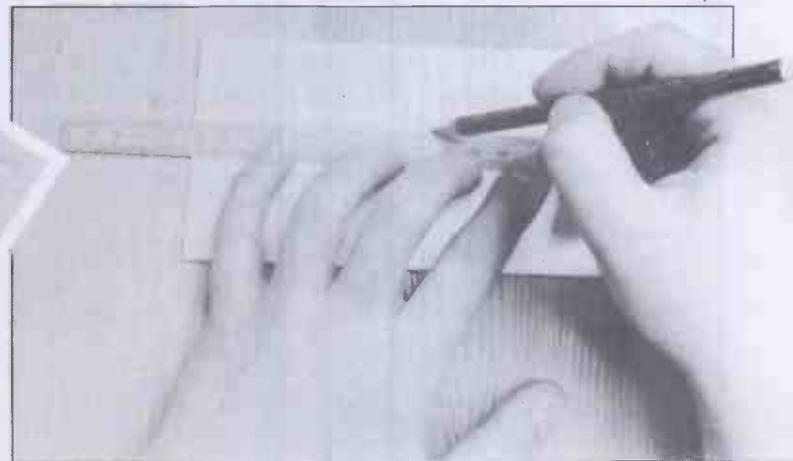
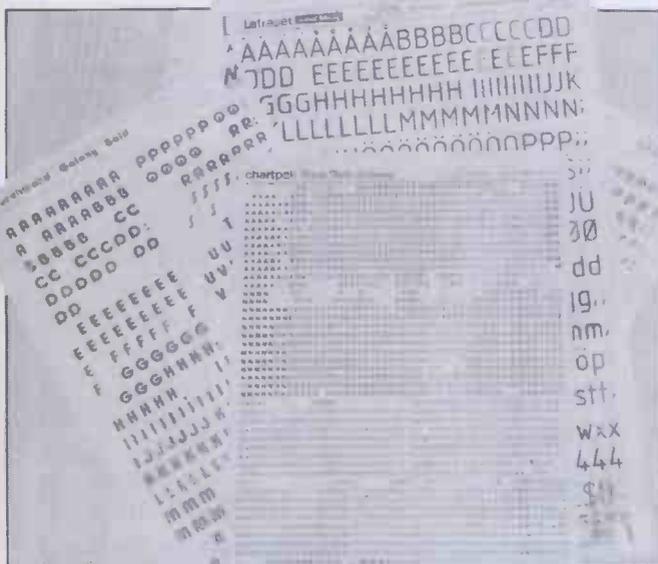


Figure 1. Examples of sheets of lettering suitable for your projects

Figure 3. To keep the character in a straight line, draw guidelines as shown to line up with the top and bottom of each character

How Do You Do It?

After you have reached the completion stages on any metalwork on the panel, such as drilling or filing, make sure the panel is grease-free — a quick wipe with a rag dampened with methylated spirits will ensure this.

Now you simply lay the sheet over the panel and position the letter you require over the correct place. By rubbing lightly with a soft pencil or, better still, a tool called a burnisher, the letter can be transferred onto the panel, as Fig.2 shows.

If you find it difficult to line up the letters, a good tip is to use a guideline. With a ruler and a sharp soft pencil simply draw lines across the panel, as in Fig.3, at every necessary height where letters are planned. Lining up is easy after this as you just position each letter slightly above the pencil line before rubbing down.

Don't worry if you make a mistake and put a letter in the wrong place, or mis-spell a word, because you can remove the boo-boo by covering it with a small piece of Sellotape and then sharply pulling the tape off. The letters will stick to the adhesive backing of the tape leaving a clear panel again.

When transferring long words, or words positioned above or below switches and knobs, it's a good idea to start with the middle letter of the word and then work backwards and forwards until the word is complete. This makes sure that the word is central and looks correct.

After you have finished labelling the panel you carefully remove the pencil lines with a good clean rubber, as in Fig.4. Make sure you don't catch any of the letters with the rubber, or you'll have to start again!

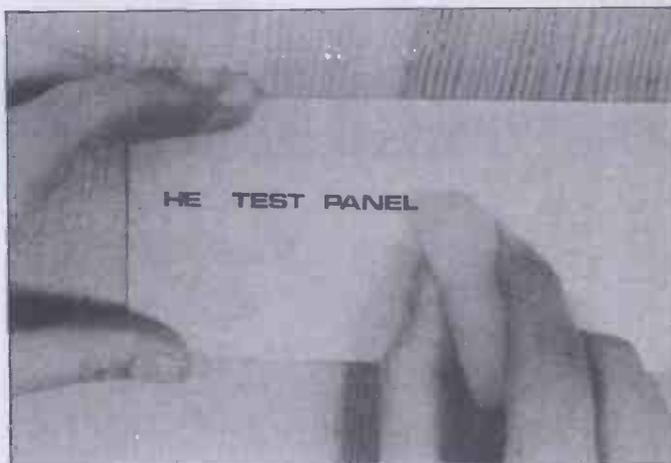


Figure 4. Great care is needed when erasing your guidelines to avoid damaging the lettering. Make sure that your rubber is soft, clean and has a sharp edge

Finally, to protect the letters and also the panel from accidental damage from scratching, spray it with an aerosol fixing spray. You'll find a suitable variety to choose from at the supply shop where you got your transfer sheets.

Now you can stand back and admire your project. See you next month.

HE

BRITAIN'S FIRST NATIONAL CB SHOW!

ROYAL HORTICULTURAL SOCIETY'S NEW HALL,
WESTMINSTER
(SEPTEMBER 11th —
13th INCLUSIVE)



September looks like being a good month for CB'ers! Modmags is making it better yet by bringing you Britain's first ever NATIONAL Citizens' Band exhibition. Companies from all over the country will be displaying their wares for you to peruse. Everything from rigs, monitors and aerials, down to components and fixing brackets, will be on show. All the latest gear will be here — some of it for the FIRST TIME IN THE UK.

WHY QUEUE? ORDER YOUR TICKETS NOW FROM:-

Advance Tickets CB81
Modmags Ltd, 145 Charing Cross Road,
London WC2H 0EE.

Please send tickets @ £2.00

..... tickets @ £1.00 (OAP or child under 10 yrs)

To

.....

.....


I enclose PO/cheque for £

This is the BIG ONE for breakers. Whether you're a confirmed fanatic or an interested beginner, this is the place to be in September!

OPENING TIMES

Friday 11th Sept 10am-7pm
Saturday 12th Sept 10am-6pm
Sunday 13th Sept 10am-4pm

THE NEW AND UNIQUE VEROBLOC

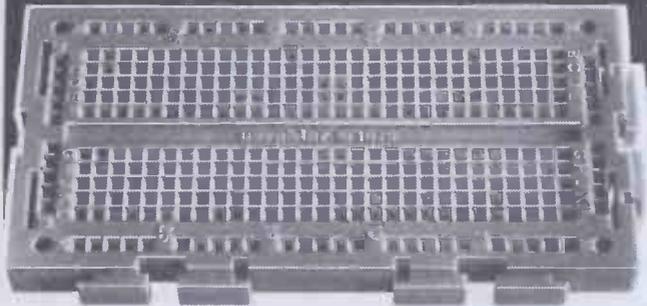


ADDS TO YOUR CAPABILITY

Already used in industry, this solderless breadboard is now available to the hobbyist. Unique because of its universal interlocking facility meaning you no longer need lots of different boards.

Send now for the unique Verobloc.

Order code 200-21092G. £4.16p inclusive.

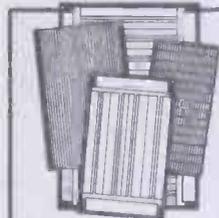

**AND VERO HAVE
ADDED TO THEIR
TRADITIONAL RANGE
OF HIGH QUALITY
BOARDS,
ALSO EX-STOCK.**

No.	Order Code	Description	Size (mm)	Price
1)	10-2845B	Microboard	160 x 100	5.66
2)	10-2846H	Microboard	160 x 233.4	12.41
3)	200-21084E	V-Q Board	147.83 x 73.66	1.65
4)	09-2196L	Veroboard	160 x 100	1.63

Carriage & VAT included.

Vero Electronics Limited, Retail Dept., Industrial Estate,
Chandler's Ford, Hampshire SO5 3ZR. Tel (04215) 62829

State quantity and order codes required

Name

Address


I enclose Cheque/PO for £ _____ or debit my Barclay Card/

Access No

Exp. date

vero

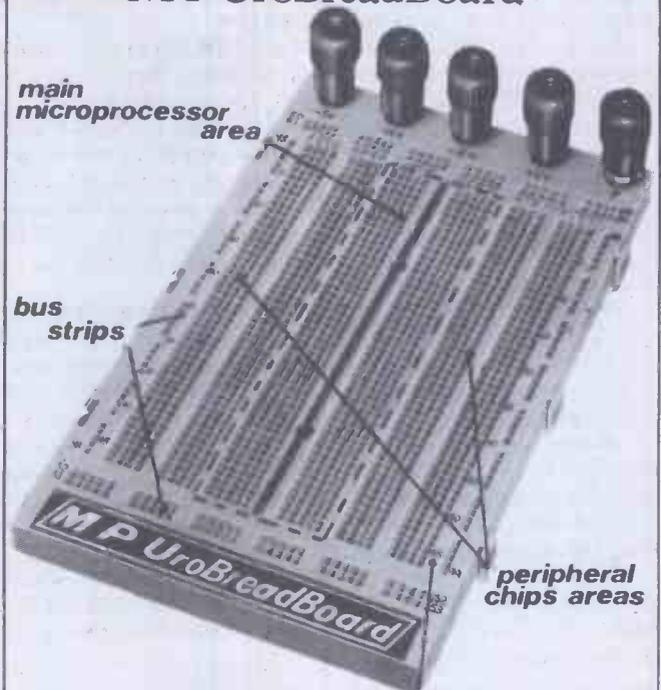If you're into
MICROPROCESSORS
then they should be into an
MP UroBreadBoard



alpha numeric indexing

- * MPU Section accepts 24, 28, 40 & 64 pin DIL microprocessors
- * Auxiliary Areas accept any .3" or .6" RAM, ROM or peripheral chip
- * Power Bus Strips on all sides
- * 5 incoming turret Power Terminals
- * Component Support Bracket included
- * Over 1400 contact points
- * Alpha-Numeric column and row indexing
- * Eurocard size (160mm x 100mm)
- * Slots onto all BIMBOARDS
- * Non-Slip rubber backing
- * Ideal for schools and colleges
- * Long life, <10m.ohms, nickel silver contacts

The PROFESSIONALS breadboard
that BEGINNERS can start on

BOSS INDUSTRIAL MOULDINGS LTD

2 Herne Hill Rd, London SE24 0AU, England
Telephone 01-737 2383 Telex 919693
Cables & Telegrams: LITZEN LONDON SE24

Please send me . . . MPUroBreadBoard(s) @ £18.

This price includes VAT & PP, is applicable from Mar. 1, '81, but please add 15% for Overseas Orders, make cheques/P.O. payable to BOSS Industrial Mouldings Ltd and allow 10 days for order processing and cheque clearance etc.

I enclose a cheque/P.O. to the value of £.....

Name

Company

Address

Telephone Number

HE681

Books from the HE Book Service

SPECIAL OFFER TO READERS OF HOBBY ELECTRONICS ONLY

ELEMENTS OF ELECTRONICS
 Book I £2.60
 Book II £2.60
 Book III £2.60
 Usual price is £7.80 inc post and packing for 3 volume set. OUR PRICE £7.00 + FREE slip case for 3 volumes + FREE Resistor Colour Code Disc.

28 TESTED TRANSISTOR PROJECTS by R. Torrens £1.50

The author has designed developed and built some completely new circuits.

BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS by R. A. Penfold £1.50
 Enables the complete beginner to tackle the practical side of electronics.

ESSENTIAL THEORY FOR THE ELECTRONICS HOBBYIST by G. T. Rabaroe £1.50
 Supplies the hobbyist with a background knowledge.

50 PROJECTS USING RELAYS, SCR'S & TRIACS by F. G. Rayer £1.50
 Gives tried and practical working circuits which should present the minimum of difficulty for the enthusiast to construct.

HOW TO BUILD YOUR OWN METAL AND TREASURE LOCATORS by F. G. Rayer £1.25

Contains complete electronic and practical details on the simple and inexpensive construction of Heterodyne Metal Locators.

HOW TO MAKE WALKIE-TALKIES by F. G. Rayer £1.75 IC555 PROJECTS by E. A. Parr £2.00

Included in this book are Basic and General Circuits, Motor Car and Model Railway Circuits, Alarms and Noise Makers as well as a section on the 556, 558 and 559 timers.

PRACTICAL ELECTRONIC CALCULATIONS AND FORMULAE by F. A. Wilson £2.50
 Units and Constants, Direct Current Circuits, Passive Components, Alternating Current Circuits, Networks and Theorems, Measurements.

ELECTRONIC SECURITY DEVICES by R. A. Penfold £1.70
 Includes both simple and more sophisticated burglar alarm circuits using light, infra-red and ultrasonics gas and smoke detectors, flood alarms doorphone and baby alarms, etc.

ELECTRONIC PROJECTS FOR BEGINNERS by F. G. Rayer £1.60

A newcomer to electronics finds a wide range of easily made projects.

POPULAR ELECTRONIC PROJECTS by R. A. Penfold £1.70

Radio Projects, Audio Projects Household Projects and Test Equipment.

HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE by F. G. Rayer £1.75

Enables the enthusiast to simply and inexpensively build his own oscilloscope.

ELECTRONIC GAMES by R. A. Penfold £2.00

In this book the author has designed, and developed a number of interesting electronic game projects using modern integrated circuits.

COUNTER DRIVER AND NUMERAL DISPLAY PROJECTS by F. G. Rayer £2.00

Author discusses and features many applications and projects using various types of numeral displays, popular counter and driver IC's etc.

BEGINNERS GUIDE TO MICROPROCESSORS AND COMPUTING by E. F. Scott £2.00

Introduction to the basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming.

ELECTRONIC HOUSEHOLD PROJECTS by R. A. Penfold £2.00

Circuits range from such things as '2 tone door buzzer' Intercom through Smoke or Gas Detectors to Baby and Freezer Alarms.

A MICROPROCESSOR PRIMER by E. A. Parr £2.00

A newcomer to electronics tends to be overwhelmed when first confronted with articles or books on microprocessors. This small book will start by designing a simple computer and because of its simplicity and logical structure the language is hopefully easy to learn and understand.

50 CIRCUITS USING 7400 SERIES IC'S by R. N. Soar £1.65

The author has compiled 50 interesting and useful circuits and applications covering different aspects of electronics using these devices.

POPULAR ELECTRONICS BOOKS

Sinclair, I. R., Introducing Electronic Systems £3.10
 Sinclair, I. R., Introducing Amateur Electronics £3.10
 Sinclair, I. R., Electronic Fault Diagnosis £4.00
 Sinclair, I. R., Repairing Pocket Transistor Radios £2.90
 Sinclair, I. R., Oscilloscope In Use £4.00
 Sinclair, I. R., Understanding Electronic Components £5.10
 Sinclair, I. R., Understanding Electronic Circuits £5.10
 Kitchen, H. T., Handtools For Electronic Workshop £3.25
 Kitchen, H. T., Electronic Test Equipment £6.20
 Capel, V., How To Build Electronic Kits £3.25
 Darr, J., How to test almost everything electronic £3.75
 Brown, R. M., How to read electronic circuit diagrams £5.60

AUDIO

Earl, J., Audio Technicians Bench Manual £5.00
 Earl, J., Pickups and Loudspeakers £5.00
 Earl, J., Tuners and Amplifiers £4.00
 Earl, J., Cassette Tape Recorders £6.00
 Earl, J., ABC of Hi-Fi £6.00
 Capel, V., Microphones in Action £6.00

Capel, V., Improving Your Hi-Fi £5.00
 Capel, V., Creative Tape Recording £5.00
 Hellyer, H. W., Tape Recorders £5.00
 Sinclair, I. R., Audio Amplifiers For Home Construction £6.00

RADIO CONTROL

Drake, J., Radio Controlled Helicopter Models £4.95
 Jeffries, C. R., Radio Control For Model Yachts £3.85
 Safford, E. L., Radio Control Manual £5.50

COOKBOOKS

Tracton, K., BASIC Cookbook £4.10
 Lancaster, D., TTL Cookbook £7.55
 Lancaster, D., RTL Cookbook £4.65
 Lancaster, D., CMOS Cookbook £8.20
 Jong, W., IC Op Amp Cookbook £10.70
 Lancaster, D., T.V. Typewriter Cookbook £7.75
 Lancaster, D., Cheap Video Cookbook £6.50
 Jong, W., IC Timer Cookbook £7.65
 Lancaster, D., Incredible Secret Money Machine (a how to cook book for setting up your computer or technical business) £4.95

QUESTIONS AND ANSWERS

SIMPLE AND CONCISE ANSWERS TO MANY QUESTIONS WHICH PUZZLE THE BEGINNER.
 Coker, A. J., Q & A On Electric Motors £2.50
 Hellyer, H., Q & A On Radios and T.V. £2.50
 Hibberd, R., Q & A On Integrated Circuits £2.50
 Jackson, K., Q & A On Electricity £2.50
 Brown, C., Q & A On Hi-Fi £2.50
 Brown, C., Q & A On Transistors £2.50
 Brown, C., Q & A On Electronics £2.50
 Reddihough, J., Q & A On Colour T.V. £2.50
 Miller, H., Q & A On Electric Wiring £2.50

CONSTRUCTOR GUIDES

Graham, P., Simple Circuit Building £3.40
 Colwell, M., Electronic Diagrams £3.40
 Colwell, M., Electronic Components £3.40
 Colwell, M., Printed Circuit Assembly £3.40
 Ainslee, A., Practical Electronic Project Building £3.40
 Colwell, M., Project Planning and Building £3.40

BEGINNER'S GUIDE

Sinclair, I. R., Beginner's Guide To Tape Recording £4.25

Sinclair, I. R., Beginner's Guide To Integrated Circuits £4.25
 Sinclair, I. R., Beginner's Guide to Audio £4.25
 King, G. J., Beginner's Guide To Radio £4.25
 King, G. J., Beginner's Guide To Television £4.25
 King, G. J., Beginner's Guide To Colour T.V. £4.25
 Guilou, F., Beginner's Guide To Electric Wiring £4.25

PROJECT BOOKS

Marston, R. M., 110 Cosmos Digital IC Projects For The Home Constructor £4.95
 Marston, R. M., 110 Wave Form Projects For The Home Constructor £4.95
 Marston, R. M., 110 Op Amp Projects For The Home Constructor £4.95
 Marston, R. M., 110 Semiconductor Projects For The Home Constructor £4.95
 Marston, R. M., 110 Thyristor/SCR Projects For The Home Constructor £4.95
 Marston, R. M., 110 Electronic Alarm Projects For The Home Constructor £4.95
 Marston, R. M., 110 Integrated Circuits Projects For The Home Constructor £4.95
 Marston, R. M., 20 Solid State Projects For The Car and Garage £4.95
 Marston, R. M., 20 Solid State Projects For The Home £4.95

Note that all prices include postage and packing. Please make cheques, etc. payable to Hobby Electronics Book Service (in sterling only please) and send to:

Hobby Electronics Book Service
 Modmags Ltd
 145 Charing Cross Road
 London WC2H 0EE

★ Prices may be subject to change without notice.

Electronic Organ-2

Here is the second part of our organ project, which gives details of how to make your own keyboard contacts at a small fraction of the cost of commercially-available types

IF YOU'RE UP-TO-DATE with your project so far, you will have a baseboard with all hardware attached, including the keyboard, control panels and PCBs. You will also have built and tested Board 1 which contains the project's power supply, pre-amplifier and power amplifier, and filter and stops circuitry.

There are two jobs to do this month: build and wire up Board 2 (the master tone generator PCB), and make and fit all the key contacts to the keyboard.

Construction

Construction of the PCB is straightforward. Insert and solder all printed circuit board pins and the link first. Then do likewise to the 16-pin IC holder.

Following the overlay details in Fig. 2 insert and solder all resistors and capacitors, then semiconductors, and lastly the coil. Make sure all polarised components are correctly inserted.

Fit IC1 to its socket, checking that it is the right way round. The board can now be screwed into position on the PCB guiderails.

Using thin multi-strand wire, make all connections from Board 2 to the three potentiometer controls of vibrato depth, vibrato speed and pitch. Finally connect three power supply leads, +12 V, 0 V and -12 V, from the board to Board 1. Figure 3 shows the edge of Board 1 where power connections should be made, and also shows the positions of points 1, 2 and 3 which were accidentally not shown (oops) last month.

Now, with the aid of Board 1, you can test Board 2. Connect a loudspeaker to the speaker output jack socket of the organ and turn the organ on. Attach one end of a length of wire to one of the filter inputs at the right-hand side of Board 1 (it doesn't matter which,

but make sure you don't connect it to the point at the top edge, beside capacitor C10 — this is a power supply point).

Using the other end of the wire touch each of the 12 outputs from IC1 of Board 2 in turn. These outputs encircle the IC at a distance of about 1/2".

If all is working you will hear one note from the top octave at each point, 12 notes making the complete octave.

Useful Contacts

The contacts are made using small strips (about 1 1/2" by 3/16") of pre-cut phosphor-bronze. Figure 4 shows details of one pair of contacts and from this you can see that they are all mounted onto lengths of copper laminate PCB, which are in turn mounted onto a wooden batten. Each pair of contacts is made from one straight piece of phosphor-bronze and one shaped piece.

First, glue the lengths of PCB onto the

wooden batten using good quality contact adhesive. The lengths of PCB (two or more) with continuous areas of copper should all go along one edge, and similarly the lengths with broken areas of copper should go along the other edge. Both types of PCB lengths should be glued copper side up.

When the glue is thoroughly dry, link the lengths of continuous copper strips where they meet by soldering short pieces of tinned copper wire across the breaks.

Next glue the whole wooden batten, complete with PCBs, onto the underneath of the keyboard, parallel to and 1" away from, the key actuator tips. Allow the glue to dry.

Now comes the monotonous bit! Position one length of phosphor-bronze strip onto the left-hand edge of the continuous strip PCBs so that it rests on the key actuator plastic tip, then solder it carefully in place as shown in Fig. 4. Repeat this for the other 59 straight key contacts.


The shaped key contacts are formed with the use of (ideally) a pair of flat-nosed pliers. The contact shape is not critical as, even after soldering into position, minor adjustments can be made by hand where necessary. Make and solder each shaped contact into place, individually.

Finally, adjust the contacts so that there is approximately 1/16" gap between each shaped and straight key contact.

This whole process of making the contacts is quite time-consuming (it will probably take you about four hours) but provides a cheap yet reliable method of keyboard switching.

That's all for this month (you can breathe a sigh of relief!).

Next month we'll move on to Boards 3 and 4.

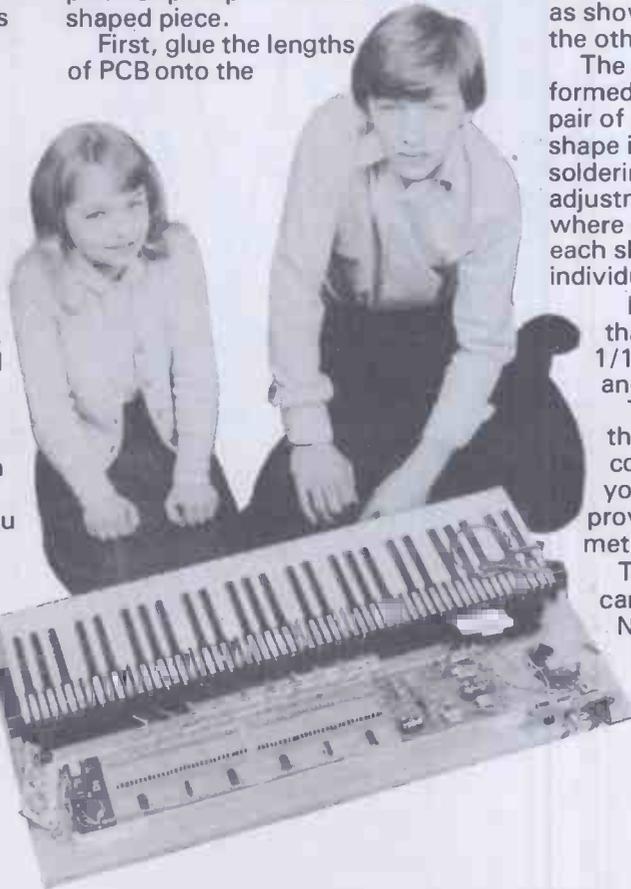


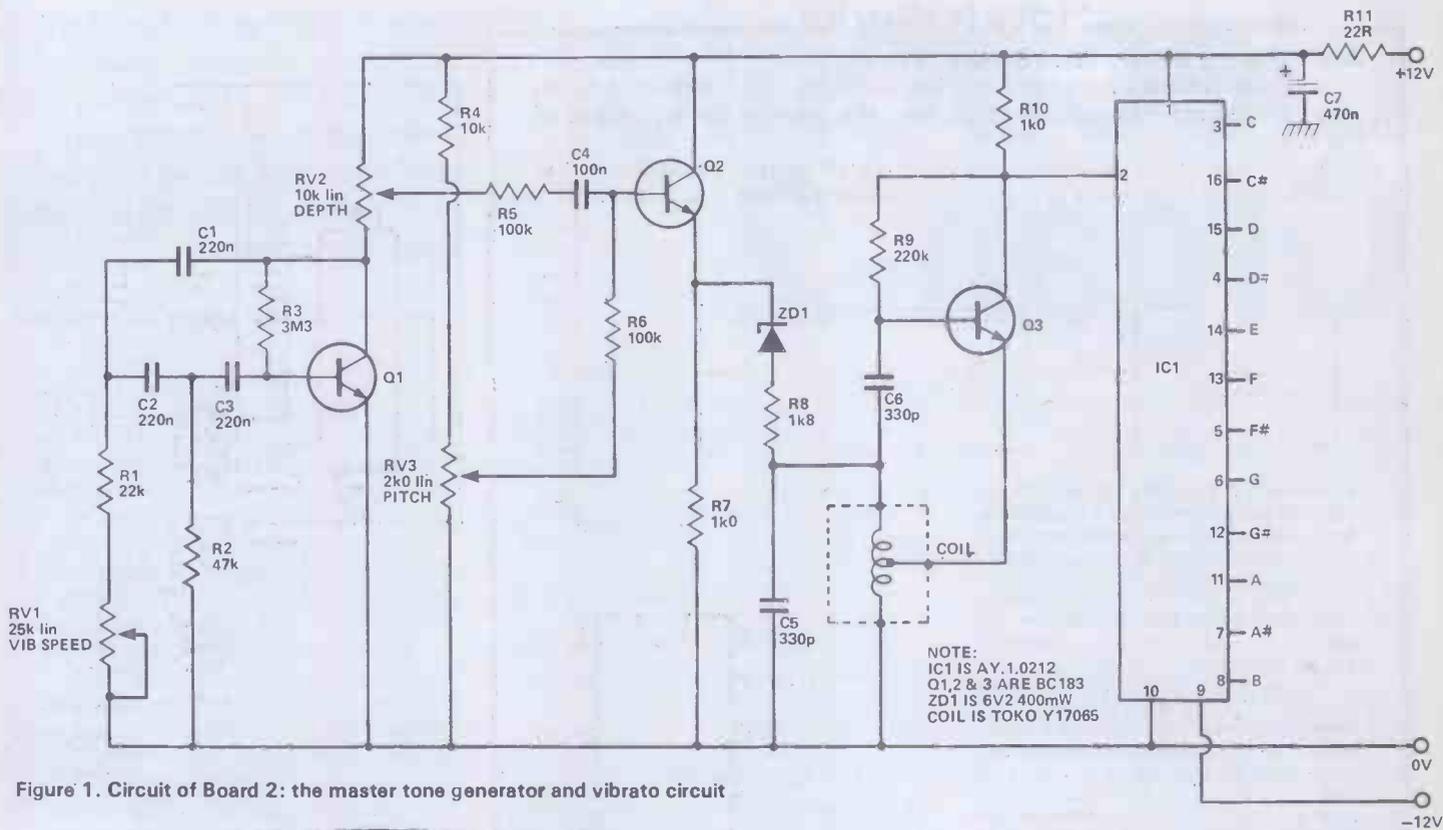


Figure 1. Circuit of Board 2: the master tone generator and vibrato circuit

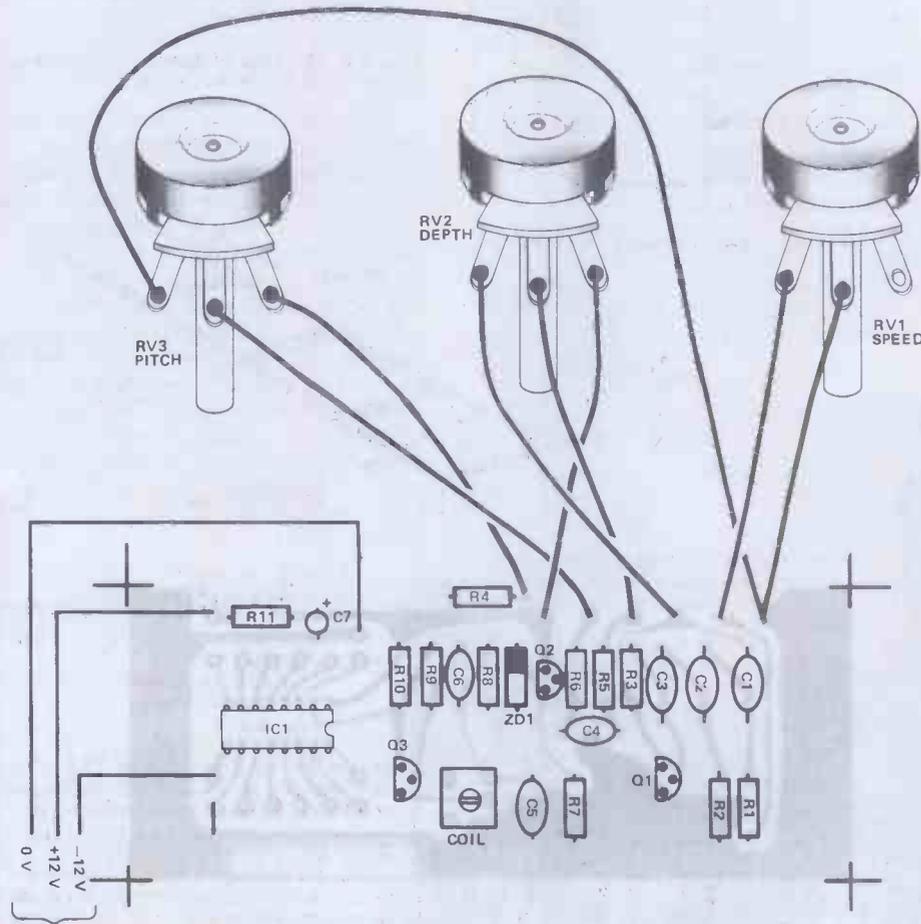

FROM BOARD 1
Figure 2. Overlay of Board 2 and connection details

Parts List

The list below consists of the parts needed for this month's constructional part of the project.

RESISTORS

R1	22k
R2	47k
R3	3M3
R4	10k
R5,6	100k
R7,10	1k0
R8	1k8
R9	220k
R11	22R

POTENTIOMETERS

RV1	25k linear potentiometer
RV2	10k linear potentiometer
RV3	2k0 linear potentiometer

CAPACITORS

C1,2,3	220n polyester
C4	100n polyester
C5,6	330p silver mica or polystyrene
C7	470n, 16 V tantalum

SEMICONDUCTORS

IC1	AY-1-0212 top-octave generator
Q1,2,3	BC183 NPN transistor
ZD1	6V2, 400 mW zener diode

MISCELLANEOUS


Coil	TOKO Y17065
	120 phosphor-bronze strips (approx size 1 1/2" by 3/16")
	Strips of copper laminate (plain and etched to suit)
	Wooden batten

How It Works

Board 2 is the Master Tone Generator Board.

The output from a voltage controlled oscillator (VCO) is divided down into 12 separate frequencies which form the notes of the top octave of the organ.

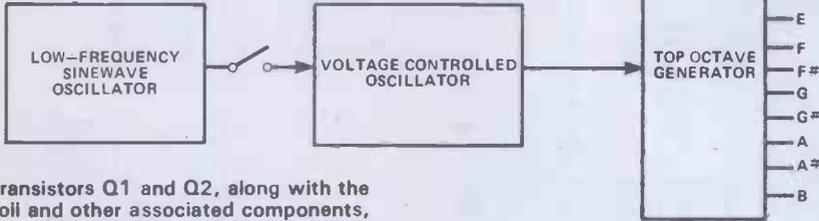A low-frequency sinewave also can be switched in, to modulate the VCO's output frequency and provide a vibrato effect.



Transistors Q1 and Q2, along with the coil and other associated components, form a high-frequency voltage controlled oscillator, the main frequency of which is adjustable by the position of the ferrite slug in the coil. Other control inputs come from pitch control RV3 and the low-frequency sinewave oscillator output from RV2.

Integrated circuit IC1 is a top-octave generator. Its job is to take the high-frequency signal from the VCO and produce from it 12 subdivided signals corresponding to the 12 semitones of a musical octave. The IC consists of 12 divider circuits, each of which divides the input signal by an exact integer to produce the scale of the top octave of the organ. Thus the pitch of the whole octave is defined by the one oscillation frequency.

A low-frequency (about 2 to 8 Hz) sinewave oscillator is formed around transistor Q1 and its frequency can be adjusted by pot RV1. The amplitude of the output signal can be varied by RV2.

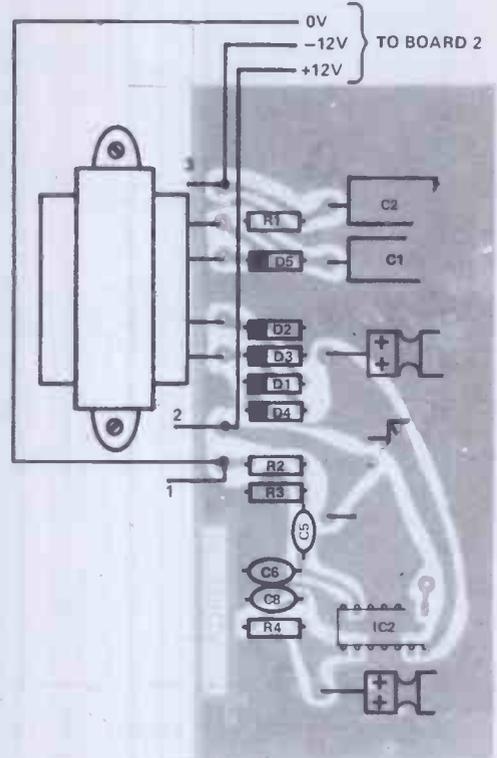
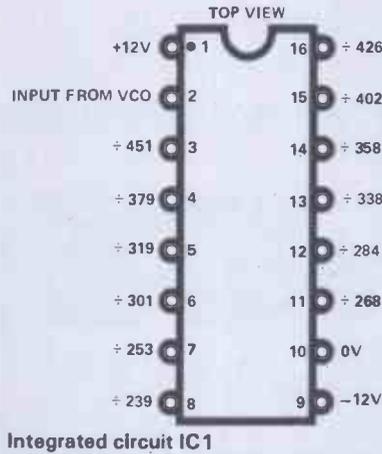


Figure 3. The edge of Board 1 where power connections are taken to Board 2

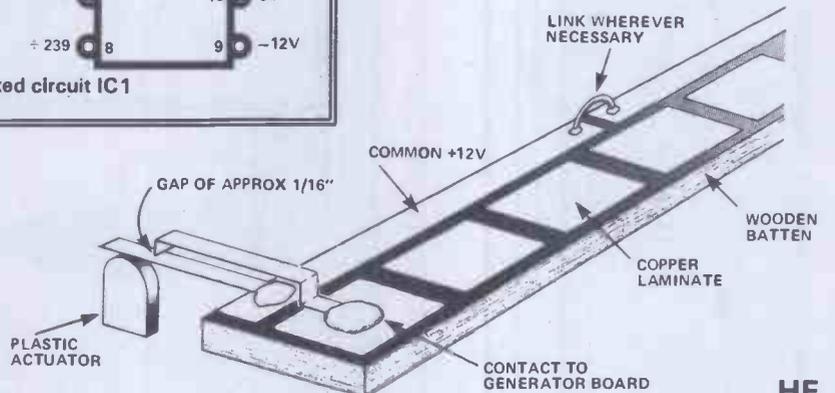


Figure 4 (above). Details of one key contact. This should be repeated along the length of the keyboard, until all 60 notes have a working contact

Buylines

A limited number of kits for the HE Organ can be obtained from:

Mr A. T. Hawkins
23 Blenheim Road
St Albans
Herts AL1 4NS

for the all-inclusive price of £95. The kits contain all metalwork, hardware and PCBs, as well as the keyboard and components. You only need to supply your own baseboard and case.

For those readers who would prefer to buy the components themselves, Mr Hawkins will supply the keyboards separately. None of the other items should be difficult to find.

FREE OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

TRANSMITTER SURVEILLANCE *

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox - all electronic parts and circuit. £2.30.

RADIO MIKE *

Ideal for discos and garden parties, allows complete freedom of movement. Plug through FM radio or tuner amp. £6.90 comp. kit.

SAFE BLOCK

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit. £1.95.

LIGHT CHASER

Gives a brilliant display - a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase patterns and a strobe effect. Total output power 750 watts per channel. Complete kit. Price £16. Ready made up £4 extra.

FISH BITE INDICATOR

Enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loudspeaker emits a shrill note. Kit. Price £4.90.

6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit includes case materials, six transistors, and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (gives best results) £3.75. Kit includes chassis and front but not case.

RADIO STETHOSCOPE

Easy to fault find - start at the aerial and work towards the speaker - when signal stops you have found the fault. Complete kit £4.95.

INTERRUPTED BEAM

This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main components - relay, photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2.30

OUR CAR STARTER AND CHARGER KIT has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

GPO HIGH GAIN AMP/SIGNAL TRACER. In case measuring only 5/16" x 3/16" x 1/16" is an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4 1/2v battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 80ohm earpiece 25p.

NEW KIT THIS MONTH!

CB RADIO - Listen in with our 40-channel monitor. Unique design ensures that you do not miss sender or caller. Complete kit with case and instructions only £5.99.

8 POWERFUL BATTERY MOTORS

For models, Meccanos, drills, remote control planes, boats etc. £2.50.

WATERPROOF HEATING WIRE

60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses - around water pipes, under grow boxes in gloves and socks. 23p per metre.

COMPONENT BOARD Ref. W0998

This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including 4 3amp 400v types (made up in a bridge) 8 transistors type BC107 and 2 type BFY-51 electrolytic condensers. SCR ref 2N 5062, 250uf 100v DC and 100uf 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

FRUIT MACHINE HEART. 4 wheels with all fruits, motorised and with solenoids for stopping the wheels with a little ingenuity you can defy your friends getting the "jackpot". £9.95. + £4 carriage.

4-CORE FLEX CABLE

White pvc for telephone extensions, disco lights, etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

MUGGER DETERRENT

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

EXTRACTOR FANS

Mains operated - ex. Computer.


5" Woods extractor £5.75 Post £1.00.

6" Woods extractor £6.90 Post £1.25

6" Plannar extractor £7.50 Post £1.00

4" x 4" Muffin 115v. £4.50 Post 50p.

4" x 4" Muffin 230v. £5.75 Post 50p.

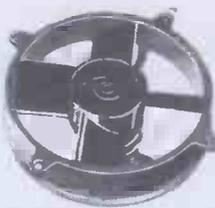

PUSH BUTTON G.P.O. TELEPHONES
FOR £25 (quickly recoverable in saved time) you will improve your image and efficiency with this push button desk telephone, ex. G.P.O. thoroughly reconditioned, can be yours in a few days, if you send today.

*(Not licenceable in the U.K.)

SUPER HI-FI SPEAKER CABINETS

Made for an expensive Hi-Fi outfit - will suit any decor. Resonance free cut-outs for 8" woofer and 4" tweeter. The front material is carved Dacron, which is thick and does not need to be stuck in and the completed unit is most pleasing. Colour black. Supplied in pairs, price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.50 the pair.




LOUDSPEAKERS

8" woofer and 4" tweeter, 4 ohms 35 watts power rating £6.90 per pair. Ditto but 8 ohms, £11.50 per pair. Post £2.00.

3 CHANNEL SOUND TO LIGHT KIT

Complete kit of

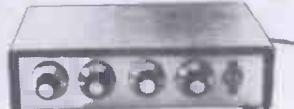

parts for a three-channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form or £19.95 assembled and tested.

THIS MONTH'S SNIP
UNIVAC KEY BOARD Model No. FI 308-00



Has 57 encoded key switches and 10 mini toggle switches. As well as a P.C.B. with many IC's etc. These keyboards are in very good condition. Price only £11.50 + post £2.00. Well worth it for the switches alone.

POCKET AUDIO COMPONENT TESTER



With it you can quickly test diodes, rectifiers, transistors, capacitors, check wiring and p.c. boards for open circuits, find the anode and cathode of a diode or rectifier and whether a transistor is PNP or NPN, which are the base collector and emitter connections. Condensers, if bad give a continuous signal but if good, give intermittent signals of varying length depending on their value. The test current is very low (2uA) and the voltage only 1.4v, so it is also possible to check MOS devices, as well as sensitive transistors with out fear of damaging them. The unit is supplied complete with internal battery, which should last many months. Price £3.45p.

MINI-MULTI TESTER Deluxe pocket size precision moving coil instrument. Jewelled bearings - 2000 p.p.v. mirrored scale. 11 instant range measures:

DC volts 10, 50, 250, 1000.
AC volts 10, 50, 250, 1000.
DC amps 0 - 100 mA.
Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 50p post and insurance.



FREE Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy-to assemble modular form this should sell at about £30 - but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16.75 including VAT and post. **FREE GIFT** - buy this month and you will receive a pair of Goodman's elliptical 8"x5" speakers to match this amplifier.




VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are new but without case, but we can supply plastic cases (base and cover) £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off's per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

DELAY SWITCH

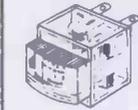Mains operated - delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps - second contact operates a few minutes after 1st contact. £1.95.



LEVEL METER

Size approximately 1/2" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.


STEREO HEADPHONES

Japanese made so very good quality. 8 ohm impedance, padded, terminating with standard 1/4" jack-plug. £2.99 Post 60p.



BRIDGE RECTIFIER

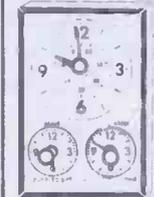1 amp 400v 30p each.
10 for £2.50. 100 for £20.00



TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with the dials. Comes complete with knobs. £2.50.

LAST MONTH'S SNIP - STILL AVAILABLE

And it still carries a free gift of a desoldering pump, which we are currently selling at £6.35p. The snip is perhaps the most useful breakdown parcel we have ever offered. It is a parcel of 50 nearly all different computer panels containing parts which must have cost at least £500. On these boards you will find over 300 IC's. Over 300 diodes, over 200 transistors and several thousand other parts, resistors, condensers, multi-turn pots, rectifiers, SCR, etc. etc. If you act promptly, you can have this parcel for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel. Surely this is a bargain you should not miss! When ordering please add £2.50 post and £1.27 VAT.



MAINS MOTORS Precision made as used in record players, blow heaters, etc.

Speed usually 1,400. All have ample spindle length for coupling fan blade, pulley, etc. Power depends on stack size. 5/8" stack £2.00; 3/4" stack £2.50; 7/8" stack £3.00; 1" stack £3.50; 1 1/4" stack £4.50. Add 25% to motor cost to cover postage, and then add 15% VAT.

YOUR LAST CHANCE FOR THIS BARGAIN

100 twist drills, regular tool shop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic, etc. from the finest holes in P.C.B. right up to about 1/4". Don't miss this snip - send your order today.

MAGNETIC LATCH

Low voltage (4 - 8 volt AC/DC operation). Only £1.50 each.



TAPE PUNCH & READER

For controlling machine tools, etc. motorised 8 bit punch with matching tape reader, Ex-computers, believed in good working order, any not so would be exchanged. £17.50/pair. Post £3.00.

J. BULL (Electrical) Ltd.
(Dept. HE), 34 - 36 AMERICA LANE,
HAYWARDS HEATH, SUSSEX RH16 3QU.

J. BULL (Electrical) Ltd - Established 25 years. MAIL ORDER TERMS:
Cash with order - please add 60p to all orders under £10, to offset packing, etc. ACCESS & BARCLAYCARD WELCOMED. Our shop is open to callers. BULK ENQUIRIES INVITED. Telephone: Haywards Heath (0444) 54563.

O Level Q & A

As we near the end of the syllabus, Nick Walton covers two main topics this month: Op Amps and Systems

LAST MONTH WE looked at amplifiers, especially the type you might find in a radio or hi-fi — though in practice these would have much more sophistication. There is, however, another type of amplifier called the operational amplifier, or op amp for short, which we will consider this month, along with the way we can come to terms with difficult circuits by what is known as a 'systems approach'. This will bring together what we have seen in previous articles, and enable us to look at how more complicated systems might be put together.

Understanding Op Amps

So let's start with the op amp and see why it is such a useful and versatile little beast. Actually, the operative word is little because these days about the most common form of operational amplifier is the 741 integrated circuit package, which as you can see from Fig. 1 does not need a crane to lift it, in spite of the fact that a typical circuit for the 741 contains 20 to 25 transistors and 10 to 15 resistors. It has eight legs often in a dual-in-line (DIL) configuration; that is, in two rows of four, as opposed to the pins going round in a circle. When you think that back in the old days an operational amplifier would contain several valves, and now you could fit several 741s into the volume occupied by one valve, you really do see how things have shrunk. Indeed, all the circuitry lies in an area 1 or 2 mm square, so much of what Fig. 1 shows is merely encapsulation.



Figure 1. Comparison in size between a 741 operational amplifier and a 2p coin

However, enough of the lyrical 'small is beautiful' bit: let's try to answer the question 'What does it do?' One of its fundamental uses is to perform mathematical operations like add, subtract, multiply and divide, differentiate and integrate in analogue computers. 'What is an analogue computer?' did you say? Well, computers can be divided into two classes: digital and analogue. The first of these uses electronic logic and strings of binary digits 0 and 1, and bases all its working on the possible logic gates (NOT, AND, OR, NOR and NAND,

so well expounded by Ian Sinclair's series). The other class uses some quantity, most commonly voltage values to stand for numbers; that is, voltage value being analogous to number, or the analogue of it. Thus, for example, 1 V might represent the number one, 2 V the number two and so on. Perhaps the neatest illustration of the difference between analogue and digital devices lies in contrasting the electronic calculator (a digital computer at heart) with what people used before calculators became widespread — the slide rule. This uses the length of the slide to be analogous to number, so it is a simple form of analogue computer.

To understand the function of an op amp properly we must take a look at what it does, and throw in a little theory for good measure. The ideal op amp will have four properties. First, it will have an infinitely high gain when there is no feedback (from the output back round to the input). The no-feedback gain is properly called the 'open loop gain', and this is very high — for the 741, it is typically about 10,000 or 100,000. We shall see in a moment that the gain *with* feedback can be set entirely by the feedback resistor and the input resistor. The second property is that it needs to have an infinitely high input impedance so that the signal is not reduced by the amplifier drinking up everything that is being offered. In other words it must not *load* the input signal. Third, it needs to have a low output impedance: theoretically it should be zero but in practice it will be about 100Ω. This really comes back to something we met in an earlier article where if your voltage source, a battery at simplest, has an internal resistance then the more current you take from it the more voltage you lose across the internal resistance, and the less appears actually across the output terminals. The fourth property is that ideally it will amplify all frequencies by the same amount, from zero (DC) to very high frequencies (a few megahertz).

The circuit representation of an amplifier is a triangle and Fig. 2 is the usual way of representing an op amp. Something you notice immediately is that it has one output but two inputs, called the inverting input and the non-inverting input. You might remember from last month's O Level Q&A that the non-inverting amplifier will give an increase in output voltage for an increase in input, while the inverting input does the opposite: the output goes *up* if the input comes down (like umbrellas and rain!).

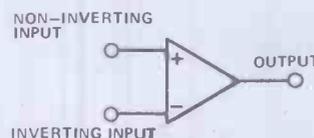


Figure 2. Circuit representation of an op amp



Virtual Earth

Whichever input you happen to be using, the actual input point where it enters the amplifier is known as a 'virtual earth' and it is not difficult to see how this comes about when one considers the high gain aspect of the amplifier. (Strictly speaking, what is being amplified is the difference in voltage between the two input terminals, though quite often one of these will be earthed.) Consider an op amp with an open-loop gain of 100,000 and suppose also that the positive supply rail is +10 V, which will then of course also be the maximum positive voltage to which the output can swing. Now ask yourself what change of input voltage will cause a swing to +10 V (given this gain of 100,000). Since gain A_v is equal to

$$A_v = \frac{V(\text{out})}{V(\text{in})}$$

$V(\text{in})$ becomes one ten-thousandth of a volt, or 0.1 mV, which is really nothing at all between friends, hence the name virtual earth.

In practice you can easily pick up a stray tenth of a millivolt without wanting to, and thus get a spurious value for the output voltage. It is in these circumstances that the 'offset null' pin can be used to compensate for such a stray voltage.

It is now fairly easy to see how the gain of the op amp can be fixed by means of the resistances round it. Consider Fig. 3. Resistor $R(\text{in})$ is what we call the input resistor and R_f is called the feedback resistor. The input voltage $V(\text{in})$ will be applied as shown in Fig. 3, and the output voltage $V(\text{out})$ will appear as shown. Focusing on $R(\text{in})$, the voltage at the amplifier end is earth (virtually!) and at the other end it is $V(\text{in})$. Thus the voltage across it is $V(\text{in})$ and the current through it (by courtesy of Georg Simon Ohm yet again) is derived from $V(\text{in})/R(\text{in})$.

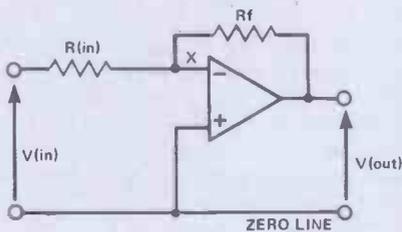


Figure 3. Circuit arrangement to show that voltage A_v is equivalent to $R_f/R(\text{in})$

Similarly for R_f , one end is at virtual earth and the other is at $V(\text{out})$, giving a voltage across it of $V(\text{out})$ and a current of $V(\text{out})/R_f$ or strictly minus $V(\text{out})/R_f$.

Assuming these currents as being equal we get:

$$\frac{V(\text{in})}{R(\text{in})} = -\frac{V(\text{out})}{R_f}$$

and this gives the gain

$$\frac{V(\text{out})}{V(\text{in})} = -\frac{R_f}{R(\text{in})}$$

as the ratio of the feedback resistor to the input resistor. Notice that to get this result we had to use two of the basic properties of the op amp mentioned earlier, namely that it had an infinitely high gain (to justify saying X was virtually at

earth potential) and that it had infinitely high input impedance (so that no current was actually siphoned off into the amplifier itself — it all went through $R(\text{in})$ and R_f).

The same two vital properties are used when thinking of the op amp as an adding amplifier, as a thoughtful look at Fig. 4 will show. Since X is a virtual earth, then each of the currents i_1 , i_2 , and i_3 (also equal to V_1/R , V_2/R and V_3/R respectively) must flow through R_f . In other words:

$$i_1 + i_2 + i_3 = \text{current in } R_f = i$$

so

$$\frac{V_1}{R} + \frac{V_2}{R} + \frac{V_3}{R} = -\frac{V(\text{out})}{R_f}$$

making the output voltage depend on the sum of the input voltages.

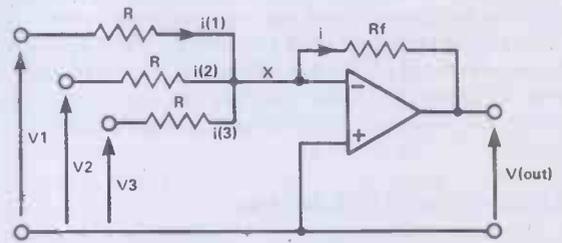


Figure 4. Op amp used as a summing amplifier

If we were to put a capacitor into the feedback position as in Fig. 5 we get a circuit which produces a steadily rising output voltage for an input consisting of a step. If you are familiar with integration you will see that the output can be regarded as the integral of the input and such an arrangement is called an integrator.

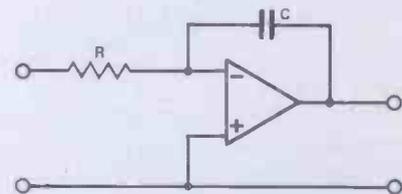


Figure 5. Op amp used as an integrator

We will take as our final brief example the set-up in Fig. 6. Before you read on you might like to try to see why we can regard this as the op amp in a non-inverting mode, and an example of a negative-feedback amplifier. You may remember from the previous article that the use of negative feedback stabilises an amplifier. Here, the effect is to stabilise the output at 10 V. If we imagine an initial condition with the input at 5 V and the output at 10 V, then the voltage at Y between the two equal resistors will be 5 V which is fed back to the inverting input. So, if for any reason the output voltage drifts above 10 V, the voltage at Y will go up and because it is fed into the *inverting* input, will pull the output down again. The overall picture is that the output is stabilised at 10 V. There's a lot of fun to be had with op amps and much more to them than this brief survey can express.

Systems

I don't suppose there is a single person with an interest in electronics who at some time or another has not taken one

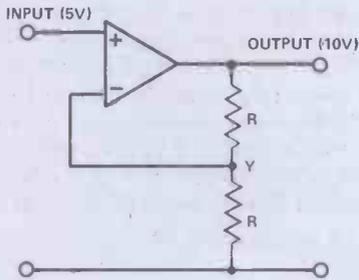


Figure 6. Op amp in non-inverting mode as a negative-feedback amplifier

look at a complicated circuit diagram and thought: "How will I ever understand what is happening in all that maze?"

Even the circuit of a not-very-complicated radio can induce this effect and if you still frequently feel bemused then this part of the article is for you. Help lies in one simple word: *systems*. In fact, it is rapidly coming into everyday use. We would not, for example, be surprised to hear that a friend had been saving up and was now going out to buy a hi-fi system. What is meant is that this friend will go and buy several different boxes, all of which must be connected together correctly. One box might contain the turntable and pickup. The pickup will be connected first to a pre-amplifier, the function of which is to amplify the minute signals coming in from the pickup (a few millivolts) up to a voltage that could be fed to the power amplifier input. This voltage could be around 1 V. When the signals come out of the power amplifier, they are fed to the speakers. The final voltage at the speaker terminals could be as high as 20 V. It is possible that under some bizarre set of circumstances a complete circuit diagram for the whole lot might be produced, but it is really much more useful to see the various parts of the whole and forget about individual circuit components. The system would look something like that in Fig. 7. Within these boxes we might say there are subsystems; the speaker box could well contain two or three speakers, one for high frequencies (a tweeter), one for low frequencies (a woofer), and perhaps something for the mid range, and this in turn would give rise to the need for a system to feed the correct frequencies to the appropriate speaker by some sort of filter system. Again, the amplifier might have a system (a scratch filter) to cut out very high frequencies that are produced by a scratch on the record. You might also want the facility at the input of the pre-amplifier to allow signals from other sources (with different impedances) to be fed in, for instance from a tape pickup or a radio tuner.

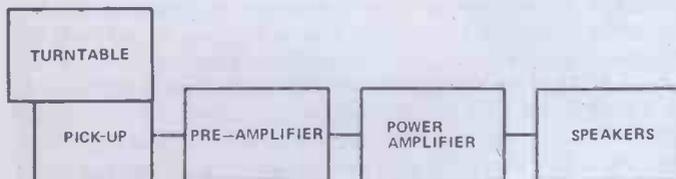


Figure 7. Systems approach to a hi-fi system

Practical Systems

Ramifications are almost endless but the important thing to do is to look initially at the system that concerns you and leave the individual components to a much later stage. In-

centally, this is how any troubleshooter will work. He or she will isolate the system or subsystem that is playing up and then narrow the field in logical stages. The garage man who comes to rescue you when you have broken down by the roadside will start by trying to establish whether it is the petrol system or the electrical system that is faulty (or something else altogether). If the fault is electrical, is it the high-voltage system or the low-voltage system?

Our own bodies are a complex mass of interacting systems (with, incidentally, lots and lots of feedback) and while it would be a fiendishly difficult task to represent ourselves fully in a systems block diagram, it would be a very good exercise for you to try to put together a block diagram for a radio system, and perhaps as a useful revision exercise you could look back over some of the previous articles in this series where some of the subsystems (tuning, detection, amplification) have been dealt with.

That just about completes matters for this month. Next month will be the end of the series, signing off with multivibrators and information storage — all coming out about a fortnight before the exam itself. Cheers! **HE**



'YOUR CALCULATOR BROKEN DOWN AGAIN?'

REMOTE CONTROL KITS

- MK6** - Simple Infra Red TRANSMITTER. A Pulsed infra red source which comes complete with a hand held plastic box. Requires a 9V battery. **£4.20**
- MK7** - Infra Red RECEIVER. Single channel, range approximately 20 ft. Mains powered with a triac output to switch loads up to 500W at 240Vac, but can be modified for use with 5 to 15V dc supplies and transistor or relay outputs. **£9.00**
- * **SPECIAL PRICE** * MK6 and MK7 together. Order as RC500K. **£12.50**
- MK8** - Coded Infra Red TRANSMITTER. Based on the SL490, the kit includes 2 IR LEDs, measures only 6x2x1.3 cms. and requires a 9V (PP3) battery. **£5.90**
- MK9** - 4 Way KEYBOARD. For use with the MK8 kit, to make a 4-channel remote control transmitter. **£1.90**
- MK10** - 16-Way KEYBOARD. For use with the MK8 kit, to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. **£5.40**
- MK11** - 10 On-OFF Channel IR RECEIVER with 3 analogue outputs (0-10V) for controlling such functions as lamp brightness, volume, tone, etc. Other functions include an on/standby output and a toggle output, which may be used for sound muting. Based on ML922 decoder IC. Includes its own mains supply. **£12.00**
- MK12** - 16 Channel IR RECEIVER. For use with the MK8 kit with 16 on/off outputs which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Outputs may be latched, or momentary, depending on whether the ML926 or ML928 is specified. Includes its own mains supply. Size 9x4x2 cms, excluding transformer. **£11.95**
- MK13** - 11-Way KEYBOARD. For use with MK8 and MK11 kits. Transmits programme step + and - analogue + and - (3), mute, normalise analogue outputs, an on/standby. **£4.35**

INTEGRATED CIRCUITS

- 555 Timer **21p**
- 741 Op. Amp **19p**
- AY-5-1224 Clock **£2.60**
- AY-5-1230/2 Clock/Timer **£4.50**
- AY-3-1270 Thermometer **£8.20**
- ICL7106 DVM (LCD drive) **£7.00**
- LM377 Dual 2 W Amp **£1.45**
- LM3795 Dual 6W Amp **£3.50**
- LM380 2W Audio Amp **80p**
- LM382 Dual/low noise Preamp **£1.00**
- LM386 250mW low voltage Amp **75p**
- LM1830 Fluid Level Detector **£1.50**
- LM2907 I_v Converter (8 pin) **£1.40**
- LM2917 I_v Converter (14 pin) **£1.60**
- LM3909 LED Flasher/Oscillator **60p**
- LM39-1 Thermometer **£1.20**
- LM3915 - Dot Bar Driver (Log) **£2.20**
- MK74C911 4 digit display controller **£6.50**
- MM74C915 7 segment BCD converter **96p**
- MM74C915 4 digit cr. with 7 seg o.p. **£4.50**
- S5668 Touchdimmer **£2.50**
- SL440 A.C. Power Control **£1.75**
- SN76477 Complex Sound Generator **£2.52**
- T8A800 5W Audio Amp **68p**
- T8A10A5 7W Audio Amp **£1.00**
- TDA1024 Zero Voltage Switch **£1.20**
- TDA2020 20W Audio Amp **£2.85**
- TMS1121 Clock/7-Day Timer **£8.50**
- TMS1121 Data **50p**
- 2N1034E Timer **£1.80**
- All ICs supplied with data sheets
- Data Sheets only 10p each device.

V MOS POWER FETS

- VN10K M 0.5A/60V (T092) **52p**
- VN66AF 2A 60V (T0220) **88p**

BOXES

- Moulded in high impact ABS Supplied with lids and screws. Black
- B1 75x6x35mm **65p**
- B2 95x71x35mm **85p**
- B3 115x95x37mm **95p**

EVERY DOOR SHOULD HAVE ONE


Whatever kind of door you have, our New Electronic Combination Lock will enable you to open it easily but make things very difficult for unwelcome visitors. The unit, which comes complete with a 10-way keypad, requires an easily remembered four digit code to be entered before the door can be opened, while the intruder has over 5,000 combinations to choose from. The code can be easily changed by means of a pre-wired plug and a momentary or latched output version can be made. The kit has even more uses in a car where it may be used to disable the ignition. Another useful feature is the Save Button. This stores the combination number, enabling the car to be used by authorised persons such as garage personnel without disclosing the code.



The complete kit measures 7 x 6 x 3 cms. deep and consumes a mere 40uA when not in use, and will drive a 5V to 15V (750mA) solenoid or relay coil (not supplied) directly. So why not treat your door to a new lock for

ONLY £10.50

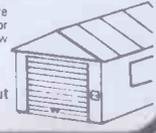and think about all the keys you can lose or forget without ever locking yourself out. As featured in PF May 81.



TRIACS

- 400V Plastic Case (Texas)
- 3A TIC206D **49p**
- 8A TIC226D **58p**
- 12A TIC236D **85p**
- 16A TIC246D **95p**
- 25A TIC263D **190p**
- 6A with trigger Q4006LT **80p**
- 8A isolated tab TXAL226B **65p**
- Diac **18p**

ARE YOU SITTING COMFORTABLY?

Our new TDR300K Touch Dimmer Kit will ensure that you are. Based on our highly successful TD300K touch controlled dimmer kit, the TDR300K incorporates an infra red receiver, enabling the lamp brightness to be varied and switched on or off by touch or remotely by means of a small hand held transmitter. The complete kit, which includes easy to follow instructions, will fit into a plaster depth box and the plastic front plate has no metal pads to touch, ensuring complete safety. Even a neon is included to help you locate the switch in the dark.



For the more athletic of you, the TD300K Touchdimmer kit is still available at £6.50 and the TDE/K Extension Kit for 2-way switching, etc. is £2. **DON'T FORGET** to add 50p P&P and 15% VAT to your total purchase.

MINI TRANSFORMERS



Standard mains primaries 240V a.c. 100mA secondaries

6-0-6V **80p**

9-0-9V **85p**

12-0-12V **90p**

LEDs



- 0.1" Red **9p**
- 0.1" Green **12p**
- 0.1" Yellow **12p**
- 0.2" Red **9p**
- 0.2" Green **12p**
- 0.2" Yellow **12p**
- 0.2" blue **3p**
- Rectangular Red **16p**
- Rectangular Green **17p**
- Rectangular Yellow **17p**
- Flat Face Rectangular, Triangular, Arrowhead Square
- Red **17p**
- Green **20p**
- Rec. Yellow **20p**



TK Electronics

(HE) 11 BOSTON ROAD, LONDON W7 3SJ. 01-579 9794/2842

ALL COMPONENTS ARE BRAND NEW AND TO SPECIFICATION. Add 50p P&P and 15% VAT to TOTAL OVERSEAS CUSTOMERS ADD £1.50 (Europe), £4 (elsewhere) for P&P. Send s.a.e. for price list and with all enquiries. Callers welcome 9.30-5.00 (Mon-Fri) 10.00-4.00 (Sat).

LOW-COST, RUGGED TEMPERATURE CONTROL HIGH QUALITY



TEMP. GAUGE 0° - 120° C Remote sensor on 38" capillary, panel mounting dial 55mm. dia. **ONLY £1.85** (Incl. P&P)

16A 240V RANCO THERMOSTAT Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. **£2.30**, including control knob.

RANCO THERMAL CUT-OUT 100° C 15A 240V. Sensing coil on 41in. capillary. panel mounting with reset button. **£1.20**.

BUY ONE EACH OF ABOVE FOR £4.85

LIGHT DEPENDENT RESISTORS in plastic housing with window, heavy-duty lead. Similar to ORP 61. You normally pay well over double for resistor alone. **Only 30p or £2.35 for 10.**

DOUBLE ENDED SMITHS BLOWERS 2 output apertures, 53 x 103 mm. Large flange. **Only £5.50.**

SMALL INDUCTION MOTOR (shaded pole), double ended with 1/4" x 3/8" shafts, 240V. **£3.25.**

BULGIN STRAIN RELIEF SLEEVE 10 FOR 30p

USEFUL RUBBER GROMMETS. Fit 1/4" hole. **10 for 20p.**

POWER RESISTOR, wire-ended, 20-watt. 410Ω ± 5%. Only 50p.



L.E.M. SERVICES
239 RUGBY ROAD
LEAMINGTON SPA CV32 6DY
WARWICKSHIRE

RELAYS BY KEYSWITCH

10A 2-Pole C/O 240V Coil. **ONLY 80p**
2 for **£1.50**
5 for **£3.50**

BULGIN GLASS FUSES 20 mm 1A Quick Blow **10 for 40p**
1" (same size as 13A plug fuse but not to BS1362). Will fit most 1 1/4" chassis mount fuse holders, 10A quick blow 5A anti-surge, 3A quick blow. **10 (any mix) 40p**
100 for £3

GEC CONTACTOR 3 heavy duty normally open contacts 600V 35A. 240V coil. **ONLY £4.50.**

TOP QUALITY CHROME TOGGLE SWITCHES 2 pole C/O centre off 10A 240V. **80p, 2 for £1.50, 5 for £3.50.**
2 Pole make, biased off 2A 240V. **30p, 4 for £1**

CAPACITOR, 800V AC, RMS, 0.01 MFD. 30p each


ADD 50p P&P
ORDERS OVER
£2.50 post free

PRECISION PETITE MINIATURE DRILLS AND ACCESSORIES for all your modelling needs



A choice of three power drills that fit snugly in the hand, so light they enable you to carry out the most intricate tasks — drilling, shaping, cutting, polishing, etc., in the minimum of time.

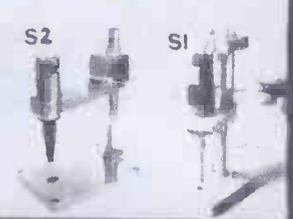There are two types of drill stand, plus all the necessary accessories in a range that fills every need. Send 9" x 4" S.A.E. for full details.



Sole UK Distributors **PRECISION PETITE LTD., Dept. H.E.**
119a HIGH ST. TEDDINGTON, MDX. Tel: 01-977 0878

Envelope Generator

Another simple-to-build yet fascinating musical effect from HE

NO! AN ENVELOPE generator is not a machine that keeps the postman in a job. It is, of course, a musical effect commonly used with an electric guitar (although there is little reason why it can't be used with other instruments) to increase the instrument's already versatile range. It does this by altering the envelope of the signal coming from the guitar in such a way that the overall sound gives you the impression that it is *not* a guitar at all. Instruments such as oboes, violins etc, can be successfully simulated in this way.

Attack and decay rates are altered by potentiometers and the length of the sound (the sustain) is controlled directly by the musician, holding down the pedal with his

foot for as long as he wants. Thus the major variables of the envelope are all under the guitarist's command.

If you built the Fuzzbox in the March issue of Hobby Electronics (pp 54 to 56), and housed it inside the same style of case that we used, we feel sure that you were impressed by the neat appearance and versatility of the case. Our designers were so pleased with it that they decided to use it for the Envelope Generator too. In fact, the projects can be used as complementary effects to produce further exciting possibilities.

Construction

Build up the printed circuit board (PCB) first, according to its overlay in Fig 2. It's a good idea to use PCB pins for each connection point to controls, switches etc, as this means you can fasten the board into its final position and wire it up last.

Insert and solder components in the following order: resistors, IC socket, capacitors

and the transistor.

Finally, push the IC into its socket — making sure it is the right way round. Remember that the IC will be marked with either a dot or a notch which indicates the end where pin 1 is, and this end should be lined up with the notch shown in the overlay.

Put the board aside now and concentrate on the case.

Assuming that you use the same



style of case as us, your first job is to adapt the internal switch so that it doesn't latch. Unsolder the screened lead which comes attached to the switch and remove it completely from the case for the time being. Unscrew the two self-tapping screws which hold the switch in place and then remove the switch itself. Underneath the coiled spring which winds around the push-button section of the switch you will see a thin metal catch which engages inside the switch body as the button is pressed, holding it in and releasing it, alternately. Pull back the spring with your finger and, with a pair of fine, snipe-nosed pliers pull out the catch. The switch should now form a momentary action, push-button ie, push in — on, release — off.

Next, mark and drill the case for the two pots, the bypass switch, and the jack socket and mount them all in their positions. You will have to bend the tags on the jack socket at right angles, in order that the case bottom fits. Secure the PCB to the inside of the case (we found that a pad of double-sided adhesive tape is ideal for this purpose) and then commence wiring up the project. Wire between the pots, SW 1 & 3, the battery clip and the PCB first, using thin multi-strand wire, as shown in Fig 2. Finally, all audio signal leads should be made using thin screened cable, to help prevent interference and noise pickup. The output lead is, of course, the lead supplied with the case, and comes complete with jack plug.

Now you can try out the Envelope Generator with your guitar and see how it sounds. With practice and care you should be able to imitate other instruments very rapidly.



Parts List

RESISTORS (All 1/4 W, 5%)

R1	10k
R2	4k7
R3	1k0

POTENTIOMETERS

RV1	220k linear potentiometer
RV2	100k linear potentiometer

CAPACITORS

C1	220n polycarbonate or ceramic
C2	22u, 16 V tantalum
C3	10n polyester or ceramic
C4	100n polyester

SEMICONDUCTORS

IC1	MC3340 voltage controlled attenuator
Q1	BC183 NPN transistor

MISCELLANEOUS

SW2	single-pole, double-throw latching push-button switch
JK1	1/4" jack socket (with SW3)

Case to suit (with SW1 — see Buylines)
Knobs to suit
PP3-type battery + clip
8-pin IC socket

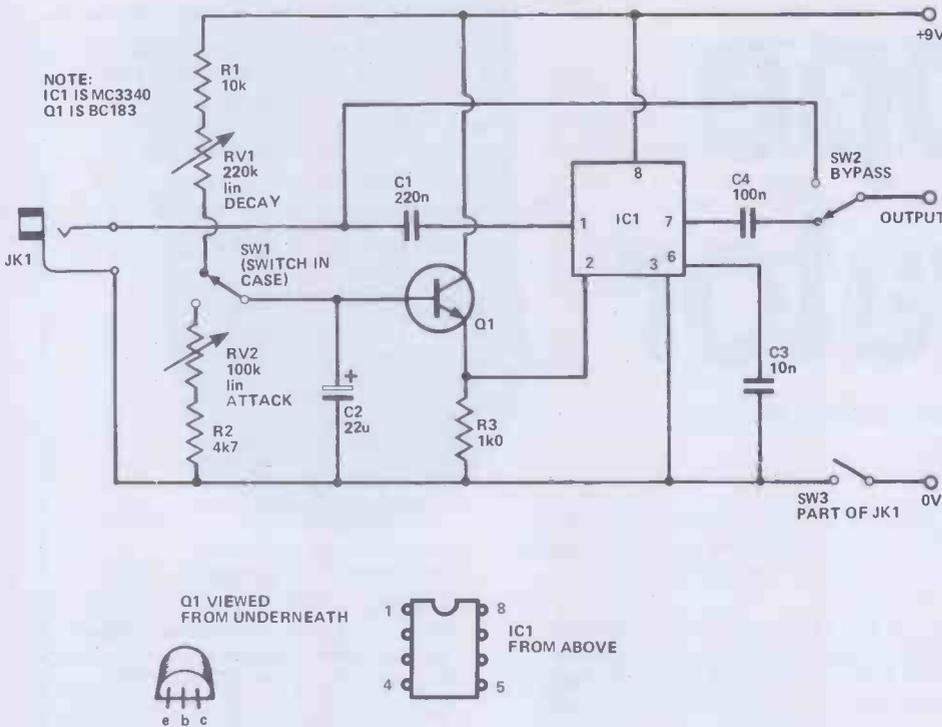


Figure 1. Circuit of HE Envelope Generator

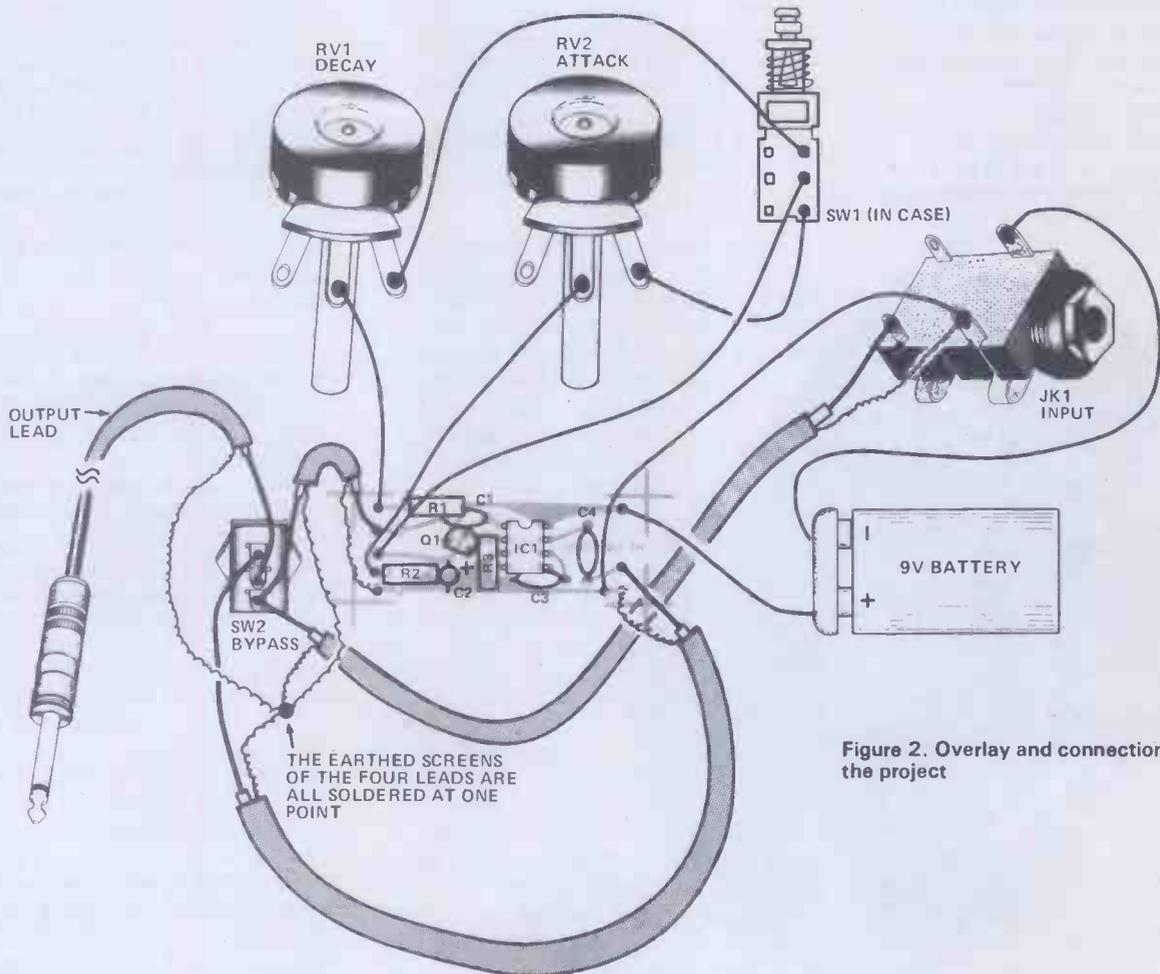


Figure 2. Overlay and connection details of the project

How It Works

One of the main parameters which allows us to differentiate between classes of musical instrument is the envelope of an instrument's sound output. Typical envelopes of four common instruments are shown in Fig. 3. Some, like the oboe or the guitar, have a fast attack (rise rapidly in volume at the beginning of the note) and others, like the violin, have a slow one. Similarly, sustain (the overall length) and decay (the fall in volume at the end) vary from instrument to instrument. The HE Envelope Generator controls these variables so that when a guitar is played through it, a different envelope can be impressed on the note. Figure 4 shows how a voltage controlled amplifier (VCA) is used along with a control voltage (which varies as the required envelope) to produce the desired effect.

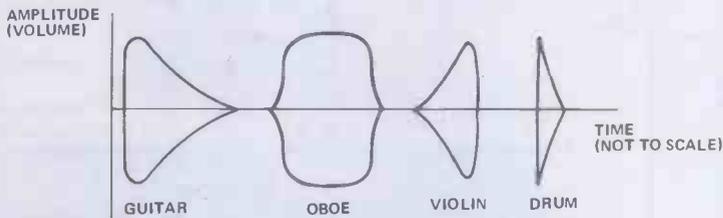


Figure 3. Envelopes of some common musical instruments

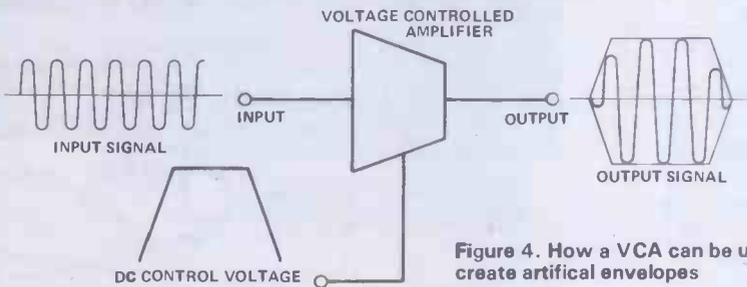


Figure 4. How a VCA can be used to create artificial envelopes

Integrated circuit IC1 is a complete, single-chip VCA and the guitar signal is applied via C1, to pin 1. The output signal comes from pin 7.

Pin 2 of IC1 is the control voltage input and a DC voltage of 0 V gives maximum output; ie, all the guitar signal is fed straight through to the output. Actually, the IC amplifies the signal

somewhat, so the output will be larger than the input by a factor of four. A voltage of 6 VDC at the control input reduces the output signal to zero. Voltages in between the two produce a corresponding level of output.

All we need now is a source of control voltage which varies between 6 V and 0 V (down, then up — not up, then

down, as in Fig. 4) in the form of an envelope.

The pedal's internal switch SW1 is shown in its resting position in Fig. 1. Capacitor C2 is charged up to about 7 or 8 VDC via R1 and RV1. Transistor Q1 acts as a high impedance buffer (ie, it has a high input resistance, therefore it does not discharge the capacitor) in a circuit configuration known as an emitter follower. In other words, the emitter voltage is almost at the same voltage as the base (which is connected to C2). Because of the semiconductor junction between base and emitter, the emitter voltage is about 0.7 V lower than that of the base. Pin 2 of IC1 is therefore at a voltage of about 6 to 7 V and thus no output is obtained, whatever the amplitude of input signal to the IC.

When the foot pedal is pressed, SW1 connects C2 to RV2 and R2. Therefore, C2 discharges down to 0 V at a rate determined by the value of RV2. Thus the VCA control voltage falls likewise to 0 V and the guitar signal increases to maximum at the output. Potentiometer RV2 therefore controls the attack rate.

Sustain is set by the length of time the pedal is held down and SW2 is connected to RV2. When the pedal is released, RV1 is re-connected and C2 charges up (the decay control voltage) at a rate determined by the pot. Consequently the output signal volume decreases back down to zero.

Buylines

Magenta Electronics produce a kit for the HE Envelope Generator which includes case, PCB and all components and parts for £15.32. This price includes VAT but not p & p.

The case is obtainable separately from Magenta for £5.65, again inclusive of VAT but not p&p.

Please add 40p p&p, whatever size order you place with Magenta.

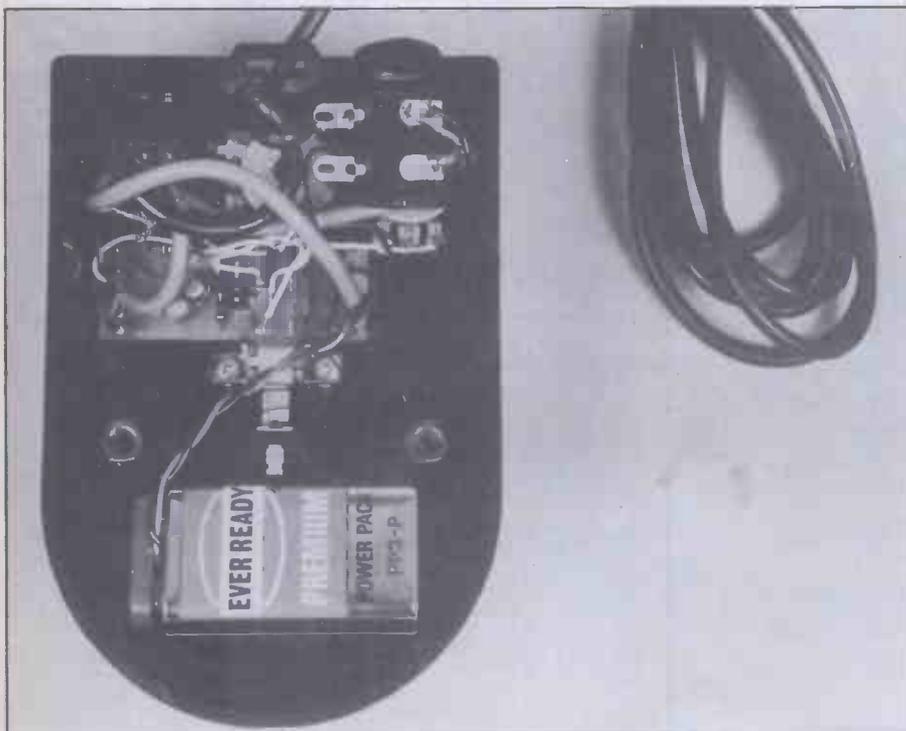


Figure 5. Internal view of the case showing how tight a fit it is. Note the use of screened cable for all audio signal-carrying leads

Get a great deal from Marshall's

CRIMSON ELEKTRIK HI FI MODULES		
CE 608	Power Amp	£20.09
CE 1004	Power Amp	£23.43
CE 1008	" "	£26.30
CE 1704	" "	£33.48
CE 1708	" "	£33.48
CPS 1	Power Unit	£19.52
CPS 3	" "	£23.52
CPS 6	" "	£30.00
CPR 1	Pre Amp	£32.17
CPR 1S	" "	£42.52


SINCLAIR INSTRUMENTS		
Digital Multimeter		
	PDM35	£ 34.50
"	DM235	£ 52.50
"	DM350	£ 72.50
"	DM450	£ 99.00
Digital Frequency Meter		
	PFM200	£ 49.80
Low Power Oscilloscope		
	SC110	£139.00
TF200 Frequency Meter		
		£145.00
TGF 105 Pulse Generator		
NEW		£ 85.00
LCD Multimeter		
	TM351	£99.00
LCD Multimeter		
	TM352	£49.95
Prescaler		
	TP600	£37.50

I/LP HI FI MODULES	
Power Amplifiers	
HY30	£ 7.29
HY60	£ 8.33
HY120	£17.48
HY200	£21.21
HY400	£31.83
Pre Amplifiers	
HY6	£ 6.44
HY66	£12.19
Power Supplies	
PSU30	£ 4.50
PSU36	£ 8.10
PSU60	£13.04
PSU70	£13.04
PSU180	£21.34
MULTIPLEX NICKEL CADMIUM CELLS	
Type S101 (HP4)	£ 0.98
Type SubC (HP11)	£ 1.75
Type SubD (HP2)	£ 1.95
Friwo Chargers for above	
Penlight 4: accommodates 1-4 size HP7	£ 5.50
Combibox FW611: accommodates HP7, HP11	
	£13.25

NOTE ALL PRICES NET. EXCLUDING VAT. POSTAGE/PACKING

New
Presensitised PC Boards, Developer. U.V. units.
Toyo miniature Fans 230v AC £9.95
Mini Metal Detector/Voltage Tester for locating cable under plaster £9.95
Flow/Speed Sensors for monitoring fuel consumption electronically in vehicles

Just one of the exciting Leader range

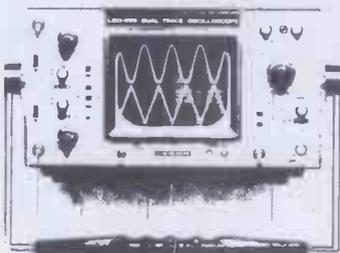

£299 + VAT

LB0508A OSCILLOSCOPE
With 20MHz DC bandwidth and 10 mv input sensitivity on a 5" screen this universal oscilloscope is suitable for a wide range of applications.

Send SAE for details of full range.

Marshall's 80/81 catalogue is now available by post, UK 75p post paid Europe 95p post paid: Rest of world £1.35 post paid.

A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW8 4TA.
Industrial Sales: 01-328 1009
Mall Order: 01-624 8582 24hr service.

Also retail shops: 325 Edgware Road, London W2, 40 Cricklewood Broadway, London NW2, 85 West Regent St., Glasgow, 108A Stokes Croft, Bristol.



68
LARGE
PAGES

The larger Catalogue that means
FREE POSTAGE IN U.K.
ADDITIONAL DISCOUNTS
KEEN PRICES
GUARANTEED SATISFACTION
GOOD STOCKS
We pay postage

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

ELECTROVALUE
FREE FOR THE ASKING
ELECTROVALUE LTD. (Dept. HE6) 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB
Telephone: (STD 0784) (London 87) 33603. Telex: 264475

GLOBAL ELECTRONIC ENTERPRISES

ELECTRONIC CONSTRUCTION KITS

SUPER CHIP 2
Full MW coverage, uses I.C. ZN414+2 transistors, easy to build diagrams. Good beginners project complete with case and loudspeaker. £8.25+P&P 75p

SUPER CHIP 1
Pocket earpiece radio. Performance and looks as above, complete with easy build plans. £6.95+P&P 65p

CRYSTAL RADIO
For beginners, no batteries required, complete with case and easy build plans. £2.25+P&P 60p

Money refunded if not satisfied provided goods are returned undamaged.
Post and packing included unless stated.
All units are checked and tested prior to despatch. All items suitable to availability.
P/Os and Cheques made payable to:

GLOBAL ELECTRONIC ENTERPRISES St. John's Works, St. John's, Bedford

PLASTIC INSTRUMENT CASES 110mm x 75mm in grey-black.....95p+P&P 35p
CAR RADIO Manual with speaker/fixing kit.....£9.25+ P&P 75p
OCEAN CAR STEREO, with built-in auto. stop.....£15.95+P&P 95p
STEREO Headphones, 8 ohm.....£7.75+P&P 45p
POCKET RADIO AM/FM/AIR band with speaker.....£8.75+P&P 75p
POCKET RADIO AM/FM with speaker and EIP.....£6.95+ P&P 75p
HAND ELECTRONIC Football Game.....£10.95
QUARTZ HALOGEN Handheld spotlamps. Plugs into car cigar lighter.....£8.75+ P&P 75p
800 watts Mains Dimmer with magic eye facility.....£4.95
SITCO CASSETTE Recorder D/C, small size 1.....£17.95+P&P £1.50
B.S.R. C175 Turntable with ceramic cartridge.....£19.95+ P&P £2.50
B.S.R. C182 with A.D.C. cartridge plinth and cover.....£38.50 P&P £2.50
LLOYTRON Professional Headphones 4-16 ohm coiled cord vol/control.....£12.95+P&P 95p

OHIO SCIENTIFIC COMPUTERS. Superboard 3 £159. Power supply kit £11.95. Modulator £3.50. Guard band kit £10 (converts the display to 50Hz and 32 lines of 32 chrs., gives 1,200 and 300 Baud tape speeds and increases the computing speed by 50%). Special offer: Superboard 3 + power supply and modulator kit + guard band kit ONLY £172. 4K extra ram £15.60. Wemon £19.95. Case £27. Cassette recorder £18. Caprom improved monitor rom £29.50. Assembler/Editor £25. Word processor £10. Display expansion kit 30 lines x 54 characters for superboard TWO £14.

PRINTERS supplied with free interface and word processor for Superboard and UK101, Seikosa GP80 £225. Oki Microline 80 £299. Epsom MX70 £295.

***SINCLAIR PRODUCTS** only are post free. sc110 oscilloscope £139, adaptor £4, rechargeable batteries £7.95, xl probe £8.05, x10 probe £8.86, carry case £8.80, pfm200 £52.40, adaptor £4, case £1.73, connector kit £11.27. PDM35 £32.95, adaptor £4, case £1.73, dm235 £56.50, dm350 £78, dm450 £107, adaptor £4, case £8.50, rechargeable bats. £7.95. Microvision TV £69. Adaptor £6.95.

***BATTERY ELIMINATOR KITS** 100ma radio types with press studs 9v £1.79, 9+9v £2.50, stabilized 9 way types 3/4/2/6/7/2/9/12/15/18v 100ma £3.12, 1 Amp £8.50. Stabilized power kits 2-18v 100ma £3.12, 1-30v 1A £8.50, 1-30V 2A £15.30. TTL and computer supplies 5V stabilized 1/2A £9, 3A £14, 6A £20. 12v car converter 6/7/2/9v 1A £1.62.

***T-DEC AND S-DEC. BREADBOARDS** t-dec £4.59, exp4b £2.84, exp300 £8.61.

***BATTERY ELIMINATORS** 3-way type 6/7/2/9v/300ma £3.50. 100ma radio types with press studs 9v £4.95, 9+9v £8.25. Car converter 12v input, output 4/2/6/7/2/9v 800ma £3.04.

***TV GAMES** AY-3-8600 + kit £12.99 AY-3-8550 + kit £9.26.

MEMORIES 2114 450ms £1.95, 4116 200ms £1.99, 4027 £1.30. All low current.

SWANLEY ELECTRONICS

Dept. HE, 32 Goldsel Road, Swanley, Kent
Postage £3.50 on superboard, £4.50 on printers and 45p on other orders. Lists 27p post free. Please add VAT except to sections marked with a * which already include it.

Clever Dick

Is he a man, a machine or just a figment of HE's imagination? Clever Dick, in whatever form, is back on duty

First letter I received this month, from G.S. Pierce of Halifax, West Yorkshire, contained two rude cards: one for the Editor's car and the other for the smallest room in the building. Thanks for cheering us up, and we'll see if a binder will cure your stomach problem.

Number one letter this month is yet another query about the HE Minisynth.

Dear Clever Dick
I have a question:

How can you prevent "Mini Synth With Memory" (HE, Nov. '80) from making its ignorance warning hum?

I would like to inform you that I have successfully built and installed the "Home Security System" (HE August '79). I have just turned 12 on the 5th February, 1981. I have been reading HE since the first issue appeared in Nov. 1978.

W.E. Meyer
Pretoria, Republic of South Africa

Minisynth is designed around one clever chip, the TMS 1000N MPO 121, and the warning it gives you if a note hasn't been played for several minutes cannot be suppressed. So you'll have to live with that one.

Congratulations on building the Home Security System: you'll need it to protect all those back-issues.

Nice short one next.

Dear CD

1) Could you tell me where I can get 1:1 transformer; 50 V, 2 A for use in a power supply to isolate the outputs from each other?

2) How about publishing a design for CB in the near future?

R. Sewell
London
P.S. Thanks for a great Mag
P.P.S. Short enough?

The transformer you describe would be very difficult to come by and is likely to be expensive. One way to get the isolation is to use two transformers (each 240/50 VAC) back-to-back (240 V windings coupled) but this arrangement would be costly and inefficient. I don't know what you're trying to do, so it's difficult to give any other suggestions.

For an answer to your second question, see the answer that the Editor gave to V.M. Holness in Your Letters on page 47 of last month's issue.

Dear C.D.

I would like to make the diesel horn (Feb '81) for my 00 scale railway. This works

from 12 volts, whereas your project only uses 9 volts. Not being made of money, would it be possible to use the track's 12 volt supply.

The IC's could take the 12 volts but the capacitors would have to be 16 or 25 volts.

I know it is not your fault, but if there are any of those other people in your office, tell them to use 12 volts instead of the 9 volt power supply.

Peter Day
Camberley, Surrey

Yes you can make use of the 12 V supply, but make sure that it comes directly from the power supply and not through the speed controller first (some of these controller/power supply units only provide a controlled output). If you did use 12 V direct then the electrolytic capacitors would have to be replaced with higher-voltage types. A better suggestion is to derive a regulated 9 V supply from your 12 V supply.

The trouble with your last suggestion is that most people here are not model train addicts.

Call for help next.

Dear CD

This is the first time I have written to your magazine so could you please please answer my questions.

I would like to know who sells the AY-3-8610 IC and how much it costs. Also could you have a project on making a TV game as I am dying to make one.
P. Smith

The AY-3-8610 is a Superspace TV games chip and, as we discovered, difficult to get hold of. We doubt whether most suppliers want to sell it 'one off' because it is so specialised.

In answer to your second query, we have no plans to publish a TV game project. Because the electronics is so complex in these games we leave them to our sister mag ETI. (A space invasion game was published in the November '80 issue of ETI.)

Dear C.D.

I've been wanting to construct a decent spec amp for ages. Seeing the project advertised in March edition of HE for the preamp in April's issue, I looked forward to it with enthusiasm.

Now that I've found it's going to cost me about £62, just for a preamp, I'm quite dejected.

Surely you could've struck a deal for your fans whereas a Hobby Print could be available.

I mean £12 just for a P.C.B.; it's



ridiculous.

Come on now, do your ever faithful fans a favour. We're not all rich.

PK Lad
Ashton U. Lyne, Lancs

I had better make something absolutely clear about HE's hi-fi project: the pre-amplifier and power amplifier together make a true hi-fi system. Trouble is, good (even moderate) hi-fi costs money. A good hi-fi pre-amp can cost you a lot more than £62. And if you saw that PCB with all the component position marked out and the copper tracks pre-tinned, you'd see that it's good value for £12.

But stick with us: we hope to be featuring another much lower-priced system in coming issue — provided we think it is up to scratch.

Last one is from someone describing himself as Prof. S. Unwin.

Dearus Mastermindibold Dick,
Oh, deep joy, deep joy, at writing to your column there is! Howeverlode, problem there is, mine for the asking. Recently fitted headphone socketer fittilode on the tape-recording contraption had speakibolds in parallel and sound was very much coming from the centre of the Id. Thenilode, with speakilodes in series, the musipoo was very much surroundsoundibold, although actual watts was reduced oh yes. Could you possibold supply answer in next few weeks?

Await deep joy at your reply,
Prof. S. Unwin
P.S. Remember, T.X. Radials give maximost milodes.
P.P.S. Actual Question: Why is this?

Well, why is it? Maybe some of you out there will be willing to help the 'Professor'. Binder to the reader sending the best suggestion.

Enough is enough for this month. Oh yes, there was something I had to mention: we will be unable to send replies by post for the time being, even for letters sent with an SAE. Sorry about this, but we need some time to clear the backlog of your queries. Stay lucky — and patient.

HE

Famous Names

Heinrich Rudolf Hertz

With 'Radio' as the main feature this month, it seems appropriate to devote this third part of our Famous Names series to Heinrich Hertz - the man who discovered radio waves

AFTER SO MANY years of calling the units of frequency cycles-per-second, it still takes old-timers a while to get accustomed to using the name Hertz. Surprisingly few people associate the name Heinrich Rudolf Hertz with the discovery of radio waves, but the use of Hertz (usually shortened to Hz) to denote frequency shows a deserving recognition of this fact.

Hertz was born in 1857 and after a distinguished school life, he entered Berlin University to study under the celebrated Helmholtz. Helmholtz was one of the last of the great Victorian scientists — one of those men who are equally happy in any branch of science. Two of his contributions to Physics are still remembered in the textbooks: the Helmholtz coils and the Helmholtz resonator. A pair of Helmholtz coils consists of identical coils spaced one coil-radius apart, and their peculiarity is that the magnetic field between them varies only slightly from place to place between the coils. The Helmholtz pair is therefore the starting point for any TV deflection coil design. The Helmholtz resonator is a bottle with a narrow neck, and its resonance to sound waves is decided by the volume of the bottle and the dimensions of the neck. If you happen to be in the business of designing cabinets for hi-fi loudspeakers, then the Helmholtz resonator is pretty important. All in all, young Hertz must have had a good grounding both in electromagnetism and in wave motion, and the success of his studies was recognised in the award of a doctorate by the University in 1880.

He started on a career of research in electromagnetism. In 1883 he became aware of Clark Maxwell's work on electromagnetic theory, a brilliant but neglected work which predicted the existence of waves which would be invisible, but which could travel at the speed of light. Hertz was convinced that Maxwell's theory was correct, and that these waves existed in reality as well as in mathematical equations.

Hertz directed his very considerable experimental ability to the problem of generating and detecting electromagnetic waves. He reasoned that very high frequency oscillations should behave in a way similar to light waves, and decided that the resonant circuit around a spark-gap would probably provide the best conditions for generating suitable oscillations.

His apparatus, shown in Fig. 1, is now one of the famous landmarks in radio history. It consisted of an induction coil



capable of generating about 30 kV of low-frequency AC, and a spark gap between two copper spheres. The inductance of the leads to the spheres plus the capacitance between the spheres constituted a resonant circuit. The resonant frequency was high, much higher than the frequencies which were to be used later by Marconi and others. Recreation of Hertz's experiment has, in fact, shown that the strongest transmitted frequencies were in the lower microwave range.

The receiver was equally simple, as can be seen from Fig. 1 — a pair of copper spheres at the ends of short pieces of wire. This constitute what we would now call a dipole aerial, and the principle on which Hertz was pinning his hopes was that electromagnetic waves picked up on the wires would create a sufficiently large electrostatic field to ensure a high voltage across the gap between the spheres. Hertz's ideas worked out perfectly. When the transmitter was sparking away, sparks could also be seen between the spheres of the 'receiver'. There was no connection of any sort between the transmitter and the receiver. None, that is, apart from the electromagnetic waves which Maxwell had so confidently predicted in 1864. It was a perfect vindication of Maxwell's theory — but the evidence was not strong enough for Hertz.

Hertz felt that, in order to vindicate Maxwell's theory fully, he must show that there were waves passing from the transmitter to the receiver, and that these waves were physically similar to light waves. He started on a long and ambitious project of discovery using methods which were ideally suited to the short wavelengths which his equipment generated. Oddly enough, had he generated lower frequencies, his measurements would have failed — these are the sort of happy accidents which continually seem to occur in the history of science.

Practical Measurements

Measurement of the wavelength of the radio waves was the first objective. The standard method of measuring the wavelength of light makes use of wave interference. Light

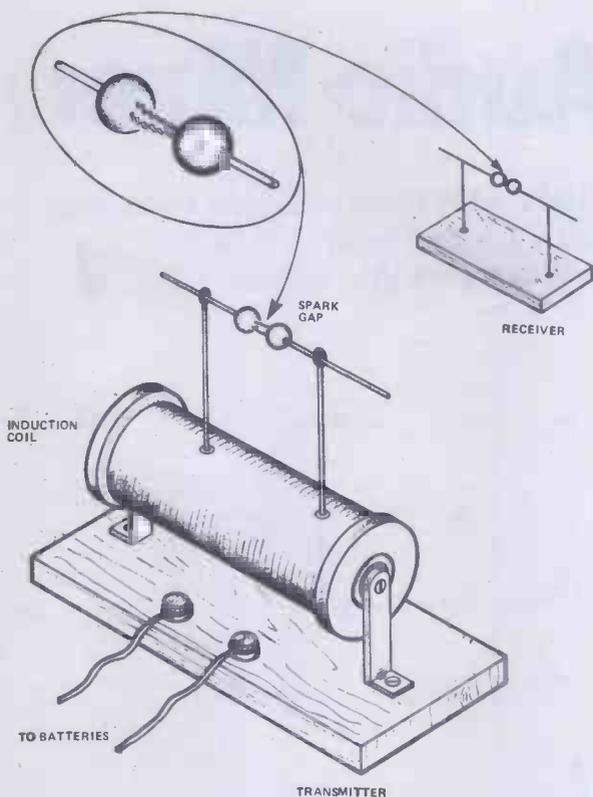


Figure 1. Hertz's transmitter and receiver. The induction coil is a DC to AC converter producing high-voltage pulses (about 40 kV)

from a source is split into two beams (Fig. 2) and these beams are aimed at a screen. Light rays which have travelled exactly the same distance will reinforce, causing a bright spot, but when the distance difference between the paths is half a wavelength, or any odd multiple (3,5,7,9, etc) of half a wavelength, the waves cancel causing a shadow. By measuring the distances between these 'fringes' of light and dark, the wavelength of light can be calculated.

Hertz used this technique, but since the waves could not be seen he had to use small spark-gap detectors instead of a screen. The wavelength of his apparatus turned out to be a few centimetres.

Hertz also measured the speed of the waves, using once again a version of the classic methods for measuring the speed of light. These make use of mirrors revolving so fast that a ray of light which has been delayed by travelling a long distance to a reflector and back finds the mirror at a

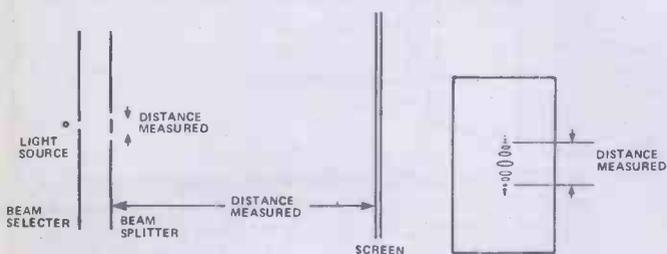


Figure 2. The method Hertz used to measure wavelength of light: (a) a slit in an opaque sheet selects one ray of light, which is then split into two by close-spaced splits in another sheet. The image projected on the screen (b), when examined with a microscope, consists of alternate dark and light bands caused by wave interference. The wavelength can be calculated from the distances indicated

different angle when it returns, so shifting the reflection. The amount of the shift, together with the speed of rotation of the mirror and the path distance, can be used to calculate the speed of the light.

To make this measurement, Hertz had first to establish that radio waves were reflected, and he was delighted to find that the newly discovered waves reflected from metal sheets in exactly the same way as light waves do, with the angle of reflection equal to the angle of incidence (Fig. 3). He also found, incidentally, that radio waves were refracted; that is, they changed direction as they passed from one material to another exactly as do light waves.

Having made these points, Hertz succeeded in measuring the speed of the new waves. This speed turned out to be 300 million metres per second, the well established value for the speed of light. Hertz now felt that he had indeed discovered some of the waves which Maxwell had predicted. The work had taken him four years, from 1885 to 1889.

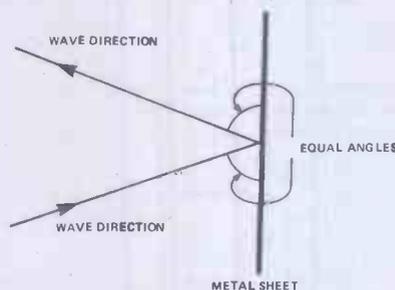


Figure 3. Wave reflection. Radio waves are reflected from a metal sheet in just the same way as light waves are reflected from any mirror

Road To Radio

In 1889, Hertz was appointed Professor of Physics at Bonn University. His work with electromagnetic waves was over for the time being, and his new line of research was to be on gas discharges, following the work of Geissler. His report, 'Electric Waves', was not published until 1893, because his health was seriously declining — a lung infection which he had disregarded was now recurring.

He died in 1894, aged 37, with a brilliant career behind him, and a promise of much more to come. His 'Miscellaneous Papers' was published in 1894, and his 'Principles of Mechanics' in 1899. These works were not his epitaph, though they hinted at the remarkable discoveries which he might have made. There is little doubt that long-distance radio would have been established much earlier than 1910 had Hertz lived. As it was, his work started an immense frenzy of experimental activity, of which the work of Marconi is best known to us. We shall remember, though, that Hertz's work caused immense excitement, and practically every country can boast of a radio pioneer. Of these who disputed Marconi's claim to be first with long-distance radio transmission, Tesla in Czechoslovakia and Popov in Russia were both serious contenders.

There is no dispute about the source of the work, though. Maxwell blazed the trail, and Hertz built the road along which all the later radio experimenters travelled. Now that we no longer measure magnetic flux in maxwells, it seems entirely appropriate to measure frequency in hertz.

Quick Project: Audio Mixer

Can it be true — a complete multichannel audio mixer project which uses only one transistor? This easily-constructed Reader's Design proves that it is. It's cheap, too — less than just a couple of pounds will buy you all the components.


This simple circuit sums the three audio signals entering at the transistor's base and produces an amplified output from the collector. More inputs can be added if required, each additional input needing a potentiometer, capacitor, resistor and input socket.

Output of the circuit is approximately 500 mV (sufficient to drive most amplifiers) for an input signal of 5 to 500 mV. Thus guitars, microphones and low-level audio signals from tape-decks etc, can be mixed to personal requirements.

Use a small metal box to house the project — a die-cast aluminium one is ideal.


All leads from input sockets to potentiometer controls, from the controls to the board, and from the board to the output socket should be made using screened cable. Make sure that you connect the screen (not the signal lead) of the cable to 0 V.

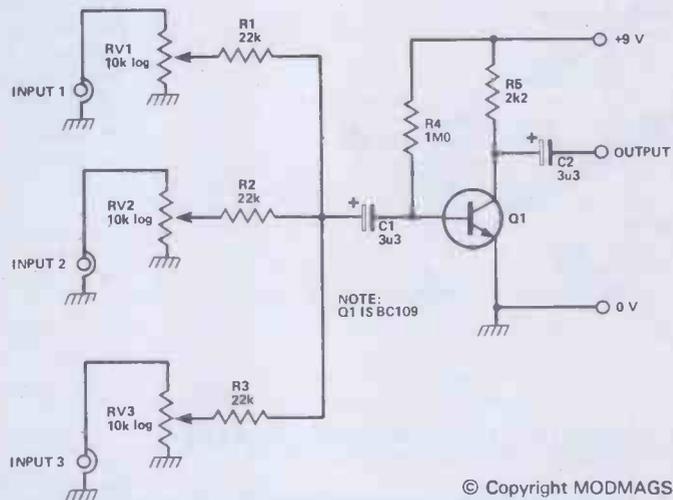Switched potentiometers can be used if you want complete isolation of any one signal.



© Copyright MODMAGS Ltd.

Figure 1. Circuit diagram

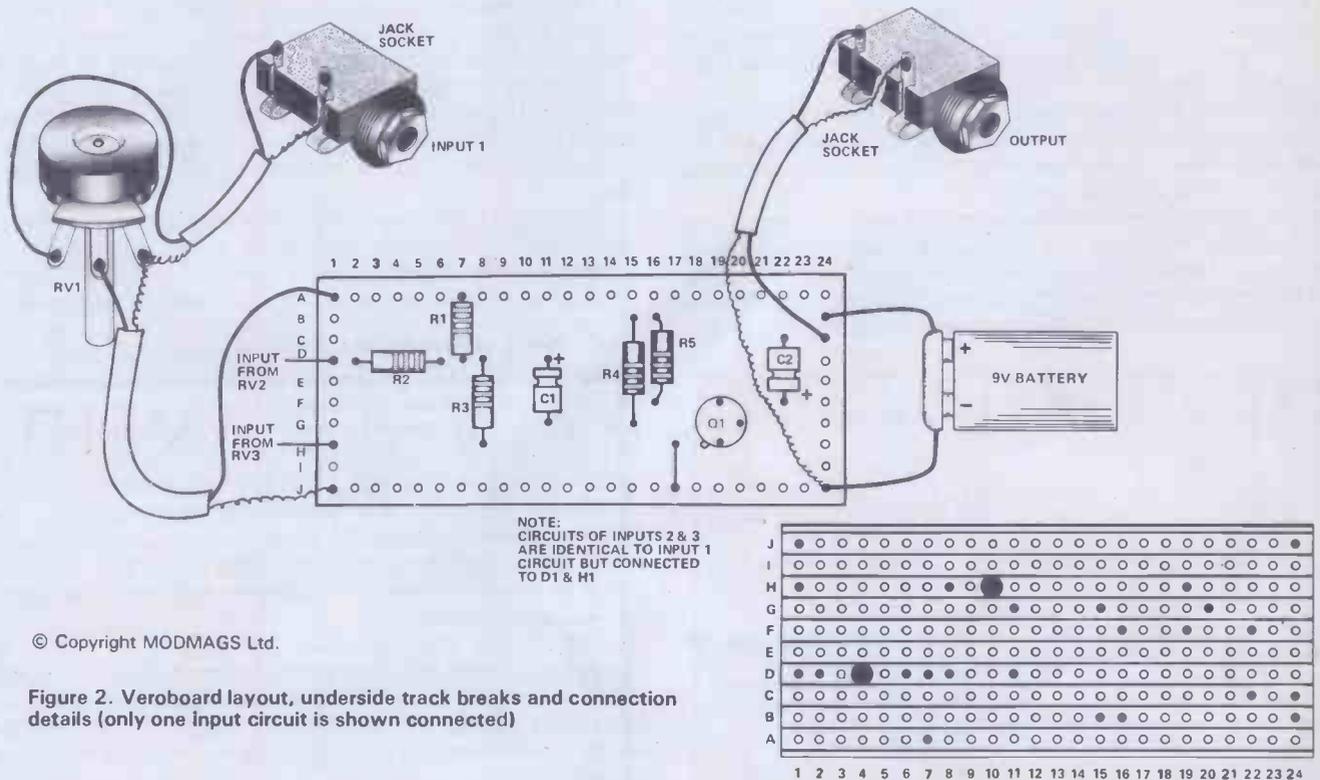

© Copyright MODMAGS Ltd.

Figure 2. Veroboard layout, underside track breaks and connection details (only one input circuit is shown connected)

Video Disc Update

Hugh Davies describes recent developments in video disc systems

IN THE DECEMBER issue of HE, the article View Into Video Discs (pp 18 to 22) opened with the statement about the video disc systems: '...in 1981 we should start to see them in the UK'. The article went on to describe the activities of the three largest companies — Philips, RCA and JVC — concerned with the development of video disc players (the hardware) and the discs (the software).

At the time of writing (April '81) there are still no discs and players available in the UK. This article gives you a brief update on events.

LaserVision

Philips was originally on target for a May '81 launch of its LaserVision system but has delayed the launch until the autumn. Until December 1980, the system was called VLP — video long play.

According to Philips, a mid-year launch was commercially less attractive because of the unexpected impact of the recession, and it considered that the autumn would be the right time.

Philips said that, although the players and discs were already in production, several problems had been experienced. One of these had been associated with the master tapes submitted by some of the film companies. A spokesman for Philips said: 'We've been very strict about quality'. Although accurately specified, tapes of inferior quality or incorrect cutting lengths had been submitted. It was also said that the quality of LaserVision is such that any defects in the master tapes are immediately apparent — much more so than would be noticed on video cassette systems.

Another problem was that of low initial yield from the factory producing the discs at Blackburn. Philips has used a different production process in the UK than the one used by Magnavox, its subsidiary in the US. The spokesman said that the factory was not up to sufficient yield yet.

Not only does Philips want to have enough discs for the launch but it also wants enough in reserve for back-up orders.

The LaserVision players are being produced in Holland and Belgium.

Selectavision

RCA launched its Selectavision video disc system to the US trade in March this year. A satellite transmission from New York was used to reach 5,000 dealers. RCA claimed that Selectavision was its biggest launch of a product in business history, with \$20 million spent on advertising and promotion and with 500,000 disc albums delivered to dealers in 50 American states.

According to Ken McKee, manager of RCA's European Technical Relations, hi-fi dealers handling video cassette recorders were less receptive to Selectavision than were other dealers, and saw it as a threat to their existing market. A VCR system having many technical features can cost between \$600 and \$700, while the Selectavision player has been selling for between \$450 and \$500. It appears that customers with money to spend prefer VCR players with all the extra features — including the ability to record. The irony is that although you can't record material onto a video disc, it is likely to produce a higher-quality picture and have a longer life than a video cassette.

RCA's target for a launch in the UK is still vaguely pitched at 1982.

VHD

Compared with the other two companies, JVC has been bold about the launch dates for its VHD (video high density) disc system. These are October '81 for Japan, February '82 for the US and June '82 for the UK. A total of 150 disc titles are planned for each launch.

According to a spokesman for JVC, the VHD system is undergoing some changes to make it comply with the American consumer standards. One change is to make the player less susceptible to interference from radio transmissions in the band 900 to 1200 MHz — a band likely to be allocated to radio hams in the US and CB-ers in the UK.

The spokesman went on to say that there had been less problems with the discs, which were at present undergoing test pressings with Thorn-EMI in the UK.

HE

PARNDON ELECTRONICS LTD.

Dept. No. 22, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.
 £1.00 per hundred mixed. (Min 10 per value)
 £8.50 per thousand mixed. (Min 50 per value)
 Special stock pack 60 values, 10 off each £5.50

DIODES: IN4148 3p each. Min order quantity — 15 items.
 £1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base — solve those programming problems.
 4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each.

DIL SOCKETS: High quality, low profile sockets.
 8 pin — 10p. 14 pin — 11p. 16 pin — 12p. 18 pin — 19p. 20 pin — 21p.
 22 pin — 23p. 24 pin — 25p. 28 pin — 27p. 4C pin — 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
 MIN. ORDER — U.K. £1.00. OVERSEAS £5 — CASH WITH ORDER PLEASE

Bargain Packs

a. 200 mixed ceramic capacitors £2.00
 b. 100 mixed polystyrene capacitors £2.20
 c. 300 mixed P.C.B. components £1.95
 d. 1lb. hardware pack inc. B/A mitso bolts, P. clips cable markers, clamps, fuse holders, etc. £1.00
 e. 300 mixed 1/4 and 1/2-watt resistors £1.95
 f. 150 mixed 1/4 and 2-watt resistors £1.95

Mini relays
 12v Mini Relays (conventional type).
 2 pole change over type 1, 700R 10 for £3.50
 2, 430R or £0.40 ea.

12v Mini Relays (conventional type).
 4-pole change over type 1, 1280R 10 for £5.00
 2, 430R or £0.80 ea.

Plug in bases to suit 10 for £2.50. £0.30 ea.

Project Boxes
 High impact boxes (ABS) black. Lids retained by four screws into brass inserts. Internal printed circuit slots are provided in boxes. Internal dimensions (W x D x H).
 MB1 Length 75 x Breadth 56 x Depth 35 (3in. x 2.2in. x 1.4in.) £0.88
 MB2 95 x 71 x 35 (3.7in. x 2.8in. x 1.4in.) £0.95
 MB3 115 x 95 x 35 (4.5in. x 3.7in. x 1.5in.) £1.20
 MB4 207 x 122 x 77 (8.1in. x 4.8in. x 3.0in.) £2.60
 T3 71 x 46 x 22 (3in. x 2in. x 1in.) approx. ins 84p

Plastic Project Boxes
 Blue Box built to house power supplies, speed con-

trols, etc. with two compartments. One to house the transformer the 3in. x 2 1/2in. x 2in. One to house P.C.B. etc. Size 1 1/4in. x 2 1/4in. x 2in. ED.50. Small Blue Box, will house 500VA transformer and/or small P.C.B., etc. Size 2 1/2in. x 1 1/2in. x 1in. £0.40

Sub-Minature Toggle Switches
 Ideal for models, etc. Rating 2 Amp at 240V A.C. with fusing hole 7mm.

a. S.P.S.T. at £0.65
 b. S.P.D.T. at £0.75
 c. D.P.D.T. Centre off at £0.95
 d. D.P.D.T. at £0.90

SPECIAL OFFER

270 off modern Jap full spec. caps, comprising of:

QTY.	QTY.
25-22mf-50v	25-47mf-25v
25-47mf-250v	25-100mf-25v
25-10mf-25v	25-150mf-16v
25-22mf-16v	25-150mf-16v
25-22mf-35v	25-220mf-16v
25-33mf-25v	10-470mf-35v
	10-1000mf-35v

ALL P.C.B. MOUNTING
 ABSOLUTE BARGAIN £17.50
 (Rec. retail price £47.00)

P.&P. 50p. Send s.a.e. for list. Many bargains in plugs and sockets, leads, aertials, microphones, etc, etc.

POP'S COMPONENTS

38/40 LOWER ADDISCOMBE ROAD
 CROYDON, SURREY. 01-688 2950

★ POWERFET AMPLIFIERS ★

Conservatively rated, high quality designs with substantial heatsink/mounting bracket.

VAT inc. prices Post & packing 75p on P.F.A. orders

CA3080E	70p
CA3140E	45p
MC3401	30p
TL081	29p
TL082	55p
2102	60p
2114	240p
4001B	17p
4011B	17p
4013B	40p
4016B	40p
555	25p
709	15p
710	25p
733	50p
741	18p
78L05	29p
78L12	29p

POWERFETS
 BD512 (60v, 1 1/2A, Pchan.) 90p
 BD522 (60v, 1 1/2A, Nchan.) 85p
 VN67AF (60v, 2A, Nchan.) 80p
 2SJ49 (140v, 100w, Pchan.) 340p
 2SK134 (140v, 100w, Nchan.) 340p

SCOPE TRACE DOUBLER P.C.B.
 Built CW shift, chan. select, chopper controls and instructions, useful display from DC to 10MHz. Runs from 9V battery £9.95

H.A. 1388 £1.95. Heatsink for above 40p.

H.E. PUBLIC ADDRESS AMPLIFIER.
 Component set including H.A. 1388 and super low noise input transistor. (Excludes, board, box and controls). £2.95.

J. W. RIMMER

P.&P 35p Mail orders to 148
 Quarry Street, Liverpool L25
 6HO. Tel 051 428 2651.

Technical enquiries to 367 Green Lanes, London N4 1DY. Tel 01-800 6667

ADVERTISEMENT INDEX

Ambit International	2	Maplin	68
Arrow Audio Centre	32	Marshalls	54
Bi-Pak Semiconductors	38	NIC Models	32
BK Electronics	30	Parndon Electronics	59
BNRS	63	Popps Components	59
Boss Industrial	41	T. Powell	28
J. Bull (Electrical)	46	Precision Petite	50
Butterworths	29	J. W. Rimmer	59
Circolec	30	Selray Shop Co	63
E.D.A.	30	Silica Shop	34
Electron-Kit	30	Swanley Electronics	54
Electronize Design	32	Tangerine Computers	67
Electrovalue	54	Technomatic	14
Global Electronics	54	Tempus	36
G.S.C.	19 & 65	TK Electronics	50
ICS	19	Two & One Components	19
ILP	4 & 5	Unilab Ltd	32
LEM	50	Vero Electronics	41
Magenta Electronics	22 & 23	Watford Electronics	9

Infra-red Remote



Controller - 2

The second part of this simple-to-build project, designed by TK Electronics, gives details of the Transmitter

IF YOU REMEMBER, last month we gave details of the Receiver/Controller construction, so this month's episode is taken up with that of the Transmitter. It is a somewhat trickier circuit to build, not because it is any more complex than the Receiver/Controller, but because it is a lot more compact. Design of the printed circuit board (PCB) is, in fact, almost a work of art. When building it up take great care not to form solder bridges across copper tracks on the board and not to overheat components. The procedure is as follows.

Construction

First, insert and solder all components into the PCB, including the push-button PB1, but not the two LEDs or capacitor C1. The overlay in Fig. 2 shows component locations.

Next, fasten the two LEDs to the case using mounting clips, so that

the cathodes of both devices are positioned nearest to the side of the case which the hole for the push-button is closest to. Now, cut the LED leads to a length of 7 mm from the box side.

Position the PCB into the case underneath the LED leads so that PB1 fits into its mounting hole, and solder the LED leads to the pads on the board. *Do not overheat the LEDs* as damage may result and, because they do not emit visible light, it is thus impossible to see if they are not working.

Solder the battery clip to the correct pads on the copper track, ie red to that marked '+' and black to that marked '-', then solder capacitor C1 on to the same pads making sure that you polarise it correctly.

Finally, connect a battery to the clip, insert it in the case and screw on the case back. The Transmitter is now complete, and you can try it out with the Receiver/Controller.



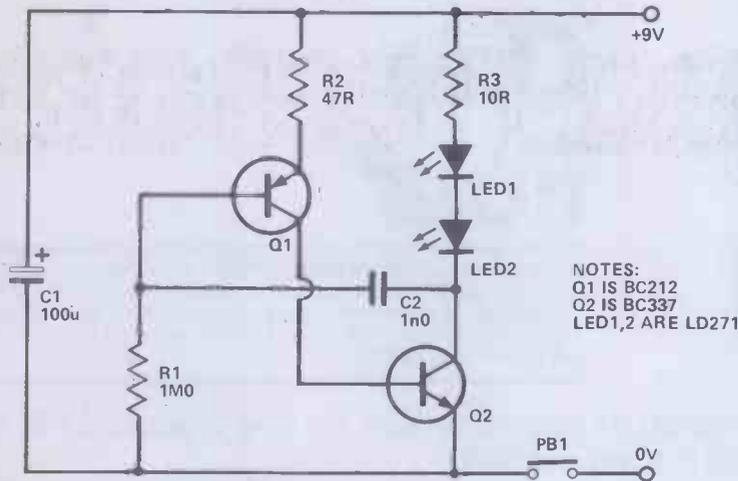


Figure 1. Circuit of the infra-red transmitter

Parts List

RESISTORS (All ¼W, 5%).		Q2	BC337, NPN transistor
R1	1MΩ	LED 1,2	LD271, Infra-red LED
R2	47R		
R3	10R		
CAPACITORS		MISCELLANEOUS	
C1	100μ, 10 V electrolytic	PB1	printed circuit mounting push-button switch
C2	1nF ceramic	PP3-size battery + clip	
SEMICONDUCTOR		Case	
Q1	BC212, PNP transistor	PCB	

Left. View of the project after the PCB and the two LEDs have been soldered.

Below. Capacitor C1 and the battery leads solder to the back of the PCB.



NOTE:
C1 AND BOTH LEDs MOUNT UNDERNEATH THE BOARD AFTER INSTALLATION INTO THE CASE

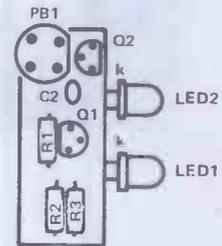


Figure 2. Overlay of the PCB


Buylines

Kits for the receiver (£4.83 including VAT) and the transmitter (£10.35 including VAT) are available from TK Electronics (HE) 11 Boston Road London W7 3SJ.

Please add 50p p&p to the total order. The receiver kit includes the PCB and all parts to make up the board; the transmitter kit includes PCB, all parts and the hand-held case. Also supplied with each kit is an instruction leaflet. When building your two kits, follow either the supplied leaflet or our instructions, as small discrepancies will occur in component numbering. Both sets of instructions are, however, correct.

How It Works

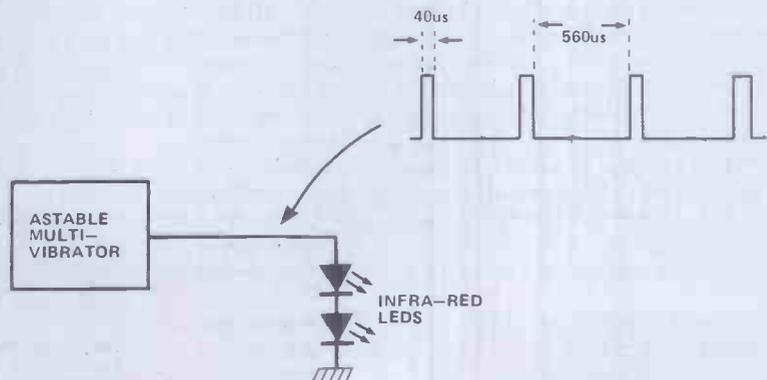The transmitter consists of an astable multivibrator producing a rectangular waveform, at a frequency of approximately 1700 Hz. Two infra-red LEDs are driven by this multivibrator oscillator and thus emit infra-red light, pulsed at the same frequency.



Transistors Q1, Q2 form a standard multivibrator circuit, the frequency of which is determined by the value of components R1, R2 and C2. Power to the circuit is controlled by push-button PB1, thus when the transmitter is not in use no current is drawn from the battery.

Infra-red LEDs 1 and 2 are inserted in the collector circuit of Q2 so that whenever the transistor is on, the LEDs emit infra-red light.

The values of R1, R2 and C2 are such that the two transistors are on, ie they conduct, for about 40×10^{-6} s (40 μs) and then remain off for 560 μs in every cycle. In this way the average current drain on the battery is kept to approximately 20 mA, while the LEDs are actually being driven by pulses of over 400 mA. This current is supplied by C1. Because of the short periods for which the transmitter is in operation, long battery life can be expected.

CB

Breaker One Four

The publishers of HOBBY ELECTRONICS would like to point out that it is as present a contravention of the Wireless Telegraphy Act of 1949 and 1968 to use, manufacture, install or import CB transmitting equipment. It is not the intention of Modmags Ltd to incite, encourage or condone the use of such equipment.

Now that the Home Office has published its specifications for the proposed FM CB service, Rick Maybury comments on the implications

AT LAST! The specifications for the new FM CB service have been published, after considerable delay and much speculation. Regular readers to Hobby Electronics and Citizens' Band will find few surprises but before we look at them in detail let's look at some of the background to the campaign so far.

Back in January 1980 the Home Office claimed that there was no possibility of introducing a CB type service in the UK due to lack of frequency space and interference problems. In September the Home Office issued a document entitled 'Open Channel', which set out proposals for a two-way radio service operating on or around 928 MHz. At that time it was claimed that a service operating on 27 MHz was impractical. In February 1981 the Home Office issued a statement saying that it was considering setting up an Open Channel service on or around 27 MHz, but using frequency modulation instead of the American AM (amplitude modulation) system. It also pointed out at that time that there was a potential for a European band that would allow CB equipment from various Common Market countries to operate side by side.

In the last week or so details of the new service have been released to enable manufacturers to prepare for the legalisation in the autumn. Now here's the interesting bit: the service is no longer referred to as Open Channel — in all the documents we've seen so far, it is called Citizens' Band. The frequency allocations for UKCB are outside any other allocation in the world, effectively creating a non-standard system, unusable anywhere other than in this country. The band in question has somehow been found where apparently no space existed a year ago. One could construe this as being slightly perverse, but taken overall and considering the alternatives it could have been a whole lot worse. We came pretty close to getting nothing at all.

Thank you for being so patient: and now, for anyone who's interested, here are the basic specifications.

Summary Of New Specs

Two services are to be introduced, one on 934 MHz and one on 27 MHz. First 934 MHz:

Frequency range:	934.025 to 934.975 MHz
Number of channels:	20
Channel spacing:	50 kHz
Max RF power:	8 watts
Max ERP:	25 watts (3 watts limit on hand-held equipment)

Next 27 MHz:

Frequency range:	27.60125 to 27.99125 MHz
Number of channels:	40
Channel spacing:	10 kHz
Max RF power:	4 watts
Max ERP:	2 watts

The above is the bare bones of it. Figures for harmonic emission, maximum frequency deviation etc, are well within normal international standards.

The first thing that most of you will have noticed is the starting point for 27 MHz — yes, it is well above the FCC and FTZ channels. In fact, it's right out on its own up with the unlicensable and largely undocumented band used by foreign embassies to keep in touch with their mother countries.

Reaction From AM CBers

So far the reaction to this announcement has raised the expected protests from the stalwart AM CBers, and the long-time campaigners for any CB system have raised the odd eyebrow. Radio modellers have naturally pointed out that the ideal solution would be for them to take this new band and let the existing illegal CBers keep what they undoubtedly already have.

I will be reporting on the ultimate outcome of this proposal in next month's BOF after the Home Office has held a series of meetings scheduled for the next few weeks. In these meetings it will be seeking the reactions of interested parties, ranging from radio modellers to the manufacturers. Meanwhile, I suspect that the figures that I have quoted will not be changed by any significant degree — not because I suppose that the objections will not be raised but simply because of the incredibly short notice given to the interested parties to respond. The specs were published on April 21 and the first of the three crucial meetings was held on April 24. The second meeting is (at the time of writing) scheduled for April 29 and the third for May 5. See what I mean about perverse?

Three FM transceivers from Binatone (these cannot be licenced for use in the UK)



All these advantages...


- Instant all-weather starting
- Smoother running
- Continual peak performance
- Longer battery & plug life
- Improved fuel consumption
- Improved acceleration/top speed
- Extended energy storage

..in kit form

SPARKRITE X5 is a high performance top quality inductive discharge electronic ignition system designed for the electronics D I Y world. It has been tried, tested and proven to be utterly reliable. Assembly only takes 1.2 hours and installation even less due to the patented 'clip on' easy fitting.

The superb technical design of the Sparkrite circuit eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R P M. Contact breaker burn is eliminated by reducing the current by 95% of the norm.

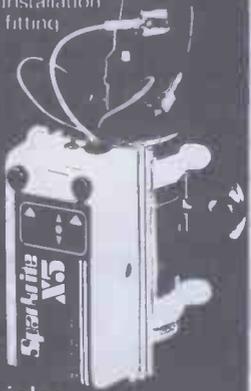There is also a unique extended dwell circuit which allows the coil a longer period of time to store its energy before discharging to the plugs. The unit includes built in static timing light, systems function light, and security changeover switch. Will work all rev counters.



Fits all 12v negative-earth vehicles with coil/distributor ignition up to 8 cylinders.

THE KIT COMPRISES EVERYTHING NEEDED
Die pressed case. Ready drilled, aluminium extruded base and heat sink, coil mounting clips and accessories. All kit components are guaranteed for a period of 2 years from date of purchase. Fully illustrated assembly and installation instructions are included.



Roger Clark the world famous rally driver says "Sparkrite electronic ignition systems are the best you can buy."

Sparkrite

HIGH PERFORMANCE ELECTRONIC IGNITION

Electronics Design Associates, Dept. HE/6/81
2 Bath Street, Walsall WS1 3DE
Phone: (0922) 614791

Name _____
Address _____

Phone your order with Access or Barclaycard

Inc. V.A.T. and P.P.

QUANTITY REQD.

X5 KIT £16.95

ACCESS OR BARCLAY CARD No.

I enclose cheque/PO's for

£

Cheque No.

Send SAE if brochure only required.



ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.
Bound in stiff linen. Cover size 8 1/2 in x 5 in.
Price £10.00 per set (we pay the postage)

- Book 1. Introducing Electronics Book 4. Meters/Voltage dividers
Book 2. Resistors/Capacitors Book 5. Transistor Project Circuitry
Book 3. Inductors/Diodes

The manuals are unquestionably the finest and most up-to-date available and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting way, providing an approach to acquiring knowledge that is a very enjoyable experience. Suitable for industrial trainees, City and Guilds students, DIY enthusiasts and readers of electronic journals.

Each part explains electronics in an easy-to-follow way, and contains numerous diagrams and half tone blocks with construction details and circuit diagrams for making the following transistor projects: Lamp Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm, Electronic Organ, Battery Eliminator, Anemometer, Sound Switch, Light and Water-operated Switches, Pressure-operated Switches, Light meter, Radio Thermometer, Ice Alarm,

Order Now:
Selray Book Company
11 Aspen Copse,
Bromley,
Kent. BR1 2NZ

OUR 100% GUARANTEE
Should you decide to return the set after 10 days examination, your money will be refunded by return of post.

Amount enclosed: £ _____

Name: _____

Address: _____

HE6

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.

FREE

Please send your **FREE** brochure without obligation to -

Name _____

Address _____

BLOCK CAPS PLEASE

I am interested in -

PRACTICAL ELECTRONICS.....

COMPUTER TECHNOLOGY.....

OTHER SUBJECTS.....


(Please state your interest)

HE/5/817


BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

PCB FOIL PATTERNS

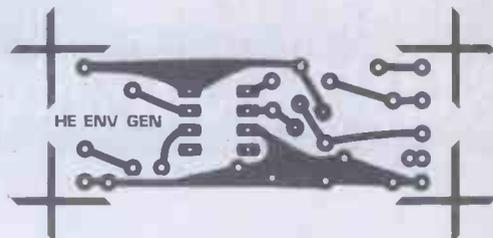

Foil pattern of the Envelope Generator

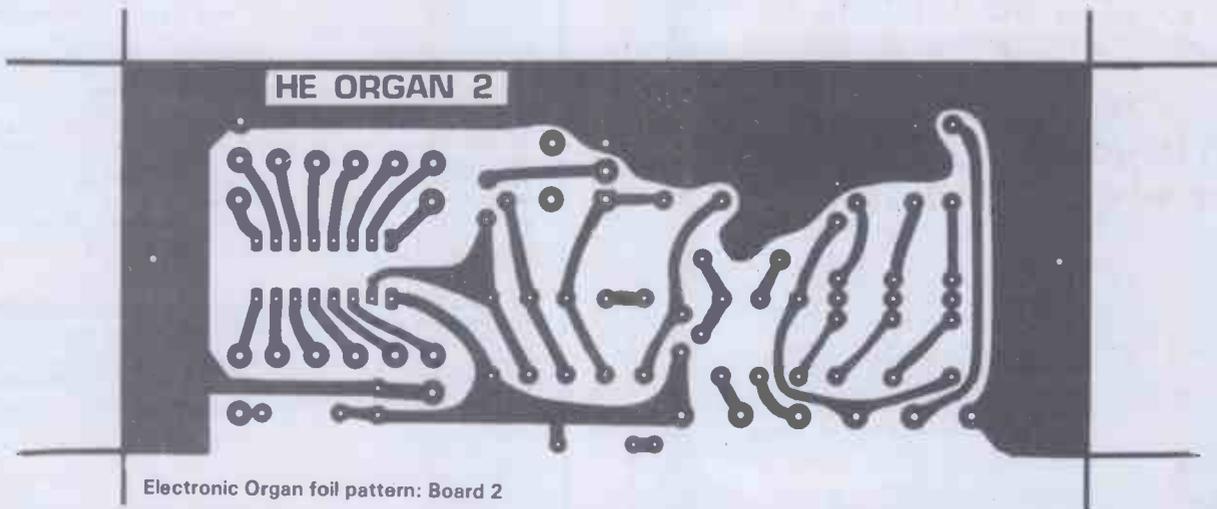

Electronic Organ foil pattern: Board 2

HE BACKNUMBERS



Any gaps in your HE library? There's still time to fill them. listed below are all the currently-available backnumbers.

	1979	1980	1981
	June	February	All
	July	March	
	August	May	
	September	June	
	October	July	
	December	August	
		September	
		October	
		November	
		December	

Each issue cost **£1.00** (surface mail anywhere in the world). Please specify the months required in the coupon below and send it, together with a cheque or postal order (made payable to Modmags Ltd.) to:

HE Backnumbers Dept.,
Modmags Ltd.
145 Charing Cross Road,
LONDON WC2H 0EE



Please send me the following backnumbers of HE (indicate number required alongside the appropriate month)

1979	1980	1981
Jun	Feb	Jan
Jul	Mar	Feb
Aug	May	Mar
Sep	Jun	
Oct	Jul	
Dec	Aug	
	Sep	
	Oct	
	Nov	
	Dec	

I enclose a cheque/postal order* for £..... for copies at £1.00 each

NAME
(BLOCK CAPITALS)
ADDRESS

*Delete as appropriate

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASE WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture. Tested & fully guaranteed. Ex-stock delivery.

£6.95 inc. VAT
Post & Pack 60p

Ideal for the experimenter
COMPLETE WITH DATA

Henry's

404 EDGWARE ROAD, LONDON W2 1ED



WANTED. Electronic components and test equipment. Good prices given. — Q Services, 29 Lawford Crescent, Yately (0252) 871048, Camberley, Surrey.

DIRECT ETCHING KIT by Chartpak, eight sheets symbols and rules, burnisher, etc. Simply and quickly draft your P.C.B. design ready for etching. £4.50 incl. P. & P. — A.S.R. Business Services, 24 Catherine Street, Salisbury SP1 2DA.

EXPRESS PCB DRILLING SERVICE: All PCB's 0.9p per hole; postage 18p (additional boards 4p). Quantity drilling; any required diameters. PCB, stripboard assembly. Components at low prices. Enquiries welcome. S.A.E. details, list, cheque/PO.: RKS Electronics, 13h Queen's Terrace, Sherborne, Dorset DT9 4ED. Tel. (093581) 2488.

HAVE YOU SEEN THE GREEN LIST?

1000s of components (radio, audio and electronic) and electronic items and accessories at unbelievably low prices. Something for everyone. Send 20p stamps or large S.A.E. for list and receive FREE RECORD SPEED INDICATOR. MYERS (Dept. H.E.), 14-16 Clifton Grove, Harehills, Leeds 9.

CLASSIFIEDS

ETI RATES

1-4 Insertions £9.00 per scc
5-11 Insertions £8.00 per scc
12+ Insertions £7.00 per scc
30p per word (min 12 words)
Box No. £2.00
Closing date 1st Friday in month preceding publication.

HE RATES

1-3 Insertions £5.00 per scc
4-11 Insertions £4.50 per scc
12+ Insertions £4.00 per scc
18p per word (min 15 words)
Box No. £1.50
Closing date 2nd Friday in month preceding publication.

Classified Advertisements must be prepared subject to the terms and conditions printed on the advertisement rate card (available on request).

SEND TO: ETI/HE CLASSIFIED, 145, CHARING CROSS ROAD, LONDON WC2H 0EE. TEL: 01-437 1002 Ext. 50.

BARGAINS FOR THE ELECTRONIC HANDYMAN BRANDED L.E.D. DIGITAL ALARM CLOCKS



Returned to Service Department within guarantee period.

1. With alarm repeat S.R.S.P. of £17.00. Offered at £3.95, inc. VAT, or 3 for £9.95, inc. VAT.
2. With luxury lamp and repeat alarm. S.P.S.P. £31.00. Offered at £7.95 inc. VAT each, or 3 for £19.95 inc. VAT.

These will be sold as received from our customers with the existing fault(s) and without guarantee.

U.K. only

Discounts available on large bulk purchase.

PRESCOTT CLOCK & WATCH CO. LTD.

PRESCOTT HOUSE, HUMBER ROAD, LONDON NW2 6ER

PARAPHYSICS JOURNAL. Russian / Czech translations. Autogenics (self-training) improves vitality. Psychotronic Generators, UFOs, contacting extraterrestrials, Kirlianography, telinesis, levitation, gravity lasers. S.A.E. 4x9": Paralab, Downton, Wilts.

POCKET COMPUTERS

AT LAST - THE PRINTER FOR PC1211

CE-122 Printer/Cassett interface £79.95
PC1211 with CE-122 printer £172.00
PC1211 with CE-121 cassette interface £105.95
PC-1211 only £92.15

FREE PAPERMATE PEN WITH ALL ORDERS
All prices include (15%) VAT and UK Delivery

ELKAN ELECTRONICS
28 Bury New Road
Prestwich, Manchester M25 8LD

SUPERBOARD II

STILL the best value in Home Computers. Just compare the features:

- ★ 8K floating point BASIC in ROM
- ★ Full ASC11 keyboard
- ★ Standard cassette / TV interface
- ★ RS232 printer interface
- ★ 4K user RAM
- ★ Expandable to 32K & dual mini floppy

AVAILABLE NOW from:

C.T.S.
31 / 33 Church Street
Littleborough
Lancs.

Please ring or write for latest prices

Tel: Littleborough (0706) 74342 any time.

1000's OF ELECTRONIC COMPONENTS FOR SALE. 35p for lists. — John E. Harris, 9 Ivybridge, Broxbourne, Herts. EN10 7LH.

METAL DETECTORS

ALPHA TRIB £29.50. DISC £44.90.

Alpha Sales: 11 Mile End Row
Blackburn, Lancs. Tel: 0254 54105
TRADE ENQUIRIES WELCOME

ZX80 & ZX81. Join ZX guaranteed. All games/programs guaranteed to work. £5 year. Frustrated National ZX80 club people are welcome. — Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

PRINTED CIRCUITS. Make your own simply cheaply and quickly! Golden Fotolak light-sensitive lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25; developer, 35p; ferric chloride, 55p; clear acetate sheet for master, 14p; copper-clad fibreglass board, approx. 1mm thick, £1.75 sq. ft. Post/packing 75p. — White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

EDUCATION

Inner London Education Authority

LONDON COLLEGE OF FURNITURE

41-71 COMMERCIAL ROAD, LONDON E1 1LA

Department of Musical Instrument Technology

COURSES IN ELECTRONICS FOR THE MUSIC INDUSTRY

TEC DIPLOMA IN MUSICAL INSTRUMENT STUDIES

(2-year full time specialising in electronics)


TEC HIGHER DIPLOMA IN MUSICAL INSTRUMENT TECHNOLOGY

(2-year full time specialising in electronics)

The electronics options of these TEC courses allow the student to specialise in music industry application. Suitable students would be interested in both music and electronics and wish to combine them within this course. Application forms and further details are obtainable from the Senior Administrative Officer at the College.

If it's a case of making your project look good, then use one of ours.

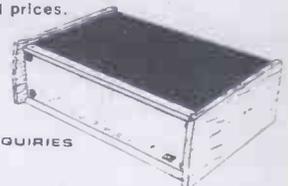Simply send a S.A.E. for Details and prices.



TRADE ENQUIRIES INVITED.


H. M. ELECTRONICS

271a/275a Fulwood Road.
Broomhill
Sheffield S10 3BD

microtan

designed with expansion in mind

Tangerine
Computer Systems Ltd

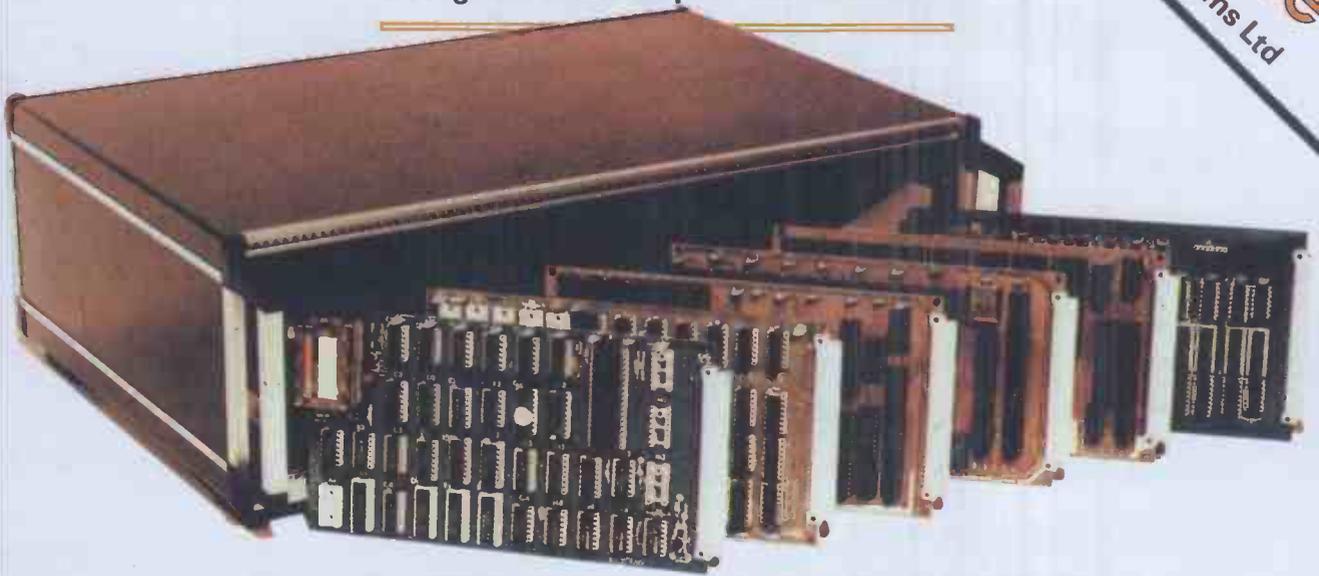

TANGERINE COMPUTERS get you into computing for less than £80 with

microtan 65

a one-board 6502-based microcomputer

But it doesn't stop there - Microtan is a SYSTEM

Start your expansion with **TANEX** - cassette interface, 16 I/O lines, two 16 bit counter timers, data bus buffering, memory mapping and a further 1K of RAM. Just plug in extra chips for 8K of RAM, 16 more I/O lines, two more counter timers and a serial I/O line with RS232/20 mA loop and full modem control.

XBUG - a firmware package with cassette file handling routines, a line-by-line assembler/dis-assembler, 10K extended Microsoft BASIC (as used by Apple, Tandy and NASCOM).

TANRAM - up to 40K of extra memory.

The system rack houses up to 12 boards. Extra serial and parallel I/O boards offer up to 128 I/O lines (16 eight bit ports) and eight serial I/O ports.

The full system will include high definition colour graphics, A to D and D to A boards, IEEE 488 interface, PROM programmer, disc controller and TANDOS, a 6502 CPM system.

Tangerine
Computer Systems Ltd
FOREHILL WORKS,
FOREHILL, ELY,
CAMBS.
SEND NOW FOR THE LATEST INFORMATION
AVAILABLE ON THE MICROTAN SYSTEM.
PLEASE ENCLOSE A 12p STAMP.

MAPLIN make it easy...

in
HAMMERSMITH

159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

in
SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our
CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith  price £1.

In case of difficulty check the coupon below.

by
MAIL ORDER
A fast service
You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

make it easy... with **MAPLIN**

The
Maplin Matinée

Amazing value for
only £229.95 plus £99.50
for cabinet if required

Easy to build,
superb specification.
Comparable with organs selling for
up to £1,000. Full construction details
in Electronics & Music Maker commencing
March, 1981 issue. Back numbers available.



Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name
Address

HE681

MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911