

# Hobby

MAY '82

ISSN 0142-6192

70p

# Electronics

Project Electronics For Everyone


## Projects for all



Digital Thermometer▲

Audio Signal Generator▶

### HE CABLE TRACKER

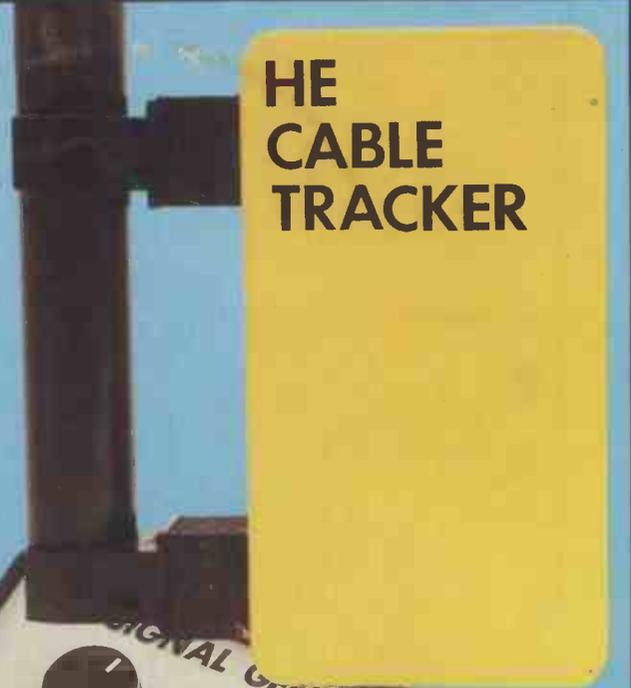

▲Cable Tracker



Echo-Reverb Unit▲



**New Series • New Series •**  
The Electronic Revolution  
From Volta to Video  
**• New Series •**

## Scaling the Hi-fi Heights - the final installment

## NEW NEW NEW NEW Popular Computing Series Into Radio - First steps

# NICADS: UK's LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW -


Available at your newsagent or direct, for 70p inc.

Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 £1 discount vouchers. In a recent supplier survey, we were one of only two suppliers listed in all categories!

There's a few examples of some super low prices

|                             |        |
|-----------------------------|--------|
| 78XX 1A                     | 37p    |
| BC237/8/9                   | 8p     |
| 3SK51                       | 54p    |
| 10MHz XTALS                 | £2     |
| 8 Pole 10.7MHz XTAL filters | £14.50 |
| 2GHz coax relay 150W        | £10.95 |

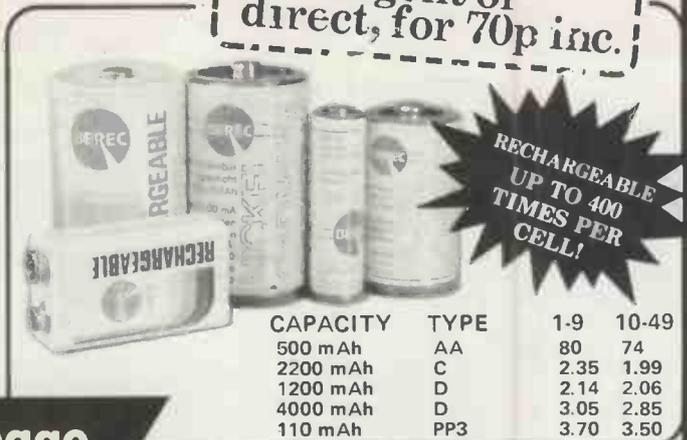All the "usual" stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micro metals toroids, Fairite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.




**RECHARGEABLE UP TO 400 TIMES PER CELL!**

| CAPACITY | TYPE | 1-9  | 10-49 |
|----------|------|------|-------|
| 500 mAh  | AA   | 80   | 74    |
| 2200 mAh | C    | 2.35 | 1.99  |
| 1200 mAh | D    | 2.14 | 2.06  |
| 4000 mAh | D    | 3.05 | 2.85  |
| 110 mAh  | PP3  | 3.70 | 3.50  |

**Price on the page**

## CMOS

|        |      |       |      |        |      |
|--------|------|-------|------|--------|------|
| 4000   | 0.11 | 4514  | 1.25 | 7406N  | 0.22 |
| 4001   | 0.11 | 4515  | 1.25 | 7407N  | 0.22 |
| 4002   | 0.12 | 4516  | 0.80 | 7408N  | 0.15 |
| 4007   | 0.13 | 4518  | 0.35 | 7409N  | 0.15 |
| 4008   | 0.50 | 4520  | 0.60 | 7410N  | 0.12 |
| 4008AE | 0.80 | 4521  | 1.30 | 7411N  | 0.18 |
| 4009   | 0.25 | 4522  | 0.89 | 7412N  | 0.19 |
| 4010   | 0.30 | 4527  | 0.80 | 7413N  | 0.27 |
| 4011AE | 0.24 | 4528  | 0.85 | 7414N  | 0.51 |
| 4011   | 0.11 | 4529  | 0.70 | 7416N  | 0.27 |
| 4013   | 0.25 | 4531  | 0.65 | 7417N  | 0.27 |
| 4015   | 0.50 | 4532  | 0.80 | 7420N  | 0.13 |
| 4016   | 0.22 | 4534  | 4.00 | 7421N  | 0.28 |
| 4017   | 0.40 | 4536  | 2.50 | 7423N  | 0.22 |
| 4019   | 0.38 | 4538  | 0.85 | 7425N  | 0.22 |
| 4020   | 0.55 | 4539  | 0.80 | 7426N  | 0.22 |
| 4021   | 0.55 | 4543  | 0.80 | 7427N  | 0.22 |
| 4022   | 0.55 | 4549  | 3.50 | 7430N  | 0.12 |
| 4023   | 0.15 | 4553  | 2.70 | 7432N  | 0.23 |
| 4024   | 0.33 | 4554  | 1.20 | 7437N  | 0.22 |
| 4025   | 0.15 | 4555  | 0.35 | 7438N  | 0.22 |
| 4026   | 1.06 | 4556  | 0.40 | 7440N  | 0.14 |
| 4027   | 0.26 | 4557  | 2.30 | 7441N  | 0.54 |
| 4028   | 0.50 | 4558  | 0.80 | 7442N  | 0.42 |
| 4029   | 0.55 | 4559  | 3.50 | 7443N  | 0.62 |
| 4030   | 0.35 | 4560  | 2.50 | 7444N  | 0.62 |
| 4035   | 0.67 | 4562  | 2.50 | 7445N  | 0.62 |
| 4040   | 0.50 | 4566  | 1.20 | 7446N  | 0.62 |
| 4042   | 0.50 | 4568  | 1.45 | 7448N  | 0.62 |
| 4043   | 0.50 | 4569  | 1.70 | 7450   | 0.56 |
| 4043AE | 0.93 | 4572  | 0.22 | 7451N  | 0.14 |
| 4044   | 0.60 | 4580  | 3.25 | 7453N  | 0.14 |
| 4046   | 0.60 | 4582  | 0.40 | 7454N  | 0.14 |
| 4047   | 0.88 | 4583  | 0.80 | 7460N  | 0.14 |
| 4049   | 0.24 | 4584  | 0.27 | 7472N  | 0.28 |
| 4050   | 0.24 | 4584  | 0.27 | 7473N  | 0.28 |
| 4051   | 0.55 | 4585  | 0.45 | 7474N  | 0.28 |
| 4052   | 0.55 | 4702  | 4.48 | 7475N  | 0.35 |
| 4053   | 0.55 | 4703  | 4.48 | 7476N  | 0.30 |
| 4054   | 1.30 | 4704  | 4.24 | 7480N  | 0.26 |
| 4055   | 1.30 | 4705  | 4.24 | 7481N  | 0.20 |
| 4056   | 1.30 | 4706  | 4.50 | 7482N  | 0.75 |
| 4059   | 5.75 | 4723  | 0.95 | 7485N  | 0.75 |
| 4060   | 0.75 | 4724  | 0.95 | 7486N  | 0.24 |
| 4063   | 1.15 | 4725  | 2.24 | 7489N  | 1.05 |
| 4066   | 0.30 | 40014 | 0.54 | 7490N  | 0.30 |
| 4067   | 4.30 | 40085 | 0.99 | 7491N  | 0.55 |
| 4068   | 0.16 | 40098 | 0.54 | 7492N  | 0.35 |
| 4069AE | 0.14 | 40106 | 0.69 | 7493N  | 0.35 |
| 4070   | 0.16 | 40160 | 1.05 | 7494N  | 0.70 |
| 4071   | 0.16 | 40161 | 1.05 | 7495N  | 0.50 |
| 4072   | 0.16 | 40162 | 1.05 | 7496N  | 1.40 |
| 4073   | 0.16 | 40163 | 1.05 | 7497N  | 1.40 |
| 4075   | 0.16 | 40174 | 1.05 | 74100  | 1.10 |
| 4076   | 0.55 | 40175 | 1.05 | 74104  | 0.62 |
| 4077   | 0.18 | 40192 | 1.08 | 74105  | 0.62 |
| 4078   | 0.18 | 40193 | 1.08 | 74107  | 0.26 |
| 4081   | 0.12 | 40194 | 1.08 | 74109N | 0.35 |
| 4082   | 0.18 | 40195 | 1.08 | 74110N | 0.54 |
| 4083   | 0.30 |       |      | 74111N | 0.68 |
| 4089   | 0.80 |       |      | 74112N | 1.90 |
| 4175   | 0.80 |       |      | 74116N | 0.78 |
| 4502   | 0.80 |       |      | 74118N | 0.85 |
| 4503   | 0.50 |       |      | 74119N | 1.20 |
| 4506   | 0.70 |       |      | 74120N | 0.95 |
| 4507   | 0.37 |       |      | 74121N | 0.34 |
| 4508   | 1.50 |       |      | 74122N | 0.34 |
| 4510   | 0.55 |       |      | 74123N | 0.40 |
| 4511   | 0.45 |       |      |        |      |
| 4512   | 0.55 |       |      |        |      |

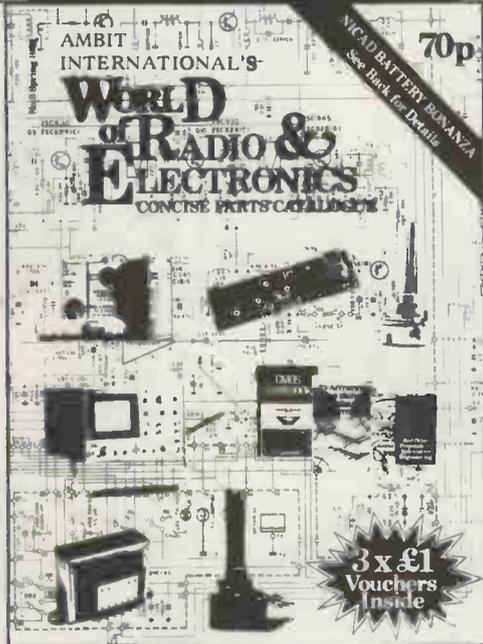

**70p**

**3 x £1 Vouchers Inside**

Prices shown EXCLUDE VAT. Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO.

**POSTAGE and PACKING 50p per order**

|        |      |        |      |        |      |
|--------|------|--------|------|--------|------|
| 74125N | 0.40 | 74153N | 0.55 | 74170N | 1.25 |
| 74126N | 0.40 | 74154N | 0.55 | 74173N | 1.10 |
| 74128N | 0.65 | 74155N | 0.55 | 74174N | 0.75 |
| 74132N | 0.50 | 74156N | 0.55 | 74175N | 0.75 |
| 74136N | 0.65 | 74157N | 0.55 | 74176N | 0.75 |
| 74141N | 0.45 | 74159N | 1.90 | 74177N | 0.75 |
| 74142N | 1.85 | 74160N | 0.55 | 74178N | 0.90 |
| 74143N | 2.50 | 74161N | 0.55 | 74179N | 1.35 |
| 74144N | 2.50 | 74162N | 0.55 | 74180N | 0.75 |
| 74145N | 0.75 | 74163N | 0.55 | 74181N | 1.22 |
| 74147N | 1.50 | 74164N | 0.55 | 74182N | 0.70 |
| 74148N | 1.09 | 74165N | 0.55 | 74184N | 1.20 |
| 74150N | 0.79 | 74166N | 0.70 | 74185N | 1.20 |
| 74151N | 0.55 | 74167N | 1.25 | 74188N | 3.00 |

|        |      |          |      |          |      |        |      |
|--------|------|----------|------|----------|------|--------|------|
| 74190N | 0.55 | 74LS74N  | 0.16 | 74LS248N | 1.35 | 74C76  | 0.48 |
| 74191N | 0.55 | 74LS75N  | 0.22 | 74LS249N | 1.35 | 74C83  | 0.98 |
| 74192N | 0.55 | 74LS76N  | 0.20 | 74LS251N | 0.35 | 74C85  | 0.98 |
| 74193N | 0.55 | 74LS78N  | 0.19 | 74LS253N | 0.35 | 74C86  | 0.26 |
| 74194N | 0.55 | 74LS83N  | 0.40 | 74LS257N | 0.40 | 74C89  | 2.68 |
| 74195N | 0.55 | 74LS85N  | 0.60 | 74LS258N | 0.37 | 74C90  | 0.80 |
| 74196N | 0.55 | 74LS86N  | 0.14 | 74LS259N | 0.80 | 74C93  | 0.80 |
| 74197N | 0.55 | 74LS90N  | 0.32 | 74LS260N | 0.50 | 74C95  | 0.94 |
| 74198N | 0.85 | 74LS91N  | 0.28 | 74LS266N | 0.22 | 74C107 | 0.48 |
| 74199N | 1.00 | 74LS92N  | 0.31 | 74LS273N | 3.20 | 74C151 | 1.52 |
| 74221N | 1.00 | 74LS93N  | 0.31 | 74LS275N | 3.20 | 74C154 | 2.26 |
| 74246N | 1.50 | 74LS95N  | 0.40 | 74LS279N | 0.35 | 74C157 | 1.52 |
| 74247N | 1.51 | 74LS96N  | 1.20 | 74LS280N | 2.50 | 74C160 | 1.05 |
| 74248N | 1.89 | 74LS107N | 0.25 | 74LS283N | 0.42 | 74C161 | 1.05 |
| 74249N | 0.11 | 74LS109N | 0.20 | 74LS290N | 0.50 | 74C162 | 1.05 |
| 74251N | 1.05 | 74LS112N | 0.20 | 74LS293N | 0.40 | 74C163 | 1.05 |
| 74255N | 0.66 | 74LS113N | 0.20 | 74LS295N | 1.50 | 74C164 | 0.80 |
| 74273N | 2.67 | 74LS114N | 0.19 | 74LS298N | 0.76 | 74C165 | 0.84 |
| 74278N | 2.49 | 74LS122N | 0.35 | 74LS365N | 0.32 | 74C173 | 0.72 |
| 74279N | 0.88 | 74LS123N | 0.35 | 74LS366N | 0.34 | 74C174 | 1.05 |
| 74283N | 1.30 | 74LS124N | 1.80 | 74LS367N | 0.32 | 74C175 | 1.05 |
| 74284N | 3.50 | 74LS125N | 0.24 | 74LS368N | 0.35 | 74C192 | 1.08 |
| 74285N | 3.50 | 74LS126N | 0.24 | 74LS373N | 0.70 | 74C193 | 1.08 |
| 74290N | 1.00 | 74LS132N | 0.42 | 74LS374N | 0.70 | 74C195 | 1.08 |
| 74293N | 1.05 | 74LS133N | 0.24 | 74LS375N | 0.40 | 74C200 | 4.52 |
| 74297N | 2.36 | 74LS136N | 0.20 | 74LS377N | 0.85 | 74C221 | 1.06 |
| 74298N | 1.85 | 74LS138N | 0.30 | 74LS378N | 0.65 | 74C901 | 0.38 |
| 74365N | 0.85 | 74LS139N | 0.30 | 74LS379N | 0.60 | 74C902 | 0.38 |
| 74366N | 0.85 | 74LS145N | 1.20 | 74LS394N | 2.50 | 74C903 | 0.38 |
| 74367N | 0.85 | 74LS151N | 0.30 | 74LS395N | 2.05 | 74C904 | 0.38 |
| 74368N | 0.85 | 74LS153N | 0.27 | 74LS396N | 0.29 | 74C905 | 0.38 |
| 74390N | 1.85 | 74LS154N | 0.99 | 74LS399N | 0.68 | 74C906 | 0.38 |
| 74393N | 1.85 | 74LS155N | 0.35 | 74LS393N | 0.61 | 74C907 | 0.38 |
| 74490N | 1.85 | 74LS156N | 0.37 | 74LS395N | 2.10 | 74C908 | 0.84 |
|        |      | 74LS157N | 0.30 | 74LS396N | 1.99 | 74C909 | 1.52 |
|        |      | 74LS158N | 0.30 | 74LS398N | 2.75 | 74C910 | 3.62 |
|        |      | 74LS160N | 0.37 | 74LS399N | 2.30 | 74C914 | 0.86 |
|        |      | 74LS161N | 0.37 | 74LS445N | 1.40 | 74C918 | 0.98 |
|        |      | 74LS162N | 0.37 | 74LS447N | 1.95 | 74C925 | 4.32 |
|        |      | 74LS163N | 0.37 | 74LS490N | 1.10 | 74C926 | 4.32 |
|        |      | 74LS164N | 0.40 | 74LS668N | 1.05 | 74C927 | 4.32 |
|        |      | 74LS165N | 0.80 | 74LS669N | 1.05 |        |      |
|        |      | 74LS166N | 0.80 | 74LS670N | 1.70 |        |      |
|        |      | 74LS168N | 0.70 |          |      |        |      |
|        |      | 74LS169N | 0.85 |          |      |        |      |
|        |      | 74LS170N | 0.80 |          |      |        |      |
|        |      | 74LS173N | 0.80 |          |      |        |      |
|        |      | 74LS174N | 0.40 |          |      |        |      |
|        |      | 74LS175N | 0.40 |          |      |        |      |
|        |      | 74LS181N | 1.05 |          |      |        |      |
|        |      | 74LS183N | 1.75 |          |      |        |      |
|        |      | 74LS189N | 1.28 |          |      |        |      |
|        |      | 74LS190N | 0.45 |          |      |        |      |
|        |      | 74LS191N | 0.45 |          |      |        |      |
|        |      | 74LS192N | 0.45 |          |      |        |      |
|        |      | 74LS193N | 0.42 |          |      |        |      |
|        |      | 74LS194N | 0.35 |          |      |        |      |
|        |      | 74LS195N | 0.35 |          |      |        |      |
|        |      | 74LS196N | 0.55 |          |      |        |      |
|        |      | 74LS197N | 0.60 |          |      |        |      |
|        |      | 74LS200N | 3.40 |          |      |        |      |
|        |      | 74LS202N | 3.45 |          |      |        |      |
|        |      | 74LS221N | 0.50 |          |      |        |      |
|        |      | 74LS240N | 0.80 |          |      |        |      |
|        |      | 74LS242N | 0.80 |          |      |        |      |
|        |      | 74LS243N | 0.80 |          |      |        |      |
|        |      | 74LS244N | 0.60 |          |      |        |      |
|        |      | 74LS245N | 0.80 |          |      |        |      |
|        |      | 74LS247N | 1.35 |          |      |        |      |

|                   |       |
|-------------------|-------|
| <b>Processors</b> |       |
| 8080AFC/2         | £7.30 |
| 8212              | 2.30  |
| 8214              | 3.50  |
| 8216              | 1.85  |
| 8224              | 3.50  |
| 8251              | 6.21  |
| 8255              | 5.40  |
| <b>RAM</b>        |       |
| 2102              | 1.70  |
| 2112              | 3.40  |
| 2114 2            | 1.49  |
| 4027              |       |

# Hobby Electronics

MAY 1982  
Vol 4 No 5

## PROJECTS

|   |    |
|---|----|
| ★ DIGITAL THERMOMETER . . . . .                     | 10 |
| <i>Reads Fahrenheit or Celsius.</i>                 |    |
| ★ HE ECHO-REVERB . . . . .                          | 33 |
| <i>The beat goes On, on, on, on, on.</i>            |    |
| ★ AF SIGNAL GENERATOR . . . . .                     | 49 |
| <i>A simple, useful test generator.</i>             |    |
| ★ QUICK PROJECT . . . . .                           | 55 |
| <i>Light Seeker.</i>                                |    |
| ★ CABLE TRACKER . . . . .                           | 65 |
| <i>An essential accessory for the DIY handyman.</i> |    |

## FEATURES

|  |    |
|--|----|
| ★ POPULAR COMPUTING                                    |    |
| THE ZX81 REVIEWED . . . . .                            | 20 |
| <i>Sinclair's micro-masterpiece reconsidered.</i>      |    |
| ★ MICRO-HISTORY . . . . .                              | 26 |
| <i>A short, short history of the computer.</i>         |    |
| ★ SCALING THE HIFI HEIGHTS . . . . .                   | 44 |
| <i>The final installment — adding a cassette deck.</i> |    |
| FAMOUS NAMES . . . . .                                 | 53 |
| <i>Charles Babbage.</i>                                |    |
| INTO RADIO   |    |
| ★ RADIORULES . . . . .                                 | 57 |
| <i>Sines of the Times.</i>                             |    |
| INTO ELECTRONIC COMPONENTS . . . . .                   | 61 |
| <i>Part 1 1: Digital Dealing.</i>                      |    |

## SPECIALS

|                                     |    |
|-------------------------------------|----|
| THE ELECTRONIC REVOLUTION . . . . . | 39 |
| <i>The Electric Society begins.</i> |    |

## REGULARS

|                                     |    |
|-------------------------------------|----|
| Monitor . . . . .                   | 6  |
| ★ BUYLINES . . . . .                | 68 |
| ★ POINTS OF VIEW . . . . .          | 16 |
| Clever Dick . . . . .               | 30 |
| HE Subscriptions . . . . .          | 38 |
| Backnumbers . . . . .               | 56 |
| Bookshelf . . . . .                 | 70 |
| What's On Next . . . . .            | 18 |
| PCB Service . . . . .               | 60 |
| PCB Print Out . . . . .             | 72 |
| Index to Advertisers . . . . .      | 73 |
| Classified Advertisements . . . . . | 73 |

Editor: Ron Keeley  
 Editorial Assistants: Paul Coster BSc  
 Tina Boylan  
 Senior Art Editor: Kieran Wade  
 Assistant Art Editor: Enzo Grandi  
 Advertisement Manager: Gary Price  
 Managing Editor: Ron Harris BSc  
 Managing Director: T.J. Connell



Hobby Electronics is normally published on the second Friday of the month prior to the cover date.  
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.  
 Distributed by Argus Press Sales & Distribution Ltd, 12-18 Paul St, London EC2A 4JS. Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.  
 Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © Copyright 1982 Argus Specialist Publications Ltd. Member of the Audit Bureau of Circulation.

# 20

## SIMPLE ELECTRONIC PROJECTS FOR THE ZX81 and other computers



by Stephen Adams

## 20 SIMPLE ELECTRONIC PROJECTS FOR THE ZX81 AND OTHER COMPUTERS

Make the most of your micro with this great book of construction projects.

Projects include: a numeric keypad; giant seven-segment display; score board; light pen; thermometer; shift lock; computerised voltmeter; and an 'unbeatable' burglar alarm.

### INTERFACE

Department HE,  
44-46 Earls Court Road,  
LONDON W8 6EJ

Please send me a copy of Stephen Adams' book 20 SIMPLE ELECTRONIC PROJECTS FOR THE ZX81. I enclose £6.45, plus 30p p&p

Name \_\_\_\_\_

Address \_\_\_\_\_

# THE PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL the electronics and hardware needed. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- CABLE TRACKER May 82 £9.37
- DIGITAL CAPACITANCE METER Apr 82 £21.69
- SIGNAL TRACER Apr 82 £3.61
- BIKE ALARM Apr 82 £10.98
- DUAL ENGINE DRIVER Apr 82 £48.78
- DIGITAL DICE Mar 82 £6.82
- BICYCLE SIREN Mar 82 £10.18
- NOISELESS FUZZBOX Feb 82 £9.77
- SOUND SWITCH Feb 82 £8.31
- MASTHEAD AMPLIFIER Feb 82 £13.74
- DRUM SYNTHESIZER Dec 81. Full kit £19.98
- GUITAR HEADPHONE AMPLIFIER Dec 81 £3.48
- IN CAR CASSETTE POWER SUPPLY Dec 81 £4.46
- SCRATCH FILTER Nov 81 Mono £5.44 - Stereo £8.40
- LED VU METER Nov 81 less case £4.56
- SIMPLE STYLUS ORGAN Nov 81 less case £4.74
- METRONOME Nov 81 £11.88
- TELEPHONE BELL REPEATER Oct 81 £12.78
- Med Linking wire extra 14p metre
- COMBINATION LOCK Oct 81 less solenoid £17.43
- BABY ALARM Oct 81 £8.14, Fig 8 linking wire 7p metre
- 'DIANA' METAL LOCATOR Sept 81 £33.85
- POWERPACK Sept 81 £9.58
- REACTION TESTER GAME Sept 81 £11.98
- VARIABLE BENCH POWER SUPPLY Aug 81 £25.35
- ULTRASOUND BURGLAR ALARM July 81 £18.67
- ELECTRONIC DOOR BUZZER July 81 £5.65
- ELECTRONIC METRONOME July 81 £4.67
- CONTINUITY CHECKER June 81 £5.34
- ENVELOPE GENERATOR June 81 £16.85
- AUDIO MIXER June 81 £4.99
- PUBLIC ADDRESS AMPLIFIER March 81 £18.21, Extras — horn speakers £6.83 each, PA MIC £4.40
- FUZZBOX March 81 £10.35
- WINDSCREEN WIPER CONTROLLER March 81 £7.67
- STEAM LOCO WHISTLE March 81 £12.26
- PHOTOGRAPHIC TIMER March 81 £3.28
- HEARTBEAT MONITOR Feb 81 £23.40
- AUDIO SIGNAL GENERATOR Feb 81 £18.93
- TWO-TONE TRAIN HORN Feb 81 £5.24 less case
- MEDIUM WAVE RADIO Feb 81 £7.67
- BENCH AMP Jan 81 £10.10
- NICARD CHARGER Jan 81 £7.67
- CHUFFER Jan 81, less case £7.04
- BATTERY CHARGE MONITOR Dec 80 £5.40
- MEMORY BANK — MINI SYNTHESISER Nov & Dec 80 £28.40
- TRANSISTOR TESTER Nov 81 £6.12 inc test leads
- GUITAR PRE-AMP Nov 80 £5.65 case (diecast) extra £2.29
- INTRUDER ALARM Oct 80 £19.61
- TOUCH SWITCH Sept 80 £2.57 less case & contacts
- GUITAR PHASER Sept 80 £15.22
- SOUND OPERATED FLASH TRIGGER July 80 no skt £4.99
- FOG HORN June 80 £6.21
- SPEED CONTROLLER FOR R/C April 80 £16.41 (less case)
- DIGITAL FREQUENCY METER April 80 £39.35
- DIG-DICE Jan 80 £10.97
- GUITAR TUNER Nov 79 £11.99
- CAR ALARM Feb 79 £12.07

### CABLE TRACER

AS FEATURED IN THIS ISSUE

A SUPERB PROJECT FOR THE HOME HANDYMAN — PICKS UP NAILS, SCREWS, CABLES AND PIPES (and other buried metal objects).

QUICKLY SAVES ITS OWN COST  
BE SURE — BE SAFE

FULL KIT INCLUDES ALL HARDWARE, ELECTRONICS & PCB

**£9.37** + P&P

### MEMORY BANK SYNTHESIZER

Miniature synthesiser featuring vibrato, envelope, tempo, volume + pitch controls. Uses 24 push button switches in a keyboard style layout. Based on a custom designed L.C. The accessible memory stores a 32 beat length sequence of notes + spaces. Can be played 'live'. Fitted with an internal speaker. Jack socket allows the use of an external amplifier if wished.

Memory Bank Synthesizer £28.40

Complete kit inc. case, pcb's etc. Reprint extra 45p. Available separately 45p + 45p p&p.

### MORE PROJECT KITS — SIMILAR STYLE TO H.E. INSTRUCTIONS INCLUDED (SEPARATELY 45p EACH) PLEASE QUOTE REF. NO. WHEN ORDERING

- B1 PEST CONTROL 'Ultrasonic cat scarer' £6.98
- B2 COMPONENT TESTER £8.38
- B3 ENLARGER TIMER — relay output £26.99
- B4 GUITAR NOTE EXPANDER £16.87
- B5 CAMERA OR FLASH GUN TRIGGER Infra red system £11.98
- B6 SIMPLE INFRA RED REMOTE CONTROL £16.39
- B7 0-12V POWER SUPPLY £16.99
- B8 SOIL MOISTURE MONITOR £4.23
- B9 SOUND TO LIGHT — single channel £7.97
- B10 THREE CHANNEL SOUND TO LIGHT £19.98
- B11 IN SITU TRANSISTOR TESTER £6.73
- B12 WEIRD SOUND EFFECTS GENERATOR £5.68
- B13 AUDIBLE VISUAL METRONOME £5.98
- B14 ELECTRONIC DICE £5.71

## SOLDERING/TOOLS

**ANTEX XS SOLDERING IRON 25W £5.48**  
**SOLDERING IRON STAND £2.40**  
**SPARE BITS** Small, standard, large. For XS and X25 irons 65p each  
**SOLDER HANDY size 99p**  
**SOLDER CARTON £1.84**  
**DESOLDER BRAID 69p**  
**DESOLDER PUMP £6.48**  
**HEAT SINK TWEEZERS 29p**  
**HOW TO SOLDER LEAFLET 12p**  
**LOW COST CUTTERS £1.69**  
**LOW COST LONG NOSE PLIERS £1.68**  
**WIRE STRIPPERS + CUTTERS £2.69**  
**HELPING HANDS JIG £6.30**  
 Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (2.5x) magnifier attached. Used and recommended by our staff.  
**VERO SPOT FACE CUTTER £1.49**  
**PIN INSERTION TOOL £1.98**  
**VEROPINS (pk of 100) 0.1" 52p**  
**MULTIMETER TYPE 1 (1,000 ohm) £6.66**  
**MULTIMETER TYPE 2, 20,000 ohm with transistor tester. Very good £14.75**  
**ILLUMINATED MAGNIFIERS Small 2"**

dia (5 x mag) £1.14. Large 3" dia (4 x mag) £2.40  
**DENTISTS INSPECTION MIRROR £2.85**  
**JEWELLERS EYEGLASS £1.50**  
**HAND MAGNIFIER 3" £2.99**  
**CAST IRON VICE (Small) £2.98**  
**SCREWDRIVER SET £1.98**  
**POCKET TOOL SET £3.98**  
**PCB ETCHING KIT £4.98**  
**PLASTIC TWEEZERS 69p**

★ **USEFUL BITS & PIECES**  
 ★ **CROCODILE CLIP TEST LEAD SET 10** leads with 20 clips 99p  
 ★ **RESISTOR COLOUR CODE**  
 ★ **CALCULATOR 21p**  
 ★ **CONNECTING WIRE PACK (5 x 5 yd coils) 65p**  
 ★ **LETTERS/NUMBERS TRANSFERS £2.48**  
 ★ **SCREWS/NUTS/WASHERS 40p each**  
 ★ **M2 pack £1.80. M3 £1.78. M4 £1.84**  
 ★ **SOLDER TAGS M3 33p/50. M4 54p/50**  
 ★ **INSULATING PILLARS + SCREWS SET 65p**  
 ★ **STICK ON FEET 23p/4**

## BOOKS . BOOKS . BOOKS

**BASIC ELECTRONICS.** A super book covering theory and practice. Educational. Suits age 14 upwards. Lots of useful projects — circuits built on an S-Dec breadboard. Approx 525 pages . . . £7.98

### CONSTRUCTOR'S PROJECT BOOKS

Specialty written for the electronics enthusiast. Each book contains a collection of constructional projects, giving details of how the circuit works, how it may be assembled and how setting up and trouble shooting problems may be solved. The colour in the text helps to clarify details. Delightful books.

|   |       |
|---|-------|
| <b>ELECTRONIC GAME PROJECTS</b> Rayer . . . . .                                 | £3.35 |
| <b>ELECTRONIC PROJECTS FOR HOME SECURITY</b> Bishop . . . . .                   | £3.35 |
| <b>ELECTRONIC PROJECTS IN AUDIO</b> Penfold . . . . .                           | £3.35 |
| <b>ELECTRONIC PROJECTS IN MUSIC</b> Find . . . . .                              | £3.35 |
| <b>ELECTRONIC PROJECTS IN PHOTOGRAPHY</b> Penfold . . . . .                     | £3.35 |
| <b>ELECTRONIC PROJECTS IN THE CAR</b> George . . . . .                          | £3.35 |
| <b>PROJECTS IN AMATEUR RADIO &amp; SHORT WAVE LISTENING</b> Rayer . . . . .     | £3.35 |
| <b>PROJECTS IN RADIO AND ELECTRONICS</b> Sinclair . . . . .                     | £3.35 |
| <b>ELECTRONIC PROJECTS IN HOBBIES</b> Rayer . . . . .                           | £3.35 |
| <b>ELECTRONIC PROJECTS IN THE HOME</b> Bishop . . . . .                         | £3.35 |
| <b>ELECTRONIC PROJECTS IN THE WORKSHOP</b> Penfold . . . . .                    | £3.35 |
| <b>ELECTRONIC TEST EQUIPMENT PROJECTS</b> Ainslie . . . . .                     | £3.35 |
| <b>MORE ELECTRONIC PROJECTS IN THE HOME</b> Find . . . . .                      | £3.35 |
| <b>110 ELECTRONIC ALARM PROJECTS FOR THE HOME</b> Constructor Marston . . . . . | £5.35 |

### PAPERMAC — ELECTRONIC PROJECTS

A set of 4 books full of interesting circuits and projects.

★ **SPECIAL OFFER PRICES** ★★

|   |       |
|---|-------|
| <b>COST EFFECTIVE PROJECTS AROUND THE HOME</b> Watson . . . . . | £3.25 |
| <b>PROJECTS FOR THE CAR AND GARAGE</b> Bishop . . . . .         | £3.25 |
| <b>AUDIO CIRCUITS AND PROJECTS</b> Bishop . . . . .             | £3.95 |
| <b>TEST GEAR PROJECTS</b> Dixon . . . . .                       | £3.25 |

|  |       |
|--|-------|
| <b>SEMICONDUCTOR DATA BOOK</b> Newnes . . . . .                            | £5.90 |
| <b>MICROPROCESSORS FOR HOBBYISTS R. Coles</b> . . . . .                    | £3.65 |
| <b>PRACTICAL ELECTRONIC PROJECT BUILDING</b> Ainslie and Colwell . . . . . | £3.35 |

### POPULAR LOW COST BOOKS

Most titles new this month

|  |       |
|--|-------|
| <b>RADIO CONTROL FOR BEGINNERS</b> Rayer . . . . .                               | £1.75 |
| <b>INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE.</b> 320 pages, Michaels . . . . . | £2.95 |
| <b>ELECTRONIC PROJECTS FOR CARS AND BOATS</b> Penfold . . . . .                  | £1.95 |
| <b>SECOND BOOK OF CMOS IC PROJECTS</b> Penfold . . . . .                         | £1.50 |
| <b>50 SIMPLE L.E.D. CIRCUITS BOOK 2.</b> . . . . .                               | £1.35 |
| <b>ELECTRONIC MUSIC PROJECTS</b> Penfold . . . . .                               | £1.75 |
| <b>ELECTRONIC PROJECTS IN THE HOME</b> Bishop . . . . .                          | £1.75 |
| <b>ELECTRONIC GAMES</b> Penfold . . . . .  | £1.75 |
| <b>PROJECTS IN OPTO ELECTRONICS</b> Penfold . . . . .                            | £1.25 |
| <b>52 PROJECTS USING IC 741</b> Redmer . . . . .                                 | 95p   |
| <b>ELECTRONIC TIMER PROJECTS</b> Rayer . . . . .                                 | £1.95 |
| <b>POWER SUPPLY PROJECTS</b> Penfold . . . . .                                   | £1.75 |
| <b>REMOTE CONTROL PROJECTS</b> Bishop . . . . .                                  | £1.95 |
| <b>SOLID STATE SHORTWAVE RECEIVERS FOR BEGINNERS</b> Penfold . . . . .           | £1.25 |
| <b>BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS</b> Penfold . . . . .         | £1.50 |
| <b>MODEL RAILWAY PROJECTS</b> Penfold . . . . .                                  | £1.95 |
| <b>IC 555 PROJECTS</b> Parr . . . . .  | £1.95 |
| <b>ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING</b> Berry . . . . .              | £1.75 |
| <b>POPULAR ELECTRONIC CIRCUITS BOOK 2</b> Penfold . . . . .                      | £2.35 |

## MORE KITS AND COMPONENTS IN OUR LISTS

**FREE PRICE LIST**  
 Price list included with orders or send see (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

## 1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 70p in stamps or add 70p to order.

**MORE H.E. KITS PLUS E.E. AND E.T.I. PROJECT. KITS IN THE PRICE LIST.**

|               |            |             |
|---------------|------------|-------------|
| C106D 58p     | 2N5457 58p | BFY51 24p   |
| TIC46 48p     | 2N5444 63p | BFY52 23p   |
| OA47 11p      | 40673 98p  | 4011 20p    |
| OA90 9p       | AC118 29p  | 4013 32p    |
| O.A202 16p    | AC141 39p  | 4017 62p    |
| W005 33p      | AC142 39p  | 4020 60p    |
| W06 47p       | AC176 37p  | 4024 20p    |
| Z5J £2.92     | BC182 11p  | 4069 20p    |
| IN4901 5 1/2p | BC182L 11p | 4081 20p    |
| IN4005 6p     | BC183 11p  | 4083 38p    |
| IN4148 5p     | BC184 11p  | 40174 £1.20 |
| IN5404 11p    | BC134L 11p | 4522 £1.25  |
| IN5408 19p    | BC212 11p  | TP2955 69p  |
| BF244 87p     | BC212L 11p | TP3055 69p  |
| MPP102 69p    | BC213 11p  | TPS A13 35p |
| TIS88 A 57p   | BC214 11p  | SN3053 25p  |
| VN67A £1.21   | BC214L 11p | 2N3055 59p  |
| 2N3819 78p    | SD131 48p  | 2N3702 11p  |
| 2N3820 78p    | BFY50 25p  | 2N3704 11p  |

**ICW CARBON FILM RESISTORS**  
**1/2 SERIES. 1R-10M . . . . . 1p each**  
**MIN. HORIZ. PRESETS. 100R-4M7. 12p each**  
**MIDGET POTS. LINEAR. 470R-4M7 37p each**  
**LOG. 4K7-2M3 . . . . . 34p each**  
**SWITCHED POTS. 4K7-1M. LIN. 75p. LOG 76p**

**POLYESTER (C280) CAPACITORS, 250V**  
 10nF, 15nF, 22nF, 33nF, 47nF 7p each, 68nF, 100nF 8p, 150nF, 220nF 12p, 330nF 15p, 470nF 20p, 680nF 25p, 1µF 33p, 1.5µF 45p, 2.2µF 65p.

**SUB MINIATURE PLATE CERAMICS, 63V**  
 Values in pF: 2, 2; 3, 3; 4, 7; 5, 6; 6, 8; 8, 2; 10, 15; 22, 33; 47 & 56pF 7p each, 68pF, 100pF 7p each, 150pF, 220pF, 330pF 11p each, 330pF, 470pF, 1000pF 5p each, 2200pF 8p each, 3300pF, 4700pF 7p each, 10nF 13p, 100nF 22p, 47nF 14p.

**ELECTROLYTIC CAPACITORS**  
**AXIAL Leads: 1µF/16V 11p; 1µF/63V, 1µF/100V 12p; 2.2µF/63V, 3.3µF/63V, 4.7µF/63V 12p; 10µF/16V 11p; 10µF/25V, 10µF/63V 12p; 22µF/10V, 22µF/25V 12p; 22µF/63V 15p; 33µF/40V, 47µF/25V 12p; 47µF/40V 15p; 47µF/63V 18p; 100µF/16V 12p; 100µF/25V 15p; 100µF/40V 18p; 100µF/63V 29p; 220µF/10V 15p; 220µF/25V 19p; 470µF/16V 29p; 470µF/25V 36p; 470µF/40V 55p; 680µF/16V 32p; 1000µF/10V 30p; 1000µF/16V 33p; 1000µF/25V 48p; 1000µF/40V 58p; 1000µF/63V 79p; 2200µF/10V 39p; 2200µF/25V 64p; 2200µF/63V £1.10.**

**SWITCHES**  
**MIN. TUGGLE spst 59p; spdt 69p; dpdt 79p.**  
**MIN. PUSH ON. 13p. PUSH OFF. 22p.**  
**FOOTSWITCH & ALT. ACTION spco £1.39;**  
**dpco £1.88.**  
**ROTARY SWITCHES. 1p 12 way, 2p 6w, 3p 4w, 4p 3w . . . . . 69p each**  
**12V 165R DPCC RELAY . . . . . £2.98**

|   |       |
|---|-------|
| <b>SPEAKERS. Miniature, 8 ohm . . . . .</b> | 87p   |
| 64-75 ohm . . . . .                         | 89p   |
| <b>CRYSTAL EARPIECE . . . . .</b>           | 65p   |
| <b>MONO HEADPHONES . . . . .</b>            | £2.96 |
| <b>TELEPHONE PICK-UP COIL . . . . .</b>     | 72p   |

### INTEGRATED CIRCUITS

|               |               |
|---------------|---------------|
| LM386N 92p    | LM386N 92p    |
| LM387 £1.10   | LM387 £1.10   |
| LM389N £1.10  | LM389N £1.10  |
| LM1830 £1.98  | LM1830 £1.98  |
| LM3303 £2.99  | LM3303 £2.99  |
| LM3314 £2.99  | LM3314 £2.99  |
| LM3915 £3.96  | LM3915 £3.96  |
| MC3340 £2.15  | MC3340 £2.15  |
| NE570N £4.98  | NE570N £4.98  |
| NE571N £4.84  | NE571N £4.84  |
| OM335 £8.98   | OM335 £8.98   |
| SN76477 £2.69 | SN76477 £2.69 |
| TL064 £1.84   | TL064 £1.84   |
| TL071 47p     | TL071 47p     |
| TL082 74p     | TL082 74p     |
| TL083 £1.52   | TL083 £1.52   |
| TL084 £1.54   | TL084 £1.54   |
| TL430 95p     | TL430 95p     |
| U237B £1.69   | U237B £1.69   |
| U267B £2.20   | U267B £2.20   |
| ULN28B £1.57  | ULN28B £1.57  |
| 2N414 98p     | 2N414 98p     |
| 2N419CE £2.21 | 2N419CE £2.21 |
| 7400 22p      | 7400 22p      |
| 7447 £1.14    | 7447 £1.14    |
| 7490 56p      | 7490 56p      |
| 7495 80p      | 7495 80p      |

**OPTO**  
**BPX25 . . . . . £2.24**  
**2N5777 . . . . . 60p**  
**ORP12 . . . . . 99p**  
**TIL32 . . . . . 81p**  
**TIL78 . . . . . 74p**  
**LEDS WITH GLASS**  
 3mm. Red15p. Green18p. Yellow 20p.  
 5mm. Red16p. Green28p. Yellow 29p.

**FLASHING LED . . . . . 75p**  
**RECTANGULAR Red . . . . . 24p**  
**MAINS PANEL Neon . . . . . 32p**

**ZENER DIODES. 400mW.**  
**BZV88. Range 2V7 to 33V. 12p each.**

**I.C. SOCKETS**  
 8 pin . . . . . 15p  
 14 pin . . . . . 17p  
 16 pin . . . . . 15p

**JACKSON**  
 300pF dilecon . . . . . £2.36  
 500pF dilecon . . . . . £2.92  
 C804 Ver. Cap. 100pF £2.24  
 25pF £2.46, 50pF £2.48, 100pF £2.83, 150pF £3.48, '01' 365pF £3.48, '02' 365pF £4.49, '01' 208 & 176pF £3.98.

|  |           |
|--|-----------|
| <b>MIN. BUZZERS. 6V. 50p. 9V. £1.10.</b> | 12V. 65p. |
| <b>MAGNETIC EARPIECE . . . . .</b>       | 15p       |
| <b>STEREO HEADPHONES . . . . .</b>       | £4.35     |
| <b>F.M. AERIAL . . . . .</b>             | 49p       |

|  |  |       |
|--|--|-------|
| <b>VEROBOARD 0.1" COPPER STRIPS</b>      | <b>PP3 CLIPS 10p</b>                   |       |
| 10 strips 24 holes . . . . . £1.20 per 5 | <b>PP9 CLIPS 11p</b>                   |       |
| 24 strips 37 holes . . . . . 78p         | <b>PANEL METERS</b>                    |       |
| 24 strips 50 holes . . . . . 89p         | 50µA, 100µA, 1mA,                      |       |
| 36 strips 37 holes . . . . . 89p         | 1A, 25V, 100µA 0-                      |       |
| 36 strips 50 holes . . . . . 99p         | £3.98                                  |       |
| Terminal pins 0.1" . . . . . 52p/100     | <b>BIMBOARD 1 BREADBOARD . . . . .</b> | £5.98 |
|  | <b>VEROBOARD BREADBOARD . . . . .</b>  | £4.20 |

## ADVENTURES WITH MICROELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering. Uses a Bimboard 1 breadboard, gives clear instructions with lots of pictures. 11 projects based on integrated circuits — includes dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard 1 breadboard and all the components for the projects.  
**Adventures with Microelectronics £2.55. Component pack £29.64 less battery.**

## ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects.  
**Adventures with Electronics £2.40. Component pack £17.98 less battery.**

MAGENTA gives you **FAST DELIVERY OF QUALITY COMPONENTS & KITS.** All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

## MAGENTA ELECTRONICS LTD.

HJ24, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS., DE14 2ST. 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY. ADD 45p P&P TO ALL ORDERS.

**OFFICIAL ORDERS WELCOME.**  
**IRISH REPUBLIC & B.F.P.O. EUROPE:** Deduct 10% from prices shown Payment, must be in Sterling.  
**ACCESS AND BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST.**  
**SAE ALL ENQUIRES.**  
 Normal despatch by return of post.



# MONITOR



IT NEVER rains but it pours, quite often. This month's new releases include, for the first time, a selection of video monitors suitable for use as computer VDUs.



Most home computers are equipped with a 'video' output intended for use with ordinary domestic television sets. This output is, in fact, a frequency modulated RF signal which is tuned in on Channel Six. This system provides a cheap and convenient display, but the definition is not as good as it could be, due to lack of stability and bandwidth of most video modulators — and there is often a conflict over the use of the set! The simple solution to the second problem has been to buy or hire a monochrome TV which can be used solely as a VDU. Until now, however, there has been no easy, *safe* method of achieving improved display resolution (most domestic TVs cannot be safely modified to accept video input), so the appearance of a range of monitors designed for home computer users is especially welcome.

The most attractive of the new monitors is the 12" Monochrome Data Display Monitor (above) from Chable Electronics Limited. It operates from either 12 V DC or 240 V AC, measures a compact 370 x 290 x 30 mm and can be lifted with one hand; the display area is 24 x 80 characters. However, the DDM's most appealing feature, to the home computer user, is its price — £85.68 including VAT and carriage. For further information contact Chable Electronics Limited, 3A Commercial Street, Batley, West Yorkshire WF17 5HJ or 'phone (0924) 441128.

The range of monitors from Thandar (middle) are intended for professional users, although they are also suitable for the home user. The range starts with the TV2S, a 2" model, and extends through 5", 9" to 12" types. They are supplied in chassis format, with a choice of B/W or green phosphor tubes and the option of standard or non-glare screens. Prices range from £119, including VAT, up to £155. Colour monitors, from 14" to 26", are also available on application. Thandar Electronics Limited are located at London Road, St. Ives, Huntingdon, Cambs PE17 4HJ; Tel. (0480) 64646.

Two new monitors (below right) from Stotron Ltd. are intermediate in price. The 12" model costs £99.50 and the 9" one, £92.75; both prices include VAT and carriage. The picture tubes are green phosphor, showing 1920 characters in 80 x 24 format and comply with DHEW regulations on X-radiation. Video input is via either RCA phono jack or SO-239 UHF connectors.

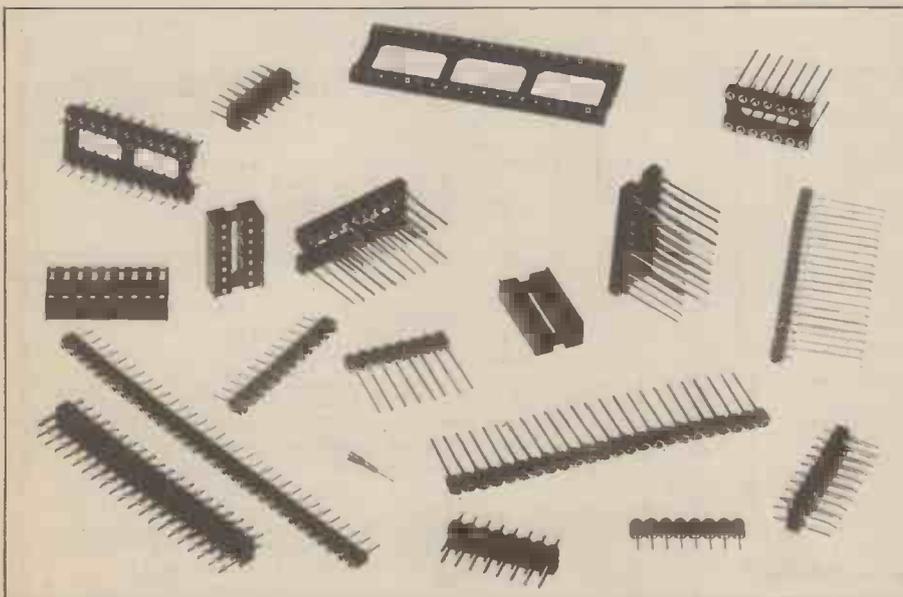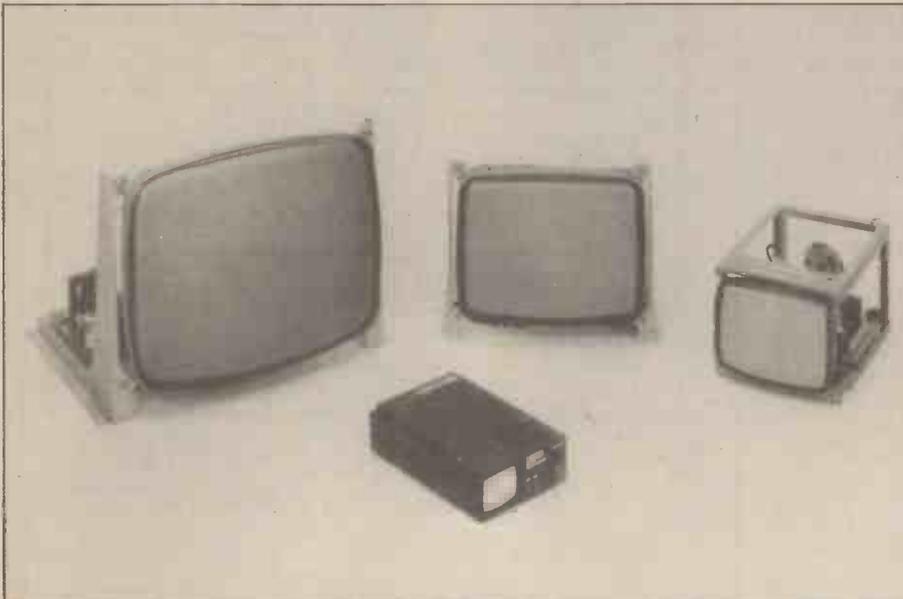Another new product line from Stotron is a range of low-profile IC sockets (left), featuring beryllium copper four-jaw gold plated contacts and insulation resistance of  $10^{14}$  ohms. Full details of these and other new lines from Stotron appear in their 1982 catalogue, which is available from Stotron Ltd, Haywood House, Ivyhouse Lane, Hastings, East Sussex TN35 4PL; Tel. (0424) 442160.



# MONITOR




The best of the test equipment releases, this month, is a new hand-held digital multimeter (above) made by Sabtronics International Inc., of Tampa Florida (they don't just grow oranges there, you know) and marketed in the UK by Black Star Ltd. The Model 2033 features 0.5% basic DC accuracy, a large 3½ digit LCD, push-button range and function switches and is powered by either a single PP3 battery or an optional AC adaptor. The 2033 will measure AC or DC voltages from 100 uV to 1000 V in five ranges, resistance from 1R0 to 20M in five ranges and AC or DC current from 10 uA to 2 Amps in three ranges. It is supplied complete with test leads for £42.26 including VAT; a high voltage probe is available as an optional accessory. The Sabtronics 2033 is available from various distributors around the country or directly from Black Star Ltd., 9A Crown Street, St. Ives, Huntingdon, Cambs PE17 4EB or 'phone (0480) 62440 for the location of our nearest dealer.

Readers of our new POPULAR COMPUTING section who are also owners of Sharp, Casio or similar pocket computers will be interested in a Manchester based mail order firm who specialise in pocket and portable computer systems. They are Elkan Electronics of 28, Bury New Road, Prestwich, Manchester M25 8LD. Their new catalogue, shortly to be released, will include the Sharp PC-1211 and PC-1500 and Casio's FX-702P, together with new software and books.

Obtaining the mechanical parts for a project is often more difficult than actually constructing the circuit, so new sources for hardware are always welcome. Fieldtech Heathrow Limited are marketing a new range of midget toggle switches, both single and double-pole, with switching from basic ON/OFF to variations of ON/OFF/ON through, various retailers, nationwide. The new range, called Type 550, is also available direct from Fieldtech Heathrow at prices ranging from 32 pence to 51 pence each. Data sheets will be supplied to interested readers who write to Fieldtech Heathrow Limited, Components Division, Huntavia House, 420 Bath Road, Longford, Middx UB7 0LL; Tel. (01) 897 6446.

Still on the subject of cases, Adsum Ltd have a range of standard instrument cases designed to suit a wide variety of applications. They are made from ABS plastic in standard colours (black or grey) and supplied blank, with internal fixing points. Two sizes are made, with external dimensions of 170 x 250 mm or 310 x 250 mm, and a range of heights. The maximum PCB size is, in each case, 10 mm less than each of the external dimensions. Details are available from Adsum Ltd., Kiln Acre, Wickham Road, Fareham, Hants PO16 7ZH, Tel. (0329) 285858.

Latest news from the leading edge of technology concerns the introduction of stereo sound video machines. Leading the way will be Grundig, the West German manufacturers of almost everything electronic, with Philips and JVC not far behind. This long awaited (and long overdue) innovation will be welcomed by all — but particularly those who have been disappointed by the quality of sound on video cassettes of pop music or spectacular movies such as Flash Gordon, Superman or Star Trek. Already, producers of video-pop are preparing sound versions of popular tapes, as they will almost certainly benefit most from the improved quality of stereo.

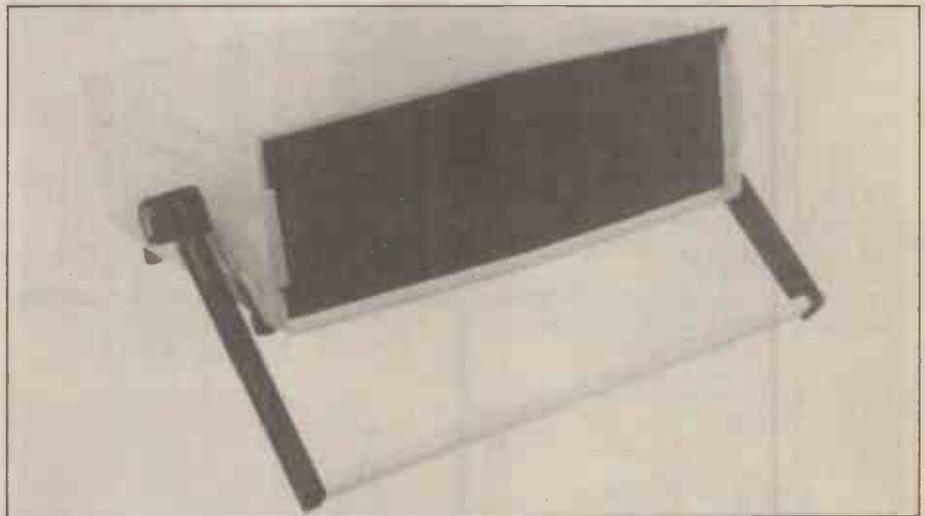

Still on the subject of hardware, OK Machine & Tool (UK) Ltd have announced a new addition to their PacTec case range. The Series CLH (above) has a handle which doubles as a tilt-leg and is moulded from heavy weight ABS plastic. The basic size is 318 x 296 mm, with heights ranging from 115 to 146 mm. The cases accept a variety of mounting systems — PC card guides, mounting rails and other hardware — so allowing considerable flexibility for creating a number of internal configurations. The Series comes in four standard colours (blue, black, tan and grey) and can be supplied in kit form. The CLH Series is available direct from OK Machine & Tool (UK) Ltd, Dutton Lane, Eastleigh, Hants SO5 4Aa (Tel. 0703 610944) or from Watford Electronics.

Grundig are also reported to be the first company ready to introduce stereo TV receivers to the UK. However, although stereo sound is broadcast in West Germany, it is unlikely to broadcast in the UK for some time, yet. True stereo TV will almost certainly come into general use when satellite television commences. Several European countries, notably West Germany and France, have their satellite TV systems well under way while, in the UK, a joint venture by three major companies, British Aerospace, British Telecom and Marconi Avionics, will put a UK satellite into orbit around 1986.

There are two possible methods by which satellite TV can be received — directly, by a small dish antenna on the roof, or via cable from a central receiving station. The Government appears to favour the idea of cable distribution, so it is likely that cable and satellite TV will be closely linked in this country.



# BI-PAK BARGAINS

## "IRRESISTABLE RESISTOR BARGAINS"

| Pak No. | Qty* | Description                             | Price |
|---------|------|---|-------|
| SX10    | 400  | Mixed "All Type" Resistors              | £1    |
| SX11    | 400  | Pre-formed 1/4-watt Carbon Resistors    | £1    |
| SX12    | 200  | 1/4 watt Carbon Resistors               | £1    |
| SX13    | 200  | 1/4 watt Carbon Resistors               | £1    |
| SX14    | 150  | 1/2 watt Resistors 22 ohm 2m2 Mixed     | £1    |
| SX15    | 100  | 1 and 2 watt Resistors 22 ohm 2m2 Mixed | £1    |

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.

\*Quantities approximate, count by weight.

## "CAPABLE CAPACITOR PAKS"

| Pak No. | Qty* | Description                               | Price |
|---------|------|---|-------|
| SX16    | 250  | Capacitors Mixed Types                    | £1    |
| SX17    | 200  | Ceramic Capacitors Miniature Mixed        | £1    |
| SX18    | 100  | Mixed Ceramics 1µf-560µf                  | £1    |
| SX19    | 100  | Mixed Ceramics 68µf-0.5mf                 | £1    |
| SX20    | 100  | Assorted Polyester/Polystyrene Capacitors | £1    |
| SX21    | 60   | Mixed C280 type capacitors metal foil     | £1    |
| SX22    | 100  | Electrolytics, all sorts                  | £1    |
| SX23    | 50   | Quality Electrolytics 50-1000µf           | £1    |
| SX24    | 20   | Tantalum Beads, mixed                     | £1    |

\*Quantities approximate, count by weight.

## AUDIO PLUGS, SOCKETS AND ACCESSORIES

**25** pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240°, Inline 3-6 Pin, Speakers, Phono, Jack, Stereo and Mono, etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

|      |   |     |
|------|---|-----|
| SX26 | 3 Pcs of 6 pin 240° DIN Plugs and Chassis Sockets                                   | 50p |
| SX27 | 1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket. | 30p |
| SX28 | 4 Phono plugs and 2 dual phono connectors   | 30p |
| SX29 | 1 x 2.5mm Plug to 3.5mm Socket adaptor.   | 20p |
| SX30 | 1 x 3.5mm Plug to 2.5mm Socket adaptor.   | 20p |
| SX31 | 1 x 3.5mm Plug to Phono Socket adaptor.   | 20p |

## BARGAINS

|      |  |     |
|------|--|-----|
| SX42 | 20 small .125 Red LED's  | £1  |
| SX43 | 10 Rectangular Green LED's .2  | £1  |
| SX46 | 30 Assorted Zener Diodes 250mw 2 watt mixed voltages all coded. New.                                 | £1  |
| SX47 | 4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fit size 29 x 20mm                 | 50p |
| SX49 | 20 Assorted Slider Knobs Black/Chrome, etc.  | £1  |
| SX80 | 12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting | £1  |

## TRIACS — PLASTIC

|                                  |         |
|----------------------------------|---------|
| 4 AMP — 400v — T0202 — TAG 136G. | 100 OFF |
| 1 OFF                            | 10 OFF  |
| 40p                              | £3.75   |
| 8 AMP 400v — T0220 — TAG 425     | 100 OFF |
| 60p                              | £5.75   |

**2N3055** The best known Power Transistors in the World — 2N3055 NPN 115w. Our BI-PAK Special Offer Price:  
10 off £1.50 50 off £10.00 100 off £3.50

**BD312** COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055. Equivalent M12955 — BD312 — T03 SPECIAL PRICE £8.70 each 10 off £6.50

## TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical. Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish! all identifiable and valued in current catalogues well over £25.00. Our Fight Against Inflation Price —

— Beat the Budget  
— Down with Depression

**JUST £6.50.**  
O/no SX85

## £1 FREE PAK

Get a £1 FREE PAK! Orders over £10 excluding VAT. Choose £1 Pak free (or 2 x 50p) add it to your order and save even more money!

This offer only applies to this advertisement

## Guarantee

Satisfaction or your money back has always been BI-PAK'S GUARANTEE and it still is! All these Sale items are in stock, in quantity and we will despatch the same day as your order is received

## MORE BARGAINS!

|      |  |    |
|------|--|----|
| SX51 | 60 metres PVC covered Hook-up wire single and stranded. Mixed colours. | £1 |
| SX58 | 25 Assorted TTL Gates 7400 Series 7401-7460.                           | £1 |
| SX59 | 10 Assorted flip Flops and MSI TTL                                     | £1 |
| SX60 | 20 Assorted Slider Potentiometers                                      | £1 |
| SX61 | 25 Assorted Potentiometers, Rotary, Dual, etc.                         | £1 |
| SX62 | 40 Assorted Pre-Sets Hor/Vert etc.                                     | £1 |
| SX79 | 10 Reed Switches — glass type<br>3 Micro Switches — with lever         | £1 |

## STILL MORE! SLIDER POTENTIOMETERS

|      |                  |      |               |
|------|------------------|------|---------------|
| SX63 | 5 x 470 ohms Lin | SX67 | 5 x 47k Lin   |
| SX64 | 5 x 1k Lin       | SX68 | 5 x 47k Log   |
| SX65 | 5 x 22k Lin      | SX69 | 5 x 100k Lin  |
| SX66 | 5 x 22k Log      | SX70 | 5 x 1 meg Lin |

All at 50p per pack.

SX71 50 BC108 "Fallouts", Manufacturers out of spec on volts or gain. You test. £1

SX72 A mixed bundle of Copper clad Board, Fibre glass and paper. Single and double sided. A fantastic bargain. £1

SX78 Genuine MULLARD OC71 Germanium PNP Transistors Brand New 10 for £1

## 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncoded — you select for VLTS ALL perfect devices — NO duds Min 50v 50 for £1.00 — worth double ORDER NO SX76

|  |        |         |         |          |
|--|--------|---------|---------|----------|
| Silicon General Purpose NPN Transistors TO-18 Case | 50 off | 100 off | 500 off | 1000 off |
| Lock fit leads — coded CV7644 Similar to BC147     | £2.00  | £3.80   | £17.50  | £30.00   |
| — BC107 — ZT89 ALL NEW! VCE 70v IC500mA Hfe 75-250 | £2.50  | £4.00   | £19.00  | £35.00   |

Order as CV764

## Silicon NPN'L' Type Transistors

TO-92 Plastic centre collector Like BC182L — 183L — 184L VCB0 45 VCE0 30 IC200mA Hfe 100-400

|        |         |         |          |
|--------|---------|---------|----------|
| 50 off | 100 off | 500 off | 1000 off |
| £1.50  | £2.50   | £10.00  | £17.00   |

## PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line VCE0 40 VCB0 35 Ic 300mA Hfe 50-400 Brand New — Uncoded — Perfect Devices  
50 off 100 off 500 off 1000 off  
£2.00 £3.50 £15.00 £25.00  
Order as ZTXPNP

## BI-PAK'S OPTO BARGAIN OF THE YEAR!

Valued at over £10—Normal Retail—we offer you a pack of 25 Opto devices to include LED's Large and Small in Red, Green, Yellow and Clear. 7 Segment Displays both Common Cathode and Common Anode PLUS bubble type displays—like DL-33. Photo Transistors—similar to OCP71 Photo Detectors—like MEL11-12. This whole pack of 25 devices will cost you just

# £4.00

AND we guarantee your money back if you are not completely satisfied. FULL data etc included.  
Order No. SX67.

## The Third and Fourth Hand...

.... you always need but have never got 'untill now' This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO 1402 £5.50 Without magnifier ORDER NO 1400 £4.75



## MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch. LED indicators at each of the five charging points

|                    |                  |
|--------------------|------------------|
| Charges: —         | Power —          |
| PP3 (9V)           | 220-240V AC      |
| U12 (1.5V penlite) | Dims —           |
| U11 (1.5V "C")     | 210 x 100 x 50mm |
| U2 (1.5V "D")      | £6.95            |

## POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket Fused for safety. Polarity reversing socket Voltage switch. Lead with multi plug Input — 240V AC 50HZ Output — 3 4 5 6 7 5. 9 & 12V DC. Rating. — 300 ma MW88

## 5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module

Specification  
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 kHz — 3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%  
BI-PAK'S give away price

# £2.25

You could not build one for this price.

## BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK'S policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a BI-PAK Catalogue. Have one by you all the time—it pays to buy BI-PAK

To receive your copy send **75p** plus 25p p&p.

# BI-PAK

Send your orders to Dept HE5 BI-PAK PO BOX 6 WARE HERTS. SHOP AT 3 BALDOCK ST, WARE, HERTS  
TERMS cash with order, SAME DAY DESPATCH, ACCESS BARCLAYCARD ALSO ACCEPTED TEL (0920) 3182, GIRD 388 7006  
ADD 15% vat and 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order. Total. Postage add 75p per Total order.

# Rapid Electronics

Tel: 0206 36412  
Hill Farm Industrial Estate  
Boxted, Colchester  
Essex CO4 5RD



### CAPACITORS

Polyester Radial Leads, 250V 280 type  
0.01, 0.015, 0.022, 0.033, 6p; 0.047, 0.068, 0.1, 7p;  
0.15, 0.22, 0.33, 0.47, 13p; 0.68, 20p; 1u 23p.

Electrolytic Radial or Axial Leads  
0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 10/25V, 7p;  
22/25V, 47/25V, 8p; 100/25V, 9p; 220/25V, 14p;  
470/25V, 22p; 1000/25V, 30p.

Polyester Siemens PCB  
1n, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 7p; 22n, 33n, 47n, 68n, 80p;  
100n, 9p; 151n, 11p; 221n, 13p; 330n, 20p; 470n, 26p;  
680n, 29p; 1u, 33p; 2u, 50p.

Tantalum bead  
0.1, 0.22, 0.33, 0.47, 1.0 @ 35V 12p; 2.2, 4.7, 10 @  
25V, 20p; 15/16V 30p; 22/16V, 27p; 33/16V, 45p;  
47/16V, 27p; 47/16V, 70p; 68/6V, 40p; 100/10V, 90p.

Ceramic 22p-0.1u, 50V, 3p each.  
\* Mullard Miniature ceramic plate.  
\* 1.8pF to 100pF, 6p each.  
Polystyrene, 5% tolerance  
10p-1000p 6p, 1500-4700p 8p, 6800-0.012 10p.  
Trimmers, Mullard 808 Series.  
2-10pF, 22p-22pF 30p, 5.5-65pF 35p.

### COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at reduced prices

1/4W 5% Resistor Kit. Contains 10 of each value from 4.7k to 1M (65 resistors) 48p.

Ceramic Capacitor Kit. Contains 5 of each value from 22p to 0.01 (135 caps) 137p.

Polyester Capacitor Kit. Contains 5 of each value from 0.01 to 1uF (65 caps) 157p each.

Presst Kit. Contains 5 of each. Value from 1000k to 1M (total 65 presets). 425p each.

Nut and Bolt Kit. Total 300 items. 140p.  
25 6BA 1/2" bolts 25 4BA 1/2" bolts  
50 6BA nuts 25 4BA 1/2" bolts  
50 6BA washers 50 6BA washers

### POTENTIOMETERS

Rotary. Carbon track Log or Lin 1K-2M2.  
Single 32p. Stereo 85p  
Single switched 80p  
Slide 60mm travel single Log or Lin 5K-500K, 63p.  
Preset. Submin horiz. 100M-1M. 7p each.

### BRIDGE RECTIFIERS

|           |    |          |     |
|-----------|----|----------|-----|
| 1A 50V    | 22 | 18.0M    | 240 |
| 1A 400V   | 35 | 18.432M  | 220 |
| 2A 200V   | 40 | 19.968M  | 200 |
| 2A 400V   | 45 | 38.6667M | 220 |
| 6A 100V   | 60 | 48.0M    | 320 |
| 6A 400V   | 95 | 116M     | 300 |
| VM18 DIL  |    |          |     |
| 0.9A 200V | 50 |          |     |

### OPTO

|              |    |              |    |
|--------------|----|--------------|----|
| * 3mm red    | 8  | * 5mm red    | 8  |
| * 3mm green  | 12 | * 5mm green  | 12 |
| * 3mm yellow | 12 | * 5mm yellow | 12 |

Clips to suit 3p each

|             |    |       |    |
|-------------|----|-------|----|
| Rectangular | 12 | TL132 | 40 |
| * red       | 12 | TL178 | 40 |
| green       | 17 | TL111 | 60 |
| yellow      | 17 | ORP12 | 85 |
| TL138       | 40 | TL100 | 90 |

Seven Segment Displays

|               |     |             |     |
|---------------|-----|-------------|-----|
| Com. cathode  |     | Com. anode  |     |
| DL704 0.3"    | 95  | DL707 0.3"  | 95  |
| * FND500 0.3" | 80  | FND507 0.5" | 90  |
| TL1313 0.3"   | 105 | TL1312 0.3" | 105 |
| TL1322 0.5"   | 115 | TL1321 0.5" | 115 |

All seven segment displays are supplied with connection details.  
2N5777 45 Dual Colour LED 60

### CRYSTALS

|          |     |
|----------|-----|
| 100KHz   | 290 |
| 200KHz   | 370 |
| 1MHz     | 300 |
| 1.008M   | 370 |
| 1.8432M  | 300 |
| 2.0M     | 270 |
| 2.4576M  | 220 |
| 3.276M   | 240 |
| 3.579M   | 120 |
| 4.0M     | 150 |
| 4.194M   | 150 |
| 4.43M    | 125 |
| 5.1M     | 240 |
| 6.0M     | 200 |
| 6.144M   | 180 |
| 7.00M    | 250 |
| 8.0M     | 170 |
| 10.0M    | 290 |
| 12.0M    | 240 |
| 16.0M    | 240 |
| 18.0M    | 240 |
| 18.432M  | 220 |
| 19.968M  | 300 |
| 38.6667M | 320 |
| 48.0M    | 220 |
| 116.8M   | 300 |

### BOXES

Dimensions in inches. Aluminium.

|               |      |           |      |
|---------------|------|-----------|------|
| 3 x 2 x 1     | 70p  | 6 x 4 x 2 | 120p |
| 4 x 3 x 1 1/4 | 85p  | 6 x 4 x 3 | 150p |
| 4 x 3 x 2     | 100p | 8 x 6 x 2 | 180p |

Plastic Project Boxes  
Complete with lid and screws.  
3 x 2 x 1in. 55p  
4 1/2 x 3 x 1 1/2in. 88p  
7 x 4 x 2in. 160p.

### SWITCHES

|                  |             |                   |                     |                             |
|------------------|-------------|-------------------|---------------------|-----------------------------|
| Submin Toggle    |             | SPST 50p          | DPDT 60p            | * DPDT 50p                  |
| Miniature toggle |             | SPDT 80p          | SPDT centre off 90p | DPDT 90p                    |
| Standard toggle  |             | SPST 35p          | DPDT 48p            | * Miniature DPDT slide 12p  |
| * Push to make   | 12p         | Push to break     | 22p                 | Rotary type adjustable stop |
| 1P12W            | 2P6W, 3P4W, | 4P3W all 55p each |                     | DIL switches                |
| 4 FSPT 80p       | 6 SPST 80p  | 8 SPST 100p       |                     |                             |

### CABLES

20 metre pack single core connecting cable, ten different colours 65p  
Speaker cable 10p/m  
Standard screened 16p/m  
Twin screened 24p/m  
2.5A 3 core mains 23p/m  
10 way ribbon 65p/m  
20 way ribbon 120p/m

### OPTO SPECIALI

Special pack containing thirty 5mm LEDs. Ten red, ten green, ten yellow.  
Our normal price is 320p.  
Special Offer price just 250p!  
Offer expires 30th May 82.  
Please note these are top quality grade 1 devices.

### HARDWARE

PP3 Battery clips 6p  
Red or black crocodile clips 6p  
Black pointer control knob 15p  
Pair Ultrasonics 350p  
\* 6V Electronic buzzer 60p  
\* 12V Electronic buzzer 65p  
\* PB270 Piezo transducer 75p  
TO18 transistor socket 15p  
64mm 64 ohm speaker 70p  
64mm 8 ohm speaker 70p

### PCB MATERIALS

Aflac PCB transfer sheets - please state type (e.g. DIL pads etc.) 45p  
Dalo etch resist pen 100p  
Fibre glass board 3.75" x 8" 75p  
Ferric Chloride 250ml bottle 100p

### TRANSISTORS

|         |     |          |    |          |     |         |     |          |         |          |       |          |     |
|---------|-----|----------|----|----------|-----|---------|-----|----------|---------|----------|-------|----------|-----|
| AC125   | 35  | * BC158  | 8  | BCY71    | 18  | BFX86   | 25  | TIP30A   | 45      | * ZTX107 | 8     | 2N3054   | 55  |
| AC126   | 25  | * BC159  | 8  | BCY72    | 18  | BFX87   | 25  | TIP30B   | 40      | * ZTX108 | 8     | 2N3055   | 50  |
| AC127   | 25  | BC160    | 45 | BCY73    | 18  | BFX88   | 25  | TIP30C   | 60      | ZTX109   | 12    | 2N3442   | 120 |
| * AC128 | 20  | BC169C   | 10 | BD111    | 35  | BFY50   | 23  | TIP31A   | 45      | ZTX301   | 16    | 2N3703   | 9   |
| AC176   | 25  | BC170    | 8  | BD132    | 35  | BFY51   | 23  | TIP31B   | 55      | ZTX304   | 17    | 2N3705   | 9   |
| AC187   | 22  | BC171    | 10 | BD133    | 50  | BFY52   | 23  | TIP31Z   | 45      | ZTX341   | 30    | 2N3706   | 9   |
| AC188   | 22  | BC172    | 8  | BD135    | 50  | BFY53   | 32  | TIP32B   | 55      | ZTX500   | 15    | 2N3707   | 10  |
| AD142   | 120 | BC177    | 18 | BD136    | 30  | BFY55   | 32  | TIP32C   | 60      | ZTX501   | 15    | 2N3708   | 10  |
| AD149   | 80  | BC178    | 18 | BD137    | 40  | BFY56   | 32  | TIP33A   | 50      | ZTX502   | 15    | 2N3709   | 10  |
| AD161   | 40  | BC179    | 18 | BD138    | 30  | BRY39   | 40  | TIP33C   | 75      | ZTX503   | 18    | 2N3722   | 190 |
| AD162   | 40  | BC182    | 10 | BD139    | 35  | BSX20   | 20  | TIP34A   | 60      | ZTX504   | 25    | 2N3773   | 210 |
| AF124   | 60  | * BC182L | 8  | BD140    | 35  | BSX29   | 35  | TIP34C   | 85      | ZN697    | 20    | * 2N3819 | 18  |
| AF126   | 50  | BC183    | 10 | BD214    | 110 | BSY95A  | 25  | TIP35A   | 160     | ZN698    | 40    | 2N3820   | 40  |
| AF139   | 40  | BC183L   | 10 | BD206    | 60  | BU205   | 160 | TIP35C   | 180     | ZN706A   | 20    | 2N3823   | 65  |
| AF176   | 70  | BC184    | 10 | BD222    | 85  | BU206   | 200 | TIP36A   | 170     | ZN708    | 20    | 2N3866   | 10  |
| AF239   | 75  | * BC184L | 7  | BF180    | 35  | BU208   | 170 | TIP36C   | 195     | ZN918    | 35    | 2N3903   | 90  |
| BC107   | 10  | BC212    | 10 | BF182    | 35  | MJ2955  | 95  | TIP41A   | 60      | ZN1132   | 22    | 2N3904   | 10  |
| BC107B  | 10  | BC212L   | 10 | BF184    | 25  | MJE340  | 50  | TIP42A   | 60      | ZN1613   | 30    | * 2N3905 | 6   |
| * BC108 | 9   | BC213    | 10 | BF185    | 25  | MJE520  | 65  | TIP120   | 90      | ZN2218A  | 45    | 2N3906   | 15  |
| BC108B  | 12  | BC213L   | 10 | BF194    | 12  | MJE521  | 95  | TIP121   | 90      | ZN2219A  | 25    | 2N4037   | 45  |
| BC108C  | 12  | BC214    | 10 | BF195    | 12  | MJE3055 | 70  | TIP122   | 90      | ZN2221A  | 25    | 2N4058   | 10  |
| * BC109 | 9   | * BC214L | 8  | BF196    | 12  | MPF102  | 40  | TIP141   | 120     | ZN2222A  | 20    | 2N4060   | 10  |
| BC109C  | 12  | BC237    | 8  | BF197    | 12  | MPF104  | 40  | TIP142   | 120     | ZN2368   | 25    | 2N4061   | 10  |
| BC114   | 12  | BC238    | 14 | BF198    | 10  | MPY408  | 22  | TIP147   | 120     | ZN2369   | 16    | 2N4062   | 10  |
| BC115   | 22  | BC308    | 15 | BF199    | 18  | MPSA06  | 25  | TIP295   | 60      | ZN2484   | 25    | 2N4547   | 36  |
| BC117   | 22  | BC327    | 14 | BF200    | 30  | MPSA12  | 10  | TIP305   | 55      | ZN2646   | 45    | 2N4548   | 36  |
| BC119   | 35  | BC328    | 14 | * BF244Z | 22  | MPSA55  | 30  | TIS43    | 40      | ZN2904   | 20    | 2N4549   | 30  |
| BC137   | 40  | BC337    | 14 | BF245    | 30  | MPSA56  | 30  | TIS44    | 45      | ZN2904A  | 20    | 2N4585   | 36  |
| BC139   | 40  | BC338    | 14 | BF256B   | 35  | TIS45   | 45  | 2N2905   | 22      | 2N2977   | 45    | 2N4587   | 45  |
| BC140   | 30  | BC477    | 30 | BF257    | 32  | MPSU55  | 35  | TIS92    | 30      | ZN2905A  | 22    | 2N4588   | 45  |
| BC141   | 30  | BC478    | 30 | BF258    | 25  | MPSU55  | 60  | TIS91    | 30      | ZN2906   | 25    | 40360    | 40  |
| BC142   | 25  | BC479    | 30 | BF259    | 35  | MPSU56  | 60  | * VN10KM | 2N2906A | 25       | 40361 | 50       |     |
| BC143   | 25  | BC517    | 40 | BF337    | 40  | TIP29   | 35  | 45       | 2N2907  | 25       | 40362 | 50       |     |
| BC147   | 8   | * BC547  | 7  | BF340    | 23  | TIP29A  | 40  | VN46AF   | 75      | 2N2907A  | 25    | 40408    | 70  |
| BC148   | 8   | BC548    | 10 | BF341    | 25  | TIP29B  | 55  | VN66AF   | 85      | 2N2926   | 7     | 40594    | 100 |
| BC149   | 9   | BC549    | 10 | BF342    | 25  | TIP29C  | 60  | VN67AF   | 85      | 2N3053   | 25    |          |     |

### LINEAR

|             |     |          |     |         |     |          |     |           |     |
|-------------|-----|----------|-----|---------|-----|----------|-----|-----------|-----|
| CA3189E     | 290 | * LM380  | 65  | LM3900  | 50  | NE566    | 150 | TL071     | 45  |
| * 709       | 25  | ICL7106  | 790 | * LM381 | 120 | LM3909   | 70  | * NE567   | 100 |
| * 741       | 12  | ICL8038  | 320 | LM382   | 120 | LM3911   | 120 | NE571     | 425 |
| 748         | 35  | ICM7555  | 80  | * LM386 | 65  | * LM3914 | 200 | RC4136    | 65  |
| AY-3-1270   | 840 | * LF351  | 45  | LM387   | 120 | * LM3915 | 220 | SAT6018   | 150 |
| * AY-3-8912 | 700 | LF356    | 90  | LM393   | 100 | LM3600   | 120 | * SN76477 | 250 |
| LM100       | 625 | LM130    | 395 | * LM709 | 25  | MC3302   | 150 | TBA801    | 95  |
| CA3046      | 60  | * LM301A | 25  | LM710   | 50  | MC3340   | 135 | TBA820    | 80  |
| CA3080      | 65  | LM311    | 70  | LM725   | 350 | NE515    | 270 | TBA950    | 290 |
| CA3089      | 215 | LM318    | 120 | LM733   | 75  | NE529    | 225 | TCA940    | 170 |
| CA3090A     | 375 | * LM324  | 40  | * LM741 | 14  | NE531    | 150 | TDA1008   | 330 |
| CA310E      | 90  | LM339    | 50  | LM747   | 75  | NE544    | 185 | TDA1008   | 330 |
| CA3140E     | 45  | LM348    | 65  | LM748   | 35  | * NE555  | 16  | TDA1010   | 225 |
| CA3160E     | 100 | LM358    | 50  | LM1458  | 40  | * NE556  | 45  | TDA1022   | 560 |
| CA3161E     | 140 | LM377    | 150 | LM2917  | 200 | NE565    | 120 | TAD1024   | 125 |

### CMOS

|        |    |        |     |        |     |        |     |        |     |        |     |
|--------|----|--------|-----|--------|-----|--------|-----|--------|-----|--------|-----|
| * 4001 | 43 | 4036   | 285 | 4055   | 115 | 4082   | 20  | 4502   | 70  | 4529   | 150 |
| 4002   | 14 | 4019   | 35  | 4040   | 55  | 4060   | 85  | 4065   | 65  | 4503   | 50  |
| * 4001 | 12 | * 4020 | 55  | 4041   | 75  | 4063   | 90  | 4089   | 140 | 4508   | 200 |
| 4006   | 65 | 4022   | 65  | 4042   | 55  | 4066   | 35  | * 4093 | 33  | 4510   | 65  |
| 4007   | 17 | 4023   | 18  | 4043   | 60  | 4067   | 395 | 4094   | 14  | 4511   | 60  |
| 4008   | 58 | 4034   | 40  | 4044   | 65  | * 4068 | 15  | 4095   | 90  | 4512   | 70  |
| 4009   | 30 | 4025   | 18  | 4047   | 70  | 4069   | 18  | 4097   | 340 | 4514   | 180 |
| 4010   | 35 | * 4026 | 96  | 4048   | 55  | 4071   | 18  | 4098   | 85  | 4515   | 180 |
| * 4011 | 13 | 4027   | 30  | * 4049 | 28  | 4072   | 18  | 4099   | 95  | 4516   | 75  |
| * 4012 | 37 | 4028   | 55  | 4050   | 25  | 4073   | 20  | 4100   | 100 | 4520   | 70  |
| * 4013 | 26 | 4029   | 75  | 4051   | 60  | 4075   | 20  | 4103   | 100 | 4521   | 200 |
| 4014   | 40 | 4030   | 35  | 4052   | 70  | 4076   | 60  | 4073   | 100 | 4526   | 80  |
| 4015   | 60 | 4031   | 170 | 4053   | 60  | 4077   | 25  | 4075   | 100 | 4527   | 90  |
| * 4016 | 26 | 4034   | 170 | 4054   | 110 | 4081   | 18  | 4093   | 120 | * 4528 | 75  |

### TTL

# Digital Thermometer

Owen Bishop

**A neat, compact project for indoor or outdoor use.**

THIS PROJECT was designed as a battery-powered, digital thermometer giving a readout on a seven-segment LED display. Its neat appearance makes it equally at home in the study or the living-room, or it can be used for remote temperature sensing.

The sensor is an IC which generates a current proportional to the temperature of its surroundings. One useful feature of this IC is that the current is completely unaffected by the length of the wire connecting the sensor to the rest of the circuit. Changes in resistance of the connecting wire have no effect either. The project, therefore, is suitable for remote sensing of temperature. The sensor could easily be situated in the greenhouse, for example, allowing you to monitor the temperature from indoors and warning of the risk of overheating in summer, or of frost in winter.

Although weather forecasts, nowadays, are given in degrees Celsius (some people wrongly persist in calling it Centigrade — why not pay our respects to Celsius, the man who invented this scale?), many people still think in terms of degrees Fahrenheit, so this circuit can be built to measure temperature in either scale.

## The Circuit

IC1 is a constant-current generator, the current being determined by the value of R1 and by the ambient temperature. The current flowing to R2 is given by:

$$I = 227 \times T/R,$$

where I is in microamperes, R is the value of R1 in ohms, and T is the absolute temperature, in Kelvin. Absolute Zero, on the Kelvin scale is approximately equal to -273°C or -459°F. A room temperature of 20°C is, therefore,  $273 + 20 = 293$  K. Thus at room temperature,  $I = 227 \times 293/220 = 302$   $\mu$ A. As this current flows through R2 it generates a potential of 3V02 across it. Note that if IC1 is to be used as a remote sensor, R1 must be mounted as close to it as possible; the leads to V+ and V- may be as long as necessary. Current flowing

from V- is constant and *all* of it flows to R2. Hence the length of the lead and its resistance do not affect the voltage across R2.

IC2 is a CMOS phase-locked-loop IC, which is used because of the VCO it contains (among other functions). With a fixed capacitance across pins 6 and 7, the rate of oscillation at any given voltage is determined by the resistance at pin 11. The resistor at pin 12 determines the minimum (or offset) frequency. With no resistor at pin 12, the rate is 0 Hz at 0 V. We choose minimum (offset) and maximum frequencies which correspond to the correct temperatures when the 'hundreds' digit is omitted. The scale maximum is, in practice, only 799 (99°F) for Fahrenheit.

Timing for the system is under the control of IC3, a CMOS timer wired as an astable, operating at 0.5Hz. The dual monostable (IC4) is wired to generate a short pulse at the beginning and end of each pulse from IC3. The count is 'enabled' as the output of IC3 goes high and the counter is reset to zero, by the pulse from IC4a. When the high pulse from IC3 ends, the counter is disabled; simultaneously, the low-going pulse from IC4b to the drivers (ICs 6 and 7) stores the resulting count, which is then decoded and displayed.


IC5 contains two decade counters; the units counter (IC5b) is enabled whenever input 'EN' (pin 2) is taken

low. Its '8' output (pin 6) goes low whenever the count changes from 9 back to 0; this low-going edge triggers the other counter (IC5a) which is incremented and counts 'tens'. Enabling or disabling IC5 automatically has the same effect on IC5a. Note that the input to IC5b is the clock input (pin 1), which triggers a count on a positive-going edge; the input to IC5a is at its 'enable' input (pin 10) which is negative-triggered; its clock input (pin 9) is wired to 0 V to hold it permanently low.

To ensure that all the digits are equally bright, there should be a resistor in each lead between ICs 6 and 7 and the displays. We have economised by using only a single resistor (R9) in the common cathode line. When the displayed value alters, there is a small change in brightness because the number of illuminated segments has changed. In practice this is not worth bothering about, since the display does not change often.


The regulator circuit is fairly conventional. A constant voltage of 2V7 is maintained at the junction of Q2 and D1; with the forward voltage drop across the base-emitter junction of Q2, the voltage at R12/R13 must be  $2.7 + 0.6 = 3V3$ . Since R12/R13 is a potential divider across the output, the circuit is only stable when the output voltage is 4V5, giving 3V3 at the base of Q2. As the supply voltage or load varies, the negative feedback through



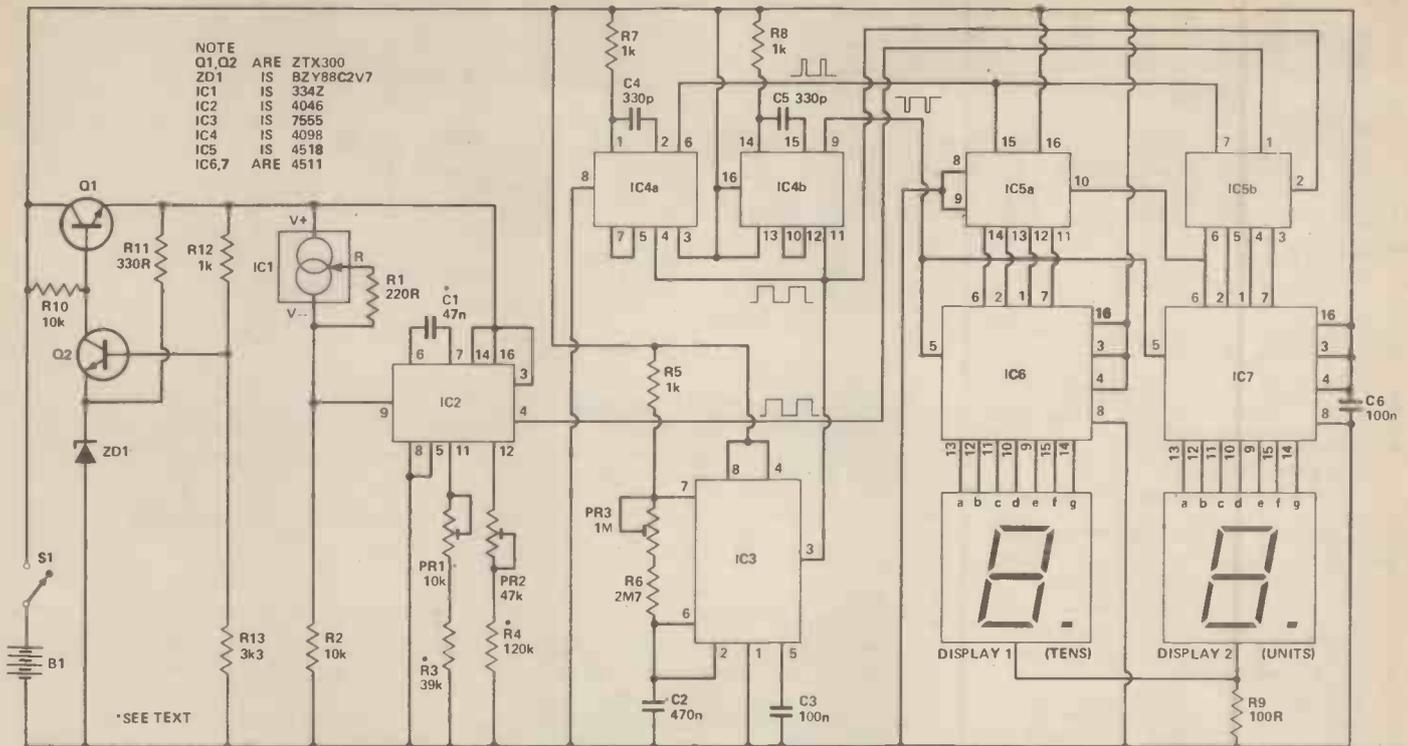

▲ Figure 1. The complete Digital Thermometer circuit. Although it uses quite a few chips, all except the displays are mounted on one board. The sensor IC may be taken off-board for remote sensing of temperature.

Figure 2. Cut-away view of internal layout, showing the PCB mounted upside down.

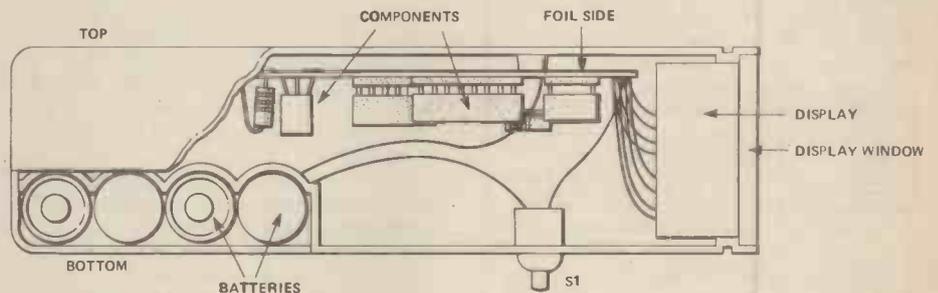


Q2 (via R12, 13) will either turn Q1 on harder or turn it off slightly, to maintain an output of 4V5. This circuit gives good regulation over the voltage range to be expected from batteries, as they gradually discharge.
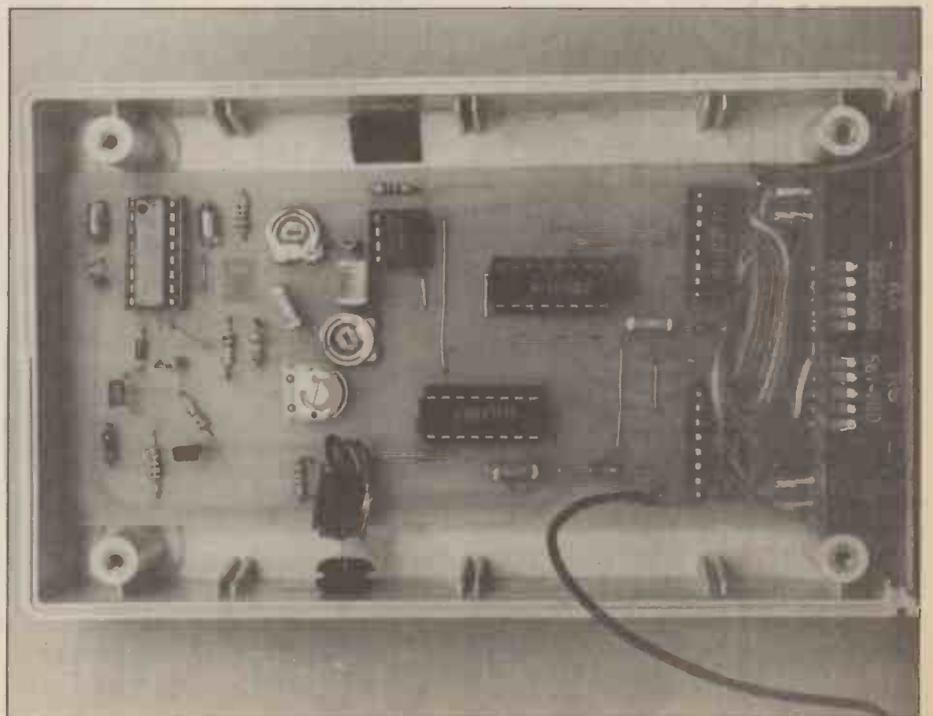
### Construction

The thermometer circuit is built on a single PCB mounted *upside down* in the top section of the case. The case we used has a built-in battery compartment, holding the four HP7 cells which provide the power supply of 6 V. The circuit will work directly from the batteries, but it is affected by falling voltage, as the cells age, as mentioned. For this reason the simple voltage regulator is included, though it is not essential if you are willing to renew the cells fairly frequently. The regulator is mounted at the rear of the PCB, away from the sensor. It supplies only the sensor and oscillator, the remainder of the circuit being supplied directly from the battery.

The switch is a push-on/push-off type, mounted on the bottom of the case, near the front; it also acts as a tilting leg, giving a better view of the display. To switch the thermometer on or off, simply place your hand on top of the case and press down!



## Parts List

### RESISTORS

(All 1/4 W, 5%)

|     |      |
|-----|------|
| R1  | 220R |
| R2  | 10k  |
| R3* | 3k9  |
| R4* | 120k |
| R5  | 1k   |
| R6  | 2M7  |
| R7  | 1k   |
| R8  | 1k   |
| R9  | 100R |
| R10 | 10k  |
| R11 | 330R |
| R12 | 1k   |
| R13 | 3k3  |

\* See Text

### POTENTIOMETERS

(All sub-miniature horizontal presets)

|     |     |
|-----|-----|
| PR1 | 10k |
| PR2 | 47k |
| PR3 | 1M  |

### CAPACITORS

(All polyester, except where indicated)

|     |                    |
|-----|--------------------|
| C1* | 47n polycarbonate  |
| C2  | 470n polycarbonate |
| C3  | 100n polycarbonate |
| C4  | 330p polystyrene   |
| C5  | 330p polystyrene   |
| C6  | 100n polycarbonate |

### SEMICONDUCTORS

|       |  |
|-------|--|
| IC1   | 334Z<br>constant current generator                 |
| IC2   | 4046B phase-locked loop                            |
| IC3   | 7555 CMOS timer                                    |
| IC4   | 4098B or 4528B<br>dual monostable                  |
| IC5   | 4518B dual BCD counter                             |
| IC6,7 | 4511B<br>BCD-to-7-segment latch/<br>decoder/driver |
| Q1, 2 | ZXT300 NPN transistor                              |
| ZD1   | Zener diode, 2V7                                   |

### MISCELLANEOUS

|              |  |
|--------------|--|
| DISP1, DISP2 | 7-segment LED<br>display (2 off)           |
| SW1          | Push-to-make/push-to-break<br>switch, SPST |

Battery instrument case (Vero type 2) 2.5 mm matrix stripboard, 127 mm x 63 mm main board, 63 mm x 25 mm for regulator, 55 mm x 28 mm (20 strips x 11 holes) for displays; 1.0 mm terminal pins, (7 off); Small angle bracket, 4BA bolt and nut set (2 off); Self-tapping screws for 2 mm holes (4 off).

BUYLINES . . . . . page 68


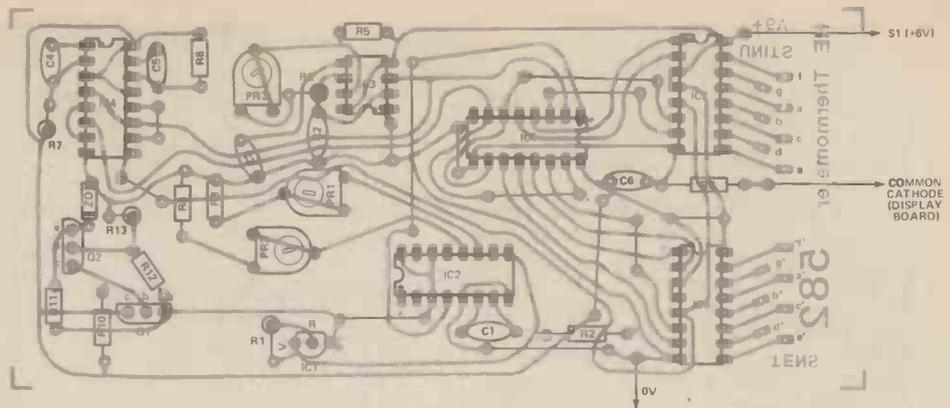


Figure 3. The component layout. Be careful to make the correct connections between the display board (right) and the main board.

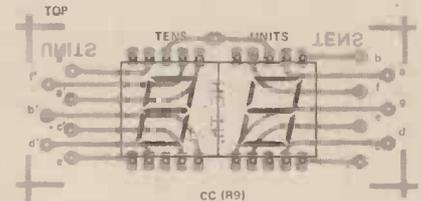

It is more convenient if you leave mounting the board and wiring the switch until the thermometer board is complete and working. We strongly advise that sockets are used for the ICs, as this allows them to be removed, if necessary, when attempting to locate faults. Soldercon pins were used to mount IC1 and proved perfectly satisfactory. Since the circuit uses CMOS ICs, take the usual precautions to avoid static charges and wire up all the connections to each IC before inserting it.

Begin by building the regulator board; this is very simple so there should be no problems. When the regulator is connected to the 6 V supply, its output voltage should be about 4V5. Continue with IC1 and its resistors (R1, R2); use a heat sink when soldering this IC to the board. Test this section by switching on the power and measuring the voltage across R2. This should be about 3 V, whether you are using the 4V5 supply or the direct 6 V supply. Hold the IC between your finger-tips for a minute or two (or hold a warm soldering iron near it, but don't actually touch it); the voltage should rise. When the heat source is removed, the voltage should fall back to its original level.

Next, wire up IC3 (the CMOS timer), together with R5, R6, RV3, C2 and C3. To test this section you will need to take out IC1. The output of IC3 (pin 3) should rise and fall at approximately 0.5 Hz (2 seconds between successive pulses). Run it for one minute, counting the pulses. Use a 'scope', if you have one; if not, connect a high impedance earphone or audio probe between pin 3 and 0 V; you should hear a 'click' each time the edge of a pulse rises or falls. Adjust RV5 for 30 pulses per minute (60 clicks per minute); the pulses should have a 50% mark-space ratio ie, 1 Sec high, 1 Sec low.

Now you are ready to fit IC2, the voltage-controlled oscillator (VCO). At this stage, you need to decide whether

the thermometer is to read degrees Fahrenheit or Celsius, and to choose the appropriate values for C1, R3 and R4. Those given in the Parts List are for degrees Fahrenheit; for Celsius, change these to 100n, 10k and 56k, respectively.

Next, mount PR1 and PR2 and, with IC1 still out of the circuit and IC3 removed, look at pin 4 of IC2. A 'scope is preferable but, if you do not have one, the frequencies can be adjusted by matching them against audio tones from an accurately calibrated audio oscillator or, if you have a musical ear, from a piano or organ, using a high impedance earphone or probe, as before.




The 'offset' frequency of IC2, pin 4 should be 241 Hz (about B below Middle C) for the Fahrenheit scale or 127 Hz (C below Middle C) for reading Celsius; adjust PR2 for the correct frequency (PR1 is not adjusted at this stage). If you find it impossible to obtain the frequency, replace R4 with a higher or lower value, to reduce or increase the frequency accordingly.

Before going on to wire up the counting and display circuits we must put together the pulse generators of IC4. The output of the leading-edge pulse generator (pin 6) is normally low (0 V), with a very brief (250 nS) high-going pulse as the output from IC3 goes low. If you have doubts that IC4 is working, connect a 100nF capacitor in parallel with C4 or C5, to stretch the pulses.

Now, replace all the ICs in their sockets and mount ICs 5, 6 and 7. The two LED digits are mounted on a small, separate PCB, plugged in to Soldercon pins. Run wires from the display board to the pins beside ICs 6 and 7, being careful to follow the wiring diagram (a goes to a, b' goes to b' and so on). Remember that the main board will be mounted upside down in the top of the case; the displays must be mounted with their upper edges nearest the main board. Securing the display board is
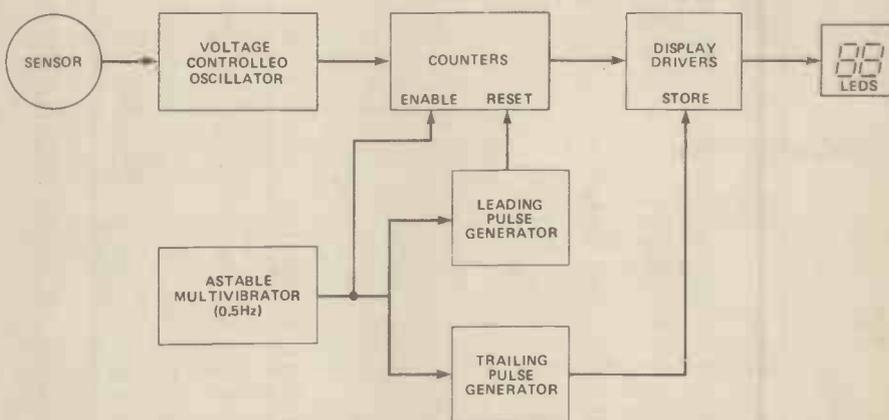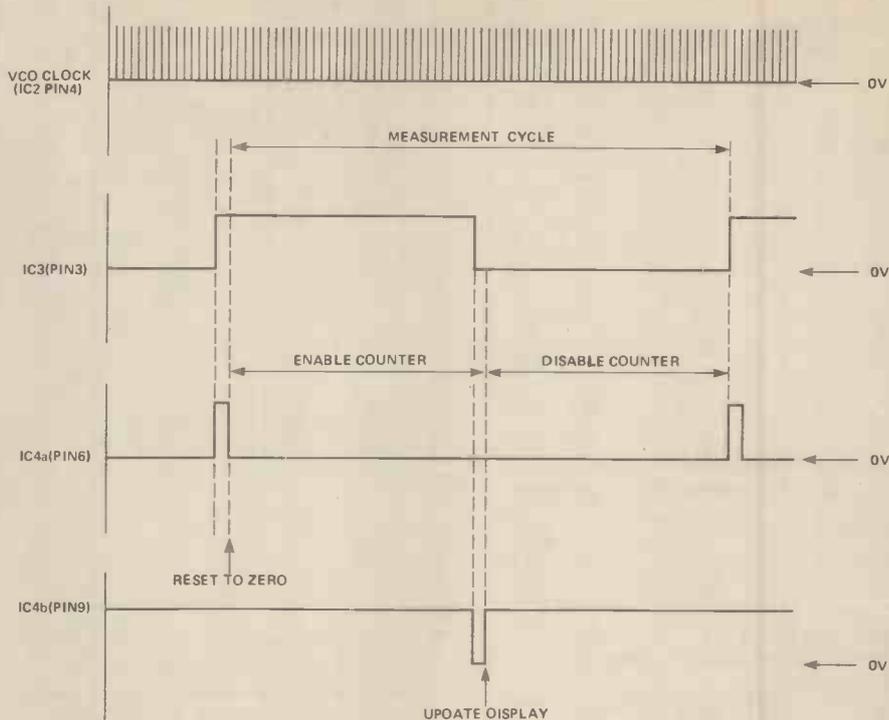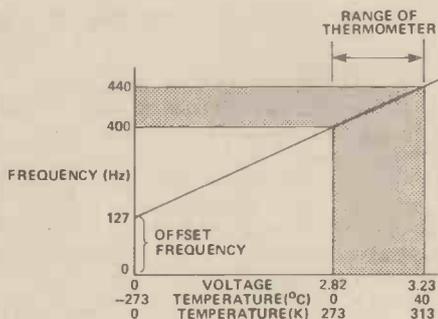
## How It Works

The sensor produces a voltage which is proportional to its temperature and this is fed to a voltage controlled oscillator; the frequency of the VCO is therefore, proportional to temperature. When switched on, the counter is reset to zero, then allowed to count for a fixed length of time (approximately 1 second). At 0°C it counts to 400, and at 40°C it counts to 440 — or, if the device has been built to operate on the Fahrenheit scale, it counts to 732 at 32°F and to 804 at 104°F. The counter has only two stages, for units and tens; hundreds are ignored, so the counter actually shows '00' at 0°C and '40' at 40°C (or '32' at 32°F and '04' at 104°F). The astable multivibrator is a slow oscillator which controls the timing of events in the system. It turns the counter on (enables it) for one second in every two. It is also connected to two pulse generators. One gives a rising pulse (high) to reset the counter, the other gives a falling pulse (low) to store the result, as counting finishes.



easy if you use the bolts on the LED bezel; if your budget can't afford these, you will have to mount the display board to the main board using small L-shaped angle brackets.

Assuming that all connections have been correctly made, and the ICs plugged in the display should show '00' when first switched on. About one second later it should change to a number between '00' and '99'. It will then remain at that number, or change by one or two as the temperature changes. To begin with, you will probably obtain a nonsensical reading, but don't panic — here are some things which may be wrong:

- 1) Both displays blank — check the power supply and the display connections.
- 2) Some segments never light — faulty wiring between the display and IC6 or IC7.
- 3) Peculiar symbols — wires between IC6 and 7 and the display are crossed or shorted; you may have wired in the

decimal point instead of one of the segments.

- 4) Certain figures never displayed but a blank occasionally appears on one (possibly both) displays — wires crossed between IC5 and ICs 6-7.

When the display is working properly, all that remains is to set the device to indicate the correct temperature. At average room temperature, the frequency from IC2 should be about 768 Hz (G in the octave above Middle C) for the Fahrenheit scale or 420 Hz (Ab above Middle C) for Celsius. Adjust PR1 to obtain this, but on no account re-adjust PR2. It is possible, though unlikely, that you may need to replace R3 at this stage, if the correct frequency cannot be obtained. The display should now be within range of the correct temperature, but could be as much as 30 or 40 degrees out, in either direction. Now adjust RV1 to bring the display reading to its correct value, using an ordinary room thermometer as reference. Both

thermometers will take several minutes to acquire the temperature of their surroundings — do not attempt this calibration until both have been at steady temperature for at least 10 minutes.

Before mounting the boards, drill the case to take the switch. Also drill plenty of ventilation holes to allow air to circulate to the sensor or, for greater accuracy and rapid response, drill a hole large enough to accept the package of the sensor IC and attach some leads so that it protrudes slightly out of the hole, into the air outside.

Secure the main board in the top half of the case, using self-tapping screws or 'Sticky Fixers'. Cut a rectangular opening in the front panel, level with the displays and slip the panel into its slots. If you're using the display bezel, drill two holes to take the mounting bolts. Before closing the case, read the display to check that PR1 and PR2 have not accidentally been altered. The HE Digital Thermometer is then complete!

**HE**



# SALE ELECTRONIC GAMES



**NOW £40 OFF**

## ATARI T.V. GAME

THE GAME WITH 50 CARTRIDGES  
R.R.P. £129.95 (inc. VAT)

**OUR PRICE**  
**£78.22 + VAT**

(= £89.95 inc. VAT)

The Atari is supplied with a free mains adaptor, a pair of paddles, a pair of joysticks and a combat cartridge and is the most popular television game on the market and has a range of over 40 different cartridges. In addition to the standard Atari range we also now stock the new Activision cartridges which are currently on special offer reduced from £18.95 to **£16.95 inc. VAT**

### ATARI CARTRIDGES

20% OFF R.R.P.

Atari Soccer £29.95  
**NOW £23.95**  
Activision Dragster £18.95  
**NOW £14.95**  
Activision Boxing £18.95  
**NOW £14.95**

**ATARI OWNERS CLUB** — Why not join our **FREE** Silica Atari Owners Club and receive our bi-monthly newsletter with special offers and details of the latest new cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.

## MATTEL INTELLIVISION

THE ULTIMATE T.V. GAME  
R.R.P. £229.95 (inc. VAT)

**OUR PRICE**  
**£156.48 + VAT**

(£179.95 inc. VAT)

6 NEW CARTRIDGES JUST RELEASED:  
**ASTROSMASH \* SNAFU \* BOWLING**  
**SPACE ARMADA \* BOXING**  
**TRIPLE ACTION**

All 19 current cartridges + the six new ones above now retail at £19.95 — Silica special offer price **£17.95 inc VAT**

**NOW £50 OFF**



The Mattel Intellivision is the most advanced T.V. game in the world with a range of over 25 different cartridges all at our special offer price of £17.95. This game uses a 16-bit microprocessor giving 16 colours and three-part harmony sound. The picture quality is incredible with 3D effects and realistic animation. An add on keyboard will be available in the Spring 1982 to convert the Mattel into a full home computer with 16K RAM which will be fully expandable and programmable in Microsoft Basic. Other accessories will be added later in the year. The normal price of the Intellivision + free soccer cartridge is £229.95 but our special offer price is £179.95 inc. VAT saving you £50.00.

**MATTEL OWNERS CLUB** — Why not join our Mattel Owners Club and receive our regular newsletters containing details of all the latest cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.


**FREE 16 PAGE CARTRIDGE CATALOGUE** — If you are interested in owning a Mattel, we now have available a 16 page catalogue describing the latest six cartridges to be released, as well as a new Mattel colour leaflet with brief descriptions of all 25 cartridges. Telephone us for further details.

## T.V. GAME CARTRIDGES

We specialise in the whole range of T.V. games and sell cartridges for the following games: **ATARI \* MATTEL \* ACETRONIC \* PHILIPS \* DATABASE \* ROWTRON \* INTERTON \* TELENG**. Let us know if you own any of these games and we will let you have details of the range of cartridges available.

Attention **INTERTON & ACETRONIC** owners we have over 75 assorted used cartridges in stock all with 1 year guarantee — **SPECIAL OFFER £8.95 each**

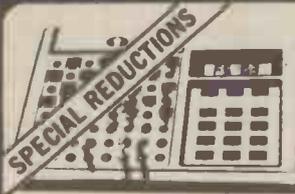We also have a number of secondhand games and cartridges.



## ELECTRONIC CHESS

Liquid crystal battery chess computer with 100-200 hrs battery life and two levels of play. Comes with separate chess board and pieces.

**NOW £5 OFF**  
R.R.P. £24.95  
**SALE PRICE**  
**£19.95**

## GRADUATE CHESS

A de luxe version of the electronic chess set with integral chess board. The ideal portable chess set — see illustration.

**NOW**  
**£29.95**  
INC VAT

## FIDELITY MINI-SENSORY CHESS COMPUTER

The very first chess computer of its price to offer a portable computer with integral sensory board. Battery (6-8 hrs) or mains operated. This is a modular game and additional plug-in modules are patented for 1982 for advanced chess, popular openings, greatest master games, draughts and reversi.

**MINI-SENSORY COMPUTER WITH STANDARD CHESS MODULE** WAS £54.50 **NOW £49.95** INC VAT

Silica Shop are one of the country's leading specialists in Chess Computers and now stock an range of more than 20 Chess Computers, including Challenger 7/10/Voice, Sensory 8 and Sensory Voice, Diplomat, System 3, Morphy, Great Game Machine, Voice Champion, and the new Scizys Mark V.

**LESS THAN 1/2 PRICE**

**COLOUR CARTRIDGE T.V. GAME**  
Semi Programmable T.V. game  
8 cartridges  
+ mains transformer  
**NOW £63.50 OFF**  
R.R.P. £73  
**SALE PRICE £29.50** (inc. VAT)

**SCOOP PURCHASE NOW 1/2 PRICE**

**BACKGAMMON COMPUTER**  
Silica stock a wide range of Backgammon computers from £29.95 upwards. Special offers now available on Gammomaster.

**NOW £48.95** inc VAT

**CALL JOTTER 3 — THE AFFORDABLE ANSWER**  
The Post Office certified telephone answering machine

"Sorry darling, I will be late home — Love John"  
The Call Jotter 1 brings the affordable answer at the amazing price of £69 (or £99 for the Call Jotter 2 with built-in remote recall facilities). These amazing telephone answering machines are Post Office certified and guaranteed for one year. They make a thoughtful gift for home or business use.

Call Jotter 3 illustrated **NOW £69.00** inc VAT  
WINTAPE £139

**NOW £75 OFF**

**RADOFIN TELETEXT**  
Plug the adaptor into the serial socket of your colour TV and receive the CEEFAX and ORACLE television information services.

**THIS NEW MODEL INCORPORATES**  
"Double height character facility" "True PAL Colour" "Meets latest BBC & IBA broadcast specifications" "Push button channel change" "Unnecessary to remove the unit to watch normal TV programmes" "Gold plated circuit board for reliability"

**ADD-ON ADAPTOR**  
WAS £199 inc VAT  
**SALE PRICE £124** inc VAT


**FOR FREE BROCHURES — TEL: 01-301 1111**



For free illustrated brochure and reviews on our range of electronic games, please telephone 01-301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/ARC/VCARD number, and leave the rest to us. Post and packing Free of Charge. Express 48 hour delivery service available.

- **CALLERS WELCOME** Demonstrations daily at our Sidcup shop open from 9am-6pm Monday-Saturday (Early Closing Thursday 1pm. Late Opening Friday 8pm).
- **2 YEAR GUARANTEE** All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee
- **MONEY BACK UNDERTAKING** If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.
- **AFTER SALES SERVICE** Available on all machines out of guarantee
- **COMPETITIVE PRICES** We are never knowingly under-sold
- **HELPFUL ADVICE** Available on the suitability of each machine
- **CREDIT FACILITIES** Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
- **PART EXCHANGE SCHEME** Available on second hand machines
- **CREDIT CARDS WELCOME** Access, Barclaycard, Diners Club, American Express

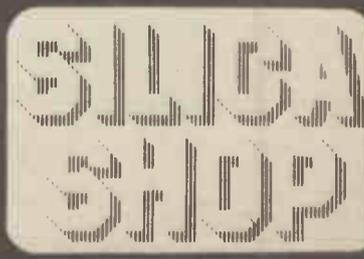**SILICA SHOP LIMITED HE0582**  
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX  
Telephone: 01-301 1111 or 01-309 1111



# POINTS OF VIEW

## Clubbing Together

Dear Sir,  
I became interested in electronics a few years ago, just before your first issue came out, so I was pleased to see it appear on the shelves. Since then I have come a long way, with your help. I have every copy from Issue one on my bookshelf, although I must admit that some of the earlier ones are becoming a bit tatty, now. I also attended night school for two years and, between night school and your magazine, I have been able to build a lot of my own test equipment.

I sometimes pick out a couple of old issues and read through them. In September 1980 you printed a letter from a Mr. George Edwards, who asked about clubs. You replied that you would mention any clubs that wrote to you but, as you have not printed any (apart from the one mentioned in the reply), I take it that either no other clubs exist or that they are very secretive about their existence.

There must be thousands of people who're interested in electronics and who are pursuing the subject on their own, like myself. I would be very interested in contacting anyone in my area so that we can share ideas and help one another. Perhaps people interested in forming a club could write to you. Then others in the area, whether they live in London or Edinburgh, would be able to contact them. Electronics is a fast-growing industry, but the hobbyist seems to be left out, to fend for himself.

I think the potential for this is endless — who knows what might be developed through the sharing of equipment and ideas? Perhaps you could spare a page of HE to be used for Club News and similar ideas?

Just one other thing — what happened to 'Short Circuits'? I used to enjoy experimenting with them.

R. Mitchell,  
Portslade,  
Sussex.

Mr. Mitchell is apparently correct in his assumption that no other electronics clubs exist — certainly, none have contacted us. The club mentioned in the September 1980 issue is still going strong, however. They are the British Amateur Electronics Club and interested readers should contact the Chairman, Mr. Cyril Bogod, at the BAEC, 'Dickens', 26 Forrest Road, Penarth, South Glamorgan. Tel: 0222 707813. The BAEC is a national organisation and they should be able to put you in touch with other electronics hobbyists in your area.

We will shortly be re-introducing a new series of circuits for experimenters under the title "Breadboards". Look out for them in the June issue!

## Reactions Tested

Dear Sir,  
I have just completed the Reaction Tester (September '81 issue) and it doesn't work. The bottom LED lights up when switched on but pressing the 'go' button has no effect whatsoever. I have checked everything I can think of, including the PCB and the two ICs.

Maplin recommended a C106 thyristor instead of the C103 — could they have different gate voltages and therefore be the cause? The 4017 I bought has CD4017 printed on it — could this be the fault?

The only other thing I can think of is that there is a mistake in the instructions. If there is, could you please advise me?

A. Bricknell,  
Leigh-on-Sea,  
Essex.

PS Keep up the good mag.

The 'CD' is simply the maker's code name for the IC — the type or 'generic' as it is sometimes called, is 4017; that's what counts. Since it appears that either the 555 IC is not oscillating, or the 4017 is not counting, indicated by the fact that it is 'stuck' in reset condition (zero count), it's unlikely that the thyristor is at fault (the gate voltages are the same, anyway).

The circuit has no errors, other than that the IC types are interchanged (which should be immediately obvious), and the PCB layout seems correct. Having eliminated all those possibilities, we can only suggest that you check, very carefully, all the circuitry associated with the 555 astable and the input to pin 14 of the 4017.

## Mast Head Amplification

Dear Sir,  
I purchased your magazine this month for the first time and I find it excellent, but for one thing; no information on where to buy the kit for the TV Mast Head Amplifier (February '82 issue). Who and where are RS Components, please?

Yours,  
(signature indecipherable)  
South Wigston

We're not even sure about the address, but hopefully the writer will recognise his own letter! Our misplaced comments about RS Components continue to haunt us — RS Components will accept orders only from "Full time industrial, educational and trade users.", however the mail order firm Crewe Allen, of 51 Scrutton Street, London EC2A 4PJ (Tel: 01 739 4846) can supply components from the RS catalogue.

The TV Mast Head Amplifier is not available as a kit, as such, but Magenta

Electronics can supply all of the parts, including the double-sided PCB. Would Oliver Davis of Co. Donegal, Ireland and G. Inchbald in Manchester please copy!

## Delay Time

Dear Sir,  
I have been trying, without success, to obtain a circuit diagram for a solid state echo unit using Bucket Brigade Delay technology.

Can you suggest where I might obtain such a circuit?

D. Vanderwolf  
Torpoint,  
Cornwall.

This is one letter we are happy to answer without delay. Look no further, Mr. Vanderwolf! The circuit you seek is on page 41 — the HE Echo-Reverb project.

## Overseas Mail

Dear Editor,  
I have read with great interest your magazine, Hobby Electronics.

I am particularly interested in books about trouble-shooting in electronics — these are particularly lacking on the HE Bookshelf. I will be very glad if you could suggest any suitable books. I am very interested in regulators, audio, radio and test equipment.

R. Kimura,  
Swaziland,  
Southern Africa.

Trouble-shooting (fault-finding) is a very interesting topic — one that we will be giving detailed attention to, in the near future. However, Mr. Kimura and other interested readers might also like to read Ian Sinclair's book, "Electronics Fault Diagnosis", published by Keith Dickson (Publishing) Ltd., 17, Hendon Lane, London N3 1RT.

## Satisfaction Guaranteed.

Dear Sir,  
I own a stereo radio/cassette player which is still under guarantee and it has a very annoying defect; when recording from FM, especially from stereo FM, the motor causes definite distortion to the recording.

I have isolated the motor as the source of the interference by playing a tape while in the FM radio mode. While the motor was running the interference could be heard distinctly and as soon as it was stopped, the interference stopped. Obviously this should not happen, as it means I cannot get satisfactory recordings from the radio and this defeats my purpose in buying the machine. I wondered if there is anything I could do to remedy the situation or whether I should return it

under guarantee. I would be very grateful if you could give me your opinion.

E. Weeks,  
Godalming,  
Surrey.

We do not, normally, advise on anything to do with commercial equipment but this case is so clear that we decided to make an exception — also, it is an excellent example of fault-finding technique! Our opinion is: do not even think about fiddling with it — return it at once.

## Specifically Speaking

Dear Sir,  
Recently I have been thinking of building your power amplifier from the March 1980 issue of *Hobby Electronics*, the System 5080A. The amplifier seems excellent but you did not supply the specifications — power output, distortion, frequency response, etc. I should be grateful to receive a copy of the specifications and, in future, I suggest that you supply them with the projects, as I am sure many people would be interested.

Yours,  
P. Upton,  
Salisbury,  
Zimbabwe.

To the best of our knowledge, a set of specification figures for the 5080A was never produced — or if they were, they are now lost! However, the following information can be extracted from the text: the power output is 25 W per channel; distortion is "so low as to be inaudible" and the frequency response is "well above and below the human hearing range". As you say, it seems pretty good. Nevertheless, your suggestion is a good one, and in future we'll certainly publish the full specification figures for any quality audio project.

## Famous Names

Dear Sir,  
The article *Famous Names* (HE, December 1981) paying tribute to the visionary Campbell-Swinton, contained a serious error. We read: "The unanimous rejection of Baird's 30-line system in favour of Schoenberg's 405-line system, in 1936, proved how right Campbell-Swinton was." In fact, no such choice was ever made.

The Baird 30-line system was started as early as 1929 and, by 1930, had become fairly refined. In 1931 the BBC took over all responsibility for the daily broadcasts as a light entertainment programme on the medium waveband, receivable nationwide. This left Baird with time to develop his 120 and 180 line systems, which he broadcast on the seven meter band. Later, he developed a 240-line system.

So the contest of the two rival systems in 1936 (transmitted on alternate weeks) was between the Schoenberg 405-line system and the

Baird 240-line system. The BBC (30-line) transmissions had actually ceased the previous year. The number 240 has been chosen, not by Baird directly, but by the Postmaster General's Television Committee, under the chairmanship of Lord Selsdon, which commenced sitting in May 1934 and gave its decision on recommended standards in February 1935. The choice may well have been influenced by the choice of 240 lines by RCA, in the United States of America, which was trying to develop Zworykin's Ikonoscope camera, without much success.

J.L. Baird was not only the first person to demonstrate true television (ie, moving half-tone portraits of live subjects) anywhere in the world, but one of the quite small number of pioneers in the field of high-definition television.

D.B. Pitt,  
Chairman,  
Narrow Bandwidth Television  
Association,  
Nottingham.

Ian Sinclair, the author of the Famous Names series, replies:

I regret that my efforts to compress a lot of information into a short phrase was the cause of a serious error of fact. As you rightly point out, the old experimental 30-line system had ceased by the time the dual broadcasts started. The Baird system had moved to higher definition and also to a more electronic system. Whether this would have been done but for the determined work of Schoenberg, Blumlien and McGee, on the completely electronic system, is a moot point.

At one time, in fact, the only way in which live TV could be transmitted on the Baird high-resolution system was by scanning the light source and, even by the time of the experimental broadcast, the Baird system could not cope well with live working. For that reason, he developed a fast film processor and it was usual to film each programme, then transmit from a flying-spot scanner a few minutes after the end of the show. It was extremely dangerous to stand in the corridor after a concert because the whole orchestra, brandishing instruments, would come running from the studio to the processing rooms to see themselves on film as the programme was being transmitted. Some of this film was preserved, but the short processing cycle made most of it useless after a few months.

Thank you for your comments. This series has aroused a lot of interest and some most interesting personal recollections.

We certainly agree and would be most interested to hear from any other readers with personal knowledge of the pioneers or recollections of the early days of electronics.

## Kit Fever

Dear Sir,  
Please could you tell me if you can do a kit of the Bicycle Speedometer (March

'81 issue)? I intend to build this as part of my course at Technical College.

A.E. Davis,  
Weston-Super-Mare,  
Avon.

M.A. Elatta, of Portsmouth and P. Longman, from Hull also wrote in with similar requests.

It seems to be a common misunderstanding, among some of our readers, that we supply kits for our projects; we don't. Kits are available for some projects, true, but not from us. If you have a copy of the issue in which the project appears, the Buylines make it clear whether or not there is a kit and, if so, who is supplying it and the cost.

Dear Sir,  
I have been buying *Hobby Electronics* since the first issue and I am generally very impressed.

I was, therefore, annoyed to find that two projects in the December 1981 issue (*Drum Synthesiser* and *Guitar Graphic Equaliser*) had no PCB foil patterns printed in the magazine. They do seem to be available, but only as part of a full kit.

I stopped buying another electronics magazine a few years ago because it was becoming a 'kit catalogue' and I hope *Hobby Electronics* is not on the same downhill path.

Yours sincerely,  
D. Squibb,  
Weymouth, Dorset.

The issue of the PCBs for these projects has been dealt with in previous issues, but to clear up this matter once and for all:

We try to present, in *Hobby Electronics*, projects that are useful, interesting or instructive. To achieve this, we accept material from a number of sources; many of our contributors are private individuals, but some are small companies, designing and making up circuits for industry and private sale, as well as for magazines such as ours. In the past, several of these contributors have wished to retain the copyright acknowledgement to the relevant company. We also attempt to persuade the kit supplier to make PCBs — and any other special components — available separately.

While we would prefer no restrictions whatsoever attached to our projects, the continual and difficult search for new, innovative ideas the kit supplier to make PCBs — and any other special components — available separately.


While we would prefer no restrictions whatsoever attached to our projects, the continual and difficult search for new, innovative projects demands that we accept such projects whenever they become available, from whatever source. This new arrangement, while less than ideal, at least permits the individual at home to make a project from the PCB upwards, as many of our readers prefer.

We hope that this long-winded explanation closes the subject!

**HE**

# WHAT'S ON NEXT?

## POPULAR COMPUTING

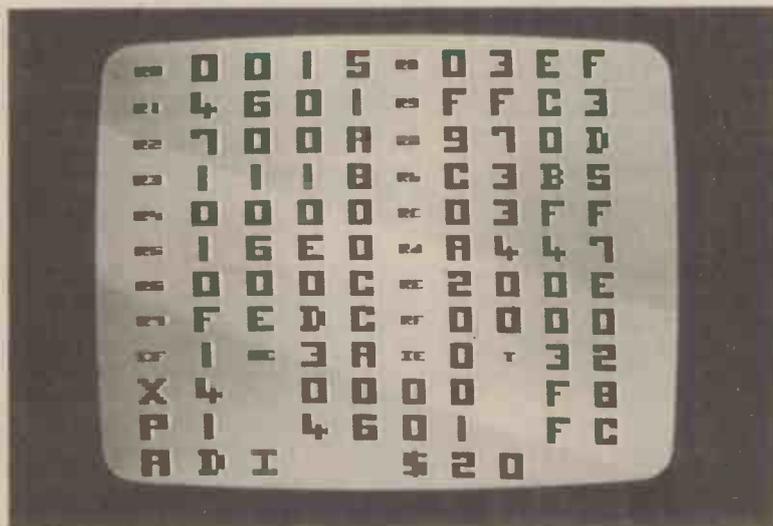

### The HE MicroTrainer.

## PROJECTS FOR EVERYONE

- \* Light-Operated Power Switch
- \* Auto-Wah Effect
- \* Greenhouse Monitor
- \* Telephone Timer
- \* Power Supply Design Project

Next month we begin a brand new computer hardware project, the HE MicroTrainer. Based on the 1802 microprocessor, it is simple to construct and easy to operate, the perfect machine to introduce the 'nuts and bolts' of microcomputer technology. The MicroTrainer has been designed specifically for Hobby Electronics' readers, and offers a number of distinct advantages over other development systems:

- \* Low cost.
- \* Modulated video output for direct input to a domestic television receiver, permitting more information to be displayed than is possible with LED readouts. The 12 line x 12 character display shows the complete set of 1802 registers or 32 bytes of program memory.
- \* Displays the current instruction, in mnemonic form.
- \* Unique single-step operation from RAM or ROM based software.
- \* Cassette tape storage of user programs.
- \* Twenty command functions, eg RUN, STEP, STOP, RESET, INTERRUPT, INSERT, DELETE, SAVE, LOAD,
- \* Twenty key keypad for direct input of Hexadecimal data or command functions.
- \* Includes 1.5 KBytes of RAM for user programs.
- \* Optional 24 line I/O port
- \* High quality, double-sided through-hole-plated printed circuit board simplifies construction.

## PLUS

A New Feature Series  
The Electronic Revolution  
The development of electricity and electronics,  
from Vota to Video.

## AND


All our regular stars . . . . .  
MONITOR  
POINTS OF VIEW  
INTO RADIO  
CLEVER DICK

The June issue of Hobby Electronics will be in  
your newsagents on May 14th  
DON'T MISS OUT . . . . PLACE YOUR ORDER  
NOW

Simply fill out the coupon and hand it to your  
local newsagent so that your copy will be  
reserved for you.

Please reserve . . . . . copies of the May issue of  
**Hobby Electronics**  
for  
Name . . . . .  
Address . . . . .  
.  
.  
.

# THE CASE FOR

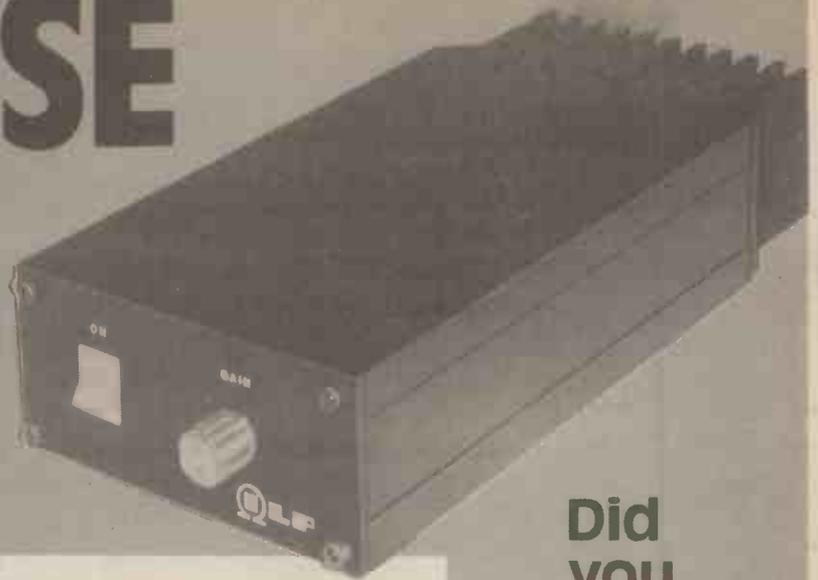


## It's the chance every constructor wants



**POWER AMPS**



**P.S.U.'s**

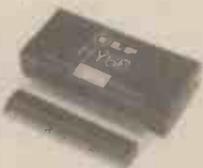

**PRE-AMP MODULES**

It's something you have always wanted...something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

### WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. **ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN.** It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, **FREE.** You don't even have to stamp the envelope if you address it the way we tell you.



**FREEPOST 6**  
 GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP  
 Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

**FREEPOST**  
 Mark your envelope clearly **FREEPOST 6** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

## Did you know

**I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?**

**I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?**

**There are TWENTY power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?**

**TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?**

**I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?**

**Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?**

**SEND COUPON**  
 (NO STAMP NECESSARY)  
**FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE**

To: **I.L.P. ELECTRONICS LTD.**

**PLEASE SEND ME I.L.P. CATALOGUE, POST PAID BY RETURN**

I HAVE/HAVE NOT PREVIOUSLY BUILT WITH I.L.P. MODULES

Name: \_\_\_\_\_

Address: \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

*I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.*



# THE ZX81 REVISITED

The ZX81 is a remarkable machine for many reasons — not the least of which is its price.

Phil Cohen

I REMEMBER from my adolescence (I'm not as old as I feel) the first of the Sinclair devices to hit the British market. These included a matchbox sized radio, a calculator (which hit *before* the Japanese ones), a digital watch kit at a fraction of the cost of competitive ones, and so on.

Although these may raise a yawn nowadays, at the time they were at the forefront of the market. Imagine the reaction of the public to the *first* digital watch, the *first* calculator — real 'Boys' Own Paper' stuff.

Sinclair entered the computer market with a little development kit based on the SC/MP processor, then moved very quickly up-market with the ZX80 (the forerunner of the ZX81).

I remember my reaction on first seeing the ZX80 advertised — I looked at the date of the magazine to see whether

it was an April edition. I really believed that it was a joke! I didn't think anyone could put so much into so small a package at so low a price.

The ZX80 had a couple of dozen chips and primitive BASIC capabilities. The ZX81 has as powerful a BASIC as many other machines on the market, and has five ICs (ignoring the three-terminal regulator).

## Amazing!

To look at, the ZX81 seems to be a mock-up of itself — it weighs about as much as a paperback book, it has no moving parts, it has no trailing wires, its case is plastic.

The keyboard looks as if it has simply been printed onto the front of the case. In fact, it's 'elastometric', made up of a conductive rubber sheet over a set of printed circuit contacts. When you press

the sheet down, it makes contact with the circuit board. It's just difficult to believe that it is what it's claimed to be.


## Hardware

Input and output for the ZX81 could not be simpler — literally. Output is direct to a TV set (not a monitor), and there are a couple of sockets for connection of a cassette recorder for program and data storage.

The power for the ZX81 comes from 9 V DC and that's it! Unless you want to add peripherals.

There is an exposed section of edge connector pads at the rear of the machine designed for the addition of the two peripherals so far released. One is a RAM pack which brings the total memory from its existing, rather limited, 1K up to a more sensible 16K. The other peripheral available is a printer. It features full alphanumeric plus graphics and prints 32 characters to the line, nine lines every 25 mm.

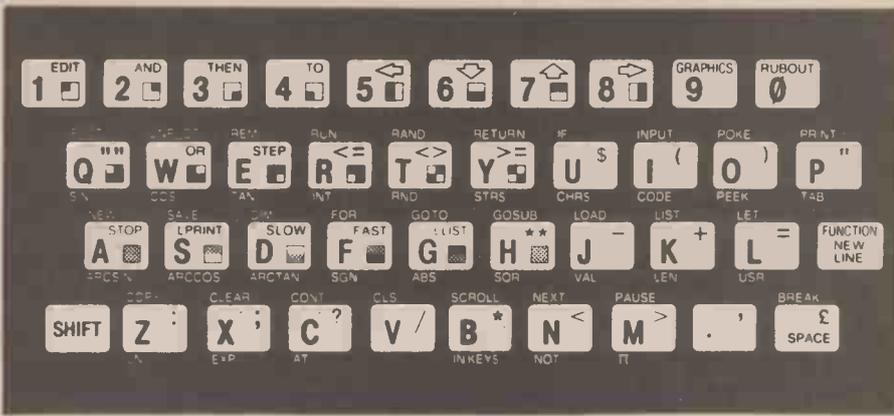The processor used in the ZX81 is a version of the ubiquitous Z-80. The keyboard is laid out in the normal typewriter 'QWERTY' manner — although *much* smaller than a typewriter



The ZX81's multi-function keyboard supports a very large number of operations. Graphics characters are called up by the GRAPHICS key (SHIFT/9); alternate characters (+, =, etc) by holding down the SHIFT key; functions (AND, etc) or any of the words printed beneath the keys are called by FUNCTION (SHIFT/NEWLINE) while program keywords are entered automatically after entering a program line number. If all this sounds confusing — don't worry. The keys are all colour-coded (eg, SHIFT and SHIFTeD keys are red) and the input mode is indicated by the cursor character.

keyboard. One user I heard from (he's ten) said it was just the right size.

I, unfortunately, have normal sized adult hands, so it's a bit small for me. In fact, that's one of the few criticisms I have of the ZX81 — you can't type on it, you have to use it like a calculator.

In fact, there's no 'feedback' to tell you that you've pressed a key — so you have to keep moving your eyes from the screen to the keyboard and back again. After a while (particularly during program entry) this gets very tedious indeed, but I suppose that most of the buyers (myself included, if I'd bought one instead of being loaned one for review) would rather have the cash than a better keyboard. It's very tempting for reviewers to catalogue the facilities that are missing from a device while at the same time forgetting that if they had been included, the buyer would inevitably have to pay. The incredibly low price of the ZX81 is one of its main attractions.

The other difference between ZX81 keyboard and those normally found on

computers is the fact that the key function don't stop at the letters of the alphabet.

### Statement Entry

This 'doubling up' of function is due to the extremely clever way in which Sinclair have arranged their program entry.

Say you want to enter the line "10 PRINT A". In most computers, you would press the '1' key, then the '0' key... through to the 'A' key at the end of the line. On the ZX81 you start with the line number, then simply press the 'P' key. Up on the screen comes "10 PRINT". There's no need to type the rest of the word in. Then you press the 'A' key (no need for a space — the computer supplies that).

The ZX81 BASIC is arranged so that the first word on each line is a keyword (like PRINT, FOR etc). So when you press the 'P' key, the machine *knows* that you mean PRINT, because the next entry *must* be a keyword. On the keyboard, the word PRINT appears over the 'P' key.

In fact, nearly all of the keys have a keyword associated with them. One consequence of using this system is that the old 'LET' statement (introduced in the very first version of BASIC, nearly 20 years ago) is resurrected. Most systems these days allow you to miss out the word LET in an assignment statement.

Another consequence of the system is that the software doesn't have to check the spelling to see if it's a keyword. Each of the keywords is entered and stored as a single character (although it appears spelt out on the screen). This is not only faster, it also saves memory.

There is also a SHIFT key, and a combination of other keys (FUNCTION and GRAPHICS) to select other options from the same letter key. In fact, some of the letter keys have *five* different functions crammed onto their ultra-small face!

The ZX81 is not for those who have trouble with small print!

### Display

The display on the screen is rather unusual for two reasons: the first is that all characters are shown normally black on white. I found this a rather pleasant, and less of a strain on the eye than the normal white-on-black.

The second rather unusual feature is that there is no automatic scrolling of the display. In most systems, when the PRINT statements in the program have put enough lines out to fill the available space, the screen 'scrolls' up one leaving a blank line at the bottom for the next line of output. The ZX81 does not have this feature — and in fact, if the PRINT statements try to put too much onto the screen, an error will result and the program will halt!

There are two ways to get round this. One is a SCROLL statement, which moves the screen up one line. The second is the CLS statement, which clears the screen.

It is rather surprising that Sinclair have chosen not to implement the automatic scroll — perhaps they have some good reason. I can't think of one.

The character set consists of upper-case letters, numbers, and the very minimum of other symbols. In fact Sinclair have kept the character set so small that I think some users may run into problems. For example, the symbol for multiplication is an asterisk '\*', and the symbol for exponentiation (ie raising to a



A ZX81 disassembled.

## The ZX81 Revisited

higher power) is two asterisks '\*\*'. Now, it is quite possible to put two of the multiplication symbols into line side by side. However, this is not interpreted by the computer as exponentiation. That has to be the special '\*\*' symbol. Unfortunately, there is no easy way that the user can tell the difference between the two on the screen. So it is quite possible to do as I did — to type two multiplication symbols to mean exponentiation, and then wonder why it didn't work.

### Syntax Checking

Each line of the program is checked for syntax as it is entered. Not only does this mean that problems will be shown up as they occur, but also that the machine doesn't have to check the syntax again as it runs the program.

The graphics symbols are fairly complete — allowing each character position to be split into four segments each of which can be black or white.

There are also symbols which allow shading of each character position, split horizontally into two segments (see photo of the keyboard). Each of the symbols in the alphanumeric set can be shown 'reversed', also.

As each line of program is entered, it appears on the screen in its correct position. So the normal method of looking at the program — a LIST command which scrolls the listing onto the screen — is not used.

Instead, the bottom couple of lines of the screen are an 'entry area', where the cursor appears. The top part of the screen then shows whatever part of the

program the last line was entered into.

In fact, this method of entry is very much easier to use than the normal 'scroll' method. It means that you can actually see the program change as you enter lines — this is very useful for beginners, who sometimes have trouble visualising what is happening inside the machine.

There is also an EDIT facility — one of the already-entered lines can be called in to the bottom part of the screen and modified, before being replaced in the main part of the program.

The operating system has a couple of features which are unique to the ZX81 — one of these is the ability to run in two modes — SLOW and FAST.

In the SLOW mode, the machine gives a 'flicker-free' display — the screen display is constant while calculations are in progress.

In the FAST mode (about four times as fast), the screen blanks while the machine is calculating, only coming on when it is paused for input (or during execution of the PAUSE command). This is because Sinclair are using the CPU to output the display!

The cassette saving routines have the ability to label the programs with an alphanumeric string, and to search for that string when the program is read off tape, only starting to load when they find the right program.

Another unusual feature is that when a program is saved, all the current variable values are saved, too. This is nice for fitting very 'tight' programs into the machine — the data initialisations do

not need to take up any memory. The only space they need would already be used by the variables themselves.

### Manual

The documentation that comes with the ZX81 is really excellent — the author, has taken a very down-to-earth approach, and the whole thing (over 200 pages of it) hangs together very nicely indeed. It is well peppered with explanatory examples, and is written in an easy style that will not confuse or frighten anyone. It's also spiral bound, so that it will lie flat while you copy programs from it!

The manual for a machine like the ZX81 is almost as important as the hardware itself — it is, after all, primarily a teaching machine.


The only thing that's missing from the manual is any sort of comprehensive hardware details. I suppose, though, that given the probable audience this would not be worthwhile.

The manual not only describes the ZX81 BASIC in loving detail, it also goes on to describe the internal software in some depth, including a full listing of the system variables and their interpretation, and a section on how to use machine code programs with BASIC.
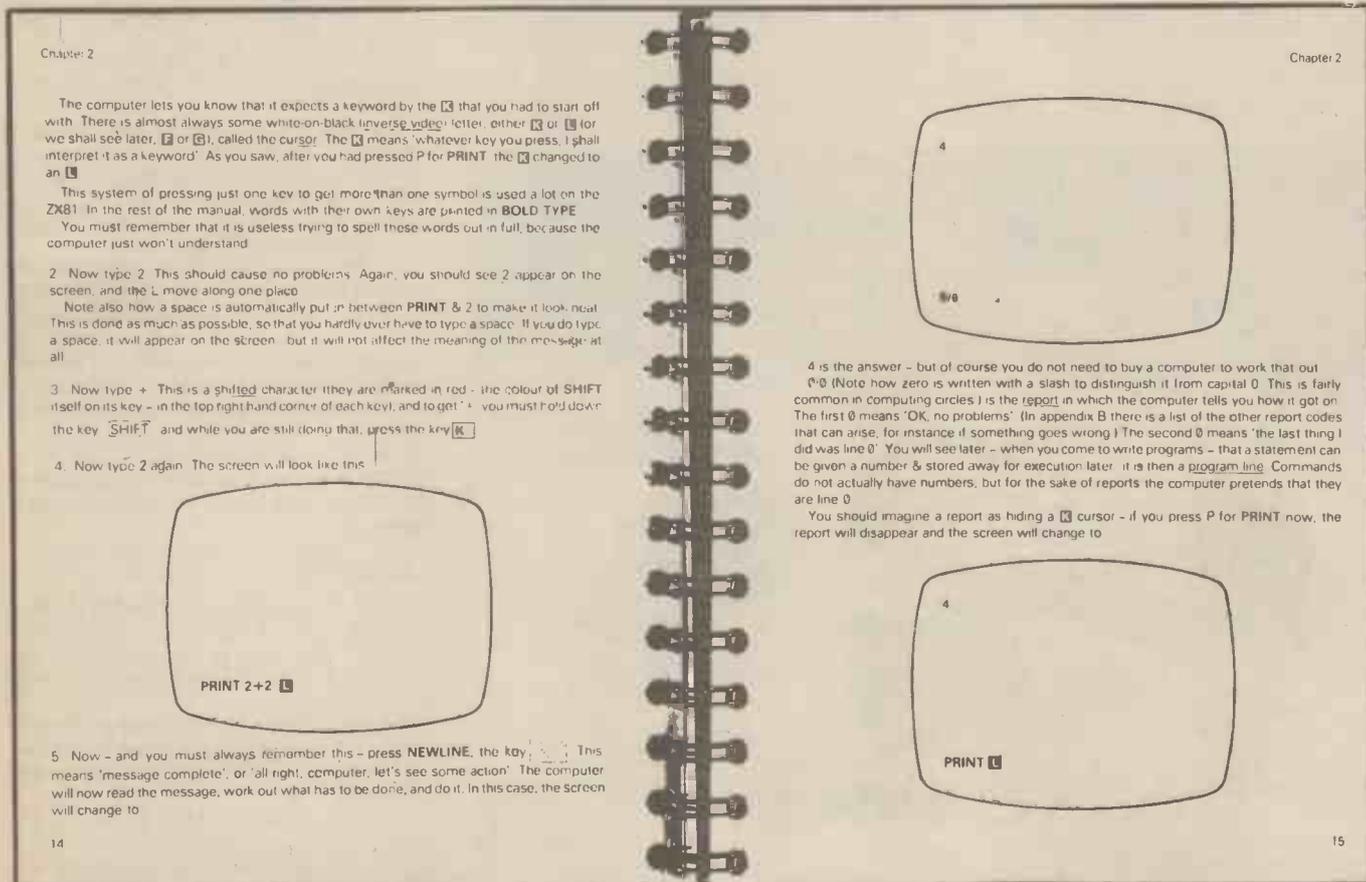
### Using it

Now we come to the most important part — how the machine performs.

I didn't try any 'benchmark' programs on the ZX81 — there's not much point, because all they would show is that the



A sample page from the excellent manual which is supplied with the machine.

machine is significantly slower than almost any other on the market.

I say again — it's a teaching machine. So the speed doesn't *really* matter.

I wouldn't recommend the ZX81 to someone who wants to do a lot of number-crunching, though — you'd be better off with a programmable calculator.

The display is sharp enough to be read without too much strain — even on my little portable. The characters are a little 'blocky', but not outrageously so.

Apart from the problem I mentioned earlier about the keyboard having no feedback, the only other major trouble in using the ZX81 is that 1K of RAM is really rather small — even with one character per keyword.

Then again — if it's the only computer that you can afford, and it's the first one that you've used, then it's not likely to trouble you.


### ZX81 Basic

Finally, I've included a list of the commands and features of the ZX81 BASIC so that you can see that the ZX81's language is every bit as comprehensive as that of other machines on the market. Variables may have an alphanumeric name of any length, starting with a letter continuing with letters and numbers — and *spaces!* This is due to the unique keyword entry method.

Values are stored to 9 digits, with a range between about  $10^{-38}$  and  $10^{38}$ . Array names are a single letter, and arrays may have any number of dimensions of any size.

String arrays are allowed — but all of the strings in the array are the same length. String variables are any length, but the string name is only a single letter.

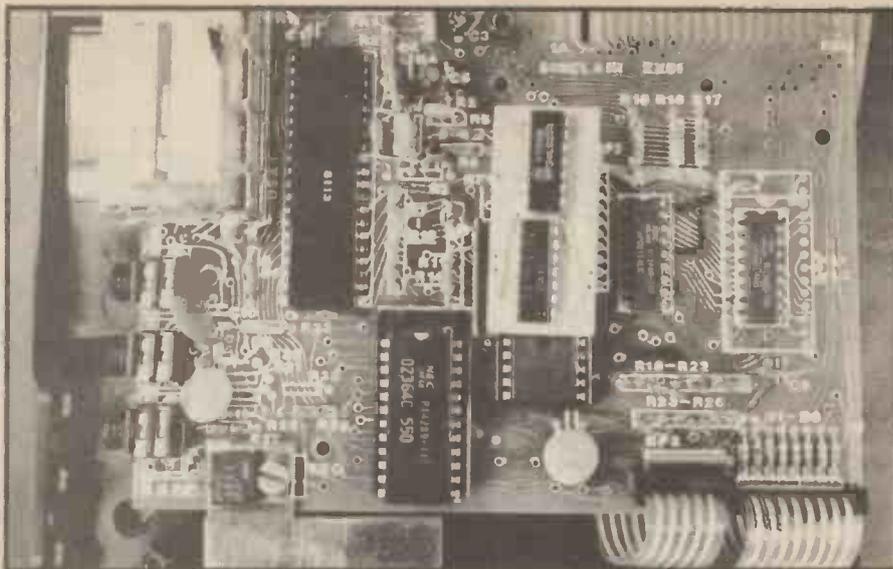Functions supported include: absolute value, arccos, AND, arcsin, arctan, CHR\$, CODE (the same as ASC in other BASICs — but it's not ASCII), cos, X°, INKEY\$ (gets a key press from the keyboard), integer part of a numC in other BAISCS — but it's not ASCII), cos, X°, INKEY\$ (gets a key press from the



The inside. That's all — true!

keyboard), integer part of a number length of a string, NOT, OR, PEEK, pi, random number, sign of a number, sin, square root, STR\$ tan, user machine code routine call, and VAL.

#### Statement types are:

- CLEAR deletes all variables
- CLS clears the screen
- CONT after 'break', continues execution
- COPY sends a copy of the screen contents to the printer
- DIM dimensions arrays
- FAST sets machine into fast mode (see text)
- FOR . . . TO . . . STEP forms a loop (the variable used must have only one letter in its name)
- GOSUB sends program to a line number (line number may be expressed as an expression)
- IF . . . THEN allows changes in program flow — but multiple statements per line are not supported
- INPUT allows the user to input a string or numeric characters

LET is required for assignment statements

LIST allows the user to call up any part of the program on the screen's display area

LLIST sends it to the printer

LOAD searches for the program name on the tape, then loads it

LPRINT sends output to the printer

NEW initialises the whole system

NEXT ends a FOR loop

PAUSE stops the program for a set period from 1/50 of a second to about 10 minutes

PLOT makes one quarter of a character print in the position specified

POKE allows the program to alter memory directly

PRINT puts information onto the screen.

Features supported are: comma (giving fixed tab), semi-colon (at the end of the statement, preventing line feed and carriage return) and TAB

RAND allows randomisation

RND variable sequence

REM for remarks

RETURN ends subroutine

RUN runs a program. RUN (line number) starts the program from the line number

SAVE puts the program onto tape, with a name of any length

SCROLL moves all the lines in the display area up one

SLO puts the machine into slow mode (see text)

STOP halts execution

UNPLOT turns off one quarter of a character position, in the position specified

### Summary

The ZX81 is a very high value-for-money machine. It's designed as a teaching machine, and at a price of £49.95 for the kit or £69.95, ready assembled it is very well targeted.

It is not a machine for those who have number-crunching applications in mind. For that is rather slow and a bit awkward.

It does, however, have almost all the advanced features found on other BASIC systems. Having mastered the ZX81, you will be able to drive almost any other machine after a couple of days.

HE



# Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

## Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



**New BASIC manual**

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

## Kit: £49.<sup>95</sup>

### Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



## Built: £69.<sup>95</sup>

### Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



# uter-



## Available now- the ZX Printer for only £49.<sup>95</sup>

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha-numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings - particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer - using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

## 16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software - the Business & Household management systems for example.

### How to order your ZX81

BY PHONE - Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST - use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY - please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt - and we have no doubt that you will be.

| To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.        |   |      |                 | Order         |
|--|---|------|-----------------|---------------|
| Qty  | Item  | Code | Item price<br>£ | Total<br>£    |
|  | Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.       | 12   | 49.95           |               |
|  | Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor. | 11   | 69.95           |               |
|  | Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).  | 10   | 8.95            |               |
|  | 16K-BYTE RAM pack.  | 18   | 49.95           |               |
|  | Sinclair ZX Printer.  | 27   | 49.95           |               |
|  | 8K BASIC ROM to fit ZX80.   | 17   | 19.95           |               |
|  | Post and Packing.   |      |                 | 2.95          |
| <input type="checkbox"/> Please tick if you require a VAT receipt        |   |      |                 | TOTAL £       |
| *I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ |   |      |                 |               |
| *Please charge to my Access/Barclaycard/Trustcard account no.            |   |      |                 |               |
| *Please delete/complete as applicable.                                   |   |      |                 | Please print. |
| Name: Mr/Mrs/Miss  |   |      |                 |               |
| Address:   |   |      |                 |               |
| FREEPOST - no stamp needed. Offer applies to UK only.                    |   |      |                 | HEL05         |

# sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: (0276) 66104 & 21282.



Pictured above is ACE, the National Physical Laboratory's first computer. The vertical sliding panels are to allow access for maintenance — and also to provide better cooling for the racks of valves. (Courtesy NPL, Crown Copyright).

# MICRO-HISTORY

A slice through the years, as we look at some of the men and machines that preceded today's powerful computers.

ALMOST every day, we read in the national press, or in other publications, that the age of computers is upon us. This is undoubtedly true, but it is nevertheless worthwhile looking back at some of the developments which have led to the current 'state of the art', before the technology overwhelms us! In writing about computers, there is often a temptation to baffle readers with science — the jargon looks good, and sounds authoritative. In fact, we should be trying to do the opposite; explain exactly what computers are and how they effect our lives, in plain, simple language. So, let's

start at the beginning, and get the whole thing in perspective.

Looking at the names associated with early computers, three stand out as beacons of foresight and understanding.

Taking them in chronological order, which is logical, we first meet Blaise Pascal.

Born in France, in the Seventeenth Century, he was best known as a mathematician. His father was a tax collector, an unpopular occupation, even then, and the sight of his father spending long hours over columns of figures was young Blaise's first inspiration; he pro-

duced a mechanical engine that removed the drudgery of the work. The basic design was a success, which was a considerable feat of purely mechanical engineering, and it enjoyed a limited commercial success, too. The main disadvantage was that it was only capable of either addition or subtraction — one operation at a time.

This machine was called the 'Pascalline' and it is still, surprisingly, in use today, recording the mileage that your car has covered. Its improved successor, which was capable of multiplication, survived for nearly as long. Only the

first electronic calculators sent it to the Science Museum. If you should see it there, it's worth remembering that it was invented when the Inducalculators sent it to the Science Museum. If you should see it there, it's worth remembering that it was invented when the Industrial Revolution was still to come and that even simple mechanical parts could not be manufactured accurately. It was this difficulty that caused the failure of the next innovator in computer science.

### The Difference Engine

Charles Babbage (who is the subject of this month's Famous Names), also began life as a child prodigy and it was his early interest in tables of logarithms that inspired his life's work. His first achievement was to produce a machine for calculating log tables which were more accurate than those previously published. His next task, the construction of the Difference Engine, was more challenging, but after eleven years' work and a Government grant of £17,000 (an enormous amount of money, in those days), the mechanical problems finally defeated him.

Despite this failure, he conceived an even more spectacular device, the great Analytical Engine, which incorporated all of the concepts of the Difference Engine but was, in addition, programmable; it was intended to carry out mathematical operations as required, on whatever data was available. This was the first visualisation of the computer as we understand it today — it actually included most of the features incorporated in modern microcomputers. Once more, though, the inability to make precision parts spelled

the doom of the Analytical Engine. Babbage died, aged 80, with not much left to his name except a pile of cogs and gear wheels. His son finally managed to put together a working model, which can be seen in the Science Museum.

### Herman the Wise

Less than twenty years later, the third great inventor in the history of computers, Herman Hollerith, made the final link in the chain of innovations that led to modern computers. His 'Tabulator' was designed as an entry in a competition to develop a system to analyse the mass of information collected for the 1890 American Census. It was an electro-mechanical device and completed the Census results in record time, making Hollerith a very rich man. Indeed, the company he founded (International Business Machines — IBM) is still one of the largest mainframe computer manufacturers and it is only recently that its dominance of the business has been challenged.

Hollerith's Tabulator was by no means an ideal computer; it was designed to do just one specific job and its 'programming' could not easily be changed. This was not the flexible, all-purpose machine conceived by Babbage. However, it is interesting to note that, following Babbage's adaptation of the punched cards used to control weaving machinery, Hollerith used similar cards to enter the Census data. These cards are still in use in many computer systems, today — some things never seem to change!

The breakthrough was made shortly after World War II. The development of ballistic computers and code-breaking

machines during the War produced some extremely sophisticated electro-mechanical devices but, like all such devices, they were 'dedicated' machines limited to a specific application. The first true electronic computer was, in fact, developed in Britain, in 1948 by a Manchester University team.

The development of the true electronic computer rested largely on the work of two mathematicians; Alan Turing, a Britian whose work on code-breaking laid the foundations and the American, John Von Neumann. Another vital step was the introduction of the binary numbering system. If Pascal or Babbage had designed their systems to use binary numbers they would have simplified their problems by a factor of nine and it is possible that the world would have had steam-powered computers before it had electricity.


Having made the key evolutionary leap, computers went from strength to strength. The first ones were monsters, its true (Ferranti's first commercial computer stood 32 feet long, eight feet high and four feet deep, used 3,500 valves, 2,500 capacitors, 15,000 resistors and six miles of wire) and rejoiced in names such as UNIVAC, ENIAC and ACE, but they were true general-purpose, programmable computers, consisting of the same basic elements as are found in today's computers.

The growth of computers, since then has been by a series of steady refinements, rather than by revolutionary developments. The thermionic valve was a notoriously unreliable device, slow and costly in terms of power consumption and space and they were soon replaced

A first generation computer — thousands of circuit cards and transistors beyond counting!

(Courtesy NPL, Crown Copyright).



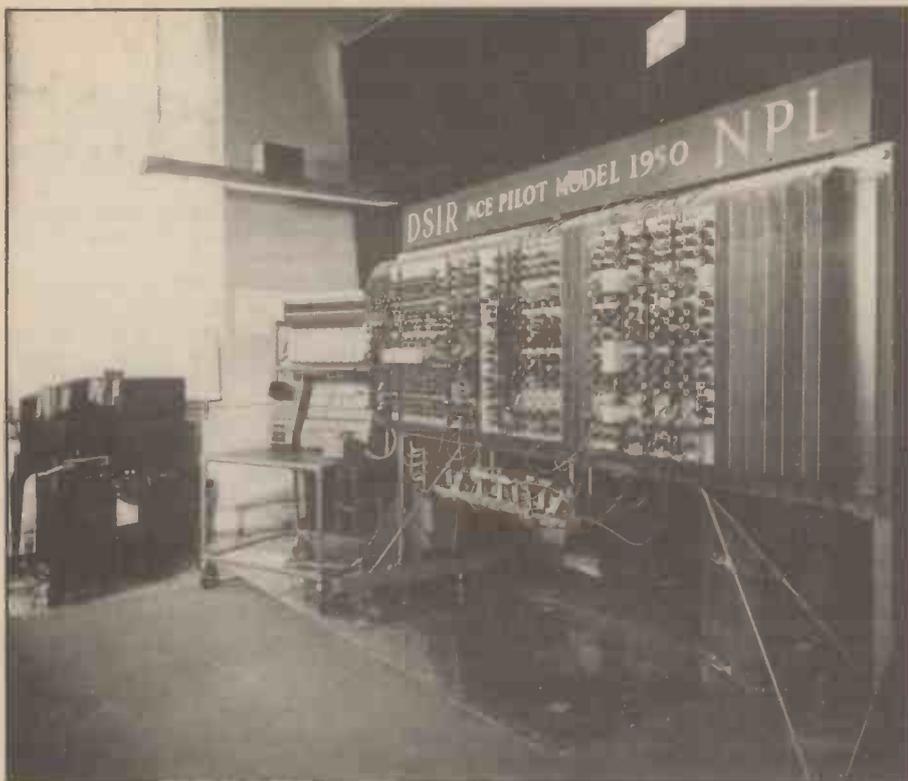

Pilot model of the NPL's ACE. (Courtesy NPL, Crown Copyright).

by the newly invented transistor. However, the replacement of valves by transistors did not involve any change in the basic design of computers.

The introduction of the transistor produced the 'second generation' of computers. A 'generation' in computer terms is loosely defined as a tenfold decrease in size with a tenfold increase in processing power at a tenth of the original cost. As the transistor became the descendent of the valve, so the chip or integrated circuit became the descendent of the transistor. In those days (some ten to twelve years ago), the first integrated devices consisted of perhaps a half dozen transistors on a single chip of silicon. Rapid advances were made and soon a new kind of computer was born.

### The Minis


Just as the Mini car revolutionised the way the world looked at motoring, so the minicomputer changed the face of computers. Up till the advent of the integrated circuitry there had been only 'computers'; now there were 'mainframes' and 'minis'. These were rigidly divided into sectors of operation — the mainframes were used for serious purposes, the minis were 'toys' used in research. Among the names of companies who were to make their fortunes producing minis was DEC who are, probably, still the world leader. Soon, the mini was to be found everywhere from research labs to classrooms and their spread was due simply to the fact that they were small, cheap and relatively easy to use. They were even built into pieces of equipment, such as machine tools. Indeed, it is fair to say that the mini paved the way for the micro, although the actual distinctions between them have been rapidly eroded.

Firms involved in the business of integrated circuit production tend to follow a natural progression in the devices that they make. First off the production line come the standard logic elements, the AND/OR type gates and, once the production of these is running at a profitable level, they attempt to squeeze a little more onto the slab of silicon. As soon as this stage is proved they take another leap forward and so on. In the terminology of the business, this is a progression from

SSI (Small Scale Intergration) with about 10-20 actual devices on the 'chip' through MSI (Medium Scale Integration), which has a dozen or so gates (rather than discrete elements) up to LSI (Large Scale Integration), which is taken as being greater than 100 gates on the chip. At this stage of the game we are still talking about, complex TTL type packages, the next jump is to VLSI which, believe it or not, stands for Very Large Scale Integration. We are now in the realm of memory devices and microprocessors.

If we take a look at Figure 1 we can see a generalised block diagram of a computer; what kind of computer is not important because they all have the same functional blocks within them, be they micro or mainframe. The common misconception is that the 'mighty chip' is a computer — far from it. Your average microprocessor still needs all the memory circuits, control circuits, mass storage devices and other components that even the old valve machines needed; they are merely smaller. The very first microprocessor came about in 1971 simply because it was realised that it would be possible to make a device of that complexity on a single chip. The device was called the 4004 and the company that made it was Intel. The next device they produced was the 8008 and that was followed by the microprocessor chip which, ten years after its initial introduction, still dominates the microcomputers of the world — ubiquitous 8080.

The rest of the story is not history; since the 8080, new chips have been introduced almost every year and so the future is still wide open. Indeed, the future probably holds as many new and exciting developments as the past and another revolution in computer technology is still possible, considering the work currently being done on the 'biological computer'. We may yet see computing 'brains' which more closely live up to the description!

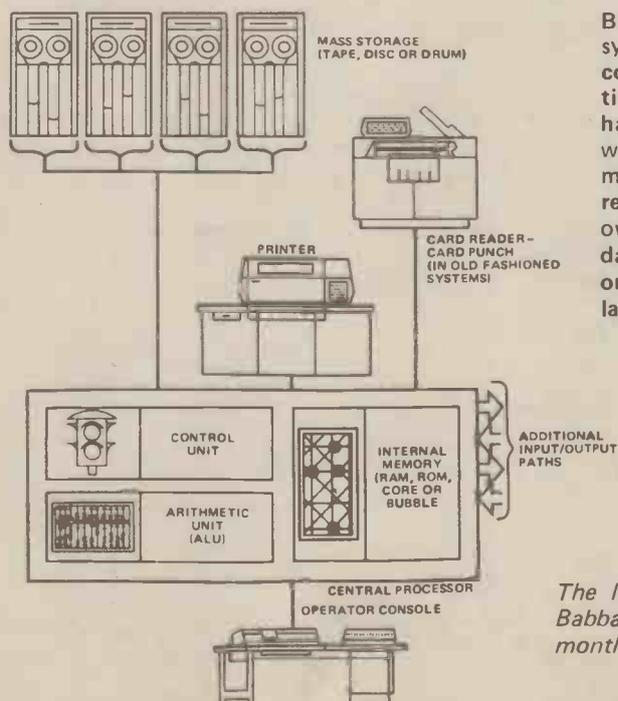

Block diagram of a computer system. A modern microcomputer is essentially identical — mass storage (usually hard disc) is quite possible with larger, more powerful microcomputers. Card readers, however, are a hold-over from the very earliest days of computing. They are only used, now, with very large mainframe systems.

*The life and career of Charles Babbage is the subject of this month's Famous Names feature.*

# Lack of ZX81 memory giving you headaches..?



## The Memotech 64K Memopak

The growth of interest in computer use caused by the introduction of the Sinclair ZX81 has made new and exciting demands on the ingenuity of electronic engineers. At Memotech we have focused our attention on the design of an inexpensive, reliable memory extension.

The Memopak is a 64K RAM pack which extends the memory of the ZX81 by a further 56K. Following the success of our 48K memory board the new memory extension is designed to be within the price range expected by Sinclair users. It plugs directly into the back of the ZX81 and does not inhibit the use of the printer or other add-on boards. There is no need for an additional power supply or for leads.

The Memopak together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts such basic commands as 10 DIM A(9000) 0-8K ...Sinclair ROM

8-16K...This section of memory switches in or out in 4K blocks to leave space for memory mapping, holds its contents during cassette loads, allows communication between programmes, and can be used to run assembly language routines.

16-32K...This area can be used for basic programmes and assembly language routines.

32-64K...32K of RAM memory for basic variables and large arrays.

With the Memopak extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

**DEALER  
ENQUIRIES  
WELCOME**



Memotech Ltd  
3 Collins Street  
Oxford · OX4 1XL  
Tel · 722102/3/4/5

Please debit my  
BARCLAYCARD/ACCESS\*  
account number:

\*Please delete  
whichever does not apply

Signature



Date

NAME

ADDRESS

Please rush me:

|  | Quantity | Price   | Total |
|--|----------|---------|-------|
| 64K RAM, Assembled                               |          | £68.69  |       |
| HINTS & TIPS FOR ZX81<br>(BOOK BY ANDREW HEWSON) |          | £4.25   |       |
| Stock Control Programme                          |          | £ 25.00 |       |
| Payroll Programme                                |          | £ 25.00 |       |

VAT @ 15%

Postage £2.00

HE1 TOTAL

To: Memotech Ltd., 3 Collins Street, Oxford, OX4 1XL Telephone (0865) 722102

# Clever Dick

Who is this mysterious person? Did Charles Dickens discover Hovis? Did Robert the Bruce discover Australia?

OK. Lets get it out of the way.

Dear CD,  
I am writing to you about your reply to Mr Belfield's letter in the March '82 issue of HE. You said that you would award next month's binder to anyone who could politely and in one sentence explain what chocolate digestives have to do with you.

I believe I have the answer — here goes. Chocolate digestives have the initials CD and C.D. = Clever Dick. I hope it is the right answer.  
Paul Procter,  
Chester.

PS Your mag is the best one out.

Dear CD,  
I write to you claiming a binder, with no grovelling whatsoever. You offered a binder to anyone who could explain D. Belfield's PPS; well, here is the explanation.

Clever Dick (CD) and chocolate digestives (cd) both have the same initials, so by saying that his sister likes chocolate digestives, he is implying that she also likes you — is this grovelling?

Was that polite enough?  
In expectation of a binder,  
R. Hart,  
Mansfield,  
Notts.

PS Charles Dickens also has the initials CD — any relation?

Dear CD,  
In the March issue (we know that by now, thanks all the same) you asked for the connection between yourself and Mr Belfield's sister's craving for chocolate digestives.

Well, firstly you should be honoured to have the same initials as a Chocolate Digestive and, secondly, it is a clue to your real identity.

If you remove all the letters from Clever Dick that also occur in Chocolate Digestive, you are left with the letters R, K. This would therefore, suggest that you are in fact Ron Keeley, the Esteemed Editor.

I hope this answers your question and you will keep your promise of an award?  
I.M.A. Bruce.

PS I have been reading HE for almost three years and in that time have not only developed a warped sense of humour but also a very warped stock of HEs.

Dear Chocolate Digestives,  
Isn't Mr Belfield's PPS obvious? He thinks that CD stands for Chocolate Digestives and his sister has fallen in love with you (but then, which girl wouldn't).

Anyhow, down to business. Why are all these people complaining about the few mistakes made in HE? Don't they know that it is all done on purpose to keep us hobbyists on our toes? After all, how can two whole diagrams (Figures 9 and 10, page 43) in the oscilloscope article in the March issue be misplaced and then merely attributed to 'gremlins'.

I'm sure that the HE team, in their ultimate wisdom, know exactly what they are doing.  
Yours, CanIhaveabinderpleasingly,  
J. Sylvester,  
Ilkeston,  
Derbyshire.

PS Why is it that, in some project component lists, it says, for example, "50k — 5 off" instead of "5 off"?  
PPS I wouldn't mind a binder.  
PPPS If you send a binder, I might just get back in from this three-stories-high window ledge.  
PPPPS Remember, if I do accidentally fall off (of?) this ledge, I won't be able to buy HE anymore!

Oh what clever, witty readers you are. I should have known that the question was far too easy for such erudite, intelligent and perspicacious people. Never mind. You can't win them all — nor can all win. So.

Paul Procter is straight to the point, even blunt, one might say — but is that

polite? G. Adamson, I'm afraid, loses immediately. What a dreadful pun!

Mr R. Hart has a strong claim, but loses points for subdued grovelling — if your going to do it, lad, do it properly, like. Besides, Charles Dickens is older than I am. I.M.A. Bruce came up with a very clever answer (although his 'name' is another dreadful pun) which, unfortunately for HIM, has nothing to do with ME. My real identity, sir, is the most closely guarded secret since Superman fell out of the 'phone box. Not even the Editor knows who I really am — and sometimes I'm not too sure myself.





That leaves J. Sylvester (any relation to Victor?), who has probably jumped by now. Just in case he's still hanging about, a binder is on its way to him, awarded for the most concise answer to the question; his salutation was plain enough. A belated binder is also awarded to D. Belfield, together with a packet of Chocolate Digestives for his sister (but he'll have to write again, with his full address this time).

This late reply seems to have missed the point, though he's quick enough to claim the reward.

Dear CD,  
In reply to D. Belfield's letter, the SAB0600 is, in fact, the IC used in the Doorchime project (December 81) and can be obtained from TK Electronics.

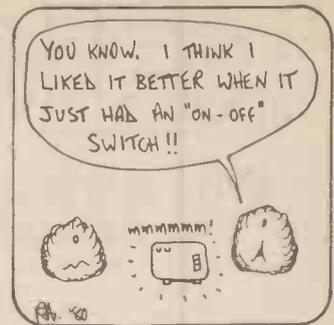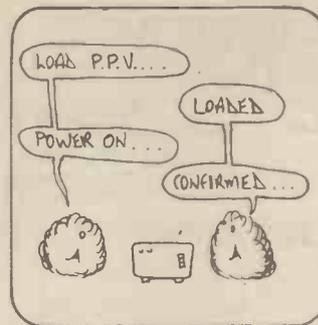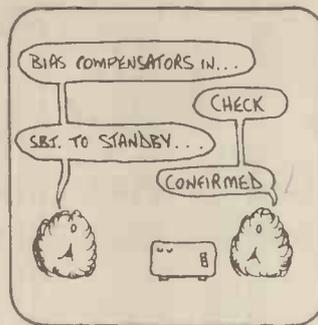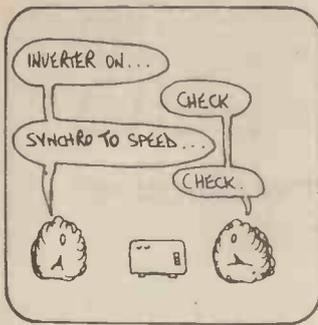Now a suggestion for a project; how about a Flanger? I am interested in making electronic music — December's HE was excellent and I have built the Graphic Equaliser and the Drum Synth (with modifications) and they worked extremely well.





Don't forget the binder, thank you.  
S.C. Bonnell,  
Wolverhampton.  
PS Keep up the good work.

Right! The Doorchime! I knew I'd seen it somewhere. This is a good as time as any to remind you all that I can only give detailed replies to exact questions — the IC referred to could have been in any project published anytime in the past four years and I certainly don't have time to check them all!

The Flanger project is a good idea, which follows naturally from the HE Echo-Reverb in this issue. I'll see what I can do to push it, OK? As for the binder — sorry, you're too late.

It's always nice to receive 'love letters', but this one is just slightly dubious.

Dear CD,  
I often buy decent magazines on electronics from my newsagent and often have a laugh at HE. Most of the projects are, to say the least, pathetic tea-break rejects.

But what was this I saw in the April '82 issue? A useful project! Amazing! I must congratulate you for the Digital Capacitance Meter (usually, any sensible projects are to be found in ETI). I actually bought the magazine and the last three pages weren't on CBI!  
M. Garton,  
Purveyor of Messy Writing,  
(Address illegible).

He's right about the writing, if nothing else. All Hobby Electronics projects are designed to be useful for some purpose, even if the aim is only to instruct — we do have a number of readers who are just getting into electronics for the first time, you know.

The next letter raises a most interesting question — is it 1984, already?

Dear Dick,  
I remember reading, some time ago, that a Japanese camera company fitted their remote control cameras with infra red control so they could get around the Wireless Telegraphy Act of 1947/1969. But, after reading the 1969 Act, I noticed that any form of transmission, including infra red, could only be considered legal if used by the Post Office or by people with licenses.

It seems that they do not yet have control over shouting or singing, but I expect that they're working on it. Is it true, Dick? Are these infra red cameras and remote control units against the law?

M. Scholes,  
Telford,  
Salop.

PS Why do all these people waste time buying or grovelling for binders? Have they no floors on which to pile their HEs? I keep mine in suitcases and old box files under the bed!

The implication, here, is that anyone who uses an infra red remote control system for any purpose (changing TV channels, for example), is breaking the law. That is not the case. The Act referred to defines Wireless Telegraphy (for which a license is required) as follows:

Wireless Telegraphy means the emitting or receiving, over paths which are not provided by any material substance constructed or arranged for that purpose, of electromagnetic energy of a frequency not exceeding  $3 \times 10^6$  Megahertz.

Fortunately for all of us, the infra-red band starts at  $3 \times 10^6$  MHz and, therefore, operating an infra-red remote system does not require a license, under the Act. Imagine the trouble Buzby would have, if IR was illegal! He'd probably lose all his feathers from over-work.

Now here's a classic plea for HELP.

Dear CD,  
I have built the Power Pack (September '81) and — lo and behold — it worked. Yesterday I put in the fuse holder and, instead of 5 to 15 volts, I now get 7V5 to 23 V and sparks jump between the carbon track and the connector. What have I done wrong?  
C. Basnett,  
Quarry Bank,  
West Midlands.

See what I mean? On the face of it, this project is so simple that nothing should go wrong (so what do you mean, "lo and behold"?). The only answer that occurs to me is that you've got a solder bridge between — or nearly between — the PCB tracks and the mains voltage is arcing across. Check the board carefully for lumps of solder.

Sometimes, it seems, people just don't read the magazine — we go to an awful lot of trouble to get all this information in. Why, of why won't you just READ IT!

Dear CD,  
Please can you answer my simple question; where do you get the boxes for projects, ie Bike Alarm and Digital Capacitance Meter (April '82). Do you have to build them yourself?  
C. Mathews,  
Egham,  
Surrey.

No, I certainly don't — and neither do you. The Buylines page is there to let you know where to obtain components and parts for all our projects — but you must read it, you know. If you had, you'd know that cases for both these projects are available from BICC Vero. OK?

Then, reading does not always lead to understanding.

Dear CD,  
After reading Ian Sinclair's Into Digital Electronics, I'm hooked on digital circuits and displays. The only thing is, I'd like to be able to check IC pins with a logic probe, for fault finding, but I'm not sure what the logic state of the pins should be in the first place. I wonder if you could help me?  
K. Goonan,  
Preston,  
Lancs.

You may be beyond all help, buy I'll try. Without repeating the series, the simple answer is that the logic state is a given IC pin will usually be either a 1 (high voltage) or a 0 (low voltage), but exactly which state the pin assumes depends on the type of IC (AND gate? OR gate? Timer? Counter?) and how it is connected. For example, a 555 may be wired as an astable multivibrator or as a monostable, to choose two common circuit configurations. Before you can know what the logic state of a pin *should* be, therefore, you must understand the circuit. I believe that a very special logic probe is being designed and will be published in the near future. Perhaps you will be able to use it to gain a better understanding of digital logic. In the meantime I can only suggest that you go back and read Ian Sinclair's series from the beginning!

HE

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED.  
ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS:  
CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT  
AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED.  
TRADE AND EXPORT INQUIRY WELCOME. P&P ADD 50p TO ALL  
ORDERS.

## VAT

All prices exclusive of VAT. Please add 15% VAT to the total cost incl. P&P

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest underground/BR Station: Watford High Street. Open Monday to Saturday: 9 a.m. to 6 p.m.

**POLYESTER CAPACITORS: Axial Lead Type**  
100V: 1nF, 1.5n, 2n2, 3n3, 4n7, 6n8 11p; 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 100n, 150n 20p; 220n  
30p; 330n 42p; 470n 52p; 680n 60p; 1uF 68p; 2uF 82p; 4uF 85p  
160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n, 38p; 1uF 42p; 1.5uF 45p; 2uF 48p  
1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 48p; 100n 50p; 470n 99p.

**POLYESTER RADIAL LEAD CAPACITORS: 250V:**  
10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p.  
330n, 470n 13p; 680n 19p; 1uF 23p; 1.5uF 40p; 2uF 48p; 4uF 70p.

**ULTRASONIC TRANSDUCERS:**  
40kHz 395p/pr

**ELECTROLYTIC CAPACITORS:** (Values are in  $\mu$ F 500V: 10 52p; 47 78p; 250V: 100 65p; 63V: 0.47, 1, 1.5, 2.2, 2.5, 3.3 8p; 4.7 9p; 6.8, 10 10p; 15, 22, 33 15p; 47 12p; 100, 150, 220 18p; 330, 470 22p; 680 28p; 1000 35p; 2200 48p; 4700 78p)  
100V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 30p; 680n, 38p; 1uF 42p; 1.5uF 45p; 2uF 48p  
1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 48p; 100n 50p; 470n 99p.

**TAG-END TYPE:** 70V: 4700, 245p; 64V: 3300 198p; 220 139p; 50V: 3300 154p; 2200 110p; 40V: 4700 160p; 25V: 10,000 320p; 15,000 345p.

**TAN ALUM BEAD CAPACITORS:**  
35V: 0.1uF, 0.22, 0.33 15p; 0.47, 0.68, 1.0uF, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10uF 28p; 16V: 2.2, 3.3 16p; 4.7, 6.8, 10 18p; 15, 36p; 22, 30p; 33, 47, 40p; 100 75p; 220 98p; 10V: 15, 22, 26p; 33, 47 35p; 100 55p; 6V: 10, 40 22p.

**MYLAR FILM CAPACITORS:**  
100V: 1nF, 2, 4, 4n7, 10 6p; 15nF, 22n, 30n, 40, 47 7p; 56 100n, 200 8p; 470n 50n, 12p.

**MINIATURE TYPE TRIMMERS:**  
2.6pF, 2.10pF, 2.25pF, 5.56pF 30p.

**COMPRESSION TRIMMERS:**  
3.40pF; 10.80pF 20p; 20.25pF 28p; 100.580pF 38p; 400.1250pF 48p.

**SILVER MICA (Values in pF):**  
2, 3.3, 4.7, 6.8, 8.2, 10, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 82, 85, 100, 120, 150, 180pF 15p each  
200, 220, 250, 270, 300, 330, 360, 390, 470, 600, 800, 820 21p each  
1000, 1200, 1800, 2200 30p each  
3300, 4700pF 60p each

**CERAMIC CAPACITORS 50V: 0.5pF to 10nF 4p; 22n to 47n 5p; 100n 7p.**

**GAS & SMOKE DETECTORS:**  
TGS812 or TGS813 575p

## ACCESS ORDERS

Just phone your order through and we do the rest

## VOLTAGE REGULATORS

1A 103 +ve -ve  
5V 7805 145p 7905 220p  
12V 7812 145p 7912 220p  
15V 7815 145p  
18V 7818 145p

1A TO220 Plastic Casing  
5V 7805 45p 7905 55p  
12V 7812 50p 7912 55p  
15V 7815 50p 7915 55p  
18V 7818 50p 7918 55p  
24V 7824 50p 7924 55p

100mA TO92 Plastic Casing  
5V 78L05 30p 79L05 60p  
6V 78L02 30p  
8V 78L02 30p  
12V 78L12 30p 79L12 60p  
15V 78L15 30p 79L15 60p

CA3085 95p LM317 99p TBA6258 75p  
LM3004 170p LM323K 99p TDA1412 150p  
LM3054 140p LM323K 99p 78H05 55p  
LM309K 135p LM723 35p 78H45 55p  
LM317K 350p TAA550 50p 79HG 785p

**JACKSONS VARIABLE CAPACITORS**  
Dielectric 0.2 365pF with slow motion Drive 495p  
500pF 220p 0.208/176 435p  
6.1 Ball Drive 0.208/176  
4511/DAF 185p with slow motion Drive 495p  
6.1/36.1 775p C804-SF: 10: 15:  
Drum 54mm 59p 25: 50pF 278p  
0.1-365pF 350p 100, 150pF 350p  
0.02-365pF 435p 'L' 3x310pF 725p  
0.03x25pF 575p

**DENCO COILS**  
"DP" VALVE TYPE RFC 5 chokes 140p  
Range 1 to 5 BL, RFC 7 (19mH)  
RD, TL Wh. 122p  
6-7-Y-R 110p  
15 Green 150p  
RD Wh. YI 150p  
B9A Valve Holder TOC 1 124p  
42p MW5FR 122p  
RDT2 145p MW/LW SFR 154p

**VEROBOARD**  
0.1 Patch clad plain  
2 1/2 x 3 1/2 73p 52p  
2 1/2 x 5 83p  
3 1/2 x 3 1/2 83p  
3 1/2 x 5 95p 79p  
4 1/2 x 17 326p 211p  
4 1/2 x 17 426p  
Pvt 100pins 50p  
Spot face cutter 118p  
Pin insertion tool 162p

**SWITCHES**  
TOGGLE: 2A/280V  
SPST Standard 33 1/2 A SPST 13  
DPDT Standard 44 1/2 A DPDT 14  
SUB-MIN TOGGLE 1A DPDT 13  
SPST on/off 54 1A DP c/off 15  
SPDT (c/over) 60  
DPDT 6 tags 75  
DPDT c/off 80  
DPDT Base 145  
ROCKER: SPST on/off 10A/250V 78  
ROCKER: DPDT 10A/250V 78  
ROCKER: DPST ILLUMINATED 85  
ROTARY: (Adjustable Stop) 1 pole/2 to 12 way; 2 pole/2 to 6 way; 3 pole/2 to 4 way; 4 pole/2 to 3 way

**DIL SOCKETS**  
Low Wire Prof. wrap Euroboard 620  
8 way 8p 25p S Dec 450  
14 pin 8p 35p Binboard I 450  
16 pin 10p 42p Binboard 375  
18 pin 16p 52p  
20 pin 22p 60p  
22 pin 25p 70p  
24 pin 27p 70p  
28 pin 28p 80p  
40 pin 30p 89p

**DIODES**  
BY126 12 Range 2V7 to 35V 40mW  
CR033 250 8p each  
OA9 40 Range 3V3 to 33V 1.3W  
OA47 12 15p each  
OA70 12  
OA79 15  
OA85 15  
OA90 8  
OA91 8  
OA95 8  
OA200 8  
IN914 4  
IN916 5  
IN4001/2 5  
IN4003 6  
IN4004/5 6  
IN4148 7  
IN4149 7  
IN5401/2 15  
IN5404 16  
IN5406 17  
IN5408 17  
IN541 9  
15821 9  
6A/100V 4  
6A/400V 50  
6A/800V 65

**BRIDGE RECTIFIERS**  
(plastic case)  
1A/50V 18  
1A/100V 22  
1A/400V 22  
1A/600V 34  
2A/50V 35  
2A/100V 46  
2A/400V 46  
2A/600V 65  
6A/100V 50  
6A/400V 95  
6A/800V 125  
8A/100V 115  
8A/200V 115  
10A/100V 78  
10A/200V 240  
25A/200V 395  
25A/600V 55  
16A/100V 133  
16A/200V 133  
16A/400V 220  
25A/100V 120  
VM18 50

**TRIACS**  
3A100V 48  
3A200V 54  
3A400V 56  
8A100V 95  
8A200V 69  
8A400V 115  
8A800V 115  
2A100V 78  
12A/200V 80  
12A/400V 80  
12A/800V 158  
BT106 158  
BT116 180  
C106D 38  
TIC45 24  
TIC45 29  
TIC47 35  
N25062 32  
N25064 38  
2N4444 130

**DIAC**  
2T80000 420  
2T80000 480

|      |    |       |     |       |     |      |      |            |      |         |      |
|------|----|-------|-----|-------|-----|------|------|------------|------|---------|------|
| 7400 | 11 | 74153 | 45  | LS124 | 105 | 4048 | 56   | AY-3 8500  | 390  | MC1495  | 350  |
| 7401 | 11 | 74154 | 45  | LS125 | 30  | 4049 | 30   | AY-3 8910  | 600  | MC1496  | 70   |
| 7402 | 11 | 74156 | 75  | LS126 | 30  | 4050 | 30   | AY-5 1224A |      | MC1496  | 70   |
| 7403 | 14 | 74157 | 75  | LS127 | 35  | 4051 | 78   |            | 235  | MC1596  | 225  |
| 7404 | 14 | 74159 | 99  | LS133 | 35  | 4052 | 78   | AY-5 1230  | 450  | MC1648  | 280  |
| 7405 | 18 | 74160 | 60  | LS136 | 28  | 4053 | 78   | CA3011     | 130  | MC1709G | 90   |
| 7406 | 28 | 74161 | 60  | LS138 | 35  | 4054 | 125  | CA3018     | 86   | MC1710  | 79   |
| 7407 | 28 | 74162 | 62  | LS139 | 38  | 4055 | 125  | CA3020     | 210  | MC3302  | 150  |
| 7408 | 16 | 74163 | 64  | LS145 | 75  | 4056 | 120  | CA3023     | 210  | MC3340P | 120  |
| 7409 | 16 | 74164 | 64  | LS147 | 199 | 4057 | 191  | CA3028A    | 95   | MC3360P | 120  |
| 7410 | 16 | 74165 | 62  | LS148 | 99  | 4059 | 480  | CA3034     | 280  | MC3401  | 65   |
| 7411 | 20 | 74166 | 65  | LS149 | 62  | 4060 | 480  | CA3035A    | 365  | MC3403  | 65   |
| 7412 | 20 | 74167 | 185 | LS155 | 39  | 4061 | 1225 | CA3046     | 70   | MC3403  | 110  |
| 7413 | 24 | 74170 | 168 | LS157 | 35  | 4062 | 995  | CA3048     | 220  | MFC6040 | 97   |
| 7414 | 32 | 74172 | 290 | LS158 | 35  | 4063 | 99   | CA3059     | 285  | MK50398 | 65   |
| 7415 | 25 | 74173 | 65  | LS160 | 41  | 4064 | 399  | CAA3075    | 213  | ML924   | 230  |
| 7416 | 25 | 74174 | 72  | LS161 | 41  | 4068 | 22   | CA3087E    | 70   | MMS303  | 635  |
| 7417 | 20 | 74175 | 72  | LS162 | 41  | 4069 | 20   | CA3081     | 95   | MMS307  | 1285 |
| 7421 | 20 | 74176 | 55  | LS163 | 41  | 4070 | 26   | CAA3085    | 200  | MMS387  | 47   |
| 7422 | 20 | 74177 | 75  | LS164 | 48  | 4071 | 20   | CA3090AQ   | 375  | NE531   | 14   |
| 7423 | 20 | 74178 | 95  | LS165 | 145 | 4072 | 20   | CA3123E    | 150  | NE543   | 225  |
| 7425 | 28 | 74180 | 95  | LS173 | 72  | 4075 | 20   | CA3130     | 48   | NE544   | 210  |
| 7426 | 27 | 74182 | 75  | LS174 | 72  | 4076 | 60   | CA3136     | 48   | NE555   | 45   |
| 7427 | 27 | 74184 | 99  | LS175 | 58  | 4077 | 26   | CA3189     | 295  | NE660   | 325  |
| 7428 | 28 | 74185 | 99  | LS181 | 130 | 4078 | 26   | HA1336E    | 240  | NE661   | 398  |
| 7430 | 16 | 74186 | 99  | LS182 | 58  | 4079 | 26   | ICL7107    | 75   | NE662   | 410  |
| 7432 | 26 | 74188 | 290 | LS183 | 58  | 4080 | 21   | ICL7107    | 975  | NE664   | 420  |
| 7433 | 27 | 74190 | 70  | LS191 | 58  | 4082 | 21   | ICM7204    | 550  | NE665   | 120  |
| 7437 | 27 | 74191 | 70  | LS192 | 58  | 4085 | 65   | ICM7205    | 1150 | NE666   | 155  |
| 7438 | 27 | 74192 | 70  | LS193 | 65  | 4086 | 70   | ICM7205    | 1150 | NE667   | 155  |
| 7440 | 17 | 74193 | 65  | LS195 | 40  | 4089 | 140  | ICM7215A   | 950  | NE670   | 120  |
| 7441 | 68 | 74194 | 65  | LS196 | 58  | 4093 | 43   | ICM7216A   | 1150 | NE671   | 425  |
| 7442 | 38 | 74195 | 65  | LS221 | 60  | 4095 | 90   | ICM7217A   | 790  | NE672   | 425  |
| 7444 | 90 | 74197 | 65  | LS240 | 96  | 4096 | 90   | ICM7222A   | 785  | NE5534  | 16   |
| 7445 | 65 | 74198 | 99  | LS241 | 96  | 4097 | 320  | ICM7556    | 150  | SC435   | 60   |
| 7446 | 55 | 74221 | 80  | LS242 | 96  | 4098 | 88   | LA3350     | 250  | SAB3209 | 245  |
| 7447 | 50 | 74246 | 150 | LS243 | 96  | 4099 | 88   | LA3350     | 250  | SAB3210 | 245  |
| 7448 | 50 | 74248 | 150 | LS244 | 80  | 4160 | 95   | LA3350     | 250  | SAB3211 | 245  |
| 7449 | 16 | 74249 | 150 | LS247 | 40  | 4162 | 99   | LA3350     | 250  | SAB3212 | 245  |
| 7451 | 16 | 74250 | 150 | LS248 | 65  | 4163 | 99   | LA3350     | 250  | SAB3213 | 245  |
| 7452 | 16 | 74251 | 150 | LS249 | 68  | 4174 | 109  | LA3350     | 250  | SAB3214 | 245  |
| 7454 | 16 | 74252 | 150 | LS251 | 40  | 4175 | 109  | LA3350     | 250  | SAB3215 | 245  |
| 7456 | 18 | 74253 | 40  | LS253 | 40  | 4174 | 105  | LA3350     | 250  | SAB3216 | 245  |
| 7457 | 30 | 74254 | 40  | LS254 | 48  | 4408 | 790  | LA3350     | 250  | SAB3217 | 245  |
| 7458 | 30 | 74255 | 40  | LS255 | 48  | 4409 | 790  | LA3350     | 250  | SAB3218 | 245  |
| 7459 | 30 | 74256 | 40  | LS256 | 48  | 4410 | 790  | LA3350     | 250  | SAB3219 | 245  |
| 7460 | 30 | 74257 | 40  | LS257 | 48  | 4411 | 790  | LA3350     | 250  | SAB3220 | 245  |

**7ALS**  
74LS00 12  
74LS01 13  
74LS02 13  
74LS03 14  
74LS04 14  
74LS05 15  
74LS06 15  
74LS07 15  
74LS08 15  
74LS09 15  
74LS10 15  
74LS11 15  
74LS12 15  
74LS98 15  
74LS99 15

## CMOS

|      |    |      |     |        |    |        |     |
|------|----|------|-----|--------|----|--------|-----|
| 4000 | 14 | 4412 | 695 | LM301A | 26 | TA7120 | 250 |
| 4001 | 14 | 4413 | 695 | LM301B | 26 | TA7121 | 250 |
| 4002 | 14 | 4414 | 280 | LM301C | 26 | TA7122 | 250 |
| 4003 | 14 | 4415 | 280 | LM301D | 26 | TA7123 | 250 |
| 4004 | 14 | 4416 | 280 | LM301E | 26 | TA7124 | 250 |
| 4005 | 14 | 4417 | 280 | LM301F | 26 | TA7125 | 250 |
| 4006 | 14 | 4418 | 280 | LM301G | 26 | TA7126 | 250 |
| 4007 | 14 | 4419 | 280 | LM301H | 26 | TA7127 | 250 |
| 4008 | 14 | 4420 | 280 | LM301I | 26 | TA71   |     |



# HE Echo-Reverb Unit

A superb project for creative musicians and audiophiles.

AN ECHO-REVERB unit is an accessory that can be added to virtually any existing audio or electronic music system and used to impart new life to existing sounds. In any audio system, the unit is simply interposed between the output of the preamp and the input of the main amplifier, so that the audio signals have to pass through the echo-reverb unit on their way to the main amplifier.

Some modestly-priced echo-reverb units use a crude mechanical spring-line to create the time-delayed echo-reverb and provide only a single, fixed delay

time. Commercial (all electronic) echo-reverb units can be rather expensive, but provide fully-variable delay times. Many use clocked CCD (charge-coupled device) analogue ICs to implement the delays (see *How It Works*). The best commercial units use digital techniques to implement the delays, but these are extremely expensive!

We have used the analogue CCD technique to implement the time delays and the HE Echo-Reverb gives a performance that is at least as good as some commercial units using CCDs. The

important thing about our unit, however, is that the design uses some cunning techniques to reduce the hardware costs of its circuitry, while at the same time enhancing the overall performance and facilities.


## Echo-Reverb

As the audio signals enter the echo-reverb unit they split into two paths, which are re-united again near the output of the unit via a built-in low-distortion audio mixer. One of these

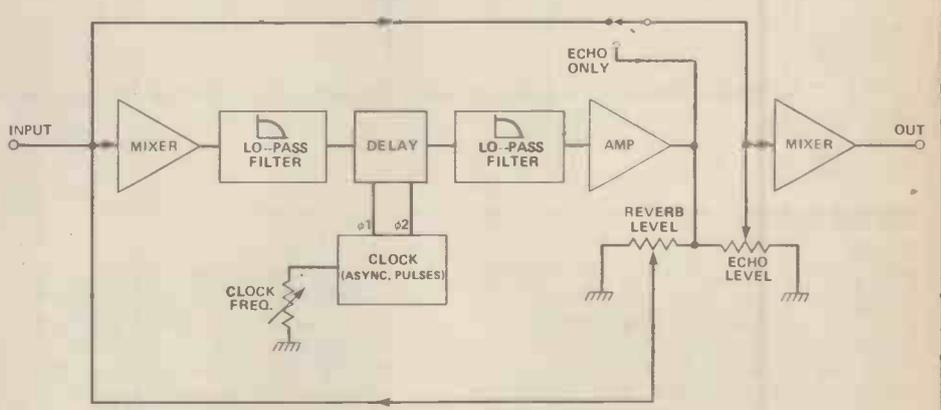
## How It Works


THE STAGES for producing the various reverb effects from the HE Echo-Reverb, are shown in the block diagram. The main signal path comes from the output of the first mixer and through a 7 kHz low-pass filter. This filter is necessary to limit the audio bandwidth to less than half the clock frequency, because the audio input is being *sampled* at the clock frequency (variable, to change the length of delay), and it is a fundamental principle of sampling (Shannon's Law) that the sampling frequency must be at least twice the maximum input frequency. The filtered signal then passes through the delay line to a second low pass filter (at 15 kHz), which removes any clock signal residuals. This second filter includes a buffer amplifier to give the unit an overall gain of one. The output then splits into two paths; one is sent back to the input, to provide the reverb effect, the other goes to a final mixer via a switch. In the other position, the final mix can be varied from 'straight through' to full reverberation.'

The delay circuitry comprises two charge coupled devices (CCD's) with 1024 delay stages. The diagram right shows an example of the internal structure of a MOS CCD IC. The principle may be compared to a line of firemen



passing buckets of water from one end to the other — hence the name 'bucket brigade'. In electrical terms the 'buckets' are capacitors and the 'water' is an electric charge which is proportional to an instantaneous value of the input waveform — a sample. Each sample is stored briefly, then passed on to the next stage at the time of a clock pulse. Although each sample is stored for a very short time, at each stage, the time taken to 'clock' a sample from input to output can be as much as 50 mS.

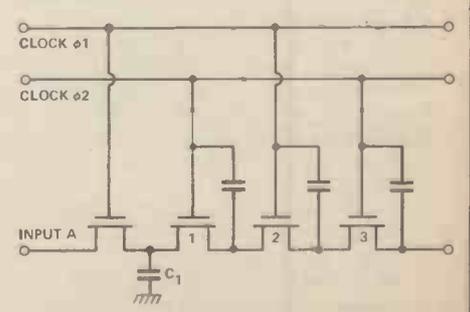

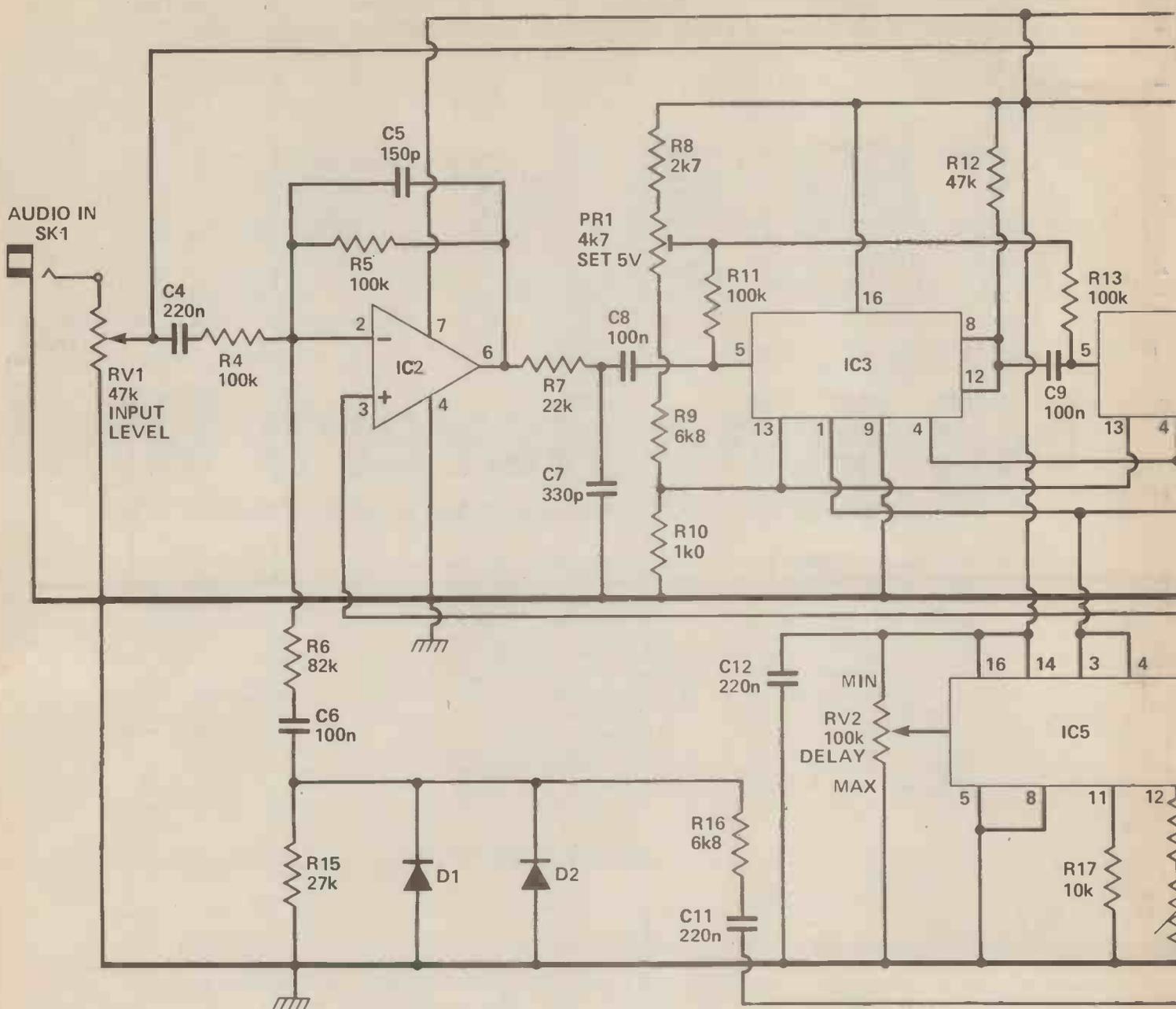

paths is a direct link from the input of the echo-reverb to the input of the mixer stage; the other path is via a variable signal-delay network. By varying the signal delay and then the mixture of direct and delayed signals, a variety of interesting effects can be obtained. Here are a few ideas to try:

- (1). With equal levels of direct and delayed signals, and a few milliseconds of delay, a 'double-tracking' or 'mini-chorus' effect is obtained. This makes a single input sound like a pair of independent but time-synchronised outputs. Thus, a single violin can be made to sound like a duet and a duet is made to sound like a quartet.
- (2). With a reduced level of delayed signal in the mix, and with a delay time of tens of milliseconds, a simple

echo effect is obtained. The audio sounds as if it were being played in a softly furnished room where there is a single hard wall or reflective surface, facing the sound source. The apparent size of this room is directly proportional to the milliseconds delay time of the echo unit, and is fully variable up to 50 feet (50 mS delay).

A standard feature of most echo units (including ours) is a Reverb facility. This allows a fraction of the output signal from the delay line to be fed back and added to the delay line input, so that you end up getting echoes of the echoes of echoes. By using only small amounts of feedback (often called 'Recirculation' or 'Regeneration' on commercial units), you get 'soft' reverb or, by adding lots of

feedback you get 'hard' reverb. A variety of impressive effects can be obtained from the reverb facility, as follows:

- (3). When equal levels of mixing are used with maximum (50 mS) delay and maximum feedback, the sounds seem as if they are being played in a large hard-faced cave or chamber. The apparent dimensions of this 'chamber' can be varied via the delay-time control, while the apparent 'hardness' of the chamber can be varied by altering either the mixing or reverb level controls. Thus, the apparent sounds can be varied from those of a hard cave, to a small church, or down to a large but softly furnished lounge.
- (4). When equal levels of mixing are used with short (a few mS) delays and a large amount of feedback, all

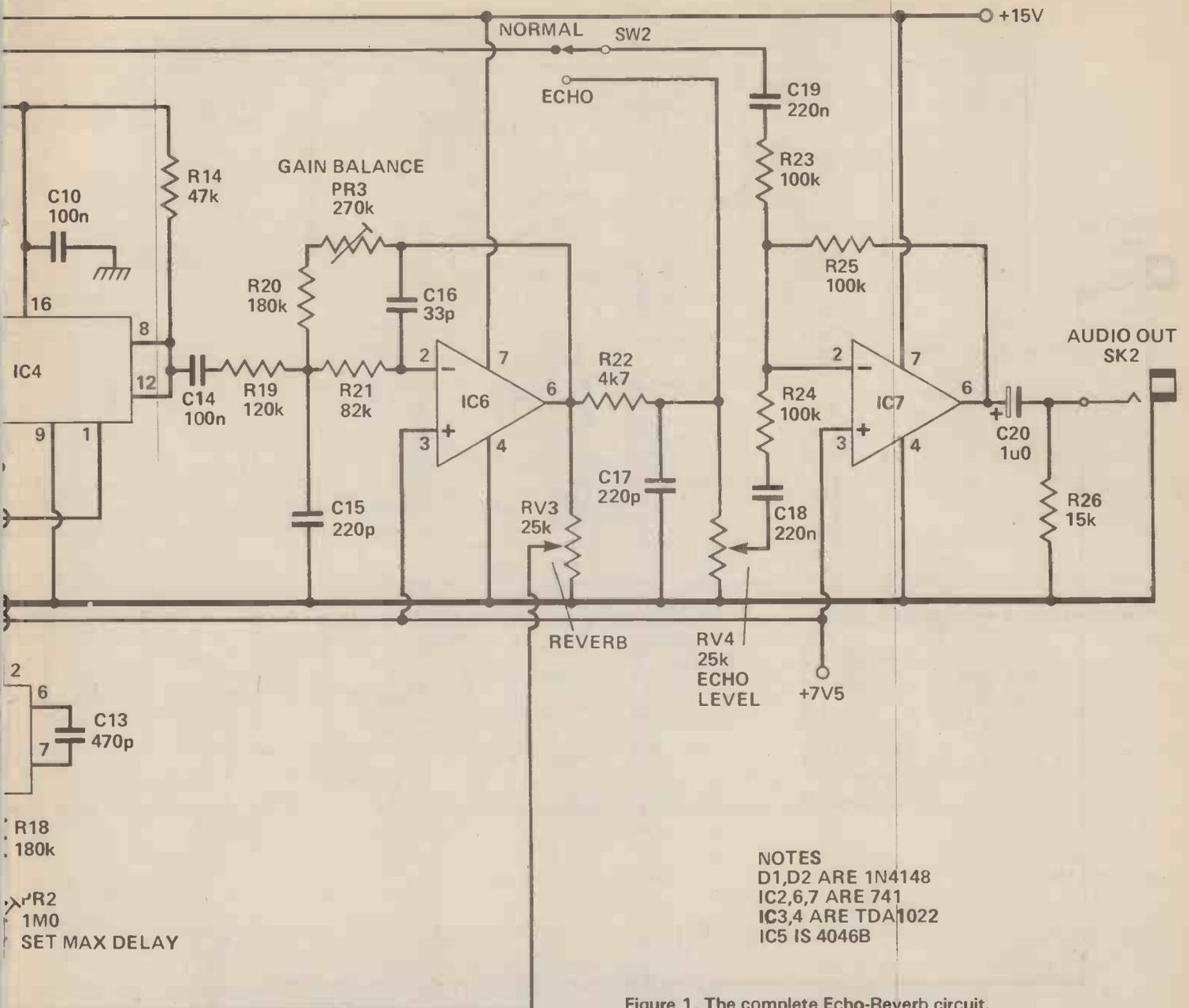


Figure 1. The complete Echo-Reverb circuit.

audio signals sound as if they are being played inside a small-diameter hard-faced pipe or drum. The apparent dimensions of the 'pipe' are variable via the time-delay controls and the apparent hardness of the 'pipe' is variable via the mixing or reverb controls. The sounds can therefore be varied from those of, say, a sewer pipe, to a dustbin or bucket!

### The Circuit

The principle of the echo-reverb unit is described in How It Works. Audio signals enter the unit via RV1 and split into two paths which are re-united again, near the output, via a low-distortion audio mixer (IC7). One of these paths is virtually a direct link from the input of the unit (RV1 wiper) to one

input of the IC7 mixer. Thus, by varying the delay time and the setting of RV4, a range of different echo times and characteristics can be added to the original audio signals.

A fraction of the buffered output of the delay line can be tapped off via RV3 and fed back to the input of the delay line via the IC2 mixer stage. This produces echoes of echoes, etc ('regeneration' or 'recirculation'), and is the standard characteristic of a reverb sound. The quality of the sound depends on the setting of RV3 (Reverb) and the delay time.

The delay line is formed by IC3 and IC4, a pair of series-connected TDA 1022 CCD (Charge-Coupled Device) "bucket-brigade" analogue ICs. They are clocked by a two-phase variable frequency

oscillator formed by IC5, a 4046B phase-locked-loop chip. The TDA 1022s are 512-stage delay lines, so our circuit uses a total of 1024 CCD stages. The delay time available from these chips is:

$$D = \frac{P}{2} \times S$$

where P is the clock-cycle period and S is the total number of delay stages in the line. Our prototype is set up so that the clock periods are fully variable (via RV2) from a minimum of 2.5  $\mu$ s (400 kHz) to a maximum of 60  $\mu$ s (16.6 kHz), thus giving a delay range of 1.28 ms to 30.7 ms. In practice, however, the delay times can be extended to 50 ms by adjusting PR2 to give a maximum clock period of 97.6  $\mu$ s (10.24 kHz) if some clock-signal breakthrough is acceptable


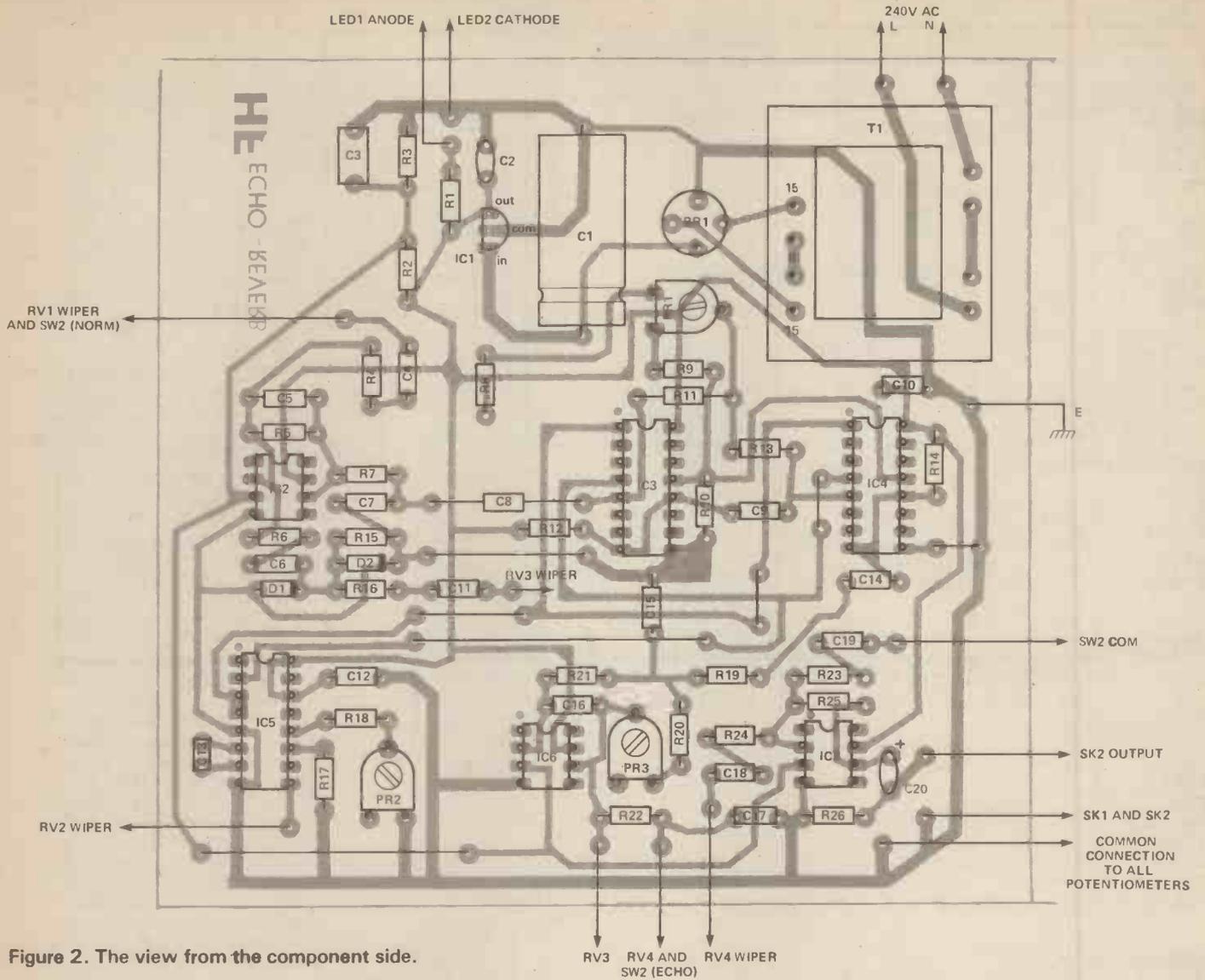


Figure 2. The view from the component side.

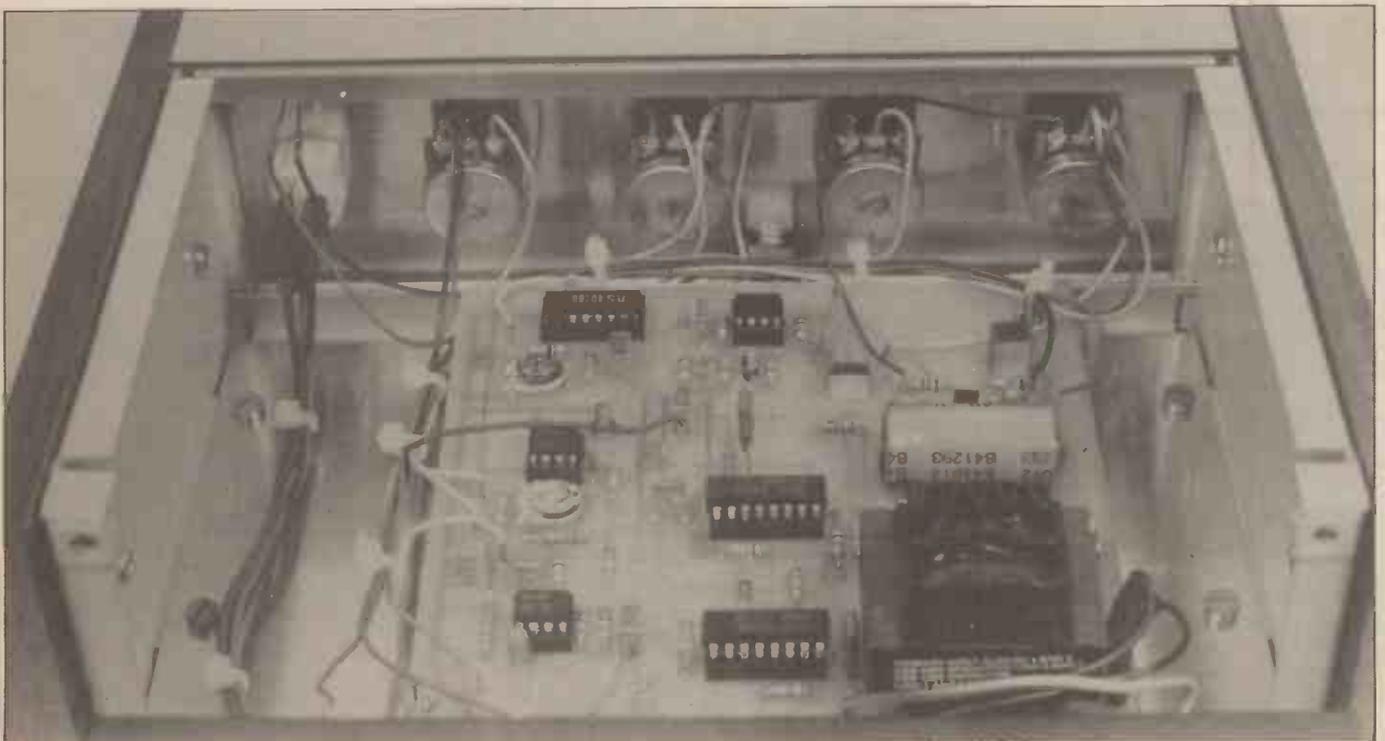

## Parts List

## RESISTORS

(all 1/4 W 5% carbon)

|                     |      |
|---------------------|------|
| R1                  | 1k5  |
| R2,3                | 1k2  |
| R4,5,11,13,23,24,25 | 100k |
| R6,21               | 82k  |
| R7                  | 22k  |
| R8                  | 2k7  |
| R9,16               | 6k8  |
| R10                 | 1k0  |
| R12,14              | 47k  |
| R15                 | 7k   |
| R17                 | 10k  |
| R18,20              | 180k |
| R19                 | 120k |
| R22                 | 4k7  |
| R26                 | 15k  |

## POTENTIOMETERS

|       |                        |
|-------|------------------------|
| RV1   | 47 linear carbon       |
| RV2   | 100k linear carbon     |
| RV3,4 | 22k linear carbon      |
| PR1   | 4k7 miniature pre-set  |
| PR2   | 1M0 miniature pre-set  |
| PR3   | 220k miniature pre-set |

## CAPACITORS

|                |                                |
|----------------|--------------------------------|
| C1             | 1000u 40V electrolytic (axial) |
| C2             | 10u 35v tantalum               |
| C3             | 680n polycarbonate             |
| C4,11,12,18,19 | 220n polycarbonate             |
| C5             | 150p ceramic                   |
| C6,9,14        | 100n                           |
| C7             | 330p polystyrene               |
| C8,10          | 100n polyester C280            |
| C13            | 470p ceramic                   |
| C15,17         | 220p ceramic                   |
| C16            | 33p ceramic                    |
| C20            | 1u0 35V tantalum               |

## SEMICONDUCTORS

|         |                                  |
|---------|----------------------------------|
| IC1     | 78L15 voltage regulator          |
| IC2,6,7 | 741 op-amp                       |
| IC3,4   | TDA1022 bucket bridge delay line |
| IC5     | 4046B CMOS phase locked loop     |
| BR1     | 50V 1A bridge rectifier          |
| D1,2    | 1n4148 signal diode              |

## MISCELLANEOUS

|       |                                       |
|-------|---------------------------------------|
| T1    | 15-0-15V 3VA PCB mounting transformer |
| SW1   | DPDT miniature mains rocker switch    |
| SW2   | SPDT miniature toggle switch          |
| Sk1,2 | Phono Sockets                         |

Case, PCB, fixing bolts, knobs etc.

BUYLINES . . . . . page 68

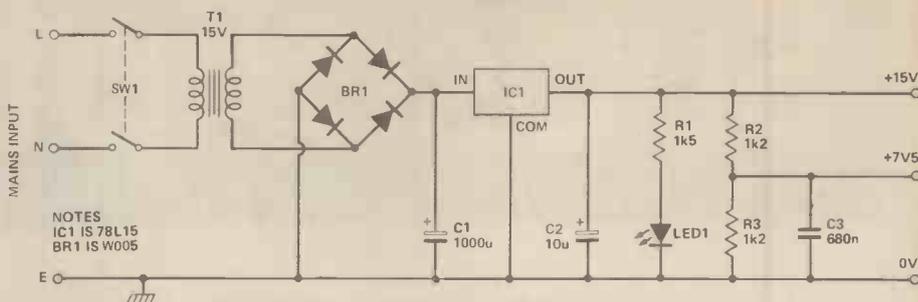


Figure 3. Circuit diagram of the regulated power supply.

on the output signal (see setting-up instructions, Max Delay Time).

When using CCD delay lines it is important that the clock frequency must be at least *double* the maximum audio signal frequency that will be used. The delay line output signal must be well filtered to cancel residual clock signals and the input to the delay line must be low-pass filtered, to avoid intermodulation problems by ensuring that the maximum input frequency is no higher than half the clock frequency. With these points in mind, the mixer IC2 with R7 and C7 are configured to give a 12 dB/octave slope, rolling off at 7kHz at the front of the delay line. IC6 acts as a 12 dB/octave, 15 kHz low-pass filter at the output of the line.

Final points to note about the circuit are that D1 - D2 - R15 - R16 are configured to give a degree of self-limiting on the reverb signals. This protects the delay line against destructive reverb overloads. The entire circuit is powered from a regulated mains-derived 15 volt supply via IC1 (Figure 3 above).

## Construction

Most of the circuitry for this project is built on a single PCB, and construction should, therefore present very few problems. Before you start, however, a word of warning: the circuit includes a high frequency clock generator which tends to produce a fair amount of RFI (Radio Frequency Interference). Consequently, you should build it into a metal box and take lots of care over RF screening.

Begin construction by fitting the seven wire links and the PCB-mounting mains transformer. Then proceed with the assembly of the remaining components, taking the usual care to observe component polarities, etc. Use sockets to mount the two delay-line chips (IC3 and IC4) and IC5; handle the chips with care, when fitting them into place.

When the PCB is complete, temporarily wire the unit to all control pots, switches and sockets, then set-up the pre-sets.

## Setting Up Procedure

The HE Echo-Reverb unit contains three pre-set pots which must be correctly adjusted to make the unit fit for use; once these have been set correctly initially, they require no further adjustment. The pre-sets (PR1, PR3 and

PR2) control the delay line biasing, the delay line loop gain and the maximum delay time, respectively. The setting up procedure is as follows:

**Delay Line Biasing:** With no input signal present, set all three pre-sets to zero, set SW2 to Echo Only, RV4 (Echo Level) to maximum and RV2 (Delay) to mid value. Connect a DC voltmeter between the +15 V line (+ve) and the wiper of PR1 (-ve). Then adjust PR1 for a reading of precisely 5 volts. Remove the meter. Now connect an audio (voice or music) signal to the input and check that it can be played through the unit without excessive audible distortion (ie the sound never becomes harsh).

**Delay Line Loop Gain:** With RV2 (Delay) set to mid-range but with RV3 (Reverb) and RV4 (Echo Level) set to zero, connect a voice-range (350 Hz - 3kHz) input signal of about 1 V peak-to-peak and monitor the output signal. Switch SW2 between the Normal and Echo Only positions, adjusting PR3 so that equal output levels are obtained in both positions (this test can be done with test gear or simply 'by ear', using a tape or disc signal source). When this adjustment is complete, set SW2 to the Echo Only position. Pass a music/voice signal through the system and use RV2 to check the Reverb sound is satisfactory.

**Max Delay Time:** Set SW2 to Normal, RV3 (Reverb) to zero, RV4 (Echo Level) to maximum (wiper at zero volts). Adjust PR2 while monitoring the output of the unit and note that high-pitched tone (whistle) is produced when PR2 is turned beyond a certain point. Now pass a voice signal through the unit; note that the echo effect is obtained, then trim PR2 to find a compromise setting at which a good delay (echo) is obtained with minimum acceptable intrusion from the 'whistle' sound. Finally, check that the delay can be varied over a wide range (roughly 2 mS to 50 mS) via RV2 and the reverb can be varied with RV3.

The setting-up procedure is now complete and the unit can be cased and made ready for use, as already described.



# ELECTRONIC REVOLUTION

Part One of our new bi-monthly series following the history of the Electric Society — from Volta to Video.

IF you had to name the great, central pillar of modern society, the one technological aid it couldn't do without, it would have to be electricity. Coal had its day back in the 19th Century and, though it seems to be having something of a renaissance now, this is only as a means of generating electricity. Oil rules the world's economy, but only because so few hands have the power to turn the taps off. Nuclear power is the coming force we are told, but it has been coming for the past quarter-century without showing much sign of actually arriving. Electricity is the great common thread which binds together the various primary sources of power. The world might survive an oil embargo, but just try to imagine the darkness and confusion that would fall on the face of the land if some genius hit upon a way of turning off the electricity worldwide: no lighting, very little heat, (even North Sea gas is driven by electric pumps), no radio, no TV, no computers, no telephones, no industry and very little agriculture. You only have to look at the few large *partial* supply failures of the past two decades to see the sort of chaos which would descend as the generators slowed down and stopped: the famous New York blackout one night in 1965, or the power cuts of February 1974 during the Miner's strike. Or, if you want a practical demonstration, try reading the rest of this article by the light of an unpressurised paraffin lamp, which is the best you would have had in most English villages until the late 1940s.

Try as they might, no one has come up with a cheaper, cleaner and more easily handled form of power transmission for applications other than road and air transport. Now, as we get towards the end of electricity's second century, the silicon chip and the society it is creating looks set to make us more, rather than less, dependent on the movements of electrons — invisible to all and still rather mysterious to most.

Few people these days, it is true, would go as far as James Thurber's aunt, who used to roam around the



Cooke and Wheatstone's five-needle telegraph, first installed alongside the Euston-Camden railway and later used by the Great Western Railway for communications between Paddington and West Drayton.

house sticking light-bulbs into empty sockets in case the electricity dripping out of them formed dangerous, invisible puddles on the floor. Nor are there quite as many people, as there once were, who replace fuses with stout copper wire saying that they can't understand why folk use that inferior silvery stuff you buy in Woolworths! But even if electricity is not regarded by people at large with the same superstitious horror as nuclear energy (though the author did once see a poster saying "Ban Electricity NOW") it is still a rather strange and unfathomable force — which makes you realise just how strange it must all have seemed when the first serious experimenters began their work, back at the beginning of the 19th Century.

Electricity has been with us, now, for just over a century as a public utility. But, it took a hundred years of trial and

error and laborious experimentation before that to turn it from a useless scientific curiosity into the driving force of the second Industrial Revolution. That movement, beginning in the 1880s, turned the USA and Germany into great industrial powers because they hitched themselves to it but began Britain's long, slow decline because she took it up only half-heartedly and late. The century before 1880 produced some remarkably far-sighted inventions, projects far ahead of their time like Davidson's electric locomotive or the transatlantic telegraph of 1858. But, on the whole, progress was slow, a hesitant, haphazard clearing of the runway for the great electrical take-off at the end of the century.

## Myth and Magic

Ever since men first began to wonder

about the world around them, they had noticed some inexplicable happenings which could best be put down to witchcraft or angry gods. Lightning was the most spectacular, of course, but the first Stone Age settlers in South America must soon have learnt to steer clear of a certain clumsy-looking, sluggish river-fish. As early as 321 BC, the Greek natural philosopher Theophrastus remarked on the strange attractive properties of amber — though he couldn't explain them. The Chinese seem to have used lodestone compasses about 800 AD and, by the 1560s, scientists were familiar enough with large artificially-made permanent magnets for the surgeon Ambroise Pare to have had the brainwave of using one to extract a steel splinter from a patient's eye. It was, presumably, about this time, as seagoing ships grew larger, that shipwrights learnt the inadvisability of using copper fastenings near iron nails. But it was left to Elizabeth I's Court Physician, William Gilbert, to tie some of these phenomena together in his treatise "De Magnete" of 1600 in which he coins the word "electricity", associates static electricity with magnetism and divines that the Earth is a huge magnet. It also seems that Gilbert constructed the first recorded static generator, direct ancestor of the 50-foot diameter Van der Graaf machine currently used in nuclear research at Harwell.

Speculation about the nature of electricity — or rather, "the electricities", since no one had yet linked static, magnetism and lightning conclusively together as aspects of the same thing — went on in a desultory way for the next two centuries. It was not until the last two decades of the 18th Century that serious investigation was able to begin and the Electric Machine became something more than a toy for amusing the ladies at a philosophical society lecture. Franklin made his famous kite-flying experiment to investigate lightning — and his less famous, inspired but incorrect guess at polarities, which has bedevilled electronics ever since. In Italy, the two Professors Galvani — the frog's legs man — and Count Volta worked away at the problem of chemical electricity until, in 1800, Volta was able to produce his first pile battery. The world's men of learning now had their first controllable, storable, measurable source of electricity and the experiments began in earnest.

Sir Humphry Davy gave his famous arc-light demonstration in 1809 and, eleven years later, in 1820, Professor Oersted of Copenhagen made the momentous discovery that a compass needle could be deflected by an electric current passing through a



Part of the Gauss and Weber telegraph system.

wire. It was left to Michael Faraday, in the summer and autumn of 1831, to make the imaginative leap by standing Oersted's 'current + wire + magnet + movement = current'. It may seem obvious, now, but it was a stroke of genius at the time and Faraday's demonstration of a crude magneto-electric generator to the Royal Institution on 24 November 1831 marks the birth of the electronic age.

The child was born, perhaps, but it was remarkably slow a-growing during the half-century after Faraday's discovery. An increasingly powerful range of magneto generators were built in Europe and the USA during the 1830s and 1840s, but the trouble was that nobody really had much idea of what to do with the current they produced. Arc lighting developed slowly during the middle decades of the century and a breed of wandering electricity generators grew up (Samuel Crompton was one of the first), roaming Europe with mobile steam-driven apparatus to illuminate railway tunnelling work, circuses and fairgrounds. But arc lighting was too harsh and too expensive to rival colza oil or kerosene as a source of domestic illumination. A few avant-garde scrap-metal dealers invested in electro-magnets for lifting and Birmingham factory proprietors found electro-plating an excellent way of poshing up cheap and nasty tableware, while rheumatism sufferers were made momentarily forgetful of their aches by the even worse pains resulting from patent Therapeutic Electrical Machines (which could still be seen at country fairs in the 1930s) Of course, the demand for lighthouses pushed forward the development of large generators, like Clarke's 2 kW machine which supplied the one at the South Foreland, near Dover, in 1858, but it was all a primitive, haphazard business, this early public electricity supply.

The men of science were still only beginning to grope their way towards an understanding of this mysterious force, so it is hardly surprising that theoretical knowledge among the early practitioners was sketchy in the

extreme. It was not until the 1860s, for instance, that any idea began to emerge of there being a distinction between force and current — the power of the early generators was reckoned by the size of the spark, or the loudness of the howls, which they produced. Power requirements were judged, rule-of-thumb fashion, by the number of acid-cell batteries needed to make the thing work. Ammeters, where they existed, were simply calibrated by the man who built them without any reference to a common scale. As we have seen, it took a very long time to dispose of the notion of several different, independent kinds of electricity. Electricity supply was plagued well into the 1890s by a persistent folk-belief that direct current was not only less dangerous than alternating but, in some curious way, a different kind of power altogether, a belief which led to all the early generators being fitted with commutators to convert their output to DC. In fact, some historians go so far as to say that the obsession with DC over AC held back the development of industry by a good half-century.

All the same, there were some remarkably far-sighted experiments made in these early days, projects like Davidson's battery-powered electric railway locomotive of 1842 which managed to reach 40 mph on a run between Edinburgh and Glasgow, only to be smashed up at the end of the journey by enraged steam-engine drivers who were frightened that it would take away their living. They need not have worried, though. Old King Coal was to remain unchallenged on his throne for another fifty years as the main source of power for the railways and factories. It was not until the self-taught Serbian inventor Nikolai Tesla developed phase-induction, at the end of the 1880s, that electric motors were able to start up under their own power and drive the trams which were to do so much to change the geography of European and American cities, around the turn of the century.

### First Light

If a public electricity supply industry was to develop, in the way gas had developed early in the 19th Century, it would have to find itself some simple domestic service which it could perform more cheaply than any of the alternative forms of energy then on offer. Domestic lighting was the obvious candidate and, throughout the late 1870s, Crompton and Swan, in Britain, and Edison in the United States worked feverishly to develop a cheap, mass-produceable incandescent light bulb. They fiddled

about with filaments of paper, horse-hair, silk, bamboo and platinum until — just about simultaneously, in the autumn of 1879 — both Swan and Edison hit upon the trick of making a bulb which would last more than a few hours — exhausting the air in the bulb while the filament was hot, in order to get rid of the combustion gases. A vicious patents battle ensued — Edison was a devil for litigation — but from 1880 onwards, progress was as rapid as it had been sluggish over the previous fifty years. Edison, being a most unusual combination of inventive genius and shrewd businessman, set up his first public supply power station at Pearl Street, New York City, in September 1882. It served 85 buildings at first but, by the end of 1884, no less than 60,000 lamps were connected up to the supply.

In Britain, things were done more haphazardly and Godalming, rather than London, had the honour of being the first town to go electric, in September 1881. The local gas company had attempted an early OPEC — unilateral price-hike. The town council demurred and turned, instead, to a pair of wandering electrical entrepreneurs, Messrs. Calder and Barrett, who undertook to light the streets from a mobile steam generator and, later on, from an old water mill. The new arrangement was not a technical success. The lights were connected in series, like those on a Christmas tree, with the result that those nearest the generator were noticeably brighter than those further away, while a single blown bulb plunged the whole town into darkness. Nor was it much better off financially and in May 1884, it closed down, the brothers Siemens (who had taken over the contract) having been unable to find the 500 domestic subscribers, at £3 per annum, who were necessary to make the project break even. Later, town supply systems were more successful. London got its Grovesnor Gallery, Holborn and Kensington Court Power stations in the early 1880s, each with an output of about 60 kW and equipped with standby batteries to provide off-peak power in the small hours, so that the machinery could be oiled and cleaned.

Despite gas lighting's new lease of life, thanks to the invention of the incandescent mantle in 1880, electric lighting caught on rapidly with the better-off and from the early 1880s onwards, there appeared a succession of gadgets to make use of this new, clean, convenient form of power: kettles, flatirons, hotplates, and heaters, all ornately decorated in the fashion of the time and all guaranteed to cause today's BEAB safety inspec-

tors a collective heart attack. True, with the power supply pitched at 110 volts, in most cases, the danger wasn't too great, but a cavalier attitude to safety lasted well into the 240 volt era, in many countries. Most of Eastern Europe still does without earthing, which keeps the fire brigades busy, if nothing else, and the French were long famous for the nonchalance with which they stapled bare wires around the attics of their houses. Only a few years ago, a British engineer working on an Anglo-French joint construction project in the Middle East was watching a French electrician wiring up a street lamp. Horrified by what he saw, he remarked that if anyone broke into the control box they would be killed for sure. "Ah M'sieur" said the electrician, "You do not understand. In France, it is forbid the public to open these boxes."

### AC/DC

By the end of the 1880s in Europe and the USA, demand for electricity was fast outstripping what the small, city-centre power stations were able to supply. The answer was to build out-of-town, but this meant high transmission voltages, if the method was to be economically worthwhile. High voltage meant transformers, to step it down to domestic supply level, and transformers — unfortunately for Edison and the other champions of direct current — meant AC, unless they wished to tinker with alternators and commutators on either side of the iron core. The result was de Ferranti's Deptford power station, in 1891, which drove 10,000 volts an unprecedented 8 miles along underground cables to London's centre. Edison published pamphlets to warn the public that AC and DC were different things, the former being "fit only to power the electric chair", but the battle was lost, especially as Parsons steam turbines came to replace the inefficient and failure-prone reciprocating engines in the power stations, making accurate frequency regulation possible for the first time. However, this all took time and, in the mid-1920s when the Government was trying to unify the electricity supply system, the UK still had over 200 DC town supply systems plus no less than 17 different AC frequencies. At the start of the First World War, only one British home in ten was on the mains and by the outbreak of World War Two the figure had barely reached one household in two.

So it was not in the area of public service supply that electricity established itself in the public consciousness during the 19th Century. Al-

though the power used was much smaller, it was the telegraph and its younger near-cousin, the telephone, that made the Victorian man-in-the-street familiar with electricity and built up the manufacturing and operating skills which were to be drawn upon by power engineering at the end of the century. Where would the electricity supply companies have been in the 1880s, for instance, if the telegraphs hadn't first inspired the factories which specialised in cables, insulated with that now-forgotten 19th Century wonder material, gutta-percha?

Where electric power supply was concerned, the trouble in the early 1830s was that, while people knew more or less *how* to do it, they couldn't find any really convincing reason *why*, a question which would be answered only when Swan and Edison came along with the electric light bulb. But with the telegraph, things were very different; the need was there, ready-made, just waiting for electricity to come its way.

### Long Distance Information

Telegraphing information over long distances had excited a great deal of interest since the late 18th Century. In France, a semaphore telegraph system, developed by one M. Chappe, had been crucial during 1792-93 in enabling the Revolutionary government in Paris to move its rattle-taggle armies about the country to beat back the invading Allies. As is so often the case with inventors, they were so grateful to M. Chappe afterwards, that the poor man cut his throat in despair. However, the British Admiralty was more appreciative and soon set up its own chain of telegraph towers which, on one famous occasion, got a message to Portsmouth and back in three minutes flat. But these telegraph systems were slow, useless in fog or at night and so expensive to man — one from Warsaw to Moscow needed 1,300 men on duty at any one moment — that only the most urgent government business could justify them. They never really caught on though the Admiralty, conservative as ever, kept its semaphore network going well into the 1850s on the ground that fiddling about with copper wires was damned un-seamanlike.

It had been known for some time that, among its many other properties, electricity travelled at amazing speeds. A French *savant* had proved as much in the 1760s, by connecting a circle of 200 Carthusian monks holding hands to a static generator (what a pity that photography had not been invented). So it is scarcely surprising that, by 1830, some 30-40 different

electric telegraph systems had been invented; some were merely ingenious, like Soemmering's electrolytic telegraph of 1810 (the operator watched the lettered electrodes in a glass tank of water to see where the bubbles formed) and some very promising, like the Russian diplomat Baron Schilling's electro-magnetic telegraph of 1825, the first to use a simple code. What the telegraph needed, in order to become a practicable system, was a large-scale non-governmental user to furnish the sort of market which would make it worthwhile for someone to develop a cheap, fast, simple method. That customer materialised in the shape of the railways, which were spreading across Britain and the Eastern USA in the mid-1830s. They had soon found that they would need some quick and reliable method for all-weather, 24-hour long-distance signalling if the countryside wasn't to resound with the crunch of colliding locomotives. They also needed (people often forget) common time for their trains to run to, something which simply hadn't existed in the pre-telegraph days when every time for their trains to run to, something which simply hadn't existed in the pre-telegraph days when every town set its clocks to its own midday, with the result that noon at Plymouth was 12.20 GMT. In Britain, the answer was provided by an invalided Indian Army subaltern and half-hearted medical student named William Cooke, who saw Schilling's telegraph at Munich and rushed home to team up with the scientist Charles Wheatstone in developing an electric telegraph to sell to the railways.

Though slow by later standards, their alphabetic needle-deflection apparatus could be used by an untrained operator. It was installed between Euston and Camden stations, in June 1937, and two years later a line was rigged up alongside the Great Western Railway between Paddington and West Drayton. Cooke and Wheatstone soon parted company amid great bitterness, but the idea of the electric telegraph remained, first coming into the headlines in January 1845, when a notorious murderer was arrested at Paddington after a message from the booking office at Slough station — "hanged by a copper wire" they said. The real breakthrough came, also in 1845, when the minor portrait painter Samuel Morse invented his code-based key telegraph which, in the end, did as much to open up the American West as the railways themselves (though you can't help wondering whether all the operators did, in fact, wear eyeshields and sleeve-bands as the TV Westerns portray them).



Baron Schilling's magnetic needle detector.

The first telegraph line was laid across the English Channel at the end of August 1850. So, the age of international telecommunications began — though it was cut off rather abruptly the next morning, when a fisherman hauled up the fragile unarmoured wire that was fouling his anchor and hacked off a length of this queer, gold-filled seaweed for a souvenir. Later attempts were more successful and in 1855, the line laid beneath the Black Sea from the Allied HQ in the Crimea to link up with the overland cable at Constantinople provided dramatic proof of the advantages of electric telegraphy. The British could get a message from Sebastopol to London in a couple of hours while the War Ministry in St. Petersburg had to wait weeks for news to come on horseback, across the steppes. In fact it is said that they ordered the London "Times" to find out what was going on at the front. It was only a matter of time before someone attempted a transatlantic link and, after several frustrating failures, the American entrepreneur Cyrus Field succeeded in laying a cable between Ireland and Newfoundland in August 1858 — almost a miracle in view of the primitive technology and crude theoretical knowledge available to him. The link failed after less than a month of garbled, fitful operation, probably because the project's scientific adviser had insisted on using 2,000 volt spark coils to try to ram messages along the thin wire, thus burning out the insulation.

Further attempts were made, as business got back to normal after the American Civil War, and success was finally and permanently achieved on 27 July 1866, when the end of the cable was brought ashore from the vast, redundant passenger vessel the "Great Eastern" — the only ship in the world large enough to carry the amount

of cable necessary for the job. From then on, it was merely a question of extending the telegraph around the world. Technical improvements were few, until the advent of Frederick Creed and the telex machine in the early 1900s. In 1902, Creed found telegraph paper-tape messages being prepared, exactly as they had been in 1860, by the operator pouding three metal plungers with a rubber-tipped stick held in each fist, a process which led to a crippling occupational illness called Telegraphist's Wrist.

### Dirty Deeds

The possibilities of the copper wire were not exhausted (for the time being) until the late 1870s when two inventors arrived — once again simultaneously — at a solution to the problem of transmitting human speech down the wire. This time it was a real photo-finish with Alexander Graham Bell and Elisha Gray registering their reed-and-electro magnet telephone systems at the US Patents Office within hours of each other, on 14 February 1876. The result was a long and nasty lawsuit which was only resolved by the indefatigable Thomas Edison stealing both parties clothes with his carbon diaphragm mouthpiece, the ancestor of the modern telephone. The Strowger automatic telephone exchange was invented, some twenty years later, by a New York undertaker who had been brought to the verge of bankruptcy by an unscrupulous rival, who had bribed an exchange girl to route calls to Strowger through to his firm instead! With that, the telephone and telegraph systems had achieved very much the shape they still have, eighty years later, on the verge of the digital telecoms era.

The telegraph brought about drastic changes in the world. Newspapers, as we know them today, were built up around the telegraph office; the "Daily Telegraph" acknowledged as much in its title, when it was founded in 1855. In international relations, crises grew more difficult to handle, if anything, as the ambassador declined from being a minor potentate, acting on his own initiative, into a kind of decorative monkey at the end of a wire. The world grew a smaller place, but it still comes as something of a shock to remember that in September 1914, Admiral von Spees German Pacificsquadron could be warmly greeted and sold supplies by the French community in the Marquesas Islands who, being hundreds of miles from the telegraph lines, were unaware that France and Germany had been at war for nearly two months. It was not until wireless telegraphy came along that instant worldwide communication began to make the Global Village, and Global Village Idiots, a possibility. **HE**

### SUPER HI-FI SPEAKER CABINETS

Made from an expensive Hi-Fi outfit — will suit any decor. Resonance free. Cut-outs for 6½" woofer and 2½" tweeter. The front material is Dacron. The completed unit is most pleasing. Supplied in pairs, price £8.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.00 the pair.



### GOODMANS SPEAKERS

6½" 8 ohm 25 watt £4.50. 2½" 8 ohm tweeter. £2.50. No extra for postage if ordered with cabinets. Xover £1.50.

### UNIVAC KEYBOARD BARGAIN

50 keys, together with 5 miniature toggle switches all mounted on a p.c.b. together with 12 i.c.'s, many transistors and other parts. £13.50 + £2.00 post.

This is far less than the value of the switches alone. Diagram of this keyboard is available separately for £1.



### SOLENOID WITH PLUNGER

Mains operated £1.99  
10 — 12 volts DC operated £1.50.

### POPULAR KITS

#### 3 - 30v VARIABLE VOLTAGE POWER SUPPLY UNIT

With 1 amp DC output, for use on the bench, students, inventors, service engineers, etc. Automatic short circuit and overload protection. In case with a volt meter on the front panel. Complete kit £13.80

#### IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — complete mains operated kit, case £11.95 post £2.00

#### MORSE TRAINER

Complete kit £2.99.

#### DRILL SPEED CONTROLLER

Complete kit £3.95.

#### MAINS POWER SUPPLY

Gives any voltage from 3v to 16v at up to 300mA. Complete kit less case £1.95. Case 90p.

**OUR CAR STARTER AND CHARGER KIT** has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage whichever suits you best. Price £12.50 + £3.00 post.

### BUMPER BARGAIN PARCEL

10 kilo of unused parts. Minimum 1000 items. Includes — relays, switches, motors, drills, taps and dies, thermostats, neons, i.f. coils, oscillator coils, variable condensers, variable resistors and at least one each of the following: panel meter, timer, thermal trip, and other expensive items. Individually would cost well over £100. Yours for only £11.50 + £3.00 post.

### MILLIONS OF HOMES WILL BE BURGLED THIS SUMMER — SAY THE EXPERTS

Don't let yours be one of them. Install our burglar alarm. Install our burglar alarm. Complete kit includes 6" external alarm bell, mains power unit, control box with key switch, 10 window/door switches, 100 yards of wire. With instructions £29.50.

### TINIEST MICROPHONE

Not much bigger than a pea, 600 ohm condenser type. Ideal for bugging and similar applications. 50p each or 10 for £4.50.

### LEVEL METER

Size approximately ¾" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.



### THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pod which can be immersed in an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

### 3 CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by ¼" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form or £25.00 assembled and tested.



### ULTRA SMALL 12v RELAYS

Single pole gold plated contacts. Tubular construction, 17mm long 10mm dia. Ideal for models, PCB or freemounting. £2.30 ea.

### MINATURE PLUG IN RELAYS

12v operated. 3 changeover. £2.45, base 45p.  
12v operated. 2 changeover. £1.87, base 35p.

## THIS MONTH'S SNIP

### ROTARY WAFER SWITCHES

5 amp silver plated contacts. ¼" shaft, 1" dia. wafer.

Single wafer types, 29p each, as follows:

1 pole 12 way    2 pole 6 way    3 pole 4 way  
4 pole 3 way    6 pole 2 way    4 pole 3 way

Two wafer type, 59p each, as follows

2 pole 12 way    4 pole 5 way    4 pole 6 way  
6 pole 2 way    8 pole 3 way    12 pole 2 way

3 wafer types 99p each.

3 pole 12 way    6 pole 5 way    6 pole 6 way  
9 pole 4 way    12p 3 way    18p 2 way

### EXTRACTOR FAN

Mains operated — ex-computer

5" Woods extractor £5.75, Post £1.25.

5" Plannair extractor £6.50, Post £1.25

4" x 4" Muffin 115v. £4.50, Post 75p.

4" x 4" Muffin 230v. £5.75, Post 75p.



### 8 POWERFUL BATTERY MOTORS

For models, maccanos, drills, remote control planes, boats, etc. £2.95.

### TAPE PUNCH & READER

For controlling machine tools, etc, motorised 8 bit punch with matching tape reader. Ex-computers, believed in good working order, any not so would be exchanged. £17.50 pair. Post £4.00.



### MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 — 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

**FREE** Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

### 12V FLUORESCENT LIGHTING

For camping — car repairing — emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer an inverter for 21" 13 watt miniature fluorescent tube. £3.45. (tube not supplied).



## FREE OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

### TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox — all electronic parts and circuit. £2.30. (not licenceable in the U.K.)

### RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit. (not licenceable in the U.K.)

### FM RECEIVER

Made up and working, complete with scale and pointer needs only headphones, ideal for use with our surveillance transmitter or radio mike. £5.85.



### VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case but we can supply a plastic base £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

### STEREO HEADPHONES

Very good quality, 8 ohm impedance, padded, terminating with standard ¼" jack-plug £2.99 post 60p.



### TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs. £2.50.

### DELAY SWITCH

Mains operated — delay can be accurately set with pointers knob for periods of up to 2½hrs. 2 contacts suitable to switch 10 amps — second contact opens a few minutes after 1st contact. £1.95.



### MOTORS FOR ROBOTICS

If it's a toy robot you are making then one of our eight battery motors (see centre column) may do. If it's a bigger one, however, then see below. If still not big enough then enquire — we have larger motors but these are usually mains driven.

### 12v MOTOR BY SMITHS

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3½" long by 3" dia. These have a good length of ½" spindle — price £3.45. Ditto, but double ended £4.25.



### EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to ½ h.p., so it could be used to power a go-cart or to drive a compressor, etc. etc. £6.90 + £1.50 post. (This is easily reversible with our reversible switch - Price £1.15).

### SPIT MOTORS

These are powerful mains operated induction motors with gear box attached. The final shaft is a ½" rod with square hole, so you have alternative coupling methods — final speed is approx. 5 revs/min, price £5.50. — Similar motors with final speeds of 80, 100, 160 & 200r.p.m. same price.



### REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Framco Company this is a very robust motor, size approximately 7½" long, 3½" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

- 1 Framco motor with gear box
- 1 manual reversing and on/off switch
- 1 push to start switch
- £19.50 plus postage £2.50.
- 1 x 100w auto transformer
- 2 limit stop switches
- 1 circuit diag. of connections.

# J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU.

Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £10, add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclaycard orders phone Haywards Heath (0444) 454563. Bulk Orders: Write for quote. Delivery by return.

# SCALING the Hi-Fi HEIGHTS Part 5



The final installment looks at adding a cassette deck to a basic system.

CASSETTE RECORDERS appear in just about all rack systems, these days, and continue to outsell tuners as the most popular addition to a record player system. Home recording of LPs and singles (with the appropriate license of course!) is a widespread and popular method of enlarging a music collection; in addition there is the advantage of taping an LP-length selection of the best tracks of several records or artists. Miss out the boring bits, to order!

Reel-to-reel tape recorders have all but faded from the home hi-fi scene. There are only a handful of models remaining and these tend to be at the 'top-end' of the market, with prices in the £500+ bracket. They are outside our scope at present, as they are an unlikely addition to a first system.

## Basic Theory

A music signal is recorded on to tape by the process of magnetisation. It is mixed with a high-frequency sinewave, at around 100-170 kHz, and fed to a coil and magnetic pole-piece arrangement, past which travels a magnetically coated plastic strip — the tape! The high-frequency signal is referred to as the 'bias', while the coil and poles form the 'recording head'.

Bias is required to ensure that the amount of magnetisation of the tape particles is directly proportional to the audio signal strength.

Even so, the music has to be passed through an equalisation stage, both before and after recording, to get a 'flat' response. This compensates for the varying sensitivity of the tape at different frequencies and — in theory, anyway — the equalisation circuitry produces the same result in all tape recorders, regardless of manufacture. Tapes recorded on one machine should be able to be replayed satisfactorily on another!

Years ago, the equalisation was set to produce large amounts of bass cut (7 dB at 50 Hz) but, with the ever increasing quality of tape and improved noise reduction systems, this has been substantially modified to suit the new, better quality tapes.

## Biased View

Too little bias, for a given tape, results in lacking of frequency extremes, ie bass and treble. As the amount of bias is increased, treble response improves rapidly followed by the bass, some dBs of bias strength later. Unfortunately, there is not a single level which optimises both HF and LF. To compound matters still further, distortion and some noise effects are also highly dependent upon bias level.

A compromise level is usually selected, but this still results in a considerably reduced HF level, a problem which is overcome by boosting the top end of the signal before recording (pre-equalisation).

## Reducing Noise

Partially because of this high frequency boost, signal-to-noise levels (ie, how much louder the music appears above the unwanted hiss and hum, etc) would be unacceptable by hi-fi standards without some method to control tape hiss.

The most popular system is the Dolby 'B' noise reduction system, which is to be found on 99% of all cassette machines sold today. It operates by 'sloping' the frequency response to a degree dependent upon the signal level, so that the treble signal is boosted still further before recording and then cut by exactly the same amount upon replay. Since the noise added during recording is nearly all above 5 kHz, the cut in response upon replay will not only balance the boost in the recorded signal, but will cut down the added noise by the same amount — usually around 10 dB. The difference is

dramatic, and sufficient to take the cassette medium to an acceptable noise performance.

A recent development is the Dolby C System which is claimed to not only improve noise performance still further, but to also increase the dynamic range (the difference between the loudest and the softest signal replayable) of the recording machine.

Of late, the dbx company have been pushing their 'compressor' method of reducing noise on tape quite hard and have succeeded in having it adopted by some professional machine manufacturers. The system operates differently to the Dolby variations, in that it compresses, or squashes down, the entire signal before recording, considerably reducing the variations in signal level. Upon replay the original differences are restored to the signal (expansion) once more pushing tape noise down to irrelevant levels. Much greater reduction in noise is possible with dbx, but it continues to have problems producing a playback as smooth as that which went into the record head!

There have been variations upon these themes; Philips and JVC have both produced their own noise reductions systems neither of which are compatible with Dolby B. Interestingly, the JVC machine carried the Dolby system alongside their own 'ANRS' system.

## Performance Parameters

There are a fair number of specifications connected with tape machines and very few are irrelevant. Some are accorded an importance they do not actually possess — much in the same manner that a particular feature of an amplifier, operating class for example, can be made into an advertising lead story for no other reason than that of convenience. We will be taking a brief look at the specs concerned with performance and working through

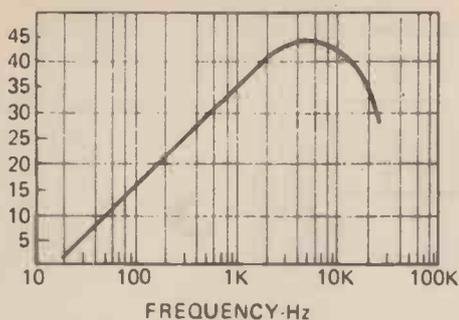


Figure 1. The frequency response generated by a tape head. This is the curve produced by recording a set of frequencies which have identical levels. As you can see, they don't stay that way!

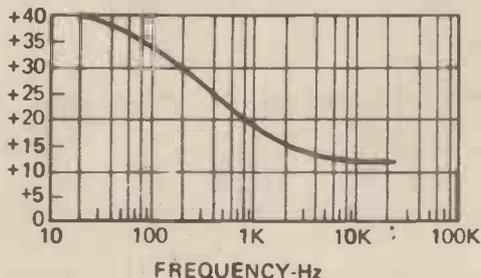


Figure 2. This is the equalising response required by the tape pre-amp circuitry to compensate for the curve of Figure 1. This will also help reduce the noise generated by the machine.

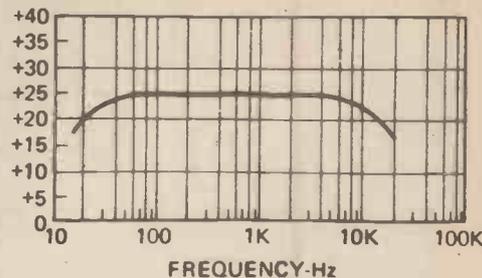


Figure 3. The result of combining the responses of Figures 1 and 2. A much more linear signal is recorded onto the tape.

the pros and cons of the different tape types on the market.

**Ratios of noise:** With whatever noise-reducer it has operating, a cassette machine should be able to better 65 dB (weighted) signal-to-noise ratio. What happens with the noise reduction out is really irrelevant, unless you happen to enjoy hiss!

**Responding to frequencies:** As the limits of human hearing are approximately 20 Hz-20 kHz, it is the aim of all hi-fi equipment to reproduce this range as faithfully as possible. Early cassette machines and tapes could hardly better 10 kHz as an upper limit of performance. Nakamichi took the art to 20 kHz before anyone else, but have since been followed beyond 15 kHz by the majority of manufacturers with metal and/or C<sub>02</sub> tapes. A good tape deck, these days, should achieve 15 kHz without too much strain. When choosing a tape deck, pay particular attention to the manner in which it replays the extremes of the frequency spectrum; all too often, an incorrectly adjusted machine will produce an uneven bass end.

**Speedy Variations:** Speed control of the tape itself is obviously of prime importance. Wow and flutter will be as noticeable on cassette machines as it is on record decks. On all but the most

budget of budget models there should be no audible speed variations. As long as the peak W + F lies below 0.2%, all will be well. (Wow is the term applied to long-term speed changes and flutter refers to short-term, rapid oscillations in speed). Some of the better (ie higher priced) decks produce figures in the order of 0.05%, some four times better than the acceptable threshold.

**Distorting the Truth:** There are two types of distortion produced by a cassette deck; that generated by the electronics, and the odd harmonic distortions produced by the act of recording onto the tape itself — some intermodulation distortion (one frequency interfering with another) is also added to an signal by the process of recording. The electronics will add something of its own but, if the specified input levels are kept to, then the additions will be minimal. If they are exceeded, then, just like the free-standing amplifier, the deck will 'clip' the tops off the incoming waveform, distorting it badly. Acceptable *total* distortion figures — bearing in mind that results will vary with different types of tape — are anything less than 1%. Considerably more than for amplifiers, is it not? With the correct tape, and if the machine is set up *perfectly*, it is possible to better 0.2%, but it's a struggle!

### Non-Facile Facilities

Of all the many, many facilities you will be offered on decks these days, which are worth having? Not many, but these are worth consideration.

**Variable bias:** The most useful add-on you can have. It must be backed-up with test oscillators, which allow you to set up the correct level of bias for good results at both low and high frequencies. Setting up the correct bias will optimise noise, frequency response and distortion; simple switching for different tape types is not really sufficient, any longer.

**Peak metering:** Or as near to peak as you can get, anyway. It is imperative for best quality results that the meters read as close to signal peaks as they can. Those parts of the signal which exceed the recommended maximum recording level will be grossly distorted and heavily compressed. Not good for the aural. Good metering is expensive so if you are serious about making your own tapes, look closely at what each machine in your price range offers. Don't assume that just because the display is electronic, ie LCD, or LED, that the meters are brilliant. The circuitry behind the displays might not be set up to peak-read.

**Three heads:** Are not necessarily better

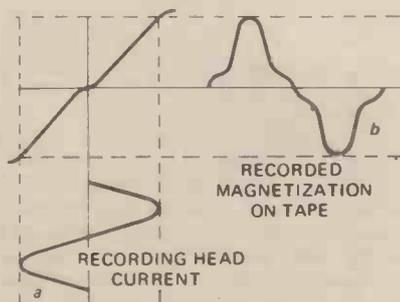


Figure 4. Without bias, distortion will occur when signals are recorded (above). Using high-frequency bias shifts the signal into a more linear region of the magnetisation curve. Result: less distortion.

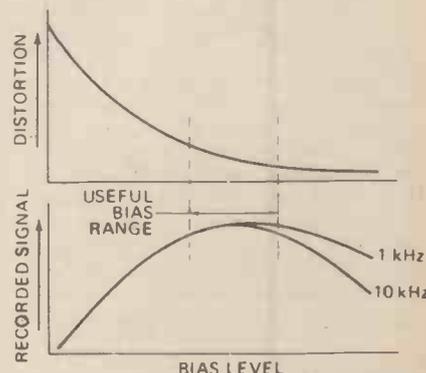
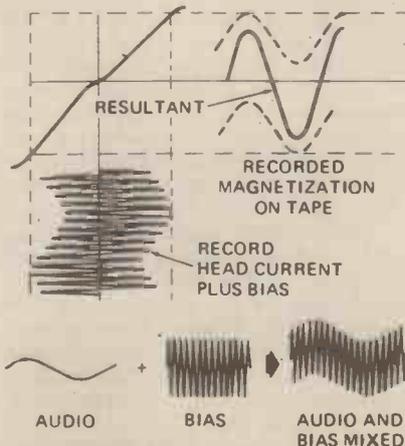


Figure 5. Bias level has a critical point, beyond which, high frequencies are attenuated. Reduction of distortion has to be balanced against loss of treble.

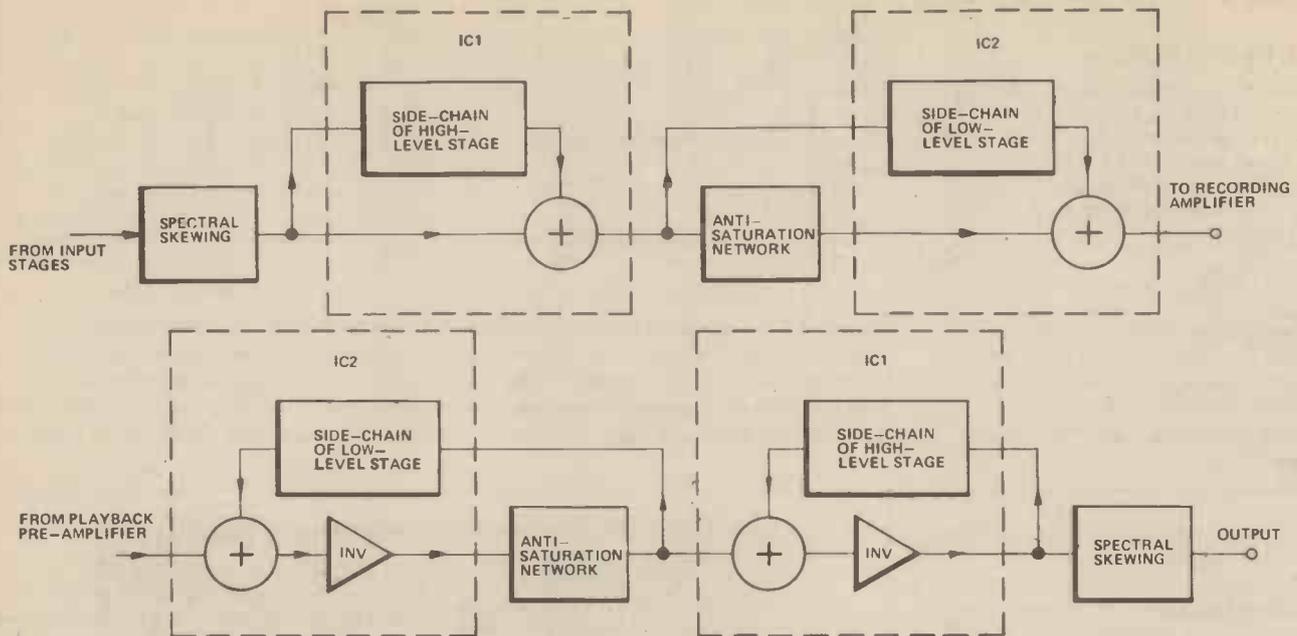


Figure 6. Block diagram of the Dolby C noise reduction system. The top circuit is the encoder, the lower is the decoder.

than two. Without the third head monitoring what is actually being recorded on to the tape is impossible. The importance of this, however, depends upon your personal taste; it's nice to have, but unless you're making your own music, not essential. Don't spend on the extra price of metal unless the rest of the package is right for you.

**Two Speeds:** Some decks are now offering another speed in addition to the universal 1 7/8 ips. Not all manufacturers offer the same alternative, however. The excellent, but now deceased, Elcaset ran at 3 3/4 ips and obtained higher performance as a result. There are now machines to be bought which offer 15/16 ips — but with reduced performance, naturally. Their main usage is for background music.

**MPX Filters:** FM radios employ a tone at 19 kHz and another at 38 kHz as part of their method of operation. These should be filtered out at the tuner itself, but might not be completely removed from the signal presented to the tape deck. As the bias signal is also a high frequency tone, if the two are in any way connected, ie one a whole number multiple of the other, they will interact and 'beat' like two tuning forks. An MPX filter is there to remove these multiplex (MPX) tones, ensuring clean recording. With the advanced state of tuner technology today, the MPX filter is probably a bit redundant, although it is good insurance to have one somewhere on the front panel, should you wish to make tapes off-air.

## Tape Types

There are four categories of tapes available for cassette machines, nowadays and even manufacturers are beginning to refer to them as "groups

I-IV". Bias controls can thus be labelled 1-4 to avoid any possible confusion. Tape packaging should carry either a bias/equalisation setting or a simple "Group X" indication. The four types are: —

- (i) Ferric (or normal)
- (ii) Chromium dioxide
- (iii) Ferri-Chrome (or Fe<sub>2</sub>C<sub>3</sub>)
- (iv) Metal (or iron)

Taking the four in order, let's have a look at the pros and cons of the different formulations.

**Group 1: Ferric Oxide.** These were the first tapes to be released and were set up by the Philips specification for equalisation, etc. A fairly severe bass roll-off was employed; the equalisation time constant associated with this was 120 μs. Setting the equalisation switch to '1' or 'Normal' achieves this figure.

Advantages: the tapes are cheap, widely available and compatible with cheap portable recorders.

Disadvantages: limited output levels, high noise (comparatively) and high frequency compression.

Generally *not* recommended for hi-fi usage.

**Group 2: Chromium Dioxide.** Introduced to overcome the drawbacks of ferric formulations, CrO<sub>2</sub> allowed a reduction in replay boost, thus cutting down perceived hiss considerably. The main drawback to chrome tapes is their low 'headroom' at mid-range frequencies — they will not take a high recording level at all; the particles 'saturate' and refuse to accept further magnetisation. Around 5 dB more bias must be used with CrO<sub>2</sub> tapes, applied by switching to position '2'. For several other reasons, their manufacture is being discontinued by some manufacturers; chrome tapes may soon be seen as a short term answer, since superseded.

Some manufacturers have produced tapes which are basically ferric oxide, in chemical make-up, but are designed for use at the higher bias and different equalisation settings of Group 2 tapes.

**Group 3: Ferrichrome.** Since ferric oxide had problems and chrome tapes had failed to solve them, some bright spark had the idea of producing a tape using layers of both ferric and chrome — Ferrichrome! The idea was to overcome the need for excessive bias levels and provide a better noise performance. Ferric bias and Chrome equalisation settings were recommended, but quite a few machines have no position '3' — use half of '1' and half of '2'! Improved noise performance over ferric was achieved and some newer decks work well with these formulations.

Disadvantages: Increased mid-range distortions and higher cost.

**Group 4: Metal.** Iron is the most easily magnetised material of all and it follows, therefore, that if you could coat a tape with iron filings, it would hold a music signal beautifully! Group 4 tapes are an attempt to gain the maximum possible performance by using this best of all materials. Very high bias currents are required to imprint the signal on to the iron coating of the material — some 9 dB more than for normal tapes, in fact. This has led to improvements in recording head technology, simply to accept all this extra bias signal. The early metal decks gave little, if any, improvement in replay quality over Ferrichrome, but this has changed dramatically recently and the latest models offer superlative performance with Group 4 formulations. Immediate advantages are an improved high frequency response, less noise and cleaner mid-range with lower distortion.

Disadvantages: Cost, cost and more cost. Very expensive approximation to perfection, this. Try a couple on your machine before buying in any numbers.

**Some Model Models**

Once more, we round off by offering a shopping list of units with which we have had some experience. All the decks listed herein have been tested by us at some stage and found to offer good value for money and high performance. All are worth a look.

**Under £100**

- Pioneer CT-320
- Aiwa AD3100

**£100 – £200**

- Technics RSM250
- Pioneer CT-200
- Trio KX-800

**£200 – £300**

- Sony TCK81
- Nakamichi N480

**Expensive**

- Alpage AL300
- Nakamichi N1000XL
- Nakamichi N681Z

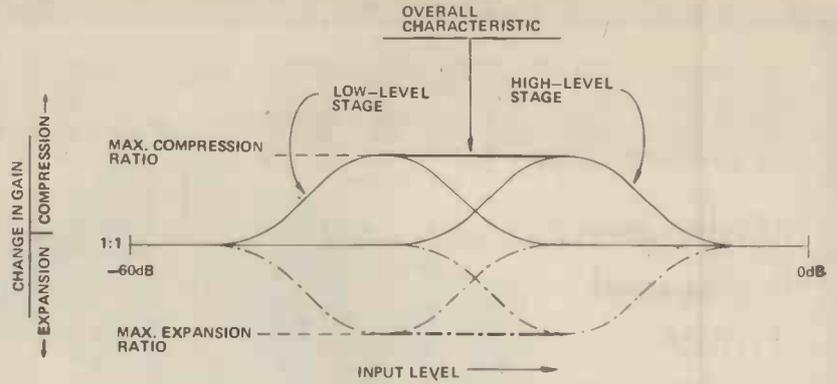


Figure 7. Dolby C actually operates in two stages. At no time is the signal processed by more than a single stage. Combined, the two stages produce 20 dB noise reduction.



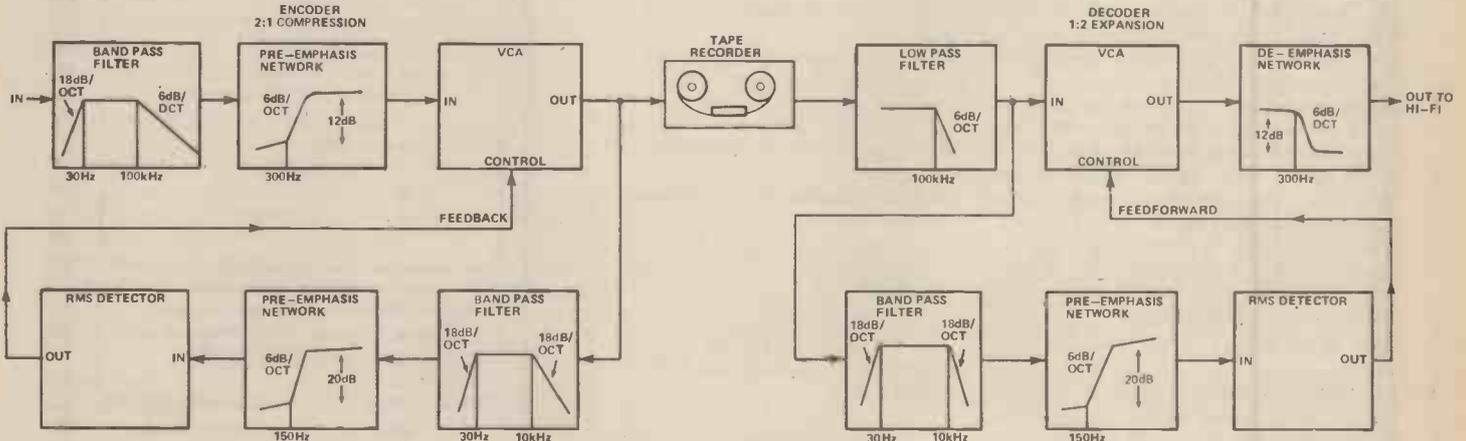


Figure 8. The dbx Type II noise reduction system in block diagram form. Although shown being used for a tape recorder, the system is equally applicable to disc.

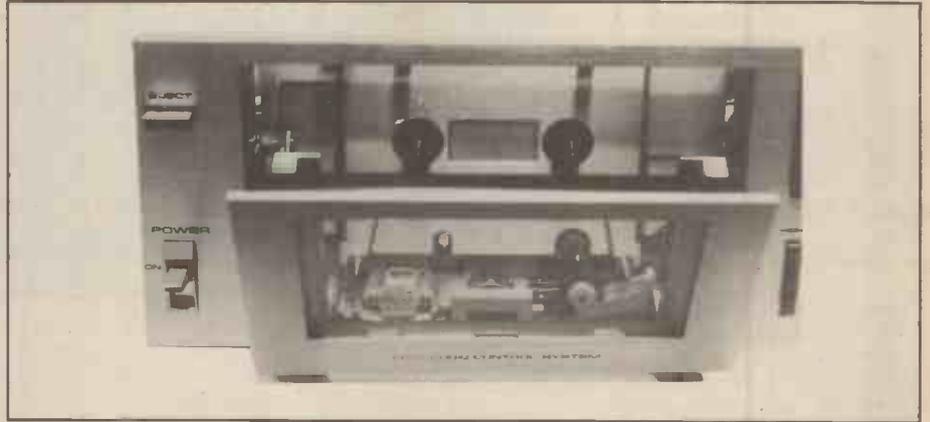

Figure 9. By introducing 2:1 compression when recording — and accurately reversing the process on playback, the dbx system can reproduce almost the original dynamic range of the signal. Tape noise is also reduced, as a by-product!

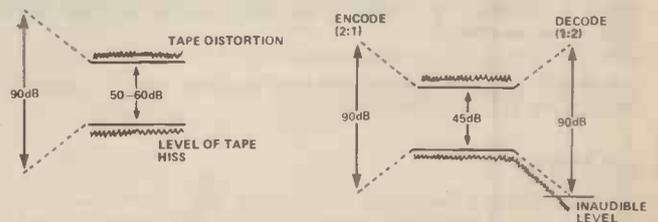

# ELECTRONIC KITS

## Micro-processor universal Timer

This incredibly versatile programmable timer can control up to 20 functions at accurately timed intervals over a period of a week. Originally developed for industrial and laboratory use it offers many interesting and exciting possibilities for the amateur constructor. Based on a pre-programmed TMS 1000 Microprocessor, the unit provides a 24 hour clock with four independent relay controlled outputs with a programmable period of one week. Up to 20 daily or weekly programmable functions can be set via a keyboard. Any of the timer functions can be assigned to control any one of the four relay outputs thus providing almost unlimited programming possibilities.

No previous experience of microprocessor programming is necessary since the manual explains all the possible operations, clearly and simply, enabling the inexperienced user to be fully conversant within one hour. Completed programme steps are indicated by LED's

The kit comes complete with printed panel and may be installed either as a 'built-in' or a 'free-standing' unit. A stabilised power supply mounted on a separate printed circuit board is supplied with the unit. It requires the addition of a 12V, 1A transformer. There is space on the board for up to four output control relays. One is supplied with the kit. Further relays maybe ordered separately as required. Price: *(excluding wooden housing as illustrated)* £48.37 inclusive of VAT and **DELIVERED FREE** on U.K. mainland.

### APPLICATIONS

The programmable timer can provide central control of domestic electrical cooking, heating and entertainment equipment. The possibilities are limited only by the imagination of the user. Control of house lighting to discourage intruders; control of TV or audio equipment; sound or video recording control; automatic plant watering; automatic pet doors or feeding—are a few simple examples. For the professional or industrial user many uses in this area of process control will be found.

### TECHNICAL DATA:

Power supply:  
Mounted on separate pcb with space for up to four output control relays. Requires 12V/1A transformer.

### CONTROL SWITCHING:

Standard relays (one supplied with kit) will switch 2A.  
Additional relays may be ordered separately.  
National relay, order no. HT 12V.  
Siemens relay, order no. R1 INV12.

### MICROPROCESSOR:


TMS 1000

### DISPLAYS:

12mm 7 segment LED numerical display. LED programme function indicators.

### DIFFICULTY GRADE: 3

KIT NUMBER: K1682

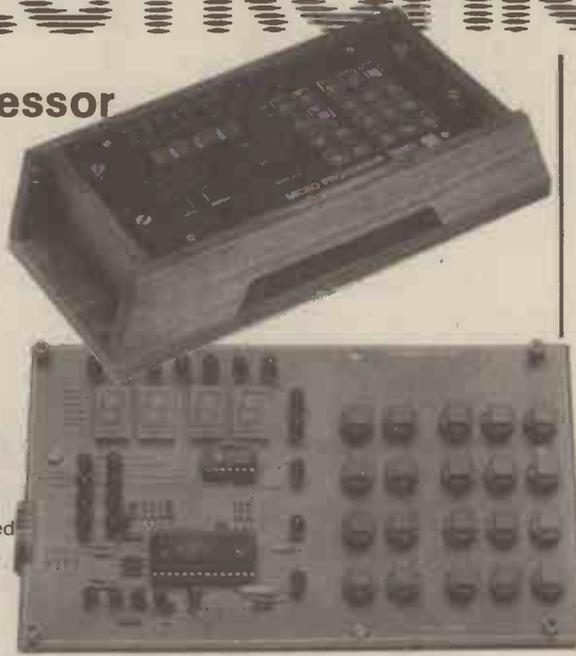

### THE VELLEMAN KIT RANGE

2.2 Watt mini amplifier  
Mono VU using LED's  
7 Watt amplifier  
Dimmer 1000 Watt  
Dimmer 1000 Watt(deparasite)  
High precision stopwatch  
Microprocessor Universal timer  
20 Watt monolithic amplifier  
FM oscillator  
Stereo VU using LED's  
Universal mono pre-amplifier  
60 Watt power amplifier  
Power supply 1 Amp  
Power supply for stereo 60 Watt amplifier  
Running light  
Digital panel meter  
Single digit counter  
Transistor ignition  
Complex sound generator  
50 Hz crystal base  
4 channel infra-red remote control (transmitter or receiver)  
Infra-red detection system (transmitter or receiver)  
Central alarm unit  
FM stereo decoder  
High quality FM tuner  
Digital frequency counter for receivers  
CB power supply 3.5 Amp 12V  
Digital thermometer  
FM stereo receiver (19 in. rack-mounting)  
2 channel infra-red remote control light dimmer (transmitter or receiver)  
Infra-red receiver for tuner K2558  
Infra-red transmitter for tuner K2558  
Tape/slide synchronizer  
3 channel coloured light organ  
20 cm display (common anode)  
20 cm display (common cathode)  
Three tone bell  
5-14V DC 1 Amp Universal power supply  
Light computer  
Universal stereo pre-amplifier  
Stereo RIAA corrector amplifier  
Universal 4 digit up/down counter with comparator  
Microprocessor doorbell with 25 tunes  
40 Watt audio amplifier  
Electric drill speed control  
Microprocessor-controlled EPROM programmer (kit form)  
Microprocessor-controlled EPROM programmer (built and tested)  
Universal start/stop timer

**Repair Service available (for a nominal charge) if your soldering technique is not quite what it should be!**

**Any technical enquiries welcomed—in writing—and will be answered promptly by letter.**

**TRADE ENQUIRIES  
WELCOME**



# VELLEMAN UK

P.O. Box 30, St. Leonards-on-Sea, East Sussex TN37 7NL Tel: Hastings (0424) 753246


Limited

Please send me your free catalogue of Velleman electronic kits:

Name .....

Address .....

HE

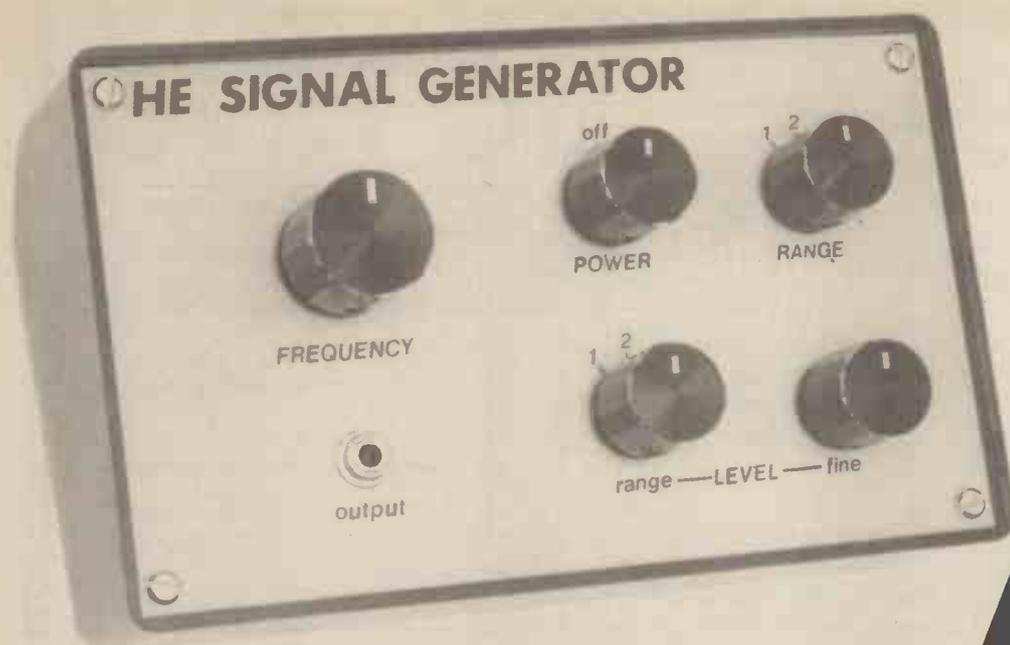

# Audio Signal Generator

R.A. Penfold

A useful and inexpensive addition to your workshop.

IF you are interested in building, servicing, or perhaps even designing audio frequency (AF) equipment of any kind, you are unlikely to get very far without the aid of a few basic items of test equipment. One of the most essential is a signal generator. For most audio tests and measurements, what is required is a good quality sinewave signal at any frequency within the audio spectrum. It should provide an output level that can be adjusted from zero to at least 1 volt RMS and that does not change significantly with alterations of the output frequency.

Our design fulfills these requirements, as it covers a frequency range of approximately 20 Hertz to 30 kHz in three ranges (20 Hz to 300 Hz, 200 Hz to 3 kHz, and 2 kHz to 30 kHz) and has a built-in stabilisation circuit that allows no significant change in the output level over this range. It is important that the output should be reasonably pure sinewave since any distortion of the waveshape may produce unwanted frequencies at the output. These could result in misleading readings when making frequency response tests and similar measurements. The total noise and distortion on the output of our design is less than 0.05%, which is good enough for any normal audio testing.

The unit has a maximum output level of about 1.6 volts RMS and this is continuously variable down to zero by means of a potentiometer and a three position switched attenuator. The low output impedance of the unit helps to


maintain the output level under high load conditions.

## The Circuit

The full circuit diagram of the unit is shown in Figure 1. It is built around an audio power amplifier IC and, although this may seem an unusual choice, it is actually ideal for this for this application since it gives low levels of noise and distortion plus a low output impedance, so that loading of the output is unlikely to cause a significant reduction in the

output level or an increase in distortion.

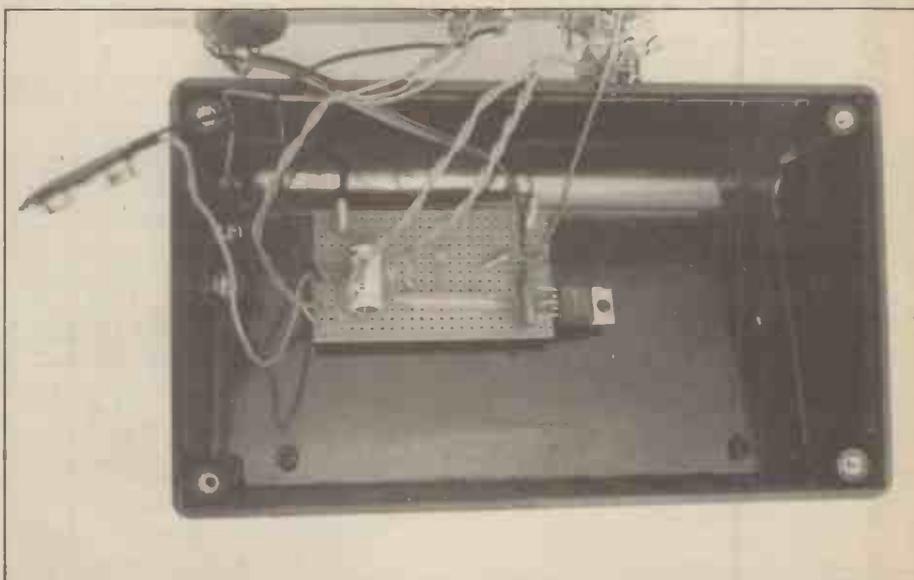The IC employed in the circuit is the TDA2006 which is similar to an ordinary operational amplifier IC, but has a high power output stage. This enables it to be readily used in a Wien Bridge oscillator, the configuration normally used in high quality sinewave generators. Like many operational amplifier circuits this one has dual balanced supplies, provided by two 9 volt batteries.



The internal view — not much of it, is there?

# Audio Signal Generator

A Wien bridge oscillator uses two capacitors and two resistors to provide zero phase shift at the operating frequency of the circuit, but appreciable phase shift at all other frequencies. The Wien network, therefore, gives maximum positive feedback at its operating frequency and, provided the amplifier has sufficient voltage gain, oscillation occurs at this frequency. The loss through Wien network, at its operating frequency, is about 10 dB (three times), so the amplifier needs to have some voltage gain to sustain oscillation.

In this circuit the two capacitors in the Wien network are whichever two are switched into circuit by SW1; the use of three switched sets of capacitors gives the unit three ranges. One resistance of the Wien network is formed by R1 and RV1a in series, while the other is formed by R3 and RV1b. By making the two resistances adjustable, the unit can be tuned over each of the three frequency ranges. The operating frequency of a Wien network, incidentally, is  $f_o = 1/2 RC$ .

The voltage gain provided by IC1 is controlled by TH1 and R2, which form a simple negative feedback network; the voltage gain of the circuit is equal to the resistance of TH1 plus R2, divided by the resistance of R2. TH1 is a self heating, negative temperature coefficient thermistor. This simply means that it is enclosed in a glass envelope (in a vacuum) so that it is isolated from the surrounding temperature. It is intended to respond to the heating effect of a current passed through it, with a rise in temperature giving a reduction in resistance.

At switch-on TH1 will be 'cold' and will have a high resistance, giving IC1 a high voltage gain. This results in the circuit oscillating very strongly and a fairly high current fed through TH1 and R2 from the output. This current has a strong heating effect, so that the resistance of TH1 drops sharply; IC1's voltage gain is reduced and the circuit oscillates gently, but reliably, giving a good output waveform. If loading on the output, or some other factor, should cause a reduction in the amplitude of the signal at the output, the current through TH1 will be reduced slightly, its resistance increases and the output signal level will be restored to its original level. If the output level should increase for some reason, the opposite effect occurs; the current through TH1 rises, the voltage gain of IC1 is reduced and the output signal level falls back down again. Thus the thermistor AGC circuit ensures a pure output signal of constant amplitude. The output of IC1 is coupled by C8 to variable attenuator (RV2) and then to a conventional three step switched attenuator attenuation factors of 0, 20, and 40 dB. Although this attenuator might seem to be excessive, with VR2 in the circuit, it is in fact useful for reducing the output level when a very low amplitude signal is required — adjustments using RV2 alone would otherwise become very critical and difficult!

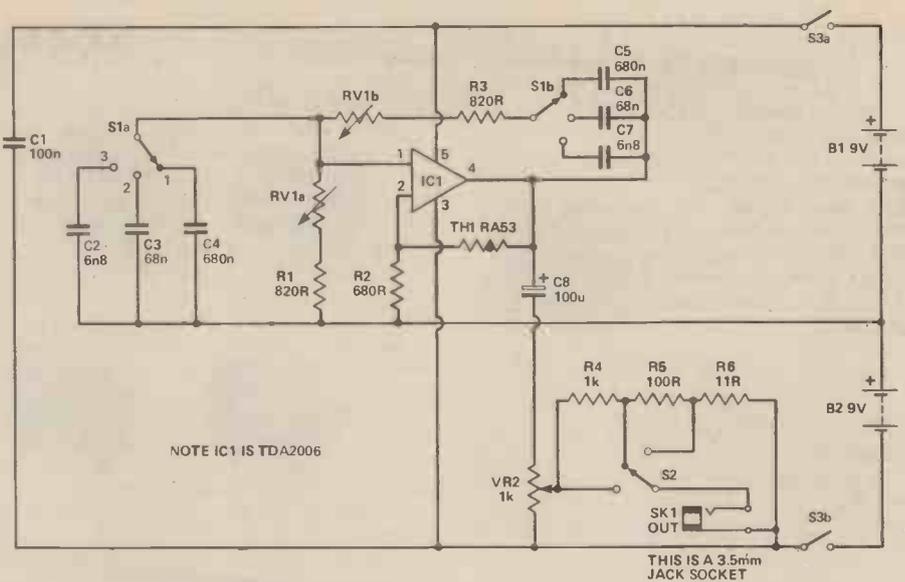


Figure 1. The circuit diagram.

## Construction

Start by cutting the stripboard to size (13 strips by 24 holes) using a hacksaw, and drill the two mounting holes to take 6BA or M3 fixings (about 3.2 mm in diameter in either case). Next, solder the components into place (there are no breaks in the copper strips) following the component layout shown in Figure 2. TH1 is mounted horizontally

on the board and should be treated reasonably carefully as it has a glass encapsulation. Splay the leadout wires of IC1 slightly to compensate for a different pitch to that of the board. Make sure C8 is connected the right way round.

Now drill the front panel of the case to take the five controls and output socket. We used a sloping front case but you can of course, use an ordinary

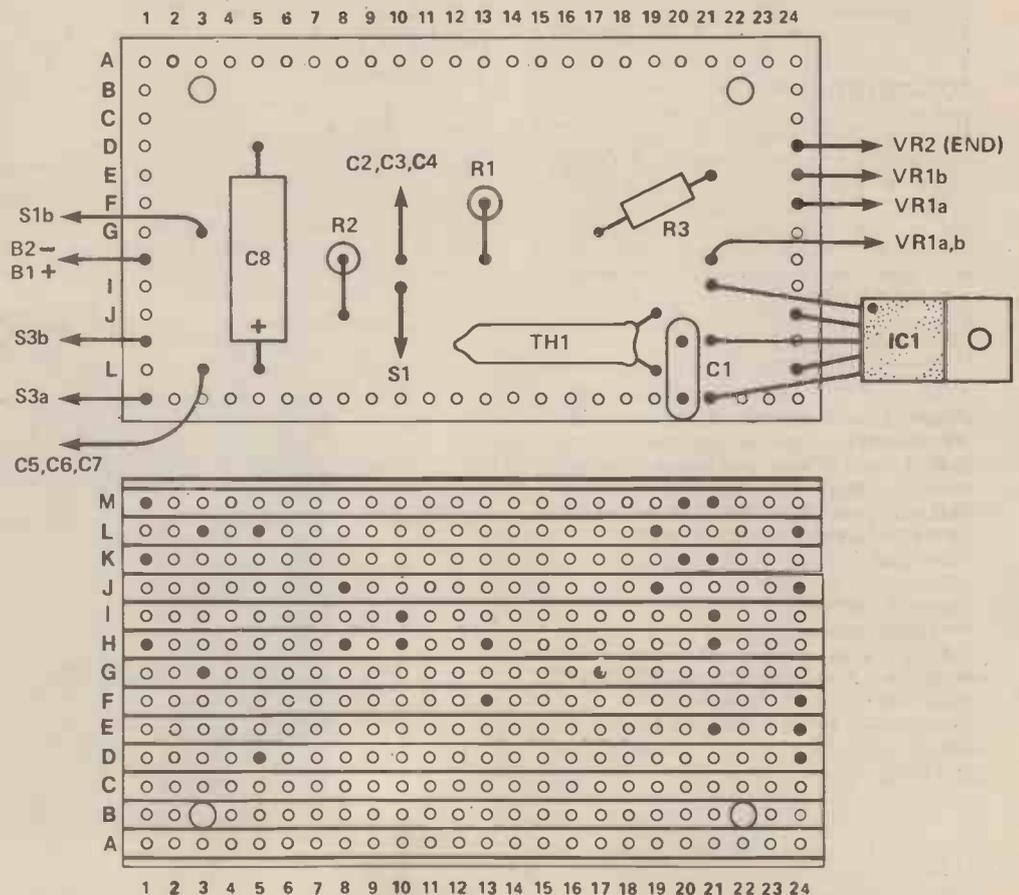


Figure 2. The component layout (top) and the solder 'dot pattern' (bottom). Note that there are no cuts in the Veroboard tracks.

type is you prefer. Mount C2, C3, C4, C5, C6 and C7 and R4, R5 and R6 on SW2, as shown in Figure 3. Then complete the rest of the wiring — this is also illustrated in Figure 3.

A couple of PP3 batteries are used to power the unit, and have a reasonably long operating life. However, the current drain from each battery is about 15 mA, and it would be advisable to use larger batteries (say a couple of PP6s or PP7s) if the unit is likely to receive a great deal of use.

### Parts List

#### RESISTORS

(All 1/4 W 5%)

- R1,3 ..... 820R
- R2 ..... 680R
- R4 ..... 1k
- R5 ..... 100R
- R6 ..... 11R

#### POTENTIOMETERS

- RV1 ..... 10k linear dual gang carbon
- RV2 ..... 1k linear carbon

#### CAPACITORS

- C1 ..... 100n polyester (C280)
- C2,7 ..... 6n8 polycarbonate
- C3,6 ..... 68n polycarbonate
- C4,5 ..... 680n polycarbonate
- C8 ..... 100u 10V electrolytic

#### SEMICONDUCTOR

- IC1 ..... TDA2006 Audio Amplifier

#### MISCELLANEOUS

- S1,2 ... 3 way 4 pole rotary switches
- S3 ..... Rotary DPST switch
- B1,2 ..... PP3 size batteries
- SK1 ..... 3.5 mm jack socket
- TH1 ..... RA 53 Thermistor

Case, veroboard, control knobs, two PP3 type battery connectors, test leads, wire, solder, etc.

BUYLINES page 68

### How It Works

The circuit is built around an audio power amplifier IC which, as usual, has two inputs — an inverting (−) input and a non-inverting (+) input. Positive feedback is applied from the output to the non-inverting input and it is made frequency selective so that the frequency of oscillation can be set. However, the circuit will oscillate only if the amplifier has sufficient gain. Excessive gain will result in the output waveform becoming distorted and producing unwanted frequencies, so the gain is maintained at just the right level by an AGC circuit in the negative feedback loop from the output to the inverting input. A switched attenuator at the output enables the amplitude of the signal to be reduced by a factor of 10 or 100; there is also a 'volume control' attenuator which enables the signal to be continuously varied from zero up to the maximum level permitted by the switched attenuator.


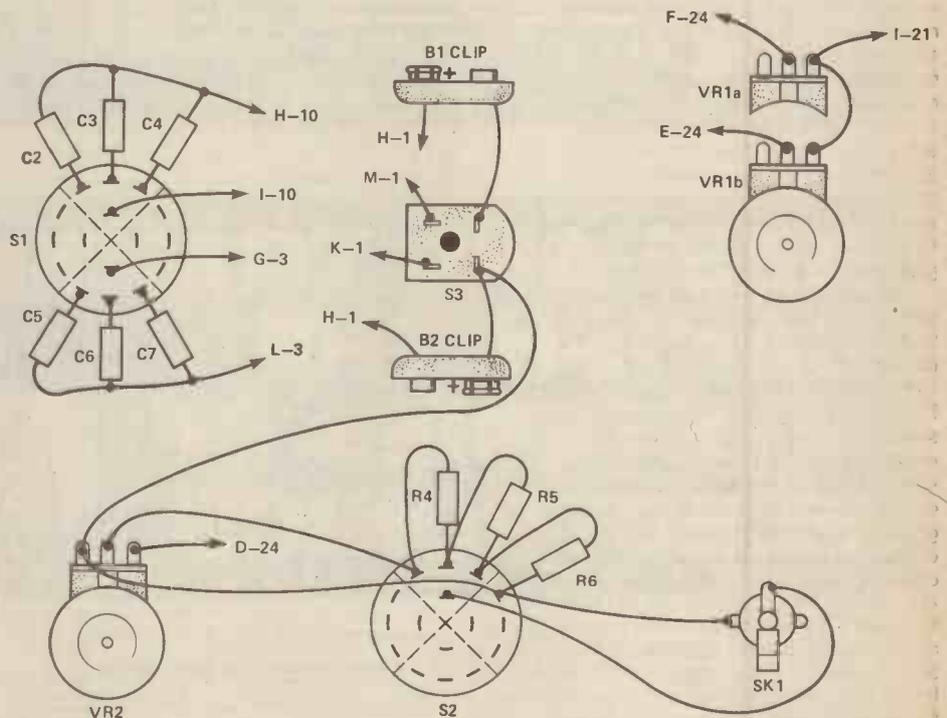
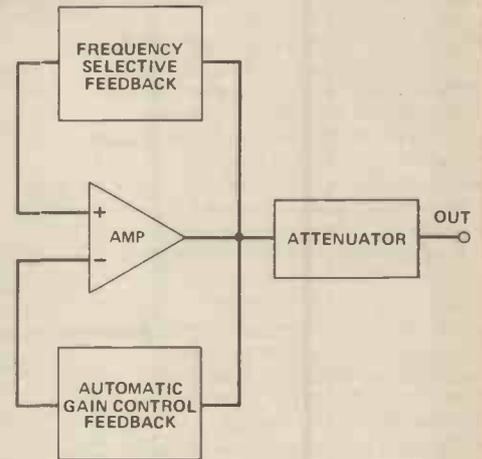


Figure 3 (top). One of the reasons the Veroboard layout is so straightforward is that most of the components are wired to the panel controls! Follow the diagram carefully, making sure that the wires go to the connection points indicated.

Figure 4 (bottom). Templates for the frequency scale (left) and the fine level control (right). They are not intended to be accurate, only to give an indication of the frequency or output level. The frequency scale is multiplied by one on Range 1, by 10 on Range 2 and by 100 on Range 3.

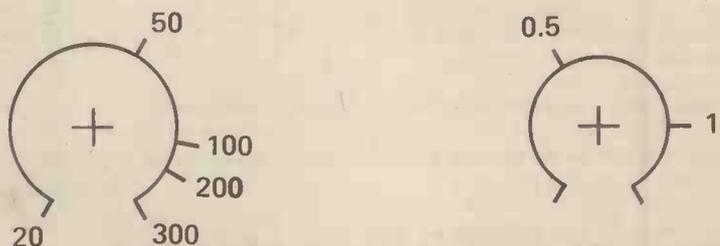

# KITS & COMPONENTS

## DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequence (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button. This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most households. It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one mA from a 9PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions.

**IDEAL PROJECT FOR BEGINNERS—Only £5**

## HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

|         |  |        |
|---------|--|--------|
| TDR300K | Remote Control Dimmer                        | £14.30 |
| MK6     | Transmitter for above                        | £ 4.20 |
| TD300K  | Touchdimmer                                  | £ 7.00 |
| TDE/K   | Extension kit for 2 way switching for TD300K | £ 2.00 |
| LD300K  | Rotary Controlled Dimmer                     | £ 3.50 |



**FOR FREE SHORT FORM CATALOGUE SEND SAE TODAY**

## DISCO LIGHTING KITS

DL1000K. This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.80

DL21000K. A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DL A1 60p  
Allowing audio 'beat'—light response

## REMOTE CONTROL

Published remote control systems tend to be quite complex requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infra-red, our K175 range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling a g TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, traces, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices.

We have compiled a booklet on remote control containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself—SEND US 30p and a stamped addressed envelope for your copy TODAY!

## 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, traces, PCBs and full instructions.



|  |                  |
|--|------------------|
| CT1000K Basic Kit                                      | £14.90           |
| CT1000K with white box (56 x 131 x 71mm) (Ready Built) | £17.40<br>£22.50 |

**SPECIAL OFFER**  
5mm RED, GREEN OR YELLOW 10 FOR 60p OFFER ENDS MAY 20TH OR WHILE STOCKS LAST

## LEDs

|                 |     |     |        |     |
|-----------------|-----|-----|--------|-----|
| 3mm & 5mm Round | Red | 09p | Green  | 12p |
| Clip: 3mm & 5mm |     | 03p | Yellow | 12p |

## [Shaped Led] Red Green Yellow

|                       |     |     |     |
|-----------------------|-----|-----|-----|
| Rectangular (1x2.5mm) | 16p | 16p | 16p |
| Rectangular (2.5x5mm) | 17p | 20p | 20p |
| Square (5x5mm)        | 17p | 20p | 20p |
| Triangular (5mm)      | 17p | 20p |     |
| Arrowhead (2.5x5.5mm) | 17p | 20p |     |

## [Flashing Led]

|                  |     |                     |     |
|------------------|-----|---------------------|-----|
| 5mm diameter Red | 39p | Flashing/Continuous | 42p |
|------------------|-----|---------------------|-----|

## [Tri Colour Led]

|           |     |                 |     |
|-----------|-----|-----------------|-----|
| 5mm round | 30p | 5mm Rectangular | 32p |
|-----------|-----|-----------------|-----|

Add 55p postage & packing + 15% VAT to total.

Overseas Customers:

Add £1.75 (Europe), £4.50 (elsewhere) for p & p.

Send S.A.E. for further STOCK DETAILS.

Goods by return subject to availability.

**OPEN** 9am to 5pm (Mon to Fri)

10am to 4pm (Sat)

## DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (—50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.50

**FAST SERVICE · TOP QUALITY · LOW LOW PRICES**

No circuit is complete without a call to—

**ELECTRONICS**


11 Boston Road  
London W7 3SJ

ALL PRICES EXCLUDE VAT

DEPT.

Telephone  
01 579 9794 2842
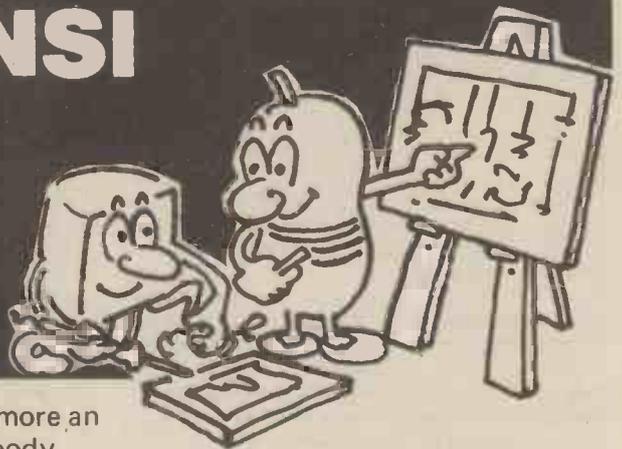
# RESI AND TRANSI BANISH THE MYSTERIES OF ELECTRONICS



**ONLY £4.75 inc. p & p (Plus 25p p & p overseas).**

With electronics becoming more and more an essential part of every day life, everybody would benefit from an understanding of the

basics - this revolutionary book represents a breakthrough in the understanding of electronics!

- ★ Fully illustrated in colour with easy to follow cartoons.
- ★ FREE circuit board for initial practical work.
- ★ The easy, entertaining way for beginners aged 7 - 70 to get started.

**THERE'S NOTHING ELSE LIKE IT - ORDER NOW!**

Please send me details of the book 'Resi and Transi Banish the Mysteries of Electronics'.

NAME.....

ADDRESS.....

Post to: ELEKTOR PUBLISHERS LIMITED, ELEKTOR HOUSE, 10 LONGPORT, CANTERBURY CT1 1PE.  
Telephone: Canterbury (0227) 54430. Telex: 965504

HE

# CHARLES BABBAGE

Charles Babbage was born in Teignmouth, South Devon, to wealthy parents who gave him that most precious gift — a good education, with considerable encouragement to his mathematical talents. These were evident, as is often the case, at a very early age. By the age of 20 he had founded the Analytical Society, which was intended to encourage the teaching of mathematics in this country and, in particular, to make better known in Britain the developments in mathematics which were taking place across the Channel. His work earned him a place as a Fellow of the Royal Society in 1816, making him one of the youngest men ever to have been elected as FRS.

By that time, he had started the work which was to win him a place in history. In 1812, he had been captivated by the thought that mathematical tables, such as logarithms, could be calculated mechanically instead of being laboriously computed by hand, as it were. During 1813, he constructed a small mechanical calculator, similar in principle to the kind of thing that is nowadays sold as a toy, but able to calculate values to eight decimal places. His work revealed several mistakes in earlier sets of tables, and led to a considerable improvement in the accuracy of engineering calculations.

The Industrial Revolution was accompanied by a demand for some method of coping with more complicated calculations, particularly for solving those problems in mechanical engineering which would be very laborious to carry out by traditional pen-and-paper methods. In 1823 Babbage was commissioned by the Government of the day to construct a mechanical calculator which would work to 20 decimal places, a task which he completed despite the formidable difficulties involved. The problem of backlash in gear trains, for example, was one that plagued any attempt to use mechanical methods for precision equipment. Remember that in 1823 the idea of using electricity for performing calculations was a century too early. It was, after all, in the same decade that Michael Faraday, demonstrating the first dynamo, was asked what use could possibly be made of it! Don't laugh — the opponents of electricity, then, used exactly the same arguments as the opponents of nuclear power do now.

By 1828, Babbage's career was sufficiently distinguished to ensure his appointment as Lucasian Professor of Mathematics at Cambridge, a post which he held with distinction until 1839. It was in 1834 that he embarked on a scheme which, though doomed to failure by the inadequate technology of the time, was to prove his masterpiece. This was the 'analytical engine' — to us, us, a computer. His design owed a debt



a computer. His design owed a debt to an earlier engineer, Jacquard. Jacquard was a designer of looms for weaving complicated patterns and he had devised a system of loom control that can only be described as programming. A set of punched cards was fed into a controller and holes in the cards were detected by a set of rods which were then used to select the threads for the weaving. The Jacquard system was fast and accurate, once the program was correctly punched, and gave its users an enormous advantage over their competitors, putting thousands into work. Another demonstration of the fact that success comes by chasing new ideas, not by propping up old ones.

Babbage reasoned that Jacquard's loom system could also be used to control a calculating machine and he started work on a specification, for which he received another Government grant. His specification shows that he thoroughly understood all the ideas that we now deem essential in computing. He realised, for example, that there could be several types of inputs to the machine, which he called number codes (data, as we now call it), direction codes to control the movement of numbers (addressing), and operation codes to determine what would be done with a number (opcodes).

His anticipation of modern computing methods was complete. He made it clear, for example, that an essential operation of his analytical engine would be the conditional transfer — what we now call a branch or jump. The idea, then as now, was that when the result of an operation was well defined, like being

zero, negative, or positive, it could be used to decide what the next operation should be, choosing between two or more options. This, undoubtedly, is the feature that distinguishes the programmable calculator and the computer from the ordinary calculator and there is plenty of evidence to show that Babbage was well aware of its importance.

He also seems to have followed up the possibility that the results of a calculation could be used to change some of the operating codes, so that the program could modify itself — even nowadays, this is considered as pretty advanced programming. Babbage's ideas were never very well circulated, and few among his contemporaries had any idea of what he was aiming at and how important his work would be. One notable exception was Ada, Countess Lovelace, daughter of the poet, Lord Byron. She goes down in history as the first computer programmer, because she seems to have grasped Babbage's designs well enough to write several programs for the machine — even though it was never completed.

All they needed was technology. There was simply no way that mechanical methods using gears, with all the problems of backlash, could cope with such advanced designs and electricity was still a curiosity. By 1842, the Government, which had been remarkably patient, withdrew its support and the Babbage computer was never completed.


Another attempt to make a Babbage machine was made by a Swedish mathematician in Stockholm in 1855, but this too had to be abandoned. Babbage, disheartened, made no attempts to follow up his own work and died in 1871, in London, without having seen his dream fulfilled.

His working life was one of continual problem-solving and invention but few people realise, to this day, the extent of his work. It was Babbage who compiled the first actuarial tables (expectance of life), on which all life insurance is based and these tables still give a better picture of our health than any other evidence. They show, for example, the remarkable rise in life expectancy over the past 100 years. (If you think that the simple life is a healthy one, look up the actuarial tables for the 1860s — they make chilling reading; the simple reason for the Victorian families of 10 to 20 children was the hope that one or two of them might actually survive to adulthood.) Babbage should be remembered, as the man who brought these awful statistics to our attention. He also invented the cow-catcher, used on US railway locomotives in the pioneer days, and the speedometer; but his pioneering effort on computers, rediscovered in 1937, are the greatest monument to his genius. **HE**
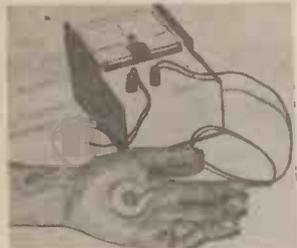
# GREENWELD

443F Millbrook Road, Southampton, SO1 0HX

All prices include VAT at 15% — just add 50p post



## LIE DETECTOR

Not a toy, this precision instrument was originally part of an "Open University" course, used to measure a change in emotional balance, or as a lie detector. Full details of how to use it are given, and a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 4 1/2 batts. Overall size 155 x 100 x 100mm. Only £7.95 — worth that for the case and meter alone!

## AMAZING! COMPUTER GAMES PCBs FOR PEANUTS!

A bulk purchase of PCBs from several well-known computer games including Battleships, Simon and Starbird enable us to offer these at incredible low prices:

### COMPUTER BATTLESHIPS

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value: SN76477 sound IC; TMS1000 u-processor; batt clips, R's, C's etc. Size 180 x 140mm. Only £1.50  
Instruction book and circuit 30p extra

### STARBIRD

Gives realistic engine sounds and flashing laser blasts — accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt clip. (Needs PP3). PCB size 130 x 60mm. Only £2.95

### MICROVISION CARTRIDGES

These are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag is, we don't have any consoles! However, they can be used as an oscillator with 4 different freq. outputs simply by connecting a battery and speaker. Tested and working (as an oscil with pin out data. PCB size 72 x 60mm  
ONLY 25p each!!

### 'SIMON'

The object of this game is to repeat correctly a longer and longer sequence of signals in 3 different games. (Instructions included) PCB contains chips, lampholders and lamps, and is tested working, complete with speaker. Needs PP3 and 2 x HP11. PCB size 130 x 130mm Only £3.95

### LOGIC 5 PANEL

Tested Logic 5 now sold out — but we have some PCB's with 10 LEDs and chip on, but no keyboard. Not tested. 50p

### OPTO/REGS/OP-AMPS

FN5220 2 digit 1/2" 7-seg. display on PCB, CC. With data. £1.50  
7-seg. displays: FND360, 367, 501, all 50p; 530, 347, 850, all £1.50.  
Regs. TO3 case: 7924 120p, 7885 100p, 7808 100p, 7912 100p, 78CB 230p. Others on B/L 13.  
Op-Amps: uA4136 130p; uA776 145p; uA777 300p; uA318 245p  
Isolators: FC08, 11, 15, TL118, all 60p.  
TL311 Hexadecimal display with decoder, 0-9 and A-F. With data. £3.50

### COMPONENT PACKS

K503 150 wirewound resistors from 1W to 12W, with a good range of values £1.75  
K505 20 assorted potentiometers, all types including single ganged, rotary and slider £1.70  
K511 200 small value poly, mica, ceramic caps from a few pF to 0.2uF. Excellent variety £1.20  
K514 100 silver mica caps from 5pF to a few thousand pF. Tolerances from 1% to 10% £2  
K520 Switch Pack, 20 different, rocker, slide, rotary, toggle, push, micro, etc. Only £2.  
K521 Heatshrink Pack, 5 different sizes each 200mm, 50p

### PANELS

Z521 Panel with 16236 (2N3442) on small heatsink, 2N2223 dual transistor, 2 BC108, diodes, caps, resistors, etc. 60p  
Z482 Potted Oscillator Module works from 1.20V, can be used as LED flasher (3V min.). Supplied with connection data, suitable R, C & LED £1  
Z527 Reed relay panel — contains 2 x 6V reeds, 6 x 2S030 or 2S230, 6 x 400V reeds + Rs 50p  
Z529 Pack of ex-computer panels containing 74 series ICs. Lots of different gates and complex logic. All ICs are marked with type no. or code for which an identification sheet is supplied. 20 ICs £1; 100 ICs £4.  
A504 Black case 50 x 50 x 78mm with octal base. PCB inside has 24V reed relay, 200V 7A SCR, 4 x 5A 200V recs, etc. 60p

### RELAY/TRIAC PANEL

Z537 PCB 100 x 75mm containing a wealth of components:  
2 x 12V DPCO min. relays, 2 x 47uF 16v tants, SC146E 10A 500v triac, C112d BA 400V SCR, 555 timer, 10 x IN4001 diodes, 2N5061, 2 x 3mm leds 3 x 2N3704, also R's and C's.  
Amazing value!! — if bought separately parts would cost around £8!! — Price for the panel just £2.00

### 1W AMP PANELS

A011 Compact audio amp intended for record player on panel 95 x 65mm including vol control and switch, complete with knobs. Apart from amp circuitry built around LM380N or TBAB20M, there is a speed control circuit using 5 transistors. 9V operation, connection data supplied ONLY £1.50.

### TOROIDAL TRANSFORMER

110mm dia. x 40mm deep. 110/240V pri., sec. 18V 4A, 6.3V 1A, 240V 0.3A. Ideal for scopes, monitors, VDUs etc. Reduced to £5.95

### 1,000 RESISTORS, £2.50

We've just purchased another 5 million preformed resistors, and can make a similar offer to that made two years ago, at the same price!! K523 — 1,000 mixed 1/4 and 1/2W 5% carbon film resistors, preformed for PCB mtng. Enormous range of preferred values. 1,000 for £2.50; 5,000 £10; 20k £36.

### 200 ELECTROLYTICS, £4

K524 Large variety of values/voltages, mostly cropped leads for PCB mtng. 1:1000uF; 10:63V. All new full spec. components, not chuck-outs!! 200 £4; 1,000 £17.50.

### FILAMENT DISPLAYS

Z553 7 seg display 12.5mm high. Ideal for TTL operation, taking 5V 8mA per seg. Std 14 DIL package. Only £1 each, 4 for £3.00. Data supplied.

### RELAY

24 ac coil, but works well on 6V DC. 2 x 10A. c/o contacts Ex-equip. only 60p

### REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only £7.75. Suitable transformer and pots £6. Send SAE for fuller details.



### ELECTRO-DIAL

Electrical combination lock — for maximum security — pick proof, 1 million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close these can be used to operate a relay or solenoid. Overall dia. 65 x 50mm deep Only £9.95 Also available without combination Only £3.95

### DEVELOPMENT PACKS

These packs of brand new top quality components are designed to give the constructor a complete range so the right value is to hand whenever required. They also give a substantial saving over buying individual parts.

K001. 50V ceramic plate capacitors. 5%, 10 of each value 22pF to 1,000pF. total 210. £4.00.  
K002 Extended range 22pF to 0.1. Values over 1000pF are of a greater tolerance. 10 of each value 22 27 33 39 47 56 68 82 100 120 150 180 220 270 330 390 470 560 680 820 1000 1500 2200 3300 4700 6800. 01 .015 .022 .033 .047 .1. PRICE: £7.00

K003 C280 or similar Polyester capacitors. 10 each of the following: .01, .015, .022, .033, .047, .068, .1, .15, .22, .33 and .47uF. PRICE: £5.40.

K004 Mylar capacitors. Small size, vertical mounting 100V. 10 each of the following: .001, .0012, .0015, .0018, .0022, .0027, .0033, .0039, .0047, .0056, .0068, .0082, .01. Total 130 capacitors. PRICE: £4.70.


K007 Electrolytic capacitors 25V working small physical size axial or radial leads. 10 each of the following: 1, 2.2, 4.7, 10, 22, 47, 100uF. Total 70 capacitors. PRICE: £3.59.  
K008 Extended range, as above, also including 220, 470 and 1000uF all at 25V. Total of 100 capacitors. PRICE: £8.35.

K021 CR25 resistors or similar, miniature 1/4 watt carbon film 5%, as used in nearly all projects. 10 of each value from 10 ohms to 1M, E12 series. Total 610 resistors. PRICE: £5.95.

K041 Zener diodes 400mW 5%. 10 of each of all the values from 2V7 to 36V. Total 280 zeners. PRICE: £15.95.  
K051 LEDs — pack of 60, comprising 10 each red, green and yellow 3mm and 5mm, together with clips. PRICE: £8.95.
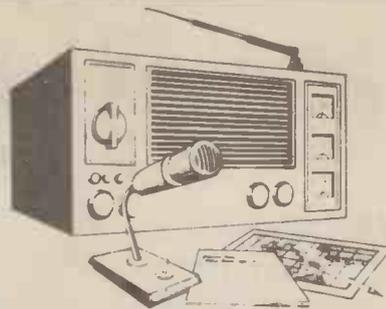
### CAPACITOR BARGAINS

2200uF 100V cans 77 x 35mm dia. 75p; 10/£5.50.  
220uF 10V axial 5p; 100 £2.30; 1000 £16.  
400 x 100uF 275V 102 x 44mm dia. 75p; 10 £5.50.  
200uF 350V, 100 x 100 x 50uF 300V can. 75 x 44mm dia. 40p; 10/£3; 100/£20.  
100uF 25V axial 100/£3.



# BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.  
No previous knowledge required.

Brochure without obligation to:—

**British National Radio & Electronic School**  
READING, BERKS. RG1 1BR

Free!

Name .....  
Address .....

HE/5/815

BLOCK CAPS PLEASE

## PCB HOLDERS

- PCB's may be rotated through 360 degrees and locked at any angle
- Simple adjustment for different board sizes
- Foam pad available enabling a number of components to be inserted prior to soldering

### CNC 6

PCB Capacity: 10" x 7"

PCB's held by spring clips which also allow the holder to be used as a small soldering jig.

PRICE: £13.80 INC. VAT

### CNC 9

PCB Capacity: 8" x 8"

PCB's held by adjustable Vee Clamps which eliminate the risk of damage to the face sides of the PCB and allow a high degree of accessibility.

PRICE: £15.95 INC. VAT

### FOAM PAD

Size: 8" x 8" Clips onto Holder. PRICE: £5.50 INC. VAT

AVAILABLE DIRECT FROM THE MANUFACTURER. PLEASE ADD £1.50 TO COVER POST AND PACKING.

**CARLTON NICHOL & CO. LTD.,**  
GOLDKEY INDUSTRIAL ESTATE, KELVEDON, ESSEX

# QUICK PROJECT:

## LIGHT SEEKER



The warning tone means 'Shut the door, quickly'!

If you've ever worked with photographic materials, you'll know how important it is to ensure that there is no light present when handling sensitised materials (ie light sensitive paper). This is not a problem if you can be there all the time. However, if you need to leave the room, it would be handy to have some means of protecting those valuable films.

One way of doing this is to use a device which provides an audible tone upon exposure to light — the Light Seeker circuit does this admirably. In fact it will produce a pulsed warbling tone that increases in frequency depending on the intensity of light present.

The circuit is a simple combination of two unijunction relaxation oscillators, one modulating the other. Relaxation oscillators are the most common application of unijunction transistors because very few external components are needed to get the thing oscillating (a single resistor and capacitor will do). In our design there are two oscillators; one produces around five pulses per second and this modulates the second one, which is oscillating at a frequency of about 300 Hz rising to 4000 Hz when bright light is shone on the LDR (light dependent resistor). The frequency of oscillation is determined by the resistor and capacitor networks connected across the supply lines and to the emitter of each transistor. For instance, the circuit around Q2 is composed of R3, R4 and C2. The resistor from b1 (base one of Q2) connects to ground via the current limiting resistor R4. The other two components effectively control the frequency of oscillations. Each time C2 charges up via R3, there is a point where the emitter of Q2 no longer acts as a high impedance and the capacitor discharges through R4. After discharging, b1 is zero volts and so the emitter again appears as a high impedance. This exponential charge/discharge cycle repeats at a rate determined by the values of R3 and C2 and produces a rounded sawtooth output. With two such oscillators, the seeker provides an audible pulsed tone, whose frequency is dependent on the resistance of LDR1, which in turn depends on the amount of light present. Resistor R2 acts to couple both oscillators to a degree which allows C1 and C2 to fully complete their respective charge/discharge cycles. Current consumption is about six milliamps, and so a PP3 should last quite some time.


NOTES  
LDR1 IS ORP61  
Q1,Q2 ARE TIS 43

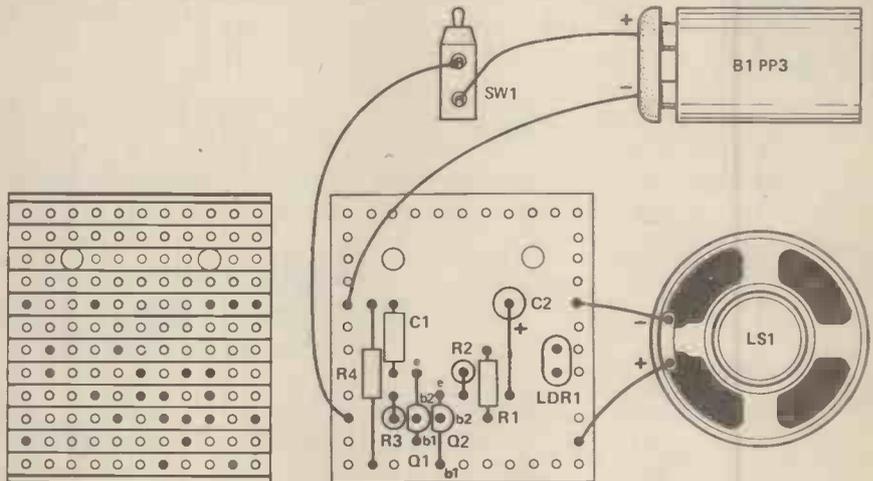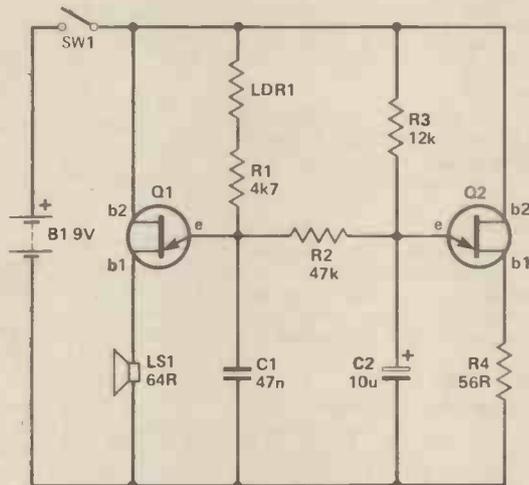

### Parts List

|  |  |
|--|--|
| <b>RESISTORS</b><br>(All 1/4 W 5% carbon)      | LDR1 . . . . . ORP 61<br>light dependent resistor            |
| R1 . . . . . 4k7                               | <b>MISCELLANEOUS</b>   |
| R2 . . . . . 47k                               | SW1 . . . . . SPST on/off toggle switch                      |
| R3 . . . . . 12k                               | LS1 . . . . . speaker (64R or greater)                       |
| R4 . . . . . 56R                               | B1 . . . . . PP3 9V Battery                                  |
| <b>CAPACITORS</b>                              | PP3 clips, veroboard (11 strips, 11 holes), case, wire etc.  |
| C1 . . . . . 47 n polyester C280               |  |
| C2 . . . . . 10 u 10 V radial electrolytic     |  |
| <b>SEMICONDUCTORS</b>                          |  |
| Q1, Q2 . . . . . TIS 43 unijunction transistor | See Buylines (page 68) for availability of these components. |

HE

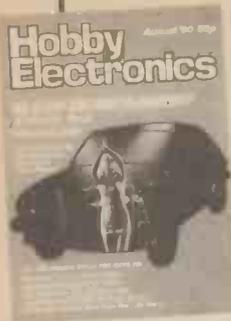

# BACKNUMBERS



**February 1980**  
Passion Meter, Win Indicator, Short Circuit Special, Kit Review Special, Into Electronics Construction Part 1.

**September 1980**  
MicroMixer, Reaction Tester, Guitar Phaser, Development Timer, Teletext Explained, Into Digital Electronics Part 1.

**April 1981**  
Pre-Amplifier Part 1, Super Siren, Guitar Tremolo, Russian Roulette Game, Doorbell Monitor, Anatomy of a Space Shuttle.

**May 1980**  
MiniClocks, 5080 Preamp, Model Railway Track Cleaner, 5080 Loudspeakers, Loudspeaker Crossover Design, Radio Controlled Model Survey.

**October 1980**  
Kitchen Timer, Tug 'o' War Game, Light Dimmer, Freezer Alarm, Intruder Alarm, Temperature-Controlled Soldering Iron.

**May 1981**  
Electronic Organ, Voice-Operated Switch, Infra-Red Controller, Pre-Amplifier Part 2, Audio Millivoltmeter.

**June 1980**  
Microbe Radio Control System, Egg Timer, Two Watt Amplifier, Fog Horn, Short Circuits, LEDs and LED Displays.

**January 1981**  
Car Rev-Counter, Bench Amplifier, Sound-Into-Light Converter, Chuffer, Electronic Games reviewed.

**June 1981**  
Power Amplifier Part 1, Continuity Checker, Envelope Generator, Early Radio, Gadgets, Games and Kits Supplement.

**July 1980**  
Sound-Operated Flash Trigger, 18 + 18 Car Stereo Booster, Hazard Flasher, Electronics in Photography, Electronic Espionage, Piezo Electricity.

**February 1981**  
Heartbeat Monitor, High-Impedance Voltmeter, Medium Wave Radio, Two-Tone Train Horn, Audio Signal Generator.

**July 1981**  
Burglar Alarm, Doorbuzzer, Treble Booster, Electronic Aids for the Disabled, Power Amplifier Part 2.

**August 1980**  
EquiTone Car Equaliser, Pass-The-Loop Game, Gaztec Gas Detector, OP-Amp Checker, In-Car Entertainment Survey, Introducing Microprocessors.

**March 1981**  
Public Address Amplifier, Windscreen Wiper Controller, Bicycle Speedometer, Photographic Timer, Microcassettes.

**August 1981**  
Electronic Ignition, Thermometer, Electronic Organ (final part), RPM Meter, Bench Power Supply, Radio Control Survey, Into Electronic Components Part 1.

All of the 1980 issues, except January and April, are still available together with the remaining issues from 1981.

All backnumbers cost £1.25 each. For those of you who only want copies of articles, we do offer a photocopying service. Each copy costs £1.25 and information as to its title and publication date should be given. Ordering backnumbers and photocopies could hardly be easier, just fill in the coupon, cut it out and send it to:

**Hobby Electronics,  
145 Charing Cross Road,  
London WC2H 0EE**

Please remember to mark your envelope with the service you require, **BACKNUMBERS** or **PHOTOCOPIES**, otherwise our mailroom won't like you.

## HOBBY ELECTRONICS BACKNUMBER ORDER FORM

Please send me the following items:

NAME .....

ADDRESS .....

Back issues ..... at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

## HOBBY ELECTRONICS PHOTOCOPY ORDER FORM

Please send me the following items:

NAME .....

ADDRESS .....

Photocopies of ..... in the  
..... issue at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

# RADIO RULES SINES OF THE TIMES

Part 2 of our new series introduces the most important building block in radio circuits.

Ian Sinclair

IF YOU'VE DABBLED a bit in electronics construction, you've probably found out, by now, how easy it is to make oscillator circuits such as multivibrators, which generate square, or nearly square, waves. Generating sinewaves seems much more difficult, at low frequencies at least. It all seems a bit odd, when everyone tells you how important sinewaves are, that they should be so difficult!

In the early days, no-one had any difficulty generating sinewaves. All you had to do was to rotate a coil of wire between the poles of a magnet and, behold, you had a sinewave at the ends of the wire! Add a pair of slip-rings to make the connections to the rotating coil (Figure 1) and you had an alternator. That's one of the reasons why the sinewave is important — you can generate it mechanically. In the early days of radio, alternators like this were used, spinning at high speeds, to generate the carrier waves for Morse signals.

The use of alternators is fine so long as we don't need really high frequency signals, but it causes a bit of difficulty when we want frequencies around 1 MHz. A large coil revolving one million times per second is a device no-one would want to be close to, so other methods are needed. The 'other methods' all end up with that useful circuit, an inductor in parallel with a capacitor — otherwise call-


ed a parallel resonant circuit. Now let's be clear about one thing right away. The parallel resonant circuit doesn't, by itself, generate sinewaves. What it does is to grow sinewaves. Grow them? It's as good a description as any, for what happens. If, somehow, you start a current flowing in the inductor of a parallel resonant circuit then that current can't just keep on flowing, because it charges up the plates of the capacitor until the voltage builds up enough to make the current first fall to zero, then reverse direction. Then, the current builds up in the inductor in the *opposite* direction until, once again, it has charged the capacitor to a voltage (the other way round now) which will make the current reverse. This cycle creates, (as naturally as the rotation of a coil between the poles of a magnet), a sinewave. It can't keep going, though, any more than the alternator coil can keep spinning, without some outside help. That help, as far as the parallel resonant circuit is concerned, is provided by a transistor, a valve or whatever else we can use to keep the current flowing.

There's the snag of course. We can make a transistor pass current between its collector and its emitter by bringing the voltage between the base and the emitter above about 0V55. (that's the magic figure for a silicon transistor). Now this current is in one direction, from collector


to emitter if the transistor we use is an NPN type, but the current won't flow the other way. If we connect our parallel resonant circuit to the collector circuit of an NPN transistor, then, we can't just start the transistor conducting at any old time. The sinewave which is shaped by the parallel resonant circuit will have a definite frequency, whose value depends on the values of inductance and capacitance in the circuit. If we briefly made the transistor conduct by applying a short positive voltage to the base (a positive pulse), the parallel resonant circuit would oscillate — but only for a short time. Certainly, it oscillates for a lot longer than the time of the pulse at the base of the transistor (just as a bell rings for some time after it has been struck), but the oscillations die out — just as the sound of the bell does. Because of the similar behaviour, in fact, a circuit used in this way is called a 'ringing' circuit (Figure 3).
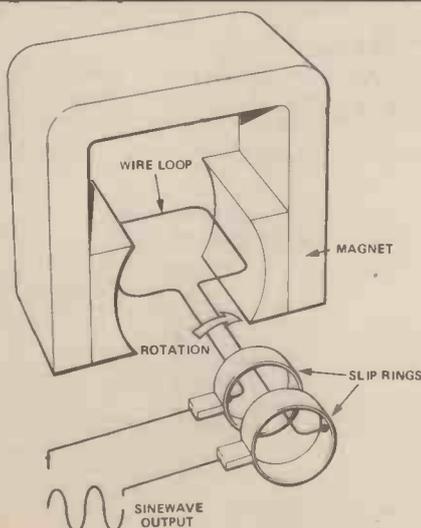
## The Positive Answer


To keep the oscillation going, we have to make the transistor conduct each time the current through the coil is flowing in the *right* direction — that is, from supply to earth. When the current reverses, the transistor has to shut off otherwise it will simply take all the current which should be going into charging the capacitor. The



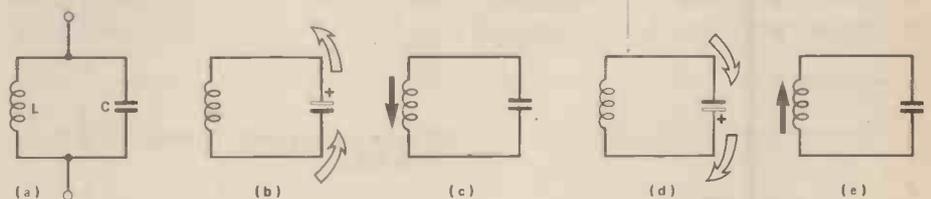
◀ Figure 1. The alternator principle. As the wire loop rotates between the poles of the magnet, a sinewave signal is generated. The frequency of the sinewave is equal to the number of complete revolutions per second of the coil.



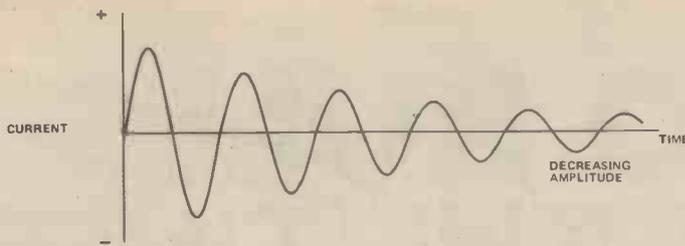
▲ Figure 2. Charge and discharge in a parallel resonant circuit; (a) the circuit; (b) the capacitor discharge (c) causes current to flow through the coil and then the recharging of the capacitor (d); the process then reverses, reversing the direction of current through the coil (e).



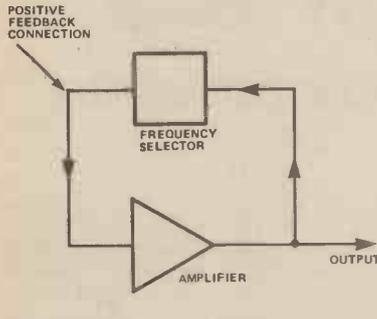◀ Figure 3. The waveform produced by a 'ringing circuit'. A current pulse applied to a parallel resonant circuit causes the charge/discharge cycle of Figure 2, but eventually the current dies away.



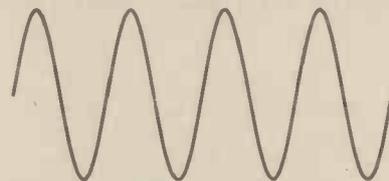◀ Figure 4. To produce continuous oscillation, the ringing circuit needs to be 'stuck' by a succession of current pulses, at exactly the right moments. This is achieved by a positive feedback connection, via the parallel resonant circuit, arranged so that the amplifier conducts only when its output voltage is in phase with the voltage across the tuned circuit.



way we can ensure the base voltage of the transistor causes it to conduct at the right time is by feeding it with a bit of the sinewave generated by the parallel resonant circuit (Figure 4). This is a positive feedback connection; just as the current in the inductor starts to flow earthwards, the transistor starts to conduct, helping the current on its way and so generating a voltage which turns the transistor harder on, helping the action a bit more. When the current reverses, the voltage at the base of the transistor drops, cutting off the current and allowing the inductor to get on with the job. The result is a sinewave oscillator. Any sinewave oscillator which uses a parallel resonant circuit must include a circuit which feeds signal to the base of the transistor to provide the current drive for the oscillations. Seems simple enough but in fact there are a remarkable variety of sinewave oscillators, many of which carry names that date back to the very early days of radio.

A circuit for a sinewave oscillator — an old reliable favourite — is shown in Figure 5. Two windings are needed; one (L1) is part of the resonant circuit, while the other (L2) is a feedback winding which switches the base voltages of the transistor up and down as needed. To make the circuit self-starting, a little bit of bias is needed to start the transistor conducting and this is provided by R1, decoupled by C1. If the oscillator is to operate at a high


frequency, L1 may consist of a few turns of wire on a ferrite rod or a hollow former. L2 should have about 1/4 to 1/5 the number of turns of L1, as a rough rule-of-thumb. Lower frequency sinewaves can be generated if L1 and L2 are windings of a transformer with a ratio of around 1 : 5, using the larger winding for L1. Sinewaves of 20 kHz or less can be generated when a capacitor of about 0.01 is used to tune L1, but the windings must not have a high resistance, otherwise oscillation may not start.

**Bright Idea**

When you make or use a pair of coils in this circuit, there's a 50:50 chance that the oscillator won't work — this is because you can seldom be sure about which way the currents flow in the windings. The easiest cure is the practical one — if it doesn't oscillate, reverse the connections to L2. But how do you know if it's oscillating, without using a 'scope? One old-fashioned way to find out if a high frequency oscillator is working is to use a low-wattage torch bulb, something using less than 60 mA at around 2V5, connecting it to a few turns of a coil, as shown in Figure 6. Hold this lot near L1 and the bulb will light as the coil picks up the frequency generated by the oscillator. Don't go too close, though, otherwise the load on the oscillator may be enough to stop it working.


Another type of oscillator, called a Hartley after its inventor, is shown in Figure 7. There are several varieties of this design, all recognisable by the use of a tapped coil, and Figure 7 shows two of them. The one shown in Figure 7 (a) uses the tap on the coil to connect the supply line, and feedback is taken from the end of the coil opposite the collector connection. Because the collector and the base of the transistor cannot be allowed to be at the same DC voltage, a capacitor is used to couple the feedback to the base. The value of this coupling capacitor, C1, must be considerably greater than the value of capacitor C2, which is used to tune the coil. Another variety of the Hartley circuit is shown in Figure 7(b), with the feedback, this time, taken to the emitter of the transistor. A resistor must be connected between the emitter and the earthline, to avoid shorting out the signal or, as an alternative, an inductor called a radio frequency choke (RFC) can be used. Resistor R1 and R2 are used to bias the transistor, so ensuring that the circuit will start oscillating when it is switched on. The capacitor, C1, is also important; it ensures that no signal reaches the base of the transistor from the collector circuit. Any signal reaching the base will kill the oscillation, so that C1 is essential — it 'decouples' the base.

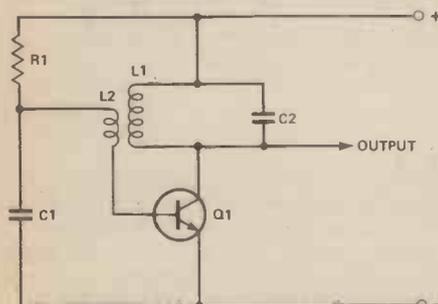One version of a circuit called a Colpitts oscillator is shown in Figure 8. The coil, this time, is a single winding with no



◀ Figure 5. An oscillator using a feedback coil, L2.

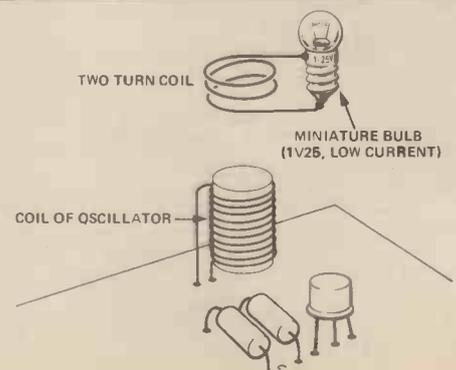▶ Figure 6. Detecting oscillation. Unless the oscillator is a powerful one, the bulb will have to be a miniature low-voltage, low current type. These are not easily obtainable, but an LED can be substituted if more turns of the coil are used.



tapping — a convenient arrangement! The tapping is still there, though, in the form of capacitors C2 and C3. The tuning

of the parallel resonant circuit is carried out by the combination of C2 and C3 in series while the signal to feed to emitter is

tapped by C2 and C3 acting as a potential divider. Once again, capacitor C1 has the essential job of decoupling the base.

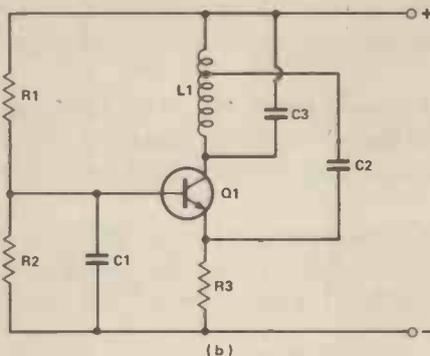
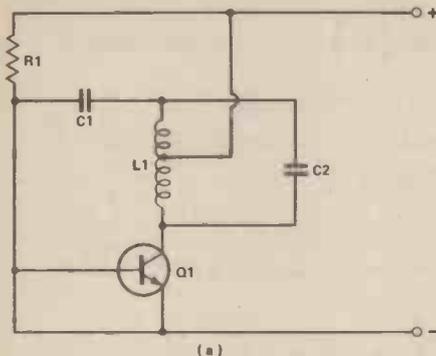


Figure 7. Two versions of the Hartley oscillator; (a) feedback to base; (b) feedback to emitter.

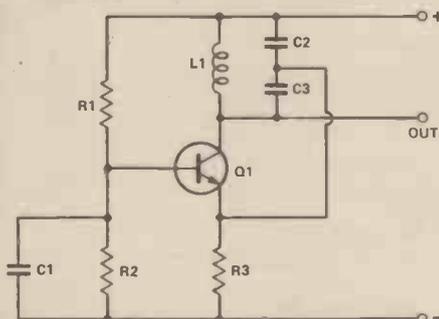


Figure 8. One version of the Colpitts oscillator.

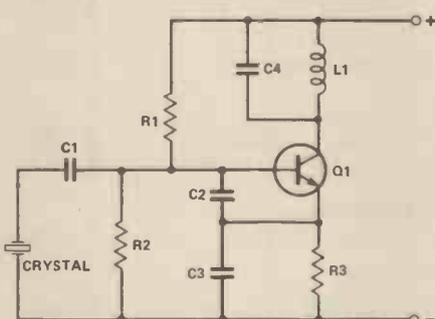


Figure 9. A crystal oscillator, one of a large number of circuits using the method of obtaining a precise and stable frequency.

### Crystal Gazing

The best sinewaves, though, are shaped not be a conventional parallel resonant circuit but by a quartz crystal, connected as if it were an inductor. An example of a crystal oscillator which can generate a very precise and perfectly shaped sinewave, is shown in Figure 9.

It's not so difficult, then, is it? Well, no — not as long as you want high frequency oscillations, anyway. But what happens if you want low frequency oscillations — a few kHz or less? Then, inductors get large and expensive because of the large values you would need for operating these frequencies. Worse still, all that wire makes for high resistance, which causes the shape of the sinewave to distort. In fact we have to abandon parallel resonant circuits at low frequencies — but that's another story!

In radio circuits, however, the parallel resonant circuit is vital. It crops up, in one form or another, in almost every 'block' of every radio. This month, we have had a broad look at parallel tuned circuits and how they work — soon, we will get to grips with the theory, showing how to work out the resonant frequency and other important factors. Later we will go onto look at oscillator circuits in more detail, together with the other basic blocks of radio circuitry.

HE

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



## New Job? New Career? New Hobby? Get into Electronics Now!

**FREE!**  
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

HE/5/821

NAME \_\_\_\_\_

COURSE IN ELECTRONICS as described above

ADDRESS \_\_\_\_\_

RADIO AMATEUR LICENCE

OTHER SUBJECTS \_\_\_\_\_

MICROPROCESSORS

LOGIC COURSE

BLOCK CAPS PLEASE

POST NOW TO:

**British National Radio & Electronics School Reading, Berks. RG1 7BR**



# INTO ELECTRONIC COMPONENTS

THE FIRST ICs ever made were (mainly) digital types, and by far the majority of ICs manufactured today are digital ICs. The reason is that digital signals are peculiarly suited for ICs, and it is much easier to design complex digital ICs than equally complicated linear ICs.

A digital signal is an OFF or ON signal, without any state between. A square wave is a type of digital signal, because the voltage is either at a positive or negative peak; it spends only a negligible time getting from one to the other. Now why should this be important? Imagine for a moment a transistor with a load resistor of 500R, operated from a 5V supply. Suppose that the transistor is passing no current. The power dissipated in the transistor is then zero — no current means no watts. If we now suppose that the transistor is passing about 10 mA, then its collector voltage will be low (saturated at 0V2) and the power dissipated by the transistor must also be low, only 0.2 x 10 mW or 2 mW. If we had biased the transistor to half the supply voltage, as we do when we want linear amplification, then it would pass 5 mA at 2V5 and the power dissipation would then be 5 x 2.5 mW (12.5 mW), a lot more than it dissipates at full current. In a digital IC, no transistors are biased 'half-way'; they are either fully off or fully on. In this way, each transistor dissipates only a small amount of power, so large numbers of transistors can be packed together in an IC without causing the chip to run excessively hot.

Over the years of IC development there have been many digital types produced. By types, we mean the types of

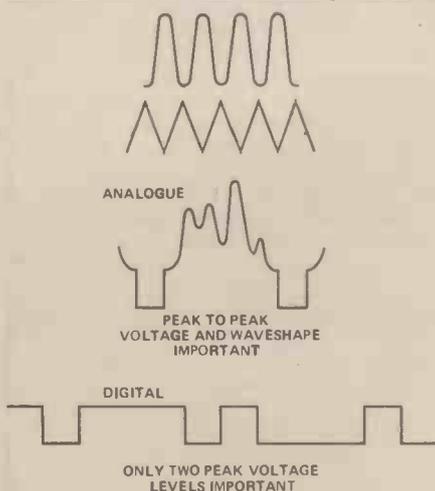


Figure 10.1 Digital and analogue signals. The difference is that the digital signals have only two important voltage levels and the voltage switches very rapidly between the two.

circuits that were used, rather than the jobs that the chips performed. For example, in old books you will find references to DTL, RTL and other long-forgotten types of ICs — some of these are now so completely forgotten that it is impossible to even get pinout diagrams for them. The only types worth considering today are TTL and CMOS chips; these are the ones we shall look at this month.

The most important differences between these two types of digital ICs are that TTL ICs are based on bipolar transistors (PNP and NPN types) and CMOS are based on MOSFETs, TTL has low input resistance and can pass currents of several milliamps, while CMOS has very high input resistances and can pass only small amounts of current, often less than a milliamp.

## TTL Tale

TTL digital ICs are intended to operate from a 5V stabilised supply, whose voltage must be held close to 5V at all times. Though the ICs will generally work in supply voltages as low as 4V5, correct operation cannot be guaranteed unless the supply voltage is maintained within the limits of 4V75 to 5V25. Voltages above 5V5 are risky because some TTL circuits will overheat at such levels, and most of them will be damaged if they are operated for any length of time at 6V.

The reason for this fussiness about voltage is that the input stage of a TTL digital IC is a common-base transistor (Figure 10.2), whose base is connected to the supply voltage through a resistor of a few thousand ohms. This results in a feature of TTL circuits which many beginners find most confusing; the input of any TTL circuit is the emitter lead of a transistor. When this input is at logic level 1 (+5V for TTL), the input transistor is cut off because both base and emitter are at the same +5V level and the collector voltage is also high, around +5V. When the input emitter is connected to logic level zero, which is earth, current will flow from base to emitter. The value of the resistor which connects the base to the +5V supply ensures that the transistor is thoroughly saturated and passing enough base current to make the collector-to-emitter path a very low-resistance one. In this condition, the collector voltage is low, and a current passes from the emitter to earth. The 'standard' TTL circuit will then pass 1.6 mA from its input terminal to earth.

Unlike most transistor circuits, then, in which a current has to pass into the input when it is taken positive, the TTL input passes current out from its input when the input is taken to zero volts. Any circuit which is connected to the input of a TTL

IC must therefore be able to pass this current — to sink this current, in the jargon of the TTL designers — when it forces the TTL input low. Because of this, an emitter-follower is not a good circuit for passing signals to (driving) a TTL IC. When the emitter-follower is cut-off, the IC current will have to pass through the emitter resistor of the emitter-follower (Figure 10.4), and the voltage across this resistor may be too high to guarantee that the IC will be at logic 0.

For example, if the IC can pass 1.6 mA, and is guaranteed to behave correctly if the logic 0 voltage is below 0V8, then an emitter-follower with a 1k emitter resistor is completely unacceptable as a driver. With 1.6 mA flowing through 1k, the voltage drop would be 1V6, which is

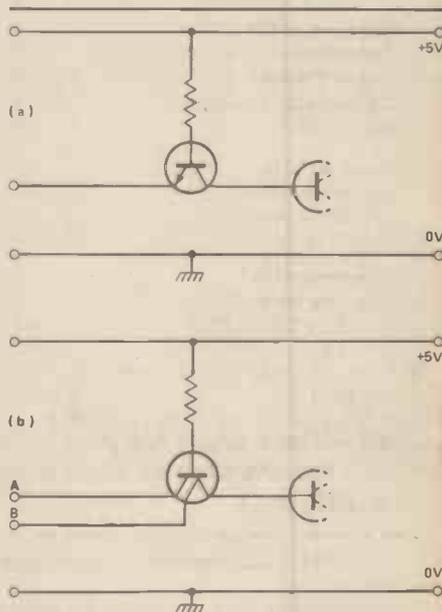


Figure 10.2 The usual TTL input stage; (a) a common-base stage; multiple emitter contacts can be formed; (b) if more than one input is needed.

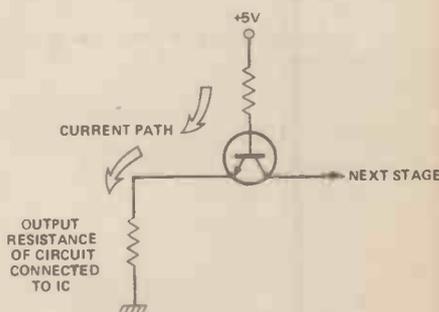


Figure 10.3 Why current passes out from input of a TTL IC at logic 0 input.

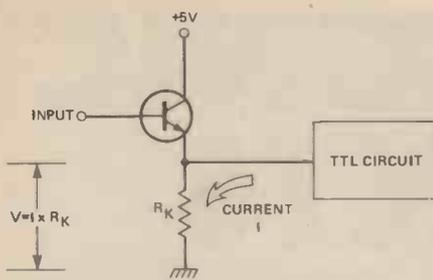


Figure 10.4 Using an emitter-follower to drive TTL is unsatisfactory.

much too high. It might work with a few ICs, but what counts is that it must work with *all* ICs.

A common-emitter circuit (Figure 10.5), by contrast, is very much better. With the transistor cut-off, the load resistor connected to +5V will ensure that the input of the IC goes to +5V. When the transistor is switched on, the collector-to-emitter circuit will easily pass 1.6 mA to earth, with a voltage drop of only about 0V2 if the transistor is saturated.

Digital circuits make use of TTL ICs connected together, so that we can expect to find the output of one IC connected to an input of another. This is possible only if the output of one IC can sink the input current of the next and, because the output of one IC may have to

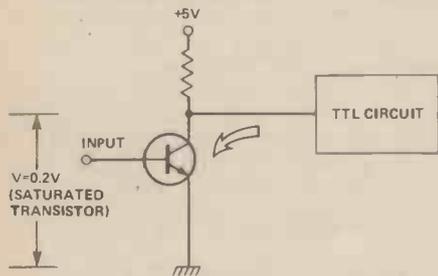


Figure 10.5 Using a common-emitter amplifier circuit to drive TTL is much better.

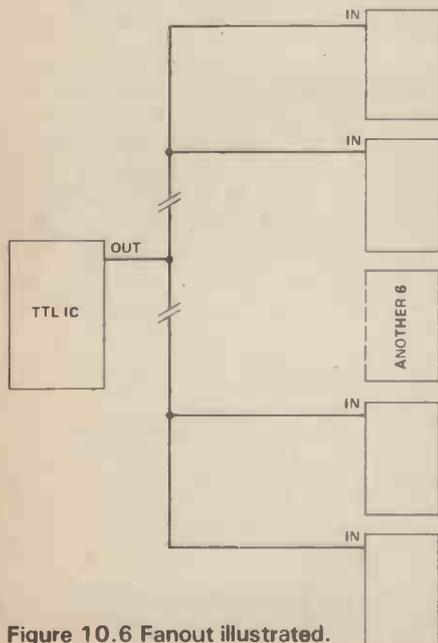


Figure 10.6 Fanout illustrated.

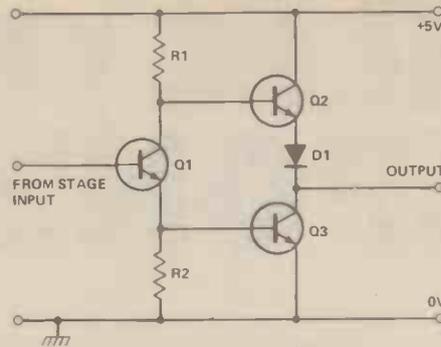


Figure 10.7 A typical TTL output stage

drive several inputs, the manufacturers usually arrange the output circuit so that it can sink the current of ten inputs. If an input needs to pass 1.6 mA, for example, the output must be able to sink a current (pass current to earth) of 16 mA if it is to drive ten inputs. This requirement is called a 'fanout of ten'.

The usual output circuit uses two transistors in series with a diode (Figure 10.7), directly coupled to the collector and emitter leads of a driver transistor. First, imagine that the base of the driver transistor Q1 is cut-off. This will make the emitter voltage zero and the collector voltage high, so that current will pass through R1 into the base of Q2, which passes current. This makes the output voltage high, though, because of the 0V6 difference between base voltage and emitter voltage of Q2. The emitter voltage of Q2 cannot rise above 4V4 which is 0V6 below 5V; the output voltage cannot rise above about 3V8 because of the 0V6 drop across diode D1.

Now, say the base voltage of Q1 is raised, so it is saturated. The collector voltage will be low, and the emitter voltage will rise, until Q3 is switched on. Because the base of Q3 is connected directly to the emitter of Q1, the emitter voltage will not be able to rise higher than 0V6, and the collector voltage only will be about 0V2 higher, at about 0V8. This would, normally, be enough to switch Q2 on, but the diode D1 prevents this (a silicon diode needs about 0V6 to conduct) so that the base voltage of Q2 would have to be at least 1V2 above zero to make Q2 conduct. Therefore, Q3 conducts and this will make the voltage at the output about 0V2, well within the guaranteed voltage for a zero logic level.

The low voltage is really important, because it is only the low voltage which allows the input to pass current, which the output will have to sink. Because all of the transistors in the chip are made at the same time, and are therefore similar, the circuit can also pass current out from the output when the output voltage is high, around 3V8. This voltage cannot be guaranteed by the manufacturers, however, because if a lot of current is passed, the high voltage can fall quite noticeably, to less than 3V. For experimental purposes, though, there is no objection to using an output to drive an LED like the circuit of Figure 10.8 (the recommended method is to use an additional IC, an inverter, in the circuit of Figure 10.9).

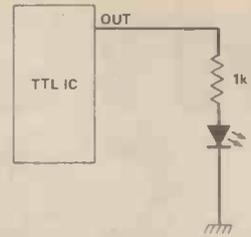


Figure 10.8 Using a TTL output to operate an LED — simple method.

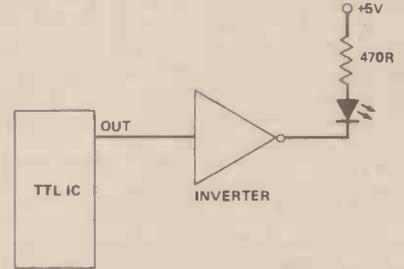


Figure 10.9 The recommended circuit for driving LEDs.

This business of guaranteed voltage levels is important, because it affects trouble-shooting measurements. You cannot expect to read +5 V as the high voltage at an output unless there is a resistor, called a 'pull-up' resistor, connected between the output and the +5V supply line. Neither can you expect to find a true zero reading at an output which is driving several inputs because there may be enough current flowing to raise the voltage to more than 0V2. What you can expect, though, is that the voltage in the high state, logic 1, will be above the manufacturer's guaranteed level (usually 2V4) and that the voltage in the low state will be below the manufacturer's guaranteed level (0V4 typically).

### Identity Crisis

There are several variations of TTL circuits which are still with us. The original range of TTL circuits, pioneered by Texas Instruments and also manufactured by many other suppliers, used code numbers starting with 74. These ICs employed the techniques described in this article, with input currents of 1.6 mA and output sinking capability of 16 mA, so that a fanout of ten could be achieved. For some computer applications, the speed of switching of standard TTL circuits, which is around 30 nanoseconds, is too slow, so a (smaller) range of high-speed TTL circuits, the 'S' series was manufactured. These used higher currents flowing inside the chips to achieve higher switching speeds. The chips carried numbers starting with 74S, so that a 7408 was a stan-

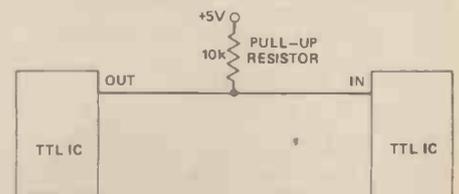


Figure 10.10 Using a pull-up resistor to ensure the logic 1 voltage.

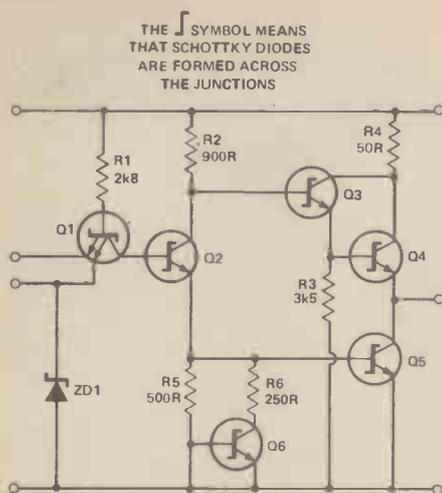


Figure 10.11 The equivalent circuit of an LS type of TTL gate, using Schottky diodes, which have a very low forward voltage drop.

standard AND gate and the 74S08 would be a high-speed AND gate.

Later on, a new principle, the low-power Schottky circuit, was used to make a range of TTL-type circuits which combined lower currents with high-speed operation. These were distinguished by the 74LS type numbers, and are now the main type of TTL ICs. The 74LS series use input currents of 0.4 mA and output currents of only 4 mA for the same fanout of ten, but are as fast or faster than the standard range. The standard 74 range is now, in fact, no longer produced for new equipment, though stocks should last for some time to come.

### Gather No MOS?

CMOS ICs use MOSFETs, with entirely different circuitry. The circuits contain both N-channel and P-channel MOSFETs, arranged so that only one of the pair is ever turned on at a particular time. The range of power supply voltages that can be used is much more flexible than the TTL +5V — in general CMOS circuits can operate with supplies in the range 3V to 15V. Practically no current is needed to hold the inputs at either voltage level, high or low, and only very small currents can be passed either out from, or into, the outputs. Most CMOS circuits which we see here are from the RCA series, bearing serial numbers from 4000 upwards, but National Semiconductor manufacture a range with type numbers starting with 74C and which, very usefully, follow the same numbering system as TTL, so that a 74C08 is a CMOS version of the 74LS08.

Early CMOS chips suffered from a reputation for being easily damaged by static and users were recommended to take remarkable precautions such as being chained to a metal bench, with wrist straps, to ensure discharging of static. Nowadays, CMOS ICs can be handled with few special precautions (unless you work in a room where static is a problem). One of these is that CMOS chips should never be plugged into or removed from a circuit which is switched on. Another is that an earthed soldering iron should

always be used — never use an iron which is not earthed, in any case!

By keeping any CMOS chip in its packaging until ready for use, using holders and plugging in the chip only when the circuit is nearly complete — and with the +ve and -ve leads of the board shorted — you should have no problems. The most important thing is that CMOS chips should be the last items put on the board and that each input should have a resistor connected either to earth or to the +ve supply line.

When you take a quick look at CMOS and TTL, you might find it difficult to see why CMOS has not completely superseded TTL. CMOS can, after all, use a much greater range of power supply voltages and pass much lower currents so that battery-operated circuits can be designed. What makes the difference is that a lot of circuits still require very fast operating times, so CMOS circuits do not generally find much application in computing or in digital control equipment where speed is important. For most home-constructed circuits, however, CMOS ICs or similar (PMOS, NMOS) are more likely to be used.

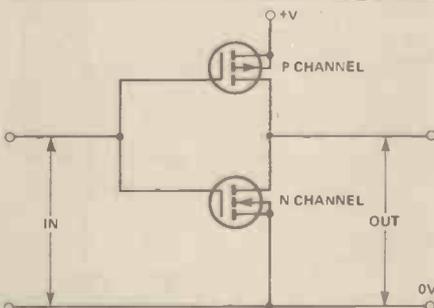


Figure 10.12 Circuit of a CMOS inverter, which uses both P- and N-channel MOSFETs.

### Open And Shut Case?

We've called this series Into Electronic Components and we've tried to stick to components, and what they do, rather than become involved in circuit theory. Digital ICs, however, can't easily be separated from circuitry because each digital IC is itself a complete circuit. So, we now have to spend some time on the types of circuits built in to digital ICs, whether TTL or CMOS.

All digital ICs can be grouped into two types: combinational or sequential. The difference between the types is important. Combinational circuits have several inputs and one output, and each combination of inputs will give pre-determined output. For example, a chip which has two inputs can have four possible sets of input voltages; these are 0,0; 0,1; 1,0; and 1,1 (where 1 means high voltage and 0 means low voltage). For each set of inputs there will be a definite output voltage (0 or 1) and that chip can never produce any other result. The simplest combinational circuits are 'gates' and the easiest way of summarising their action is by using what are called 'truth tables'. A truth table is just a list of all the possible inputs to the gate, along with the output voltage (0 or 1) that is produced by each set of inputs. Different types of gates have dif-

| GENERAL COMPARISONS          | TTL                   | CMOS            |
|------------------------------|-----------------------|-----------------|
| Supply Voltage               | 4V75-5V25             | 4V-12V          |
| Fanout                       | 10 max.               | 50 or more      |
| Operating Temperature        | 0 to 70 deg.C         | -40 to 80 deg.C |
| COMPARING 4-INPUT NAND GATES |                       |                 |
| Input Current                | 40 uA (1), 1.6 mA (0) | 10 pA           |
| Output Current (max)         | 30 mA                 | 0.25 mA         |
| Switching Time               | 11 nS                 | 300 nS          |

Figure 10.13 CMOS and TTL compared.

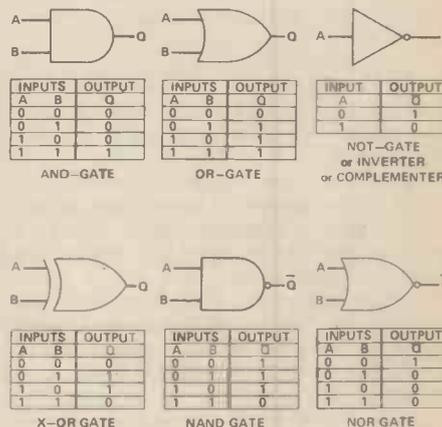


Figure 10.14 Symbols and truth tables for gates.

ferent truth tables, and the types that are available in IC form are the AND, OR, NOT, X-OR (Exclusive-OR) NAND (NOT-AND) and NOR (NOT-OR). Their symbols and truth tables, for two-input gates, are shown in Figure 10.14.

It would be possible to build any type of gate circuit using only NAND or only NOR gates, but simpler circuits can usually be achieved by using the full range of gates though designers often prefer to make use of one type of gate as much as possible, just to simplify the parts list for a circuit.

A circuit for checking the action of logic gates is shown in Figure 10.15. The gate is placed on the Eurobreadboard and LEDs, along with current-limiting 1k resistors are used to monitor the output (or outputs). The inputs are provided by DIL changeover switches, obtainable from Electrovalue and other suppliers. The switches must be wired so that the inputs of the gate are always connected either to 1 or 0; inputs should never be left 'floating', ie unconnected.

When several gates are connected, the truth table can be worked out trying all the combinations of inputs and observing the outputs (taking a lit LED as logic 1), as outlined above. The alternative is to draw

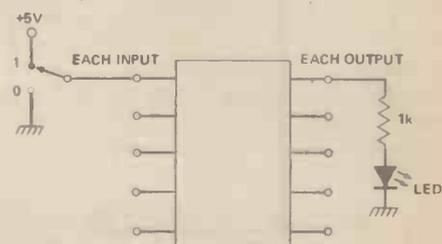


Figure 10.15 Checking the action of a gate or gate circuit by finding its truth table experimentally

## Feature

an extended truth table (Figure 10.16). Each connecting line from an output to another input is labelled with a letter and the outputs of the first set of gates are then entered into the truth table. The next set of gates can then be treated, using the outputs of the first lot as inputs to the second, and so on until all the columns of the truth table have been filled in.

The other type of digital circuit is the sequential circuit, in which the *sequence* of inputs determines the output, rather than the combination of inputs. A counting flip-flop is a typical sequential circuit, and a sequence table for such a flip-flop is shown in Figure 10.17. The input consists of pulses which, in this example, are at regular intervals, qualifying for the name 'clock' pulses. The output of the circuit switches over for each clock pulse, so that one pulse will switch the output from 0 to 1, the next will switch it from 1 to 0. The action is rather like a 'push-on-push-off' light switch.

There is another type of flip-flop, the latching flip-flop, which uses the clock pulse to 'transfer' an input to the output terminals. Looking at a typical example of this type, Figure 10.18, the voltage at the output is made equal to the voltage at the input on each clock pulse and is kept at the value until the next clock pulse arrives. All sequential circuits are based on flip-flops, just as all combinational circuits are based on gates.

Next month we move on from active components and take a look at transducers — devices for transforming other forms of energy into electrical signals.

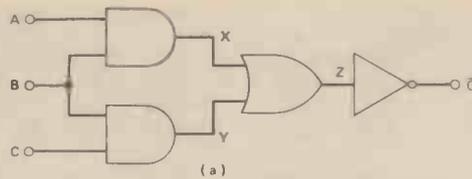


Figure 10.16 Finding the truth table of a gate circuit by paperwork; (a) circuit; (b-d) stages in filling in truth table.

| A | B | C | X | Y | Z | Q |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 |   |   |   |   |
| 0 | 0 | 1 |   |   |   |   |
| 0 | 1 | 0 |   |   |   |   |
| 0 | 1 | 1 |   |   |   |   |
| 1 | 0 | 0 |   |   |   |   |
| 1 | 0 | 1 |   |   |   |   |
| 1 | 1 | 0 |   |   |   |   |
| 1 | 1 | 1 |   |   |   |   |

(b)

| A | B | C | X | Y | Z | Q |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |   |   |
| 0 | 0 | 1 | 0 | 0 |   |   |
| 0 | 1 | 0 | 0 | 0 |   |   |
| 0 | 1 | 1 | 0 | 1 |   |   |
| 1 | 0 | 0 | 0 | 0 |   |   |
| 1 | 0 | 1 | 0 | 0 |   |   |
| 1 | 1 | 0 | 1 | 0 |   |   |
| 1 | 1 | 1 | 1 | 1 |   |   |

(c)


| A | B | C | X | Y | Z | Q |
|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 |

(d)

Figure 10.17 A sequence table for counting flip-flop.



Figure 10.18 The action of the edge triggered latching flip-flop. The output changes only when the trailing edge of the clock pulse arrives, in this example.

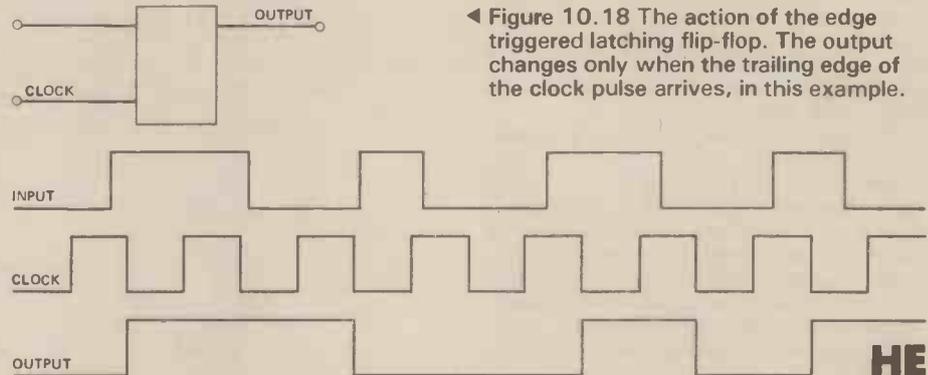

# Now our name means more, than ever before.

If the name BICC-Vero sounds only half familiar, that's not the only difference you're going to notice.

Because not only have we added to our name we've also added to our technology. Building upon our well established industrial product range and incorporating the very latest ideas and techniques to ensure that you too are working at a state-of-the-art standard.

But you will of course still recognise the old favourites. Products like Veroboard, which pioneered in so many ways, today's thriving pastime of electronics.


Bigger means better in other respects. Being part of the giant BICC-Vero Electronics Group ensures that we're a major force in electronics technology. Our R and D scope is enlarged, and our supply and distribution facilities improved.

And because we're professionals we appreciate the very real professionalism of the hobbyist market — and service it accordingly.

Yes, we're sure you'll notice the difference. As well as that pleasantly familiar personal touch.

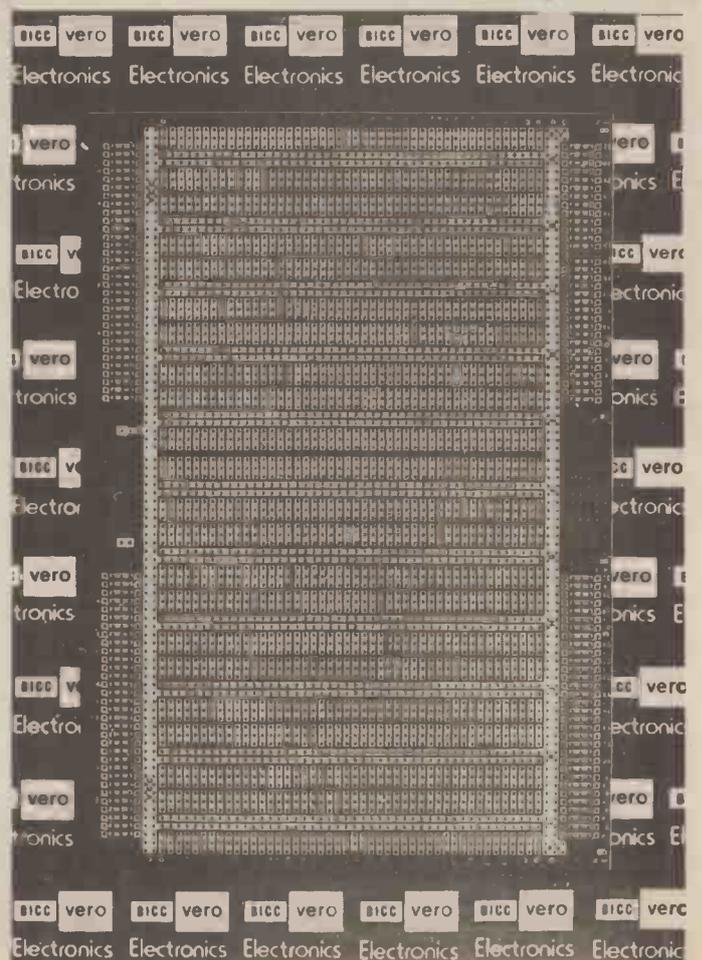**BICC-VERO ELECTRONICS LTD.**

Industrial Estate, Chandlers Ford,  
Eastleigh, Hampshire SO5 3ZR.  
Tel: Chandlers Ford (04215) 62829.



# Cable Tracker

## A D-I-Y Useful

THIS nifty little project is a must for the handyman — even if your Do-It-Yourself experience is limited to the occasional shelf! Our Cable Tracker will detect not only cables, but also pipes and nails buried in wood, thus saving the extra work — and expense — that would result if you should accidentally drill into a central heating or water pipe. Safety is another important aspect of this project, as it will allow you to avoid live cables and gas pipes. Have you ever cut into a piece of wood with a saw and struck a hidden nail? Not much good for the blade, is it! Well, the HE Cable Tracker will also detect nails in wood, to a depth of at least 1 cm.


The Cable Tracker is very simple to use — just run it over the wall, about 1 cm from the surface, where you suspect there may be a hidden pipe or cable. We have used an audible output to indicate the presence of metal, which allows you to watch where you're going, rather than having to look at the Tracker.

### The Circuit

Transistors Q1 and Q2 are connected in an oscillator circuit using L1, C1 and C2 as a high 'Q' tuned circuit resonant at 100 kHz. A high 'Q' circuit is very efficient, producing a generous output at one specific frequency. If even a small piece of metal is brought close to the search coil (L1), however, the inductance of the coil will be altered, reducing the 'Q' of the circuit and hence its output voltage. This change in voltage is detected by the remainder of the circuit.

The oscillator output is full-wave rectified by D2, 3, producing a steady DC voltage across C5. This voltage is AC coupled (so only sudden changes in the DC level will be passed) via C6 to the non-inverting (+) input of IC1a. The inverting input is held at a fixed level by ZD1, R5 and R6 and, provided the voltage across C5 remains constant, the output of IC1a is held at 3V9.

If the oscillator output falls, though, the change is amplified by IC1a and passed to the inverting input of IC1b, which is wired as a comparator. It compares the voltage at the inverting input with a reference voltage, from the sensitivity preset PR1. When the output from IC1a drops below this preset level, IC1b output goes high and switches on the audio oscillator, IC1c. This drives the piezo transducer with a frequency of a few kHz, giving an audible warning that metal is present near the detector head.

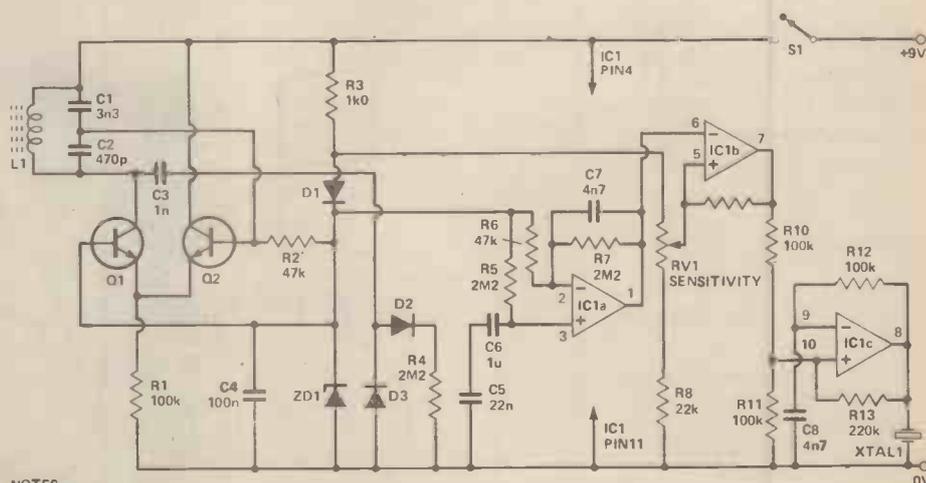

NOTES  
 Q1,Q2 ARE BC183  
 D1,D2,D3 ARE 1N4148  
 ZD1 IS BZY88C3V9  
 L1 SEE PARTS LIST  
 XTAL1 IS PIEZO TRANSDUCER  
 IC1 IS TLOG4

Figure 1. The Cable Tracker circuit diagram.


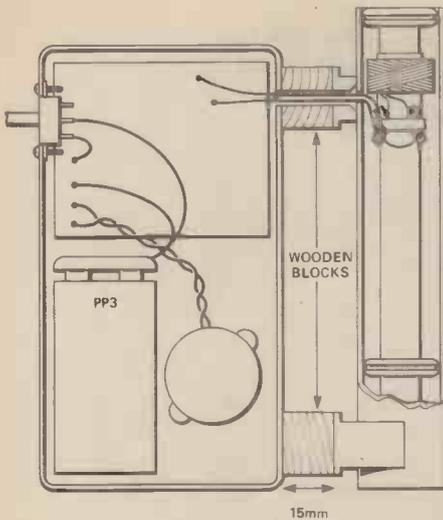


Figure 2 (above). Fitting the pipe in to the clips.

Figure 3 (below). Assembling the detector head. Don't forget to thread the wires through the hole in the pipe, then into the case. Grommets are used to seal both ends of the pipe, as shown.

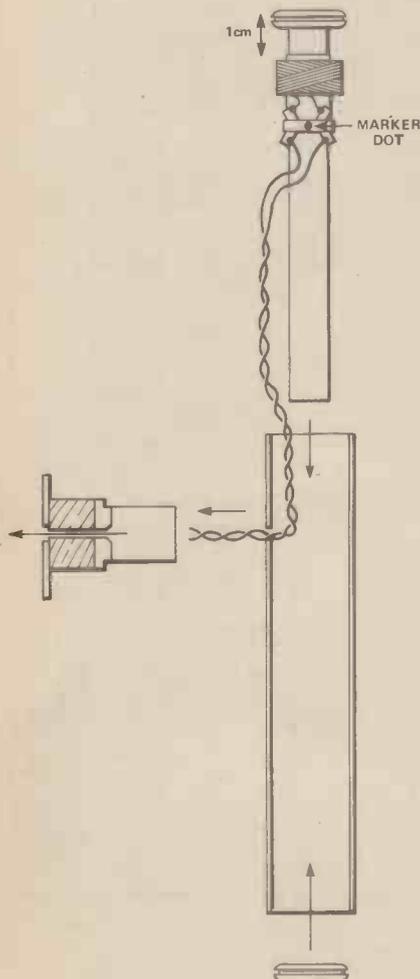

## Construction

Assembly of the Cable Tracker is simplified by the use of a printed circuit board and a ready-wound coil.

Start with the 'detector head'. Using a suitable adhesive, stick the clips to the wooden blocks and drill a hole (about 5 mm) through one of the clip/block assemblies. Position the pipe in the clips, as shown in Figure 2, and drill through the pipe, using the previously drilled hole as a guide. Now take the pipe out of the clips and glue the block/clip assemblies in position on the case — take care to put the one with the hole in it at the top, as shown. When the glue has set, drill through the case, again using the pre-drilled hole as a guide.

Other holes must be drilled near the resonator, to allow the sound out, and for the on/off switch. Remember to leave plenty of room below the switch for the assembled PCB.

Tape the coil in position on the ferrite rod, about 1 cm along from the end, with the coil tabs towards the centre of the rod. Solder two 150 mm lengths of wire to the coil and put a grommet on the 'coil end' of the ferrite rod to seal it into the pipe. Twist the coil wires together and push the ferrite rod down the pipe, at the same time threading the wires through the hole in the pipe as shown in Figure 3. Push the pipe into its mounting clips, remembering to thread the wires through the pipe clip into the case. Fitting the second grommet needs patience; lubricate it with washing-up liquid and gently push it into place using a screwdriver.

Next the PCB is assembled with the help of the PCB overlay, Figure 4. Start by soldering the terminal pins for the coil connections. Insert the resistors round and solder into place, then solder all the capacitors — all types in *this* circuit can go either way round. The preset may

also be soldered in place. Take care to insert and solder the diodes (the broad band is the cathode end) and transistors the correct way round. Solder the IC socket with pin number 1 in the correct place, but leave out the IC until later.

Now solder the following; the black lead (-ve) of the battery clip, the leads from the resonator and a length of wire ready to go to the switch. The PCB can now be fastened to the bottom of the case, using small pieces of double-sided adhesive tape. The ceramic resonator and battery can also be taped to the case — these are a snug fit, so position them carefully before fixing. The battery must also be fixed in position, to avoid interference with the detection circuit.


Fix the switch and solder the lead from the PCB, and the red lead from the battery clip, to it. Finally, solder the leads from the coil to the terminal pins on the PCB. The IC can now be inserted — take care, it must be the right way round.

## Setting Up

Connect the battery and move to an area away from the metal — this includes your watch and rings! Switch on; the circuit adjusts its sensitivity after switch on, so wait for approximately 10 seconds. Using a non-metallic trim tool, turn the preset clockwise until a bleep sounds, then turn it back approximately 1/8th turn — this is the most sensitive position, but if you are using the tracker to find large objects you can lower the sensitivity. To use the tracker, hold the box and pass the detector tube over the wall. The optimum distance is about 1 cm away. Note that a very damp wall will interfere with the detection circuit.

Now you can put up your shelves or pictures — with the confidence that you will not need to rewire or replumb!

Figure 4. The PCB component overlay. The foil pattern is reproduced on page 72.

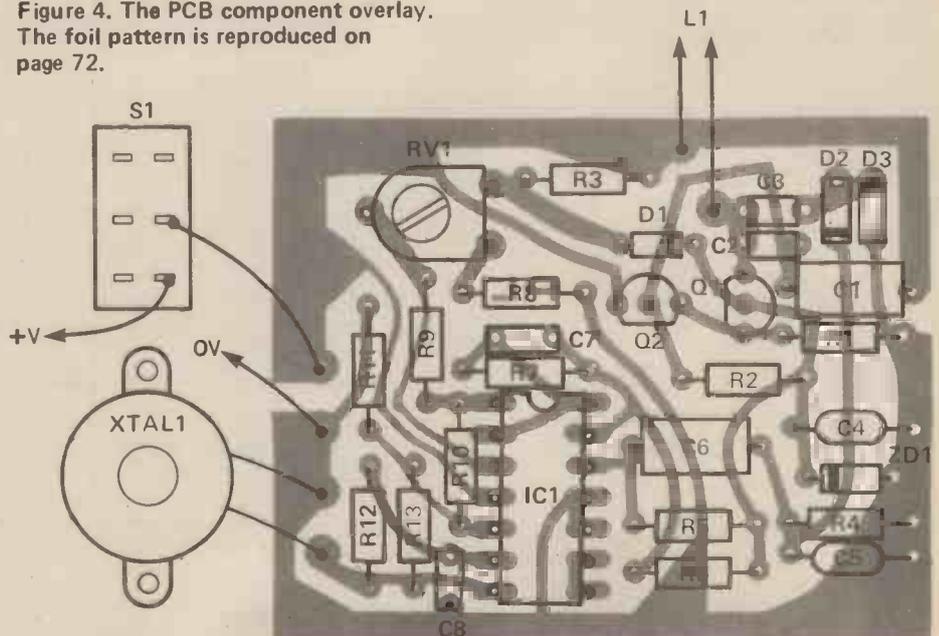


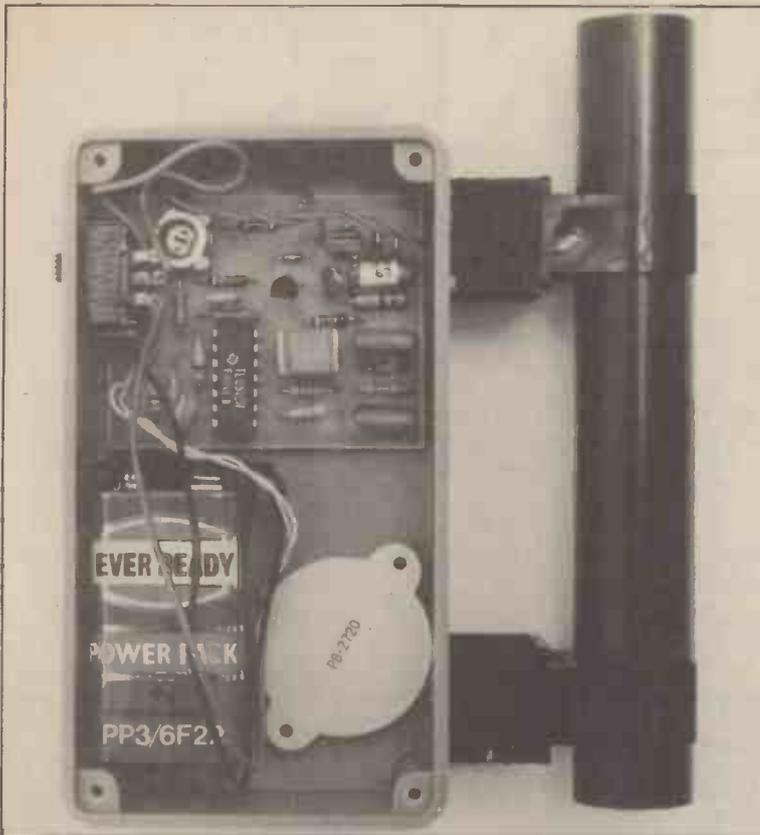


Figure 5 (above). End view of the pipe, with grommet in place.

Figure 6 (left). Internal view of the completed Cable Tracker.
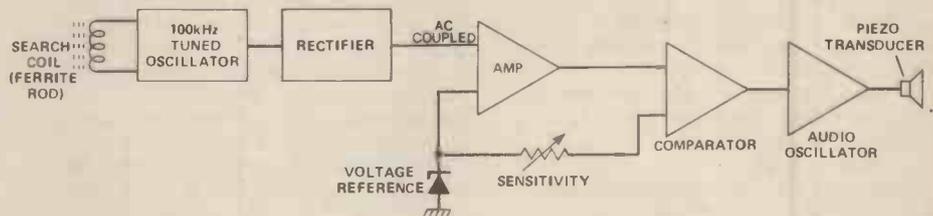
## How It Works

The circuit for the HE Cable Tracker can be divided into six basic blocks (see diagram). The detector part of the circuit consists of a tuned oscillator; when even a small piece of metal is brought near the search coil, the output from the oscillator falls significantly. This change is amplified and compared with a preset reference level, set by the sensitivity control. The comparator detects any sudden change in the output of the oscillator and will switch on the audio oscillator, which drives the transducer.



## Parts List

### RESISTORS

(All 1/4 watt carbon film 5%)  
 R2 R6 . . . . . 47k  
 R3 . . . . . 1k  
 R4, 5, 7, 9 . . . . . 2M2  
 R8 . . . . . 22k  
 R1, 10, 11, 12 . . . . . 100k  
 R13 . . . . . 220k

### POTENTIOMETERS

RV1 . . . . . 22k min horizontal preset

### CAPACITORS

C1 . . . . . 3n3 polystyrene 63 V  
 C2 . . . . . 470p ceramic (low temperature coeff) or polystyrene  
 C3 . . . . . 1n ceramic  
 C4 . . . . . 100n C280 polyester  
 C5 . . . . . 22n C280 polyester  
 C6 . . . . . 1u multilayer min polyester (100 V)  
 C7, 8 . . . . . 4n7 ceramic


### SEMICONDUCTORS

Q1, Q2 . . . . . BC183 NPN transistors  
 D1, 2, 3 . . . . . 1N4148 signal diodes  
 ZD1 . . . . . BZY88C 3V9 zener diode  
 IC1 . . . . . TL064CN quad BIFET op-amp  
 X1 . . . . . Piezo sounder (ceramic transducer)  
 S1 . . . . . min. slide switch SPST

### MISCELLANEOUS

L1 . . . . . 100 mm x 9.5 mm dia ferrite rod with long wave coil type CTL  
 Printed circuit board; plastic case; plastic pipe & clips; wood, grommets, and wire. 14 pin dil socket. PP3 battery clip.

BUYLINES . . . . . page 68

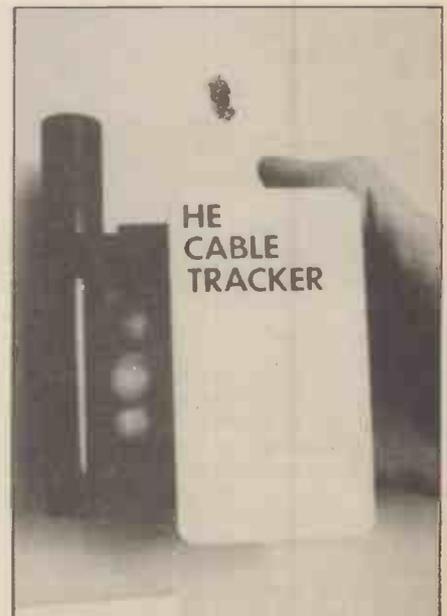

# BUYLINES

## A Digital Thermometer

THERE ARE two things to note about the thermometer project; first, it uses two separate boards and, second, if you buy our recommended case everything fits inside *exactly*. So, you will have to cut and shape the boards carefully and also make sure you mount them as shown in the diagrams.

The components are spaced on the main PCB to ensure that the temperature around the sensor (IC1) is not influenced by any of them — wiring it off the board is even better. This component will probably be the most difficult to obtain, but you can get it from **Crewe Allan & Co. Ltd.**, of 51, Scrutton St., London.

The CMOS ICs (including the 7555) can be bought from **Technomatic** along with the seven-segment displays. You will generally find that **Technomatic** can supply most of the semiconductors used in our projects. So, if you want to save on postage you know where to go!

Another source for semiconductors, and some hardware items, is **Watford Electronics**. They stock the ZTX300 transistors and the low voltage Zener diode; you will also find a range of suitable presets in their catalogue.

The only other parts that might be hard to buy are all available direct from **BICC-Vero**. They make and supply the case with battery compartment, the two-digit LED bezel and the Veropins. If you want further details of any of their products, just drop them a line (enclosing an SAE).

The cost of components (excluding case, PCBs and the optional bezel) should be under £13.



## Light Seeker

THE Light Seeker is probably one of the simplest, yet most versatile quick projects, we've ever run. None of the component values are particularly critical, since oscillation occurs readily. Make sure you put the transistors in the right way round, though — they only work when base 1 is feeding the load. These unijunction transistors seem to be going out of fashion, sad to say, but they can still be bought from **Electrovalue** (T1S43) in their

catalogue), who also sell the 64 ohm speaker — don't use a lower impedance, as the transistors will overheat.

The light-dependent resistor is available from **Maplin**. We used the ORP61 with a side-on sensitive element, though the ORP60 will work just as well.

Due to the large tolerance of electrolytic capacitors, it may be worth buying a pack of ten, say, and choosing the one which gives a nice even 'warble'. A good bargain on these commonly used capacitors can be obtained from **Delta Tech & Co. Ltd.**, of 82, Naylor Road, London N20 0HN.

The cost of this Quick Project is around £4.

## Signal Generator

THIS DESIGN must be one of the easiest signal generator circuits around, for the quality. It uses only a single IC! Most of the cost is in the switches and controls and the only hard-to-obtain component is the thermistor (RA53), which is sold by **Maplin**, or **Watford's** R53 type is a suitable equivalent.

The heart of the project, IC1 (TDA2006), is available from **Technomatic**, where you can also get the rotary switches (they call them wafer switches).

The resistors and potentiometers can be purchased from **Watford** or **Electrovalue**, who will be able to supply all the capacitors between them.

The case used on our prototype was a plastic type with a single metal panel on the top. This was used because of its neat appearance, but any small case can be used. A glance through the **West Hyde** catalogue will give you some idea of the wide range available.

The cost of this project, complete, is about £7, depending on which case you choose.

## Echo-Reverb

THE HE Echo-Reverb is a single PCB project, making construction straightforward if you follow the instructions in the article carefully. The only component requiring special handling is the 4046 CMOS IC. Luckily, they are quite easy to obtain should you have to replace one.

The remaining semiconductors are quite a mixed bunch, but not unusual. The voltage regulator, bridge rectifier and signal diodes are stocked by **Watford**, who are also one source for the PCB mounting transformer. If you happen to get a type that doesn't fit our board, it is sometimes possible to change the position of the tags — but be careful you don't break the thin wires from the primary windings.


The delay line ICs (TDA1022) are quite expensive and it's worth shopping

around a bit for the cheapest. **Rapid Electronics** offer them at a reasonable price, with the added bonus of a quick turn around for mail order customers.

The 1000 microfarad capacitor, though not an unusual component, will have to be chosen to fit on the PCB. **Electrovalue** supply the correct size capacitor, as well as the others in the project.

Most of the hardware and switches, etc are to be found in the **Bi-Pak** catalogue, along with a good selection of knobs and the pots that go with them.

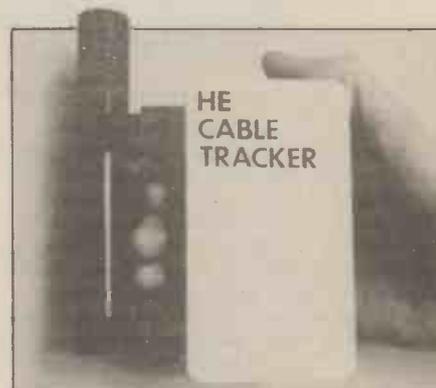We used quite an expensive case for the prototype, to give it a professional finish. It also provided the necessary screening, being a totally enclosed metal box. A suitable alternative may be found in the range of instrument cases offered by **BICC-Vero**. If you leave out the case in estimating your total outlay, it should come to around £24.



## Cable Tracker

The design feature of the Cable Tracker is its neat construction, enabling it to be hand-held. Some of the components were specially selected for the project and they may, therefore, be difficult to obtain. However, **Magenta Electronics** are offering a full kit of parts, including the PCB, for £9.37 plus 45p postage. They will also supply any individual components you can't get hold of, though most of them are generally available from mail order suppliers.

A good bet for the capacitors is always **Electrovalue**, but you must ensure that low temperature coefficient types are used where specified; an alternative to this is to use polystyrene types.

The semiconductors, including the transistors, diodes and IC, are available from **Watford**, **Rapid** or **Technomatic**.

This leaves the piezo transducer and the coil. Both these items were specially selected for the circuit, however, the transducer can be replaced with any device of high impedance (a few kilohms or so) and the coil can be any long wave type, though you may lose some sensitivity.

HE

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained man. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

### City & Guilds Certificates

**Telecommunications Technicians  
Radio Amateurs  
Electrical Installation Work**

### Certificate Courses

**Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting**

**POST OR PHONE TODAY FOR FREE BOOKLET**

**To: International Correspondence  
Schools**

**ICS** Dept 262U, Intertext House, London SW8 4UJ  
or telephone 622 9911

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel: \_\_\_\_\_

## PARNDON ELECTRONICS LTD.

Dept. No. 22, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range  $\pm 5\%$  tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.

£1.00 per hundred mixed. (Min 10 per value)

£8.50 per thousand mixed. (Min 50 per value)

Special stock pack: 60 values, 10 off each £5.50

**DIODES:** IN4148 3p each. Min order quantity - 15 items  
£1.60 per hundred

**DIL SWITCHES:** Gold plated contact in fully sealed base - solve those programming problems.  
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each.

**DIL SOCKETS:** High quality, low profile sockets.

8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.  
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

**ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS**  
MIN. ORDER - U.K. £1.00. OVERSEAS £5. CASH WITH ORDER PLEASE

**DESOLDERING TOOL** Now everyone can afford one of these superb, blue anodised aluminium high pressure hand desoldering tools at nearly half our normal price. Normal Price £6.50 + VAT. With this ad £3.85 + VAT. Spare Teflon screw-in noses 75p + VAT.

**JAPANESE TRANSISTORS** Equivalents available for most types. Please call, phone or write.

**LOW COST VERSATILE MULTIMETER**

**THE MIGHTY MINI MULTI-TESTER** 2,000 ohms per volt. DC & AC Voltage ranges: 10v, 50v, 250v, 1000v. DC current ranges 100mA. Resistance ohms  $\times 10$   $\times 100$  ohm from -10ohm to +220ohm. Mirror arc scale, overload protected, complete with battery, test leads & instructions. Usual price £8.65 + VAT; with this Ad: £4.95 + VAT.

**ORDER FORM**

Name \_\_\_\_\_

Address \_\_\_\_\_

..... Desoldering tools at £3.85 = £ .....

..... Spare Teflon noses at 75p = £ .....

..... Mighty Mini Testers at £4.95 = £ .....

Postage, packing and insurance at 60p per one device, 25p for each additional device £ .....

Sub total £ .....

Add 15% VAT £ .....

I enclose cheque no/P.O. no. \_\_\_\_\_

Alternatively please credit my VISA/ACCESS No. \_\_\_\_\_

Signature \_\_\_\_\_

This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow to cover postage. TRADE ENQUIRIES WELCOME.

**CRICKLEWOOD ELECTRONICS LTD.**

40 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161

## ELECTRONIC IGNITION

Makes a good car  
better



As a  
KIT  
or  
READY  
BUILT

### TOTAL ENERGY DISCHARGE

electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** — no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

### PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

### IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

### AS REVIEWED IN

**ELECTRONICS TODAY INTERNATIONAL** June '81 Issue  
and **EVERYDAY ELECTRONICS** December '81 Issue

**FITS ALL NEGATIVE EARTH VEHICLES,**  
6 or 12 volt, with or without ballast

### OPERATES ALL VOLTAGE IMPULSE TACHOMETERS

Some older current impulse types (Smith's pre '74) require an adaptor — PRICE £2.95

**STANDARD CAR KIT** £14.85

**Assembled and Tested** £24.95

**TWIN OUTPUT KIT** £22.95

**Assembled and Tested** £34.70

PLUS  
£1.00  
U.K.  
P. & P.  
Prices  
include  
VAT.

## ELECTRONIZE DESIGN

Dept: D., Magnus Road, Wilnecote  
Tamworth, B77 5BY

Phone: (0827) 281000





# EXPO DRILLS

KITS TOOLS ACCESSORIES

## TITAN DRILL AND STAND

Engineering in miniature, the most powerful British, 12 Volt D.C. drill made, producing 10,000 R.P.M., 1740 C.M.P. comes complete with tommy bar, allen key, steel chuck + 4 collars, size zero, 1/16, 3/32, 1/8. Specially designed for drilling P.C. Board, mild steel, and many other uses in electronics, other crafts and hobbies.

Also available specially designed Dura Life P.C.B. Drills, very hard and durable, but not brittle like Tungsten

Price £1.10



Titan Drill, complete  
4 collars, Cat No 0175

£10.28

Dual purpose Stand  
Cat No 0209

£12.00

Hundreds of tools  
and kits to choose  
from

Transformer Rectifier  
also available

Available from your local stockists


EXPO Prices are approximately 40% cheaper than all other makes. Distributors, Wholesale, Retail and Export enquiries welcome

Many other Expo drills, tools, kits available  
Send for your copy of latest catalogue  
and price list today

EXPO (DRILLS) LTD Unit 10, Sustanum Works  
Titchfield, Hants Tel Titchfield (03294) 41752


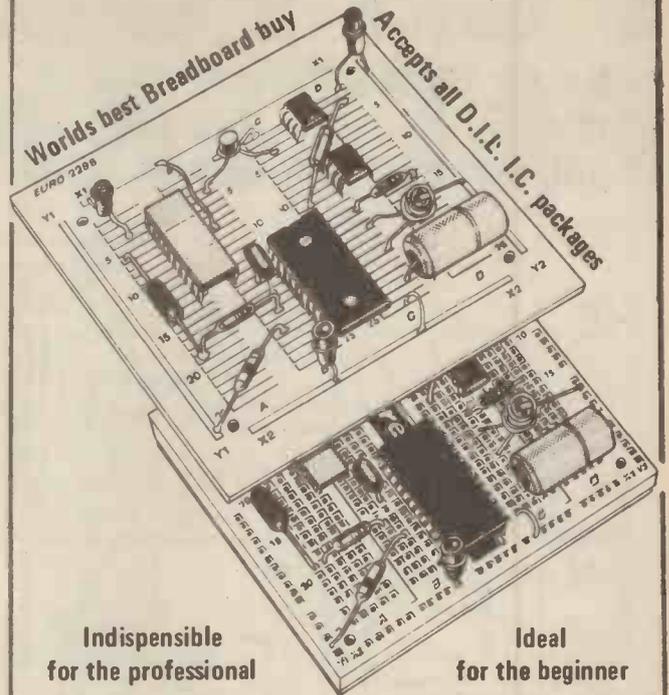
## First the EuroBreadBoard Now the EuroSolderBoard



Indispensible  
for the professional

Ideal  
for the beginner

Design on a EuroBreadBoard — Instal on a EuroSolderBoard

### First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths.

All rows and columns numbered or lettered for exact location indexing (ideal for educational projects)

Long life, low resistance (<10m ohms) nickel silver contacts  
£6.20 each or £11.70 for 2

### Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern.

Four 2.5mm dia fixing holes.  
£2.00 for set of three ESB's

### And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales,  
James Carter Road, Mildenhall, Suffolk IP28 7DE

David George Sales, HE3  
James Carter Road, Mildenhall, Suffolk IP28 7DE  
Please send me:-

- |                       |          |                       |        |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard      | @ £ 6.20 | <input type="radio"/> |        |
| or 2 EuroBreadBoards  | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick   |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> |        |

All prices are applicable from Jan. 1st, 1981 and include VAT and PP but add 15% for overseas orders.

Name . . . . .

Company . . . . .

Address . . . . .

. . . . .

Tel. No . . . . .

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

AMAZING  
HARD-TO-FIND  
SCIENCE PRODUCTS

## EDMUND SCIENTIFIC ILLUSTRATED CATALOGUE

At last this famous range of products is now available in the U.K. and Ireland from RHEINBERGS SCIENCES LIMITED. Over 2000 products for industry, education and the enthusiast.

Send 60p for your colour catalogue and you'll receive £1 off your first order. Or visit our showroom

- |                          |                      |
|--------------------------|----------------------|
| Magnifiers & Microscopes | Optics/Lasers        |
| Light/Infrared Products  | Magnets              |
| Fibre Optics             | Laboratory Equipment |
| Motors & Pumps           | Photography          |
| Polarizing Material      | Educational Kits     |
| Tools                    | Diffraction Gratings |
| Solar Energy             | Holography           |



RHEINBERGS SCIENCES LIMITED, Dept. HE4  
Sovereign Way, Tonbridge, Kent TN9 1RN. Tel: 0732 357779

### Your Leading OPTOELECTRONIC Supplier

Excellent Quality - Very Good Prices - Broad Range



|  | Price |   | Price |
|--|-------|---|-------|
| 3½ digit DPM kit                         | 19.95 | LED's                                     |       |
| LCD 3½ digit module                      | 7.50  | Packs of 10                               |       |
| 3½ digit LCD display & driver            | 11.00 | red 3 mm                                  | 0.90  |
| 4 0.5 inch LED's                         | 4.00  | green 3 mm                                | 0.95  |
| 3½ digit LED A/D driver                  | 6.00  | yellow 3 mm                               | 1.15  |
| IL74 Optocoupler                         | 0.70  | red 5 mm                                  | 0.90  |
| Optoelectronic photointerrupter module   | 2.50  | green 5 mm                                | 0.95  |
| IR emitter/phototransistor (pair)        | 0.75  | yellow 5 mm                               | 1.15  |
| LCD 3½ digit module & backlighting panel | 13.00 | Electrofluorescent backlighting LCD panel | 6.00  |
| 3½ digit LCD panel meter module          | 19.95 |   |       |

Contact us for other opto products All prices are exclusive of VAT.

ELECTRONIC HOBBIES LTD Add P&P at 0.45 to total order

17 Roxwell Road, Chelmsford, Essex CM1 2LY Tel (0245) 62149



# PCB FOIL PATTERNS

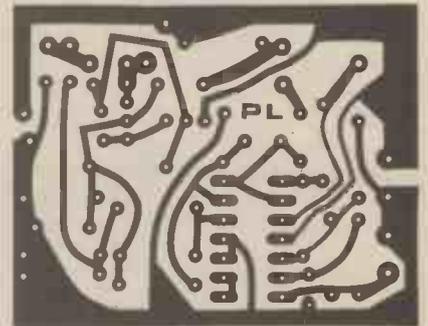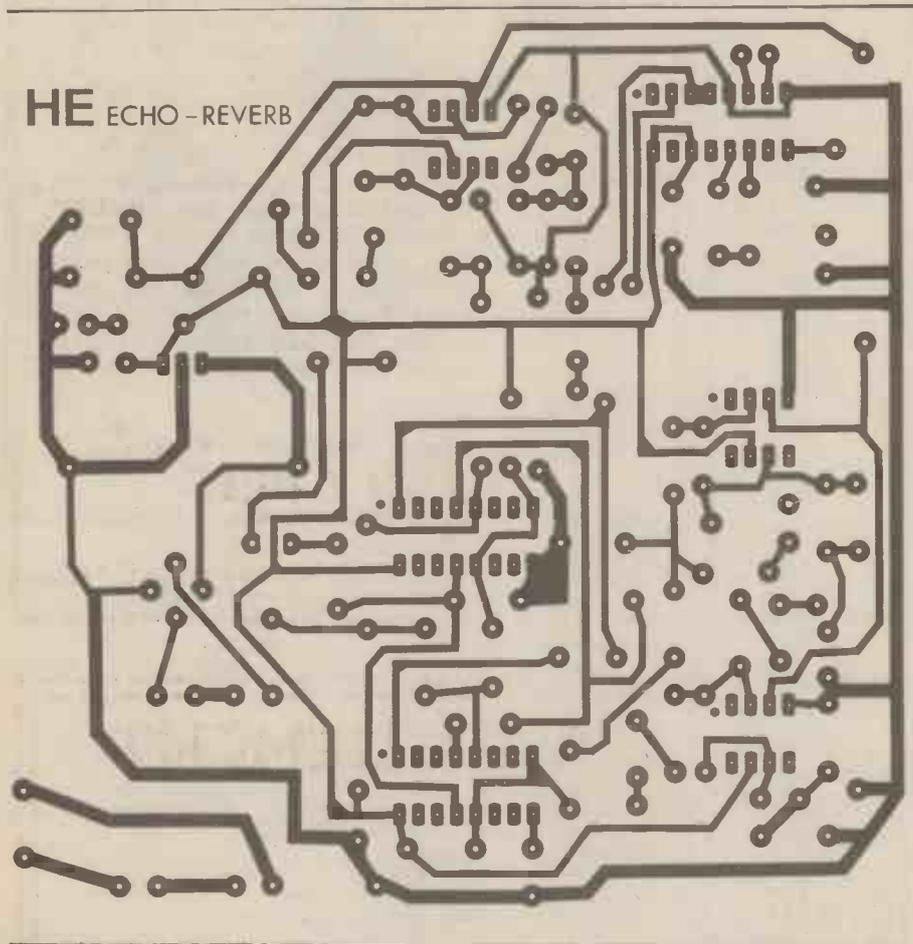

Above: PCB foil pattern for the HE Cable Tracker; don't forget to drill the three lead-out holes on the left.

Left: The HE Echo-Reverb PCB foil pattern. This board will take the mains voltage inputs at the bottom left, so make sure all the copper is etched away. The tracks contain sharp angles at some places — be careful to check these have not been dissolved by the ferric chloride.

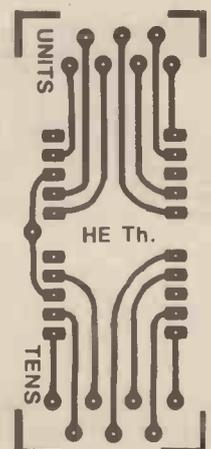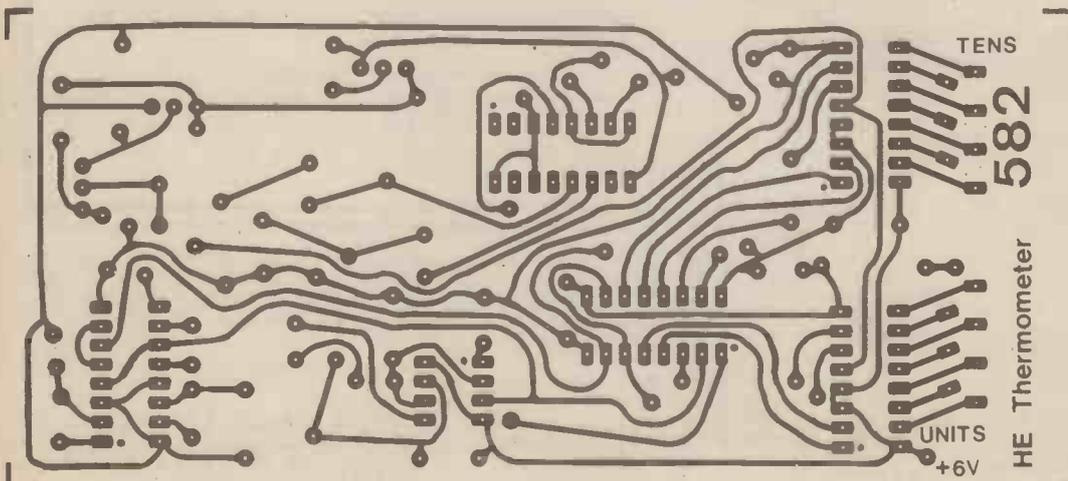Below: The two foil patterns for the Digital Thermometer. Some of the tracks on this board run quite close together, so make a thorough check of the underside before switching on! The main board fits snugly inside the case and must be made to fit — the small board's width must also be controlled, as there is a limited gap beneath the top of the case.



## COMPONENTS IN BIRMINGHAM

### CMOS-LSTTL-LINEAR-ICs NOW!!! IN DEPTH STOCK

From National Semiconductor:

|           |        |     |        |     |         |      |
|-----------|--------|-----|--------|-----|---------|------|
| Some Egs: | 4011   | 15p | 4013   | 34p | 4017    | 42p  |
|           | 4033   | 38p | 40161  | 69p | 4543    | 134p |
|           | 74LS00 | 12p | 74LS90 | 33p | 74LS386 | 28p  |
|           | LM380  | 75p | TBA120 | 90p | TDA2640 | 216p |

Full range list available + Quantity discounts. Ask for details . . . . .

PCBs. The FOTOWay - Brochure on Request.

#### NEW BARGAIN Packs:

|                      |       |                          |       |
|----------------------|-------|--------------------------|-------|
| 16 - TTL ICs         | £1.10 | 6 - Slide Switches       | 60p   |
| 9 - CMOS ICs         | £1.10 | 100 - 1/8 Watt Resistors | 60p   |
| 10 - Croc Clips      | £0.60 | 30 - 1 Watt Resistors    | 60p   |
| 5 - Ex Equipment Bds | £1    | 5 - Large Elect Caps     | £1    |
| 8 - Knobs            | £1.20 | 4 - Rotary Switches      | £1.20 |

Post & packing 60p per order. FREE over £10

ALL PRICES + VAT

**P.A.T.H. Electronic Services Wholesale + Retail**  
369 Alum Rock Road, Birmingham B8 3DR. Tel: 021 327 2339

Open 10 till 6 weekdays. 9.30 till 5 Saturdays

Distributors for: Antex - Altai - Babani - Hills - Servisol - PATH FOTOWay -  
PATH Box - Safgan - Vero Electronics + MUCH MUCH MORE . . .

## JOIN UP WITH LITESOLD

Litesold's new 'L' Series soldering iron - now at a bargain price.

Outstanding performance. Lightweight. Easy to maintain.

Elements are enclosed in Stainless Steel shafts,

insulated with mica and ceramic. Non-seize

interchangeable bits, choose from

'copper' or 'long life'. A very special

tool at a very special 'direct' price.

Just £5.58 for iron fitted with 3.2mm

copper bit. Just £2.40 for 3 spare

copper bits (1.6; 2.4; 4.7).

A mere £4.58 for

professional spring

stand! Or buy the

lot for £11.12!

and save 10%.

All prices inc. VAT P.&P.

Please allow 14 days delivery.

Write today. Send Cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN  
or phone 01-689 0674 for Barclaycard/Access sales.



£5.58

**LITESOLD**  
LIGHT SOLDERING  
DEVELOPMENTS LTD

## Send for my CATALOGUE ONLY 75p

(plus 25p post/packing)

My VAT and post/packing inclusive prices are *the* lowest. All below normal trade price - some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS . . . ELECTROLYTIC; CAN; WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS. 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE. DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

**BRIAN J. REED**  
TRADE COMPONENTS

ESTABLISHED 25 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ

Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 5016

**CLASSIFIED**  
THE PATH TO  
SUCCESSFUL SALES!  
01-437 1002

## ADVERTISEMENT RATES

Semi-Display (min 2 cms)

1-3 insertions **£6.00** per cm

4-11 insertions **£5.50** per cm

12+ insertions **£5.00** per cm

Lineage 21p per word (min 15 words)

Box Nos. **£2.00**

Closing date 2nd Friday of the month preceding publication date.

All advertisements in this section must be prepaid. Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

Send your requirements to:

**HOBBY ELECTRONICS CLASSIFIED**  
ADVERTISING, 145, CHARING CROSS RD,  
LONDON WC2H 0EE.

**ANY SINGLE** service sheet £1/L.S.A.E. Largest stockists service/repair manuals. Named T.V. repair data £6.50 (with circuits £8.50). S.A.E. pricelists. Free publications, quotations. Aushe, 76 Churches, Larkhall, Lanarkshire.

**DIGITAL WATCH BATTERIES** any type £1.20 each. Send SAE or 15p with number or old battery to DISCLEC Y, 511 Fulbridge Road, Werrington, Peterborough.

**CLOSE ENCOUNTERS GROUP** Personal introductions and social events. Meet interesting, attractive people. Local, 051-931 2844 (24 hours).

**16K ZX81 SUPER INVADERS.** Machine code sophistication, 54 manoeuvring aliens, saucers, defence bases, laser firing, on-screen scoring. On cassette with graphic HANGMAN, SWAT, GOLF and BREAKTHRO', £3.50, J. Prince, 29 Brook Ave., Levenshulme, Manchester M19.

**LOTS OF USEFUL ITEMS** for constructors. Cases, transformers, P.C.B.'s etc. S.A.E. for list. Mr. Hyde, 3 Rosebery Road, Smethwick Warley, West Midlands B66 3R7.

**PRINTED CIRCUIT BOARDS** 4 1/2" x 6" copper clad resin paper. 10 for £4.00 including U.K. post. Hill, 22-26 Bath Road, Worcester WR6 3EL.





### MULLARD SPEAKER KIT

40 watt R.M.S. 8ohm DESIGNED BY MULLARD SPECIALIST TEAM IN BELGIUM comprising a Mullard 8" woofer with foam rolled surround, Mullard 3" high power dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loudspeaker terminals and recessed mounting panel. Supplied complete with assembly and cabinet details. Recommended cabinet size 240 x 216 x 445mm.

PRICE £13.90 + £1.50 P&P per kit



### LEADER LSG

#### WIDE BAND SIGNAL GENERATOR

- 100KHz to 100MHz in five ranges
- Up to 300MHz (Harmonics)
- Slow motion tuning
- Internal modulation 1KHz
- External mod. input facility
- Power supply 240v AC
- Size - 150x250x130mm
- Price - £63.25 - UK. Post Free

PRICE £63.25  
UK Post FREE

### 1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
  - Compact size 4 1/4" x 1 3/16" x 2 1/2"
  - Easy snap in fixing through panel/cabinet cut out
  - Insulated plastic case
  - Full wave control using 8amp triac
  - Conforms to BS800
  - Suitable for both resistance and inductive loads
- Innumerable applications in industry, the home, and discos/theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)

### BSR P256 TURNTABLE

- P256 turntable chassis
  - S shaped tone arm
  - Belt driven
  - Aluminium platter
  - Precision calibrated counter balance
  - Anti-skate (bias device)
  - Damped cueing lever
  - 240 volt AC operation (Hz)
  - Cut-out template supplied
  - Completely manual arm.
- This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price: £28.50 + £2.50 P&P




### GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems etc.

- Rolled fabric surround
- Twin cone
- 8ohm impedance
- 15 watt RMS
- 1" voice coil
- 13oz magnet
- Frequency range 50/15000Hz

Price: £6.90 each + 75p P&P

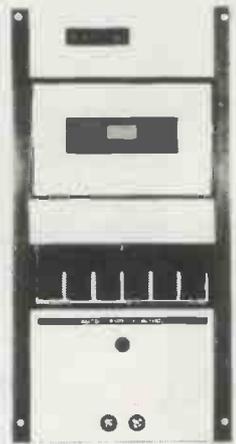

**STEREO CASSETTE TAPE DECK MODULE.** Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2in x 11 1/2in. Clearance required under top panel 2 1/2in. Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

**Price £26.70 + £2.50 postage and packing.** Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

6 piano type keys

**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price: -


15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each. £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. Price £23.70 each. £2.50 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz, Frequency Response to 6KHz, Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: White cone £8.90 each. Black cone/grill £9.50 each. P & P £1.25 each.
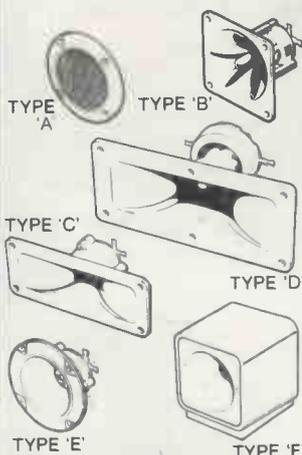
### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**TYPE 'A'** (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £3.45 each.

**TYPE 'B'** (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.35 each.

**TYPE 'C'** (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £5.45 each.


**TYPE 'D'** (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £6.90 each.

**TYPE 'E'** (KSN1038A) 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.35 each.

**TYPE 'F'** (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each. U.K. post free for SAE for Piezo leaflets).



### POWER AMPLIFIER MODULES

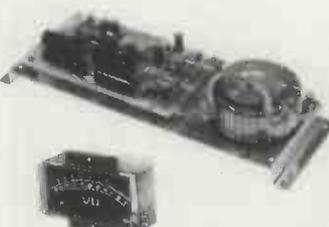

Vu Meter

### 100 WATT R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. V.u. meter, available as an optional extra.

**SPECIFICATION:**  
Max. output power 100 watts R.M.S. (OMP100)  
Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response 20Hz-25KHz ± 3dB  
Sensitivity for 100 watts 500mV at 10K T.H.D. 00.1%  
Size: 360 x 115 x 80mm  
Prices: OMP 100W £29.99 £2.00 P&P  
V.u. Meter £6.50

### Matching 3-way loudspeakers and crossover


Build a quality 60 watt RMS system 8ohms  
Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover

Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring-loaded loudspeaker terminals and recessed mounting panel. **Price £22.00 per kit + £2.50 postage and packing.** Available separately, prices on request.
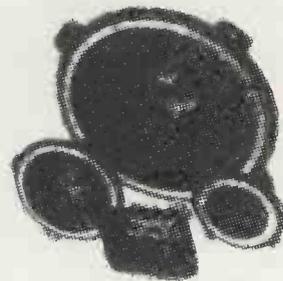
### 12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz. magnet, 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome. **Price £17.99 each + £2.50 P&P.**



# B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite


## BRANDEADING ELECTRONICS

### NOW AVAILABLE IN KIT FORM



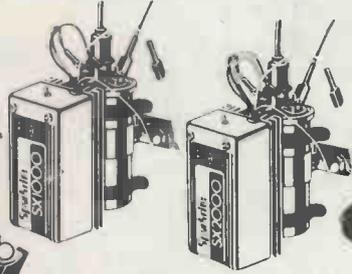
#### SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles





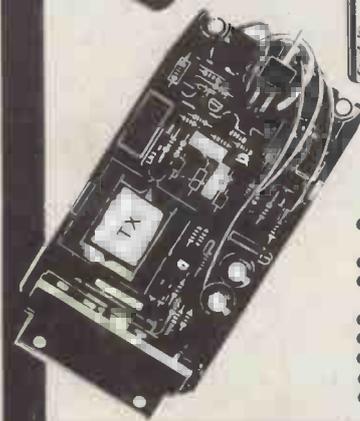
#### SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles



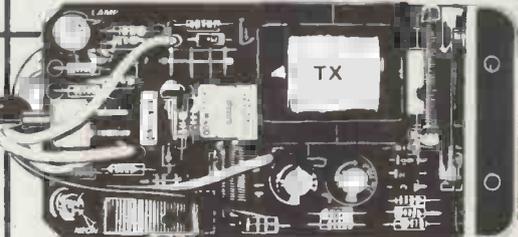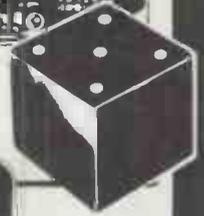
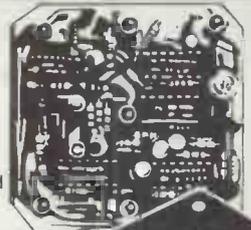
#### MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble
- Supplied in superb presentation gift box


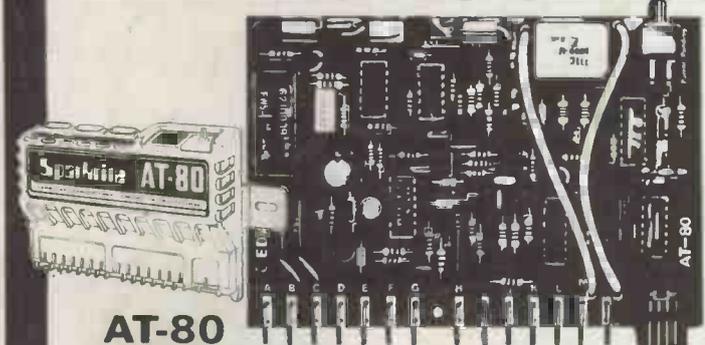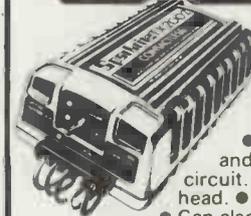
#### TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive.
- Extended coil energy storage circuit.
- Magnetic contactless distributor triggerhead.
- Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble




#### AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble
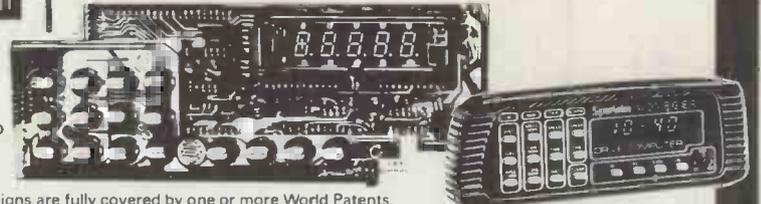
#### VOYAGER Car Drive Computer

- A most sophisticated accessory.
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time.
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on.
- Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity.
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%.
- Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours.
- Full Imperial and Metric calibrations.
- Over 300 components to assemble.
- A real challenge for the electronics enthusiast!



All EDA-SPARKRITE products and designs are fully covered by one or more World Patents.

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

|          | SELF ASSEMBLY KIT | READY BUILT UNITS |
|----------|-------------------|-------------------|
| SX 1000  | £12.95            | £25.90            |
| SX 2000  | £19.95            | £39.90            |
| TX 2002  | £29.95            | £59.90            |
| AT. 80   | £29.95            | £59.90            |
| VOYAGER  | £59.95            | £119.90           |
| MAGIDICE | £9.95             | £19.90            |

PRICES INC. VAT. POSTAGE & PACKING

NAME \_\_\_\_\_ HE582  
ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR  
£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO. \_\_\_\_\_  
24 hr. Answerphone  
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD  
SEND ONLY SAE IF BROCHURE IS REQUIRED  
Allow 28 days for delivery

BRANDEADING BRITISH ELECTRONICS  
CUT OUT THE COUPON NOW!