

Hobby

JUNE '82

ISSN 0142-6192

70p

Electronics

Project Electronics For Everyone

**POPULAR
COMPUTING
PROJECT**

**The HE
MicroTrainer**
Introducing the
Nuts and Bolts
of Microcomputers



PROJECT: MUSIC Auto-Wah
DESIGN FEATURE Power Supplies
SUMMER SPECIAL Auto Greenhouse Sprinkler

NICADS: UK's LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW -

Available at your newsagent or direct, for 70p inc.

Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 £1 discount vouchers. In a recent supplier survey, we were one of only two suppliers listed in all categories!

There's a few examples of some super low prices

- 78XX 1A 37p
- BC237/8/9 8p
- 3SK51 54p
- 10MHz XTALS £2
- 8 Pole 10.7MHz XTAL filters £14.50
- 2GHz coax relay 150W £10.95

All the "usual" stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micrometals toroids, Fairite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.

RECHARGEABLE UP TO 400 TIMES PER CELL!

CAPACITY	TYPE	1-9	10-49
500 mAh	AA	80	74
2200 mAh	C	2.35	1.99
1200 mAh	D	2.14	2.06
4000 mAh	D	3.05	2.85
110 mAh	PP3	3.70	3.50

Price on the page

CMOS		TTL N	
4000	0.11	4514	1.25
4001	0.11	4515	1.25
4002	0.12	4516	0.60
4007	0.13	4518	0.35
4008	0.50	4520	0.60
4008AE	0.80	4521	1.30
4009	0.25	4522	0.89
4010	0.30	4527	0.80
4011AE	0.24	4528	0.65
4011	0.11	4529	0.70
4013	0.25	4531	0.65
4015	0.50	4532	0.80
4016	0.22	4534	4.00
4017	0.40	4536	2.50
4019	0.38	4538	0.85
4020	0.55	4539	0.80
4021	0.55	4543	0.80
4022	0.55	4549	3.50
4023	0.15	4553	2.70
4024	0.33	4554	1.20
4025	0.15	4555	0.35
4026	1.05	4556	0.40
4027	0.26	4557	2.30
4028	0.50	4558	0.80
4029	0.55	4559	3.50
4030	0.35	4560	2.50
4035	0.67	4561	1.00
4040	0.50	4562	2.50
4042	0.50	4566	1.20
4043	0.50	4568	1.45
4043AE	0.93	4569	1.70
4044	0.60	4572	0.22
4046	0.60	4580	3.25
4047	0.68	4581	1.40
4049	0.24	4582	0.70
4050	0.24	4583	0.80
4051	0.55	4584	0.27
4052	0.55	4585	0.45
4053	0.55	4702	4.50
4054	1.30	4703	4.48
4055	1.30	4704	4.24
4056	1.30	4705	4.24
4059	5.75	4706	4.50
4060	0.75	4720	4.00
4063	1.15	4723	0.95
4066	0.30	4724	0.95
4067	4.30	4725	2.24
4068	0.16	40014	0.54
4069AE	0.14	40085	0.99
4070	0.16	40098	0.54
4071	0.16	40106	0.69
4072	0.16	40160	1.05
4073	0.16	40161	1.05
4075	0.16	40162	1.05
4076	0.55	40163	1.05
4077	0.18	40174	1.05
4078	0.18	40175	1.05
4081	0.12	40192	1.08
4082	0.18	40193	1.08
4093	0.30	40194	1.08
4099	0.80	40195	1.08
4175	0.80		
4502	0.60		
4503	0.50		
4506	0.70		
4507	0.37		
4508	1.50		
4510	0.55		
4511	0.45		
4512	0.55		

AMBIT INTERNATIONAL'S
World of Radio & Electronics
CONCISE PARTS CATALOGUE

70p
See Back for Details

3 x £1 Vouchers Inside

Prices shown EXCLUDE VAT.
Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO.

POSTAGE and PACKING
50p per order

74190N	0.55	74LS74N	0.16	74LS248N	1.35	74C76	0.48
74191N	0.55	74LS75N	0.22	74LS249N	1.35	74C83	0.98
74192N	0.55	74LS76N	0.20	74LS251N	0.35	74C85	0.98
74193N	0.55	74LS78N	0.19	74LS253N	0.35	74C86	0.26
74194N	0.55	74LS83N	0.40	74LS257N	0.40	74C89	2.68
74195N	0.55	74LS85N	0.60	74LS258N	0.37	74C90	0.80
74196N	0.55	74LS86N	0.14	74LS259N	0.80	74C93	0.80
74197N	0.55	74LS90N	0.32	74LS260N	0.50	74C95	0.94
74198N	0.85	74LS91N	0.28	74LS266N	0.22	74C107	0.40
74199N	1.00	74LS92N	0.31	74LS273N	0.70	74C151	1.52
74221N	1.00	74LS93N	0.31	74LS275N	3.20	74C154	2.26
74246N	1.50	74LS95N	0.40	74LS279N	0.35	74C157	1.52
74247N	1.51	74LS96N	1.20	74LS280N	2.50	74C160	1.05
74248N	1.89	74LS107N	0.25	74LS283N	0.42	74C161	1.05
74251N	1.05	74LS109N	0.20	74LS290N	0.50	74C162	1.05
74255N	0.66	74LS112N	0.20	74LS293N	0.40	74C163	1.05
74273N	2.67	74LS113N	0.20	74LS295N	1.50	74C164	0.80
74278N	2.49	74LS114N	0.19	74LS298N	0.76	74C165	0.84
74279N	0.89	74LS122N	0.35	74LS355N	0.32	74C173	0.72
74283N	1.30	74LS123N	0.35	74LS366N	0.34	74C174	1.05
74284N	3.50	74LS124N	1.80	74LS367N	0.32	74C175	1.05
74285N	3.50	74LS125N	0.24	74LS368N	0.35	74C192	1.08
74290N	1.00	74LS126N	0.24	74LS373N	0.70	74C193	1.08
74291N	1.05	74LS132N	0.24	74LS374N	0.70	74C195	1.08
74292N	1.05	74LS133N	0.24	74LS375N	0.40	74C200	4.52
74297N	2.36	74LS136N	0.20	74LS377N	0.85	74C221	1.06
74298N	1.85	74LS138N	0.20	74LS378N	0.65	74C901	0.38
74365N	0.85	74LS139N	0.30	74LS379N	0.60	74C902	0.38
74366N	0.85	74LS145N	1.20	74LS384N	2.50	74C903	0.38
74367N	0.85	74LS151N	0.30	74LS385N	2.05	74C904	0.38
74368N	0.85	74LS153N	0.27	74LS390N	0.29	74C905	5.64
74390N	1.85	74LS154N	0.89	74LS393N	0.68	74C906	0.38
74393N	1.85	74LS155N	0.35	74LS396N	0.61	74C907	0.38
74490N	1.85	74LS156N	0.37	74LS398N	2.10	74C908	0.84
		74LS157N	0.30	74LS399N	1.99	74C909	1.52
		74LS160N	0.30	74LS400N	2.75	74C910	0.86
		74LS161N	0.37	74LS401N	2.30	74C911	0.86
		74LS162N	0.37	74LS402N	1.40	74C912	0.98
		74LS163N	0.37	74LS403N	1.95	74C913	0.98
		74LS164N	0.40	74LS404N	1.10	74C914	4.32
		74LS165N	0.80	74LS405N	1.10	74C915	4.32
		74LS166N	0.80	74LS406N	1.05	74C916	4.32
		74LS168N	0.70	74LS407N	1.05	74C917	4.32
		74LS169N	0.85				
		74LS170N	0.80				
		74LS171N	0.80				
		74LS172N	0.80				
		74LS173N	0.80				
		74LS174N	0.40				
		74LS175N	0.40				
		74LS176N	1.05				
		74LS177N	1.05				
		74LS178N	0.90				
		74LS179N	1.35				
		74LS180N	0.75				
		74LS181N	1.22				
		74LS182N	0.70				
		74LS183N	1.20				
		74LS184N	1.20				
		74LS185N	1.20				
		74LS186N	3.00				
		74LS187N	3.00				
		74LS188N	3.00				
		74LS262N	3.00				
		74LS26					

Hobby Electronics

JUNE 1982
Vol 4 No 6

PROJECTS

★ TELEPHONE TIMER	9
<i>Save money when you dial a friend.</i>	
★ POWER SUPPLY DESIGN	12
<i>A simple design scheme with a practical example.</i>	
PROJECT: MUSIC	
AUTO-WAH	25
<i>A very special guitar-triggered effect unit.</i>	
★ BREADBOARDS	31
<i>Our new circuits page for the experimenter.</i>	
★ AUTOMATIC GREENHOUSE SPRINKLER	48
<i>A summer special — saves time and your plants, too.</i>	
POPULAR COMPUTING PROJECT	
THE HE MICROTRAINER	60
<i>A four-part project introducing the nuts and bolts of microcomputers.</i>	

FEATURES

INTO RADIO	
RADIO RULES	19
<i>Part 3 gets down to brass tracks.</i>	
FAMOUS NAMES	29
<i>Sebastian de Ferranti — the founding father.</i>	
PROJECT: MUSIC	
REVERB REVEALED	38
<i>The inside story of sound inside.</i>	
INTO ELECTRONIC COMPONENTS	43
<i>The penultimate part investigates transducers.</i>	
POPULAR COMPUTING	
ZX HARDWARE REVIEWED	65
<i>Memotech's 64K RAM Pack.</i>	
ZX SOFTWARE REVIEWED	66
<i>The Sinclair Tapes</i>	

SPECIALS

★ UNDERSTANDING COMPONENT VALUES	55
<i>The first of a new series for constructors.</i>	
★ DIGITAL COUNTERS AND TIMERS	71
<i>Digital measurements explained.</i>	

REGULARS

Monitor	6
★ POINTS OF VIEW	16
What's On Next	18
★ BUYLINES	23
PCB Service	33
★ BUILDING BLOCKS	35
Clever Dick	37
Bookshelf	53
Backnumbers	68
PCB Print Out	72
Index to Advertisers	73
Classified Advertisements	73



Editor: Ron Keeley
 Editorial Assistants: Paul Coster BSc
 Tina Boylan
 Advertisement Manager: Gary Price
 Managing Editor: Ron Harris BSc
 Managing Director: T.J. Connell

Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.
 Distributed by Argus Press Sales & Distribution Ltd, 12-18 Paul St, London EC2A 4JS. Printed by QB Ltd, Colchester. Covers printed by Alabaster Passmore.
 Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © Copyright 1982 Argus Specialist Publications Ltd. Member of the Audit Bureau of Circulation.

SALE ELECTRONIC GAMES



NOW £40 OFF

ATARI T.V. GAME
THE GAME WITH 50 CARTRIDGES
R.R.P. £129.95 (inc. VAT)

OUR PRICE
£78.22 + VAT

(= £89.95 inc. VAT)
The Atari is supplied with a free mains adaptor, a pair of paddles, a pair of joysticks and a combat cartridge and is the most popular television game on the market and has a range of over 40 different cartridges. In addition to the standard Atari range we also now stock the new Activision cartridges which are currently on special offer reduced from £18.95 to **£16.95 inc. VAT**

ATARI CARTRIDGES

20% OFF R.R.P.
Atari Soccer £29.95
NOW £23.95
Activision Dragster £18.95
NOW £14.95
Activision Boxing £18.95
NOW £14.95

ATARI OWNERS CLUB — Why not join our **FREE Silica Atari Owners Club** and receive our bi-monthly newsletter with special offers and details of the latest new cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.

MATTEL INTELLIVISION

NOW £50 OFF



THE ULTIMATE T.V. GAME
R.R.P. £229.95 (inc. VAT)

OUR PRICE
£156.48 + VAT

(£179.95 inc. VAT)
6 NEW CARTRIDGES JUST RELEASED:
ASTROSMASH * SNAFU * BOWLING
SPACE ARMADA * BOXING
TRIPLE ACTION
All 19 current cartridges + the six new ones above now retail at £19.95 — Silica special offer price **£17.95 inc VAT**

The Mattel Intellivision is the most advanced T.V. game in the world with a range of over 25 different cartridges all at our special offer price of £17.95. This game uses a 16-bit microprocessor giving 16 colours and three-part harmony sound. The picture quality is incredible with 3D effects and realistic animation. An add on keyboard will be available in the Spring 1982 to convert the Mattel into a full home computer with 16K RAM which will be fully expandable and programmable in Microsoft Basic. Other accessories will be added later in the year. The normal price of the Intellivision + free soccer cartridge is £229.95 but our special offer price is £199.95 inc. VAT saving you £50.00.

MATTEL OWNERS CLUB — Why not join our Mattel Owners Club and receive our regular newsletters containing details of all the latest cartridge releases. Telephone us with your name and addresses and we will add your name to our computer mailing list.

FREE 16 PAGE CARTRIDGE CATALOGUE — If you are interested in owning a Mattel, we now have available a 16 page catalogue describing the latest six cartridges to be released, as well as a new Mattel colour leaflet with brief descriptions of all 25 cartridges. Telephone us for further details.

T.V. GAME CARTRIDGES

We specialise in the whole range of T.V. games and sell cartridges for the following games: ATARI * MATTEL * ACETRONIC * PHILIPS * DATABASE * ROWTRON * INTERTON * TELENG. Let us know if you own any of these games and we will let you have details of the range of cartridges available.

Attention INTERTON & ACETRONIC owners we have over 75 assorted used cartridges in stock all with 1 year guarantee — **SPECIAL OFFER £8.95 each**

We also have a number of secondhand games and cartridges.



NOW £8 OFF

HAND-HELD GAMES
EARTH INVADERS

These invaders are a breed of creature hitherto unknown to man. They cannot be killed by traditional methods — they must be buried. The battle is conducted in a maze where squads of aliens chase home troops. The only way of eliminating them is by digging holes and burying them.

R.R.P. £26.95 **NOW £18.95 inc. VAT**

PAC MAN 2

Pac Man 2 is based on the latest pub game. It is a two-colour game of strategy, tactical pursuit and destruction pitting Pac Man against the large Ghosts. The object of the game is for Pac Man to attain as high a score as possible by capturing and destroying Ghosts. Bugs and Energizers without being himself destroyed by the Ghosts. Pac Man 2 incorporates the most modern and complex status displays ever produced and is now on release for the first in the UK offering an ideal present.

R.R.P. £34.95 **NOW £24.95 inc. VAT**



SPECIAL REDUCTIONS

ELECTRONIC CHESS

Liquid crystal battery chess computer with 100-200 hrs battery life and two levels of play. Comes with separate chess board and pieces.

NOW £5 OFF
R.R.P. £24.95
SALE PRICE
£19.95

GRADUATE CHESS

A de luxe version of the electronic chess set with integral chess board. The ideal portable chess set — see illustration.

(inc. VAT)
NOW
£29.95
INC VAT

FIDELITY MINI-SENSORY CHESS COMPUTER

The very first chess computer of its price to offer a portable computer with integral sensory board. Battery (6-8 hrs) or mains operated. This is a modular game and additional plug-in modules are planned for 1982 for advanced chess, popular openings, greatest master games, draughts and reversi.

MINI-SENSORY COMPUTER WITH STANDARD CHESS MODULE WAS £54.50 **NOW £49.95 INC VAT**

Silica Shop are one of the country's leading specialists in Chess Computers and now stock a range of more than 20 Chess Computers, including Challenger 7/10/Voice, Sensory 8 and Sensory Voice, Diplomat, System 3, Morphy, Great Game Machine, Voice Champion, and the new Scicys Mark V.



NOW £10 OFF

SPACE INVADERS

Based on one of the most popular arcade games, Space Invaders™ packs in lots of action with multi-shaped, brilliant LED vessels, including attack ships, bombs, defenders, missile rockets and a beam force cannon, plus exciting electronic sound effects. The attack ships attempt to bomb the ground defenders as they are moving. You manoeuvre the missile rockets — avoiding alien bombs — and destroy the invader force as quickly as you can. Progressive degree of difficulty. Includes automatic digital scoring. For ages 6 to adult.

R.R.P. £24.95 **NOW £16.95 inc. VAT**

LESS THAN 1/2 PRICE

COLOUR CARTRIDGE T.V. GAME
Semi-programmable T.V. game + 8 cartridges + mains transformer
NOW £43.80 OFF
R.R.P. £73
SALE PRICE £29.50 inc. VAT

500P PURCHASE NOW 1/2 PRICE

BACKGAMMON COMPUTER
Silica stock a wide range of Backgammon computers from £28.95 upwards. Special offers now available on Gammomaster.
NOW £48.95 inc. VAT

CALL JOTTER — THE AFFORDABLE ANSWER
The Post Office certified telephone answering machine

"Sorry darling, I will be late home — Love John"

The Call Jotter 1 brings the affordable answer at the amazing price of £69 (or £99 for the Call Jotter 2 with built-in remote recall facilities). These amazing telephone answering machines are Post Office certified and guaranteed for one year. They make a thoughtful gift for home or business use.

NOW £69.00 inc. VAT

NOW £75 OFF

RADOFIN TELETEXT

Plug the adaptor into the serial socket of your colour TV and receive the CEESAT and ORACLE television information services.

THIS NEW MODEL INCORPORATES

- *Double height character facility "True PAL Colour"
- *Meets latest BBC £16A broadcast specifications
- *Push button channel change
- *Unnecessary to remove the unit to watch normal TV programmes
- *Gold plated circuit board for reliability

ADD-ON ADAPTOR
WAS £199 inc. VAT
SALE PRICE £124 inc. VAT


FOR FREE BROCHURES — TEL: 01-301 1111



For free illustrated brochure and reviews on our range of electronic games, please telephone 01-301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/BARCLAYCARD number, and leave the rest to us. Post and packing free of charge. Express 48 hour delivery service available.

- **CALLERS WELCOME** — Demonstrations daily at our Sidcup shop open from 9am-6pm Monday-Saturday (Early Closing Thursday 1pm. Late Opening Friday 8pm).
- **2 YEAR GUARANTEE** — All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee.
- **MONEY BACK UNDERTAKING** — If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.
- **AFTER SALES SERVICE** — Available on all machines out of guarantee.
- **COMPETITIVE PRICES** — We are never knowingly undersold.
- **HELPFUL ADVICE** — Available on the suitability of each machine.
- **CREDIT FACILITIES** — Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
- **PART EXCHANGE SCHEME** — Available on second hand machines.
- **CREDIT CARDS WELCOME** — Access, Barclaycard, Diners Club, American Express.

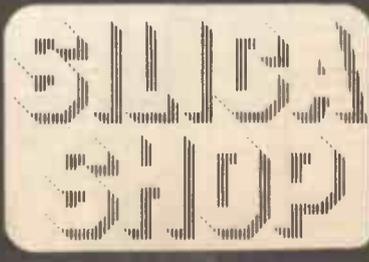SILICA SHOP LIMITED HE0682
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX
Telephone: 01-301 1111 or 01-309 1111



MONITOR

JUST in time for the summer is what may be the first of a new trend in holiday activities — a leisure-learning holiday. The organiser of Britain's first such holiday, a **Computer Holiday Camp** at the University of Southampton, is Dr. Lionel Wardle, of Management and Personal Services.

The Computer Camp will be not only for teenagers, but for anyone interested in computers; beginners, enthusiasts, professional people and even those suffering from "computer-phobia". Computer Campers will have access to a variety of popular microcomputers and can either learn by themselves, taking advantage of expert advice if they get stuck, or attend the tuition sessions, workshops and demonstrations which will be provided, before going on to get hands-on experience. Recognising the obsession that people sometimes develop with computers, machines will be available 20 hours a day, allowing the dedicated computer-phile maximum time at the keyboard.

On particular weeks, specially designed courses can be scheduled for common-interest groups, while an experienced management consultant will be on hand with advice for the small businessman and the self-employed.

The Computer Camps are being organised as family holidays; to help people who might otherwise be prevented from attending because of family arrangements, accommodation will be provided for family or kids at half price. Each participant will have his or her own study-bedroom in a flat or house on the University campus and all its sporting and recreational facilities will be available, free, plus the South Coast and the New Forest thrown in for good measure.

The cost of a week's Computer Camping at the University of Southampton is £115, self-catering; details and bookings from Dr. Lionel Wardle, Management and Personnel Services, 37 University Road, Highfield, Southampton SO2 1TL; Tel. 0703 558621.

Finally, just in case it seems like more work than play, a variety of computer games will also be available, but the organisers warn that these can be highly addictive — as if we didn't know!

News on the NiCad front, this month, from Verospeed. Their new 'Combisix' battery charger is a mains-powered unit which can handle up to six rechargeable Ni-Cad cells in AA, C or D sizes. The six individual charging points are located in two banks of three, on either side of the charger, and each bank can be adjusted to accept up to three cells.

Cells of different sizes can be mounted on either side and AA and C cells can be intermixed. A selector switch offers four charging rates; 50, 120, 180 or 400 mA. The Combisix is priced at around £22. Further information is available from Verospeed, Stanstead Road, Boyatt Wood, Eastleigh, Hants SO5 4ZY; Tel. 0703 618525.

Further to our survey of **The Affordable Computer**, in the April '82 issue, we would like to report that **Watford Electronics**, suppliers of everything electronic for the hobbyist, are also distributors of the **Superboard II** computer. Contact them at 35 Cardiff Road, Watford, Herts or 'phone 92 40588.

A soldering iron is probably the single most important tool for an electronics enthusiast, hence a new range of irons (middle), manufactured by **Adcola for OK Machine & Tool (UK) Ltd**, look quite interesting for the hobbyist. At the moment the range consists of two thermostatically controlled, thermally balanced instruments plus one temperature controlled iron. They conform to a number of safety standards including BS3456.

Model OK-001 operates from 240 V and has a short element barrel for effective tip control and a handle which remains cool even after hours of continuous use; it weighs just 43 gr and the barrel is only 51 mm. Model OK-002 is similar, but the barrel is 88 mm long and it weighs 50 gr. Temperature ranges of these irons are 380°C and 400°C respectively.

The proportional control iron, Model OK-003, operates from 24 V 50 Hz and has a variable temperature range of 250°C-450°C. Control is by means of a special IC built in to the handle. It can be totally earthed and has a burn-proof siliconised rubber cable. For further information contact **OK Machine & Tool (UK) Ltd**, Dutton Lane, Eastleigh, Hants SO5 4AA or 'phone 0703 610944.

New from **Global Specialities Corporation**, this month, is a new breadboarding system which is ideally suited to microprocessor based projects and applications involving large numbers of IC packages.



The 'Superboard' PB-105 measures 9.2 x 11.4 inches and can carry up to 48 14-pin DIL packages.

For further information contact **Global Specialities Corporation**, Shire Hill Industrial Estate, Saffron Walden, Essex GB11 3AQ.

Let's face it, nothing works perfectly, even (or is it especially?) electronic equipment and occasionally it will be necessary to remove components from a PCB. A rather handy tool for the job is a de-soldering tool or solder-sucker, as the Americans call them; the latest additions to the **Tele-Production Tools** range for the electronic enthusiast are two new de-soldering guns (bottom).

The first, 200 mm long and 19 mm in diameter, is intended for most general work while the second, only 165 mm long and 14 mm dia., is a miniature de-solder gun for fine work. Both have plunger guards, can be operated one-handed and they have powerful suction action and low recoil, to leave joints clean and tidy; solidified solder is ejected each time the gun is reset.

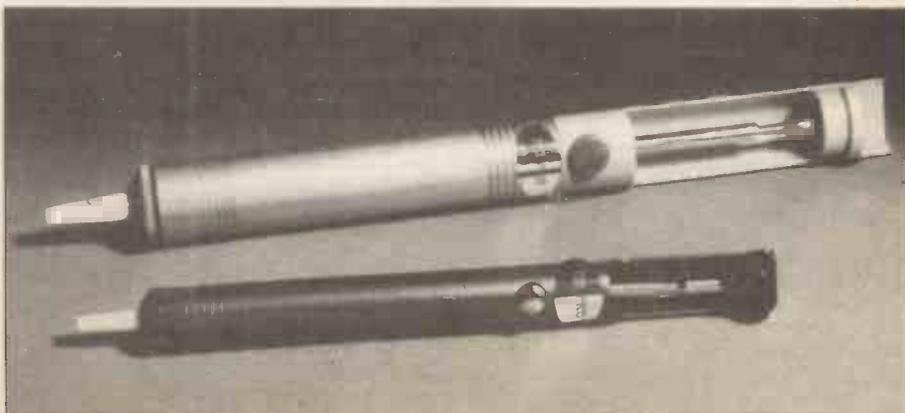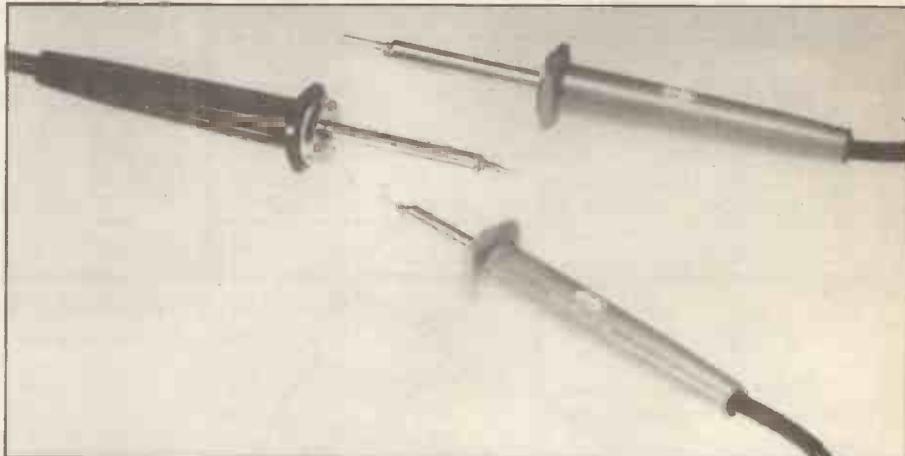The guns cost £5.95 each, including VAT and carriage, or £10 the pair. For details contact **Tele-Production Tools**, Stiron House, Electric Avenue, Westcliff-on-Sea, Essex SS0 9NW; Tel. 0702 352719.



MONITOR

For the benefit of our readers who own or rent video cassette machines, we pass on the following warning from Panasonic.

Recently, quantities of counterfeit video cassette tapes bearing the brand-name "PANASONIC" have been found circulating throughout the UK. These cassettes copy the Panasonic design and packaging and may not be immediately noticeable as counterfeits. However, the tape is reported to be "substantially inferior" to the genuine article and, besides producing poor picture quality, they could cause damage to the video machine.

Potential customers are urged to buy Panasonic video cassettes only from authorised Panasonic dealers throughout the UK. If in doubt — don't buy; the price may be attractive but the picture and sound quality probably won't be. Official Panasonic dealer lists are available from their Sales Promotion Departments at Slough, Berks (Tel. 75 34522) or Normanton, West Yorks; Tel. 0924 890980.

Catalogue Collectors take note: Clairtronic Ltd, a specialist distributor of low voltage transformers, have produced an illustrated brochure detailing their stock of miniature mains transformers covering powers from 0.2 to 50 VA. The prices listed included p&p within the UK and range from around £1.30 up to £5.98; VAT is not included.

The range comprises four constructions; double bobbin transformers in both chassis and circuit mounting forms, an encapsulated series including the square box 'top hat' type plus a low-profile range with heights as low as 17 mm. The brochures are available from Clairtronic Ltd, Churchfield Road, Chalfont St. Peter, Bucks; Tel. 49 87277.

Still on the popular subject of Computing, PET owners everywhere will be interested in the Third International Commodore Computer Show, to be held at the Cunard Hotel, Hammersmith, London, between 3rd and 5th June 1982. It will be, we are assured, the "biggest and best" Commodore Show ever, with over 100 exhibitors displaying their wares.

The Show will include many innovative products from Commodore and a number of original software programs by "approved product suppliers". Hardware will include the Commodore Ultimax, the VIC-20, VIC-40, the Commodore 64, the 4000 and 8000 series and the CBM 128 and 256 machines. Specialist applications demonstrations will cover the needs of specialist businesses, educational users and communications applications. The VIC Colour Computer and a range of VIC software will also be on display while special seminars, with guest speakers, will introduce businessmen and other professional users to the microcomputer. See you there?

Also received from OK Machine & Tool, recently, was their new Electroware catalogue. The Electroware division supplies tools and accessories for "everyone" (that certainly means us!) involved in building electronic equipment.

The catalogue lists products from OK's bench tool range, wire-wrapping kits, IC tools, PCBs, cases and enclosures, connectors and sockets, plus Ni-Cad battery chargers, soldering equipment and instruments such as multimeters, pH meters and capacitance meters. The Electroware range is available nationally from leading electronic and computer stores or directly from OK, at the address noted earlier. Write for a free catalogue, but send 30p for postage.

One of the greatest attractions of computing is that it can be fun. Of course, when the program has failed for the umpteenth time or the keyboard has locked out for some totally inexplicable reason, fun is replaced by frustration — but then life's like that (to paraphrase Alexei Sayle).

Putting greater emphasis on the "fun" aspect, B&B Ltd, of Bolton, have launched a new game package for the VIC computer, called VIC 6. The six games on the cassette are designed to challenge the hobbyist — and the professional user. They cover old favourites such as the three-reel fruit machine, Hangman and Roulette and go on to missile game, a wall brick game and a "stay out of trouble under fire" game. The company intends to produce six more packs, enabling the VIC user to build up a library of cassettes; they have set up a mail order operation to handle all enquiries about the VIC 6 and future products. For further information 'phone Beelines on 0204 382741.

A new point-to-point wiring system, just released by BICC-Vero, is mainly intended for circuit prototypes and small-scale production runs. It would also prove useful for the hobbyist who is developing a project too large to be handled by the usual breadboarding methods.

The Speedwire system provides rapid wiring using novel insulation-displacement joints and a special hand wiring tool. Continuous joints are easily made without the need to cut and strip the wire.

The heart of the system is a double-sided push-fit contact and the wiring pen, which pushes the wire between the terminal's tines. Each double-forked terminal will accept one or two wires; the component side of the contact is gold-plated beryllium copper, designed to give a very low contact resistance.

Full details are available from BICC-Vero Packaging Ltd., Industrial Estate, Chandlers Ford, Eastleigh, Hants. SO5 3ZR; Tel 04215 66300.


HE

Top quality transformers



CLAIRTRONIC LTD, CHURCHFIELD ROAD, CHALFONT ST PETER, BUCKS. HP8 5EP. TEL: 49 87277. TELEX: 147777 ULRAY G ATTR CLAIRTRONIC

Miniature mains transformers

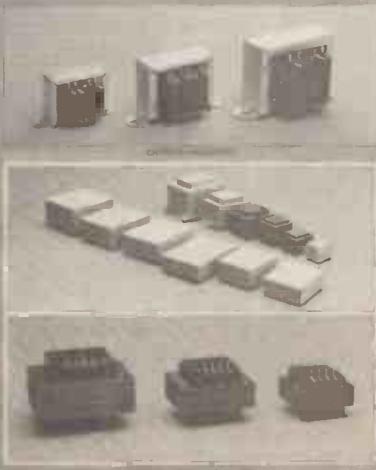

TEMPERATURE AND INSULATION	MINI-TRANS		ENCAPSULATED	
	0-50	100-125	100-125	100-125
WARRANTY PERIOD	1 YEAR	1 YEAR	1 YEAR	1 YEAR
MATERIALS	WAX	WAX	WAX	WAX
PROTECTIVE TUBING	NO	NO	NO	NO
TESTED TO	100%	100%	100%	100%
PRICE PER UNIT	£1.30	£1.30	£1.30	£1.30



ELECTROWARE

CATALOGUE

The Rapid Electronics

Tel: 0206 36412
Hill Farm Industrial Estate
Boxed, Colchester
Essex CO4 5RD



LINEAR

★ 555 CMOS 80	ICL7106	790	LM382	120	LM3302	150	SL480	170	★ KR2206	300
★ 556 CMOS 150	ICL7611	95	LM386	65	★ ML922	400	SL490	250	ZN414	100
★ 709	ICL7622	180	LM387	120	ML924	195	SN76477	250	ZN423	135
★ 741	ICL8038	320	LM393	100	ML925	210	TBA800	80	ZN424	135
★ 748	ICM7555	80	LM709	25	ML926	140	TBA800	96	ZN425E	330
★ 9400CJ	ICM7556	150	LM710	50	ML927	140	TBA820	80	ZN426E	630
★ AY-3-1270	LF351	45	LM725	350	ML929	140	TBA950	290	ZN428E	480
★ AY-3-8910	LF353	85	LM711	60	ML928	140	TCA940	170	ZN1034E	200
★ AY-3-8911	LF356	90	LM733	75	NE515	270	TDA1004	300		
★ 625	LM10	395	★ LM741	14	NE529	225	TDA1008	120		
★ CA3046	LM301A	25	LM747	75	NE531	150	TDA1022	560		
★ CA3080	LM311	70	LM748	35	NE544	300	TDA1024	125		
★ CA3089	LM318	120	LM750	35	NE555	16	TL071	45		
★ CA3090AQ	LM324	40	LM2917	200	★ NE556	45	TL072	65		
★ CA3130	LM339	50	LM3900	50	NE565	120	TL074	65		
★ CA3140E	LM348	65	LM3911	120	NE566	150	★ TL081	30		
★ CA3160E	LM358	50	LM3914	200	NE567	100	TL082	50		
★ CA3160	LM357	150	LM3915	220	NE571	425	TL084	95		
★ CA3189	★ LM380	65	LM13600	120	SC4136		TL170	50		
★ CA3240	LM381	120	MC1310	150	SN76018	150				

TRANSISTORS

★ AC125	35	★ BC157	10	★ BC158	10	★ BC159	8	★ BC170	18	★ BC171	18	★ BC172	18	★ BC173	18	★ BC300	18
---------	----	---------	----	---------	----	---------	---	---------	----	---------	----	---------	----	---------	----	---------	----

CMOS

★ 4001	14	★ 4002	14	★ 4003	14	★ 4199	14	★ 4200	14
--------	----	--------	----	--------	----	--------	----	--------	----

TTL

★ 7411	24	★ 7412	24	★ 7413	24	★ 7563	24	★ 7564
--------	----	--------	----	--------	----	--------	----	--------



Telephone Timer

Keep Buzby at bay with this money-saving project.

Part 1: The circuit and How It Works.

Part 2, next issue, will cover the construction and wiring details.

TELEPHONE RATES in Britain are based on the number of seconds allowed for a certain charge — which went up to 5p even as this project was being designed (thanks, Buzby). There are three rates, depending on the time of day and three distance rates. The charge system is outlined in your Telephone Directory and also in Table 1. This shows, for example, that for a Local call at the Cheap rate, 5p buys 480 seconds of telephone-time, whereas a long-distance call during Peak time costs 5p for only 12 seconds. Looking at it another way, 5p buys 95 five-second 'units' for a Cheap rate Local call, while the same 5p buys 2.4 'units' for long-distance at the Peak rate.

This method of using five-second intervals has been adopted because it allows a very straightforward circuit — the Telephone Timer may look complicated but in fact it is quite simple, in principle. It just counts a

certain number of five-second units — 96, say — and increments the display when this number is 'up', to give a direct read-out in pounds and pence. When the device is reset at the beginning of a call, the display shows '5p' because this is the cost of the first time period — 480 seconds or 96 units, in our example; each subsequent period costs another 5p.

On the front panel, a 10 position rotary switch selects any of the nine possible areas and charge-band times. The final switch position gives direct time readout, ie the display shows seconds rather than pounds and pence. This position is intended for international calls, because there is such a variety of costs and times that it would not be practical to include switch positions for international dialling.

Operation is quite simple. When you want to make a call, first switch the

Telephone Timer on and Reset the display. Dial the number and press down the Start Button when the line is ringing. When the call is answered, release the button and the Timer will start. When the call is finished, repeat the process and read off the cost of the call. Place hand into pocket, remove the appropriate amount and place it into telephone box! Should you be making more than one call, area just press the start button again; to zero the display, simply press the Reset button.

The Telephone Timer will never go out of date, either. This is because it can be programmed for any rate! The 'unit table', which is translated into a wired patch-board, is shown in Table 1. Thus, when the cost rises (it isn't getting cheaper) you simply adjust the patches on the board. All the values are rounded up, where necessary, so that your bill is covered. ▶

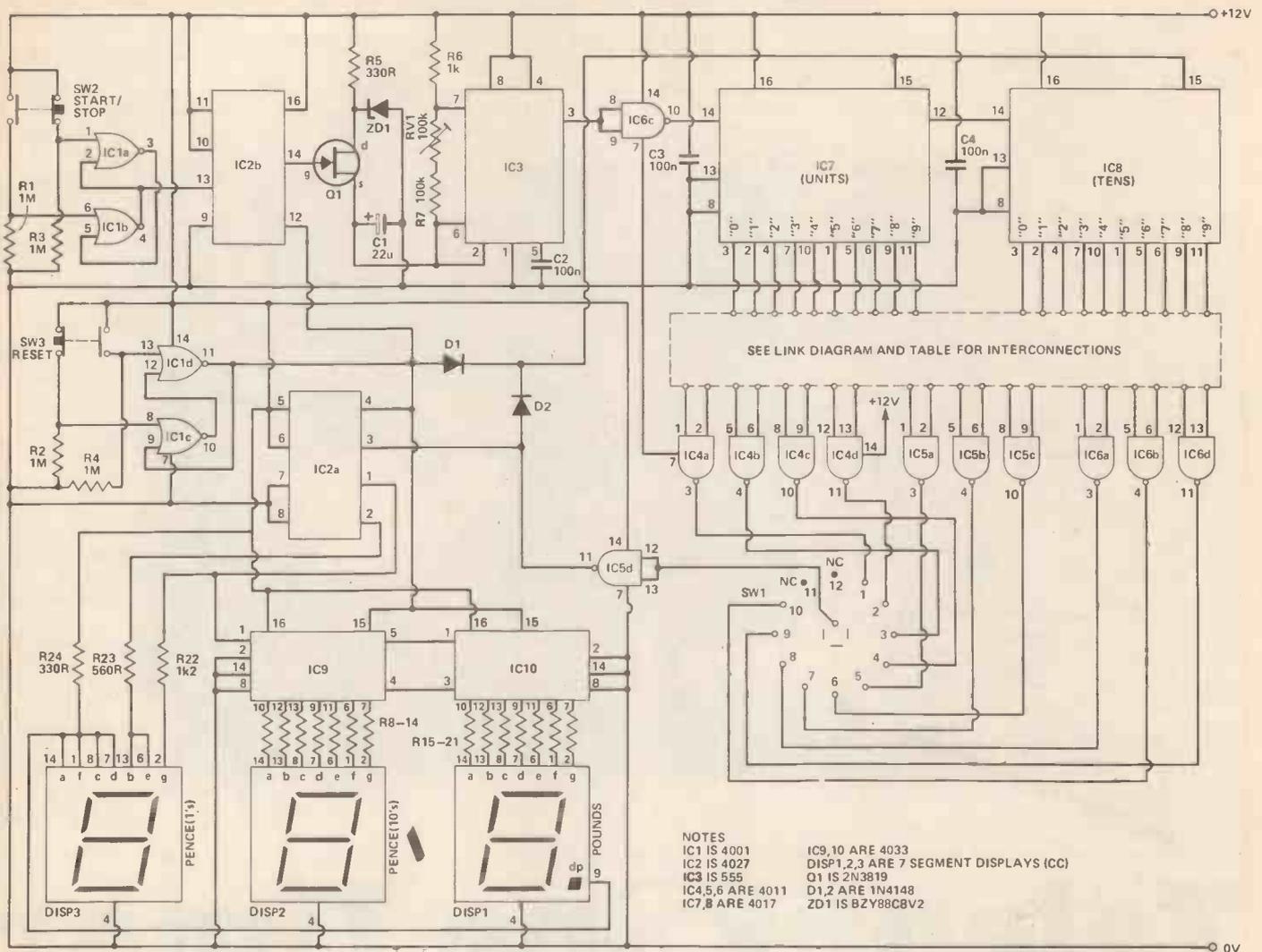


Figure 1. The complete circuit diagram of the Telephone Timer. The Link Diagram, which shows how to program the Timer for the various charge-bands, will be published in the July issue.

TARGET TIME (SECONDS)	TIME RECORDED (SECONDS)	ACCURACY (PERCENT)
480	468.0	-2.5%
120	117.5	-2.1%
90	88	-2.2%
145	141.5	-2.4%
45 (90)	44 (88)	-2.2%
30 (90)	29.5 (88.5)	-1.7%
50 (100)	49 (98)	-2.0%

Figure 2. Tests on our prototype show that the Timer is accurate to within +0/-2.5%.

The Circuit

The design is based on the fact, mentioned earlier, that the times allowed for a fixed charge (currently 5p) is approximately divisible by five. Therefore, a 555 timer, IC3, is used to supply a square wave with a Period of five seconds (a frequency of 0.2 Hz). This signal is fed to a pair of 4017 decade counters, ICs 7 and 8, which directly count the number of 0.2 Hz clock pulses.

The NAND gates, IC4a, b, c, d, IC5a, b, c and IC6a, b, d, are used to

decode the counter inputs. By connecting the relevant counter outputs to the gate inputs, each gate will produce an output pulse when the count corresponds to the preselected number of 5 S intervals. The appropriate output is selected by SW1, a 10-position switch. This pulse is used to reset the decade counters, via IC5d and D2, and also to drive a divide-by-two flip-flop, IC2a. The flip-flop is triggered by a rising edge (ie a transition from 0 to 1).

The squarewave produced by IC2a is used as the clock input for the 7-segment display decoder/drivers, ICs 9 and 10, which are the 'pounds' and '10p' display drivers. The third ('pence') display is driven directly by the Q and Q outputs of the flip-flop; since this only ever shows either '0' or '5', no further decoding is necessary.

The system is started and stopped by operating a push-button switch, debounced a bistable flip-flop, IC1a, b. When the button is pressed the output is one state — either high or low — and when it is released, the output reverses. The start/stop pulse is fed to

another flip-flop, IC2b; when a rising edge appears at its clock input, its output changes state. IC2b controls the 555 (IC3) so that when the start/stop button is first pressed, the 555 starts running and when it is re-pressed, the timer stops, freezing the displays. The frequency of the timer is controlled by the voltage on its trigger pin (pin 2), supplied by a field effect transistor, Q1. The Zener diode is used to supply 8V2 to the trigger pin when the FET is conducting, since an error would arise in the initial time period if the trigger line was simply driven between +12 V and 0 V, due to the time it would take C1 to charge and discharge. The reset push-button simply resets all the devices in the circuit, via bistable IC1c, d and D1, returning the system to the 'start' condition.



Next month, we will give detailed instructions for assembling the Telephone Timer and describe how the device may be programmed for the nine Buzby charge bands. In the meantime, see the **Buylines** page for helpful hints on where to get the components for this money-saving project.

How It Works

The Telephone Timer simply counts a preset number of five-second 'units' and increments the display at the end of each group of units. The display gives a direct read-out, in pounds and pence. The Timer is set up to produce 0.2 Hz clock pulses (ie a Period of 5 S) to drive the decade counter/dividers, which directly count the number of clock pulses. The counter outputs (tens and units) are decoded by a group

of NAND gates to select the appropriate number of 5 S intervals corresponding to the telephone charges (see text and Table 1); each gate will produce an output pulse at the end of a certain number of 5 S intervals. The required charge-rate is selected by a 10-position switch which feeds the pulse to a divide-by-two flip-flop. This pulse also resets the decade counters to zero so that another timing period can commence. The complementary outputs of the flip-flop are used to

directly drive the 'pence' display (which always alternates between '0' and '5') and the '10p' decade counter/7-segment decoder — this increments by one at half the rate of the 'pence' display; the 'pounds' decoder/driver is driven by the Carry output from the '10p' counter. The 5 S interval timer is started and stopped by a debounced push-button switch. The Reset switch is also de-bounced and resets all counters to zero — the display shows '5' at this time.

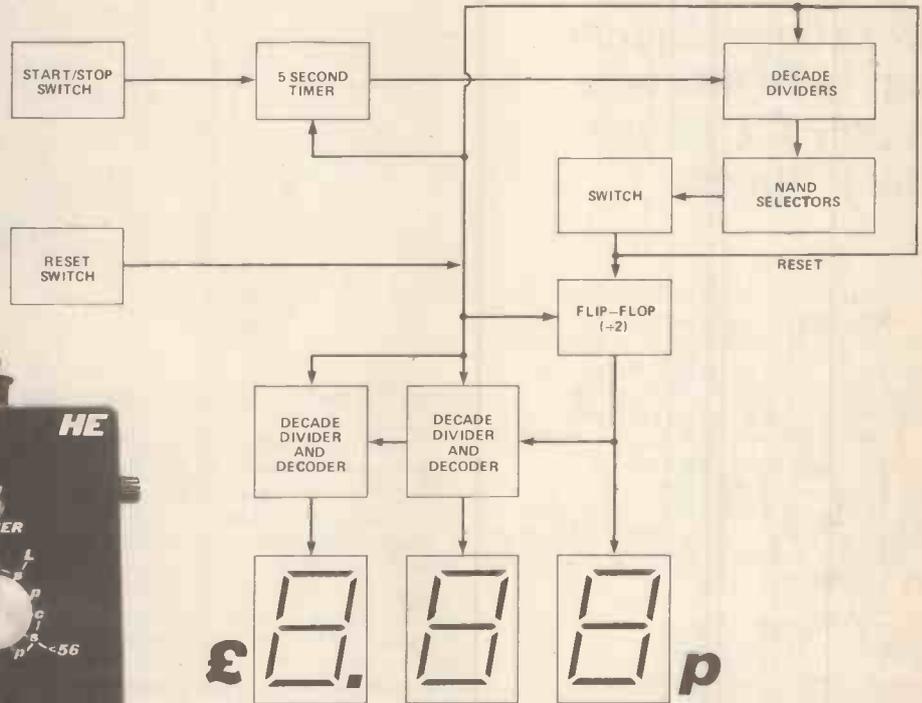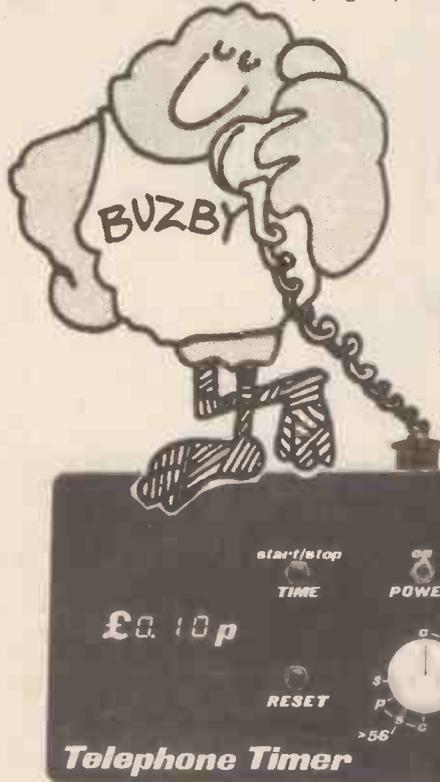

Parts List

Table 1.

Distance	Rate	Rate seconds for 5p	No. of 5 S units*
LOCAL	CHEAP	480	96
	STANDARD	120	24
	PEAK	90	18
< 56 km	CHEAP	144	29
	STANDARD	45	9
	PEAK	30	6
> 56 km	CHEAP	48	10
	STANDARD	16	*4
	PEAK	12	*3

* ROUNDED UP.

Table 1. The telephone charge bands and the times allowed for a 5p unit. The last column shows the number of five second units in each band; the bottom two figures are rounded-up so that the amount calculated by the Timer will be slightly higher than the actual charge.

RESISTORS

(All ¼ watt 5% carbon)
 R1,2,3,4 1M
 R5 330R
 R6 1k
 R7 100k
 R8-22 1k2
 R23 560R
 R24 330R

POTENTIOMETERS

RV1 100k
 sub-min. horizontal preset

CAPACITORS

RV1 100n
 disc ceramic or polyester
 C2 22u 25 V
 tantalum bead

SEMICONDUCTORS

D1,2 1N4148
 signal diode
 ZD1 BZY88C8V2
 zener diode
 Q1 2N3819
 N-channel FET
 IC1 4001
 CMOS quad 2-input NOR

IC2 4027
 CMOS dual J-K flip-flop
 IC3 NE555 timer
 IC4,5,6 4011
 CMOS quad 2-input NAND
 IC7,8 4017
 CMOS decade counter/divider
 IC9,10 4033
 CMOS counter/decoder/divider
 DISP1,2,3 DL704 or similar
 common cathode 7-segment display


MISCELLANEOUS

SW1 rotary switch,
 1-pole 12-way
 SW2,3 SPDT miniature
 push-to-change switch
 SW4 DPDT miniature
 toggle switch
 Bulgin 3-pin mains plug, socket;
 20 mm panel mounting fuseholder;
 750 mA fuse; knob; plastic for display
 window (red); PCBs; mains cable;
 mains plug; ribbon cable; case; screws,
 nuts and bolts; 12 V power supply (see
 PSU Design project); Veropins; IC
 sockets (optional); solder; wire etc.

BUYLINES page 23

Designing Power Supplies

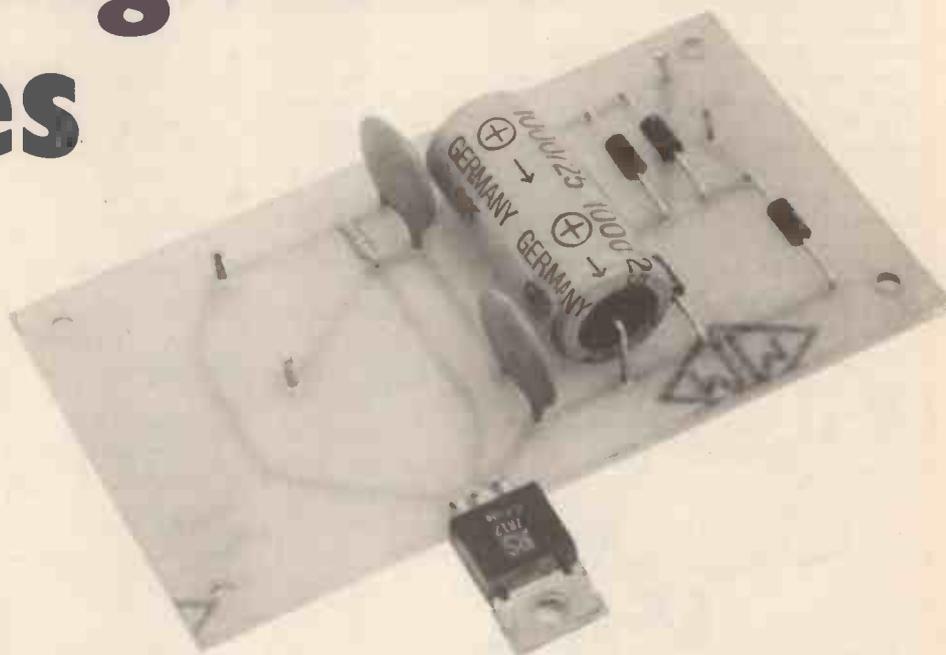Using this simple procedure, anyone can build a simple supply for almost any purpose.



THE POWER SUPPLY is one of the most fundamental circuits in all electronics. It is also one of the easiest circuits to design yourself, once you have the 'know how'. This article is intended to give you just that skill.

This month, we feature a project for a digital Telephone Timer which requires a 12 V, 400 mA regulated supply (Figure 1) and this will be used as an example, to demonstrate how the component values of a simple supply are calculated.

The Theory

Before you can begin to design a circuit, there is certain information that you must have at your fingertips. For power supplies, it is necessary to know the peak input voltage and the output voltage. The 'input' is the voltage delivered by the transformer to the rectifier. Unfortunately, this is not the voltage usually specified by transformer manufacturers, but it is easily obtained by multiplying the RMS voltage (which is specified) by 1.4 (see Figure 2). You might expect that this is the voltage delivered by the power supply — not so. Some voltage will be lost across the bridge rectifier. Most diodes produce a forward voltage drop (ie, when they are conducting) of about 0.7 and, since there are always two diodes passing current in a bridge, the drop across the bridge will be roughly 1.4V.

The makers of voltage regulator ICs always specify some minimum voltage input to their device and it is generally about 2V5 higher than the required output voltage (eg, a 5 V regulator needs 7V5). To be on the safe side, assume that the minimum is 3 V higher. Now we know the maximum voltage which we can expect from the bridge rectifier, V_{BRIDGE} , and the minimum voltage needed to drive the regulator IC. The next step is to calculate the value of the filter capacitor, C1, which is there to

'smooth' the rectified mains voltage for the regulator IC.

The effect of the smoothing capacitor is shown in Figure 3. It charges up with each voltage peak, then discharges slowly as the rectified voltage falls to zero. The discharge time is such that C1 will not discharge completely, however, so the voltage never falls below a certain level which (aha!) must be the regulator minimum input voltage. The difference between the voltage peaks and the regulator minimum is the ripple voltage, V_R . Obviously, the value of the smoothing capacitor must be chosen so that the input voltage to the regulator never falls below the specified minimum.

The diagram of Figure 3 shows cycles of the rectified mains voltage, enlarged. The quantity 'T' is the time (Period) between voltage peaks and it is equal to twice the mains frequency of 50 Hz ie, 100 Hz. Since the period, T, is the inverse of the frequency, T is 0.01 seconds.

Now a capacitor in a circuit which has resistance (and every circuit will have at least some resistance) will take a definite time to discharge the voltage

stored on its plates. This time is the familiar RC time constant:

$$t = RC,$$

where t is the time, in seconds; C is the capacitance in Farads and R is the resistance in Ohms. Now from Ohm's Law, we also know that:


$$R = \frac{V}{I},$$

therefore, substituting the second equation into the first, we get:

$$t = \frac{CV}{I}$$

where I is the current required from the circuit; t is the time period over which the capacitor discharges and V is the voltage discharged in time t.

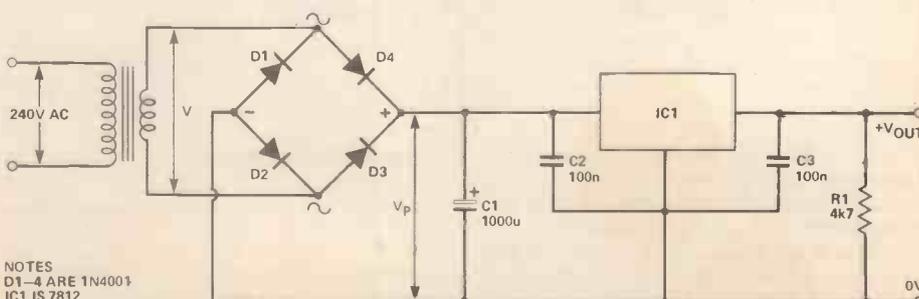Now, since we don't want the capacitor voltage to drop below a certain minimum, V is the ripple voltage V_R , the difference between the rectified voltage peaks and the regulator minimum, and t is the period of the full-wave rectified mains.



NOTES
D1-4 ARE 1N4001
IC1 IS 7812

Figure 1. A simple regulated supply using one of the common three-terminal regulator ICs.

For Example

The remainder of the procedure is best illustrated by a practical example. The Telephone Timer requires a 12 V, 400 mA supply, as mentioned earlier. To choose a suitable transformer, select one which produces a slightly higher voltage than that required — usually the next one up in the range will do the trick, ie one with a 15 V winding. The power handling of a transformer is sometimes specified as Watts, but more often in terms of VA (Volt Amps). To calculate how many Watts (or VA) are required, use the simple power formula:

$$W = VI = 12 \times 400 \times 10^{-3} = 4.8 \text{ VA (Watts).}$$

In fact, the most suitable transformer available was one with twin 15 V windings, each supplying 3 VA; the windings were simply connected in parallel to give the required voltage and a power capability of 6 VA.

The next step is to calculate the voltage output from the bridge rectifier:

$$\begin{aligned} V_{\text{BRIDGE}} &= V_p - 1.4 \\ &= (V_{\text{RMS}} \times 1.4) - 1.4 \\ &= (15 \times 1.4) - 1.4 \\ &= 19.6 \text{ volts.} \end{aligned}$$

The regulator IC needs at least 15 V, so we are on the safe side with 19V6. The difference is the ripple, V_R :

$$V_R = 19.6 - 15 = 4.6 \text{ V.}$$

Now, using the formula for calculating the value of the smoothing capacitor C_1 , we have:

$$\begin{aligned} C &= \frac{tI}{V_R} = \\ &= \frac{0.01 \times 400 \times 10^{-3}}{4.6} \\ &= 870 \text{ uF} \end{aligned}$$

This is not a preferred value, so use the next highest in the range, which is 1000 uF. It must cope with peak voltages of $15 \times 1.4 = 21 \text{ V}$, so use a 25 V working electrolytic type.

Another point to consider is that the bridge diodes must be able to handle both the current and the peak voltage; the popular 1N4001 diodes, rated at 50 V and 1 A, are quite suitable here.

Finally, there is the regulator IC. The one used for this supply is the common 7812 variety, a 12 V 1 A three-terminal device. It would need a heatsink if used to pass current greater than 500 mA so in this case, a sink is not needed. Capacitors $C_2, 3$ are essential to prevent high frequency oscillations; the values are generally specified in the maker's data so they are not a problem; the point to note, however, is that they should be mounted as close to the IC as possible. Resistor R_1 is included to prevent the IC from running into an open circuit;

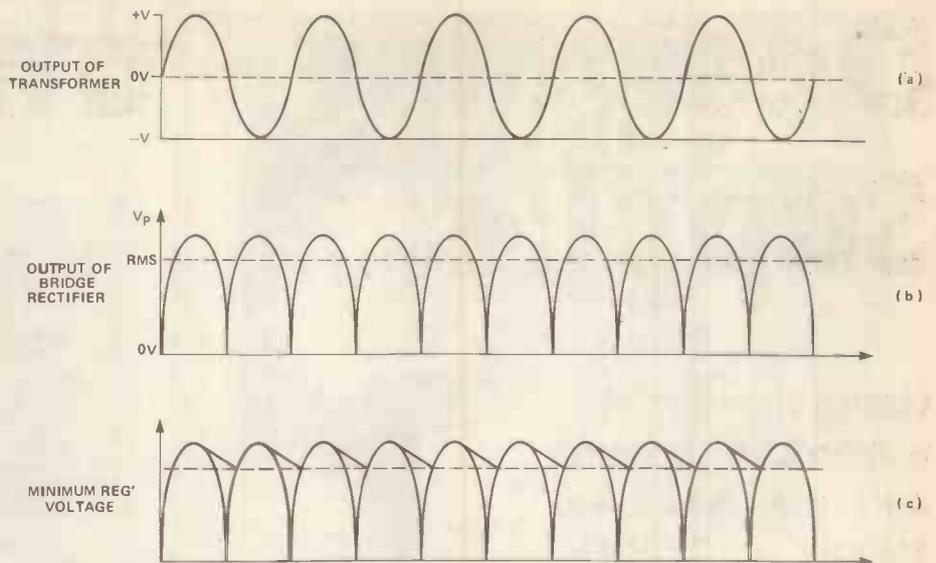


Figure 2. Power supply waveforms: (a) The output of the transformer; (b) Output of the bridge rectifier; (c) Input to the regulator IC.

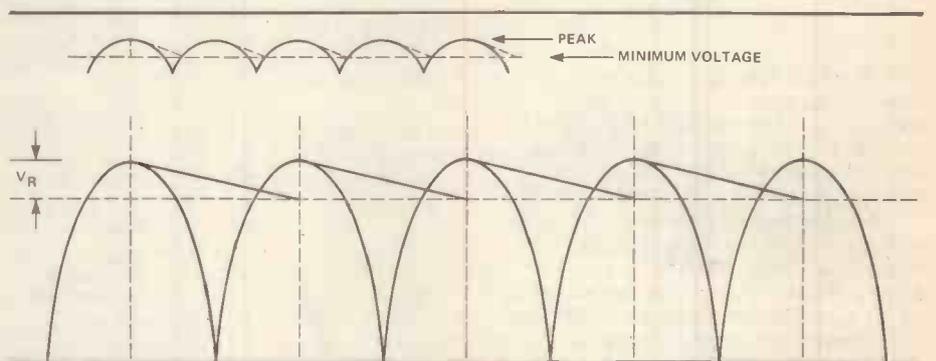


Figure 3. An enlarged view of Figure 2(c), showing the effect of the smoothing capacitor.

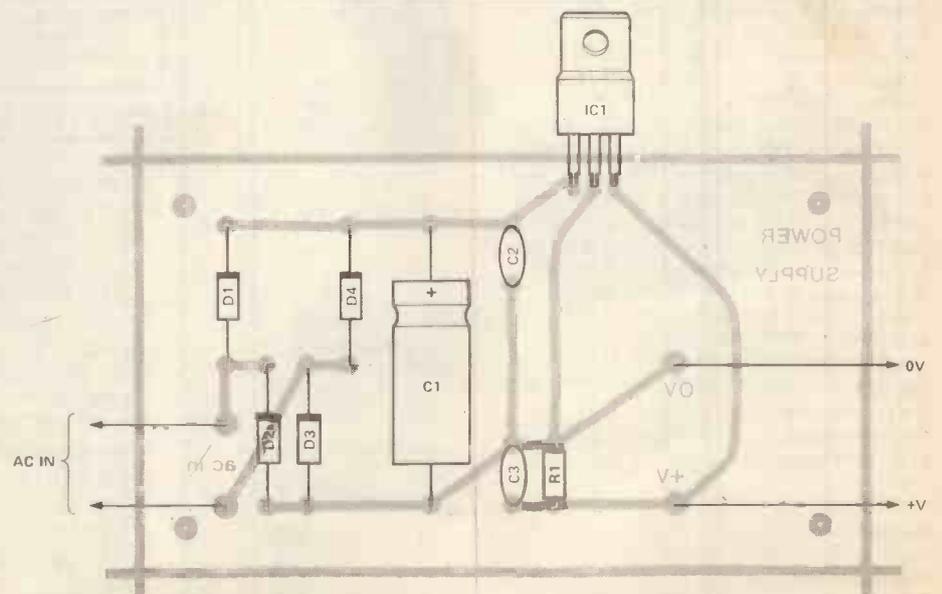


Figure 4. A PCB layout for the supply for the Telephone Timer. The foil pattern is reproduced on the PCB page.

this could result in damage to the device so R_1 is used to draw some current (2.5 mA) even if the output is open circuited.

And that completes the circuit design — it's as easy as that! Although

we have illustrated this procedure with a specific supply (12 V at 400 mA), it can be used with any three-terminal regulator IC to design a supply for any voltage and current. The next step is one you must make yourself!

Beginners' luck

30% OFF
10 selected kits
for first-time
builders



Shortwave
Listener's
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need

Digital Clock



is there. Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud

of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.



Metal
Locator



Windspeed and Direction
Indicator

To Heath Electronics
(UK) Limited, Dept (HE6),
Bristol Road, Gloucester GL2 6EE.

HE6

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____

Address _____



HEATH **You build on our experience**

HEATHKIT

HE PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL the electronics and hardware needed. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- ECHO REVERB UNIT May 82. Less case £31.82. Economy case WB3 £3.76 extra
- DIGITAL THERMOMETER May 82 excluding case + bezel £15.80
- LIGHT SEEKER May 82 £4.99
- AUDIO SIGNAL GENERATOR May 82 £19.69
- CABLE TRACKER May 82 £9.37
- DIGITAL CAPACITANCE METER Apr 82 £19.98
- SIGNAL TRACER Apr 82 £3.61
- BIKE ALARM Apr 82 £10.98
- DUAL ENGINE DRIVER Apr 82 £48.78
- DIGITAL DICE Mar 82 £6.82
- BICYCLE SIREN Mar 82 £10.18
- NOISELESS FUZZBOX Feb 82 £9.77
- SOUND SWITCH Feb 82 £8.31
- MASTHEAD AAMPLIFIER Feb 82 £13.74
- DRUM SYNTHESIZER Dec 81. Full kit £19.98
- GUITAR HEADPHONE AMPLIFIER Dec 81 £3.48
- IN CAR CASSETTE POWER SUPPLY Dec 81 £4.46
- SCRATCH FILTER Nov 81 Mono £5.44 Stereo £8.40
- LED VU METER Nov 81 less case £4.56
- SIMPLE STYLUS ORGAN Nov 81 less case £4.74
- METRONOME Nov 81 £11.88
- TELEPHONE BELL REPEATER Oct 81 £12.78
- Med Linking wire extra 14p metre
- COMBINATION LOCK Oct 81 less solenoid £17.43
- BABY ALARM Oct 81 £8.14, Fig 8 linking wire 7p metre
- 'DIANA' METAL LOCATOR Sept 81 £32.25,
- POWERPACK Sept 81 £9.58
- REACTION TESTER GAME Sept 81 £11.98
- VARIABLE BENCH POWER SUPPLY Aug 81 £25.35
- ULTRASOUND BURGLAR ALARM July 81 £18.67
- ELECTRONIC DOOR BUZZER July 81 £5.65
- ELECTRONIC METRONOME July 81 £4.67
- CONTINUITY CHECKER June 81 £5.34
- ENVELOPE GENERATOR June 81 £16.85
- AUDIO MIXER June 81 £4.99
- PUBLIC ADDRESS AMPLIFIER March 81 £1821, Extras — horn speakers £6.83 each, PA MIC £4.40
- FUZZBOX March 81 £10.35
- WINDSCREEN WIPER CONTROLLER March 81 £7.67
- STEAM LOCO WHISTLE March 81 £12.26
- PHOTOGRAPHIC TIMER March 81 £3.28
- HEARTBEAT MONITOR Feb 81 £23.40
- AUDIO SIGNAL GENERATOR Feb 81 £18.93
- TWO-TONE TRAIN HORN Feb 81 £5.24 less case
- MEDIUM WAVE RADIO Feb 81 £7.67
- BENCH AMP Jan 81 £10.10
- NICARD CHARGER Jan 81 £7.67
- CHUFFER Jan 81, less case £7.04
- BATTERY CHARGE MONITOR Dec 80 £5.40
- MEMORY BANK — MINI SYNTHESIZER Nov & Dec 80 £28.40
- TRANSISTOR TESTER Nov 81 £8.12 inc test leads
- GUITAR PRE-AMP Nov 80 £5.65 case (diecast) extra £2.29
- INTRUDER ALARM Oct 80 £19.61
- TOUCH SWITCH Sept 80 £2.57 less case & contacts
- GUITAR PHASER Sept 80 £15.22
- SOUND OPERATED FLASH TRIGGER July 80 no skt £4.99
- FOG HORN June 80 £6.21
- SPEED CONTROLLER FOR R/C April 80 £16.41 (less case)
- DIGITAL FREQUENCY METER April 80 £39.35
- DIGI-DICE Jan 80 £10.97
- GUITAR TUNER Nov 79 £11.99
- CAR ALARM Feb 79 £12.07

CABLE TRACKER

AS FEATURED IN
MAY 82 H.E.

A SUPERB PROJECT FOR THE HOME HANDYMAN — PICKS UP NAILS, SCREWS, CABLES AND PIPES (and other buried metal objects).

QUICKLY SAVES ITS
OWN COST
BE SURE — BE SAFE

FULL KIT
INCLUDES ALL
HARDWARE,
ELECTRONICS & PCB

£9.37 + P&P

MORE PROJECT KITS — SIMILAR STYLE TO H.E.

INSTRUCTIONS INCLUDED (SEPARATELY 45p EACH)

PLEASE QUOTE REF. NO. WHEN ORDERING

- B1 PEST CONTROL 'Ultrasonic cat scarer' £6.98
- B2 COMPONENT TESTER £8.38
- B3 ENLARGER TIMER — relay output £26.99
- B4 GUITAR NOTE EXPANDER £16.87
- B5 CAMERA OR FLASH GUN TRIGGER Infra red system £11.98
- B6 SIMPLE INFRA RED REMOTE CONTROL £16.39
- B7 0-12V POWER SUPPLY £16.99
- B8 SOIL MOISTURE MONITOR £4.23
- B9 SOUND TO LIGHT — single channel £7.97
- B10 THREE CHANNEL SOUND TO LIGHT £19.98
- B11 IN SITU TRANSISTOR TESTER £6.73
- B12 WEIRD SOUND EFFECTS GENERATOR £5.68
- B13 AUDIBLE VISUAL METRONOME £5.98
- B14 ELECTRONIC DICE £5.71
- B15 2K RAM PACK Less case for ZX81 £13.34
- B16 MINI EGG TIMER £4.14
- B17 AUDIO EFFECTS UNIT FOR WEIRD SOUNDS £12.71
- B18 LED JEWELLERY — Cross brooch £2.77
Star brooch £9.71 Spiral brooch £7.50

MEMORY BANK SYNTHESISER

Miniature synthesiser featuring vibrato, envelope, tempo, volume + pitch controls. Uses 24 push button switches in a keyboard style layout. Based on a custom designed L.C. The accessible memory stores a 32 beat length sequence of notes + spaces. Can be played 'live'. Fitted with an internal speaker. Jack socket allows the use of an external amplifier if wished.

Memory Bank Synthesizer £28.40

Complete kit inc. case, pcb's etc. Reprint extra 45p. Available separately 45p + 45p p&p.



curacy. Portable. Battery powered. Easy to use — Easy to build. Complete kit includes pcb, all components and case.

DIANA METAL LOCATOR H.E. Sept 81 (Ha) £32.25

A powerful pulse induction metal locator. Exciting design using modern technology. Simple to set up and use.

Complete kit includes all hardware for the handle and coil, cases, meter, pcb and all components. Available less handle and coil hardware and cases **£19.29**

MULTIMETER TYPE 2 - £14.75

20,000 opv. Includes transistor tester. AC+ DC volts. DC current. 4 very useful resistance ranges.

We've used it and we like it.

DIGITAL CAPACITANCE METER H.E. April 82 (H1) £19.98

Fast and accurate. Reads from 100pF to 9,900uF with 2 digit ac-

ECHO REVERT UNIT H.E. May 82 (H3) £31.82 less case. Economy case WB3 £3.76 extra.

A modern all electronic CCO design with independent echo and reverb controls. Delay fully variable up to 50 m sec.

METRONOME H.E. Nov 81 (H4) £11.88

A comprehensive battery powered instrument with audible and visual outputs. Switch selectable accented beat 2/4, 3/4, 4/4 and 5/4 times. Speed range 40-240 beats per minute. Variable volume and pitch.

BOOKS

SEMICONDUCTOR DATA BOOK. Newnes	£5.90
MICROPROCESSORS FOR HOBBYISTS. R. Coles	£3.65
PRACTICAL ELECTRONIC PROJECT BUILDING. Ainalie & Colwell	£3.95
CONSTRUCTORS PROJECT BOOKS	
ELECTRONIC GAME PROJECTS. Rayer	£3.35
ELECTRONIC PROJECTS FOR HOME SECURITY. Bishop	£3.35
ELECTRONIC PROJECTS IN AUDIO. Penfold	£3.35
ELECTRONIC PROJECTS IN MUSIC. Flind	£3.35
ELECTRONIC PROJECTS IN PHOTOGRAPHY. Penfold	£3.35
ELECTRONIC PROJECTS IN THE CAR. George	£3.35
PROJECTS IN AMATEUR RADIO & SHORT WAVE LISTENING. Rayer	£3.35
PROJECTS IN RADIO AND ELECTRONICS. Sinclair	£3.35
ELECTRONIC PROJECTS IN HOBBIES. Rayer	£3.35
ELECTRONIC PROJECTS IN THE HOME. Bishop	£3.35
ELECTRONIC PROJECTS IN THE WORKSHOP. Penfold	£3.35
ELECTRONIC TEST EQUIPMENT PROJECTS. Ainalie	£3.35
MORE ELECTRONIC PROJECTS IN THE HOME. Flind	£3.35
110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR. Marston	£5.35
MODEL RAILWAY PROJECTS. Penfold	£1.95
SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS. Penfold	£1.30
BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS. Penfold	£1.50
ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING. Berry	£1.35
IC555 PROJECTS. Parr	£1.90
BASIC ELECTRONICS. A super book covering theory and practice	£7.95
RADIO CONTROL FOR BEGINNERS. Rayer	£1.75
INTERNATIONAL TRANSISTOR EQUIVALENTS GUIDE. 320 pages. Michaels	£2.05
ELECTRONIC PROJECTS FOR CARS AND BOATS. Penfold	£1.95
SECOND BOOK OF CMOS IC PROJECTS. Penfold	£1.50
50 SIMPLE L.E.D. CIRCUITS: Book 2	£1.35
ELECTRONIC MUSIC PROJECTS. Penfold	£1.75
ELECTRONIC HOUSEHOLD PROJECTS. Penfold	£1.75
ELECTRONIC GAMES. Penfold	£1.75
PROJECTS IN OPTO ELECTRONICS. Penfold	£1.25
52 PROJECTS USING IC 741. Redmer	£1.25
ELECTRONIC TIMER PROJECTS. Rayer	£1.95
POWER SUPPLY PROJECTS. Penfold	£1.75
REMOTE CONTROL PROJECTS. Bishop	£1.95
POPULAR ELECTRONIC CIRCUITS: Book 2	£2.35

MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST
Price list included with orders or send sae (9 x 4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Sends 80p in stamps or add 80p to order.

MORE H.E. PLUS E.E. and E.T.I. PROJECT. KITS IN THE PRICE LIST


SOLDERING / TOOLS

- ANTEX X5 SOLDERING IRON 25W £5.48
- SOLDERING IRON STAND..... £2.40
- SPARE BITS. Small standard, large, 65p each. For X5 + X25
- SOLDER. Handy size..... 99p
- SOLDER CARTON..... £1.84
- DESOLDER BRAID..... 69p
- HEAT SINK TWEEZERS..... 29p
- DESOLDER PUMP..... £6.48
- HOW TO SOLDER LEAFLET..... 12p
- LOW COST CUTTERS..... £1.69
- LOW COST LONG NOSE PLIERS..... £1.68

HELPING HANDS JIG £6.30

Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/2" diameter (25x) magnifier attached, used and recommended by our staff.

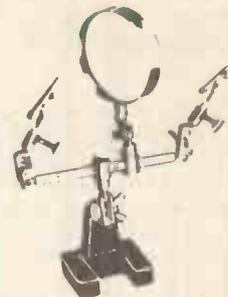- VINO SPOT FACE CUTTER... £1.49
- PIN INSERTION TOOL... £1.98
- VEROPINS (pk of 100) 0.1"..... 52p
- MULTIMETER TYPE 1 (1,000 opv)..... £6.66
- MULTIMETER TYPE 2 (20,000 opv) with transistor tester. Very good..... £14.75
- CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips..... 99p



- RESISTOR COLOUR CODE..... 21p
- CALCULATOR..... 49p
- CONNECTING WIRE PACK TYPE ED. 11 colours..... 49p
- ILLUMINATED MAGNIFIERS
- Small 2" dia. (5 x mag.)..... £1.14
- Large 3" dia. (4 x mag.)..... £2.40
- CAST IRON VICE..... £2.98
- SCREWDRIVER SET..... £1.98
- POCKET TOOL SET..... £3.98
- DENTISTS INSPECTION MIRROR..... £2.85
- JEWELLERS EYEGLASS..... £1.50
- PLASTIC TWEEZERS..... 69p
- PAIR OF PROBES WITH LEADS (cc)..... 77p

- SPEAKERS. Miniature, 8 ohm..... 87p
- 64-75 ohm..... 89p
- CRYSTAL EARPIECE..... 65p
- MONO HEADPHONES..... £2.96
- TELEPHONE PICK-UP COIL..... 72p
- MIN. BUZZERS. 6V. 50p. 9V. £1.10. 12V. 65p.
- MAGNETIC EARPIECE..... 15p
- STEREO HEADPHONES..... £4.35
- F.M. AERIAL..... 49p

VEROBOARD 0.1" COPPER STRIPS	PP3 CLIPS 10p	PANEL METERS
10 strips 24 holes..... £1.20 per 5	PP9 CLIPS 11p	50uA; 100uA; 1mA, 1A; 25V. 100uA-0-100uA; 5A. AU £4.98 each. State value.
24 strips 37 holes..... 78p	EUROBREADBOARD..... £6.20	
24 strips 50 holes..... 89p	5 DEC BREADBOARD..... £3.98	
36 strips 37 holes..... 89p	BIMBOARD 1 BREADBOARD..... £6.98	
36 strips 50 holes..... 99p	VEROBLOC BREADBOARD..... £4.20	
Terminal pins 0.1"..... 52p/100		

INTEGRATED CIRCUITS

CMOS4001	20p	LM301A	36p
CMOS4011	20p	LM317K	£3.20
CMOS4017	62p	LM334Z	£1.50
CMOS4046	69p	LM380N	89p
CMOS4049	32p	LM386N	92p
CMOS4050	30p	LM387	£1.10
CMOS4093	38p	LM389	£1.11
CMOS4098	66p	LM3909N	82p
CMOS4511	68p	MC3340	£2.15
CMOS4518	60p	OM335	£8.98
555	26p	SN76477	£2.89
556	79p	TDA1022	£5.58
741	22p	TL064	£1.64
7555	99p	TL071	47p
Ca3130E	98p	TL082	74p
CA3140E	52p	TL083	£1.52
HA1388	£3.50	U237B	£1.69
ICL7611	88p	U267B	£2.20
LF351N	58p	ULN2283	£1.57
LF353N	99p	ZN414	98p
LF355N	£1.14	ZN419CE	£2.21
LF356N	£1.15		

PCB ETCHING KIT £4.98

Virtually all you need to make your own printed circuit boards. Includes tray, etch resist pen, ferric chloride + even drills.

OPTO

LEDS with clips.
3mm Red 15p. Green 18p.
Yellow 20p. 5mm Red 18p.
Green 22p. Yellow 23p. 0.5" C.C. 7 segment display 99p.
ORP12 99p.
PB2270 ceramic resonator 65p. BC650 transistor 22p.
71x300 11p.

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio, etc. Based on Bimboard 1 bread board. Adventures with Microelectronics..... £2.55
Component pack £29.64 less battery.

ADVENTURES WITH ELECTRONICS by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.40. Component pack £17.98 less battery.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

MAGENTA ELECTRONICS LTD

HK25, HUNTER ST., BURTON-ON-TRENT, STAFFS, DE14 2ST. 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY. ADD 45p P&P TO ALL ORDERS.

PRICES INC VAT



OFFICIAL ORDERS WELCOME. IRISH REPUBLIC & B.F.P.O. EUROPE. Deduct 10% from prices shown Payment, must be in Sterling. ACCESS AND BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST. SAE ALL ENQUIRES.

POINTS OF VIEW

Pointed Suggestions

Dear Sir,
May I take advantage of your invitation in *Points of View* and submit two circuit ideas I have not yet seen published anywhere, but which would be very useful to amateur photographers who are interested in colour printing.

The first one is a mains stabiliser suitable for the transformer system of the Durst and many other colour enlargers. The second is a good colour analyser for colour balancing negatives while printing. This would be a great saver of time, paper and temper.

Thank you for a friendly and informative magazine. I am off, now, to make the Digital Capacitance Meter (April '82 issue). I've needed one as good as that for a long time!
G. Walton,
Darlington,
Co. Durham.

We receive many and varied requests for photographic equipment projects. Unfortunately, many of them have to be ruled out because of the complications involved (optics, mechanics, reliability and accuracy, to mention just a few of the difficulties) and the colour analyser certainly falls into this group. There are several commercial units, though, that should not "break the bank". The Melico range, for example, starts at about £80, while Durst's analysers are priced from around £90. They are available from Wallace Heaton's, New Bond Street, London. The mains stabiliser is a more practical project and, after lengthy discussions with our photographic staff, we have commenced work on a suitable design. Our Digital Capacitance Meter, incidentally, has proved to be one of our all-time most popular projects. Thanks are due to the designer, Owen Bishop.

CB Circuits

Dear Sir,
Please could you help me. I have a CB radio and sometimes, when talking to people, the conversation comes round to professions and I am asked if I could do something about an ailing rig — my profession is telecommunications.

Okay, when you look at a transmitter or receiver, you can pick out the various stages, ie RF stages, mixers, IF and so on, but when it comes to actually fault-finding and there is no circuit diagram to work from, the trouble really starts.

Could you tell me where I can get hold of CB radio circuit diagrams? I have thought of writing to the

manufacturers, but I think they would turn me down. I hope you can help me.
N.J. Trécher,
RAF Henlow,
Beds.

This is a problem often encountered by those who know something about electronics and, as a consequence, are often asked to do a repair job on friend's hi-fi or CB rig. Without a circuit diagram, what could be a simple job can turn into a nightmare. Unfortunately, there is no easy solution; we certainly don't keep circuits for commercial equipment of any kind, so we can't help you. In fact about the only thing you can do is try the manufacturers — you might be lucky!

Filter Scratched

Dear Sirs,
I have recently completed the Scratch and Rumble Filter project from your *Projects Special Vol. 1*.

Everything in the filter seems to be working but — the power output from the amplifier has dropped. I don't know by how many watts, but the loss is considerable. Wearing headphones, before fitting the filter, number '8' on the volume slider would have blasted my head off; now the volume almost disappears at about '3', going down the scale.

I would like to add that I have built the unit into my record player and not in a separate box. Is it possible that the pick-up lead is now too long, thereby increasing the resistance to the signal from the stylus? If not, maybe you could shed some light on what has gone wrong.

I have, by the way, made the unit in stereo. I would be very grateful for any help.

L.T. Daniels,
Havant,
Hants.

The clue to this problem is in the suggestion that the pick-up lead may be too long — though this is not actually the cause of the fault. The suggestion hints that the filter is connected between the pick-up and the pre-amplifier. If this is so, it's the cause of the problem. The filter does not include a pre-amplifier, so it simply cannot work well in this position. Place it between the pre-amplifier output and the main amp input, and full volume should be restored to you!

Circuit Diagrams and Backnumbers

Dear Sir,
I am doing an electronics project on

various types of remote control, ie infra-red, ultrasonic and radio control. I would be grateful if you could send me any circuit diagrams of transmitters or receivers for each particular type; also applications and the project layouts.
P.A. Robinson,
Birmingham.

Once more, we have to point out that we simply cannot accept blanket requests, such as Mr. Robinson's, for circuit diagrams of HE projects. Of course we have published many remote control projects, of all types, and they are always available from our Back Numbers department (see page XX), but they too can only deal with specific requests. The essential information they need is the name of the project and the issue in which it appeared. If you do not have this information, then why not send in for photocopies of the Indexes to Volumes 1, 2 and 3? We strongly recommend this to anyone who requires either a single circuit or a number of circuits, for a particular project.

0-60 In 3 Hours

Dear Sir,
I have recently made the Speed Controller for R/C models featured in the April 1980 issue of *Hobby Electronics*. I bought the *Hobbyprint* and constructed the circuit, making slight alterations to fit it in my Tamiya Rough Rider, namely; mounting the relay alongside, instead of on the board, changing the two parallel TIP3055s for a single 2N3055 and putting in an 18R, 1 W resistor on the base. After making the checks explained in the magazine, I tried out the Controller.

The motor reaches full speed in both directions and the proportional speed control also works — but the acceleration of the car is seriously impaired. It used to reach full speed in a couple of yards but now it takes ten times that distance and, at the start, it just crawls along. This is no use, for this type of car. Please can you help me?

A. Anderson,
Glasgow.

There are a number of possible reasons why your super-car has turned into a plodder. For example, are you using heavy gauge wire for the motor cables, and the correct battery? The most likely cause, however, is the substitution of a single transistor where the design called for two. The current gain of any transistor falls off at high currents — such as those passed when the motor is building up speed — so it is unlikely that one 2N3055 will handle the peak current. Remember, the design is intended to supply up to

15 A, which is the absolute maximum current rating of a 2N3055! The solution must be to either revert to the original circuit or, if you are cramped for space (and also wish to indulge a taste for over-kill), substitute an MJ11016; this is a high power Darlingtion rated up to 30 A and with a minimum current gain of 1000 at 20 A. One of those, and you can really burn up the track!

CB Supplies

Dear Sir,
I am writing to ask if you can produce for me, and the many others who read *Hobby Electronics*, a circuit for a Citizens' Band radio power supply, ie a supply producing 12 V DC at between 3.5 and 5 amps, at a budget price. For a small unit such as this, one can easily spend £12 for something quite plasticky.

I would be extremely grateful if you could publish one as a project in *HE*. I'm sure that such a project would sell like 'hot cakes'. If it is not possible, please could you send me a copy of a suitable circuit? Many thanks, and thanks also for a great mag.

A. Postle,
Letchworth,
Herts.

PS. It would be nice if you had an article about how CB is getting on!

A CB power supply project has already been published — by our cousins, *Citizens' Band* magazine. It appeared in their January 1981 issue and a copy is available from their Backnumbers Department, at our usual address. Alternatively, you might like to try designing and building your own — see our Power Supply Design feature on page XX. The only additional precautions you should take are to make sure that the smoothing is adequate (you don't want 50/100 Hz hum on the speaker) and to use a good heatsink.

Baby's Alarming

Dear Sir,
I have been trying to build the Baby Alarm project from the October 1981 issue of *Hobby Electronics*. Unfortunately, despite a lot of experimentation, I cannot get it to work. When I connect a microphone and speaker, all it produces is a constant high pitched note. As far as I can see, I've made no mistakes in the construction.

The microphone I have used is a 600R capacitance mic running from a 1V5 battery. Is this inappropriate? The article mentions that several track breaks are required on the board, yet they are not shown on the diagram and I can see no need for them. Is this an error?

If you have any idea of what mistakes I have made, I would be grateful if you could tell me.

Secondly, I have been trying to obtain a dual-gang variable capacitor

(208pF plus 176pF, Jackson type 'O'). If you have any idea where I might obtain one I would appreciate your advice.

Thank you very much.

P. Lusley,
Islington,
London.

No track breaks are actually needed, as the circuit is laid out — however, if the board is mounted using metal machine screws, breaks will be required between the mounting holes and the components. The "high pitched note" described above sounds suspiciously like acoustic feedback; eliminate this possibility by separating the mic and speaker by at least six feet — more, if it can be arranged. If the howl persists, other causes must be sought. There is no reason why a capacitance mic should be unsuitable, provided it is AC coupled to the base of Q1, as shown in the circuit. The variable capacitor you're after is listed in the Maplin catalogue as a Type 00.

Reader's Mods

Dear Sir,
With reference to the *Intruder Alarm* (*HE*, October 1980), could you please tell me how to incorporate a delay in to the system so that one has, say, fifteen to thirty seconds in which to close the outside door when leaving the house, and a similar delay time in which to switch off the system when you return?

I cannot see any reference to this facility, although I would have thought it to be a logical requirement.

Also, could you recommend a suitable source of supply for the components, including the reed switches and magnets, alarm box for external fitting and the control box?

I thank you in anticipation of your kind attention.

M. Toogood,
Southampton.

An excellent idea, which has been passed to our design team. A satisfactory modification should not be too difficult to devise. As to a source for the components, try Magenta Electronics, 135 Hunter Street, Burton-on-Trent, Staffs. DE14 2ST.; Tel. 0283 65435.

Alarm Wanted

Dear Sir,
I am a student attending *The College*, Swindon, where I am studying a course in *Technology and Engineering*.

As part of the course I am required to carry out a project to design and build a device to detect the presence of a human or animal intruder in a building. Some system of control monitoring is required and if an intruder is detected it should activate a control monitor.

I am writing to ask for a design for a simple circuit that I can use. It should work as a movement detector or light detector, sound detector or an all-in-one device.

Yours,
G.A. Kembo,
Swindon,
Wilts.

We have published a great many burglar or intruder alarms, over the years — the latest was the *Ultrasound Alarm*, mentioned above. A photocopy of the article can be obtained from our Backnumbers Department.

Errata

Clever Dick has passed on a letter from G. Beckingham of Gloucester, who has noted an error in the *HE Echo-Reverb* (May '82 issue). The mains transformer should be a 7V5-0-7V5 type, if it is to be connected as shown in the component overlay, ie the windings in series. An alternative, for anyone who already has the transformer, is to connect the windings in parallel by modifying the PCB as follows: cut the track joining the two windings and, using insulated wire links, join the two 15 V pins together, then join the 0 V pins.

The Parts List for the *Digital Capacitance Meter* (April '82) shows PR2 as 47k; it should be 4k7, as shown on the circuit diagram. In addition, R3 and R5 on the component wiring diagram (Figure 3, page 28) should be in reverse order ie, R3 should be at the top and R5 at the bottom.

W.D. Hughes of Bristol has a problem with the *Infra-Red Remote* unit, from the February 1980 issue; the fault probably lies with R24 which should be 1k0 as shown in the Parts List, not 1M0 as indicated on the circuit. Also, the last paragraph on page 32 should read: "(1) The EARTHS of the mains input cables . . .", not the neutrals, as stated.

J. Reed of Edinburgh has noted (yet another) error in the *Intruder Confuser* (January '82). On the *Veroboard* layout, a track-break should be made between the ends of C1. This project is the only one this year which has contained major errors; they arose from our misguided attempts to 'tidy up' the circuit and layout — unfortunately, we "got our wires crossed" in the process, but at least we've learnt from the experience (leave well enough alone!).

A correction for the *Kitchen Timer* (October 1980), which we published in these pages in the March '82 issue, may interest Mr. P.S. Woodward, from Worthing in West Sussex; R17 should be 3k9, not 82k.

Writing to Hobby Electronics

Would readers please note that we cannot reply personally to letters unless a stamped, self-addressed envelope is included. This applies particularly to ALL technical enquiries.

HE

Hobby Electronics

NEXT MONTH . . .

SOLAR CELLS

A practical guide to the essential technology of solar power, together with some simple Breadboard-style ideas for experimenters.

SOLAR POWERED RADIO

Ideal for sunny summer days at the beach. Costs little to build, nothing to run!

SUNBURN TIMER

The Sun's power is all too obvious if you stay out too long . . . this year, control your tan with our Sunburn Timer — just dial Rare, Medium or Well-Done!

POPULAR COMPUTING

The HE MicroTrainer

Next month we describe the circuit and commence the construction, beginning with the power supply unit.

INTO RADIO

Television Interference Filter

Tired of listening to — and looking at — CB-chat while trying to watch Dallas? Our simple TVI Filter will remove the symptoms, if not the cause of your annoyance.

PROJECT: MUSIC

Equalisation — It's Easy

Looking beyond bass and treble, this feature explains what equalisation is and how it is used to compensate for frequency distortion in both recorded and live music.

INTO ELECTRONIC COMPONENTS —

Concluding our long-running and popular beginner's series. If you've followed it so far, don't miss the final chapter!

PEDOMETER/ODOMETER

No, it's not an instrument for detecting smelly feet, but a digital device which can be individually programmed to read the distance travelled by a walker or jogger, or as a bike mileage indicator.

Get it?

Please reserve copies of the July issue of

**Hobby
Electronics**

for
Name

Address



Then get the July issue of

**Hobby
Electronics**

On sale at your newsagent
from 14th May.

Place your order now!

Although these articles are being prepared for the next issue, circumstances may alter the final content.

RADIO RULES

Getting to grips with the theory.

Ian Sinclair

THE MOST important type of wave, for radio, is the sine wave. The name, incidentally comes from a Latin word meaning "snake" and the shape of the graph of voltage plotted against time for a sinewave shows why the name was chosen! The name 'sine' is also given to a mathematical function; it is the ratio of two of the sides of a triangle, as shown in Figure 2. The sine of an angle is a number whose value lies between 0 and 1 and which is negative if the angle is between 180° and 360°. If we plot the sine of an angle against the size of the angle, then we end up with a perfect sinewave.

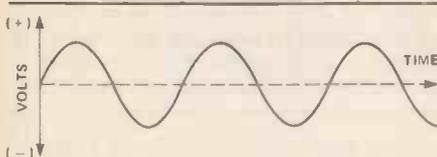


Figure 1. A sine wave — voltage (or current) plotted against time.

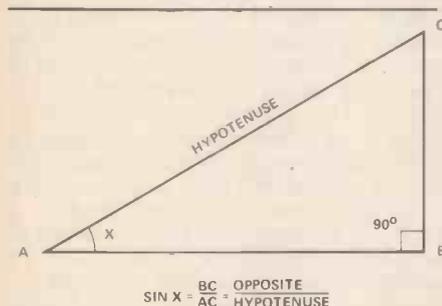


Figure 2. In mathematics, the sine of an angle is the ratio of two sides of a triangle, ie the side opposite the angle, X, divided by the hypotenuse.

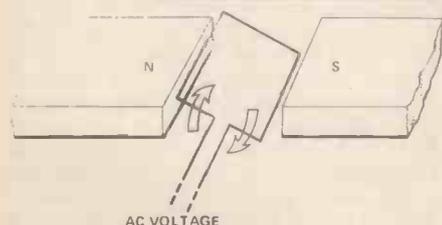


Figure 3. A sine wave is generated when a coil of wire rotates between the poles of a magnet.

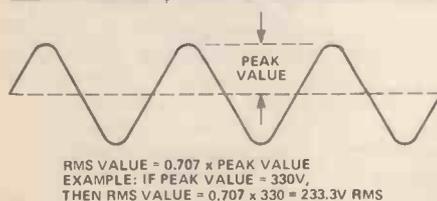


Figure 4. Peak and RMS values of a sinewave. Peak values are more useful in radio work because they are easily measured on an oscilloscope. Meters give RMS values.

Like any other wave, a sinewave will have a frequency, ie the number of complete cycles of the wave in one second. It will also have an amplitude, which we measure as a peak value (Figure 4) or as an RMS value, which is 0.707 x Peak value (or Peak divided by 1.4, which comes to the same thing). Two sinewaves with the same amplitude and the same frequency may not be identical, however, because there may be a phase angle difference. This means that the peaks of the waves do not coincide; it's the effect you would expect to see if one wave started before the other, or if one were delayed. The instantaneous voltage of a sinewave at any time is the voltage at that instant (logically enough) and it is given by the equation:

$$V_i = V_p (\sin 2\pi f_t + \phi)$$


We aren't forced to use this mathematical way of working with phase and instantaneous voltage, because there is a simpler way, using what are called phasors. A phasor (no, it isn't Capt. Kirk's ray-gun) is a line whose length represents the peak value of a sinewave and whose angle to the horizontal represents the phase of the wave. Figure 6 shows a simple phasor diagram — this method of representing phase is very useful and we'll return to it when we start to look at the behaviour of inductors, capacitors and resistors in AC circuits. But now it's time to look at some even more basic ideas.

Magnetic Appeal

Magnetism is one topic we need to know something about. Ignoring permanent magnets for the moment, we can create magnetism by passing a current along a piece of wire. Doing that (Figure 7) causes the shape of space (yes, invisible space), around the wire to change, so that when you hold a compass needle at different points round the wire, at the same distances, the needle points in directions which indicate a circle. We call this particular distortion of space a magnetic field and it affects all materials; but a few materials, like iron and its alloys, are very strongly affected. We can, therefore, use these materials to trace the shape of the magnetic field.

The field around a straight wire does

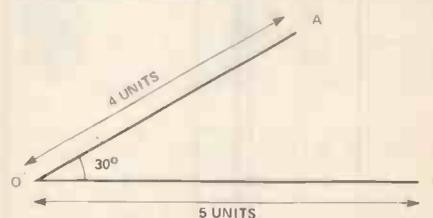not extend for a great distance beyond the wire — it tails off to almost zero at a distance of a few centimetres. When wire is wound into a coil, however, and current is passed through it, the magnetic field becomes much stronger because the effect of each turn of the coil is added to the effect of the other turns. The shape of the new field is



IF OB REPRESENTS A 50V SIGNAL, THEN OA REPRESENTS A 40V SIGNAL WHOSE PHASE IS 30° AHEAD OF OB

Figure 6. A phasor diagram. Imagine that both lines are revolving anticlockwise around point 'O'; the line OB is the zero-phase position. As both lines revolve, the line OA passes through zero before the line OB; OA is said to 'lead' OB, by 30 in this example.

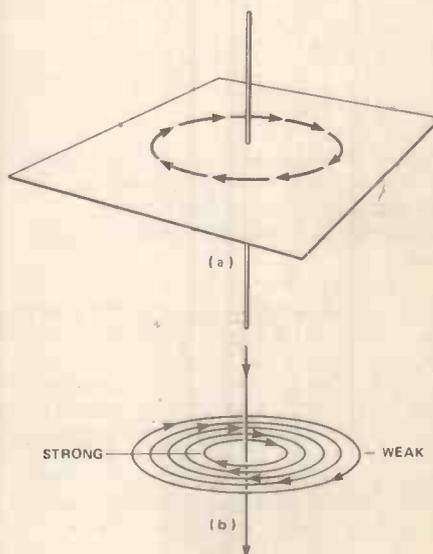


Figure 7. The magnetic field around a wire carrying a Direct Current. The shape of the field is circular and it is very weak at distances of more than a few centimetres.

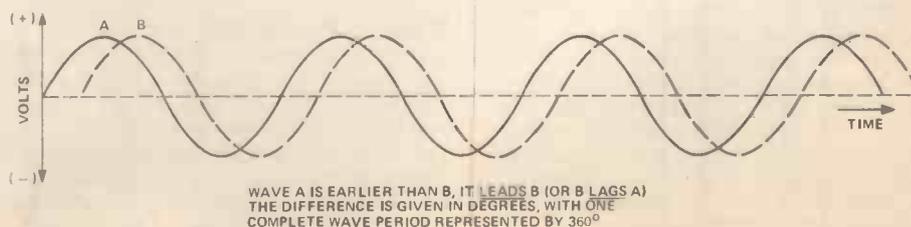


Figure 5. The phase relationship between two sine waves.

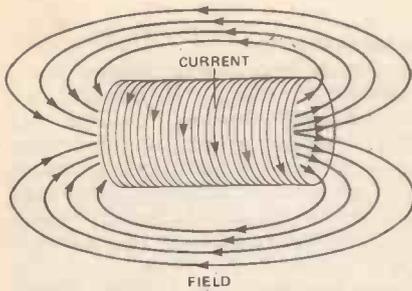


Figure 8. The shape of a field produced by a solenoid is almost identical to that of a bar magnet.

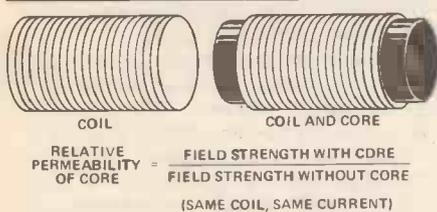


Figure 9. A mathematical definition of relative permeability.

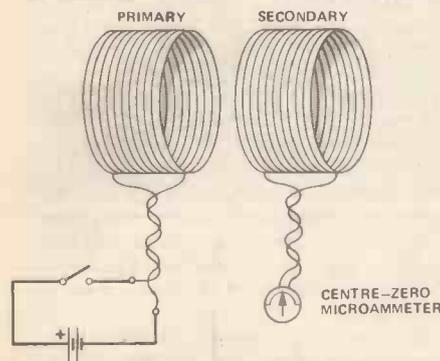


Figure 10. Induction without movement — the transformer effect; changing current in the primary coil causes a voltage to be induced in the secondary coil.

shown in Figure 8 and it's pretty much the same as the shape of the field that you get from a bar-shaped permanent magnet. The strength of the magnetic field of any coil is greatly increased by placing magnetic materials inside the coil (a core) and the shape of the field also becomes more compact, particularly when the materials are of the type called "soft" magnetic materials. The word "soft" doesn't mean that you can squeeze them out of shape — some of these materials are, in fact, very hard and brittle — it simply means that they are magnetically "soft"; you can't magnetise them permanently. Unlike hard magnetic materials, which are used to make permanent magnets, soft magnetic materials lose their magnetism whenever they are removed from the coil, or when the current is switched off.

The ratio by which the strength of the magnetic field is increased by the presence of a core is called the *relative permeability* of the core; it is the quantity defined in Figure 9. The word "relative" is sometimes omitted though, strictly speaking, this changes the meaning. Soft magnetic materials can have very

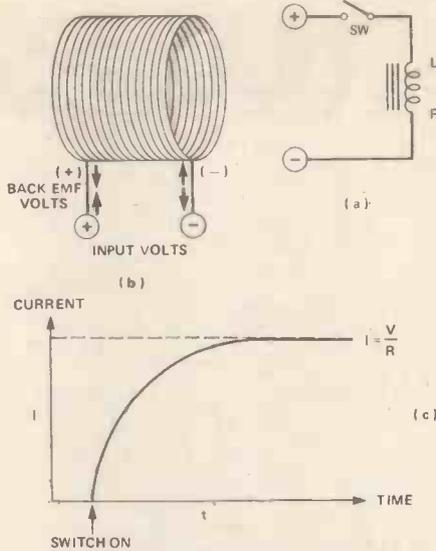


Figure 11. (a) A Back-EMF is always produced when a voltage is switched across a coil; (b) Its direction is such that it always opposes the current, and hence the voltage, which is actually causing the Back-EMF; (c) The result is that when a voltage is applied, the current changes only gradually.

large values of relative permeability — one million or more — but the value is not constant; it depends on a lot of factors like the previous history of the material (was it magnetised before, was it heated?) and the way in which it has been magnetised.

Electricity From Mag

Just as we can produce a magnetic field from the current flowing in a wire, so we can also produce electricity from a moving magnetic field — this was the great contribution that Michael Faraday made to electrical history. A permanent magnet, for example, moved into a coil of wire (a solenoid) will cause a voltage to be generated and we can obtain a similar effect, without any visible movement if we place two coils close together (Figure 10) and switch a current on and off in the circuit connected to one coil, the primary coil. This will cause a voltage to be generated in the second coil, the secondary, but only for as long as the current in the primary coil is changing. A steady (DC) current causes no voltage to be generated. The effect is called electromagnetic induction and the voltage produced in the second coil is an induced voltage. This principle is that of the transformer, which can be used with AC only, because only in AC circuits will the current in the primary coil be changing continually.

Induce Yourself

Changing the current through a coil of wire won't just induce a voltage in another nearby coil, though, it will also induce a voltage in itself! This effect is called self-induction and the voltage which is induced will be in a direction which *opposes* the changing current that actually causes it (Figure 11). This is a *back-EMF* (the EMF means Electro-

$E = L \times \text{RATE OF CHANGE OF CURRENT}$
WRITTEN AS

$$E = L \frac{\Delta I}{\Delta T}$$

WHERE Δ MEANS 'CHANGE OF'

Figure 12. The equation for the self-inductance of a coil.

$$L \propto \frac{AN^2}{l}$$

A = AREA OF CROSS SECTION
N = NUMBER OF TURNS
l = MAGNETIC LENGTH
 \propto = 'PROPORTIONAL TO'

Figure 13. This formula cannot be used for calculating the inductance of a coil, but it does show how changing dimensions changes the inductance.

$$N_2^2 = \frac{N_1^2 \times L_2}{L_1}$$

L ₁ = INDUCTANCE	} FIRST EXAMPLE
N ₁ = TURNS	
L ₂ = INDUCTANCE	} SECOND EXAMPLE
N ₂ = TURNS	

Figure 14. The formula of Figure 13 can be rearranged to calculate the number of turns that must be removed (or added) to change the inductance of a given coil.

Motive Force, an old word for a generated voltage) and we can use this voltage to measure a useful quantity, the self-inductance of the coil, usually indicated by the letter 'L' in radio formulae. The equation that links inductance with back-EMF is shown in Figure 12. The unit of self-inductance is the Henry, named after the American physicist, Joseph Henry; one Henry is the self-inductance when a current changing at the rate of one amp per second produces a back-EMF of one volt. One Henry is a very large amount of inductance — a quantity we aren't likely to use except in smoothing inductors for power packs or in loudspeaker cross-over networks — so that smaller quantities such as the millihenry (mH), one thousandth of a henry (0.001 H) and the microhenry (uH), which is one millionth of a henry (0.000001 H), are more usually found.

The inductance of a coil can be measured, but it can't be calculated simply from its dimensions and the number of turns, so that we need to use charts, nomograms and other aids to calculation. One useful, approximate, relationship is shown in the formula of Figure 13, however — the inductance is proportional to the area of cross-section of the wire multiplied by the square of the number of turns and divided by the 'magnetic length'. This last quantity refers to the length of the magnetic field in the core and isn't necessarily equal to the physical length of the coil but, all other things being equal, it means that if you separate the turns of a coil you will increase its magnetic length and reduce its inductance. Similarly, increasing the number of turns will considerably increase the inductance — doubling the number of turns without changing the length (by using thinner wire) will make the self-inductance four times as great (because $2^2 = 4$).

Because this formula applies reasonably well to a coil which has already been designed, it is a useful way of adjusting the value of inductance

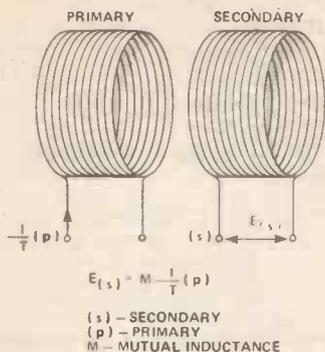


Figure 15. Mutual inductance is the basis of the transformer effect of Figure 10.

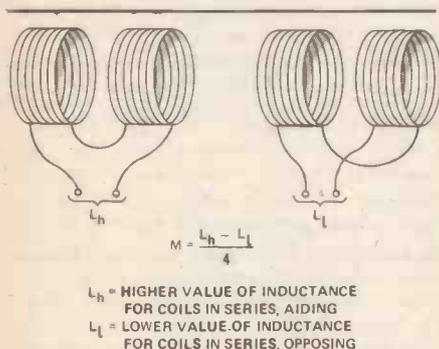


Figure 16. Mutual inductance cannot be easily calculated but it can be measured.

slightly. For example, suppose you have a coil of 80 turns which has an inductance, with the core in place, of 300 uH. How many turns do you have to take off to make the inductance 280 uH? The answer can be obtained by chopping the formula around to the form shown in Figure 14, retaining only the number of turns because the other quantities can be kept approximately constant. Yes, the length will change, but not by much and you could, if you wanted to be fussy, adjust the remaining turns to take up the same length on the core. Using

$$N_2^2 = \frac{N_1^2 \times L_2}{L_1}$$

we have

$$N_2^2 = \frac{80^2 \times 280}{300}$$

which is 5973.3. The square root of N_2^2 is 77.3, equal to N_2 . That's only about three turns off the coil (told you it wouldn't change much!) to make the adjustment. In practice, you don't have to worry about fractions of a turn, except for VHF coils, because you can make fine adjustments by pulling out the turns of the coil (increasing length) or compressing them closer (decreasing length).

It's Mutual

A pair of coils arranged as a transformer will have mutual inductance as well as two lots of self-inductance and this quantity is defined in the same way as self-inductance, except that the change of current is measured in one coil and the induced voltage in the other (Figure 15). The mutual inductance is also measured

in units of Henrys but is a lot more difficult to calculate, because it depends on how closely the coils are coupled — meaning how much of the magnetic field of one coil affects the other. Mutual inductance can very seldom be satisfactorily calculated; it normally has to be measured by a bridge circuit or by making two separate measurements of the self inductance of the coils, connected in series with each other. Two measurements are made and the connections to one coil are reversed for one of the measurements. The readings are then used to find mutual inductance using the formula in Figure 16.

In practice, there's a huge variation in the shapes and sizes of inductors, according to the job that they are intended to do. Basically, the slower the rate of change of current (which means lower frequency), the bigger the inductor needs to be and the heavier the core. For smoothing 50 Hz ripple in a half-wave power supply, you might need a couple of thousand turns of fine wire wound on a paxolin bobbin with a set of soft-iron laminations inserted tightly into the centre of the bobbin to make a core inside and outside the coil, guiding the magnetic field around it. At the other end of the scale, if you were dealing with VHF, where the rate of change of current is extremely fast, a couple of turns of thick wire in air, with no core, might be all the inductance you needed. For UHF, you find that you don't need coils at all — a straight strip of metal a few centimetres long is as much inductance as you need.

Between these extremes, a very useful form of construction that sees a lot of use is the iron-dust or ferrite cored inductor. This consists of a plastic tubular former with a core of a non-conducting magnetic material. The coil is wound on to the former and its inductance value is varied by screwing the core up or down inside the former. Transformers for frequencies ranging between 100 kHz and 50 MHz or so can be made in this way.


In general, if you are constructing equipment and you are instructed to wind a coil of 30 turns on a 10 mm diameter former which is fitted with a specified type of core, don't be tempted to deviate from this specification unless you know how much inductance is needed — and you have some method of measuring exactly how much you end up with.

$$C = \frac{E_r A}{d} \times 0.884 \text{ PICO FARADS}$$

E_r = RELATIVE PERMITTIVITY

A = AREA IN SQUARE cm (ONE PLATE)

d = SPACING IN mm

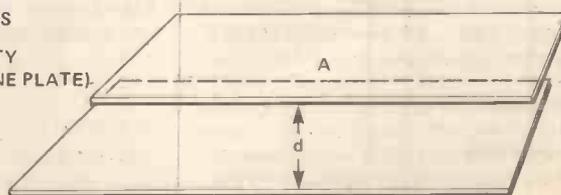

EXAMPLE: A CAPACITOR HAS A PLATE AREA OF 7cm² SPACED 0.03mm APART AND USING MICA WITH RELATIVE PERMITTIVITY = 5, WHAT IS ITS CAPACITANCE ?

SOLUTION: CAPACITANCE = $\frac{5 \times 7}{0.03} \times 0.884p = 1031p$ OR 1n03

Figure 17. The capacitance of two parallel metal plates, slightly separated.

Capacitance

The other electrical quantity which is important in AC circuits is capacitance. Capacitance is the ability to store electric charge, the stuff whose movement we call electric current, and there is always some capacitance between any two points which are at different voltages, even momentarily. Capacitance is defined as the ratio of charge stored to the voltage between the points. Some capacitances in our circuits are 'stray', meaning that they exist simply because there are pieces of metal close to each other in the circuit, but most of the capacitors we use have been deliberately designed and manufactured.

The simplest type of capacitor consists of two plates of metal which are separated by an insulator; this arrangement is called a parallel-plate capacitor. The amount of capacitance — how much charge the arrangement can store, per volt placed across the plates — depends on the area of the plates (assumed to be identical and aligned with each other), the distance between the plates and the type of insulating material placed between the plates. The formula is shown in Figure 17 — note, in particular, that the capacitance is increased by putting the plates closer together and is also increased by using materials like ceramics, which have a large 'relative permittivity' as insulators. Don't confuse relative permittivity with relative permeability (of a magnetic material); permittivity is quite a different quantity and its values are lower; a relative permittivity of 100 or more is very unusual.

The insulating material, or dielectric, between the plates also provides the insulation for the capacitor and the voltage applied between the plates must never be so great that it will break down this insulation. The type of dielectric also depends on the frequency of the signals that are to be handled. Mica, for example, can be used at the highest frequencies for which we make capacitors, whereas paper is useful only to about 20 MHz and is seldom used nowadays.

The value of a capacitance is measured in units called Farads — you have a capacitance of one farad when a charge of one coulomb causes the voltage across the plates to increase by one volt. Unfortunately, the Farad is a huge unit and we need to use smaller units, such as microfarads (uF, 0.00000

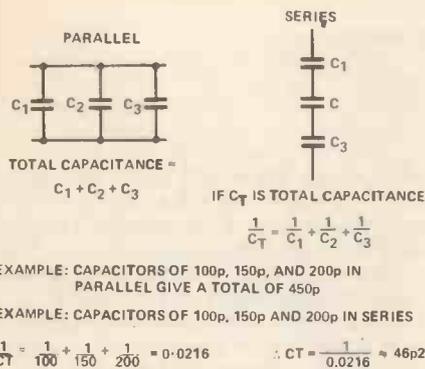


Figure 18. Calculating the overall value of capacitors connected in series or in parallel.

1 F), even smaller units such as nanofarads (nF, 0.001 uF) or picofarads (pF, 0.000001 uF). Watch carefully which values are used in equations, because some make use of the capacitance measured in Farads, some in microfarads and some in picofarads.

Fixed capacitors can be made from metallised mica or ceramics and the metallized plates can be stacked together to provide larger values, because connecting capacitors in parallel gives an increased value — see Figure 18 for capacitor connections in series and in parallel. Mica capacitors are used in 'important' parts of radio circuits, where any change in the value of a capacitor would cause de-tuning, for ex-

ample. Ceramics, by contrast, are used mainly in less important places in which the precise value is less important.

Paper and (particularly nowadays) plastic dielectric capacitors are made by metallising both sides of a thin film of the dielectric material, which is in the shape of a long strip. The strip is then wound into a cylinder with another metallised strip to act as insulator (Figure 19). This type of construction is used for the larger values of capacitance, normally in audio stages or in some supply decoupling ap-

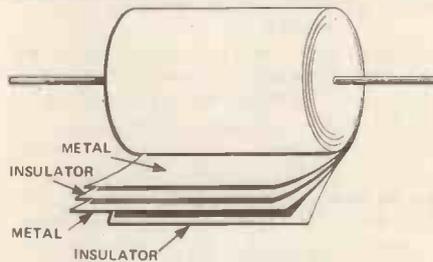


Figure 19. The rolled-strip construction commonly used for paper and plastic film capacitors.

plications. Electrolytic capacitors use 'plates' (usually thin foil, wound into a spiral) made from aluminium or tantalum and separated by sheets of paper or cloth which have been impregnated with chemicals (ammonium perborate, if you must know). The chemicals are conducting — the insulator is the very thin film of aluminium oxide (or tantalum oxide, if

this is the metal that is used) that forms on the metal surface when a voltage is applied to the capacitor to 'form' it. Once an electrolytic capacitor has been formed, the voltage should never be reversed, hence the polarity markings on electrolytic capacitors. Very large values of capacitance can be obtained in very small sizes, using electrolytics because the insulating film is so thin, but there is always a 'leakage' of DC current through an electrolytic and the voltages at which they can be used are comparatively low. Their main application is for smoothing power supply voltages and signal coupling in transistor audio circuits.

Finally, variable capacitors allow us to alter capacitance and this is one of the main methods of tuning radio circuits, as we shall see later. Variables can be air-spaced, as they usually are in transmitter circuits, or solid-dielectric spaced, as they usually are in pocket radios, but the principle is the same — one set of plates is fixed, and the other can be meshed with them, so that the area of overlap changes. It is the changing area of overlap that accounts for the change of capacitance. The radio receiver types usually have minimum and maximum values of 30 pF and 300 pF respectively, but miniature types with much smaller values and ranges are used in radio transmitters and in short-wave receivers.

Join us next month to find out about time constants, reactance and tuned circuits.

HE

IT LIVES AGAIN!

From the past it came, growing daily, striking terror into the hearts of lesser publications, and spreading its influence across the country in its quest to infiltrate every town, every home, every mind.

Not a horror story, but a success story. And if electronics theory strikes terror into you, then you need the help of **Electronics — It's Easy**. Originally a long-running series in Electronics Today International, **Electronics — It's Easy** was printed as a set of three books. They sold out. It was reprinted as a single volume. It sold out. Now this phenomenally successful publication is available again, in its third reprint. **Electronics — It's Easy** is a comprehensive and simply-written guide which explains the theory (and the practice) of electronics step by step. Every aspect of the subject is covered, starting with the basic principles and working through to the how and why of today's technology.

You can obtain your copy of **Electronics — It's Easy** by mail order using the coupon below. Make cheques or postal orders payable to ASP Ltd; alternatively you may pay by Access or Barclaycard.

Send to: Sales Office (Specials),
513 London Road, Thornton Heath
Surrey CR4 6AR

Please send me copies of **Electronics — It's Easy**. I have enclosed £ (£4.95 each including p&p).

NAME

ADDRESS

Please debit my account

My Access/ Barclaycard No. is

Signature



BUYLINES

ANOTHER month, another Buylines Page — making sure you know exactly where to buy ALL our project components. The listed suppliers are not the only sources for particular items, but are those companies we know who generally stock the components mentioned. Of course, if you intend buying a complete kit for a project, then you need not worry about getting separate parts. However, don't abandon this page, since we often include new suppliers and handy construction tips — both worth further investigation.

Power Supply

FOR such a straightforward project, the parts will be easy to obtain. However, the suppliers mentioned here are a good source for the necessary components.

The voltage regulator (7812), and other similar types are stocked by **Rapid Electronics** and **Delta Tech**; take your pick — you might also find a local stockist of these often-used ICs. Transformers can be bought from specialist suppliers — such as **Barrie Electronics** — or from other sources like **Watford** and **Technomatic**. If you fancy a toroidal type then you can order one direct from **ILP Electronics** using their freepost service.


The large value smoothing capacitor is available from **Electrovalue**, or you may be able to pick up a bargain from **Crimson Components** — remember, a higher voltage rating is fine, so long as the capacitor still fits on the board!

The cost for components will vary according to the voltage selected, but will be between £6-£10.

Auto-Wah

The Auto-Wah uses a few rare components but, in most cases, more standard types can be substituted for those used in the prototype. If you want to stick with the original design, the polycarbonate capacitors (6n8) are available from **Electrovalue**, though the commoner C280 variety will do; either way, you will find their range quite comprehensive. They have also assured us that they can obtain the unusual 'make' contact jack-sockets used to switch on the unit.

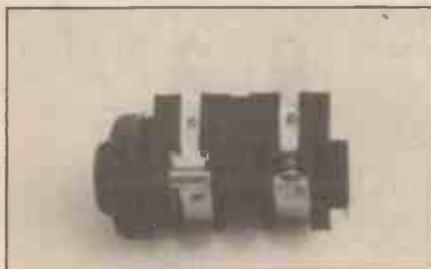The semiconductors should not be hard to find, but you might like to try a



new company for the 2N5088 transistors. **Benning Cross** are getting together their stock lines at the moment, so if you want anything particular then drop them a line. The only other supplier of 2N5088s that we could find, is **Cricklewood Electronics**. However, a suitable equivalent is the BC109C — a lot easier to buy.

The RC4558 is a relatively new IC that combines two 741s in an 8-pin DIL package. It is equivalent to the 1458, which is stocked by most companies. If you have any problems, try **Bi-Pak** or **Summit Electronics** (another new name for your checklist).

The case for our Auto-Wah (and rather smart it is too) is from the RS Components catalogue (No. 508-201); it can be ordered from any component supplier who normally stocks parts from the RS range. If you'd like to try a different one, then take a look at the new **West Hyde** catalogue, where you'll also find the PCB supports (standoffs to you!).


The total cost — using our PCB — will be around £15.

Auto Greenhouse

SOMETHING to bear in mind, when you're testing the HE Sprinkler, is to make sure you have a plentiful supply of water and somewhere to spray it — an early bath awaits those who don't heed this warning!

The components for this project are all fairly easy to obtain. The ZTX300 transistors are to be found in just about every supplier's list, so it's worth shopping around for the best buy. **Crimson Electronics** offer these, and other components, at very reasonable prices.

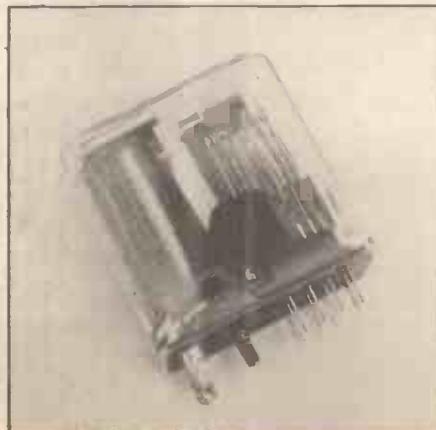The CMOS ICs are all stocked by **Technomatic** who can also supply an alternative to the relay we used (RS catalogue No. 349-658). The siren is also from the RS catalogue (No. 249-794) and can be ordered from most suppliers. On the mechanical side, the water pump included in the design is, in fact, from a car-spares



shop — just ask for a 12 V windscreen washer pump! Again, it's worth shopping around since you don't need anything elaborate.

One final point concerning the power supply circuit. The bridge rectifier in our prototype had a much higher spec than necessary so, unless you intend to run other items from the supply, any bridge that can handle 6 A at 50 V will do — **Delta Tech** are worth a call for a good deal on these and other commonly used components.

Without the case or windscreen-washer pump, the cost of the sprinkler will be around £12 (including our PCB).

Telephone Timer

BEFORE starting this project, it's a good idea to sort out exactly where you want to put it. Ours is intended to be wall mounted, so the display was placed on a flat front panel. If you want yours to lay on the telephone table, you can try a case with a slanting top. Take a browse through one of **BICC-Vero's** catalogues for something suitable.

Now for the components themselves. The CMOS ICs are no problem with a company like **Technomatic** — their range is quite staggering. Another company well-known for its semiconductors is **Cricklewood Electronics**. For this project they can also supply the 22u tantalum capacitors, along with the small 7-segment displays. The ceramic disc capacitors are usually very easy to buy but, in this case, the required values are quite high (although you could try fitting a C280). The specified components are stocked by **Electrovalue** and, at the other end of the parts list they also keep the Bulgin mains connectors. **Bi-Pak**, who don't just sell bargain component packs, stock the rotary switches (Lorlin) and the push-to-break switches; alternatively, **Benning Cross** are stocking up on a wide range of switches and other associated hardware.

The only remaining parts you might have trouble with are the fuseholder (panel mounting) and the ribbon cable. Conveniently enough, both of these are available from **Watford Electronics**.

The components for the timer will be about £15, excluding the case, power supply and PCBs.

HE



TTLS	74367	55p	4014	60p	LINEAR I.Cs	MC1445	325p
7400	11p	74368	55p	4015	AN103	MC1458	30p
7401	11p	74390	100p	4016	AY1-0212	600p	MC1495L
7402	12p	74393	100p	4017	AY1-1313	668p	MC1496
7403	12p	74490	120p	4018	AY1-1320	320p	MC3340P
7404	12p	74LS SERIES			AY1-5050	140p	MC3403
7405	18p	74LS00	12p	4019	AY3-1350	420p	MK50398
7406	25p	74LS01	14p	4020	AY3-8910	550p	ML920
7407	25p	74LS02	14p	4021	AY5-400/12	850p	MM57160
7408	14p	74LS03	14p	4022	CA3028A	520p	MM6221A
7409	15p	74LS04	15p	4023	CA3019	80p	NE531
7410	15p	74LS05	15p	4024	CA3046	70p	NE556
7411	20p	74LS08	15p	4025	CA3048	225p	NE564
7412	20p	74LS09	15p	4026	CA3059	300p	NE565
7413	22p	74LS10	15p	4027	CA3086	300p	NE566
7414	35p	74LS11	15p	4028	CA3088	200p	NE571
7415	25p	74LS12	25p	4029	CA3090A	375p	NE571A
7416	25p	74LS13	25p	4030	CA3130E	50p	RC4136
7417	25p	74LS14	40p	4031	CA3140	100p	RC4151
7420	17p	74LS20	15p	4032	CA3161E	140p	SA01024A
7421	30p	74LS21	15p	4033	CA3162	450p	SFF96364
7422	20p	74LS22	16p	4034	CA3189E	300p	SL490
7423	22p	74LS26	16p	4039	CA3230	120p	SN76477
7425	28p	74LS27	16p	4040	CA3280C	200p	SN76488
7426	30p	74LS30	15p	4042	DAC1408-8	200p	SN76495
7427	35p	74LS32	15p	4043	HA1366	300p	SPR515
7428	30p	74LS37	16p	4044	HA1388	270p	TA7120
7430	15p	74LS38	16p	4044	ICL7106	850p	TA7204
7432	25p	74LS42	36p	4046	ICM7216B	£18	TA7205
7433	27p	74LS47	40p	4048	ICM7217	700p	TA7222
7437	27p	74LS51	15p	4048	ICL8038	70p	TA7310
7438	30p	74LS52	15p	4049	ICM7555	80p	TA821
7440	17p	74LS73	25p	4050	LC1210	400p	TBA651
7441	70p	74LS74	16p	4051	LC7130	400p	TBA800
7442A	36p	74LS75	24p	4052	LF347	160p	TBA810
7443	30p	74LS76	20p	4053	LF351	48p	TBA820
7445	60p	74LS83	45p	4055	LF353	100p	TCA950
7446A	93p	74LS85	45p	4055	LF356P	95p	TCA990
7447A	45p	74LS86	20p	4056	LF357	120p	TCA990
7448	45p	74LS90	28p	4059	LM10C	425p	TDA1004A
7451	17p	74LS92	40p	4060	LM301A	27p	TDA1008
7453	17p	74LS93	30p	4063	LM310	120p	TDA1010
7454	17p	74LS95	45p	4063	LM318	200p	TDA1022
7460	17p	74LS96	45p	4067	LM319	225p	TDA1024
7470	36p	74LS107	45p	4068	LM324	30p	TDA1038
7472	30p	74LS109	30p	4068	LM334Z	100p	TDA11040
7473	30p	74LS112	34p	4070	LM335Z	140p	TDA2002V
7474	20p	74LS113	30p	4072	LM339	50p	TDA2006
7475	30p	74LS121	45p	4071	LM348	75p	TDA2020
7476	30p	74LS122	30p	4073	LM358P	60p	TLO64
7480	50p	74LS123	50p	4075	LM377	175p	TL071/81
7481	100p	74LS124	120p	4076	LM380	75p	TL072/82
7482	100p	74LS125	30p	4081	LM381A	180p	TL074
7483A	45p	74LS126	30p	4081	LM382	120p	TL084
7484	100p	74LS127	30p	4082	LM386	95p	TL084
7485	90p	74LS133	30p	4089	LM388	95p	TL170
7486	20p	74LS136	30p	4093	LM389	95p	TL340C
7489	210p	74LS138	34p	4094	LM391	150p	TL340C
7490A	25p	74LS139	36p	4095	LM393	100p	UAA170
7491	60p	74LS145	75p	4097	LM394	300p	UAZ240
7492A	30p	74LS147	160p	4098	LM395	100p	UDN6118
7493A	30p	74LS148	160p	4098	LM399	95p	UDN6184
7494	50p	74LS151	70p	4099	LM399	95p	UDN6184
7495A	50p	74LS153	60p	40085	LM399	95p	UDN6184
7496	45p	74LS154	90p	40097	LM399	95p	UDN6184
7497	120p	74LS155	40p	40102	LM399	95p	UDN6184
7498	85p	74LS156	40p	40103	LM399	95p	UDN6184
74107	22p	74LS157	35p	40103	LM399	95p	UDN6184
74109	40p	74LS158	36p	40106	LM399	95p	UDN6184
74116	90p	74LS160	40p	40109	LM399	95p	UDN6184
74118	75p	74LS161	40p	40163	LM399	95p	UDN6184
74119	90p	74LS162	40p	40173	LM399	95p	UDN6184
74120	70p	74LS163	40p	40174	LM399	95p	UDN6184
74121	25p	74LS164	48p	40175	LM399	95p	UDN6184
74122	45p	74LS165	100p	40193	LM399	95p	UDN6184
74123	48p	74LS166	90p	40257	LM399	95p	UDN6184
74125	40p	74LS170	120p	40257	LM399	95p	UDN6184
74126	40p	74LS173	70p	4507	LM399	95p	UDN6184
74128	40p	74LS174	42p	4508	LM399	95p	UDN6184
74132	45p	74LS175	45p	4508	LM399	95p	UDN6184
74136	32p	74LS181	140p	4510	LM399	95p	UDN6184
74141	65p	74LS190	50p	4511	LM399	95p	UDN6184
74142	200p	74LS191	50p	4512	LM399	95p	UDN6184
74147	100p	74LS192	50p	4515	LM399	95p	UDN6184
74148	75p	74LS193	40p	4515	LM399	95p	UDN6184
74148	75p	74LS194	40p	4516	LM399	95p	UDN6184
74150	80p	74LS195	48p	4518	LM399	95p	UDN6184
74151A	45p	74LS196	60p	4520	LM399	95p	UDN6184
74153	45p	74LS197	65p	4521	LM399	95p	UDN6184
74154	70p	74LS221	60p	4522	LM399	95p	UDN6184
74155	50p	74LS240	70p	4527	LM399	95p	UDN6184
74156	50p	74LS241	70p	4528	LM399	95p	UDN6184
74157	50p	74LS242	80p	4532	LM399	95p	UDN6184
74159	100p	74LS243	80p	4534	LM399	95p	UDN6184
74160	60p	74LS244	65p	4536	LM399	95p	UDN6184
74161	60p	74LS245	90p	4538	LM399	95p	UDN6184
74162	60p	74LS246	90p	4539	LM399	95p	UDN6184
74163	60p	74LS247	40p	4543	LM399	95p	UDN6184
74164	50p	74LS257	45p	4553	LM399	95p	UDN6184
74165	55p	74LS258	45p	4555	LM399	95p	UDN6184
74166	70p	74LS259	90p	4556	LM399	95p	UDN6184
74170	140p	74LS260	90p	4560	LM399	95p	UDN6184
74172	300p	74LS266	25p	4568	LM399	95p	UDN6184
74173	65p	74LS273	75p	4569	LM399	95p	UDN6184
74174	60p	74LS279	45p	4572	LM399	95p	UDN6184
74175	60p	74LS283	45p	4583	LM399	95p	UDN6184
74176	50p	74LS298	160p	4584	LM399	95p	UDN6184
74177	70p	74LS323	250p	4585	LM399	95p	UDN6184
74178	100p	74LS324	150p	14495	LM399	95p	UDN6184
74180	50p	74LS348	150p		LM399	95p	UDN6184
74181	160p	74LS352	100p		LM399	95p	UDN6184
74182	90p	74LS353	90p		LM399	95p	UDN6184
74184A	90p	74LS363	160p		LM399	95p	UDN6184
74185	120p	74LS364	160p		LM399	95p	UDN6184
74186	500p	74LS365	36p		LM399	95p	UDN6184
74188	325p	74LS367	36p		LM399	95p	UDN6184
74190	50p	74LS368	36p		LM399	95p	UDN6184
74191	50p	74LS373	70p		LM399	95p	UDN6184
74192	50p	74LS374	70p		LM399	95p	UDN6184
74193	50p	74LS375	50p		LM399	95p	UDN6184
74194	12p	74LS377	90p		LM399	95p	UDN6184
74195	12p	74LS378	70p		LM399	95p	UDN6184
74196	14p	74LS390	55p		LM399	95p	UDN6184
74198	14p	74LS393	50p		LM399	95p	UDN6184
74199	15p	74LS399	200p		LM399	95p	UDN6184
74221	14p	74LS541	135p		LM399	95p	UDN6184
74251	70p	74LS670	170p		LM399	95p	UDN6184
74273	75p	4000 SERIES	74241	450p			
74278	150p	4000	74241	450p			
74279	80p	4001	74241	450p			
74283	80p	4002	74241	450p			
74284	200p	4006	65p				
74285	200p	4007	16p				
74290	100p	4008	60p				
74293	100p	4009	35p				
74298	100p	4010	40p				
74365	55p	4011	14p				
74366	55p	4012	14p				

* MICROTRAINER *

(as described in the current issue)

- Hobbyists can now learn and explore the workings of microprocessors. This project opens the mystical field of computers to enthusiasts.
- A truly low cost teaching aid useful for training centres, schools and industries. In fact a short step towards developing new ideas and systems. Gives effective insight into micros to engineers, technicians, etc. not directly involved in the computer field.
- Expansion facilities provided for serious constructors (watch for further articles).
- A professional grade high quality thru plated PCB is included. Please phone for kit price.

SWITCHES		DIGITAST SWITCHES		VERO BOARDS	
Toggle	1xP	Push to make (R, G, B)	15p	2.5" x 5"	90p
Summiture	15p	Push to break (Black)	15p		

HE Auto-Wah

HE's auto-effect takes the work out of wah-wah.

Steve Giles

IT IS some sixteen years since the first guitar processing units became available. Those first effects units paved the way for controlled distortion and sophisticated filtering systems. Eventually, the development of phasers and flangers, in the seventies, gave the musician versatility and control from circuitry entirely within the unit's case. Other effects, like the wah-wah pedal, have external controls (a foot pedal attached to a pot which sweeps the filter up and down). Phasers and flangers are voltage controlled, by a slow oscillator, to provide their characteristic cyclic sweeping effect. So, no matter how hard the strings are plucked, the sound processing remains the same. This led to a desire for some additional responsiveness and, towards the end of the 1970s, guitar processing units appeared which were triggered by command signals from the guitar. This is similar to the way commands from a keyboard synthesiser can trigger envelope generators when a key is played. Of course, in the case of a guitar, this occurs when a string is plucked. The HE Auto-Wah is one such 'guitar triggered' effects unit. It can be built for a fraction of the cost of similar commercial units and will process signals in a number of interesting ways.

The usual circuit for a device of this type first feeds the guitar signals through an envelope follower. This produces a DC voltage that corresponds to the overall amplitude of the output from the instrument — strumming harder produces a higher DC output voltage. This feeds a comparator which goes high when the envelope follower voltage exceeds a certain threshold. It then drops back to zero when the envelope drops below this threshold. However, there is a problem in the case of guitar notes. Although the initial peak of a note will be more than sufficient to trigger the comparator, as the amplitude falls, there may be one or two extra peaks among the generally decaying level. These cause the envelope voltage to momentarily rise and retrigger the comparator. This is illustrated in Figure 1 which shows two additional peaks after the envelope voltage has fallen below the comparator threshold. A considerable amount of circuitry is necessary to minimise such false triggering. Apart from being outside the scope of this article, it was not too much of a problem with our prototype unit, which simply used a high gain input amp to trigger a comparator. This allows the production of a new 'frequency-band' sweep each time a note is played (dependent on the



settings of the sweep controls), so long as you don't pick too quickly.

With such sudden changes of state — a high output or zero — it's important to ensure that a complete filter cycle sweeps smoothly across the frequency range. To do this we used a field effect transistor, as a variable resistor, to control a bridge-T filtering network around an op-amp. By carefully adjusting the threshold control, it's possible to play chords with virtually no false triggering and produce quite a deep wah-wah effect.

Circuit Description

The circuit of Figure 2 has two basic sections, one consisting of 1C1, Q1 and Q2 to produce the control voltage,

and the other formed by IC2 and Q3 — the inverting bandpass filter. The signal is fed to IC1a, a non-inverting amplifier, whose gain is set at a high level by a large feedback resistor (R3). This ensures the unit functions properly from even low output guitars. The output from IC1a is then fed to pin 5 of IC1b via R4, where threshold control RV1 sets the point at which it will be triggered by IC1a. The output from the comparator is rectified by D1 and passed to emitter follower Q1 (via R6) after charging C4, which is in parallel with R15. When IC1b goes high, it is followed by Q1, providing a smooth charging action on C2 until the emitter voltage is attained. At this point, C2 discharges through R7, RV2 and RV3 to the 0 V rail. The voltage level for Q1 is set by RV2, since it controls the point at which C2 begins to discharge. The ramp voltage on C2 is fed to RV4 and also via R9 to an inverter, based around Q2. The inverted signal goes to the other end of RV4, which acts as a balance control to provide some control over the shape of the envelope. The voltage at RV4's wiper is then passed to the gate of Q3, a field effect transistor (FET), which operates as a part of the input, via C8 and R17. In this way the signal is band-pass filtered, with C5 and C6 chosen for optimum sound effect. These two capacitors determine which narrow band of the guitar signal is boosted. This band is moved up and down the audio spectrum by varying the drain-source resistance of Q3 — producing the familiar wah-wah effect. The voltage fed to Q3's gate is therefore affected by the setting of RV4, which sweeps the filter from the bass or treble end. Since this type of FET requires a control voltage negative to half the supply rail, the series combination of R14 and RV5 provide a bias to shift the gate voltage between 0 V and half the supply.

Filter decoupling is provided by C7

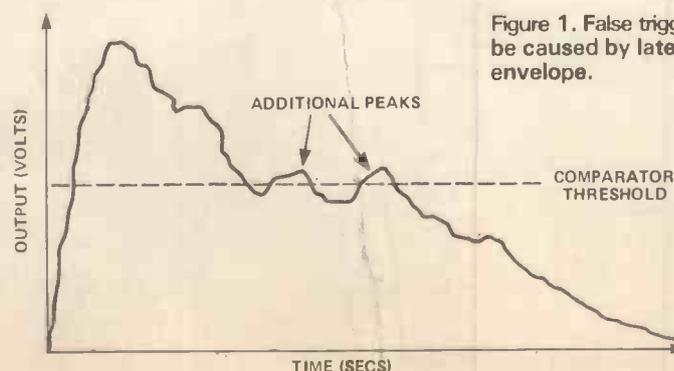


Figure 1. False triggering of an auto-wah can be caused by late peaks in the voltage envelope.

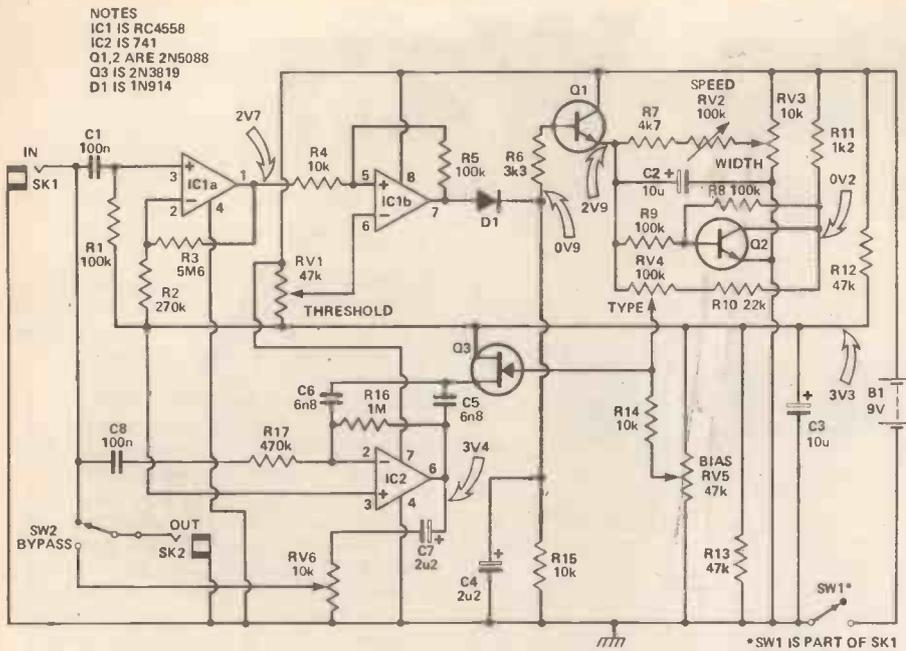


Figure 2. The complete Auto-Wah circuit with some typical DC voltages indicated. Note these measurements apply with no input signal applied.

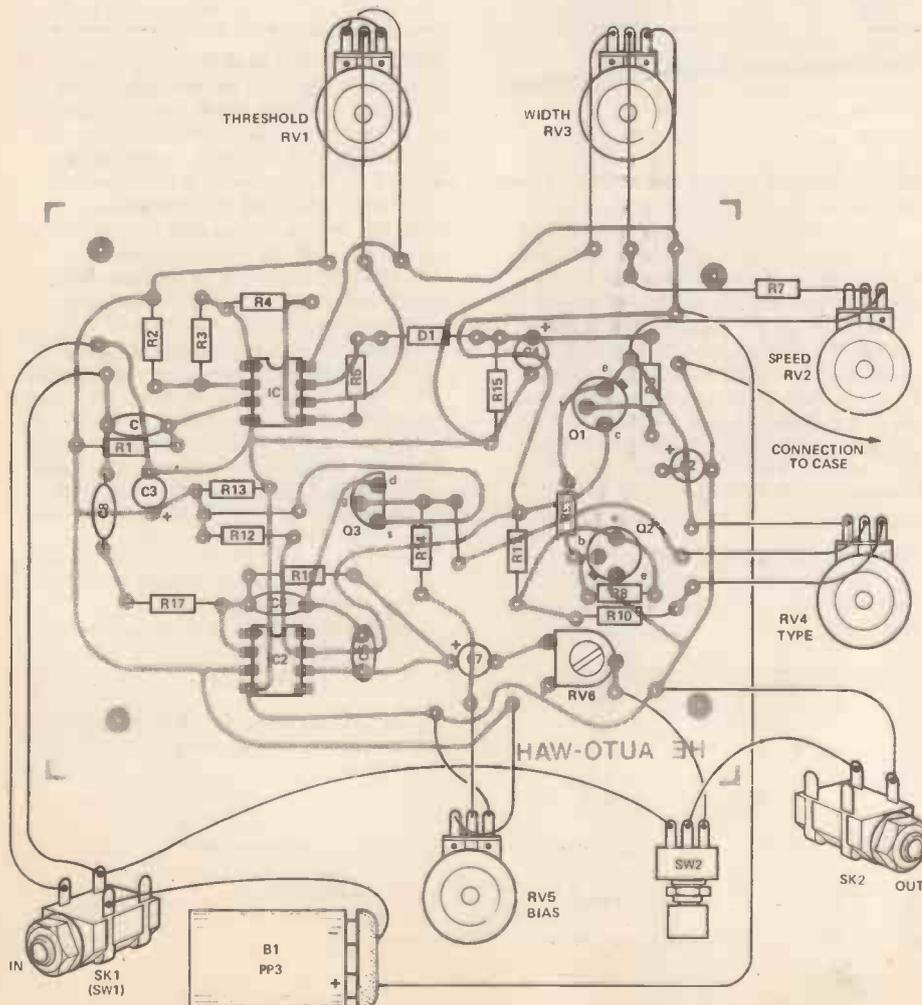


Figure 3. View from the component side of the PCB.

and attenuated by RV6, allowing the output to match the input level. As a single-ended supply is used, R12 and R13 set the mid-supply voltage, which is by-passed by C3. Current consumption is rather high at 12.5 mA, so we recommend you use a long-life (alkaline) PP3 type battery for extended use.

Construction

Referring to the component overlay diagram of Figure 3. Begin by soldering the two wire links and resistors. Next, the capacitors, making sure that correct polarities are observed for the tantalum types. Now, assemble the three transistors and the diode (D1). You must ensure these are placed with their leads in the proper positions. The diode must have its banded end (cathode) nearest R15. Transistor Q2 needs its base lead bent to fit the right

Parts List

RESISTORS (All 1/4 W, 5%, Carbon)

R1,5,8,9	100k
R2	270k
R3	5M6
R4,14,15	10k
R6	3k3
R7	4k7
R10	22k
R11	1k2
R12,13	47k
R16	1M
R17	470k

POTENTIOMETERS

RV1,5	47k linear carbon
RV2,4	100k linear carbon
RV3	10k linear carbon
RV6	10k sub-miniature preset

CAPACITORS

C1,8	100n C280 polyester
C2,3	10u 10 V radial electrolytic
C4,7	2u2 10 V radial electrolytic
C5,6	6n8 polycarbonate (metallised)

SEMICONDUCTORS

IC1	RC4558 dual op-amp
IC2	741 op-amp
Q1,2	2N5088 silicon NPN transistor
Q3	2N3819 N-channel FET
D1	1N914 silicon diode

MISCELLANEOUS

SK1 (SW1)	1/4" jack socket with make contacts
SK2	1/4" jack socket
SW2	push-to-make switch
B1	PP3 9 V alkaline 'Long Life' Battery

Case (RS 508-201), PP3 battery clips, 8-pin DIL socket, collet knobs (3 off), shallow knobs (2 off), short standoffs (4 off), PCB, solder, wire, etc.

positions; the other two transistors fit without changing the position of any leads. The IC's are not fitted yet, but if you are using sockets these can be soldered into place, ready to take the IC's.

Lastly, wire up the five pots, two sockets and footswitch — don't forget the battery connector. The (red) positive wire from the connector, is soldered direct to the PCB. The negative (black) wire is taken to one earth tag on the input jack. The other earth tag is connected to the board so that the battery is only switched on when a jack-plug is inserted.

To make sure you have the leads connected to the right tags, put a standard jack-plug into the input socket. This should push the earth connector to link the two earth tags together. If your jack socket has 'break' rather than 'make' contacts, you will have to bend the short tag connector backwards and over the top of the other one. Of course, this is avoided if you buy a socket with 'make' contacts, in the first place.

When you have completed all the off-board wiring, it only remains to plug in the ICs and switch the unit on by inserting a jack-plug into the input socket. However, before starting to play with the effect, it's a good idea to check on some voltage readings. These are shown on the circuit diagram (Figure 2), and apply when no input signal is present. The control settings are as follows: RV1, RV4 and RV5 — full rotation; RV2 and RV3 midway along the track. It is essential you set the pots in this way, since some of them have a large effect on quiescent voltages. One final point to note is that readings must be taken using a high-impedance DC meter.

If everything seems OK, you can hook the output up to an amplifier and set RV4 for maximum downwards sweep. Pluck a string on your guitar: gently, so as not to trigger the comparator, and set RV5 at the base end of the filter's passband. Now pluck the string hard and the filter should sweep from treble to bass.

Now try setting RV4 at the other end — this point may lie halfway along its track. You will then hear the pass-

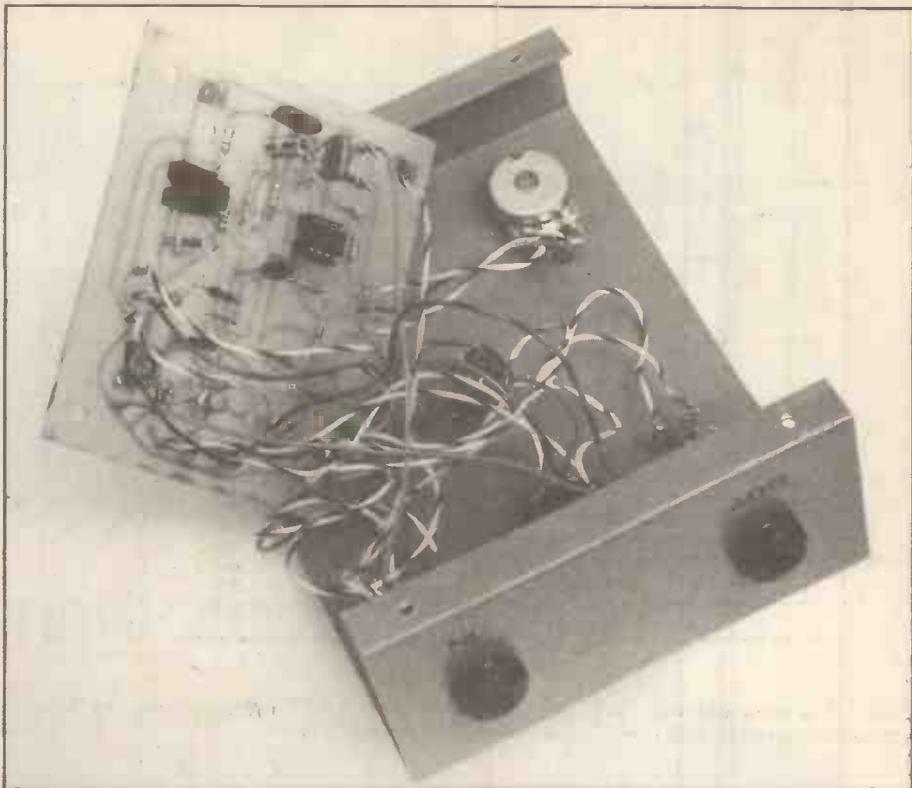


Figure 4. The internal wiring will be neater if sections of 2 and 3-core strip cable are used.

band sweep from bass to treble. Somewhere close to the mid-setting of RV4, the filter acts in a confused manner, giving some very interesting effects, especially to chords. Altering RV3's setting changes the width of the sweep and produces a gentler effect.

However, the most effective way of setting up the unit is to adjust RV2 and RV3 to their minimum rotations. Then, with RV4 set about two-thirds along its travel and RV1 full-on, adjust RV5 until the unit produces a wah-wah sound. Finally, turn back RV5 so that triggering only occurs as you pluck the string. Once this is done, RV1, and RV5 can be left alone while you 'play' with the others.

After getting used to the various control settings, drill holes for the pots,

sockets and footswitch in the case. Our prototype used short 'stand-offs' to secure the PCB. With the unit fully assembled, you can mark the positions of the threshold and bias controls, as necessary. However, the bias control can still be adjusted to produce some weird variations to the basic sound. It's really up to you to discover just how versatile this unit is. It is also possible to alter the basic effect by changing certain component values. For instance, for a less pronounced bass response, change C8 to a smaller value (say 10n). The mid position of RV4 will give different effects if R10 is changed. Lastly, a different filter response will be achieved if the values of C5 and C6 are changed — try 10n for starters.


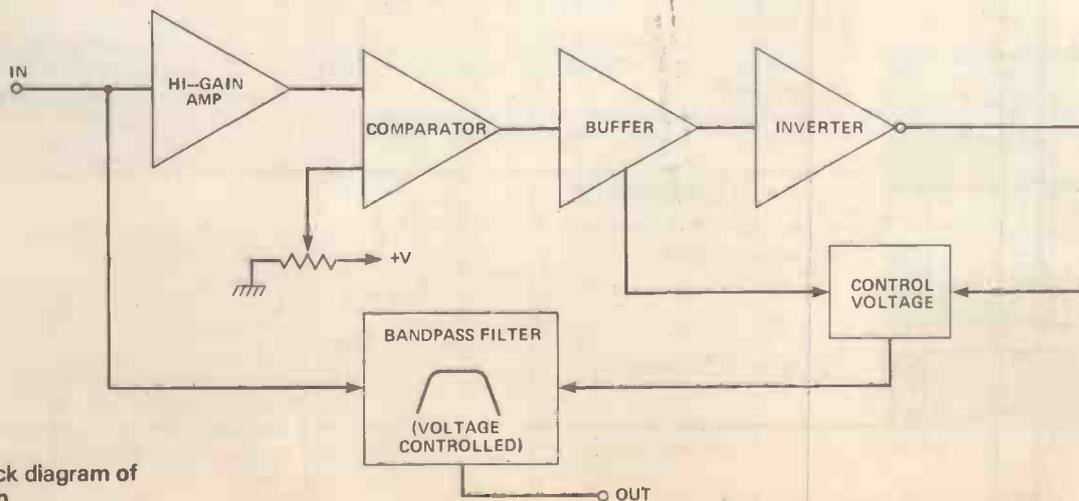
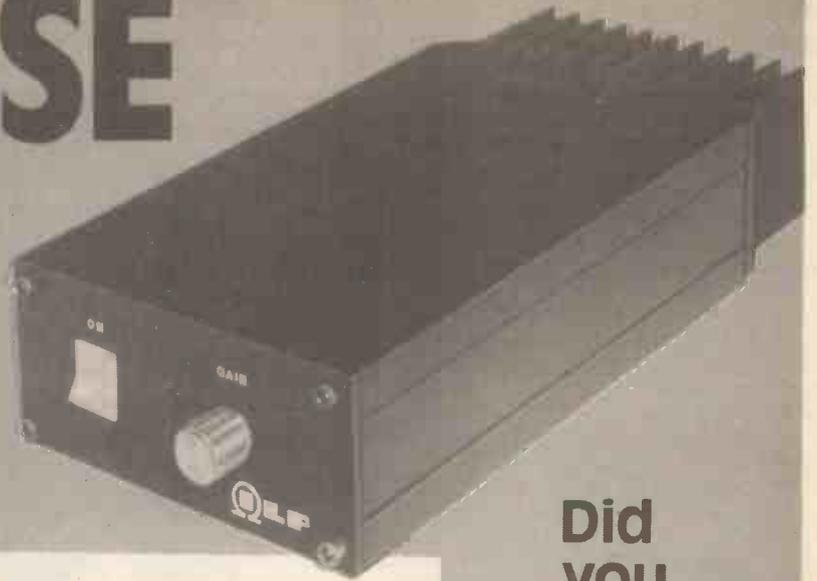


Figure 5. Block diagram of the Auto-Wah.

THE CASE FOR

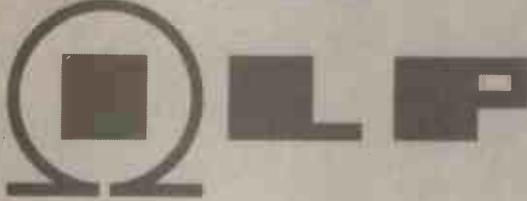

It's the chance every constructor wants

Did you know



POWER AMPS



P.S.U's



PRE-AMP MODULES

It's something you have always wanted...something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U's, the range will shortly be extended to house any other modular projects.

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. **ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN.** It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, **FREE.** You don't even have to stamp the envelope if you address it the way we tell you.

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are **TWENTY** power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?



FREEPOST 6
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

FREEPOST
Mark your envelope clearly **FREEPOST 6** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

SEND COUPON
(NO STAMP NECESSARY)
FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE

To: I.L.P. ELECTRONICS LTD.
PLEASE SEND ME I.L.P. CATALOGUE,
POST PAID BY RETURN

I HAVE/HAVE NOT PREVIOUSLY
BUILT WITH I.L.P. MODULES

Name: _____

Address: _____

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

Sebastian De Ferranti

Kelvin J Williams

The founder of one of Britain's leading technological organisations.

BORN IN LIVERPOOL in 1864, Sebastian Ziani de Ferranti was a direct descendant of a Doge of Venice, Sebastian Ziani, one of the more respected and influential Doges during the twelfth century. The family later added 'Ferranti' to the name during the eighteenth century. His father owned a photographic studio in Liverpool, while his mother was a talented concert pianist who gave recitals all over Europe.

Sebastian showed scientific tendencies at a very early age and, while still at school, he devised an electric arc lamp and generator, the forerunner of a machine he was to develop later.

He left University at 17 and went to London where he was given employment by the Siemens Company, at Woolwich, for £1 a week. Here, he was asked to assist Sir William Siemens himself in research work and superintended the installation of electric lighting plants. He did not stay with Siemens for long, however. His potential was quickly recognised by a Mr Alfred Thomson, a photographer, and Mr Francis Ince, a lawyer with interests in electrical work. They persuaded Ferranti to leave Siemens and form a company, 'Ferranti Thomson and Ince Ltd', to manufacture an alternator with an ingenious zig-zag armature which Ferranti had designed himself. This was a most efficient machine, with a much greater power output than others of the same size and weight, at the time. It was found, however, that the generator which Ferranti had patented, with Alfred Thomson, had very similar features to a machine designed by Sir William Thomson (later Lord Kelvin). The machine became known as the Ferranti-Thomson dynamo and firmly established a reputation for the young engineer.

The company broke up in 1883, so Ferranti formed his own company, based in a small workshop in Hatton Garden, London, where he continued his work on electricity meters. The new company expanded quickly with products such as dynamos, meters, transformers, power switches and fuses. Ferranti's design and development of accurate meters for the measurement of electricity was a great asset to the new, fast growing technology. At the time, much of London was still lit by gas, oil and candles.

Battle of the Systems

Electric lighting was a rare sight and there was great controversy between DC and AC systems. Ferranti, who was fast becoming an expert on AC, was approached by the proprietor of the Grosvenor Gallery, in London, to review a small installation which had been in-

stalled to enhance the display of the exhibits. The small plant had become so successful that a profitable business had been formed to supply neighbouring customers. The demand for electric lighting was so great, though, that the system was soon overloaded and in need of urgent redesign. As a result of his advice, Ferranti, at the age of 22, was offered the position of engineer to the Grosvenor Gallery Company. Using transformers and switchgear of his own design, he quickly reformed the entire system, changing from serial to parallel operation, doubling the working voltage from 120 volts to 240 volts and extending the network to cover over 100 miles of streets in just three years.

By now, the controversy over the different supply methods had become known as the 'Battle of the Systems', although the Electric Lighting Act of 1882 had encouraged low voltage DC systems. Ferranti, however, had his mind on bigger and better things. He proposed a large central generating station for transmission of AC at high voltages. These plans were taken up by the Grosvenor Gallery Company and, in 1887, the London Electric Supply Company Ltd. was formed to set up a large generating plant at Deptford — with Ferranti as chief engineer.

Ferranti was responsible for the whole venture, from the design of the building, its architecture and materials, the generating plant itself, transformers, switchgear, meters and supply cables.

The Deptford Experiment

The Deptford site was ideal, as there was easy access by road, rail and water for the supply of materials, equipment and coal. His decision to transmit at 10,000 volts was received by many as highly dangerous and foolhardy, but Ferranti's solution was to use a specially designed underground cable with concentric conductors and an outer sheath connected to earth. Unfortunately, this was contrary to the Board of Trade Regulations but, so convinced was Ferranti of the correctness of his idea, that he disregarded the Regulations and pressed on. Fortunately, his courage and determination won the day and he laid down the first, safe system for high voltage distribution.

He made the cables, in 20 foot lengths and they consisted of hollow copper tubes insulated with wax impregnated paper; the outer cable was wrapped around the paper and the two were contained in a protective iron tube, filled with molten wax forced in under pressure. To prove the safety of his system Ferranti organised a demonstra-

tion where his foreman held a metal chisel, in his bare hands, over a live cable while an assistant hammered the chisel through the cable using a sledgehammer. He was protected by fuses and switchgear designed by Ferranti and so, as the chisel pierced the cable, no harm was brought to man or machine. According to the story, somebody asked the foreman if he had been afraid of the possible consequences; his reply was, "Yes, my assistant had never used a sledgehammer before!"

In 1889, the Deptford generating station was visited by Thomas Edison and, although he was the leading exponent of the DC system, he was very impressed with Ferranti's work and surprised at the advances made with AC transmission.

Generation of electricity from Deptford began in 1891 and the two cables laid between Belvedere Road and the Grosvenor Gallery, over Charing Cross Bridge, remained in use until 1933 when the whole network was finally closed down to make way for more modern systems.

After the opening of the Deptford station, Ferranti went back to manufacturing again and set up a business in London to continue production and development of generators, transformers, switchgear and meters. By 1896, the company acquired new premises at Hollingwood, in Lancashire. Soon he employed over 700 workers and enjoyed a profitable business from his new designs and developments. His engineering interests were many, outside the field of electrical work, and some of his major ventures included turbines, cotton spinning gyroscopes and radio transformers.

Ferranti had been elected a member of the I.E.E. (Institute of Electrical Engineers) in 1891 and he became President of the Institute during the year 1910/11. He received the degree of Doctor of Science of the University of Manchester in the following year. Ferranti died in 1930, at a hospital in Switzerland. His restless mind, however, was active to the last and he was described by many of his contemporaries as both a visionary and a practical engineer.

BIBLIOGRAPHY

The Life and Letters of Sebastian Ziani de Ferranti by G.Z. de Ferranti and R. Ince.

Pioneer of Electric Power Transmission — An Account of Some of the Early Work of S. de Ferranti 1864-1930 by S.Z. de Ferranti.

S.Z. de Ferranti — His Influence Upon Electrical Development by W.L. Randell.

Ferranti Company Brochure Sept. 1979.

ELECTRONIC IGNITION

Makes a good car
better



As a
KIT
or
READY
BUILT

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue
and EVERYDAY ELECTRONICS December '81 Issue

FITS ALL NEGATIVE EARTH VEHICLES,
6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS
Some older current impulse types (Smiths pre '74) require an adaptor —
PRICE £2.95

STANDARD CAR KIT £14.85
Assembled and Tested £24.95

TWIN OUTPUT KIT £22.95
For MOTOR CYCLES and CARS with twin ignition systems
Assembled and Tested £34.70

PLUS
£1.00
U.K.
P. & P.
Prices
Include
VAT.

ELECTRONIZE DESIGN

Dept. E, Magnus Road, Wilnecote,
Tamworth, B77 5BY

Phone: (0827) 281000



COMPONENTS IN BIRMINGHAM

CMOS-LSTTL-LINEAR-ICs NOW!!! IN DEPTH STOCK

From National Semiconductor:

Some Egs:	4011	15p	4013	34p	4017	42p
	4093	38p	40161	69p	4543	134p
	74LS00	12p	74LS90	33p	74LS366	28p
	LM380	75p	TBA120	90p	TDA2640	216p

Full range list available + Quantity discounts. Ask for details

PCBs. The FOTOWay — Brochure on Request.

NEW BARGAIN PACKS:

16 — TTL ICs	£1.10	6 — Slide Switches	60p
9 — CMOS ICs	£1.10	100 — 1/8 Watt Resistors	60p
10 — Croc Clips	£0.60	30 — 1 Watt Resistors	60p
5 — Ex. Equipment Bds	£1	5 — Large Elect Caps	£1
8 — Knobs	£1.20	4 — Rotary Switches	£1.20

Post & packing 60p per order. FREE over £10

ALL PRICES + VAT

P.A.T.H. Electronic Services Wholesale + Retail
369 Alum Rock Road, Birmingham B8 3DR. Tel: 021 327 2339

Open 10 till 6 weekdays. 9.30 till 5 Saturdays

Distributors for: Antex — Altai — Babani — Hills — Servisol — PATH FOTOWay —
PATH Box — Safgan — Vero Electronics + MUCH MUCH MORE . . .

DESOLDERING TOOL Now everyone can afford one of these superb, blue anodised aluminium high pressure hand desoldering tools at nearly half our normal price. Normal Price £8.50 + VAT. With this ad £3.85 + VAT. Spare Teflon screw-in noses 75p + VAT.

JAPANESE TRANSISTORS Equivalents available for most types. Please call, phone or write.

LOW COST VERSATILE MULTIMETER

THE MIGHTY MINI MULTI-TESTER 2,000 ohms per volt. DC & AC Voltage ranges: 10v, 50v, 250v, 1000v. DC current ranges 100mA. Resistance ohms x 10 x 100db from —10db to +22db. Mirror arc scale, overload protected, complete with battery, test leads & instructions. Usual price £8.65 + VAT; with this Ad: £4.95 + VAT.



ORDER FORM

Name:

Address:

..... Desoldering tools at £3.85 = £

..... Spare Teflon noses at 75p = £

..... Mighty Mini Testers at £4.95 = £

Postage, packing and insurance at 60p per one device, 25p for each additional device £

Sub total £

Add 15% VAT £

I enclose cheque no/P.O. no.

Alternatively please credit my VISA/ACCESS No.

Signature

This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow to cover postage. TRADE ENQUIRIES WELCOME.

CRICKLEWOOD ELECTRONICS LTD.

40 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161

RECHARGEABLE BATTERIES AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE SEND SAE
FOR LISTS. £1.45 for Booklet "Nickel
Cadmium Power" plus Catalogue.
Write or call:

* NEW SEALED
LEAD RANGE AVAILABLE *

SANDWELL PLANT LTD.

2 Union Drive, Boldmere
Sutton Coldfield, West Midlands
021-354 9764

After hours 0977 84093

Breadboards

THIS MONTH in order to revive the popular 'Short Circuits', we are beginning a new series of circuits for the experimenter's among you. The idea is that we will present a circuit design that works and is easy to put together, but which can be modified as required. In order that you can play around with the designs, we've provided a breadboard (hence the name) layout. These layouts are by no means critical and you may make up your own, if you wish. One last point: the circuits presented here are for experimentation and development only. We cannot offer any technical back-up or further advice about *any* of them. However, each has been tested in its original form, and will function as stated in the accompanying text. Also, we will accept designs from readers for *possible* publication, so if you've got a particular circuit that you'd like to see in Hobby Electronics, send it right away — mark the envelope 'Breadboards' and enclose an SAE if you want your design returned.



To start the series, we're providing two circuits based on that most widely used of all ICs, the 741. The first design is for an ultra-simple square wave generator. It produces quite a well defined square wave at the lower end of the audio spectrum. Possible uses include; calibration of test gear, tone generators for models and toys, and as a pulse generator.

The second circuit uses two 741s in a 14-pin DIL package designated a 747 (not a Boeing). One op-amp provides the rectification and the other is a simple mixer to allow both halves of the wave to be added together. One novel application for this arrangement is as an audio frequency doubler. With the addition of decoupling and stabilising components, some quite unusual 'musical' effects can be produced.

Square Wave Oscillator

IF you thought that the only way of producing a square wave was to use a 555 timer IC, then here's a circuit to change your mind. It's a square wave generator requiring only five components, including the IC — a 741 op-amp. The circuit consists of a Schmitt Trigger with positive feedback provided by the 10k resistors. The timing components, C1 and R3, control the frequency of oscillation and this can be varied over quite a large range (50 Hz to about 7 kHz) before the shape of the wave is no longer square.

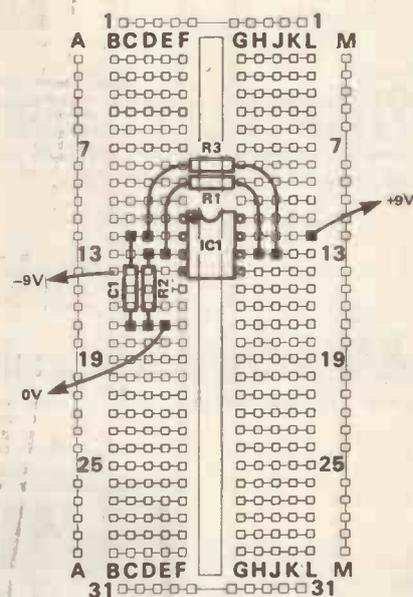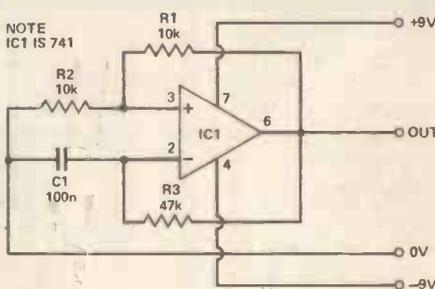
If you monitor the voltage at pin 2, it can be seen to follow an exponential charge/discharge pattern, determined by the RC constant of R3 and C1. The mark-to-space ratio can be altered by placing a 10k resistor and a series signal diode in parallel with R3. This makes C1 discharge 11 times faster than it charges up. Current consumption is about 1.5 mA per rail.



Circuit (top) and Veroboard layout (bottom) of the square wave oscillator.

Full Wave Rectifier/ Frequency Doubler

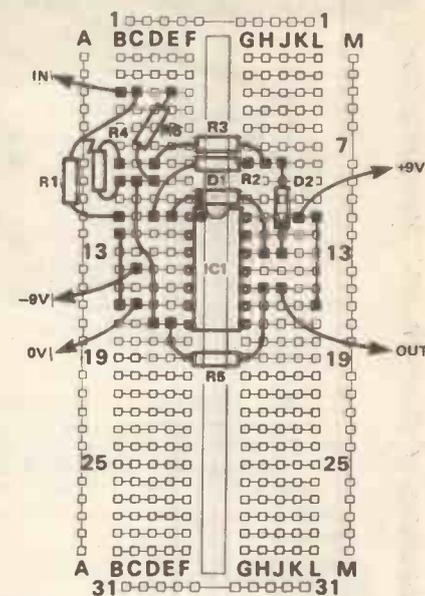
THE EASIEST way of converting AC into something resembling DC is to use a bridge rectifier followed by a large smoothing capacitor. Without the capacitor, the resulting waveform consists of positive half waves, at twice the original AC frequency. This is fine for typical power supply voltages; but at lower levels a problem arises. The voltage drop across the diodes



Rectifier/doubler layout.

(about 600 mV for silicon) becomes significant and the usual bridge circuit is unsuitable. A simple way to overcome this problem is to use an op-amp, like IC1a, in the circuit shown. This consists of an inverting amplifier with negative feedback (pin 12 to pin 1), so there is a 'virtual earth' at pin 1. When the input is positive, D1 maintains the virtual earth (D2 is reverse biased) by conducting and leaving the output 'looking at' 100k to the 0 V rail. When the input goes negative, D2 is turned on and D1 turned off. The output is then the exact inverse of the input — positive going half sinewaves. We now have half wave rectification from a low-level AC input. By adding the original waveform to the output in the right amount, the result is full wave rectification (with some distortion). This mixing is carried out by the summing amplifier IC1b.

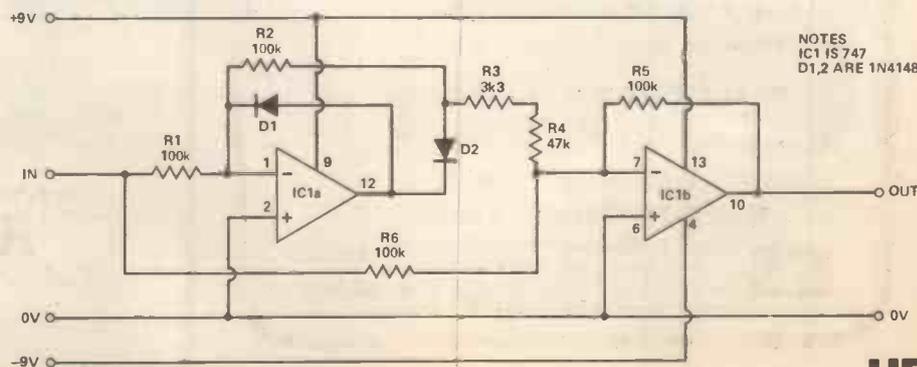If R3 and R4 are replaced by a 100k pot, the output is fully adjustable from half wave rectified, through full wave to a sloping edge square wave — dependent on the input level. Current consumption is around 2 mA per rail.



Circuit of the full wave rectifier/doubler

MASTER ELECTRONICS NOW!

The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

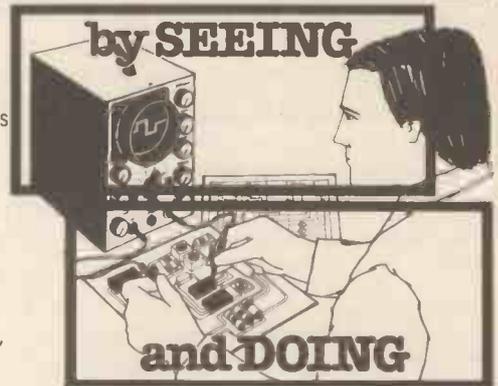

New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE



POST NOW TO:

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE
- OTHER SUBJECTS _____

HE/6/821

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 7BR

MARC DOUBLE CONVERSION 12-Band world receiver

Space Commander
with DIGITAL-
FREQUENCY
COUNTER

Full coverage
of 12 bands:
LW, MW, SW x 4,
VHF x 5 and UHF
5W power output



NIKJAN 833 CB 6-Band receiver

Frequency range!
88-176 MHz and 40 Ch CB

For more information ask:
General Importers for U.K.

Albrecht Electronic GmbH
Otto-Hahn-Str. 7a
D-2077 Trittau

Tel. 04154 / 3055 · Telex 2 189 406 Agru d

Send for my CATALOGUE ONLY 75p

(plus 25p post/packing)

My VAT and post/packing inclusive prices are *the* lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS . . . ELECTROLYTIC; CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS. 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE. DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

BRIAN J. REED
TRADE COMPONENTS

ESTABLISHED 25 YEARS

161 St. Johns Hill, Battersea, London SW11 1TQ

Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 5016

GREENWELD


443F Millbrook Road, Southampton, SO1 0HX

All prices include VAT at 15% — just add 50p post

1982/3 CATALOGUE

Bigger! Better! Buy one!!
Only 75p inc. post
Look what you get!!

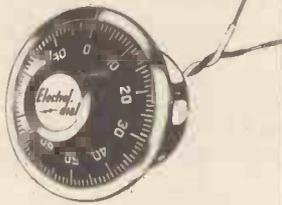- Vouchers worth 60p
- 1st class reply paid envelope
- Wholesale list for bulk buyers
- Bargain List with hundreds of surplus lines
- Huge range of components
- Low, low prices
- Sent free to schools, colleges etc.



ELECTRO-DIAL

Electrical combination lock for maximum security, absolutely pick-proof! One million combinations! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid etc. Overall dia 65mm x 60mm deep. Finished in bright chrome. With a combination the price is £9.95. Also available without combination, but instructions are provided on how to find it. Takes about 20 mins. £2.95

5V 3A REGULATED PSU KIT
A197 All components + heat sink to build this simple yet useful power supply. A regulated output of 5V at up to 3A for just £2.50. Suitable transformer (9V 3A) £4.85

741 OP-AMP — 12 for £1

A recent purchase of Raytheon IC's included a large quantity of 14 DIL 741 op-amps, so take advantage while stocks last! 12 741's £1.00

SOLENOIDS AND RELAYS

W921 Solenoid rated 48V at 25% duty cycle, but work well on 24V (700gm pull, 10mm travel) push or pull 27 x 18 x 15mm 55p
W922 Mains 240V ac solenoid, 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50
W895 9V DC relay 500R SPCO 28 x 24 x 19.50p
W733 11 pin plug in relay, 240V ac, 3PCO 5A contacts £2.50. Base 36p
W838 700R 24V 4PCO "continental" relay 35 x 30 x 18mm, only 84p, 10/£7.00
W847 37R 5-10V relay, SP 3A contact, PCB mntg 11 x 33 x 20.95p, 10/£7.50
W893 Omron LY4 mains relay, 4PCO 5A contacts. £2.50

MIXED LED PACK

All new full spec by Micro, Fairchild, etc. Red, Yellow, Green, Amber, Clear, 3mm & 5mm. Pack of 50 asstd £3.95; 250 £15

AMAZING! COMPUTER GAMES PCB's for PEANUTS!!

A bulk purchase of PCB's from several well known computer games including Battleships, Simon, Logic 5 and Starbird enable us to offer these at incredibly low prices:

'STARBIRD'

Gives realistic engine sounds and flashing laser blasts — accelerating engine noise when module is pointed up, decelerating noise when pointed down. Press contact to see flash and hear blast of lasers shooting. PCB tested and working complete with speaker and batt. clip (needs PP3). PCB size 130 x 60mm. Only £2.95

'SIMON'

The object of this game is to repeat correctly a longer and longer sequence of signals in 3 different games. (Instructions included). PCB contains chips, switches, lampholders and lamps, and is tested working, complete with speaker. Needs PP3 and 2 x HP11. PCB size 130 x 130mm. Only £3.95

'COMPUTER BATTLESHIPS'

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value only (PCB may be chipped or cracked): SN76477 sound IC; TMS1000 u-processor; batt clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

'MICROVISION' Cartridges

These are a small PCB with a micro-processor chip, designed to plug in to the microvision console. Only snag is we don't have any consoles!! However, they can be used as an oscillator with 4 different freq. outputs simply by connecting a battery and speaker. Tested and working (as an osc) with pin out data. PCB size 72 x 60mm.

ONLY 25p each!!

LOGIC 5 PANEL

Tested Logic 5 now sold out — but we have some PCB's with 10 LED's and chip on, but no keyboard. Not tested. 50p

1W AMP PANELS

A011 Compact audio amp intended for record player on panel 95 x 65mm including vol control and switch, complete with knobs. Apart from amp circuitry built around LM380N or TBA820M, there is a speed control circuit using 5 transistors. 9V operation, connexion data supplied. ONLY £1.50.

PACKS PACKS PACKS

K517 Transistor Pack. 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114, 117, 172, 182, 183, 198, 239, 251, 214, 255, 320, BF198, 255, 394, 2N3904 etc etc. Retail cost £7+. Special low price 275p
K523 Resistor Pack. 1000 — yes, 1000 ¼ and ½ watt 5% hi-stab carbon film resistors with pre-formed leads for PCB mounting. Enormous range of preferred values from a few ohms to a several megohms. Only 250p. 5000 £10; 20,000 £36

K524 Electrolytic pack. Large variety of mostly PCB mounting caps with cropped leads. All new full spec. — no chuck-outs or floor sweepings!! 200 £4.00; 1000 £17.50

K520 Switch Pack. 20 different assorted switches — rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 20p

K521 Heatshrink pack, 5 different diameters each 200mm long. What a bargain 50p
K522 Copper clad board. All pieces too small for our etching kits. Mostly double sided fibreglass. 250g (approx 110 sq ins) for 100p

K541 It's back!! Our most popular pack ever — Vero offcuts. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq ins of vero copper clad offcuts, average size 4 x 3". Offered at around ¼ the price of new board 320p



LIE DETECTOR

This beautifully made precision instrument is not a toy or gimmick, it was originally used on an Open University course to measure changes in emotional balance by detecting small changes in skin resistance. Full details of how to use it are provided, together with a circuit diagram. Supplied complete with probes, leads and conductive jelly. Needs 2 x 4½V batteries. Overall size 155 x 100 x 100mm. The 100-0-100uA 4" panel meter is worth more than we're asking for the whole unit!! £7.95

10W AMP PANEL

Neat board 115 x 62mm with Class B output. Uses 2 x 2N5293, 2 x BFY50, BFX29. Supply can be either 36V or 18-0-18V Input sensitivity 1V for 10W output. Small H/S on board: £2.95. Suitable transformer, bridge rect., smoothing and o/p capacitor: £5.50. Supplied with circuit/connexion data.

£1 BARGAIN PACKS


K201 25 1000uF 6.3V PC mntg electrolytics
K202 25 330uF 10V PC mntg electrolytics
K203 20 22uF 50V radial lead electrolytic caps
K204 16 47uF 50V radial lead electrolytic caps
K205 40 0.33uF 50V radial lead elec. caps
K206 40 0.47uF 50V radial lead elec. caps
K207 15 in line fuseholders, 1¼ in for cars etc.
K208 15 push-on push-off 'table' lamp switches

TEST INSTRUMENTS

THANDAR

Quality British Made Portable Instruments

DM450	£107.10
DC 10uV-1200V	AC 100uV-750V
DC 0.1nA-10A	AC 1nA-10A
0.01 -20M	4% digit LED
TM351	£99.00
DC 100uV-1000V	AC 100uV-750V
DC 100nA-10A	AC 100nA-10A
0.1 -2020M	3½ digit LCD

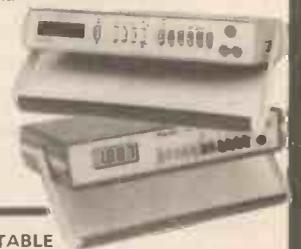

FUNCTION GENERATOR

TG102

£145.00

Freq. Range: 0.2Hz-2MHz

PORTABLE OSCILLOSCOPES

SC110

£139.00

Bandwidth 10MHz

Carriage for all Thandar Orders £1.00

SABTRONICS

Making Performance Affordable

Handheld DMMs	Assm/Kit
2033	£36.75
AC/DC 100uV-1000V	AC/DC 100uV-1000V
AC/DC 10uA-2A	AC/DC 0.1uA-2A
Ohms 1 -20M	Ohm 0.1 -20M

FREQUENCY METERS: 8 digit LED

8110A 20Hz-100MHz	Assm Kit
8610A 20Hz-600MHz	£67 £49
	£82 £68

FREQUENCY METERS: 9 digit LED

8610B 10Hz-600MHz (0.1Hz Resolution)	Assm Kit
8000B 10Hz-1000MHz (0.1Hz Resolution)	£99 £84
	£155

Carriage for all Sabtronics orders £1.00

SAFGAN

BRITISH MADE SCOPES

- DUAL TRACE
- Sm/ViRiv Sensitivity
- XY Facility
- Z Modulation
- Calibration Output
- Portable/Lightweight

DT410 10MHz	£179.00
DT415 15MHz	£185.00
DT420 20MHz	£198.00
X1-REF-X10 probe	£11.50 p8p £2.00



LEADER

When Quality Counts

LAG-16

£55.00
A compact solidstate RF signal Generator, most suited for checking the IF Circuits and tuners in AM, FM and TV sets



Frequency range up to 100MHz (300MHz on Harmonics)
Carriage £1.00



LCR-740

£149.00
A highly efficient impedance bridge for measuring resistance, capacitance and inductance. The D factor of a capacitor and the Q factor of a coil can also be measured.
Carriage £1.00

Many more instruments available from all these ranges

ADD 15% VAT ON ALL PRICES

All prices correct at 2.2.82 E&OE

Cash with Order or Credit Card

CALLERS WELCOME

OPEN MONDAY TO FRIDAY 9.00am - 5.30pm

DAROM SUPPLIES

4 SANDY LANE,
STOCKTON HEATH,
WARRINGTON,
CHESHIRE WA4 2AY
(0925) 64764

CATALOGUE
AVAILABLE
JUST SEND
A4 SIZE!
22p SAE

Building Blocks

WITH SUMMER fast approaching (hopefully), we thought you might like something to help while away those long evenings. What better way than to get acquainted with the more technical details of some ICs used in our projects? In this and subsequent issues, we are including a page or two on the workings of various ICs and other interesting semiconductors.

Out For The Count

The 4017 is a fairly cheap, but very useful little chip. As a decade counter or dividing network, it has obvious applications in counting circuits; several ICs can be wired in cascade (one following the other) to produce the count required. However, a more exciting feature of this chip is its ability to drive LEDs to give novel opto-effects, or to drive astables to produce musical tone generators — rather like those musical watches you can buy.

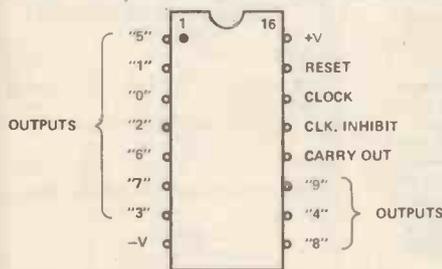


Figure 1. The pin-outs for the 4017 decade counter/divider IC.

The basic pin layout for the IC is shown in Figure 1. As you can see, the arrangement of the outputs is not in the same order as the pins (if anyone knows why, please let us in on the secret). This means you need to be careful about 'what goes to where'.

The way this IC works is quite simple and can best be understood by referring to the timing diagram of Figure 2. A clock signal is fed into pin 14 (the clock input)

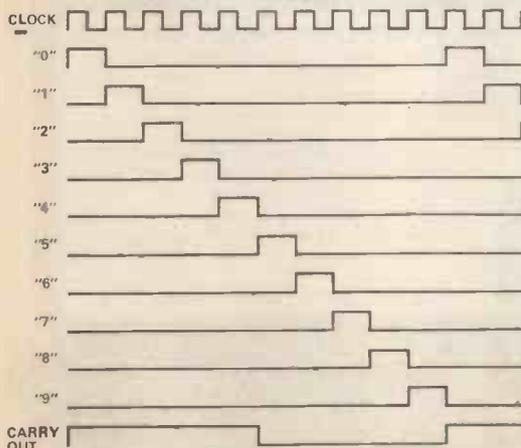


Figure 2. Timing diagram of the outputs from the 4017.

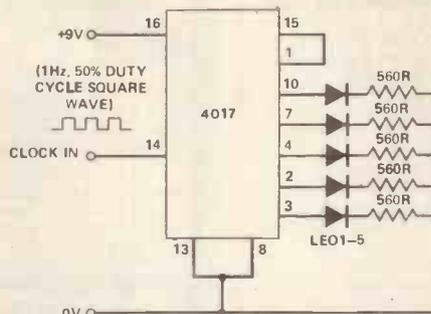


Figure 3. Circuit to provide a 'one-to-five' count. The reset pulse comes from pin 1, so the display keeps repeating.

which is then divided to produce ten separate outputs. These run sequentially from '0' to '9', each at one-tenth of the clock frequency (assuming the reset is enabled at the end of every tenth pulse). If the clock frequency is set low enough (around one pulse per second) then it's possible to create some interesting displays with LEDs on the outputs. These are wired in series with a resistor and then to ground. This circuit produces the familiar light chaser. Another application is shown in Figure 3, where five LEDs are used to provide a one-to-five second count.


The counter can be prevented from repeating a cycle by simply providing a high input to the clock inhibit pin. This is done by taking the output from the final pin in the sequence back to the inhibit pin. The sequence can still be re-started, though, by momentarily connecting pin 15 (reset) to the positive supply. A more *tuneful* application is to connect up a 555 astable to the decoded outputs, via a resistor chain from pin 7 on the 555. If you set it up properly, you can obtain a sequence of pulsed tones — you can even add a bit of rhythm (man) by missing out one or two of the outputs!

Flippin' Ripple Counters

The versatile count/divide function of the 4017 can be compared to our other device for this month; the 4027 dual J-K flip-flop. The 4027 is a more basic chip than the 4017 and, rather than divide-by-ten, it offers a divide-by-two (per flip-flop) facility. Figure 4 shows the pin configuration for this IC, which is divided into two identical sections with a shared power supply. The divide-by-two function is achieved by connecting together the 'set', 'reset' pins and taking them to 0V, then taking the 'J-K' inputs up to the positive supply. Incidentally, the clock signal must have a fast rise and fall time (<5 uS) for reliable operation. When the J and K inputs are held high (the input frequency being divided by two), the output states of Q and \bar{Q} will be changed or 'flipped' over. The other input states are shown in Figure 5, but it should be noted that the flipping action only occurs when J and K are *both* high.

The set and reset inputs operate asynchronously (independently of the clock). This means the outputs are forced into high and low states (set and reset respectively) whenever each set or reset input is taken high (unlike TTL). The 4027 will operate in this mode at frequencies up to 8 MHz.

However, the reason for using this type of circuit in the first place is that some applications (shift registers, for example, which are discussed later) must have no change in the output state whilst the clock pulse is high. In other words, whatever is occurring at the inputs must not affect the output. The system used is rather like a master control, followed by a slave back-up which is only engaged when the clock goes back to zero. This is achieved, within the chip, by using an inverter in series with the slave section; when the clock input is low, the slave is receiving a high level. However, the master section is locked and stores what was left from the last high on the clock pulse. When the clock goes high *again*, the master circuit is reacting to the 'set/reset' inputs and when the pulse reaches zero, the Q output is held in the new state. Now the slave can be enabled and it *seems*, from the output's position, we are changing states on the falling edge of the clock signal. This means the Q output can be in one of four conditions; high, low, unchanged or 'toggled', and it is this which makes the chip so versatile.

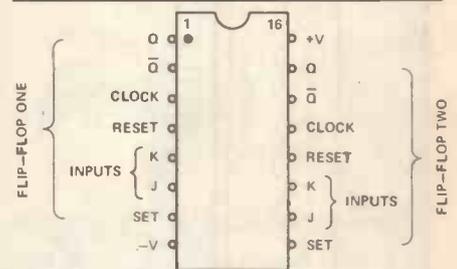

J	K	Q	\bar{Q}
0	0	UNCHANGED	UNCHANGED
0	1	0	1
1	0	1	0
1	1	TOGGLES	TOGGLES

Figure 4. Pin designations for the 4027 dual J-K flip-flop.

One obvious application for a chip which halves a given input frequency is to wire several in series to give division by powers of two — 2, 4, 8, 16 etc. The clock signal appears to 'ripple' down the dividing chain, which is why ICs with many such stages are called 'ripple counters' — an example is the 4040, with twelve stages. Another type of counter is known as the 'Johnson' or 'Walking Ring', where the stages are clocked in parallel.

The main reason for using this arrangement rather than the ripple counter, is that parallel clocking of the 'walking ring' type only produces a single stage of delay, since each stage is clocked simultaneously. This produces clean decoding of signals. A useful consequence of this is in shift register circuits, where signals are transferred down the line — one stage for every rising edge on the clock pulse.

BI-PAK BARGAINS



5121 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case
Sizes - 0.8, 1.4, 2.2, 4, 2.9 and 3.8mm **£1.75**

5131 NUT DRIVER SET
5 precision nut drivers in hinged plastic case
With turning rod
Sizes - 3, 3.5, 4, 4.5 and 5mm **£1.75**

5141 TOOL SET
5 precision instruments in hinged plastic case
Crosspoint (Phillips) screwdrivers - H 0 and H 1 Hex key wrenches - 1.5, 2 and 2.5mm **£1.75**

5151 WRENCH SET
5 precision wrenches in hinged plastic case
Sizes - 4, 4.5, 5, 5.5 and 6mm **£1.75**
BUY ALL FOUR SETS 5121-5151 and get HEX KEY SET FREE
HEX KEY SET ON RING
Sizes 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm
Made of hardened steel
HX/1 **£1.25**



BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
*3 1/2 digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single-handed, pushbutton operation *Over range indication *12.5mm (1/2-inch) large LCD readout *Diode check *Fused circuit protection *Test leads, battery and instructions included
Max indication 1999 or -1999
Polarity indication Negative only
Positive readings appear without + sign.
Input impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range -5°C to 50°C
Power Supply 1 x PP3 or equivalent 9V battery
Consumption 20mW
Size 155 x 88 x 31mm
RANGES
DC Voltage 0-200mV
0-2-20-200-1000V Acc. 0.8%
AC Voltage 0-200-1000V
Acc. 1.2% DC Current 0-200uA
0-2-20-200mA 0-10A Acc. 1.2%
Resistance 0-2-20-200K ohms
0-2 Megohms Acc. 1%
BI-PAK VERY LOWEST POSS PRICE
£35.00 each



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects
*Quantities approximate, count by weight.

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pf-56pf	£1
SX19	100	Mixed Ceramics 68pf-0.5mf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000mf	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240°, Inline 3-6 Pin, Speakers, Phono, Jack, Stereo and Mono, etc. etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money

SX26 3 Pcs. of 6 pin 240° DIN Plugs and Chassis Sockets **50p**
Sockets
SX27 1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket **30p**
Sockets
SX28 4 Phono plugs and 2 dual phono connectors **30p**
Sockets
SX29 1 x 2.5mm Plug to 3.5mm Socket adaptor **20p**
Sockets
SX30 1 x 3.5mm Plug to 2.5mm Socket adaptor **20p**
Sockets
SX31 1 x 3.5mm Plug to Phono Socket adaptor **20p**

BARGAINS

SX91	20 x Large 2" RED LED	£1
SX42	20 small 125 Red LED's	£1
SX43	10 Rectangular Green LED's 2	£1
SX46	30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded. New	£1
SX47	4 Black Instrument Knobs-winged with pointer 1/4" Standard screw. Fit size 29 x 20mm	50p
SX49	20 Assorted Slide Knobs Black/Chrome, etc.	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains - various types and colours - some panel mounting	£1

MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm
Bi-Pak's Mini Vice at a Mini Price only

£2.50

ORDER NO. SX82



The Third and Fourth Hand...

.... you always need but have never got "until now"
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier
Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
Without magnifier ORDER NO. T400 **£4.75**



MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer. MM100G suitable for guitar pre-amp mixer.
The MM100 and MM100G mono pre-amplifiers are compatible with the AL6Q, AL80, AL120 and AL250 power amplifiers and their associated power supplies.
MM100 Supply voltage 40-65v inputs. Tape Mag P.A.L. Microphone Max output 500mw ~~£12.45~~ MM100G Supply voltage 40-65v inputs: 2 Guitars, Microphones Max output 500mw

each **£10**



SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. Ins.	Price
FB1	4	9 x 2 1/2"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD


FB4	2	14 x 4"	110	£2.00
-----	---	---------	-----	-------

SILICON POWER TRANSISTORS - T03

NPN like 2N3055 - but not full spec 100 watts 50V min.
10 for £1.50 - Very Good Value
100s of uses - no duds
Order No. SX90

BI-PAK SOLDER - DESOLDER KIT

Kit comprises ORDER NO. SX80
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit
1 Quality Desoldering pump High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle
1.5 metres of De-soldering braid on plastic dispenser
2 yds (1.83m) Resin Cored Solder on Card
1 Heat Shunt tool Tweezer Type
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£8.95**

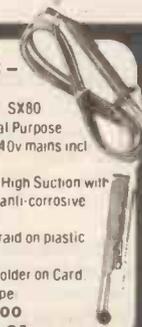

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit
1 Sheet PCB Transfers 210mm x 150mm.
1 Etch Resist Pen
1 1/2 lb pack FERRIC CHLORIDE crystals
3 sheets copper clad board
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards.
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.75**
ORDER NO. SX81



MW398 NI-CAD BATTERY CHARGER

Universal Ni-Cad battery charger. All plastic case with lift up lid. Charge/Test switch LED indicators at each of the five charging points
Charges - Power -
PP3 (9v) 220-240V AC
U12 (1.5v penlite) Dms -
U11 (1.5v C) 210 x 100 x 50mm
U2 (1.5v D) **£6.95**

POWER SUPPLY OUR PRICE £3.25

Power supply fits directly into 13 amp socket Fused for safety. Polarity reversing socket Voltage switch Lead with multi plug Input - 240V AC 50HZ Output - 3, 4, 5, 6, 7, 5, 9 & 12V DC Rating - 300 ma MW88

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module

Specification
● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz-3db ● Sensitivity 70 mw for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%
BI-PAK'S give away price

£2.25

You could not Build one for this price.



TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers - rotary and slider, presets - horizontal and vertical. Resistors of mixed values 22ohms to 2M2 - 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and lyes, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation

Price -
Beat the Budget
Down with Depression
JUST £6.50.



BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time - it pays to buy BI-PAK

To receive your copy send **75p** plus 25p p&p.



BI-PAK

Send your orders to Dept HE6, BI-PAK PO BOX 6 WARE HERTS
SHOP AT 3 BALDOCK ST, WARE HERTS
TERMS CASH WITH ORDER, SAME DAY DESPATCH, ACCESS
BAHCLAYCARD ALSO ACCEPTED, TEL (0920) 3182, GYRO 388 7006
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order. Total Postage add 75p per total order.

Clever Dick

The results of Hobby Electronics' latest survey (the one that carried a grossly distorted caricature of myself on the back — I do not look like that, nor am I in the habit of grovelling, like one of you!) are currently cluttering the already papered floor of the HE office. The results, when they are finally tabulated, should be interesting. One not entirely unexpected result of the previous survey was that most Hobby readers are male (surprise, surprise). That is apparently changing; I've already had one letter, this year, from a charming lady from Portsmouth, so imagine my surprise when I received the following letter shortly afterwards.

*Dear Clever Dick,
Your ending to your column in February, "Grovelling isn't everything", intrigued me. As a female reader and practitioner of your magazine and an anti-female-libber, I now propose to take extremely unfair advantage of my sex and offer you unlimited kisses (on paper) if you can donate one HE binder to the above address. I possess a total of five HEs but I definitely don't like untidiness about the place, so a binder would be much appreciated. Of course, if you can't send one I will cry.
Yours hopefully,
Maggie,
Biggleswade,
Beds.*

*PS My organ didn't work, either.
PPS I enclose a couple of stamps — I believe in going 'Dutch'.
PPPS I didn't think much of Wilding's cartoons.
PPPPS [Here follows an embarrassingly large number of 'Xs']*

Don't worry, Maggie. Ladies have been taking unfair advantage of me for years!

Some of the reasons invented to try and coax a binder from my special store are more imaginative than others. Here's a good one!

*Dear CD,
"Hello". Due to unavoidable circumstances, ie my dog ate it, my August '81 edition of HE has gone, never to return. So could you please send me a copy of the wiring for the HE Organ. I enclose a large stamped addressed envelope.
J. Pullen,
N. Yorks.*

*PS I've been reading HE since I was eleven so please send me a binder because I started so young and to stop my dog eating my HEs. Great mag, keep it up.
PPS Clever Dick for King.*

Thank you, thank you, but my natural modesty forbids, you see. I've already decided to send a binder, this month, to Maggie — her stamps are now speeding back to Biggleswade (always assuming the trains are still running) wrapped around one of my precious binders. As a consolation prize, though, I'll send the circuit you need, even though you are supposed to get it from the Backnumbers Department.

When I was an electronics constructor myself (many years ago, of course) I remember that the mechanical details — metalwork, lettering and getting a 'professional finish' — were usually the most difficult bits. Now, I have minions who take care of all these details — and it's all plastic now, which is much easier to work than sheet aluminium. However, this letter reminds me of the mechanical problems that still make life difficult for the electronics hobbyist.

*Dear CD,
Can you suggest ways for me to cut holes in the boxes that are used for your projects? I have great difficulty with this and regularly make a mess of it. I would be grateful if you could give me some ideas.*

*Keep up the good work. I'm pleased to see quite a few cheap projects and I will be making the Digital Dice, soon.
R. Mitron,
Nottingham.*



PS Please can I have a binder as I have spent all my money on your Universal Relay Driver (grovel, grovel).

I have suggested to the Ed that this is a good subject for Hobby and he is looking in to it. I'll keep reminding him.

I do enjoy the occasional odd-ball letter; it makes a change from the usual desperate pleas for help and the pathetic grovelling.

*Dear Clever Dick,
The circumjacent to which this field of enquiry is intrinsic is sacrosanct to the amplitude that is relevant to this leit-motiv. Professionals have hortated over the denouement of this milieu, but ineffectively. Strategists pontificate the derivative of this, but advocates are unauthorised to evaluate the efficacy of such measures.*

The encompassment to which supposition is symbiotic to the relative quantity is appositive to this field of enquiry. Savants have sat in conclave over the contingencies of this situation, negatively. Virtuosos dialogise the consequence of this, but coadjutors are unqualified to assess the advantages of this action.

*Yours sincerely,
I. McAlpine,
Co. Armagh,
N. Ireland.*

PS How about a medium HE T-shirt? They are much cheaper than a binder. It almost makes sense, doesn't it? Doesn't it? Well, all except the PS, then; can't understand that at all.

Finally, this month, I am happy to say that Mr. Lawrence has not suffered greatly from the mistaken advice I passed on to him.

*Dear Sir,
I wish to thank you very much for your reply to my letter in the February issue and also for your letter of 15th January. I would also like to thank Mr. Thomas for the enclosed sheet, which has been a great help to me.*

*The response and the consideration displayed by your magazine has been very much appreciated.
A. M. Lawrence,
Chessington,
Surrey.*

I would also like to thank, personally, those many readers who wrote in with advice for Mr. Lawrence. There are far too many to acknowledge individually — so thank you, all. 'Bye now.

HE

REVERB REVEALED

Paul Coster

STAND inside any large, bare room and you'll notice how sounds tend to linger on after you first hear them. A similar, though less marked, effect occurs in smaller rooms, especially if they contain plenty of hard, bare surfaces (such as a bathroom). This effect is reverberation.

A single pulse of sound, eg a handclap, will send a set of waves out across a room and, if they strike objects in the room, the direction and intensity of the wave will be changed (the intensity of a sound wave is just the amount of energy 'flux' it contains, measured in Watts per square metre). Changes in direction are caused by sound waves being reflected, as light is reflected from a mirror, and it is these reflections which are the main cause of reverberation — if there are no objects to cause reflections, there can be no reverberation!

In most rooms, the 'objects' which are the main reflecting surfaces are, of course, the walls but anything large, in relation to the wavelength of a sound, can cause reflection.

The other important factors in determining the amount of reverberation are the intensity of the reflections themselves (if most of the sound is absorbed by the walls, the reflected sound wave will be too weak to carry back to a listener), the intensity of the sound (a weak sound won't carry to the walls whereas a very loud sound might bounce around for some time) together with the size of the room and the frequency of the sound.

All the factors play a part in how long it takes a sound to fade away. This period is called the Reverberation Time (RT); it is the time it takes for the intensity of a sound to fall to one millionth of its initial value. This is rather a clumsy figure, so it is more usual to express this ratio in decibels.

For Whom the Bel Tolls

Decibels are a relative measurement, like percentages, often used to express a relationship between the very large numbers which are so often encountered in acoustics (and in electronics). A ratio is expressed in decibels (abbreviated as 'dB') by taking its logarithm and multiplying by a constant — 20 for pressure (or voltage) ratios and 10 for intensity (or power) ratios. So, an intensity level difference of one millionth is equal to

$$10 \times \log \frac{1}{1000\ 000} \\ = 10 \times -6 = -60 \text{ dB}$$

The minus sign is a natural result of the calculation and indicates that the level we are measuring is 60 dB lower (60 dB 'down', in the jargon) than the original

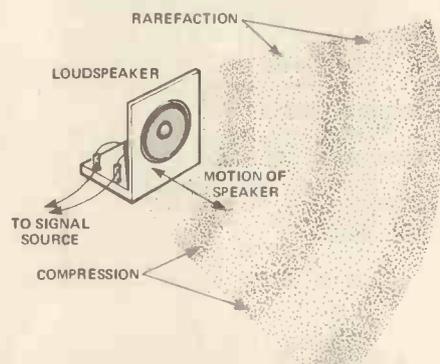


Figure 1. Sound travels through the air as alternate bands of compression (high pressure) and rarefaction (low pressure), created by the rapid motion of a vibrating source. The progression of the sound waves is a physical transference of energy.

sound — a sound one million times louder would be +60 dB because $\log 10^6 = +6$.

This raises an important point; since a sound intensity expressed in decibels is a ratio, it is meaningless in itself. It's no help being told that a sound is, say, 10 dB down, unless we know what its 10 dB down from. It's rather like asking "How far is it from London to Liverpool?" and being told, "Oh, about twice as far." Twice as far as . . . what? If, on the other hand, we're told that it's "twice as far as from London to Birmingham" then we have a base by working out the distance from London to Liverpool. The London-Birmingham distance is a *reference*.

In acoustics, it is usual to describe sound levels in terms of the ratio, in decibels, between two Sound Pressure

Levels (dB SPL). The reference level for all acoustic measurements, in dB SPL, is the Threshold of Hearing, ie the lowest sound pressure level that can, on average, be heard; that is a sound pressure of 0.00002 Pascals (Pa). This is made clear in Figure 2, which shows some examples of typical sound pressure levels, in Pa and dB SPL.


Mirror, Mirror

A single pulse of sound has a definite start and finish but, as this pulse, or 'wave set', travels around a room, it is influenced by the structure and contents so that, by the time it reaches a listener, it is no longer so sharply defined. Instead, it looks more like the shape of Figure 4.

The first thing heard is the original sound that has not encountered any objects en route; this is the 'direct sound' and is usually closely followed by a few distinct reflections from nearby surfaces. After these, the remaining sound is composed of reflections and re-reflections of ever decreasing intensity. Eventually, (a matter of seconds), the sound dies away, having been absorbed completely by the air and by absorbant surfaces.

In a room with mainly smooth, hard surfaces there will be numerous reflections followed by reflections of reflections and re-reflected reflections, and so on. This process is the building block on which reverberation depends. Absorption determines how long the reflections continue; that is, the Reverberation Time.

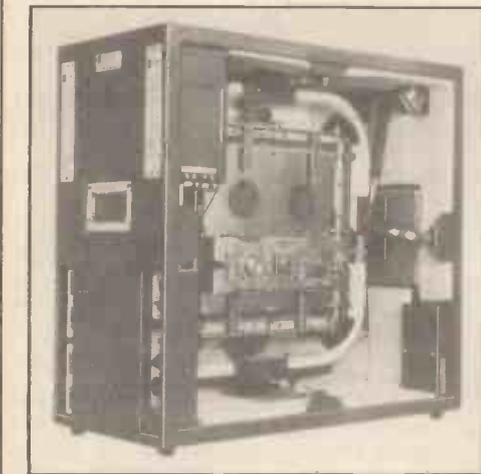If a single reflected sound seems distinct from the other reflected sounds, it is called an echo. Echoes are a repeat of the original sound, as a separate entity. The more distinct they sound, the more marked the effect.



The EMT 240 Reverb Foil (left) is probably the finest plate reverb unit made. Two tiny piezoelectric drivers induce bending waves throughout the 24 karat, 18 micron thick, gold foil plate. Reproduction of the signal is achieved by miniature pickups, also bonded directly to the foil surface. Our own Echo-Reverb unit (above) uses more modest techniques!

Another distinct effect is the emphasis of particular frequencies. These are 'resonances' and they occur when a dimension of the room equals, or is a multiple of, the wavelength of one of the frequencies of the sound. When this happens, the wavelength tends to remain long after the others have decayed. Such 'standing waves' can be extremely objectionable and unpleasant.

Walls Have Ears

Whenever a sound wave 'bumps into' an object, some of the energy in the wave is absorbed and dissipated as heat. Although the amount of heat produced is very small, the reduction in the sound intensity is significant. The amount by which a material will absorb sound, in this way, is called its Coefficient of Absorption. For example, cork tiles have a coefficient of absorption of 0.2 (at a frequency of 500 Hz and with an angle of incidence of 90°) whereas the value is ten times smaller (0.02) for concrete. In other words the tiles will absorb 20%, but concrete only 2%.

In the case of concrete, this means that nearly all (98%) the sound is either reflected or transmitted. The main factor of how well a material transmits sound is its mass, it's weight. Concrete is quite heavy and, therefore, a good sound insulator (doesn't transmit very much). So, for frequencies around 500 Hz, at least, concrete must be a good reflector because it's a bad absorber/transmitter of sound!

The reason for specifying a particular frequency (and angle of incidence) is that absorption coefficients are frequency dependent. The change is often quite large; cork tiles, for instance, have a coef-

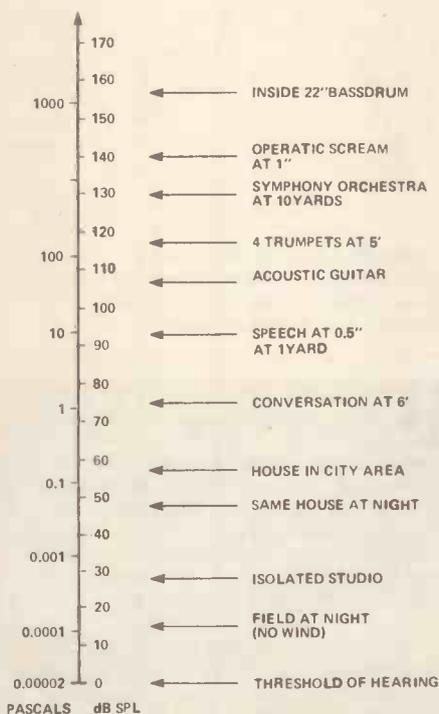


Figure 2. The Sound Pressure Levels, in Pascals and dB SPL, of fairly typical sounds.

ficient ranging from less than 0.1 up to 0.6, across the audio frequency spectrum (20 Hz - 20 kHz). If you are still unsure of the difference between an insulator and an absorber of sound, just think of an open window; its a good absorber of sound (it does not reflect), but is useless at preventing sound from reaching the outside!

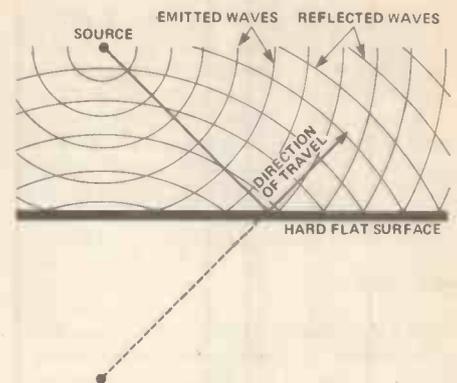


Figure 3. Sound reflections from a flat surface are analogous to the reflection of light from a mirror.

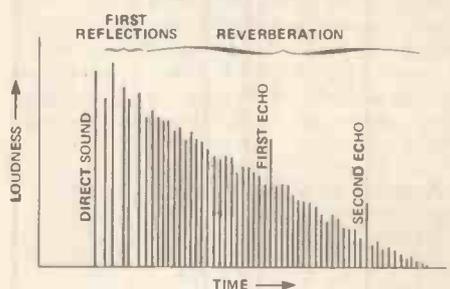


Figure 4. The profile of reflections of a single pulse of sound.

Growing Strong

Since reverberation is the result of the combined effects of reflection and absorption, we would expect that sound emitted at a constant intensity would not get louder and louder but, rather, tail off due to the amount being absorbed. This is indeed what happens, in a very short time, as shown in Figure 5. The growth in sound intensity is quite rapid at first, but as more and more is absorbed, the rate of growth decreases until a steady state is reached. At this point the amount of sound energy being absorbed is equal to the amount being produced - the sound has reached saturation level. If the source is switched off, the sound intensity falls off steeply, then more gradually, until it eventually fades away. The final diagram in Figure 5 is a graphical representation of this process and fairly typical of the growth/decay characteristics encountered in most rooms or halls.

Although the basic shape of the 'sound energy' curve is fairly constant, the time taken to reach steady state and then decay depends on the particular room. In free space, (open air), a series of sharp sounds (pulses) will have almost vertical rise-and-fall slopes (Figure 6a) corresponding to when the source is turned on and off. In a room with a short RT, though, the familiar curve returns (Figure 6b), showing a small overlap at each end. A longer RT produces more of an overlap and this can be disastrous in some cases, as the sounds of speech, for example, will tend to merge before they have decayed (Figure 6c). Consequently, it's not difficult to see that reverberation time is an important consideration when using

Reverb Revealed

a hall for a particular purpose. A lecture theatre, for instance, requires a short RT (less than a second) for speech to be heard clearly, but that same value would produce a very 'dead' sound in a large concert hall — it would also be difficult to achieve without using an enormous amount of absorbent material all around the 'sound stage'. Organ music presents quite a different problem, requiring a reverb time between three and five seconds. So, to fully realise a rich organ sound, the hall must be large and contain plenty of reflecting surfaces — something like a church or cathedral would do nicely!

As a mark of importance of reverberation, some concert halls have the seats upholstered with material that has a similar absorption coefficient to clothing, in an attempt to ensure that the quality of the sound is not dependent on the number of people in the audience! Of course, most rock music venues pay little attention to such details, so the acoustics during a 'sound check' are not reproduced when the crowds arrive (in some cases, this lack of sonic continuity makes little difference!).

Reverb On Demand

Room acoustics are extremely hard to alter. Equalisation techniques can be used to flatten-out the peaks (due to resonances) and dips (due to 'dead spots' at particular frequencies), within limits, but there's nothing that can be done *electronically* to reduce reverberation. On the other hand, if you're stuck with a 'dead' room — or just like 'playing in the bathroom' — then it is possible to add artificial reverberation. There are commercial units that can produce quite realistic effects, but it should be realised that electronic reverb is, at best, only a substitute for the real thing. In practice, its impossible to duplicate the hundreds and thousands of reflections and absorptions that are produced in a particular room or hall. For this reason, it's better to view 'add-on' reverberation as an effect in its own right — it is, after all, the final sound that counts.

All electronic systems used for adding reverberation depend on the same basic principle; the signal is delayed for a short time and part of it is fed back to the input. By carefully controlling the delay and amount of feedback, quite effective reverb can be produced. The best units, using multiple delay paths and complex mixing circuitry create something approaching genuine reverb. In reality, all that's being done is to recirculate a series of short echoes' — a process labelled 'regeneration' or, sometimes, 'recirculation'. If this is taken to extreme levels, oscillation results; this is hardly surprising when you consider that signals are being added, one on top of the other. However, when proper attention is paid to setting the levels, the sound can be quite impressive.

The most effective device for creating reverb is the reverberation plate. It is an electro-mechanical device which consists of a large steel plate mounted in a suspending framework, with transmit and pick-up transducers at either end. Sound waves travel through the plate, more slowly than they do through the air,

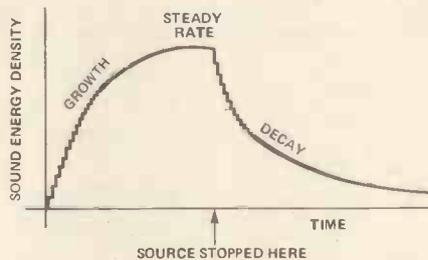
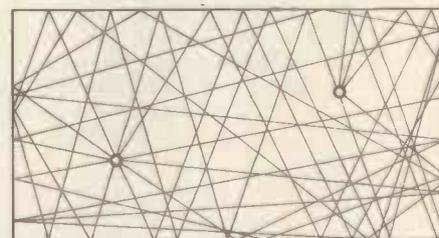
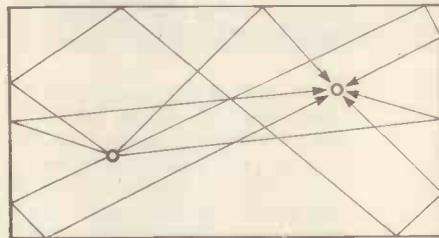
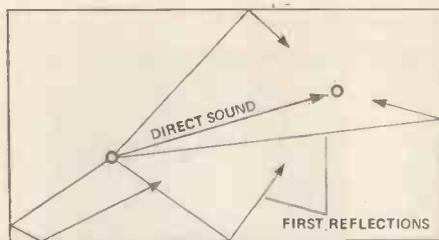


Figure 5. The energy density growth/decay characteristic of a sound pulse (after Olson, H.F., "Music, Physics and Engineering").

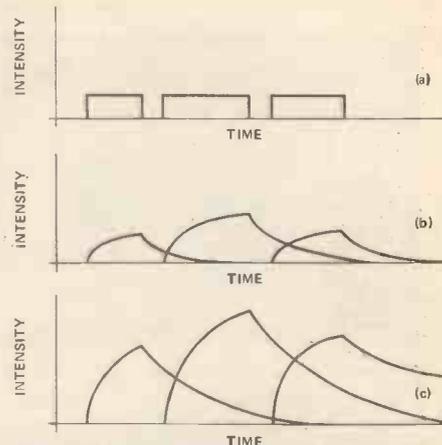


Figure 6. Growth/decay characteristics of a series of sound pulses produced by different reverb times; (a) free field (short); (b) medium; (c) long (after Olson).

and are reflected by the *edges* of the plate, before being picked-up. This results in a distinctive and high quality effect; the major drawbacks are a lack of mobility (the plates are heavy) and prohibitive costs (mortgages are available!).

A cheaper, more popular, but less effective alternative is the springline. This takes the form of one or more springs, suspended at each end and fitted with transmit and pick-up transducers. A small power amplifier is used to send signals down the springline which then appear at the other end with the characteristic 'twangy' sound. Indeed, the springline is often used specifically because of its unique 'sound'. The disadvantage of this arrangement is that the slightest knock causes a loud 'boing' sound.

Electronic reverb units are basically variable delay lines. There are two types; analogue (like the HE Echo-Reverb) and digital. Analogue delay lines are based on specialised ICs known as Charge Coupled Devices (CCDs), which 'sample' the input signal and 'clock' each sample through to



MXR's Digital Delay unit provides a variety of effects, ranging from discrete echoes, doubling and hard reverb through to flanging, frequency modulation (vibrato etc) and infinite repeats. The Flanger/Doubler (top) uses analogue methods to produce a more limited range of effects.

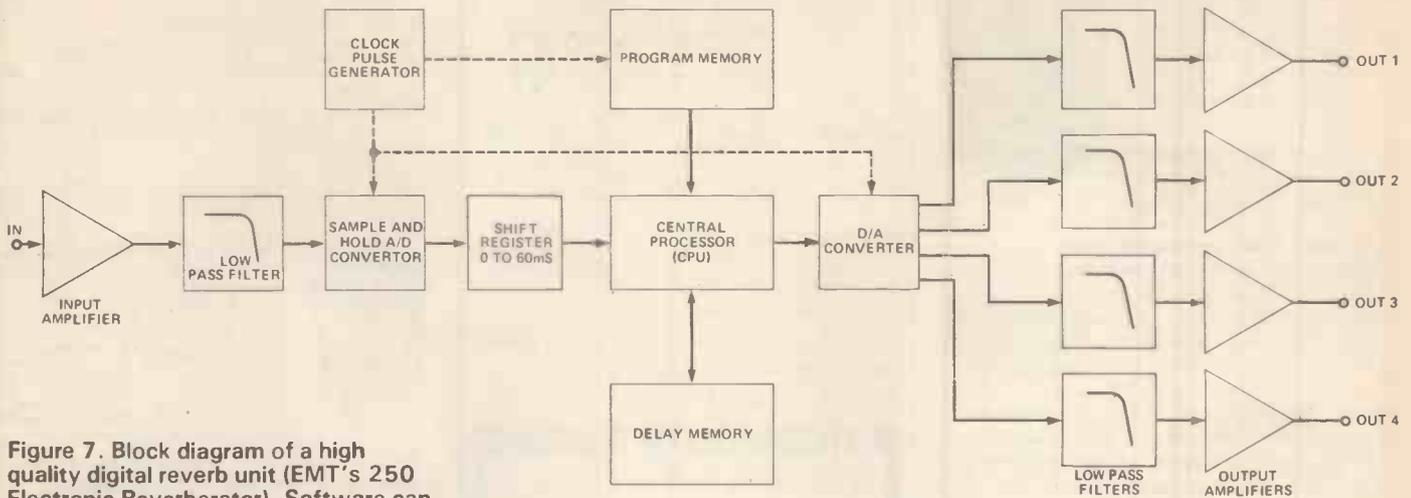


Figure 7. Block diagram of a high quality digital reverb unit (EMT's 250 Electronic Reverberator). Software can be written to generate almost any kind of delay effect.

output. (The operation of CCDs is described more fully in the 'How it Works' section of our reverb project, in last month's issue).

Digital reverberation units are much more sophisticated and versatile (Figure 7). If the software is clever enough, these units can create just about any type of sound! They do this by converting samples of analogue signal into a digital word using an ADC (Analogue to Digital Converter) which can then be stored in a Random Access Memory and manipulated in various ways, limited only by the type of program used. After processing, the signals are converted back into their original analogue waveforms by an ADC (Analogue to Digital Converter). Digital reverb provides opportunities for creating reverberation effects that exist only in the mind of the programmer! Obviously, such capabilities don't come cheaply.

One of the original techniques for adding reverberation (and still used today, for quick, easy echo) was to use a tape


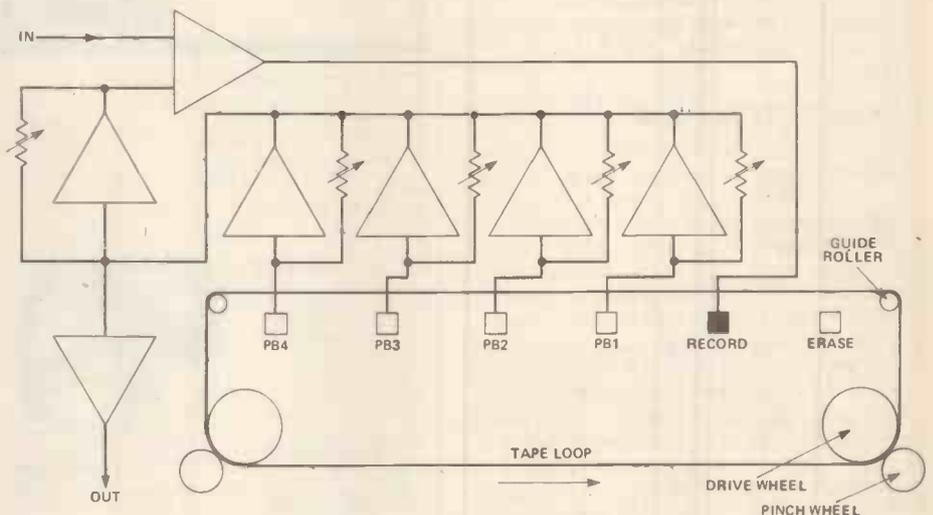


Figure 8. Block diagram of a tape-loop reverb system, using multiple playback heads to produce closely spaced discrete echoes.

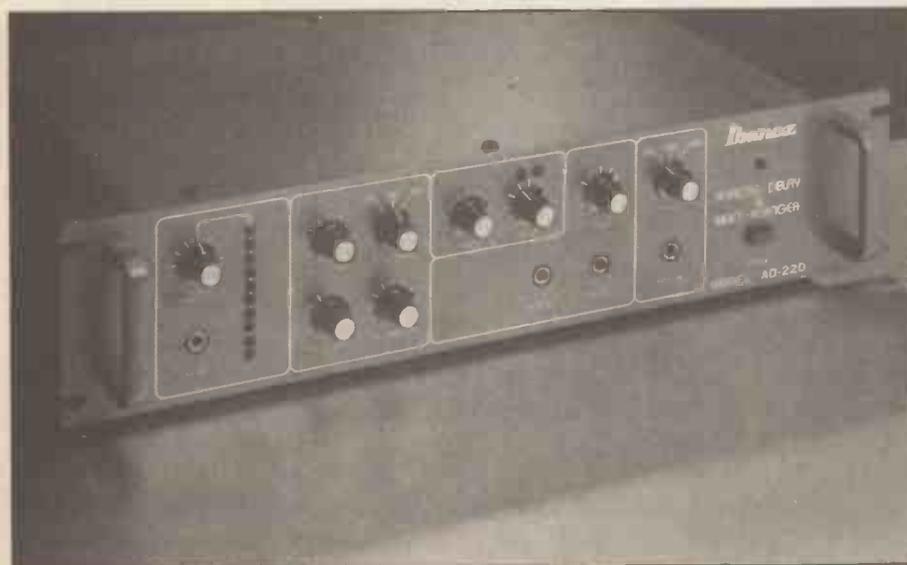

The Ibanez Analog Delay/Multi-Flanger is a budget priced unit suitable for producing a number of interesting delay effects, including echo, reverb and flanging.

loop strung out between two tape recorders. Special tape machines, with multiple playback heads (Figure 8) were also produced and these were capable of some quite good sounds. The heads were arranged with different spaces between them, so that a set of delays got progressively longer; each head had its own playback level circuitry, feeding a mixer, allowing the response to be accurately controlled.

Listen to the Music

With all the electronic equipment available and working knowledge of reverberation effects, the creative musician should be able to use both the gear and his knowledge to create some really outstanding sounds. Unfortunately, it is virtually impossible to do much about strong resonances in a room, although equalisation can help (this will be the subject of the next Project: Music feature). The most important thing to remember is that, if the room is at all 'live' (you can get a good idea of the sound of the room by clapping hands once, sharply, and listening to the reflections, if any), playing *loud* will only make the sound worse!

SUPER HI-FI SPEAKER CABINETS

Made for an expensive Hi-Fi outfit — will suit any decor. Resonance free. Cut-outs for 6 1/2" woofer and 2 1/4" tweeter. The front material is Dacron. The completed unit is most pleasing. Supplied in pairs price £6.90 per pair (this is probably less than the original cost of one cabinet) carriage £3.00 the pair.



GOODMANS SPEAKERS

6 1/2" x 8 ohm 25 watt £4.50. 2 1/4" x 8 ohm tweeter. £2.50. No extra for postage if ordered with cabinets. Xover £1.50.

UNIVAC KEYBOARD BARGAIN

50 keys, together with 5 miniature toggle switches all mounted on a p.c.b. together with 12 i.c.'s, many transistors and other parts. £13.50 + £2.00 post.

This is far less than the value of the switches alone. Diagram of this keyboard is available separately for £1.



SOLENOID WITH PLUNGER

Mains operated £1.99
10 — 12 volts DC operated £1.50.

POPULAR KITS

3 - 30v VARIABLE VOLTAGE POWER SUPPLY UNIT

With 1 amp DC output, for use on the bench, students, inventors, service engineers, etc. Automatic short circuit and overload protection. In case with a volt meter on the front panel. Complete kit £13.80

IONISER KIT

Refresh your home, office, shop, work room, etc. with a negative ION generator. Makes you feel better and work harder — complete mains operated kit, case included £11.95 plus £2.00 post.

MORSE TRAINER

Complete kit £2.99.

DRILL SPEED CONTROLLER

Complete kit £3.95.

MAINS POWER SUPPLY

Gives any voltage from 3v to 16v at up to 300mA. Complete kit less case £1.95. Case 90p.

OUR CAR STARTER AND CHARGER KIT has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage whichever suits you best. Price £12.50 + £3.00 post.

CHANCE OF A LIFETIME

We have to clear a big store. 100 tons of stock must go. 10 kilo parcel of unused parts. Minimum 1,000 items includes panel meters, timers, thermal trips, relays, switches, motors, drills, taps and dies, tools, thermostats, coils, variable condensers, variable resistors, etc. etc. Individually these must cost in excess of £100. **YOURS FOR ONLY £11.50 plus £3.00 post.**

MILLIONS OF HOMES WILL BE BURGLAD THIS SUMMER — SAY THE EXPERTS

Don't let yours be one of them. Install our burglar alarm. Install our burglar alarm. Complete kit includes 6" external alarm bell, mains power unit control box with key switch 10 window/door switches 100 yards of wire. With instructions £29.50.

TINIEST MICROPHONE

Not much bigger than a pea, 600 ohm condenser type. Ideal for bugging and similar applications. 50p each or 10 for £4.50.

LEVEL METER

Size approximately 3/4" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.



THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pad which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

3 CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it



is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by 1/4" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form of £25.00 assembled and tested.

STANDARD RELAYS

3 changeover 10 amp contacts, single screw fixing, mains operated. £1.25. 12 volt operated £1.50. 6 volt model 99p. Other coil voltages — please enquire.

ULTRA SMALL 12v RELAYS

Single pole gold plated contacts. Tubular construction, 17mm long 10mm dia. Ideal for models. PCB or freemounting. £2.30 ea.

MINIATURE PLUG IN RELAYS

12v operated, 3 changeover. £2.45, base 450. 12v operated, 2 changeover. £1.87, base 350.

THIS MONTH'S SNIP

0 - 100 MICRO AMP PANEL METER

Japanese made, flush mounting, size approximately 45mm x 50mm x 30mm deep. PRICE £2.95.



ROTARY WAFER SWITCHES

5 amp silver plated contacts. 1/4" shaft, 1" dia. wafer.

Single wafer types, 29p each, as follows:

1 pole 12 way	2 pole 6 way	3 pole 4 way
4 pole 3 way	6 pole 2 way	4 pole 3 way
Two wafer type, 59p each, as follows:		
2 pole 12 way	4 pole 5 way	4 pole 6 way
6 pole 2 way	8 pole 3 way	12 pole 2 way
3 wafer types. 99p each,		
3 pole 12 way	6 pole 5 way	6 pole 6 way
9 pole 4 way	12p 3 way	18p 2 way

EXTRACTOR FAN


Mains operated — ex-cupboard

5" Woods extractor £5.75. Post £1.25.

5" Plannair extractor £6.50. Post £1.25

4" x 4" Muffin 115v. £4.50. Post 75p.

4" x 4" Muffin 230v. £5.75. Post 75p.

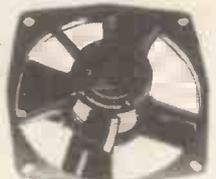

8 POWERFUL BATTERY MOTORS

For models, macanos, drills, remote control planes, boats, etc. £2.95.

TAPE PUNCH & READER

For controlling machine tools, etc, motorised 8 bit punch with matching tape reader. Ex-computers, believed in good working order, any not so would be exchanged. £17.50 pair. Post £4.00.



MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument, Jewelled bearings - 2000 o.p.v. mirrored scale. 11 instant range measures: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0 — 100 mA.



Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and instruction book showing how to measure capacity and inductance as well. Unbelievable value at only £6.75 + 60p post and insurance.

FREE Amps range kit to enable you to read DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but if you already own a Mini-Tester and would like one, send £2.50.

12V FLUORESCENT LIGHTING

For camping — car repairing — emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer an inverter for 21" 13 watt miniature fluorescent tube. £3.45. (tube not supplied).



FREE OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox — all electronic parts and circuit. £2.30. (not licenceable in the U.K.)

RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit. (not licenceable in the U.K.).

FM RECEIVER

Made up and working, complete with scale and pointer needs only headphones, ideal for use with our surveillance transmitter or radio mike. £5.85. or kit of parts £3.95.



VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case, but we can supply a plastic base £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24 hr. time switch but with the added advantage of up to 12 on/off's per 24 hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30.

STEREO HEADPHONES

Very good quality, 8 ohm impedance, padded, terminating with standard 1/4" jack-plug £2.99 post 60p.



TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs. £2.50.

ZX81 OWNERS

Make yourself a full size keyboard! Key switches complete with plain caps. 6 for £1.15.



RESISTORS

Carbon film, 1/4 or 1/3 watt, standard leads, not pre-formed, all 5% values: 1p each 100's, 2p each 10, 5p each less than 10 per value. OR — INVENTOR'S PACK, containing 10 of each of 60 different values from 1 ohm to 10 megohm, packed separately, £5.75.

DELAY SWITCH

Mains operated — delay can be accurately set with pointers knob for periods of up to 2 1/2 hrs. 2 contacts suitable to switch 10 amps — second contact opens a few minutes after 1st contact. £1.95.

MOTORS FOR ROBOTICS

If its a toy robot you are making then one of our eight battery motors (see centre column) may do. If its a bigger one, however, then see below. If still not big enough then enquire — we have larger motors but these are usually mains driven.

12v MOTOR BY SMITHS

Made for use in cars, these are series wound and they become more powerful as load increases. Size 3 1/2" long by 3" dia. These have a good length of 1/4" spindle — price £3.45. Ditto, but double ended £4.25.



EXTRA POWERFUL 12v MOTOR

Made to work battery lawnmower, this probably develops up to 1/2 h.p., so it could be used to power a go-kart or to drive a compressor, etc. etc. £5.90 + £1.50 post. (This is easily reversible with our reversible switch — Price £1.15).

SPIT MOTORS

These are powerful mains operated induction motors with gear box attached. The final shaft is a 1/2" rod with square hole, so you have alternative coupling methods — final speed is approx. 5 revs/min, price £5.50. — Similar motors with final speeds of 80, 100, 160 & 200r.p.m. same price.



REVERSIBLE MOTOR WITH CONTROL GEAR

Made by the famous Framco Company this is a very robust motor, size approximately 7 1/2" long, 3 1/4" dia. 3/8" shaft. Tremendously powerful motor, almost impossible to stop. Ideal for operating stage curtains, sliding doors, ventilators etc., even garage doors if adequately counter-balanced. We offer the motor complete with control gear as follows:

- 1 Framco motor with gear box
 - 1 manual reversing and on/off switch
 - 1 push to start switch
 - 1 x 100w auto transformer
 - 2 limit stop switches
 - 1 circuit diag. of connections.
- £19.50 plus postage £2.50.

J. BULL (Electrical) Ltd.

(Dept. HE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. Established 30 YEARS

MAIL ORDER TERMS: Cash, P.O. or cheque with order. Orders under £10, add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclaycard orders phone Haywards Heath (0444) 454563. Bulk Orders: Write for quote. Delivery by return.

INTO ELECTRONIC COMPONENTS

Nearing the end of the Series, we consider Transducers — electrical Input/Output devices.

A TRANSDUCER is simply a converter and, though neither of the signals (input or output) need be electrical, the transducers that are of most interest to us are the ones which have, as either input or output, an electrical signal. These signals can be AC or DC or a mixture of both, according to the type and design of transducer.

Though transducers can be as different as a light-bulb and a microphone, they have one factor in common — none are ever 100% efficient. The efficiency of a transducer can be measured in terms of the energy of the signals into it and out of it. A 100% efficient transducer would produce an output whose energy was exactly the same as that of the input signal, over the same time. Efficiencies ranging from 0.1% to 80% are more usual, with the lower values, alas, predominating. The efficiency is officially defined as:

$$\frac{\text{Energy out}}{\text{Energy in}}$$

In the same time. There are so many transducers used with electronic equipment that we cannot hope to cover more than a few, here, but we can at least look at those which are of greatest interest.

One important point to note is that an electrical input or output will have a measurable resistance. The input resistance will be stated as a parallel resistance, the output resistance as a series resistance (Figure 11.1) and these resistances will form potential-divider circuits with any other resistances in the external circuits, cutting down the amount of electrical signal which enters or leaves the transducers. The principle

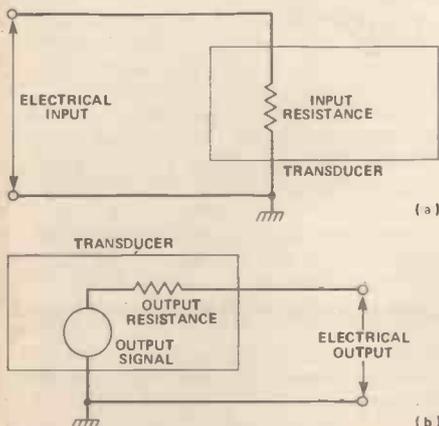


Figure 11.1. Input and output resistances of transducers.

should already be familiar to you after the discussion of transistors, a few months ago. The values of input and output resistances vary very greatly from one transducer to another, so that circuits which are used with transducers have to be tailored to the characteristics of the particular device — you cannot necessarily use an amplifier which has been developed for a microphone on a strain-gauge, for example.

Over to You, Mike

A microphone is a sound-wave to electrical signal transducer which converts a reasonable percentage (around 10%, for some examples) of the sound energy reaching it into electrical energy. Since what we call sound is composed of waves of pressure in the air, the electrical output of a microphone is also in the form of a wave and, if the microphone is to be of any use, the waveshape should not be changed. That means a graph of air-pressure plotted against time (the waveshape of the sound) should look the same as a graph of electrical voltage, from the microphone, plotted against time (the electrical waveshape).

There are a lot of different microphone types and we don't have space to go into details of them all, but one important point is that they all belong to one of two groups — velocity operated or pressure operated. A velocity-operated microphone uses the movement of the air to obtain its signals, whereas the pressure-operated type uses (you guessed!) the pressure. The most important difference between them is that the pressure-operated microphones are omnidirectional — they will pick up sounds from any direction, no matter which way the microphone is facing. By contrast, velocity-operated microphones are unidirectional — they have to be pointed at the source of sound and they pick up much less sound from other directions. The way in which a microphone responds to sounds from different directions is shown in a polar diagram for that microphone (Figure 11.2) An omnidirectional microphone should give a round polar diagram, a directional microphone a sharply pointed one.

In the early days of tape-recording, crystal microphones were used but nowadays most microphones are of a type which make use of electromagnetic induction. The principle is that the soundwaves move a stretched diaphragm, and the movement of the diaphragm causes a magnet to move in

and out of a coil (dynamic microphone) or a coil to move in and out of a magnet (moving-coil microphone). A variation on this theme is the ribbon microphone, in which a thin metal strip is vibrated by the air and, because the metal ribbon is located between the poles of a magnet, it generates a signal. Of these types, the dynamic type produces the greatest amount of signal for a given amount of sound, and also has the highest resistance. The ribbon types produce least signal and also have very low resistance; the particular virtue of the ribbon type is that it is particularly easy to make in velocity-operated form.

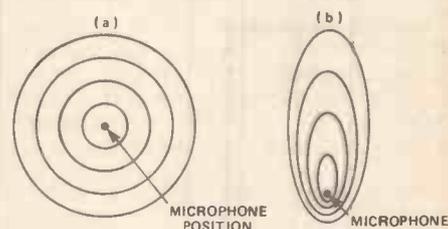


Figure 11.2. Polar diagrams for microphones; (a) omnidirectional; (b) unidirectional.

The Other 'Arf

The other end of the amplification system needs a transducer for electrical signals to sound — the loudspeaker. One type of loudspeaker has dominated for many years and that one is the moving-coil type. In a moving-coil speaker (Figure 11.3), a cone, which is usually made from stiff paper with a corrugated support to act as a suspension, is held in a frame and a coil of wire is wound on to a cylindrical former at the narrow end of the cone. This former fits in the poles of a cylindrical magnet, magnetised so that one pole is at the centre and the other pole is all round the outside. This

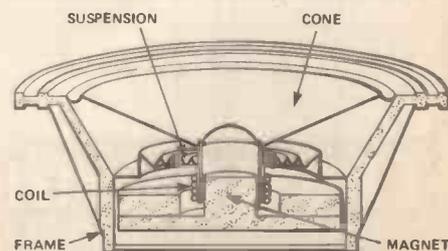


Figure 11.3. The moving-coil loudspeaker.

arrangement produces a strong magnetic field, cutting directly across the turns of wire on the former so that, when a current is passed through the coil, a force is generated which will move the coil, taking the core along with it. The direction of the force, and so the movement, is reversed when the direction of the current is reversed, so that an alternating current will produce alternating movement, to and fro, which is what we need to create a sound wave.

Moving-coil loudspeakers (and the principle is used for many types of ear-phones as well) have low resistance values, mostly in the range of 3R to 16R, which is why we have so many problems with power amplifiers. Another problem is that loudspeakers are very inefficient — only a tiny fraction of the electrical energy put into them results in useful sound energy output. The snag is that the size of the loudspeaker is tiny compared with the size of the sound source it is trying to re-create. We try to get over this by mounting the loudspeakers in cabinets but, unless we use truly gigantic cabinets, the efficiency is only slightly improved. The most efficient type of cabinet (or enclosure, to use a more technical word) for loudspeakers is the exponential horn (Figure 11.4) which, if you're prepared to tolerate a length of nine feet or more and a mouth which can be the size of a doorway, can give efficiency figures of 10% or more. At the other end of the scale, small 'bookshelf' speakers of good quality may have efficiency figures of less than 0.5%.

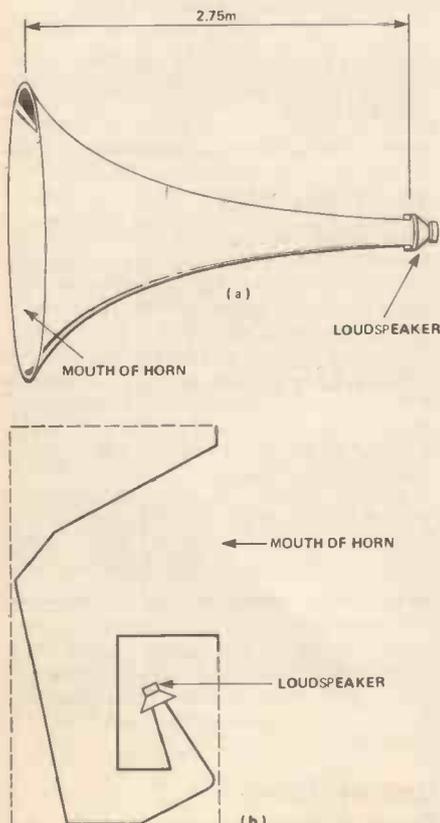


Figure 11.4. Cross-section of a small exponential horn; folded horns are more usual because of the enormous length of a straight horn.

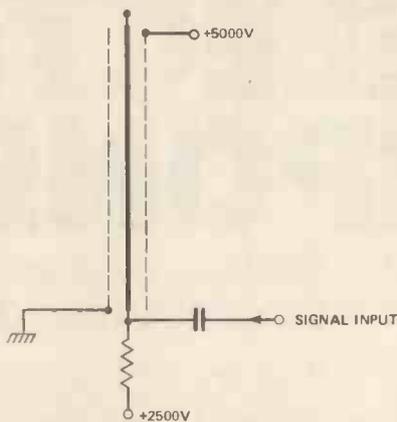


Figure 11.5. The principle of the electrostatic loudspeaker — as the voltage on the diaphragm changes, the electrostatic forces move the diaphragm in and out.

Though the moving-coil principle dominates loudspeaker design, it is by no means ideal. Very fine results can be achieved with electrostatic speakers, in which a large sheet of metal-coated plastic is moved between wire meshes (Figure 11.5) by electrostatic forces. A high 'polarising voltage' is needed, as a bias for the diaphragm, and the resistance of the speaker is very high — almost infinite. The speaker manufacturers Quad are the only company who have used the electrostatic principle seriously and their speakers are very highly regarded by those who can afford them. The use of electrostatics has been more widespread in headphone design, where size is less of a problem and some excellent results have been achieved by Sennheiser, the pioneer of electrostatic headphones.

A few types of loudspeakers are produced using other effects. For hi-fi, it is impossible to produce a moving-coil loudspeaker which deals adequately with both very high notes and very low notes, so that moving-coil speakers are used for the low and mid-range notes and small units, called 'tweeters', are used, sometimes in large numbers, for the highest notes. Both ribbon and ceramic crystal tweeters are found, the ribbon type being of almost the same construction as a ribbon microphone. Ceramic tweeters work on the principle that a thin plate of certain materials, called piezoelectric crystals, will vibrate when an alternating voltage is applied to metal contacts on each side of the sheet. These ceramic tweeters have a very high resistance, but the ribbon types have a very low resistance.

Strike a Light

Our first lot of transducers dealt with conversions between sound waves and electrical waves. The next lot is different because, although light is also a wave, it is an electromagnetic wave like radio waves, whose frequency is very much higher than any we can deal with by electronic methods. Transducers for light to electrical signals, therefore, do not give out an electrical wave when light strikes

them unless the light itself is modulated, with its amplitude varying at a rate that we can cope with. Transducers of this type are called photocells and several varieties, classed as photoconductive, photovoltaic, photoemissive, photodiode or phototransistor exist. Let's take them one by one.

A photoconductive cell is made from a material whose resistance changes as the amount of light falling on it changes. Obviously, a cell of this type does not have a steady value of output resistance and we must use it in a circuit similar to that which we use for a transistor, with a constant value load resistor connected in series across a steady supply voltage (Figure 11.6) The photoconductive cell does not generate any signal; it simply controls the current from an external power supply, so that whenever a photoconductive cell is used there must also be a battery, or other power source. The most commonly used photoconductive material is cadmium sulphide and Figure 11.7 shows the arrangement of a typical cell, along with its measurable characteristics. These cells are reasonably sensitive, but they suffer from a time-lag — once they are conducting, they will stay conducting for a fraction of a second after the light is cut off. Such cells are, therefore, useless if the light is modulated with a signal whose frequency is more than a few Hertz.

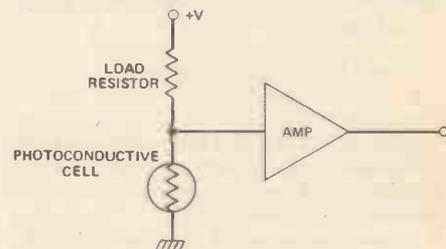


Figure 11.6. Connecting a photoconductive cell to a circuit.

Photovoltaic cells have a very long history. The first photovoltaic material to be discovered was the element selenium, a close relative, chemically, of sulphur; its photovoltaic effects were noted more than a century ago. As the name suggests, you don't get a change of resistance across a selenium element when you shine light on to it, you get a voltage. This happens only when the selenium is in contact with another material and it is, in fact, a primitive type of semiconductor junction. Like cadmium sulphide cells, selenium photovoltaic cells have a time lag which makes them unsuitable for anything but low-frequency operation. This was the problem which hindered the advance of television in the 1870s, when Nipkow demonstrated the system which was later to be improved by Baird.

Nowadays, we have found ways of making photovoltaic cells using silicon, and these are a great improvement, both in sensitivity and in response time, over the old selenium cells. They can, for example, be combined in one package with LEDs as an opto-coupler, so that signals can be transferred between points which

TYPICAL CHARACTERISTICS FOR THE ORP12

MAX. DISSIPATION	200 mV
MAX. VOLTAGE	100 V
DAYLIGHT RESISTANCE (APPROX)	2k
RESISTANCE RANGE	75R TO 10M
RESISTANCE RISE TIME (APPROX)	75 mS
RESISTANCE FALL TIME (APPROX)	350 mS

Figure 11.7a. Characteristics of an ORP12 photoconductive cell.



Figure 11.7b. The physical arrangement of a typical photoconductive cell.

are at very different voltages. The advantage of the photocoupler, as compared to capacitors or transformers, is that it can transfer DC signals, not just a limited range of AC frequencies.

Photoemitting cells also have a surprisingly long history, dating back to research in the latter part of the 19th century. A photoemissive cell uses one of the chemically-active metals, such as sodium, potassium, rubidium or, most commonly, caesium. All of these are extraordinarily soft and light metals (sodium will float on water, for instance) which are violently chemically active (but it dissolves, almost explosively).

Lenard discovered that when a block of sodium was contained in a vacuum and the surface scraped clean (using a knife operated by a magnet), the clean sodium surface would emit electrons when it was struck by light. These electrons can then be attracted to an 'anode', a metal surface a few hundred volts positive, relative to the sodium surface, and this flow of electrons constitutes a current. Like the photoconductive cell, the photoemissive cell is used with a power supply and a load resistor; a cross-section of a cell, and a circuit, is shown in Figure 11.8. The response time of a photoemissive cell is very much faster than that of a photoconductive type, however, so that the photoemissive cell was, at one time, the only type of cell that could be used for the conversion of flickering light, from the soundtrack of movie films, into electrical signals. The television camera tubes which were in use until comparatively recently were all photoemissive, although modern cameras make use of new, fast-response photoconductors, such as lead oxide.

Photodiodes and phototransistors are the most recent types of photocell to be

discovered. When a diode junction is created, the current which can flow when the diode is biased in the reverse direction is controlled by the depletion region, because this region is the main obstacle to the movement of carriers. Anything which alters the number of carriers in the depletion region will greatly affect the conductivity of the diode and so will allow the current to increase for as long as the light is affecting the depletion region.

This effect is not normally noticeable with diodes, because the reverse currents are very small and we seldom use them in circuits which are sensitive to changes in reverse current. For diodes which must have very low values of reverse current, however, it is essential to exclude light from the junction.

The phototransistor is a logical development of the photodiode. If light is allowed to strike the base layer of a transistor which is biased off, the extra electrons and holes which are generated by the light will cause a base current (assuming there is a voltage applied to the collector). This makes the phototransistor a much more sensitive device than the photodiode, though at the ex-

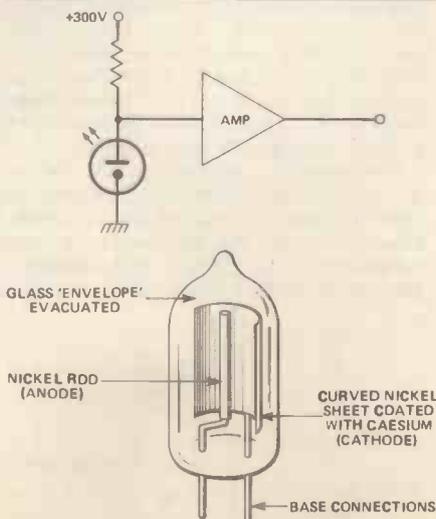


Figure 11.8. The photoemitting cell and how it is used in a circuit.

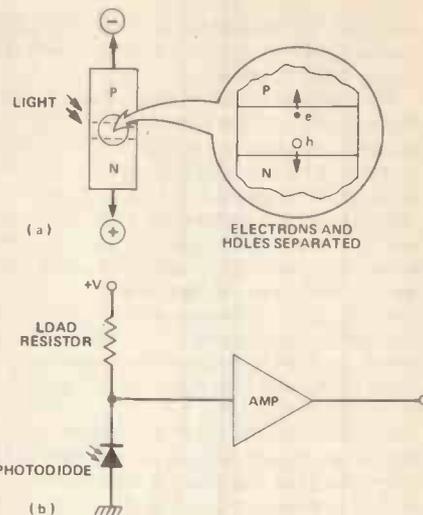


Figure 11.9. How light can cause the reverse current of a diode to increase (a), and the circuit (b) which makes use of this.

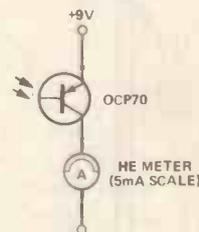


Figure 11.10. Testing a phototransistor with the HE meter.

pense of a slower response.

Early types of germanium transistor, such as the classic OC72s, used glass cases which had to be coated with black paint to prevent light from affecting the bias currents. If the paint is scraped away, an OC72 can be used as a phototransistor, equivalent to the OCP70. The difference is that the OC72s can usually be picked up as scrap, but people still want money for OCP70s.

If you can get hold of one of these old-timers, scrape off the black paint, and set up the circuit of Figure 11.10. Remember that the OC72 was a PNP transistor, which is why the collector is connected to the negative terminal. The HE meter will show a considerable increase in current when a light is shone on to the transistor, demonstrating the photoelectric effect.

All of these transducers can change light signals into electrical signals and so there just have to be transducers which operate the other way round. An ordinary light bulb is, of course, an electrical-signal-to-light transducer, but it suffers from an unacceptably long time-lag, so that it is useful only for steady light signals. The LED (described in Part 6) is much more useful in this respect.

Heated Topic

Temperature is another quantity for which we have transducers. All conductors operate as electrical-to-heat transducers; because of their resistance, electrical energy is converted to heat energy,

causing the temperature of the material to rise. Normally, this is a conversion we do our best to avoid.

The opposite conversion uses temperature levels, rather than heat. A thermocouple consists of a pair of different metals, arranged in two junctions as indicated in Figure 11.11. These are not junctions in the transistor or diode sense, but simply wires of different types soldered together. When the junctions are at different temperatures, a small voltage will be measurable at the ends of the wire. This is only a few millivolts, at most, so that it is not easily measurable but it is enough to pass current through a sensitive meter and we can use the HE meter, along with lengths of iron and copper wire, to demonstrate the action of a thermocouple. With one junction in ice and the other in air, the thermocouple will pass a noticeable current when the HE meter is switched to a low-current range (Figure 11.12).

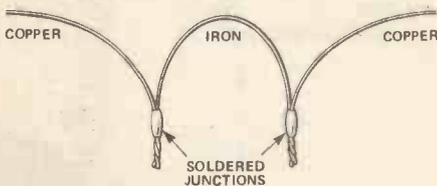


Figure 11.11. A thermocouple arrangement, using copper and iron wires.

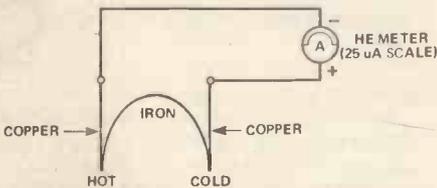


Figure 11.12. Demonstrating thermocouple action, using the HE meter on its most sensitive current range.

The trouble with thermocouples is that they can be operated reliably only over a limited range of temperatures. At some high temperature (the inversion temperature), the voltage output of any thermocouple reaches a maximum and the voltage then reduces as the temperature is taken over this value (Figure 11.13). Despite this drawback, thermocouples are widely used for temperature measurements in industry. Their advantages are small size, quick response to changes of temperature, and the ability to measure high temperatures such as are found for furnaces, for example.

A device that is more familiar to users of electronic circuits is the thermistor. It is a form of resistor, which is made from metal oxides rather than from carbon. Depending on the types of materials that are used, thermistors can be PTC or NTC. The TC part of the name (no, it's not Top Cat) means Temperature Coefficient and the P and the N mean positive and negative, respectively (Figure 11.14). A positive temperature coefficient thermistor has a resistance value which increases as the tempera-

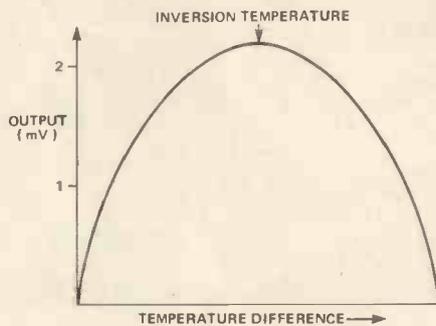


Figure 11.13. The graph of thermocouple output plotted against temperature has a maximum value, so that very high temperatures will give the same readings as low temperatures.

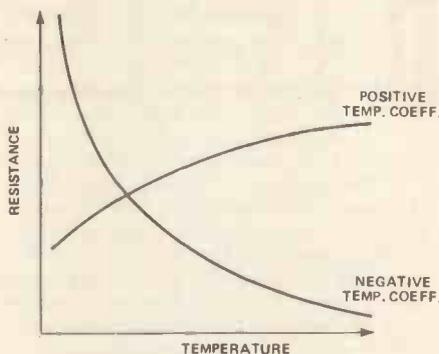


Figure 11.14. Graphs of resistance plotted against temperature for two typical thermistors.

ture increases; a negative temperature coefficient thermistor has a resistance value which decreases as the temperature increases. The NTC types are more common, for most electronics applications.

Since it's the resistance of the thermistor which changes, they must be used with a voltage supply and a load resistor. Though thermistors are excellent for detecting temperature levels in thermostat applications, controlling the central heating for example, they do not make ideal thermometers, because the change in resistance per unit change of temperature is not a constant. (Our Digital Thermometer, last month, used, instead, a current-source whose output current varied with temperature).

Thermistors are made in various shapes and sizes, with resistance values ranging from a few ohms to several megohms (at the conventional room temperature of 20°C), and ranging in size from pinhead dimensions to large

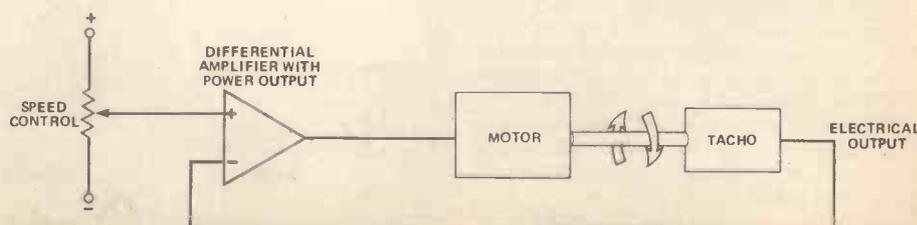


Figure 11.16. Using a tachometer in a motor speed control circuit.

blocks. The pinhead types are used for temperature measurements on small objects and also for stabilising the amplitude of oscillations in R-C oscillator circuits (for example, the Audio Signs Generator project in the May issue). This depends on 'self-heating'; the temperature of the thermistor depends on the amount of current which is flowing through it, rather than the temperature of the air around it.

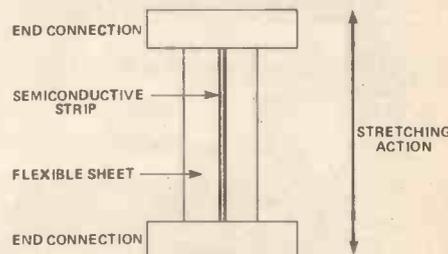



Figure 11.15. The semiconductor strain gauge. The resistance of the material increases as it is stretched.

Some of the Others.


We have only scratched the surface of transducers, looking at a few types which are common and familiar. In fact, there is a transducer for almost every physical quantity and two which are less familiar, but very useful, are the strain gauge and the tachogenerator. A strain gauge, nowadays, consists of a thin strip of semiconductor deposited on a flexible material. The resistance of the strip can be measured and the flexible carrier can be glued to almost any structure — a beam of a bridge, the wall of a house, the side of a container. Even very small changes in the length of the strip will cause noticeable changes of resistance so that strain, which means small changes of length, can be measured. Strain gauges are an essential part of modern civil engineering — they show how much your bridge is affected by loads and winds, how secure the foundations of your building are, how well your tank stands up to high pressure.

Tachogenerators are little dynamos; spin the shaft of a tachogenerator from another revolving shaft and the output voltage of the tachogenerator will be proportional to the speed of the shaft. They're used increasingly in disc turntables as part of a negative feedback system for keeping the motor speed constant.

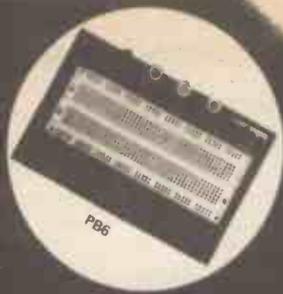That's only a flavour of transducers, but it should be enough to show what a varied bunch they are, and how they can be used to couple electronics circuits to almost anything else we like. Electronics wouldn't amount to much without them!



NEW & FREE FROM GSC

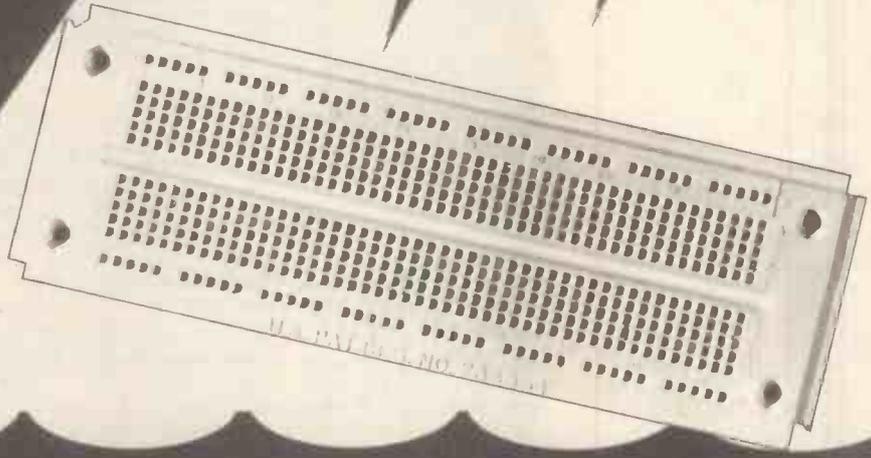

NEW AND FREE FROM GSC.

NEW an exciting range of projects to build on the EXP300 breadboards.

NOW anybody can build electronic projects using "Electronics-by-numbers", its as "Easy as A, B, C with G.S.C!"

FREE project **MUSICAL DOORBELL OF THE 3RD KIND** You've seen the film, now haunt your visitors with the tune!

Each time the doorbell is pushed the eerie tune plays out, then switches off to conserve battery power.

HOW DO YOU MAKE IT.

Our **FREE** project gives you clear "step-by-step" instructions. For example "take Resistor No.1 and plug it into hole numbers B45 and B47".

"Take IC No.1 and plug it into hole numbers E35 to E42 and F35 to F42, (pin 1 on the IC goes into F35)"

"Take. . ."Well! why not "clip-the-coupon" and get your **FREE** step-by-step instruction sheet and your **FREE** 12 projects with each EXP300 bought and your **FREE** catalogue and.


EXPERIMENTOR BREADBOARDS

The largest range of breadboards from GSC. Each hole is identified by a letter/number system. EACH NICKEL-SILVER CONTACT CARRIES A LIFE TIME GUARANTEE


All modular construction means that any Experimentor breadboard can be 'snap-locked' together to build breadboards of any size.



EXP325
The 'one-chip' breadboard Takes 8, 14, 16 and up to 22 pin IC's Has 130 contact points including 2 bus bars.

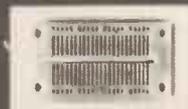

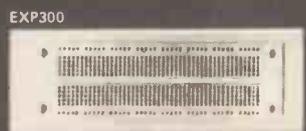EXP350
The 'beginners breadboard' For limited period you can have **FREE** 12 'Electronics by Numbers' PROJECTS



The most 'widely-bought' breadboard Don't miss out on our 'NEW AND FREE' projects They can be built on the EXP300

- EXP600**
The Hobbyist microprocessor' board
- EXP650**
The 'one-chip microprocessor' board
- EXP4B**
'Snaps-on' four extra bus bars
- PB6**
The ultimate breadboard kit
- PB100**
The most kit for the least money

NEW AND FREE FROM G.S.C. 24 HOUR SERVICE.

Tel (0799) 21682 with your Access, American Express, Barclaycard number and your order will be put in the post immediately.

TO ORDER JUST CLIP THE COUPON.

Experimentor Breadboards	Unit Price Inc. P & P + 15% VAT	Quantity Required
Exp 325	£ 2.70	
Exp 350	£ 4.48	
Exp 300	£ 7.76	
Exp 600	£ 8.39	
Exp 650	£ 5.00	
Exp 4B	£ 3.50	
PB 6	£11.73	
PB 100	£14.72	

NAME

ADDRESS

.....

enclose cheque/PO for £

Debit my credit card No.

Expiry date

Please send free catalogue Tick Dept. 9P

GLOBAL SPECIALTIES CORPORATION



GSC Unit 1, Shire Hill Ind. Estate Saffron Walden, Essex, CB11 3AQ. Telephone (0799) 21682. Telex 817477.

Automatic Greenhouse Sprinkler

Owen Bishop

A summer plant-saver that works automatically, triggered by the falling moisture level in a plant pot.

THE HOT sunny days that we hope to be having from now until September can play havoc with plants in a greenhouse. You need only to forget to water them once, or forget to open the windows on a warm day, and the plants are soon in a sorry state. Last-minute watering *might* revive them but, on the other hand, it *might not!* This device not only warns you when the plants are beginning to need some water, but actually does the watering for you. You might need to supplement its action each evening by using the old-fashioned watering-can, but it will take care of those times during the day when a light sprinkling makes all the difference to the health of the plants.

The circuit consists of two sections. One part is concerned with sensing the water state of the plants and sounding an alarm when it gets too low. The other part turns on the pump to sprinkle the water. If you simply need a warning and are prepared to do the sprinkling yourself, there is no need to build the pumping section. If you are going to include the pump, you will certainly want the warning device, too. This sounds for about 30 seconds *before* the pump is turned on. Should you or the family happen to be admiring the tomatoes as the soil goes dry, the warning gives you plenty of time to retreat — out of range of the sprinkler. The warning period can be extended if 30 seconds is not long enough.

Anyone who has ever watered a potted plant knows that it is more effective to water for a short period, and then stop and allow the water to soak in before repeating the watering. The sprinkler works in this fashion too. The pump is turned on for 30 seconds, off for 30 seconds, repeating until the soil has been moistened to the right degree.

The Circuit

The amount of water in the soil is sensed by a circuit which measures the resistance of the soil between two metal rods buried in the soil (the probe). If we pass a *direct current* through the soil, the water and dissolved salts in the soil act as an electrolyte. In a few



minutes, polarisation occurs and the resistance changes. Instead, we use an *alternating current*, to avoid polarisation. This is generated by a 1 kHz oscillator (IC1) in the sensor circuit. The alternating potential is rectified by a diode (D1) and smoothed by a capacitor (C7) to give a steady potential. As the soil becomes drier, its resistance increases. This gives the alternating voltage greater amplitude and so the steady DC potential rises. This rising potential eventually triggers a Schmitt trigger (IC3) causing its output to change abruptly from low to high (0 V to 12 V). The level at which this change occurs can be controlled by adjusting the 'Set Level' control, RV1.

The output of the sensor is combined with the output from the 1 Hz timer (IC2) by a NAND gate. When the output of the sensor is low (moist soil), the output of the gate is steady at 12 V. When the soil dries,

the output begins to alternate between 0 V and 12 V at a rate of 1 Hz. These pulses switch an audible warning device on and off, providing a bleeping tone. The pulses are counted and, after a fixed number (say 32), the selected output of the counter goes to 12 V. This switches on the pump. The output alternates from 0 V to 12 V regularly at (say) 1/32 the rate of the timer, giving periods of sprinkling followed by equal periods during which the water soaks in to the soil.

When the soil is sufficiently wet, the reverse actions occur. As the soil resistance drops, the DC potential falls and the Schmitt trigger output (IC3, pin 10) goes low, stopping the alarm. The low-going edge triggers a pulse generator (two gates of IC4) which sends a single high pulse to the reset input of the counter. This makes all its outputs go low, so turning off the pump.

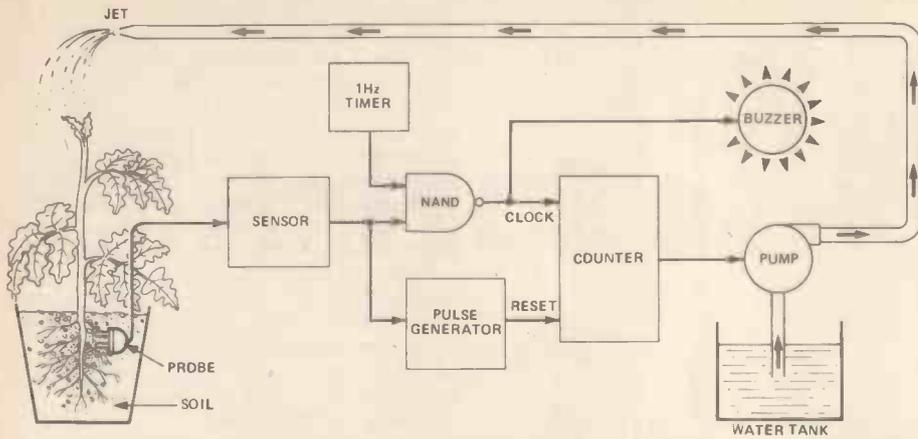


Figure 1. Block diagram of the Auto Sprinkler.

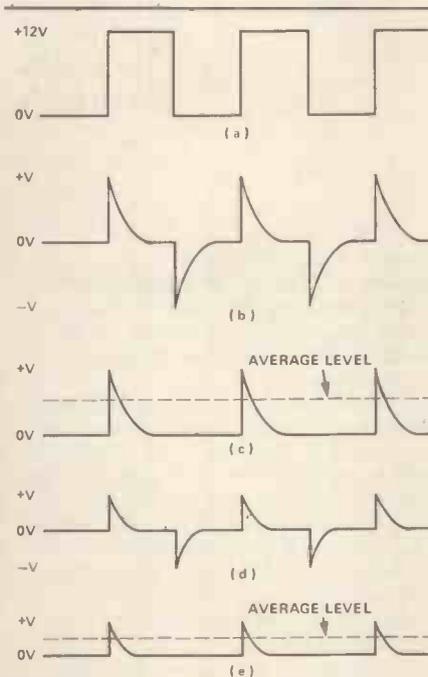
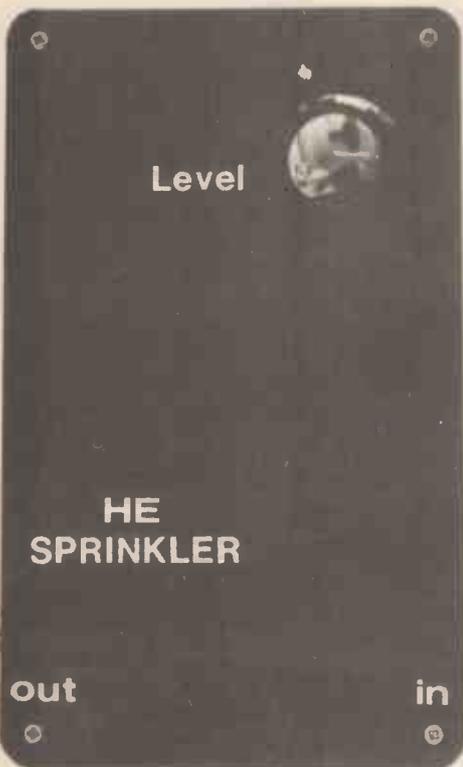



Figure 2. The timing diagram shows: (a) Output from IC1; (b) Waveform at the 'live' pin of the probe; (c) Junctions of D1 and C7; (d) As (b) but with wetter soil; (e) As (d) with wet soil — the average level is lower so the alarm is not triggered.

Power Supplies

Before going on to construction details, we must consider the matter of power supplies. The circuit uses an unregulated 12 V DC supply. This is best taken from a power-pack located indoors, with a light-duty lead to carry the current to the device in the greenhouse. The pump is a windscreen-washer pump, which needs at least 2 A. A circuit for a suitable power-pack is given later. If you have decided to use this only as a warning device, the power requirements are much less. Without the pump and its relay, the circuit uses only about 45 mA and almost any small power-pack can be used to provide this. Then it would be more suitable to locate the circuit indoors, with a lead running to the probe in the greenhouse. A low-current power supply could easily be fitted into the case.

Construction

The circuit is best built and tested stage by stage, beginning with the sensor circuit. The 1 kHz oscillator based on IC1 is the first part to assemble, including C6. If an earphone is connected between the free terminal of C6 and the 0 V line, a high-pitched tone should be heard, indicating that the oscillator is working. If all is in order, wire up RV1, D1, C7 and the probe. In the prototype, the probe is a 2-pin 5-amp mains plug of the old type, which was found in the scrap box. The essentials are two stout metal rods, preferably of brass or some other corrosion-resistant metal or alloy. They should be about 1.5 cm long and mounted on an insulating base about 1.5 cm apart. Connect these to the circuit board with ordinary lighting flex. While testing, you need a potted plant, or at least a pot of moist potting compost or good loamy soil. The probe can be simply pushed into the soil when testing. Later when the system is in use, it is better to bury the probe one to 2 cm deep in a pot of soil or the

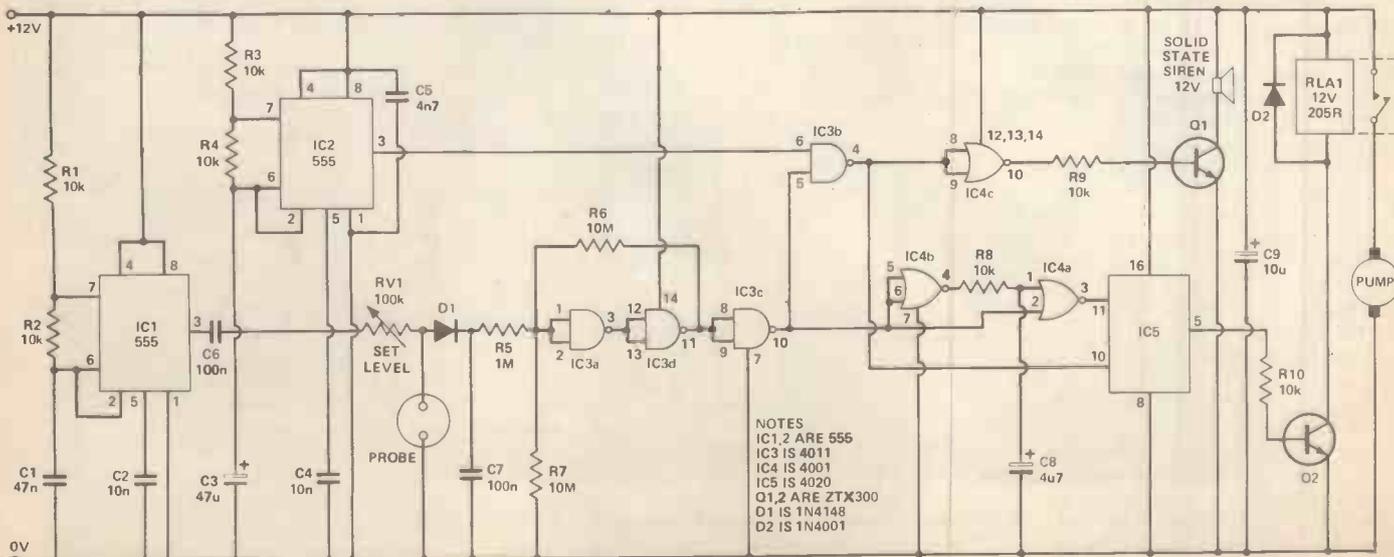

NOTES
 IC1,2 ARE 555
 IC3 IS 4011
 IC4 IS 4001
 IC5 IS 4020
 Q1,2 ARE ZTX300
 Q1 IS 1N4148
 Q2 IS 1N4001

Figure 3. Complete circuit of the Auto Greenhouse Sprinkler. The power supply unit is shown over the page.

Auto Sprinkler

greenhouse bed. Place it on its side, so that the base does not prevent water from reaching the soil surface directly above the rods.

If you have an oscilloscope or FET voltmeter, the rectifying stage can be tested by connecting the probe of the scope to the junction of D1 and C7. As RV1 is turned, the voltage should range from about 1 V to about 10 V. Pulling the probe slightly out of the soil (simulating drying out) results in a fall in output voltage. Incidentally, the circuit does not work unless there is at least some conduction across the probe, so remember to water the plant occasionally, or your tests (and the plant) will probably fail.

Next build the Schmitt trigger circuit (IC3). Its output should flip neatly from 0 V to 12 V as RV1 is turned from one extreme to the other (with the probe in the plant-pot).

The next stage is to build the 1 Hz timer, based on IC2. Unless there is effective decoupling of the supply line between IC1 and IC2, the timer is triggered by noise from IC1. Decoupling capacitor (C5) was therefore placed as close as possible to the terminals of IC2. Too large a capacitor affects the operation of the sensor circuit, so keep to the value specified. The remaining gate of IC3 may now be wired in. With RV1 at one extremity (minimum resistance), the output of pin 4, IC3b, should be 12 V. At the other extremity it should alternate from 0 V to 12 V at approximately 1 Hz (the exact frequency does not matter).

One gate of IC4 simply inverts the output from IC3, so there should be no problems here. The other two gates form the reset pulse generator. This is not needed if you want only a warning, and no water pump. The pulse

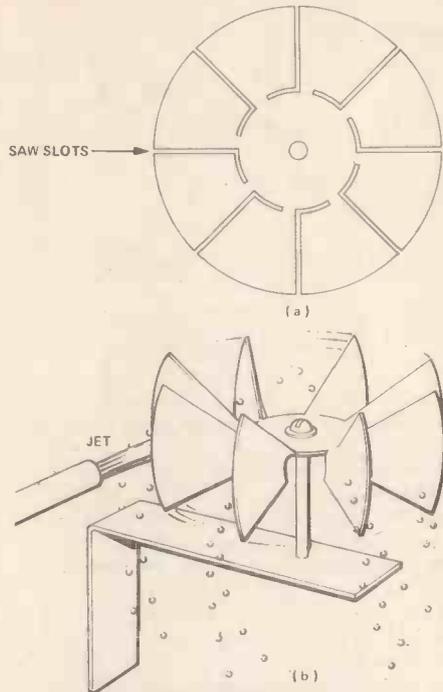


Figure 4. A simple turbine sprinkler: (a) cutting the wheel from a disc of sheet aluminium; (b) the turbine in operation. Note that the jet should be quite narrow or the plants will be flooded.

generator should normally have a low output which goes high very briefly when the output from IC3 goes low (ie when the soil has been watered enough). This pulse can be detected as an upward kick of the needle of a voltmeter connected to pin 3, IC4a.

The pump is controlled by the counter (IC5). First check the connections from IC3 and IC4. The output from IC5, pin 4, has 1/64 the

frequency of the input and with a 1 Hz input, the output is low for 32 S and high for 32 S. This gives 32 S warning — to evacuate the greenhouse. If you think this is more than enough, take the output from pin 5 (as in Figure 3), which gives a 16-second warning. Since your timer may not be running at 1 Hz, anyway, the best thing is to test the output from the various pins — dotted lines on the component overlay — and find the one which gives the timing you prefer. Mount the relay with its protective diode, D2, and the switching transistor Q2. Join the base of Q2 to the selected output pin of IC5 by way of R10. The tracks to which the relay switch terminals are soldered were made as short as possible but, since they are to carry heavy current, it is advisable to run a thick coating of solder along them to aid conduction. Finally, mount the circuit board, RV1, and the pump in the case.

Installing The Sprinkler

The case housing the circuit should be sited well away from any area of the greenhouse which is to be sprayed or dripped on. A few trials may be needed to establish optimum operating conditions and methods, so perhaps it is best to mount the case temporarily, to begin with. The probe should be buried in a pot of soil. Preferably, this should have a plant in it too, to ensure that the soil loses water at the same rate as the soil in other pots. The probe can be buried in a bed if preferred, but it should be placed where it will receive an average amount of water and where it is likely to lose water at an average rate (ie not in the sunniest or shadiest part of the greenhouse).

The pump needs a supply of water. This is best held in a tank inside the

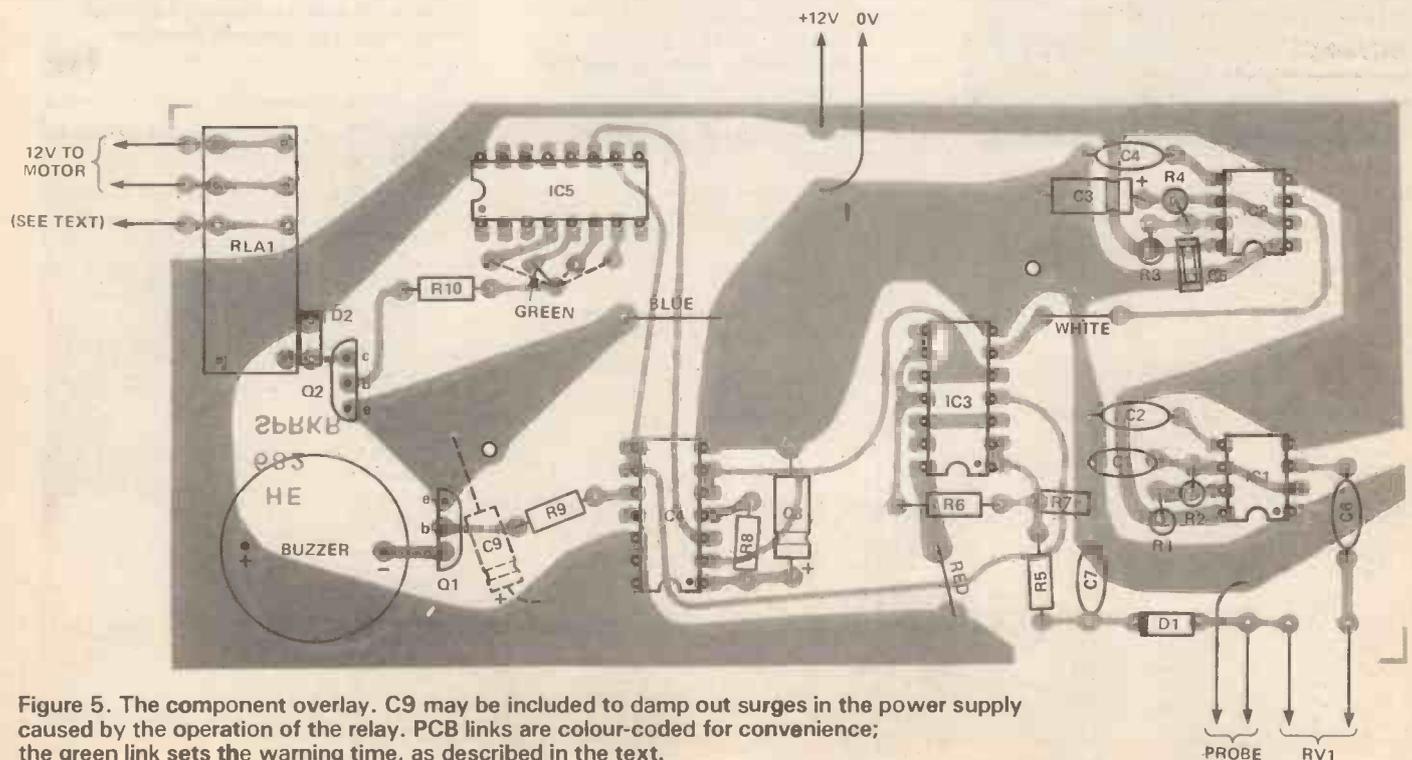


Figure 5. The component overlay. C9 may be included to damp out surges in the power supply caused by the operation of the relay. PCB links are colour-coded for convenience; the green link sets the warning time, as described in the text.




You'll find it just as enjoyable... cruising on the motorway.

Now! No matter where you live in Britain you can enjoy the pleasure of cruising. Any boat in the Shetland range of family cruisers can be towed behind the average family car.

Think of the advantages to be enjoyed—the rivers, the lakes, the Broads, estuary and coastal waters whenever the fancy takes you.

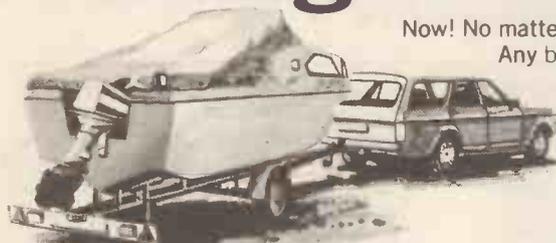This year take the cruise you always promised yourself...buy Shetland. Clip the coupon for free brochure and name of your nearest dealer.



Shetland

FAMILY CRUISERS

BRITAIN'S NO.1 SETS THE STANDARD

To: Shetland Boats Ltd.,
Stanton, Nr. Bury St. Edmunds, Suffolk. Tel: (0359) 50355.

H66/82

Name _____

Address _____

Tel _____

For towing: Make of car _____

Model _____ c.c.

Please tick for further information: Family Cruisers
 Dories Stratos Sportsboat Fisherboats



DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequence (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button. This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most household. It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one 1uA from a PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions. **IDEAL PROJECT FOR BEGINNERS—Only 65**



REMOTE CONTROL

Published remote control systems tend to be quite complex requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infra-red, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs of three analogue outputs for controlling, e.g., TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e., relays, triacs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices. We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself! **SEND US 30p and a stamped addressed envelope for your copy TODAY!**



KITS & COMPONENTS


HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

TDR300K	Remote Control Dimmer	£14.30
MK6	Transmitter for above	£ 4.20
TD300K	Touchdimmer	£ 7.00
TDE/K	Extension kit for 2-way switching for TD300K	£ 2.00
LD300K	Rotary Controlled Dimmer	£ 3.50



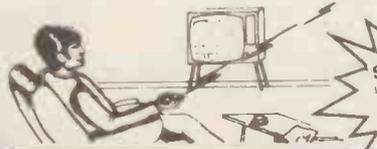FOR FREE SHORT FORM CATALOGUE SEND SAE TODAY



24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



CT1000K Basic Kit	£14.90
CT1000K with white box (56x131 x 71mm)	£17.40
(Ready Built)	£22.50

SPECIAL OFFER
Integrated circuit S.N. 76477
Sound generator £1.65
L.M. 3915 bar/dot driver £1.95
LS 7220 electronic lock £2.40
supplied with data and circuits

LEDs

3mm & 5mm Round Red...09p Green...12p
Clips 3mm & 5mm...03p Yellow...12p

[Shaped Lens]

Rectangular (Gravesstone)	16p	16p	16p
Rectangular	5x2.5mm	17p	20p
Square	5x5mm	17p	20p
Triangular	Δ5mm	17p	20p
Arrowhead	<2.5x5mm	17p	20p

[Tri Colour Led's]

5mm round...30p
5mm Rectangular...32p

[Flashing Led's]

5mm diameter Red...39p Flashing/Continuous...42p



DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.50




FAST SERVICE · TOP QUALITY · LOW LOW PRICES

ALL PRICES EXCLUDE VAT

No circuit is complete without a call to -

TK

ELECTRONICS
11 Boston Road
London W7 3SJ

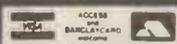

TEL: 01-567 8910 ORDERS
01-579 9794 ENQUIRIES
01-579 2842 TECHNICAL (AFTER 3PM)



CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

A PRACTICAL DIGITAL ELECTRONIC KIT FOR ★ LESS THAN £20 ★



SUITABLE FOR
BEGINNERS

NO SOLDERING!

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains: seven LS TTL integrated circuits, breadboard, LEDs, and all the

DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19-90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits. This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

It is supported by our theory course

DIGITAL COMPUTER LOGIC AND ELECTRONICS ~~£8.50~~ £6.00 for beginners, and our latest, more advanced text,

DIGITAL DESIGN £7.00

Please send for full details (see coupon below).

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 96 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND.
TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK

Please send me:

.....SUPERKIT(S) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No.....


Signature.....

Telephone orders from card holders accepted on 0480 67446 Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

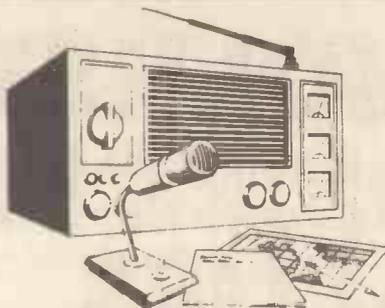Cambridge Learning Limited, Unit 96 Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).



BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-
British National Radio & Electronic School
READING, BERKS. RG1 1BR

Name

Address

HE/6/815

BLOCK CAPS PLEASE

PARNDON ELECTRONICS LTD.

Dept. No. 22, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

RESISTORS: ¼ Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded/enclosed and colour coded.
£1.00 per hundred mixed (Min 10 per value)
£8.50 per thousand mixed. (Min 50 per value)
Special stock pack 60 values. 10 off each £5.50

DIODES: IN4148 3p each. Min order quantity - 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems.
4 Way 86p each. 6 Way £1.00 each. 8 Way £1.20 each

DIL SOCKETS: High quality, low profile sockets.
8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS
MIN. ORDER - U.K. £1.00. OVERSEAS £5 CASH WITH ORDER PLEASE

Goodmans Fane Richard Allan Celestion Altai

Multimeters & Accessories

UK P/P 65p or £1.00 for two
KRT 100 12 range pocket
1K/volt £4.95
NH55 10 range pocket
2K/volt £5.95
NH56R 22 range pocket
20K/volt £10.95
YW360TR 19 range plus hfe test 20K/volt. £14.95
5T303TR-21 range plus hfe test 20K/volt. £17.95
TMK500 23 range plus 12 adc plus cont. buzzer £23.95



High Quality Speakers

8" 25W to 50W
10" 25W to 100W
12" 30W to 200W
15" 100W to 250W
18" 100W to 350W



PIELO ELECTRIC TWEETERS

Up to 100 watts each. No x-over required. Flared Horns. 4KHz range. Flared Horns. In stock now. Large range of speakers, public address equipment, microphones, masts, ham equipment. Heavy chromed Floor Stand. £9.95
Boom Arm £8.90
Echo Chamber £99.95
Analogue Echo Chamber £99.95

CROSSOVERS

2 way	100W	8 ohm
3 way	100W	8 ohm
4 way	80W	8 ohm

Power Amplifier Modules 100W to 200W

Stockists of leading makes of Disco Units & Lighting Equipment.

CITRONIC, FAL, TK, ICE, OPTIKINETICS, PLUTO.

SEND LARGE SAE FOR LIST
ALLOW 10 DAYS FOR DELIVERY

All prices include VAT at 15%. Mail Orders welcome
MUSICRAFT
303 EDGWARE ROAD,
LONDON W 2 ENGLAND
TELEPHONE: 01 402 9729. 01 402 2898

UNDERSTANDING COMPONENT VALUES

Roger Harrison
William Fisher

0.001 μ 100n OR1
4R7 6p8 120,150,180
1k02
33, 47, 56, 68, 82, 100

To the beginner in electronics, and to quite a few not-so-beginners, the values and units given to electronic components such as resistors, capacitors and RF chokes seem confusing. This article should clarify things for you.

THE DECIMAL point has been almost abolished in electronics. The little dot was so small it often disappeared when things were printed, and in any case not everybody recognises its meaning. The French, who invented the decimal system, use a comma instead and so do most Europeans. Other countries use commas for different purposes, like separating hundreds from thousands in large numbers. So when you see a number written 1,500 you don't immediately know whether it's meant to be fifteen hundred or one-and-a-half to three decimal places! When engineers from all over the world sat down to decide on a standard international numbering system, they decided that the best thing to do with the decimal point/comma was to get rid of it altogether.

It has been replaced by a letter. To show where the decimal point was, any letter would do. For example, you might write one-and-a-half as 1a5 or 1b5 or 1c5, or you could use a capital letter, say 1P5 or 1Q5.

Normally in electronics you're not dealing with pure numbers. You're dealing with numbers of *some things* — so many volts, so many watts, amps, ohms and so forth. Most of these quantities have letters that are used as abbreviations for them. 5V means 5 volts, for example, 5A means 5 amps, 5W means 5 watts. When you want to express fractional amounts of these quantities you use the abbreviation letter in place of the decimal point, like this: 5V6, 1A5, 3W7. You don't have much trouble seeing that these last three mean 5-point-6 volts, 1-point-5 amps and

3-point-7 watts. Unfortunately, there isn't a letter of our alphabet that stands for ohms, but we're all quite used to seeing a capital R for resistance, so we use that to indicate ohms, like this: 4R7, 2R2, 100R. These mean of course 4-point-7 ohms, 2-point-2 ohms and 100 ohms.

Mini And Maxi Units

Lots of things aren't commonly or conveniently measured in the standard size units. Capacitors, for example, are never measured in Farads, because a whole Farad is an enormous capacitance. Practical capacitors have values measured in thousandths, millionths and even smaller fractions of a Farad. At the other extreme, resistors often have values of thousands and millions of ohms. Now it's obviously inconvenient and confusing to write 0F000001 for one microfarad or 100 000R for one hundred kilohms, so what you do is alter the decimal-point-indicating letter to show the size of the units you are using. For example, 1k5. Clearly this means one-and-a-half somethings and from kilograms and kilometres everyone knows that the little letter 'k' indicates a thousand. So 1k5 must mean one-and-a-half thousand that is 1500. Similarly, 4k7 means 4700, 2k2 means 2200 and so forth. It's usually clear enough from the context whether you're talking about resistance or capacitance or frequency or whatever, so you don't need to write ohms or anything afterwards.

As well as for one thousand, there are a number of other letters that stand for multiples of the basic unit. Here they are:

G (Giga) = 1 000 000 000 (one thousand million, 10^9)

M (Mega) = 1 000 000 (one million, 10^6)

k (kilo) = 1 000 (one thousand, 10^3)

m (milli) = 1/1000 (one thousandth, 10^{-6})

μ (micro) = 1/1 000 000 (one millionth, 10^{-6})

n (nano) = 1/1 000 000 000 (one thousand millionth, 10^{-9})


p (pico) = 1/1 000 000 000 000 (one billionth, 10^{-12})

Occasionally you'll come across *tera* (T) which is one million million (10^{12}) and *femto* which is one thousand billionth (10^{-15}).

Armed with this information, you should be able to read almost any printed value of an electronic quality. For practice, here are a few examples of values you might not be too familiar with. A capacitor marked as 47p has a value of 47 picofarads, which is 47 billionths of a Farad. One marked 4p7 has only a tenth the value, 4-point-7 billionths of a Farad. A 100n capacitor is 100 nanofarads or $100 \div 1 000 000 000$ Farads = $1/10 000 000$ farad. At the other end of the scale, a resistor marked as 15M has a value of 15 Megohms, ie: 15 million ohms; one marked 1M5 has a value ten times less at 1-point-5 million ohms.

Translation Problems

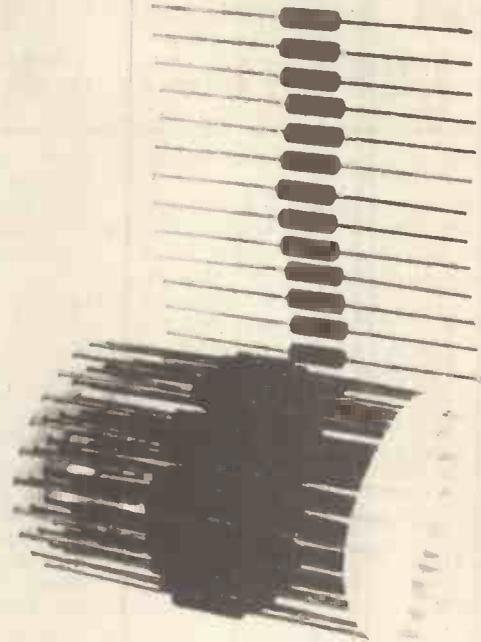The standard international numbering system makes everything simple as long as everybody sticks to it, but unfortunately there are still some occasions when you come across values written in an older style and you have to translate them into a



Understanding Components

new style. This mainly happens with capacitors.

The first problem is that the old symbol for 'micro' was different. It was a Greek letter called mu, which is pronounced like the noise a pussycat makes, and looks like this: μ . This symbol caused some confusion in the past, because it sometimes got mistaken for 'm', which has always meant 'milli', a thousand times larger. So was officially replaced by 'u'. If you see a capacitor marked, for example 10 μ , you can translate that directly into 10u and know that it means 10 microfarads. Nevertheless, is still widely used.

Another confusing thing is the still common practice of marking or specifying capacitor values in *fractions* of a microfarad like 0.001u (1000p, or better, 1n). To convert fractions of a microfarad into modern values, you have to multiply by 1000 to get the answer in nanofarads, or multiply by 1 000 000 and get the answer in picofarads. Don't panic! To save you trouble, here is a list of typical old-style values and how they translate into new style. From this list you should be able to work out very quickly the new-style version of any old-style capacitor value.

0.1u = 100n 0.47u = 470n
 0.01u = 10n 0.047u = 47n
 (10 000p)
 0.001u = 1n 0.0047u = 4n7
 (1000p)
 0.001u = 100p 0.00047u = 470p

Small Resistances

Resistors with small values sometimes cause difficulties. Because small resistances are not very commonly used, most people are not accustomed to thinking in terms of milliohms (thousandths of an ohm), so the little letter 'm' isn't used for resistors. A resistance of one-tenth of an ohm is not written 100m (for one hundred milliohms), but 0R1 (for one-tenth of an ohm). As usual, the letter R indicates the position of the decimal point and shows that the unit of measurement is whole ohms. In the same way, 2R2 means 2-point-2 ohms, 5R6 means 5-point-6 ohms and so forth. Even smaller values are still written as fractions of an ohm, but the 0 before the decimal-point-indicating letter is usually omitted. For instance, R01 means point-01 ohms (one hundredth of an ohm), R001 means point-001 ohms (one thousandth of an ohm), R33 means 33/100ths of an ohm and R068 means 68/1000ths of an ohm.

Zeros

Some component values are written with a zero before or after the multiplier character to indicate the value quite unambiguously. For example, a 1000 pF capacitor, rather than being written '1n' may be written 1n0. Or a point-1 (0.1) ohm resistor, rather than being written R1, may be written 0R1.

Preferred Values

Why is it that resistors and capacitors only seem to come in certain values? You almost never see a 25R resistor, only 22R or 27R ones. 600k resistors are likewise as rare as hens' teeth, but there are any number of 560k and 680k ones. For one thing, manufacturers can't make every

possible value of resistor. If they made resistors in every whole number of ohms between 1R and 10M, they'd be making ten million different products and selling only a few of each. Very capital inefficient, as they say. Resistors would be ridiculously expensive and manufacturers would go bankrupt. Obviously, only a restricted number of values can be produced.

But why these particular values that actually are produced? What's so special about 4k7 or 56R or 820R? Why not stick to simple numbers? The reason is that these particular values allow the least number of different values to be made. How come? Well, resistors are not made with absolute accuracy — that costs too much and isn't usually necessary. Most circuits will accept a variation of 10% in resistor values without problems. So resistors are made with values that are anything up to 10% higher or lower than their marked value. This is called a tolerance of 10% and such a resistor is usually called a 10% resistor. For example, a 100R, 10% resistor might have a value anywhere between 90R and 110R. Given this amount of variation, there would obviously be no point in also making 10% resistors with nominal values like 94R or 107R, because these values are already covered by the $\pm 10\%$ spread of the 100R resistor.

So in a series of 10% resistors, what should be the next highest value above 100R? A value of, say, 111R would be too low, because the 111R resistor would also have a tolerance of 10%, so its possible values would spread down to below 100R, completely overlapping the upper range of variation of the 100R resistor. To avoid this kind of overlap, the next highest value 10% resistor needs to be about 120R. A 120R 10% resistor has its possible values spread between 108R and 132R. There's still a small overlap, but to get rid of the overlap completely without leaving a gap you'd need a value of one hundred and twenty two and two ninths ohms (work it out for yourself if you like algebra), which is rather an awkward number. 120R is a nice round number, so that's the 'preferred value' next in the series. By similar reason-

ing, the next value in the series of 10% resistors is 150R, then 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R and then 1k. It doesn't take much to see that the obvious next preferred value after 1k must be 1k2, then 1k5, 1k8 and so on. In other words, the same sequence of values keeps repeating, multiplied by ten at each repetition. This series of preferred values is known as the *E12 series*, because there are 12 values in the series. For reference, here are two 'decades' of the E12 series:


10	100
12	120
15	150
22	220
27	270
33	330
39	390
47	470
56	560
68	680
82	820

Even though resistors are nowadays more commonly made with a tolerance of 5%, the old E12 series of preferred values is still the most widely used. There is a similar series, called E24, which is worked out in just the same way as the E12 series, except that a tolerance of only 5% is assumed.

For closer tolerances, there's the E48 series (2%) and E96 series (1%) with, respectively, 48 and 96 values per decade.

Capacitors are made to wider tolerances than resistors — 20% is not at all uncommon, so they are usually supplied in a restricted range of preferred values. The significant figures in this series are 10, 15, 22, 33, 47 and 68. As there are only six values per decade, it is called the E6 series.

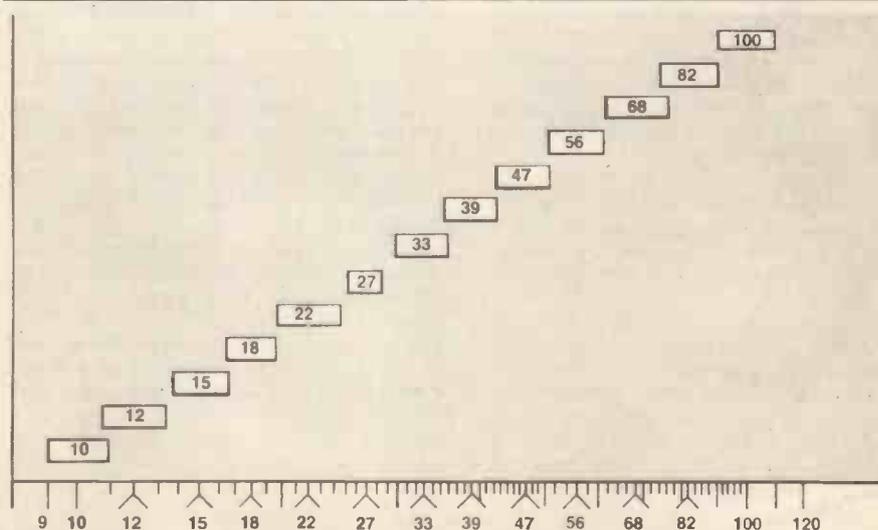Close tolerance values are written in the same way as we've described previously, so if you come across a 1k02 resistor or a 34p8 capacitor you'll know you're dealing with close tolerance components. In the first case, you have a 1020 ohm resistor, in the second case you have a 34.8 pF capacitor.



This shows the tolerance extremes of all the values in E12 series, represented by a horizontal bar. The left-hand end and right-hand ends of each bar represent, respectively, the lower limit and the upper limit of the value. Most overlap, you will note.

Preferred numbers in decade for the E6, E12, E24 & E96 series						
E6 20%	E12 10%	E24 5%	E96 1% and 2%			
10	10	10	10.0	10.2	10.5	10.7
		11	11.0	11.3	11.5	11.8
		12	12.1	12.4	12.7	
15	15	13	13.0	13.3	13.7	14.0 14.3 14.7
		15	15.0	15.4	15.8	
		16	16.2	16.5	16.9	17.4 17.8
22	22	18	18.2	18.7	19.1	19.6
		20	20.0	20.5	21.0	21.5
		22	22.1	22.6	23.2	23.7
33	33	24	24.3	24.9	25.5	26.1 26.7
		27	27.4	28.0	28.7	29.4
		30	30.1	30.9	31.6	32.4
47	47	33	33.2	34.0	34.8	35.7
		36	36.5	37.4	38.3	
		39	39.2	40.2	41.2	42.2
68	68	43	43.2	44.2	45.3	46.4
		47	47.5	48.7	49.9	
		51	51.1	52.3	53.6	54.9
		56	56.2	57.6	59.0	60.4
		62	61.9	63.4	64.9	66.5
		68	68.1	69.8	71.5	73.2
		75	75.0	76.8	78.7	80.6
		82	82.5	84.5	86.6	88.7
		91	90.9	93.1	95.3	97.6

Top: The 'preferred values' of E6, E12, E24 and E96 series components.
 Right: The tolerance spread (possible values, above and below the nominal value) of components in the E6, E12, and E24 preferred value series.


Tolerance extremities for the E6, E12 and E24 preferred series value						
-20%	-10%	-5%	nominal value	+5%	+10%	+20%
8	9	9.5	10	10.5	11	12
		10.5	11	11.6		
		10.8	11.4	12	12.6	13.2
12	13.5	12.4	13	13.7		
		14.3	15	15.8	16.5	18
		15.2	16	16.8		
17.6	19.8	16.2	17.1	18	18.9	19.8
		19.0	20	21.0		
		20.9	22	23.1	24.2	26.4
26.4	29.7	22.8	24	25.2		
		25.7	27	28.4	29.7	
		28.5	30	31.5		
37.6	42.3	29.7	31.4	33	34.7	36.3 39.6
		34.2	36	37.8		
		35.1	37.1	39	41.0	42.9
54.4	61.2	40.9	43	45.2		
		44.7	47	49.4	51.7	56.4
		48.5	51	53.6		
		50.4	53.2	56	58.8	61.6
		58.9	62	65.1		
		64.6	68	71.4	74.8	81.6
		71.3	75	78.8		
		77.9	82	86.1	90.2	
		86.5	91	95.6		

E6 E12 E24 E24 E12 E6
 lower extremities upper extremities

HE

AITKEN BROS.

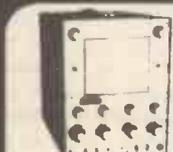ELECTRONIC COMPONENTS AND TEST EQUIPMENT
 35, HIGH BRIDGE, NEWCASTLE
 UPON TYNE NE11EW TEL: 0632 326729



SAFGAN OSCILLOSCOPES - 5 mV/div sensitivity. Choice of Bandwidth 10, MHz, 15 MHz, 20 MHz. 1S/div-100n S/div. Calibrated timebase. Solid trigger with bright line auto, normal and TV. XY facility. Z modulation. Calibration output. Bright and clear display. Portability. • Model DT410-10 MHz £205.85 + 6.00 carr. Model DT415-15 MHz £217.35 + 6.00 carr. • Model DT420 20 MHz £228.85 + 6.00 carr. Send S.A.E. FOR FULL spec



THANDAR PDM35 3 1/2 DIGIT L.E.O. DIGITAL POCKET MULTI-METER. • DC volts (4 ranges) 1mV to 1000V. • AC volts 1V to 500V • DC current (6 ranges) 1nA to 200mA • Resistance (5 ranges) 1Ω to 20 meg. £2. £39.95. • AC adaptor £5.95. • carrying case £3.65 • MN1604 Battery £1.57.



THANDAR TM354 3 1/2 DIGIT LCD DIGITAL POCKET MULTIMETER • DC volts 1 mV to 1000V • AC volts 1V to 500 V AC rms • DC current 1µA to 2A • Resistance 1Ω to 2 MΩ • Diode check • Basic accuracy ± (0.75% of reading + 1 digit) • Battery life typically 2000 hrs • leads inc. • £45.94 • 40KV Probe £34.95 • Universal test lead set £12.95.



THANDAR TM352 3 1/2 DIGIT LCD DIGITAL POCKET MULTIMETER • DC volts: 100µV to 1000V • AC volts: 1V to 1000V • DC current: 100 nA to 10A • Resistance 1Ω to 2 MΩ • Diode check • hFE measurement • Audible continuity check • Basic accuracy ± (0.5% of reading + 1 digit) • Battery life 150 hrs + • £57.44 inc. leads • Battery • Universal test lead set £12.95 • 40 KV probe £34.95



THANDAR SC110 SINGLE TRACE LOW POWER 2" OSCILLOSCOPE • Bandwidth DC to 10 Mhz • Sensitivity: 10mV/div to 50 V/div. • Sweep speeds: 0.1µ secs / div to 0.5 secs/div. • Power requirements 4-10V DC 4 "C" cells • Size & weight 255x150x40mm • 800gms £159.85 a truly portable and superb instrument • Carrying case £8.86 • AC Adaptor £5.69 • Nicad Batt. pack £8.63 • x1 probe £9.78 • x10 probe £11.50 Complete range of Thandar instruments available from stock S.A.E. for CAT. & prices.




G.S.C. SOLDERLESS BREADBOARDS • Accepts all components with leads up to .033" • Replaceable nickel-silver spring clip contacts. • Combines bus strip with board • Unlimited expansion • .3" and .6" centre channels • Three free experimental circuits with every purchase

	Centre Channel	Strip Length	Strip Width	Tie Points	Term Clips	i.c. Cpty.	Price
EXP-600	15mm	152mm	61mm	550	110	28pin	£7.25
EXP-300	8mm	152mm	53mm	550	110	14pin	£6.62
EXP-48	n/a	152mm	25mm	160	32	n/a	£2.65
EXP-650	15mm	91mm	61mm	270	54	40pin	£4.14
EXP-350	8mm	91mm	53mm	270	54	14pin	£3.62
EXP-325	8mm	48mm	53mm	130	26	12pin	£1.84

Please send S.A.E. for catalogue listing complete range of G.S.C. Instruments and Boards.



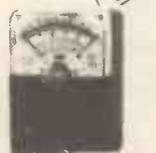SABTRONICS LCO MULTIMETER MODEL 2033. • DC volts 100 µV-1000V Accuracy + 5% • AC volts 100µV-1000 V Accuracy ± 1% • DC current 10µA-2A Accuracy ± 1% • AC current 10µA-2A Accuracy ± 1% • Resistance 1Ω-20 MΩ Accuracy ± 1% • £42.27. • Please send 30p for full Sabtronic catalogue and price list



TMK 500 MULTIMETER • 30 kopv. • AC volts 2.5 10 25 100 250 500 1000V • DC volts 0.25 1 2.5 10 25 100 250 1000 • DC current 50µA 5MA 50MA 12 amp • Resistance 0-6K 60K, 60 meg. • Decibels -20 to + 56 dB • Buzzer continuity test • Size 160x110 x65 • Batteries and leads inc. £26.95



YN360 TR MULTIMETER • AC volts 10 50 250 1000 • DC volts 0.1, 0.5, 2.5, 10V 150V 250V, 1000V. • DC current 50µA 2.5 MA, 25MA, 250 MA • Resistance 0-2K 20K 2M Ω, 20 MΩ. • Transistor check • DB -10db --+ 22db £16.95



DESOLDERING TOOL £6.45



SCHOOLS, COLLEGES, UNIVERSITIES SUPPLIED. PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER. PRICES INCLUDE VAT. PLEASE ADD 75p POSTAGE TO ORDERS UNDER £10.00

ZX COMPUTING

Britain's Biggest Magazine For The Sinclair User

Over 100 pages of information and programs for the ZX81 and ZX80 user including a 1K Chess routine!

ZX Computing is a quarterly magazine with over 100 pages of programs, articles, hints and tips for the ZX81 and ZX80. We've put the magazine together with just one aim in mind — to make sure you get the most use and enjoyment out of your Sinclair computer.

In the first issue, as well as a host of 1K and 16K programs (the majority dumped directly onto the printer), we've got two articles to help dispel the mysteries of machine code, a chess routine which takes up just 1K, an explanation of PEEK and POKE, an entire section on business uses of the ZX81 (complete with a program to handle the accounts of up to 100 customers) and a construction article which will show you — even if you've never used a soldering iron before — how to cheaply double the memory on your ZX81.

If you're serious about exploring the full potential of your Sinclair computer, and you want an easy-to-understand series of articles to improve and develop your programming skills, then ZX Computing is for you. Issue one is on sale now.

- **Software Reviews** — which programs are the best buy?
- **Business Routines** — put your ZX to work!
- **Expansion Systems** — how good and how much?
- **Machine Code for ZX81** — secrets revealed at last!
- **DIY Memory Upgrade** — cheap way of adding bytes

SUBSCRIPTION ORDER FORM

Cut out and SEND TO :



513 LONDON ROAD,
THORNTON HEATH,
SURREY,
CR4 6AR.

**POST FREE
SUBSCRIPTION**

Please use **BLOCK CAPITALS** and include post codes.

Name (Mr/Mrs/Miss)

delete accordingly

Address

Signature

Date

Please commence my subscription to ZX Computing with the issue.

(tick as appropriate)

£7.00 for 4 issues U.K.

£1.75 for a single copy of the issue

I am enclosing my (delete as necessary) Cheque/Postal Order/International Money Order for £.....

(made payable to ASP Ltd)

OR

Debit my Access/Barclaycard* (*delete as necessary)



HE 4/6

Insert card no.

POPULAR COMPUTING

In this issue we present the first instalment of our microcomputer project, especially developed with Hobby Electronics readers in mind. It is more than just a teaching aid — it is also a powerful machine for control applications. In future issues, we'll be presenting a number of projects designed to be controlled by a computer, but first you'll need

THE HE MICROTRAINER . . . 60

If any single microcomputer can be said to have started an industry, that computer is Sinclair's ZX81. Add-on extras now available for the ZX81 include ASCII keyboards, controllers and memory packs. In the months to come we'll be reviewing many of these products. We start with

MEMOTECH'S 64K RAM PACK 65

Of course, a computer is only as good as the software — the programs — written for it. A vast number of programs have already been developed for the ZX81 and more are appearing every month. What better place to start than Sinclair Research's own ZX Software, which we've called

THE SINCLAIR TAPES . . . 66



Colour television monitor courtesy of JVC and Which Video?

HE MicroTrainer

A powerful and flexible Hex Trainer/Controller based on the popular 1802 microprocessor also used as the main MPU on board UOSAT, the University of Surrey Satellite). This month we introduce the 1802 and in July, we get down to nuts and bolts with the constructional details.

HOBBY ELECTRONICS, as well as offering projects and features for the more advanced electronics enthusiast, has always been very much a magazine for beginners, too. Whatever direction is taken by the technology of electronics, in industry and commerce, this magazine will always aim at offering the hobbyist a foothold in basic, applied electronics. In this series of articles, covering a major computer project, we present an alternative to the view that microprocessors are of a complexity beyond the abilities of the average hobbyist.

The microprocessor has been around for close to a decade, now, and its success is clearly evident in the vast range of

microprocessor-based consumer products that have flooded the market; computers, toys, timers, heating controllers, and cash registers, to name but a few. The very factors that make the device attractive to these applications, namely low cost and high flexibility, equally justify its use by the amateur constructor.

In this article, we present a discussion of the basic principles of microprocessor operation. This will be expanded and illustrated, through applied examples, in later issues and next month we will start the full constructional details of our microprocessor training machine. Later, we will be specifically concerned with in-

terfacing this machine (and machines in general) to the real world in controller-type applications.

A Bit Of This And That

A microprocessor is an electronic device that processes digital information (data). The term 'digital' means that the signal voltages that are being dealt with are in discrete levels, commonly just two levels, a low voltage (0V) and a high voltage (+5V); these are usually referred to as logic 0 and logic 1 respectively. Most of you will already be familiar with simple digital circuitry.

If you pause to think of applications for

solid-state electronics, you will see that a large number of them are immediately suited to digital electronic design. In an industrial control system, for example, we may have a number of devices (motor, valves etc) which switch either on or off, open or closed, as a logical function of the state of other devices (switches, sensors etc). Other systems, which use transducers, pick-ups and variable-speed motors, on the other hand, are not immediately adaptable to digital techniques. Nevertheless, even in this latter case digital designs are widely applied, by the method of converting from analogue signals to digital, and from digital to analogue, before and after the signal processing stages, respectively. The reward is improved system reliability and, often, greatly simplified circuitry, which equates with low cost.

Ultimately, we reduce each problem to a set of logic signals, each one of which we term a bit (of information or data). These bits may individually represent the state of an external device (switch, motor etc on or off) or collectively represent a number or variable, such as would be derived from an analogue to digital conversion process. In this latter case, and particularly when using microprocessors, it is usual to collect and process data bits in groups of a fixed number; most of the common microprocessors handle data in groups of eight bits and each group is called a 'byte'. We can use a byte to represent a maximum of 256 numbers, using binary representation. For example, 10010110 is the binary representation of the number 150; it is worked out by assuming that the left most bit (the Most Significant Bit or MSB) has a value of 128 (when set at logic 1) and that bits to the right are half the value of their left-hand neighbours, down to a value of one for the right or Least Significant Bit (LSB) Thus:

$$10010110 = (1 \times 128) + (0 \times 64) + (0 \times 32) + (1 \times 16) + (0 \times 8) + (1 \times 4) + (1 \times 2) + (0 \times 1)$$

There is one other number system that some microprocessors use, in addition to binary, which is called Binary Coded Decimal (BCD). In this system, a byte is notionally separated into two four-bit fragments each of which represents a decimal number, eg 0011, 1001 = 2 + 1, 8 + 1 = 3, 9 = 39. Binary codes higher than 1001 are invalid in BCD and should never occur.

Rarely will you see lists of binary encoded data appearing in print; a much more compact system of notation, called Hexadecimal, is usually applied. In Hexadecimal notation, each of the four bit fragments of the byte are replaced by one of sixteen characters as listed below:

0000 = 0	1000 = 8
0001 = 1	1001 = 9
0010 = 2	1010 = A
0011 = 3	1011 = B
0100 = 4	1100 = C
0101 = 5	1101 = D
0100 = 6	1110 = E
0111 = 7	1111 = F

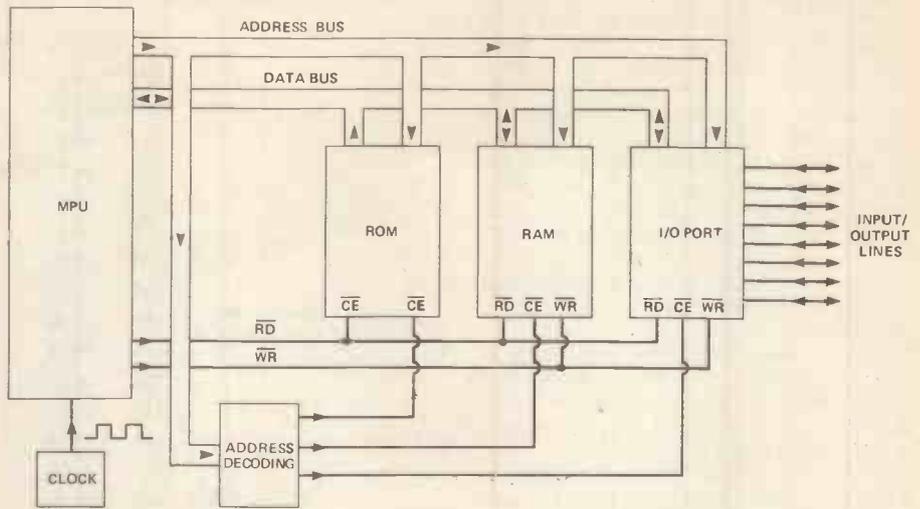


Figure 1. A simple microprocessor system for controller applications.

Hexadecimal and binary are very easily interconverted, eg:

$$01011101 = 0101\ 1101 = 5D$$

$$10101011 = 1010\ 1011 = AB$$

The Microprocessor

The block diagram, Figure 1, shows a minimum-hardware microprocessor system that would be used for industrial controller applications. The main components of the system are a Microprocessor Unit (MPU), a Read Only Memory (ROM), a Random Access Memory (RAM) and an Input/Output device (I/O port).

The RAM is used, essentially, to store the data which is being processed by the MPU. It is internally organised as a number of locations (typically 1024), each of which may store a single byte of data. Any of these locations may be selected at random, ie addressed, so that data may be 'read' from the location without altering it or written into the location, thus changing it. A RAM chip which has 1024 byte capacity (eg, Mostek MK4118) will have ten input terminals called 'address lines' which select between the locations (a ten bit binary number has 2¹⁰ possible values, ie 1024).

The ROM has a similar organisation to the RAM, except that the stored data has been fixed at the time of manufacture and cannot be altered or written into during normal operation. There is, however, a very popular variation of this device called an EPROM (Electrically Programmable Read Only Memory) which is programmed using a high voltage (+25V) and erased with a source of UV light; there are several machines on the market designed to program these devices. Data which is stored in the ROM, in this application, is called 'Firmware' or, more generally, 'Software'. It is interpreted by the MPU as instructions or commands and therefore controls the operation of the entire system.

Finally, the system has an I/O port — or several I/O ports — which interface the MPU to the outside world. Each of

the I/O lines, which are normally programmed as either an input or an output, will connect to any of the external devices (switches, motors, valves etc) devices discussed earlier, via suitable buffering such as a transistor or relay, of course.

All of these components are interconnected by two main buses (a set of lines carrying parallel data), namely the address bus and data bus. Data can be transferred between the MPU and any other device, in both directions (bi-directional), along the data bus. Addresses are placed on to the address bus by the MPU in order to select a particular memory device and location within that device. The address decoding logic uses high-order address bits to determine which of the devices is to be accessed and selects the appropriate device by pulling its Chip Enable (CE) pin to logic zero. This will be explained in detail next month, so for the moment let's just say that each device is selected by a unique range of address numbers. An active low Read Line (RD) or active low Write Line (WR) indicates to the selected device the direction of data transfer on the bi-directional data bus. These two signals, together with the chip enable lines, are often referred to as the control bus.

The 1802

The remainder of our discussion on the operation of microprocessors will be with specific reference to the RCA 1802. This device, which is used in our Micro Trainer project, has been chosen as a good MPU for controller applications and, more importantly, for its relatively simple instruction set. Also, it illustrates most of the techniques that apply to the more common eight bit MPUS such as the Z80 and 6502 and, therefore, is an excellent starting point for learning about microprocessors.

Looking firstly at the 1802 pin assignment diagram of Figure 2, you should be able to identify the data bus (D0-D7) the address bus (A0-A7), the control signals RD and WR, the clock input and the power supply connections VDD, VCC

and VSS. The address outputs, in fact, provide 16 address lines, giving a total addressing capacity of 65536 (64K) bytes, however, they are time-multiplexed onto just 8 lines. As will be seen later, the most significant byte of the address lines must be first loaded into an 8 bit latch, timed by signal TPA (pin 34), allowing the least significant byte to then appear on pins 25-32. Apart from the CLEAR signal, used to reset the MPU after power-up, the remaining signal lines are not required in the simple design of Figure 1, therefore do not worry about them too much, at this stage.

Before describing the sequence of operations that cause the data transfers to and from the MPU (which are called bus cycles, incidentally) we need to take a look inside the 1802 itself.

The model of the 1802 MPU shown in Figure 3, reveals everything that the user or programmer needs to know about the internal architecture of the device, ie the registers that store data within the MPU. There are 16 registers of 16 bits, each able to store 2 bytes of data (the high byte is designated R.1 and the low byte R.0). More important than data storage, these registers will also hold 16 bit addresses, pointing to instructions and data stored in the external memory system. There are, additionally, two 4-bit registers X and P, which may contain any value from Hex 00 to Hex 0F, and they assign a special meaning to the register to which they point. The Program Counter, R(P) points to the address from which the MPU fetches data or instructions. After resetting the machine (by a low pulse applied to the CLEAR input) the program counter is always R.0 and has an initial value of 0000H. The index register, R(X), points to data in memory during some arithmetic, logic or transfer operations. All arithmetic and logic operations produce an eight bit result which is placed in the Accumulator (AC). This has an associated Carry Flag (CF), which is a one bit register indicating, for example, an overflow condition arising from certain arithmetic operations. The temporary register (T), the Interrupt Enable flag (IE) and the Q flag will be explained in later issues.

The 1802 MPU carries out instructions in a sequence of two bus cycles, the 'fetch cycle' followed by the 'execute cycle'. A high frequency (2 MHz) clock applied to pin 1 of the MPU provides the timing necessary for these cycles; in fact there are eight clock periods to one bus cycle and all other timed signals, such as WR or RD, are also referenced to the clock. If we assume that the MPU has just been released from a reset condition (CLEAR taken high), the MPU will read its first instruction, from the initial program counter address of 0000H, in the first fetch cycle. This instruction, having been interpreted by the MPU will initiate an execute cycle which will do exactly that which RCA promise it will do, by means of the MPU's internal operation, which is of no real concern to us, the users. In this execute cycle, the MPU may output the address of any of the 16 bit registers to fetch a further data byte from memory, although many of the instructions act on

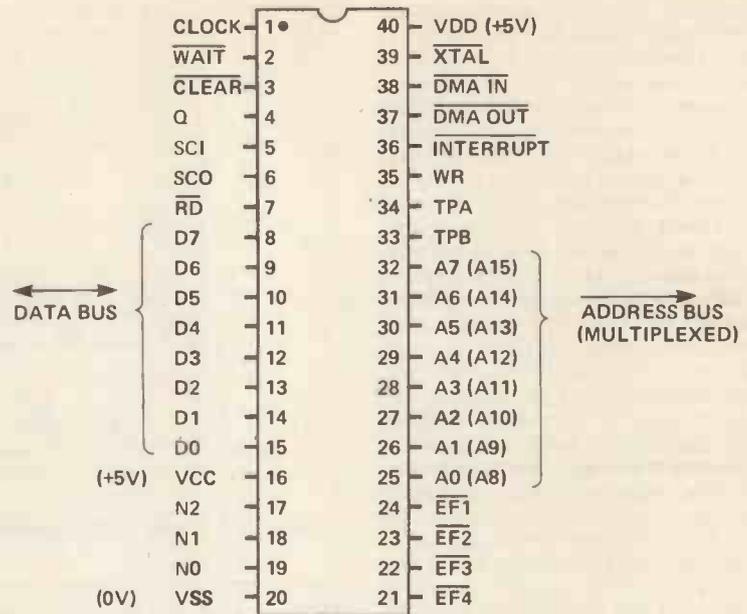


Figure 2. The pin designations of the 1802 microprocessor.

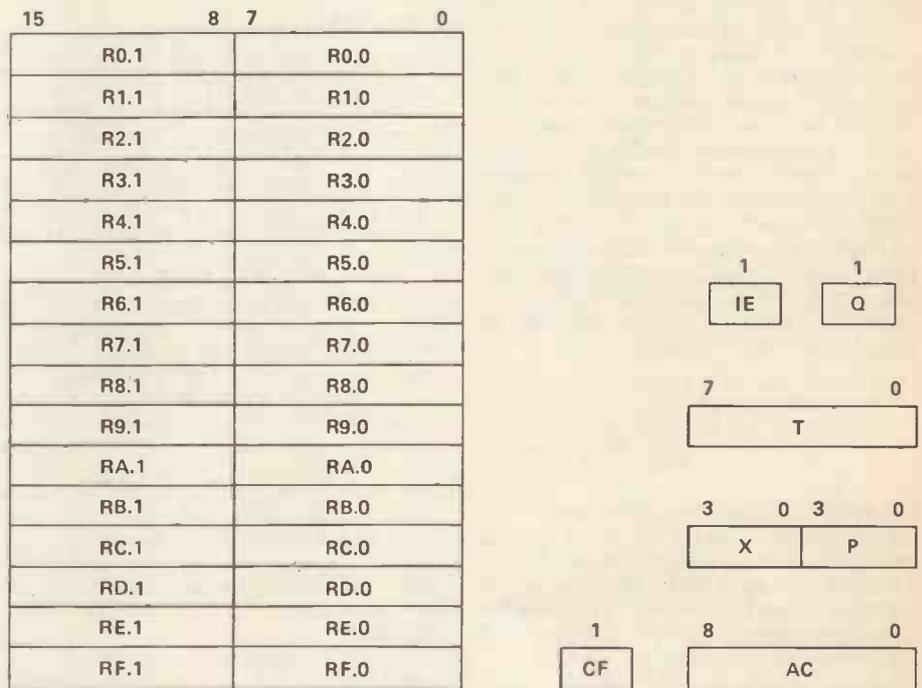


Figure 3. A programming model of the 1802. This is not the 'architecture' of the MPU but a model of how the processor 'appears' to the programmer.

the MPU's internal registers alone and therefore have a so-called non-memory execute cycle.

A comprehensive list of the 1802's instruction set appear in Table 1, in which we give the Hexadecimal machine code instruction, functional description of the instruction and the associated mnemonic that one would use in writing machine code programs. The precise meaning of all these will be made clearer in later examples, although we also

strongly recommend the purchase of RCA's "User Manual for the CDP1802 COSMAC Microprocessor".

The set includes instructions for transfers between registers and accumulator and between accumulator and memory, arithmetic and logic operations on data in the accumulator and instructions which alter program flow control (branches) and numerous special instructions. We will discuss all these categories at a later date, however here

are a few examples to whet your appetite:

16 (mnemonic, INC R6) when fetched, will cause '1' to be added to the 16 bit value of register 6.

F4 (mnemonic, ADD) will cause the byte of data pointed to in memory, by the index register, to be added to the value stored in the accumulator and the result placed in the accumulator.

32 (mnemonic BZ) followed immediately by a single data byte, will cause that byte to be copied into the low-order half of the program counter if the accumulator has a zero value, otherwise execution will continue with the next instruction.

This latter instruction is used to generate a loop in the program and is termed a 'branch'; in this case a conditional branch. After each instruction execution, the program counter normally advances automatically to the next instruction. The specimen (useless) program below should illustrate these points:

Address	Code	Mnemonics
00000	16	INC R6
00001	30	BR 00
00002	00	

This will cause register six to count from 0000 to FFFF, ad infinitum!

If you have followed all this so far, and are beginning to wonder where the edges of the page merge with reality, do not despair; our applied examples, in later issues, will make things clearer, particularly if you build our Micro Trainer, which will enable you to try things out for yourself.

The HE MicroTrainer has been designed for Hobby Electronics readers by Paul Kelly and will only be available as a complete kit from Technomatic Ltd. The MicroTrainer has been developed as a powerful teaching tool — but it also has many other uses and offers many advantages over existing development kits:

- LOW COST
- SIMPLE CONSTRUCTION
- HIGH QUALITY DOUBLE-SIDED, THOROUGH-HOLE PLATED PCB
- MODULATED VIDEO OUTPUT RATHER THAN LED DISPLAY
- DISPLAY SHOWS EITHER 32 BYTES OF PROGRAM MEMORY OF THE COMPLETE SET OF 1802 REGISTERS
- UNIQUE SINGLE-STEP FEATURE
- SINGLE LINE MNEMONIC DECODES CURRENT INSTRUCTION
- 20-KEY PAD FOR DATA ENTRY AND COMMANDS
- 1.5 KBYTES ON-BOARD MEMORY FOR USER PROGRAMS
- CASSETTE 'SAVE' AND 'LOAD' INSTRUCTIONS
- LEARN BY BUILDING
- OPTIONAL 24-LINE I/O PORT
- VERSATILE CONTROLLER FOR EXTERNAL SYSTEMS

HE

IDL	00	Wait for interrupt or DMA request	SHLC	7E	Shift left with carry (accumulator)
LDN	0N	Load accumulator, via register N	SMBI	7F	Subtract with borrow, immediate data from accumulator
INC	1N	Increment register N	GLO	8N	Load accumulator with low order byte of register N
DEC	2N	Decrement register N	GHI	9N	Load accumulator with high order byte of register N
BR	30	Branch always	PLO	AN	Store accumulator in low order byte of register N
BQ	31	Branch if Q = 1	PHI	BN	Store accumulator in high order byte of register N
BZ	32	Branch if accumulator is zero	LBR	CO	Long branch always
BPZ	33	Branch if positive or zero	LBQ	C1	Long branch if Q = 1
B1	34	Branch if EF1 = 0	LBZ	C2	Long branch if accumulator is zero
B2	35	Branch if EF2 = 0	LBPZ	C3	Long branch if positive or zero
B3	36	Branch if EF3 = 0	NOP	C4	No operation (long skip never)
B4	37	Branch if EF4 = 0	LSNQ	C5	Long skip if Q = 0
BRN	38	Branch never	LSNZ	C6	Long skip if accumulator not zero
BNQ	39	Branch if Q = 0	LSMI	C7	Long skip if minus
BNZ	3A	Branch if accumulator not zero	LSKP	C8	Long skip always
BM	3B	Branch if minus	LBNQ	C9	Long branch if Q = 0
BN1	3C	Branch if EF1 = 1	LBNZ	CA	Long branch if accumulator not zero
BN2	3D	Branch if EF2 = 1	LBMI	CB	Long branch if minus
BN3	3E	Branch if EF3 = 1	LSIE	CC	Long skip if IE = 1
BN4	3F	Branch if EF4 = 1	LSQ	CD	Long skip if Q = 1
LDA	4N	Load accumulator, via register N, then increment register N	LSZ	CE	Long skip if accumulator zero
STR	5N	Store accumulator in memory, via register N	LSPZ	CF	Long skip if positive or zero
IRX	60	Increment index register	SEP	DN	Set program counter to register N
OUT	6N (N = 1, 7)	Transfer via index register to output device N, then increment index register	SEX	EN	Set index register to register N
***	68	Illegal instruction	LDX	FO	Load accumulator via index register
INP	6N (N = 9, F)	Transfer to accumulator from input device (N-8), then store via index register	OR	F1	Logic OR, memory with accumulator, via index register
RET	70	Return from interrupt or subroutine	AND	F2	Logic AND, memory with accumulator, via index register
DIS	71	Return from interrupt with interrupts disabled	XOR	F3	Logic XOR, memory with accumulator, via index register
LDXA	72	Load accumulator, via index register, and increment index register.	ADD	F4	Add memory to accumulator, via index register
STXD	73	Store accumulator in memory, via index register, and decrement index register	SD	F5	Subtract accumulator from memory, via index register
ADC	74	Add with carry, via index register, to accumulator	SHR	F6	Shift right accumulator
SDB	75	Subtract with borrow, accumulator from memory, via index register	SM	F7	Subtract memory from accumulator, via index register
SHRC	76	Shift right with carry (accumulator)	LDI	F8	Load accumulator with immediate data
SMB	77	Subtract with borrow, memory from accumulator, via index register	ORI	F9	Logic OR, accumulator with immediate data
SAV	78	Save T register in memory, via index register	ANI	FA	Logic AND, accumulator with immediate data
MARK	79	Push X, P registers on stack, via index register	XRI	FB	Logic XOR, accumulator with immediate data
REQ	7A	Reset Q flag to zero	ADI	FC	Add to accumulator, immediate data
SEQ	7B	Set Q flag to one	SDI	FD	Subtract accumulator from immediate data
ADCI	7C	Add with carry, immediate data to accumulator	SHL	FE	Shift left accumulator
SDBI	7D	Subtract with borrow, accumulator from immediate data	SMI	FF	Subtract from accumulator, immediate data

Table 1. 1802 Instruction Set (Mnemonics, Hexadecimal code and operations)

Memotech's New Memory System for the ZX81

It grows as you progress



Memopak 16K Memory Extension

- £39.95 incl.VAT

It is a fact that the ZX81 has revolutionised home computing, and coupled with the new Memopak 16K it gives you a massive 16K of Directly Addressable RAM, which is neither switched nor paged. With the addition of the Memopak 16K your ZX81's enlarged memory capacity will enable it to execute longer and more sophisticated programs, and to hold an extended database.

The 16K and 64K Memopaks come in attractive, custom-designed and engineered cases which fit snugly on to the back of the ZX81, giving firm, wobble-free connections. See below for ordering information.

Coming Soon...

A complete range of ZX81 plug-in peripherals
 Memotech Hi-Res Graphics
 Centronics Interface and Software Drivers
 Memotech Digitising Tablet RS232 Interface



All these products are designed to fit 'piggy-back' fashion on to each other, and use the Sinclair power supply. WATCH THIS SPACE for further details. We regret we are as yet unable to accept orders or enquiries concerning these products – but we'll let you know as soon as they become available.

How to order your Memopak.

By Post: Fill in the coupon below and enclose your cheque/P.O./Access or Barclaycard number.

By Phone: Access/Barclaycard holders please ring Oxford (0865) 722102 (24-hour answering service).

Please make cheques payable to Memotech Limited
 Please debit my Access/Barclaycard* account number

*Please delete whichever does not apply

SIGNATURE _____ DATE _____

NAME _____ ADDRESS _____

Memopak 64K Memory Extension

- £79.00 incl.VAT

The 64K Memopak is a pack which extends the memory of the ZX81 by a further 56K, and together with the ZX81 gives a full 64K, which is neither switched nor paged, and is directly addressable. The unit is user transparent and accepts basic commands such as 10 DIM A(9000).

BREAKDOWN OF MEMORY AREAS

0-8K ... Sinclair ROM

8-16K ... This section of memory switches in or out in 4K blocks to leave space for memory mapping, holds its contents during cassette loads, allows communication between programmes, and can be used to run assembly language routines.

16-32K ... This area can be used for basic programmes and assembly language routines.

32-64K ... 32K of RAM memory for basic variables and large arrays.

With the Memopak 64K extension the ZX81 is transformed into a powerful computer, suitable for business, leisure and educational use, at a fraction of the cost of comparable systems.

Unique 3 month trade-in offer!

When your programming needs have outgrown the capacity provided by 16K RAM, and you find it necessary to further extend your ZX81's capacity, we will take back your 16K Memopak and allow a discount of £15.00 against your purchase of our 64K model.*

*We reserve the right to reject, for discounting purposes, units which have been either opened or damaged in any way.

Please send me:

	Quantity	Price	Total
16K RAM, Assembled		£39.95	
64K RAM, Assembled		£79.00	
		Postage	£2.00
		Total Enclosed	

HE6

We want to be sure you are satisfied with your Memopak – so we offer a 14-day money back Guarantee on all our products.
 Memotech Limited, 3 Collins Street, Oxford OX4 1XL, England Telephone: Oxford (0865) 722102/3/4/5

ZX 81 64K RAM PACK

IF there is one indisputable drawback to the ZX-81 it is its lack of memory. The basic machine has a mere 1K of user RAM (Random Access Memory) and this is quickly eaten up by program lines. Ironically, it is the less experienced computer enthusiast who requires the larger amounts of memory. Once you have become a little practised in the art, it is relatively easy to produce more efficient programs, ie those which take up less memory.

The Sinclair add-on pack offers 16K of RAM at a price comparable with that of the computer. For a large number of home users, this amount of memory will suffice for quite a time. Fairly ambitious creations can be undertaken within the confines of 16K! However, anyone who wishes to use his Sinclair for any form of data handling — address lists, stock control, etc, would very quickly run out of space and could end up sending 100 letters to himself — because that's the only address the computer had room to store.

Memories Are Made Of This

The Memotech 64K RAM is designed to overcome this problem. First let me say that there is only 56K of actual memory present in the box itself. Presumably the 64K legend is derived from the fact that the pack expands the ZX81 to 64K and not by 64K. Furthermore, the 56K is divided up, to make it more usable for programs requiring large amounts of data. Sinclair complicate things, however, by designing their hardware so that the section of memory that holds all the screen characters has to be positioned somewhere within the first 32K of memory that the ZX-81 finds itself hooked up to. The diagram of Figure 1 gives an idea of what the various parts of the total 64K can be employed for.

When referring to large amounts of memory it is usual to refer to the position of something within it by the number of locations the computer has to count through to reach it (a 'location' is simply a place to store a byte — eight bits — of information). For example, if the Sinclair stores a particular screen character in the 32,000th location it could have used, then that character "resides" at 32K.

Somewhere A Place For Us?

Using this terminology then, your BASIC programs reside between 16K and 32K, with arrays and variables from 32K upwards. The locations between 8K and 16K can be switched in and out of the overall plan, using little DIL switches on the back of the expansion pack. In addition the top 4K of this, between 12K and 16K, is protected against being cleaned out when you load another program from tape.

Routines can thus be appended

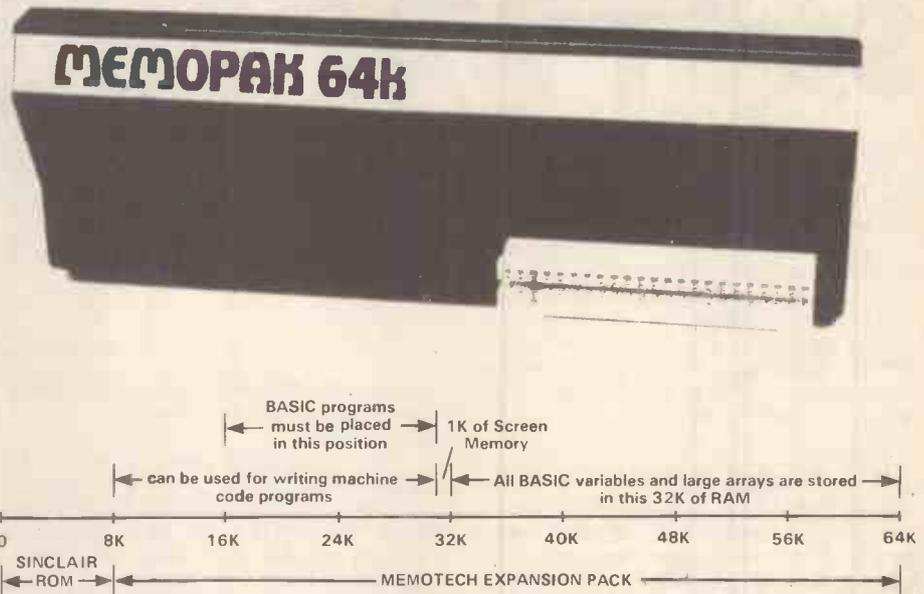


Figure 1. The layout of the 64K of memory available to the ZX-81 when used with the Memotech 64K RAM pack. Note that only about 15K is actually usable for BASIC program text. Note also, however, that 32K more is reserved for storing all the variables used in your programs and for large arrays of information. That 15K is thus actually far more powerful than it might seem!

together, further extending the possibilities of the computer. As with Sinclair's own expansion, the Memotech plugs directly onto the back of the ZX-81 and requires no leads. It is beautifully made and looks very much at home with the computer. The printer can be connected to the reverse of the pack plug too, making it "stackable".

Included with the box are a couple of the ubiquitous "sticky pads", apparently recommended to attach the machines together. Pretty strong things these, so beware — what Memotech hath joined together, no man shall put asunder. Not easily anyway.

The DIL switches which control the 4K 'blocks' of switchable RAM are accessible through a hole in the back panel of the case. Most users will probably set them to obtain maximum RAM — and leave them there. Business users might be tempted to have a dabble, in which case they're going to need a pretty small screwdriver to keep toggling them back and forth.

Down Memory Lane

In use, the 64K is simple to operate. Upon switch-on, the usual little 'K' appears in the bottom left of the screen. The ZX-81 thinks it has 16K connected to it. This is where it gets a surprise. Type:

```
POKE 16388, 255
POKE 16389, 255
NEW
```

It will now *have* to believe that 56K has, in fact, been added to its capabilities,

since you have just modified the locations in the memory where it stores the value of RAM in use.

If for some reason you do not wish to use all the memory space available to you, the Sinclair manual notes (Chapter 26) still apply and will work in this case. The available BASIC space is, as previously explained, around 15K-16K but in practise, that 32K of extra storage is brought rapidly into play. It is especially useful for programs such as mailing lists where the information to be handled by the program takes up more space than the actual program listing itself. If you reset the ZX-81, then the machine will lose all knowledge of any memory space beyond 32K. You have to POKE back in again to locations 16388 and 16389 as outlined previously, to remind it that other locations are available.

Conclusions

Whether or not you will find the Memotech 64K RAM value for memory, at £79, will depend largely upon your application for a ZX-81. At £30 more expensive than the Sinclair expansion, it is better engineered, more versatile, and capable of much greater storage. It does not actually contain 64K RAM and I think that title is a little misleading. This is an expansion to 64K and is more properly referred to as a 56K RAM pack.

Users wishing to try their hands at some more workman-like applications for the Sinclair will find the Memotech very useful, if not indispensable. The out-and-out home user will have to weigh the added cost very carefully.

ZX 81 SOFTWARE

THE ZX-81 and the ZX-80 before it have, without question, revolutionised the awareness of the computer in the home: not only as an introduction to computing, but as a teaching tool and also as a fun thing to play with.

Hopefully, we will be looking at software that will enable the ZX-81 to control its external environment — but that still lies a little way in the future. For the present let us look at some of the software available *now*.

ZX Software

Where better to start than with some of the tapes promoted by Sinclair themselves. There are six of these available at the present and we will look at three of them, first of the series is 'Games of Skill', Sinclair Cassette No. 1. This has six programs, three on each side of the tape, and will run in 1K of memory so no extra RAM pack is required.

ORBIT uses fairly simple graphics to represent a spaceship orbiting a star (planet?) and a valuable piece of cargo which the spaceship has to 'capture'. You may manoeuvre your spaceship by altering the distance of the orbit around the star and when you get the ship in the right position over the cargo, the cargo will enter the ship and you will be informed how many days (!) it has taken you to dock. The game can be somewhat frustrating and, because of this, one tends to persevere a number of times, trying to better the previous score. On the whole, the game leaves one with the feeling that control of the situation is not perhaps as easy or definitive as one would like but, although I suspect that I will go back to this game occasionally, I am unlikely to become addicted.

SNIPER displays forty men, one at a time, at different positions across the screen. Your task is to quickly determine at which of the ten possible positions the man is displayed and, within the brief interval that he is visible, 'shoot' him with the appropriate position key (1, 2, 3, 4, 5, 6, 7, 8, 9 and 0). Your score appears continuously throughout the game but not at the end (pity that). The graphics are simple but quite effective; a good game for young kids as speed and co-ordination are called for. The average adult should be able to master this one very quickly.

METEORS places you in control of a spacecraft that appears at the top of the screen; a storm of meteors approaches you from the bottom of the screen. Your task is to steer your craft through them without collision. Each collision reduces your 'life' and you have five 'lives'. On the fifth collision, the game ends and the distance you have travelled (in light years) is displayed on the screen. A

thoroughly enjoyable game to play with simple but effective graphics . . . could be addictive.

Side B of the cassette has LIFE, WOLFPACK and GOLF. LIFE is based on the 'Game of Life' devised by J.H. Conway, in 1970, and represents the growth and decay of cells. Their 'life' is determined by the following rules: 1). If a space is empty and there are three and only three adjacent live cells, a new cell is born in that space. 2). If a cell has two or three neighbours, it survives. 3). any cell with only one neighbour or more than three neighbours dies. The implementation of LIFE on the 1K Sinclair is a credit to the programmer. You may place cells anywhere on a 16 x 16 grid and watch the outcome as generation follows generation. Altogether a fascinating display. Some patterns remain constant but move across the screen; some will develop into stable oscillating patterns while some will die out after only a few generations. A good example, considering the size of memory and the size of the screen.

In WOLFPACK you have control of a destroyer and you may move left or right and drop depth charges. The aim being to hit the enemy submarine travelling below you. Reasonable skill is required to judge when and where to drop the depth charge.

GOLF was a disappointing game that would be much improved if the ball progressed down the fairway, instead of always returning to the tee.

Sinclair cassette No. 5 is entitled 'Junior Education' and has six programs running in 1K.

Kid Stuff?

MATHS gives you the option of problems involving addition, subtraction, multiplication and division. You are then given 10 problems to answer and, after this, your score out of ten is displayed. This is a straightforward program, certainly improving your mental arithmetic (I needed a pencil and paper!).

BALANCE deals with your appreciation of couples and levers. You are offered difficulty levels of 1-3; a graphic representation of a see-saw is displayed with a weight at a distance from the pivot on one side — you have to decide what weight, at a specified distance on



the other side, is needed to balance the first weight. Again, a pencil and paper is handy for level three . . . my mental arithmetic isn't what it was!

VOLUMES provides a graphic representation of a cube displayed on the screen, with its dimensions; you have to enter the correct volume. There are two levels of difficulty and, on this one, you have to make a note of your score as this is not displayed.

AVERAGES is a program intended to help you understand the concepts of MEAN and MEDIAN and it will draw a bar graph to help you understand! The program will accept up to 50 entries, with the maximum value of any entry being 1,000. The bar graph is crude but the more entries there are, the cleaner the intention of the display becomes. Sadly, this program is not protected against a value outside the previously specified limits and will CRASH so be warned — think before you type. A useful teaching exercise, this one, but one where the data should have been collected before RUNNING the program, for it to have maximum impact.

BASES will test your ability to convert from decimal (base 10) to other bases in the range two to nine. My mind is still reeling. I'm glad I tried this one after my son had gone to bed. Base two is reasonable — even I could interpret decimal 17 as 10001 — but when it comes to 72 in base seven (1381) or 69 in base three (2112) I am beginning to flounder without my trusty pencil and paper. But, having put pencil to paper, I found that this program occasionally gave the wrong answers! The two examples above being a case in point: 72 in base seven should be 132 and 69 in base two should be 2120!

The TEMP program displays two barrels full of water. Each barrel has its volume displayed in litres and its temperature in degrees centigrade and you have to calculate the temperature that would result if the two barrels had their contents thoroughly mixed together. Answers have to be correct to 0.001 degrees C for you to be 'correct' . . . well, obviously you need pencil and paper for that . . . don't you?

The Sinclair cassette tapes tried so far all load easily and have given us a great deal of fun, even if I feel I should go back to 'skool' for a refresher course! **HE**

Hobby Electronics

BACKNUMBERS

TWO NEW FEATURES & CR NEWS INSIDE
Hobby Electronics
May 87
60p
For A Down-To-Earth Approach To Electronics



February 1980
Passion Meter, Win Indicator, Short Circuit Special, Kit Review Special, Into Electronics Construction Part 1.

September 1980
MicroMixer, Reaction Tester, Guitar Phaser, Development Timer, Teletext Explained, Into Digital Electronics Part 1.

April 1981
Pre-Amplifier Part 1, Super Siren, Guitar Tremolo, Russian Roulette Game, Doorbell Monitor, Anatomy of a Space Shuttle.

May 1980
MiniClocks, 5080 Preamp, Model Railway Track Cleaner, 5080 Loudspeakers, Loudspeaker Crossover Design, Radio Controlled Model Survey.

October 1980
Kitchen Timer, Tug 'o' War Game, Light Dimmer, Freezer Alarm, Intruder Alarm, Temperature-Controlled Soldering Iron.

May 1981
Electronic Organ, Voice-Operated Switch, Infra-Red Controller, Pre-Amplifier Part 2, Audio Millivoltmeter.

June 1980
Microbe Radio Control System, Egg Timer, Two Watt Amplifier, Fog Horn, Short Circuits, LEDs and LED Displays.

January 1981
Car Rev-Counter, Bench Amplifier, Sound-Into-Light Converter, Chuffer, Electronic Games reviewed.

June 1981
Power Amplifier Part 1, Continuity Checker, Envelope Generator, Early Radio, Gadgets, Games and Kits Supplement.

July 1980
Sound-Operated Flash Trigger, 18+18 Car Stereo Booster, Hazard Flasher, Electronics in Photography, Electronic Espionage, Piezo Electricity.

February 1981
Heartbeat Monitor, High-Impedance Voltmeter, Medium Wave Radio, Two-Tone Train Horn, Audio Signal Generator.

July 1981
Burglar Alarm, Doorbuzzer, Treble Booster, Electronic Aids for the Disabled, Power Amplifier Part 2.

August 1980
EquiTone Car Equaliser, Pass-The-Loop Game, Gaztec Gas Detector, OP-Amp Checker, In-Car Entertainment Survey, Introducing Microprocessors.

March 1981
Public Address Amplifier, Windscreen Wiper Controller, Bicycle Speedometer, Photographic Timer, Microcassettes.

August 1981
Electronic Ignition, Thermometer, Electronic Organ (final part), RPM Meter, Bench Power Supply, Radio Control Survey, Into Electronic Components Part 1.

All of the 1980 issues, except January and April, are still available together with the remaining issues from 1981.

All backnumbers cost £1.25 each. For those of you who only want copies of articles, we do offer a photocopying service. Each copy costs £1.25 and information as to its title and publication date should be given. Ordering backnumbers and photocopies could hardly be easier, just fill in the coupon, cut it out and send it to:

THE BACKNUMBERS
513 London Road,
Thornton Heath,
Surrey CR4 6AR.

OR

THE PHOTOCOPIES
Hobby Electronics,
145 Charing Cross Road,
London WC2H 0EE.

HOBBY ELECTRONICS BACKNUMBER ORDER FORM

Please send me the following items:

NAME

ADDRESS

Back issues at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

HOBBY ELECTRONICS PHOTOCOPY ORDER FORM

Please send me the following items:

NAME


ADDRESS

Photocopies of in the


..... issue at £1.25 each

I enclose £.....

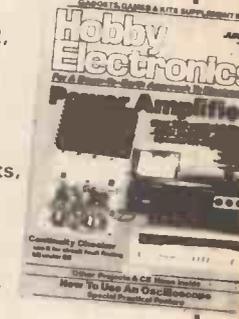Cheques and Postal Orders should be made payable to ASP Ltd.



DIGITAL COUNTERS and TIMERS

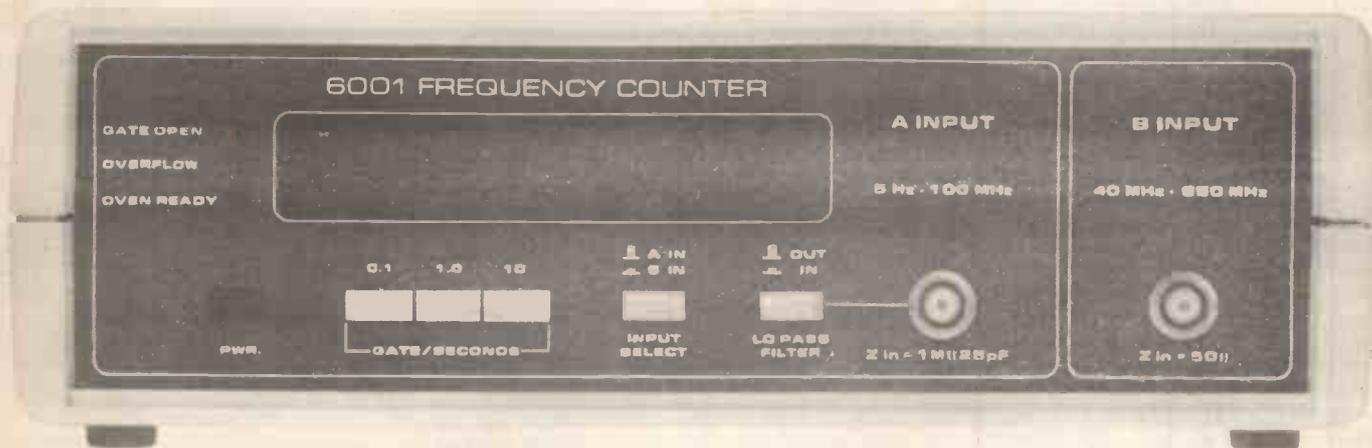

Several HE projects, recently, have used digital measurement techniques. This article explains the basic principles of digital timers and frequency meters.

MEASURING frequency and time intervals to a known accuracy is often important in many areas of electronics: in communications, broadcasting and audio applications, in digital work and particularly in computer applications — from micros to mainframes. Digital frequency meters (DFMs), or counter/timers as they are also called, have become such an essential item of test equipment that many manufacturers are offering a range of instruments ranging in price from a £100 instrument covering the range 20 Hz to 200 MHz to many thousands of pounds for a microprocessor-controlled instrument capable of measuring frequencies well into the gigahertz region and time intervals in the picosecond range.

Frequency and time interval measurement is an area where digital techniques come into their own. The object is to accurately quantify a measurement. Prior to the development of digital instrumentation to do this job, analogue techniques were used — often ingenious and highly refined, but laborious. Heterodyne frequency meters were used widely. These consisted of a stable, accurately calibrated, variable oscillator (VFO) driving one input of a wideband mixer, the unknown frequency being applied to the other input. The output of the mixer was monitored on headphones or an audio amplifier while tuning the VFO. As the unknown frequency was approached an audible 'beat note' would be heard, decreasing in pitch as the VFO was tuned closer to the frequency being measured. At 'zero beat' you could then read off the unknown frequency from the instrument's calibrated dial. The

method will no doubt be familiar to many of our older readers. It was laborious, especially when you didn't even know the 'ballpark' of the unknown frequency, and to get a measurement accuracy better than several hundred Hertz (... maybe that's cycles/second!) was tantamount to magic: Top frequency was about 20 MHz.

These days *pocket* DFMs can measure frequency to within ± 50 Hz or better, up to 200 MHz! That's at least a factor often better all round than the old BC221. And readout is obtained in a few seconds or less.

Time interval measurement was, and still is, very much left to that old workhouse — the CRO. But, a CRO has its limitations and quantifying a time measurement to the accuracies required these days is best done with a digital counter.

Frequency Measurement

The block diagram of a basic digital frequency meter is shown in the accompanying illustration. The input signal first encounters a 'trigger' or 'squaring stage' which ensures that the measurement always commences on the same part of the input waveform. The output of the trigger then enters a gate. The gate is 'opened' for a period and allows a number of input cycles through to the counter. The period for which the gate remains open is determined by the output from a divider/scaler driven by a very stable, accurate clock oscillator. A number of outputs from the

divider/scaler may be selected to vary the period the gate is open. Usually, a number of decade steps are provided.

The output of the gate drives a counter which provides a binary coded decimal (BCD) output for the display. A 'hold' or 'latch' stage is generally added so that a steady group of numerals is displayed.

The timing diagram below the block diagram illustrates the sequence of events. The input signal, often sinusoidal, is shaped by the trigger stage into a train of rectangular pulses. The gate allows a number of pulses through to the counter, in this case three, during the period it is 'open'. The circuit selects only the positive-going pulses in this example, though negative-going pulses from the trigger stage could equally well be used.

If, say, a gate period of one millisecond (1 mS) were selected the counter would display '3000'. In other words, the input frequency would be 3 kHz.

Practical instruments will have selectable gate periods ranging from one microsecond (1 μ S) to as much as 10 seconds. The display may have five digits, though eight digit displays are more common.

Many modern digital frequency meters incorporate a high speed divider immediately following the gate, the output of this divider being used to derive the first and second digits of the display. To extend the range of the instrument, a 'prescaler' may be included. This is a high speed divider providing a fixed division ratio of ten. Its output may drive either the trigger stage or the gate directly.

Period Measurement

Measuring the period between 'events' is done by re-arranging things a little. The gate, counter and display are used as before but the gate is turned 'on' and 'off' by the input events and the clock signal is passed through to the counter. As the clock is a highly stable, accurate oscillator, the period between input events can be measured with great precision. The accompanying block diagram shows the general arrangement of the instrument for period measurement.

Separate input signals in the arrangement shown are used to trigger the gate on and off. However, a single repetitive input signal may be used to trigger the gate with a slightly different circuit arrangement. The timing diagram with the period counter block diagram shows the sequence of events. If the clock was running at 1 kHz, for example, the time interval between pulses would be one millisecond. As 17 pulses passed through the gate in the example, the period between the A input event and the B input event was 17 mS and the display would read, say, 17 000 (resolution of one microsecond).


Pulse widths can be measured with a period counter, too. In this instance, the gate is triggered on the positive-going and negative-going edges of the input pulse. However, some difficulties arise. If the input pulse had a perfectly 'square' shape, the on and off gating points would always give an accurate result because the triggering transitions would occur precisely on the rise and fall of the pulse. Trigger level would not affect the interval measured. Real-life pulses however, are seldom perfect, the edges having definite rise and fall times. In this case, the trigger level becomes critical in determining the width of a pulse. The diagram here shows why and how it is overcome. Counters are usually provided with a 'slope selection' control which determines whether the trigger operates on the positive or negative slope — (a), or (b) respectively in the diagram.

Noise Error Reduction


The above descriptions give the basic operating modes of the various counter/timer/frequency-meter combinations. In practice, a number of refinements may be incorporated to obtain better practical performance.

Noise can be reduced by incorporating a fixed amount of backlash in the trigger circuit; this produces what is called the 'trigger window'. On the way up the trigger level is at a higher level than on the way down, as shown in the Trigger Window Diagram here. Provided the noise added to the signal has an amplitude smaller than the window width, the counter will only trigger once on the way up and once on the way down. This method works well for high-frequency measurements where the noise is usually a small percent of the signal-plus-noise amplitude.


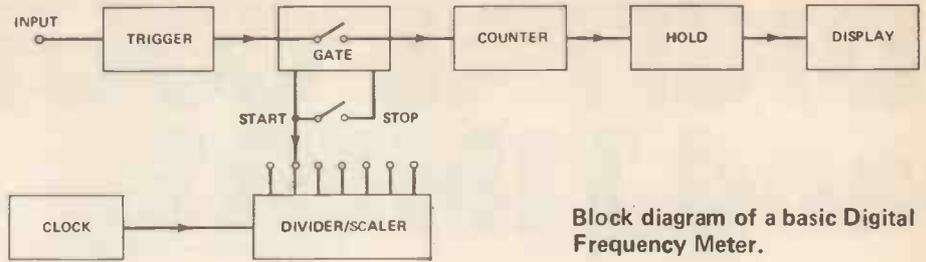
Low frequency measurements can often involve interference sources that



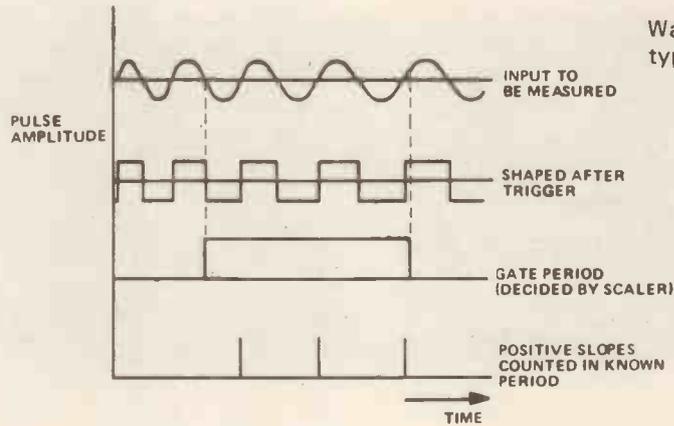
Block diagram of a basic Digital Frequency Meter.




Waveforms produced by a typical DFM.

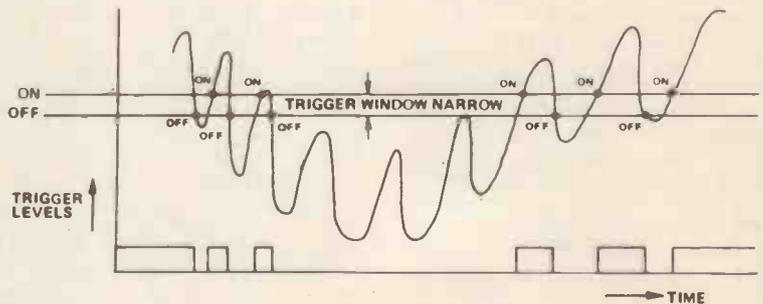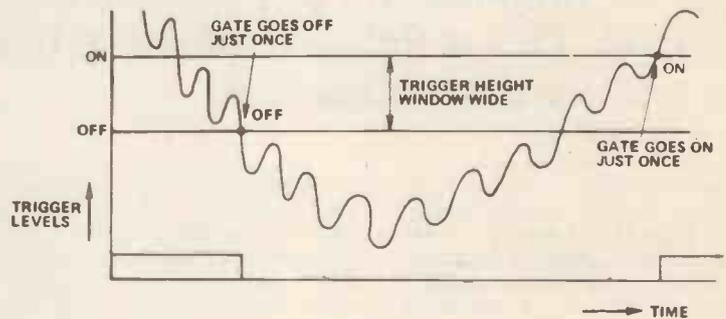

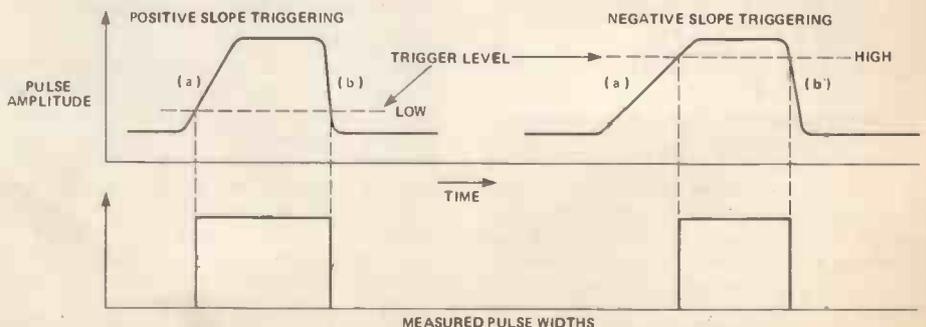
The Trigger Window diagram. Setting the Window too low (below) will cause inaccurate measurements.



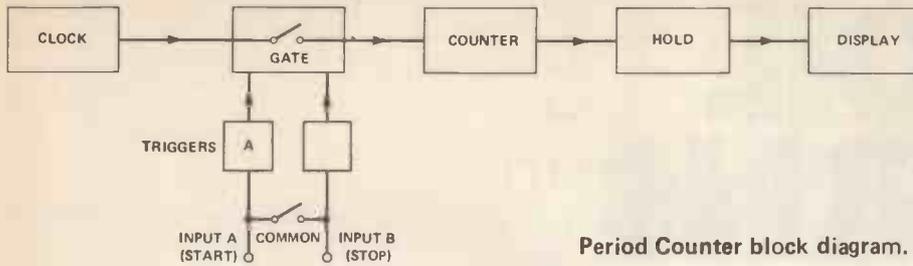
When measuring pulse widths, the accuracy will depend on whether positive or negative slope triggering is selected, and on the trigger level setting.



Period Counter block diagram.

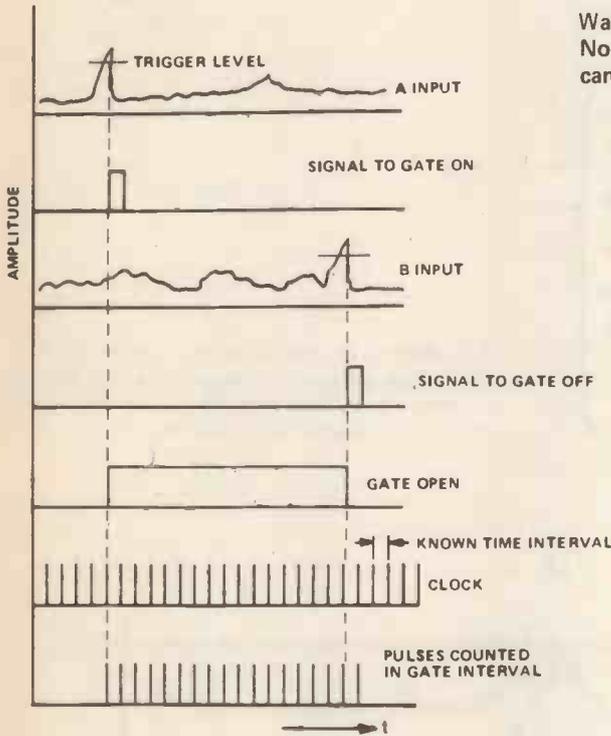

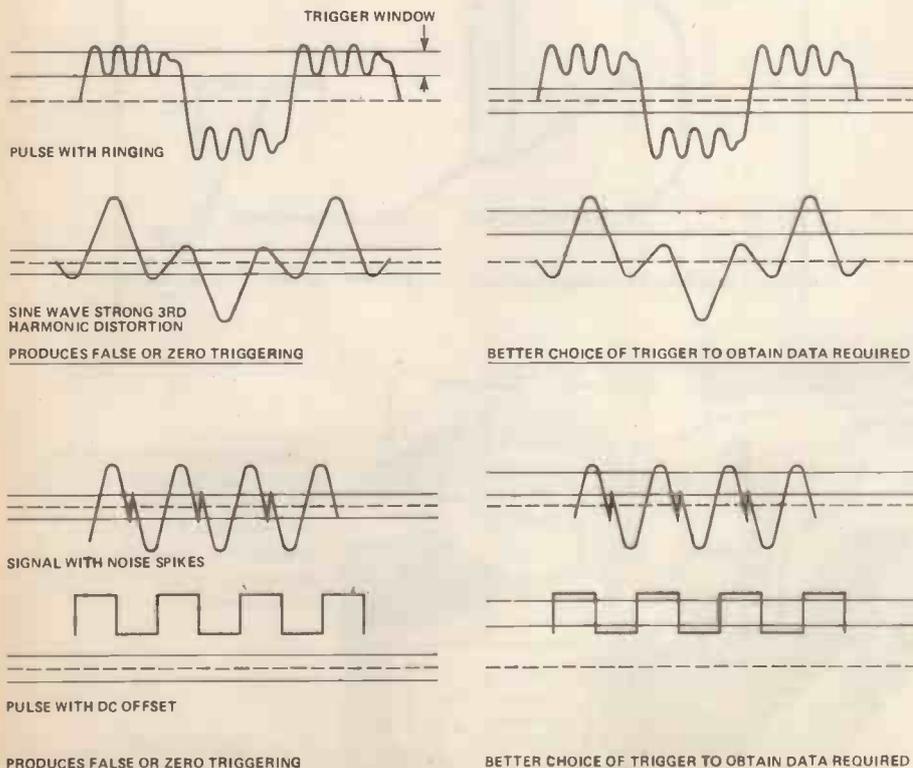Waveforms of a Period Counter. Note that input signals A and B can be the same.



The Trigger Window level can be set to reject false triggering caused by spurious signals (noise, harmonic distortion, ringing etc.) on the main signal.

produce rapid spike transients. One simple method of reducing this is to use filters. Advanced designs contain filter systems that reject all frequencies higher than that being tested, the appropriate filter being automatically selected by the counter itself after it has made a determination of the frequency of the signal.

A recent approach to the noise problem is to set up a time-window (as opposed to the trigger height window) that, once the counter gate is on, inhibits the off-state chance until after a time just shorter than the expected interval. This is known as trigger masking. It is very useful in eliminating contact-bounce retriggers.

Before using a counter/timer on an unknown waveform, it is good practice where ever feasible to look at the wave-shape on an oscilloscope in order to decide the best strategy for trigger-level and height-window width settings.

As the readout is in digital form it is necessary to hold the display at the determined value for a period long enough to allow the value to be read. Some units incorporate a control that gives the operator a choice of hold time.

How To Choose

First, look in your piggybank! Prices for a straight digital frequency meter start at around £70. Next step in the price/features bracket for a DFM is around £125. Instruments range right up to several thousand pounds, which is beyond most hobbyists!


Next step is to look at your applications. But, keep in mind future applications and get something a little better — if your budget will stretch that far. The number of digits in the display will certainly be a deciding factor, depending on your applications. The majority of instruments available have either six- or eight-digit displays. Next consideration is the number of ranges offered (gate time selection). Resolution is important and is related to the display, an eight-digit instrument has a better resolution than a six-digit instrument, naturally enough.

The clock oscillator stability determines the inherent accuracy of the instrument and it is instructive to compare the specifications of different makes and models when considering this parameter. Generally, a temperature range over which the accuracy is maintained will be quoted along with this specification. Accuracy will be quoted in parts-per-million (ppm) or parts in 10^n . A reasonable figure for accuracy, for most hobbyist applications, would be one ppm (one in 10^6) over a temperature range of 15°C to 50°C .

Whether you get a battery operated or a mains/battery operated instrument will depend largely on your applications.



Refinements like filters, trigger window control, gate time delays, frequency ratio, totalizing etc depend entirely on your application — and your budget!

PCB FOIL PATTERNS

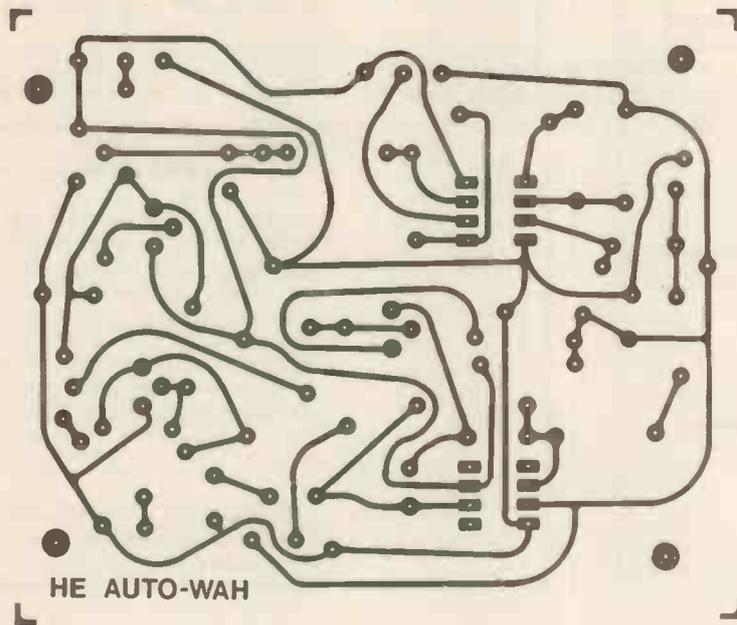

Foil pattern for the Auto-Wah (left). The large spots are to locate the PCB pillars — make sure the holes are the correct size, so that the board clips in place.

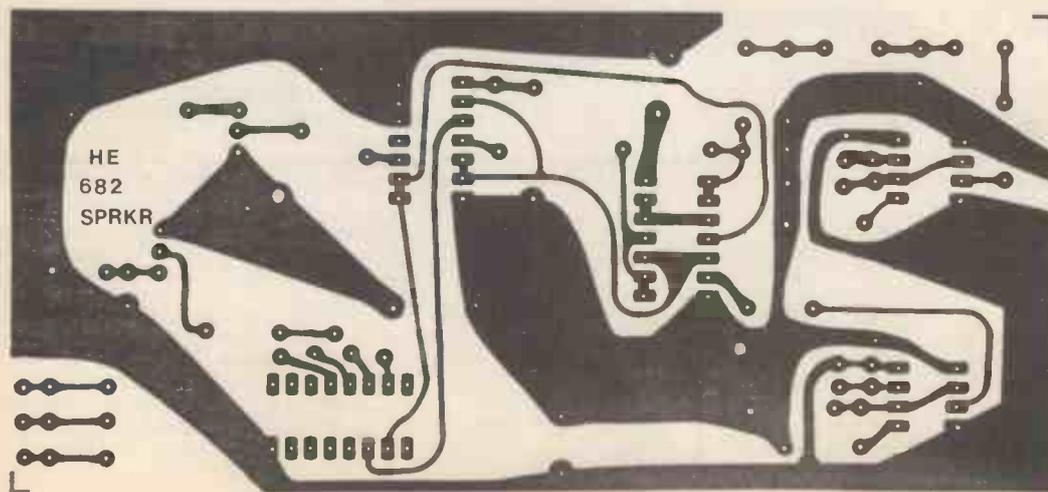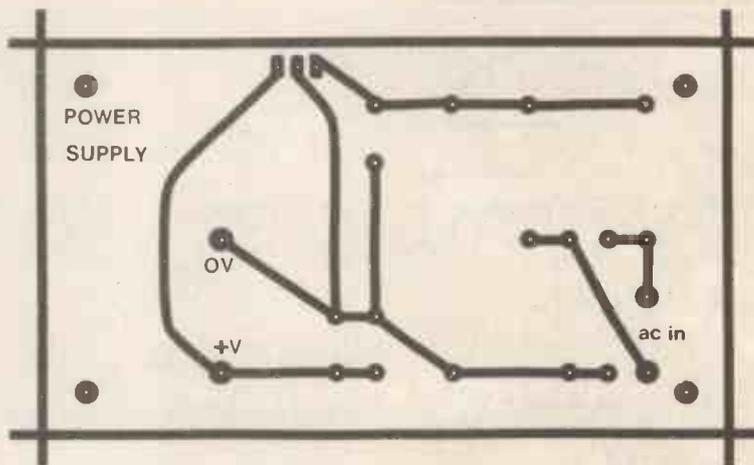The Power Supply Design PCB pattern (right). This board should present no problems, as the layout is not critical.



The HE Auto Greenhouse Sprinkler PCB pattern (left). The large areas of copper are present to improve stability — they can be omitted if you include C9 on the board.

RADIATION DETECTORS

BE PREPARED

VIEW THRU LENS

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture. Tested & fully guaranteed. Ex-stock delivery.

£6.95 inc. VAT
Post & Pack 60p

Ideal for the experimenter
COMPLETE WITH DATA

Henry's

404 EDGWARE ROAD, LONDON W2 1ED



PROGRAMMABLE GRAPHICS £19.95 (first ever for ZX80/1). Works with printer — no hidden bugs — edge connector not used. Repeating keymodule £3.45. Keyboard £17.50 (P&P £1.00). Edge connector £2.20. Inverse Video/I.O. Port/Memory/Colour (extended sheet available) POA.

ZX81 reverse graphics, white on black background, made from easily obtainable components. PCB and instructions £3 or SAE for details. R. Mitchell, 20 Gorse Close, Portslade, Sussex.

HAVEN HARDWARE (winner of the Daily Express/Philishave Business Award). ZX Kits (SAE for built prices/details), 4 Asby Road, Asby, Workington, Cumbria.

GUITAR/PA MUSIC AMPLIFIERS

100 watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50. 60 watt £44; 200 watt £66; 100 watt twin channel sep. treble/bass per channel £65; 60 watt £52; 200 watt £78; 100 watt four-channel sep. treble/bass per channel £75; 200 watt £98; slaves 100 watt £37; 200 watt £60; 250 watt £70; 500 watt £140; fuzz boxes, great sound, £12; bass fuzz £12.90; overdriver fuzz with treble and bass boosters, £28; 100 watt combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £100; twin channel, £115; bass combo £118; speakers 15m 100 watt £36; 12in 100 watt £24; 60 watt £18; microphone shure unidyn B £28.

Send cheque/P.O. to: **WILLIAMSON AMPLIFICATION**
62 Thorncliffe Avenue, Dukinfield, Cheshire. Tel. 061 308 2064

ANY SINGLE service sheet £1/L.S.A.E. Largest stockists service/repair manuals. Named T.V. repair data £6.50 (with circuits £8.50). S.A.E. pricelists. Free publications, quotations. Aushe, 76 Churches, Larkhall, Lanarkshire.

BUILT TRANSMITTERS £2.90. Receive on FM. Range 150yds. Refund Guarantee. (Unlicensable). P. Faherty, 37 College Dr., Ruislip.

PRINTED CIRCUIT BOARDS 4½" x 6" copper clad resin paper. 10 for £4.00 including U.K. post. Hill, 22-26 Bath Road, Worcester WR5 3EL.

SPARE PARTS For all digital watches. Batteries, crystals, displays etc. Send SAE for full list. Profords, Copnersdrive, Holmergreen, Bucks HP15 6SGE.

CLOSE ENCOUNTERS GROUP Personal introductions and social events. Meet interesting, attractive people. Local, 051-931 2844 (24 hours).

LOTS OF USEFUL ITEMS for constructors. Cases, transformers, P.C.B.'s etc. S.A.E. for list. Mr. Hyde, 3 Rosebery Road, Smethwick Warley, West Midlands B66 3R7.

BURGLAR ALARM equipment. Ring Bradford (0274) 308920 for our catalogue, or call at our large showrooms opposite Odsal Stadium. C.W.A.S. Ltd.

PARAPHYSICS JOURNAL (Russian translations); Psychotronic Generators; Kirliano-graphy, gravity lasers, telekinesis. Details: S.A.E. 4 x 9" Paralab, Downton, Wilts.

ELECTRONICS component shop in MAIDSTONE, KENTI Thyronics Control Systems, 8 Sandling Road, Maidstone, Kent. Maidstone 675354.

OSCILLOSCOPE £12. Easy built unit plugs into T.V. aerial socket and converts it to large screen oscilloscope. Costs approx. £12 to make. Circuit and plans £3. J. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

IONISER KIT (MAINS OPERATED)

This Negative Ion Generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions £12.50
A suitable case including front panel, neon switch, etc £10.50
Price includes Post & VAT Barclaycard/Access welcome

T. POWELL

ADVANCE WORKS
44 WALLACE ROAD, LONDON N.1.
TEL: 01-226 1489

Hours: Mon-Fri 9-5 p.m. Sat 9-4.30 p.m.

ADVERTISEMENT INDEX

Aitken Bros	57	ICS	73
Albrecht Elec GmbH	32	ILP	28
Ambit Int.....	2	Lightning Elec	73
Benning Cross Elec	22	Litesold	73
Bi-Pak	34	Magenta Elec.....	14, 15
BK Electronics	75	Memotech	64
BNRS	32, 54	Musicraft	54
J. Bull (Electrical)	42	Parndon Elec	54
Cambridge Learning	54	P.A.T.H.	30
Cricklewood Elec	30	Rapid Elec	8
Darom Supplies.....	34	Brian J Reed.....	32
Eda Sparkrite	76	Sandwell Plant	30
Electronize Design	30	Shetland Boats	52
Greenweld Elec	34	Silica Shop	5
Global Spec Corp	47	Technomatic	24
Heath Electronics	14	Watford Elec	52



MULLARD SPEAKER KIT

40 watt R.M.S. Bohm DESIGNED BY MULLARD SPECIALIST TEAM IN BELGIUM comprising a Mullard 8" woofer with foam rolled surround, Mullard 3" high power dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loudspeaker terminals and recessed mounting panel. Supplied complete with assembly and cabinet details. Recommended cabinet size 240 x 216 x 445mm.

PRICE £13.90 + £1.50 P&P per kit



LEADER LSG


WIDE BAND SIGNAL GENERATOR

- 100KHz to 100MHz in five ranges
- Up to 300MHz (Harmonics)
- Slow motion tuning
- Internal modulation 1KHz
- External mod. input facility
- Power supply 240v AC
- Size - 150 x 250 x 130mm
- Price - £63.25 - UK. Post Free

PRICE £63.25
UK Post FREE

BK ELECTRONICS

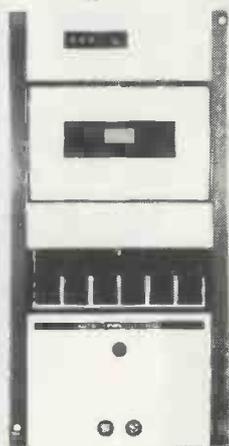Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader



6 piano type keys

STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/2". Clearance required under top panel 2 1/2". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

1K.WATT SLIDE DIMMER

- Controls loads up to 1KW
- Compact size 4 3/4" x 13" x 2 1/2" 16
- Easy snap in fixing through panel/cabinet cut out
- Insulated plastic case
- Full wave control using 8amp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads

Innumerable applications in industry, the home, and discos/theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)

BSR P256 TURNTABLE

- P256 turntable chassis
 - S shaped tone arm
 - Belt driven
 - Aluminium platter
 - Precision calibrated counter balance
 - Anti-skate (bias device)
 - Damped cueing lever
 - 240 volt AC operation (Hz)
 - Cut out template supplied
 - Completely manual arm.
- This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price: £28.50 + £2.50 P&P



GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems etc.

- Rolled fabric surround
- Twin cone
- 8ohm impedance
- 15 watt RMS
- 1" voice coil
- 13oz magnet
- Frequency range 50/15000Hz

Price: £6.90 each + 75p P&P



NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons.

Specification and Price:-


15" 100 watt R.M.S. Impedance 8ohm 59 oz. magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each. £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz magnet. 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. Price £23.70 each. £2.50 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: White cone £8.90 each. Black cone/grill £9.50 each. P & P £1.25 each.

PIEZO ELECTRIC TWEETERS - MOTOROLA

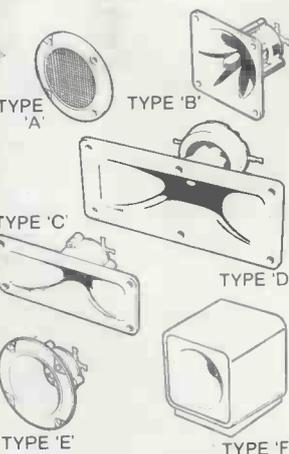Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-Fi speakers. Price £3.45 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.35 each.

TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-Fi systems and quality discos etc. Price £5.45 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £6.90 each.

TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £4.35 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each. U.K. post free (or SAE for Piezo leaflets).



POWER AMPLIFIER MODULES



Vu Meter

100 WATT R.M.S.

Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. V.u. meter, available as an optional extra.

SPECIFICATION:

Max. output power 100 watts R.M.S. (OMP100)
Loads: (Open and short circuit proof) 4-16 ohms
Frequency Response 20Hz-25KHz + 3dB
Sensitivity for 100 watts 500mV at 10K T.H.D. 00.1%

Size: 360 x 115 x 80mm
Prices: OMP 100W £29.99 £2.00 P&P
V.u. Meter £6.50



Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms
Build a quality 60 watt R.M.S. system.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover

Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.
Price £22.00 per kit + £2.50 postage and packing. Available separately, prices on request.

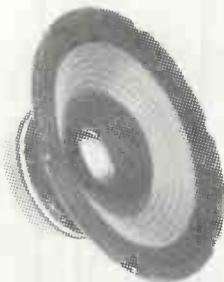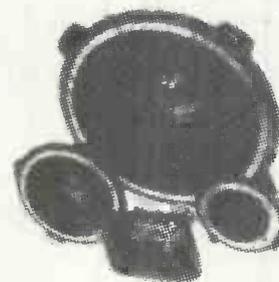12" 80 watt R.M.S. loudspeaker.
A superb general purpose twin cone loudspeaker. 50 oz. magnet. 2" aluminium voice coil. Rolled surround. Resonant frequency, 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.
Price £17.99 each + £2.50 P&P.



B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.




Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDLEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM

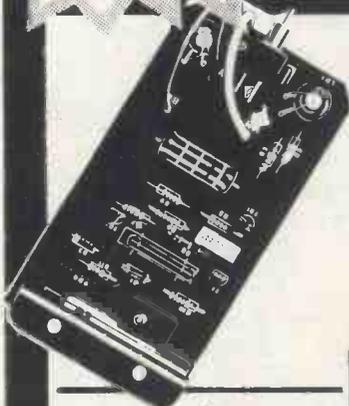

SX1000 Electronic Ignition

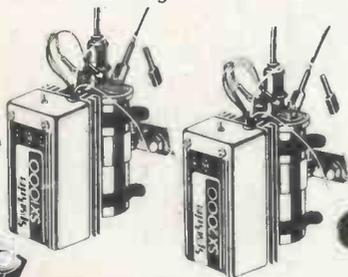- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles





SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles


MAGIDICE Electronic Dice

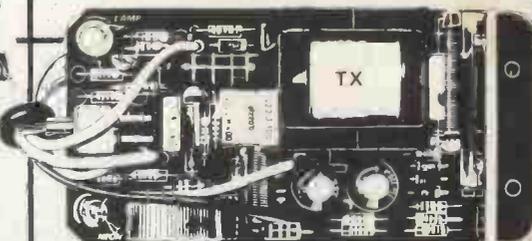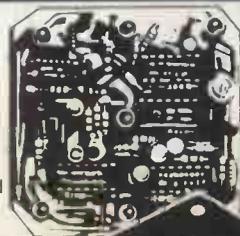- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble
- Supplied in superb presentation gift box



TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive.
- Extended coil energy storage circuit.
- Magnetic contactless distributor triggerhead.
- Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble

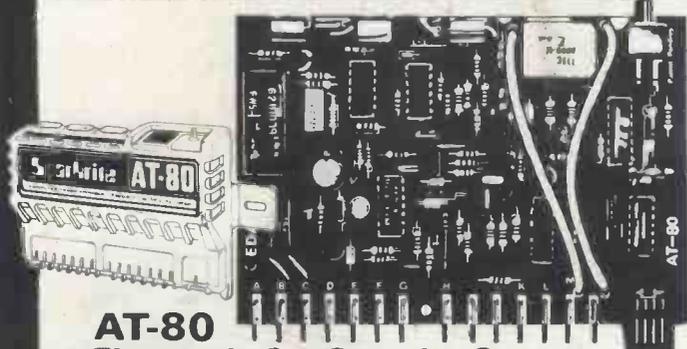


AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg-earth vehicles
- Over 250 components to assemble

VOYAGER Car Drive Computer

- A most sophisticated accessory
- Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
- Affords 12 functions centred on Fuel, Speed, Distance and Time
- Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
- Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity
- Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
- Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours.
- Full Imperial and Metric calibrations
- Over 300 components to assemble
- A real challenge for the electronics enthusiast!

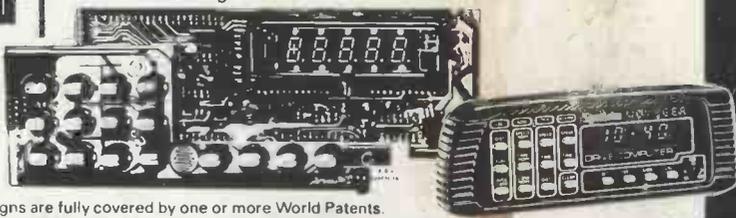

All EDA-SPARKRITE products and designs are fully covered by one or more World Patents.

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

NAME _____ HE682
 ADDRESS _____
 I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR
 £ _____ KIT REF. _____
 CHEQUE NO. _____
 24 hr. Answerphone
 PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
 SEND ONLY SAE IF BROCHURE IS REQUIRED
 Allow 28 days for delivery

BRANDLEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!