

OCTOBER '82

ISSN 0142-6192

70p

Hobby

Electronics

Project Electronics For Everyone

FREE

**DIRECTORY OF
ELECTRONIC
COMPONENT
& HARDWARE
SUPPLIERS**

**Over 60 sources
surveyed !!!**



**Introduction
to Electronics**
**Fault-finding
made easy**

**Look inside for....
PROJECTS • FEATURES
VIEWS • NEWS • REVIEWS**

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST.

BAND 2 TUNERHEADS (Varicap Tuning) EF5804

2 MOSFET of stages MOSFET mixer, JFET IF preamp, with internally amplified PIN diode AGC. Tuning voltage for 88-108MHz is 2-8V. Buffered LO output. AGC input. 145 x 70 x 24mm. Stock No. 1-24 25+
40-05804 Bit 24.95 19.65

7255 The latest complete FM tunerhead from RF input to stereo output. MOSFET RF stages, HA11225 IF and KB4437 stereo decoder. 7255 special offer price: £30.00 plus VAT

911225A The 911225A is the 7230 'edited' and shrunk into a screened metal case, 97 x 56 x 24mm. The unit is ideally suited to use with synthesised tuner systems. Stock No. 1-24 25+
40-91225 Built 20.82 16.25

944378 'Hyperfi' series decoder module with the TOKO KB4437 pilot cancel PLL IC birdy filter and the KB4438 muting stereo audio preamp with 26/38kHz pilot tone filtering. Stock No. 1-24 25+
40-04378 Built 19.95 18.05

DFCM500 Wide range digital frequency/capacitance meter. Frequency ranges: 0-1MHz, 1-50MHz and 80-500MHz. 8 digit LED display, mains or Ni-Cad battery operation. Stock No. 1-24 25+
40-01500 Kit 95.95 86.50

AUTOBRIDGE
An Automatic power tracking VSWR and self-ranging power meter. Complete Kit: All PCBs, board mounted components, meters, case (undrilled), transformer etc. Stock No: 40-40400 £52.86 + £1.50 P&P

FET DIP OSCILLATOR
An essential piece of test equipment for the RF constructor. GDO or WM function covering 1.6-215MHz in five ranges. Audio and meter indication. Kit includes: fibre glass PCB, all components, all hardware, punch, painted and screen printed case, wire etc. for coils and printed scale. Stock No: 1-24 25+
40-16215 Kit 17.90 16.20

10.MHz SSB GENERATOR
PCB. All components, eight-pole crystal filter. Stock No. Price
40-10700 £29.65

R&EW PROJECT AND DATABRIEF PCBs
High quality glass fibre printed circuit boards for projects and Databriefs published in Radio & Electronics World. £1.98
27MHz Deviation Meter PA105 £3.39
TV Pattern Generator MC145151 £5.70
2m Pre-amp MC145151 £2.57
2m Pre-amp KB4417 (Undrilled) £0.60
0-30V PSU £3.92
2m PA Mk II £5.14
ULN3859 (Undrilled) £0.84
SSB Exciter HA12017 £3.37
Up Converter £2.16
£4.75

2m PRE-AMP
Very compact low-noise MOSFET 2m pre-amp. Gain 22dB. Noise figure; less than 1.5dB. I/p and o/p impedance; 50 ohm size; 34 x 9 x 15mm. From April '82 R&EW. Stock No. 1-24 25+
40-14400 Kit 2.55 2.30

70cm PRE-AMP
Compact low-noise pre-amp. Gain at 433 MHz; 13dB. I/P and O/P impedance 50ohms. Size 50 x 10 x 17mm. From March '82 R&EW. Stock No. 1-24 25+
40-07000 Kit 3.90 3.60

2m POWER AMP
20 watt 144MHz linear power amplifier. 10dB gain, 2W input - 20W output. Automatic switched relay. By-passes power amp in receiver mode. Developed from original class C version in Dec 81 R&EW. High power output relay. Pre-drilled heatsink, optional RX pre-amp. Kit only. Stock No. 1-24 25+
40-14421 Less Preamp 28.50 25.65
40-14422 With Preamp 30.40 27.36

CMOS-TTL :

4001	0.11	4515	1.25	74LS10	0.12	74LS138	0.30
4007	0.13	4516	0.80	74LS11	0.12	74LS139	0.30
4009UB	0.25	4518	0.35	74LS12	0.12	74LS145	1.20
4010	0.30	4520	0.60	74LS13	0.20	74LS151	0.30
4011	0.11	4521	1.30	74LS14	0.30	74LS153	0.27
4012	0.14	4522	0.89	74LS20	0.12	74LS154	0.99
4013	0.25	4526	4.00	74LS21	0.12	74LS155	0.35
4016	0.22	4527	0.87	74LS22	0.12	74LS156	0.37
4017	0.40	4528	0.65	74LS26	0.14	74LS157	0.30
4019	0.38	4529	0.70	74LS27	0.12	74LS158	0.30
4020	0.55	4531	0.65	74LS28	0.15	74LS160	0.37
4021	0.55	4532	0.80	74LS30	0.12	74LS161	0.37
4022	0.85	4534	4.00	74LS32	0.12	74LS162	0.37
4023	0.15	4536	2.60	74LS33	0.15	74LS163	0.37
4024	0.33	4538	0.85	74LS38	0.14	74LS164	0.40
4025	0.15	4539	0.80	74LS40	0.13	74LS165	0.60
4026	0.26	4543	0.80	74LS42	0.30	74LS168	0.70
4030	0.35	4549	3.50	74LS47	0.35	74LS169	0.85
4043	0.30	4553	2.70	74LS48	0.45	74LS170	0.90
4044	0.60	4554	1.20	74LS49	0.55	74LS173	0.60
4046	0.60	4555	0.35	74LS51	0.13	74LS174	0.40
4049UB	0.24	4556	0.40	74LS54	0.14	74LS175	0.40
4050	0.24	4557	2.30	74LS55	0.14	74LS181	1.06
4051	0.55	4558	0.80	74LS57	0.12	74LS190	0.60
4060	0.75	4559	3.50	74LS74	0.16	74LS191	0.60
4066	0.30	4560	2.50	74LS75	0.22	74LS192	0.45
4068	0.16	4561	1.00	74LS76	0.20	74LS193	0.42
4069UB	0.14	4562	2.50	74LS78	0.19	74LS194	0.35
4070	0.16	4566	1.20	74LS83	0.40	74LS195	0.35
4071	0.16	4568	1.45	74LS85	0.60	74LS196	0.55
4072	0.16	4569	1.70	74LS86	0.14	74LS221	0.50
4073	0.16	4581	1.18	74LS90	0.28	74LS240	0.80
4075	0.16	4572UB	0.22	74LS92	0.31	74LS241	0.80
4076	0.55	4580	3.25	74LS93	0.31	74LS242	0.70
4077	0.18	4581	1.40	74LS95	0.40	74LS243	0.70
4078	0.18	4582	0.70	74LS96	1.20	74LS244	0.80
4081	0.12	4583	0.80	74LS107	0.25	74LS245	0.80
4093	0.30	4584	0.27	74LS109	0.20	74LS257	0.40
4175	0.80	4585	0.45	74LS112	0.20	74LS258	0.37
4502	0.60	40174	1.05	74LS113	0.20	74LS260	0.50
4503	0.50	40195	1.08	74LS114	0.19	74LS266	0.20
4506	0.70	74LS00	0.10	74LS122	0.35	74LS273	0.70
4507	0.37	74LS01	0.10	74LS124	1.80	74LS279	0.35
4508	1.50	74LS02	0.11	74LS123	0.35	74LS365	0.32
4510	0.55	74LS03	0.11	74LS125	0.24	74LS366	0.34
4511	0.45	74LS04	0.12	74LS126	0.24	74LS367	0.32
4512	0.55	74LS05	0.13	74LS132	0.42	74LS368	0.35
4514	1.25	74LS08	0.12	74LS133	0.24	74LS373	0.70

Memory Micros Linears:

LM10CN	3.88	SL1611	1.60	KB4433	1.52	U265	3.16
L149	1.86	SL1612	1.60	KB4413	1.95	U266	2.43
U237B	1.28	SL1613	2.06	KB4436	2.53	LC7137	7.50
U247B	1.28	SL1620	2.17	KB4437	1.75	ICM7216B	19.50
U257B	1.28	SL1621	2.17	KB4445	1.29	ICM7216C	19.95
U267B	1.28	SL1623	2.44	KB4446	2.75	ICM7217A	9.50
LM324	0.45	SL1625	2.17	NE5044	2.26	SP8647	6.00
LM339N	0.66	SL1630	1.62	MC5229	9.60	95H90	7.80
LF347	1.60	SL1640	1.89	SL6270	2.03	HD10551	2.45
LM348	0.90	SL1641	1.89	SL6310	2.03	HA12009	6.00
LF351	0.49	TDA2002	1.25	SL6440	3.38	HD44015	4.45
LF353	0.76	ULN2242	3.05	SL6600	3.75	HD44752	8.00
LM380N	1.00	ULN2283	1.00	SAS6610	1.48	MC145151P	6.00
ZN419CE	1.98	CA3089	1.84	SL6640	2.75	Z80A	3.75
ZN427E/B	6.28	CA3130E	0.80	SL6690	3.20	Z80A P10	3.50
NE544	1.80	CA3130T	0.80	SL6700	2.50	Z80A CTC	4.00
NE555N	0.20	CA3140E	0.46	SAS6710	1.48	Z80A DMA	9.95
SL560C	1.98	CA3189E	2.20	LS7225	3.65	Z80A DART	7.50
NE564	4.29	CA3240E	1.27	ICM7555	0.94	Z80A S10/1	11.00
NE567	1.30	MC3357	2.85	ICL8038CC	4.50	Z80A S10/2	11.00
UA741CN	0.20	ULN3859	2.95	TK10170	1.87	Z80A S10/9	9.95
TB820M	0.78	LM3900	0.60	TK10321	2.75	Z8001	65.00
ZNA1034	2.10	LM3909N	0.68	HA11223	2.15	8255	2.58
LM1035	4.50	LM3914N	2.80	HA11225	1.45	6800P	2.90
TDA1062	1.95	KB4412	1.95	HA12002	1.22	6809	8.75
TDA1093	1.95	KB4417	1.80	HA12402	1.95	6802	3.50
TDA1090	3.05	KB4420B	1.09	HA12411	1.20	68A00P	4.25
HA1197	1.00	KB4423	2.30	HA12412	1.55	68B00P	4.65
MC1350	1.20	KB4424	1.65	LF13741	0.33	2114-L2	1.49
HA1370	1.90	KB4430	2.30	MK50375	3.85	4116-2	1.59
HA1388	2.75	KB4431	1.95	MM53200	3.90	2732	4.00
SL1610	1.60	KB4432	1.95	U264	2.27	2716	3.00

Coils, Filters: Toko, Murata, NTK, Cathodeon.

SFE6.0MA	0.80	CDA10.7MA	0.70	10M15D	14.50
CFSE10.7	0.80	SFE27MA	0.94	LFB4	1.95
SFE10.7MA	0.45	SAF10.7MC-Z	3.75	LFB6/CFU455H	1.95
CFSB10.7	0.50	MF45510AZ12118.55	1.95	LFB8	1.95
SFE10.7MJ	0.50	MFL45501L	11.95	LFB10	1.95
SFA10.7MF	0.75	10M15A	1.99	LFB12/CFU455F	1.95
SFE10.7ML	0.70	21M15A	3.45	LFH65/	
SFE10.7MX	0.95	45M15A	5.95	CFW455HT	2.45
CFSH10.7M1	0.50	10M22D	17.20	LFH8S	2.45
CFSH10.7M2	0.50	10M8D	15.50	LFH12S/	
CFSH10.7M3	0.50			CFW455FT	2.45

TOKO FIXED VALUE CHOKES (E12 Values)

7BA - 1 to 1000uH	16p	10RB - 1 to 120mH	33p
8RB - 1 to 33mH	19p	10RB - .15 to 1.5H	43p

RETAIL SHOP OPENING HOURS

Monday to Thursday 8.30-6.30
Friday 8.30-8.30 Saturday 9.00-5.30
(Access + Barclaycard orders accepted)

NOW IN STOCK

MF10 - National's new Dual Switched - Capacitor Filter: Price £5.05

ALL PRICES SHOWN EXCLUDE VAT. P&P 50p per order.

AMBIT INTERNATIONAL DEPT.HE

200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 5G

AND THERE'S PLENTY MORE IN THE CATALOGUE 70p inc.

Hobby Electronics

PROJECTS

- ★ FLASH POINT ALARM 9
Prevent chip-pan fires!
- ★ NEGATIVE VOLTAGE GENERATOR 24
Split supplies for ICs.
- INTO RADIO**
- CB SQUELCH UNIT 58
Stamp out noise.
- ★ BREADBOARDS 75
Three circuits for experimenters.


FEATURES

- ★ FAULT-FINDING MADE EASY 15
A Beginner's Guide Special
- ★ FAMOUS NAMES 21
Valdemar Poulsen.
- SPECIAL FEATURE**
- DIRECTORY OF ELECTRONIC SUPPLIES 33
A complete shopping guide for the electronic hobbyist.
- GADGETS, GAMES AND KITS**
- CM 100 CIRCUIT MAKER 63
Making PCBs by the photographic process.
- INTO RADIO**
- RADIO RULES 68
Modulation and other matters.

REGULARS

- Monitor 6
- Whats On Next 18
- Points of View 27
- Buylines 30
- COMPONENT ORDER FORM 31
- HE Book Service 73
- HE Backnumbers 74
- Breadboard Exhibition 76
- PCB Service 77
- PCB Printout 80
- Classified Advertisements 81

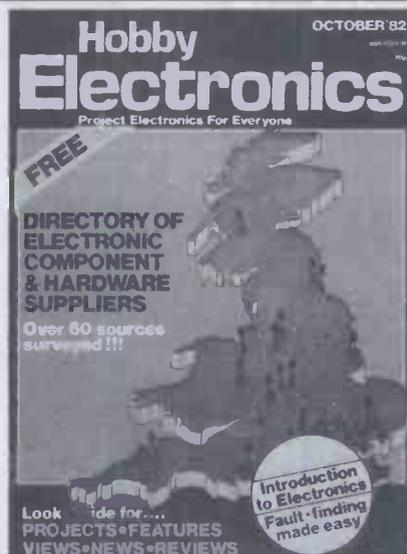Editor: Ron Keeley
 Editorial Assistant: Paul Coster BSc
 Advertisement Manager: Gary Price
 Assistant Advert. Manager: Jolyn Nice
 Managing Editor: Ron Harris BSc
 Managing Director: T.J. Connell



Hobby Electronics is normally published on the second Friday of the month prior to the cover date.
 Hobby Electronics, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002. Telex No 8811896. Published by Argus Specialist Publications Ltd.
 Design and Organisation by MM Design and Print Ltd, 145 Charing Cross Road, London WC2H 0EE, 01-437 1002.
 Distributed by S. M. Distribution Ltd, 18/18 Trinity Gardens, London SW9 8DX.
 Printed by Q8 Ltd, Colchester. Covers printed by Alabaster Passmore.

Notice: The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of International copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. All reasonable care is taken in the preparation of the magazine to ensure accuracy, but Argus Specialist Publications Ltd cannot be held responsible legally. © Copyright 1982 Argus Specialist Publications Ltd. Member of Audit Bureau of Circulation.

100 FREE PROGRAMS

FROM SILICA SHOP — WITH EVERY PURCHASE OF AN

ATARI 400 800



ATARI PRICES REDUCED!

We at Silica Shop are pleased to announce some fantastic reductions in the prices of the Atari 400/800 personal computers. We believe that the Atari at its new price will become the U.K.'s most popular personal computer and have therefore set up the Silica Atari Users Club. This club already has a library of over 500 programs and with your purchase of a 400 or 800 computer we will give you the first 100 free of charge. There are also over 350 professionally written games and utility programs, some are listed below. Complete the reply coupon and we'll send you full details. Alternatively give us a ring on 01-301 1111 or 01-309 1111.

ATARI 400 with 16K	£199
ATARI 400 with 32K	£248
ATARI 800 with 16K	£449

400/800 SOFTWARE & PERIPHERALS

Don't buy a T.V. game! Buy an Atari 400 personal computer and a game cartridge and that's all you'll need. Later on you can buy the Basic Programming cartridge (£35) and try your hand at programming using the easy to learn BASIC language. Or if you are interested in business applications, you can buy the Atari 800 + Disk Drive + Printer together with a selection of business packages.

Silica Shop have put together a full catalogue and price list giving details of all the peripherals as well as the extensive range of software that is now available for the Atari 400/800. The Atari is now one of the best supported personal computers. Send NOW for Silica Shop's catalogue and price list as well as details on our users club.

THE FOLLOWING IS JUST A SMALL SELECTION FROM THE RANGE OF ITEMS AVAILABLE:


ACCESSORIES Cables Cassettes Diskettes Joysticks Le Stick - Joystick Misc. Supplies Paddles ADVENTURE INT Scott Adams Adv No 1 Adventure Int No 2 Pirate Adv No 3 Mission Imp No 4 Voodoo Cast No 5 The Count No 6 Strange Ody No 7 Mystery Fun No 8 Pyramid of D No 9 Ghost Town No 10 Sav Island 1 No 11 Sav Island 2 No 12 Golden Voy Angle Worms Deflections Galactic Empire Galactic Trader Lunar Lander	Mountain Shoot Rearguard Star Flite Sunday Golf AUTOMATED SIMULATIONS Crush Crumble Cmp Dates of Ryn Dragons Eye Invasion Orion Rescue at Rigel Ricochet Star Warrior Temple of Aphai Upper Reaches Aps BOOKS Basic Ref Manual Compute Atari: DOS Compute Bk Atari Compute Magazine De Re Atari DOS Utilities List DOS2 Manual Misc. Atari Books Op System Listing Wiley Manual	BUSINESS Calculator Database Management Decision Maker Graph-It Invoicing Librarian Mort & Loan Anal Nominal Ledger Payroll Personal Finl Mgmt Purchase Ledger Sales Ledger Statistics 1 Stock Control Teletink 1 Vitacalc Weekly Planner Word Processor CRYSTALWARE Beneath The Pyram Fantasyland 2041 Galactic Quest House Of Usher Sands Of Mars Waterloo World War III	DYNACOMP Alpha Fighter Champelo Crystals Forest Fire Intruder Alert Monarch Moonprobe Moving Maze Nominoes Jigsaw Rings of The Emp Space Tilt Space Trap Stud Poker Triple Blockade EDUCATION from APX Alpicalc Atlas of Canada Cubbyholes Elementary Biology Frogmaster Hickory Dickory Int. Compng Dem Lemonade Letterman Mapware	Maths Tac-Toe Metric & Prob Solv Mugwump Music Terms/Notatn Musical Computer My First Alphabet Number Blast Polycalc Presidents Of U.S. Quiz Master Starware Stereo 3D Graphics Three R Math Sys Video Math Flash Wordmaker EDUCATION from ATARI Conv French Conv German Conv Italian Conv Spanish Energy Czar European C & Caps Hangman Invite To Prog 1/2/3 Kingdom Music Composer	Scream States & Capitals Touch Typing EMI SOFTWARE British Heritage Cribbage/Dominoes Darts European Scene Jig Hickory Dickory Humpty Dumpty Jumbo Jet Lander Snooker & Billiards Submarine Comdr Super Cubes & Tilt Tournament Pool ENTERTAINMENT from APX Alien Egg Anthill Artank Avalanche Babbel Blackjack Casino Block Buster Block 'Em Bumper Pool	Castle Centurion Solitaire Space Chase Space Trek Sultans Palace Tact Trek Terry Wizards Gold Wizards Revenge ENTERTAINMENT from ATARI Asteroids Basketball Blackjack Centipede Chess Entertainment Kit Midas Touch Minotaur Outlaw/Howitzler Preschool Games Pro Bowling Pushover Rabbottz Reversi II Salmon Run 747 Landing Simul Seven Card Stud	Jawbreaker Mission Asteroid Mouskattack Threshold Ulysses/Golden Fl Wizard & Princess PERIPHERALS Centronics Printers Disk Drive Epson Printers Program Recorder RS232 Interface Thermal Printer 16K Memory RAM 32K Memory RAM PERSONAL INT from APX Adv Music System Banner Generator Blackjack Tutor Going To The Dogs Keyboard Organ Morse Code Tutor Personal Fitness Prg Player Piano Sketchpad	PROGRAMMING AID from Atari Assembler/Editor Dsembler (APX) Microsoft Basic Pascal (APX) Piles (Consumer) Pilot (Educator) Programming Kit SANTA CRUZ Basics of Animation Bob's Business Display Lists Graphics Machine Kids 1 & 2 Horizontal Scrolling Master Memory Map Mini Word Processor Page Flipping Player Missile Gr Player Piano Sounds Vertical Scrolling
---	---	--	---	---	--	--	---	---

FOR FREE BROCHURES - TEL: 01-301 1111

For free brochure and reviews on our range of electronic products, please telephone 01-301 1111. To order by telephone, just quote your name, address, credit card number and order requirements and leave the rest to us. Postal and packing is FREE OF CHARGE in the UK. Express 24 hour delivery available at an additional charge.

- SHOW DEMONSTRATION FACILITIES - we provide full facilities at our shop in Sidcup, Monday to Saturday 9am to 5.30pm (closing Thursday 1pm, Friday 6pm).
- MAIL ORDER - we are a specialist mail order company and are able to supply goods direct to your door.
- MONEY BACK UNDERTAKING - if you are totally unsatisfied with your purchase, you may return it to us within 15 days. On receipt of the goods in satisfactory condition, we will give you a full refund.
- PART EXCHANGE SECOND-HAND MACHINES - we offer a part exchange scheme to take in many makes of TV games for personal computers.
- COMPETITIVE PRICES - our prices, offers and service are very competitive. We are never knowingly under-sold and will normally match any lower price quoted by our competitors.
- HELPFUL ADVICE - available on the suitability of various computers.
- AFTER SALES SERVICE - available on all computers out of guarantee.
- VAT - all prices quoted above include VAT at 15%.
- CREDIT FACILITIES - we offer credit over 12, 24 or 36 months. Please ask for details.

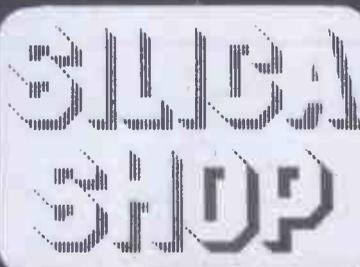SILICA SHOP LIMITED
 Dept HE 1082, 1-4 The Mews, Hatherley Road, Sidcup,
 Kent DA14 4DX Telephone 01-301 1111 or 01-309 1111



FREE LITERATURE

I am interested in purchasing an Atari 400/800 computer and would like to receive copies of your brochure and test reports as well as your price list covering all of the available Hardware and Software.

Name

Address

.....

Postcode

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS., ENGLAND
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT ENQUIRY WELCOME. P&P ADD 50p TO ALL CASH ORDERS. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. ACCESS ORDERS WELCOME.

VAT

All prices exclusive of VAT. Please add 16% VAT to the total cost incl. P&P

We stock thousands more items. It pays to visit us. We are situated behind Watford Football Ground. (Nearest underground/BR Station: Watford High Street. Open Monday to Saturday: 9am to 6pm)

POLYESTER CAPACITORS: Axial Lead Type
400V: 1nF, 1.5n, 2n, 3n, 4n, 6n, 8n 11p; 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 16p; 100n, 150n 20p; 220n 30p; 330n, 470n, 680n 30p; 1uF 68p; 2.2u 82p; 4.7u 85p.
160V: 10nF, 12n, 100n 11p, 150n, 220n 17p; 330n, 470n 30p; 680n, 39p; 1uF 42p; 1.5u 45p; 2u 48p.
1000V: 1nF 17p; 10nF 30p; 15n 40p; 22n 36p; 33n 42p; 47n 48p; 100n 50p; 470n 99p.

POLYESTER RADIAL LEAD CAPACITORS: 250V:
10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p.
330n, 470n 13p; 680n 19p; 1uF 23p; 1.5u 40p; 2u 46p; 4u 60p.

ELECTROLYTIC CAPACITORS: (Values are in μ F) 500V: 10 52p; 47 78p; 250V: 100 66p; 63V: 0.47, 1.0, 1.5, 2.2, 2.5, 3.3 4p; 6.8, 10, 15, 22, 12p; 33 15p; 47 12p; 100, 19p; 1000 7p. 50V: 47 12p; 100 22p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 15, 22 29p; 3300, 90p; 470, 120p; 25V: 1.5, 6.8, 10, 22 8p; 33 9p; 47 8p; 100 11p; 150 12p; 220, 15p; 330 22p; 470 25p; 680, 1000, 34p; 2200, 50p; 330p, 76p; 4700 52p; 16V: 4.7, 100p; 12p, 22p; 220 13p; 470, 20p; 680 34p; 1000 27p; 1500, 31p; 2200 36p; 3300 74p; 4700 79p.

TAG-END CAPACITORS: 64V: 2200 130p; 3300 198p; 4700 245p; 50V: 2200 110p; 3300 154p; 40V: 4700 190p; 25V: 2200 90p; 3300, 4000, 4700 96p; 10,000 320p; 15,000 345p; 16V: 22,000 350p.

TANTALUM BEAD CAPACITORS
35V: 0.1uF, 0.22, 0.33 15p; 0.47, 0.68, 1.0uF, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10uF 25p; 16V: 2.2, 3.3 16p; 4.7uF, 6.8, 10 18p; 15, 36p; 22 30p; 33, 47 40p; 75p; 220 88p; 10V: 15, 22, 26p; 33, 47 35p; 100 55p; 6V: 10u 42p.

POTENTIOMETERS: Rotary, Carbon, Track, 0.25W Log or 0.5W Lin, 5000, 10K & 20K (Linear only) Single Gang
5K-20K Single Gang 30p
5K-20K Double Gang D/P Switch 75p
5K-20K Double Gang 85p

SLIDER POTENTIOMETERS
0-25W Log and linear values 60mm
5K-50K Single Gang 70p
10K-50K Dual Gang 110p
Self Stick Graduated Bezel 40p

MYLAR FILM CAPACITORS
100V: 1nF, 2, 4, 4n7, 10, 16pF; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 470n/50V: 12p.

MINIATURE TYPE TRIMMERS
2.4pF, 2-10pF, 2-25pF, 5-50pF 30p.

COMPRESSION TRIMMERS
3.40pF, 10-80pF 20p; 20-250pF 28p; 100-580pF 39p; 400-1250pF 48p.

PRESET POTENTIOMETERS
Vertical & Horizontal
0.1W 50 M Miniature 7p
0.25W 100 M-3.3 MO horiz 10p
0.25W 200 M-4.7 MO vert 10p

VOLTAGE REGULATORS
1A TO3 +ve -ve
5V 7805 145p 7905 220p
12V 7812 145p 7912 220p
15V 7815 145p
18V 7818 145p

1A TO220 Plastic Casing
5V 7805 40p 7095 45p
12V 7812 40p 7912 45p
15V 7815 40p 7915 45p
18V 7818 40p 7918 45p
24V 7824 40p 7924 45p

100mA TO92 Plastic Casing
5V 78L05 30p 79L05 60p
6V 78L02 30p
8V 78L02 30p
12V 78L12 30p 79L12 60p
15V 78L15 30p 79L15 60p

CA3085 95p LM137P 99p T8A625B 75p
LM3080 170p LM323K 50p TDA1412 150p
LM305H 140p LM337 175p 78H05 50p
LM309K 185p LM723 35p 78M12 50p
LM317K 50p TAA550 50p 78H05 50p
78H05 78p

DIL SOCKETS
Low Wire Prof. wrap
8 way 8p 25p
14 pin 3p 35p
16 pin 10p 42p
18 pin 15p 52p
20 pin 22p 60p
22 pin 25p 70p
24 pin 27p 70p
28 pin 28p 80p
40 pin 30p 99p

PROTO DEC
Euroboard 520
S Dec 450
Bimboard I 600
Veroblock 375
Adventures with Electronics
by Tom Duncan
Complete Kit £15

DENCO COILS
'D' VALVE TYPE
Rd. 1 to 5 BL.
Rd. 1, 10, 12, 12p
6.7 B-Y-R 110p
1.5 Green 150p
T type to 1, 5, BL.
Rd. Wht. YI 150p
B9A Valve Holder
42p
RDT2 146p

VEROBOARD
0.1" Pitch clad plain
2 1/2 x 3 1/2" 73p 52p
2 1/2 x 5" 83p
3 1/2 x 3 1/2" 83p
3 1/2 x 5" 95p
3 1/2 x 17" 326p 211p
4 1/2 x 17" 426p
Pkt of 100 pins 50p
Spot face cutter 118p
Pin insertion tool 162p

COPPER CLAD BOARDS
Fibre glass
6 x 6" 90p
6 x 12" 150p
6A/100V 40p
6A/100V 50p
S.R.B.P.
9 x 8" 95p

We stock a wide selection of electronic Books and Magazines.

7400	74147	90	LS124	90	4053	50	CA3020	210	MC3886	250
7401	74150	50	LS125	24	4054	80	CA3023	210	MC1709G	90
7402	74151	40	LS126	36	4055	85	CA3026	36	MC1710	79
7403	74152	40	LS127	45	4056	85	CA3035	256	MC3302	150
7404	74153	40	LS128	55	4057	191	CA3045	365	MC3340P	120
7405	74154	30	LS129	26	4058	435	CA3046	70	MC3360P	120
7406	74155	80	LS130	28	4060	45	CA3048	220	MC3401	60
7407	74156	60	LS131	28	4061	1196	CA3059	286	MC3403	75
7408	74157	48	LS147	150	4063	85	CA3075	213	MC3405	110
7409	74158	48	LS148	150	4066	85	CA3080E	70	MC3407	60
7410	74159	48	LS149	150	4067	245	CA3081	150	MC3409	60
7411	74160	48	LS150	150	4068	14	CA3085	96	MC3412	60
7412	74161	48	LS151	40	4069	13	CA3089A	376	MM5303	635
7413	74162	48	LS152	30	4070	13	CA3090A	376	MM5307	1275
7414	74163	150	LS153	30	4071	13	CA3123E	150	MM5387	47
7415	74164	125	LS154	37	4072	13	CA3140	40	NE529	225
7416	74165	275	LS161	37	4073	13	CA3160	86	NE544	210
7417	74166	54	LS162	37	4074	13	CA3181	160	NE554	225
7418	74167	54	LS163	37	4075	50	CA3189	296	NE555	16
7419	74168	50	LS164	43	4076	50	HA1336W	240	NE556	32
7420	74169	45	LS165	60	4077	15	ICL7108E	750	NE560	325
7421	74170	80	LS170	70	4078	15	ICL7109	975	NE561	398
7422	74171	115	LS174	55	4085	50	ICM7204	560	NE562	420
7423	74172	40	LS175	40	4089	125	ICM7215A	1950	NE565	120
7424	74173	90	LS181	95	4093	20	ICM7217A	1950	NE567	140
7425	74174	35	LS190	35	4094	30	ICM7224	785	NE570	410
7426	74180	250	LS192	36	4095	75	ICM7555	80	NEB71	400
7427	74181	250	LS193	37	4096	290	ICM7556	160	NEB534	225
7428	74182	48	LS194	33	4097	190	LA3350	250	RC136	69
7429	74183	46	LS195	33	4098	75	LA4031	340	SN7613	89
7430	74184	46	LS196	33	4099	190	LA4032	295	SAB3209	425
7431	74185	46	LS197	48	4100	75	LA4040	340	SAB3210	325
7432	74186	46	LS221	65	4101	99	LC7120	300	SAB3271	485
7433	74187	46	LS240	55	4102	99	LC7137	395	SN7613	596
7434	74188	56	LS241	56	4103	99	LF347	150	SN7613	596
7435	74189	56	LS242	56	4104	105	LF351	150	SN7647	450
7436	74190	56	LS243	56	4105	105	LF353	50	SN7648	480
7437	74191	56	LS244	56	4106	105	LF355	50	SN7660	120
7438	74192	56	LS245	56	4107	105	LF356	90	SL490	350
7439	74193	56	LS246	56	4108	105	LF357	110	SP829	299
7440	74194	56	LS247	56	4109	105	LF358	475	TA4621	295
7441	74195	56	LS248	56	4110	105	LF359	475	TA7120	150
7442	74196	56	LS249	56	4111	105	LF360	475	TA7120	150
7443	74197	56	LS250	56	4112	105	LF361	475	TA7120	150
7444	74198	56	LS251	56	4113	105	LF362	475	TA7120	150
7445	74199	56	LS252	56	4114	105	LF363	475	TA7120	150
7446	74200	56	LS253	56	4115	105	LF364	475	TA7120	150
7447	74201	56	LS254	56	4116	105	LF365	475	TA7120	150
7448	74202	56	LS255	56	4117	105	LF366	475	TA7120	150
7449	74203	56	LS256	56	4118	105	LF367	475	TA7120	150
7450	74204	56	LS257	56	4119	105	LF368	475	TA7120	150

7ALS

7451	7452	7453	7454	7455	7456	7457	7458	7459	7460	7461	7462	7463	7464	7465	7466	7467	7468	7469	7470	7471	7472	7473	7474	7475	7476	7477	7478	7479	7480	7481	7482	7483	7484	7485	7486	7487	7488	7489	7490	7491	7492	7493	7494	7495	7496	7497	7498	7499	7500
------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------

CMOS

4000	4001	4002	4003	4004	4005	4006	4007	4008	4009	4010	4011	4012	4013	4014	4015	4016	4017	4018	4019	4020	4021	4022	4023	4024	4025	4026	4027	4028	4029	4030	4031	4032	4033	4034	4035	4036	4037	4038	4039	4040	4041	4042	4043	4044	4045	4046	4047	4048	4049	4050	4051	4052	4053	4054	4055
------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------

ICs

2114L-2	2708	2716	2728	4816 (BBC)	5116	6502	6503	6504	6505	6506	6507	6508	6509	6510	6511	6512	6513	6514	6515	6516	6517	6518	6519	6520	6521	6522	6523	6524	6525	6526	6527	6528	6529	6530	6531	6532	6533	6534	6535	6536	6537	6538	6539	6540	6541	6542	6543	6544	6545	6546	6547	6548	6549	6550	6551	6552	6553	6554	6555	6556	6557	6558	6559	6560
---------	------	------	------	------------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------	------

TRANSISTORS

AC125	AC126	AC127	AC128	AC141/2	AC176/87	AC177/8	AC179/10	AC180/11	AC181/12	AC182/13	AC183/14	AC184/15	AC185/16	AC186/17	AC187/18	AC188/19	AC189/20	AC190/21	AC191/22	AC192/23	AC193/24	AC194/25	AC195/26	AC196/27	AC197/28	AC198/29	AC199/30	AC200/31	AC201/32	AC202/33	AC203/34
-------	-------	-------	-------	---------	----------	---------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------	----------

MONITOR

BIMDAPTORS

All 2000 Series BIMBOXES from **Boss Industrial Mouldings** now include BIMDAPTORS, which enable flat mounting of PCBs by using the vertical slots moulded into the sides of the boxes (right).

The simple plastic adaptors have 1.5 mm wide horizontal slots spaced 5 mm apart, and are normally slid onto each corner of the PCB — or at closer intervals if required. Two or more PCBs can be sandwiched together and the whole assembly simply slipped into position in the box. The BIMDAPTORS are snipped off to length, just below lid-level, so that the units are firmly held down when the lid is screwed on.

Boss now offer six basic sizes within the 2000 Series, ranging from 100 x 50 x 25 mm to 190 x 110 x 60 mm. Available colours are blue, black, grey, orange or white; some have standard profile clear plastic lids and are the ideal containers for devices such as controller/timers, where it is necessary to see inside the box.

For further information, contact **Boss Industrial Mouldings Ltd**, James Carter Road, Mildenhall, Suffolk IP28 7DE; Tel. 0638 716101.

Save Your Memory

MEMIC, from **Cambridge Microelectronics**, is a family of CMOS memory units with an integral backup battery for saving up to 2K of program without the need to blow EPROMs. The units plug directly into 24-pin EPROM/ROM sockets or byte-wide RAM sockets. A flying-lead connector allows MEMIC to be used as random access memory even when plugged into a ROM socket.


The 2K bytes of fast, static memory and the lithium backup battery are built into a box measuring must 4" x 2.4" x 1"; as many units may be used as there are spare sockets. The access time is better than 200 nS; no special signals or hardware are required for use with most systems and the very low power consumption on stand-by gives months of memory storage.

MEMIC units (right) are available for an all-inclusive price of £29.95, fully assembled, tested, and with clear operating instructions, from **Cambridge Microelectronics Ltd**, 1, Milton Road, Cambridge CB4 1UY; Tel. 0223 314814.

We also understand that a MEMIC unit for the ZX81 (the MEMIC 81), with up to 4K of memory, will shortly be available. It is expected to be in the same price range, so watch this space for further details!

The £50 Computer

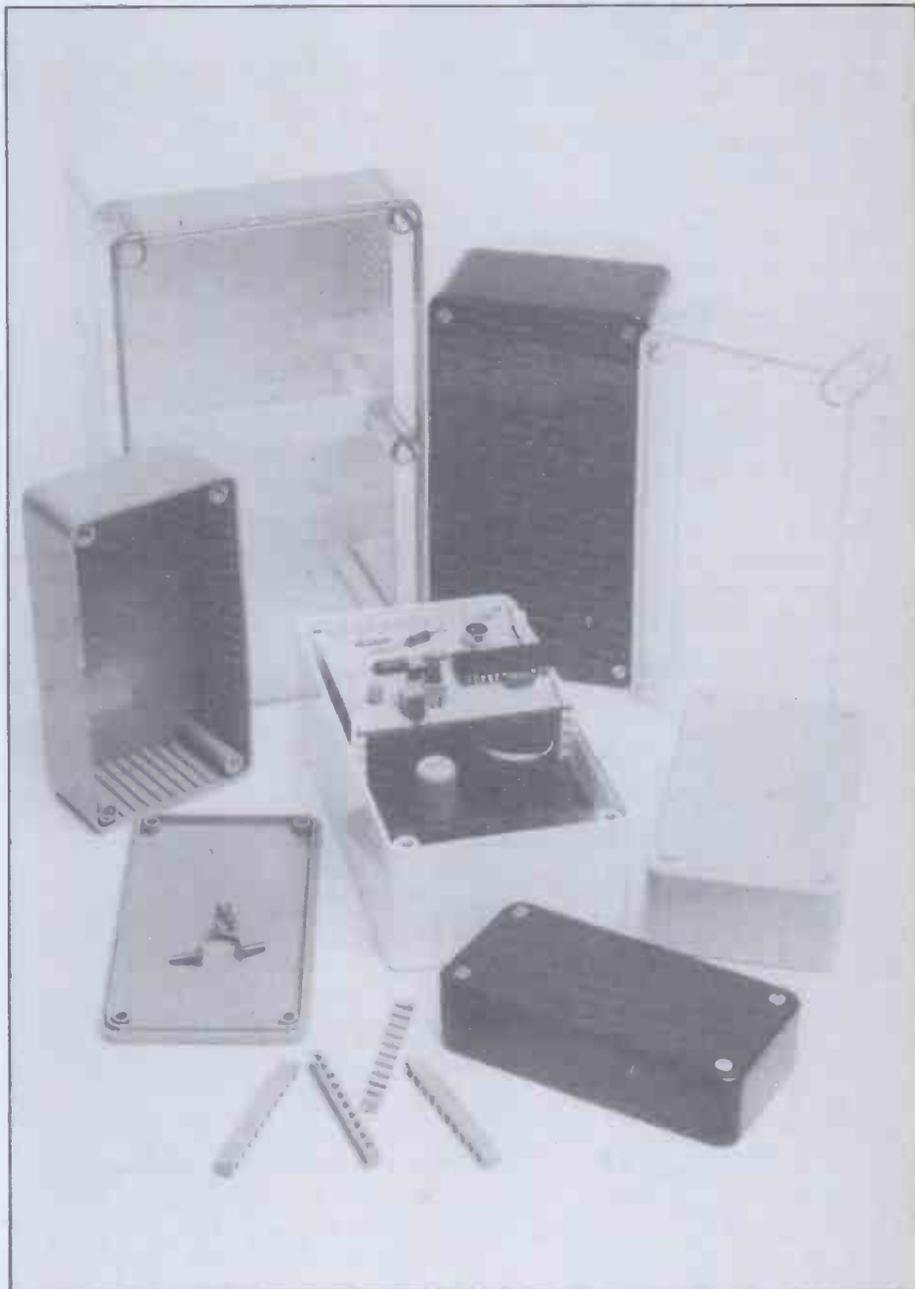Sinclair Research have broken the £50 barrier for personal computers by reducing the price of the ZX81 from £69.95 down to £49.95. The move reflects Clive Sinclair's belief that "The personal computer is no longer the preserve of the hobbyist but (is) rapidly becoming as much a



MONITOR

household item as the TV or hi-fi".


From August, the ZX81 will also be sold at selected branches of Boots and Greens (in Debenhams), as well as at branches of W.H. Smith.

Tooling Up

The only really essential tools of the electronics trade are a soldering iron, a pair of pliers, cutters and some screwdrivers. There are many other items, though, whose usefulness only becomes obvious if they aren't to hand when needed!

Miniature files, such as those (below) recently released by Neill Tools, are a good example; this new six-pack of Stubs precision needle files are ideal for construction and maintenance of electronic equipment of all kinds.

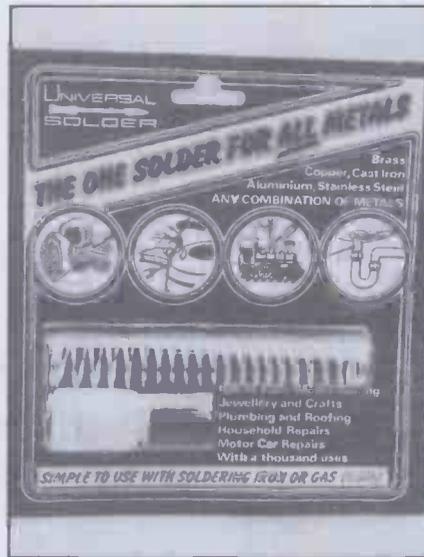The clear plastic pack contains six 16 mm files — hand, flat, round, half round,



square and three-square — and sell at a recommended retail price of £9.45. Details from Neill Tools Limited, Napier Street, Sheffield S11 8HB; Tel. 0742 71281.

Hobbyists with a sideline in DIY or craft-work will also be interested in Universal Solder, from Jimi-Heat Limited; it has the ability to join all metals to themselves or to each other. The joint is formed at a temperature of 210° using either a low-pressure gas flame or soldering iron and it will join metals such as aluminium or zinc easily and without distortion.

The solder is non-toxic and is supplied in a pack together with the flux. It is available for £2.95, including VAT, from branches of Woolworth and Halfords.

Gold Tested Here

The Mitsubishi Electric Corporation have produced an Ultrasonic Gold Ingot/Bar Tester (below) that can be used by "the average person" to detect the presence of cavities or foreign matter inside gold bars/ingots, detect gold plating or pinpoint the presence of substances other than gold.

We would be happy to review a sample unit for the benefit of our many gold-investing readers, but it seems unlikely that we could persuade anyone to supply the several dozen pure gold bars that would be necessary for us to carry out a thorough test!




Double First

Murphy Electronics are currently leading the way in new developments in audio marketing techniques with the release of a twin-cassette recorder/radio. The MTC 2506 has a "double-play" facility which allows recording from one cassette deck to the other. Deck One functions in both play and record modes, while Deck Two works in playback only.

Also included in the set is a three-band stereo radio, tone and balance controls, auto-stop feature, twin condenser microphones, and sockets for headphones and extension speakers. The set operates either from mains or battery and will be available for around £99 at retail outlets.

HE

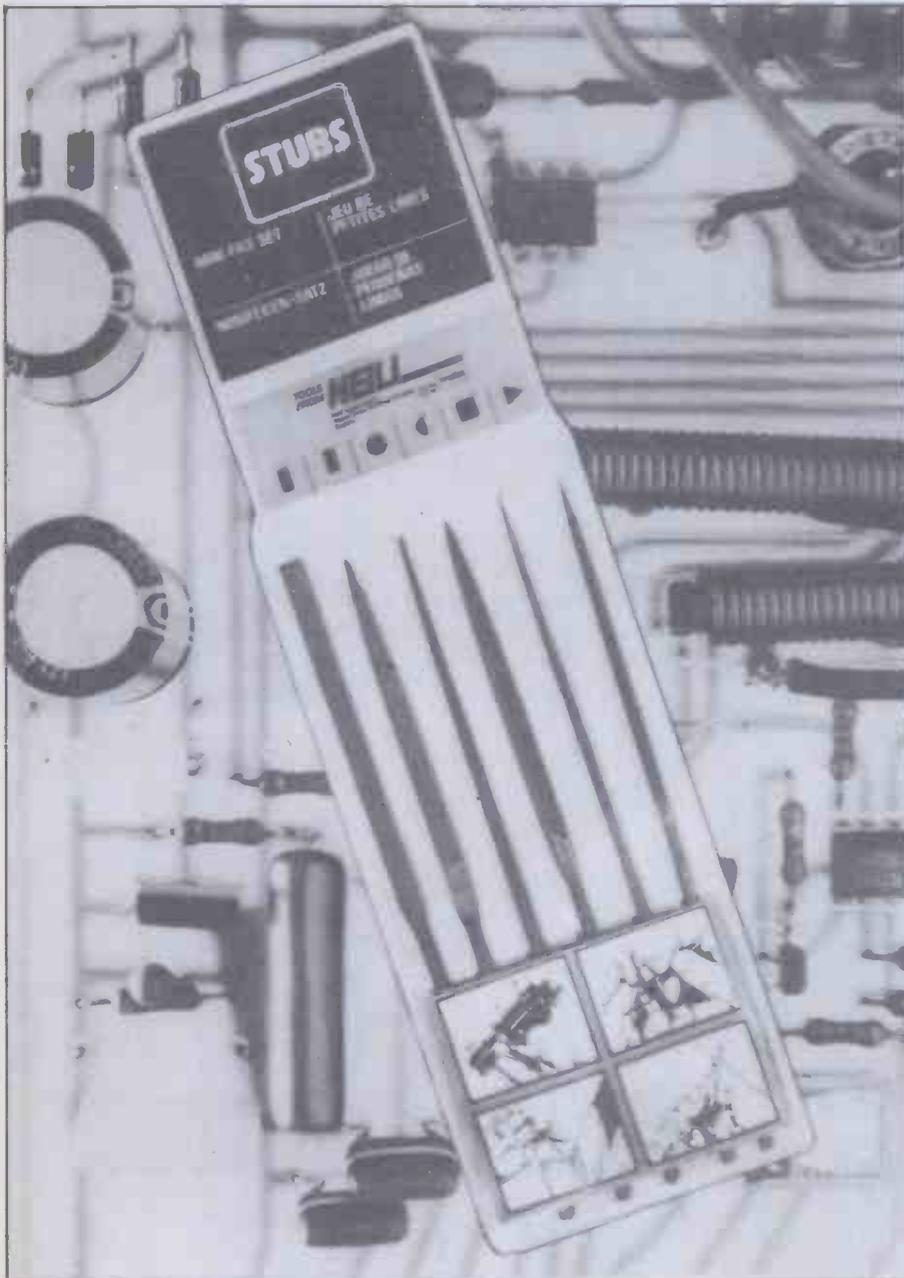

CRICKLEWOOD ELECTRONICS LTD.

40 Cricklewood Broadway, London NW2 3ET. tel 01 452 0161 tlx 914977

This is a small list from our vast stocks. Full price list free on request. You may order by phone quoting Access, Visa or American Express no., or by normal mail order. Callers welcome. All in stock items (95% ex stock) go out same day. Please add 15% VAT & 70p p&p. Govt Depts, schools, etc. orders welcome. Overseas orders no VAT but allow extra p&p. Qty discounts negotiable.

CRICKLEWOOD - STOCKING PARTS OTHER STORES CANNOT REACH

SUPERIOR QUALITY CARBON FILM RESISTORS, HI STAB		Rechargeable Batteries		TRANSISTORS		2N5401 35p		BC121 10p		4F 457 40p	
1W 10% 1.0M 5% E24 2p		Minimum 500		Probably the largest retail variety in UK.		2N5415 1.10		BC121A 12p		4F 458 40p	
1W 10% 1.0M 5% E24 2p		Guaranteed		If you don't see what you want please phone or write as follows		2N5416 1.54		BC121B 13p		4F 459 40p	
1W 10% 1.0M 5% E24 2p		500				2N5417 1.6p		BC121C 14p		4F 460 40p	
2W 10% 1.0M 5% E12 18p						2N5418 1.6p		BC121D 15p		4F 461 40p	
						2N5419 2.1p		BC121E 16p		4F 462 40p	
						2N5420 2.3p		BC121F 17p		4F 463 40p	
						2N5421 2.3p		BC121G 18p		4F 464 40p	
						2N5422 2.3p		BC121H 19p		4F 465 40p	
						2N5423 2.3p		BC121I 20p		4F 466 40p	
						2N5424 2.3p		BC121J 21p		4F 467 40p	
						2N5425 2.3p		BC121K 22p		4F 468 40p	
						2N5426 2.3p		BC121L 23p		4F 469 40p	
						2N5427 2.3p		BC121M 24p		4F 470 40p	
						2N5428 2.3p		BC121N 25p		4F 471 40p	
						2N5429 2.3p		BC121O 26p		4F 472 40p	
						2N5430 2.3p		BC121P 27p		4F 473 40p	
						2N5431 2.3p		BC121Q 28p		4F 474 40p	
						2N5432 2.3p		BC121R 29p		4F 475 40p	
						2N5433 2.3p		BC121S 30p		4F 476 40p	
						2N5434 2.3p		BC121T 31p		4F 477 40p	
						2N5435 2.3p		BC121U 32p		4F 478 40p	
						2N5436 2.3p		BC121V 33p		4F 479 40p	
						2N5437 2.3p		BC121W 34p		4F 480 40p	
						2N5438 2.3p		BC121X 35p		4F 481 40p	
						2N5439 2.3p		BC121Y 36p		4F 482 40p	
						2N5440 2.3p		BC121Z 37p		4F 483 40p	
						2N5441 2.3p		BC121AA 38p		4F 484 40p	
						2N5442 2.3p		BC121AB 39p		4F 485 40p	
						2N5443 2.3p		BC121AC 40p		4F 486 40p	
						2N5444 2.3p		BC121AD 41p		4F 487 40p	
						2N5445 2.3p		BC121AE 42p		4F 488 40p	
						2N5446 2.3p		BC121AF 43p		4F 489 40p	
						2N5447 2.3p		BC121AG 44p		4F 490 40p	
						2N5448 2.3p		BC121AH 45p		4F 491 40p	
						2N5449 2.3p		BC121AI 46p		4F 492 40p	
						2N5450 2.3p		BC121AJ 47p		4F 493 40p	
						2N5451 2.3p		BC121AK 48p		4F 494 40p	
						2N5452 2.3p		BC121AL 49p		4F 495 40p	
						2N5453 2.3p		BC121AM 50p		4F 496 40p	
						2N5454 2.3p		BC121AN 51p		4F 497 40p	
						2N5455 2.3p		BC121AO 52p		4F 498 40p	
						2N5456 2.3p		BC121AP 53p		4F 499 40p	
						2N5457 2.3p		BC121AQ 54p		4F 500 40p	
						2N5458 2.3p		BC121AR 55p		4F 501 40p	
						2N5459 2.3p		BC121AS 56p		4F 502 40p	
						2N5460 2.3p		BC121AT 57p		4F 503 40p	
						2N5461 2.3p		BC121AU 58p		4F 504 40p	
						2N5462 2.3p		BC121AV 59p		4F 505 40p	
						2N5463 2.3p		BC121AW 60p		4F 506 40p	
						2N5464 2.3p		BC121AX 61p		4F 507 40p	
						2N5465 2.3p		BC121AY 62p		4F 508 40p	
						2N5466 2.3p		BC121AZ 63p		4F 509 40p	
						2N5467 2.3p		BC121BA 64p		4F 510 40p	
						2N5468 2.3p		BC121BB 65p		4F 511 40p	
						2N5469 2.3p		BC121BC 66p		4F 512 40p	
						2N5470 2.3p		BC121BD 67p		4F 513 40p	
						2N5471 2.3p		BC121BE 68p		4F 514 40p	
						2N5472 2.3p		BC121BF 69p		4F 515 40p	
						2N5473 2.3p		BC121BG 70p		4F 516 40p	
						2N5474 2.3p		BC121BH 71p		4F 517 40p	
						2N5475 2.3p		BC121BI 72p		4F 518 40p	
						2N5476 2.3p		BC121BJ 73p		4F 519 40p	
						2N5477 2.3p		BC121BK 74p		4F 520 40p	
						2N5478 2.3p		BC121BL 75p		4F 521 40p	
						2N5479 2.3p		BC121BM 76p		4F 522 40p	
						2N5480 2.3p		BC121BN 77p		4F 523 40p	
						2N5481 2.3p		BC121BO 78p		4F 524 40p	
						2N5482 2.3p		BC121BP 79p		4F 525 40p	
						2N5483 2.3p		BC121BQ 80p		4F 526 40p	
						2N5484 2.3p		BC121BR 81p		4F 527 40p	
						2N5485 2.3p		BC121BS 82p		4F 528 40p	
						2N5486 2.3p		BC121BT 83p		4F 529 40p	
						2N5487 2.3p		BC121BU 84p		4F 530 40p	
						2N5488 2.3p		BC121BV 85p		4F 531 40p	
						2N5489 2.3p		BC121BW 86p		4F 532 40p	
						2N5490 2.3p		BC121BX 87p		4F 533 40p	
						2N5491 2.3p		BC121BY 88p		4F 534 40p	
						2N5492 2.3p		BC121BZ 89p		4F 535 40p	
						2N5493 2.3p		BC121CA 90p		4F 536 40p	
						2N5494 2.3p		BC121CB 91p		4F 537 40p	
						2N5495 2.3p		BC121CC 92p		4F 538 40p	
						2N5496 2.3p		BC121CD 93p		4F 539 40p	
						2N5497 2.3p		BC121CE 94p		4F 540 40p	
						2N5498 2.3p		BC121CF 95p		4F 541 40p	
						2N5499 2.3p		BC121CG 96p		4F 542 40p	
						2N5500 2.3p		BC121CH 97p		4F 543 40p	
						2N5501 2.3p		BC121CI 98p		4F 544 40p	
						2N5502 2.3p		BC121CJ 99p		4F 545 40p	
						2N5503 2.3p		BC121CK 100p		4F 546 40p	
						2N5504 2.3p		BC121CL 101p		4F 547 40p	
						2N5505 2.3p		BC121CM 102p		4F 548 40p	
						2N5506 2.3p		BC121CN 103p		4F 549 40p	
						2N5507 2.3p		BC121CO 104p		4F 550 40p	
						2N5508 2.3p		BC121CP 105p		4F 551 40p	
						2N5509 2.3p		BC121CQ 106p		4F 552 40p	
						2N5510 2.3p		BC121CR 107p		4F 553 40p	
						2N5511 2.3p		BC121CS 108p		4F 554 40p	
						2N5512 2.3p		BC121CT 109p		4F 555 40p	
						2N5513 2.3p		BC121CU 110p		4F 556 40p	
						2N5514 2.3p		BC121CV 111p		4F 557 40p	
						2N5515 2.3p		BC121CW 112p		4F 558 40p	
						2N5516 2.3p		BC121CX 113p		4F 559 40p	
						2N5517 2.3p		BC121CY 114p		4F 560 40p	
						2N5518 2.3p		BC121CZ 115p		4F 561 40p	
						2N5519 2.3p		BC121DA 116p		4F 562 40p	
						2N5520 2.3p		BC121DB 117p		4F 563 40p	
						2N5521 2.3p		BC121DC 118p		4F 564 40p	
						2N5522 2.3p		BC121DD 119p		4F 565 40p	
						2N5523 2.3p		BC121DE 120p		4F 566 40p	
						2N5524 2.3p		BC121DF 121p		4F 567 40p	
						2N5525 2.3p		BC121DG 122p		4F 568 40p	
						2N5526 2.3p		BC121DH 123p		4F 569 40p	
						2N5527 2.3p		BC121DI 124p		4F 570 40p	
						2N5528 2.3p		BC121DJ 125p		4F 571 40p	
						2N5529 2.3p		BC121DK 126p		4F 572 40p	
						2N5530 2.3p		BC121DL 127p		4F 573 40p	
						2N5531 2.3p		BC121DM 128p		4F 574 40p	
						2N5532 2.3p		BC121DN 129p		4F 575 40p	
						2N5533 2.3p		BC121DO 130p		4F 576 40p	
						2N5534 2.3p		BC121DP 131p		4F 577 40p	
						2N5535 2.3p		BC121DQ 132p		4F 578 40p	
						2N5536 2.3p		BC121DR 133p		4F 579 40p	
						2N5537 2.3p		BC121DS 134p		4F 580 40p	
						2N5538 2.3p		BC121DT 135p		4F 581 40p	
						2N5539 2.3p		BC121DU 136p		4F 582 40p	
						2N5540 2.3p		BC121DV 137p		4F 583 40p	
						2N5541 2.3p		BC121DW 138p		4F 584 40p	
						2N5542 2.3p		BC121DX 139p		4F 585 40p	
						2N5543 2.3p		BC121DY 140p		4F 586 40p	
						2N5544 2.3p		BC121DZ 141p		4F 587 40p	
						2N5545 2.3p		BC121EA 142p		4F 588 40p	
						2N5546 2.3p		BC121EB 143p		4F 589 40p	
						2N5547 2.3p		BC121EC 144p		4F 590 40p	

The Flash Point Alarm is designed to warn when the temperature of fat or oil in a chip pan or deep fryer reaches a dangerous level. It will not prevent fires — only you can do that.

WARNING

**NEVER TURN YOUR
BACK ON A CHIP PAN**



Flash Point Alarm

Owen Bishop

FIRE Statistics for the UK clearly show that a large and increasing proportion of fires in the home begin in the kitchen. Of these, about 90 percent are fat fires. It does not seem to matter what kind of cooking fat is used; it could be vegetable oil, lard, dripping or margarine. Most people prefer chips and other fried food to be crisp rather than soggy, and for this the fat must be made really hot before the food is put into it. This is where the danger arises. Fat takes an appreciable time to warm up to a suitable cooking temperature (about 205°C). While this is happening, the cook may decide to get on with some other job (or even to pop quickly down the road to the corner store!) leaving the fat unattended.

Though it may heat slowly at first, the rate increases as the cooker warms up. After cooking temperature has been reached, it does not take that much longer for the fat to reach a temperature at which it is likely to catch fire. At temperatures higher than 310°C the fat is above its flash-point and may ignite spontaneously, even though it is not in contact with a naked flame. When the cook returns from that task which was to take "only a moment", the fat may well be alight — and possibly the house as well.

This project won't prevent chip-pan fires but it will give an alarm when the temperature reaches a dangerous level. It uses a thermocouple to sense the temperature of the fat; a thermocouple was chosen because it is able to operate over the range 0°C to 400°C. The circuit is set to trigger an alarm when the temperature of the fat is more than about 200 degrees higher than room temperature. The temperature of most kitchens is

between 10°C and 25°C, so the alarm sounds when the fat is at about 210°C. This allows the optimum cooking temperature of 205°C to be attained without triggering the alarm, yet provides a good margin between the triggering temperature and the lowest flash-point of commonly-used cooking fats.


The alarm signal takes two forms. There is an intermittent audible alarm loud enough to be heard in the next room (though it is *not* loud enough to be heard when you are down at the corner store!) and for those who are hard of hearing, there is also a visual alarm of two lamps, which flash alternately. The alarms can be external

How It Works


A THERMOCOUPLE is simply an electrical circuit formed by joining two dissimilar metals, eg copper and iron, into a loop. If the two junctions of the metals are held at different temperatures, an EMF is developed in the loop. The size of the EMF is proportional to the temperature difference between the junctions, so if one junction is held at a constant temperature, the EMF must be proportional to the temperature at the other junction.

The graph of the output of a Nickel-Chromium/Nickel-Aluminium thermocouple, similar to the type used in this project, shows the EMF developed versus the temperature difference between the thermocouple probe temperature and a reference temperature of 0°C.

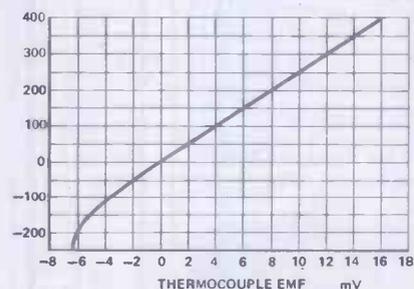The HE Flash Point Alarm uses room temperature as the reference



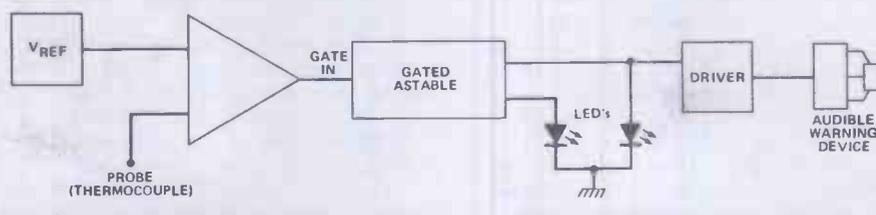temperature, and compares the EMF developed by the thermocouple with a reference voltage. The Alarm is triggered when the EMF rises to about 8 mV, corresponding to a temperature around 200° above room temperature. Note that the unit itself must not be placed where it can become heated above room temperature!



Project

to the device if required; for example, you may prefer to site the audible alarm in the hall or living room, rather than in the kitchen.

The instrument is battery-powered and takes only 6mA quiescent current. In this condition, LED2 glows to indicate that the device is switched on. The amount of current required when sounding the alarm is rather greater, but the instrument should never be left for long in this state, for obvious reasons!

The Circuit

The temperature sensor used in this project is a thermocouple, made by joining together two wires of different metals or metal alloys. Usually the wires are twisted together, then welded and owing to the 'contact potential difference', an EMF appears across the junction of the dissimilar metals.

The size of the EMF increases with temperature and in the thermocouple used in this project, it increases by about 4 μV per degree Celsius. The circuit is designed to trigger at about 200 degrees above room temperature. This gives a triggering temperature of around 210°C to 225°C, which means that fat at cooking temperature (205°C) does not trigger the alarm but fat which is hot enough to catch fire spontaneously (310°C or hotter) readily triggers it.

The EMF generated by the thermocouple is detected by an operational amplifier, IC1. This has an extremely high input impedance (10^{12} ohms) so that the full EMF appears at the input pin. The op-amp is wired as a comparator and there is no feedback, so the full gain of the amplifier (about 100,000) is available. The EMF of the thermocouple is compared with a voltage reference generated by a potential divider, R1/RV1, set to give 8 mV at pin 2 of the op-amp. If the EMF of the thermocouple is less than 8 mV, the output of the comparator is -3 V; if the EMF exceeds 8 mV, even by a small amount, the output swings sharply from -3 V to +3 V, as a result of the high gain.

Because IC1 is a CMOS op-amp, the output swings fully between -3 V and +3 V, giving a clean signal to control the alarm logic. This is made up from four NAND gates in a single IC (IC2). Two of these gates, IC2a and b are wired as an astable multivibrator with a frequency of about 1 Hz. When the output of the comparator is low (-3 V), the astable is inhibited and its output (IC2a) is high. This is inverted by IC2d, the output of which (pin 11) is low. Thus no current flows to Q1 and the audible warning device is inactive. LED 1 connected to this output is not lit but the output from the other gate of the astable (IC pin 4) is low (0V); this is inverted by IC2c, causing LED 2 to light, indicating that the circuit is switched on.

When the EMF of the thermocouple exceeds 8 mV (at a temperature more than 200 degrees warmer than room

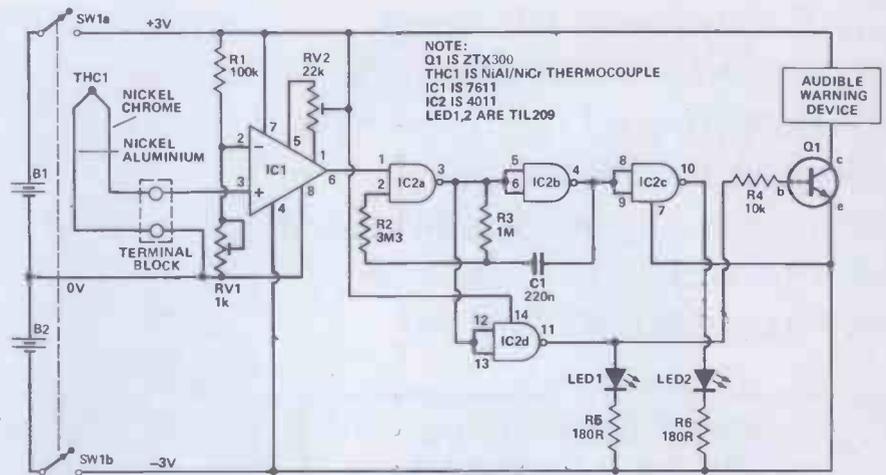


Figure 1. The circuit diagram.

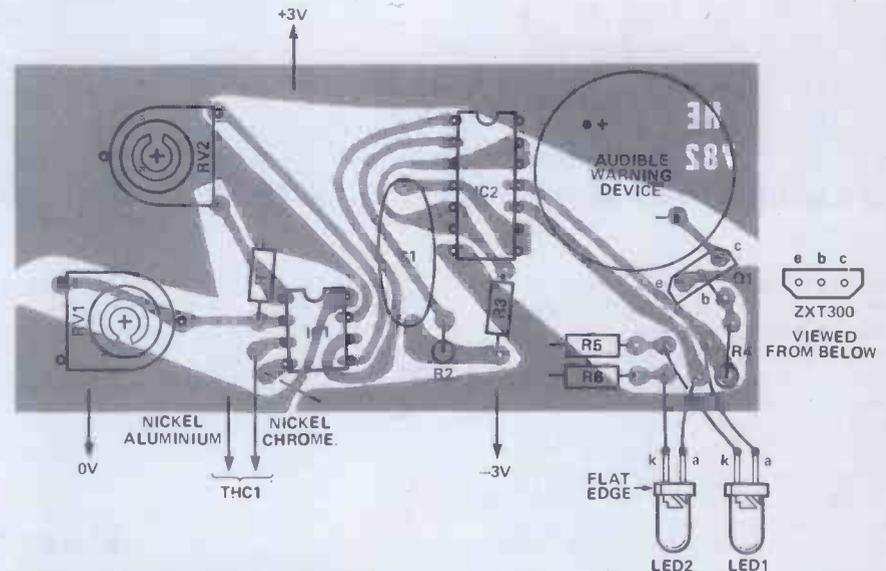


Figure 2. PCB assembly diagram. Remember not to handle the CMOS ICs!

temperature), the output of the comparator goes high, allowing the astable to oscillate. The LEDs flash alternately and the audible warning device is switched on intermittently, to give a bleeping alarm sound.

Construction

The layout (Figure 2) is designed for standard size presets, not the sub-miniature types. The ICs are both CMOS, so take the usual precautions to avoid static electrical charges on your clothes or body, and use a soldering iron with an earthed bit. Mount the ICs and all other on-board components except for R4 (the omission of R4 spares you, and your family, the piercing sound of the audible alarm while you are testing and setting up the remainder of the circuit). Note that single-sided terminal pins may be used, but those which connect to the LEDs should project through the copper side of the board, not the component side — the alternative is to use double-sided pins throughout.

The LEDs used in the prototype were a special kind, ready-mounted in a

chromium-plated bezel. These give a stylish appearance to the instrument, but the standard type with plastic mounts can be used instead. Mount the LEDs on the front panel and connect them by short wires to the pins on the circuit board.

The power supply is split to provide 3 lines; +3 V, 0 V and -3 V. The operational amplifier, IC1, was specially chosen for its ability to be able to operate from voltages as low as ± 3 V. The recommended case incorporates a battery compartment with metal tags, to which power leads may be soldered as shown in Figure 3. The switch is a double-pole double-throw (DPDT) type, connected to the +3 V and -3 V lines and mounted on the upper half of the case. Wire up the power lines at this stage, and connect them to the circuit board.

The circuit may be tested at this stage. Since the EMF of the thermocouple is only a few millivolts, the op-amp must be balanced by using the offset null adjustment, RV2, which connects pins 1 and 5 of the IC. While the op-amp is being balanced, both

Parts List

RESISTORS (All 1/4 W 5% carbon)
 R1 100k
 R2 3M3
 R3 1M
 R4 10k
 R5,6 180R

POTENTIOMETERS
 RV1 1k carbon preset
 RV2 22k carbon preset

CAPACITORS
 C1 220n
 C280 polyester

SEMICONDUCTORS
 Q1 ZTX300
 silicon NPN transistor
 IC1 7611
 CMOS op-amp
 IC2 4011B
 CMOS quad 2-Input NAND
 LED1,2 TIL209
 light emitting diode

MISCELLANEOUS
 S1 DPDT
 slide switch
 THC1 thermocouple
 (see Buylines)
 B1,B2 2 x 'AA' cells
 (3 V each pair)
 Audible warning device (see Buylines);
 case; two-way terminal block; veropins;
 plastic stick-on feet; connecting wire,
 solder etc.

BUYLINES page 30

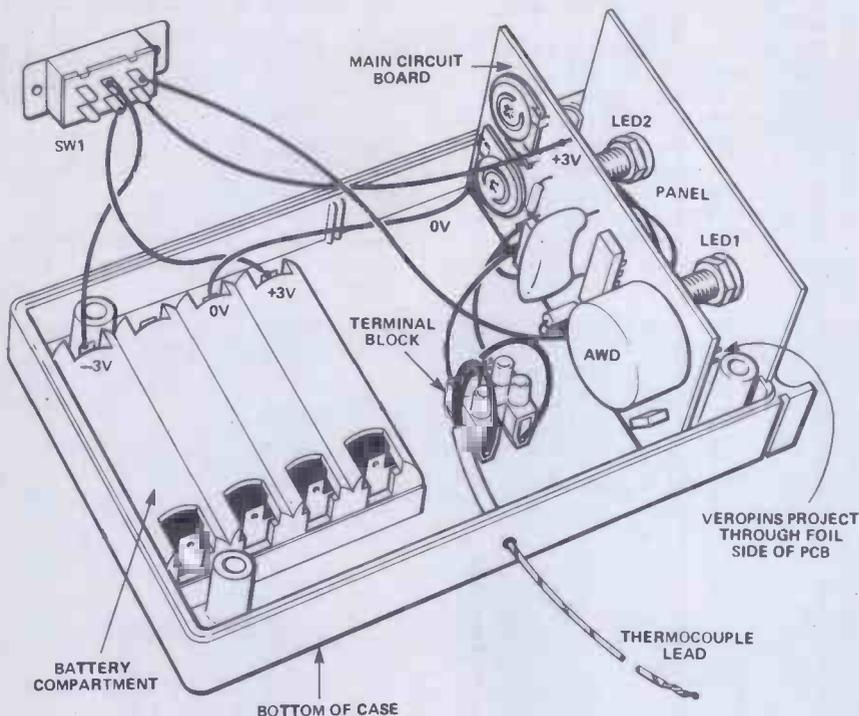


Figure 3. Fitting it all together.

inputs (pins 2 and 3) must be connected to the 0 V line using two test leads with crocodile clips. The easiest method is to join the two terminal pins (to which the thermocouple is to be attached later) with one lead and to connect the junction of R1/RV1 to 0 V with the other. A voltmeter or oscilloscope must be used to measure the output voltage between pin 6 of IC1 and the -3 V line. When all the above connections are made, switch on the power. LED2 comes on to show that the circuit is active. Ideally, RV2 should be adjusted so that the output is steady at 0V (the meter would read +3V, because you are measuring from the -3V line), but this is difficult. If it cannot be set exactly, adjust RV2 so that the output is just on the point of swinging from -3V to +3V (ie, 0V to 6V on the meter).

Remove the two test leads before proceeding further. Now connect the thermocouple (temporarily) to the terminal pins on the circuit board. A thermocouple normally has red (+ve) and blue (-ve) wires. The red wire (nickel-chrome) goes to pin 3 of IC1 and the blue wire (nickel-aluminium) goes to the 0V line. For the next stage, you will need a sensitive millivoltmeter with a high-impedance input - an ordinary low-cost multimeter may draw too much current to allow the levels to be set correctly. As an alternative, use an oscilloscope, but if neither of these instruments is to hand, you'll have to construct the HE Digital Millivoltmeter (August issue).

The first step is to set the potential at pin 2 of IC1; connect the millivoltmeter between the 0V line and pin 2, and adjust RV1 until the reading is 8 mV. Now attach the meter

between the 0V line and pin 3 of IC1 (the red wire of the thermocouple). It will probably show no reading at first, since the junction will be close to room temperature, so heat the junction by placing it in a hot oven (set to 230°C, 450°F or Gasmark 8).

As the temperature of the thermocouple rises, the reading on the meter should increase steadily. As the reading passes 8 mV, the circuit is triggered and the LEDs will begin to flash alternately, at about 1Hz. If you now remove the thermocouple from the heat, the flashing stops after a second or two.

If the LEDs fail to flash, check the operation of the oscillator, IC2a,b, by testing the output from pin 4. It should rise to +3 V and fall to -3 V sharply and regularly, at about 1Hz. The output at pins 10 and 11 (IC2c and d) should be similar, though 180° out of phase with pin 4.

If the circuit is not triggered by a thermocouple EMF of 8 or even 9 mV; it is likely that the offset null adjustment is not properly set. Keeping the thermocouple at a steady heat, so that its EMF is close to 8mV, adjust RV2 *very slightly* so that the output of IC1, at pin 6, swings from 0 V to +3 V and triggers the LEDs.

Assuming that all is in working order, solder R4 in position and re-test the circuit with the audible warning device (AWD) in operation. If it is to be mounted externally, solder long leads to the mounting holes on the PCB and run them through a hole cut in the side of the case. It is possible to wire two or more AWDs in parallel, all switched by Q1, should you want to make the alarm sound in several rooms at once.

Mount the two-way connector block on the lower half of the case and insert

the PCB and front panel in the slots. Run wires from the connector block to the thermocouple terminal pins on the PCB. The thermocouple itself is supplied with a long lead which may be cut shorter, if desired, but take care to insert the leads in the correct sockets; if the polarity is wrong the alarm will not be triggered, even by a raging inferno. For the same reason, make certain that the screws of the terminal block are firmly tightened. Every time you renew the cells, it is best to check that the connector block screws have not been loosened.

The two halves of the case may now be bolted together and stick-on feet applied to the lower surface. The Flash-Point Alarm is now ready for use. At this point, it would be advisable to make another test run, with the thermocouple in the oven as before, to check that all is as it should be. Always remember, the only certain way to prevent, a chip-pan fire is to keep a close watch on it at all times!

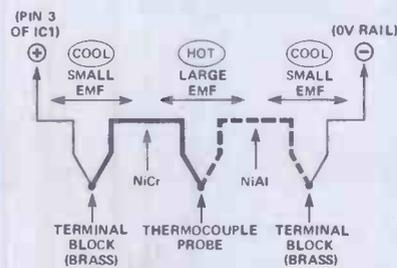


Figure 4. Three thermocouples.

Project

Three Thermocouples

Although you have purchased only one thermocouple, the circuit really contains three (Figure 4)! The other two are made when you screw the ends of the thermocouple wires into the metal contacts of the connector block; each of these wire-connector junctions is between dissimilar metals, so an EMF is produced. However, both of these junctions are at room temperature and their EMFs are relatively small; in addition, they are opposing EMFs, and so they cancel out. This leaves only the EMF at the nickel-chrome/nickel-aluminium junction in the chip pan, which is the one used to trigger the alarm.

Using It

The instrument should not be placed where it can be overheated by the cooker, because this could affect the triggering temperature. The thermocouple lead must be left long enough to allow the unit to stand on a table or work-top, a few feet from the cooking area. The lead can be bent into an inverted U shape, so that it hooks neatly on to the rim of the pan, with the thermocouple immersed in the fat (the lead could be clipped to the rim of the pan, using a small bull-dog clip). Switch on the instrument *before* beginning to heat the fat and check that the indicator, LED1, is glowing. The fat reaches cooking temperature before the circuit is triggered so, in

normal use, you should never hear or see the alarms in action.


If the alarms are triggered, there is immediate danger of fire, especially if the alarm has been going for several minutes with the heat still on. Switch off the heat immediately and do not leave the pan unattended until the alarm has stopped. If you attend to the pan as soon as the alarm is raised, it should not be hot enough to ignite spontaneously but, if you leave it longer, it might! Should the fat catch

fire, this is how the deal with it:

- 1) Turn off the heat.
- 2) Cover the pan with a large lid or a large damp cloth, to keep air away from the fire.

Two things you should NOT do are to try to move the pan, or to throw water over it. And never panic! — but with the Flash-Point Alarm, you should never need to worry about anything except how brown you want the chips to be!

HE

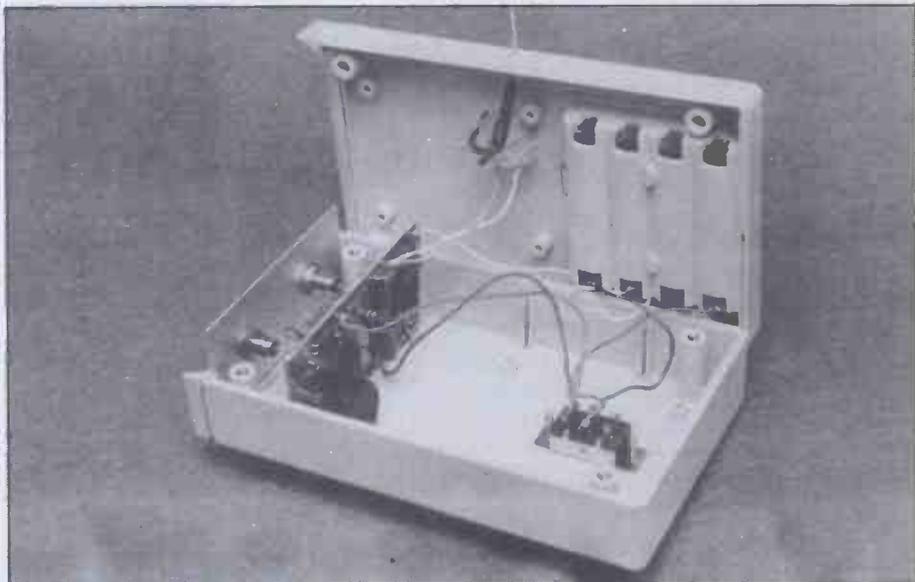

MODULES FOR SECURITY & MEASUREMENT

INTRUDER ALARM CONTROL UNIT CA 1250

AS FEATURED IN PRACTICAL ELECTRONICS



only £19.95 + VAT

- Built-in electronic siren drives 2 loud speakers
- Provides exit and entrance delays together with fixed alarm time
- Battery back-up with trickle charging facility
- Operates with magnetic switches, u/sonic or I.R. units
- Anti-tamper and panic facility
- Stabilised output voltage for external units
- 2 operating modes - full alarm/anti-tamper and panic facility
- Screw connections for ease of installation
- Separate relay contacts for switching external loads
- Test loop facility

This exciting new module offers all the possible features likely to be required when building an intruder alarm system. Whether used with only 1 or 2 magnetic switches or in conjunction with several ultrasonic alarm modules or infra-red units, a really effective system can be constructed at a fraction of the cost of comparable ready-made units. Supplied with a fully explanatory Data Sheet that makes installation straight forward, the module is fully tested and guaranteed.

*available in kit form £16.95 + VAT

ULTRASONIC ALARM MODULE US 4012

Fully built & tested

only £10.95 + VAT



Adjustable range from 5ft. to 25ft.

A really effective fully built module containing both ultrasonic transmitter and receiver and circuitry for providing false alarm suppression. This module, together with a suitable 12V power supply and relay unit as shown, forms an effective though inexpensive Intruder alarm. Supplied with comprehensive Data Sheet, it is easily mounted in a wide range of enclosures. A ready-drilled case and necessary hardware is available below.

DIGITAL VOLTMETER MODULE DVM 314

Fully built & tested



only £11.95 + VAT

- Positive & negative voltage with an FSD of 999mV which is easily extended
- Requires only single supply 7-12V
- High overall accuracy - 0.1% + 1 digit
- Large bright 0.43" LED displays
- Supplied with full applications data

With this fully built and calibrated module a wide range of accurate equipment such as multimeters, thermometers, battery indicators etc. can be constructed at a fraction of the cost of ready-made units. Full details are supplied for extending the voltage range, measuring current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, government departments, etc.

Temperature Measurement Kit DT.10

£2.25 + VAT

Using the I.C. probe supplied, this kit provides a linear output of 10mV°C over the temperature range from 10°C to +100°C. The unit is ideal for use in conjunction with the DVM module providing an accurate digital thermometer.

Power Supply PS.209

£4.95 + VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V, 250mA each. The unit is ideally suited for operating the DVM at Temperature Measurement module.

Power Supply & Relay Units PS 4012

£4.25 + VAT

Provides a stabilised 12V output and relay with 3A contacts. The unit is designed to operate one or two of the above ultrasonic units. Fully built and tested.

Siren Module SL 157

£2.95 + VAT

Produces a loud and penetrating sliding tone operating from 9-15V. Capable of driving 2 off 8 ohm speakers to SPL of 110db at 2M.

Contains an inhibit facility for use with shop lifting loops etc. or other break to activate circuits

Hardware Kit HW 4012

£4.25 + VAT

A suitable ready-drilled case with the various mounting pillars, mains switch socket and nuts and bolts. Designed to house the ultrasonic alarm module together with its power supply. Size: 153mm x 120mm x 45mm.

ACCESSORIES

- 3-position Key Switch for use with CA 1250 supplied with 2 keys £3.43
- Magnetic switch (with magnet) £1.17
- 5" Horn speaker for use with SL 157 £4.95

Add VAT & 50p post and packing to all orders.

Shop hours 9.00 - 5.30 p.m. (Wed. 9.00 - 1.00 p.m.)

Units on demonstration - callers welcome. S.A.E. with all enquiries.



RISCOMP LIMITED

Dept: ETI 10
21 Duke Street,
Princes Risborough, Bucks.
Princes Risborough (084 44) 6326

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

A PRACTICAL DIGITAL ELECTRONIC KIT FOR

★ LESS THAN £20 ★



SUITABLE FOR BEGINNERS

NO SOLDERING!

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains: seven LS TTL integrated circuits, breadboard, LEDs, and all the DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19.90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits.

DIGITAL COMPUTER DESIGN £8.50 NEW!

An up-to-date course on the design of digital computers - from their individual logic elements and from integrated circuits. You are first shown the way in which simple logic circuits operate and then, through a series of exercises, arrive at a design for a working machine.

This course, as well as our beginners' theory course, Digital Computer Logic and Electronics, supports the practical Superkit series.

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 98 RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND. TELEPHONE: ST IVES (0480) 67446. VAT No 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159. Please allow 28 days for delivery in UK.

-SUPERKIT(S) @ £19.90
-DIGITAL COMPUTER DESIGN(S) @ £8.50
-DIGITAL COMPUTER LOGIC AND ELECTRONICS @ £6.00

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club
Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446
Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, UNIT 99, Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No 1328762).

Bradley Marshall

LTD
OF EDGWARE ROAD

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS

Tel: 723-4242

PROBABLY THE LARGEST STOCK OF ICs & TRANSISTORS IN THE SOUTH TRY US FIRST

LARGE RANGE OF ACCESSORIES

Plugs
Sockets
Audio Connectors
Veroboards
IC Sockets
Soldering equipment
Screw drivers
(BAHCO)
Sifam Knobs
etc.

LARGE RANGE OF ICs

Transistors
Capacitors
Diodes
Triacs
Thyristors
Opto
Resistors
Potentiometers
Fuses
Bridges
Please send S.A.E. for list.

SPECIAL OFFER

STEINAL
MULTICHECK
£7.50
+ VAT

Normal price £10.26

BUY WITH ACCESS BARCLAYCARD A/EXPRESS DINERS

Just phone we do the rest

MAIL ORDER FASTER SERVICE PHONE 723-4242

16, 24, 40 WAY
RIBBON CABLE
£1.10; £1.40; £2.20
metre

Header plugs 14 way,
16 way, 24 way, 40 way

BAHCO TOOLS SIDE CUTTERS

2132 £7.10
2112 £9.40

END CUTTERS
2211 £10.43

PLIERS

2411 £6.75
2415 £6.78

ICE MULTIMETERS

Microtest 80 £16.60
Supertest 680 R £32.00
Supertest 680E £24.50

EXPERIMENTER BREADBOARD'S

EXP 325 EXP 600
EXP 350 EXP 650
EXP 300 EXP 4B

LOGIC PROBES

LP1 £31.00
LP2 £18.00

EXPERIMENTER KITS

PB6 £9.20
PB100 £11.80

PLEASE REMEMBER To ADD 15% VAT

BRADLEY MARSHALL LTD FOR

Crimson Elektrik

PROFESSIONAL AMPLIFIER MODULES


PRICE LIST -
ELECTRONIC MODULES & ASSEMBLIES - APRIL 1981

CODE	DESCRIPTION	Less VAT	INC	WT (Kg)
		VAT	VAT	
		£	£	£
CE 608	Power Amplifier Module	18.26	2.74	21.00 0.16
CE 1004	Power Amplifier Module	21.30	3.20	24.50 0.20
CE 1008	Power Amplifier Module	23.90	3.60	27.50 0.21
CE 1704	Power Amplifier Module	30.43	4.57	35.00 0.22
CE 1708	Power Amplifier Module	30.43	4.57	35.00 0.22
CE 3004	Power Amplifier Module	42.60	6.40	49.00 0.40
BD 1	Bridge Driver Module	7.13	1.07	8.20 0.06
TR 80	Toroidal Transformer 80VA	18.00	2.70	20.70 2.00
TR 150	Toroidal Transformer 150VA	20.07	3.01	23.08 2.35
TR 250	Toroidal Transformer 250VA	25.43	3.81	29.24 3.35
TR 250Q	Toroidal Transformer (low noise)	33.20	4.98	38.18 2.80
B 6	Bridge Rectifier (6 amp)	0.99	0.15	1.14 0.02
B12	Bridge Rectifier (12 amp)	1.80	0.27	2.07 0.03
C4700/40	Reservoir Capacitor and Clip	1.91	0.29	2.20 0.09
C4700/63	Reservoir Capacitor and Clip	2.40	0.36	2.76 0.11
C4300/63	Reservoir Capacitor and Clip	2.60	0.39	2.99 0.11
CPS 80	Power Supply	22.82	3.42	26.24 2.10
CPS 80D	Dual Power Supply	27.63	4.14	31.77 2.25
CPS 150	Power Supply	25.86	3.88	29.74 2.50
CPS 150D	Dual Power Supply	31.65	4.75	36.40 2.60
CPS 250	Power Supply	32.03	4.80	36.83 3.50
CPS 250D	Dual Power Supply	39.43	5.91	45.34 3.65
TS 70	Thermal Switch 70°C	1.92	0.29	2.21 0.02
HS 50	50mm Heatsink	1.60	0.24	1.84 0.15
HS 100	100mm Heatsink	2.60	0.39	2.99 0.30
HS 150	150mm Heatsink	3.65	0.55	4.20 0.45
FM 1	Fan Mounted on 2 x HS 100	32.13	4.82	36.95 1.20
FM 2	Fan Mounted on 2 x HS 150	36.10	5.42	41.52 1.50
CPR 1X	Pre-Amplifier Module	31.30	4.70	36.00 0.15
MC 2	Moving Coil Pre-Pre-Amplifier Module	20.00	3.00	23.00 0.07
REG 1	Regulated Power Supply	8.09	1.21	9.30 0.07
TR 6	6VA Mains Transformer	2.87	0.43	3.30 0.21
XO 2	2 Way Crossover Module	17.39	2.61	20.00 0.07
XO 3	3 Way Crossover Module	26.09	3.91	30.00 0.07
MU 1	Muting Circuit for XO 2 or XO 3	8.35	1.25	9.60 0.04
CK 1010	Complete Pre-Amplifier Kit	78.26	11.74	90.00 2.50
CK 1040	Complete 40 Watt Power Amplifier Kit	103.48	15.52	119.00 7.30
CK 1100	Complete 100 Watt Power Amplifier Kit	129.56	19.44	149.00 7.30
MC 2K	Add On Moving Coil Kit	21.74	3.26	25.00 0.12
PSK	Pre-Amplifier Power Supply Kit	17.39	2.61	20.00 0.75

SOLE DISTRIBUTION BRADLEY MARSHALL LTD OF EDGWARE RD
325 EDGWARE RD, LONDON W21 BN
TEL: 01-723 4242

ELECTRONIC IGNITION

Makes a good car better

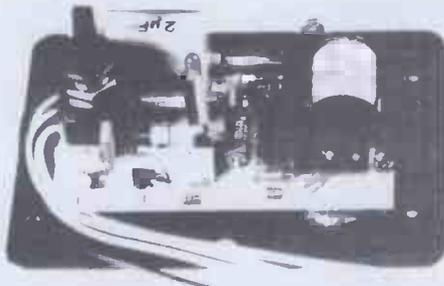

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

- PEAK PERFORMANCE** — higher output voltage under all conditions.
- IMPROVED ECONOMY** — no loss of ignition performance between services.
- FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.
- ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.
- SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

- SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.
- OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.
- BETTER STARTING** — full spark power even with low battery.
- CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.
- L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.
- LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.
- DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue
and EVERYDAY ELECTRONICS December '81 Issue

FIRES ALL NEGATIVE EARTH VEHICLES,
6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS
Some older current impulse types (Smiths pre '74) require an adaptor —
PRICE £2.95

STANDARD CAR KIT £14.85
Assembled and Tested £24.95

TWIN OUTPUT KIT £ 22.95
For MOTOR CYCLES and CARS with twin ignition systems
Assembled and Tested £ 34.70

PLUS
£1.00
U.K.
P. & P.
Prices
include
VAT.

ELECTRONIZE DESIGN

Dept. D Magnus Road, Wilnecote
Tamworth, B77 5BY
Phone: (0827) 281000



DIMENSIONS:
Length 12.5 cm
Width 8.9 cm
Height 4.3 cm
Lead length 100.0 cm

TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µs at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the **TOTAL ENERGY DISCHARGE** system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

SUPER POWER DISCHARGE CIRCUIT A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

HIGH EFFICIENCY INVERTER A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

PRECISION SPARK TIMING CIRCUIT This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

TYPICAL SPECIFICATION

	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY	36 mJ	10 mJ
(STORED ENERGY)	135 mJ	65 mJ
SPARK DURATION	500 µs	160 µs
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	28 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µs	30 µs

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

FAULT-FINDING FOR BEGINNERS

Fault-finding, on a newly completed project or even on commercial equipment, is easy — once you know the rules!

FAULT-FINDING on a project can be a time-consuming job. Even experienced electronics engineers will sometimes spend hours looking for a reason why a particular circuit doesn't work - so what chance has the hobbyist got, of quickly locating faults? Occasionally, a fault will be obvious, but more often than not it will remain hidden away, after many hours' of hard slog to detect and then repair it.

Prevention Is Better Than Cure

There are many categories of possible faults, but the more usual ones occur because of a mistake. For instance, it's all too easy to misread the resistor colour code and put an incorrect value into the circuit. Of course, in some cases a small change may not make any difference, but in other circuits resistances can be critical — and you may find that a project simply doesn't work at all just because you've inserted a 100k resistor instead of a 120k. The moral of the story is to *make sure you know the colour code.*


Similarly, an incorrect capacitor value may prevent a circuit from operating according to plan while polarised components ie, transistors, integrated circuits, diodes and certain capacitors, have to be inserted the right way round, for obvious reasons.

Another builder-originated source of faults is to do with soldering. A single dry-joint can affect performance and may prevent the circuit from working at all. Soldering technique improves with practice, so fewer and fewer soldering problems should arise the more projects you make. But dry-soldered joints aren't the only type of fault which can be caused by slap-happy soldering; in its hot state solder is, of course, molten, and unless care is taken it can form conducting bridges to copper tracks close by the soldering joint. Even a microscopically thin solder bridge can form a short circuit and prevent your project from working.

Occasionally, too, a circuit will malfunction due to a faulty component, but it is the exception to the rule.

Most suppliers thoroughly screen the components they sell and it is unlikely that a component will be faulty at the time of purchase. It can happen however, that a component may be damaged by mis-handling — some components are quite 'fragile'. Always take particular care with CMOS ICs, which can be easily destroyed by static discharge. Never touch the pins, and always solder the supply pins before moving onto the input/output connections.

Beasties

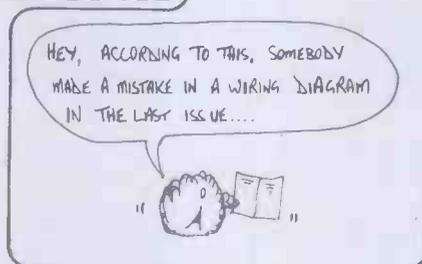

Begin At The Beginning

OK, you've taken all the right precautions, worked carefully and finally completed the project. Now the magic moment — power on! WAIT! There's something you should do first; *check everything once more.* Many faults can actually be detected before you switch on, and that's the best time to find them. A smoking resistor may precisely pinpoint a fault — but it could also destroy many valuable components in the process. Far better to check first.

- Look at the components; are they all in the right places, according to the component overlay diagram? Are all the polarised components inserted the right way round?
- Look underneath the PCB or Veroboard, on the copper side; check carefully for solder bridges or stray bits of wire, component leads not trimmed etc. Particularly check around the power supply connections; if something is going to 'blow', it will probably be caused by an incorrect connection to the power rails. Solder bridges can be very fine and difficult to detect, so if your project is using expensive components, the time spent going over the board (with a jeweller's eyeglass, if possible) is time well spent.
- Finally, check for dry joints. All soldering connections should be clean and bright. A dull, mottled joint is probably a dud, though they aren't always that obvious.

Once these pre-switch-on observations have been completed, it's time to apply the volts. But remember, those first few seconds, just after you hit the switch, can tell you a lot about the nature of a fault. For example, if the project is an amplifier, say, you might get a high pitched whine for a very few seconds, after which the project just lies there like a stale loaf in a bakers shop or it may be some other strange, unexpected results. The point is

that those first few moments just may be the only clue you have!

Crash, Bang, Wallop

There, you've done it, now. Switched on the power, only to find well, something other than what you expected. But wait a minute. What did you expect? Very few circuits will actually do anything, at first, since there are usually a series of adjustments, setting-up operations and so on to be completed before a project will 'work'. Never mind just for the moment, you are simply looking to see that nothing disastrous is happening. If it's a common or garden variety mutant-blaster (originally from the planet Zorg), then why is R23 glowing red hot?

If R23 is glowing, then switch off immediately. It takes only fractions of a second to 'cook' an expensive component so, at the first sign of a serious fault, the sooner you switch off the better.

At this stage you should be using your eyes, ears and nose (an overheated resistor has a very distinctive smell which you will probably come to recognise!) but not your fingers, please. It's a good idea to take notes, too, because it's all too easy to forget something which may provide the vital clue to the location of the fault.

What happens next depends on the results after power-on. If the project immediately began to smoke, then something is obviously very wrong. On the other hand, perhaps it just lays there, harmlessly. A third possibility is that everything looks alright but, after performing all the adjustments and so on, it still lies there, uselessly.

The Golden Rules

Assuming, for the moment, that something is drastically wrong, it's time to follow the First Rule of Fault-Finding, which is this: "Look For The Simplest Faults First". If the circuit was overheating, check the board again, looking

Feature

for incorrect resistor values, short circuits, incorrect supply connections etc. Here's where those first observations will pay off; if R23 was smoking then it's safe to assume that the fault lies in that area of the circuit.

Check the supply voltages; it's surprising how often a 'brand new battery' will turn out to be an old, overused one that should have been thrown out but somehow got mixed up with a new one! If the circuit is mains-powered, disconnect the DC supply to the circuit and check the off-load voltage. If the positive supply is fused, have you remembered to put a fuse in? (don't laugh, it could happen to you!).

After checking and re-checking all the obvious things, without finding a clue to the fault, it is time to consider the Second Law: "When In Doubt, Read The Manual" (or the Circuit Description/How It Works or whatever). Read all about it and try to understand, firstly, the result you should be getting and secondly, the result you are getting. You should assume, at this stage, that the fault is caused by an error on your part. Yes, of course you're perfect (aren't we all?) but it is nevertheless true that 99% of faults are caused by an error in construction, so don't immediately write off to the editor, or complain to the component supplier.

Even if you suspect that your problem is caused by that stray 1%, don't just give up. Study the circuit closely, comparing it with the component overlay and all the other information printed in the magazine. Errors in published projects are usually very obvious, once you know where and how to look. With stripboard construction, for example, a common problem is the omission of one or two track breaks — cuts in the copper strips — so if you suspect this, check the component layout against the circuit, making sure that there are no components connected on the board which are not connected in the circuit. Ask yourself, for example, should the collector of that transistor *really* be connected to the OV rail? This procedure will often produce results with projects on PCB, too.

Look for circuit blocks which are repeated, eg, op-amp units, and try to 'spot the difference'. The more work you can put in at this stage, the sooner your project will be alive and well — and the more you will learn about electronics, too. Also, a single dead component is a lot easier to replace than an entire circuit board!

Blocks And Chains

Now, we're just about out of rules. The remaining one is best expressed as "Divide And Conquer". It works like this.

Most circuits consist of a number of circuit elements — amplifiers, oscillators, filters and so on — linked in chains, or connected together in some other, more complicated fashion.

The block diagram, Figure 3, shows an example of the circuit blocks of HE's Echo-Reverb project, from the May '82 issue.

The principle of the last rule is simply to isolate sections of the circuit until the

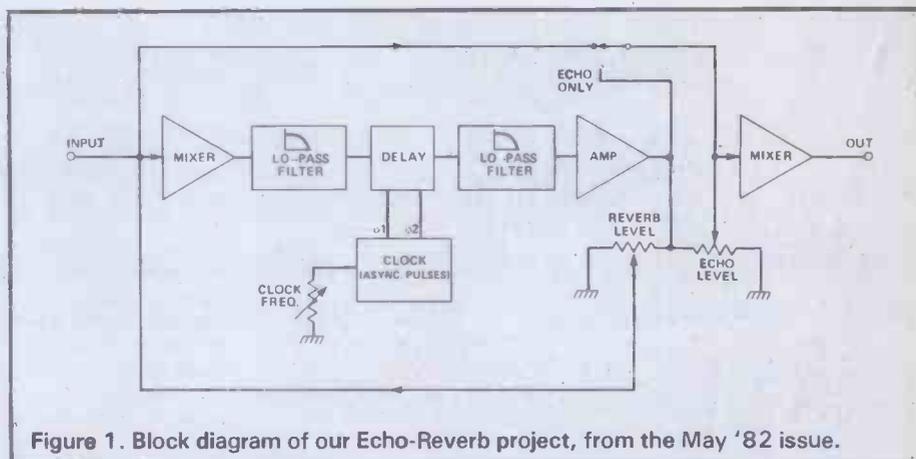


Figure 1. Block diagram of our Echo-Reverb project, from the May '82 issue.

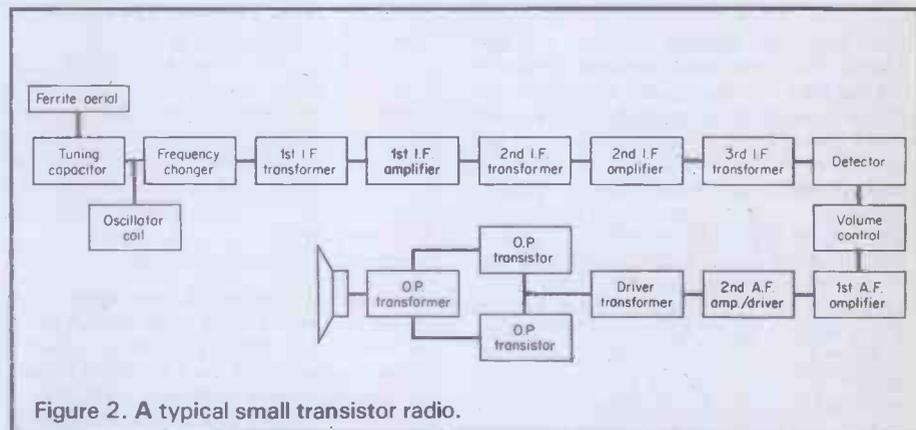


Figure 2. A typical small transistor radio.


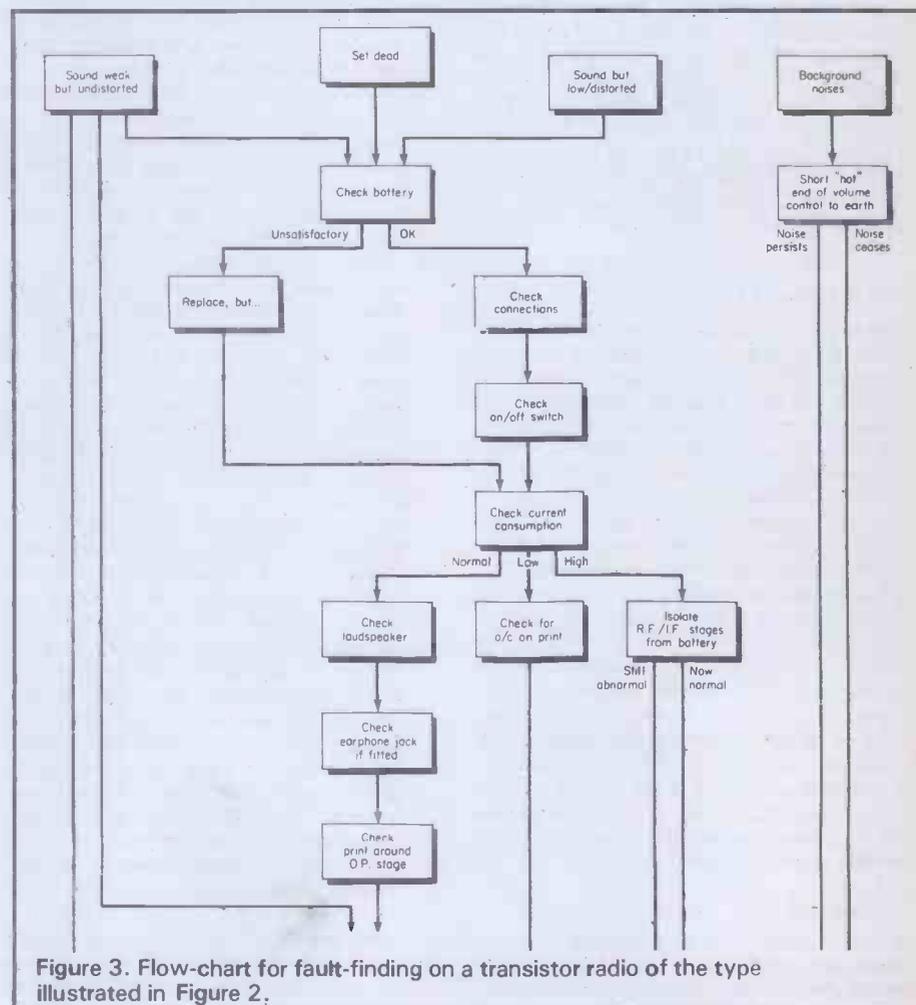


Figure 3. Flow-chart for fault-finding on a transistor radio of the type illustrated in Figure 2.

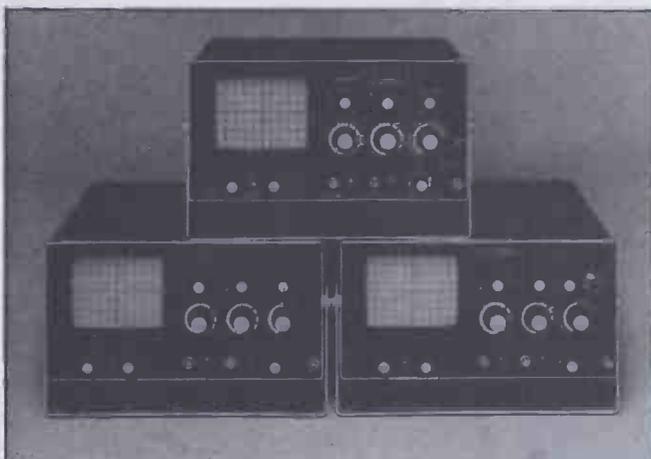

A 'scope is a technician's best friend! A small model, such as any one of the Scopex models shown, will more than repay the investment if you are working on a good number of projects, while for professional (or even semi-professional) work, a 'scope is essential.

fault has been pinned down to a single block. The exact method used depends on the type of circuit; with straight-chain circuits, such as an audio amplifier or an AM radio receiver, the recommended approach is to start in the middle. If the circuit is working correctly at that point proceed towards the output end, until you locate the stage where the signal is lost. If there is no signal present at the mid-point, then the fault obviously (well, probably) lies towards the 'input' end of the chain, so work back in that direction.

Above all, fault-finding at this level requires a calm, logical common-sense approach. If you know how the circuit works and what it is supposed to be doing, you stand a good chance of being able to figure out the block in which the fault lies. The diagrams of Figures 2 and 3 show the block diagram of a typical, small transistor radio, together with a section of a fault-finding chart. The chart illustrates the advantages of a logical approach; simply by asking the right questions, the correct answer becomes obvious and the location of the fault can be found.

What Next?

Once you've decided in which block the fault lies, look at the circuitry of the block itself and once again apply the Golden Rules. Carefully check the PCB area and each component for physical defects. You know the fault is there, somewhere — it's just a matter of finding it! Perhaps the body of a resistor is cracked, or one of the IC's pins has been bent underneath. Try tapping components very lightly with the insulated end of a small screwdriver; this trick will often turn up a bad solder joint or duff component. If overheating seems to be the problem, use an aerosol freezing spray to cool down the suspect component; if the fault suddenly vanishes, you've at least isolated the component. Now you only have to find out why its overheating! These two 'tricks of the trade' are the most effective methods for locating intermittent faults — those which come and go!

Tools of the Trade

Fault finding without instruments is impossible. If you've come this far without even a multimeter then you're some undiscovered genius who should be writing

this, rather than reading it!

A multimeter is simply the most common and most useful tool of the electronics trade. Already, a multimeter will have been used to isolate the fault to a particular circuit block, but it's when you're locating the faulty component that a meter is really essential for the following tests:

- Measure the supply voltages on all ICs; be sure to use probes with sharp points for this, to avoid bridging two adjacent pins. You should know the voltages (or range of voltages — they're rarely exactly as marked on the circuit) to expect, and where to find them. If you find an incorrect reading, track along the copper, looking for breaks, shorts etc.
- Measure the voltages around suspect transistors; although the actual readings will depend on the circuit configuration, in general the collector of an NPN transistor that is normally conducting will be positive with respect to the emitter (negative for PNP), but the voltage will be somewhat less than the positive rail. The base should be at least 0V6 more positive than the emitter (0V6 negative, for PNP). If the transistor is normally cut off, the base voltage will be less than 0V6 above the emitter, or even negative (for NPN), while the collector will be at the positive supply voltage, give or take a volt or so.
- Measuring in-circuit resistance, eg, when checking for a high resistance dry joint, it can be quite frustrating because the components in the circuit will obviously affect the reading; the only certain way to measure resistance in-circuit is to isolate, by lifting components or (in extreme cases only) cutting the circuit tracks. These measures may also be necessary if you suspect that a faulty component or group of components are responsible for an incorrect voltage reading (Divide And Conquer, remember?). Some meters, such as the Teston meter reviewed in last month's issue, have a special range for measuring in-circuit resistance, and this facility is very useful (as the reviewer mentioned) for taking resistance readings around transistors or diodes.

Scope For Improvement

For most hobbyists, owning test equipment other than a multimeter is something of a luxury. However, there are several other items which can be built cheaply; an audio signal generator (HE May 82 issue) is quite adequate for work on audio circuits. A simple audio amplifier with a high impedance, AC-coupled input (to isolate DC levels in the circuit under test) or even a high impedance earphone, is invaluable for tracing the signal path through an amplifier. An audio/RF signal injector/tracer (HE August 79; April 82) is slightly more versatile, as it can be used on AM radio circuits as well.

This list could go on indefinitely, because the more complicated circuit-require more specialised test equipment. In general, though, there is one item which, though expensive, is useful for almost all fault-finding and totally essential for work on some kinds of circuits, and that is an oscilloscope. If you are going to be 'into electronics', either as a long-term hobbyist or as a semi-professional, say, then a 'scope is a very worthwhile investment.

Extracting The Digit

A 'scope is usually necessary for fault-finding on digital circuits, where correct operation depends not on voltage levels but on the presence (or absence) of a fixed-level pulse which is too fast to register on a multimeter. The only way pulses can be observed is either on a 'scope, or by using a special logic probe. It is also important to understand the logic of the circuit, from the truth tables of simple AND, OR, NOR and NAND gates through flip flops, registers and so on, to the logical combination of the elements used in the circuits. The Model Train Lights Controller project, published last month, for instance, was a good example of a sequential logic circuit in which correct operation depends on the logic state of particular inputs and the state of the logic elements which resulted from the last sequence of inputs! The timing diagrams, tracing the effect on the circuit of a sequence of inputs, are an important fault-finding tool for this type of circuit!


The Final Secret

To conclude, I will now reveal the most important secret of fault-finding: experience. There is no substitute, so when your project just lies there limply, don't get frustrated and annoyed, or throw it against the wall! Roll up your sleeves and get on with it. Sooner or later the circuit will burst into life, and you will discover that you've learned a lot about electronics, in the process. Happy Hunting!

Our thanks to Bernard Babani (publishing) Ltd. for permission to reproduce the diagrams of Figures 2 and 3 from their "Transistor Radio Fault-Finding Chart" by Chas E. Miller; publication number BP70, price 50p.

COMING SOON TO . . .

Hobby Electronics

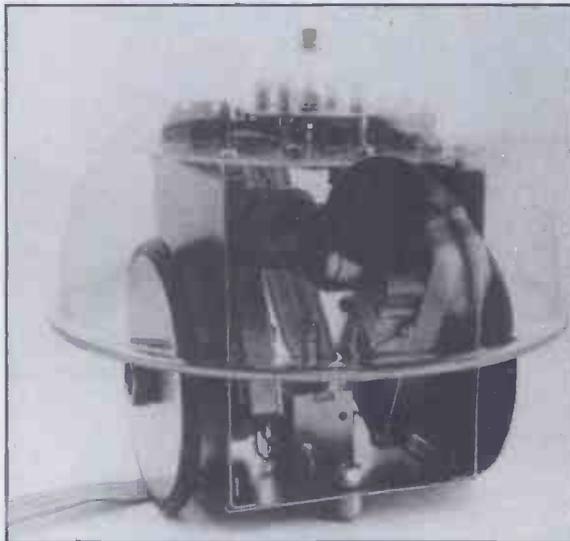

HEBOT II

HEBOT Rolls Again

Way back in November 1979 we published one of the first ever mobile robot projects, which we christened HEBOT. It proved to be enormously popular and, judging by the mail we still receive, reader's enthusiasm for simple robotics has not decreased over the years!

HEBOT has long since 'passed on' but now, in conjunction with Powertran Ltd., we are proud to present its successor.

HEBOT II is a very similar animal — er, robot — but using today's more sophisticated circuitry and operating under the control of a microcomputer. Like the original, it is a 'turtle' robot, propelled by two large, independently controlled rubber wheels which enable it to perform a wide variety of movements. Obstacle-sensors allow it to explore its environment, discovering the limits of movement or the shape of a room, or it can draw patterns or graphs using a pen, which presses down on command. Its blinking eyes and on-board beeper can be programmed to communicate with the operator, eg to indicate that it has finished a task.

The projected cost of this educational and inspirational robot is around £75, and it is initially intended to be controlled via a Sinclair ZX81 microcomputer — though future developments will open still greater possibilities. Look out for HEBOT II in the November issue of Hobby Electronics.

BREADBOARD SHOW GUIDE

A free guide to the most popular hobby electronics show of the year.

THE HE PEDOMETER/ODOMETER

Promised long ago and now, finally, delivered!

The Pedometer/Odometer is a digital device which can be individually programmed to read the distance travelled by a walker or jogger or used as a bicycle mileage indicator.

Please reserve copies of the November issue of

**Hobby
Electronics**

for

Name

Address



**Hobby
Electronics**

**November issue on sale at
your newsagent
from 15th October.**

Place your order now!


Although these articles are being prepared for the next issue, circumstances may alter the final content.



makes soldering easy fast & reliable

Ersin Multicore

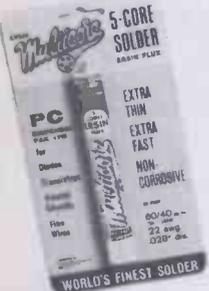Ersin Multicore, solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required. Comes in handy dispensers and tool box reels in two different alloys 40/60 tin/lead for general purpose electrical soldering and 60/40 tin/lead ideal for small components and fine wire soldering.



Size 3 40/60 tin/lead
£4.37 Per reel 1.6mm dia
Size 10 60/40 tin/lead
£4.37 Per reel 0.71mm dia



Size PC115 60/40 tin/lead
£1.38 Handy pack 0.028mm dia

Multicore Savbit

Multicore Savbit, solder increases the life of your soldering bit by 10 times, for better soldering efficiency and economy. Comes in two handy dispensers and tool box reels.



Size 12 Savbit
£4.37 Per reel 1.2mm dia



Size SV130 Savbit
£1.73 Per pack 0.048mm dia

Multicore Alu-Sol

Multicore Alu-Sol, solder contains 4 cores of flux, suitable for most metals especially aluminium. Comes in handy dispensers on tool box reels.

Size AL150 Alu-Sol
£2.07 Per pack .048mm dia



Size 4 Alu-Sol
£7.82 Per reel 1.6mm dia



Multicore Solder Wick

Multicore Solder Wick, absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.

Size AB10 Solder Wick
£1.43 Per pack



Multicore Tip Kleen

Multicore Tip Kleen, soldering iron tip wiping pad. Replaces wet sponges.



Size 2 Tip Kleen
£0.92 Per pack

Bib Wire strippers and cutters

Wire strippers and cutters, with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.



Size 9 Wire Strippers
£2.69 Per pair

Bib Audio/Video Products Limited
(Solder Division), Kelsey House,
Wood Lane End, Hemel Hempstead,
Hertfordshire, HP2 4RQ.
Telephone: (0442) 61291
Telex: 826437

All prices inclusive of VAT.
Available from most electrical and DIYs stores. If you have difficulty in obtaining any of these products send direct with 50p for postage and packing. For free colour brochure send S.A.E.

Probably the fastest microcomputer
in the universe

the **JUPITER ACE** only £89.95.



All inclusive Price

For £89.95 you receive your Jupiter Ace, a mains adaptor, all the leads needed to connect to most cassette recorders and T.V.s (colour or black and white), a software catalogue and a manual.

The manual is a complete introduction to the world of personal computing and a course in FORTH programming on the Ace.

Even if you are a complete newcomer to computers, the manual will guide you step by step from first principles to confident programming.

The price includes postage packing and V.A.T.

Key Features

- Revolutionary microcomputer language FORTH.
- Full-size moving-key keyboard.
- User-defined high-resolution graphics.
- Programmable sound generator.
- Floating point arithmetic.
- Fast cassette interface.
- Upper and lower case ascii character set.
- 24 x 32 character flicker-free display.

The Jupiter Ace uses FORTH

The Ace is set apart from all other personal computers on the market by its use of a revolutionary language called 'FORTH'. Some computer languages are easy for humans to understand, others are easy for computers; FORTH is most unusual in being both. Its underlying principles are so simple that it takes even a newcomer to computers only a few minutes to learn how to do calculations on the Ace, yet the very same principles are powerful enough to allow you to invent your own extensions to the language itself.

At the same time, the memory-saving coded form used to store your programs inside the Ace allows it to obey them very fast — typically in less than a tenth of the time it would take to do the same thing using a different language. Amongst other things, this makes the Ace ideal for games.

FORTH's unique combination of speed, versatility and ease of programming has already made it a prime choice for professional applications as diverse as pub games and radio telescopes, and gained it an enthusiastic national user group. Now the Jupiter Ace can bring this addictive language into your own home.

Designed by Jupiter Cantab

Leading computer Designers Richard Altwasser and Steven Vickers have a reputation for pushing technology forwards. After playing the major role in creating the ZX Spectrum they formed Jupiter Cantab to develop their latest brainchild the Jupiter Ace.

Technical Specification

Hardware

Processor/Memory

Z80A running at 3.25 MHz.
8K bytes ROM 3K bytes RAM.

Input

40 moving-key keyboard with auto-repeat on every key.

Output

Memory-mapped 32 x 24 character display with high resolution user graphics. Output to drive normal UHF TV set on channel 36.

Sound

Provided by internal loudspeaker.

Cassette

Load Save & Verify at 1500 baud, separate data storage.

Software, FORTH

Data Structures

Integer, Floating point and String data may be held as constants, variables or arrays with multiple dimensions and mixed data types.

Control Structures

IF-THEN-ELSE, DO-LOOP, BEGIN-WHILE-REPEAT, BEGIN-UNTIL, all may be mixed and nested to any depth.

Operators

Mathematical +, -, X, ÷.
Logical AND, OR, NOT, XOR.
Comparison <, >, =.

Program Editing

FORTH words may be listed, edited and redefined. Comments are preserved when words are compiled.

Order Form



The Jupiter Ace is available only by mail order. Please allow up to 28 days for delivery.

Send cheque or postal order with the form to:—
JUPITER CANTAB, 22 FOXHOLLOW, BAR HILL, CAMBRIDGE CB3 8EP

Please send me:—

JUPITER ACE MICROCOMPUTER(S) @ £89.95.

Name. Mr/Mrs/Miss

Address

Valdemar Poulsen

Ian Sinclair

The inventor of the wire-recorder (the precursor of the modern tape recorder) and the first practical method of modulating radio frequencies.

If you haven't heard of him, it's certainly not because of any lack of publicity. Poulsen's invention of magnetic recording, which is still the basis of most tape and magnetic disc recording systems, has been well-documented; but some of his work, notably such achievements as modulation of radio waves, are not quite so well-known. Poulsen was born in 1869 in Copenhagen, Denmark. He doesn't seem to have distinguished himself much at school, but was fascinated by telegraphs and telephones and so progressed from school to Technical College.

When he left College, Poulsen fulfilled his ambitions by joining the Copenhagen Telephone Co as a technical assistant, and it was during his time there that he invented a device to record telephone conversations, a device which he christened the Telegraphone. This was patented in 1898 and a working model of the device aroused considerable interest at the Paris Exposition in 1900. What exactly was it?

A Record First

The drawings are still around and there is absolutely no doubt that it was the first magnetic recorder. Since the discovery of magnetic hysteresis by Charles Steinmetz, engineers were much more aware of how to deal with magnetism, and Poulsen had thoroughly absorbed Steinmetz's work. He realised that if an AC signal were superimposed over DC in an electromagnet and if, at the same time, a magnetic material moved past the poles of the electromagnet then the material would be left permanently magnetised, but with different strengths of magnetism in different places. This remaining magnetism would surely bear some relationship to the amplitude of the AC signal at each instant.

Leading The Way

In any case, Poulsen was not just a theorist; he constructed a prototype in which the recording medium steel wire wound on a drum, with an electromagnet pressed against the wire. The poles of the electromagnet were shaped to fit closely to the wire, and the whole electromagnet (the record/replay head, as we would now call it) was raised or lowered by a lead-screw (as on a screw-cutting lathe) so that, as the drum revolved, the head was kept in contact with the wire. When the head reached the top of the drum, it was automatically lifted from the wire and returned to its starting position.

The prototype worked, and worked well enough to be a big success at the Paris Expo, but its uses were not so obvious. Home entertainment was out of the question, but Edison's Phonograph had

scooped the market and, in any case, the Phonograph had the great advantage that the sound output was loud enough for everyone in a room to hear it. Poulsen's Telegraphone gave only a feeble signal from its replay head, enough for a pair of sensitive earphones, but no more. Its advantage, though, was that the recording system was electrical, using a microphone. To cut a phonograph record, on the other hand, it was necessary for the singer to perform into the wide end of the large trumpet-shaped horn, at the other end of which was a diaphragm carrying a stylus which cut the wax of the recording cylinder directly.

Despite this advantage, Poulsen could not raise any finance for his invention in Europe and, like so many before and even more since, he travelled to the US with his patents. In 1903, with some newly-acquired US associates, he formed the American Telegraphone Co, for manufacturing and selling his recorder. The production model permitted 30 minutes of recording, much longer than was possible on any Phonograph wax cylinder; it achieved this by using fine steel wire, wound on reels, as the recording medium, moving past the record/replay head at the very high speed of 84 inches per second. The market he was aiming at was the rapidly expanding one of office dictaphones which, at that time, used wax cylinders or discs, with all of their disadvantages.

Private Practices

Poulsen's dictaphone offered: more private operation, using a microphone; the possibility of remote operation and even the recording of telephone conversations; private replay, using earphones; a very much longer playing time than rival machines based on wax cylinders or discs could offer. These advantages won the machine quite a substantial share of the booming office equipment market. A few of Poulsen's machines were still in use in the 30s, but when electrical recording and replay became possible on aluminium discs, using phonograph techniques, interest in Poulsen's recorder diminished.

For Better Or Morse

Poulsen's inventive life was by no means confined to the Telegraphone, however. Like most inventors of the time, he concentrated from 1902 onwards on radio communication and, in particular, on the problem of modulation. In the dawn of radio, only telegraphy was possible, and Morse ruled. Morse ruled, in fact, for so long, and became such a millstone round the neck of

amateur radio, that CB just *had* to come to prove that the 20th Century had arrived!

Poulsen also thought that Morse code was out of date by 1902—after all, teletypes using Baudot or Murray 5-bit digital codes had been in use for all of Poulsen's working life. He set out to go one step better and design a way of carrying speech by radio and, by chance, picked up a copy of a British Patent by W. Duddell for a 'singing arc'. This was a way of creating sound from an electrical discharge, similar to an arc lamp, using an electromagnet to move the discharge (which we now call a plasma) and so create the airwaves of sound.

Plasma loudspeakers, incidentally, are by no means completely dead—look out for developments! Duddell's device worked, but it needed large amounts of power and the principle, called the lonophone, was not greatly developed at the time. Poulsen realised that it might be possible to reverse the action of this 'singing arc' and, by having the arc as part of radio frequency circuit, modulate it by the effect of sound-waves on the arc.

His Latest Flame

His first experiments looked frighteningly dangerous. An induction coil was used to generate high frequency AC, and a pair of carbon electrodes provided the arc, with one electrode connected to the earth and the other to the aerial. By speaking into the flame of the arc, Poulsen achieved amplitude modulation of the signal, and his transmissions were received ten miles away using a crude crystal detector and earphones.

This modulator was not really a practical proposition, but Poulsen went on to develop an arc between copper electrodes in gas, held in a glass tube. With the gas at lower than atmospheric pressure, a steady arc could be achieved with lower voltages and modulated by an electromagnet connected to a microphone circuit. Using this arrangement, Poulsen was able to achieve enough depth of modulation to make long-wave broadcasting of sound signals possible, and his arc-modulation system was used until high-power transmitting valves became available.

Poulsen continued his inventive career, making small and generally unnoticed contributions to radio. He tended not to advertise his successes and it is for that reason his work is not widely appreciated. As it was, his working life covered all the pioneering days of electronics, though his death in 1942 robbed him of the chance to see his first invention reach its triumphant maturity, as the tape recorder.

LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder and hook-up wire.

Featured in April issue P.E. Reprint 50p. Free with kit.

Self assembly simulated wood cabinet — Only £4.50 + £1.50 p&p.

£32.95
+ £2.75 p&p.

ELECTRONICS ONLY!


Ideal for updating your existing cassette. Includes pcb diagram, all semiconductors, IC's, Capacitors, resistors. **£18.95** +£1.40p&p



HI-FI STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.Q.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1
- RECORD PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

STEREO AMPLIFIER KIT

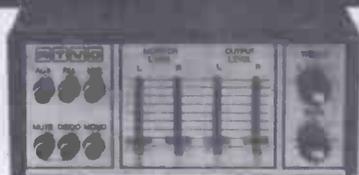

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Preamp/Filter Module.
- Attractive black vinyl finish cabinet, 9" x 8" x 3" (approx).
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.

£16.50
+ £2.90 p&p.

SPECIFICATIONS: Suitable for 4 to 8 ohm speakers
40Hz - 20KHz
P.U. 150mV. Aux. 200mV.
Mic. 1.5mV.
Bass ±12db @ 60Hz
Treble ±12db @ 10KHz
0.1% typically @ 8 watts
220 - 250 volts 50Hz.

8" SPEAKER KIT Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately £6.75 & £1.70 p&p.

125W HIGH POWER AMP MODULE

KIT: **£10.50** BUILT: **£14.25**
+ £1.15 p&p + £1.15 p&p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Suitable mains power supply kit with transformer: £7.50 plus £3.15 p&p.
Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



SPECIFICATIONS:

Max. output power (RMS): 125W.
Operating voltage (DC): 50 - 80 max.
Loads: 4 - 16 ohms.
Frequency response measured @100 watts: 25Hz - 20KHz.
Sensitivity for 100 watts: 400mV @ 47K.
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.
Dimensions: 205 x 90 and 190 x 36 mm.

HI-FI SPEAKERS AT BARGAIN PRICES

GOODMANS TWEETERS

8 ohm soft dome radiator tweeter (3 3/4" sq.) for use in up to 40W systems; with 2 element crossover.

£3.50 each (p&p £1) or £5.95 pair (p&p £2).



35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIFIJSM. Complete with 2 element crossover. Total impedance of system 4 ohms.

£7.95
PER SET + £2.70 p&p.



P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

FEATURES: VHF, MW, LW Bands, Interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied to be P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

£17.95
Plus £2.50 p&p.

Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/2" x 8 1/2" x 3 1/4". **£3.50** Plus £1.50 p&p.



SPECIAL OFFER! TUNER KIT PLUS:

• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider controls for bass, treble and volumes. **£21.95** + £3.80 P&P.

PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II



2 WAVE BAND, MW - LW

• Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits. All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a Bird pre-aligned push button tuning unit.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p&p. **£12.95** + £2.00 p&p.

TV SOUND TUNER KIT

£11.45
+ £1.50 p&p.

As featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. £1.95 + 75p p&p.



MONO MIXER AMP

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. for use with 4 to 8 ohm spkrs. **£39.95** + £3.70 p&p.



BIRD AUDIO STEREO CAR RADIO BOOSTER

To boost your car radio or radio cassette to 15W r.m.s. per channel.

£9.95 + £1.50 p&p.



All mail to: HE10 21E HIGH STREET, ACTON, W3 6NG. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/8/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. Send S.A.E. for full list.

ALL CALLERS TO: 323 Edgeware Road, London W2. Tel: 01-723 8432. 9.30 - 5.30, closed all day Thurs. Prices include VAT. Telephone or mail orders by ACCESS are welcomed.



Rapid Electronics

Tel: 0206 36412
Hill Farm Industrial Estate
Boxted, Colchester
Essex CO4 5RD



TRANSISTORS			
AC125	35	BC157	10
AC126	25	BC158	10
AC127	25	BC159	8
*AC128	20	BC160	45
AC176	25	BC168C	10
AC187	22	BC169C	10
AC188	22	BC170	8
AD142	120	BC172	8
AD161	40	BC177	18
AD162	40	BC178	18
AF124	60	BC179	18
AF126	50	BC182	10
AF139	40	*BC182L	8
AF186	70	BC183	10
AF239	75	BC183L	10
BC107	10	BC184	10
BC107B	12	*BC184L	7
BC108	12	BC212	10
BC108B	12	BC213	10
*BC109	9	BC213L	10
BC109C	12	BC214	10
BC114	22	*BC214L	8
BC115	22	BC215	10
BC117	22	BC238	14
BC119	35	BC308	15
BC137	40	BC327	14
BC139	40	BC328	14
BC140	30	BC337	14
BC141	30	BC338	14
BC142	25	BC347	30
BC143	25	BC348	30
BC147	8	BC349	7
BC148	8	BC347	7
BC149	8	BC347	7

LINEAR			
*555CMOS	80	ICL7621	180
*555CMOS	150	ICL7622	180
709	25	ICL8038	320
741	14	ICL8211A	100
9400CJ	350	ICM7224	785
AY-3-1270	840	ICM7555	80
AY-3-8910	600	LF353	85
AY-3-8912	625	LF356	90
CA3046	60	LM10	360
CA3090	65	LM301A	25
CA3098	215	LM311	60
CA3099A	375	LM318	120
CA3130E	90	LM324	40
CA3140E	90	LM334Z	100
CA3161E	100	LM336Z	125
CA3169	280	LM339	280
CA3240E	110	LM348	60
ICL7610	790	LM358	50
ICL7611	95	LM377	150

CMOS			
4000	10	4019	45
*4001	10	4020	50
4002	12	4021	50
4005	50	4022	50
4007	15	4023	16
4008	48	4024	16
4009	24	4025	16
4010	24	4026	80
*4011	11	4027	24
4012	16	4028	50
*4013	25	4029	60
4014	60	4030	125
4015	50	4031	125
4016	20	4034	140

LS TTL			
*LS00	11	LS21	12
LS01	11	LS22	12
LS02	11	LS23	12
LS03	12	LS24	13
LS04	12	LS25	13
LS05	13	LS26	13
LS08	13	LS27	13
LS09	12	LS28	13
LS10	12	LS29	13
LS11	12	LS30	13
LS12	12	LS31	13
*LS13	22	LS32	13
LS14	38	LS33	13
LS15	12	LS34	13
LS20	12	LS35	13

TTL			
*7400	11	7416	24
7401	11	7417	24
7402	11	7418	24
7403	12	7419	24
7404	13	7420	24
7405	15	7421	24
7406	24	7422	24
7407	25	7423	24
7408	14	7424	24
7409	14	7425	24
7410	14	7426	24
7411	16	7427	24
7412	18	7428	24

CRYSTALS			
100KHz	290	6.0M	200
200KHz	370	6.144M	180
1MHz	300	7.0M	250
1.038M	370	8.0M	170
1.8432	300	10.0M	180
2.0M	270	12.0M	290
2.4576M	220	18.0M	240
3.276M	240	18.0M	240
3.579M	120	18.432	220
4.0M	180	38.687	320
4.194M	125	41.66M	300
4.43M	125	41.66M	300
5.0M	240		

The Rapid Guarantee

NEW CATALOGUE

Our latest catalogue has just been released containing over 2000 stock lines at extremely competitive prices backed by Rapid's return of post service. Stocks include Denco coils, totes, Verocases, data sheets etc. Send 46p for your copy now (sent free of charge with all orders over £10).

TRANSFORMERS

Miniature mains 608V, 909V, 12012V all @ 100mA 100p each PCB mounting. Miniature 3VA 0-5, 0-6 @ 0.25A; 0-9, 0-9 @ 0.15A; 0-12, 0-12 @ 0.12A 200p each 6VA 0-6, 0-6 @ 0.5A; 0-9, 0-9 @ 0.3A; 0-12, 0-12 @ 0.25A 270p each High quality split bobbin construction 6VA 0-8, 0-6 @ 0.5A; 0-9, 0-9 @ 0.4A; 0-12, 0-12 @ 0.3A 220p each 12VA 0-6, 0-5 @ 1A; 0-9, 0-9 @ 0.8A, 0-12, 0-12 @ 0.6A, 0-15, 0-15 @ 0.4A 295p (plus 40p carriage) High quality split bobbin construction @ 1A; 0-15, 0-15 @ 0.8A 330p each (plus 60p carriage) 50VA 0-12, 0-12 @ 2A, 0-15, 0-15 @ 1.5A 440p each (plus 75p carriage)

CABLES

20 metre pack single core connecting cable ten different colours 50p Shielded cable 100p/m Standard screened 16p/m Twin screened 24p/m 2.5A 3 core mains 23p/m 10 way rainbow ribbon 65p/m 20 way rainbow ribbon 120p/m

CAPACITORS

Polyester. Radial leads. C280 type. 0.01, 0.015, 0.022, 0.033 6p; 0.047, 0.068, 0.1 7p; 0.15, 0.22 9p; 0.33, 0.47 13p; 0.68, 20p; 1u 23p Electrolytic. Radial or axial leads. 0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 10/25V 7p; 22/25V, 47/25V 8p; 100/25V 9p; 220/25V 14p; 470/25V 22p; 1000/25V 30p; 2200/25V 50p Tag and Power Supply Electrolytics. 220/40V 110p; 470/40V 160p; 2200/63V 140p; 4700/63V 230p Polymer. Miniature Siemens PCB 1n, 2n2, 3n3, 4n7, 6n8, 10n, 15n 7p; 22n, 33n, 47n, 68n 8p; 100n 9p; 150n 11p; 220n 13p; 330n 20p; 470n 26p; 680n 29p; 1u 33p; 2u 50p Tantalum bead 0.1, 0.22, 0.33, 0.47, 1.0 @ 35V 12p; 2.2, 4.7, 10 @ 25V 20p; 15/16V 30p; 22/16V 27p; 33/16V 45p; 47/16V 27p; 47/16V 70p; 68/16V 40p; 100/10V 30p Ceramic disc. 22p-0.01u 50V 3p each Mullard miniature ceramic plate 1.8pF to 100pF 6p each Polyesterene. 5% tolerance 10p-1000p 6p; 1500-4700p 8p; 6800-0.012u 10p Trimmers. Mullard 808 Series 2.2k-20k 2.2k-30p; 5.5k-65p 5F 35p

MULTIMETERS

HT-120 4,000 opv A smart looking 11 range pocket sized multimeter with an impressive spec. Complete with battery etc. 650p each HT-320 20,000 opv Highly sensitive 19 range multimeter including transistor tester. Overload protection, DC volts - 100uA, AC volts - 1000V; DC current 0.25A, 4 resistance ranges. Complete with batteries, leads etc. 1395p each

OPTO

*3mm red 8 *5mm red 8 *3mm green 12 *5mm green 12 *3mm yellow 12 *5mm yellow 12 Clips to suit 3p each Rectangular TL32 40 *red 12 TL178 40 *red 17 TL111 40 yellow 17 ORP12 85 TL335 40 TL100 90 ZN5777 45 Dual color 60p each Seven segment displays Common cathode DL704 0.3" 96 DL707 0.3" 96 *FN500 0.5" 100 *FN501 0.5" 100 TL1310 0.3" 105 TL1312 0.3" 105 TL1322 0.5" 115 TL1321 0.5" 115 LCD: 3j digit 680p 4 digit 620p

BOXES

Aluminium Plastic 3 x 2 x 1in 70p with lid + screws 4 x 3 x 1 1/2in 85p 3 x 2 x 1 1/2in 55p 4 x 3 x 2 1/2in 100p 4 1/2 x 3 1/2in 88p 6 x 4 x 2 1/2in 120p 7 x 4 x 2 1/2in 160p 6 x 4 x 3 1/2in 150p

BRIDGE RECTIFIERS

1A 50V 22 6A 100V 80 1A 400V 35 6A 400V 95 2A 200V 40 VM18 DIL 70p 2A 400V 45 0.8A 200V 50

POTENTIOMETERS

Rotary. Carbon track Log or Lin 1K-2M Single 32p; Stereo 85p; Single switched 80p; Slide 60mm travel single Log or Lin 5K-500K 63p each Preset. Submin. hor. 100 ohms-1M 7p each Cermet precision multiturn, 0.75W 2in 100 ohms to 100K 88p each

TOOLS

Small trimming tool 22p Small pocket screwdriver 16p Large pocket screwdriver 13p 6 piece precision screwdriver set in plastic case 170p Low cost side cutters 160p High quality side cutters 850p Low cost pliers 160p High quality pliers 650p Wire strippers 120p Expo Reliant Drill 65p Expo Titan Drill 1025p Drill stand 1200p Reduced Shank drill bits for above 0.8mm, 1mm, 1.4mm 60p each

DIODES

BY127 12 *1N4001 3 5 0A47 10 1N4006 7 15p 0A50 8 1N4008 7 1N4007 7 0A200 8 1N5401 15 0A202 8 1N5404 16 1N914 4 1N5405 16 *1A148 2 400MVA zen 6 BZK61 Series zeners 1.3W 4V7-39V 15p each

ORDERING INFO

All prices exclude VAT. Please add to total order. Please add 50p carriage to all orders under £15 in value. Send cheque/PO or Access/Visa number with your order. Please note new address. Callers most welcome - we are just 10 minutes from the centre of Colchester. Telephone orders welcome with Access and Visa. Official orders welcome from colleges and schools etc. Export orders no VAT but please add carriage. All components brand new and full spec.

COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. 1W 5% Resistor kit. Contains 10 of each value from 4.7 to 1M (650 resistors) 480p Ceramic Capacitor Kit. Contains 5 of each value from 22p to 0.01u (135 caps) 370p Polyester Capacitor Kit. Contains 5 of each value from 0.01 to 1uF (65 caps) 575p each Preset Kit. Contains 5 of each value from 100 ohms to 1M (total 65 presets) 425p each Nut and Bolt Kit. Total 300 items 180p

TRIACS

400V 4A 50 400V 8A 65 400V 16A 95 BR100 25

PANEL METERS

Size 60 x 46 x 35mm 0-50uA 0-0.500mA 0-100uA 0-10A 0-800uA 0-50V AC 0-1mA VU 0-10mA 0-300V AC 0-50mA 0-25V DC 0-100mA 0-30V DC All 495p each

CONNECTORS

OIN Plug Jack Plug Skt 2 pin 9p 3p 2.5mm 9p 10p 3 pin 12 10p 3.5mm 9p 9p 5 pin 13p 11p Standard 16p 20p Phono 10 pin 12p Stereo 24p 25p 10 pin 12p 13p 4mm 18p 17p UHF (CB) Connectors PL259 Plug 40p Reducer 14p SO239 square chassis skt 38p SO239S round chassis socket 40p IEC 3 pin 250V/6A Plug chassis mounting 38p Socket free hanging 60p Socket with 2m lead 120p

RESISTORS

1W 5% Carbon film E12 series 4.7-10M 10p each 1W 5% Carbon film E24 series 4.7-10M 2p each 1W 1% Metal film E24 series 100-1M 6p each

PCB MATERIALS

Alfac transfer sheets - please state type (e.g. DIL pads etc) 45p Dato etch resist pen 100p Fibre glass board 3.75" x 8" 80p Ferric Chloride 250ml bottle 100p

Same day despatch **Competitive prices**
Top quality components **In-depth stock**

Negative Voltage Generator

Owen Bishop

A simple circuit on a postage stamp sized PCB, but it has 1001 uses!

IT IS handy to have one or more of these devices in the electronics workshop. If you are building or designing a circuit which uses op-amps, a split power supply is nearly always required. There are other applications too; for example, this version of the circuit was built up to provide a split supply for the prototype of the Digital Millivoltmeter (HE August '82 issue). Not having enough cells to hand to make up a +4V5 battery, and being unable to get out to the shops, the only solution was to use the available batteries for the positive supply and make up this circuit for the negative supply. In the DVM project, the circuit takes up less room than the 3 cells it replaces. It also makes the power switching and wiring simpler since, instead of a double-pole switch (one pole for positive, one for negative), only a single-pole switch is required.

Construction

There is almost nothing to say about this, since it can be built up on almost any scrap of stripboard (Figure 2) or on

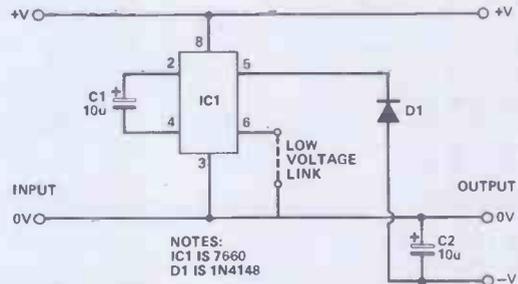
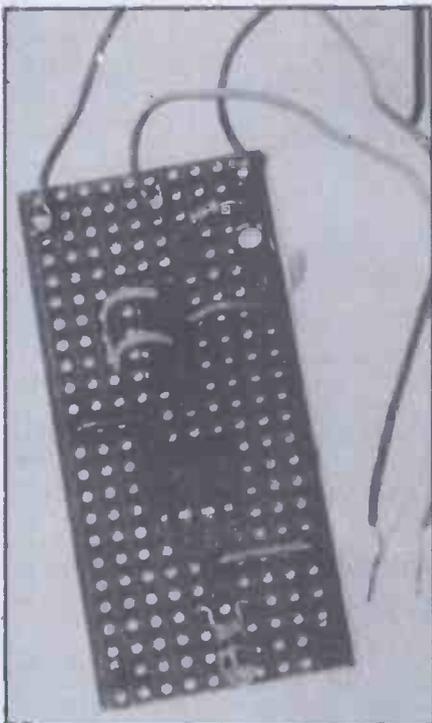


Figure 1. The circuit uses just one IC.

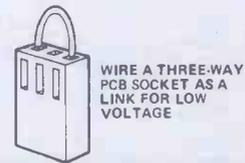


Figure 2. A three-way PCB socket can be used as the low-voltage link.

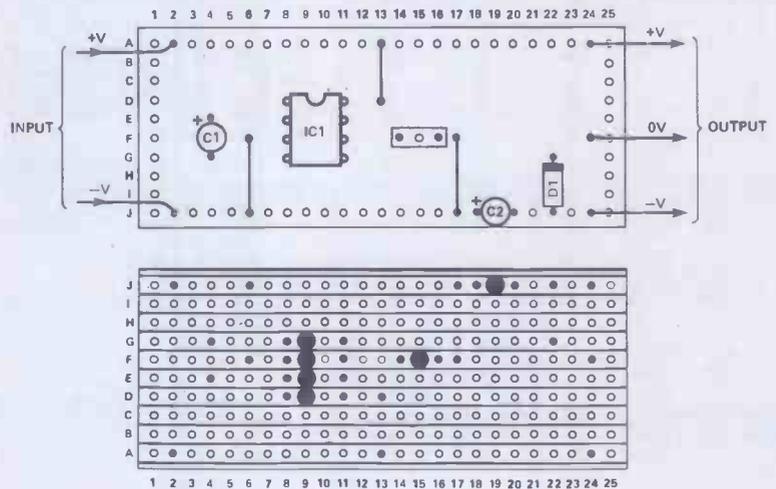


Figure 3. The Veroboard layout.

a PCB (Figure 3) the size of a postage stamp. Also, the circuit can be incorporated in any odd space on the main board of any other project that requires it.

It works for a wide range of supply voltages (+1V5 to +10V). Pin 6 must be joined to the 0V rail when the supply is less than +3V5 and for these low voltages, the diode may be omitted. The PCB design allows a wire link to connect pin 6 to the 0V rail for low-voltage operation. If the unit is to be used at various voltages, some high,

some low, a switch may be wired in place of the link.

The circuit works straight away — no adjustments are needed.

The Circuit

The positive voltage comes straight through from the supply, so there is no mystery about this. The negative voltage is generated by voltage level translation. See what happens when the unit is connected to a +6V supply. There are two stages in the operation (Figure 4):

Parts List

CAPACITORS

C1, 2 10 μ 16V
tantalum bead

SEMICONDUCTORS

IC1 7660
voltage converter (see Buylines)

D1 1N4148
signal diode

MISCELLANEOUS

Small veroboard or PCB; veropins;
3-pin PCB plug and socket, or SPST
switch; wire, solder etc.

Buylines page 30

Stage 1: C1 is charged directly from the power supply, so that its negative terminal is at 0V and its positive terminal is at +6V.

Stage 2: The switches are altered under the control of the logic circuits; the +6V plate of C1 is now connected to the 0V rail, resulting in a fall of potential of 6V. This causes a corresponding drop on its other plate, formerly at 0V but now forced down to -6V. Since this plate is now connected to C2, one side of C2 now becomes charged to -6V, the other side being at 0V.

The IC then returns to Stage 1, recharging C1 and leaving C2 charged

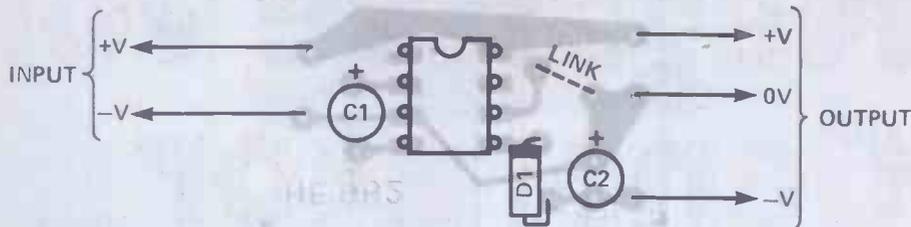


Figure 4. A full-sized PCB is reproduced on the PCB Printout page; note that the low-voltage link is hard-wired, here.

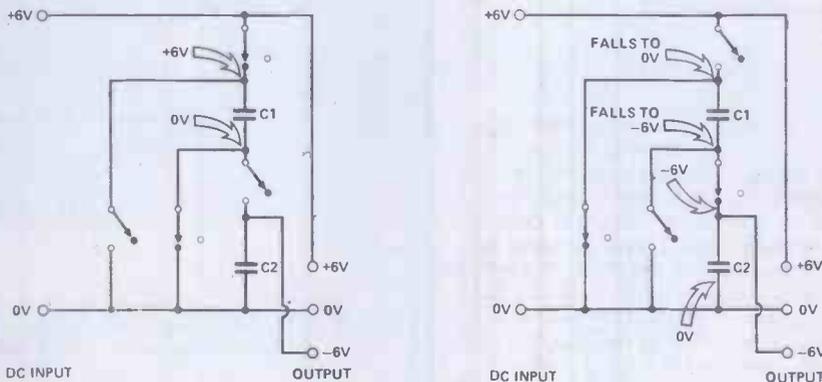


Figure 5. How the 7660 IC works: left, Stage 1; right, Stage 2.

to -6V. The states alternate very rapidly (at about 10kHz), under the control of an on-chip oscillator and various logic circuits, so that a virtually smooth DC supply is obtained. Naturally, if current is being drawn from C2 to supply the external circuit,

its charge may not be renewed sufficiently rapidly from C1 and the negative voltage may fall slightly. For many applications (eg, the DVM) the negative supply is called on for relatively small currents, so usually this effect can be ignored.

THE ELECTRONICS FILE

POSSIBLY THE ONLY GUIDE YOU WILL EVER NEED.

**Chapters on;
Electricity.**

**Electronic Components and Circuits,
Computers and how to Program them,
Robots (and more).**


ALL PROCEEDS TO
"SAVE THE CHILDREN"
FUND.

MONEY BACK IF NOT
DELIGHTED.

**JUST £ 5.95
P&P FREE**

P. RICKARD, 46, HOWEY LANE,
FRODSHAM, CHESHIRE.

THE CASE FOR

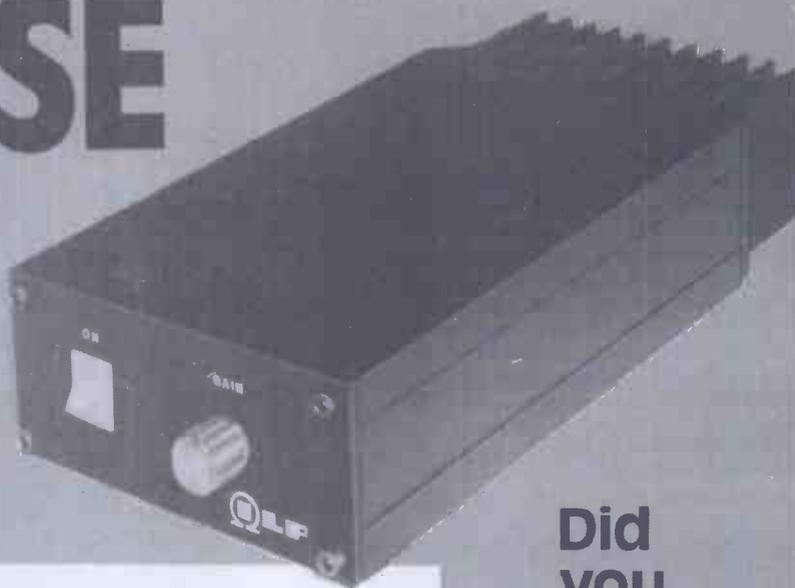

It's the chance every constructor wants



POWER AMPS



P.S.U's



PRE-AMP MODULES

It's something you have always wanted....something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U's, the range will shortly be extended to house any other modular projects.

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN. It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



FREEPOST 6
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

FREEPOST
Mark your envelope clearly **FREEPOST 6** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

Did you know

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are **TWENTY** power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?

SEND COUPON
(NO STAMP NECESSARY)
FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE

To: I.L.P. ELECTRONICS LTD.
PLEASE SEND ME I.L.P. CATALOGUE,
POST PAID BY RETURN

I HAVE/HAVE NOT PREVIOUSLY
BUILT WITH I.L.P. MODULES

Name: _____

Address: _____

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

POINTS OF VIEW

Feel like sounding off?
Then write to the Editor stating your Point Of View!

Stretching A Point

Dear Sir,
I am writing to you for help in obtaining a reel of 35 SWG and 39 SWG enamelled copper wire. I have looked in many catalogues advertised in your magazine but they only stock 34 and 40 SWG wire. If you know of any company who could supply 35 and 39 SWG could you please inform me. I would be very grateful.
B. Cook,
Tamworth,
Staffs.

We can't imagine why you need 35 and 39 rather than 34 and 40 — the difference is 0.01 and 0.02 mm, respectively! However, the Scientific Wire Company (PO Box 30, London E4) will sometimes supply custom gauges. Ask them nicely and tell them Hobby Electronics sent you!

Getting Started

I have just completed my first year studying a broad engineering course which includes a substantial amount of electronics. I have found this part slightly difficult, mainly because I cannot get practice at its application.

I very much want to begin constructing electronic circuits but, being a complete novice, I have very little idea where to start! It seems that kits are the easiest initial projects.

I have a soldering iron and some screwdrivers, but would like advice on what tools to obtain and what projects to opt for first. Yours was the first electronics magazine I have ever bought. The theory I can understand but the practical details seem very difficult without knowledge of the components.

I would be most grateful if you could spare the time to advise me.
L.M. Gair,
London.

Difficult questions to answer in a few lines, but we'll try! First, our aim in HE is to present projects for the beginner in electronics, and many of our long-running feature series are devoted to introducing both the theory and practice of electronics. The best place to start, then, is in your local library! We suggest you look closely at lan

Sinclair's "Into Electronic Components" series (August '81 — July '82) which explains in detail what the various items are, and how and why they are used. On the practical side, we'd recommend Keith Brindley's "Building Site" articles, in issues from August 1980 through to December 1981. Any article you feel should be kept for future reference can be obtained from our Backnumbers Department.

The three essential tools for the electronics constructor are a soldering iron, sidecutters and a pair of long-nosed pliers. For mechanical assembly, you'll need a selection of screwdrivers, and there are many other tools which, while not "essential" are quite handy; nut drivers, small spanners, and so on. A set of miniature files is extremely useful, and so is a "seizer" or surgical clamp; the jaws clamp firmly together to hold wires for soldering, act as a heat sink etc, and are handy for retrieving small things that drop into inaccessible places! You'll find all these items in the catalogue published by Cooper Tools. Their address is: Sedling Road, Wear, Washington, Tyne and Wear NE38 9BZ.

Kit projects are probably simpler because all the components are supplied, along with the odds and ends that an inexperienced constructor would not have to hand. Kits are available for most Hobby Electronics projects, but pick an easy one to start on. Be sure to follow the instructions carefully; you'll make mistakes, of course, but there's no other way to go about it; experience is the best teacher, after all

Speakers Without Peer

Dear Sir,
Thank you for such an excellent magazine, Hobby Electronics.
We do have a problem though; quite a lot of the projects have certain components that are either not stocked at the local electronic shops, or the man behind the counter gives you a blank look when you ask for it. That usually means he hasn't got a clue what you're talking about.

Such was the case with your stereo hi-fi, System 5080A, in the March 1980 issue. After I had completed the preamp, power amp and the power supply, I started looking around for the speakers specified. Alas, nobody knew anything about a speaker called "Peerless".

I then decided to contact one of the

suppliers mentioned in *Buylines*. The company was Badger Sound Services Ltd. They sent me a price list as well as the order forms, which I completed and returned to them with my cheque. At this stage I thought my problems were over, when disaster struck. They sent me a letter to inform me that they were having difficulty in obtaining a set of the speakers, but that they expected them within two or three weeks.

That was six months ago, and I regret to say that my patience is running out. It seems to me that they are not eager to satisfy overseas customers because I last heard from them three months ago.

Are there other customers from foreign countries also experiencing problems in this respect, or has my luck run out? I always had my doubts about importing goods from other countries and after this I don't think I'll attempt such a thing again.

I have written to the company asking them if they can or cannot supply the goods within the next six months, because that is as long as I'll be able to wait. The project is costing me a fortune and the fact that I have to wait so long for these speakers makes it a total loss.

I sincerely hope there is someone who can help me with this problem, or to advise me on the true state of affairs.

H. Beukes,
Volksrust,
South Africa.

The speakers (or more accurately, the driver units) are still manufactured by Peerless, but the number of tweeters being produced keeps them in short supply and this is where the problem lies. We have contacted Badger Sound and they have assured us that they are doing everything possible to obtain the units for Mr. Beukes. We understand that they have written to explain the situation, and have offered alternative drivers which would suit the system.


We fully appreciate the difficulties sometimes experienced by our overseas readers, but there is very little we can do about it other than point out that it would be safer to make enquiries about the supply of unusual components before actually sending off for them.

For our South African readers, we can pass on the name of a shop recommended by an expatriate colleague; it is: A1 Radio of West Street, Durban 4001.

Sinclair ZX Spectrum

**16K or 48K RAM...
full-size moving-
key keyboard...
colour and sound...
high-resolution
graphics...**

**From only
£125!**

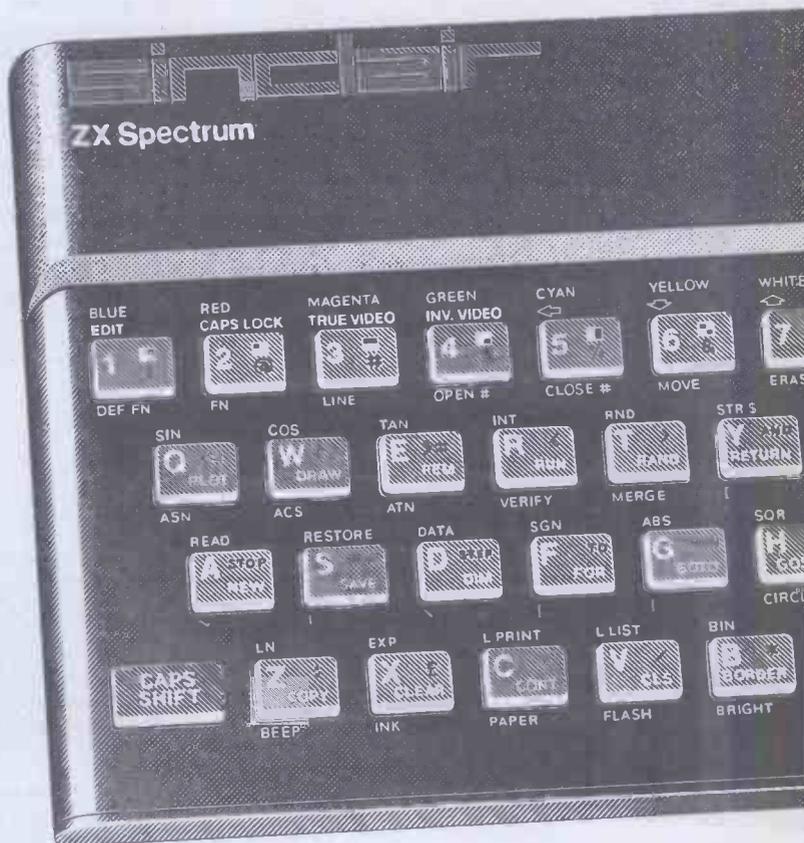

First, there was the world-beating Sinclair ZX80. The first personal computer for under £100.

Then, the ZX81. With up to 16K RAM available, and the ZX Printer. Giving more power and more flexibility. Together, they've sold over 500,000 so far, to make Sinclair world leaders in personal computing. And the ZX81 remains the ideal low-cost introduction to computing.

Now there's the ZX Spectrum! With up to 48K of RAM. A full-size moving-key keyboard. Vivid colour and sound. High-resolution graphics. And a low price that's unrivalled.

Professional power— personal computer price!

The ZX Spectrum incorporates all the proven features of the ZX81. But its new 16K BASIC ROM dramatically increases your computing power.

You have access to a range of 8 colours for foreground, background and border, together with a sound generator and high-resolution graphics.

You have the facility to support separate data files.

You have a choice of storage capacities (governed by the amount of RAM). 16K of RAM (which you can update later to 48K of RAM) or a massive 48K of RAM.

Yet the price of the Spectrum 16K is an amazing £125! Even the popular 48K version costs only £175!

You may decide to begin with the 16K version. If so, you can still return it later for an upgrade. The cost? Around £60.

Ready to use today, easy to expand tomorrow

Your ZX Spectrum comes with a mains adaptor and all the necessary leads to connect to most cassette recorders and TVs (colour or black and white).

Employing Sinclair BASIC (now used in over 500,000 computers worldwide) the ZX Spectrum comes complete with two manuals which together represent a detailed course in BASIC programming. Whether you're a beginner or a competent programmer, you'll find them both of immense help. Depending on your computer experience, you'll quickly be moving into the colourful world of ZX Spectrum professional-level computing.


There's no need to stop there. The ZX Printer—available now—is fully compatible with the ZX Spectrum. And later this year there will be Microdrives for massive amounts of extra on-line storage, plus an RS232 / network interface board.



Key features of the Sinclair ZX Spectrum

- Full colour—8 colours each for foreground, background and border, plus flashing and brightness-intensity control.
- Sound—BEEP command with variable pitch and duration.
- Massive RAM—16K or 48K.
- Full-size moving-key keyboard— all keys at normal typewriter pitch, with repeat facility on each key.
- High-resolution—256 dots horizontally x 192 vertically, each individually addressable for true high-resolution graphics.
- ASCII character set—with upper- and lower-case characters.
- Teletext-compatible—user software can generate 40 characters per line or other settings.
- High speed LOAD & SAVE—16K in 100 seconds via cassette, with VERIFY & MERGE for programs and separate data files.
- Sinclair 16K extended BASIC—incorporating unique 'one-touch' keyword entry, syntax check, and report codes.

um

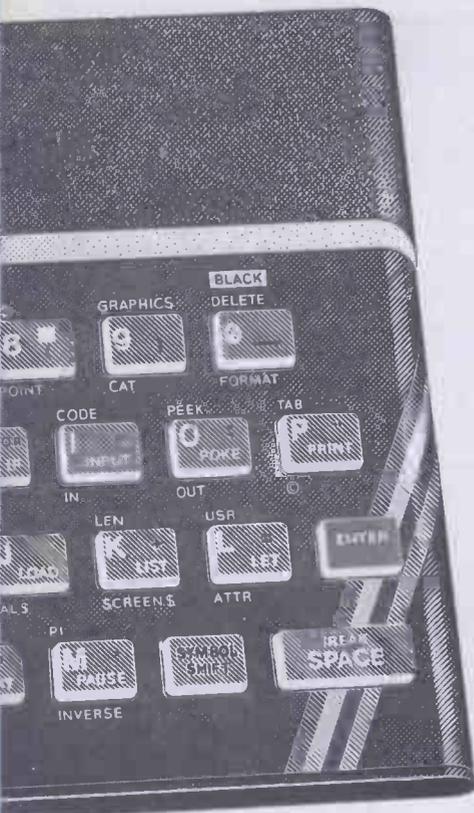

RS232/network interface board

This interface, available later this year, will enable you to connect your ZX Spectrum to a whole host of printers, terminals and other computers.

The potential is enormous. And the astonishingly low price of only £20 is possible only because the operating systems are already designed into the ROM.

ZX Spectrum

Available only by mail order and only from

sinclair

Sinclair Research Ltd,
Stanhope Road, Camberley,
Surrey, GU15 3PS.
Tel: Camberley (0276) 685311.

The ZX Printer—available now

Designed exclusively for use with the Sinclair ZX range of computers, the printer offers ZX Spectrum owners the full ASCII character set—including lower-case characters and high-resolution graphics.

A special feature is COPY which prints out exactly what is on the whole TV screen without the need for further instructions. Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your ZX Spectrum. A roll of paper (65ft long and 4in wide) is supplied, along with full instructions. Further supplies of paper are available in packs of five rolls.



The ZX Microdrive—coming soon

The new Microdrives, designed especially for the ZX Spectrum, are set to change the face of personal computing.

Each Microdrive is capable of holding up to 100K bytes using a single interchangeable microfloppy.

The transfer rate is 16K bytes per second, with average access time of 3.5 seconds. And you'll be able to connect up to 8 ZX Microdrives to your ZX Spectrum.

All the BASIC commands required for the Microdrives are included on the Spectrum.

A remarkable breakthrough at a remarkable price. The Microdrives are available later this year, for around £50.



How to order your ZX Spectrum

BY PHONE—Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST—use the no-stamp needed coupon below. You can pay by cheque, postal order, Access,

Barclaycard or Trustcard.

EITHER WAY—please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt—and we have no doubt that you will be.

To: Sinclair Research, FREEPOST, Camberley, Surrey, GU15 3BR.

Order

Qty	Item	Code	Item Price £	Total £
	Sinclair ZX Spectrum—16K RAM version	100	125.00	
	Sinclair ZX Spectrum—48K RAM version	101	175.00	
	Sinclair ZX Printer	27	59.95	
	Printer paper (pack of 5 rolls)	16	11.95	
	Postage and packing: orders under £100	28	2.95	
	orders over £100	29	4.95	
			Total £	

Please tick if you require a VAT receipt

*I enclose a cheque/postal order payable to Sinclair Research Ltd for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____

*Please delete/complete as applicable

Signature

PLEASE PRINT

Name: Mr/Mrs/Miss

Address

HEL 810

FREEPOST—no stamp needed. Prices apply to UK only. Export prices on application.



MICRO-PROFESSOR

YOUR GUIDE TO THE WORLD OF MICROPROCESSORS

A low cost tool for learning, teaching & prototyping.



(by phone or post)

Complete the coupon today!

Please allow 28 days for delivery.

Please send me:	Price	Qty	p&p
Micro-Professor	£79.95		£2.95
SSB-MPF board	£69.95		£2.95
EPB-MPF board	£84.95		£2.95
PRT-MPF board	£74.75		£2.95
		Total	

I enclose cheque/P.O. for £.....

Name

Address

Micro-Professor is a low-cost Z80 based microcomputer which provides you with an interesting and inexpensive way to understand the world of microprocessors and utilise their unlimited potential.

Micro-Professor is a complete hardware and software system whose extensive manual gives you detailed schematics and examples of programme code. A superb learning development tool for students, hobbyists and microprocessor engineers, as well as an excellent teaching aid for instructors of electrical engineering and computer science courses.

Technical specification

Z80 CPU, 2K RAM, 2K monitor, 24 I/O lines, LED display, cassette interface, CTC/PIO facility, 2.25" speaker, three manuals, 36 keyboard. Options include; EPROM board, speech board and printer board.

Please send or telephone for full details.

Now includes 2K BASIC

£79.95 + p&p

FLIGHT ELECTRONICS LTD. Flight House, Quayside Rd, Southampton, Hants SO2 4AD. Tel: (0703) 34003/27721. Telex: 477793.

Mail order only • Trade enquiries welcome • Bulk order discounts • Prices include VAT

ATTENTION!

UNDER NORMAL CIRCUMSTANCES YOU WOULD POSSIBLY PASS OVER THIS ADVERT WITHOUT READING IT!

HOWEVER, IF YOU CAN SPARE 30 SECONDS PLEASE READ ON ...

Are any of the following products of interest?

- *Roadrunner Wiring System
- *Prototyping Eurocards
- *S100 Prototyping Boards
- *Eurocard Prototyping Assemblies
- *DIN 41612 2 Part Connectors
- *DIP Sockets
- *19" Eurocard Subracks
- *Roadrunner 'Handi-raks'
- *Soldering Irons & Accessories
- *Assembly Tools

FROM LARGE STOCKS WE CAN ENSURE 'SAME-DAY' SERVICE ON ALL ITEMS.

Offering a combination of competitive pricing and excellent service we are working hard at customer satisfaction.

FOR FURTHER DETAILS CALL US ON 0428 53850.

Ask for our 1982 Catalogue.



We welcome orders using Access & Barclaycard.

Roadrunner Electronic Products Ltd.

116 BLACKDOWN RURAL INDUSTRIES
HASTE HILL, HASLEMERE,
SURREY GU27 3AY
TEL: 0428 53850 TELEX: 858485 DEVCOM G


The name to remember in electronics.



'Electronic manufacturers and distributors'

DIRECTORY OF ELECTRONICS SUPPLIES

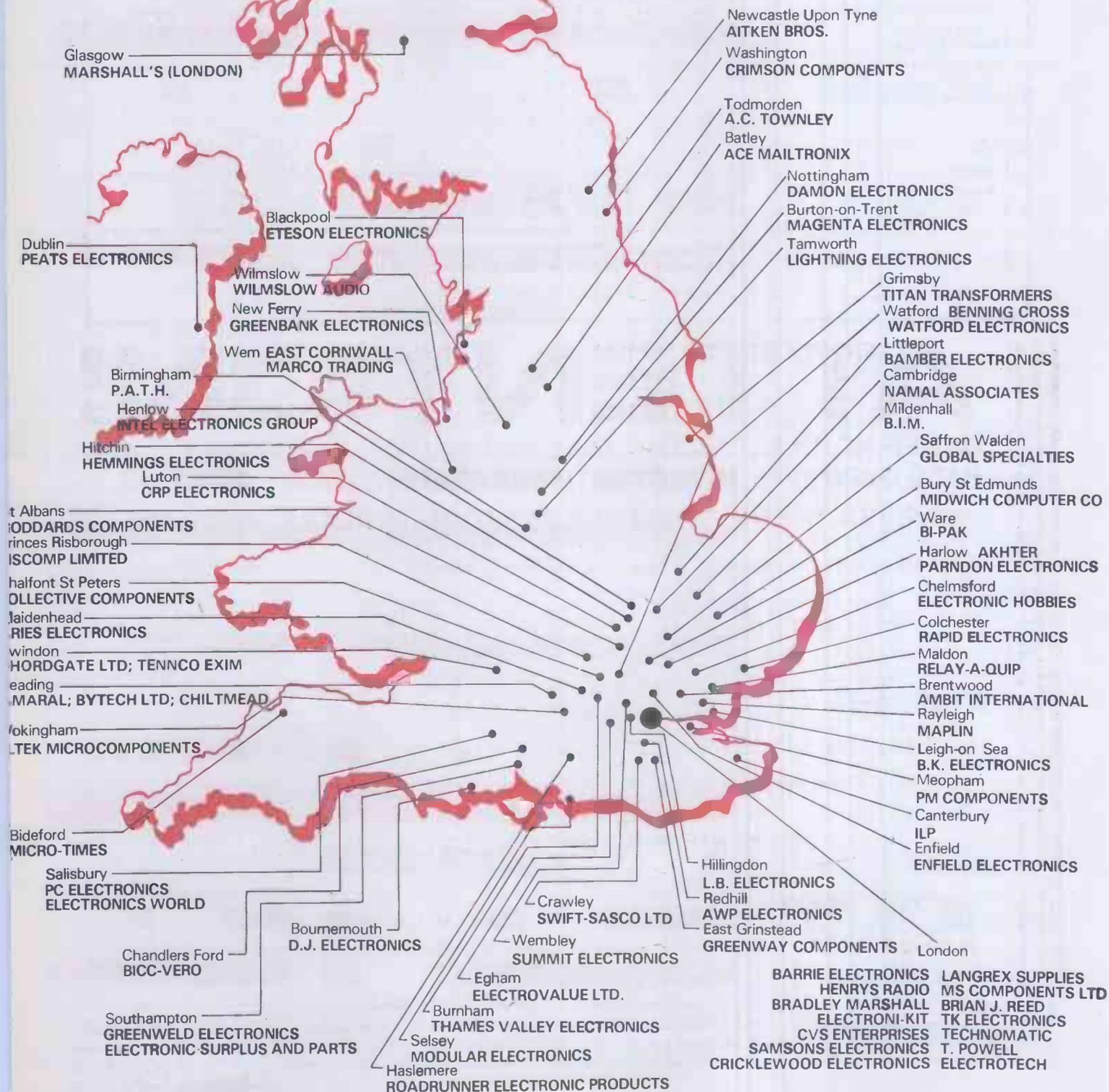A comprehensive guide to electronic components and hardware supplies in the United Kingdom.



NOTES:

- (1) Including ferrites, RF chokes etc.
- (2) Discrete devices.
- (3) Other than optoelectronic.
- (4) Access and Barclaycard, where marked.
- (5) See company listing.
- (6) In pence unless otherwise noted.
N = NIL (no charge).

	RESISTORS	CAPACITORS	POTENTIOMETERS	TRANSFORMERS	INDUCTORS (1)	DIODES, SCRs TRIACS	TRANSISTORS (2)	LINEAR ICs	DIGITAL ICs	LINEAR MSI/LSI	DIGITAL MSI/LSI	OPTOELECTRONICS	VALVES	RELAYS	SWITCHES	FUSES AND PROTECTION	BATTERIES AND PSUs	ANALOGUE PANEL METERS	TRANSDUCERS (3)	PCB HARDWARE
ACE MAILTRONIX																				
AITKEN BROS.																				
AKHTER INSTRUMENTS																				
ALTEK																				
AMARAL LIMITED																				
AMBIT INTERNATIONAL																				
ARIES ELECTRONICS																				
AWP ELECTRONICS																				
BAMBER ELECTRONICS																				
BARRIE ELECTRONICS																				
BENNING CROSS																				
BICC-VERO																				
BI-PAK																				
B.K. ELECTRONICS																				
B.I.M.																				
S & R BREWSTER																				
BYTECH LTD.																				
CHILTMEAD																				
CHORDGATE LTD.																				
CLEF ELECTRONICS																				

PLUGS AND SOCKETS	ENCLOSURES, CASES	HEATSINKS	KNOBBS, MISC. HARDWARE	CABLE AND WIRE	BREADBOARDS	TOOLS	PCBs and/or MATERIALS	CHEMICALS	CUSTOM KITS, MODULES	SURPLUS SUPPLIES	BARGAIN PACKS	BOOKS	CATALOGUE/PRICE LIST	MAIL ORDER MINIMUM (6)	P&P (6)	OVERSEAS ORDERS	CREDIT CARDS (4)	SHOPS	OTHER
-------------------	-------------------	-----------	------------------------	----------------	-------------	-------	-----------------------	-----------	----------------------	------------------	---------------	-------	----------------------	------------------------	---------	-----------------	------------------	-------	-------

- NOTES:
 (1) Including ferrites, RF chokes etc.
 (2) Discrete devices.
 (3) Other than optoelectronic.
 (4) Access and Barclaycard, where marked.
 (5) See company listing.
 (6) In pence unless otherwise noted.
 N = NIL (no charge).

													N (5)						ACE MAILTRONIX
													N (5)						AITKEN BROS.
													N (5)						AKHTER INSTRUMENTS
													(5)						ALTEK
													N 50						AMARAL LIMITED
													N 50						AMBIT INTERNATIONAL
													£5 138						ARIES ELECTRONICS
													£5 (5)						AWP ELECTRONICS
													£5 (5)						BAMBER ELECTRONICS
													£2 (5)						BARRIE ELECTRONICS
													N 50						BENNING CROSS
													N N						BICC-VERO
													N 75						BI-PAK
													N (5)						B.K. ELECTRONICS
													N (5)						B.I.M.
													N (5)						S & R BREWSTER
													£5 £2						BYTECH LTD.
													£3 150						CHILTMead
													£1 (5)						CHORDGATE LTD.
													£1 (5)						CLEF ELECTRONICS

INTRODUCING TWO NEW HANDHELD DIGITAL MULTIMETERS

200 μ A — 10 AMP AC-DC

MODEL 6010

DC accuracy 0.5%

£29.95
plus VAT

MODEL 7030

DC accuracy 0.1%

£35.95
plus VAT



SPECIFICATION 6010 & 7030

BATTERY: Single av dry cell

BATTERY LIFE: 200 hours

DIMENSIONS: 170 x 89 x 38mm

WEIGHT: 400g inc battery

MODE SELECT: Push button

AC DC CURRENT: 200 μ A to 10A

AC VOLTAGE: 200mV to 750V — 6 Ranges

DC VOLTAGE: 200mV to 1000V — 5 Ranges

RESISTANCE: 200 Ω to 20M Ω — 5 Ranges

INPUT IMPEDANCE: 10M Ω — 6 Ranges

DISPLAY: 3½ Digit 13mm LCD

O/LOAD PROTECTION: All ranges

OTHER FEATURES:


Auto polarity. Auto zero. Battery-low indicator.

Strong ABS plastic case with tilt stand.

Battery and test leads included.

Optional carrying case.

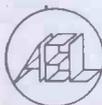Please add 15% to your order for VAT. Postage & Packing is free of charge. Trade enquiries invited.



ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England

Telephone: 01-902 4321 (3 lines)

TELEX No. 923985

ELECTRONICS IS A FINE HOBBY

VELLEMAN-KIT



In less than a year we have become well-known for our varied and interesting range of electronic kits and our efficient service.

Graded by difficulty, the kits are of high quality, well packaged and have applications covering a wide field.

The range includes kits using microprocessors, infra-red systems, power supplies, dimmers, motor control units, amplifiers, sound and light units, digital counters, timers, VU's and many, many more.

New kits are:

K2580 — electronic powerswitch dimmer.....£9.34
K2581 — stereo volume and tone control£11.27
K2582 — stereo audio input selector£11.27

Velleman kits are also obtainable from:

S & R Brewster Ltd., Union Street, Plymouth, Devon.

Priest Electronic Systems, Lindley, Huddersfield.

Baxol Tele Exports Ltd., Post Rathdrum, Co. Wicklow, Rep. of Ireland.

The Velleman 'top ten' are:

K1682 — Microprocessor timer£48.37
K1771 — FM Oscillator£5.45
K1798 — Stereo VU using LED's£16.91
K1823 — 1 amp Power supply£6.99
K2544 — Complex sound generator£8.28
K2569 — Three tone chime.....£6.56
K2575 — Microprocessor doorbell.....£15.53
K2577 — Motor speed control£7.57
K2578 — Eprom programmer£207.00
K2579 — Start stop timer£6.21

(prices include VAT)

ENQUIRIES FROM RETAILERS INVITED

SEND FOR FREE ILLUSTRATED CATALOGUE OF COMPLETE RANGE

VELLEMAN (U.K.) LIMITED

P.O. Box 30, St. Leonards-on-Sea, East Sussex,
TN37 7NL, England. Telephone: 0424 753246.



7400	11p	74181A	36p	74LS73	18p	74LS377	60p	4553	245p	LM391	150p	TL430C	70p	8279	560p	KEYBOARD ENCODER	AY-6-2376	700p	2N3702/3	12p	1A 600V	30p
7401	11p	74153	40p	74LS74	16p	74LS378	60p	4556	35p	LM393	150p	UA2240	160p	MJ2955	75p	MJ3001	220p	2N3794/5	12p	2A 50V	30p	
7402	11p	74156	40p	74LS76	16p	74LS380	60p	4556	35p	LM394	300p	UAA170	170p	MJ4502	£4	MJ4503	£4	2N3796/7	14p	2A 100V	35p	
7403	12p	74157	30p	74LS83	36p	74LS383	45p	4560	120p	LM709	36p	UDN6118	320p	MJ4508	60p	MJ4509	60p	2N3708/9	12p	2A 400V	45p	
7404	12p	74158	30p	74LS85	48p	74LS386	48p	4568	250p	LM710	50p	UDN6184	320p	MJ2991B	£8	MJ2992	£8	2N3773	225p	3A 200V	60p	
7405	15p	74159	75p	74LS86	16p	74LS389	160p	4569	170p	LM723	70p	ULN2003	100p	ZBOP10	250p	MJ2993	£8	2N3819	25p	3A 600V	72p	
7406	20p	74161	48p	74LS90	22p	74LS392	22p	4572	30p	LM733	70p	ULN2068	200p	ZBOPCTC	250p	MJ2994	£8	2N3823	40p	4A 100V	95p	
7407	20p	74162	48p	74LS93	22p	74LS395	22p	4583	90p	LM741	18p	ULN2802	200p	ZBOPACTC	200p	MJ2995	£8	2N3866	90p	4A 50V	80p	
7408	14p	74163	48p	74LS96	40p	74LS398	40p	4585	75p	LM747	70p	UPC575	400p	ZBODART	700p	MJ2996	£8	2N3902	70p	6A 100V	100p	
7409	14p	74164	48p	74LS99	40p	74LS401	40p	4585	75p	LM748	36p	UPC592H	200p	ZBODAMA	£10	MJ2997	£8	2N3903/4	18p	6A 400V	120p	
7410	14p	74165	48p	74LS102	40p	74LS404	40p	4585	75p	LM750	36p	UPC1156H	300p	ZBODAO	£10	MJ2998	£8	2N3905/6	20p	10A 400V	200p	
7411	18p	74166	150p	74LS103	27p	74LS407	27p	4585	75p	LM751	36p	XR204	300p	ZBODAO-0/1/2	£7	MJ2999	£8	2N4027	40p	25A 400V	400p	
7412	18p	74167	150p	74LS109	27p	74LS410	27p	4585	75p	LM752	36p	XR221	600p	CRT CONTROLLER		MJ3000	£8	2N4123/4	20p			
7413	18p	74170	120p	74LS113	22p	74LS413	22p	4585	75p	LM753	36p	XR2216	675p	AD161/2	46p	MJ3001	£8	2N4401/3	27p			
7414	20p	74172	275p	74LS114	22p	74LS416	22p	4585	75p	LM754	36p	ZN414	22p	BC107/8	13p	MJ3002	£8	2N4427	90p			
7415	20p	74173	60p	74LS122	28p	74LS419	28p	4585	75p	LM755	36p	ZN419C	22p	BC107/9	14p	MJ3003	£8	2N4871	60p			
7416	20p	74174	60p	74LS123	34p	74LS422	34p	4585	75p	LM756	36p	ZN424E	13p	BC117	20p	MJ3004	£8	2N5006	60p			
7417	20p	74175	60p	74LS124	34p	74LS425	34p	4585	75p	LM757	36p	ZN426E	35p	BC169C	12p	MJ3005	£8	2N5089	27p			
7420	15p	74176	40p	74LS125	24p	74LS428	24p	4585	75p	LM758	36p	ZN427E	62p	BC172	12p	MJ3006	£8	2N5172	27p			
7421	20p	74177	40p	74LS126	24p	74LS431	24p	4585	75p	LM759	36p	ZN428E	50p	BC177/8	17p	MJ3007	£8	2N5194	30p			
7422	20p	74178	80p	74LS132	35p	74LS434	35p	4585	75p	LM760	36p	ZN434E	70p	BC177/9	17p	MJ3008	£8	2N5194	30p			
7423	20p	74179	80p	74LS133	25p	74LS437	25p	4585	75p	LM761	36p	ZN434E	70p	BC178	19p	MJ3009	£8	2N5298	65p			
7426	28p	74180	40p	74LS136	25p	74LS440	25p	4585	75p	LM762	36p	ZN434E	70p	BC182/3	11p	MJ3010	£8	2N5401	60p			
7427	28p	74181	115p	74LS138	27p	74LS443	27p	4585	75p	LM763	36p	ZN434E	70p	BC187	30p	MJ3011	£8	2N5457	30p			
7428	26p	74184A	90p	74LS139	27p	74LS446	27p	4585	75p	LM764	36p	ZN434E	70p	BC212/3	11p	MJ3012	£8	2N5460	30p			
7430	14p	74185	90p	74LS145	70p	74LS449	70p	4585	75p	LM765	36p	ZN434E	70p	BC214	12p	MJ3013	£8	2N5460	30p			
7432	22p	74186	470p	74LS147	120p	74LS452	120p	4585	75p	LM766	36p	ZN434E	70p	BC217	15p	MJ3014	£8	2N5460	30p			
7433	22p	74187	470p	74LS148	120p	74LS455	120p	4585	75p	LM767	36p	ZN434E	70p	BC218	11p	MJ3015	£8	2N5460	30p			
7434	25p	74189	45p	74LS151	70p	74LS458	70p	4585	75p	LM768	36p	ZN434E	70p	BC219	11p	MJ3016	£8	2N5460	30p			
7435	25p	74190	45p	74LS153	60p	74LS461	60p	4585	75p	LM769	36p	ZN434E	70p	BC220	11p	MJ3017	£8	2N5460	30p			
7438	15p	74192	45p	74LS156	30p	74LS464	30p	4585	75p	LM770	36p	ZN434E	70p	BC221	11p	MJ3018	£8	2N5460	30p			
7441	55p	74193	48p	74LS156	30p	74LS467	30p	4585	75p	LM771	36p	ZN434E	70p	BC222	11p	MJ3019	£8	2N5460	30p			
7442A	32p	74194	45p	74LS156	30p	74LS470	30p	4585	75p	LM772	36p	ZN434E	70p	BC223	11p	MJ3020	£8	2N5460	30p			
7443	32p	74195	45p	74LS157	27p	74LS473	27p	4585	75p	LM773	36p	ZN434E	70p	BC224	11p	MJ3021	£8	2N5460	30p			
7445	50p	74196	45p	74LS157	27p	74LS476	27p	4585	75p	LM774	36p	ZN434E	70p	BC225	11p	MJ3022	£8	2N5460	30p			
7446A	60p	74197	45p	74LS158	30p	74LS479	30p	4585	75p	LM775	36p	ZN434E	70p	BC226	11p	MJ3023	£8	2N5460	30p			
7447A	36p	74198	85p	74LS160	36p	74LS482	36p	4585	75p	LM776	36p	ZN434E	70p	BC227	11p	MJ3024	£8	2N5460	30p			
7448	46p	74199	85p	74LS162	36p	74LS485	36p	4585	75p	LM777	36p	ZN434E	70p	BC228	11p	MJ3025	£8	2N5460	30p			
7451	15p	74221	55p	74LS163	36p	74LS488	36p	4585	75p	LM778	36p	ZN434E	70p	BC229	11p	MJ3026	£8	2N5460	30p			
7452	15p	74225	55p	74LS164	36p	74LS491	36p	4585	75p	LM779	36p	ZN434E	70p	BC230	11p	MJ3027	£8	2N5460	30p			
7454	15p	74273	140p	74LS164	40p	74LS494	40p	4585	75p	LM780	36p	ZN434E	70p	BC231	11p	MJ3028	£8	2N5460	30p			
7460	17p	74278	100p	74LS165	50p	74LS497	50p	4585	75p	LM781	36p	ZN434E	70p	BC232	11p	MJ3029	£8	2N5460	30p			
7470	36p	74279	50p	74LS170	70p	74LS500	70p	4585	75p	LM782	36p	ZN434E	70p	BC233	11p	MJ3030	£8	2N5460	30p			
7472	25p	74283	50p	74LS173	55p	74LS503	55p	4585	75p	LM783	36p	ZN434E	70p	BC234	11p	MJ3031	£8	2N5460	30p			
7473	25p	74284	160p	74LS174	40p	74LS506	40p	4585	75p	LM784	36p	ZN434E	70p	BC235	11p	MJ3032	£8	2N5460	30p			
7474	20p	74290	100p	74LS175	40p	74LS509	40p	4585	75p	LM785	36p	ZN434E	70p	BC236	11p	MJ3033	£8	2N5460	30p			
7475	30p	74293	100p	74LS175	40p	74LS512	40p	4585	75p	LM786	36p	ZN434E	70p	BC237	11p	MJ3034	£8	2N5460	30p			
7476	30p	74298	100p	74LS176	40p	74LS515	40p	4585	75p	LM787	36p	ZN434E	70p	BC238	11p	MJ3035	£8	2N5460	30p			
7480	48p	74351	190p	74LS191	36p	74LS518	36p	4585	75p	LM788	36p	ZN434E	70p	BC239	11p	MJ3036	£8	2N5460	30p			
7481	100p	74356	35p	74LS192	36p	74LS521	36p	4585	75p	LM789	36p	ZN434E	70p	BC240	11p	MJ3037	£8	2N5460	30p			
7482	55p	74366	35p	74LS193	36p	74LS524	36p	4585	75p	LM790	36p	ZN434E	70p	BC241	11p	MJ3038	£8	2N5460	30p			
7483A	36p	74368	35p	74LS194	36p	74LS527	36p	4585	75p	LM791	36p	ZN434E	70p	BC242	11p	MJ3039	£8	2N5460	30p			
7484	65p	74368	35p	74LS194	36p	74LS530	36p	4585	75p	LM792	36p	ZN434E	70p	BC243	11p	MJ3040	£8	2N5460	30p			
7485	90p	74376	100p	74LS195	36p	74LS533	36p	4585	75p	LM793	36p	ZN434E	70p	BC244	11p	MJ3041	£8	2N5460	30p			
7486	20p	74390	70p	74LS197	45p	74LS536	45p	4585	75p	LM794	36p	ZN434E	70p	BC245	11p	MJ3042	£8	2N5460	30p			
7489	170p	74393	90p	74LS221	50p	74LS539	90p	4585	75p	LM795	36p	ZN434E	70p	BC246	11p	MJ3043	£8	2N5460	30p			
7490A	20p	74490	95p	74LS240	55p	74LS542	55p	4585	75p	LM796	36p	ZN434E	70p	BC247	11p	MJ3044	£8	2N5460	30p			
7491	35p	74492	95p	74LS241	55p	74LS545	55p	4585	75p	LM797	36p	ZN434E	70p	BC248	11p	MJ3045	£8	2N5460	30p			
7492A	25p	74493	95p	74LS242	55p	74LS548	55p	4585	75p	LM798	36p	ZN434E	70p	BC249	11p	MJ3046	£8	2N5460	30p			
7493A	24p	74494	24p	74LS243	55p	74LS551	55p	4585	75p	LM799	36p	ZN434E	70p	BC250	11p	MJ3047	£8	2N5460	30p			
7494	36p	74495	36p	74LS244	55p	74LS554	55p	4585	75p	LM800	36p	ZN434E	70p	BC251	11p	MJ3048	£8	2N5460	30p			
7495A	35p	74496	35p	74LS245	70p	74LS557	70p	4585	75p	LM801	36p	ZN434E	70p	BC252	11p	MJ3049	£8	2N5460	30p			
7496	40p	74497	40p	74LS246	70p	74LS560	70															

NOTES:

- (1) Including ferrites, RF chokes etc.
- (2) Discrete devices.
- (3) Other than optoelectronic.
- (4) Access and Barclaycard, where marked.
- (5) See company listing.
- (6) In pence unless otherwise noted.
N = NIL (no charge).

	RESISTORS	CAPACITORS	POTENTIOMETERS	TRANSFORMERS	INDUCTORS (1)	DIODES, SCRs TRIACS	TRANSISTORS (2)	LINEAR ICs	DIGITAL ICs	LINEAR MSI/LSI	DIGITAL MSI/LSI	OPTOELECTRONICS	VALVES	RELAYS	SWITCHES	FUSES AND PROTECTION	BATTERIES AND PSUs	ANALOGUE PANEL METERS	TRANSDUCERS (3)	PCB HARDWARE
COLLECTIVE COMPONENTS																				
CRICKEWOOD ELECTRONIC																				
CRIMSON COMPONENTS																				
CRIMSON ELECTRIK																				
CRP ELECTRONICS																				
CVS ENTERPRISES																				
DAMON ELECTRONICS																				
D.J. ELECTRONICS																				
EAST CORNWALL																				
ELECTRONIC HOBBIES																				
ELECTRONIC SURPLUS																				
ELECTRONICS WORLD																				
ELECTRONI — KIT																				
ELECTROTECH																				
ELECTROVALUE LTD.																				
ENFIELD ELECTRONICS																				
ETESON ELECTRONICS																				
GLOBAL SPECIALITIES																				
GODDARDS COMPONENTS																				
GREENBANK ELECTRONICS																				

PLUGS AND SOCKETS	ENCLOSURES, CASES	HEATSINKS	KNOBS, MISC. HARDWARE	CABLE AND WIRE	BREADBOARDS	TOOLS	PCBs and/or MATERIALS	CHEMICALS	CUSTOM KITS, MODULES	SURPLUS SUPPLIES	BARGAIN PACKS	BOOKS	CATALOGUE/PRICE LIST	MAIL ORDER MINIMUM (6)	P&P (6)	OVERSEAS ORDERS	CREDIT CARDS (4)	SHOPS	OTHER
-------------------	-------------------	-----------	-----------------------	----------------	-------------	-------	-----------------------	-----------	----------------------	------------------	---------------	-------	----------------------	------------------------	---------	-----------------	------------------	-------	-------

NOTES:
 (1) Including ferrites, RF chokes etc.
 (2) Discrete devices.
 (3) Other than optoelectronic.
 (4) Access and Barclaycard, where marked.
 (5) See company listing.
 (6) In pence unless otherwise noted.
 N = NIL (no charge).

													£5	(5)					COLLECTIVE COMPONENTS
													N	70	(5)				CRICKLEWOOD ELECTRONIC
													N	20	(5)				CRIMSON COMPONENTS
													£3	(5)					CRIMSON ELECTRIK
													N	(5)					CRP ELECTRONICS
													£5						CVS ENTERPRISES
													£1	(5)					DAMON ELECTRONICS
													(5)						D.J. ELECTRONICS
													N	30					EAST CORNWALL
																(5)			ELECTRONIC HOBBIES
													£1	N					ELECTRONIC SURPLUS
													N	50					ELECTRONICS WORLD
													(5)						ELECTRONI — KIT
													£5	(5)					ELECTROTECH
													1	(5)					ELECTROVALUE LTD.
													50	(5)					ENFIELD ELECTRONICS
													N	35					ETESON ELECTRONICS
													N	(5)	(5)				GLOBAL SPECIALITIES
																			GODDARDS COMPONENTS
													2	50					GREENBANK ELECTRONICS

AITKEN BROS.

ELECTRONIC COMPONENTS AND TEST EQUIPMENT
 35, HIGH BRIDGE, NEWCASTLE
 UPON TYNE NE11EW TEL: 0632 326729



SAFEGAN OSCILLOSCOPES— 5 mV/div sensitivity. Choice of Bandwidth 10, 1MHz, 15 MHz, 20 MHz. 1S/div—100nS/div. Calibrated timebase. Solid trigger with bright line auto, normal and TV. XY facility. Z modulation. Calibration output. Bright and clear display. Portability. • Model DT410-10 MHz £205.85. Model DT415-15 MHz £217.35. • Model DT420 20 MHz £228.85. Send S.A.E. FOR FULL spec.

THANDAR PDM35 3 1/2 DIGIT L.E.D. DIGITAL POCKET MULTI-METER. • DC volts (4 ranges) 1mV to 1000V. • AC volts TV to 500V • DC current (6 ranges) 1nA to 200mA • Resistance (5 ranges) 1Ω to 20 meg. £2. £39.95. • AC adaptor \$5.95. • carrying case \$3.65 • MN1604 Battery \$1.57.

THANDAR TM354 3 1/2 DIGIT LCD DIGITAL POCKET MULTIMETER • DC volts 1mV to 1000V • AC volts TV to 500 V AC rms • DC current 1µA to 2A • Resistance 1Ω to 2 MΩ • Diode check • Basic accuracy ± (0.75% of reading + 1 digit) • Battery life typically 2000 hrs • leads inc. • £45.94 • 40KV Probe \$34.95 • Universal test lead set £12.95.

KD30C LCD DIGITAL MULTIMETER
 • 3 1/2 digit • Auto zero • Auto polarity • Full overload protection • 10 MegΩ input impedance • Over range and low battery indication • DC volts 200 mV-1000 V 5 ranges • AC volts 200 mV-700 V 5 ranges • DC current 200 µA 10 A 6 ranges • AC current 200 µA-10 A 6 ranges • Resistance 200 Ω-200 MegΩ
 • Complete with battery, test leads, spare fuse and carrying case £39.95

THANDAR SC110 SINGLE TRACE LOW POWER 2" OSCILLOSCOPE • Bandwidth DC to 10 Mhz • Sensitivity: 10mV/div to 50 V/div. • Sweep speeds: 0.1µ secs / div to 0.5 secs/div. • Power requirements 4-10 V DC 4 'C' cells • Size & weight 255x150x40mm • 800gms £159.85 a truly portable and superb instrument • Carrying case \$8.86 • AC Adaptor \$5.69 • Nicad Batt. pack \$8.63 • x1 probe \$9.78 • x10 probe \$11.50 Complete range of Thandar instruments available from stock S.A.E. for CAT. & prices.



G.S.C. SOLDERLESS BREADBOARDS • Accepts all components with leads up to .033" • Replaceable nickel-silver spring clip contacts. • Combines bus strip with board • Unlimited expansion • 3" and 8" centre chanel • Three free experimental circuits with every purchase

	Centre Channel	Strip Length	Strip Width	Tie Points	Term Clips	I.C. Cpty.	Price
EXP-600	15mm	152mm	61mm	550	110	3 28pin	\$7.25
EXP-300	8mm	152mm	53mm	550	110	3 14pin	\$6.62
EXP-4B	n/a	152mm	25mm	160	32	n/a	\$2.65
EXP-650	15mm	91mm	61mm	270	54	1 40pin	\$4.14
EXP-350	8mm	91mm	53mm	270	54	3 14pin	\$3.62
EXP-325	8mm	48mm	53mm	130	26	1 22pin	\$1.84

Please send S.A.E. for catalogue listing complete range of G.S.C. Instruments and Boards.

SABTRONICS LCD MULTIMETER MODEL 2033. • DC volts 100 µV-1000V Accuracy + -5% • AC volts 100µV-1000 V Accuracy ± 1% • DC current 10µA-2A Accuracy ± 1% • AC current 10µA-2A Accuracy ± 1% • Resistance 1Ω-20 MΩ Accuracy ± 1% • £42.27. • Please send 30p for full Sabtronic catalogue and price list

TMK 500 MULTIMETER • 30 kapv. • AC volts 2.5 10 25 100 250 500 1000V • DC volts 0.25 1 2.5 10 25 100 250 1000 • DC current 50µA 5MA 50MA 12 amp • Resistance 0-6K 60K, 60 meg. • Decibels -20 to + 56 dB • Buzzer continuity test • Size 160x110 x65 • Batteries and leads inc. £26.95

YN360 TR MULTIMETER • AC volts 10 50 250 1000 • DC volts 0.1, 0.5, 2.5, 10V 150V 250V, 1000V. • DC current 50µA 2.5 MA, 25MA, 250 MA • Resistance 0-2K 20K 2M Ω, 20 MΩ, • Transistor check • DB -10db -+ 22db \$16.95

DESOLDERING TOOL \$6.45


SCHOOLS, COLLEGES, UNIVERSITIES SUPPLIED. PHONE OR SEND YOUR ACCESS OR BARCLAYCARD NUMBER.

PRICES INCLUDE VAT, PLEASE ADD 75p POSTAGE TO ORDERS UNDER £10.00

HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

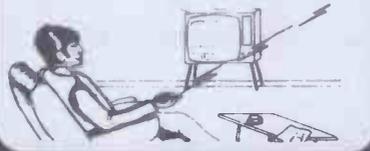- TDR300K Remote Control Dimmer £14.30
- MK6 Transmitter for above £4.20
- TD300K Touchdimmer £7.00
- TDE/K Extension kit for 2-way switching for TD300K £2.00
- LD300K Rotary Controlled Dimmer £3.50



DISCO LIGHTING KITS

DL 1000K
 This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **Only £14.60**

DL2100K
 A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched off at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1 Allowing audio ("beat")—light response. **60p**

NEW DL3000K
 This 3 channel sound to light kit features zero voltage switching, automatic level control & built in mic. No connections to speaker or amp required. No knobs to adjust—simply connect to mains supply & lamps. **Only £11.95** (1Kw/Channel)

DISPLAYS

- CQX87A 0.5" dual, c.a. Red £1.80
- DL340M 0.1" 4-Digit c.c. £4.50
- FND 501 0.5" c.c. 85p
- FND 507 0.5" c.a. 85p
- MP463 4-digit 0.5" multiplexed c.c. £2.20
- LED Clock Display £2.20

Liquid Crystal Display, 3 1/2 digit, 0.5" digits, d.I.I. package £6.00

KL901 9-digit, 7-seg, 0.1" c.c. LED calculator display with red filter £5.5p

TRIACS

- 400v Plastic case (Texas) 3AT1C206D 49p
- 8AT1C226D 58p
- 12AT1C236D 85p
- 16AT1C246D 96p
- 25AT1C263D 190p

- 5A with trigger Q4006LT 85p
- 8A isolated tab TXAL228B 65p
- Diac 18p
- Opto isolated triac MOC3020 0.1A/400v 110p

LCD 3 1/2 DIGIT MULTIMETER
 16 ranges including DC and AC voltage, DC current and resistance +NPN & PNP transistor gain and diode check. Input impedance 10M. Size 155x88x31mm. Requires PP3 9v battery. **ONLY £31.00**

TRANSISTORS

- BC108 8p
- BC109 15p
- BC182 8p
- BC182L 8p
- BC212 9p
- BC212 9p
- BC327 12p
- BC337 13p
- BFY50 20p
- TIP31A 40p
- TIP32A 40p
- 2N3055 45p
- 2N3442 115w/140v
- 115w/140v 90p
- 2N3819 N ch fet 20p

VMOS POWER FETS

- VN10KM 0.5A/60v 52p
- VN66AF 2A/60v 88p

Add 55p postage & packing +15% VAT to total Overseas Customers; Add £1.75 (Europe), £4.50 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability. **OPEN** 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)



REMOTE CONTROL

Published remote control systems tend to be quite complicated requiring difficult-to-get components and a well-equipped lab to get them to work. If you have put you off making your own system we have just the kits for you. Using infra red, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling, e.g. TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices. We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself!—SEND US 30p and a stamped addressed envelope for your copy TODAY!

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at preset times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.



- CT1000K Basic Kit £14.90
- CT1000K with white box (56/131 x 71mm) £17.40
- (Ready Built) £22.50

DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.



Price £15.50

FREE SHORT FORM CATALOGUE— send SAE (6" x 9"). We also stock Vero, Books, Resistors, Capacitors, Semi-Conductors etc.

FAST SERVICE · TOP QUALITY · LOW LOW PRICES

ALL PRICES EXCLUDE VAT

No circuit is complete without a call to

TK ELECTRONICS
 11 Boston Road
 London W7 3SJ

TEL: 01-567 8910 ORDERS
 01-579 9794 ENQUIRIES
 01-579 2842 TECHNICAL AFTER 3PM

HE PROJECT KITS

I.C.s TRANSISTORS CAPACITORS TOOLS RESISTORS HARDWARE CASES KITS

MAGENTA

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for H.E. Projects. We supply carefully selected sets of parts to enable you to construct H.E. projects. Kits include ALL the electronics and hardware needed. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of H.E. which includes the project — you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- 'JUNIOR' SLOT CAR CONTROLLER** Sept 82 £5.60 less case.
ZX INTERFACE BOARD Sept 82 inc edge con £11.33.
AUDIO ANALYSER Aug 82 less case £83.97.
SWR METER Aug 82 £8.95.
T.V.I. FILTER July 82 £5.33
AUTO WAH June 82 £18.98 inc case or £12.28 less case.
AUTO GREENHOUSE SPRINKLER June 82 £15.38 less pump and power supply (12V 2A).
TELEPHONE TIMER June 82 £33.42 less power supply (suitable type below).
POWER SUPPLY DESIGN 12V 500mA June 82 £9.98
ECHO REVERB UNIT May 82. Less case £33.98. Economy case WB3 £3.76 extra
DIGITAL THERMOMETER May 82 excluding case + bezel £16.90
AUDIO SIGNAL GENERATOR May 82 £20.98.
CABLE TRACKER May 82 £9.98
DIGITAL CAPACITANCE METER Apr 82 £21.37
SIGNAL TRACER Apr 82 £3.86
BIKE ALARM Apr 82 £11.74
DIGITAL DICE Mar 82 £7.29
BICYCLE SIREN Mar 82 £10.89
NOISELESS FUZZBOX Feb 82 £10.45
MASTHEAD AMPLIFIER Feb 82 £14.74
DRUM SYNTHESIZER Dec 81. Full kit £21.37
GUITAR HEADPHONE AMPLIFIER Dec 81 £3.72
IN CAR CASSETTE POWER SUPPLY Dec 81 £4.77
SCRATCH FILTER Nov 81 Mono £5.82 Stereo £8.98
LED VU METER Nov 81 less case £4.87
SIMPLE STYLUS ORGAN Nov 81 less case £4.98
METRONOME NOV 81 £12.71
TELEPHONE BELL REPEATER Oct 81 £13.67
 Med linking wire extra 14p metre
COMBINATION LOCK Oct 81 less solenoid £18.65
BABY ALARM Oct 81 £8.70, Fig 8 linking wire 7p metre
'DIANA' METAL LOCATOR Sept 81 £34.50
POWERPACK Sept 81 £10.25
- REACTION TESTER GAME** Sept 81 £12.81
VARIABLE BENCH POWER SUPPLY Aug 81 £26.98
ULTRASOUND BURGLAR ALARM July 81 £19.98
ELECTRONIC DOOR BUZZER July 81 £5.98
ELECTRONIC METRONOME July 81 £4.99
CONTINUITY CHECKER June 81 £5.71
ENVELOPE GENERATOR June 81 £17.98
AUDIO MIXER June 81 £5.33
PUBLIC ADDRESS AMPLIFIER March 81 £19.48. Extras - horn speakers £6.83 each, PA MIC £4.40
FUZZBOX March 81 £10.98
WINDSCREEN WIPER CONTROLLER March 81 £8.20
STEAM LOCO WHISTLE March 81 £12.98
PHOTOGRAPHIC TIMER March 81 £3.50
HEARTBEAT MONITOR Feb 81 £24.98
TWO-TONE TRAIN HORN Feb 81 £5.60 less case
 medium wave radio Feb 81 £8.20
BENCH AMP Jan 81 £10.80
NICAD CHARGER Jan 81 £8.20
CHUFFER Jan 81, less case £7.53
BATTERY CHARGE MONITOR Dec 82 £5.77
MEMORY BANK - MINI SYNTHESISER Nov & Dec 80 £29.98
TRANSISTOR TESTER Nov 81 £6.54 inc test leads
GUITAR PRE-AMP Nov 80 £6.65 case (diecast) extra £2.29
INTRUDER ALARM Oct 80 £20.98
TOUCH SWITCH Sept 80 £2.75 less case & contacts
 guitar phaser Sept 80 £16.28
SOUND OPERATED FLASH TRIGGER July 80 no sct £5.33
FOG HORN June 80 £6.64
SPEED CONTROLLER FOR R/C April 80 £17.55 (less case)
DIGITAL FREQUENCY METER April 80 £39.98
DIGI-DICE Jan 80 £11.73
GUITAR TUNER Nov 79 £12.82
CAR ALARM Feb 79 £12.91

MORE PROJECT KITS — SIMILAR STYLE TO H.E.

INSTRUCTIONS INCLUDED (SEPARATELY 45p EACH) PLEASE QUOTE REF. NO. WHEN ORDERING

- | | |
|--|--|
| B1 PEST CONTROL Ultrasonic cat scarer £7.65 | B11 IN SITU TRANSISTOR TESTER £6.98 |
| B2 COMPONENT TESTER £8.88 | B12 WEIRD SOUND EFFECTS GENERATOR £5.98 |
| B4 GUITAR NOTE EXPANDER £17.98 | B13 AUDIBLE VISUAL METRONOME £5.98 |
| B6 GUITAR NOTE EXPANDER £17.98 | B14 ELECTRONIC DICE £5.71 |
| B5 CAMERA OR FLASH GUN TRIGGER Infra red system £12.51 | B16 MINI EGG TIMER £4.34 |
| B6 SIMPLE INFRA RED REMOTE CONTROL £17.20 | B17 AUDIO EFFECTS UNIT FOR WEIRD SOUNDS £12.98 |
| B7 0-12V POWER SUPPLY £17.98 | B18 LED JEWELLERY — Cross brooch £2.77 Star brooch £9.91 Spiral brooch £7.98 |
| B8 SOIL MOISTURE MONITOR £4.68 | |
| B9 SOUND TO LIGHT — single channel £8.42 | |
| B10 THREE CHANNEL SOUND TO LIGHT £21.44 | |

MORE KITS AND COMPONENTS IN OUR LISTS
 FREE PRICE LIST
 Price list included with orders or send sae (9x4) CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Sends 80p in stamps or add 80p to order.

MORE H.E. PLUS E.E. and E.T.I. PROJECT. KITS IN THE PRICE LIST

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

MAGENTA ELECTRONICS LTD

HP29, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS, DE14 2ST. 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY ADD 45p P&P TO ALL ORDERS PRICES INC VAT

ACCESS and BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST. SAE ALL ENQUIRIES.

Prices inc. VAT OFFICIAL ORDERS WELCOME OVERSEAS. Payment must be in sterling. IRISH REPUBLIC and BFPO: UK PRICES. EUROPE: UK PRICES plus 10%. ELSEWHERE: write for quote.

SOLDERING / TOOLS

- ANTEX X5 SOLDERING IRON 25W** £5.48
SOLDERING IRON STAND £1.98
SPARE BITS. Small standard, large, 65p each. For X5 + X25
SOLDER. Handy size. 99p
SOLDER CARTON £1.84
DESOLDER BRAID 69p
HEAT SINK TWEEZERS 29p
DESOLDER PUMP £6.48
HOW TO SOLDER LEAFLET 12p
LOW COST CUTTERS £1.69
LOW COST LONG NOSE PLIERS £1.68
WIRE STRIPPERS & CUTTERS £2.69

- RESISTOR COLOUR CODE** 21p
CALCULATOR 49p
CONNECTING WIRE PACK TYPE ED. 11 colours 49p
ILLUMINATED MAGNIFIERS
 Small 2" dia. (5x mag.) £1.14
 Large 3" dia. (4x mag.) £2.40
CAST IRON VICE £2.98
SCREWDRIVER SET £1.98
POCKET TOOL SET £3.98
DENTISTS INSPECTION MIRROR £2.85
JEWELLERS EYEGLASS £1.50
PLASTIC TWEEZERS 69p
PAIR OF PROBES WITH LEADS (cc) 77p



HELPING HANDS JIG £6.30

Heavy base. Six ball and socket joints allow infinite variation of clips through 360°. Has 2 1/4" diameter (25x) magnifier attached, used and recommended by our staff.
VERO SPOT FACE CUTTER £1.49
PIN INSERTION TOOL £1.98
VEROPINS (pk of 100) 0.1" 52p
MULTIMETER TYPE 1 (1,000 opv) £5.48
MULTIMETER TYPE 2 (20,000 opv) with transistor tester. Very good £14.75
CROCODILE CLIP TEST LEAD SET. 10 leads with 20 clips 99p

MULTIMETER TYPE 2 - YN360 TR, £14.75

20,000 opv. Includes transistor tester. AC + DC volts. DC current. 4 very useful resistance ranges. We've used it and we like it.

- | | |
|---|--|
| SPEAKERS. Miniature, 8 ohm 87p | MIN. BUZZERS. 6V. 50p. 9V. £1.10. |
| 54-75 ohm 89p | 12V. 65p. |
| CRYSTAL EARPIECE 65p | MAGNETIC EARPIECE 15p |
| MONO HEADPHONES £2-96 | STEREO HEADPHONES £4-35 |
| TELEPHONE PICK-UP COIL 72p | F.M. AERIAL 49p |

- VEROBOARD 0.1" COPPER STRIPS**
 10 strips 24 holes £1.20 per 5
 24 strips 37 holes 78p
 24 strips 50 holes 89p
 36 strips 37 holes 89p
 36 strips 50 holes 99p
 Terminal pins 0.1" 52p/100

- PP3 CLIPS** 10p
PP9 CLIPS 11p

- PANEL METERS**
 50uA; 100uA; 1mA, 1A, 25V, 100uA-0-100uA; 5A, AU £4-98 each. State value.

- EUROBREADBOARD** £6.20
S-DEC BREADBOARD £3.98
BIMBOARD 1 BREADBOARD £6.98
VEROBLOC BREADBOARD £4.20

BOOKS

- SEMICONDUCTOR DATA BOOK** Newnes £5.90
ELECTRONIC PROJECTS FOR HOME SECURITY £3.36
ELECT. PROJECTS IN PHOTOGRAPHY £3.36
110 ELECT. ALARM PROJECTS £5.35
MODEL RAILWAY PROJECTS £1.95
BASIC ELECTRONICS. Theory & practice £7.98
BEGINNERS GUIDE TO BUILDING ELECT. PROJECTS £1.50

ADVENTURES WITH MICROELECTRONICS

Similar to 'Electronics' below. Uses I.C.s. Includes dice, electronic organ, doorbell, reaction timer, radio, etc. Based on Bimboard 1 breadboard. Adventures with Microelectronics. £2.55
 Component pack £29.64 less battery.

by Tom Duncan

ADVENTURES WITH ELECTRONICS

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.40. Component pack £18.98 less battery.

ADVENTURES WITH DIGITAL ELECTRONICS

New book by Tom Duncan in the popular 'Adventures' series. This book of entertaining and instructive projects is designed for hobbyists, and students. It provides a stepping stone to the microprocessor. The first part deals with the properties of some basic ICs used in digital electronics. The second part gives details of how to build eight devices — shooting gallery, 2 way traffic lights, electronic adder, computer space invaders game etc. For each project there is an explanation of 'how it works' and also suggestions for 'things to try'. No soldering — all circuits built on 2 Bimboard 1 breadboards. Adventures with Digital Electronics book £3.25. Component pack £42.50 ref EHDC. All the components needed including 2 breadboards and hexadecimal keyboard. Available less breadboards £29.98 ref EHDF. Both less battery.

NOTES:

- (1) Including ferrites, RF chokes etc.
- (2) Discrete devices.
- (3) Other than optoelectronic.
- (4) Access and Barclaycard, where marked.
- (5) See company listing.
- (6) In pence unless otherwise noted.
N = NIL (no charge).

	RESISTORS	CAPACITORS	POTENTIOMETERS	TRANSFORMERS	INDUCTORS (1)	DIODES, SCRs TRIACS	TRANSISTORS (2)	LINEAR ICs	DIGITAL ICs	LINEAR MSI/LSI	DIGITAL MSI/LSI	OPTOELECTRONICS	VALVES	RELAYS	SWITCHES	FUSES AND PROTECTION	BATTERIES AND PSUs	ANALOGUE PANEL METERS	TRANSDUCERS (3)	PCB HARDWARE
GREENWAY																				
GREENWELD																				
HART ELECTRONIC KITS																				
HEMMINGS ELECTRONICS																				
HENRYS RADIO																				
ILP																				
INTEL ELECTRONICS																				
LANGREX SUPPLIES																				
L.B. ELECTRONICS																				
LIGHTNING ELECTRONICS																				
MAGENTA ELECTRONICS																				
MAPLIN																				
MARCO TRADING																				
MARSHALL'S (LONDON)																				
BRADLEY MARSHALL																				
MICRO-TIMES,																				
MIDWICH COMPUTER CO																				
MODULAR ELECTRONICS																				
MS COMPONENTS LTD																				
MYERS ELECTRONICS																				

PLUGS AND SOCKETS	ENCLOSURES, CASES	HEATSINKS	KNOBS, MISC. HARDWARE	CABLE AND WIRE	BREADBOARDS	TOOLS	PCBs and/or MATERIALS	CHEMICALS	CUSTOM KITS, MODULES	SURPLUS SUPPLIES	BARGAIN PACKS	BOOKS	CATALOGUE/PRICE LIST	MAIL ORDER MINIMUM (6)	P&P (6)	OVERSEAS ORDERS	CREDIT CARDS (4)	SHOPS	OTHER
-------------------	-------------------	-----------	-----------------------	----------------	-------------	-------	-----------------------	-----------	----------------------	------------------	---------------	-------	----------------------	------------------------	---------	-----------------	------------------	-------	-------

NOTES:
 (1) Including ferrites, RF chokes etc.
 (2) Discrete devices.
 (3) Other than optoelectronic.
 (4) Access and Barclaycard, where marked.
 (5) See company listing.
 (6) In pence unless otherwise noted.
 N = NIL (no charge).

													£2	50					GREENWAY
													£1	50	(5)				GREENWELD
													N	(5)					HART ELECTRONIC KITS
													N	(5)					HEMMINGS ELECTRONICS
													N	(5)					HENRYS RADIO
													90	(5)			(5)		ILP
													N	(5)					INTEL ELECTRONICS
													£1	50					LANGREX SUPPLIES
													N	(5)					L.B. ELECTRONICS
													N	(5)					LIGHTNING ELECTRONICS
													N	45		(5)			MAGENTA ELECTRONICS
													(5)	(5)					MAPLIN
													N	35					MARCO TRADING
													N	60		(5)			MARSHALL'S (LONDON)
													£1	40		(5)			BRADLEY MARSHALL
													N	50					MICRO-TIMES
													N	(5)					MIDWICH COMPUTER CO
													175	50					MODULAR ELECTRONICS
													N	N					MS COMPONENTS LTD
													£3	60					MYERS ELECTRONICS

Beginners' luck

30% OFF
10 selected kits
for first-time
builders



Shortwave
Listener's
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need is there.



Digital Clock

Follow the steps and you'll end up with a hand-crafted, well-designed piece of equipment. One you'll be proud


of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of kits from a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.



Windspeed and Direction
Indicator

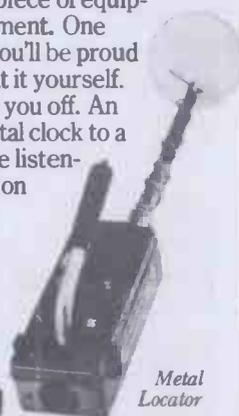

Metal
Locator

To Heath Electronics
(UK) Limited, Dept (HE10),
Bristol Road, Gloucester GL2 6EE

To start me off, please send me
a copy of the new Heathkit catalogue.
I enclose 28p in stamps.

HE10

Name _____

Address _____

HEATH

You build on our experience

HEATHKIT

EVEN MISERS CAN'T RESIST OUR PRICES

KNOBBS

Round Stylish Knobs, Black and/or Satin Chrome finish. Various sizes. Our choice

.....10 for £1.50

V.U. Meters by Rank Audio. 5cms x 5cms. Scaled -20 to +5. Removable cover for re-scaling if required£1.00 for each or 10 for £9
Slide Switches. Std size. 240 volt. DP/DT/ Centre Off, DP/ST, SP/ST. Drum or Belt Drive with reset. Silly price

.....25 pence each or 5 for £1.00

Push Button signal switches. 4 to 12 way, latching and non latching. Bargain Price. Asst Pack (10 switches).....£1.50

Slide Pot Knobs. Chrome Finish. Various sizes our choice10 for £1.20

Panel Fuseholders5 for £1.00

A.M. One way, 2 pin Plug and Socket. Give-away price10 for 50 pence

Resistors. Preferred values, mixed, our choice£1.00 per 100

4 Digit, 7 Segment, Fluorescent Displays with decimal point and colon and + or - segment. Compatible with MOS LSI. 15cms high digits. Unbeatable value at£1.75 each
Data Sheet supplied

Interconnecting cable, multi strand, our choice of colour2 pence per metre

BOOKS

Beginners Guide to Building Electronic Projects£1.50

Electronic Projects for Beginners£1.35

How to make Walkie Talkies£1.50

Model Railway Projects£1.95

Electronic Music Projects£1.75

Remote Control Projects£1.95

Digital I/C Projects£1.95

I/C 555 Projects£1.95

A Microprocessor Primer£1.75

An Introduction to Basic Programming Techniques£1.95

Postage & Packing on Books

1 book 40p, 2 books 55p, 3 books 75p,
Over 4 £1

ALL ITEMS BRAND NEW - NO SECONDS



D'JUSON LTD

PO BOX 298, ASCOT, BERKS SL5 9UR

Telephone: Ascot 27013

BI-PAK BARGAINS



5T21 SCREWDRIVER SET

6 precision screwdrivers in hinged plastic case. Sizes: — 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET

5 precision nut drivers in hinged plastic case. With turning rod. **£1.75**
 Sizes: — 3, 3.5, 4, 4.5 and 5mm.

5T41 TOOL SET

5 precision instruments in hinged plastic case
 Crosspoint (Phillips) screwdrivers: —
 H 0 and H 1 Hex key wrenches: —
 1.5 2 and 2.5mm **£1.75**

5T51 WRENCH SET

5 precision wrenches in hinged plastic case.
 Sizes: — 4, 4.5, 5, 5.5 and 6mm. **£1.75**

BUY ALL FOUR SETS: 5T21-5T51 and get

HEX KEY SET FREE
 HEX KEY SET ON RING.
 Sizes: 1.5, 2, 2.5, 3,
 4, 5, 5.5 and 6mm.
 Made of hardened steel.
 HX/1. **£1.25**



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm-2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects
 *Quantities approximate, count by weight.

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°-240° Inline 3-6 Pin, Speakers, Phono, Jack Stereo and Mono etc Valued at well over £3 normal Order No. SX25.

Our Price **£1.50** per pak.

Guaranteed to save you money.

SX26	3 Pks of 6 pin 240° DIN Plugs and Chassis Sockets	50p
SX27A	60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD	£1.00
SX28A	50 Assorted Silver Mica Caps. 5.6pF-150pF	£1.00
SX29A	50 Assorted Silver Mica Caps. 180pF-4700pF	£1.00
SX30A	50 High Voltage Disc Ceramic 750v min up to 8KV Assorted useful values	£1.00
SX31A	50 Wirewound 9 watt (avg) Resistors Assorted values 10hm-12K	£1.00

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1pf-56pf	£1
SX19	100	Mixed Ceramics 60pf-0.5mf	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000mf	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

BARGAINS

SX91	20 x Large 2" RED LED	£1
SX42	20 small .125 Red LED's	£1
SX43	10 Rectangular Green LED's .2	£1
SX46	30 Assorted Zener Diodes 250mw 2 watt mixed voltages, all coded. New.	£1
SX47	4 Black Instrument Knobs—winged with pointer 1/4" Standard screw. Fil size 29 x 20mm	50p
SX49	20 Assorted Slider Knobs Black/Chrome, etc.	£1
SX80	12 Neons and Filament Lamps. Low voltage and mains — various types and colours — some panel mounting	£1

BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
 LCD 10 MEGOHM INPUT IMPEDANCE
 *3 1/2 digit *16 ranges plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single-handed, pushbutton operation *Over range indication *12.5mm (1/2-inch) large LCD readout *Diode check *Fused circuit protection *Test leads, battery and instructions included.
 Max indication 1999 or — 1999
 Polarity indication Negative only
 Positive readings appear without + sign.
 Input impedance 10 Megohms
 Zero adjust Automatic
 Sampling time 250 milliseconds
 Temperature range — 5°C to 50°C
 Power Supply 1 x PP3 or equivalent 9V battery
 Consumption 20mw
 Size 155 x 88 x 31mm
RANGES
 DC Voltage 0-200mV, 0-2-20-200 1000V, Acc: 0.8%
 AC Voltage 0-200-1000V
 Acc: 1.2% DC Current 0-200uA, 0-2-20-200mA 0-10 A, Acc: 1.2%
 Resistance 0-2-20-200K ohms.
 0-2 Megohms, Acc: 1%
 BI-PAK VERY LOWEST POSS PRICE
£35.00 each



MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to maximum of 1 1/2". Approx size 80 x 120 x 66mm.
 Bi-Pak's Mini Vice at a Mini Price only

£2.50

ORDER NO. SX82



The Third and Fourth Hand...

... you always need

but have never got "until now". This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier
 Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
 Without magnifier ORDER NO. T400 **£4.75**



SX52 6 Black Heatsink will fit T0-3 and T0-220. Ready drilled. Half price value. **£1**

SX53 1 Power Finned Heatsink This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre drilled.
 10-3 Size 45mm squares 20mm high. 40p
 SX54 10-66 size 35mm x 30mm x 12mm. 35p
 SX55 1 Heat Efficiency Power Finned Heatsink 90mm x 80mm x 35mm High. Drilled to take up to 4 x T0-3 devices **£1.50** each

SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. ins.	Price
FB1	4	9 x 2 1/2"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD


FB4	2	14 x 4"	110	£2.00
-----	---	---------	-----	-------

SILICON POWER TRANSISTORS — T03

NPN like 2N3055 — but not full spec
 100 watts 50V min.
 10 for **£1.50** — Very Good Value
 100s of uses — no duds
 Order No. SX90


BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80
 1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit.
 1 Quality Desoldering pump. High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle.
 1.5 metres of 0e-soldering braid on plastic dispenser.
 2 yds (1.83m) Resin Cored Solder on Card.
 1 Heat Shunt tool tweezer Type.
 Total Retail Value over **£12.00**
 OUR SPECIAL KIT PRICE **£8.95**

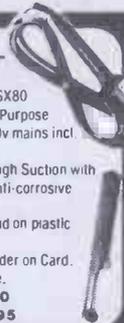

BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
 1 Expo Mini Drill 10,000RPM 12v Dc incl 3 collets & 1 x 1mm Twist bit
 1 Sheet PCB Transfers 210mm x 150mm.
 1 Etch Resist Pen.
 1 1/2 lb pack FERRIC CHLORIDE crystals
 3 sheets copper clad board.
 2 sheets Fibreglass copper clad board.
 Full instructions for making your own PCB boards.
 Retail Value over **£15.00**
 OUR BI-PAK SPECIAL KIT PRICE **£9.75**
 ORDER NO. SX81

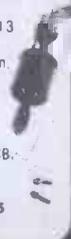

PROGRAMMABLE UNIJUNCTION TRANSISTOR "PUT" case T0106 plastic MEU22 Similar to 2N6027/6028 PNP Silicon
 Price: 1-9 10-49 50-99 100+
 Each: 20p 18p 15p 13p Normal Retail Price **£0.35** each

SX33A	6 small (min) (SDST/SPDT Toggle Switches 240v Samp	£1.00
SX35A	6 small (min) Rocker Switches 240v Samp	£1.00
SX32A	12 Assorted Jack & Phono plugs, sockets and adaptors, 2.5m, 3.5m and standard sizes	£1.00
SX71	50 BC108 "Fallouts" Manufacturers out of spec on volts or gain You test.	£1.00
SX72	A mixed bundle of Copper clad Board Fibre glass and paper. Single and double sided. A fantastic bargain	£1.00

5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification
 • Max Power Supply 30v • Power Output 5 watts RMS • Load Impedance 8-16 ohms • Frequency response 50Hz to 25KHz—3db • Sensitivity 70mv for full output • Input Impedance 50k ohms • Size 85 x 64 x 30mm • Total Harmonic distortion less than 5%
 BI-PAK'S give away price

£2.25


You could not build one for this price.



TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices in all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation — Beat the Budget — Down with Depression

Price —
JUST £6.50.

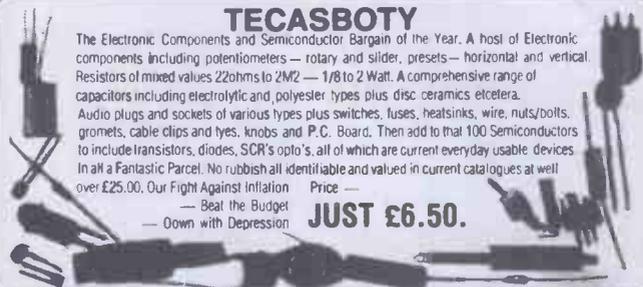

SX38 100 Silicon NPN Transistors—all perfect Coded mixed types with data and eqvt sheet. No rejects. Real value. **£3.00**
 SX39 100 Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt. sheet. No rejects. Fantastic value. **£3.00**

2N3055 The best known Power Transistors in the World — 2N3055 NPN 115w.
 Our BI-PAK Special Offer Price:
 10 off 50 off 100 off
£3.50 £16.00 £30.00

B0312 COMPLIMENTARY PNP POWER TRANSISTORS: TO 2N3055.
 Equivalent MJ2955 — B0312 — T03
 SPECIAL PRICE **£0.70** each
 10 off **£6.50**



MORE BARGAINS!

SX51	60 metres PVC covered Hook-up wire single and stranded. Mixed colours.	£1
SX58	25 Assorted TTL Gates 7400 Series. 7401-7460.	£1
SX59	20 Assorted Flip Flops and MSI TTL	£1
SX60	20 Assorted Slider Potentiometers	£1
SX62	40 Assorted Pre-Sets Hor/Vert etc.	£1
SX79	10 Reed Switches — glass type 3 Micro Switches — with lever	£1

BI-PAK

Send your orders to Dept ET1 10, BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST WARE HERTS
 TERMS CASH WITH ORDER SAME DAY DESPATCH ACCESS
 BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182, GPO 388 7006
 ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class.
 Remember, you must add VAT at 15% to your order. Total Postage add 75p per total order.

NOTES:

- (1) Including ferrites, RF chokes etc.
- (2) Discrete devices.
- (3) Other than optoelectronic.
- (4) Access and Barclaycard, where marked.
- (5) See company listing.
- (6) In pence unless otherwise noted.
N = NIL (no charge).

	RESISTORS	CAPACITORS	POTENTIOMETERS	TRANSFORMERS	INDUCTORS (1)	DIODES, SCRs TRIACS	TRANSISTORS (2)	LINEAR ICs	DIGITAL ICs	LINEAR MSI/LSI	DIGITAL MSI/LSI	OPTOELECTRONICS	VALVES	RELAYS	SWITCHES	FUSES AND PROTECTION	BATTERIES AND PSUs	ANALOGUE PANEL METERS	TRANSDUCERS (3)	PCB HARDWARE
NAMAL ASSOCIATES																				
PARNDON ELECTRONICS																				
P.A.T.H.																				
PC ELECTRONICS																				
PEATS ELECTRONICS																				
PM COMPONENTS																				
T. POWELL																				
RAPID ELECTRONICS																				
BRIAN J. REED																				
RELAY-A-QUIP																				
RISCOMP LIMITED																				
ROADRUNNER PRODUCTS																				
SAMSONS ELECTRONICS																				
SUMMIT ELECTRONICS																				
SWIFT-SASCO LTD																				
TECHNOMATIC																				
TENNCO EXIM																				
THAMES VALLEY																				
TITAN TRANSFORMERS																				
TK ELECTRONICS																				

PLUGS AND SOCKETS	ENCLOSURES, CASES	HEATSINKS	KNOBBS, MISC. HARDWARE	CABLE AND WIRE	BREADBOARDS	TOOLS	PCBs and/or MATERIALS	CHEMICALS	CUSTOM KITS, MODULES	SURPLUS SUPPLIES	BARGAIN PACKS	BOOKS	CATALOGUE/PRICE LIST	MAIL ORDER MINIMUM (6)	P&P (6)	OVERSEAS ORDERS	CREDIT CARDS (4)	SHOPS	OTHER
-------------------	-------------------	-----------	------------------------	----------------	-------------	-------	-----------------------	-----------	----------------------	------------------	---------------	-------	----------------------	------------------------	---------	-----------------	------------------	-------	-------

NOTES:
 (1) Including ferrites, RF chokes etc.
 (2) Discrete devices.
 (3) Other than optoelectronic.
 (4) Access and Barclaycard, where marked.
 (5) See company listing.
 (6) In pence unless otherwise noted.
 N = NIL (no charge).

													£10	£1		(5)			NAMAL ASSOCIATES
													£1	N					PARNDON ELECTRONICS
													N	80					P.A.T.H.
													£10	£1					PC ELECTRONICS
														50					PEATS ELECTRONICS
														N	50				PM COMPONENTS
													£1	50					T. POWELL
													1	(5)					RAPID ELECTRONICS
													(5)	(5)					BRIAN J. REED
													N	(5)					RELAY-A-QUIP
													N	50		(5)			RISCOMP LIMITED
													(5)	(5)		(5)			ROADRUNNER PRODUCTS
													£2						SAMSONS ELECTRONICS
													N	40					SUMMIT ELECTRONICS
													25	£2					SWIFT-SASCO LTD
													N	40					TECHNOMATIC
													£10	£1					TENNCÓ EXIM
													N	45					THAMES VALLEY
																			TITAN TRANSFORMERS
													N	55					TK ELECTRONICS

MIDWICH HAS MOVED. OUR PRICES HAVE TOO — DOWN!

In order to maintain our standard of service and house our ever growing range of stock, we've moved to larger premises. You can still use our old telephone number for a limited period, but please make a note of our new one and our address.

To celebrate the move we have reduced our prices still further. We know this will dispense our competitors, but we'd rather please our customers.
NB — NO SURCHARGE ON CREDIT CARD ORDERS.

Be happy — move with Midwich. And remember, we always try to give you the best deal and the best service. If we fail just let us know — we will always try to make amends.

MEMORIES ** NEW LOWER PRICES **

*2114 Low Power 200ns	0.80	*2732 350ns	4.40	*4164 200ns (TI)	4.65
*2716 450ns (5V)	2.10	*2532 450ns	3.60	*4816/4516 100ns	3.25
*2716 350ns (5V)	3.50	*4116 200ns	0.70	*5516 200ns	9.38
*2716 450ns (3 rail)	5.95	*4116 150ns	1.10	*6116P3 150ns	4.30
*2732 450ns	3.90	*4118 150ns	3.38	*6116LP3 150ns	5.75

BBC MICRO UPGRADE KITS ** NEW LOWER PRICES **

BBC1 4516/4816 X 8 100ns	25.50	BBC21 Printer cable complete	13.00
BBC2 Printer/User I/O kit (IC69.70 + PL9,10)	8.00	BBC22 Connector for user port with	2.00
BBC4 Analogue input kit (IC73.77 + SK6)	6.70	BBC44 "36" cable	
BBC5 Serial I/O and RGB kit (IC74.75 + SK3.4)	11.45	BBC55 Analogue input plug with cover	2.25
BBC6 Expansion bus and tube kit (IC71, 72, 76 + PL11, 12)	8.25	BBC66 Connector for bus port with cable	3.50


MOST KITS ARE NOW EX-STOCK!

*** We've done it again! Massive price reductions on LPS and CMOS ****

Device	Price	Device	Price	Device	Price	Device	Price
*280 FAMILY		*WD1391 KIT 45.50	45.50	CRYSTALS		09	0.11
*280CPU	3.15	*WD1393 KIT 45.50	45.50	1MHz	2.90	10	0.11
*280CPU	3.50	*WD1395 KIT 45.50	45.50	1.008MHz	2.90	12	0.11
*280CTC	2.75	*WD1397 KIT 45.50	45.50	1.8432MHz	2.20	13	0.15
*280ACT	2.95	(KITS INCLUDE		3.6864MHz	2.95	14	0.33
*280DART	5.70	FD179X + WD2143		4MHz	1.45	15	0.12
*280ADMA	11.95	+ WD1691)		6MHz	1.75	20	0.12
*280PIO	2.75			8MHz	1.70	21	0.12
*280PIO	2.95					26	0.12
*280ASIO-0	11.99					27	0.12
*280ASIO-1	11.99					28	0.12
*280ASIO-2	11.99					30	0.12
*MK3886	11.00					32	0.12
*MK3886-4	14.47					37	0.12
						38	0.12
						40	0.12
						42	0.27
						47	0.34
						51	0.14
						54	0.14
						75	0.19
						77	0.16
						9	0.14
						13	0.15
						16	0.15
						18	0.15
						22	0.15
						24	0.15
						28	0.25
						29	0.27
						31	0.31
						32	0.31
						37	0.35
						38	0.35
						40	0.35
						41	0.35
						42	0.35
						47	0.34
						51	0.14
						54	0.14
						75	0.19
						77	0.16
						9	0.14
						13	0.15
						16	0.15
						18	0.15
						22	0.15
						24	0.15
						28	0.25
						29	0.27
						31	0.31
						32	0.31
						37	0.35
						38	0.35
						40	0.35
						41	0.35
						42	0.35
						47	0.34
						51	0.14
						54	0.14
						75	0.19
						77	0.16
						9	0.14
						13	0.15
						16	0.15
						18	0.15
						22	0.15
						24	0.15
						28	0.25
						29	0.27
						31	0.31
						32	0.31
						37	0.35
						38	0.35
						40	0.35
						41	0.35
						42	0.35
						47	0.34
						51	0.14
						54	0.14
						75	0.19
						77	0.16
						9	0.14
						13	0.15
						16	0.15
						18	0.15
						22	0.15
						24	0.15
						28	0.25
						29	0.27
						31	0.31
						32	0.31
						37	0.35
						38	0.35
						40	0.35
						41	0.35
						42	0.35
						47	0.34
						51	0.14
						54	0.14
						75	0.19
						77	0.16
						9	0.14
						13	0.15
						16	0.15
						18	0.15
						22	0.15
						24	0.15
						28	0.25
						29	0.27
						31	0.31
						32	0.31
						37	0.35
						38	0.35
						40	0.35
						41	0.35
						42	0.35
						47	0.34
						51	0.14
						54	0.14
						75	0.19
						77	0.16
						9	0.14
						13	0.15
						16	0.15
						18	0.15
						22	0.15
						24	0.15
						28	0.25
						29	0.27
						31	0.31
						32	0.31
						37	

SEIKOSHA GP-100A GRAPHIC PRINTER

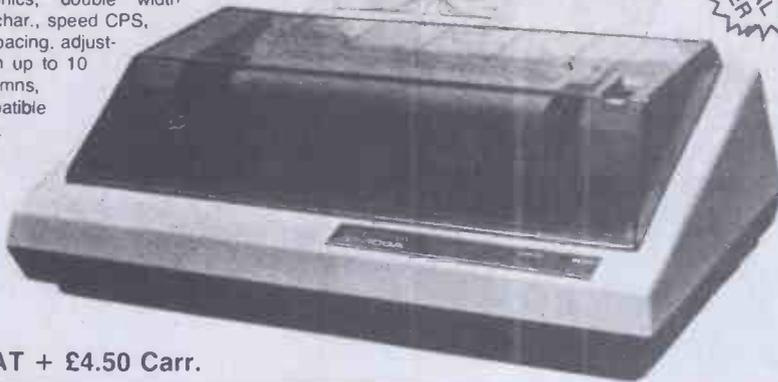
Features: Graphics, double width char., standard char., speed CPS, selectable line spacing, adjustable paper width up to 10 inches, 80 columns, centronics compatible parallel interface. 90 day warranty.



SPECIAL OFFER

Price
£179 + VAT + £4.50 Carr.

OK1 MICROLINE PRINTERS

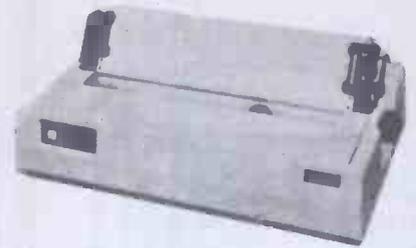

90 day warranty on all Microline printers (OK1)

MICROLINE 80

Features: 80 columns, 80 CPS, friction and pin feed, Unidirectional block graphics, Centronics parallel interface.
PRICE £249 + VAT + £4.50 Carr.

MICROLINE 82A

Features: 80 columns, 80 CPS, friction and pinfeed, bi-directional printing, parallel and serial (1200 bauds) interface.
PRICE £379 + VAT + £4.50 Carr.

MICROLINE 83A

Details as 82A but 120 CPS and includes tractor up to 15 inches width.
PRICE £569 + VAT + £4.50 Carr.

NEW EPSON TYPE 3 PRINTERS



MX80T-3

Features: 80 columns, 80 CPS, Bit image printing, super and sub scripts, Auto-underlining, tractor feed, 32 print fonts, Bi-directional, logic seeking, 9x9 matrix, centronics parallel interface.
PRICE £319 + VAT + £4.50 Carr.

MX80 F/T-3

Features: As above but with tractor or friction paper feed.
PRICE £325 + VAT + £4.50 Carr.

MX100-3

Features: 136 columns, 100 CPS, Auto-underlining, 32 print fonts, friction or tractor paper feed, Bi-directional logic seeking, true decenders, adjustable paper width up to 15 inches, Centronics parallel interface.
PRICE £429 + VAT + £4.50 Carr.


MX82

Features: 80 CPS, plotter print, bit image printing, bi-directional printing with logic seeking.
PRICE £329 + VAT + £4.50 Carr.

MX82 F/T

PRICE £339 + VAT + £4.50 Carr.

GREEN MONITORS

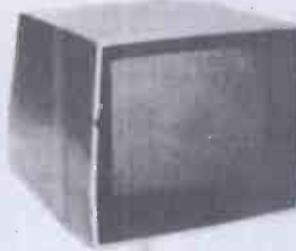


SANYO PROFESSIONAL MONITOR

SM12H — Green/black 12 inches screen, 18 MHz bandwidth, removable antiglare filter, ideal for high res graphics, attractive beige case — illustrated above.
1 year warranty (SANYO)
PRICE £89 + VAT + £4.50 Carr.

BMC 12A GREEN MONITOR

12 inch green/black screen, 80 x 24 char. format, composit video input. 15 MHz bandwidth.
1 year warranty (BMC)
PRICE £69 + VAT + £4.50 Carr.

COLOUR MONITOR

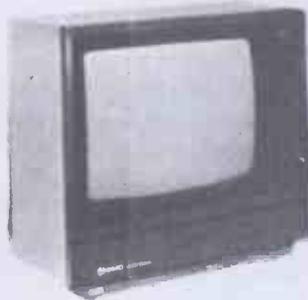

BM1401 RGB COLOUR

Medium resolution RGB colour monitor, 15 MHz.
400 dots (at the centre)
40 x 25 characters, 5 x 7 dot format.
1 year warranty (BMC)
PRICE £219 + VAT + £4.50 Carr.

TOSHIBA DOUBLE SIDED/DOUBLE DENSITY 5 1/4" DISK DRIVES FOR THE PRICE OF A SINGLE SIDED/SINGLE DENSITY.



Industry standard interface, compatible with VIDEO GENIE, ATOM, TRS80, BBC COMPUTER, SUPER BRAIN, NASCOM, and lots of others. 3.5 MEGABITS. Unformatted storage capacity, track density 48 TPI. Daisy chain up to 4 drives.

90 day warranty.

DISK DRIVE ND-02D

£169 + VAT + £2.50 Carr.
SINGLE BOXED WITH POWER SUPPLY
£199 + VAT + £4.50 Carr.
DUAL BOXED WITH POWER SUPPLY
£369 + VAT + £4.50 Carr.
2 DRIVE CABLE
£15 + VAT + £1 Carr.

DOUBLE SIDED/DOUBLE DENSITY DISKETTES

1 - 9 **£2.75 + VAT + 50p Carr.**
10-49 **£2.50 + VAT + £1 Carr.**

CASIO AX-210/AX-250 ANALOG AND DIGITAL WATCHES



Dual time, 12 or 24 hour option, countdown timer with memory function, chronograph with lap time, optional hourly time signal, daily alarm, 3 optional melodies or ordinary bleeper. Calendar display, lithium battery. Stainless steel br.

THE BEST SELLING WATCH

AX-210 or AX-250 **£21 + VAT + 50p Carr.**


WATER RESISTANT ALARM/CHRONO

W20 Black resin case **£10 + VAT + 50p Carr.**
W30 Metal case **£16 + VAT + 50p Carr.**

SILENT ALARM/POCKET PAGER

This is an individually coded 4 WATTS Radio transmitter and pocket pager receiver. The alarm system has connections for door contacts and vibration sensors. 2 vibration sensors are included. It has a range of 2 miles. Ideal for protection of vehicle or property. Power requirements for transmitter is 12V dc. Not licensible in UK.

PRICE £78 + VAT + £2.95 Carr.

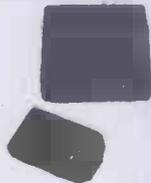

RECHARGEABLE BATTERIES

CODE	TYPE	CAPACITY	PRICE
S401	AAA	200 mA	£1.10
S101	AA	500 mA	£0.75
C1200	C	1200 mA	£1.90
D1200	D	1200 mA	£2.05
RX22	PP3	110 mA	£3.50
BC2204	Universal Charger for AA, C, D & PP3		£9.50

Please add VAT to all above prices plus 75p Carr per order

6809 BASE MICRO COMPUTER

COMPLETE WITH 32K RAM

Extended micro soft, colour Basic parallel printer Interface. High resolution colour graphics (256 x 192) UHF or colour monitors, cassette recorder interface and mains adapter included.

£169 + VAT + postage £4.50



AKHTER INSTRUMENTS LTD,
DEPT HE
UNIT 19, ARLINGHYDE ESTATE,
SOUTH ROAD, HARLOW, ESSEX. UK.
TEL: HARLOW (0279) 412639.

ORDERING INFORMATION:

Please add 15% VAT to all prices. All orders which accompany a cheque or cash are carriage free. Please add carriage for all other orders as specified on each item.

WE ACCEPT BARCLAYCARD AND ACCESS

NOTES:

- (1) Including ferrites, RF chokes etc.
- (2) Discrete devices.
- (3) Other than optoelectronic.
- (4) Access and Barclaycard, where marked.
- (5) See company listing.
- (6) In pence unless otherwise noted.
N = NIL (no charge).

	RESISTORS	CAPACITORS	POTENTIOMETERS	TRANSFORMERS	INDUCTORS	DIODES, SCRs TRIACS	TRANSISTORS (2)	LINEAR ICs	DIGITAL ICs	LINEAR MSI/LSI	DIGITAL MSI/LSI	OPTOELECTRONICS	VALVES	RELAYS	SWITCHES	FUSES AND PROTECTION	BATTERIES AND PSUs	ANALOGUE PANEL METERS	TRANSDUCERS (3)	PCB HARDWARE	
A.C. TOWNLEY																					
WATFORD ELECTRONICS																					
WILMSLOW AUDIO																					

DIRECTORY OF ELECTRONIC

Listing over 80 companies supplying electronic components

If the name of your favourite component supplier does not appear in these pages, please write and tell us about him.

Aitken Bros. and Co.,

35 High Bridge, Newcastle on Tyne, NE1 1EW. Tel. 0632 326729
Aitken Bros. can also supply schools, colleges and other companies, and can quote special prices for larger quantities. They also sell a good range of test equipment: analogue and digital multimeters, frequency meters, function generators, pulse generators, signal generators and oscilloscopes. Their shop is in Newcastle upon Tyne, at the above address. Post and packaging charges are 75p for orders under £10.

ACE Mailtronix Ltd.

3A, Commercial Street, Batley, West Yorks WF17 5HJ. Tel: 0924 441129. ACE mention that they specialise in resistors, transformers, transistors, linear and digital ICs, optoelectronic devices and tools. "In addition, we specialise in 'hard to get' items. Enquiries for quotation should include an SAE".
Other items of electronic equipment include home computer monitors, PCB drafting aids (a speciality), data entry keyboards and switches, and loudspeakers. Post and packaging charges are 30p for orders under £3.

Akhter Instruments Ltd.,

Unit 19, Arlinghyde Industrial Estate, South Road, Harlow Essex. Tel. 0279 412639.
Microcomputer peripherals (floppy disc drives, monitors, printers etc.) are also carried. P&P is charged by weight.

Altek Microcomponents Ltd.,

22, Market Place, Wokingham, Berks RG11 1AP. Tel. 0734 791579.
Distributors for Mitsubishi and Sharp LSI products. Post and packaging is charged pro-rata.
Amaral Limited,
26, Highfields, Earley, Reading, Berks. Tel. 0734 864745.
P&P 50p minimum.

Ambit International,

200, North Service Road, Brentwood, Essex CM14 4SG. Tel. 0277 230909.
Specialists in inductors, ferrites etc, but, "it's all a bargain at Ambit". See for yourself at their Brentwood headquarters or at the franchised shop in Acton.

Aries Electronics Ltd,

159 Boyn Valley Road, Maidenhead, Berks SL6 4DT. Tel. 0628 37431.
"Specialists in optoelectronic devices and power diodes".

AWP Electronics Ltd.,

Dalma House, Kings Mill Lane, South Nutfield, Redhill, Surrey RH1 5ND. Tel. 073 782 3421.
AWP are specialists in coaxial and multiway plugs and sockets, ribbon and coaxial cables, crimp tools and custom made patch panels and cable assemblies.
"Whilst the majority of our business is applicable to industry, we find that the growth of electronics generally has created a need for assisting any customer, however large or small."

AWP's head office is in Surrey and they have further premises at Alva, in Scotland.

Bamber Electronics,

5, Station Road, Littleport, Cambs CB6 1QE. Tel. 0353 860185.
Specialists in surplus equipment and components, particularly for radio telephones and test equipment.

Barrie Electronics,

3, The Minorities, London EC3. Tel. 01 488 3316.
Specialists in transformers; p&p charges are at cost.

Benning Cross Electronics,

67, Vicarage Road, Watford, Herts. Tel. 0923 36234.
"All brand new, full-spec components, manufacturer guaranteed". Other items stocked include test equipment, hand-held CB gear, headphones, aeriels and audio tapes.

BICC-VERO Electronics Ltd.,

The Retail Department, School Close, Industrial Estate, Chandlers Ford, Hants SO5 3ZR. Tel. 04215 62829.
"The professional company with the personal touch!"
Vero are well known for their breadboarding systems, eg Verobloc and Veroboard, and their range of enclosures and cases.
Vero products are available world-wide from retail stockists and mail-order companies.

BI-PAK,

3, Baldock Street, Ware, Herts. Tel. 0920 3182.

PLUGS AND SOCKETS	ENCLOSURES, CASES	HEATSINKS	KNOBS, MISC. HARDWARE	CABLE AND WIRE	BREADBOARDS	TOOLS	PCBs and/or MATERIALS	CHEMICALS	CUSTOM KITS, MODULES	SURPLUS SUPPLIES	BARGAIN PACKS	BOOKS	CATALOGUE/PRICE LIST	MAIL ORDER MINIMUM (6)	P&P (6)	OVERSEAS ORDERS	CREDIT CARDS (4)	SHOPS	OTHER
													£5 (5)						A.C. TOWNLEY
													N	50					WATFORD ELECTRONICS
													N	(5)	(5)				WILMSLOW AUDIO

NOTES:
 (1) Including ferrites, RF chokes etc.
 (2) Discrete devices.
 (3) Other than optoelectronic.
 (4) Access and Barclaycard, where marked.
 (5) See company listing.
 (6) In pence unless otherwise noted.
 N = NIL (no charge).

COMPONENT AND HARDWARE SUPPLIERS

and hardware to the electronic enthusiast.

RETAILERS! If your company is not included, please write and tell us about yourself, in time for the next edition of this Directory.

"BI-PAK have now been serving the public for 18 years, and the range of products over the years have ever increased — and continues to do so". From their shop in Ware, BI-PAK also supply CB accessories, radio aerials, leads, styli and cartridges, cassettes and hifi accessories, headphones and multimeters. They are a specialist supplier of many components (see main listings).

B.K. Electronics,
 Electronic Components and Equipments,
 37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY. Tel. 0702 527272.

"B.K. Electronics specialise in:

1. Loudspeakers and tweeters from 3" to 15", up to 150 watts RMS, with some speaker cabinet designs available in kit form; power amplifiers up to 300 watts RMS.

2. Test equipment, ie oscilloscopes, signal generators, pulse generators, frequency meters, digital and analog multimeters, digital thermometers etc." Turntables and cassette decks, in chassis form, are also stocked at their shop in Southend, Essex. Post and packaging charges for mail order transactions range from 50p to £3.

Boss Industrial Mouldings Ltd.,
 (David George Sales Ltd.), James Carter Road, Mildenhall, Suffolk. Tel. 0638 716101.

"We service the electronics industry mainly through a network of distributors, but we are also happy to accommodate the hobbyist".

B.I.M also carry a very large range of filament and neon indicators.

S & R Brewster,
 86-88 Union Street, Plymouth, Devon. Tel. 0752 665011.

"We are soldering specialists, manufacturing our own range, and we can offer advice on any soldering problems. We are also the main specialist retailer of electronic components in the locality".

All components in the RS catalogue can be despatched by S & R Brewster within 48 hours of ordering; there is a 15% handling charge on this service. Normal P&P is charged at cost.

Bytech Ltd,
 57, Suttons Industrial Park, Reading, Berks. Tel 0734 61031.

Bytech are franchised distributors of Fairchild components, Intel systems, single-board computers and components, Hitachi colour monitors and DEC, QUME and Centronics printers.

Chiltmead Ltd.,
 Norwood Road, Reading, Berks. Tel. 0734 669656.

Specialists in surplus electronic equipment and components.

Chordgate Ltd.,
 75, Farringdon Road, Swindon, Wilts. Tel. 0793 33877.

Their retail shops in Swindon and Deptford (London) carry a changing stock of new and surplus material. Mail order charges are dependent on the weight of the package, and Chordgate welcome official orders from schools, colleges etc.

Clef Electronic Music,
 44A, Bramhall Lane South, Bramhall, Stockport, Cheshire SK7 1AH. Tel. 061 439 3297.

"Although we started out as custom kit suppliers, most of our products are now available as manufactured goods, too".

Collective Components,
 Churchfield House, Churchfield Road, Chalfont St. Peter, Bucks. Tel 02813 89191.

Collective Components supply by mail order only; p&p charges are 25p for orders under £10.

Cricklewood Electronics,
 40, Cricklewood Broadway, London NW2 3ET. Tel. 01 452 0161.

"Formerly a branch of A. Marshall (London) Ltd., we stock one of the widest ranges of components in the country".

A range of test equipment is also carried and American Express cards are accepted.

Crimson Components Ltd.,
 66, J.F. Kennedy Estate, Washington, Tyne & Wear NE38 7AJ. Tel. 0632 467814.

"Our main role is that of an importer from France, Germany, Italy, Japan, Taiwan and the USA. Stocks include well over a million capacitors in 1500 values/types and just under half a million transistors in 2500 types".

A range of ferrites are stocked, and NiCad batteries with chargers capable of taking sizes between D and AA. Post and packaging charges are 20p for within the UK and 90p for overseas

MICRO TIMES

19 Mill St. Bideford, North Devon EX39 2JR, England
Telephone Bideford (023 72) 79798 or 5481

VAT No 321 1198 01

(10-12am)

CMOS

4001	12p
4002	12p
4006	50p
4007	15p
4008	38p
4010	30p
4011	13p
4012	15p
4013	23p
4014	47p
4015	44p
4016	20p
4017	35p
4018	48p
4019	30p
4020	48p
4023	15p
4024	32p
4028	15p
4026	1.10p
4027	22p
4028	45p
4029	50p
4030	40p
4031	£1.25
4040	48p
4042	43p
4044	43p
4046	48p
4047	47p
4048	47p
4049	25p
4050	25p
4051	45p
4052	45p
4056	30p
4060	55p
4063	98p
4066	30p
4068	15p
4069	15p
4070	15p
4071	14p
4075	14p
4077	15p
4078	16p
4081	14p
4093	28p
4503	39p
4510	50p
4511	48p
4518	48p
4820	65p
4560	£1.65p
4572	30p

74LS

74LS00	14p
74LS01	14p
74LS02	14p
74LS03	14p
74LS04	14p
74LS08	13p
74LS10	13p
74LS14	34p
74LS20	13p
74LS26	14p
74LS30	14p
74LS10	13p
74LS14	34p
74LS20	13p
74LS26	14p
74LS30	14p
74LS32	14p
74LS38	14p
74LS42	30p
74LS47	36p
74LS73	16p
74LS74	24p
74LS90	22p
74LS93	27p
74LS107	40p
74LS122	26p
74LS123	42p
74LS125	24p
74LS132	40p
74LS138	35p
74LS151	40p
74LS155	32p
74LS157	30p
74LS161	37p
74LS163	37p
74LS164	42p
74LS173	60p
74LS174	50p
74LS175	44p
74LS221	55p
74LS244	65p
74LS245	30p
74LS251	90p
74LS255	35p
74LS261	£1.38
74LS366	28p
74LS373	65p
74LS374	70p
74LS393	45p

TILs

TIL32	50p
TIL209	11p
TIL212	16p
TIL216	18p
TIL220	12p
TIL224	18p
TIL228	20p
TIL232	18p
TIL311	£5.50
TIL312/3	£1.00
TIL321/A	£1.15
TIL330A	£1.15

CPU's

6502	£4.50
6504	£6.20
6802	£5.70
6809	£9.50
8080A	£3.50
8085A	£4.66
Z80	£4.00
Z80A	£4.80

SUPPORTS

6520	£3.10
6522	£5.00
6532	£7.70
6810	£1.35
6821	£1.70
6845	£7.50
6850	£1.70
6852	£3.00
8212	£1.50
8216	£1.50
8228	£3.00
8255	£3.60
Z80CTC	£4.00
Z80PIO	£4.00
Z80ACTC	£4.00
Z80APIO	£4.50
Z80DMA	£11.50
Z80ADMA	£12.00
Z80SIO/0	£12.00
Z80SIO/1	£12.00
Z80SIO/1	£12.00
Z80SIO/2	£12.00
Z80SIO/2	£12.00

THYRISTORS

C106D	35p
-------	-----

Z80 COMBO CHIP

MK3886. 2 meg. £15.50

AY3-8910 G.I. SOUND COMPUTER CHIP

£5.95 incl. data.

MEMORIES

2114. 300ns.	£1.20
2114. 450ns.	£1.00
4116. 150ns.	£1.25
4116. 200ns.	£1.00

4164	P.O.A.
HM6116-3 (2k x 8)	£4.50

EPROMS

2708 450ns.	£2.30
2716 5v.	£2.45
2732 Intel	£4.00

2532	P.O.A.
MCM5101	£3.00

VOLT. REGS.

7805 5v.	39p
7812 12v.	39p
7905 5v.	50p
-7912 12v.	50p

78L05 5v.	29p
78L12 12v.	29p

79M05 5v.	50p
79M12 12v.	50p
UA723	31p

ICL 7660	£2.25
----------	-------

FLOPPY DISC CONTROLLERS

FD1771B-01	£17.95
FD1791-2	£32.00
WD1691D	£11.70
WD2143-01	£5.50
FD1793	P.O.A.
FD1795	P.O.A.
FD1797	P.O.A.

LOW PROFILE DIL SOCKETS

8 pin	8p
14 pin	10p
16 pin	11p
18 pin	15p
22 pin	20p
24 pin	23p
28 pin	26p
40 pin	29p

SN76477N SOUND GENERATOR CHIP.

DATA AVAILABLE 75p

LINEAR

NE555	16p
NE556	45p
RC4136	85p
HM301A	25p
LM311P	60p
LM318	£1.50
LM324N	40p
LM339N	50p
LM348N	64p
LM358P	60p
LM380	85p
LM3302	85p
LM3900N	£2.00
LM3915	£2.00
LM13600	£1.20
LM1871	£3.50
LM1872	£3.50
SN76477N	£4.45
UA709	30p
UA733	68p
UA741	16p
UA747	68p
UA748	30p
TLO74CN	£1.00
TLO81CP	38p
TLO82CP	55p
TLO84CN	90p
TL490	£1.00
MCI488	59p
MCI489	59p
8T26	£1.20
8T28	£1.20
8T95	£1.00

KITS FOR BEGINNERS:

Electronic Wheel of Fortune	£5.50
Ultronic Fly Repeller	£5.00
Light Activated Switch	£4.25

ANTEX SOLDERING IRONS

Model CX17W	£5.30
Kit SK1.15W	£7.00
Incl. Base Stand Solder.	
Kit SK3.17W	£6.90
Kit SK4.25W	£6.90
Kit MLX Repair Spare bits	£5.50
	each £0.70p

ELECTROWARE

We are distributors for all Electroware Products. Tools, kits, boards etc. Catalogue available. Send 35p. for P.&P.

LOW NOISE EQUALIZER MODULE KIT

Board Size: 1.3" x 1.1" Treble & Bass. ±15dB @ 10kHz & 50Hz. Kit: £5.95. Assem. & Tested £5.50

VERO PRODUCTS

VEROBLOC	£4.00
APPLE PROTOTYPING BOARD IIT 2020 S100 MICROBOARD	£9.50
Pattern 06-2175L S100 S.C. PAD.	£18.03
Universal Pattern	

Spot Pen: £3.56
Wiring Face Cutter £1.30
Pin Insertion Tool. 0.1" £1.78
Pin Insertion Tool. 0.15" £1.78

SUPER STEREO DRUM KIT

• 6 Rhythms, each with 3 Sub-rhythm options.
• 5 Instruments: Snare, Hi-Mat, Tom-Tom, Cymbal and Bass Drum.
• Board 4" x 5" packed with components.
• Kit includes: Rhythm selection switch and Tempo control.
PRICE: Kit £25.95. Ass. & Tested £32.60. (excl. case)

6809 SINGLE BOARD COMPUTER IEEE S-100 STANDARD.

Uses Motorola's powerful MC6809 CPU. 4K/8K/16K ROM/2K RAM. ACIA, PIA, 8080 simulated I/O RS-232 Handshake. 8 sel. Baud Rates. BARE BOARD: £56.00
COMPLETE KIT: £205.00
ASS. & TESTED: £260.00
ADSMON (2716): £38.00
ADSBASIC (2716): £49.50
& MANUAL

MB-3. /3 SLOT MOTHERBOARD £35.00

PROMBLASTER (S-100)

Programming most families of Eproms. The ADS Promblaster is controlled by software running under either CP/M or stand alone with our 6809 S.B.C.I
BARE CARD WITH SOFTWARE: £98.00
CP/M Version on 5 1/4" or 8" disk. £98.00
PROMWRITER '09 in 2716. Please state clearly version required.
COMPLETE KIT: £195.00
'09 VERSION £190.00

ASSEMBLED & TESTED: £255.00
09 VERSION £250.00

KLUGE CARD (S-100)

Simplify your projects with a prototype Breadboard with extras. BARE BOARD & MANUAL £38.00

SYNTHETALKER

A speech synthesis board using the Voxra SC-01 speech synthesis chip. COMPLETE KIT: £220.00
ASSEMBLED & TESTED: £255.00

FOR ALL ADS. PRODUCTS PLEASE ALLOW 21 DAYS DELIVERY.
FOR KITS ADD £2.00. P.&P. PLUS 15% V.A.T.
DATA AVAILABLE S.A.E. PLEASE.

Ordering Information: Please add 60p. P. & P. plus 15% V.A.T. EXPORT ORDERS ACCEPTED. Add 15% P.&P. on total order. V.A.T. not applicable. ACCESS/BARCLAYCARD ORDERS WELCOME

Schools, Universities, Official Orders Welcome.

All products are brand new, full spec. devices. Prices subject to change without notice.

METERS

Large range of types in stock; also probes, leads, accessories, etc.
PANEL MOUNTING in 50, 100, 500µA; 1, 5, 10, 50, 100 500mA; 1A either model.



MULTIMETERS

MH55A	YIN 360TR	OMM DD601
N E V -	2.0 K Ω / V	LCD 3 1/2 digit (1999)
ZKX1V -	A/C/D C/R /	Push button
A/C/D C /	dB/Transistor Test:	26 ranges
RES/dB	in 2 1	170 x 80 mm
1 2 3	145 x 35 mm	38mm
ranges:	45mm	£32.00N
130 x 85 x		
37mm		
£11.20N		

SOLDERING IRONS

Also large stocks of bits, desoldering devices, accessories, etc.
ANTEX C-240V £4.60N; X25-240V £5.30N; CSBP £5.45N; XSBP £5.55N; ST4 Stand £1.70N
ORYSK 50 watt temp. controlled £13.75N; Stand £4.00N.
SOLDER 500cm/18SWG £7.60N; Desolder braid 1.5m 54p.

SWITCHES

Wavechange
Type CK - 1P/12 way; 2P/6W; 3P/4W; 4P/3W 48p.
MIN. TOGGLES - S7101, SPDT 57p; S7201 DPDT 80p; S7301 3PDT £1.64; S7401 4PDT £2.75; Z211 1P3W £1.40; Centre of S7103 SPDT 71p; S7203 DPDT 96p.
Push button min 9531 make/9533 break 62p; 8225 DPDT £1.34 - DUAL IN LINE EGR colour coded 0.3" x 0.1" format. On/Off single throw 2P SDS2 54p; 4P SDS4 95p; 6P SDS6 £1.36; 8P SDS8 £1.87; 10P SDS0 £2.10.
LOW COST D-I-L 4P DNS04 60p; 8P DNS08 £1.

PROFESSIONAL KEYBOARD FOR USE WITH ZX81 £31.30N
Keyboard Case £13.46N

NICAD CHARGERS

For PP3 - NC75S £4.95N; for AA, C or D - NC1230 £8.20N; Power Units MW88 3/4.5/6/7.5/9/12V; 13A fitting 300mA out £3.45; HC244R DC Stabilised 3/6/7.5/9V 400mA out £6.25.

BOXES

L	W	D	ABS	PLAIN	STOVE GR		
50	50	25	-	5001P	85p		
100	80	25	2002	67p	5002P	67p	
113	63	31	2003	200p	5003P	130p	
121	66	40	2004	106p	5004P	150p	
152	82	50	2005	123p	5005P	195p	
192	113	61	2006	215p	5006P	365p	
						5006	322p

VERO RANGE plastic boxes	G RANGE professional Instrument Cases								
L	W	O	L	W	O				
72	47	25	21024	50p	134	30	44	21089	£7.28N
120	50	35	21390	75p	224	140	64	21090	£11.28N
180	110	55	21391	145p	302	170	84	21091	£14.56N

ELECTROVALUE

FOR SERVICE YOU CAN TRUST

VEROBOX CASES

ABS, lt. grey top; dk. grey bottom + 2 aii. panels				
L	D	H	TYPE	PRICE
205	140	40	21034	£4.52
205	140	75	21035	£5.02
205	140	110	21036	£6.54
180	120	39	21037	£4.11
180	120	65	21038	£4.40
180	120	90	21039	£4.89
155	85	39	21040	£3.31
155	85	60	21041	£3.61
155	85	80	21042	£4.30
125	65	30	21047	£2.22
125	65	39	21048	£2.82
125	65	50	21049	£3.18

ALL ITEMS BRAND NEW AND GUARANTEED TO SPEC.

CAPACITORS

POLYSTYRENE, SIEMENS 5% Tolerance. 160V
5, 7, 10, 12, 15, 18, 22, 27, 33, 39pF

TOROIDALS



The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within **7 DAYS** together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
30 VA 70 x 30mm 0.45 Kg Regulation 18%	1a010	6+6	2.50	£5.12 + p/p £1.04 + VAT £0.92 TOTAL £7.08
	1a011	9+9	1.66	
	1a012	12+12	1.25	
	1a013	15+15	1.00	
	1a014	18+18	0.83	
	1a015	22+22	0.68	
	1a016	25+25	0.60	
1a017	30+30	0.50		
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2a010	6+6	4.16	£5.70 + p/p £1.30 + VAT £1.05 TOTAL £8.05
	2a011	9+9	2.77	
	2a012	12+12	2.08	
	2a013	15+15	1.66	
	2a014	18+18	1.38	
	2a015	22+22	1.13	
	2a016	25+25	1.00	
2a017	30+30	0.83		
2a028	110	0.45		
2a029	220	0.22		
2a030	240	0.20		
80 VA 90 x 30mm 1 Kg Regulation 12%	3a010	6+6	6.64	£6.08 + p/p £1.67 + VAT £1.16 TOTAL £8.91
	3a011	9+9	4.44	
	3a012	12+12	3.33	
	3a013	15+15	2.66	
	3a014	18+18	2.22	
	3a015	22+22	1.81	
	3a016	25+25	1.60	
3a017	30+30	1.33		
3a028	110	0.72		
3a029	220	0.36		
3a030	240	0.33		
120 VA 90 x 40mm 1.2 Kg Regulation 11%	4a010	6+6	10.00	£6.90 + p/p £1.57 + VAT £1.29 TOTAL £9.86
	4a011	9+9	6.66	
	4a012	12+12	5.00	
	4a013	15+15	4.00	
	4a014	18+18	3.33	
	4a015	22+22	2.72	
	4a016	25+25	2.40	
4a017	30+30	2.00		
4a018	35+35	1.71		
4a028	110	1.09		
4a029	220	0.54		
4a030	240	0.50		
160 VA 10 x 40mm 1.8 Kg Regulation 8%	5a011	9+9	8.89	£7.91 + p/p £1.67 + VAT £1.64 TOTAL £11.02
	5a012	12+12	6.66	
	5a013	15+15	5.33	
	5a014	18+18	4.44	
	5a015	22+22	3.63	
	5a016	25+25	3.20	
	5a017	30+30	2.66	
5a018	35+35	2.28		
5a028	40+40	2.00		
5a029	110	1.45		
5a029	220	0.72		
5a030	240	0.66		

- ★ 294 TYPES TO CHOOSE FROM!
- ★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
- ★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
225 VA 110 x 45mm 2.2 Kg Regulation 7%	6a012	12+12	9.38	£9.20 + p/p £2.00 + VAT £1.68 TOTAL £12.88
	6a013	15+15	7.50	
	6a014	18+18	6.25	
	6a015	22+22	5.11	
	6a016	25+25	4.50	
	6a017	30+30	3.75	
	6a018	35+35	3.21	
6a026	40+40	2.81		
6a025	45+45	2.50		
6a033	50+50	2.25		
6a028	110	2.04		
6a029	220	1.02		
6a030	240	0.93		
300 VA 110 x 50mm 2.6 Kg Regulation 6%	7a013	15+15	10.00	£10.17 + p/p £2.00 + VAT £1.83 TOTAL £14.00
	7a014	18+18	8.33	
	7a015	22+22	6.82	
	7a016	25+25	6.00	
	7a017	30+30	5.00	
	7a018	35+35	4.29	
	7a026	40+40	3.75	
7a025	45+45	3.33		
7a033	50+50	3.00		
7a028	110	2.72		
7a029	220	1.36		
7a030	240	1.25		
500 VA 140 x 60mm 4 Kg Regulation 4%	8a016	25+25	10.00	£13.53 + p/p £2.35 + VAT £2.38 TOTAL £18.76
	8a017	30+30	8.33	
	8a018	35+35	7.14	
	8a026	40+40	6.25	
	8a025	45+45	5.55	
	8a033	50+50	5.00	
	8a042	55+55	4.54	
8a028	110	4.54		
8a029	220	2.27		
8a030	240	2.08		
625 VA 140 x 75mm 5 Kg Regulation 4%	9a017	30+30	10.41	£16.13 + p/p £2.50 + VAT £2.79 TOTAL £21.42
	9a018	35+35	8.92	
	9a026	40+40	7.81	
	9a025	45+45	6.94	
	9a033	50+50	6.25	
	9a042	55+55	5.68	
	9a028	110	5.68	
9a029	220	2.84		
9a030	240	2.60		

IMPORTANT: Regulation—All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalue, Maplin and Technomatic.

Please send _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd, Freepost 6 Graham Bell House, Roper Close,
Canterbury CT2 7EP, Kent, England.
Telephone Sales (0227) 54778; Technical (0227) 64723; Telex 965780.



DIGITAL MULTIMETERS

FROM ONLY £39

(plus VAT, p&P)



Get your hands on a low-cost, high-performance digital multimeter.

Choose from these three models:

EDM-101, at £39 (+VAT, p&P), has 5 functions and 19 ranges, plus diode test (200mV to 1000Vdc; 200 and 600Vac; 200µA to 2Aac; 200 Ω to 20M Ω).

T100 (illustrated), at £49 (+VAT, p&P), incorporates 7 functions and 29 ranges including diode test and a direct 10A input. (200mV to 1000Vdc or 750Vac; 200µA to 10Aac or dc; 200 Ω to 20M Ω).

T110, at £59 (+VAT, p&P), has an additional buzzer for fast continuity testing.

Send your order in today!

VAKO DISPLAY SYSTEMS LTD

Pass Street, Werneth, Oldham, Lancs OL9 6HZ
Tel: 061-652 5111 Telex: 668250

Please send me:

..... EDM-101 multimeters at £46.60 (incl.VAT, p&P)

..... T100 multimeters at £58.10 (incl.VAT, p&P)

..... T110 multimeters at £69.50 (incl.VAT, p&P)

Cheque/P.O. enclosed payable to _____
Vako Display Systems Ltd. for: £ _____

Name: _____

Address: _____

Please allow 14 days for delivery.

TRADE COUNTER CALLERS WELCOME.

orders. Turnaround is 4-12 days and everything ordered is supplied. A stock/price lists is available only for 100+ quantities, and Access is the only credit card accepted.

Crimson Elektrik,

9, Claymill Road, Leicester LE4 7JJ. Tel. 0533 761920.

"We specialise primarily in high quality hi-fi equipment, custom built amplification and active cross-over networks".

P&P is charged at cost.

CRP Electronics Ltd.,

Hazlebury Crescent, Luton, Beds LU1 1DF. Tel. 0582 411085.

P&P is at cost.

CVS Enterprises,

21-23 Bell Street, London NW1. Tel. 01 723 8545.

"We specialise in video game hardware and software. We can supply all parts for building video games, including logic, PCBs and programs to run in them, also push-buttons, four and eight-way joysticks etc.".

Damon Electronics,

99 Carrington Street, Nottingham. Tel. 0602 53880.

P&P charges are by weight; TV, FM and CB aeriels are also stocked.

D.J. Electronics,

64, Emsbury Park Road, Bournemouth, Dorset. Tel. 0202 515703.

Mail order enquiries are welcomed.

East Cornwall Components,

119 High Street, Wem, Shropshire SY4 5TT. Tel. 0939 32689.

"We offer a very comprehensive range of components not only to the more professional hobbyist but to the TV repair man, also".

Electronic Hobbies Ltd.,

17, Roxwell Road, Chelmsford, Essex CM1 2LY. Tel. 0245 62147.

Credit cards: Access only.

Electronic Surplus & Parts,

147 Foundry Road, Southampton, Hants.

"Our company specialises in surplus electronic parts and as such we do not stock a complete range of components, although various transistors, pots, transformers, meters etc are listed in our updated news/bargain sheets".

Electronics World

1A, Dews Road, Salisbury, Wilts. Tel. 0722 21262.

"The only shop in Salisbury with a comprehensive range of components". A surplus list will be supplied free on receipt of an SAE.

Electroni-Kit,

388 St John Street, London EC1 4NN. Tel. 01 278 0109.

"We are aiming at people who are just beginning in electronics. Our kits are complete in every way; nothing else is required".

Electroni-Kits are available from most High St. hobby shops. P&P charges are approximately 10% of the order value.

Electrotech,

394 Edgware Road, London W2 1SD. Tel. 01 923 8189.

Supplier to the public of general

electronics components. Handling charges are inclusive.

Electrovalue Ltd.,

28E, St Junes Road, Englefield Green, Egham, Surrey TW20 OHB. Tel. Egham 33603 (STD 0784; London 87).

"Established 1965, produced catalogue from 1967. Also sell computers and related products. Main franchises are Siemens, Radiohm, Nascom, Gemini, and Vero. Discounts based on order value have been operated since 1967. Our latest Catalogue '82 is available post free for 70p, with a refund voucher".

Other items available from Electrovalue include aeriels, buzzers, crystals and thermistors. Their shops are in Egham, Surrey, and Manchester (Burnage).

Enfield Electronics,

208 Baker Street, Enfield, Middx. Tel. 01 366 1873.

P&P from 16p to £1, maximum.

Eteson Electronics,

15B, Lower Green, Poulton-le-Fylde, Blackpool, Lancs FY6 7JL.

Global Specialities Corporation,

G.S.C. (UK) Limited, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Tel. 0799 21682.

Well known for their extensive range of instruments and test equipment, GSC have shops in Clacton, Cork, Blackpool and London. Post and packaging charges are to scale and American Express cards are accepted.

Goddards Components,

110, London Road, St. Albans AL1 1NX. Tel. 56 64162.

"We also sell a large range of aeriels, hi-fi accessories, and spares, test equipment, loudspeaker chassis, and have just opened a music department with everything for the modern musician".

Personal shoppers only.

Greenbank Electronics

92, New Chester Road, New Ferry, Wirral, Merseyside L62 5AG. Tel. 051 645 3391.

Greenbank also supply modular computer kits and are sole suppliers of the "Interak 1" modular Z80-based rack mounting computer.

Greenway Electronics Components,

62, Maypole Road, Ashurst Wood, East Grinstead, Sussex. Tel. 034282 3712.

Specialists in passive components.

Greenweld Electronics Ltd.,

443, Millbrook Road, Southampton SO1 OHX. Tel. 0703 772501.

"As well as one-off component supply for hobbyists, we also supply components in bulk - 100 off, 1000 off, etc - at very competitive prices. The catalogue also comes with a wholesale discount list, with discounts on every item from 5% to 66%, depending on part and quantity".

Greenweld's catalogue costs 75p, including postage, and contains 60p worth of discount vouchers.

They accept orders from overseas, but prefer them to be accompanied by either local currency or a bank draft. Local postal orders or cheques are not acceptable.

As well as items mentioned in the main listings, Greenweld also supply speakers, headphones, mics, buzzers and bells, morse keys, multimeters, and storage containers. See the full range at their shop, in Southampton!

Hart Electronic Kits Ltd.,

Penylan Mill, Oswestry, Shropshire SY10 9AF. Tel. 0641 2894.

"Hart Electronics are specialists in kits to the highest professional standards, which are easy even for complete beginners to assemble".

They also stock tape heads, mechanisms and test cassettes. P&P charges are based on a sliding scale.

Hemmings Electronics,

16, Brand Street, Hitchin, Herts. Tel. 0462 3303.

Also suppliers of microcomputers, printers, mono and colour monitors, computer consumables (floppy discs, paper, ribbons etc), and software.

P&P charges are 60p on orders under £10.

Henry's Radio,

404, Edgware Road, London W2. Tel. 01 402 6822.

Henry's carry large stocks at competitive prices . . . and also test equipment, leads, speaker chassis from 1½" to 15", microphones, CB and Ham equipment and accessories, calculators, microcomputer kits and digital watches!

Post and packaging is charged by weight, with a minimum of 35p.

ILP Electronics Ltd,

Graham Bell House, Roper Close, Canterbury CT2 7EP. Tel. 0227 54778.

Their products are sold by Watford Electronics, Marshalls in Bristol, London and Glasgow, and by Technomatic. ILP will also make one-off toroidal transformer for a nominal charge.

Intel Electronics Group Limited,

Henlow Trading Estate, Henlow, Beds SG16 6DS. Tel. 0462 812505.

Post and packaging charges are at cost.

Langrex Supplies Ltd.,

Climax House, Fallsbrook Road, Streatham, London SW16 6ED. Tel. 01 677 2424.

L.B. Electronics,

11, Herlies Road, Hillingdon, Middx. Tel. 0895 55399.

Post and packaging on mail orders is 50p minimum.

Lightning Electronic Components,

18, Victoria Road, Tamworth, Staffs. Tel. 0827 65767.

"Lightning Electronic Components specialise in fast turn around of mail order - and personal service for callers at the showroom. Telephone orders by credit card also accepted".

A range of test equipment is also available; post and packaging charges re 50p for orders under £10.

Magenta Electronics Ltd,

135 Hunter Street, Burton-on-Trent, Staffs DE14 2ST. Tel. 0283 65435. "Magenta Electronics is an established company which has specialised in the mail-order supply of components and kits etc to readers of Hobby Electronics. New kits are added each month. We are happy to supply either individual parts or complete kits.

All orders receive careful and prompt attention and all parts are, of course, new and full specification. P&P is a single standard charge and all prices include VAT. Our price list is free with orders or on receipt of an SAE. The illustrated catalogue is 80p, in stamps or added on to your order".

"We don't claim to be perfect, but we do try!"

There is no surcharge or minimum phone orders on credit cards.

Maplin Electronic Supplies Ltd.,

PO Box 3, Rayleigh, Essex SS6 8LR. Mail order sales Tel. 0702 552911. "Orders are despatched on the day of receipt. A price list/project book is published every three months and a brand new catalogue will be available in November".

Maplin also sell: aerials, car accessories, microcomputers and software, electrical accessories, mics, headphones, musical effects units, organ components, record and tape accessories and parts, loudspeakers and test equipment.

Shops at: 159-161 King Street, Hammersmith, London, (Tel. 01 748 0926); 284 London road, Westcliff-on-Sea, Essex. (Tel. 0702 554000); Lynton Square, Perry Bar, Birmingham (Tel. 021 356 7292).

Marco Trading,

The Maltings, Wem, Shropshire. Tel. 0939 32763.

"We supply electronic components to the public via our ever-growing mail order service, and also we offer wholesale and quantity terms to schools, universities and, of course, the trade; we believe we offer competitive prices and services".

Macro Trading's 58-page catalogue is available for 25p. A retail shop will shortly be opening in a 6000 sq ft renovated Mill; telephone for opening times.

Marshall's (London) Ltd,

85 West Regent Street, Glasgow, G2 2QD. Tel. 041 332 4133.

"All items stocked by Marshalls are top quality branded products which carry full manufacturer's guarantees."

Marshall's offer trade, retail, export and quantity discounts, and stock the extensive range of Leader and Thandar test equipment. In addition to Barclaycard and Access, credit cards from American Express, Diner's Club and Tricity Finance are also accepted.

Despite the company name, their shop is firmly located in Glasgow!

Bradley Marshall,

325 Edgeware Road, London W2 1BN. Tel. 723 4242.

This well known London firm, operating from their shop in Edgeware Road (where else?), also stock test equipment and can supply most data sheets. In addition to Barclaycard and Access, American Express and Diner's Club cards are also accepted.

Micro-Times,

19, Mill Street, Bideford, North Devon. Tel. 02372 79789.

"All brand new, full-spec devices".

Midwich Computer Co.,

Hewitt House, Northgate Street, Bury St Edmunds, Suffolk. Tel. 0284 701321.

"We specialise in microcomputer components with full technical backup if required. Delivery is by return post as all orders are despatched on the day the order is received".

Post and packaging is 75p on orders under £10.

Modular Electronics,

95, High Street, Selsey, Nr Chichester, Sussex. Tel. 024361 2916. Specialists in RF power and small signal VHF/UHF devices, and associated components.

MS Components Ltd.,

Zephyr House, Waring Street, West Norwood, London SE27 9LH. Tel 01 670 4466.

MS Components also run a trade counter, and stock power supplies, soldering equipment and suppressors, and offer a prototype transformer service.

Myers Electronics,

12-14 Harper Street, Leeds 2. Tel. 0532 452045.

"We are a new business, endeavouring to build up stocks of every item anyone in electronics could want".

The shop is in Harper Street, near Leeds Market, above the Union Jack Clothing Store.

NAMAL Associates,

25, Gwydir Street, Cambridge. Tel. 0223 355 404.

Also a manufacturer of accessories for home computers. Access is the only credit card accepted.

Parndon Electronics Ltd.,

44 Paddock Mead, Harlow, Essex CM 18 7RR. Tel. 0279 32700.

"We maintain a small product line selected for quality and aim to ship all orders within 24 hours of receipt — which we achieve 95% of the time".

P.A.T.H. Electronic Services,

360 Alum Rock Road, Birmingham B8 3DR. Tel. 021 327 2339.

PC Electronics,

"Thornhill", Romsey Road, Whiteparish, Salisbury, Wilts.

"Bulk supply of components at extremely low prices".

A price list will be sent free of charge on receipt of an SAE.

Peats Electronics,

25, Parnell Street, Dublin 1, Ireland.

PM Components,

Conningsby House, Wrotham Road, Meopham, Kent. Tel. 0474 813225. Specialists in valves of all kinds, old and antique, and valve hardware. Only wire-wound resistors are stocked.

T. Powell

Advance Works, 44, Wallace Road, London N1. Tel. 01 226 1489.

"Specialists in electronic kits, especially ioniser kits".

Rapid Electronics Ltd.,

Hill Farm Industrial Estate, Boxted, Colchester, Essex CO4 5RD. Tel. 0206 36412.

"Prime quality components at the best prices! Because we have depth of stock on all lines, all orders are despatched on the day of receipt". Post and packaging charges (50p) are made for orders under £10.

Brian J. Reed,

161 St Johns Hill, Battersea, London SW11 1TQ. Tel. 01 223 5018.

Also suppliers of . . . clamps, clips, bushes, grommets, cartridges, styli, insulator kits, tape, solder, delay lines, emergency lighting, sirens, bells, fans, loudspeakers, earphones, transistor arrays, mikes, suppressors, EHT trays, crystals, counters, bulbs, programmer/timers, solenoids and motors, . . . amongst other things.

Their catalogue costs 75p plus 25p post and packaging; orders under £5 are subject to a 50% small-order handling charge. Post and packaging charges are inclusive, other than 15½p SAE or label.

Relay-A-Quip,

Moat Lodge, Stock Chase, Maldon, Essex. Tel. 0621 58686.

"We can supply any component in quantity and we manufacture enclosures and cases to customers specifications. Trade price lists are available".

Post and package charges for mail order are 50p for orders under £5. Both Barclaycard and Access are accepted and orders may be placed by phone on 0621 57242 until 8pm, Monday to Saturday. Callers to the shop in the delightful town of Maldon are by appointment only.

Riscomp Ltd.,

21, Duke Street, Princes Risborough, Bucks HP17 0AT. 08444 6326.

Riscomp carry a full range of audio modules from 10 to 125 watts, and also a range of security modules and accessories. Their PCB-making facility is available for prototypes or production boards in quantities from 1 to 10,000. Turnaround on prototypes is inside 24 hours. Access is the only credit card accepted.

Samsons (Electronics) Ltd.,

9-10, Chapel Street, London NW1. "We are specialists in power supply

USED EQUIPMENT

500V MEGGER

Transistorised Insulation Test-er and four decade resistance bridge with four ranges. Invaluable piece of test gear. In case with carrying handle. Uses one PP9 batt. £15.00 £2 P&P

Recent Style P.O. Telephones £4.75 + £1.80 P&P
2 for £9 + £2.50, 5 for £20 + £5

COMPACT TELEPHONE

With wall-mount bell £6.50 Older style black telephones, £3. 00p as above. Our leaflet explains how to use G.P.O. phones in home intercom systems.

5 Digit Counters 48V coil. Non resettable 75p

UNISELECTORS. 50v, 4 Bank + Homing Bank, 25 way £3.50

D CONNECTOR SOCKETS with cover, 50 way £2

60V 8A TRANSFORMER. Ideal for big power supply unit or amplifier £12 Inc. p&p. BEAT THAT!

Various stabilised power supplies available - Excellent prices send for details.

FREE on request - Leaflet "D.I.Y. Telephone Systems and Automatic Exchange Design".



L.E.M. SERVICES
239 RUGBY ROAD
LEAMINGTON SPA CV32 60Y
WARWICKSHIRE

**ADD 50p P&P
ORDERS OVER
£7.50 POST FREE**
unless stated otherwise

TEL: 0926 30622 FOR QUANTITY DISCOUNTS ETC.
ALL ITEMS - MONEY BACK IF NOT DELIGHTED.

LOW-COST, RUGGED TEMPERATURE CONTROL

HIGH QUALITY



TEMP. GAUGE 0° - 120°C
Remote sensor on 38" capillary, panel mounting dial 55mm. dia.

ONLY £2.50

16A 240V RANCO THERMOSTAT

Wide control range (flow room temp. to over boiling point) Sensor on 22" capillary. £2.30, including control knob

RANCO THERMAL CUT-OUT 100°C

15A 240V. Sensing coil on 41in. capillary panel mounting with reset button £1.20

BUY ONE EACH OF ABOVE FOR £5.50

LIGHT DEPENDENT RESISTORS in plastic housing with window, heavy-duty lead. Similar to ORP 61. You normally pay well over double for resistor alone. Only 30p or £2.35 for 10.

GEARED Synchronous motor, 8 r.p.m., 240V A.C. 3 Watt £2.

SOLENOID GAS VALVE. 240V A.C. 5 P.S.I. suitable for non-corrosive fluids. £2.20

BULGIN 3 pin free plug & panel socket, 2A 240V 50p

AUTOMATIC DIAL UNIT. (mains powered). These units connect into a telephone and dial a number when a punch-card is inserted. Card & instructions supplied. Cards readily available. Many uses. Only £8 + £1 p&p

Lightning ELECTRONIC COMPONENTS

THE CHOICE IS YOURS - CALL AT OUR NEW SHOWROOM OR USE OUR VERY FAST MAIL ORDER SERVICE.

EITHER WAY WE'LL KEEP YOU HAPPY *****

Furthermore we promise if any part ordered by mail fails to please just return within 7 days for a full refund.

For a vast selection of electronic components & equipment of all kinds. Here is just a selection of our stocks. Many more items listed in our catalogue available now 70p post paid.

RESISTORS

1W 5% C.F. 1R to 10M 2p each 100 for £1.00
1/2W 5% C.F. 10R to 1M 2p each
1W 5% C.F. 10R to 820K 5p each
1/2W 1% M.F. 10R to 680K 5p each 100 for £3.00
100 off prices one value only - no mixing

POTENTIOMETERS

Preset 1W Horiz 8p
1W Vert 11p
Std single Pot 29p
Single & Switch 60p
Dual Gang 75p

CAPACITORS

Min Plate 1.8pF to 47pF 5p
Ceramics 50pF to 220pF 6p
220pF to 1000pF 7p
1200pF to 4700pF 8p

Disc .01uF 50V 8p (100 for £5)
Ceramics .1uF 50V 10p (100 for £5)

Variable 0 to 500pF 95p

100 off any one type less 30%

Electrolytics - polys - Tants - Full range in catalogue

TRANSISTORS

AC128 0-24	BD240A 0-60	BU126 2-25	TIP33C 0-85	TIP147 1-25
AF117 0-52	BD241A 0-60	BU128A 2-00	TIP34C 0-85	TIP2955 0-69
BC107 0-10	BF180 0-30	MPSA05 0-20	TIP35C 1-85	TIP3065 0-57
BC107C 0-12	BF199 0-18	MPSA06 0-21	TIP36C 1-90	TIS43 0-30
BC108 0-10	BF244B 0-29	MJ15003 4-06	TIP41A 0-45	TIS90 0-28
BC108C 0-12	BF257 0-30	MJ15004 5-04	TIP41C 0-48	2N1309 0-60
BC109 0-10	BF39 0-24	R2010B 2-60	TIP42A 0-45	2N3053 0-22
BC109C 0-13	BF40 0-24	TIP23A 0-39	TIP42C 0-48	2N3054 0-48
BC182 0-10	BF84 3-00	TIP29C 0-45	TIP110 0-82	2N3055 0-48
BC184L 0-10	BF87 0-26	TIP30A 0-39	TIP115 0-82	2N3904 0-14
BC212L 0-10	BF88 0-26	TIP30C 0-45	TIP121 0-99	2N3773 2-25
BC214L 0-10	BFW14 0-25	TIP31A 0-39	TIP126 0-99	40673 0-82
BD112 0-80	BPY53 0-21	TIP31C 0-45	TIP141 1-20	40871 1-06
BD115 0-59	BPY90 0-65	TIP32A 0-39	TIP142 1-20	40872 1-06
BD124 1-58	BLY93A 14-20	TIP32C 0-45	TIP146 1-25	

We specialise in audio power transistors - special prices available to bulk buyers - SAE please.

INTEGRATED CIRCUITS

TTL	CMOS	LINEAR	LM386 0-90	TBA440 2-52
LS00 0-12	4000 0-14	LF351N 0-49	LM387 1-18	TBA520 1-92
LS04 0-15	4011 0-14	LF353N 0-94	LM389 0-70	TBA530 1-78
LS08 0-15	4013 0-15	LF356N 0-86	LM3914N 2-08	TBA900 0-86
LS10 0-15	4017 0-42	LM301AN 0-26	LM3915N 2-15	TBA900 2-20
LS13 0-29	4022 0-66	LM308 0-94	LM3916N 2-15	TD2640 2-16
LS20 0-15	4046 0-74	LM311 0-70	MC1458 0-47	555 0-20
LS30 0-18	4049 0-30	LM324N 0-60	NE555 0-20	709 0-60
LS74 0-24	4066 0-36	LM348N 0-86	NE566 0-60	741 (8pin) 0-18
LS107 0-40	4070 0-25	LM389N 0-75	NE566 1-20	747 0-70
LS154 0-86	4093 0-38	LM381N 1-45	NE566 1-56	748 0-36
LS244 0-80	40106 0-66	LM382 1-25	NE567 1-60	
LS386 0-28	4811 0-67	LM384 1-40	TBA120 0-90	

V. REGULATORS (FIXED)

+Ve 100mA 78L05 - 78L12 - 78L15 31p
-Ve 100mA 79L05 - 79L12 - 79L15 59p
+Ve 1 Amp 7805 - 7812 - 7815 80p
-Ve 1 Amp 7905 - 7912 - 7915 65p

V. REGULATORS (VARIABLE)

LM317K 1.5 Amp £3-35
LM338K 5 Amp £4-70
LM396K 10 Amp £11-00
L723 14 DIL £0-40
L723 TO99 £0-80

PRINTED CIRCUIT BOARDS - High quality fibre glass laminate

1.6mm Single sided board 1.6mm Double sided board
6 x 6 0-85 6 x 6 0-90
6 x 12 1-65 6 x 12 1-70
12 x 12 3-05 12 x 12 3-15

FOTO COATED RESIST BOARD - High quality fibre glass laminate

precoated with positive photo resist. For small batch production of PCB's

1mm single sided 12" x 18" £8-80
1.6mm Double sided
100 x 180mm Euro 1-53 100 x 180mm Euro 1-70
203 x 114mm 1-39 203 x 114mm 2-10
203 x 228mm 3-80 203 x 228mm 4-10
467 x 305mm 9-10

Fotodeveloper concentrate £2-42 Ferric Chloride rock £1-20
Acetate Sheet £1-60 Plastic Tonge £0-95
Epoxy Sheet £0-20 Delo Pen £0-88
Transfer Pack 5 asstd. sheets £2-00

PANEL METERS

Until now panel meters have proved an expensive part of your project. Now available this new quick fit type.
32mm Square Meter



The following Dc ranges:-
50uA - 100uA - 500uA - 1mA
5mA - 10mA - 50mA - 100mA
500mA - 1A - 5A - 25V - 50V
ONLY £1-95 each

BARGAIN PACKS

12 Asstd Panel Mtd Pots £1-10	12 Asstd Presets £0-50
20 Asstd Electrolytic Caps £0-65	30 Asstd Silver Mica Caps £0-90
7 Asstd Blob Boards £1-10	5 Asstd Relays £1-10
150pF Trimmer Cap £0-20	30 Asstd C296 Polyester Caps £0-60
30 Asstd Min Ceramic Caps £0-70	250 Asstd Preformed resistors £0-75
10 Asstd 4000 Series CMOS £1-10	8 Asstd Switches Micro, side, lever, key, push, toggle
20 Plastic type BC109 trans. £0-60	Excellent value
Push Buttons SPDT 15p each 10 for £1-00	1 Electrolytic Can 15000uF 25V £0-90
	Micro SPDT 10p each 6 for 50p

Postage & Packing 50p per order (free over £10) Please add VAT at 15%.
Telephone orders welcome by Access or Barclaycard

LIGHTNING ELECTRONIC COMPONENTS

Showroom & Mail Order Distribution Centre at:-
18 Victoria Road, TAMWORTH, Staffs B79 7HR
Telephone 0827-65767.

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns	.83	.72	.66
4116 250ns	.75	.65	.60
4816 100ns for BBC comp.	2.45	2.10	1.95
4164 200ns	4.95	4.55	4.20
2114 200ns Low power	1.15	1.00	.90
2114 450ns Low power	.95	.85	.80
4118 250ns	3.25	2.85	2.65
6116 150ns CMOS	3.70	3.20	2.95
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt	2.60	2.25	2.10
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.75	3.25	3.00
2532 450ns Texas type	3.75	3.25	3.00

Z80A-CPU £4.35	Z80A-PIO £3.25	Z80A-CTC £3.25
6522 PIA £3.98	7805 reg .50	7812 reg .50

Low profile IC sockets:									
Plns	8	14	16	18	20	22	24	28	40
Pence	9	10	11	14	15	18	19	25	33

Soft-sector floppy discs per 10 in plastic library case:
5 inch SSSD £17.00 5 inch SSDD £19.25
5 inch DSDD £21.00 8 inch SSSD £19.25
8 inch SSDD £23.65 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces.

Please add 30p post & packing to orders under £15 and VAT to total. Access & Barclaycard welcome, 24hr service on (054 422) 618. Government & Educational orders welcome, £15 minimum. Trade accounts operated, phone or write for details.

Happy Memories (HE), Gladestry, Kington, Herefordshire. HR5 3NY. Tel: (054 422) 618 or 628

CB Squelch Unit

R.A. Penfold



A handy little device for CBers and radio enthusiasts alike.

WHEN USING a transmitter in a noisy environment (such as a moving vehicle or a room in which a television set is operating, for example) the intelligibility of the transmitted signal can be severely impaired by the high background noise level. Even if the words can be heard, the background noise is rather tedious for anyone trying to copy the transmission!

This problem can become more severe when using a speech processor, a transmitter having built-in speech processing or automatic modulation level control. During the brief pauses that occur during normal speech, the audio sensitivity can rise quite significantly as the audio processing circuits try to modulate the transmitter with the signal produced by the background noise!

There are several ways of combatting this problem, such as the use of a noise cancelling microphone which phases out signals that emanate some distance from the microphone, but not those which originate quite close to the microphone. There is also an electronic method of giving an apparent reduction in the transmitted ambient noise level, and this is achieved using a form of Squelch or Noise Gate circuit. A circuit of this type normally attenuates the

How it Works


The Block Diagram of the Squelch Unit is very similar to that of the Stereo Noise Gate and, in fact, it operates in a similar manner, too. The main signal path contains an amplifier, a voltage controlled attenuator and a fixed attenuator. The gain of the amplifier is balanced by losses through the attenuator so that the unit has unity gain overall. Pre-amplification is necessary to provide a high signal level to the VCA input, so that unwanted switching pulses generated by the circuit are small in comparison to the speech signal. The attenuator then restores the signal to its original level.


Some of the pre-amplifier output is amplified further, then rectified and smoothed to give a DC signal which is proportional to the average input level. This drives a trigger circuit whose output switches from a high to a low when the DC signal is more than about 2V5

positive. The output from the trigger controls the VCA and an indicator LED; a low output turns on the LED and switches the VCA to its zero attenuation state. When the trigger output is high, the LED is switched off and the VCA gives about 20 dB or so attenuation of the audio input.

The unit is adjusted so that with only noise present, the VCA is in the high attenuation condition, but when there is a voice signal, the trigger switches the VCA to zero attenuation. The LED is ON when the unit is passing a signal.

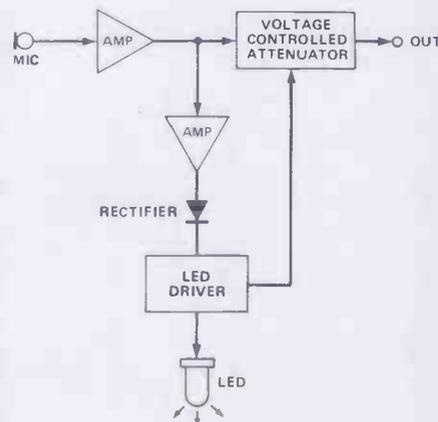The smoothing circuit is designed to give a fast attack time, switching rapidly as soon as it detects a speech signal, but a slow decay so that the ends of words are not chopped off by too rapid switching back to the high attenuation state.



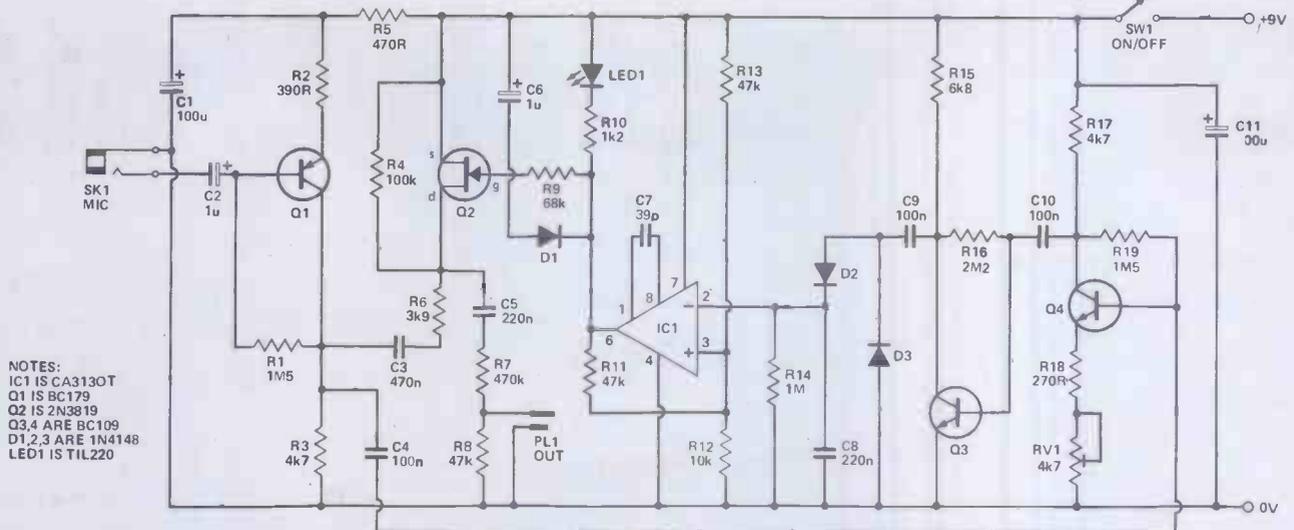

NOTES:
 IC1 IS CA3130T
 Q1 IS BC179
 Q2 IS 2N3819
 Q3,4 ARE BC109
 D1,2,3 ARE 1N4148
 LED1 IS TIL220

Figure 1. The circuit for the CB Squelch Unit.

processed signal, say by about 20 dB, but gives no attenuation when the operator is speaking into the microphone and there is somewhat higher input level.

This greatly reduces the background noise level during pauses in the speech signal, which is when the noise is most obtrusive. There is no reduction when the speech signal is present, but this signal tends to largely mask the noise and make it comparatively unimportant. The result is an apparent reduction in the noise level, with the wanted signal tending to stand out more clearly.

This Squelch Unit is designed for use with a high impedance dynamic microphone, but its sensitivity is high enough to permit its use with most low impedance dynamic types as well. The circuit is battery powered and simply connects between the microphone and the transceiver. Of course, the unit could

possibly be used to advantage with public address or disco equipment, though its companion unit, the Stereo Noise Gate, which is specifically designed for wide-band audio rather than narrow-band communications use, will give much better results. It is based on special ICs, which have excellent noise and distortion figures, operated as voltage controlled *amplifiers*, rather than as attenuators.

The Circuit


The full circuit diagram of the Squelch Unit is shown in Figure 1. The input preamplifier uses Q1 in the common emitter mode, with R2 to provide negative feedback; this boosts the input impedance of the unit to a suitably high level to match a high impedance dynamic microphone.

A simple JFET VCA is used, formed

by R6 and the drain-to-source resistance of Q2. With the gate of Q2 at or near the positive supply potential, Q2 is biased hard on and has a drain-to-source resistance of only a few hundred ohms; this gives a loss of about 20 dB or so through the VCA. When Q2 is cut off, it exhibits a drain-to-source resistance of about a thousand megohms (if its gate is taken to almost the negative supply potential) and losses through the VCA are then negligible. R7 and R8 form the output attenuator.

Some of the output from Q1 is coupled by C4 to another common emitter stage based on Q4, and from here the signal is coupled by C10 to a further common emitter amplifier, this time using Q3. A controlled amount of negative feedback is applied to Q4 by RV1 so that the gain of this stage can be varied from a little less than unity, at

Figure 2. Wiring and component overlay for the Squelch Unit. Note that the cathode of LED1 is the flat side of the case.

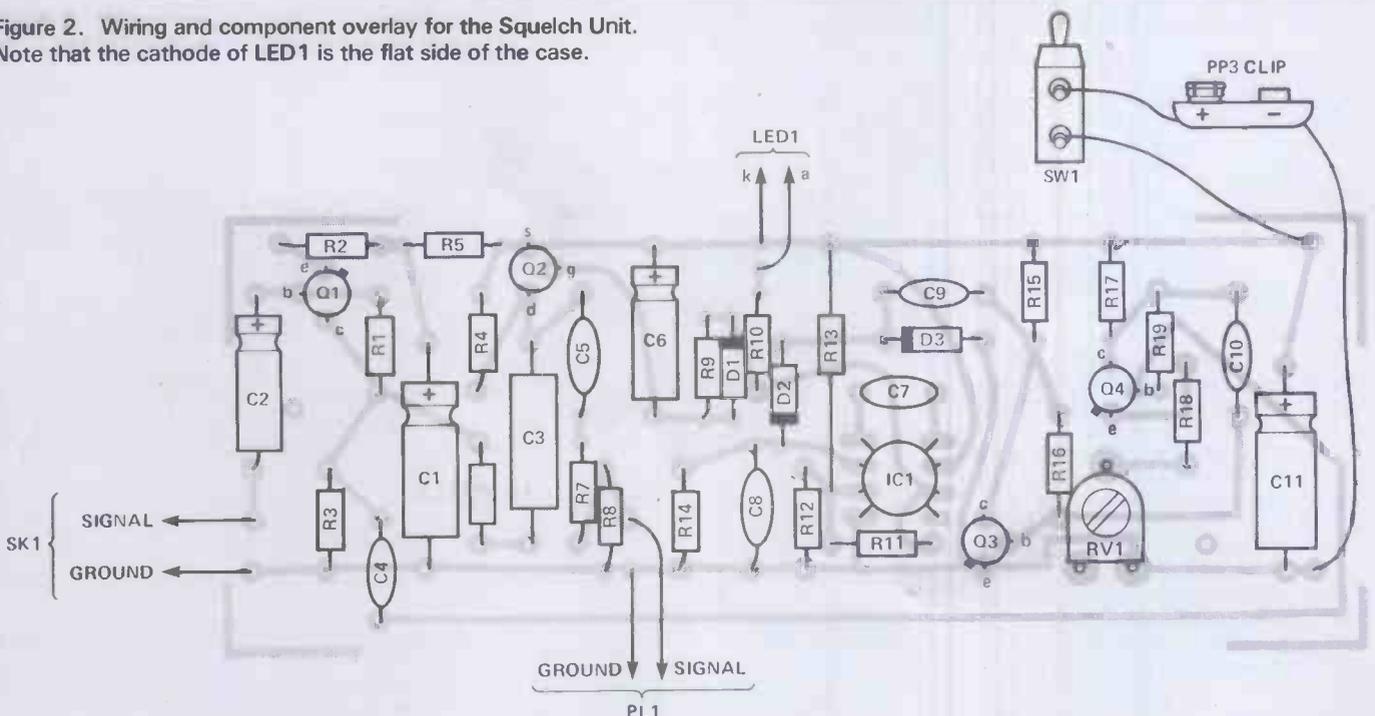

Into Radio: Project

maximum value, to around 24 dB (16) at minimum resistance. By adjusting RV1 it is possible to set the sensitivity of the unit at the correct level.

The output of Q3 is fed to the inverting input of op-amp IC1 via a rectifier and smoothing circuit consisting of D2, D3, R14 and C8. The positive output of this network will be sufficient to activate IC1 when there is a speech signal present, but not when there is only the weaker, background noise signal.

The op-amp, IC1, is used here as a variety of Schmitt Trigger. When there is no speech signal, the output is in a high state so that indicator LED1 is switched off. The JFET Q2 is biased on, providing a low impedance path to OV through Q2 and the battery, thus heavily attenuating the input (noise) signal. However, when the inverting input goes more than about 2V5 positive, as it will when there is a speech input, the output of IC1 goes low; LED1 turns on and Q2 is biased off, removing the low impedance path to OV and producing minimum attenuation of the signal.

The attack time—the time taken by the VCA to switch from low to high impedance—is very rapid, whereas the decay time is slowed down by R9 and C6; this ensures that there is minimal noise generated by the VCA as it returns to the high attenuation (low impedance) state. It can sometimes happen that, due to the nature of the input signal, the VCA will switch rapidly between states, several times in succession, the slow decay time set by R9 and C6 also prevents this undesirable effect. Diode D1 ensures that R9 and C6 do not effect the rapid attack time.

Construction

All the components, including the battery, will readily fit into an aluminium box measuring about 133 x 70 x 38mm. SK1, D4, and SW1 are mounted on the front panel; SK1 is a four-way DIN type on the prototype, however, this should obviously be varied to suit the plug fitted to the particular microphone used. An exit hole for the output lead is drilled in the rear of the case and this lead is fitted with a plug of the same type as fitted to the microphone. Many communications microphones have a press-to-talk switch and consequently use a 4 way lead and plug. If the unit is used with a microphone of this type, the appropriate two pins of SK1 simply connect direct to the corresponding two leads of the output cable.

The printed circuit board is detailed in Figure 2. Construction is mostly straight forward; IC1 is a CMOS device, though, and it is thus necessary to observe the normal handling precautions. Use pcb pins at points on the board which will later be connected to off-board components.

Mount the finished board on the base panel of the case using 6BA fixings, including spacers to prevent connections on the underside of the board short circuiting through the case. Leave sufficient space for the PP3 battery at one side of the component board. The remaining wiring is then completed, as shown in Figure 2.



Parts List

RESISTORS

(All ¼ watt 5% carbon)

R1, 19	1M5
R2	390R
R3, 17	4k7
R4	100k
R5	470R
R6	3k9
R7	470k
R8, 11, 13	47k
R9	68k
R10	1k2
R12	10k
R14	1M
R15	6k8
R16	2M2
R18	270R

POTENTIOMETERS

RV1	4k7 miniature horizontal preset
-----	------------------------------------

CAPACITORS

C1, 11	100u 10V axial electrolytic
C2, 6	1u 63V axial electrolytic
C3	470n C280 polyester
C4, 9, 10	100n C280 polyester

C5, 8	220n C280 polyester
C7	39p ceramic disc

SEMICONDUCTORS

IC1	CA3130T MOSFET op-amp
Q1	BC179 silicon PNP transistor
Q2	2N3819 silicon N-channel FET
Q3, 4	BC109 silicon NPN transistor
D1, 2, 3	1N4148 signal diode
LED1	TIL220 5mm red light emitting diode

MISCELLANEOUS

SW1	SPST miniature toggle switch
SK1	4-pin DIN socket (see text)
Aluminium case; PP3 battery clip; PCB LED fixing washer; output lead; output plug (as required); wire, solder etc.	

BUYLINES 30

Setting Up

It is only necessary to set RV1 to the correct level before the finished unit is ready for use. This is adjusted by trial and error so that the ambient noise level does

not trigger the VCA but the speech signal does so reliably. Indicator LED1 lights up when the unit is activated and this greatly simplifies setting up. Ten-Four!

HE

HOME CONSTRUCTOR TURNTABLE KITS

from

INPUT DESIGN LTD

THE LEADING MANUFACTURERS OF
TURNTABLES IN KIT FORM

NORMAL RETAIL PRICE £49.50

**SPECIAL
INTRODUCTORY
OFFER TO
READERS
OF HE**

£44
inc VAT
(P & P £1.95)

This kit includes AC Synchronous motor (as used on £350 decks), Pulley, Belt, Drive Hub, Spindle, Bearing, Glass Platter, Felt Mat, Switch, Electronics, Cable and full instructions together with blueprint for plinth assembly.

Any other parts (ie Lid) available as optional extras.

**5 YEAR GUARANTEE—
MONEY BACK IF NOT SATISFIED**

Pay by Barclaycard, Access or CWO. Export: Write for Pro-forma.




INPUT DESIGN LTD

Palace Street, Biggleswade
Beds. SG18 8DP
0767 316655

19" RACK MOUNTING CABINET.

Front Panel 480 x 150 mm Rear Case 425 x 250 x 140 mm

£23.95
£19.50

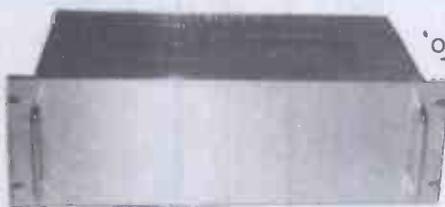

'Or Free Standing'

'Brushed
Alu Front
with
'CHROME HANDLES'

This is a professional rack mounting cabinet that will allow you to get your equipment off the bench. Rack mounting provides security for your equipment and easy access for maintenance. This Precision rack mounting cabinet has all the features you would expect from a professional unit.

★ Top, bottom and rear cover removable for access ★ Plates have heavy duty grey paint finish ★ Front panel is heavy gauge - 3mm aluminium ★ Strong, screwed, construction throughout - screws included ★ Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from ★ Front panel is of brushed aluminium finish enhanced with heavily chromed handles ★

Many sold to 'TANGERINE' users, & INDUSTRY.

ADD V.A.T AT STD RATE & ORDERS UNDER £5.00. P & P 50p. ABOVE ITEM £2 P & P

'metal cabinets'

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife!), louvre for ventilation and finished in an attractive two tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.

- | | | |
|-------------------------------|---|-------|
| a - 102(d) x 86(h) x 83(w)mm | a | £1.70 |
| b - 150(d) x 81(h) x 103(w)mm | b | £2.55 |
| c - 150(d) x 76(h) x 134(w)mm | c | £3.04 |
| d - 184(d) x 70(h) x 150(w)mm | d | £4.08 |




'TRADE'
PRICES ON
QTY ORDERS

Ask for our **FREE Catalogue.**

Slide Switches

- | | |
|-----------|-----|
| 1P 21 | 10p |
| 2P 21 | 12p |
| 2P 31 | 19p |
| 4P 21 pcb | 28p |
| 4P 31 | 35p |
| 6P 31 | 42p |
| 1P 41 | 26p |
| 4P 41 | 45p |

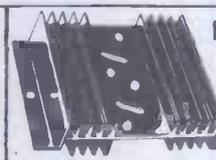

POWERSINK £1.35p

Flag mounting type with fins top and bottom. Available either undrilled or drilled to accept two power transistors of most types including TO-3, TO-18, TO-220, TO-92. Size 75(h) x 102(w) x 25(d)mm. Thermal resistance mounting surface to ambient -1°C/Watt (2.0W/sec. air velocity). Mounting surface temperature rise above ambient 60°C @ 30W heat dissipation.

RELAY-A-QUIP

We EXPORT ✓

Moat Lodge, Stock Chase,
MALDON, Essex, U.K.

Tel 0621-57242 10am - 8pm. mon - sat



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
- the definitive loudspeaker catalogue!

Everything for the speaker constructor - kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★
two listening lounges
(Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue
(cheque, M.O. or stamps - or phone with your credit card number)

★ Access - Visa - American Express accepted ★
also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



FROM A NEW COMPANY WITH NEW
IDEAS

SOMETHING SPECIAL

AIRWAVES ELECTRONICS INVITE YOU TO
OPEN YOUR OWN PERSONAL ACCOUNT.

THERE COULDN'T BE AN EASIER WAY TO
BUY COMPONENTS, ONCE YOU HAVE
OPENED YOUR ACCOUNT, JUST PHONE
OR WRITE YOUR ORDER THROUGH,
STATING YOUR ACCOUNT NUMBER TO-
GETHER WITH YOUR OWN SECURITY
CODE NUMBER AND GOODS WILL BE
DESPATCHED SAME DAY AND YOUR
ACCOUNT DEBITED WITH THE COSTS.

MAYBE YOUR THINKING—YOU'LL HAVE
TO PAY OVER THE ODDS FOR THIS, BUT
YOU WILL BE WRONG, ACCOUNT CUS-
TOMERS WILL RECEIVE OUR PRODUCT
PACKED CATALOGUE SHOWING VAT
INCLUSIVE PRICES, WHICH WE BELIEVE
TO BE VERY COMPETITIVE. AFTER ALL
YOU'RE THE BEST JUDGE AND WE DO
OFFER SOMETHING SPECIAL.

IF YOU WOULD LIKE TO OPEN YOUR
ACCOUNT, THEN PLEASE CONTACT US
FOR APPLICATION DETAILS ENCLOSING
JUST A STAMP TO COVER POSTAGE.

CALL AND SEE US AT OUR RETAIL SHOP.

AIRWAVES ELECTRONICS

151 LONDON ROAD, CAMBERLEY, SURREY
GU15 3JY. TEL. (0276) 62949

LB ELECTRONICS

PCB 16 10" x 12 1/4" Approx containing 72 x 4116, on board clock, no data £17.50p p/p £1.00p.

PCB 80 10" x 18" Approx containing 808A (socketed), 2708 x 5 (socketed), P8111A - 4 x 4, plus host of IC's (all standard) All power rails marked. £12.00p p/p £1.00p.

PCB TA 6 1/2" x 9" Approx Alpha numeric touch keyboard, ASC11, with Data £7.95 p/p 65p.

EPROMS 1702A £5.00p. 2708 £2.50p. 2516 (450NS), 5 Volts used once, erased and guaranteed by us £1.95p. 10 for £17.00p. 2732 £5.00, 2532 £6.00p.

RAM 2114L £1.25p (450NS), 4116 (200NS) £1.00p, 2114 (200NS) £1.35p p/p 35p.

CPU 8080 £2.50p, 6502 £4.50p, Z80A (4 MHZ) £4.50p, Z8671 (Basic/Debug) £21.00p.

LB ELECTRONICS

11 Herlics Road
Hillingdon
Middlesex
Tel. 0895 55399



Electronics World



1a Dews Road,
Salisbury, Wilts
Tel: (0722) 21262

16 DIGIT DISPLAYS 50p!!

Burroughs Panaplex 7-seg gas discharge type, 0.3in character height. Only 50p as we have no data. ALSO: as above but 12 digit 40p. ALSO: 9 digit 10mm high 40p. 3 each type, only £3.00

SLIDE SWITCHES

Multiposition as used on calcs, etc. 5 different types ranging from single pole 5 way, to one with 3 switches on one carrier. Pack of 10 switches (2 each type) for just £2.00

PULSE TRANSFORMER

As used on sound-to-light units etc to isolate mains. 1 : 1 ratio. 75p; 10 for £6

CMOS/74 PANEL

Neat PCB 215 x 70mm with 21 1N4148, 16 TO18 transistors, 741, R's and C's - and best of all, 2 x 4502, 4011, 2 x 74366 all in sockets. Also TO66 transistor on small heatsink. ONLY £2.00

BF257 PANEL

10 x BF257 high voltage, 11 x BC266A + R's and C's and diodes. Also 6 x 20SIL sockets (makes 3 40DIL skts) on PCB 180 x 175mm. All this for just £1.00

CALC PANEL???

Interesting panel 180 x 125mm with 15 digit gas discharge display, 7905, 7805(?) both on heatsinks, 3300uF/40V, 23 x 1N4004 40 DIL skt, 3 x 20 SIL skts, 4 x 18DIL skts + R's, C's etc. All components are mounted on the PCB but they haven't been soldered in!! (just a blob here and there). Special low price £2.50

COMPONENT PACKS

E1 Approx 300 resistors, all full length lead, carbon/carbon film mostly, few MO and WW. Wide range of values. Only £1.50

E2 Approx 200 disc ceramic capacitors Big range of values, small size 4-12mm dia. 50-500V working £1.50

E3 Approx 1000 components, mostly preformed resistors, 1/4 and 1/8W £1.50

ODDS AND ENDS

20 way SIL skt - 20 connectors on 0.1 pitch. Can be cut to any size. Pack of 10 £2.00 (RS equity price £4.96)

40 way DIL skt by TI. Limited qty. 5 for £1.00

Heatsink - T05 18mm dia x 11mm high. Pack of 10 50p; 100/£4.30; 1k £39

27 way cable 3m long with 28 DIL header plug one end and 0.1 pitch 30 way (4 pins missing) edge connector other end. Only 75p

26 way speedbloc ribbon cable connector (like RS 468-153). Special low price 60p each; 4 for £2.00

uPD566H 2 stage AVD amp £2.00

Post 50p. Prices include VAT. Free illustrated list sent with every order, or send SAE.

Come and visit our shop - Full range of new and surplus components + CB goodies

TRACKER CAR COMPUTER



"One of the neatest, most comprehensive and most useful of these car computers that we have yet come across..." Practical Motorist

- Economy - save petrol by improving your driving technique and improving the tuning of your car
- Performance - dynamic checks on time to improve performance and economy
- Security - protect your car by disabling the ignition. Enter a personalised combination to restart
- Attractive, easy to fit, easy to operate - comes complete with all parts needed. Full instructions provided
- Imperial or metric read outs

The 'Tracker' car computer has been specifically designed as an integral part of your car dashboard. using highly accurate speed and petrol flow sensors it allows you to improve the fuel efficiency of your car by providing information on fuel consumption and tuning.

In all over 30 functions including estimated time to arrival, fuel needed to complete a journey, speed needed to meet an arrival time, acceleration tests, standing quarter miles and many more.

'Tracker' car computer available at £88.50

Or as an easy-to-assemble kit of parts at £78.50

The ignition cut-out unit is optional at £7.75


All prices include VAT. Allow £1 post & package. Goods by return:

PIMAC Systems Ltd

20 Bloomfield Road, Moseley, Birmingham B13 9BY
Tel: 021-449 0384

The MINIBENCH* System

CAN YOU
AFFORD
TO BE
WITHOUT
ONE?

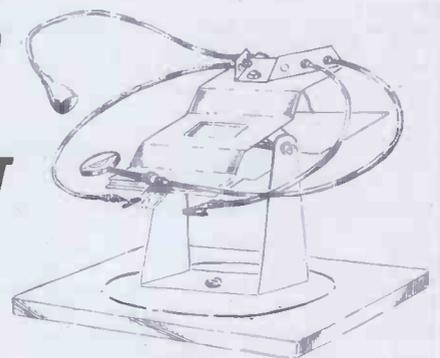

*Trade Mark

Pat App for

For details & price lists see March issue or write:-

ABSONGLEN LTD

Dept. EE4

P.O. BOX 13, HEREFORD, HR1 1EA

Owen Bishop

CM100 CIRCUIT MAKER REVIEW

Can you resist this new photo-etching kit?

IT EVOKED the atmosphere of a Christmas Day many years ago, the day on which I was given my first chemistry set. Today, the postman dumped this enormous package on the doormat and I was soon picking over the exciting assortment of items inside. In some ways the CM100 Circuit Maker is a chemistry set, for there is a lot of chemistry in the process of making a PCB by photo-etching techniques. But instead of the slightly squashed cardboard box full of logwood chips (do they still have those in modern chemistry sets?) and the little packet containing six strips of rather blotchy litmus paper, I now had in my hands a bottle of photo-resist etchant crystals and a packet of autopositive film. Then there were all the fascinating variety of bits and pieces (what's that for? And what on Earth is *that* for?) one hopes to find in a really good kit. And it turned out that this kit contains everything that you need for making your own photo-etched PCBs, even including a couple of high-speed twist drill bits for making the holes in the board after it is etched.

Why PCBs?

Before going on to discuss the process in detail and the merits or otherwise of this kit, let us look into the question of why we use PCBs at all. At some time between the arrival of my chemistry set and the arrival of the CM100 kit there was the arrival of the PCB, an invention that was hailed as a major break-through in electronics construction techniques. Until then all electronic circuits had to be laboriously hand-wired. This meant long assembly time, high labour costs and a high rate of defective circuits due to wiring mistakes, bad joints and all the other bugs which attend hand-wiring. The great advance of the PCB was that it was now possible to virtually print them by the tens of thousands; all exactly alike and free from defect. All that had to be done was to drop the components into the holes and solder them in place. The new technique meant lower labour costs, more rapid production and fewer faults. It lent itself to automation of the assembly of electronic circuits and has been a prominent factor in the lowering of their price, coupled with the improvement in specification and performance over the past few decades.

The PCB owes its success to the demands and rewards of mass production. It seems strange, therefore, that it has found favour with the lone hobbyist who rarely builds more than one device of any given design. There are several reasons for this:

1) It gives the amateur's product a professional appearance. But we don't expect a home-cooked apple pie to look or taste like a factory-made one, and would be rather disappointed if it



did! So is this a valid reason?

- 2) It makes it easier for firms to mass-produce PCBs of popular designs published in magazines such as HE, and sell them to amateurs who are too busy (or lazy?) to make their own. Without decrying the excellent service these firms render to their thousands of customers, my personal view is that using ready-made PCBs almost reduces electronics construction to the level of painting by numbers.
- 3) Editors of magazines prefer them (I'll have to be very careful what I say here!). Once a master overlay has been drawn, and a prototype built using that master then, if the prototype works, all other models built using that master will work. At least, all the connections will go to the right places and odd effects dependent upon component layout (eg, inter-lead capacitance) will be the same for all. It is notoriously difficult to ensure that a circuit diagram or strip-board layout drawing is entirely free from errors, but a verified master overlay can be reprinted in a magazine without error of any kind. This is a valid reason for favouring PCBs, but is it sufficient to account for their wide popularity?
- 4) It's fun. For me, it is reason number four which counts. I'll leave you to make your own choice, or to think up some other reasons of your own!

Making PCBs

Having found a PCB design in a magazine, or having designed one of your own, how can you get it on to the copper-clad board, ready for etching? Except for the very simplest of circuits, the hand-drawn design using a special resist pen or nail-varnish is almost out of

the question. Most circuits rely on at least one IC and it becomes very difficult to lay out the terminal pads with sufficient accuracy. The use of rub-down etch-resist transfers does a lot to improve appearance, gives accurate registration for ICs and edge-connector patterns, and makes it possible to cram lots of narrow tracks into a relatively small space. In an hour or so you can copy a published design on to your copper-clad board and have it ready for etching. This is the method I have used for several years with very satisfactory results. There really is a sense of achievement when the board is done and this is even more the case when working out one's own designs. The preliminary laying out of the main components, followed by the art-work with the transfers are something a little different from the usual run of electronics construction techniques. They are a refreshing change, though there is always the worry of making a mistake which can not easily be corrected once the board is etched. Unfortunately, thorough checking before etching does not necessarily reveal all the errors!

Copying by photographic means is a little more complicated and requires more equipment. It costs more to set yourself up with the equipment, but remember that this kit includes expendable materials such as a plentiful supply of double-sided copper-clad fibre-glass boards and the chemicals for etching, which you would have to buy for any method of PCB production. The special equipment costs relatively little.

It takes longer to produce a board by photo-etching than by other means, though if you also have photography as a hobby (developing your own film and making your own prints, I mean, not

simply snapping away and sending the film to Kodak!), you will find that the processing of the film and the resist-coated board are already familiar. A reasonable degree of judgement is required, but the process is not over-dependent on this. It is certainly an interesting procedure and gives yet another dimension to that fabulous hobby, electronics.

There is the advantage that once the master film is developed, you can produce dozens or hundreds of identical etched boards. You will probably not find this feature of benefit, unless you are intending to enter the PCB business, but a friend might appreciate a copy of one of your boards, on occasion.

One advantage of the photo-resist method is that the master drawing can be made on plain white paper. You can draw with pen and black ink, and use rub-down transfers for the more complex items. It is much easier to do this than to work directly on a copper surface as with the ordinary rub-down method. For instance, there is no need to worry about keeping greasy fingers away from the copper. If you make a mistake, you can easily correct it by scraping away the transfers or whitening out the error with Tipp-Ex or Liquid Paper. If a mistake is discovered *after* a board has been etched you do not have to start all over again, as with the rub-down-on-copper method. You simply modify the original master drawing (no need to re-draw the whole thing unless you have made a really ghastly error) and then quickly make a new photo-positive copy of this and etch a new board. The same applies if you subsequently improve the design. The original master drawing can be revisited to provide the master drawing for the improved version.

The Kit

The discussion above is intended to help you to decide whether or not you wish to delve further into the subject of photo-resist etching. If you have already decided that it is not for you, then please read no further. If, as is likely, you are keen to find out more, or are still undecided, read on. We will look at the CM100 kit in particular, to see how well it caters for the process and, in doing so, describe the main steps.

The kit is packed in a strong cardboard carton, well able to stand up to the ravages of postal transport and suitable for storing all the items of the kit before and after use. Inside, there are a number of stout cardboard trays to hold the various items, to make sure that they all stay in place and remain undamaged during transit. Some items are packed in plastic envelopes and the processing solutions are in five plastic screw-topped bottles. Each has an inner plastic plug to keep the bottle securely sealed during transit. The solutions are all concentrates, so the kit contains enough for making plenty of boards. The photoresist developer is a solution of sodium hydroxide (caustic soda) but, for safety, this is supplied in its bottle as a quantity of sodium hydroxide flakes. You are required to prepare the solution by adding water (more about this later).



The sleeve around the carton carries a full list of contents. One section of it is printed as a work-chart suitable for mounting on your workshop wall. It summarises every stage of operations, including what to do with everything at the end of the session.

Making PCBs by this method is done in four main stages. The first of these is drawing the master. You can do this on paper, using pen and black ink, rub-down transfers or any other method which produces a sharp black-and-white result. You could also make the drawing on transparent film. Alternatively you can, as I did for this review, cut a PCB design from a magazine. At this point the kit takes over.

Making the Film

This consists of making a copy of the master drawing on positive film. The copy is the same size as the master, and is a positive copy, not a negative. In other words, the tracks and pads (black on the master) come out black on the film. The kit includes a supply of auto-positive film and a special frame for holding the film and master in contact. You do not need a dark-room. You can work in an ordinary kitchen with curtains drawn during the day, or with artificial light coming through an open doorway from an adjacent room at night. The film is exposed by placing it face-down on the master (reflex printing) and exposing it to the light from a photoflood lamp (included in the kit, but you need to supply the lamp-holder, flex and plug). Full instructions are given in the manual supplied with the kit, which includes several trouble-shooting charts. It tells you how to find the correct exposure by exposing a test-strip and special test-strips are included in the packet of film (you see? They have thought of everything! — well almost). Having found the best exposure time, you can then expose a piece of film cut to the same size as the PCB design. A full sheet of film measures 100 mm x 160 mm (Eurocard size), so this is the

largest size of board that can be made with this kit. The boards provided measure 127 mm x 160 mm, thus allowing extra at the long edges for mounting the boards.

Processing the exposed film follows the normal photographic sequence of developing, rinsing and fixing. Development time depends on temperature; there is a liquid crystal thermometer in the kit and using this I found it easy to ascertain the correct time for development and soon had a crisp, high-contrast copy of the master design drying beside the sink. Incidentally, the kit includes developing dishes, film, forceps and plastic gloves (substantial ones, not the flimsy throw-away kind supplied with home perm kits).

Should the clear areas of the positive show a slight mistiness, this may be cleared by treating the film with the special Clearing Solution. The film may then be set aside to dry.

Photo-resist

At this stage it is necessary to prepare the boards by coating the copper with a photo-resist. This comes as a blue solution which is applied to the cleaned and scoured copper surface using a plastic sponge applicator. Coating must be done in a semi-darkened room and the coated boards must be stored in a light-proof box. Coating was the operation I found most difficult — especially obtaining an even coating. However, this would probably become easier with practice; if I failed to improve it is possible to buy boards already coated with resist, though these are rather more expensive than ordinary boards. You can coat several boards at once and keep them for several months.

Making the PCB

When the film and coated boards are dry, the next step is to find the correct

**TROUBLE SHOOTING CHART FOR PRODUCTION
OF PRINTED CIRCUIT BOARDS**

FAULT	CAUSE	REMEDY
1. PHOTORESIST WILL NOT 'TAKE' ON PARTS OF BOARD	GREASY PATCHES ON COPPER, PROBABLY CAUSED BY HANDLING	CLEAN BOARD THOROUGHLY. AVOID TOUCHING SURFACE BEFORE COATING
2. DIRT BURIED IN PHOTORESIST COATING	(a) SURFACE OF BOARD DUSTY BEFORE COATING (b) DUST SETTLING BEFORE PHOTORESIST COATING DRY	(a) INSPECT BY OBLIQUE LIGHT. CLEAN WITH LINT-FREE CLOTH (b) DRY IN DUST FREE CONDITIONS
3. BACKGROUND WILL NOT CLEAR COMPLETELY	(a) UNDER EXPOSURE (b) DEVELOPER EXHAUSTED (c) DEVELOPER COLD	(a) GIVE MORE EXPOSURE (sometimes an under-exposed result can be saved by slightly increasing developer concentration). (b) CHANGE DEVELOPER (c) WARM TO 20°C
4. PARTS OF COPPER WILL NOT ETCH	(a) UNDER EXPOSED PHOTORESIST (b) CONTAMINATED BOARD	SEE 3a) ABOVE SEE 1 ABOVE
5. COPPER TRACKS BROKEN AND RAGGED	(a) FAULT ON FILM MASTER (b) PHOTORESIST COATING TOO THIN (c) GROSS OVER EXPOSURE OR FILM MASTER NOT DENSE ENOUGH (d) DEVELOPER TOO STRONG	(a) INSPECT AND CORRECT (b) APPLY THICKER COATING (c) REDUCE EXPOSURE — THIS MAY ALSO 'SAVE' A THIN FILM MASTER (d) USE WEAKER DEV. AND/OR SHORTER TIME.
6. COPPER SPECKS BETWEEN TRACKS AFTER ETCHING	(a) DIRT ON EXPOSURE FRAME GLASS OR FILM MASTER (b) DIRT IN PHOTORESIST COATING	(a) CLEAN GLASS OR SCRAPE SPOTS FROM FILM MASTER (b) SEE 2 ABOVE.
7. PHOTORESIST COMES OFF COMPLETELY IN DEVELOPER	(a) PHOTORESIST 'FOGGED' BY TOO MUCH EXPOSURE TO ROOM LIGHT OR DAY-LIGHT BEFORE OR AFTER EXPOSURE (b) DEVELOPER TOO STRONG (c) BADLY CONTAMINATED COPPER SURFACE	(a) THE COATED BOARD SHOULD BE PROTECTED COMPLETELY FROM DAY-LIGHT OR STRONG FLUORESCENT LIGHT (b) FOLLOW RECOMMENDED DILUTION (c) CLEAN BOARD THOROUGHLY AND RINSE. TRACES OF DEVELOPER OR ALKALINE ON THE BOARD BEFORE COATING WILL ALSO GIVE THIS EFFECT.

exposure for the photo-resist. A coated board is used for this; its coating can be removed after the test and the board reused. The resist is sensitive to ultra-violet radiation; you can use a UV lamp or place the exposure frame outdoors in sunlight. I used sunlight and found that an exposure time of 20 minutes was correct. During this time the film is held in contact with the coated board — make sure the film is placed emulsion-side down on the board!

On the first time of use, the resist-developer solution has to be made up. Although the manual and the labels of each chemical container prominently display warnings of hazards of a general kind ("avoid eye, mouth or skin contact", "keep out of reach of young children"), there was no reference to the specific hazard of adding water to the sodium hydroxide flakes. When sodium hydroxide dissolves in water, a large

amount of heat is generated and the solution becomes very hot; in fact the bottle could become too hot to hold and this should have been mentioned in the manual. Luckily I was prepared for this event and added the water gradually, keeping the solution cool by holding the bottle under a running cold tap. The instructions stated that the cap of the bottle was to be screwed on securely, so I did this. When the cap was released the expansion of the air inside the bottle caused an outrush, carrying with it a spray of droplets of caustic soda solution. This could have damaged clothing or furniture if I had not been holding it in a sink at the time. Here we have an example of the present pre-occupation with blanket warnings covering unlikely events (such as the 1 person in 10000 who might have a skin allergy to one of the chemicals) or events which should not occur (such as bringing up children

who think it within their rights to fiddle with anything placed within their reach) while overlooking a real source of danger. It is a case of 'crying wolf'; my chemistry set had no blanket warnings yet I never came to grief! In this instance, the making up of the developer solution requires full specific warnings, especially as the identity of the solution is not disclosed. Adding water to flakes generates excessive heat; to avoid overheating, the flakes should be added to the water, a few at a time. But do not touch the flakes with bare fingers!

Once the board is exposed, it is developed for a few minutes. This removes the resist from the exposed areas (between tracks and pads), which show up as bright copper. The unexposed areas remain covered and the resist becomes black. I found that the recommended development time was rather short and that it could be trebled or quadrupled to clear the copper area completely without danger of removing the resist from unexposed areas.

Etching

The CM100 kit includes a complete PCB etching kit almost identical to the Seno System which was reviewed in HE earlier this year. I have used the Seno System for several years with good results; it avoids any handling of the ferric chloride etchant, which is very corrosive, allowing the process to be safely carried out in the kitchen. As in the Seno Kit, the CM100 kit includes a pack of neutraliser for solidifying the exhausted etchant solution; the instructions for safe disposal of the spent etchant were comprehensive, and included clear warnings of all possible hazards.

After cleaning the etched boards of photoresist, you coat the copper with the flux laquer provided. This refinement protects the copper from atmospheric corrosion and also assists the flow of solder when the components are being mounted. All you have to do then is to drill holes for the components and terminal pins (bits provided) and a perfectly etched board is ready for receiving the components.

Summing Up

This is a most comprehensive kit with clear step-by-step instructions. It can be considered to be good value for money. Any person capable of assembling an electronic circuit should be able to use the kit effectively and safely and enjoy this new aspect of the hobby. Although the process involves more stages (which at least gives you something extra to do to occupy your spare time) it has several advantages over the other methods of PCB preparation.

The CM100 Circuit Maker kit is manufactured and distributed by Electrolube Limited, Blakes Road, Wargrave, Berkshire RG10 8AW. Phone Wargrave (073 522) 3014. Contact them for the name of a retail supplier near you. Recommended retail price is £69.95 including VAT and handling. Our thanks to Electrolube Limited for supplying the kit which was the subject of this review.


Selected stages in the production of printed circuit boards using the CM100 Circuit Maker kit.




Exposing the auto-positive film to produce a film positive master. The circuit layout can be from a publication, or your own design.



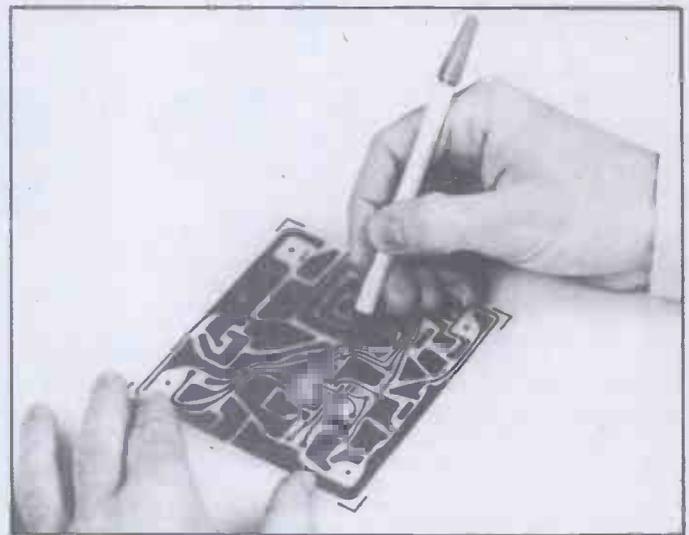
Developing and fixing the positive master film.



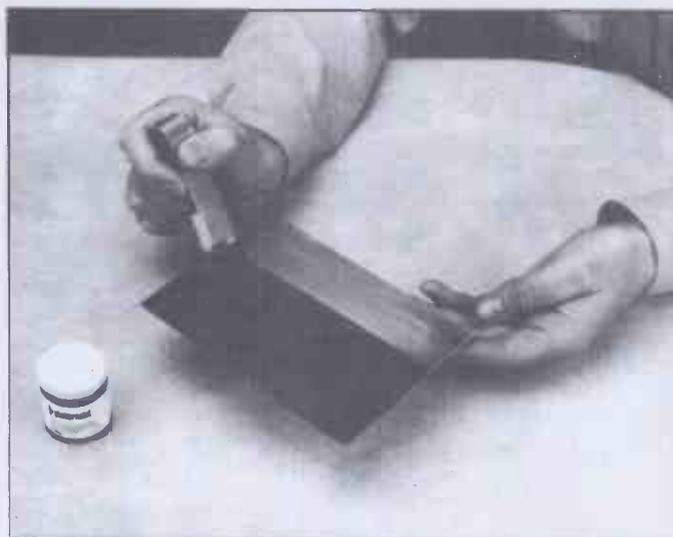After cleaning, small flaws can be touched-up with the retouching pen.



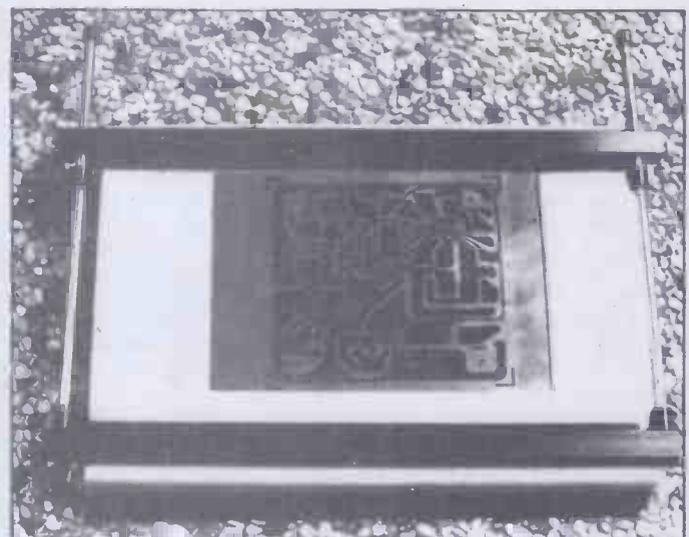
The copper-clad board is cleaned and the photo-resist solution wiped on with a sponge applicator.




The film master and resist-coated board are exposed to transfer the layout to the PCB.



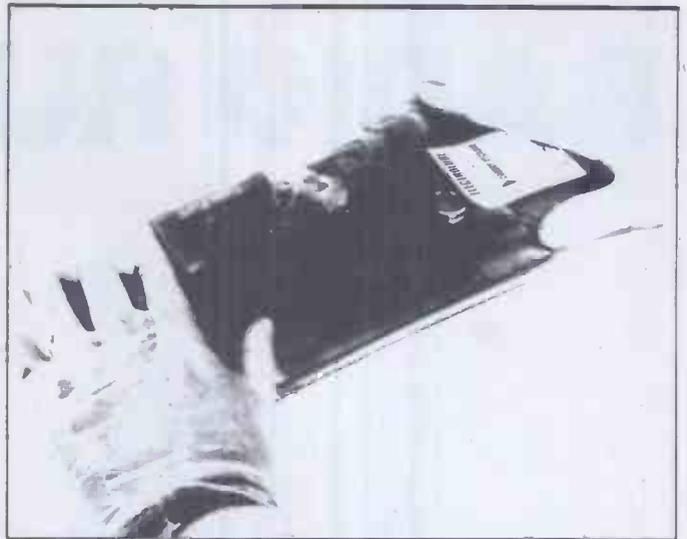
The exposed board is developed to reproduce the circuit layout.




Etching the board in the sealed bag.

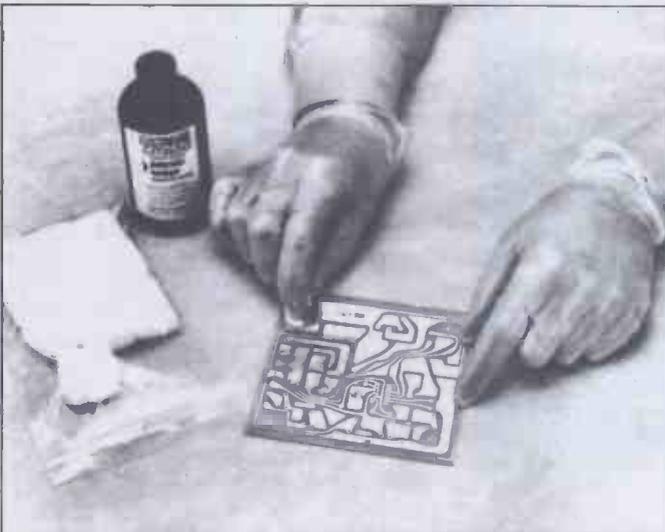

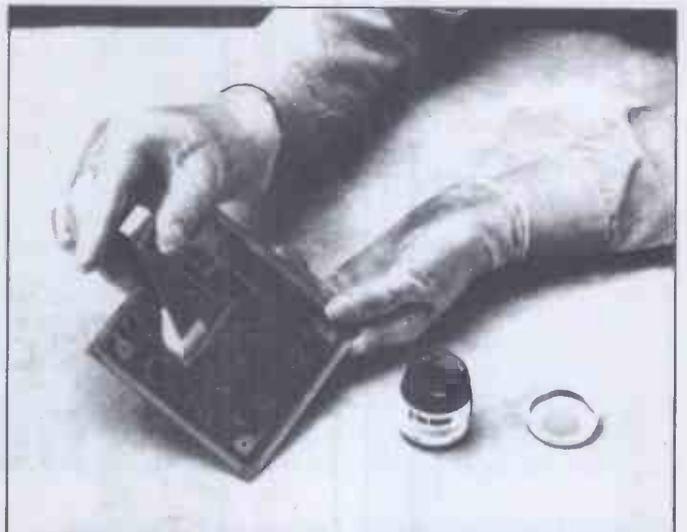After etching, the board is washed and dried and the remaining photo-resist is removed to expose the copper tracks.



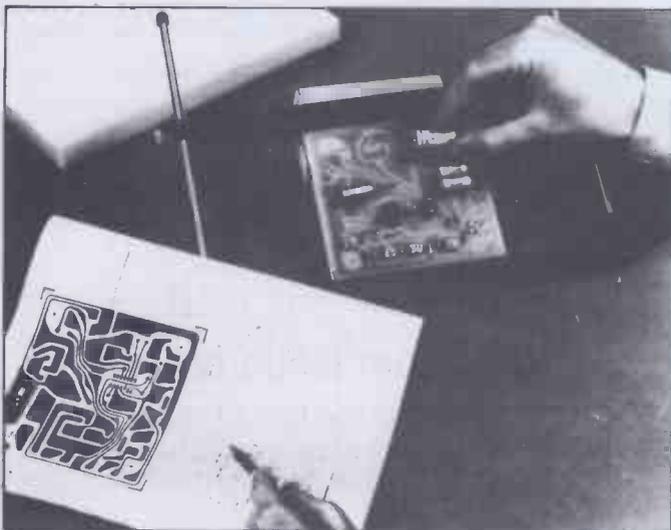Coating the copper with a protective laquer/solder flux solution.




The universal exposure frame doubles as an assembly jig for mounting components.



Finally, the component leads are cropped, ready for soldering.

RADIO RULES

Ian Sinclair

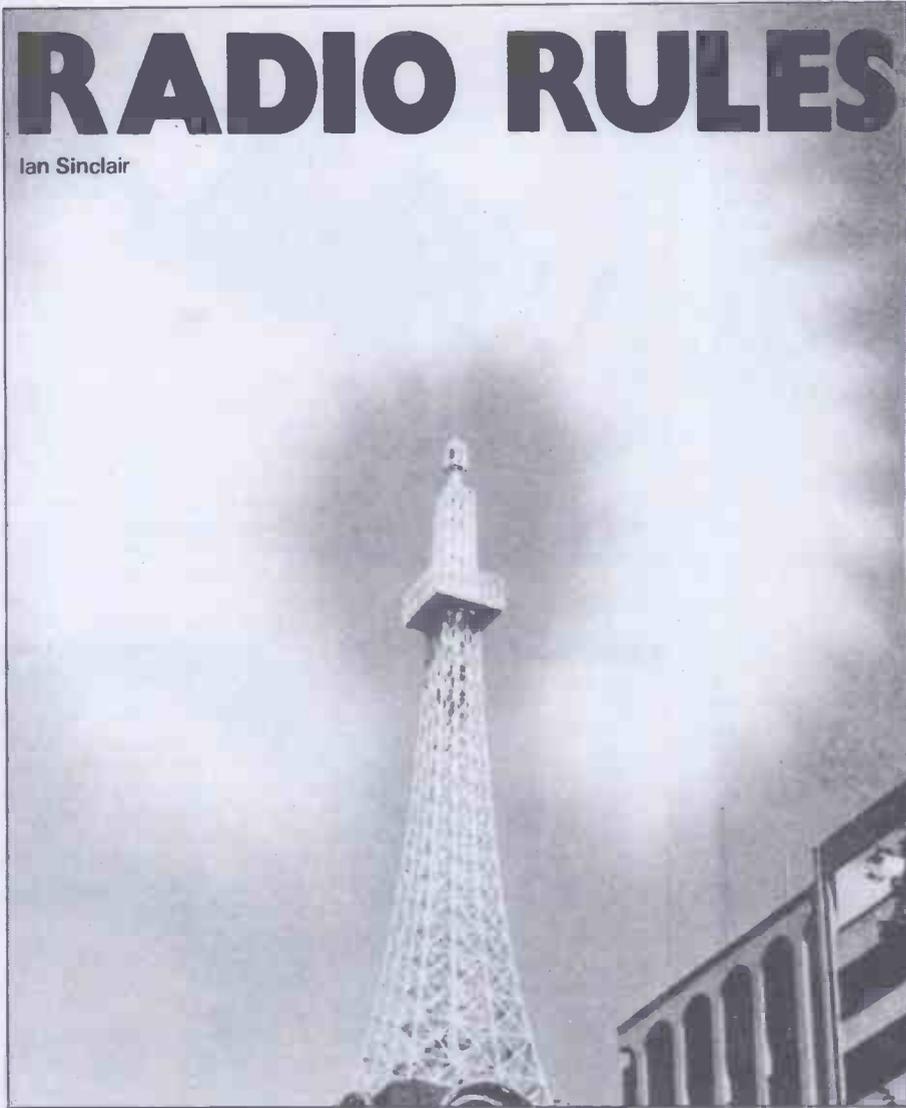

Modulation and other matters

NOW we're getting a bit closer to real radio! This month, we're going to look at AM transmitters; how they work, and what's involved. We'll kick off with a block diagram, Figure 1.

It shows a master-oscillator, which could be crystal controlled if you are operating on one frequency only, but is more likely to be variable so that you can use a number of frequency bands and be able to shift frequency within a band, to avoid interfering with somebody else. The master oscillator may be followed by buffers and multipliers, to generate the correct frequency. The signal which is to be modulated onto the carrier is your voice, so a microphone is the starting point for this signal, which is amplified and applied to the modulator. The traditional position for this kind of modulator is at the final output (power amplifier) stage, where the carrier is at its maximum amplitude.

It all looks fairly straightforward, as it was, once, but with the increasing use of radio wavebands, there are problems and restrictions which have been attended to. One restriction is 'input power', the maximum permitted DC power fed to the final amplifier (PA) stage for operation on the popular amateur radio bands (between

3.5 MHz and 29.7 MHz) is set by regulation at 150 W. This power level is more likely to be achieved by the use of valves, rather than transistors, in the PA stage, but it must not be exceeded. That's a legal restriction which isn't difficult to keep to—but some other factors are more of a worry. One major problem has been TVI (Television Interference), particularly on the older Band 1 frequencies between 45 MHz and 67 MHz, because these frequencies lie in the range of harmonics of the 14 MHz and 28 MHz amateur bands.

Harmonics, remember, are frequencies which are multiples of the operating frequency to which you are tuned, and these are generated in substantial quantities by any stage which is not operating in pure Class A conditions. Since the efficiency of a Class C final stage is a particularly attractive feature of an AM transmitter, the usual way of dealing with the TVI problem is by filtering harmonics from the output, between the final amplifier and the aerial. Filtering will also deal with another interference problem, pickup by stereo amplifiers—though a lot of this is due to poorly-designed and poorly earthed stereo equipment which would pick up anything around it!

The other major problem is frequency stability. The operating frequency of the transmitter must not stray outside the limits of the amateur bands, but even smaller changes of frequency are undesirable because they can cause the transmitter frequency to drift outside the bandwidth of a receiver. Your transmissions won't be popular if anyone who wants to hear them has to keep retuning his receiver! This isn't likely to happen with crystal control, but if you want to be able to roam over the amateur bands at will using a simple Variable-Frequency Oscillator (VFO) circuit which is not crystal controlled, frequency stability can be quite a problem. In particular, if you want to call up a station that you have been listening to, you will have to 'net' to its frequency—make your transmitter frequency approximately equal to his.

VFO Not UFO

A variable frequency oscillator is, therefore, an essential part of an AM transmitter for amateur use. Since the frequency stability of the whole transmitter is determined by the stability of the VFO, this a stage on which a lot of effort must be devoted

Circuitry is not the main problem. The traditional Colpitts oscillator circuit (Figure 2) is one which still gives excellent results, as do several other circuits, ancient and modern—but a good circuit is not the whole story. For the highest possible frequency stability, components have to be carefully constructed (eg inductors) or selected (eg capacitors) and the layout of


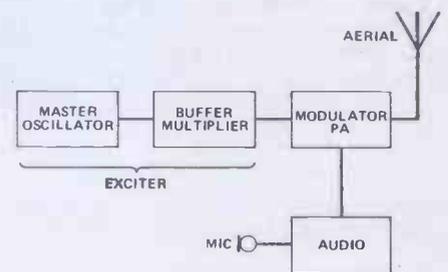


Figure 1. A simplified block diagram of an amplitude modulated (AM) transmitter.

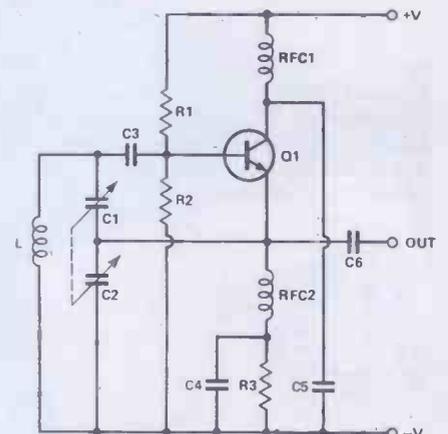

NOTES:
RFC1,2 ARE RADIO FREQUENCY CHOKES
C1,2 ARE CENTRE TAPPED GANGED VARIABLE CAPACITORS

Figure 2. A Colpitts oscillator, suitable for use as a VFO

the circuit must be good; considerable care is needed over the location of the VFO within the transmitter.

Basically, the frequency of the VFO is set, as we've seen earlier, by the L and C values of the tuned circuit. How can these vary? To start with, any change in the dimensions of the coil will cause a change of inductance, and thus a change of frequency. A self-supporting coil is unacceptable at frequencies below VHF because they carry a lot of turns, and even normally imperceptible vibration can cause the coil to behave like a spring, causing the oscillator output to be frequency-modulated by the vibration! Coils should be tightly wound on to low-loss formers, preferably high-grade ceramics, rather than being self-supporting. If the coil is wound really tightly, the turns will not shift as the wire heats and expands; it's not a bad idea to wind the coils with warm wire, so that the coils will tighten as the wire cools! If, however, you run the VFO section in a place where the temperature can be raised by, for example, a hot valve operating near it, then expansion problems are likely. Always use air-cored, as distinct from

ferrite coils (ceramic counts as 'air', in this context) because a coil with a metal or dust core does not have a constant inductance; the permeability of the core can be very greatly affected by temperature and less obvious effects, like sharp knocks.

Capacitance is the other half of a resonant circuit. Some of the capacitance is in the form of physical components and we need to select high-quality capacitors, such as silver-mica types. In addition, though, there are 'invisible' capacitors—the capacitance across transistor terminals, for example, which will vary as the temperature and the operating voltage change, and the stray capacitance in the circuit. The amount of stray capacitance is very much affected by the circuit layout and vibration can cause any such capacitance to vary; rigid construction, with short thick connecting wires, is very desirable.

One of the bonus features of the Colpitts oscillator is that the main tuning capacitors are placed across the transistor base-emitter capacitance, so that it is possible to arrange for these capacitors to have a value much greater than the transistor capacitance. When this is done, any change in the transistor capacitance has much less effect on frequency; the transistor capacitance has been 'swamped'.

We can still find that changes of frequency occur, however, as the circuit warms up. One reason is that silver-mica capacitors have a small positive temperature coefficient. This means that the capacitance increases as the temperature of the capacitor increases, there's nothing we can do to stop it. The only measure we can take is to connect a small ceramic capacitor in parallel with each silver-mica, because ceramic capacitors have a fairly large *negative* temperature coefficient, meaning that their capacitance values will *decrease* as the temperature increases. The type of ceramic has to be carefully chosen; some have a very large variation of capacitance with voltage, which can be troublesome to the extent of preventing oscillation if all the capacitance consists of such devices. One refinement, which can be helpful, is to use a stabilised voltage supply of the VFO.

If you are transmitting CW (Continuous Wave, ie morse code) it is not a good idea to 'key' the VFO, because the interruptions can cause frequency drifting. It is sometimes useful to make the VFO frequency as low as possible, because a low frequency is easier to keep stable. Against this, there is the fact that a low frequency VFO may need many stages of multiplication following it, and any change of frequency at the VFO will be multiplied, also. There's no easy way out! Finally, one last word on mechanical rigidity. One component which is very difficult to make sufficiently rigid is the tuning capacitor. Don't count your pennies here—buy the best you can get, because a vibrating set of plates on the tuning capacitor will make all you constructional efforts quite useless. If you are buying rather than constructing, look inside the case and check the construction round the VFO is rigid. Ask around—fellow amateurs will tell you in no certain terms if a make has a good reputation or not!

Buffers And Multipliers.

Our problems aren't over yet. The VFO signal must be passed on to the next stage of the transmitter. Any circuit connected to the VFO will have resistance (so that it draws current) and capacitance (so that it affects tuning) and so will affect the frequency of the VFO. If, in addition, it drains too much power from the VFO, it can cause very large frequency changes, even to the extent of stopping the VFO from oscillating. The stage following the VFO should, ideally, be a buffer operating in Class A, with high input impedance (impedance, not just resistance) and comparatively low output impedance. A typical buffer circuit is shown in Figure 3.

The VFO normally operates on the lowest frequency band that is to be covered, so that the higher band frequencies have to be obtained by frequency multiplication. As mentioned earlier, this is accomplished by operating a low-power Class B or C stage to generate harmonics, and tuning the output of the stage to the harmonic frequency that is desired. You didn't think that these amateur band frequencies came about by accident, did you!

Multiplication implies that a separate tuned circuit is needed, operating over the whole of the required band (unless you can adjust the multiplier tuned circuit each time you alter the VFO). The most usual method is to use a variable inductor (dust cored), tuned by stray capacitance to around the middle of the band, as shown in Figure 4. The really critical tuning problem is that of the VFO.

The Power Amplifier

The combination of VFO, buffers and multipliers is often known as the 'exciter' stage, because it exists simply to generate the frequency which will be used by the power amplifier (PA), the output stage of the transmitter. The design of most AM transmitters provides for modulation of this particular stage, so that PA and modulator can be considered together.

It's here that many of you may have to move into unfamiliar territory. Though transistors can offer useful output powers, very careful construction and design is needed for really high power output. The main problem with transistors is that even a momentary overload (one cycle!) can kill a transistor; valves are very much more tolerant. Overload for a transistor can be a current overload, blowing out a junction, a voltage overload, with the same effect, or a thermal overload, causing a junction to overheat. Transistor PA circuits demand a lot of attention to efficient heatsinks and mechanical construction, as well as to derating of the transistors. Derating means that the maximum power that a transistor can handle is greatly reduced when the transistor is working near its limits of frequency, voltage or temperature. This derating can be very considerable; a transistor which is rated at 40 W in ideal conditions (the conditions that the manufacturers quote—sometimes called infinite heatsink conditions) may be capable of 10 W or less under actual operating conditions. Features such as circuit layout and careful impedance

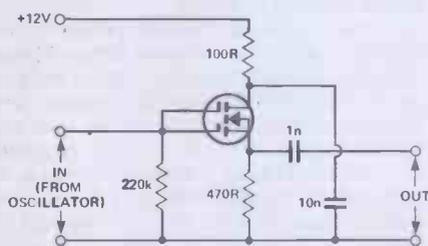


Figure 3. A buffer stage using a FET—this has very high input impedance so that it places very little load on the oscillator.

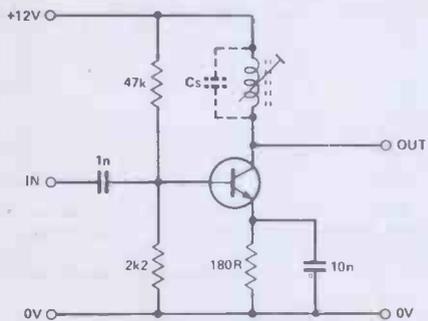


Figure 4. A frequency multiplier. The transistor bias has been arranged so that it is not quite conducting and it will square off the sine wave input, generating harmonics.

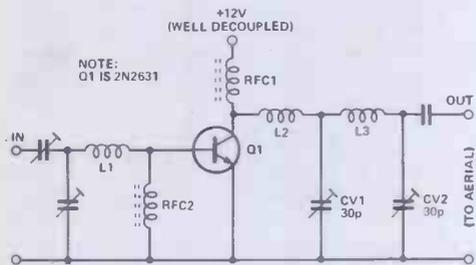


Figure 5. A simple low-power transistor PA stage operating in Class C.

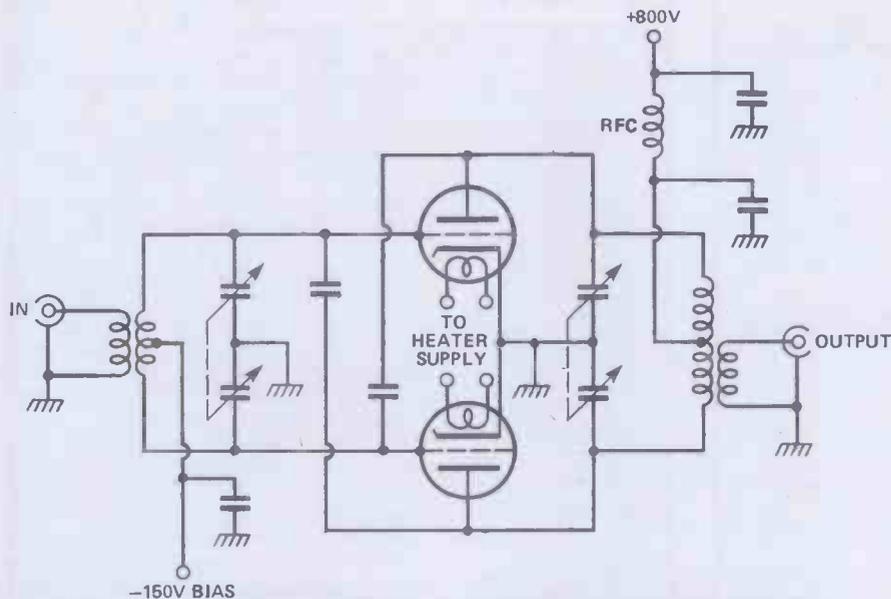


Figure 6. A high-power Class B transistor PA. The step-up and step-down auto-transformers are 4: 1 ratio and are wound on small ferrite cores, using only a few turns of wire.

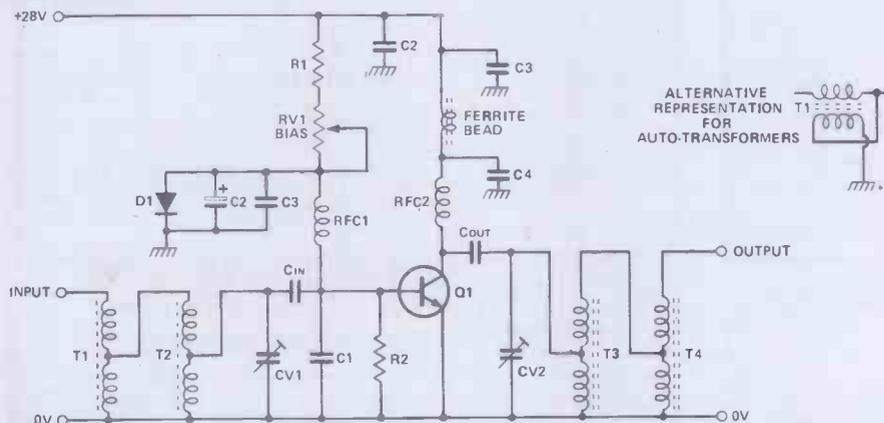


Figure 7. A push-pull valve output stage. Maximum permitted power can be easily achieved with a simpler one-valve stage.

matching of the PA to the aerial are very much more critical for transistor PA stages than they are for valve stages, because unless the RF power from the PA is all absorbed by the aerial, it will be reflected back and will cause overheating of the transistor.

Transistor Power Amplifiers

Transistors are particularly useful as power amplifiers for low powers (25 W or less) and where mobile operation is needed, since operation from a 12 V battery does not cause any design problems. The transistor type must be carefully selected because the construction of a transistor which is intended to deliver medium power output at high frequencies is quite different from the construction that serves well for audio frequencies. The US type of '2N' transistor coding gives no clue about the purpose of a transistor, whereas the European system is more informative; any transistor suitable for RF power will carry a set of code letters starting with BL, where B indicates silicon, and L means that the transistor is intended for RF uses. These letters may be followed by X, Y or Z, and then a number.

One important point of safety needs

to be stressed here: NEVER, under any circumstances, cut open a transistor of this type. One major problem in designing a PA transistor is heat dissipation; many designs make use of a remarkable material called beryllium oxide, which is a good electrical insulator but also a good conductor for heat (a combination usually said to be impossible).

Beryllium oxide, however, is one of the world's nastiest poisonous materials, especially if it's powered (as it would be if you were to saw through it). One speck of this substance in your lungs, and you should see to your last will and testament. In general, transistors which make use of beryllium oxide come with disposal instructions which specify where the defective transistor must be sent. Disregard this at your peril.

The lower the output power, the simpler the circuit, so for a few watts, circuits such as the one illustrated in Figure 5 can be used. The input is a series resonant circuit using the transistor's base-emitter capacitance as part of the series tuning capacitance. The output uses a choke load, with a filter of the type called a pi filter (from its shape, like a Greek letter pi), tuned to pass the frequency of transmission and reject harmonics—it's a

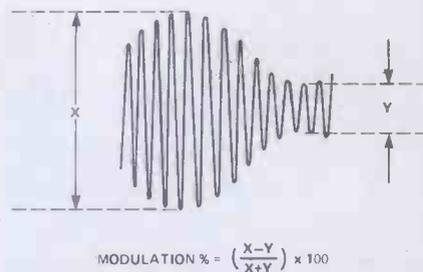


Figure 8. Calculating modulation index—this method requires the use of an oscilloscope.

low-pass filter, in fact. The pi filter also provides impedance matching between the output stage and the aerial.

Things start to get difficult when higher powers are needed. It is possible to get transistors which will operate at higher power levels in the lower frequency bands, but they are much more difficult to work with. To start off, the very large currents that flow when high-power transistors are used will call for well-stabilised and decoupled power supplies. At these current values, though, transistors have very low input and output impedances; unlike ordinary Class A preamp circuits, values of only a few ohms are common. We can't use the pi-network filter at these impedance levels, because the values of L and C that would be needed to match the low impedances would be highly impractical.

What has to be done, therefore, is to use matching transformers; wideband auto-transformers in fact, as shown in Figure 6. These step-down the signal voltage at the input and step up the current, so transforming the impedance to the correct level, and a similar device performs the opposite action at the output. The transformers are very different in construction from conventional AF, IF, or RF transformers, and usually consist of a few turns of wire with the primary and secondary wound together (bifilar winding) on a core, to ensure tight coupling. Their design and construction is one of the hardest tasks in all amateur radio so the beginner should stick to ready-made components—even with experience, you can become badly unstuck and lose a valuable transistor through mismatching, or find yourself causing disastrous interference.

Valve PA Stages

High power (150 W) PA stages using valves are so simple, by comparison with transistor high power stages, that it isn't surprising that most designers prefer valves for such purposes. There are complications, however, including the need for a comparatively high voltage power supply (350 V to 1000 V), and a heater supply which will require decoupling with low-resistance chokes and capacitors.

A typical high-power valve PA stage is shown in Figure 7. It uses a push-pull circuit of the type that can also be used for linear amplifiers for CB, in countries where this is permitted. The design is simple, and the inductors are straightforward to construct, with few really critical points of construction or of setting-up.

ELECTRONICS EMPORIUM

EASILY REACHED BY READERS IN YORKS & LANCS

Vast range of bargains in stock includes Diodes, Heat Sinks, Thyristors, Bridge Rectifiers, Resistors, Capacitors, Terminals, Connectors, Relays, Switches, Wire and Cable, PCBs, Transformers, Measuring Instruments, Nibbler and other Hand Tools.

Ex-M.O.D. Surplus: Cambridge A.C. Test Sets, Savage Amplifiers, Digital Voltmeters, Oscilloscopes, Oscillators, Power Supplies, Gyroscopes, Propeller Test Rigs and other equipment and components.

A.C. TOWNLEY LIMITED

Harehill, Todmorden,

Lancs OL14 5JY

(Off the A646

Todmorden—Burnley Road

Open Monday to Friday 8.30 a.m. to 5.30 p.m.

Saturday 9.00 a.m. to 1.00 p.m.

Tel: Todmorden 4931 (070 681 4931)

COMPUTER COMPONENTS

Part	1-9	10-49	50+	Low profile	
2101	1.16	1.04	0.95	DIL	Sockets
2114 200ns	1.05	0.95	0.85	Double	side wipe
4116 250ns	0.80	0.70	0.60	08 pin	0.07
4118 250ns	3.10	2.80	2.65	14 pin	0.09
4816 100ns					
BBC Micro	3.00	2.75	2.62	16 pin	0.10
6116 Rams	4.50	4.10	3.70	18 pin	0.12
6502	3.98	3.70	3.35	20 pin	0.14
2716 5 volt	2.20	2.10	2.00	24 pin	0.17
2716 3 rail	5.90	5.45	4.70	28 pin	0.20
2732	4.00	3.70	3.35	40 pin	0.30
2532	4.00	3.70	3.35		

Transformers & PSU's, Prices on Application

Mail Order, please add 45p p&p and VAT at 15%
Credit Card available soon

WOODFIELD SYSTEMS

1 Coedcae Road, Abertridwr, Caerphilly, S. Wales

Tel: 0222 830934 24 hour answering service

Goodmans Fane Richard Allan Celestion Altai

Multimeters & Accessories

UK P/P 65p or £1.00 for two
KRT 100 12 range pocket
1K/volt £4.95
NH55 10 range pocket
2K/volt £6.95
NH56R 22 range pocket
20K/volt £10.95
YW360TR 19 range plus hfe
test 20K/volt £14.95
5T303TR-21 range plus hfe
test 20K/volt £17.95
TMK500 23 range plus 12
adc plus cont. buzzer
..... £23.95



High Quality Speakers
8" 25W to 50W
10" 25W to 100W
12" 30W to 200W
15" 100W to 250W
18" 100W to 350W



PIELO ELECTRIC TWEETERS

PIEZO HORN TWEETERS
Up to 100 watts each. No external required. Flared Horns. Mid range Flared Horns. In stock now. Large range of speakers, public address equipment, microphone mikes, ham equipment. Heavy chromed Floor Stand. Boom Arm. Echo Chamber. Analogue Echo Chamber. £99.99

CROSSOVERS

2 way	100W	8 ohm
3 way	100W	8 ohm
4 way	80W	8 ohm

Power Amplifier Modules 100W to 200W

Stockists of leading makes of Disco Units & Lighting Equipment.

CITRONIC, FAL, TK, ICE, OPTIKINETICS, PLUTO.

SEND LARGE SAE FOR LIST
ALLOW 10 DAYS FOR DELIVERY

All prices include VAT at 15% Mail Orders welcome.

MUSICRAFT
303 EDGWARE ROAD,
LONDON W 2 ENGLAND
TELEPHONE: 01 402 9729 01 402 2898

CNC 10 PCB HOLDER

Ideal for small scale production, testing, research, service engineers, education and the home constructor.

The CNC 10 has a board capacity of 8" x 8" and longer boards (maximum 8" wide) may be accommodated since they can project beyond the ends of the rails.

Adjustment of the board rails is extremely simple and they are locked in the desired position by one central locking clamp. A further clamp enables the PCB, when in position, to be rotated through 360 degrees and locked in the required position.

An optional foam pad is available which enables a number of components to be inserted prior to soldering. Pad size 8" x 8".



CNC 10: £16.10 INC. VAT

FOAM PAD & CLIP: £5.64 INC. VAT

Please add £1.50 to cover postage.

Available direct from the manufacturer:

CARLTON NICHOL & CO. LTD.,

GOLDKEY INDUSTRIAL ESTATE,

KELVEDON, ESSEX

DESOLDERING TOOL Make life easy with this superb anodised high suction desoldering tool. Essential for desoldering multi hyphen lead e.g. transistors IC's. Especially handy for the experimenter and service engineer. Eliminating damage to PCB's and components. £4.45 + VAT Spare teflon nose 85p + VAT.

JAPANESE TRANSISTORS Equivalents available for most types. Please call, phone or write.

LOW COST VERSATILE MULTIMETER. THE MIGHTY MINI MULTI-TESTER. Ideal for beginner and service engineer (fits into shirt pocket) DC and AC voltage ranges: 10V, 50V, 250V, 1000V. DC current range 100mA. Resistance: two ranges 0-1M OHMS (60 OHMS CENTRE SCALE). DECIBELS -10 to 22 DB mirror arc scale. Overload protection, complete with battery leads and instructions. £5.65 + VAT.

ORDER FORM (ORDERS ON PLAIN PAPER ACCEPTED)

Name

Address

..... Desoldering tools at £4.45 = £

..... Spare Teflon noses at 85p = £

..... Mighty Mini Testers at £5.65 = £

Postage, packing and insurance at 60p per one device, 25p for each additional device £

Sub total £

Add 15% VAT £

I enclose cheque no/P.O. no.

Alternatively please credit my VISA/ACCESS/AMERICAN EXPRESS No.

Signature

This offer applies to UK only. Please allow 7-10 days delivery. Overseas customers please do not add VAT but allow to cover postage. TRADE ENQUIRIES WELCOME.

CRICKLEWOOD ELECTRONICS LTD.

40 Cricklewood Broadway, London NW2 3ET. Tel: 01-452 0161

NICKEL CADMIUM BATTERIES

	AA (HP7) 0.5Ah	SUB 'C' 1.2Ah	'C' (HP11) 1.65Ah	'D' (HP11) 2.0Ah	'D' (HP21) 4.0Ah	PP3 0.1Ah
1-24	£0.85	£1.38	£1.89	£2.25	£2.97	£3.79
25-49	£0.78	£1.28	£1.58	£2.10	£2.77	
50-99	£0.65	£1.24	£1.52	£2.02	£2.67	
100 up	£0.59	£1.15	£1.41	£1.87	£2.47	

All cells are brand new full spec devices from reputable mfrs. All Nickel Cadmium cells (except PP3) are supplied complete with solder tags and are 'VENTED' devices suitable for fast charge.

CHARGERS - single or dual O/P to charge PP3, AA or SUB 'C' cells in 12-14 hrs (chargers will charge 'C' and 'D' cells but with longer charging time). Units supplied complete in plug top case with flying leads. Number of cells (10 max) in series and type must be specified for each required O/P when ordering.

SINGLE O/P CHARGER £5.04
DUAL O/P CHARGER £5.72

TRANSFORMERS - as used in chargers 2 x 12 volt 0.25 amp secondaries 240V primary, tag connections £1.57 each

Data and charging circuits free with orders over £10 otherwise 30p post. P&P 10% if order less than £10, 5% if order over £10. Prices DO NOT INCLUDE VAT and this should be added to the total order. All advertised goods are ex-stock and normally despatched within 7 days.

Cheques, P.O.'s Mail Order to:-
SOLID STATE SECURITY,
Dept. (PE), Bradshaw Lane,
Parrbold, Wigan, Lancs.
Telephone 02576-3018.

MASTER ELECTRONICS NOW!

The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

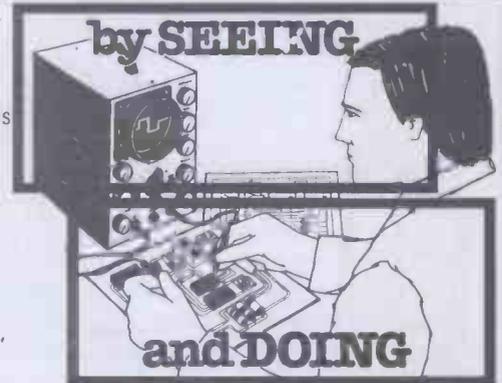

New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

HE/10/82

NAME _____

COURSE IN ELECTRONICS
as described above

ADDRESS _____

RADIO AMATEUR LICENCE

OTHER SUBJECTS _____

MICROPROCESSORS

LOGIC COURSE


POST NOW TO:

BLOCK CAPS PLEASE

British National Radio & Electronics School Reading, Berks. RG1 7BR

EXPO DRILLS

KITS TOOLS ACCESSORIES

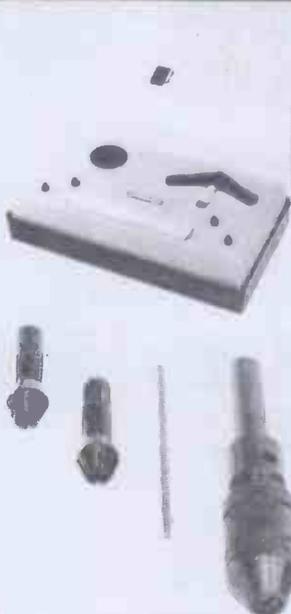

The Expo Pin Chuck and Wishbone Drill Sharpener are a must for all small engineering. The Pin Chuck comes complete with three Steel Collets and Tommy Bar, and the Wishbone with Eye Glass Gauge, Stone, and four Collets in attractive presentation box, competitively priced at £4.60. Incl. VAT, for the Pin Chuck, and £7.00. Incl. VAT, for the Wishbone, available from ourselves or any good Model Shop.


Why not send 35p for our illustrated Leaflet of Small Precision Drills, Burrs, Reamers, Grinder & Polisher, from 0.6mm to 3.0mm.

EXPO

Expo (Drills) Ltd. Clock Tower Works
Warsash, Southampton, Hants
Tel: Locks Heath (04895) 83966

NEW Quality Bench Power Unit Kit

Fully punched, two colour steel case

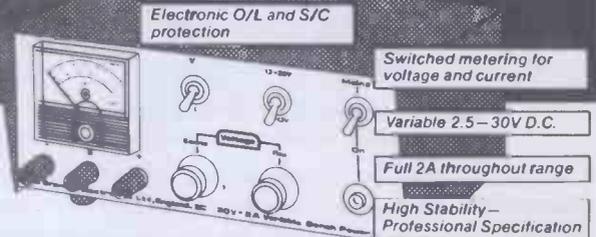

Build yourself this professional specification bench power unit. You will have a development tool as good as units sold to research laboratories and industry at more than twice the price.

The Kit comes complete with pre-punched, painted and silk-screened steel case, full assembly and setting-up instructions and every item necessary to complete the unit as shown.

Allow 14 days delivery
Send cheque or Postal Order to:

£35.00


+ £3.35 post and packing
+ £5.75 V.A.T. Also available fully built up and tested at £59
+ £3.35 post and packing
+ £9.35 V.A.T.



GRENSON ELECTRONICS LIMITED
High March Rd, Daventry, Northants,
NN11 4HQ. Telephone: 03272 5521



BACKNUMBERS

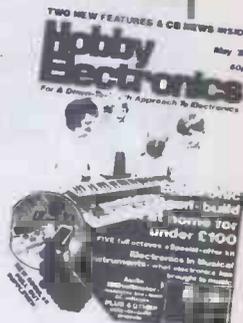

February 1980

Passion Meter, Win Indicator, Short Circuit Special, Kit Review Special, Into Electronics Construction Part 1.

September 1980

MicroMixer, Reaction Tester, Guitar Phaser, Development Timer, Teletext Explained, Into Digital Electronics Part 1.

April 1981

Pre-Amplifier Part 1, Super Siren, Guitar Tremolo, Russian Roulette Game, Doorbell Monitor, Anatomy of a Space Shuttle.

May 1980

MiniClocks, 5080 Preamp, Model Railway Track Cleaner, 5080 Loudspeakers, Loudspeaker Crossover Design, Radio Controlled Model Survey.

October 1980

Kitchen Timer, Tug 'o' War Game, Light Dimmer, Freezer Alarm, Intruder Alarm, Temperature-Controlled Soldering Iron.

May 1981

Electronic Organ, Voice-Operated Switch, Infra-Red Controller, Pre-Amplifier Part 2, Audio Millivoltmeter.

June 1980

Microbe Radio Control System, Egg Timer, Two Watt Amplifier, Fog Horn, Short Circuits, LEDs and LED Displays.

January 1981

Car Rev-Counter, Bench Amplifier, Sound-Into-Light Converter, Chuffer, Electronic Games reviewed.

June 1981

Power Amplifier Part 1, Continuity Checker, Envelope Generator, Early Radio, Gadgets, Games and Kits Supplement.

July 1980

Sound-Operated Flash Trigger, 18+18 Car Stereo Booster, Hazard Flasher, Electronics in Photography, Electronic Espionage, Piezo Electricity.

February 1981

Heartbeat Monitor, High-Impedance Voltmeter, Medium Wave Radio, Two-Tone Train Horn, Audio Signal Generator.

July 1981

Burglar Alarm, Doorbuzzer, Treble Booster, Electronic Aids for the Disabled, Power Amplifier Part 2.

August 1980

EquiTone Car Equaliser, Pass-The-Loop Game, Gaztec Gas Detector, OP-Amp Checker, In-Car Entertainment Survey, Introducing Microprocessors.

March 1981

Public Address Amplifier, Windscreen Wiper Controller, Bicycle Speedometer, Photographic Timer, Microcassettes.

August 1981

Electronic Ignition, Thermometer, Electronic Organ (final part), RPM Meter, Bench Power Supply, Radio Control Survey, Into Electronic Components Part 1.

All of the 1980 issues, except January and April, are still available together with the remaining issues from 1981.

All backnumbers cost £1.25 each. For those of you who only want copies of articles, we do offer a photocopying service. Each copy costs £1.25 and information as to its title and publication date should be given. Ordering backnumbers and photocopies could hardly be easier, just fill in the coupon, cut it out and send it to:

**Hobby Electronics,
145 Charing Cross Road,
London WC2H 0EE**

Please remember to mark your envelope with the service you require, **BACKNUMBERS** or **PHOTOCOPIES**, otherwise our mailroom won't like you.

HOBBY ELECTRONICS BACKNUMBER ORDER FORM

Please send me the following items:

NAME

ADDRESS

Back issues at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

HOBBY ELECTRONICS PHOTOCOPY ORDER FORM

Please send me the following items:

NAME

ADDRESS

Photocopies of in the

..... issue at £1.25 each

I enclose £.....

Cheques and Postal Orders should be made payable to ASP Ltd.

Breadboards

A simple wide-ranging VCO design.

THOSE of you that read last month's Breadboards will have noticed we're offering a financial incentive for any designs you send, and that are printed. Each circuit (with accompanying text) will earn you the princely sum of five pounds. So, whilst we're sorting out the best ones received so far, we've done a bit of head scratching and come up with some more circuits of the home grown variety.

This is a voltage controlled oscillator (VCO) with a wide frequency range, which uses a transconductance op-amp. The other is a logical probe or two, for checking states in TTL or CMOS circuitry. Both the probe's and the VCO need very few components, apart from the ICs, so they shouldn't take long to wire up. Furthermore, all three chips contain at least two devices, leaving you something to experiment with... and we want to see the results, remember!

A voltage controlled oscillator converts a varying voltage into a varying frequency — this principle underlies the operation of modern synthesizers.

Our VCO is based around half of the LM13600, which is a relatively new IC containing two operational transconductance amplifiers. Each amplifier features a control input, linearising diodes (allowing high input levels) and a push-pull output. These eliminate the need for complicated external circuitry, in most applications and this is certainly true of our circuit. It requires only seven other components and a control voltage (here taken from RV1 in series with R4 and D3) to operate as an oscillator in the range 25-1900 Hertz.

The frequency of the output is determined by the current passing through R3 into pin 1. This can be anything from a few microamps up to a milliamp or so, though the range will be restricted by other factors such as output power and supply voltage. Our VCO required a bias current of between 100uA and 1mA, provided by the potential divider RV1, R4 and D3 — the diode ensuring a minimum control voltage of 0V7. Negative feedback is supplied by R2 to the inverting input, pin 4. This controls the gain and therefore the output level. If you want variable output then replace R2 with a 10k resistor in series with a 100k pot. The non-inverting input is connected to two level clamping diodes D1 and D2, which prevent overloading from the positive feedback through C1. The value of C1 determines the range of frequencies that can be output, so you should experiment with different capacitors, to a few hundred picofarads.

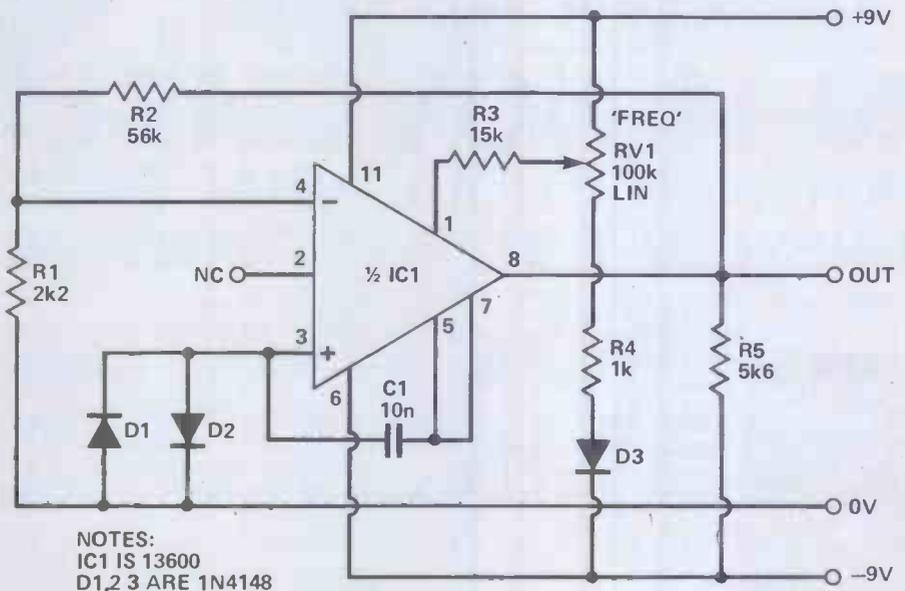


Figure 1. Circuit diagram for the VCO.


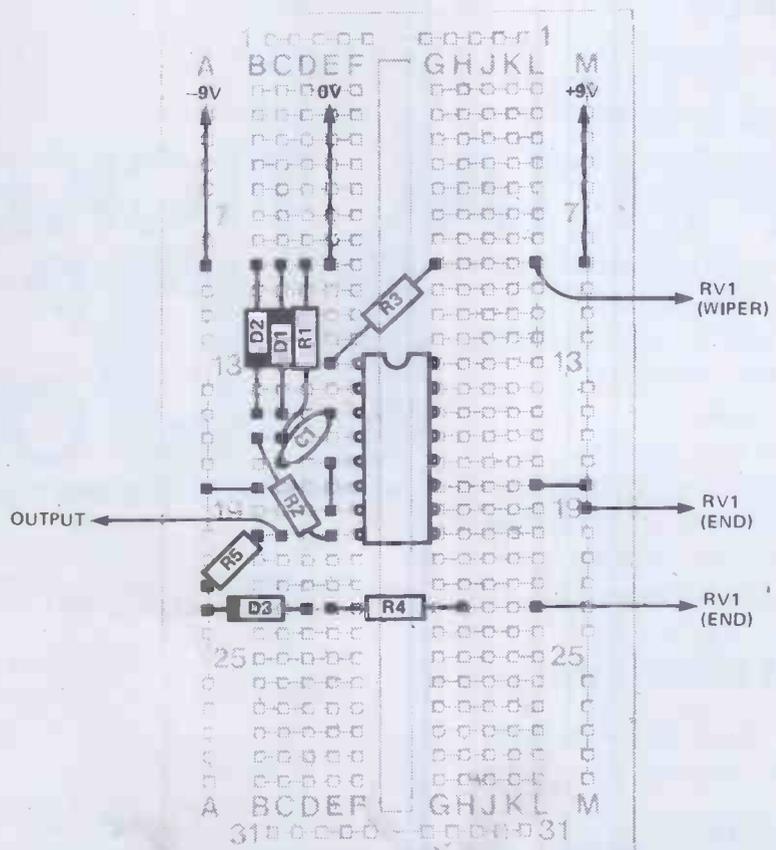
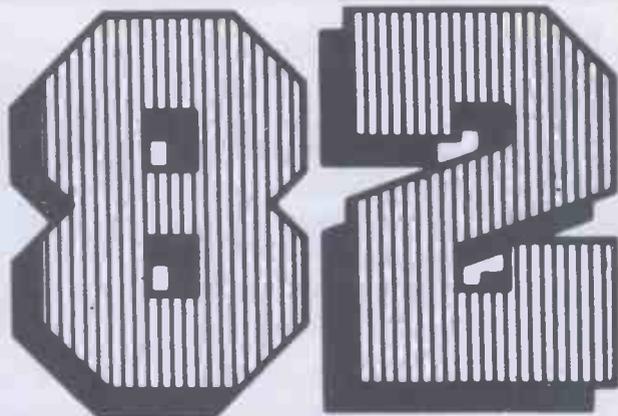



Figure 2. The breadboard layout for the Voltage Controlled Oscillator.

The 13600 can be powered from a wide variety of supplies in the range ± 2 to ± 22 volts. Current consumption in

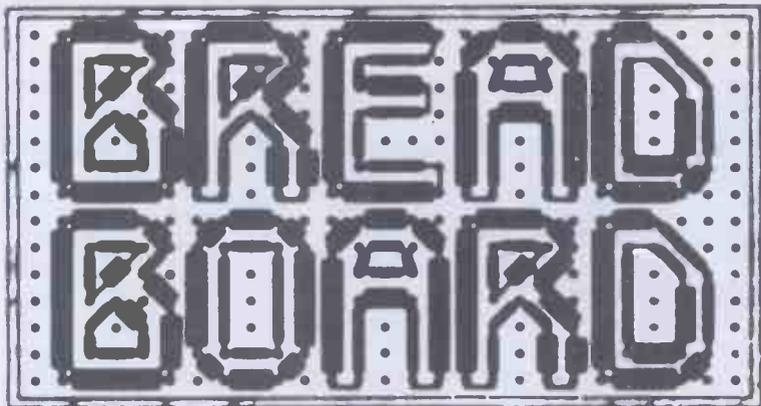our circuit (± 9 V) was around 6mA per rail; the output, 14 V peak-to-peak, is a flattened triangle wave.



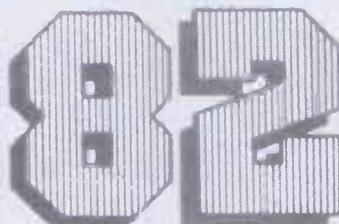10-14 NOVEMBER 1982 at:
ROYAL HORTICULTURAL SOCIETY'S NEW HALL
GREYCOAT ST, WESTMINSTER, LONDON SW1.



**MORE
COMPREHENSIVE
THAN EVER BEFORE:**

- ★ COMPUTERS
- ★ LOGIC
- ★ KITS
- ★ AUDIO
- ★ TEST GEAR
- ★ COMPONENTS
- ★ RADIO
- ★ C.B.
- ★ DEMONSTRATIONS
- ★ MUSIC
- ★ GAMES
- ★ LECTURES
- ★ MAGAZINES
- ★ BOOKS
- ★ SPECIAL OFFERS

SPECIAL TICKET OFFER

For the fifth consecutive year BREADBOARD is back with even more to offer electronics enthusiasts.

This is the best opportunity to update yourself on all the latest equipment, ideas and developments.

COME AND SEE THEM IN ACTION.

Book your tickets now at this special low rate.

50^p OFF BOOK NOW

(OFFER ENDS SEPTEMBER 30th)

SPECIAL ADVANCE BOOKING PRICE
ADULTS £1.50 — STUDENTS/SENIOR CITIZENS £1.

PLEASE SEND tickets @£1.50 and tickets @£1.
I enclose cheque/P.O. for


NAME

ADDRESS

.....

.....

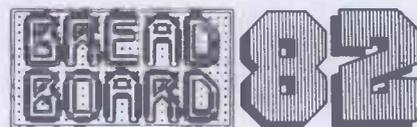Send to: BB 82, Argus Specialist Publications Ltd,
145 CHARING CROSS ROAD, LONDON WC2H 0EE.



THE EXHIBITION YOU CAN'T AFFORD TO MISS

MIGHTY NINETY PACKS

SUPER VALUE PACKS ALL AT 90p each

BUY SIX PACKS AND GET A SEVENTH FREE

Please add 20p per pack postage
Please allow 7 days delivery.

- | | |
|--|--|
| MN2. 200 $\frac{1}{2}$ & $\frac{1}{4}$ -watt Resistors. | MN36. 10 asstd switches, toggle, slide, micro etc. |
| MN3. 100 1 & 2-watt Resistors. | MN36. 10 sub-min SP, C/O slide switch. |
| MN4. 50 Wirewound Resistors. | MN37. 10 asstd audio connectors. Din phono etc. |
| MN5. 100 metal oxide Resistors. 1%, 2% and 5%. | MN40. 50 Polystyrene capacitors. |
| MN6. 12 asstd potentiometers. | MN45. 35 asstd diodes Zener, rect, signal, switching. |
| MN7. 25 asstd skeleton preset Resistors. | MN46. 15 asstd Zener diodes. |
| MN8. 50 asstd Electrolytic Capacitors. | MN48. 200 items 4BA asstd length screws, nuts & washers. |
| MN9. 100 asstd Ceramic Capacitors Pite. disc. tub and monolithic etc. | MN49. 200 items 6BA asstd length screws, nuts & washers. |
| MN10. 100 mixed capacitors. Polyester, Polystyrene, Metalised, Radial and Axial types. | MN50. 3 pieces of veroboard useful sizes, min total 35 sq inch. |
| MN11. 20 asstd Silver Mica Capacitors. | MN51. 10 x 0.2" red LED. |
| MN12. 8 Tantalum Bead Capacitors (useful values). | MN52. 10 x 0.125" red LED. |
| MN13. 20 asstd Transistors. BC, 2N Series + Power etc. | MN53. 20 x 0.1 mfd 25v ceramic disc caps. |
| MN14. 40 IN4148 Diodes. | MN54. 20 x 0.1 mfd 25v ceramic disc caps. |
| MN16. 20 min. wire-ended Neons. | MN55. 10 watt audio amp board with circuit. |
| MN17. 2 12-volt Relays. Ex nearly new equip. | MN56. 10 14 pin low profile IC skt DIL. |
| MN19. 15 P.C.B. mounting M.E.S. lampholders. | MN57. 10 16 pin low profile IC skt DIL. |
| MN20. 1 240-110 to 12-volt 100ma Transformer. | MN60. 10 asstd TTL IC's. |
| MN21. 1 240-110 to 24-volt 100ma Transformer. | MN63. 50 mixed polyester caps C280, Siemens etc. |
| MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green. | MN64. 5 Press to make min switches. |
| MN23. 300 asstd screws, nuts, washers, self-tappers etc. | MN68. 200 asstd veropins, turret tags, PCB pins etc. |
| MN25. 80 Assoc. rubber grommets. | MN69. 4 min push to break switch. |
| MN29. 75mts equipment, wire, asstd colours and sizes. | MN70. PCB with push SW with attractive chrome plastic knobs 1 x 80241, 1 x 8C300, 2 x 8C237, 1 x 8C204, 4 x 1N4002, 2 x CMOS 4025, 200mm fuse holder + 22 resistors, capacitors, diodes etc. |
| MN30. 3 x 2mm length, 3 core, mains cable. | MN71. IZN414 RADIO IC. |
| MN32. 15 30pF Beehive trimmers. | |
| MN34. 25 min glass reed switch. | |

CHORDGATE LIMITED

RETAILER SHOPS AT
75 FARRINGTON ROAD, SWINDON, WILTS.
Tel. (0793) 33877
21 DEPTFORD BROADWAY, LONDON SE8

Send for my CATALOGUE ONLY 75p

(plus 25p post/packing)

My VAT and post/packing inclusive prices are *the* lowest. All below normal trade price — some at only one tenth of manufacturers quantity trade.

See my prices on the following:

CAPACITORS . . . ELECTROLYTIC; CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR, PAPER BLOCK, CAN, POLY, MICA, CERAMIC. LOW AND HIGH VOLTAGE, RESISTORS. 1/8th WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS. FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE. DIDDIES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTORS, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS and others.

Prices you would not believe before inflation!

BRIAN J. REED

TRADE COMPONENTS

ESTABLISHED 25 YEARS
161 St. Johns Hill, Battersea, London SW11 1TQ
Open 11 am till 7 pm Tues. to Sat. Telephone: 01-223 5016

ALARMS

FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT

AT UNBEATABLE PRICES!

SEND S.A.E. OR PHONE NOW
FOR YOUR COPY
**THIEFCHECK BURGLAR
ALARM D-I-Y SYSTEM**

A.D. ELECTRONICS
DEPT ET1 10
217 WARBRECK MOOR
AINTREE LIVERPOOL
L9 0HW051 523 8440

THIEFCHECK
MAIN
DISTRIBUTOR



JOIN UP WITH LITESOLD

Litesold's new 'L' Series soldering iron — now at a bargain price. Outstanding performance. Lightweight. Easy to maintain.

Elements are enclosed in Stainless Steel shafts, insulated with mica and ceramic. Non-seize interchangeable bits, choose from 'copper' or 'long life'. A very special tool at a very special 'direct' price. Just £5.58 for iron fitted with 3.2mm copper bit. Just £2.40 for 3 spare copper bits (1.6; 2.4; 4.7).

A mere £4.38 for professional spring stand! Or buy the lot for £11.12! and save 10%.

All prices inc. VAT P.&P. Please allow 14 days delivery.

Write today. Send Cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN or phone 01-689 0674 for Barclaycard/Access sales.



£5.58

LITESOLD
LIGHT SOLDERING
DEVELOPMENTS LTD

INSTANT HEAT SOLDER GUN

ONLY £5.95



Tired of waiting for ordinary irons to heat up, but put off by high price of instant guns?

Now you can purchase a superb Instant Heat Gun for only **£5.95 plus £1.30 p. & p.**

† Money back if not delighted! †

Send Cheque or Postal Order for £7.25 for immediate despatch, to - Nash Smithfield Ltd., Mail Order Dept., 11 Victoria Road, Saltaire, Shipley, West Yorkshire Telephone 582967

RIDICULOUS RESISTOR SALE

$\frac{1}{2}$ watt carbon film resistors. 5% tol. High quality resistors made under exacting conditions by automatic machines. E12 range 1R0 to 10M0. Lot A. 1000 (25 per value). £8. Lot B. 500 (25 per value) £4.25. Lot C. 100 (25 per value) 90p. Orders over £5 post free. Otherwise postage 15p in £1.

100 PCB type RESISTORS. £2.50. Bulk purchase enables us to offer 1000 mixed preformed 5% tol. resistors of the carbon film type for PCB mounting. Huge range of preferred value £2.50 per 1000. 4000 for £8. Postage 15p in £1.

AC ADAPTORS. Ideal for powering small transistor radios and calculators. Input 240v. 50Hz. Output 6v 100 m.a. Fitted with calculator plug. Very compact. Should be £3. Our price £1.75. p.p. 25p. 2 for £3.25. 25 post free. 9v 150 m.a. version. £2.50 each. 2 for £4.50. Post free.

HAVE YOU SEEN THE GREEN CAT? 1000s of new components, for the hobbyist, including electronics, radio, audio, computers etc. at unbelievably low prices. Send 50p and receive list and FREE RECORD SPEED INDICATOR.

OVER £50 WORTH OF ELECTRONIC COMPONENTS AND ACCESSORIES FOR £12.50. With our JUMBO PACK. Contains transistors, caps, resistors, pots, switches, radio and electronic devices for £12.50. Carriage £2.50. Hundreds already sold.

MYERS ELECTRONICS

Dept H. 12
14 Harper Street, Leeds LS2 7EA. Tel. 452045
New retail premises open at the above address. Callers welcome 9 to 5.
Mon to Sat. (above Union Jack clothing store).

AMARAL Limited

26 Highfields, Earley, Reading RG6 2RZ
Tel: 0734 864745

Suppliers of
Microprocessors, Memories, Crystals,
Integrated Circuits (TTL LS, CMOS, etc.)
Resistors, Capacitors, ERG DIP Switches.

Send SAE for lists or phone for a quote

TRADE ENQUIRIES WELCOMED

Access and Barclaycard accepted

Cassette Decks & Heads/Quality Kits

HART Hi-Fi Kits are the best in the business — and have been for 20 years! We also stock some special and useful items like our SF925F Solenoid Controlled Deck Mechanism on the right — use it in HiFi or Digital Data projects, it can handle either equally well. Magic feature is the search in fast mode and the price is only £38.90 plus Vat.



Need a new or better CASSETTE HEAD? We have the best there are. Ask the manufacturers for a price first, then try us for a pleasant surprise.

Write or phone for YOUR free copy of our interesting list.

HART ELECTRONIC KITS LTD.

Dept C, Penylan Mill, Oswestry, Shropshire SY10 9AF.
Tel 0691 2894

Personal callers are always welcome but please note that we are closed all day Saturday.

BRYSTEP ELECTRONICS

10 Camphill Industrial Estate
West Byfleet, Surrey KT14 6EW
Tel: Byfleet (09323) 51676

CMOS	4066	£0.29	
4001	£0.10	4069	£0.15
4007	£0.15	4070	£0.15
4008	£0.47	4078	£0.18
4011	£0.11	4081	£0.14
4012	£0.16	4093	£0.28
4013	£0.22	4093	£0.35
4015	£0.90	4098	£1.44
4016	£0.19	4510	£0.48
4017	£0.38	4511	£0.45
4018	£0.45	4512	£0.50
4021	£0.40	4514	£1.19
4022	£0.48	4515	£1.20
4023	£0.16	4516	£0.59
4024	£0.32	4518	£0.36
4025	£0.16	4520	£0.59
4028	£0.48	4528	£0.54
4040	£0.48	4529	£0.70
4042	£0.48	4531	£0.55
4047	£0.58	4534	£3.98
4049	£0.22	4541	£0.98
4050	£0.22	4585	£0.90

D Connectors (Cannon Type)

9 Way	£0.80	£0.95	£0.90
15 Way	£1.10	1.50	£0.92
25 Way	£1.50	£2.00	£3.32
37 Way	£2.20	£3.25	£1.28

Rt Angle P.C.B. Mtg

9 Way	£1.17	£1.80
15 Way	£1.53	£2.32
25 Way	£2.20	£2.20
37 Way	£2.97	£4.20

Volt Regulators

7805	£0.39	IN4002	£0.04
7815	£0.39	IN4148	£0.02
LM309K	£1.30	IN5401	£0.15
LM323K	£4.88	IN5406	£0.16

Diodes

7805	£0.39	IN4002	£0.04
7815	£0.39	IN4148	£0.02
LM309K	£1.30	IN5401	£0.15
LM323K	£4.88	IN5406	£0.16

FREE With every order: 1 pack of 16 1/2 watt carbon film resistors

Sorry: MAIL ORDER ONLY
Please add £0.30 p&p and V.A.T.
@ 15%

SPECIAL OFFER FOR THIS ISSUE
LM323K £3.95 (1-24) £3.75
(25+) £2.716 (+5V) £2.15 (1-24)
£2.00 (25+) £2.332 £3.60 (1-24)
£3.45 (25+)

Many, many other items held in stock. S.A.E. for full stock and price list. Also separate list of items which are ex-Surplus/Liquidator stock, at bargain price. We fully guarantee your money back in FULL if any item fails, whether old or new, provided it is returned within 28 days of receipt. We have never had to return money yet.

TRAIN FOR SUCCESS

in Television, Radio & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics — now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Basic Electronic Engineering (C&G/ICS)
Radio Amateurs

Certificate Courses

TV & Audio Servicing
TV, Radio and Audio Engineering
Radio & Amplifier Construction
Electronic Engineering*
Computer Electronics*
Industrial Electronics*
Radio Frequency Electronics*
Introduction to Microprocessing*
Electrical Engineering*
Electrical Contracting & Installation

*Qualify for IET Associate Membership



Approved by CACC



Div National Education Corporation



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

FREE BOOK

Please send your FREE School of Electronics Prospectus

Subject of Interest _____

Name _____

Address _____

It's easy to complain about advertisements.

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.

ASA Ltd., Brook House, Torrington Place, London WC1E 7HN.




Dept. 265Z,
ICS School of Electronics
160 Stewarts Road,
London SW8 4UJ




01-622 9911
(all hours)


HE PCBs

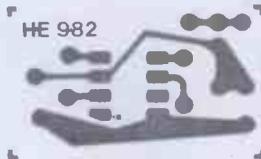

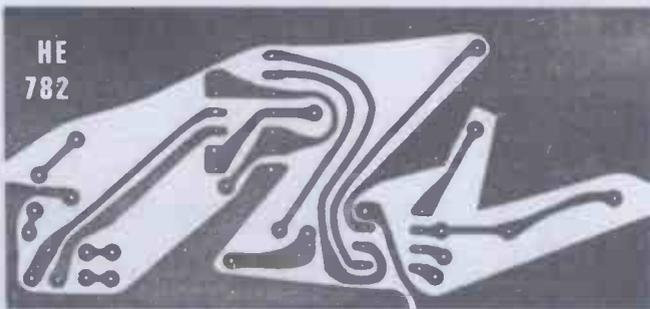Left: The foil pattern for the Negative Voltage Generator — mind you don't lose it!



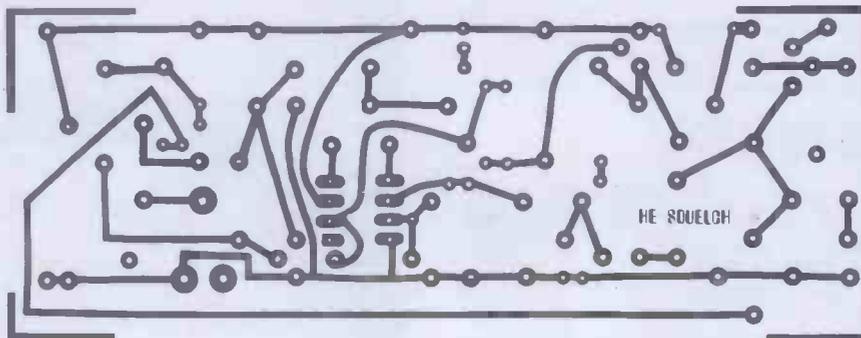The Flash Point Alarm PCB foil pattern (left) and the PCB pattern for the Squelch Unit (below). Both boards have tracks running fairly close to component pads, so make sure all the unwanted copper is etched away.





CLASSIFIED

 THE PATH TO

 SUCCESSFUL SALES!

01-437 1002

Ext 213

ADVERTISEMENT RATES

Semi-Display (min 2 cms)

 1-3 insertions £7.50 per cm

 4-11 insertions £7.00 per cm

 12+ insertions £6.50 per cm

 Lineage 26p per word (min 15 words)

 Box Nos. £2.50

Closing date 2nd Friday of the month

 preceding publication date.

All advertisements in this section must be prepaid.

 Advertisements are accepted subject to the terms and

 conditions printed on the advertisement rate card (available

 on request)

Send your requirements and cheque, P.O. 10:

HOBBY ELECTRONICS CLASSIFIED

 ADVERTISING, 145, CHARING CROSS RD,

 LONDON WC2H 0EE.

H.E. ORGAN KITS £99.50 inc. p&tp. 61 note

 keyboards £32.00. 13 note pedal boards

 £25.00 inc. p&tp. A.T. Hawkins, 23, Blenheim

 Road, St. Albans, Herts. AL1 4NS.

TELEPHONE ANSWERING MACHINE,

 build your own for under £10 plus any cassette

 recorder. Send only £1.95 for detailed circuits

 and plans. Dept. HE3, UNITECH (Midlands),

 FREEPOST, Sutton Coldfield, West

 Midlands, B74 2BR.

REMOTE TELEPHONE BELL KIT, switches

 on your siren, buzzer, bell, lamp etc. when

 the phone rings. Battery operated micro-

 power circuit draws negligible current from

 phone line. Complete kit including case and

 PCB only £9.95. Dept. HE3, UNITECH

 (Midlands), FREEPOST, Sutton Coldfield,

 West Midlands, B74 2BR. (Not British

 Telecom Approved).

ELECTRONIC GAMES, Burglar alarms,

 Data sheets. Build your own microchip

 circuits from our detailed plans. S.A.E. for

 details. G.H.T. Ltd., P.O. Box DR95, Dover,

 Kent. CT16 1UL.

KIA AMAZEING AMPLIFICATION

OPPORTUNITIES. *30W fibreglass power-

 amps £12 = £1.99 + V.C. — *100W Stereo

 To3 Chassis £28 = £10 + controls & sockets

 — 8 Cunliffe Rd, Ilkley.

METAL FILM RESISTORS 100: 80p, 200:

 £1.35, 500: £3, 1000: £5. P&P: 40p. T. Milner,

 203 Goodman Park, Slough, Berkshire.

SPECTRUM VENTURE. Exciting new game

 for the Spectrum. (7 games in 1). In colour,

 with sound & fantastic screen effects. 16K &

 48K version supplied on one cassette for £6.

 Bobker, 29 Chadderton Drive, Unsworth,

 Bury, Lancs.

SEND SAE for our catalogue details of Ads

 6809 single board computer IEEEES-100

 Standard. S100 Prom-Blaster, cluge card

 synthetalker etc. Also competitive prices for

 Linear, CMOS TTL and other kits. Micro-

 Times, 19 Mill St., Bideford, North Devon,

 EX39 2JR. Tel. (02372) 79798.

TELETEXT (ORACLE/CEEFAX) add-on

 adaptors for your existing television. Only

 £149.95 inclusive. Also Prestel. Fantastic

 colour graphics for microcomputers. Avon

 Office Services (HE), FREEPOST, Bristol,

 BS10 6BR. (0272) 502008 anytime.

CENTURION

ALARMS

We manufacture, you save £££'s

 Send s.a.e. or phone for our Free list of

 professional D.I.Y. Burglar Alarm Equip-

 ment and accessories.

 Discount up to 20% off list prices,

 e.g. Control Equipment from £15.98,

 Decoy Bell Boxes from £5.95 inc.

 TRADE ENQUIRIES WELCOME


 ☎ 0484-21000

 or 0484 35527 (24 hr. ans.)

CENTURION ALARMS (HE)

 1265 Wakefield Road, Huddersfield

 HD5 9BE, W. Yorkshire.

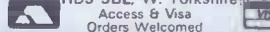

AMAZING ELECTRONICS PLANS.

 Lasers, Super-powered Cutting Rifle,

 Pistol, Light Show, Ultrasonic Force Fields,

 Pocket Defence Weaponry, Giant Tesla,

 Satellite TV Pyrotechnics, 150 more

 projects. Catalogue £1 — From Placentre,

 46, Bye Street, Ledbury, HR8 2AA.

SOLAR CELLS 3" dia. 900mA at 0.45V

 £7.59. Price lists 75p. Edencombe Ltd., 34

 Nathans Road, Wembley, Middx. HA0 3RX

BURGLAR ALARM EQUIPMENT. Please

 visit our 2,000 sq. ft. showrooms or write

 or phone for your free catalogue. C.W.A.S.

 Ltd. 100 Rooley Avenue, Bradford BD6

 1DB. Telephone 0274-308920.

AERIAL AMPLIFIERS improve weak

 television reception. Price £6.70. S.A.E. for

 leaflets. Electronic Mailorder, Ramsbottom,

 Lancashire BL0 9AGH.

PARAPHYSICS JOURNAL (Russian trans-

 lations); Psychotronic Generators, Kirliano-

 graphy, gravity lasers, telekinesis. Details:

 S.A.E. 4 x 9" Paralab, Downton, Wilts.

ZX81 INTERFACE BOARD. 8 digital, 4

 analogue inputs (200kHz sampling rate). 8

 digital, 4 analogue outputs. Compatible with

 16K RAM and printer. £48.50 fully inclusive

 — power supplies only required. Inquiries to

 Swan Electronic Designs, 6 Moncorvo Close,

 London SW7 — Mail order only.

PSU's 5v1A £10.99. 5v3A £11.99. 5v5A

 £25.99. 1.2v—25v: 100mA £14.99. 1.2A

 £24.99. 5A £31.99. Inc P&P. SAE for lists

 Edwards Electrics Unit 3 Mill Lane Bridgwater

 Somerset.

PRINTED CIRCUITS. Make your own sim-

 ply, cheaply and quickly! Golden Fotolac

 light-sensitive lacquer — now greatly im-

 proved and very much faster. Aerosol

 cans with full instructions, £2.25. Develo-

 per 35p. Ferric Chloride 55p. Clear

 acetate sheet for master 14p. Copper-clad

 fibreglass board, approx. 1mm thick

 £1.75 sq. ft. Post/packing 75p. White-

 House Electronics, Castle Drive, Praa

 Sands, Penzance, Cornwall.

SECURITY SYSTEM KITS . . . All com-

 ponents and full instructions. Send large

 S.A.E. for latest catalogue of advanced

 projects for car, caravan and home.

COMPU-TECH SYSTEMS, Worstead

 Lab's, N. Walsham NR28 9SA. Tel. (0692)

 405600.

FIND-A-FRIEND through FIND-A-FRIEND'S

 new confidential, inexpensive service. Your

 ideal friendship/relationship — all ages —

 countrywide. SAE/Telephone: FIND-A-

 FRIEND (HE), Temple House, 43-48 New

 Street, Birmingham B2 4LH. 021-429 6346.

ELECTRONICS component shop in **MAID-**

STONE, KENT! Thyronics Control Systems,

 8 Sandling Road, Maidstone, Kent.

 Maidstone 675354.

DIGITAL WATCH REPLACEMENT parts.

 Batteries, displays, backlights etc. Also

 reports, publications, charts. S.A.E. for full

 list. Profords, Copnersdrive, Holmergreen,

 Bucks HP15 6SGE.

NEW COMPONENTS!		Lists 65p Free with order
Telescopic aerials £1.30	1000/63v 55p. 220/40v	
T05 Pushon Heatsinks	48p.	
10p		TANTS!
5 pin 180° Din sockets	.1/35v, 33/35v, 1.5/35v	
10p	14p	
3.5mm Jack sockets 9p	4.7/6.3v, 1/35v 15p	
100K Lin Hoz presets	2.2/35v 17p. 10/16v	
10p	25p	
	22/25v 32p	
ELECTROLYTICS!	CERAMIC DISCS! (500v)	
8/350v 35p. 16/40v	100, 180, 220, 330, 470,	
10p.	820, 1000pF 6p each	
47/35v 10p. 100/16v	10X.01/100v axial polys	
9p	52p	
220/25v 18p. 470/40v	10X.1/250v radial polys	
30p	55p	
200 Mixed nuts, washers and screws £1.50		
500 ITEM components pack! Diodes, discs, plates,		
knobs, resistors, presets etc., £5.75 (GOOD VALUE)		
ADD £1 P&P AND VAT AT 15% TO ORDERS		
LETCHWORTH ELECTRONIC COMPONENTS		
Spirella Building, Bridge Road,		
Letchworth, Herts. SG6 4ET		
TEL: (04626) 70354		



HOBBY ELECTRONICS

CLASSIFIED ADVERTISEMENT — ORDER FORM

If you have something to sell now's your chance! Don't turn the page — turn to us!
Rates of charge: 26p per word per issue (minimum of 15 words). Box Nos. £2.50
 and post to **HOBBY ELECTRONICS, CLASSIFIED DEPT., 145 CHARING CROSS ROAD, LONDON WC2**

			£3.90
			£5.20
			£6.50
			£7.80
			£9.10
			£10.40
			£11.70
			£13.00

Please place my advert in **HOBBY ELECTRONICS** for issues commencing as soon as possible.
 I am enclosing my Cheque/Postal Order/International Money Order for: (delete as necessary) £. (Made payable to A.S.P. Ltd) Please use BLOCK CAPITALS and include post codes.



OR Debit my Access/Barclaycard
 (Delete as necessary)



Name (Mr/Mrs/Miss/Ms)
(delete accordingly)

Address

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

All classified advertisements must be paid for in advance.

Signature **Date**
Daytime Tel. No.

ADVERTISEMENT INDEX

Absonglen	62	Input Design	61
A. C. Townley	71	Jupiter Cantab	20
A. D. E.	78	ILP	26, 53
Airways Elec	61	LB Elec	62
Aitken Bros.	40	LEM	56
Akhter Inst	49	Litesold	78
Amaral Ltd	79	Magenta	41
Ambit Int.	2	Microtimes	52
Armon Elec	36	Midwich Comp.	48
Bib Audio	19	Musicraft	71
Bi-Pak	45	Myers	78
BK Elec	83	Nash Smithfield	78
BNRS	72	Pimac System	62
Bradley Marshall	13	Path/Lightning	25
Brystep Elec	79	Rapid Elec	23
Cambridge Learning	13	Brian J. Reed	78
Carlton Nichol	71	Relay-a-Quip	61
Chordgate Ltd	78	Rickard	56
Cricklewood Elec.	8, 71	Riscomp Ltd	12
D'Juson Ltd	44	Roadrunner	32
Electronize Design	14	RTVC	22
Electronics World	62	Silica Shop	4
Electrovalue	52	Sinclair Research	28, 29
Expo Drills.	72	Solid State	71
Flight Elec	32	Technomatic	37
Greenweld	48	Thames Valley	84
Grenson Elec	72	TK Elec	40
Happy Memories	56	Vako Display	53
Hart Elec	79	Velleman	36
Heath Elec	44	Watford Elec.	5
Hemmings Elec	57	Wilmslow	61
ICS	79	Woodfield Syst	71




MULLARD SPEAKER KIT

A PURPOSELY DESIGNED 40 WATT R.M.S. 8 OHM SPEAKER SYSTEM RECENTLY DEVELOPED BY MULLARD'S SPECIALIST TEAM IN BELGIUM. Kit comprises a Mullard 8" Woofer with foam surround and aluminium voice coil. Mullard 3" high power dome tweeter. B.K.E. built and tested crossover, based on Mullard circuit combining low loss components, glass fibre board and recessed loudspeaker terminals. Recommended cabinet size 240 x 216 x 445 mm.

A superb sound at a relatively low cost. Complete with instructions. Price £14.90 + £1.50 P&P per kit.

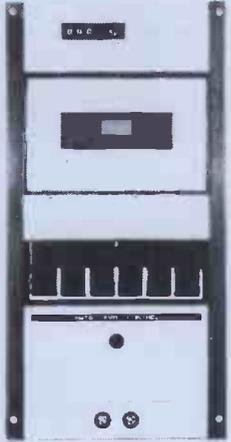New 5" 30 watt mini version of above now available. Recommended cabinet size 180 x 155 x 295 mm. Price £13.90 + £1.00 P&P per kit.



STEREO CASSETTE TAPE DECK MODULE. Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

Features: Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. Input Sensitivity: 100mV to 2V Input Impedance: 68K. Output level: 400mV to both left and right hand channels. Output Impedance: 10K. Signal to noise ratio: 45dB. Wow and flutter: 0.1%. Power Supply requirements: 18V DC at 300mA. Connections: The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). Dimensions: Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

Price £26.70 + £2.50 postage and packing. Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

6 piano type keys

NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price: -


15" 100 watt R.M.S. Impedance 8ohm 59 oz magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. Price £32 each. £2.50 Packing and Carriage each.

12" 100 watt R.M.S. Impedance 8 ohm, 50 oz magnet. 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. Price £23.70 each. £2.50 Packing and Carriage each.

8" 50 watt R.M.S. Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil. Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. Price: White cone £8.90 each. Black cone/grill £9.50 each. P & P £1.25 each.

PIEZO ELECTRIC TWEETERS - MOTOROLA

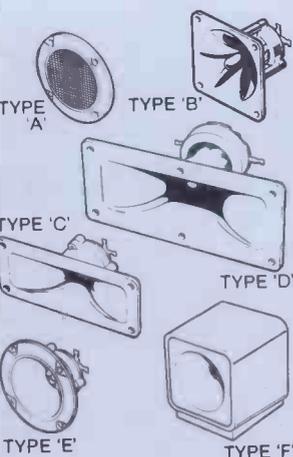Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £3.45 each.

TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £4.35 each.

TYPE 'C' (KSN6016A) 2 1/2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discs etc. Price £5.45 each.

TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discs. Price £6.90 each.

TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £4.35 each.

TYPE 'F' (KSN1057A) Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. Price £10.75 each.

U.K. post free for SAE for Piezo leaflets.



1000 MONO DISCO MIXER

A superb fully built and tested mixer/pre-amp with integral power supply. 4 Inputs 2 turntables (ceramic cartridge). Aux. for tape deck etc., plus Mic. with override switch, all with individual level controls. Two sets of active tone controls (bass and treble) for Mic. and main Inputs. Master volume control. Monitor output with select switch and volume control.

Outputs Main 750 mV Monitor 500 mV into 8 ohms. Supply 220/240V AC50/60Hz Size 22 1/2" x 4 1/2" x 2 1/2" price £39.99 + £2.50 P&P

1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
- Compact size

4 3/4" x 13 1/8" x 2 1/2"

- Easy snap in fixing through panel/cabinet cut out
- Insulated plastic case
- Full wave control using Ramp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads

Innumerable applications in industry, the home, and discos/theatres etc.

Price: £11.70 each + 50p P&P (Any quantity)

BSR P256 TURNTABLE

P256 turntable chassis ● S shaped tone arm ● Belt driven ● Aluminium platter ● Precision calibrated counter balance ● Anti-skate (bias device) ● Damped cueing lever ● 240 volt AC operation (Hz) ● Cut-out template supplied ● Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.

Price: £28.50 + £2.50 P&P



POWER AMPLIFIER MODULES



100 WATT R.M.S. AND 300 WATT R.M.S. MODULES

Power Amplifier Modules with integral toroidal transformer power supply, and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. An LED Vu meter is available as an optional extra.

SPECIFICATION:

Max Output Power: 110 watts R.M.S. (OMP 100)

310 watts R.M.S. (OMP 300)

Loads: Open and short circuit proof. 4-16 ohms.

Frequency Response: 20Hz - 25KHz ±3dB.

Sensitivity for Max. Output: 500mV at 10K (OMP 100) 1V at 10K (OMP 300)

T.H.D.: Less than 0.1%

Supply: 240V 50Hz

Sizes: OMP 100 360 x 115 x 72mm

OMP 300 460 x 153 x 66mm

Prices: OMP 100 £29.99 each + £2.00 P&P

OMP 300 £89.00 each + £3.00 P&P

Vu Meter £6.50 each + 50p P&P

Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms

Build a quality 60 watt R.M.S. system.

★ 10" Woofer 35Hz-4.5KHz

★ 3" Tweeter 2.5KHz-19KHz

★ 5" Mid Range 600Hz-8KHz

★ 3-way crossover 6dB/oct 1.3 and 6KHz

Recommended Cab-size 26" x 13" x 13"

Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring-loaded loudspeaker terminals and recessed mounting panel

Price £22.00 per kit + £2.50 postage and packing. Available separately, prices on request.

12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz magnet. 2" aluminium voice coil. Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.

Price £17.99 each + £2.50 P&P.



BK ELECTRONICS

Prompt Deliveries
VAT inclusive
prices
Audio Equipment
Test Equipment
by
Thandar
and
Leader

B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.





CMOS	TTL	TTL contd.	TTL LS contd.	OPTO	OPTO contd.	Transistors & Diodes
4001 13p	7400 13p	74173 60p	74LS162 35p	LEDs	DISPLAYS	IN4001 4p
4002 13p	7401 13p	74174 50p	74LS163 35p	0-2"	Bar Graph 295p	IN4007 6p
4006 60p	7402 13p	74175 50p	74LS164 45p	Red 10p	5"	IN5401 13p
4007 13p	7403 13p	74180 50p	74LS165 50p	Green 14p	Common Anode	IN5404 16p
4008 50p	7404 13p	74190 60p	74LS168 60p	Flashing	L.H. decimal point	IN5406 16p
4010 30p	7405 14p	74191 60p	74LS169 60p	Red 82p	Red 150p	IN4148 3p
4011 13p	7406 20p	74192 70p	74LS170 70p	Rectangular	Green 248p	IN914 3p
4012 13p	7407 24p	74193 60p	74LS173 40p	LEDs	Yellow 260p	IN916 5p
4013 22p	7408 14p	74194 60p	74LS174 45p	Red 22p	Common Cathode	BZY88C2V7 8p
4014 50p	7409 14p	74195 46p	74LS175 45p	Green 26p	R.H. decimal point	BZY88C3V3 8p
4015 45p	7410 14p	74196 46p	74LS181 110p	Yellow 22p	Red 150p	BZY88C3V6 8p
4016 25p	7411 14p	74197 50p	74LS190 45p	Bi-Colour	Green 248p	BZY88C3V8 8p
4017 40p	7412 18p	74221 75p	74LS191 45p	Red/Green 80p	Yellow 260p	BZY88C4V7 8p
4019 35p	7413 22p	74279 40p	74LS192 45p	0-125"		BZY88C6V8 8p
4020 48p	7414 26p	74290 60p	74LS193 45p	Red 11p	3"	BZY88C8V2 8p
4021 46p	7416 18p	74298 60p	74LS194 50p	Green 12p	Red 127p	BZY88C12 8p
4022 55p	7417 22p		74LS196 35p	Yellow 12p	Green 196p	BZY88C15 8p
4023 13p	7420 15p		74LS197 50p			BC107 11p
4024 42p	7421 20p		74LS240 70p			BC107A/B 11p
4025 13p	7422 15p		74LS241 70p			BC108A/B/C 11p
4027 26p	7423 15p		74LS242 70p			BC109A/B/C 12p
4028 40p	7424 15p		74LS243 70p			BC182 9p
4029 60p	7425 20p		74LS244 70p			BC183 9p
4030 13p	7426 27p		74LS245 80p			BC184 9p
4035 66p	7427 15p		74LS247 60p			BC212 9p
4040 50p	7428 18p		74LS249 40p			BCY70 17p
4042 40p	7429 18p		74LS251 40p			BCY71 18p
4044 46p	7430 15p		74LS252 35p			BCY72 18p
4047 50p	7431 14p		74LS253 35p			BFY50 28p
4049 20p	7432 18p		74LS254 35p			BFY51 28p
4050 20p	7433 18p		74LS255 55p			BFY52 28p
4051 50p	7434 24p		74LS256 55p			TIP29/A 30p
4052 60p	7435 16p		74LS257 40p			TIP30/A 35p
4053 50p	7436 18p		74LS258 40p			TIP31/A 45p
4066 28p	7437 18p		74LS259 65p			TIP32/A 45p
4067 447p	7438 18p		74LS260 30p			TIP41/A 50p
4069 13p	7439 24p		74LS261 30p			TIP42/A 50p
4070 13p	7440 16p		74LS262 22p			2N708 24p
4071 13p	7441 15p		74LS263 60p			2N918 26p
4076 50p	7442 24p		74LS264 60p			2N2218/A 26p
4081 13p	7443 18p		74LS265 60p			2N2219/A 28p
4086 45p	7444 50p		74LS266 22p			2N2221/A 24p
4093 30p	7445 50p		74LS267 60p			2N2222/A 28p
4098 70p	7446 68p		74LS268 60p			2N2904/A 29p
4503 42p	7447 55p		74LS269 60p			2N2905A 28p
4510 52p	7448 55p		74LS270 60p			2N2906A 28p
4511 45p	7449 26p		74LS271 40p			2N2907A 28p
4512 50p	7450 15p		74LS272 14p			2N3053 28p
4516 60p	7451 15p		74LS273 14p			2N3055 46p
4518 40p	7452 15p		74LS274 14p			2N3442 130p
4520 60p	7453 13p		74LS275 14p			2N3715 57p
4528 64p	7454 15p		74LS276 14p			2N3716 65p
4539 64p	7455 50p		74LS277 14p			
4555 45p	7456 25p		74LS278 22p			
4556 45p	7457 25p		74LS279 40p			
40014 50p	7458 28p		74LS280 40p			
40085 70p	7459 50p		74LS281 34p			
40097 60p	7460 26p		74LS282 40p			
40098 60p	7461 45p		74LS283 40p			
40161 55p	7462 25p		74LS284 40p			
40163 55p	7463 25p		74LS285 34p			
40175 60p	7464 47p		74LS286 22p			
40193 60p	7465 60p		74LS287 130p			
	7466 70p		74LS288 30p			
	7467 35p		74LS289 30p			
	7468 30p		74LS290 34p			
	7469 45p		74LS291 34p			
	7470 30p		74LS292 34p			
	7471 25p		74LS293 34p			
	7472 25p		74LS294 34p			
	7473 25p		74LS295 52p			
	7474 22p		74LS296 52p			
	7475 23p		74LS297 83p			
	7476 22p		74LS298 83p			
	7477 47p		74LS299 83p			
	7478 47p		74LS300 55p			
	7479 47p		74LS301 55p			
	7480 60p		74LS302 90p			
	7481 60p		74LS303 130p			
	7482 25p		74LS304 130p			
	7483 47p		74LS305 30p			
	7484 47p		74LS306 30p			
	7485 60p		74LS307 30p			
	7486 25p		74LS308 30p			
	7487 25p		74LS309 30p			
	7488 25p		74LS310 30p			
	7489 26p		74LS311 30p			
	7490 26p		74LS312 30p			
	7491 45p		74LS313 30p			
	7492 38p		74LS314 30p			
	7493 28p		74LS315 30p			
	7494 28p		74LS316 30p			
	7495 50p		74LS317 30p			
	7496 45p		74LS318 30p			
	7497 45p		74LS319 30p			
	7498 45p		74LS320 30p			
	7499 25p		74LS321 30p			
	7500 25p		74LS322 30p			
	7501 20p		74LS323 30p			
	7502 20p		74LS324 30p			
	7503 35p		74LS325 30p			
	7504 35p		74LS326 30p			
	7505 35p		74LS327 30p			
	7575 35p		74LS397 30p			
	7576 35p		74LS398 30p			</